


40 Construction Projects • SWL • Ham Radio

RADIO-TV EXPERIMENTER

By the Editors of Science and Mechanics

75c
SPRING
1960

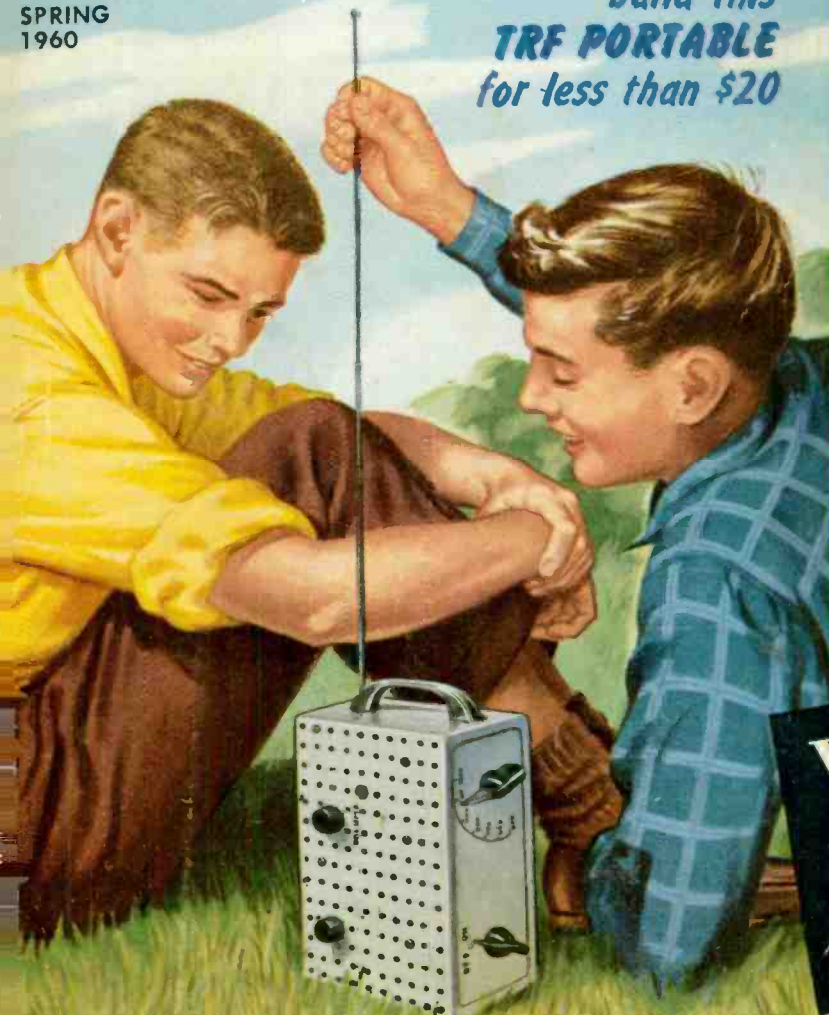*build this
TRF PORTABLE
for less than \$20*



VARIABLE PS FOR
TRANSISTOR CKTS
MEMORIZE MORSE
IN 20 MINUTES
TRANSISTOR
TESTER-VOM
TV-FM ANTENNAS
TELEPHONIC
REMOTE CONTROL
ELECTRIC GUITAR
MINIATURE
MULTIMETER
6-METER CONVERTER
ELECTRONIC
TACHOMETER
ELIMINATING TVI
JACOB'S LADDER
10/20-METER
SW RECEIVER
PLUS

**WHITE'S
RADIO
LOG**





500 Changes • New, Up-to-Date
AM-FM-TV STATIONS
WORLD-WIDE SHORT WAVE

DAVIS PUBLICATION

HOW TO GET A GOOD PAYING JOB IN RADIO-TELEVISION



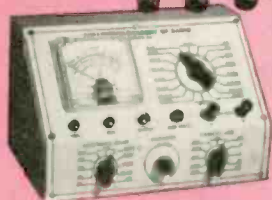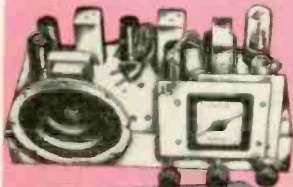Build this equipment while learning . . . it's yours to keep!



EARN WHILE YOU LEARN AT HOME IN SPARE TIME

I'll prove to you that I can prepare you to become a trained Radio and Television Serviceman in a few months' time . . . ready to step into a good paying job with a real future! Mail coupon-postcard NOW!



MASON R. WARNER, President

Only \$6 starts you On Sprayberry "Learn by Doing" Training Plan

Men by the thousands . . . trained Radio-Television Service Technicians . . . are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now—just \$6 enrolls you for America's finest, most up-to-date home study training in Radio-Television! This offer is made because Radio-Television must have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need . . . to step into a fine job or your own Radio-Television Service Business.

Get Practical Experience with 25 Kits of Radio-TV Parts

In addition to modern lessons, you train with actual parts and equipment. Build the famous Sprayberry Training Television Set, Multi-Range Tester, 2-Band Radio, other Test Equipment—all yours to keep. Get latest training on Color TV, Transistors, Hi-Fi and UHF Conversions to make your training more valuable.

Radio-TV Needs You Now! Get all the facts . . . FREE!

Radio-Television needs you! See how and why Sprayberry Radio-Television home training offers you *more*. Three training plans to suit your exact needs. Low payment . . . only \$6 starts you. Backed by over 27 years of distinguished training experience. Rush special postcard—reply coupon for catalog and free sample lesson.

The Radio-Television industry is begging for trained men for interesting, profitable service work . . . get set now!

WRITE NAME AND ADDRESS — Cut out card and mail.

YOUR NAME _____

ADDRESS _____

TOWN _____ STATE _____

No Postage Stamp Necessary If Mailed in the United States

BUSINESS REPLY MAIL
First Class Permit No. 34316, Chicago, Ill.

SPRAYBERRY ACADEMY OF RADIO-TELEVISION

Dept. 212-F 1512 Jarvis, Chicago 26, Ill.



This coupon needs no stamp or envelope. Just write name in upper left corner, cut out along dotted line and drop in any mail box. Pay no attention to printing on back of the card. By return mail you'll receive our big 60 page catalog and free sample lesson.

SPRAYBERRY

ACADEMY OF RADIO-TELEVISION
Dept. 212-F
1512 Jarvis, Chicago 26, Ill.

RADIO-TV EXPERIMENTER

Spring 1960 Edition

Terrific TRF Portable	23	Electronic Black Magic	88
Six-Meter Amateur Band Converter	27	Extra Uses for Table Radios	90
Two-Transistor Utility Amplifier	30	Tuned Antenna Coupler	91
SM-FP Unit	33	Learn by Doodling	92
Miniature Multimeter	37	Tube Tester Kit Report	95
Three-Transistor Portable	41	Loop Crystal Set	97
Noise Limiter for Ham Station	44	Printed Circuit Know-How	99
Wave Traps	45	DXing the World	102
Precision Stroboscope	47	Electronic Color Wheel	105
10-20 Short-Wave Receiver	52	VHF Station	107
Telephone Actuated Switch	55	Radio-TV Sound Dimmer	116
Compass Galvanometer	61	Using an Oscilloscope	118
Variable Power Supply	62	Soldering Iron Stand	123
Eliminating TVI	64	The Tunnel Diode	125
Car Battery Adaptor for Radio	68	Electronic Tachometer	127
DC Meter Amplifier	69	Repair That Old Meter	132
Transistorized Photo-Cell Control	72	Why Wait for Air Safety?	134
What to Listen for on Short-Wave	74	TV and FM Aerials	136
How to Memorize Morse Code	77	Learning Electronics	139
Demagnetizer	80	Portable Earphone Plug Box	145
High-Voltage Traveling Arc	82	Electric Guitar	146
Volt-Ohmmeter and Transistor Tester	85	25 Years Ago in Radio	156

WHITE'S RADIO LOG.....161

Cover by Harold R. Stluka

Curtis L. Johnson, Handbook Editor
Herb Siegel, Associate Editor, Handbooks
Bill Wadkins, Assistant Art Director, for Handbooks

Published and Copyrighted 1960 by
SCIENCE AND MECHANICS PUBLISHING COMPANY

A Subsidiary of Davis Publications, Inc.

450 East Ohio Street

Chicago 11, Illinois

The Radio-TV Experimenter contains a selection of the most popular electronics projects and radio and TV maintenance articles that have appeared in *Science and Mechanics Magazine*, plus a number of projects and helpful articles on the same subjects appearing for the first time.

Science and Mechanics Handbook Annual No. 2, 1960—No. 565

B. G. DAVIS
 Publisher

JOEL DAVIS
 Assistant Publisher

Editorial Board

DON DINWIDDIE
 Editor

ART YOUNGQUIST
 Home Workshop Editor

P. D. URBAIN
 Associate Editor

F. M. EISENZOPH
 Art Director

Advertising Offices: Chicago: 450 E. Ohio St., WH 4-0390; New York: 527 Madison Ave., PL 3-9377; Los Angeles: The Maurice A. Kimball Co., Inc., 2550 Beverly Blvd., DU 8-6178; San Francisco: The Maurice A. Kimball Co., 681 Market St., EX 2-3365.



The **AMERICAN BASIC SCIENCE CLUB** offers this

Exciting New Hobby for Everyone

Low Cost **SCIENCE LABORATORY**

Over 100 Fascinating Projects with



COMPLETE LABORATORY COMES IN 8 KITS . . . ONE A MONTH
SUPPLIES ALL THE EQUIPMENT FOR ALL THE FOLLOWING:

ELECTRICAL EXPERIMENTS

Educational fun with Electro Magnets, Transformer, Galvanometer, Rheostat, Relay, Voltmeter, Wheatstone Bridge, and other electric equipment.

RADIO RECEIVER

A sensitive three tube Regenerative Radio that has its own DC power supply. Plugs into regular 115 volt AC outlet. Complete with Head Set.

SPECTROSCOPE

Fascinating optical instrument used to identify and analyze substances by observing the spectrum of their flame. Spectrum charts are included.

PHOTOELECTRIC EYE

Photoelectric Cell, Exciter lamp — and Electronic Relay. Everything you need to control motors, bells, alarms, and do other light beam experiments.

MICROPHONE

A sensitive carbon-button microphone that greatly amplifies unsuspected noise. Also adaptable for use with your radio transmitter.

ELECTRONIC EXPERIMENTS

Explore functions of vacuum tubes and other electronic components. Build an Electronic Switch—Amplifier, and other experimental circuits.

CODE PRACTICE SET

Signal Oscillator, Key and Flasher . . . the complete outfit to learn to receive and transmit the Morse Code . . . the first step to a Ham License.

STROBE LIGHT

A variable pulse neon light. "Freezes" motion of rapidly vibrating or rotating objects for close study and checking frequencies, RPM.

BROADCAST TRANSMITTER

Sends clear transmissions of both code and voice to nearby radios. Can be used with your microphone, record player, or code oscillator.

RADIO SERVICE EQUIPMENT

All the parts to build your own Radio Signal Tracer and a Probe Light Continuity Tester. Both gears are invaluable in radio servicing.

SOUND EXPERIMENTS

Laboratory demonstration of sound waves, resonance and pitch. Includes Variable Frequency Oscillator, Sonometer and Loud Speaker.

TELESCOPE

A mounted astronomical Telescope. High quality ground lens enables you to examine details of the moon's surface and distant objects.

PHOTOGRAPHY LAB

Complete dark room equipment: Printer—Enlarger—Electronic Timer—Safe Light—Developing Trays and supply of photo and chemicals.

SLIDE PROJECTOR

Takes 16mm and 35mm slides, sharp focusing, convection cooled. G.E. Projection Lamp included. Also adaptable as a Projection Microscope.

MICROSCOPE

High and low power, precision ground lens, Substage Light and Polarizer Adaptable for photomicrography in connection with Photo Lab.

ATOMIC RADIATION EXPM.

Check radioactivity of ores and do radiation experiments with sensitive Electroscopes. Sample radioactive sources of Radium, Uranium included.

SPINTHARISCOPE

Shows you a blown up ringside view of the brilliant explosions of disintegrating radium atoms ejecting alpha particles at 11,000 miles per second.

ATOMIC CLOUD CHAMBER

See illuminated tracks of speeding nuclear particles emanating from radioactive Alpha source and mysterious cosmic rays from outer space.

ULTRAVIOLET LAMP


Produce dazzling color effects with invisible "black light". Used extensively for crime detection, mineralogy and science and industrial research. Fluorescent Tracer Chemical included.

HEAT EXPERIMENTS

Study the Molecular Theory of heat using 2 Thermometers, Thermostat, 3 foot Gas Thermometer and special Microscope arrangement that shows the effect of Molecular Movement.

WEATHER STATION

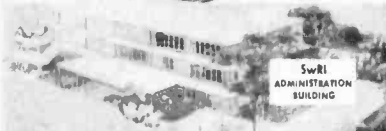Aneroid Barometer, Cup Anemometer that electronically measures wind speed. Sling Psychrometer, Humidity Gauge, Cloud Speed Indicator, Cloud Chart and Weather Map.



SWRI ADMINISTRATION BUILDING

These kits were developed with famous **SOUTHWEST RESEARCH INSTITUTE** and are a **TRUE BASIC SCIENCE COURSE**

- The 8 instruction manuals are expertly written, clearly illustrated — exciting, interesting
- **WITHOUT PREVIOUS EXPERIENCE** you can complete every project and gain a valuable, comprehensive science background.

EASY - FUN - EDUCATIONAL



Analyzing Glowing Gases with the **SPECTROSCOPE**



Trouble Shooting with the **SIGNAL TRACER**

PHOTOMICROGRAPH of a Fly's Wing made with Microscope and Photo Lab (Actual Size 3" diameter)

These 8 Kits Make Up a Valuable, Versatile Science Laboratory Containing Standard Parts by: SYLVANIA, MALLOY, G. E., PYRAMID, STACKPOLE, TRIM AND OTHER RELIABLE MANUFACTURERS. Retail value of parts alone is over **FIFTY DOLLARS**

MEMBERS ARE ENTHUSIASTIC!

I wish I could provide each of my Physics students with all of your enjoyable kits. You are doing a wonderful job. Allen T. Ayers, Physics Dept., Jamestown High School, Jamestown, New York

Designing and offering this complete laboratory to the public at such a low price is a notable service to our society.

R. M. Helm, Professor of Physics, East Carolina College, Greenville, N. C.

FOR SAFETY!

Circuits are low voltage supplied by isolation transformer that comes with this kit.



FREE! These 6 Auxiliary Textbooks

ALL THE EQUIPMENT FOR ALL THE ABOVE—only \$29.60

SEND **\$2.00** WITH ONLY **COUPON** PAY **\$3.45** FOR EACH KIT YOU RECEIVE (ONE A MONTH FOR 8 MONTHS)

FREE

SOLDERING IRON with second Kit

Your Satisfaction or Your Money Back... **AND** you may cancel at any time without obligation.

These "no risk" assurances because we know you will be...

SURPRISED! AMAZED! DELIGHTED!

AMERICAN BASIC SCIENCE CLUB, Inc.
 301 East Crockett, San Antonio 6, Texas

Start sending me A.B.S.C.'s "Home Science Lab" in eight kits, one each month. If not satisfied on inspection of first kit I may return it for immediate refund. (I choose plan checked.)
 () I enclose \$2.00 and will pay \$3.45 plus COD postage on arrival of each kit. I may cancel unshipped kits at any time.
 () I enclose \$29.60 as full payment. Postage Paid, for all 8 kits. I may cancel any time and get full refund on unshipped kits.

NAME _____
 STREET _____

CITY _____ STATE _____
 MAIL COUPON TODAY

AMERICAN BASIC SCIENCE CLUB, Inc. San Antonio, Texas


These men are getting practical training in **NEW Shop-Labs of**

ELECTRICITY

ELECTRONICS

ON REAL

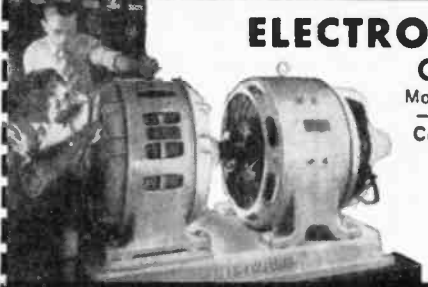Motors—Generators—
—Switchboards—
Controls—Modern
Appliances—
Automatic
Electronic
Control Units



TELEVISION

RADIO ELECTRONICS

ON REAL

TV Receivers—
Black and White
and Color
AM-FM and
Auto Radios
Transistors
Printed Circuits
Test Equipment



COYNE

in Chicago—prepare for today's **TOP OPPORTUNITY FIELD**. Train on real full-size equipment at **COYNE** where thousands of successful men have trained for over 60 years—largest, oldest, best equipped school of its kind. Professional and experienced instructors show you how, then do practical jobs yourself. No previous experience or advanced education needed. Employment Service to Graduates.

START NOW—PAY LATER—Liberal Finance and Payment Plans. Part-time employment help for students. **GET FREE BOOK**—"Guide to Careers" which describes all training offered in **ELECTRICITY** and **TELEVISION-RADIO ELECTRONICS**—no obligation; **NO SALESMAN WILL CALL**.

Coyne Electrical School, 1501 W. Congress Parkway
Chartered Not For Profit • Chicago 7, Dept. 30-9C

MAIL COUPON OR WRITE TO ADDRESS BELOW

COYNE ELECTRICAL SCHOOL
Dept. 30-9C—New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Ill.

Send **BIG FREE** book and details of all the training you offer. However, I am especially interested in:

Electricity Television Both Fields

Name _____

Address _____

City _____ State _____



COYNE offers
LOW COST

TELEVISION RADIO - COLOR TV

Training in
Spare Time AT HOME



The future is **YOURS** in **TELEVISION!**

A fabulous field—good pay—fascinating work—a prosperous future in a good job, or independence in your own business!

Coyne brings you **MODERN-QUALITY** Television Home Training; training designed to meet Coyne standards at truly lowest cost—you pay for training only—no costly "put together kits." Not an old Radio Course with Television "tacked on." Here is **MODERN TELEVISION TRAINING** including Radio, UHF and Color TV. No Radio background or previous experience needed. Personal guidance by Coyne Staff. **Practical Job Guides** to show you how to do actual servicing jobs—*make money early in course*. Free Life-time Employment Service to Graduates.

COYNE
ELECTRICAL SCHOOL

CHARTERED AS AN EDUCATIONAL INSTITUTION
NOT FOR PROFIT

1501 W. Congress Parkway • Chicago 7, Dept. 30-H9



B. W. COOKE, Jr., President
Coyne—the Institution behind this training... the largest, oldest, best equipped residential school of its kind. Founded 1899.

Send Coupon or write to address below
for **Free Book**

and full details,
including easy
Payment Plan.
**No obligation, no
salesman will call.**



COYNE Television Home Training Division

Dept. 30-H9, New Coyne Building
1501 W. Congress Pkwy., Chicago 7, Ill.

Send **Free Book** and details on how I can get Coyne Quality Television Home Training at *low cost and easy terms*.

Name _____

Address _____

City _____ State _____



The Beautiful Schober CONSOLETTA
 —only small organ with two full 61-note keyboards and 22 stops. Requires only 2x3/2" floor space! Commercial value approximately \$1600 or more.

BUILD THIS SUPERB Schober ORGAN FROM SIMPLE KITS and save over 50%!

Give Your Family A Lifetime of Musical Joy With A Magnificent Schober Electronic Organ!

Now you can build the brilliant, full-range Schober CONSOLETTA or the larger CONCERT MODEL with simple hand tools! No skills are needed; no woodworking necessary. Just assemble, clearly marked electronic parts guided by step-by-step instructions. You build from kits, as fast or as slowly as you please... at home, in your spare time — with a small table serving as your entire work shop.

ment you assemble is as fine, and technically perfect, as a commercial organ... yet you save over 50% on quality electronic parts, high-priced labor, usual store mark-up!

THE GREAT CONCERT MODEL meets specifications of American Guild of Organists

Free Booklet

Send for 16-page booklet in full color describing Schober organs you may build for home, church or school, plus articles on how easy it is to build your own organ and how pleasant it is to learn to play. Also available is 10" LP demonstration record (price \$2.00 — refundable on first order). Send for literature. No obligation and no salesman will call.

Pay As You Build!

Start building your organ at once, investing just \$18.94! The superb instru-

Mail This Coupon For FREE Schober Literature And Hi-Fi Demonstration Record TODAY!



The Schober Organ Corp., Dept. RX-1
 2248 Broadway, New York 24, N. Y.
 Please send me FREE full-color booklet and other literature on the Schober organs.
 Please send me the 10" hi-fi Schober demonstration record. I enclose \$2.00 (refundable on receipt of my first kit order).

Name.....
 Address.....
 City..... Zone... State.....



send for this **FREE** EICO Electronics Catalog

you save 50% on Top-Quality Test Instruments Hi-Fi • Ham Gear **KITS AND ASSEMBLED** Ready-to-use for professional and home use

TEST INSTRUMENTS
 battery eliminators
 battery testers
 bridges
 decade boxes
 electronic switch
 flyback tester
 oscilloscopes
 probes
 signal and sweep generators
 tube testers
 transistor tester
 vacuum tube voltmeters
 volt-ohm-milliammeters

HI-FI
 stereo and monaural tuners
 preamplifiers
 power amplifiers
 integrated amplifiers
 speaker systems

HAM GEAR
 cw transmitter
 modulator-driver
 grid dip meter

OVER 1 MILLION EICO instruments in use throughout the world.

LIFETIME service and calibration guarantee. IN STOCK at your neighborhood EICO dealer. Send now for FREE catalog RTE-3



33-00 N. Blvd., L. I. C. 1, N. Y. ... praised by the experts: as BEST BUYS IN ELECTRONICS

© 1960 ELECTRONIC INSTR. CO., INC.



.22 Cal NEW 7 SHOT REPEATER AUTOMATIC. The skilled hands of the German gunsmith is responsible for this .22 Caliber 7 shot repeater automatic with self-ejecting empty shells. Just 4 inches long, fits easily into pocket or purse. Ideal for sport, ink events, Boating. Single use. (Not available to Calif. residents). No permit needed. Money back guarantee. Comes for \$8.95 from Best Values Co., Dept. F-86, 403 Market St., Newark, New Jersey

INVENTORS

PROTECT YOUR PATENT With NEW PATENT SALES AGREEMENT

Now you can sell your patent and be SURE you are protecting your interests 100 percent. Prepared by the Dean of a leading law school, this S&M Patent Sales Contract will help you protect yourself and make sure you or your attorney overlooks no detail. Not a blank, but a true, TESTED Sales Contract that will protect your earnings and interests. Send today for a copy of our Patent Sales Agreement.

Only \$100

SOLD EXCLUSIVELY BY SCIENCE & MECHANICS MAGAZINE
 450 East Ohio Street, Dept. 411, Chicago 11, Illinois

In Spare Time at Home—Prepare for a Better Job—or
Your Own Business in One of the Many Branches of

ELECTRONICS

You build and keep this valuable Vacuum Tube VOLTMETER

You build and keep this 5-inch COLOR OSCILLOSCOPE — almost a "must" for TV servicing.



RADIO - TELEVISION - RADAR

If you are seeking a better job or a business of your own, the appealing field of Television-Radio-Electronics offers **REAL PROMISE!**

In this fast-growing field, trained Electronic technicians find many good-paying, interesting jobs in manufacturing, installing, operating, servicing. Equally important is the fact that these are **GOOD JOBS**—offering the kind of a future that an untrained man often dreams about.

No previous technical experience or advanced education needed. Prepare for this profitable field in your spare time at home, or in our modern Chicago or Toronto Laboratories. Nothing else like it! Send for **FREE** details.

EARN WHILE YOU LEARN

After you get part of DeVry Tech's training with equipment at home, you may then in your spare time, begin to earn real money servicing Radio and Television sets.



HOME MOVIES . . .

. . . make important points crystal clear. Speeds your learning. It's almost like having an instructor at your side!

MILITARY SERVICE

If you are subject to military service, the information we have should prove very helpful. Mail coupon today.

COLOR TV

DeVry Tech's program also includes training in Color Television



21 INCH

Build and keep this BIG DeVry Engineered TV set—easily converted to U.H.F. (DeVry offers another home training, but without the TV set.)

Your GUIDE

to Profitable Job Opportunities

- TV-Radio Broadcast Technician
- Color Television Specialist
- Radar Operator • Laboratory Technician
- Airline Radio Man • Computer Specialist
- Quality Control Manager
- Your Own Sales & Service Shop
- . . . PLUS MANY OTHERS

YOU GET THE SAME EMPLOYMENT SERVICE

that has helped thousands of our graduates toward fine careers in Electronics.

Send for **FREE BOOKLET TODAY!**


Accredited Member of National Home Study Council!

"One of North America's Foremost Electronics Training Centers"



DeVRY TECHNICAL INSTITUTE

CHICAGO 41, ILLINOIS

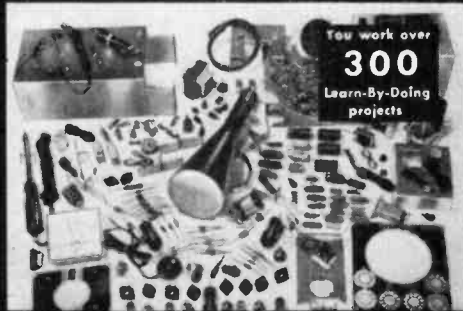

You work over **300** Learn-By-Doing projects

Build over 300 practical projects from many shipments of Radio-Electronic parts. You build and operate TV-Radio circuits . . . wireless microphone . . . and many other major projects—all designed to provide outstanding practical experience at home.

ACT NOW! Get information-packed publication **FREE!** Mail coupon today.

DeVRY TECHNICAL INSTITUTE

4141 Belmont Ave., Chicago 41, Ill., Dept. RTE-3-Q

Please give me your **FREE** booklet, "Electronics In Space Travel," and tell me how I may prepare to enter one or more branches of Electronics.

Name _____ Age _____

Street _____ PLEASE PRINT Apt. _____


City _____ Zone _____ State _____

2044 Canadian residents address DeVry Tech of Canada, Ltd. 626 Roselawn Ave., Toronto 12, Ontario

K **BUILD THE BEST!**

build quality money-saving
knight-kits[®]

A PRODUCT OF ALLIED RADIO

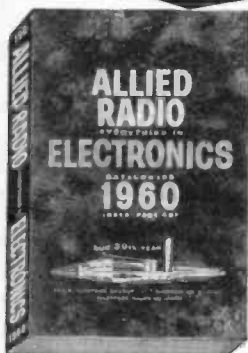

see them all in
ALLIED'S
1960 ELECTRONIC
SUPPLY CATALOG

FREE

build your own...
it's easy...it's fun!
SAVE UP TO 50%

HI-FI
KITS



INSTRUMENT
KITS



HOBBY KITS



HAM
KITS

world's
largest
stocks

See the 1960 KNIGHT-KIT line—available only from ALLIED. KNIGHT-KITS are lowest in cost, convenience-engineered for easiest assembly—the only kits with money-back guaranteed specifications. Send today for the 1960 ALLIED Catalog—select your KNIGHT-KITS—and...

**SAVE ON EVERYTHING
IN ELECTRONICS**

Get more for your money in Stereo hi-fi systems and components; save on recorders and tape; Amateur station equipment; TV tubes, antennas, accessories; test instruments; electronic parts, tubes, transistors, tools, books. Send today for your FREE 1960 ALLIED Catalog!

EASIEST TERMS
only \$2 down on
orders up to \$50

**FREE
catalog**

ALLIED RADIO

100 N. Western Ave., Dept. 64-C, Chicago 80, Ill.

Rush FREE 1960 ALLIED Catalog

Name _____

Address _____

City _____ Zone _____ State _____

ELLERY QUEEN'S 1960 ANTHOLOGY

A Who's Who of Whodunits!

"The Queen volume contains twenty-three stories . . . none has appeared in an earlier Queen anthology, and only two have been anthologized anywhere. You will, I'm sure, join me in hoping that this new kind of Queen anthology will become (as its title should indicate) an annual event."

—Anthony Boucher, *The New York Times*

**HOURS OF THRILLING
READING . . .**

collects in one volume the finest stories which have appeared in *Ellery Queen's Mystery Magazine* over the past 18 years—selected by Ellery Queen himself. Stories by such famous mystery writers as:

Agatha Christie
Erie Stanley Gardner
Mary Roberts Rinehart
Rex Stout
John Dickson Carr

Tales of mystery and of crime by such famous literary figures as:

W. Somerset Maugham
Ben Hecht
John van Druten
Mackinlay Kantor

And much, much more . . . a book everyone will be proud to add to his library—3 short novels, 20 short stories, 320 pages. If your local newsstand dealer is sold out, fill in the coupon below and we will mail your copy of this mystery treat.

Davis Publications, Inc., Dept. 565A
527 Madison Ave., New York 22, N. Y.

Please send me copies of
ELLERY QUEEN'S 1960 ANTHOLOGY.

I enclose \$1.00 for each copy.

I am an EQMM subscriber.

Name _____

Address _____

City _____ Zone _____

State _____

ON LAND·IN THE AIR and ON THE SEA..

BIG MONEY

awaits
**TRAINED
 TECHNICIANS**
in
**TELEVISION·RADIO·
 ELECTRONICS·RADAR**



EARN *As You Learn*

Christy Shop-Method Home Training makes you a more valuable and desirable technician, assures you of more money, faster progress and greater success. This practical step-by-step training makes everything interesting and easy, makes learning fun. You don't have to leave home or quit your job to learn this simple, easy way. A few hours of your spare time each week soon prepares you for earning while learning and later for a big-pay job or profitable business of your own in this fabulous, fast-growing new industry.

3 new books contain complete information. Describe the course and many opportunities in this fantastic new field. Send for your 3 free books today!

**19 TRAINING
 INSTRUMENTS
 INCLUDED**

In a few months you learn what used to take years of hard work to master, reach your goal sooner and are better prepared to make maximum progress. Send for complete information today!

CHRISTY TRADES SCHOOL
 Dept. T-211
 3214 W. Lawrence Ave.
 Chicago 25, Ill.

C.T.S.'s Complete Course!

C.T.S. training covers every phase of this fascinating new subject. You get this comprehensive training starting with your first lesson. You learn Radar, Sonar, Television, Radio and Electronics in C.T.S.'s Complete course. This broader knowledge and greater understanding means more jobs and higher pay for you. Why be satisfied with less? You learn faster and better with Christy Shop-Method Home Training. It gives you all the training you need in a clear, simple, easy-to-understand way.

Big pay, interesting work, immediate success, await those thoroughly trained in all branches of electronics. And the C.T.S. Master Shop-Method Home Training Course is the only complete course in Radar, Sonar, Television, Radio and Electronics.

MAIL COUPON TODAY!

CHRISTY TRADES SCHOOL
 Dept. T-211, 3214 W. Lawrence Ave., Chicago 25, Ill.

Gentlemen:
 Please send me, without cost or obligation, two FREE Lessons and the new 24-page illustrated book telling all about the C.T.S. Master Shop-Method Home Training Course in Radar, Sonar, Television, Radio and Electronics, and the many opportunities this new field offers.

Name Age.....

Address

City State.....



prepare for your career in

ELECTRONICS RADIO-TV COMPUTERS


and other fields of
ELECTRICAL ENGINEERING

At MSOE, you can equip yourself for a career in many exciting, growing fields:
**MISSILES • RADAR • AVIONICS
AUTOMATION • RESEARCH
DEVELOPMENT • ELECTRICAL
POWER • ROCKETRY**

When you graduate from the Milwaukee School of Engineering, you are prepared for a dynamic career as an Electrical Engineer or Engineering Technician. Under a faculty of specialists, you gain a sound technical education in modern, completely equipped laboratories and classrooms. As a result, MSOE graduates are in great demand and highly accepted by industries nationally.


At MSOE, you will meet men from all walks of life and all parts of the country — some fresh out of high school or prep school, others in their twenties — veterans and non-veterans.

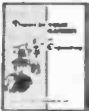You can start school in any one of four quarters and begin specializing immediately. Engineering technicians graduate in 2 years with an Associate in Applied Science degree. For a Bachelor of Science degree in Engineering, you attend 4 years. A 3-month preparatory course also is available.



FREE CAREER BOOKLET!

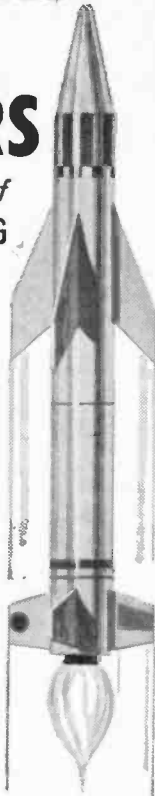If you're interested in any phase of electronics, radio or television, be sure to look into the programs of study offered by the Milwaukee School of Engineering. Just mail the coupon.



MILWAUKEE SCHOOL OF ENGINEERING

Dept. RTVE-60, 1025 N. Milwaukee St., Milwaukee, Wisconsin

Please send FREE Career Booklet. I'm interested in
 Electronics Electrical Power Television
 Mechanical Engineering Radio Computers
 Electrical Engineering Industrial Electronics

PLEASE PRINT

Name _____ Age _____

Address _____

City _____ Zone _____ State _____

I'm eligible for veterans education benefits

MS-125

Experimenters!

BACK-ISSUE BARGAINS!

**Two for \$1.00
Four for \$2.00
\$2.50 for Six**

These back issues of the **RADIO-TV EXPERIMENTER** are still available:



538 Contains over 40 projects. Radio direction finder, hidden metal detector, low-cost speedlight, remote control fireboat, shortwave receivers, radiotelephone station, radio-controlled garage door opener. Single copy, 50¢

551 Includes sun-cell TRF receiver, plans for experimenter's test bench, decade ohm box, electronic tie-tac-toe, split-powered oscillator, photoelectric controls, signal tracer, portable hi-fi record player, single-tube organ. Single copy, 75¢

559 Has 43 different project plans including 15-meter ham rig, simple signal mixer, electronic moisture tester, finger-clip radio, telethermoscope, portable phonograph, hi-fi tone arm, strobe-flash unit. Single copy, 75¢

562 Contains 53 make-it-yourself projects: transistorized intercom, Citizens Band 2-way radio, 7-tube FM tuner, 6-meter ham rig, sun-celled motor, stereo music center. Single copy, 75¢

**Two for \$1.00
Four for \$2.00**

Also available, these **SCIENCE EXPERIMENTERS**

557 Plans for 40 projects including Van de Graaff generator, Tesla coil, Wimshurst static machine, cloud chambers, light ray tracer, satellite scope, solar furnace. Single copy, 50¢

563 Contains over 50 science projects including repulsion coil, satellite camera, tone generator, atmospheric voltmeter, infrared detector. Single copy, 75¢

RUSH COUPON TODAY
Satisfaction guaranteed

SCIENCE and MECHANICS, Dept. 333
450 East Ohio St., Chicago 11, Illinois

Enclosed is \$..... Please send me:

- All SIX of the Experimenters for \$2.50.
- The TWO RADIO-TV Experimenters circled for \$1.00.

538 551 559 562

- All FOUR RADIO-TV Experimenters for \$2.00.
- Both SCIENCE Experimenters for \$1.00.
- The circled issues at single-copy prices:

538 551 559 562 557 562

NAME _____

ADDRESS _____

CITY _____

ZONE _____

STATE _____

NOW! McGraw-Hill's Low-Cost Home Course Shows

HOW TO FIX TV Radio and Record Changers RIGHT AWAY

— even if you've never looked inside a set before!



Examine Entire Course **FREE** for 10 Days!



AT LAST! at Amazing LOW COST — the Most Complete TV-Radio Repair Course Ever Published. TELLS and SHOWS how to do Every Job Quickly and Easily — Make GOOD MONEY, Full or Spare Time, in the BOOMING Repair Business

How would you like to be boss of a nice TV-radio-record changer repair business — making \$50 to \$75 spare time, or \$150 and up in your own shop?

Now, thanks to McGraw-Hill's new 6-volume Course, you can get started right away! This Course brings you EVERYTHING you need to "cash in" on the TV-Radio-Changer boom. Over 2,350 pages of money-making ideas and techniques by top factory engineers and electronics experts. TWO HUGE TROUBLESHOOTERS tell exactly WHERE to begin, WHAT tools to use. THREE GIANT REPAIR MANUALS tell and show how to FIX every trouble the easy way, "polish off" every job like a whiz. Complete Home Study Volume guides you every step of the way, tells how to build your business into a spare- or full-time MONEY-MAKER!

EARN While You Learn

Tested — and now used in repair shops and by electronics instructors — Course volumes are simple enough for green beginners, amaze "pros" with quick, easy methods. Start your doing simple repairs — and earning money — from very first chapter. ABC pictures and directions make tougher jobs a "snap." Before you finish you earn many times Course's low cost.

NO previous training needed; TV repair business pays well in good times or bad. NO complicated formulas. PLAIN ENGLISH pictures and directions cover ANY job on EVERY SET — tubes, circuits, speakers, new ac/dc, am/fm/shortwave portables, Color TV, even what to charge for every job and how to get customers!

Age and Education No Barrier

Age doesn't matter. Past experience doesn't matter. Your formal education isn't important. Over 40 MILLION TV sets, 130 MILLION radios — and the shortage of repairmen — mean big money for you. Course makes it easy to cash in, start your own secure, profitable business.

SEND NO MONEY

Try Course 10 days FREE. (We pay shipping!) If you don't agree it can get you started in a money-making repair business — return it, pay nothing. Otherwise keep it, earn while you learn; and pay the low cost on easy terms. Mail coupon NOW. McGraw-Hill Book Co., Dept. SMA-4, 327 W. 41st St., New York 36, N. Y.

PARTIAL CONTENTS

- 1 Television and Radio Repairing — Testing, repairing, replacing parts, 566 pages, 700 "This-Is-How" pictures, diagrams. By John Markus, Feature Ed., Electronics Magazine.
- 2 Practical Radio Servicing — Easy-to-follow directions, diagrams, drawings — with job sheet for every repair job, 599 pages, 473 illus. By William Marcus, Alex Levy, Electronic Training Experts.
- 3 Profitable Radio Troubleshooting — WHERE to look and WHAT to do for every trouble. How to avoid costly mistakes, handle customers profitably, 330 pages, 153 "how to" illus. By William Marcus, Alex Levy.
- 4 Profitable TV Troubleshooting — Short-cuts to SPOT and FIX every trouble—fast, for big profits. By Eugene A. Anthony, Service Consultant, General Elec. Co.
- 5 Repairing Record Changers — Step-by-step pictures and directions — how to set up service bench, etc. 278 pages, 202 A-B-C pictures. By Eugene Ecklund, Eng. DuMont Lab., Inc.
- 6 Complete Home Course Outline — Getting started in television and radio servicing. How to get the most out of your Course. How to get ahead FAST. By John Markus.

This Amazing Offer Saves You **\$12.85**
6 BIG VOLUMES
Including Home Course Outline! Shows How to Get Ahead Fast

THIS COUPON SAVES YOU \$12.85

McGraw-Hill Book Co., Dept. SMA-4 327 West 41st St., New York 36, N. Y.

Send me — postpaid — for 10 DAYS' FREE TRIAL the 6-Vol. McGraw-Hill TV, Radio and Changer Servicing Course. If okay, I'll remit \$4.95 in 10 days; then \$5.00 monthly for 5 months. (A total savings of \$12.85 on the regular price of Course and Detect-O-Scopes.) Otherwise, I'll return Course in 10 days; pay nothing.

ALSO send FREE (to KEEP whether or not I keep Course) the TV, RADIO, and CIRCUIT DETECT-O-SCOPE CHARTS, plus up-to-the-minute 1960 Transistor Detect-O-Scope — total value \$4.00.

Name..... (Please Print Clearly)
Address.....
City..... Zone No..... State.....
(if any)

CHECK HERE if you prefer to enclose first payment of \$4.95 with coupon. Same easy pay plan; same 10-day return privilege for full refund. SMA-4

Free 4 Valuable Repair Aids: TV, RADIO, CIRCUIT and TRANSISTOR Detect-O-Scopes (Total Value \$4.00)



FREE — whether you keep Course or not — FOUR DETECT-O-SCOPE Charts. TV and RADIO Scopes enable you to spot tube troubles in a jiffy. CIRCUIT and TRANSISTOR Scopes spot circuit and transistor troubles. Make fix-it jobs easier, faster. 16 x 21 inches each. ALL FOUR (worth \$4.00) yours FREE.

TRANSISTORIZED POCKET FM RADIO AND CONVERTOR KIT



Fun for the youngster or the veteran in the electronic field . . . A 3-way transistorized pocket FM radio and tuner which tunes the complete FM band from 88 to 108.6 megacycles plus aircraft band from 109 to 145 megacycles. This fantastic set can be used in your car, home, or pocket, and needs no antenna or ground wires. Completely non-directional, this compact FM radio and tuner will play where all other radios have failed. Set has been demonstrated under an X-ray beam and near other electrical devices without any static or distortion. Featuring a two-stage circuit, this FM radio and tuner will produce music of top quality from stations located many miles from the receiver. Kit comes complete with easy-to-build instructions.

KIT, Complete with Special Hi-Fi Earpiece with earmold, cord, and plug, \$29.95 postpaid. (less Earpiece, \$26.95)

RADIO-TV SERVICING AID



Powerful 7-power magnifying glass mounted on 3" tweezers. Excellent tool for

getting into difficult and hard-to-see places. Ideal for radio kit builders, model craftsmen and for the Radio-TV service technician. Special low price, \$2.25 postpaid . . . A REAL SERVICE AID BARGAIN!

TWO-STAGE TRANSISTOR AMPLIFIER OR PRE-AMP KIT



You can build a powerful two-stage amplifier or pre-amp which can be used as a phonograph amplifier or amplifier for a crystal set, and as a pre-amp for crystal or magnetic pick-up. Kit comes complete with two transistors, volume control with switch, attractive plastic case with a snap bottom, and is powered with a single penlight cell with an output of nearly $\frac{1}{2}$ of a watt. Complete with easy-to-follow instructions. \$6.95 postpaid.


SPECIAL SECTION for RADIO BEGINNERS

Crystal-Set Kit \$1.25 p p
Headphones (double) \$2.25 p p
Ball Bearing Tuning Condenser with Metal Dial and Knob \$1.50 p p
(Free Crystal with each \$10.00 order)

Beginners all Wave Kit Two Stage Circuit with Transistor, High Frequency Tube, Drilled Chassis and all Clips and Wire—\$7.95 less batteries. Many users report up to 12,500 miles on short wave plus the Broadcast Band. Tunes from 16 meters to 160 meters.

WORLD'S SMALLEST TWO BAND RADIO

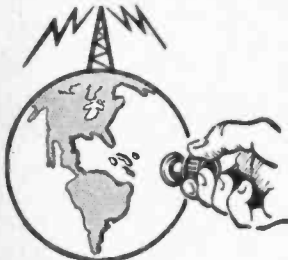TUNE IN THE WORLD OF EXCITEMENT WITH THE WORLD'S FIRST THREE STAGE TRANSISTORIZED TWO BAND RADIO KIT FOR ONLY \$5.00 FULL PRICE—READ CAREFULLY



This set tunes the broadcast band and a click on the band switch lets you enjoy exciting police calls, ship to shore, aircraft, both commercial and military, amateur phone stations, code and foreign stations from all over the world. (It's the best electronic buy ever offered.) Tunes as many stations as sets costing up to \$100.00. Kit includes the following parts: Min-Tube, Min-Tube Socket, a special detector, printed circuit plate, a band switch, a battery switch, a tuning knob, a two band coil, an (Ekeradio) electronic wand, four condensers, two resistors, two phone clips, antenna trimmer, four rubber mounting feet, hookup wire, a coil mounting clip, and a sheet of easy-to-follow instructions. A 722 or a 107 transistor can be used for the third stage (Not furnished). Any phones will work with this set. Two small batteries furnish the power (Not furnished). This can be mounted on your small board or small plastic box. Send only \$5.00, a self-addressed gummed label to facilitate shipping of this fantastic kit, and ten cents in stamps to the address below. If the above instructions are not followed, your order may be delayed several months, so read carefully.


EKERADIO ELECTRONIC DEVELOPMENTS

Dept. E • 650 North Fair Oaks Avenue

Pasadena, California
U. S. Orders Only

Let me send you this amazing- ELECTRONIC KIT!

OWN THIS ELECTRONIC KIT

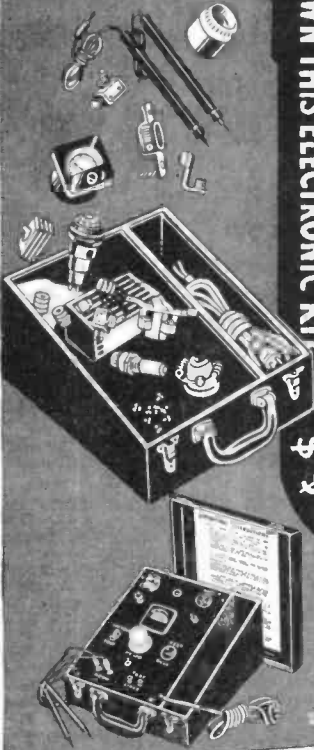

ASSURE YOURSELF OF FINANCIAL SECURITY—INDEPENDENCE

Imagine being able to fix anything electrical from the tiniest home electric shaver to large industrial motors! Having a training that makes you command a better job with higher wages or a business of your own. You do not need previous special schooling. Just the ability to read and be mechanically inclined. We furnish you with everything! One of the kits sent to you is our famous ELECTRONIC KIT, an all-purpose trouble detector which shows you where the trouble lies. Training kits whose assembly will give you practical shop training at home during your spare time!

You learn practical electricity by using your hands. Best of all, these kits are yours to keep and use forever!




FRAZER

REPAIR ELECTRICAL EQUIPMENT!

ILLUSTRATED COURSE SHOWS EVERYTHING

The Christy maintenance and repair course is written in simple, easy-to-understand language. Each section is profusely illustrated by photographs and drawings and shows you what troubles to look for and then how to correct them. In addition, our course shows you how to build power tools at low cost. Also teaches you welding, nickel plating, general repairing (saw filing, bicycle and gas stove repairing, etc.). Should complicated technical problems arise or the need for a special repair part, simply call on us. We offer YOU our FREE Advisory Service for LIFE! We teach you how to solicit business get repeat orders and what to charge. The Christy Course plus our home-shop training kits make a combination that will go a long way toward ASSURING YOUR SUCCESS.

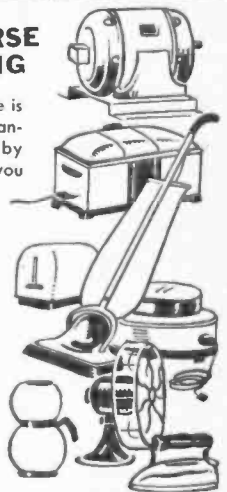

3 EASY STEPS TO SUCCESS

- 1 WE SEND YOU AN ELECTRIC KIT
- 2 WE TEACH YOU ELECTRICAL APPLIANCE REPAIRING
- 3 WE GIVE YOU LIFE-TIME ADVISORY SERVICE

RUSH THIS COUPON TODAY!

CHRISTY TRADES SCHOOL, Dept. A-511
3214 W. Lawrence Ave., Chicago 25, Ill.

Please send me your FREE book on Electric Equipment Servicing and instructions for paying later from EARNINGS WHILE LEARNING!

Name.....Age.....

Address.....

City.....Zone.....State.....

FARM TELEPHONE CABINETS



Slightly used crank style CABINETS (once used everywhere) for Home Hobby Shops. Complete with transmitter, receiver, bells, crank and shelf (Less Generator). Has all of the outside parts. Make beautiful, unique Radio Cabinets, Liquor Chests, Spice Cabinets, Flower Planters, etc. Immediate deliveries assured. \$7.00, F.O.B. Chicago.

TELEPHONES

TALK ROOM TO ROOM


to the house across the road, etc. Enjoy your own private telephone system! Reconditioned cradle phones Guaranteed!

2 for only \$5.00 **\$300**

We can supply everything you need.

WRITE FOR ILLUSTRATED BULLETIN BB-4

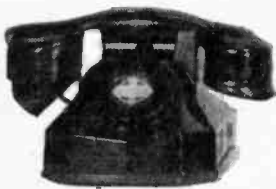MICROPHONE, Dept. BB-4, 1760 W. Lunt Ave. Chicago 28, Ill.



SO EASY IT'S SHOCKING, IF YOU USE ENLARGED PLANS

to build electronic projects. Enlarged size, step-by-step craft print plans—complete with detailed materials lists—are available for the following:

- 191. TESLA COIL. Produces 70,000 volts at 500,000 cps. Spectacular but safe.....\$1.00
- 227. REPULSION COIL. Defies law of gravity—electromagnetically.....\$1.00
- 243. DEMO ELECTRIC MOTORS. Plans for both windmill and engine types.....\$1.50
- 251. SOLAR BATTERY AND MOTOR. Battery's volt at 180 ma drives motor.....\$1.50
- 258. SUN-POWERED RELAY. Light-activated control with a variety of practical applications.....\$1.00
- 264. HI-FI FM RECORD PLAYER. Phono oscillator, arm and turntable for hi-fi reproduction.....\$1.00
- 265. ELECTRICAL COIL-WINDING MACHINE. Motor-powered with foot-controlled reactor.....\$1.00
- 279. WIMSHURST STATIC MACHINE. Constant source of static electricity.....\$1.50
- 283. VAN DE GRAAFF GENERATOR. Costs \$30 to build. Produces up to 250,000 volts.....\$1.50
- 301. VAN DE GRAAFF GENERATOR. Produces up to 400,000 volts. This is the apparatus that can stand your hair on end!.....\$1.50

SAVE MONEY! If you order two or more craft prints, deduct 25¢ from the regular price of each print. Thus, for two prints, deduct 50¢; three prints, 75¢, etc. Use handy coupon below. Satisfaction guaranteed or money back.

SCIENCE and MECHANICS, Dept. 227
450 East Ohio St., Chicago 11, Illinois

Enclosed is \$_____ Please send me the circled plans.

These plans are \$1.00 each

191	227	258	264	265
-----	-----	-----	-----	-----

These plans are \$1.50 each

243	251	279	283	301
-----	-----	-----	-----	-----

NAME _____

ADDRESS _____

CITY & ZONE _____

STATE _____

Here's 20¢. Please send me your illustrated catalog of 196 craft print plans.



YOU NEED THIS

FREE GIANT 1960 B-A CATALOG

A Complete Buying Guide for Everything in

RADIO TV ELECTRONICS

ANNUAL CATALOG 601

BA

SINCE 1927

204 KING-SIZED PAGES

EVERYTHING IN RADIO TV AND ELECTRONICS

100'S OF NEW ITEMS LISTED HERE FOR 1st TIME

21 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

BURSTEIN-APPLEBEE CO.

Dept. RE, 1012 McGee St., Kansas City 6, Mo.

Send Free 1960 B-A Catalog No. 601.

Name.....

Address.....

City..... State.....

SEND FOR IT TODAY




LET RCA TRAIN YOU IN ELECTRONICS


RCA Institutes, one of the world's largest electronic technical schools, offers a Home Study Course in . . .

ELECTRONICS FOR AUTOMATION

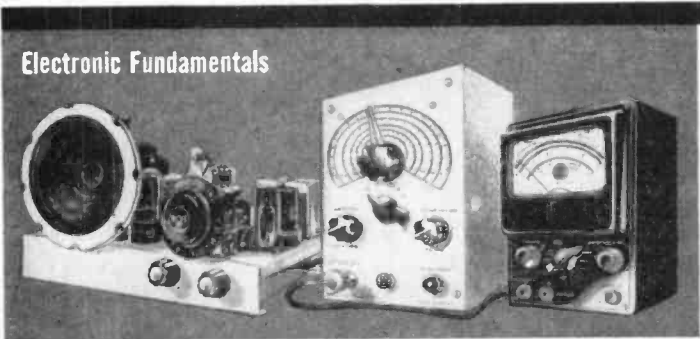
. . . Now you have four comprehensive courses for your electronic training . . . from basic electronic theory to the more advanced principles of color TV and Automation.



Electronic Fundamentals

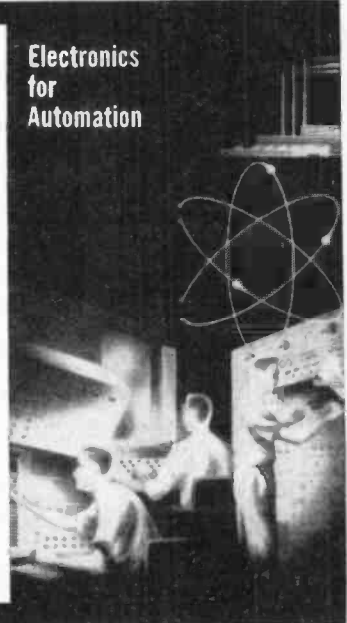

Electronics for Automation

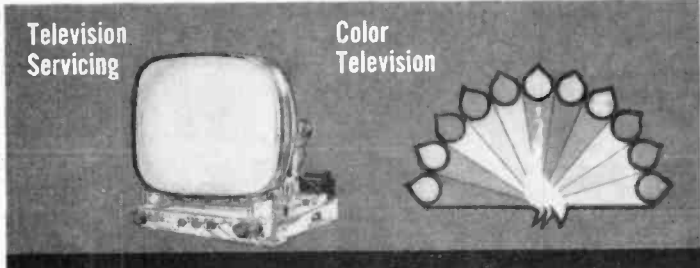


Television Servicing

Color Television

Practical work with the very first lesson. Pay-as-you-learn. You need pay for only one study group at a time.

Send for our 64 page Home Study Catalog

FREE!

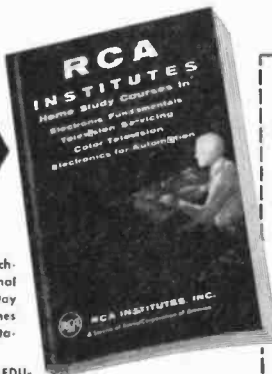

RESIDENT SCHOOL offers Technical Institute and Vocational School Courses in Electronics. Day and Evening classes start 4 times each year. Resident School Catalog sent free on request.

ANOTHER WAY RCA SERVES EDUCATION THROUGH ELECTRONICS

RCA INSTITUTES, Inc. Home Study School, Dept. RTVE-20

A Service of Radio Corporation of America
350 West Fourth Street, New York 14, N. Y.

Without obligation, send me the FREE catalog of Home Study Courses. No salesman will call.

Name Age

Address

City Zone State

Veterans: Enter discharge date

CANADIANS — Take advantage of these same RCA courses at no additional cost. No postage, no customs, no delay. Send coupon to: RCA Victor Company, Ltd., 5001 Cote de Liesse Rd., Montreal 9, Quebec To save time, paste coupon on postcard.

New Isotronic Training Method!

LEARN TV REPAIR IN ONE SHORT WEEK

Now, after 5 years research—a dynamic TV training technique that makes others obsolete! If you've waited for a chance to have your own prosperous business, here's an opportunity to make up to \$150 weekly, *almost immediately!*
NO EXPENSIVE TRAINING — NO LONG STUDY!

You want to get started *servicing* TV sets — not building them! So, why pay up to \$250 for high-priced lessons and equipment . . . study long months? Our revolutionary **ISOTRONIC** method qualifies you to handle any make TV set right away! All the complicated technical theory is already taken care of by our Scientists! This new technique — hailed the most *practical* in the field — was developed by two of the industry's most respected scientists, in cooperation with every major American TV manufacturer!

PUT YOUR "KNOW HOW" TO WORK FOR PROFIT!

In addition to the most *streamlined* training program of its type, you also benefit from a complete Business Plan that explains fully how to start, conduct, and expand your own TV Service business. Written by expert business consultants. Packed solid with practical know-how instead of theory! Yes, a complete "Business Package" designed to quickly bring you the good things in life that come with your own successful business.

FREE LESSON PROVES ISOTRONIC METHOD WORKS!

For *conclusive proof*, send now for full details and **FREE SAMPLE LESSON**. Apply it to your own ailing set or a friend's — *repair it without a single tool or testing device* — convince yourself that the amazing Isotronic method can put you in a profitable TV business of your own, *in one short week!* Write today — *free lesson supply limited!* (No obligation, no salesman will call.)
TV SERVICING SYSTEMS, Dept. D-872
1038 So. La Brea, Los Angeles 19, California

FREE!
Sample
Lesson

INVENTIONS WANTED!

**140 Wealthy Manufacturers
Ready to Pay Top Prices**

WHEN you get an idea you think may be worth thousands of dollars—a brand-new product wanted by everybody; a way to improve a product already in use; a lower-cost, easier method of servicing, making, or doing something—you can know exactly **HOW** and **WHERE** to cash in on it and make big profits.

Our book, **HOW TO FIND A BUYER FOR YOUR INVENTION**, reveals hundreds and hundreds of *needed* inventions in every type of business. Lists 140 manufacturers who are eager to buy inventions (patented or unpatented) . . . and pay top cash. Tells you **WHO** to contact and **HOW** to sell—helps you get the most cash or royalties for your ideas or inventions!

WHY SO MANY INVENTORS FAIL

Few inventors know how to cash in on their ideas. Some spend their entire lives literally sitting on a gold mine without ever getting to the right man in the right firm. The secret of selling your invention—and your short-cut to success as an idea man—is in knowing **WHERE** your ideas are actually needed, and **HOW** to contact the man who will say "Yes—BUY!"

That is exactly what the editors of **SCIENCE** and **MECHANICS** have now made easy for you to do. Their brand-new guide helps you get the *right contact* in the *right firm*. It lists hundreds of inventions urgently needed by top manufacturers. Tells you the *name and title* of the man to contact in each firm to make a quick sale!

SEND NO MONEY

Examine Guide FREE for 5 Days!

Just mail coupon below and we will rush you a copy of "How to Find a Buyer for Your Invention" to examine **FREE** for five days. If not convinced that it is worth many times its low cost, simply return it and owe nothing. You don't risk a penny.

**SCIENCE and MECHANICS, Dept. 412
450 East Ohio St., Chicago 11, Illinois**

Please send me—for 5 days' **FREE EXAMINATION**—a copy of "How to Find a Buyer for Your Invention." Unless completely satisfied with book I may return it in 5 days and owe nothing. Otherwise I will keep it and send you \$2.95, plus 25¢ to cover postage and handling.

NAME

ADDRESS

CITY ZONE

STATE

SAVE Money! Enclose only \$2.95 **WITH** this coupon. Then we prepay delivery charges. Same 5-day return privilege for full refund applies.



* **FREE**

Fill in coupon for a **FREE** One Year Subscription to **OLSON RADIO'S** Fantastic Bargain Packed Catalog — Unheard of **LOW, LOW, WHOLESALE PRICES** on Brand Name Speakers, Changers, Tubes, Tools, Hi-Fi's, Stereo Amps, Tuners and other Bargains.

NAME _____

ADDRESS _____


CITY _____ ZONE _____ STATE _____

If you have a friend interested in electronics send his name and address for a **FREE** subscription also.

**OLSON RADIO
CORPORATION**

102 S. Forge St., Akron 8, Ohio

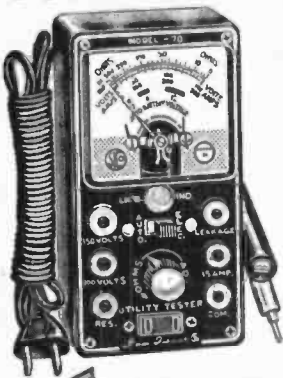Superior's New Model 70 UTILITY TESTER® FOR REPAIRING ALL ELECTRICAL APPLIANCES and AUTOMOBILE CIRCUITS



As an electrical trouble shooter the Model 70:

- Will test Toasters, Irons, Broilers, Heating Pads, Clocks, Fans, Vacuum Cleaners, Refrigerators, Lamps, Fluorescents, Switches, Thermostats, etc.
- Measures A.C. and D.C. Voltages, A.C. and D.C. Current, Resistances, Leakages, etc.
- Will measure current consumption while the appliance under test is in operation.
- Incorporates a sensitive direct-reading resistance range which will measure all resistances commonly used in electrical appliances, motors, etc.
- Leakage detecting circuit will indicate continuity from zero ohms to 5 megohms (5,000,000 ohms).

As an Automatic Tester the Model 70 will test:

- Both 6 Volt and 12 Volt Storage Batteries • Generators • Starters • Distributors
- Ignition Coils • Regulators • Relays • Circuit Breakers • Cigarette Lighters • Stop Lights • Condensers • Directional Signal Systems • All Lamps and Bulbs • Fuses
- Heating Systems • Horns • Also will locate poor grounds, breaks in wiring, poor connections, etc.



INCLUDED FREE This 64-page book—practically a condensed course in electricity. Learn by doing.

Just read the following partial list of contents: What is electricity? • Simplified version of Ohms Law • What is wattage? • Simplified wattage charts • How to measure voltage, current, resistance and leakage • How to test all electrical

appliances and motors using a simplified trouble-shooting technique.

- How to trace trouble in the electrical circuits and parts in automobiles and trucks.

Model 70 comes complete with 64 page book and test leads. **Only \$15⁸⁵**

Superior's New Model 82A A truly do-it-yourself type



TUBE TESTER

TEST ANY TUBE IN 10 SECONDS FLAT!

- 1 Turn the filament selector switch to position specified.
- 2 Insert it into a numbered socket as designated on our chart (over 600 types included).
- 3 Press down the quality button—

THAT'S ALL! Read emission quality direct on bad-good meter scale.

FEATURES:

- Tests over 600 tube types.
- Tests OZ4 and other gas-filled tubes.
- Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings.
- Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence.
- Dual Scale meter permits testing of low current tubes.
- 7 and 9 pin straighteners mounted on panel.
- All sections of multi-element tubes tested simultaneously.
- Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms.

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82A will outperform similar looking units which sell for much more—and as proof, we offer to ship it on our examine before you buy policy.

Model 82A comes housed in handsome, portable Saddle-Stitched Texon case. **Only \$36⁵⁰**
(Picture Tube Adapter available for \$5.50 additional)

SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.

Try any of the above instruments for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. No Interest or Finance Charges Added if not completely satisfied return unit to us; no explanation necessary.

MOSS ELECTRONIC, INC.

Dept. D-707 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.

- Model 70 Total Price \$15.85
- \$3.85 within 10 days. Balance \$4.00 monthly for 3 months.

Name.....
Address.....
City..... Zone..... State.....
All prices net. F.O.B., N.Y.C.

- Model 82A Total Price \$36.50
- \$6.50 within 10 days. Balance \$6.00 monthly for 5 months.

Include Model 82A Picture Tube Adapter at \$5.50

Dr. BRUNO FURST'S

*School of Memory
and Concentration*

WILL SHOW YOU HOW TO

Remember

**NAMES, FACES, FACTS,
FIGURES & BLUEPRINTS**

For Details See The Article On
Page 77 In This Issue.



**School of Memory
and Concentration**

365 West End Avenue,
New York 24 • SCHuyler 4-8299

NO MORE SMASHED FINGERS!

Atlas NAIL DRIVER and SCREW STARTER

Drives nails safe and straight into wood, concrete, metal or brick — in corners, hard-to-reach places — anywhere. No more lost tempers, bent nails or damaged surfaces due to hammer "misfiring". Ideal for Do-It-Yourselfers, Housewives — anyone who uses a hammer.

**MONEY
BACK
GUARANTEE**



Special Introductory Price **\$1 Each,** Postpaid

Send cash, check or money order. No C.O.D.'s, please.

K-J COMPANY
1423 S. 2nd St. • Milwaukee 4, Wis.

HYPNOTISM RECORD & HAND DISC



Use For
Hypnotizing
Others and
Self-Hypnosis

Use one Hypnotizes others—in groups or individually. Ends by passing hypnotic control to you. Side two—for Self-Hypnosis. Has fascinating Electric Metronome, Echo Chamber Background. Free Eye Fixation Episodes & Instructions. Unbreakable 78 rpm Extended Play Record. Satisfaction Guaranteed or Money Back. Only **\$4.95** p.p.d.



New Invention
Has Hypnotic
Revolving
Lens

Hold the Hypnotic Coin in front of the person you want to Hypnotize. Vibrate the Coin. This sets the revolving lens into motion. It captures and holds your subject's gaze. Get this amazing hypnotic aid complete with secrets and instructions. Money Back if not delighted. Only **\$7.00** p.p.d.

HYPNOTIC-AIDS, Dept. RX-1, 1133 Broadway, N. Y. C. 10


- Enc. \$1.00 — send "Hypno-Coin"
- Enc. \$4.95 — send "Record Kit"

Name

Address

City State

15 One-Evening Projects

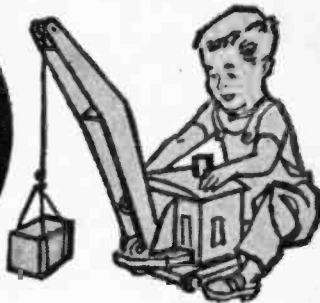

And 63 Other Toys and Games You Can Make

OUR 192-page book **TOYS AND GAMES YOU CAN MAKE** gives detailed plans for making 78 action toys, thrilling games and fascinating playthings (15 of the projects can be completed in just one evening). Only ordinary hand tools are needed, and our simple, easy-to-follow plans show you exactly **HOW** to proceed. The detailed drawings, photographs, materials lists and step-by-step instructions make it easy as A-B-C.

IT'S EASY! IT'S FUN! SAVE MONEY, TOO!

This giant collection of plans for toys ranges from those for pull toys for tiny tots to those for a suitcase-size powercycle for teenagers—it includes something for every child or young adult. You'll have fun, and you'll pocket substantial cash savings by making these projects yourself.

ORDER YOUR COPY—NOW!

Ordinarily a book like this would sell for \$3.00 or more, but while our first edition lasts we will send you a copy for only \$1.95. The quantity is limited, so act now. Attach your check or money order to the coupon below. We guarantee complete satisfaction or your money will be refunded.

SCIENCE and MECHANICS MAGAZINE, Dept. 506
450 East Ohio Street, Chicago 11, Illinois

Enclosed is \$1.95, for which send me, all charges prepaid, a copy of the deluxe edition of your 192-page handbook, **TOYS AND GAMES YOU CAN MAKE**. If I am not completely satisfied, I may return the handbook within 5 days for full refund. I take no risk.

NAME

ADDRESS

CITY ZONE STATE

NOW!
at a price
you can afford!

MAKE MORE MONEY in TELEVISION RADIO-ELECTRONICS

**BETTER...MORE COMPLETE...LOWER COST...
WITH NATIONAL SCHOOLS SHOP-METHOD
HOME TRAINING!**

BETTER... Training that is proved and tested in Resident School shops and laboratories, by a School that is the **OLDEST** and **LARGEST** of its kind in the world.

MORE COMPLETE... You learn **ALL PHASES** of *Television-Radio-Electronics*.

LOWER COST... Other schools make several courses out of the material in our **ONE MASTER COURSE** . . . and you pay more for less training than you get in *our course* at **ONE LOW TUITION!**



These
two FREE books will
show you how!

You get all information
by mail . . . You make
your own decision . . . at
home! **NO SALESMAN
WILL CALL**

TOP PAY... UNLIMITED OPPORTUNITIES LIFETIME SECURITY CAN BE YOURS!

You are needed in the Television, Radio, and Electronics industry! Trained technicians are in growing demand at excellent pay—in **ALL PHASES**, including Servicing, Manufacturing, Broadcasting and Communications, Automation, Radar, Government Missile Projects.

NATIONAL SCHOOLS SHOP-METHOD HOME TRAINING, with newly added lessons and equipment, trains you in your spare time at home, for these unlimited opportunities, including many technical jobs leading to supervisory positions.

YOU LEARN BY BUILDING EQUIPMENT WITH KITS AND PARTS WE SEND YOU. Your National Schools course includes thorough *Practical* training—**YOU LEARN BY DOING!** We send you complete standard equipment of professional quality for building various experimental and test units. You advance step by step, perform more than 100 experiments, and you build a complete TV set from the ground up, that is yours to keep! A big, new TV picture tube is included at no extra charge.

EARN AS YOU LEARN. We'll show you how to earn extra money right from the start. Many of our students pay for their course—and more—while studying. So can you!

LESSONS AND INSTRUCTION MATERIAL ARE UP-TO-DATE, PRACTICAL, INTERESTING. Every National Schools Shop-Method lesson is made easy to understand by numerous illustrations and diagrams. All instruction material has been developed and tested in our own Resident School Shops, Laboratories and Studios.

SEND FOR INFORMATION TODAY . . . it can mean the difference between **SUCCESS** and failure for you! Send for your **FREE BOOK "Your Future in Television-Radio-Electronics"** and **FREE Sample Lesson.** Do it **TODAY**, while you are thinking about your future. It doesn't cost you anything to investigate!

**GET THE BENEFITS OF OUR OVER
50 YEARS EXPERIENCE**

Approved for
GI Training



NATIONAL SCHOOLS

Los Angeles 37, Calif.

YOU GET . . .

- 19 Big Kits—**YOURS TO KEEP!**
- Friendly Instruction and Guidance
- Job Placement Service
- Unlimited Consultation
- Diploma—Recognized by Industry
- **EVERYTHING YOU NEED FOR SUCCESS!**

**SHOP-METHOD HOME TRAINING
COVERS ALL PHASES OF INDUSTRY**

1. Television, including Color TV
2. Radio AM & FM
3. Electronics for Guided Missiles
4. Sound Recording and Hi-Fidelity
5. FCC License
6. Automation and Computers
7. Radar & Micro-Waves
8. Broadcasting and Communications

RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start **NOW** in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment—professionally installed—finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school . . . and part time job while you learn. Check box in coupon for full information.

NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

MAIL NOW TO
NATIONAL SCHOOLS, Dept RKK-40
4000 S. FIGUEROA ST. LOS ANGELES 37, CALIF.
Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME _____ AGE _____


ADDRESS _____

CITY _____ ZONE _____ STATE _____

Check if interested **ONLY** in Resident School training at Los Angeles
VETERANS: Give date of Discharge _____

You are invited to become a charter subscriber to

MOBILEHOME Journal

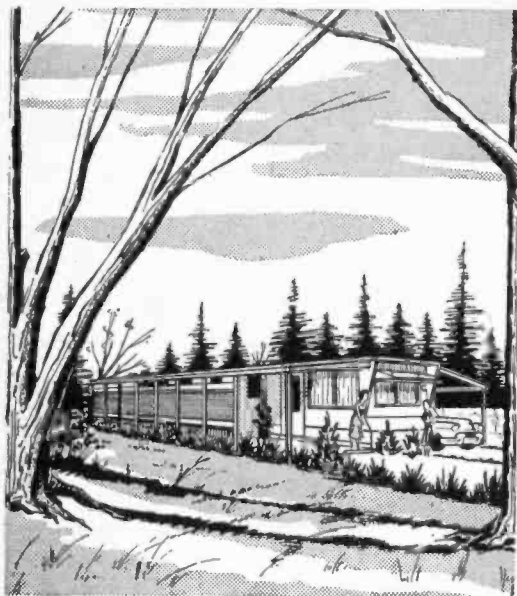

MOBILEHOME JOURNAL, unlike any other publication in its field, recognizes that the mobilehome living story has two sides—male and female. Thus it will include information not only for the head of the house, but also for the heart of the house—features on subjects of vital interest to women as well as articles for the men of the family.

ON SALE APRIL FIFTH

You are cordially invited to become a charter subscriber to MOBILEHOME JOURNAL, the first publication in its field dedicated to serving the interests and needs of the *complete family unit*. You will find features such as these in each exciting issue:

- HOW TO SELECT YOUR NEW MOBILEHOME—a wealth of information for the veteran mobilehomer—and for the novice.
- THE CASE FOR AIR CONDITIONING—a complete analysis of what this essential feature can mean to the typical mobilehomer.
- WHY THEY RELAXED THEIR ZONING—this hard-hitting article explains why a town that once fought tooth and nail against "those gypsies in the trailer camp" has done a complete about-face.
- LET'S HIT THE ROAD—pointers for travel trailer fans on how to enjoy a camp-out in high style—high in everything but cost.

The first issue of MOBILEHOME JOURNAL goes on sale April 5th. It will be an issue you won't want to miss. You can assure yourself of receiving it and the succeeding five issues—six in all—at the special *half-price* charter subscription rate, by filling in the coupon below and mailing it today. Reserve your copy of the first issue now!

HALF-PRICE CHARTER SUBSCRIPTION COUPON

MOBILEHOME JOURNAL, Dept. 565C
527 Madison Ave., New York 22, N. Y.

Please enter my Charter Subscription to Mobilehome Journal
at the special, half-price rate, six issues for \$1.00.

- Cash enclosed
 Please bill me

NAME _____
(PLEASE PRINT)

ADDRESS _____

CITY _____ ZONE _____ STATE _____

(THIS OFFER EXPIRES APRIL 4, 1960)

BECOME A RADIO TECHNICIAN For Only \$22.95

16 RADIO

Reg. U. S. Pat. Off.

CIRCUITS AT HOME **PRACTICAL** only
All Guaranteed to Work! **HOME** **\$22.95**
Progressive Radio "Edu-Kit"® **RADIO** **COURSE** **22**



- NOW INCLUDES**
- ★ 12 RECEIVERS
 - ★ TRANSMITTER
 - ★ SIGNAL TRACER
 - ★ SIGNAL INJECTOR
 - ★ CODE OSCILLATOR
 - ★ No Knowledge of Radio Necessary
 - ★ No Additional Parts or Tools Needed

Unconditional Money-Back Guarantee

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kits" Inc. for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% achievement in its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.

YOU DON'T HAVE TO SPEND HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing. **THIS IS A COMPLETE RADIO COURSE IN EVERY DETAIL.**

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester and the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for Television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a basic education in Electronics and Radio, worth many times the complete price of \$22.95. The Signal Tracer alone is worth more than the price of the entire Kit.

THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well-paying business or a job with a future, you will find the "Edu-Kit" a worth-while investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematic and study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio.

You begin by examining the various radio parts of the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kit contains tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hook-up wire, solder, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio and Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for working with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive Membership in Radio-TV Club, Free Consultation Service, Certificate of Merit and Discount Privileges. You receive all parts, tools, instructions, etc. Everything is yours to keep.

FREE EXTRAS

• SET OF TOOLS

- SOLDERING IRON
- ELECTRONICS TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- VALUABLE DISCOUNT CARD
- CERTIFICATE OF MERIT
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE & QUIZZES
- TELEVISION BOOK & RADIO TROUBLE-SHOOTING BOOK
- MEMBERSHIP IN RADIO-TV CLUB: CONSULTATION SERVICE, FCC AMATEUR LICENSE TRAINING
- PRINTED CIRCUITRY

SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of trouble in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the Dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Statalis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself, I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am asking you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits! The Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuf, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with the Kit is really swell, and finds the trouble, if there is any to be found."

PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

ORDER DIRECT FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7

- Send "Edu-Kit" postpaid. I enclose full payment of \$22.95.
- Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- Rush me FREE descriptive literature concerning "Edu-Kit."

Name

Address

PROGRESSIVE "EDU-KITS" INC.

Progressive Building, Dept. 506 NN, 1184-86 Broadway, Hewlett, N. Y.

Do YOU Like a Good Mystery?

Connoisseurs of the *best* in mystery stories read


ELLERY QUEEN'S Mystery Magazine

The World's Leading Mystery Magazine

Here are some of the reasons why it's the leader—here and abroad (six separate foreign editions):

- **WORLD'S BEST MYSTERY STORIES** selected and edited each month by Ellery Queen, the finest mystery editor in the business, able to secure the best mystery and suspense stories written. Since its inception in 1941, EQMM has published stories by no less than seven Nobel Prize and twenty Pulitzer Prize authors.
- **BEST MYSTERIES OF THE MONTH** reviewed by the famed critic Anthony Boucher, plus a complete listing of all new mystery and suspense hardbounds and paperbacks.
- **SPECIAL SUBSCRIBER COVER** conservatively designed for the home, not available on newsstands.
- **SPECIAL "INVENTORY" PRICES** on paperback titles—big savings on topflight thrillers; big savings on hardbound books, too; and a mail book shopping service that enables you to order mystery books not available at local stores.
- **THREE SPECIAL ISSUES** each year—these sell for 50¢ on the newsstands; subscribers get them at no extra cost.
- **MONEY-BACK GUARANTEE.**

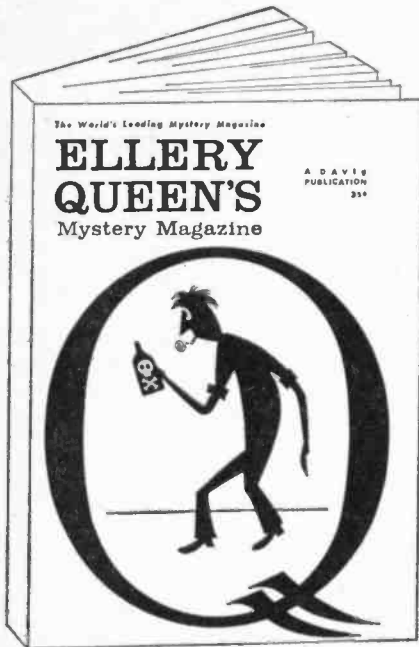These exclusive features make *every* issue of *Ellery Queen's Mystery Magazine* a special treat to everyone who enjoys stories of suspense, crime and mystery. To start receiving your copy every month, send in the coupon below today!



ELLERY QUEEN'S MYSTERY MAGAZINE, Dept. 565B, 527 Madison Ave., New York 22, N.Y.

Please enter my subscription to *Ellery Queen's Mystery Magazine* for:

- | | | |
|---|--|--|
| <input type="checkbox"/> 5 years, \$15.00 | <input type="checkbox"/> 2 years, \$7.00 | <input type="checkbox"/> Cash enclosed |
| <input type="checkbox"/> 3 years, \$10.00 | <input type="checkbox"/> 1 year, \$4.00 | <input type="checkbox"/> Please bill me |
| | | <input type="checkbox"/> Extend present subscription |

NAME _____

(please print)

ADDRESS _____

CITY _____ ZONE _____ STATE _____

Learn Electronics

PREPARE FOR YOUR F. C. C. LICENSE—YOUR TICKET TO A BETTER JOB AND HIGHER PAY!



F.C.C. LICENSE—THE KEY TO BETTER JOBS

An F.C.C. *commercial* (not amateur) license is your ticket to higher pay and more interesting employment. This license is Federal Government evidence of your qualifications in electronics. Employers are eager to hire *licensed* technicians.

WHICH LICENSE FOR WHICH JOB?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

GRANTHAM TRAINING PREPARES YOU

The Grantham Communications Electronics Course prepares you for a **FIRST CLASS F.C.C. license**, and it does this by **TEACHING** you electronics. Each point is covered simply and in detail, with emphasis on making the subject easy to understand. The organization of the subject matter is such that you progress, step-by-step, to your specific objective—a first class F.C.C. license.

CORRESPONDENCE OR RESIDENCE CLASSES

Grantham training is available by correspondence or in resident classes. Either way (residence or correspondence), we train you quickly and well—no previous training required. Even a beginner may qualify for his first class license in a relatively short time.

FOUR COMPLETE SCHOOLS: To better serve our many students throughout the entire country, Grantham School of Electronics maintains four complete Divisions—located in Hollywood, Calif., Seattle, Wash., Kansas City, Mo., and Washington, D.C. All Divisions of Grantham School of Electronics offer the same rapid courses in F.C.C. license preparation, either by home study or in resident classes.

Get your First Class Commercial F.C.C. License Quickly

GRANTHAM SCHOOL OF ELECTRONICS

HOLLYWOOD
CALIF.

1505 N. Western Ave. (HO 7-7737)
Hollywood, Calif.

SEATTLE
WASH.

408 Marion Street (MA 2-7227)
Seattle, Wash.

KANSAS CITY
MO.

3123 Gillham Road (JE 1-6320)
Kansas City, Mo.

WASHINGTON
D. C.

821 19th Street, N.W. (ST 2-3614)
Washington, D. C.

This booklet

FREE!

This free booklet gives details of our training and explains what an F.C.C. license can do for your future.



Upgrade Your Income with a First Class F. C. C. LICENSE

In resident classes or by home study, Grantham training is the easy way to learn more quickly and to prepare more thoroughly for F.C.C. examinations. And your first class F.C.C. license is the quick, easy way to prove to your employer that you are worth more money.

If you already have practical experience in radio-electronics, the Grantham course can add a knowledge of theory and an F.C.C. license to that practical experience. This is most important in qualifying you for higher pay and greater job security.

Our free booklet gives details of how you can prepare quickly for a better job in the rapidly expanding electronics industry. Clip the coupon below and mail it to the Grantham School nearest you.

MAIL COUPON TO SCHOOL NEAREST YOU

(Mail in envelope or paste on postal card)

To: GRANTHAM SCHOOL OF ELECTRONICS

1505 N. Western • Hollywood
408 Marion • Seattle
3123 Gillham Rd. • Kansas City
821 19th, NW • Washington



Gentlemen:

Please send me your free booklet telling how I can get my commercial F.C.C. license quickly. I understand there is no obligation and no salesman will call.

Name _____ Age _____

Address _____

City _____ State _____

I am interested in: Home Study, Resident Classes E-OC


for a fascinating hobby, join the **ROCKHOUNDS!**

get your copy of the **GEM HUNTER'S GUIDE**

the all-time best-selling
guide to gem hunting

The **GEM HUNTER'S GUIDE** contains:

- 1034 ACTIVE GEM MINERAL LOCATIONS** verified and confirmed by regional experts or personal exploration. This is the most comprehensive, detailed listing of North American gem locations available to the hobbyist—or specialist.
- 81 MAPS OF HARD-TO-FIND AREAS**, the largest group of such pin-point accuracy maps ever published.
- 53 FULL-COLOR PHOTOS OF GEMS**—precious and semi-precious gemstones and minerals shown as they occur in nature.

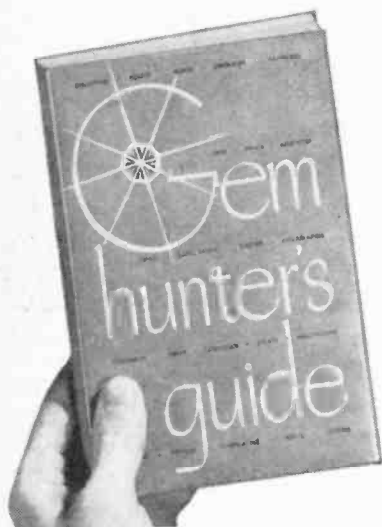

The **GEM HUNTER'S GUIDE** also has:

- 1) Chapters on how to hunt for gem material and how to recognize it when you find it.
- 2) Chapters on how to identify gem material through field testing by checking color, hardness, crystal formation, transparency and other characteristics.
- 3) Special chapters, complete with lists of important discoveries, on diamonds and pearls.
- 4) A chapter on the fascinating and popular hobby of collecting and displaying fluorescent minerals under black light, including a complete table of fluorescent minerals.
- 5) A complete list of state mining and geological bureaus from which maps and publications may be obtained.
- 6) A complete list of museums having mineral displays and the cities in which they are located.
- 7) A complete list of colleges and universities equipped to help the gem seeker.
- 8) A complete bibliography of books and periodicals of importance to the gem hunter.

Order Now! Get your copy in time for the vacation season!

SCIENCE & MECHANICS MAGAZINE, Dept. 110

450 East Ohio Street, Chicago 11, Illinois

Please send me—for 5 days' **FREE EXAMINATION**—a copy of the "Gem Hunter's Guide," packed with pictures, maps, charts, expert advice telling where gems may be found. Unless completely satisfied with the book at the end of 5 days' examination, I may return it and owe nothing. Otherwise, I will keep it and send you \$3.95, plus 50c to cover postage and handling charges.

Name

Address

City, Zone & State

Save 50c postage and handling charges . . . by enclosing only \$3.95 WITH this coupon. Then WE will prepay ALL delivery charges. Return book within 5 days for full refund if not completely satisfied.

SEND NO MONEY


Examine FREE For 5 Days

SEND NO MONEY. Just fill out and mail this coupon and we will send the "Gem Hunter's Guide" to examine Free for 5 days at our risk. If you decide to buy the book, it may be the richest investment—in enjoyment and, perhaps, in cash returns—you ever make. So rush coupon for 5 days Free examination in your own home.

Terrific TRF Portable

You'll find the Terrific outstanding from the standpoints of sensitivity, selectivity, tone and volume—and it costs less than \$20

By FORREST H. FRANTZ, Sr.

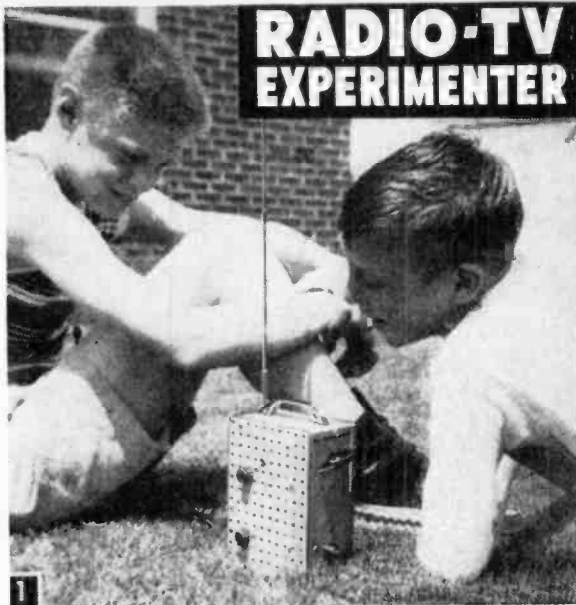

1

The Terrific has a reflexed RF-audio stage, transformerless loudspeaker operation, and is laid out for growth to a superhet or communications receiver.

IF YOU want a portable broadcast band receiver, but wish to avoid the cost and complexity of a superhet, the Terrific is the portable for you.



The first transistor, T1 (see Fig. 3.) performs the dual function of RF amplifier and first audio amplifier. The audio signal is introduced to T1 through capacitor C4. The audio output signal of T1 appears across R4 and is transferred to driver transistor T2 through capacitor C6. The RF signal is introduced to the base of T1 and appears across L2 after amplification. The high-Q tuning circuits C1A-L1 and C1B-L2 assure sharp tuning and high gain. Diode D is the detector. It rectifies the RF signal, and capacitor C7 smooths the peaks of the signal to provide an audio signal across volume control R7.

Transistor T2 is the audio output stage driver. The closed circuit jack between the driver and output stage permits headphone reception. The output stage (transistor T3) drives

the loudspeaker directly. This stage is operated class A, but current consumption has been minimized. Current drain for the entire set is approximately 20 ma. A 45-ohm

voice coil intercom-type speaker permits direct drive. Although this arrangement results in a comparatively low efficiency output impedance match, it eliminates the need for a space-consuming transformer or a miniature transformer which would compromise the frequency response and result in poor tone.

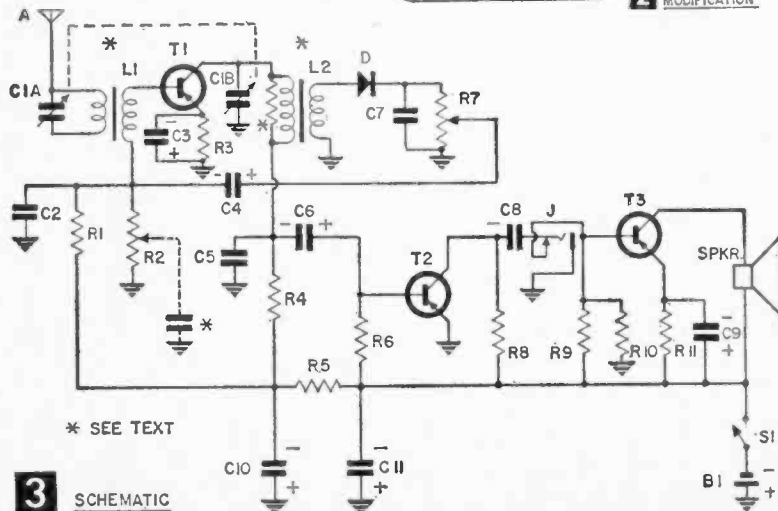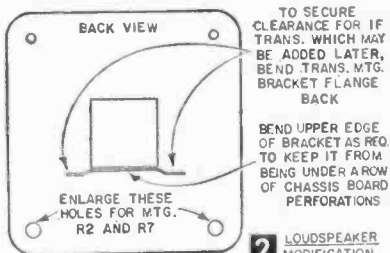Construction. Cut off the shaft of on-off switch S1 at the groove nearest the switch. Cut the shaft of tuning capacitor C1 to a 13/16-in. length. Cut the shafts of the volume control R7 and the control R2 to 7/16-in. lengths. Enlarge the speaker mounting holes on the voice coil connection side of the speaker to 1/4 in. and mount R2 and R7 in these holes. Bend out-



CUT FIBER AT THESE POINTS TO REMOVE COIL FROM MTG.




SEPARATE THE TWO WIRES THAT MAKE UP THIS LEAD

4 MODIFICATIONS TO COIL L1

LEAD REMOVED FROM LUG 2 WHICH COMPLETES CIRCUIT TO LUG 3 CONNECTED TO PIECE OF HOOK-UP WIRE WRAPPED AND TWISTED AROUND COIL AT THIS END

SLUG ADJUSTING SCREW

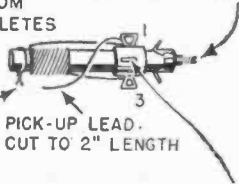

LOOSEN LEADS CONNECTED TO LUG 2. LEAD WHICH COMPLETES CIRCUIT TO LUG 1 IS RECONNECTED

MODIFICATION AND DETAILS L2

5

put transformer mounting flanges on the speaker up toward R2 and R7 slightly as shown in Fig. 2.

Remove the antenna loopstick coil L1 from its mounting board by cutting into the fiber strip that holds it on the board (Fig. 4). Separate the two leads that are soldered together to form the tap on L1. The wire on this coil is litz wire. Try not to break any of the strands, but if you do, apply solder further back on the lead ends.

Now disconnect the two leads connected to lug 2 of the interstage coil L2 (Fig. 5) and separate them. The loose lead which makes a complete circuit to lug 1 is reconnected to lug 2. Connect the other lead (which makes a continuous circuit to lug 3) to a piece of hook-up wire twisted around the end of the coil as shown. Cut the antenna pick-up lead soldered to lug 1 of the coil to a length of 2 in. for connection to the stator of C1B when the radio is assembled. Set the slug adjusting screw to protrude $\frac{1}{4}$ to $\frac{3}{8}$ in. out of the coil.

Next cut out and drill the panel and cabinet sides. These should not be metallic since complete metallic enclosure would shield the antenna coil from radio signals. Perforated Masonite was used for the top panel of the original model to simplify construction. Solid or perforated Masonite may be used for the sides. Although the Masonite perforations in front of the speaker are utilized for sound

transmission, other perforations must be blocked. A cardboard backing sheet was used to prevent front to back speaker sound interference; Fig. 6 shows the layout. Use a taper reamer to make the larger holes in the Masonite. The metal cabinet back is part of a commercially available cabinet, but you may cut and bend your own if you wish.

Cut the perforated Bakelite chassis board with a hacksaw and pocket knife (see Fig. 7). (Cut-outs A, B and C mount IF transformers if the set is converted to a broadcast superhet or a communications superhet, a procedure to be described in a future issue. They may be omitted if you do not wish to have conversion capability.)


Fasten the cardboard baffle to the perforated cabinet top with Duco cement. Mount the speaker, phone jack, tuning capacitor, and antenna coil as shown in Fig. 8. The side of the speaker on which the volume controls are mounted is held in place by a small metal clamp. This may be made from a strip

of metal or by rebending a small bracket. Place enough washers between the tuning capacitor and the Masonite board to obtain a $\frac{1}{4}$ -in. space between them. Fasten the Masonite cabinet front side to the tuning capacitor with a machine screw. Join the two pieces of Masonite to a bracket at the other end. Fasten the antenna coil to the cardboard with Duco cement in the position shown in Fig. 8.

One small piece of perforated Bakelite should be fastened to the antenna coil with Duco, another should be fastened above the speaker clamp with a nut to provide necessary lead tie-down points. Fas-

ten the Bakelite chassis board to the speaker with a machine screw in one of the tapped holes on the back of the speaker. If the output transformer mounting flange on the speaker projects into the chassis board cut-outs, bend it further to allow clearance. The chassis screw also fastens a strip of metal $\frac{1}{2} \times 1\frac{1}{2}$ -in. cut from a tin can. This strip is the common ground tie-down point. Cut gashes into the strip along all four sides so that you can crimp wires in place.

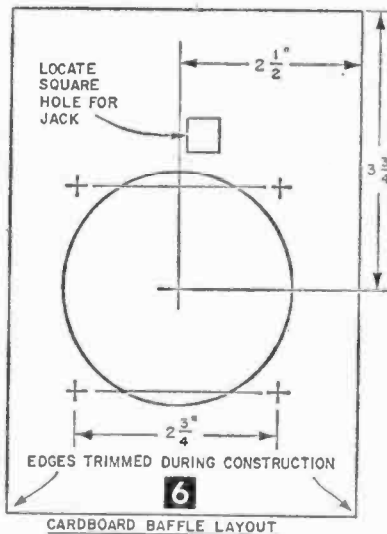Try to make your wiring and parts placement conform as nearly as possible to that shown in Fig. 8 if you wish to convert the set later. Make connections on the chassis board by passing the parts pigtailed and wire lead ends through perforations. The tight mechanical fit that results when two or three




parts pigtails are passed through one hole are very reliable electrically, but solder them for extra assurance. Cut excess lead lengths protruding through the bottom of the chassis board to about 1/16 in. Be careful to avoid passing leads through perforations so situated that leads can short circuit to the speaker frame.

Most of the resistors and capacitors mount above the chassis board as viewed from the back of the set. The transistors mount underneath. Leave transistor T1 pigtails at least an inch long for easy conversion to a superhet receiver later.

Mount the interstage coil, L2, near the back of the tuning capacitor. The resistor shown connected across the primary in the circuit diagram should be connected only if the set oscillates after it has been placed in the cabinet and aligned. It's value will be between 10K and 100K. Orient the coil approximately as shown in Fig. 8. Fasten a piece of aluminum foil 1 1/4 x 3 in. to the cardboard beneath the coil with Duco cement and make a ground connection to the ground tie-down strip from the bracket at the rear of the panel. Make battery leads about 9 in. long.

Three sections of the on-off switch are unused in this project. (They will be used if the set is expanded.) Set the on-off knob pointing straight up and down when the switch is "off." Then, when the switch is turned "on" it will point to the machine screw adjacent to it. Paint the head of this screw red to make it obvious when the set is "on."

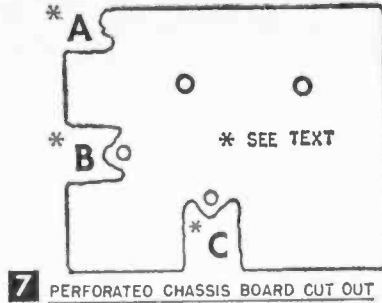The shaft of the tuning capacitor specified is slotted for a spring type push-on knob. If you wish to use a set-screw type knob, build the shaft up to full round with sol-



der. Regardless of the knob you use, a plastic pointer may be fastened to it. The fine black line on the pointer is made by scratching the line into the plastic with an ice pick and flowing India ink into the scratch.

One of the controls, R2, is used only as a fixed resistance in this circuit. It may be replaced with

a fixed resistance of 10K if you don't intend to change the set to a communications superhet receiver later. Or, you may use it as a tone control of sorts by connecting a capacitor of 0.1 to 1 mfd to it as shown in dotted lines on the circuit diagram.

The battery B1 consists of six large penlite cells connected in series to provide 9v. To fasten the six cells together, lay them side by side on a smooth surface and drop a quantity of Duco cement between them. The negative ends of the batteries should be cleaned with a small file before the battery connections are soldered. Use as little heat as possible to solder these connections.


Drill two 1/4-in. holes in the metal cabinet back adjacent to the carrying handle to provide access to the antenna and RF trimmers, and drill a hole in the bottom to provide access to the RF coil-adjusting screw.

A whip-type antenna (see Materials List) was used on this set. The antenna is furnished with a jack and plug. Mount the jack and solder the plug into it. The antenna may be screwed onto the plug for non-portable use. For portable use, the antenna is left fastened in the two fuse clips provided on the outside of the Masonite back as shown in Fig. 9. The clip nearest the antenna coil is used for the connection.

To place the radio in the cabinet, place a piece of thin cardboard 2 1/2 x 8 1/2 in. along the rear of the metal cabinet and extending about 1/2 in. up the sides. Place the 9-v. battery on the cardboard against the cabinet back and ends. Place a strip of wood 1/4 in. thick and about 6 3/4 in. long over the battery. Clamp the strip to the metal cabinet with a screw through the cabinet hole between the batteries. Push the battery leads back into the cabinet so that they won't interfere with the operation of the tuning capacitor. Ease the radio into the cabinet and fasten with self-tapping screws.

Since the radio may be used in the "handle up" or "flat on its back" positions, provide rubber feet for both positions to avoid scratching furniture. (Fasten grommets to the cabinet with rubber-to-metal cement.) Paint or ink the tuning dial calibration on the cabinet front.


Alignment. Since there's no IF alignment

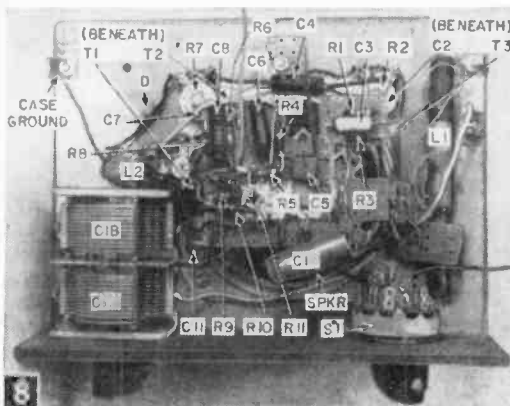

Parts layout of the Terrific.

MATERIALS LIST—TERRIFIC	
Desig.	Description ($\frac{1}{2}$ Watt Carbon Resistors)
R11	270 ohms
R5	470 ohms
R3, R8	1 K
R4, R10	2.2 K
R9	3.3 K
R1	47 K
R6	68 K
R2, R7	10K volume control (Lafayette) VC-34)
C2, C7	.001 mfd. subminiature capacitor (Lafayette C-609)
C5	.01 mfd. subminiature capacitor (Lafayette C-612)
C4, C6	4 mfd., 6v. subminiature capacitor (Lafayette CF-101)
C8	10 mfd., 15v. electrolytic capacitor (Lafayette CF-122)
C3, C9	30 mfd., 6v. subminiature capacitor (Lafayette CF-104)
C10	100 mfd., 15v. electrolytic capacitor (Lafayette CF-126)
C11	160 mfd., 15v. electrolytic capacitor (Lafayette CF-127)
C1A-B	2 gang 365 mmf. variable capacitor (Lafayette C-142)
T1	Texas Instruments 2N252 transistor
T2	Raytheon CK722 transistor
T3	Texas Instruments 2N185 transistor
D	Sylvania IN 34A germanium diode
B1	battery, 9 volts (6 Ray-O-Vac 7R, Burgess Z or Eveready 915 penlite cells in series)
J	miniature closed circuit phone jack (Telex JPM-01)
L1	antenna coil—see text for modification (Miller 2001)
L2	interstage coil—see special instruction in text (Miller 2002 antenna coil)
S1	4P, 2T switch and knob—use one section for on-off switching (Mallory 32 42J)
SPKR	$\frac{3}{2}$ " speaker, 45-ohm voice coil (Quam 3A07Z45)
1	perforated Bakelite chassis board (Lafayette MS-305)
1	perforated Masonite board (Lafayette ML-81)
2	miniature knobs (Lafayette MS-185)
1	knob for tuning dial
1	metal cabinet back (Use back of ICA 29343 or make)
1	handle for cabinet (available in hardware or variety store)
A	whip antenna (Lafayette F-440)

or mixer tracking to worry about, alignment procedure is extremely simple. The preliminary adjustment of L2 described in the construction procedure will cause the set to be nearly in alignment at the low end of the broadcast band when construction is completed. The set should be mounted in the cabinet for final alignment. Align the high-frequency end of the band by tuning in a weak station between 1400 and 1550 kilocycles and adjusting the trimmer capacitors on the side of the tuning capacitor C1 for maximum output. The antenna trimmer will

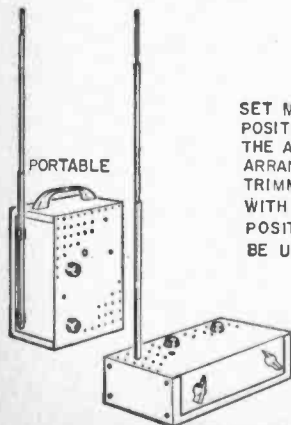


SET MAY BE USED IN EITHER OF POSITIONS SHOWN BY CHANGING THE ANTENNA MOUNTING ARRANGEMENT. THE ANTENNA TRIMMER SHOULD BE TUNED WITH THE ANTENNA IN THE POSITION IN WHICH IT WILL BE USED MOST FREQUENTLY

9

seem to have the greatest effect on tuning. Adjust it till the station comes in at a point on the dial where the RF trimmer tunes the signal to maximum without being all the way in or out. Then tune the set to a weak station between 600 and 700 kilocycles and adjust the tuning slug of the interstage coil L2 for maximum output. Reset the tuning dial to the high frequency end of the broadcast band and readjust the RF trimmer for maximum output.

Out of the metal cabinet the receiver may oscillate at the higher frequency tuning capacitor settings. If it doesn't oscillate when you fasten it in the cabinet and align it, this doesn't matter. But, if the set oscillates when fastened in the cabinet, you'll have to take remedial measures. First, check to be sure that the lead from L2 to the collector of T1 is as short as possible and is dressed against the speaker frame. The same applies to the lead to C1B. If the set still oscillates when it's fastened in the cabinet, connect a 100K resistor across the primary of L2 as shown in the circuit diagram. If oscillation still occurs, try 47K, 33K, and 10K, in turn till oscillation is eliminated. In the original receiver, the 100K resistor did the trick.

Iron Does Double Duty

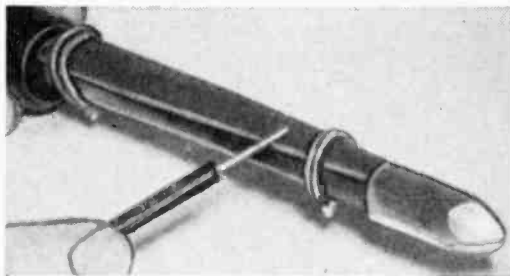

• Quite often a small file is needed to file corroded parts and wires clean before the application of solder. If you want to eliminate the necessity of hunting up such a file every time you have a soldering job to do, attach one to your iron's barrel with heavy solid wire. (You may have to break off the file's tang if it is longer than your iron's barrel.)—J.A.C.

Extending Radio Battery Life

• Many portable battery-operated receivers tend to cease operation long before the batteries have terminated their useful life. This is usually due to the set's oscillator shutting off because of reduced voltages on the tube elements. By increasing the signal feed-back voltage however, the oscillator will continue operation even on reduced voltages. A few extra turns of wire added to the "tickler" winding of the oscillator coil will boost the feedback enough to insure a longer battery life, and considerable saving in replacement dollars.

SIX-METER Amateur Band Converter

If you're a Technician or General Class Amateur interested in six-meter operation, this simple low-cost converter will prove a boon to you for either fixed or mobile use

By JOE A. ROLF,
K5JOK


THIS converter can be constructed with parts from most ham scrap-boxes, but even with new parts its cost will not run much over \$5! Naturally, with only one tube, it is not as hot as many commercial multi-tube units, but it will generally hold its own with crystal-controlled converters costing much, much more.

A 6U8 triode-pentode is used—the pentode section as a mixer, the triode as a tunable local oscillator. Tuning is done with the receiver to which the converter is connected, as with a crystal-controlled unit. But with the local oscillator tunable from 47 Mc. to 54 Mc., a number of different intermediate frequencies can be employed.


With a home broadcast or car radio, for example, the oscillator can be set at 49.4 Mc. so that 49.9 Mc. to 51 Mc. is received when the receiver is tuned across the broadcast band. With a simple screwdriver adjustment, the oscillator frequency can be changed for coverage of any desired 1-megacycle segment of the band. When used with a communications receiver, the oscillator can be set at 48 Mc. and the entire six-meter band covered by tuning from 2 Mc. to 6 Mc. This higher IF not only gives continuous tuning, but provides better image rejection than the commonly used lower IF.

A 2½ x 4-in. piece of ¼-in. Plexiglas, available at hobby shops and many radio supply houses, is used for the chassis. This material can be worked with simple hand tools and greatly simplifies construction. Construction, however, can be modified to allow the use of a mini-box or similar metal box.

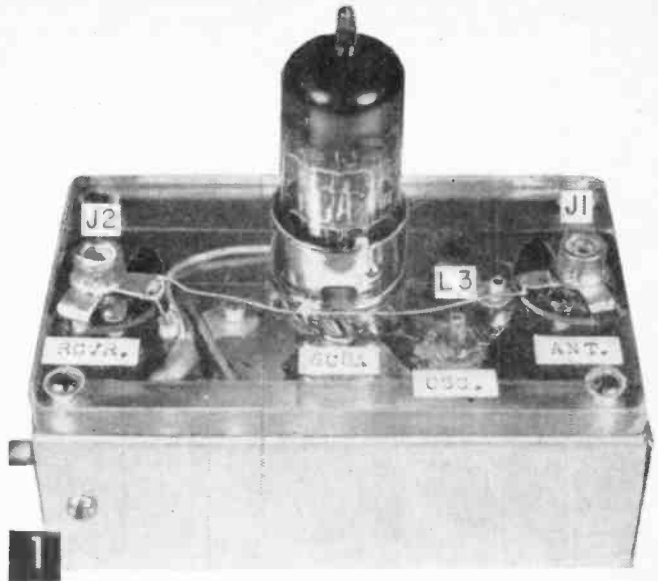Details of the chassis are shown in Fig. 2. Screw holes for the tube socket and antenna




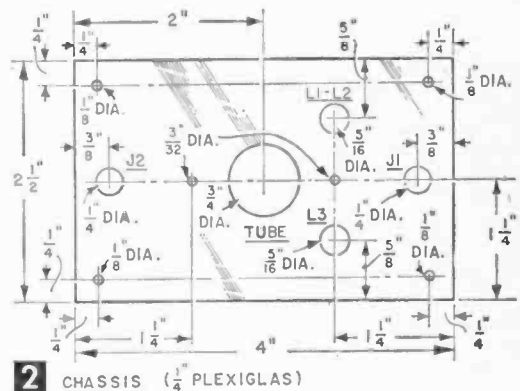Low in cost and simple in construction, the six-meter converter measures only 2½x4 in. when placed in its homemade 1/32-in. aluminum cabinet. With the tube shield in place it is less than 3½ in. high. The cabinet is made in one piece with the exception of the removable end-plate through which the power cord passes.



jacks, J1 and J2, are not shown and should be positioned for the particular sized component used; ⅛ x ¼-in. machine screws mount all parts. By using a 3/32-in. hole, the screws will tap themselves into the soft Plexiglas. The four ⅛-in. holes are for mounting the chassis to its cabinet with ⅛ x ½-in. screws.

The tube socket is placed in the middle of the chassis, the input and output jacks are centered at each end of the chassis, ⅜-in. from the edge. Phono jacks are used and are mounted on top of the chassis with the solder lugs extending through a ¼-in. hole in the chassis. One jack is designated "Antenna Input", the other, "Converter Output." If the converter is intended primarily for mobile use, auto radio antenna jacks should be used in place of the phono jacks for direct connec-

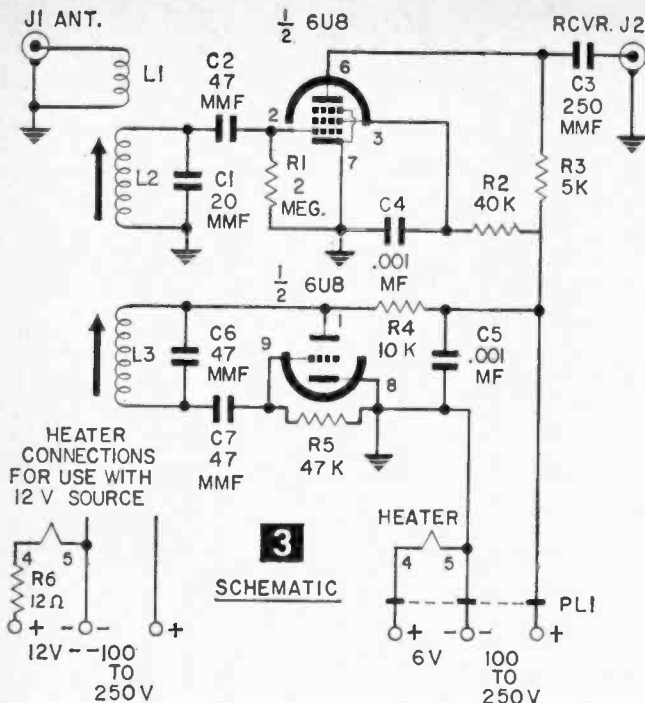

tion to the auto radio, or auto antenna.

Mount a three-lug terminal strip on the underside of the chassis between the output jack and tube socket. The ground (B-minus) and B-plus leads of the power cord and R3 connect to this strip. Capacitor C3 connects from the plate lead end of R3 to the lug on the output jack.

The oscillator and mixer coil forms are mounted midway between the tube socket and the antenna jack. It should be noted that two different types of slug-tuned forms were used. These were $\frac{1}{4}$ -in. dia. scrap-box components, one from a discarded BC radio, the other from a TV set. The form for the oscillator coil had a press-in type mounting and was pressed into a $\frac{5}{16}$ in. chassis hole and secured with Duco cement. The other, a plastic form, had no mounting clip and was glued to the chassis with the slug screw pointing downward. A hole in the bottom of the cabinet permits adjustment of the slug.

Two dissimilar coil forms were used to illustrate the two methods which can be employed in mounting the coils, depending upon the forms available. In the event your scrap-box does not contain suitable slug-tuned forms, they can be obtained from a radio service shop for only a few cents. Most servicemen save discarded coil forms and you'll probably have several dozen to choose from.

For simplest construction, lay out the converter as shown in Figs. 1, 2 and 4. However, the only critical placement (besides keeping leads short) is in the positioning of the RF coils. The mixer and oscillator coils should

be about $\frac{1}{4}$ -in. apart as there is no oscillator voltage injection other than by the coil coupling, tube capacity, and stray circuit capacity. Any form of direct coupling of the oscillator to the mixer circuit will result in excessive pulling (a change in oscillator frequency when the mixer is tuned). The oscillator has sufficient output for good conversion efficiency without direct connection to the mixer.

The cabinet is a three-sided box of $\frac{1}{32}$ -in. aluminum (see Fig. 5). The power cord of the unit passes through the removable end of the cabinet without unsoldering the power cord plug. As with the chassis, the $\frac{1}{8}$ -in. machine screws tap themselves into $\frac{3}{32}$ -in. holes.

The converter is powered by the receiver with which it is used. Requirements are low; 100 to 250v for the plate supply and 6.3 (at 450 ma.) for the filament. These voltages are obtainable from most receivers with the aid of their schematic. A power cord

from the shack's receiver or the auto radio will also prove handy for powering other equipment.

The only difficulty that might be encountered will be with a receiver having 12-v heaters or with an ac-dc set. In the case of a 12-v BC receiver or auto radio, the filament dropping resistor (R6) should be added to the circuit as shown.

If used with an ac-dc type receiver, B-plus voltage for the converter can be taken from

MATERIALS LIST—6-METER CONVERTER

Desig.	Description
C1	20 mmf. ceramic or mica
C2	47 mmf. mica
C3	250 mmf. mica
C4	.001 mmf. disc ceramic
C5	.001 mmf. disc ceramic
C6	47 mmf. ceramic or mica
C7	47 mmf. mica
J1, J2	standard phono jacks
L1	3 turns #28 DCC wire, close-wound next to grid end of L2
L2	4 turns #28 DCC wire, close-wound on $\frac{1}{2}$ " slug-tuned form
L3	3 turns #28 DCC or enamel wire, close-wound on $\frac{1}{4}$ " slug-tuned form (see text)
PL1	3-contact power plug (Cinch-Jones P-303-FHT & S-303-FHT)
R1	2 megohm, $\frac{1}{4}$ watt
R2	40,000 ohm, $\frac{1}{2}$ watt
R3	5,000 ohm, $\frac{1}{2}$ watt
R4	10,000 ohm, $\frac{1}{2}$ watt
R5	47,000 ohm, $\frac{1}{4}$ watt
R6	(for 12-v heater source only) 12 ohm, 4 watt
1	6UB tube
1	small button 9-pin socket, with shield
10	$\frac{1}{8}$ x $\frac{1}{4}$ " machine screws
4	$\frac{1}{8}$ x $\frac{1}{2}$ " machine screws
1 pc	$\frac{1}{4}$ " Plexiglas, $2\frac{1}{2}$ x 4"
1 pc	$\frac{1}{32}$ " (.0312) aluminum sheet, 6 x 7"

An underside view of the Plexiglas chassis showing the placement of components. Three-conductor cable passes through the chassis end-plate.

the receiver, but the ground connection of the converter's antenna coupling coil (L1) should be made with a .001 mfd. capacitor. Filament voltage will have to be supplied by an external 6.3-v filament transformer, or a 6-v battery.

A 2-ft. piece of 52-ohm coax connects the output of the converter to the receiver antenna terminals. This lead can be any convenient length, though an excessively long lead will result in some loss of output. The input lead will depend upon the type of antenna used. Both leads should be fitted with phono plugs.



Alignment of the converter is best done with the aid of a grid dip meter. Since this is a popular piece of equipment with hams, you should have no trouble borrowing one if you don't already have one. With power applied to the converter, check the oscillator output with the meter. Output should be from 47 Mc to 54 Mc, or can be adjusted over this range by changing the coil spacing. Once the oscillator is working, adjust its frequency for the desired IF. If the converter is to be used with a BC receiver, for instance, the oscillator should be set 550 Kc below 50 Mc, or at 49.45 Mc. You will not be able to adjust the oscillator to the exact frequency with the meter, but accurate adjustment can be made later.

Next, adjust the mixer to about 52 Mc with the meter.

With a low IF (such as 550 Kc) some pulling will be noted. This, however, is to be expected at 50 Mc. After the mixer frequency has been adjusted, readjust the oscillator frequency again.

Once the converter has been roughly aligned with a grid dip meter, accurate alignment can be made with the aid of a six-meter transmitter.

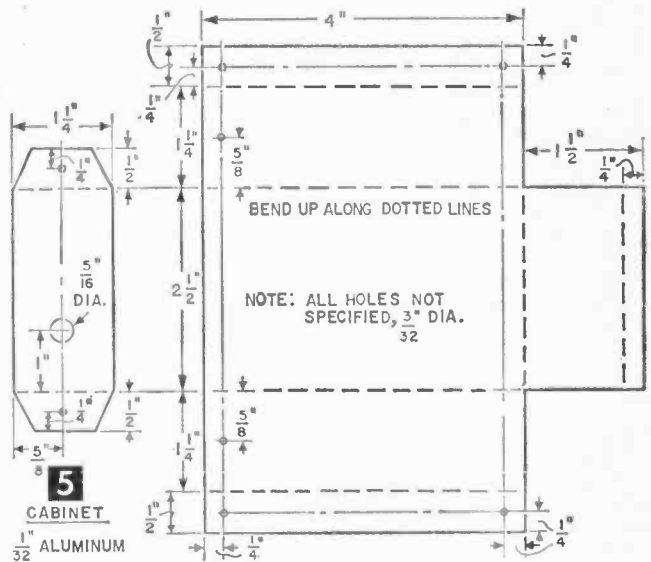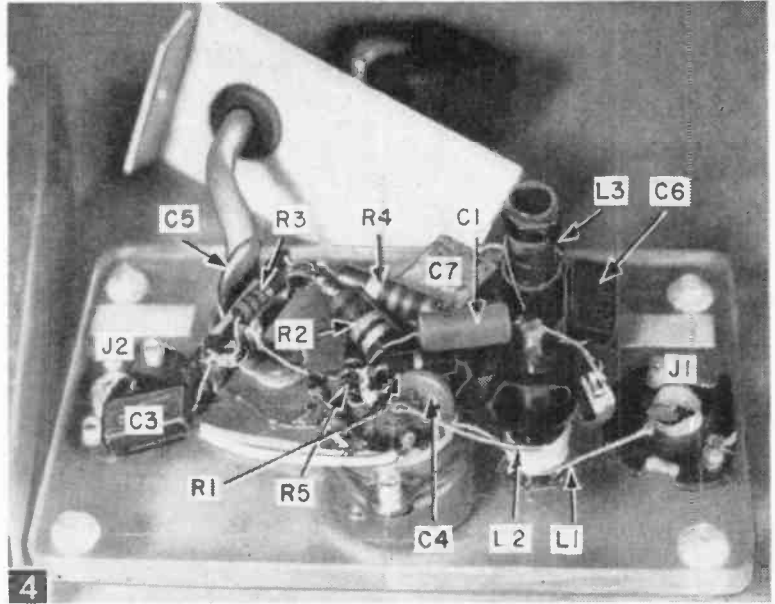While receiving a known, crystal-controlled frequency, adjust the oscillator until the sig-



nal is tuned at the proper frequency by the IF receiver. A 50.1 Mc signal should be read at 650 Kc if a BC receiver is used, or at 2.1 megacycles with a 2 megacycles intermediate frequency.

With fixed operation, excellent performance has been obtained with a simple folded dipole, while the use of a two-element beam has shown that the converter has only slightly less gain and sensitivity than a multi-tube converter using a similar antenna system. For mobile operation the converter has been used with a 51-in. BC-type antenna and has given very good performance on both ground-wave and skip reception.

Two Transistor Utility Amplifier

By FORREST H. FRANTZ, Sr.

SCIENCE and electronic experimenters need an audio amplifier as a basic piece of laboratory equipment. An audio amplifier is useful for amplifying low audio signals, detecting and measuring low audio and ac voltages, signal tracing electronic equipment, and as an auxiliary amplifier to bring earphone equipment signals up to loudspeaker level.

This amplifier will cost about \$15 to build. It is a compact, self-contained unit that has its own batteries and loudspeaker; it needs no external power source or speaker. The input impedance is sufficiently high to permit its use with vacuum-tube circuits. Output terminals are provided for connection to an external meter so that a multimeter may be used in conjunction with the amplifier for measuring very small ac voltages and for audio signal tracing. An RF-IF probe which extends its use for signal tracing is also described.

Circuit Operation. The circuit is shown in Fig. 2. The input signal is introduced at the jack J. Capacitor C1 isolates any dc components which may accompany the signal from the amplifier, but passes audio signals. The signal is presented across R1 and R2. Resistor R1 is in the circuit to keep the input impedance high. This introduces some loss, and if the amplifier is to be used with transistor circuits exclusively, R1 may be eliminated, with a direct connection from J to R2 for increased gain. R2 is the volume control, coupled to T1 through transformer TR1. The primary impedance of TR1 is 10,000 ohms, and the secondary impedance is 2,000 ohms. Thus, the input impedance of T1 is reflected back to the amplifier at 5 times its value.


Resistors R3 and R4 bias the base of T1. Capacitor C3 bypasses audio frequency signals. Resistor R5 biases the emitter of T1 and stabilizes operation over a wide range of temperature. Capacitor C4 bypasses audio signals. Without C4, gain would be reduced considerably. Capacitor C5 bypasses high-frequency signals in the collector circuit of T1 which might otherwise




The utility amplifier can be used with a microphone as above or as a voltmeter audio amplifier.

cause the amplifier to oscillate. Transistor T1 is coupled to T2 through TR2, an impedance matching transformer. Resistors R6 and R7 set base bias for T2, and C6 bypasses audio frequencies. Resistor R8 provides temperature stabilization for T2.

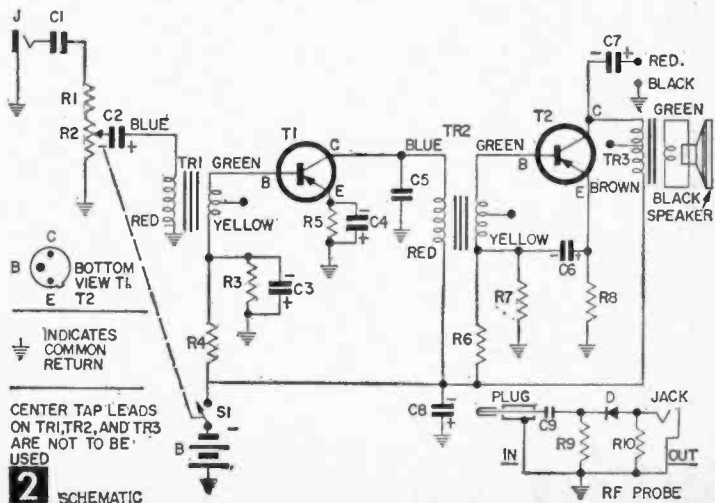
The collector of T2 is coupled to the speaker through the output transformer TR3. This transformer matches the relatively high collector load requirement (500 ohms) to the much lower (3.2 ohms) speaker impedance. Capacitor C7 carries the output signal from



the collector of T2 to an output terminal. An ac voltmeter or oscilloscope may be connected from the output terminal to monitor the output voltage. The amplifier may be constructed in the smallest amount of time if all parts are available when construction is begun (see Materials List), and if this work sequence is followed: 1) Prepare circuit board; 2) prepare panel board; 3) mount components on circuit board; 4) wire circuit board; 5) mount components on panel board; 6) wire panel board; 7) mount circuit board on panel board, and make interconnections.

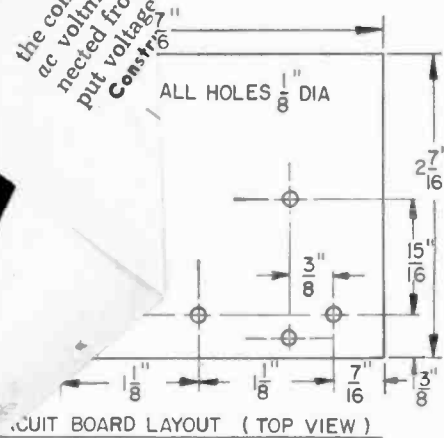

CIRCUIT BOARD LAYOUT (TOP VIEW)

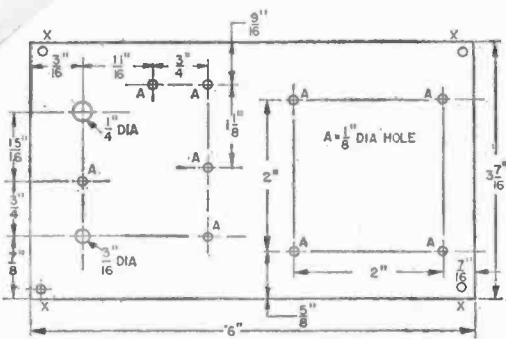

4 CORNER HOLES "X" LOCATED FOR FIT TO CASE
4 PANEL BOARD FRONT VIEW

constructed in the smallest amount of time if all parts are available when construction is begun (see Materials List), and if this work sequence is followed: 1) Prepare circuit board; 2) prepare panel board; 3) mount components on circuit board; 4) wire circuit board; 5) mount components on panel board; 6) wire panel board; 7) mount circuit board on panel board, and make interconnections.

The circuit board as purchased is the right size, but eight of its perforations must be enlarged to 1/8 in. (layout is shown in Fig. 3).


Panel board layout is shown in Fig. 4. The volume and tone of the unit will be improved if a piece of cardboard with a 2 3/8 in. dia. hole for the speaker opening is cemented to the back of the panel board. Trace dimensions from the panel board. The center for the speaker hole center is located by tracing the speaker mounting holes through the board onto the cardboard and drawing straight lines through diagonally opposite hole location marks.

Next, mount transformers TR1, TR2, and TR3 (see Fig. 5). Then, mount and wire the remaining components, making wiring connections on the bottom of the circuit board.

Now mount the components on the panel board and wire as shown in Fig. 6. Cut R2's shaft to a length of 5/16 in. before you mount it. Fill the contact eyelets on the battery holder with solder to avoid later battery contact trouble.

Note that two machine screws (Fig. 6) are 1 1/4 in. long. These are fastened to the panel board with nuts and lock-washers. One of these machine screws serves for speaker mounting, but both are provided to support the circuit board. A nut is placed on each screw with the top of the nut 7/8 in. from the panel. The circuit board is mounted on these and fastened with a nut on each screw. Don't turn them tight initially. You may want to loosen the circuit board to make inter-connections between circuit and panel board. Interconnections are:

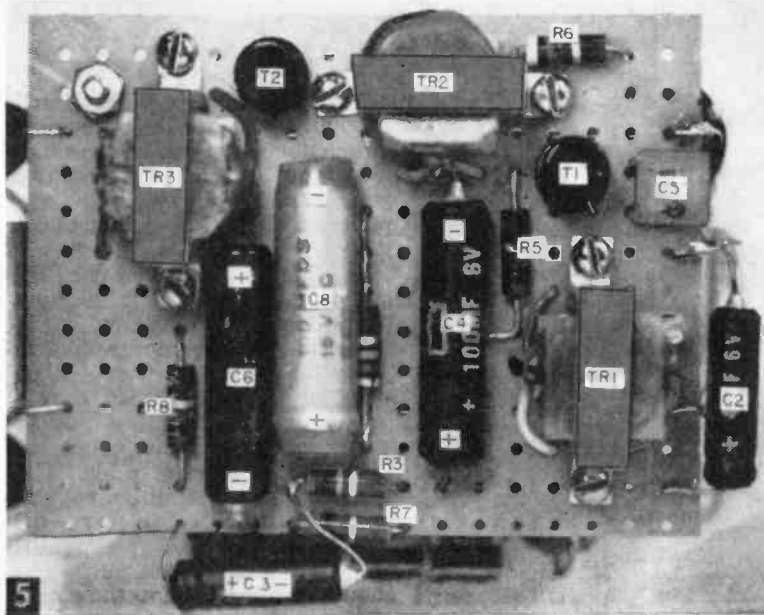- 1) TR3 secondary leads to loudspeaker;
- 2) C7 (negative) to T2 Collector;
- 3) S to circuit board negative bus;
- 4) center terminal R2 to C2 negative;
- 5) battery plus to circuit board common return.




Circuit board mountings.



MATERIALS LIST—UTILITY AMPLIFIER

Desig.	Description	Desig.	Description
R8	100 ohms	SPKR	2½", 3.2-ohm PM speaker (Lafayette MS-170)
R5, R7	1K	B	6v battery—four RCA VS074 cells series connected
R6	4.7K	J	miniature jack (Lafayette MS-282)
R3	10K		binding posts (H. H. Smith 220 Re)
R1, R4	47K		battery holder (Lafayette MS-170)
R2, S1	25K miniature volume control with switch (Lafayette VC-25)		27/16 x 33/8" miniature perforated board (MS-304)
C5	.01 mfd, 75v Ultraminiature capacitor (Lafayette C-612)		311/16 x 63/4" miniature perforated board (MS-305)
C1	.1 mfd, 400v tubular capacitor (Aerovox type P822)		2 x 33/4 x 61/4" case (Lafayette MS-216)
C2	4 mfd, 6v miniature electrolytic capacitor (Lafayette CF-101)		knob (Lafayette MS-185)
C7	10 mfd, 6v miniature electrolytic capacitor (Lafayette CF-103)	RF Probe Parts:	
C3	30 mfd, 6v miniature electrolytic capacitor (Lafayette CF-104)	R9, R10	15K, ½ watt carbon resistors (10%)
C4, C6	100 mfd, 6v miniature electrolytic capacitor (Lafayette CF-106)	C9	100 mmfd mica capacitor (Aerovox CM-20B-101)
C8	100 mfd, 15v miniature electrolytic capacitor (Lafayette CF-126)	D1	Germanium diode (RCA or Sylvania IN34A)
TR1, TR2	10K to 2K driver transformer (Lafayette TR-96)		miniature plug-plug set (Lafayette MS-370)
TR3	500 ohm to 3.2 ohm output transformer (Lafayette TR-95)		small plastic bottle approximately ½" diameter by 2" long (available at drug store prescription counters)
T1, T2	2N321 transistor (General Electric)		(Use Lafayette MS-281 plugs and about 2' of Belden 8411 shielded microphone cable for the input audio test lead)

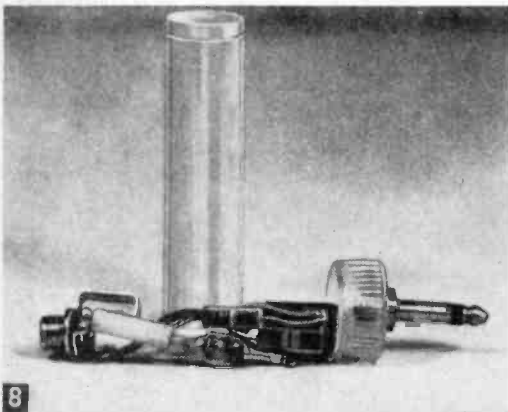All components for this project may be obtained from Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, New York



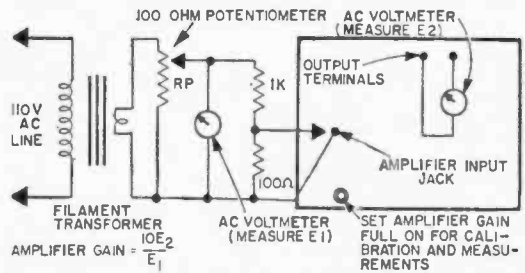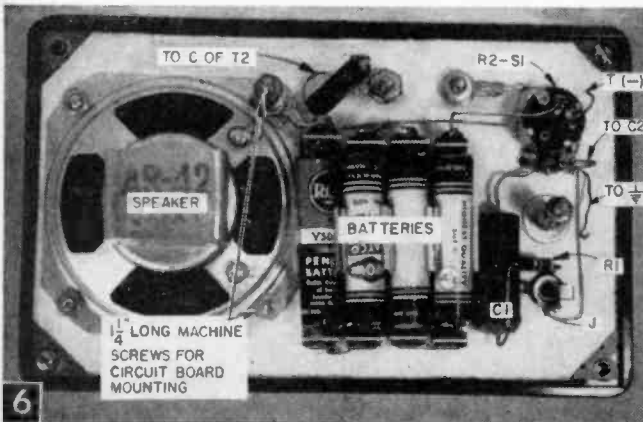8 The RF probe fits in the small plastic tube standing behind it. Below, front panel mountings.



WITH METER CONNECTED AT OUTPUT TERMINALS FOR MEASUREMENTS OF VOLTAGE TO AMPLIFIER INPUT, INPUT VOLTAGE = AMP GAIN \times E_2

7 CIRCUIT FOR CALIBRATION

Fasten the knob on the shaft of R2-S1 and turn on to full volume. Touch the tip contact on the phone jack. If everything's okay, you'll hear a faint hum, and you can mount the assembled amplifier in the case to complete the job.

The amplifier may be used for audio signal tracing. The input probe lead is shielded with Lafayette MS-281 miniature phone plugs on each end. The sleeves supplied with the jacks should be replaced with more rugged 3/8-in. Bakelite tubing such as that used on test prods. The center lead attaches to the phone plug shell. A ground lead about 5 in. long equipped with a Mueller Minigator clip should be connected to the shield

at one of the plug ends. These plugs are used at both ends to allow easy attachment of the RF probe.


The utility amplifier will drive an ac voltmeter. The red and black terminals on the front panel have been provided for connecting an external ac voltmeter. This allows the unit to be used for the measurement of small ac voltages and to check amplifier gain. To calibrate, use the circuit of Fig. 7. Set the meter to the lowest ac scale and adjust RP till the meter reads full scale. Now disconnect your meter and measure E1 with it. The full scale range of the amplifier-meter combination is 10% of E1. Since transformer

coupling has been employed without feedback, the amplifier gain varies with frequency. The full scale sensitivity at 60 cycles is less than the full scale sensitivity at 1000 cycles. Be sure to calibrate at the frequency you plan to measure.

The simple RF probe shown in Fig. 8 can be quickly attached to or detached from the input probe lead (described earlier) to trace RF and IF signals. The circuit for the RF probe is shown in Fig. 2. The level of the signal from the RF probe is low, so best results will be obtained if earphones are connected to the red and black terminals on the front panel of the amplifier.

SM-FP UNIT Increases Value of Receivers

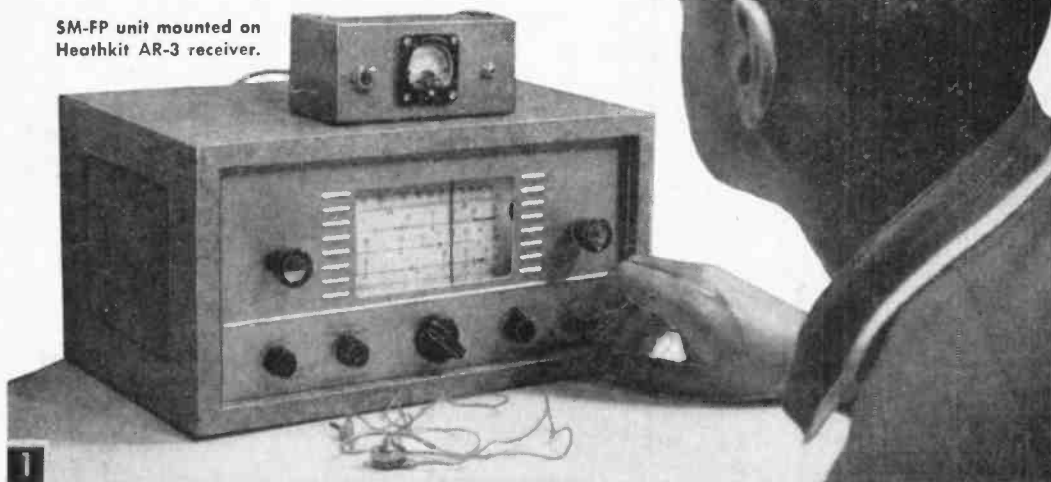SM-FP unit mounted on Heathkit AR-3 receiver.




By FORREST H. FRANTZ, Sr.

THE SM-FP ("S" Meter-Front Phone) unit increases the utility of your receiver by providing a visual indication of relative signal strength for tuning, logging and comparison purposes.


An earphone jack (regular or miniature size) on the front panel of the SM-FP unit allows you to connect earphones at the front of the receiver. No more groping around the rear of the receiver where phone jacks (and hot tubes) are frequently located. I don't know of any receivers with "S" meters which sell for less than \$100. The addition of an "S" meter, therefore, adds considerable value to your inexpensive communications receiver. All of these advantages can be yours for less than \$10.

The SM-FP unit "S" meter circuit connects to any receiver which has automatic volume control (AVC) without having to make any changes in the receiver circuit; simply tie the input terminals across the outer terminals of the receiver volume control. The secret of this simple universal type of connection? A transistor amplifier for the "S" meter.


The unit is housed in a Bud CU-2104 Minibox, $2\frac{1}{4} \times 2\frac{1}{4} \times 5$ in. and finished in grey hammertone. (The same size is available in natural aluminum as Bud CU-3004.) The hole layout for the front of this box is shown in Fig. 4. A $\frac{3}{8}$ -in. dia. hole should be drilled in the center of the Minibox back and two small holes (about $\frac{1}{8}$ -in. dia.) should be drilled in one side of the back. Location of these holes is not critical; they are provided for the connecting cable and top of set mounting re-

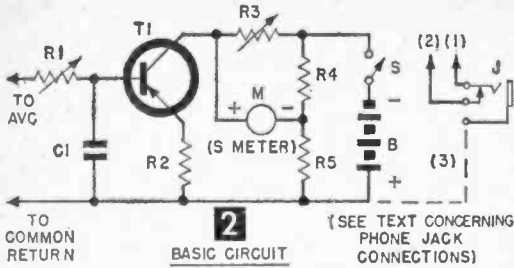

2 BASIC CIRCUIT

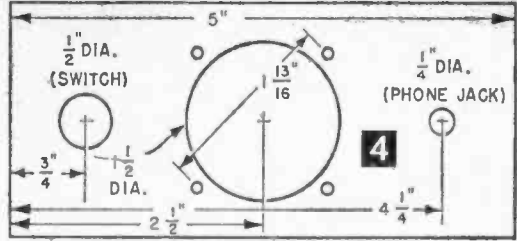

FRONT PANEL LAYOUT

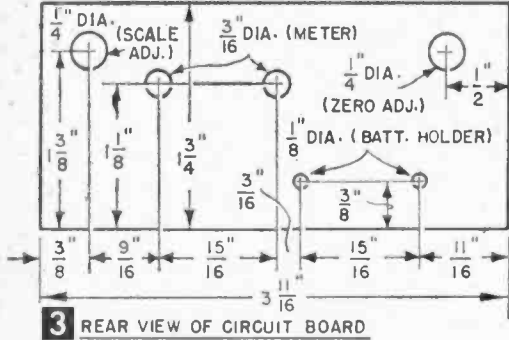

3 REAR VIEW OF CIRCUIT BOARD

spectively. Mount the meter on the front of the Minibox.

The perforated Bakelite circuit board should be prepared next. Layout for it is shown in Fig. 3. Use a hacksaw to cut out the circuit board and smooth the edges with a file. All hole centers coincide with perforations.

Mount R1, R3, and the battery holders on the circuit board. Carbon resistors, transistor, and capacitor are fastened to the board by passing the pigtail leads through the perforations. When junctions between parts occur—as with R2 and the emitter of T1—the pigtails pass through the same perforation.

The common bus from the plus terminal of the battery is the long wire running the length of the circuit board in Fig. 5. This bus is returned through the connecting cable to receiver ground. The pigtails of components which return to this common bus are bent back against the board and soldered to the bus. The meter soldering lugs, the switch and the jack are connected while board wiring is in progress. The switch and jack leads should be about 2 in. long to allow positioning in the Minibox mounting holes.

When circuit wiring has been completed, make up a four-lead cable of flexible wire for connection to the receiver. Keep the cable reasonably short. I used a 16-in. cable. It helps to use different colored leads. The leads connect to the plus battery bus, R1 and the phone jack. Since the phone jack shell connection returns to the plus battery bus, three of the four connections may be made to the phone jack as shown in Fig. 5 if your receiver is ac operated (has a power trans-

former). Connections for ac-dc receivers are discussed below.


The circuit board is held in place against the back of the meter by the meter connection screws. To assure a good fit and good electrical connections, place cardboard shims between the meter and circuit board as required to elevate the circuit board above the meter binding post studs. Then fasten the binding post screws in place. Fasten the jack and switch on the front panel to complete construction of the SM-FP unit.

To fasten the unit to the receiver, place cardboard shims or use washers to obtain 1/8-in. clearance between the receiver top and the bottom side of the Minibox back. The front of the SM-FP unit slides onto the mounted back. Insert two of the self-tapping screws furnished with the Minibox in the appropriate holes on the top of the case to complete the assembly.


The basic connection scheme for all receivers is the same, but the details obviously may differ. The Heathkit AR-3 receiver to which this unit was attached will be used as an example. The Heathkit AR-3 has an octal accessory socket on the rear of the chassis. Pin 1 of this socket is connected to receiver ground. Pins 2, 4, 5, 6, and 7 are unused. I connected a lead from socket pin 2 to the high side of the volume control of the AR-3. This is my detector voltage pick-up point which feeds to R1, the "S" meter input.

The volume control of the receiver is part of the diode load, and AVC voltage is taken from its upper terminal, the audio component being filtered off by a 3.3 Meg resistor and a .01 mfd capacitor. The correct connection point on practically any receiver may be found by locating the detector load and an RC filter with a 1 to 5 Meg resistor and a .01 to .1 mfd capacitor connected to the load. In most receivers, the volume control is part of the detector load and AVC is taken to the filter from this point. In any event, the detector voltage pick-off may be made without changing any wiring; you simply tap on.

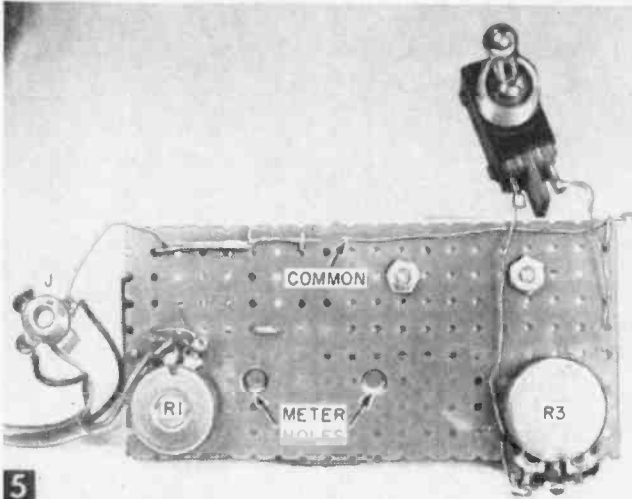The earphone jack on the Heathkit AR-3 is connected across the output transformer secondary. The third terminal on the jack is connected to the speaker voice coil and feeds the output signal to the speaker. Insertion of the phone plug breaks the connection to the



Front view of perforated board.

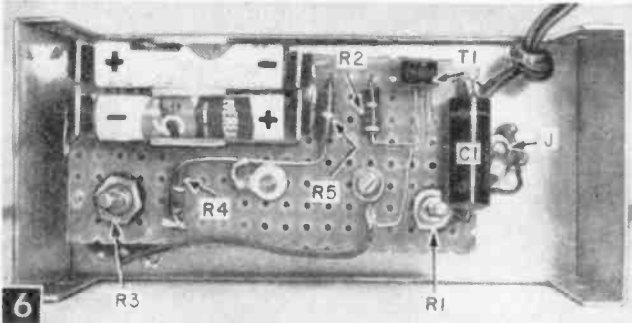

Rear view of wired SM-FP unit.

in Fig. 7. If your receiver has an arrangement of this type, you may have to shield the AVC pick-off lead in the cable to prevent audio feedback. This feedback may occur whenever the phone jack is in a high impedance circuit. But it will rarely ever occur when the phone jack is in the low impedance output transformer secondary circuit as it is in the Heathkit AR-3.

A note regarding the ground connection is in order since most inexpensive receivers other than the Heathkit AR-3 are *ac-dc* operated. Chassis ground on *ac-dc* receivers is usually isolated from the *dc* ground which is the common negative return of the set. If you're connecting the SM-FP unit to an *ac-dc* receiver, provide a fifth wire in the connecting cable.

Eliminate the connection between the phone jack and "S" meter common on the SM-FP and insulate the phone jack from the Minibox. This may be done by enlarging the jack mounting hole and using fiber insulating washers. The "S" meter common connects to the *dc* common of the receiver which is usually connected to the negative terminal of

the speaker. The phone jack on the SM-FP unit is simply an extension jack.


I disconnected the speaker lead from the jack in the receiver and ran this lead to pin 5 on the accessory socket. I ran another lead from the high side (tip connection) of the phone jack to pin 6 of the accessory socket. These pin connections are connected through a mated plug on the connecting cable to their counterparts on the SM-FP panel jack. I used a defunct octal tube for the cable plug.

Some receivers have the phone jack located between audio stages. A typical arrangement and the required change is shown

the electrolytic filter capacitor or to the "low side" of the volume control terminal. The shell of the SM-FP phone jack connects to the shell of the phone jack on the receiver which is usually at chassis ground. The connections for the other three cable wires remain unchanged.

Adjustment of the SM-FP is simple. Turn the receiver on and tune to a point on one of the short wave bands where there's no station or noise pick-up. Turn the SM-FP on and adjust R3 for zero meter reading. Then tune the receiver to the strongest station you can find. If the "S" meter circuit is working properly, the meter needle will be deflected. Adjust R1 for a meter reading just above the plus 30 db point if you're in a good signal pick-up area, or for an S-9 meter reading if you're in a relatively poor area. Now tune off station to a quiet point and readjust R3 for zero reading. You may want to readjust R1 after you get a better feel for the kind of S readings to expect.

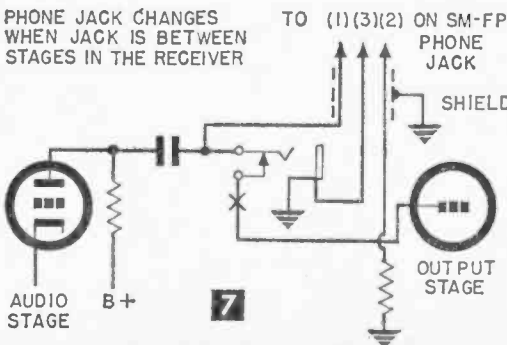Readings are relative and are influenced by your antenna, the sensitivity of your receiver, the band and the place in the band at which stations are received. The important thing is that the S meter allows you to tune your receiver for maximum input and gives



MATERIALS LIST—SM-FP UNIT


Desig.	Description
R4	100 ohm, 1/2 w carbon resistor (10%)
R2	470 ohm, 1/2 w carbon resistor (10%)
T1	2.2K, 1/2 w carbon resistor (10%)
R5	10K miniature potentiometer (Lafayette VC-32)
R3	1 Meg miniature potentiometer (Lafayette VC-38)
R1	.02 mfd, 200 v capacitor (Cornell-Dubilier Cub)
C1	2N508 transistor (GE)
J	phone jack (Lafayette MS-282 for miniature plug or Switchcraft 11 for standard phone plug)
B	two 1.5 v penlite cells series connected (Eveready 912)
M	S meter, 0-1 ma movement (Lafayette TM-11)
S	SPST toggle switch (Arrow-Hart and Hegeman 20994-BF)
	two-cell battery holder (Lafayette MS-138)
	Minibox case (See Text)
	perforated miniature Bakelite board (Lafayette MS-305) knob (Lafayette MS-185)

you a better estimate of signal strength than you would otherwise have. I point this out to emphasize that critical calibration of the meter is not required. After you've experimented with the S meter and your receiver for 30 minutes or an hour, you'll be able to set R1 for satisfactory meter deflections.

If the zero signal meter reading changes after the receiver has been operating for a few minutes, it's probable that heat from the receiver is causing the drift. Bend the transistor as near as possible to the center of the Minibox to minimize temperature drift. As

Eliminating Tape Recorder "Click"

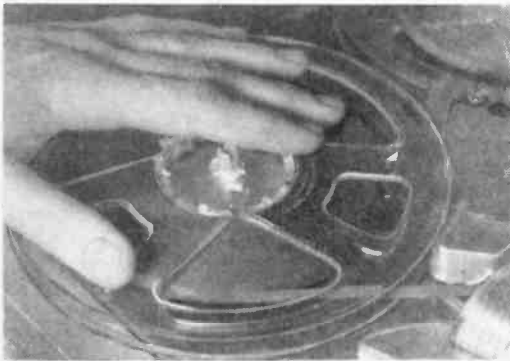• Does your tape recorder leave an audible "click" on the tape every time you depress the stop button while recording? Instead of clipping click from tape while editing, eliminate



it beforehand by manually rewinding an inch or so of the tape back on the supply spool before starting to record again.—JOHN A. COMSTOCK.

Preventing Shorts on Breadboard

To prevent short circuits on a breadboard circuit, tape the wire leads to the chassis with masking or plastic tape. This will also improve the appearance of the layout and permit easier tracing of the wires.—JOHN A. COMSTOCK.

an additional measure, the distance between the top of the receiver and the bottom of the Minibox may be increased to 1/4 in. Of course, you can mount R3 on the panel of the SM-FP unit if you wish, but this permits accidental displacement from the zero setting. This extreme should not be necessary. I might add that I didn't encounter noticeable zero drift with my Heathkit AR-3, but it has a wooden cabinet. I call attention to the possibility because it might occur if your receiver has a metal cabinet.

The "S" meter works in this way: The detection voltage of the receiver is fed through R1 to the base of transistor T1. R1 is an adjustable meter sensitivity control. The combination of R1 and C1 filters audio from the signal and passes only the negative dc level of the detection voltage (which depends on received signal strength) to the base of T1.

Transistor T1 is a dc amplifier. A very small change of current to the base of T1 is amplified to values as great as 1 ma to drive the S meter. Resistors R3, R4, R5 and the meter form the transistor collector load and meter zero (null) set circuit. Resistor R2 provides dc stabilization for transistor T1 to minimize drift and also increases the base input circuit impedance.


Signal Boosters for Portables

• In many portable radios there is no antenna loop of the conventional type, only a "loop stick." Signal sensitivity on such sets can be appreciably increased by winding two to three turns of insulated wire around the stick, one end of this added wire connected to an outside antenna. No ground is needed. You can also, if the set has a loop, wind a one- or two-turn primary over the loop, giving a step-up in voltage. Finally, if you don't wish to incorporate either of these primaries in the set's cabinet, you can make a one-turn loop of heavier insulated or bare wire stapled to a wood block and hung upside-down over the receiver as close as possible to the set's loop and in the same plane, one end of this heavy-wire loop going to an outside antenna as before.—P. M. ARMSTRONG.

Russia Gaining "Hams"

• If they can crack the language barrier, American ham radio operators may have 25,000 new correspondents by 1961—in the USSR. *Radio*, a Soviet magazine published in Moscow, reports that more than 50 radio clubs in Russia now claim 100 transmitters or more. It said that a drive is in progress to reach a goal of 25,000 Russian radio amateurs by 1961. Russian amateurs will operate in the frequency ranges 3.5 to 3.65, 7 to 7.1, 28 to 29.7, 114 to 146, and 420 to 435 megacycles.

Miniature Multimeter

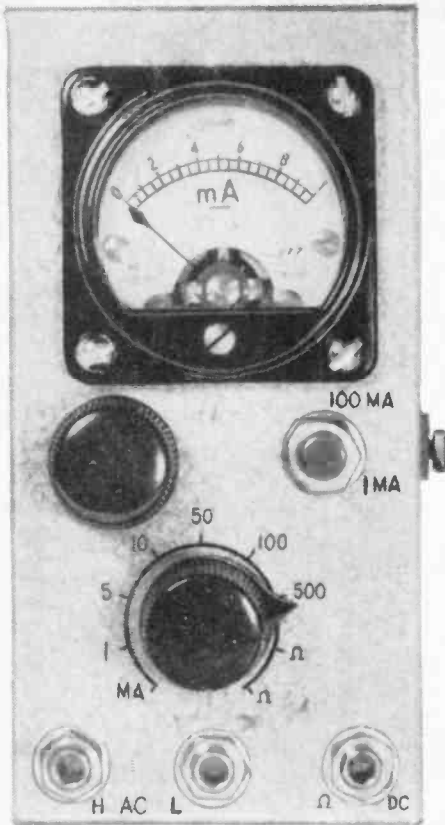

This multimeter fits in a coat pocket, has a special meter protection feature and you can build it for about \$10

IF ALLOWED only one instrument, most technicians would select a multimeter. With it, you can shoot trouble, learn how electronics equipment operates, evaluate the performance of electronic gear. You can check for shorts or opens, measure *ac* and *dc* volts and milliamperes; and measure ohms. And from these measurements you can compute power, capacitance, and inductance.

This miniature multimeter is designed to measure a wide range of electrical quantities. Accuracy on the *dc* voltage, milliampere, and ohm ranges is good; accuracy on the *ac* ranges is not quite as good—unless you calibrate the *ac* ranges—but it's adequate for most purposes. The limitations of the meter are reasonable in view of its low cost and small size. These are its ranges:

dc volts: 1, 5, 10, 50, 100, 500


ac volts: 10, 50, 100, 500

dc ma: 1, 100

ohms: 0-50K (1.5K at meter mid-scale)

0-100K (3K at meter mid-scale)

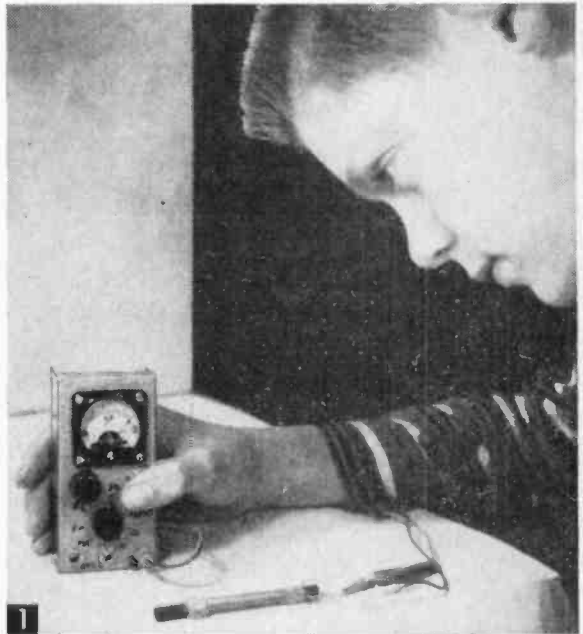Scale switching is accomplished with range




A worthwhile and gratifying construction project for beginning experimenters, this miniature multimeter is also an exceedingly practical piece of test equipment.

switch S1, the push button switch S2, and by the input jack circuit made up of J1, J2, and J3.

If you buy 1% precision resistors for R1 thru R6, the total cost will be slightly over \$10. You can save close to \$2 by selecting resistors R1 thru R6 from standard tolerance resistors. Use a Wheatstone Bridge to measure resistance (Wheatstone bridges are available in the science departments of most high schools and the physics departments of most colleges), or use the ohmmeter ranges on a good vacuum tube voltmeter (VTVM) such as the Heathkit V-7A. If you set the zero adjust and the ohms adjust controls carefully for zero and full-scale deflection of the meter, you can select resistors within plus or minus 2% very easily, and you can expect to get close to 1% if you're careful. This method is most accurate near meter center scale.

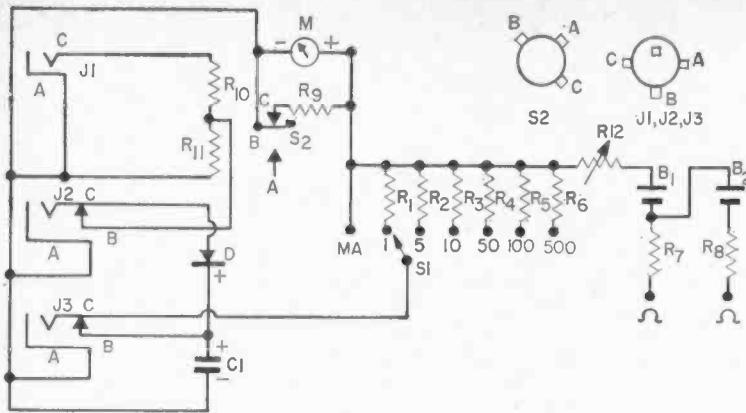
After you have all of the parts together, drill the chassis box (Fig. 3). Next, letter the front panel with India ink. Wash the box in warm sudsy water, rinse, and dry thoroughly before marking. A piece of thin plastic or clear celluloid cut to fit over the panel markings will assure permanence. Trim the holes with a pocket knife, and while you have



2 SCHEMATIC

RESISTANCE	METER READING (MA)
200 OHMS	.87
500 OHMS	.75
1 K	.6
1.5 K	.5
5 K	.23
10 K	.13
50 K	.02
500 OHMS	.86
1 K	.75
3 K	.5
5 K	.37
10 K	.23
50 K	.05
100 K	.03

4 OHMMETER TABLE

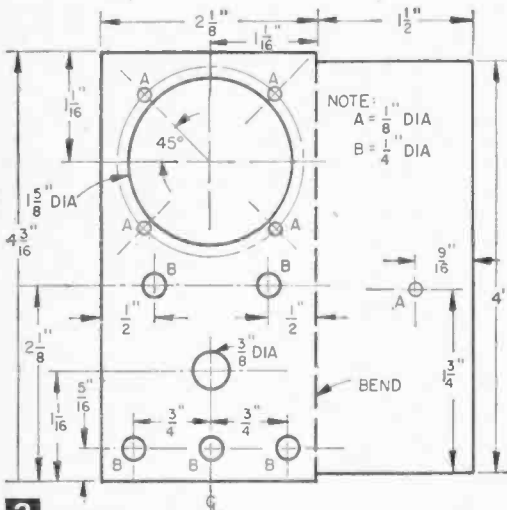

3 LAYOUT

MATERIALS LIST—MINIATURE MULTIMETER

Desig.	Description
R9	0.67 ohm resistor (6 1/2' of #30 insulated wire)
R1	935 ohm resistor, 1/2 w, 1%
R2	4,935 ohm resistor, 1/2 w, 1%
R3	10K resistor 1/2 w, 1%
R4	50K resistor, 1/2 w, 1%
R5	100K resistor, 1/2 w, 1%
R6	500K resistor, 1/2 w, 1%
R7	1K resistor, 1/2 w, 10%
R8	2.7K resistor, 1/2 w, 10%
R11	58K resistor, 1/2 w, 10%
R10	100K resistor, 2 w, 10%
R12	1K miniature volume control (Lafayette VC-32)
C1	10 mfd, 150 v miniature electrolytic capacitor (Aerovox SRE type)
J1, J2, J3	miniature phone jacks (Lafayette MS-282)
S1	single pole, 10-position miniature switch (Grayhill 5001-10)
S2	miniature push button switch (Lafayette MS-449)
M	0-1 ma miniature panel meter (Lafayette TM-400)
D	selenium rectifier (Sarkes Tarzian 50)
B1, B2	1.5 v penlite cell (Burgess #7)
	1 5/8 x 2 1/8 x 4" aluminum chassis box (LMB-00)
	miniature knob (Lafayette MS-185)
	small standard knob (Lafayette KN-19)
	miniature phone plug (Lafayette MS-281)

the rubber cement handy, cut out and fasten the meter scale (Fig. 4) on the front of the meter glass.

Next, assemble resistors R1 thru R8 on the rotary switch as shown in Fig. 5. This portion of the wiring is shown inside the dotted line on the schematic, Fig. 2. The numbers indicated on the switch contacts correspond to the numbers on the back of the Grayhill rotary switch (S1). Switch position #9 is not used.


Check push button switch S2 to be sure that it makes good contact in the normally "ON" position. If you can detect any resistance at all between these contacts on the low ohm scale of a VTVM, clean and bend them to provide a low resistance contact. Since this switch is in series with R9, the shunt for the 100-milliampere meter range, contact resistance can impair accuracy.

Cut the shaft of potentiometer R12 so that it extends 1/4 in. beyond the potentiometer

bushings, and mount R12, S2, J1, J3, the meter and the S1-R1 through R8 range switch assembly (see Fig. 6).

Wire from the meter plus terminal to the middle terminal of R12 and from there to terminal 10 on switch S1. Connect a wire to the upper terminal of R12 and let it hang loose for the moment. Connect a wire from the switch arm of S1 to the contact of J3 designated as "C" in the schematic. Connect a 2 1/2-in. length of wire from contact "B" on J3 to the plus terminal of rectifier D. Connect the other terminal of rectifier D to terminal "C" of jack J2.


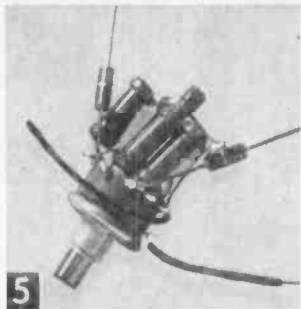
Next, mount J2 on the chassis, positioning rectifier D as shown in Fig. 7. Note that the terminals are bent to avoid the possibility of a short. The connecting wires hold the rectifier in place. Run a wire from contact "B" on S2 to the minus terminal of the meter. Connect another lead from the meter minus terminal to contact "A" on J3. Now connect the minus lead of C1 to the meter minus ter-



minal and the plus lead of C1 to the plus terminal of rectifier D. Place the negative lead of C1 under the negative terminal screw and solder the other two leads to the negative C1 lead. Connect one end of R9 to contact "C" of S2. Resistor R9 is made by folding 6½ ft. of #30 insulated copper wire on itself till it is 1 in. long. Insulate R9 with tape, and tape it to the meter case.

Next, connect R11 from A on J3 to B on J2. Connect R10 from "B" on J2 to "C" on J3. Connect the loose end of R9 to the junction of R1 thru R6 on the switch assembly (Fig. 8). Connect R7 to the terminals at the upper end of the battery holder to form a junction. Connect the loose end of the wire previously connected to the upper terminal of R12 to the remaining plus battery terminal. Connect the loose end of R8 to the remaining negative battery terminal. Then insert the batteries in the holder and fasten the holder to the chassis with a self-tapping screw. If the screw is long enough to threaten the batteries, use washers under its head. Completed construction is shown in Fig. 9. Putting the knobs on completes the work on the front side.

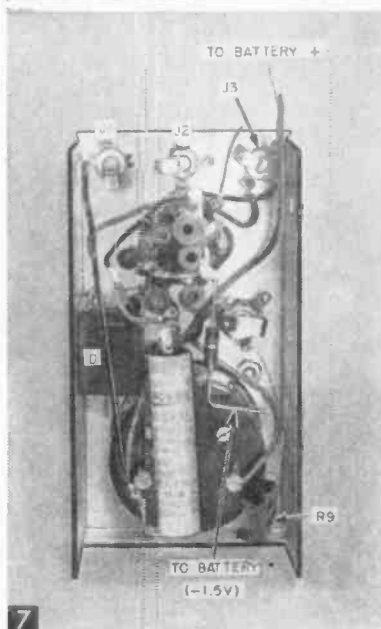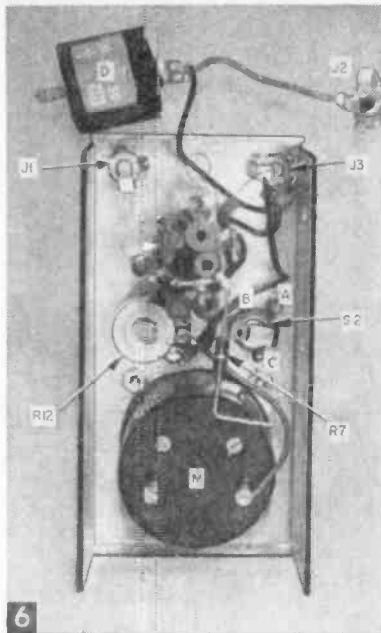The "A" terminals of jacks J1, J2 and J3 are grounded to the chassis case and therefore connect to each other through the chassis. The test leads connect to a single jack plug. You'll have to ream out the back end of the plastic plug handle to pass the wire through it. I used #20 solid hook-up wire for my test leads. Don't strip more of the wire than you must to solder to the jack ter-



Step-by-step construction of multimeter (see text).

minals, and provide tape insulation if necessary to protect against shorts. The test leads are terminated with Mueller Minigator clips at the other end. A wooden matchstick taped to the clip end of the positive lead stiffens it and allows you to use this lead as a probe.

To measure dc volts or ohms, plug the test leads in the ohm-dc jack (J3) and choose the range with S1. Use R12 to zero-set the ohmmeter with the leads shorted when you want to make the resistance measurements. You must depress S2 to get the correct reading. When S2 is not depressed, R9 shunts the meter to protect it against burnout if you should accidentally select too low a range. When you depress S2 to take a reading, the natural reaction to a pegging needle is to release the button. You're warned of very severe overloads that could damage the meter if S2 were quickly depressed and released by higher than usual readings before S2 is depressed. To measure milliamperes, select milliamperes with S1. The range is 100 ma if S2 is not depressed, 1 ma if it is depressed.

To measure ac volts up to 100, plug the test leads into the ac low jack (J2) and use the 10, 50 or 100 volt positions of S2. Again, you must depress S2 to get the appropriate reading.

You can use the 1 and 5 volt positions on S2, but they're very inaccurate on ac. To measure voltages between 100 and 500 volts, plug the leads into the high ac jack (J1) and set S1 to the 100 volt setting. Depress S2 to take the reading. Don't change jack plug-in positions with the test clips connected to a voltage!

When you feel sufficiently confident that you won't be jeopardizing the meter by picking a wrong scale or overloading it in some other way, you can change the connection on terminal "C" of S2 to terminal "A." Then the meter will read properly without depressing

S2. If this change is made, S2 is depressed only when the 100 ma range is desired. When S2 is not depressed, the 1 ma range is connected if the range switch is set to ma after the change has been made.

For current measurements, the meter is connected in series with voltage source and load as shown in Fig. 10A. For voltage measurements the meter is connected in parallel with the voltage source or dropping element as shown in Fig. 10B. To determine power, measure current thru the load and voltage across the load. The power in watts is equal to volts times amperes.




To determine capacitance or inductance use the arrangement of Fig. 10C. Adjust the variable resistor till the ac voltage across the capacitor or coil equals the voltage across the resistance. Then, measure the resistance. For a capacitor,

$$C = \frac{2650}{R}$$


where C is the capacitance in microfarads and R is the resistance in ohms. For a coil:

$$L = .00265R$$


where L is the inductance in henries and R is the resistance in ohms. This method is approximate. The accuracy is good for all types of capacitors 0.1 mfd or greater except for low-voltage electrolytics. This measurement method should not be used on electrolytic capacitors rated under 100 volts. The scheme is not as accurate for lower than 0.1 mfd capacitance because the capacitive reactance is much greater than the meter impedance. The accuracy of inductance measurements is not too good because of the resistance inherent in the coil which this method assumes as neg-

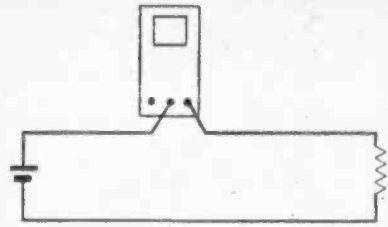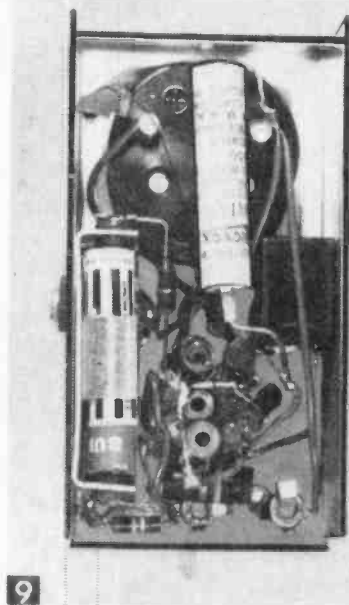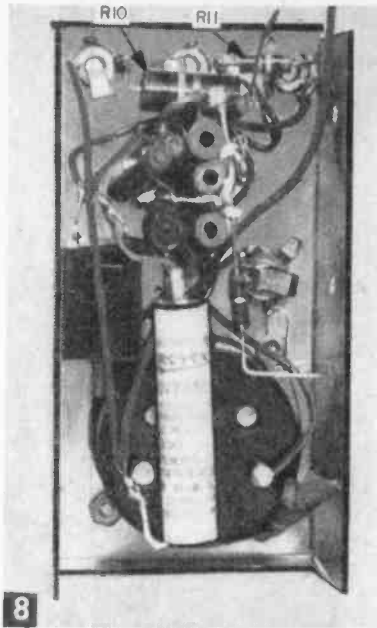

10 A CURRENT

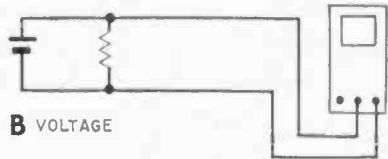

B VOLTAGE

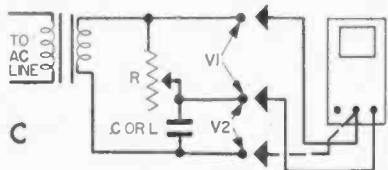

C CAPACITANCE OR INDUCTANCE (ADJUST "R" UNTIL V1 = V2)

ligible. It isn't reasonable to use this scheme for coils with inductances of less than 100 millihenries. But filter chokes and audio coils may readily be measured using this method.

Can the scheme be extended to take in lower inductances and lower capacitances under any circumstances? Yes, but you'd need a higher frequency source than the ac line 60-cycle frequency and you'd need a more sensitive meter.

Jacks J2 and J3 perform some of the switching requirements. Contact "B" is connected to "C" in any jack if the plug isn't inserted. If the test lead jack plug is inserted, "B" is disconnected from "C" in that jack. If the jack plug is inserted in J3, dc can pass directly into the switch arm of S1. If the jack is inserted in J2, the ac input is rectified by D, filtered by C1 and applied to the switch arm of S1 via contacts "B" and "C" on J3. For economy reasons, a half-wave selenium rectifier was employed in this miniature multimeter. This rectifier can't handle voltages much greater than ac line voltage. Therefore, the divider consisting of R10 and R11 was provided to reduce the voltage on inputs up to 500 volts for use with the 100 volt range switch position when the jack plug is inserted in J1.—FORREST H. FRANTZ, SR.

Three-Transistor Portable

This receiver, in spite of its simplicity and low cost, has high sensitivity and selectivity

By FORREST H. FRANTZ, Sr.

HERE'S a simple receiver that will pick up plenty of stations with loud-speaker volume. The circuit (Fig. 2) is novel in several respects. Transistor T1 is employed as a combination regenerative RF stage and stabilized audio amplifier, with base and collector circuit tuned to provide high RF gain and selectivity. The selectivity and gain characteristics are enhanced by capacitive feedback and the hi-Q ferrite antenna coil.


The amplified RF signal is detected by diode D, and the resulting audio signal is fed via capacitor C3 to the base of T1 for a second trip through. Coil L2 looks like a short circuit to the amplified audio signal and the signal appears across volume control R5. Transistor audio amplifier stages T2 and T3 build the signal up to loudspeaker driving level.

Construction. The original three-transistor portable was housed in a "do-it-yourself" case constructed from a length of 1 x 4 with a perforated Masonite front and back (see Materials List). Shave the front edges of the cabinet on the left-hand side to clear for the edges of the loudspeaker and fasten a 1/2 x 1/2



1

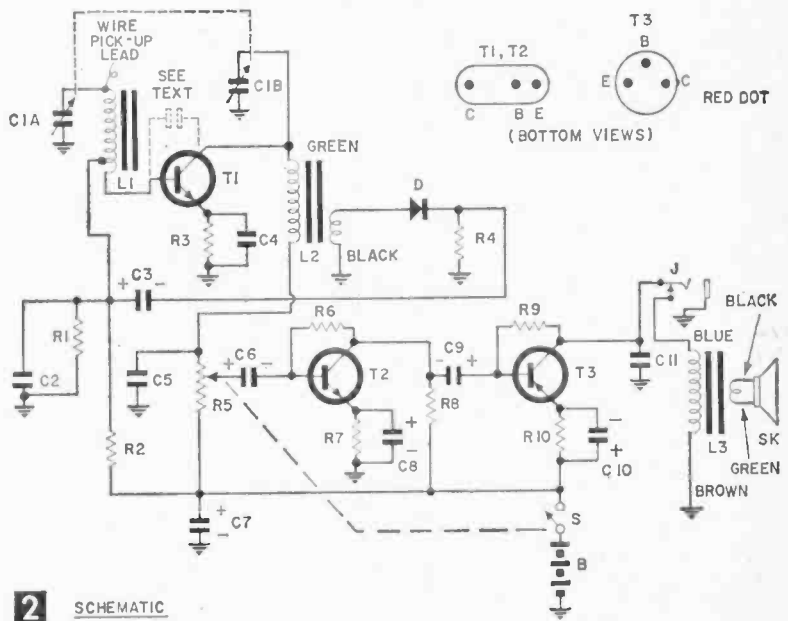
Tone of this simple portable is better than that of most small, commercial transistor receivers.




2

SCHEMATIC

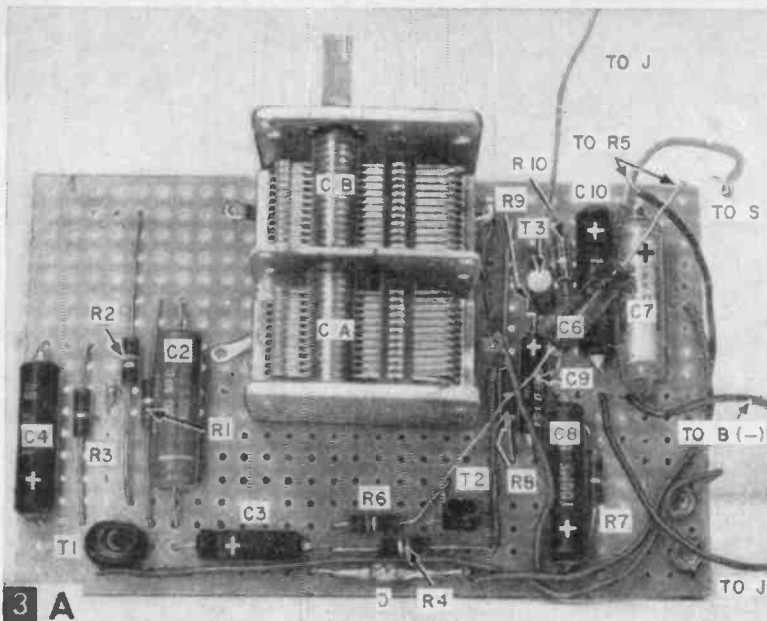x 7 in. wood strip to the bottom of the cabinet to hold the batteries. Fasten a piece of Masonite 2 1/4 x 8 1/4 in. with a 3/4 x 1 3/4 in. triangle cut from the front right corner (to allow



3 A

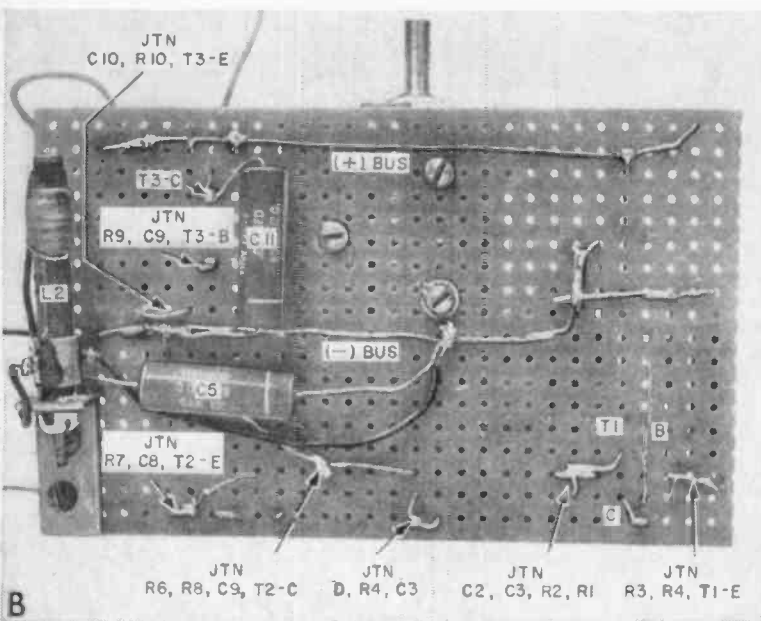

B

Circuit board layout, top (above) and bottom (below).

clearance for the volume control) to the side of the case with a small screw and bracket, and to the bottom of the case with a $1\frac{3}{4}$ -in. screw through a scrap block to complete battery holder.

The receiver proper is constructed in two basic units: circuit board (Fig. 3); and front panel (Fig. 4). The circuit board contains most of the components and fastens to the front panel with two machine screws and nuts terminating on the tuning capacitor

frame. The volume control and switch (R5-S), the phone jack (J), the loudspeaker (SK) and ferrite antenna loop (L1) mount on the front panel.

Cement a piece of cardboard to the front panel, making holes as required for mounting parts with a pocket knife. Draw a $5\frac{1}{2}$ -in. dia. circle on the cardboard with center at approximate speaker center. Punch holes in the cardboard within this circle with an ice pick, entering from the perforations on the front.

Cut the shaft of R5-S to a length of $\frac{3}{8}$ in., and mount R5-S, SK, L1, and J. Cut a square hole, $\frac{3}{8}$ in. on a side into the cardboard around the panel hole for J; the jack collar isn't long enough to accommodate the extra thickness of the cardboard. Mount L1 on two $1\frac{1}{2}$ -in. right-angle brackets fastened to the front panel, and fasten the output transformer (L3) on the loudspeaker (SK) by soldering at the mounting flanges. Connect the transformer leads and provide a ground lead from the speaker frame to the ground terminal on the jack.

Next, cut the shaft of C1 to $\frac{3}{4}$ -in. length and mount C1 on the board with 6-32 x $\frac{1}{4}$ in. machine screws.

Modify L2 by disconnecting one of the connections

to the center-tap (unmarked) lug. Heat the lug and shake off the solder. Then, with heat applied to the lug, use needle nose pliers to loosen the lead with several gentle tugs. Be careful not to damage the litz wire. This modification changes the coil from a single-winding tapped coil to a two-winding coil. Fasten the coil on the small right angle bracket and mount on the circuit board. Proceed with circuit board wiring. Determine correct pairing of the windings on L2 with

MATERIALS LIST—THREE-TRANSISTOR PORTABLE

Desig.	Description
½ Watt Carbon Resistors, 20% Tolerance	
R10	270 ohms
R3, R7	1K
R8	2.7K
R1	6.8K
R4	22K
R9	47K
R2, R6	68K
R5-S	1K miniature volume control with switch (Lafayette VC-26)
C1A,B	2-gang 365 mmf. tuning capacitor (Lafayette MS-142)
C2, C5, C11	.01 mfd., 600-v tubular capacitor (Cornell-Dubilier "Tiny Chief")
C9	6 mfd., 15-v miniature electrolytic capacitor (Lafayette CF-104)
C3, C6	30 mfd., 6-v miniature electrolytic capacitor (Lafayette CF-104)
C4, C8, C10	100 mfd., 6-v miniature electrolytic capacitor (Lafayette CF-106)
C7	100 mfd., 15-v miniature electrolytic capacitor (Lafayette CF-126)
L1	transistor loop antenna (Miller 2000)
L2	transistor antenna coil; see text for modification (Lafayette MS-299)
L3	500:3.2 ohm transistor output transformer (Lafayette TR-95)
T1	2N168A NPN RF transistor (General Electric)
T2	2N214 NPN AF transistor (Sylvania)
T3	2N408 PNP AF transistor (RCA or Sylvania)
D	diode (RCA 1N54A)
J	miniature phone jack (Lafayette MS-282)
SK	6" PM loudspeaker, 3.2 ohm (Lafayette SK-27)
B	six 1.5-v flashlight batteries, series connected (RCA VS036)
3 1/8" x 6 3/4" miniature perforated wiring board (Lafayette MS-305)	
two 7 3/4" x 11 1/8" perforated Masonite boards (cut from two Lafayette ML-81 boards)	
two 11 1/8" lengths from 1 x 4	
two 6 7/8" lengths from 1 x 4	
miniature knob (Lafayette MS-185)	
tuning capacitor knob (made from standard size surplus knob and thin plastic)	
earphones of 500-1000 ohms impedance	
handle, bracket screws	


an ohmmeter or a continuity checker.

Fasten the wired circuit board to the front panel and complete the wiring. The antenna pickup lead is a 10-in. length of hook-up wire fastened mechanically (but not electrically) to the ferrite antenna loop (L1) mounting board. Fastening the knobs to the front panel completes receiver construction.

Set the L2 slug screw to extend about 3/8 in. beyond the end of the coil. Turn the trimmer on C1A all the way in, and then release it about 1/4 turn. The trimmer on C1B should be turned all the way in and then released 2 turns. When you feel sure everything is right, solder in the batteries (using as little heat as possible), and try the set.

If the set squeals, move the lead to the stator lug of C1B away from the stator lug and associated surface of C1A. This lead provides the collector to base capacitance shown in Fig. 2. Tune to a station around 1400 kc, and adjust the C1B trimmer for maximum signal. Then tune to a station around 600 kc and adjust the slug of L2 for maximum signal. Now adjust the position of the C1B stator lead relative to the C1A stator for maximum sensitivity without oscillation.

You may find it advantageous to open the

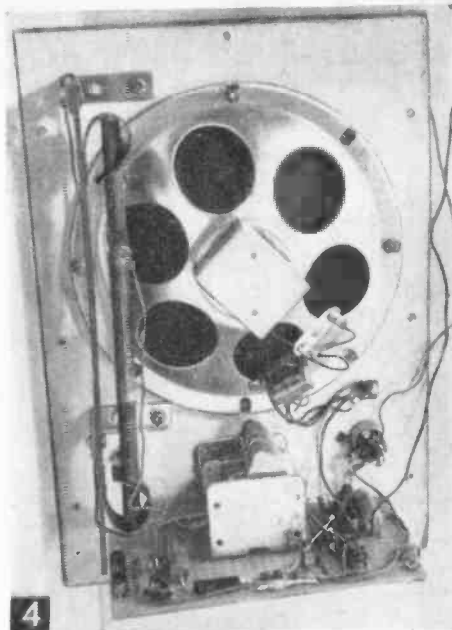


Back view of completely assembled front panel.

C1A trimmer considerably or to add turns to L1 by winding some of the "high-end" lead on the ferrite core. The plates of C1A may be bent to improve tracking. The important things are to be sure that you can tune the entire broadcast band, and that you have the greatest possible sensitivity over most

of the band. Don't overlook the fact that this receiver is very directional!

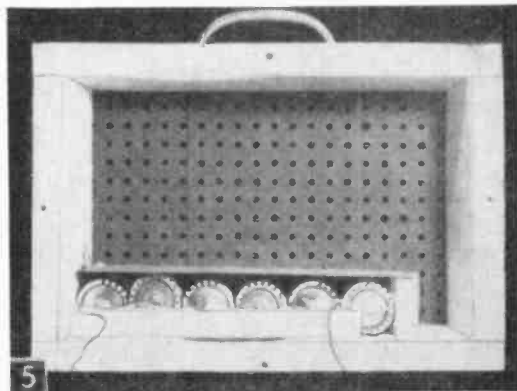If you wish to miniaturize this set, use a Miller 2001 or 2004 for L1, a Lafayette SK-65 (2 1/2 in.) for SK, and six penlite cells for B. Coil L1 should make a right angle with L2 (but keep L1 horizontal), and these two coils should be separated as much as possible. Coil L1 should be kept away from the speaker or other metal surfaces.



Looking into opened case from front.

The Little Muter


A Noise Limiter For The Ham Station

The Little Muter, simple, inexpensive and effective.



By HOWARD S. PYLE,
W7OE

Photos by John F. Hoyt

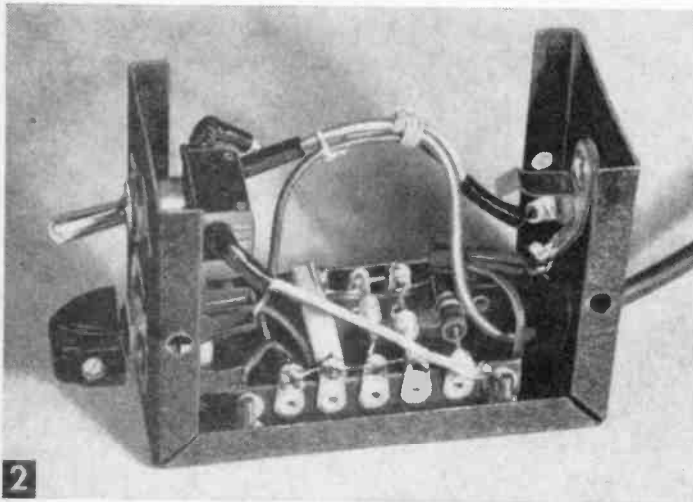

2 Internal view of noise limiter showing component mounting on tie points.

DISSATISFIED with the rather dubious noise-limiting circuits usually built into the average communications receiver, I conducted a number of experiments with the hope that they would lead to a better signal-to-noise ratio than conventional designs seemed to offer. I wanted a noise-reducing device, rather than something that took hold when the noise reached a certain level. In addition, my aim was to attempt to make such a circuit function as an audio noise reducer, with no attempt to reduce the noise pick-up in the antenna circuits, and to make such a device an accessory to the receiver, requiring no modifications or changes in receiver circuitry.


I came up with an extremely simple limiter,

or reducer, as you please, which required no battery or other source of power, was small and compact and could simply be inserted in the headphone or speaker leads from the receiver. I have used this device in CW traffic net message exchange for several years . . . I would be completely snowed under without it! While I do not habitually work in the phone bands, the listening I have done there indicates that this little limiter is every bit as effective on phone signals as with CW. Were all parts for this unit to be purchased new, the total cost would be less than \$5. With the possible exception of the crystal diodes, everything is readily available in your own station's scrap-box.

The unit is completely contained in a Bud Minibox which measures just $2\frac{1}{4} \times 2\frac{1}{4} \times 4$ in. Figure 3 gives the schematic. In my own unit

(see Fig. 2), I mounted capacitor C1, the two crystal diodes X1-X2, and the fixed resistor R1 between two Birnbach #1388 lug terminal strips (tie-points) which were in turn secured to the inside of the Minibox at a spacing of 1 in. Volume control R2 mounts on one end of the cabinet with the toggle switch S1 directly below it. The opposite end of the Minibox mounts the "Phones" jack near the bottom and, near the top center, a rubber grommet in a suitable hole to take the cord from the phone plug. Small decals, available at any radio supply store, mark the controls and add the professional's touch.

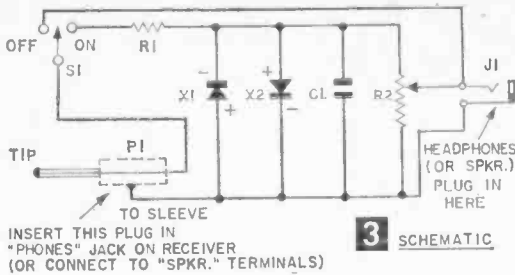Use caution in wiring the two diodes. Make sure that their polarities are in opposition—positive to negative at each end, as shown



MATERIALS LIST—NOISE LIMITER


Desig.	Description
S1	SPDT toggle switch
R1	15 megohm 2-watt resistor
X1, X2	Sylvania 1N34 crystal diodes
C1	.0025 mfd. fixed capacitor
R2	10 megohm volume control (Mallory #U-20)
J1	open circuit phone jack
P1	phone plug Bud Minibox (CU-3003)

in the schematic. Use care, too, in soldering to the pig-tails of the diodes since they are easily damaged by too much heat. Solder quickly, but be sure it's soldered.


To install, plug the phone plug into the "Phones" jack on your receiver and plug your headphones into the jack under R2 on the Little Muter. That's it! If you prefer speaker operation, insert the Muter in the same way in the speaker leads.

You'll find that Little Muter will cut your audio output, but no matter—with the excessive gain available in modern receivers, this merely means compensating for any loss of audio by running the audio gain control at a slightly higher setting. BUT, you'll find that while the signal comes up, the noise does not come with it in the same ratio! That what you want? I did, and Little Muter gave it to me! When you find conditions such that you don't need it, flip switch S1 to *Off* and you are conventionally connected to the receiver through your headphone or speaker.

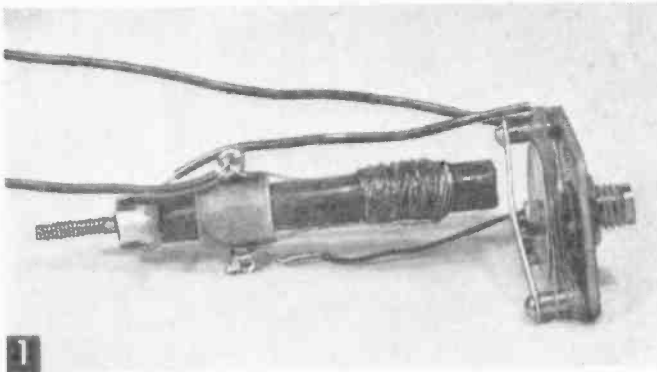Wave Traps Eliminate Station Interference



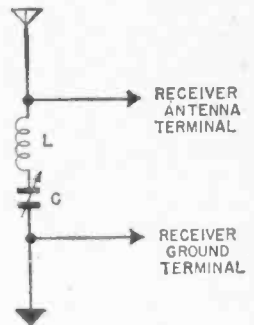Broadcast band wave traps can be connected across receiver loop antenna if coil's axis is vertical. If trap is enclosed in a metal shield (tin can), orientation is not necessary.




SERIES RESONANT WAVE TRAP "SHORTS" SIGNAL AT ITS RESONANT FREQUENCY

By FORREST H. FRANTZ, Sr.


A STRONG local radio station can interfere with reception of other radio stations in several ways. One type of interference that can affect any type of receiver circuit is adjacent-channel interference. If the strong local station is on 790 kc, it may affect stations from 700 to 900 kc in TRF receivers. The interference may cover a wider spread on the receiver tuning dial in the case of a crystal detector-amplifier type receiver. Adjacent channel interference in the more selective

superhet circuit is not severe, but it can be troublesome on closely adjacent stations (for instance, 780 kc and 800 kc when the interference local is on 790 kc).

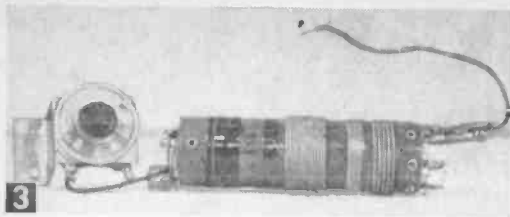Another type of local radio station interference that can affect any type of receiver circuit is harmonic interference. Although FCC regulations require radio stations to keep signal harmonics low, harmonics of strong locals can cause interference. (The second harmonic of a station on 600 kc, for



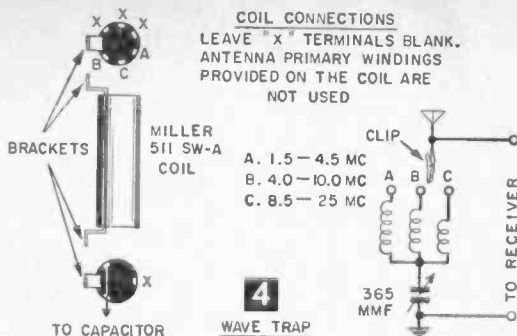3 Short-wave trap can be mounted on chassis at rear of set if capacitor is mounted on a bracket. Ground connection for capacitor is made through the bracket. The end of the clip lead connects to the antenna terminal of the receiver.



example, would be received at 1200 kc.)

Local radio stations can produce interference in superhet receivers that is peculiar to the superhet circuit. This type of interference occurs because the superhet employs a fixed intermediate frequency. The incoming signal is mixed with the local oscillator to produce the IF (usually about 455 kc in AM receivers), and the mixing process produces a number of signal frequencies at the output of the mixer tube. The desired IF signal is the oscillator frequency minus the received signal frequency. Thus, if the receiver is tuned to receive a station on 1500 kc, the local oscillator frequency is 1500 plus 455 or 1955 kc. If the receiver is tuned to 1500-2(455) or 590 kc, the local oscillator frequency is 1045 kc. If the 1500 kc station is a strong local, the amount of its signal that appears at the input to the mixer tube even when the receiver is tuned to 590 kc may be very large. One of the signals at the mixed tube output is the received frequency *minus* local oscillator frequency, in this case, 1500-1045, or 455 kc., the IF frequency of the receiver. There is interaction between the 590 kc signal to which the receiver is tuned and the 1500 kc local signal; 590 kc. is the "image" frequency of 1400 kc.

Eliminating Interference. The basic wave trap configuration shown in Fig. 2 is a series resonant wave trap. It is connected across the antenna-ground terminals of the receiver. This wave trap effectively short-circuits the signal frequency to which it is tuned, but has very little effect at other frequencies. The higher the Q of the coil, the more effective the wave trap is. This type of wave trap can be connected across a loop antenna within a broadcast receiver or across the transmission line in the case of a TV receiver. This type of wave trap is recommended for any type of receiver because it will function effectively even if the ground to the receiver is poor.

A wave trap which will suppress frequencies in the broadcast band may be most easily constructed by using a commercially available coil, the Miller #6300 high-Q ferrite antenna coil. This coil has a Q of over 250 and will provide good rejection. The coil is adjustable and will tune the broadcast band

with any capacitor having a maximum capacitance between 250 and 500 mmf.

The wave trap shown in Fig. 1 uses the Lafayette MS-445 365 mmf. tuning capacitor. This capacitor was chosen for its small size and low cost. It was housed in a tin can. The leads to the receiver antenna and ground terminals should be as short as possible. The antenna pickup lead on the coil must be unwound and may be shortened to form one of the connecting leads. The screw adjustment on the coil may be set so that the capacitor will tune the broadcast band. Or, by setting the screw for maximum inductance, the trap can tune down to about 450 kc. when the tuning capacitor is fully closed. If the screw is set for minimum inductance, the trap will tune up to about 2.5 megacycles with the capacitor fully open.

The short wave trap shown in Fig. 3 can tune the frequency range from 1.5 to approximately 25 megacycles. The coil is a Miller 511-SW-A, three-band short-wave antenna coil. The capacitor is the Lafayette MS-445, the same as for the broadcast trap. The windings on the coil cover 1.5 to 4.5, 4.5 to 10, and 10 to 25 megacycles respectively. The coil which covers the frequency to be suppressed must be connected in the wave trap circuit. A Mueller Minigator clip permits quick selection of the required coil, but this clip can be omitted and the coil may be soldered in the circuit for a more permanent installation. The schematic (Fig. 4) shows the connections. This wave trap may be fastened directly to the back of the receiver chassis. If you wish to make this wave trap easy to get at, so that it can be used to improve receiver tuning at all frequencies, house components in a metal cabinet and provide a switch for changing connections to the coil.

Save Those Dirty Radio Parts

• When dirty tube sockets, insulators, knobs, tuning capacitors and other metal, bakelite or ceramic radio parts won't come clean in ordinary cleaning solutions, try this idea. Allow the parts to soak a minute or two in a pan of boiling hot water to which a capful of liquid dishwashing detergent has been added, then brush them with a vegetable brush.—J.A.C.

Precision Stroboscope for Only \$21

This accurate "motion stopper" will enable you to analyze motor operation and trouble shoot flaws in mechanisms

By W. F. GEPHART

Adjust the frequency control to synchronize the flashing strobe lamp with the speed of the fan. The blades will appear as though stationary.

WINKING at up to 6,000 flashes per minute, this easily built portable unit will show you fast moving mechanism "stopped," or in slow motion in order to spot wear, vibration or faulty design in power tools, fans, belts, motors, and reciprocating parts.

A simplified version of equipment widely used in industry, this strobe circuit, uses only about \$21 in parts and performs as well as commercial instruments costing over \$100. The rate of flashing is adjustable between 600, and 6,000 rpm, and by doubling up, you can measure any speed above or below this range. Unlike mechanical tachometers, the stroboscope absorbs no power from a direct connection to the moving mechanism itself.

How It Works. The basic principle of the stroboscope is simple. You might, for example, want to examine a fan blade rotating at about 300 rpm, (5 times a second). The blades will be in the same place every successive fifth of a second; therefore, if you could blink your eyes that fast, you would see the fan as though it were standing still. By means of the frequency control, Fig. 1, the rate of flashing is adjusted until it synchronizes exactly with the moving part. Adjust the control to flash slightly faster, or slower, and you can see the movement in slow motion. Reciprocating motions, such as the action of a pump, or the teeth of a high speed jig saw are clearly stopped in action.

If you calibrate your unit against a standard, you will be able to use it as a tachometer to make measurements of the rpm of high speed motors,



MATERIALS LIST—STROBOSCOPE	
Desg.	Description
R1	27 ohm 1 watt 10% carbon resistor
R2	1 megohm 1 watt 10% carbon resistor
R3	7,000 ohm 5 watt wirewound resistor
R4	560K 1/2 watt 10% carbon resistor
R5	1 M 1/2 watt 10% carbon resistor
R6	2M potentiometer (linear taper)
R7	10M 1/2 watt 10% carbon resistor
R8	100K 1/2 watt 10% carbon resistor
R9	5K 5 watt wirewound 5% resistor
R10	10K 5 watt wirewound 5% resistor
R11	2K 5 watt wirewound 5% resistor
C1	8 mfd 450 V electrolytic capacitor
C2	8 mfd 150 V electrolytic capacitor
C3	8 mfd 450 V electrolytic capacitor
C4	.05 mfd 200 V electrolytic capacitor
C5	.033 mfd 200 V paper capacitor
C6	1 mfd. 400 V paper (Sprague 4TM-M1)
C7	20 mfd 450 V (Ill. Cond. 1HTE 2045)
SW1	DPST toggle switch
SW2	SPST toggle switch (for range switch)
SR1, SR2, SR3	75 ma 130 RMS selenium rectifiers (IT&T Federal #1003A)
V1, V2	RCA 0A2 150 volt voltage regulator tubes
V3	Sylvania 1021/SN4 Strobotron tube
Misc.	Bud Minibox CU-2114 (12 x 2 1/2 x 2 1/4" aluminum box and cover)
	2 ea. 7 pin miniature sockets, 1 4-prong socket, 1 knob, terminal strips, line cord, reflector, decals, misc. hardware. Walsco Stroboscope Disc #949

Note: See text and drawing for auxiliary trigger switch parts.

compact aluminum minibox. Mount the strobotron tube socket at one end, and drill the holes for the switches and frequency control in the back, as in Fig. 2. Make the sub chassis of scrap aluminum, and mount all parts including tube sockets, and tie points before starting the wiring. The reflector shown in Fig. 1 is from a used Heiland photo flashgun, and can be obtained in most camera stores. Since the design of the

phono turntables, and even of dental drills. Hobbyists have used strobe lights to check the speed of model gas engines vs. various fuel mixtures. And if your model railroad engine is balky, your strobe may quickly indicate the trouble, in a part that is vibrating at certain speeds.





Building the Case. The stroboscope is completely enclosed in a

bracket will depend on the kind of reflector that you obtain, exact dimensions are not given. Simply bend a piece of hardened aluminum strap, 1/2 x 1/8-in. to focus the center of the reflector directly behind the flashing area of the strobotron tube, which centers about 3/4 in. down from the top of the tube. Since the power supply, and the regulator tubes generate heat, drill ventilating

holes near these parts in each side of the cover as in Fig. 2.

Wiring the Circuit. Begin by wiring and testing the power supply, as in Fig. 3. It consists of a selenium rectifier tripler, with an output of about 430 volts, which is subsequently reduced to 300 volts for both the timing and strobe pulse circuits. Since one side of the power supply is connected directly to the a-c power line, be sure to isolate all interior circuits from the metal case, with the exception of the case ground resistor, which acts as a bleeder to discharge voltages which might otherwise remain stored in the capacitors when the unit was not in use. Make all connections to B- to a bus running through the strobe circuit. Check the output voltage of the power supply before connecting R3 to the regulator tubes. It should be 450 volts or less. If it is higher, increase the value of R3.

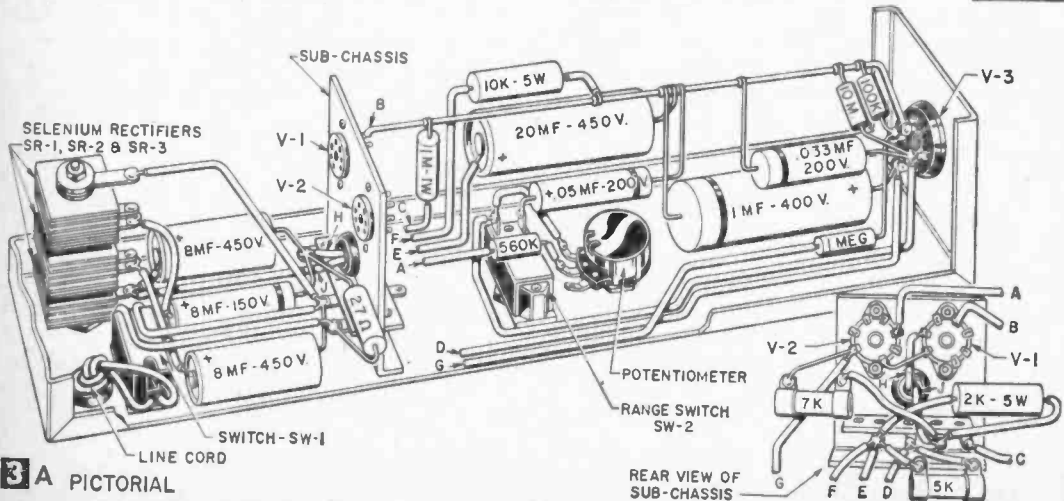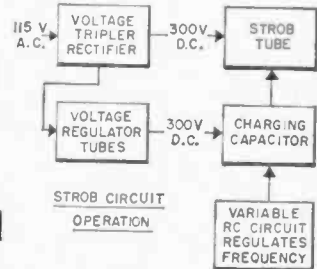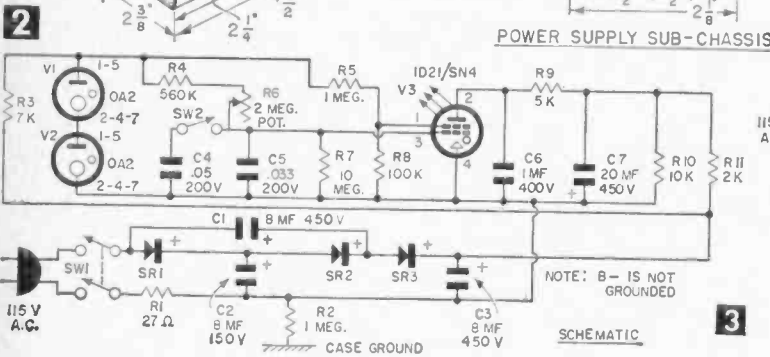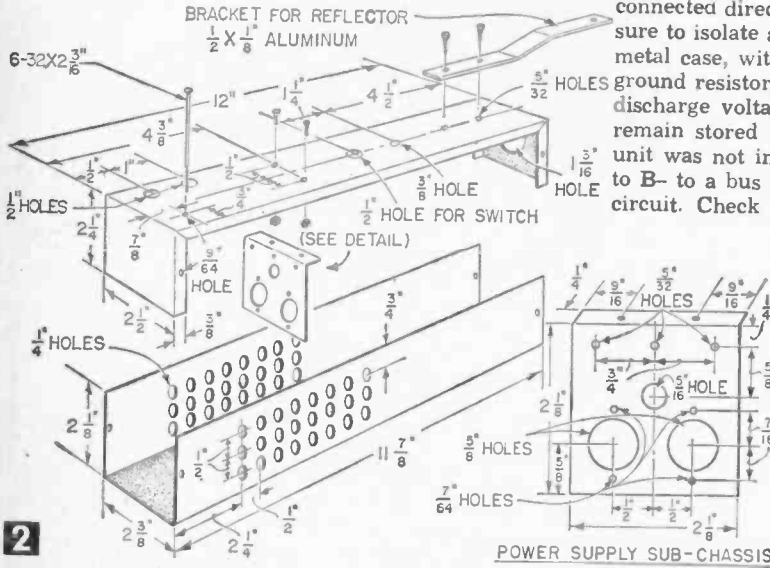CAUTION: High voltages in the power supply, and charges stored in the capacitors can be hazardous. Use extreme care to avoid shock in handling the chassis




when power is on. Never touch any live parts, or non-insulated tools, clips, etc., with bare hands.

Next wire the regulator tubes, and the stroboscope section as in the schematic and the pictorial view, taking care to connect the adjustable frequency control R6, so that it has minimum resistance when fully clockwise. Cover all bare wires with spaghetti tubing, and keep the leads to the larger capacitors, C6 and C7, short, so their leads will support them firmly in position.


After wiring, check your work carefully against the schematic. Then, turn the unit on. The strobotron tube should start firing immediately, with the flashing rate increasing as R6 is turned clockwise. The low and high ranges should overlap slightly; with R6 turned all the way clockwise on low, the flashing rate should be slightly faster than with R6 fully counter clockwise on high. The strobe tube makes a slight cracking sound as it fires on low rates, and normally makes a steady buzz at higher flashing rates.

The strobotron tube operates on the principle of placing a high positive potential on the plate with the cathode grounded. When the difference in voltage between the two grids reaches approximately 100 volts, the gas between the grids ionizes, which in turn "ignites" the gas between the cathode and plate. Once the grid voltages "fire" the tube, the plate takes over control, and the gas remains ionized, with a high current flowing between plate and cathode, until the plate voltage is lowered, even though the voltage difference on the grids is removed.

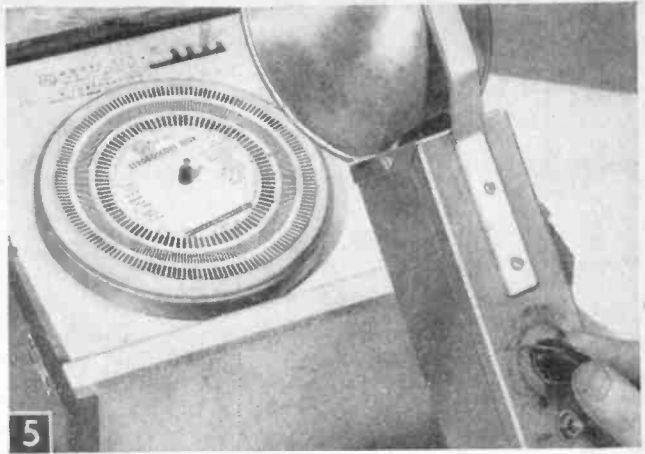In this circuit (Fig. 3) the plate resistor and capacitor are used only to prevent the tube from "firing" continually, and the timing between flashes is controlled by changing the grid voltages. The time constant of R9 and C6 is about




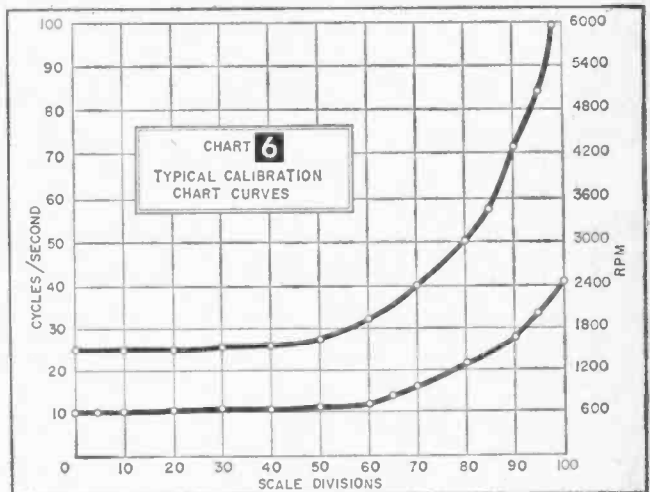An ordinary record turntable and stroboscopic disc are used to calibrate your strobe light.




.005 second, which is the duration of each flash. The grid voltage difference is controlled by a variable R-C charging circuit consisting of R4, R6, C5, SW2, and C4. When a capacitor charges through a resistor, the voltage across the capacitor increases, as shown in Fig. 4A, until it reaches the charging voltage. Notice that the voltage increases rapidly at first, and then tapers off as it approaches the charging voltage.

If arrangements are made to discharge the capacitor rapidly before it reaches the full charging voltage, a sawtooth wave, as shown in Fig. 4B is formed, and if this voltage "Y" is substantially below the full charging voltage, the curve will be more linear. Repeated charging and rapid discharging gives a series of evenly-spaced peaks, Fig. 4B. Charging of the plate and grid capacitors immediately after firing places a heavy load on the power supply, which would tend to drop the supply voltage from X to X1 as in Fig. 4C if this tendency was not minimized by the voltage regulator tubes, V1 and V2.

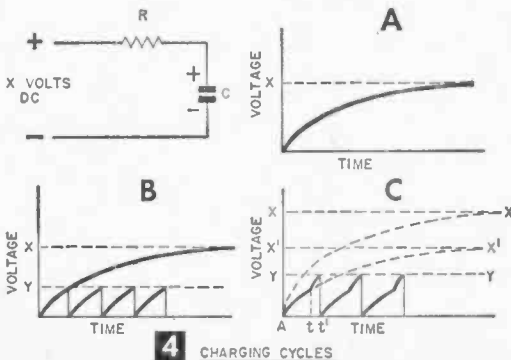

4 CHARGING CYCLES

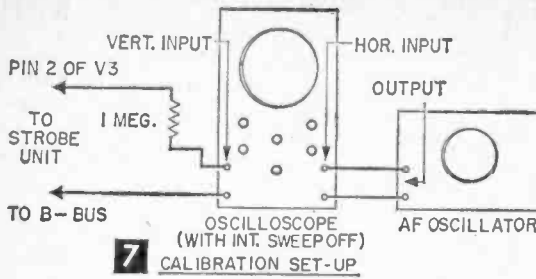



The time between the peaks of the grid capacitor charging cycle is dependent on the time constant of the capacitor and the related resistor. The range switch SW2 provides additional capacity for the low frequency range, and R6 makes it possible to vary the time constant for each range. Wired as in the schematic, your strobe unit will have a low range of 10 to 40 cycles per second (600 to 2,400 rpm) while high will cover 25 to 100 cps, (1,500 to 6,000 rpm). You can change the coverage of the unit by altering the value of the grid circuit resistance and capacitance. Reducing the values increases the charging rate, which can be increased up to the maximum flashing rate of the tube, which is 240 pulses per second, (14,400 rpm).

It is however impractical to use flashing rates below 15 cycles per second for eye observation, since persistence of vision, the principle which makes it possible for us to see a series of still pictures as a movie, would tend to blur the image. Complete construction by applying the decals to identify the controls, and protect them with a coat of lacquer, or plastic spray.

Calibrating Your Strobe. While the stroboscope will be very useful at this point, calibration will enhance its uses in measuring exact speeds. Rather than calibrate the frequency dial on the back of the case directly, it is suggested that you make a chart (Fig. 6). Two methods of calibrating can be used; the latter requires an oscilloscope, and is somewhat more accurate.

The simpler method is to use a 33½ and 78 rpm phono turntable, and a stroboscopic disc available at record stores (Fig. 5). Since the accuracy depends on the turntable, check it first, by watching the disc, with a fluorescent lamp, or neon bulb, which will flash at exactly the 60 cycle frequency of your power line. If your turntable is not equipped with a speed adjustment, you can slow it down by loading it with records.

Now, plug in the stroboscope, and allow it to warm up a few minutes. Set the range switch on high, with the control turned clockwise to the maximum flashing rate. Watching the disc, as in Fig. 5, turn the control counter clockwise until the 78 rpm ring appears to stop. Mark this dial reading on your chart, as 60 cycles per second (equal to 3600 rpm). Continuing to turn the dial counter clockwise, the ring will "stop" again at five lower points on your dial corresponding to 2400, 1800, 1440, and 1200 rpm. Repeating these

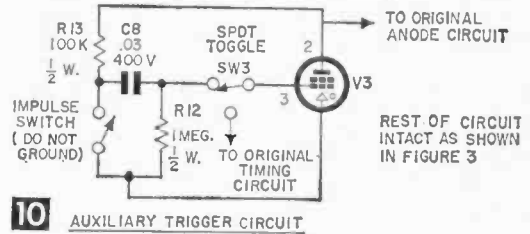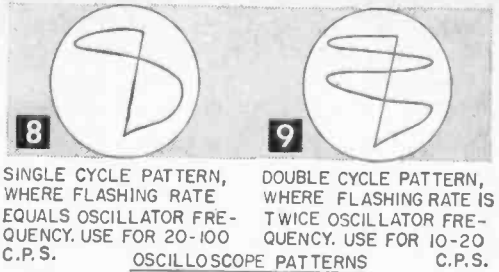

steps on low range, you will be able to obtain four calibration points representing 1200, 900, 720, and 600 rpm. With all of these points plotted on your graph, you will obtain curves indicating in-between speeds, as in the graph shown in Fig. 6.

CAUTION: Avoid looking directly at the flashing stroboscopy for more than a few moments. The light can be harmful.

The second method of calibrating requires an oscilloscope and an audio oscillator, connected according to Fig. 7, with a 1 megohm resistor input attenuator. Provided that you have constant line voltage, and warm up your equipment beforehand, it will provide more accurate results. Set the oscillator to 100 cps (equal to 6000 rpm) and adjust the strobe control to get a pattern similar to the one shown in Fig. 8. Since rpm is equal to cycles per second times 60, reduce the oscillator frequency in steps and take note of the dial settings, on your graph, required to obtain the scope pattern shown.

At frequencies below 20 cps, adjust the strobe for a two-cycle pattern (Fig. 9) since most oscillators will not go below 20 cps. To calibrate the low range, start with the high end of the scale, with the oscillator set at 40 cps, and adjust the strobe dial for the two cycle pattern. The strobe is then flashing at 20 cps, or 1200 rpm. Establish your curve points downward, using the two cycle pattern.

Accessory External Switch. If you wish to observe a motor or mechanism in stopped motion, which is changing speed, you can do it by continuously adjusting the dial, or more conveniently by means of an external switch, and the simple circuit addition shown in Fig. 10. The external switch can operate on a cam, or flattened portion of a shaft. A miniature switch with a nylon contact button which will operate at up to 9,600 rpm, without bounce is offered by Licon Division of Illinois Tool Works (Switch #16-4041).

Tips On Strobe Use. Using the stroboscope, you will notice that often you can "freeze" motion

at several different flashing rates which are multiples of the true speed. High speeds above your top flashing rate can be measured as harmonics. Generally the true speed will produce the sharpest image. When measuring motor speeds, engrave or paint a fine line out from the center of the shaft. Harmonic speeds will cause the line to appear at several points.

When adjusting the flashing rate for the true

speed of an object, the object will appear to move slowly in its true direction when the lamp is flashing too slowly, and seems to move slowly in the opposite direction when the lamp is flashing too rapidly. If a motor for example, is running at a true speed of 1800 rpm, and your strobe is set at 1801, the image will appear to be rotating slowly at 1 rpm in the direction of the motor rotation.

AMATEUR RADIO PUZZLE

By JOHN A. COMSTOCK

Do you like ham radio? Then here is an anagram puzzle on your favorite hobby. This puzzle contains many of the words, terms and abbreviations that

(For Solution, See Page 89.)

ACROSS:


- 1) A ham meeting.
- 7) A call acknowledging card.
- 9) Traffic (CW).
- 10) Code.
- 11) A ham radio outfit.
- 13) What a (.) sounds like.
- 15) Generator of frequencies.
- 17) A ham radio conversation.
- 18) One-million cycles.
- 21) A vacuum tube.
- 22) A short-wave listener.
- 24) Mutual conductance.
- 26) A circuit that is charged electrically.
- 28) A bunch of interconnected parts.
- 29) Type of tube base having eight pins and an aligning key.
- 30) No connection made.
- 33) Resistance is expressed in _____ (supply missing letters).
- 34) Break.
- 36) Call for all stations.
- 38) A bunch of frequencies.
- 39) A positive-potential grid.
- 40) A class of amateur operator license.
- 41) An effect connected with antennas.
- 43) Unit of inductance.

- 44) What is the correct time?
- 50) A radio amateur.
- 51) Class of ham license.
- 53) Reversing current.
- 54) Current flow.
- 55) A meter band used by amateurs.
- 56) A type of antenna named after its inventor.
- 61) After-all.
- 63) Medium of radio wave transmission.
- 64) Opposite of signal gain.
- 65) A type of battery cell.

DOWN:

- 1) These are troublesome to some amateurs.
- 2) One-million cycles, ohms, etc.
- 3) Di-di-di-dah, di-dah.
- 4) Safety signal (CW).
- 5) An oscillator coupled by its electron stream.
- 6) Double cotton covered (wire).
- 8) Distress call (CW).
- 12) Vacuum tube cathode current.
- 14) Plate current flow.
- 16) A carrier of intelligence in communications.
- 17) A rig's location.

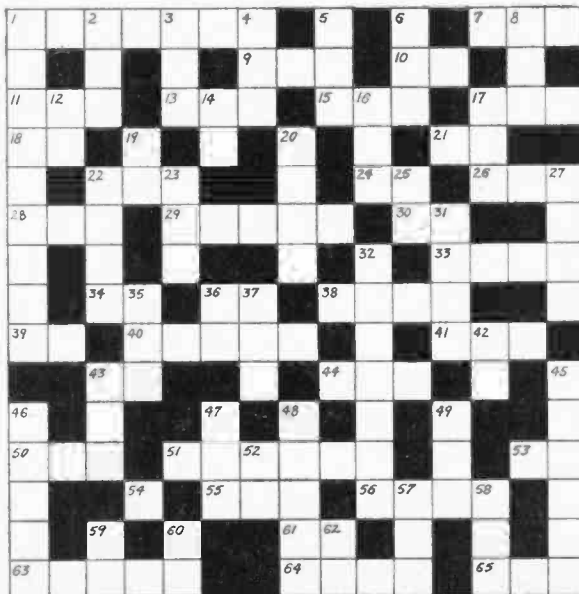- 19) A wave that is continuous.
- 20) A type of transmission line used by hams.
- 22) Matching transformer.
- 23) An amateur radio station record book.
- 25) Minute.
- 27) To check equipment for proper operation.
- 31) Something you must learn to send and receive before you can obtain your ham license.
- 32) Type of oscillator circuit having a tapped inductance.
- 35) Ham radio operators often pound one.
- 36) Mid-tap (abbr.).
- 37) Shall I send more slowly?
- 42) Neon.
- 43) It's not good for a modulator to do this.
- 45) A ham license.
- 46) An inductance used to limit the flow of ac.
- 47) Potentiometer.
- 48) Last amplifying stage of a ham transmitter.
- 49) Something current does in an inductive circuit.
- 52) Di-di-di-dah, dit.
- 57) Address.
- 58) Continuous waves that are interrupted.
- 59) Watt-hour.
- 60) Regulates voltage.
- 62) Unmodulated carrier wave.




Ten-Twenty Short-Wave Receiver

By HOMER L. DAVIDSON



HERE is a small, transistorized short-wave receiver—that the beginning experimenter can put together—that provides good short-wave listening on the 10- and 20-meter bands. And if you get a good specimen of a surface-barrier transistor, it will actually operate up to 8 meters.

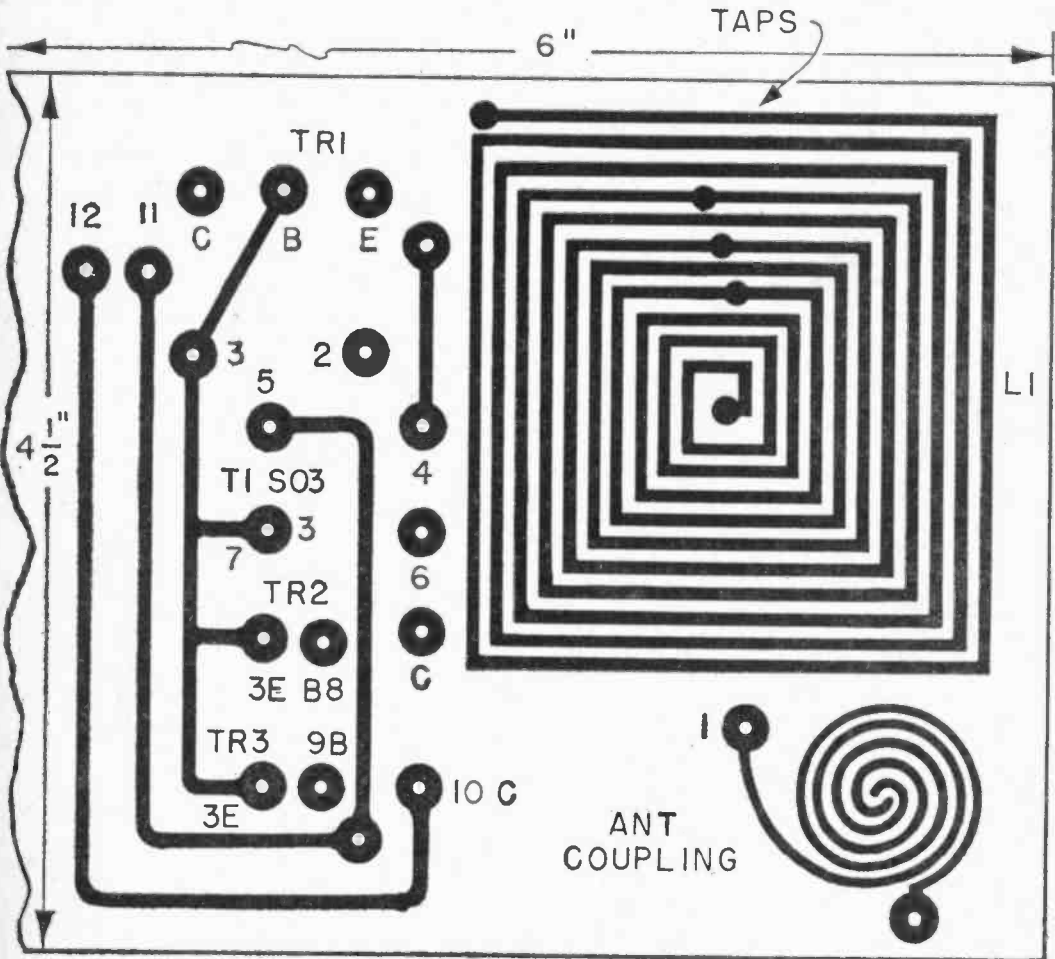The 10-20 is a novelty short-wave receiver that can be built by the novice. It will function up to 8 meters.



2 PRINTED CIRCUIT BOARD

ACTUAL SIZE

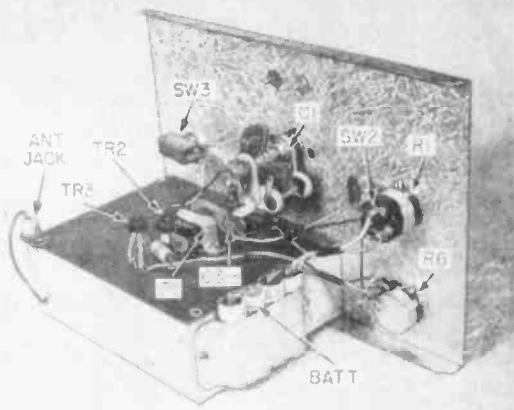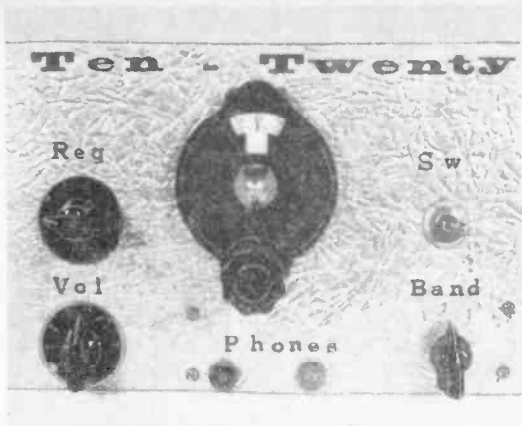

Transistor TR1, a Philco surface-barrier type, is the critical transistor. It is used as a super-regenerative detector.


The chassis for the transistor and parts is a printed circuit board (Fig. 2). Also on this board is coil L1. There is nothing complicated about laying out this coil. Follow Fig. 2, laying out 1/16-in. resist tape on the lines. Be sure the resist-tape has a spacing of its own width between each turn of the coil (a total of 10 turns). The coupling capacitor to the antenna jack and switch is also printed on the board. It is drawn with a ball point resist paint.


A homemade RF choke is wound with 35 turns of No. 28 cotton-covered wire over a 1/4-in. dowel. The regeneration control R1 and C3 form a time constant creating another oscillation that increases the sensitivity of the small receiver. Use of diode D-1 is optional. On the 10-meter band the fixed crystal diode seems to strengthen the signal and sharpens the regeneration point of oscillations. But on the lower, 20-meter band there isn't too much improvement. If you have a fixed diode on hand, solder it into the circuit. Otherwise, omit it.

There are two stages of audio incorporated here with a small volume control in the input circuit of TR3. The output of TR3 is fed directly into a earphone. Battery supply B1 furnishes voltage to the regenerative circuit. Regeneration is very smooth with this

type of operation. Battery supply B2 furnishes voltage to the collector side of TR1 and to both audio transistors.

Printed Circuit Layout. Trace the printed circuit directly on the printed copper board from Fig. 2. Place a carbon paper beneath this drawing and transfer it with pencil to the board. (Wash the printed copper side with soap and water to remove any finger marks or grease that might be on it.) A sharp pocket knife will be needed to cut off the tape at the joints. A ball point pen will make coupling loop and all round connection joints. If the paint runs into another circuit, let it dry and then take the pocket knife and cut or scratch out a separation. (This can

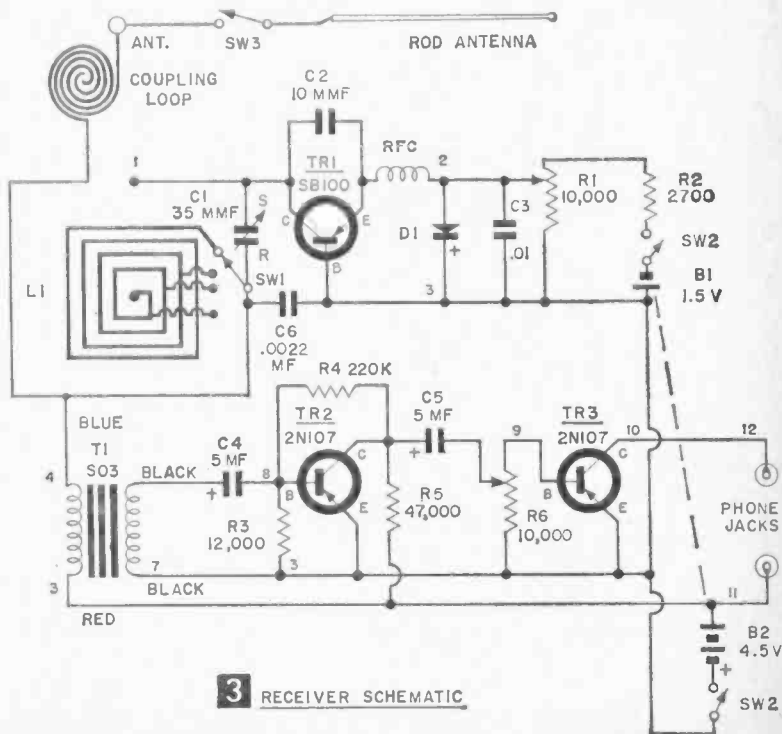

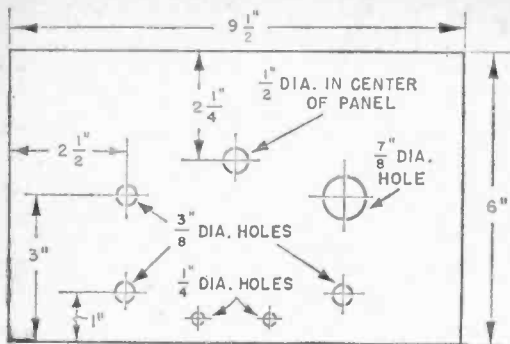

4 FRONT PANEL LAYOUT


also be done after the circuit has been etched by cutting or scratching out the jointed copper circuits.)

After the circuit has been traced on the copper board, lay down the tape resist and pen point in the rest of the circuits. Let the paint dry several hours, then pour enough etching solution into a small tray or flat dish to just cover the printed board. Rock the tray back and forth for quicker etching. It will take about an hour to complete the process.

Wash the board in clear water and pour the etching solution back into its container. (The solution can be used over and over again.) Now remove the resist material. Use a small knife point to pull off the tape and scratch off the paint resist. Drill all small holes before mounting any parts.

Set Operation. All of the small parts are mounted on the printed circuit board as they are wired into the circuit. Cut the front panel (Fig. 4) from Reynolds aluminum stock, available in

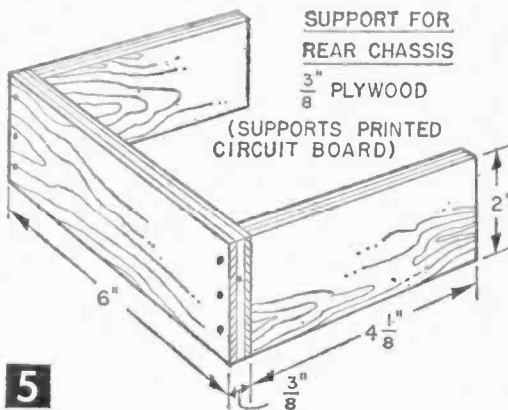sheets at the local hardware store. Figure 5 gives dimensions of the PC board support. Check correct battery polarity before throwing the on-off switch, plug in a pair of earphones and the unit is ready to go. Turn on the regeneration control in the earphone. Hook up the antenna and rotate




5

the tuning dial. Stations and whistles will be heard throughout the bands. When a station is located, turn the regeneration control down until the station is audible.

This little receiver has plenty of volume for earphone operation and some strong short-wave stations can be heard with the earphones laid beside the set. Not only will this small short-wave receiver bring in the 10- and 20-meter amateur bands but also aircraft signals and police bands.

Modified Screwdriver Lifts Tube

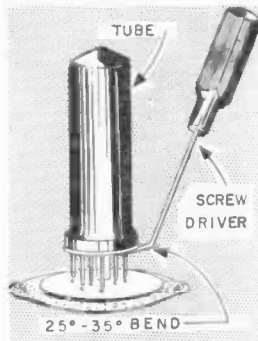• A long-stemmed screwdriver with the bit bent at a 25 or 35° angle makes a handy tube lifter for extracting tight-fitting tubes. To make the bend, heat the tip to a cherry red and let it cool slowly to remove the temper. Bend, then reheat the tip and plunge it into oil. The modified tool also makes a handy offset screwdriver for reaching into inaccessible places on a chassis.—JOHN A. COMSTOCK.



Phono Turntable Repair

• Poor reproduction from a phonograph having the rim-drive type turntable mechanism is usually caused by slippage of the rubber-tired drive wheel. To renew the grip of the rubber tire, sand it lightly with sandpaper. A non-slip dial compound (such as General Cement's *Non-Slip*) applied to the wheel will also cure slippage.

MATERIALS LIST—10-20—SHORT-WAVE RECEIVER

Design.	Description
C1	35 mmfd Hammarlund variable capacitor MC 35-5
C2	10 mmfd fixed disc capacitor
C3	.01 mfd 200-V paper capacitor
C4-C5	5 mfd 25V elec. capacitor
C6	.0022 mfd disc capacitor
R1, R6	10,000-ohm variable resistors
R2	2700 ohm, 1/4-watt fixed resistor
R4	220,000-ohm, 1/4-watt fixed resistor
R5	47,000-ohm, 1/4-watt fixed resistor
SW1	4 position, single throw rotary switch
SW2	DPDT switch on rear R1
SW3	SPST toggle switch
D1	1N64 or 1N34 fixed crystal
T1	S-03 transformer or equivalent (standard transformer)
TR1	SB100 Philco transistor
TR2-TR3	2N107 GE transistors
B1	1 1/2-v penlite cells
B2	three 1 1/2-v penlite cells
RFC	35 turn scramble wound over 1/4" form
L1	see text description

PRINTED CIRCUIT MATERIALS

Techniques Kit—Technicians #5003P obtainable from Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, N. Y.

	Alternate Kit
1-pt	PE-5 liquid etchant
1	PRLT liquid resist ball point pen
1	PCB XXXP copper Lam., 1 side 4 1/2 x 6"
1	PRT-2 tape resist 1/16 x 320"
	Also obtainable from Lafayette Radio

Telephone Actuated Switch For Remote Control

By W. F. GEPHART

Front-panel view of telephone switch remote control unit. Note circular vents in cabinet. Throat microphone is in foreground.



A **TIMER** will turn on a device at some future time, but it doesn't permit a change in plans. For example, it's nice to have the air conditioner on when you get home after a summer outing, but only if it's needed. With this telephone switch, you can be sure it turns on *only* when needed, because you turn it on by telephoning your home. The only requirement is that you have a dial telephone and the type of service where your telephone rings only when your number is called. Most metropolitan telephone service is of this type.


Switch operation is based on the timing relationship between ringing signals, and minor circuit modifications may have to be made to fit the ringing sequence of your telephone system. The circuit shown here is based on a system of one-second rings, spaced at five-second intervals. If your system operates on a different sequence, an understanding of the circuit is required to make the necessary, and minor, changes.

Tube V1 in Fig. 2 is an amplifier which closes relay Ry1 when the telephone ring is picked up by the microphone plugged into jack J1. Since this "connection" to the telephone is acoustic, it does not violate telephone company rules against devices attached to telephone lines "directly or by induction." Every time Ry1 closes, the "pulse" coil (Ry2A) energizes, moving the stepper relay arm one position. Tube V2 is a timing circuit that closes Ry4 for a given period of time when capacitor C4 is momentarily shorted out.

To operate the switch you dial your telephone number, let it ring *just once*, and hang up. You wait a few seconds, then dial your number again. Let it ring once to turn on the first device, twice to turn on a second device, etc. Ten seconds after you hang up on the second call, the device plugged into the proper outlet will come on.

The ring on the first call closes Ry1 momentarily and moves Ry2 to Position 1. This completes the circuit to the heaters of thermal relays Ry3 and Ry5, which require 12 and 25 seconds, respectively, to close. During the dialing time for the sec-

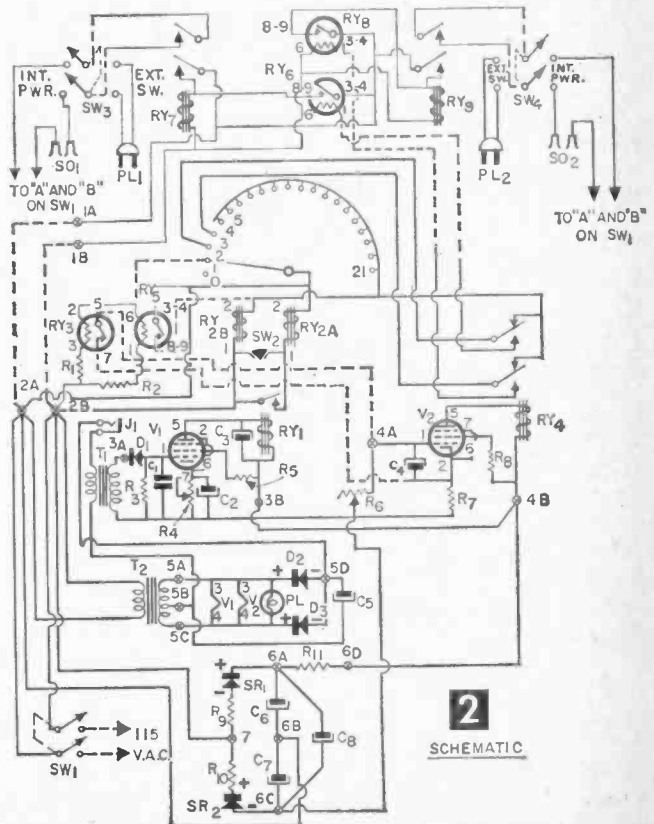ond call, Ry3 closes, shorting C4, which closes Ry4. The first ring of the second call moves Ry2 to Position 2, which removes the voltage to the heaters of Ry3 and Ry5. Ry3 opens and



Ry5 starts cooling, having had insufficient time to close. If you hang up after the first ring on the second call, Ry2 remains on Position 2, which completes the circuit to the heater of thermal relay Ry6.

After ten seconds, this relay closes, closing control relay Ry7, which turns on the device plugged into SO1. The control relay is then held closed by holding contacts.

Now the device is turned on, but the stepper relay (Ry2) is on Position 2 and Ry6 is still heated. After a time interval in the V2 circuit, Ry4 opens, removing the voltage to the heater of Ry6 and completing the circuit to the re-set coil (Ry2B) of the stepper relay. The stepper re-sets to zero position, Ry6 cools and opens, but Ry7 remains closed through its holding contacts. The unit is then back to the original condition, except that the first remote-controlled device is now turned on.

As shown here, the unit has two controlled circuits. Additional circuits for Positions 4, 5, 6, etc., could be incorporated for use by adding additional thermal and control relays. In such case, the time interval of V2 would have to be increased.

Proper timing is the key to successful operation. The timing of the thermal relays can be extended somewhat by resistance in the heater circuit, such as R1 and R2. Relay Ry3 is rated to close in 5 seconds, but closes at 12 seconds, due to R1, while R2 delays Ry5 from its rated 15


seconds to about 25 seconds. This use of resistors provides non-standard intervals and speeds up cooling (and therefore opening) time. A 25-second relay could be used for Ry5, but its normal opening time is about 90 seconds, as compared to the 15-20 seconds of Ry5 (as used here). Also, the octal version is used for Ry3, as it cools and opens faster than the miniature version. The timing of the V2 circuit is set by R6, whose adjustment will be discussed later.

Other Calls. Let's assume another caller than yourself lets your telephone ring a number of times before he hangs up. On each ring, Ry1 closes, the first ring moving the stepper relay arm to Position 1. The second ring occurs


five seconds later, so neither Ry3 or Ry5 can heat up or close. This second ring moves the stepper to Position 2, which closes the circuit to the re-set coil (Ry2B) through the contacts of Ry4 (since this relay is still open), and the stepper re-sets. The third ring moves the stepper to Position 1, the fourth to Position 2, which resets it, and the sequence continues.

When the caller finally hangs up, the stepper will either be at zero position or Position 1. At zero position, the unit is at normal position, so no further action is required. If ringing stops with the stepper on Position 1, Ry3 closes after 12 seconds, closing Ry4. Some 12 seconds later, Ry5 will close, completing the circuit to re-set coil Ry2B, and returning the stepper to zero position. In another 10-12 seconds, Ry4 will open, and the unit will be back to normal.

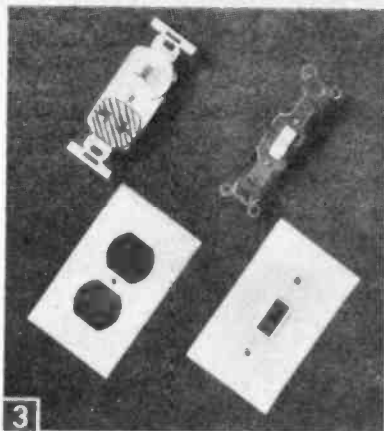
If, during the above, another call comes in after Ry4 closes, but before Ry5 can close and re-set the stepper, the first ring will move the stepper arm to Position 2. Since Ry4 is closed, the circuit to Ry6 will be completed, but the next ring




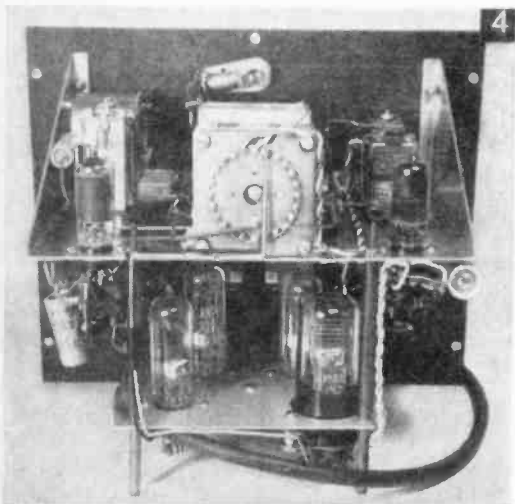3 Switch-outlet at left replaces regular switch at right (see text) when appliance controlled by wall switch is to be remote-controlled by telephone.



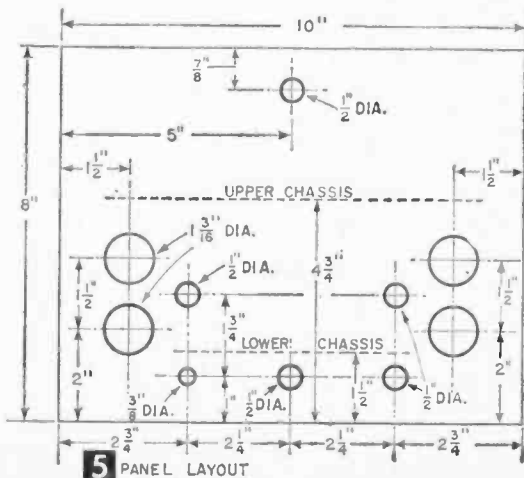4 Back view of unit showing dual chassis construction.



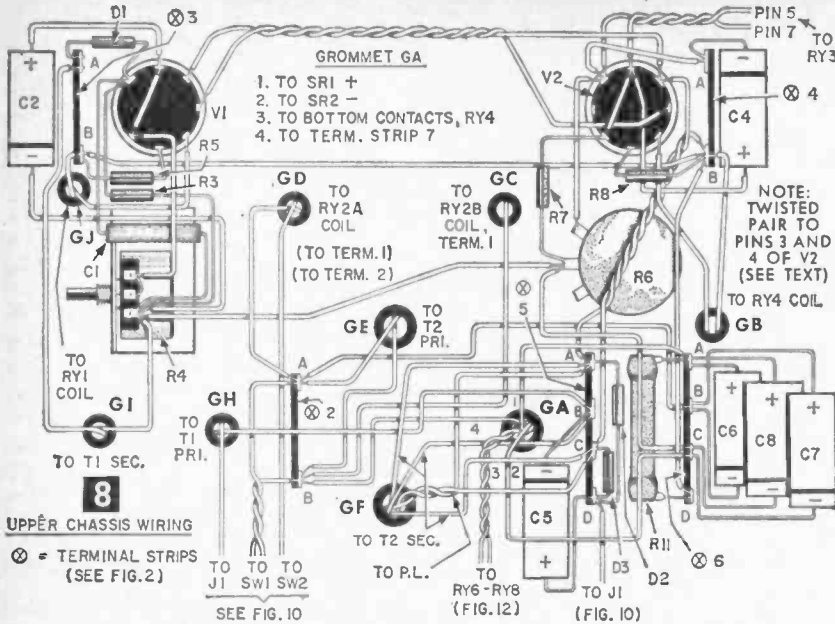

the two chassis (which rest on the bottom) will properly support the upper chassis. If scrap aluminum is not on hand, a 3½ x 6 x 8-in. "Minibox" (Bud CU-3009 or CU-2109) will provide all that is required. The flanged side of this box will make the upper chassis merely by cutting the ends of the box to make the side supports, and the other half of the box will make the lower chassis and the 2 x 2-in. mounting for R4.

After the panel and chassis sections have been drilled and punched, mount components on all three and attach the upper chassis to the panel. The upper chassis and panel must be wired before the lower chassis is attached to the panel, and the heavy lines in the schematic (Fig. 2) show this initial wiring. As it proceeds, hold the lower chassis (with components mounted) in place from time to time, to check for clearance.

Figures 8, 9, 10 and 11 show wiring. In Fig. 8 a twisted pair is shown to pin 3 of V2 and terminal 4B of the terminal strip, upper right. The twisted pair leads should be shown to pins 3 and 4 of V2; the lead now going to terminal 4B should be shown to V2's pin 4. Filament and pilot light wiring is done first, followed by the carbon microphone voltage supply. The dc power supply is wired next, and then the relay wiring. In wiring between SO1, SO2, PL1, PL2, SW3, SW4 and the contacts on Ry7 and Ry8, be sure to use at least #14 wire. The tube circuits are wired last.

Testing. Before attaching the lower chassis, temporarily attach ac leads to SW1 and make sure that filament, microphone and plate voltages are available. The filament voltage should be 6.3 v ac, the microphone voltage about 3.5 v dc, and the plate voltage around 260-280 v dc. Next, put V1 in its socket and adjust sensitivity control R4.

This adjustment is very critical and must be


set to your telephone. If your telephone has an adjustable bell, turn the bell to its loudest point to minimize the sensitivity required. Also, allow the unit to warm up 5 minutes before making adjustment.


Insert a milliammeter in the B+ lead of V1 at Tie Point 3B. Using R4 to vary the plate current, adjust the relay spring so that the relay closes at about 5.8 ma. With this adjustment, the relay should open at about 4.4

ma. Then set R4 so that the tube draws about 4 ma.

To test this adjustment, place the microphone under the telephone with the two buttons resting against the bottom of the instrument as close to the ringer openings as possible, to utilize both sound and vibration. Have a friend call you and see if Ry1 closes on each ring, and what current is drawn by V1 during the ring. The dc voltage across R3 during ringing ought to be about 6 v, increasing the plate current to over 6 ma. There is a fraction of a second delay in the relay closing, due to the charging of the capacitors in the V1 circuit, but this minimizes accidental triggering of the relay when the telephone is touched or the receiver raised. If the plate current of V1 drops during the ringing, check the polarity of D1.

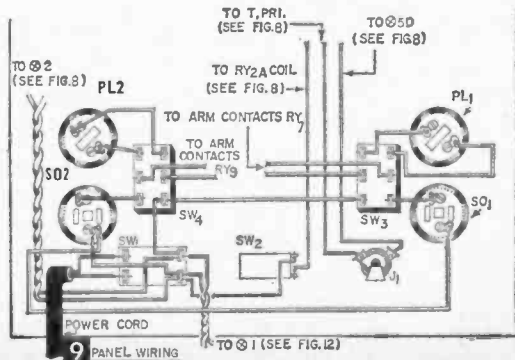After this adjustment has been made, put V2 in its socket and set R6 at mid-resistance point. As V2 warms up, Ry4 will close and reopen after a short interval. This is caused by plate current flowing as C4 charges up. After Ry4 opens, set R6 to maximum resistance and mo-



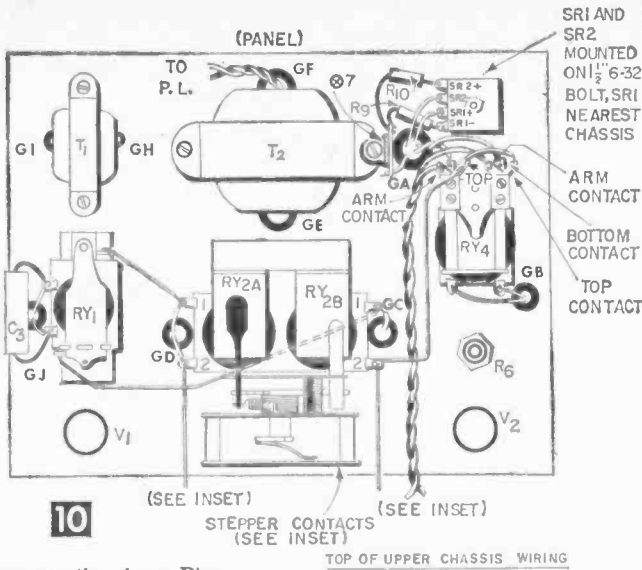

Before attaching the lower panel, pre-wire it to the extent possible, as shown in Fig. 11 and in the light lines in the schematic, Fig. 2. Then fasten it to the panel and bolt the two chassis together with two 5-in. 6-32 bolts and spacers. The spacers are made of 1/4-in. copper tubing, the ones between the chassis being 3/4-in. long, the lower ones 1 1/2-in. long. The wiring is then completed as shown by the dashed lines in Fig. 2, running some wires from one chassis to the other along the spacers.

To check final wiring and thermal relay timing, plug in both tubes and Ry3, and press the "Test" button once. The stepper relay should move to Position 1, and after about 12 seconds Ry4 should close, indicating that Ry3 has closed. This interval was selected as the average time required to hang up after the first call, re-dial a seven letter-digit number, and get the first ring. If this time is too long, or Ry3 doesn't close, reduce the size of R1, by trial and error. If the interval is too short, increase R1.



Next, remove V2, re-set the stepper manually, and plug Ry5 in. Press the "Test" button once, advancing the stepper to Position 1. After about 25 seconds the stepper should re-set, indicating that Ry5 has closed. If this timing interval is off, adjust with Ry3.

For final checks, replace V2, set SW3 and SW4 to "Internal Power," and plug a table lamp (or night light) with the lamp switch "on" into SO1 and SO2. Press the "Test" button once and as soon as Ry4 closes, press it again. After 10 seconds, Ry7 should close, turning on the lamp plugged into SO1. Repeat this test, but press the button twice after Ry4 closes to see if Ry9 and the lamp plugged into SO2 goes on. To release control relays (Ry7 and Ry9), turn the unit off momentarily.

Before adjusting timing control R6, have a friend call you so you can time the length of the rings and the interval between them. The time Ry4 stays closed must be equal to the total ring-interval time that it takes to move the stepper relay to the last control position (in this case, Position 3), plus 10 seconds. For example, in the unit shown (with two control positions) with a ringing pattern of one second rings spaced five seconds apart, the total time for Ry4 to be closed would be:


- 1 second for ring that moved Ry2 to Position 2
- 5 seconds interval between rings
- 1 second for ring that moved Ry2 to Position 3
- 10 seconds for Ry8 to close
- or a total of 17 seconds, plus 5 seconds leeway for a total of 22 seconds

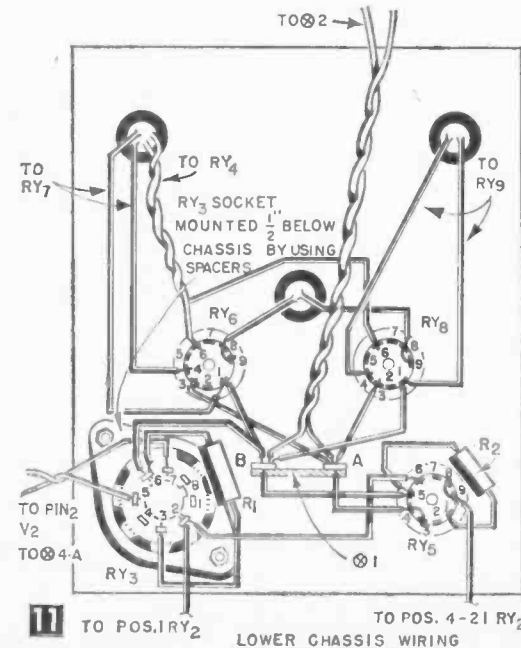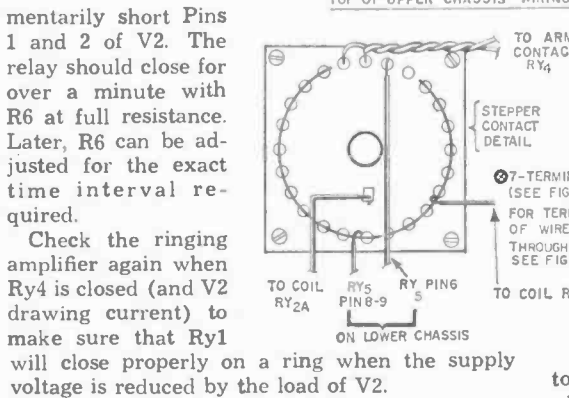Set the time on Ry6 by shorting Pins 1 and 2





mentarily short Pins 1 and 2 of V2. The relay should close for over a minute with R6 at full resistance. Later, R6 can be adjusted for the exact time interval required.

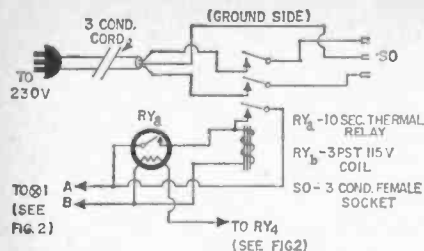Check the ringing amplifier again when Ry4 is closed (and V2 drawing current) to make sure that Ry1 will close properly on a ring when the supply voltage is reduced by the load of V2.



12 230 V CONTROL RELAY WIRING

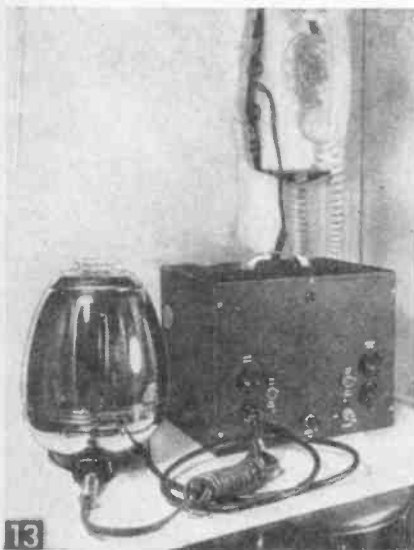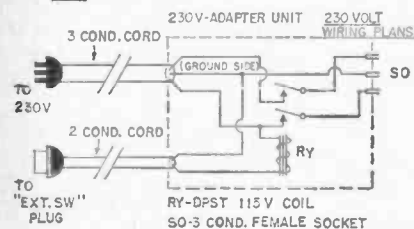

13 Unit in operation. Throat mike on wall telephone will turn on coffee maker—black box, black magic, black coffee.

of V2 together repeatedly until the desired time is reached.

Final tests consist of having a friend call to check operation under actual conditions. With table lamps plugged into SO1 and SO2, and SW3 and SW4 on "Internal Power," have your friend call, let the phone ring once, re-dial and let ring once again. If the first ring on the second call comes in before Ry4 has closed and your friend's dialing speed is average, decrease the time for Ry3 to close. If Ry4 had closed before the first ring of the second call came in, the lamp plugged into SO1 should go on about 10 seconds after the second call. Repeat this test, but let the telephone ring twice on the second call. Lamp 1 will remain on, and 10 seconds after the second ring, Lamp 2 should go on, the stepper relay re-setting shortly after. If Ry4 opens (re-setting the step-

MATERIALS LIST—TELEPHONE SWITCH

Design.	Description
R1	1200 ohm, 1 watt
R2	2000 ohm, 1 watt
R3	.27 meg. 1/2 watt
R4	2000 ohm potentiometer
R5	27K, 1 watt
R6	5 meg potentiometer
R7	3000 ohm, 1 watt
R8	12K, 1 watt
R9, R10	27 ohm, 1/2 watt
R11	3000 ohm, 10 watt
C1	.02 mfd, 200 v
C2	10 mfd, 25 v
C3	25 mfd, 25 v
C4	50 mfd, 15 v
C5	50 mfd, 6 v
C6, C7	20 mfd, 150 v
C8	20 mfd, 450 v
Ry1	SPDT, 2500-ohm coil (Potter & Brumfield LM-5)
Ry2	midget 21 pos. stepping relay (Guardian MER-115)
Ry3	5-sec. thermal relay, normally open (Amperite 115N05)
Ry4	4PDT, 5000 ohm coil (Guardian Series 200 coil, and Type 200-M5 contacts)
Ry5	15-sec. thermal relay, normally open (Amperite 115N015T)
Ry6, Ry8	10-sec. thermal relays, normally open (Amperite 115N010T)
Ry7, Ry9	4PDT, 115-v ac coil (Guardian Series 200 coil & Type 200-M5 contacts)
T1	microphone transformer (Merit A-2929)
T2	filament transformer, 6.3 v @ 2 amp. (Merit P-2945)
SW1	DPST 15-amp. toggle switch (Carling 2FB54-73)
SW2	SPST push button
SW3, SW4	DPDT 15-amp. toggle switches (Carling 2GL-53-73)
J1	open circuit jack
D1, D2, D3	1N66 or 1N34 diodes
SR1, SR2	65 ma., 130-v selenium rectifiers
PL1, PL2	male chassis plug (Amphenol 61-M)
SO1, SO2	female chassis socket (Amphenol 61-F)
PL	6.3-v pilot lamp and jeweled socket
V1	6AU6
V2	6CB6
	7 x 8 x 10" cabinet (Bud CU-879), scrap aluminum (see text), two 7-pin miniature sockets, three 9-pin miniature sockets, one octal socket, four 1" vent plugs, handle, two 5" 6-32 bolts, tie points, miscellaneous hardware. T-30 surplus throat microphone (available from G&G Radio Supply Co., 51 Vesey St., New York 7, N. Y.)

per) before Lamp 2 comes on, lengthen the time interval of the V2 circuit, by adjusting R6.

Adaptations. This unit can be used for switching 230-v circuits by altering either or both control relays (Ry7 and Ry9) or by building separate 230-v adapters.

Both means are shown in Fig. 12. Either alteration requires a power lead to a 230-v source. With relay modification, this lead can be brought out of the cabinet at the point normally used for radio normally used for SW3 or SW4.

The control relays specified have 8-amp. contacts. If additional capacity is required, either heavier relays (requiring additional chassis space and heavier internal wiring) or external power relays will be required. In the latter case, the external relay used to turn the device on should have a 115-v ac coil. It would be plugged

into SO1 or SO2. When using unit with air conditioners or other heavy-duty appliances, use a portable cord and other connected wiring from an outside relay that has adequate size to carry the current of the appliance safely. Relay contacts should also be capable of carrying the required current.

Figure 13 shows the unit in operation—using the throat microphone strapped to a wall telephone—set up to turn on an automatic coffee maker. Whenever using the unit with a telephone with a separate bell, the microphone should be strapped to the bell box, near the bells.

In operation, there are several points to keep in mind:

- 1) Let the unit warm up five minutes before using.
- 2) Place the microphone as near the bells as

possible, and tight against the bottom (or side) of the telephone or bell box, to get both sound and vibration. Where adjustable bells are available, set to loudest setting.

3) Keep in mind that, when calling, the sound you hear is not the actual bell ringing; it is a ringing "signal" indicating that ringing current is being placed on the line. If the sound is a short, fractional part of a full ring, the bell may have merely "tinkled," and Ry1 may not have closed. In such case, complete the calling procedure, and if there is any doubt in your mind, repeat it a minute later. Unless impulse relays

are used (to turn "on" and "off"), repeated calls on the same code won't hurt.

4) You can turn on the circuits in any sequence; that is, Number 2 first, followed by Number 1, or vice-versa.

5) If there is repeated difficulty in Ry1 closing on rings, check your line voltage regulation. In areas of high line-voltage variation, the plate voltage to V1 may vary enough to require different settings for R4. In such case it may be necessary to put two voltage regulator tubes (an OA2 and OB2, series-connected) in the doubler power supply circuit.

Compass Galvanometer

MANY electrical measuring instruments are based on the design of the d'Arsonval String Galvanometer, but substitute a needle-suspended coil riding on jeweled bearings for the hanging coil employed in the original precise lab instrument.



The galvanometer is usually used to indicate the polarity and presence of small currents by comparison methods.

The d'Arsonval instrument suspends a small coil between the poles of a permanent horseshoe magnet. When a current flows through the coil it becomes an electromagnet and its like poles repel the like poles of the horseshoe magnet, thus causing the coil to turn or twist on the metallic string or ribbon by which it is suspended (Fig. 2). The strength of the current determines the extent of the coil's rotation.

A small pointer attached to the moving coil registers on a curved dial, or a tiny mirror is attached to the galvanometer string. A beam of concentrated light is aimed at the mirror, bouncing the beam off to a wall screen or chart to give great magnification of tiny current changes.

Making a Simple Galvanometer. A small amount of insulated magnet wire, any pocket compass and a 2 1/4 x 3 1/2-in. scrap of plywood is what you need to make the simple galvanometer shown in Fig. 1. Cut a strip of cardboard 3/4 in. wide and 3 3/4 in. long. Score the cardboard 3/4 in. from each end, with a dull knife blade and crease so the cardboard resembles a C or bridge shape. Now glue the cardboard to the edges of the wood base.

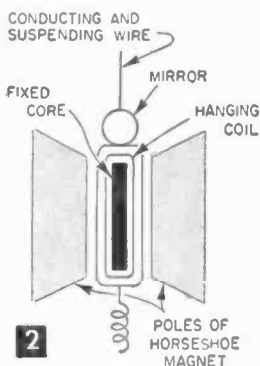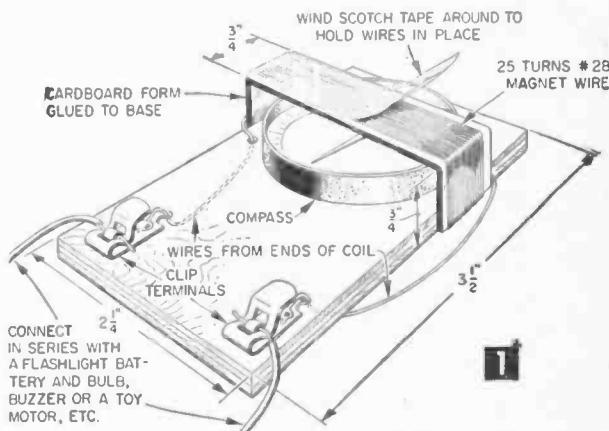Bind the cardboard with a rubber band until glue or cement dries. We wound 25 turns of #28 magnet wire around the cardboard, but heavier





wire and fewer turns will work, too, with a slight drop-off in sensitivity.

Scotch tape is wound around the finished coil to keep the wire turns in place. Connect the ends of the coil to screw terminals or clips. Slip the compass under the coil in a position where its needle comes under the coil and parallel to the coil turns.

Connect the galvanometer in series with a flashlight battery and bulb, a buzzer or a toy motor, etc. When the circuit is closed the compass needle will be drawn so that it is at right angles to the coil (Fig. 1). A slow swing of the needle indicates the circuit is drawing little current. A rapid swing denotes an increase in current flow.

To show how sensitive this simple galvanometer is, connect what appears to be a dead flashlight cell across the terminals, immediately breaking the circuit. The compass needle will spin at a merry clip.

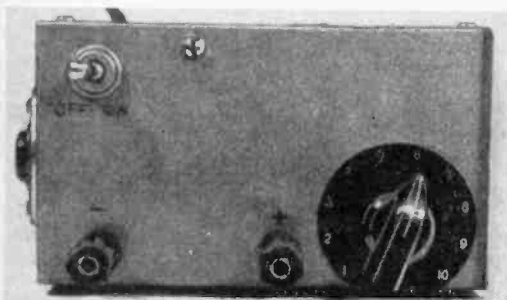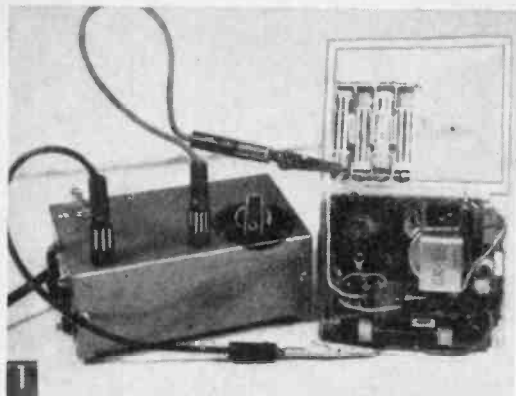The compass galvanometer's needle would be the horseshoe magnet in the d'Arsonval instrument. But, here we cause the magnet to turn with the coil remaining in a stationary position. However, the end result is the same no matter how the galvanometer is constructed.



One of the handiest instruments the serious transistor experimenter can own, this regulated power supply has variable voltage control from zero to 10 volts dc.

For Transistor Circuits—

A Regulated Variable Power Supply

By FORREST H. FRANTZ, Sr.

POWERING experimental transistor circuits with batteries is expensive and exasperating. It's difficult to keep a supply of fresh batteries on hand, and the variation of voltage requirements from one circuit to the next means frequent changes in a battery supply lash-up. Voltages that aren't multiples of single cell voltage can't be obtained from batteries without wasting some battery power, and the voltages of the cells themselves tend to drop quickly.



The obvious answer is a power supply that operates from the ac line. The power supply described in this article has extremely low ripple—good enough for the most crucial

transistor circuit, a variable output voltage control, and regulation that will keep the output voltage from varying due to changes in line voltages or changes in equipment current demand. Cost of components for this unit is approximately \$15.


Operating Principles. The common collector transistor circuit configuration (Fig. 2A) performs the regulation task in this power supply. This circuit, sometimes referred to as an "emitter follower circuit," is the transistor counterpart of the vacuum tube cathode follower. The circuit has 100% current feedback and is extremely stable under temperature variations. The voltage from emitter to ground is nearly equal to the applied voltage from base to ground. The emitter voltage remains constant in spite of relatively large fluctuations in the collector voltage or variations in the emitter to ground load resistance. The emitter current is equal to the base current times the Beta of the transistor. Thus, a battery may be used to set the base potential.

The circuit of the regulated variable power supply is shown in Fig. 2B. The transformer is a 12.6 v, 1 amp filament unit. A General Electric 1N1115 silicon rectifier is employed in a half-wave circuit with a 1,000 mfd filter capacitor. This basic dc power supply provides collector voltage for transistors T1 and T2, and in turn, voltage at relatively high currents for the load.

Base voltage for transistor T1 is supplied by a reference supply consisting of the 12-v battery B and the 5K potentiometer R1. R1 may be adjusted to present any voltage from 0 to 12 to the base of emitter follower T1. Transistor T2 is another emitter follower directly coupled to T1. The current gain of the cascaded emitter followers is so great that for reasonable power loads, the current demand on the battery (beyond the current required by R1) is negligible (R1 draws 2.4 milliamperes from the battery). The battery switch SB and the line switch SA are ganged to prevent battery current flow when the power supply is turned off. Resistor R2 permits adjustment of the

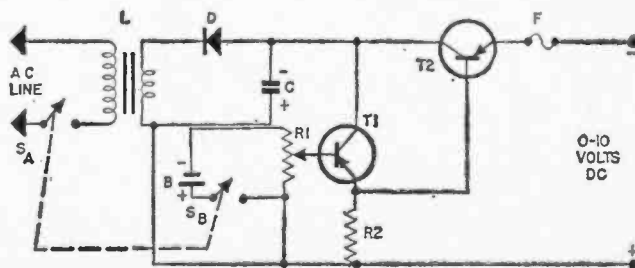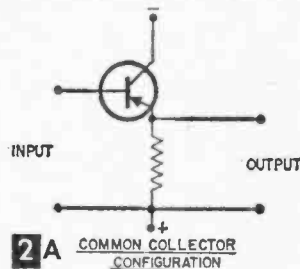

B CIRCUIT OF REGULATED POWER SUPPLY

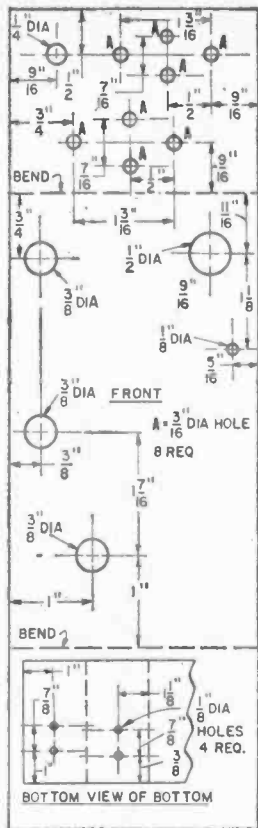


3 DRILLING LAYOUT

Side view of power supply showing transistor mounting.


terminal voltage to zero under low- or no-load conditions.

The ripple voltage with 9 v dc at 200 ma to a terminal load has a peak to peak value of only .004 volts! At higher currents the variation from straight line dc increases. The ripple increases to .04 v peak to peak when the current to the load is 1/2 amp.

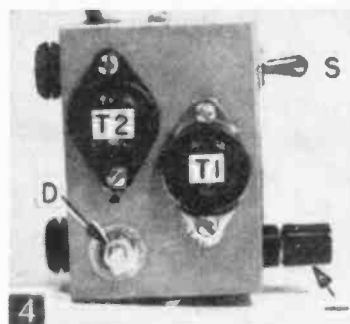Construction. The power supply is housed in a Bud CU-2106 aluminum Minibox. The layout for drilling the required holes is shown in Fig. 3. Drill small pilot holes before using



4

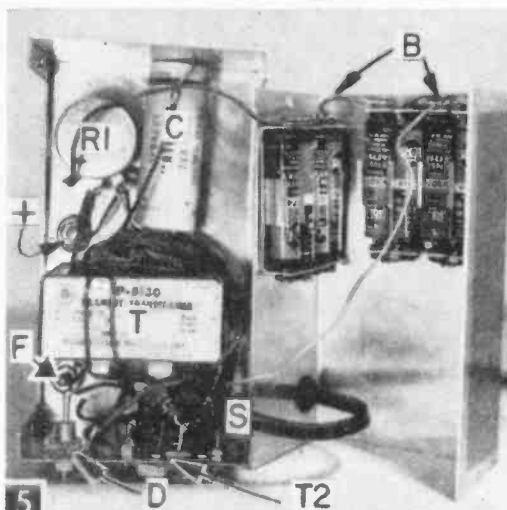

Interior view of Minibox chassis with components in place.

MATERIALS LIST—POWER SUPPLY

Desig.	Description
R2	1K, 1/2W resistor, 10%
R1	5K, 2W wirewound potentiometer (Clarostat 43-5000)
C	1,000 mfd, 12-v electrolytic capacitor (Sprague TVA-1133)
T1, T2	2N307 transistors, (Sylvania)
D	1N1115 silicon rectifier (GE)
SAB	DPST toggle switch (Cutler-Hammer 8360K7)
L	12.6-v filament transformer (Stancor P-8130)
B	12-v battery (8 RCA VS074 cells series connected)
F	fuse (see text)
two	4-cell battery holders (Lafayette MS-170)
	binding posts (Grayhill 29-1 Red and 29-1 Black)
	2 1/8 x 3 x 5 1/4" aluminum Minibox (Bud CU-2106)

3/8- and 1/2-in. drills for the larger ones. All components except the battery holders and batteries mount on the front of the box.

Cut the shaft of R1 to a length of 1/2 in. Mount R1, T1, T2, SAB, the binding posts and the rectifier D (see Figs. 4 and 5). Insulate the binding posts (which are provided with insulation "humps") are not used. Insulate the rectifier from the box with the small mica insulators provided with it. Exercise extreme care in mounting the rectifier. Don't use additional insulating washers because the aluminum box serves as a heat sink for it. The collectors of T1 and T2 terminate on the transistor shells. Note that these connect directly to the aluminum box when they're mounted.

Next, the wiring associated with transistors T1 and T2 should be completed. Then mount the transformer (cut off one of the mounting flanges) and complete the circuit wiring, including the installation of C and R2. Two leads approximately 7 in. long should be provided for connection to the battery holders. The fuse F is a 1/2-in. length of #36 copper wire with its ends soldered to the negative binding post (or to a short piece of hook-up wire on the binding post) and the hook-up wire lead from the emitter of T2. It prevents damage to the power supply components if the output terminals are accidentally short circuited.

Mount the battery holders on the back half of the aluminum box and connect the terminals in series. Fill the eyelets which will contact the batteries with solder. Insert the batteries in the holder and connect the holder to the two leads provided for this purpose. Be sure the switch is in the off position when you do this.

Assemble the front and back halves of the box. Dress the leads so they won't short or pinch when the box is completely assembled. Fasten the four screws, and your power supply is ready.

Salvaging Parts for Experiments

• A fluorescent light starter contains several parts that can be used by radio-electronics experimenters, such as a thermal switch, small paper capacitor, and neon glow lamp.—J.A.C.







Eliminating TV Interference

How simple filters can cut out annoying TVI from home appliances, neon lights, aircraft, ham broadcasts or other sources

By W. F. GEPHART

TELEVISION interference (TVI) comes from a number of sources, and to eliminate it we must first determine the type and, if possible, the source (Figs 1, 2 and 3).

For best results, the interference should be filtered out at the offending device; if that is not possible, it probably can be eliminated at your TV set. Interference is classified into two types as in Table A, (1) broad-band, where the source consists of many frequencies and harmonics; and (2) narrow-band, where the source has one fundamental frequency and normal harmonics. Most narrow-band inter-

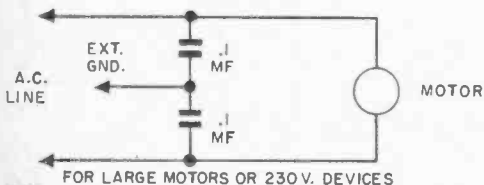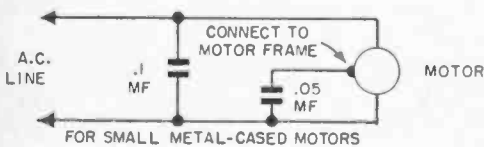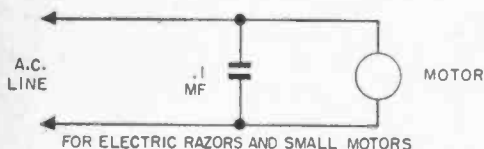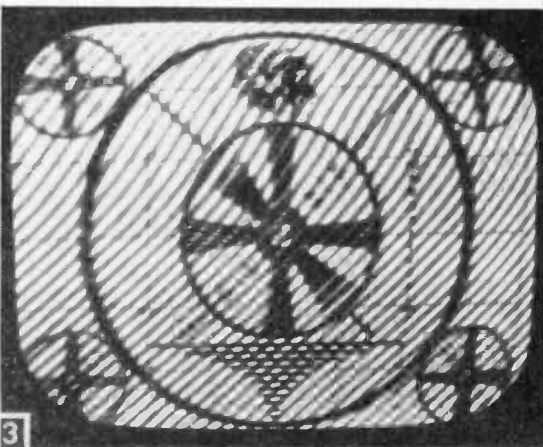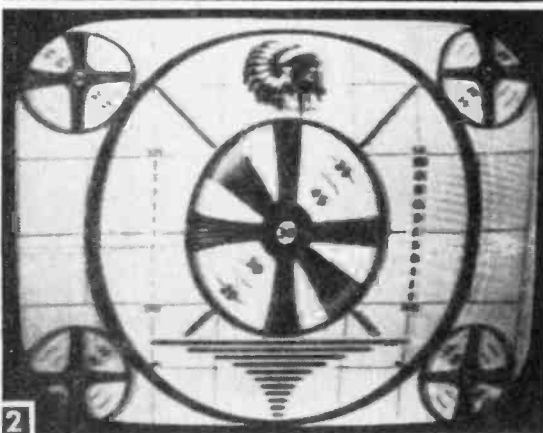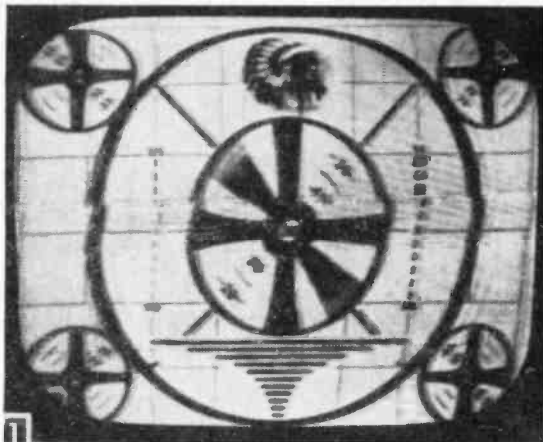

4 SIMPLE POWER LINE FILTERS

1 Ignition or "spark" interference is characterized by multiple bands of "hash" moving up and down the screen, displacement of picture and often a popping noise in the speaker.

2 A-C interference caused by small motor results in a single unmoving band of "hash."

3 Diagonal lines (sometimes a herringbone or chicken-wire pattern) indicate R.F. or oscillator interference.



A-C line filter plugged into outlet, with TV set plugged into top. Other half of outlet can be utilized.

ference is due to other radiating electronic equipment.

Many cases of broad-band, a-c motor interference can be traced by noting what appliances in your home are operating when the interference is present. Cure by connecting one of the line filters detailed in Fig. 4 to the troublesome motor or device itself to eliminate the interference before it gets into your TV set through the power lines or through the antenna's picking up the radiated interference from power lines.

If you can't install the filter at the trouble source, plug a line filter made as in Figs. 5 and 6 into the wall outlet, and plug the TV set into the filter. Connect the binding post on the top to a good ground such as a water pipe. Mount the male chassis-type plug in one side of the filter chassis as near the bottom as possible as in Fig. 6, and the female socket in the top, slightly off-center to allow for binding post. The coils should not touch the metal case; the wire is stiff enough to make


TABLE A—COMMON TYPES OF TVI SOURCES

Broad-band Interference

Type	Enters Set Thru	Remedy
Ignition & spark noise Fig. 1 (most common type)	Usually through A-C lines; sometimes thru antenna if interference is near and intense	Wide-band A-C line filter on set or filter on trouble causing device
Electric Motor noise Fig. 2	A-C line	Filter at motor or on set; Wide-band A-C line filter on set
Non-communication electronic equipment such as neon lights, diathermy units, infra-red heat drying equipment, etc. (characterized by wide bands of curved lines across picture)	A-C line	Same as electric motor

Narrow-band Interference
(Entering through antenna)



Type	Appearance	Remedy
Oscillator radiation from another TV set Fig. 3	Diagonal black lines or herringbone or chickenwire pattern across screen	Shield offending set (line cabinet with foil or screening) ground receiver (if designed for it), wave trap
Low frequency radio (B.C., police, Hams, etc.)	Diagonal black lines, lines across the screen, usually shifting and moving	Line filter or wide-band R.F. antenna filter
Medium frequency radio (S.W., Hams, aircraft, etc.)	Same as low frequency radio	Specific frequency high-pass filter, wide-band R.F. antenna filter, re-orient antenna
High frequency radio (F.M., aircraft, T.V., etc.)	Same as low frequency radio	Wave trap (stub), re-orient antenna

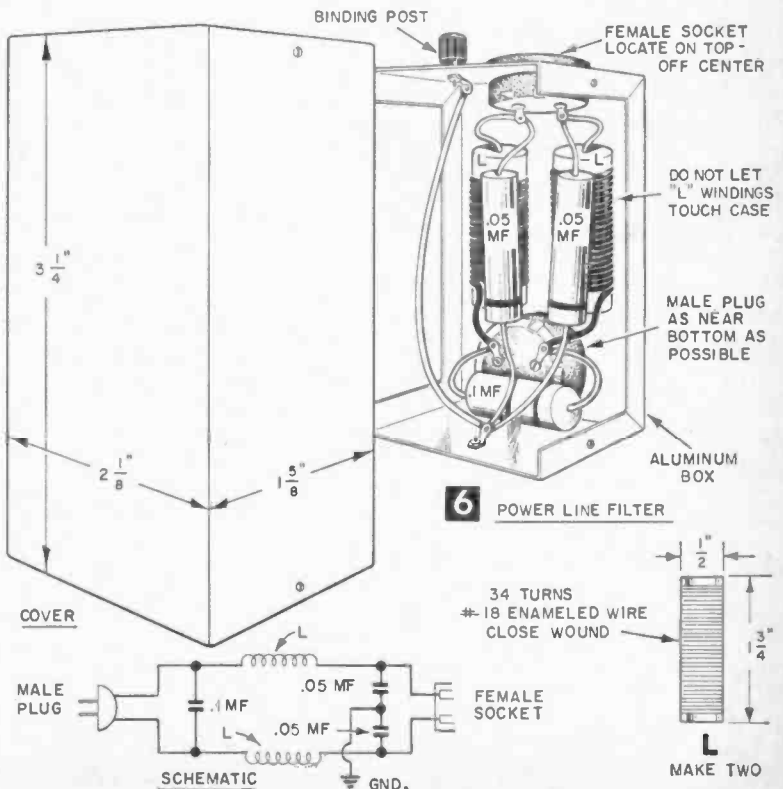


them self-supporting.

Sometimes turning (re-orienting) the antenna slightly, or moving it to another location eliminates narrow-band radio frequency (R.F.) interference without affecting the signal. If moving within 20 ft. doesn't improve the signal, further moving probably won't help.

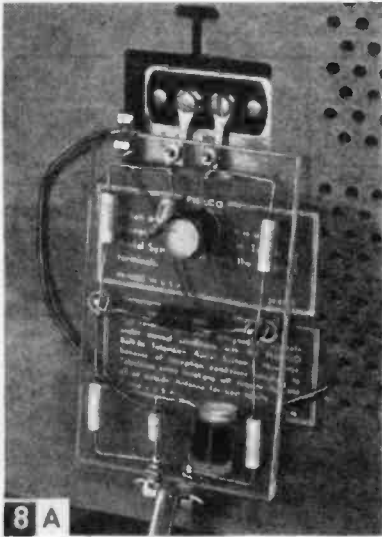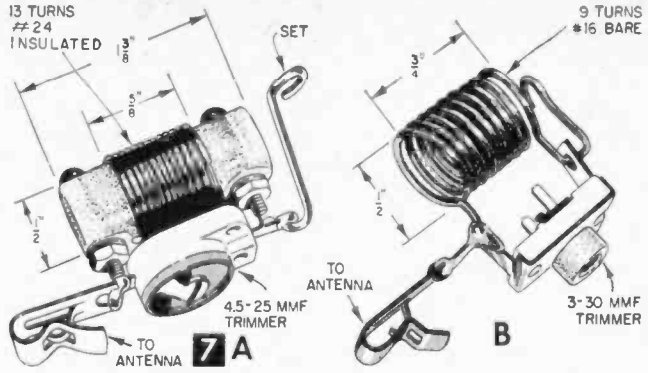Other types of R.F. interference such as FM transmissions, hams or aircraft are eliminated by simple high-pass filters in the antenna leads which allow high frequency TV signals to pass readily but tend to



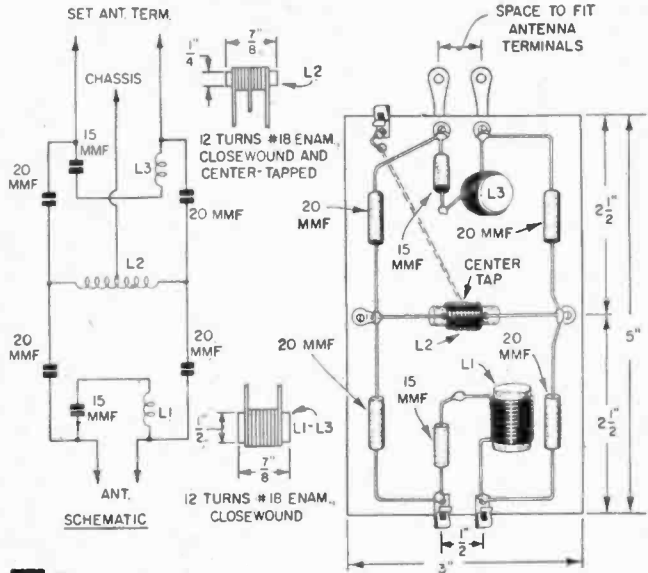Wide band R.F. filter attached to set. Wire from top clip goes to chassis.



WIDE-BAND R.F. FILTER


MATERIALS LIST—TVI FILTERS

Amt.	Description
	A-C Line Filter (Figs. 5 and 6):
2	1/2" dia. x 1 3/8" long coil rods
1	.1 mf. 400 volt condenser
2	.05 mf. 400 volt condenser
1	male chassis plug (Amphenol 61-M)
1	female chassis socket (Amphenol 61-F)
1	blinding post (not insulated)
1	1 3/8 x 3/4 x 2 1/8" aluminum box (Bud CU-2101)
9' (approx.)	#18 enameled wire
	10-32 mc. Antenna Filter (Fig. 7A):
1	1/2" dia. x 1 3/8" long coil rod
1	4.5-25 mmf ceramic trimmer (Centralab 822-AZ)
1	Fahnestock clip
20" (approx.)	#24 Insulated wire
	30-120 mc Antenna Filter (Fig. 7B):
1	3-30 mmf mica trimmer
1	Fahnestock clip
15" (approx.)	#16 bare wire
	Wide-band R.F. Antenna Filter (Figs. 8A and B):
2	1/2" dia. 7/8" long coil rods
1	1/4" dia. 7/8" long coil rod
4	20 mmf ceramic condensers
2	15 mmf ceramic condensers
3	Fahnestock clips
1 pc	3 x 5" plastic
5' (approx.)	#18 enameled wire

block out low frequency signals. If the interfering frequency is known, make a "tuned" filter (Figs. 7A or B) that will cover the signal frequency, connecting one to each antenna terminal at the set in such a way that the coils are at right angles to each other, and adjust the capacitors with an insulated screwdriver for best results. If tightening the capacitor on the filter does not eliminate interference, install the other filter shown in Figs. 7A and B.

If the interfering frequency is unknown, or if several frequencies may be involved, install the wide-band R.F. filter in Fig. 8A and B. While not as efficient for any single frequency as a "tuned" filter, it does weaken all frequencies below the TV frequencies. The filter must be made the size shown so the coils are separated to prevent interaction and are at right angles to each other. While it's best to enclose the unit in a metal case, with the side of the case at least 3/4 in. from any coil, and the case grounded, you can assemble the unit on a piece of plastic as in Fig. 8A.

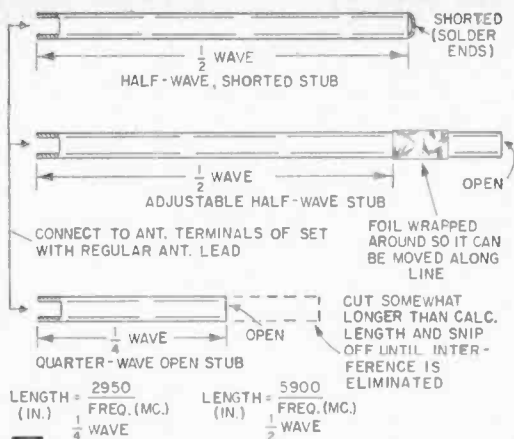If the frequency of the interfering signal is so



9 TRANSMISSION LINE WAVE TRAPS (300-OHM ANT. LEAD-IN)

close to a TV channel frequency that an antenna filter might also filter out the desired signal, connect a simple filter or trap to the antenna terminals of the TV set (with the regular antenna lead). If you know the TVI frequency, make the filter of a section of 300-ohm antenna lead-in cut to exactly $\frac{1}{2}$ the wavelength of that signal as in Fig. 9; solder the free ends of the stub together. If you don't know the TVI frequency, cut the

lead-in somewhat longer than the calculated length (around 30 in.) and tightly wrap a 2-in. section of aluminum foil around the end (Fig. 9) as a short. Move the foil until best results are obtained, then fasten with cellophane tape. Somewhat less efficient is the simply made $\frac{1}{4}$ -wavelength trap. Cut the lead-in longer than needed, fasten in place and snip off sections until the interference disappears.

If the TVI source is so close that even with the antenna lead filtered, wiring within the TV set picks up the signal, shield the set by lining the cabinet with aluminum foil or copper screening and connecting this shield to the chassis. Also connect the chassis to a good ground, provided the set is designed to have a grounded chassis. Where chassis is not grounded, set should be so labeled according to U.L. standards. Speaking of shielding, check all shields, such as those on tubes, within your TV set, as omission or loosely-connected shielding can cause interference on your set or your neighbor's.

Eliminating TVI is often a relatively simple matter, but there is no single remedy. Sometimes in apartments or industrial areas, complete elimination is virtually impossible though some improvement can usually be made by the right combination of antenna orientation, shielding, filtering and wave traps.

Try a Lemon or Tomato Battery

THE principles of dry cell battery operation involve the use of two dissimilar materials such as zinc and carbon, placed in an electrolyte, usually a moist mixture of charcoal or gypsum, zinc chloride and ammonium chloride (or sal ammoniac). The electrolyte acts more strongly on the zinc, slowly consuming it in the process. The zinc is the negative side of the cell and the carbon is usually used for the positive or other material.

Another action that takes place is that hydrogen is released with a load, from the action of the current on the electrolyte. The hydrogen bubbles released tend to collect around the carbon and act as an insulator, thus increasing the cell's internal resistance. This would normally cause a voltage drop were it not for another chemical element that is added, called a depolarizer, which may be powdered carbon and manganese dioxide.

To demonstrate a simple cell and its action, cut a lemon or tomato in half; the half will be the cell container and its juice the electrolyte. Then break up an old flashlight cell to recover the carbon rod and a piece of the outer zinc container (Fig. 2). (Use a cell that is not decomposed to the extent that the zinc is destroyed).


Wash the carbon rod and the zinc container from the battery in hot water. Then cut a $1\frac{1}{2}$ in. wide strip from the zinc container, press the carbon rod in one side of a cut lemon, and the zinc strip in the opposite side.

By connecting the carbon and zinc terminals

to a high resistance voltmeter, we can then obtain about a 1.2 volt reading (Fig. 2) which is pretty good for a lemon! However, switching the meter switch to the 10 mil scale shows us that the current capacity is small, for a maximum of about .5 mils will be recorded. Now, put salt on the lemon; the current will rise.

If you put a light load on the cell, however, it will quickly polarize, since it has no depolarizer, and a second check on the voltmeter scale will show a decided drop in voltage. This will slowly rise again and come back practically to its original value.

How Does It Work?

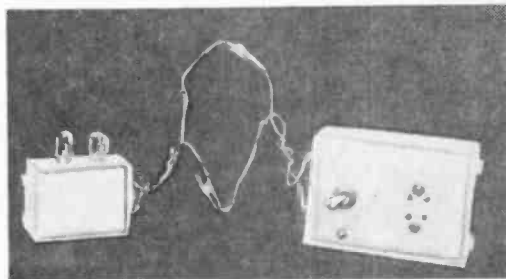

★ Two cases, a pair of wires, one switch, two lamps—Throw switch left and the left lamp turns on; throw switch right and the right lamp turns on, left lamp turns off.

How does it work? The secret is revealed on page 88 together with full details on how to build the unit.

Car Battery Adaptor Operates Portable Transistor Radio

By THOMAS A. BLANCHARD

YOU'LL never have to worry about your portable transistor radio batteries going dead when on a car outing or camping trip if you have this tiny car-battery adaptor tucked away in the glove compartment of your car.

Simply plug the adaptor cord into your car's cigaret lighter or map light socket, attach the cord clips to the radio battery terminals and tune in your favorite program. In this way you save the radio batteries for times when you really need them.


The adaptor will supply power to sets designed for either 6 or 9-volt operation having NPN or PNP transistors. It can be used with 6 or 12-volt car batteries grounded positive or negative to the car chassis.

The plastic box into which the adaptor was




assembled will be familiar to many of you radio experimenters since a leading line of radio hardware items are packed in these $\frac{3}{4} \times 1\frac{3}{8} \times 2\frac{1}{2}$ -in. slide-cover containers. Drill or ream three holes in the side of the box and install three phone tip or banana jacks as in Figs. 1 and 2. Mount a 2-lug tie-strip to the bottom of the box with a 6-32 $\times \frac{1}{4}$ -in. screw for securing the various components. These consist of a 25 ma. instrument fuse with pigtail leads, a 600 and 300 ohm 1-watt resistor and wire components.

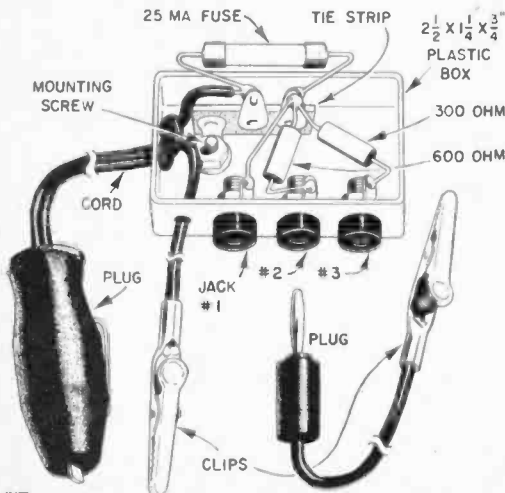To connect the adaptor to the car in the side of the a cord and plug



1 PICTORIAL DIAGRAM

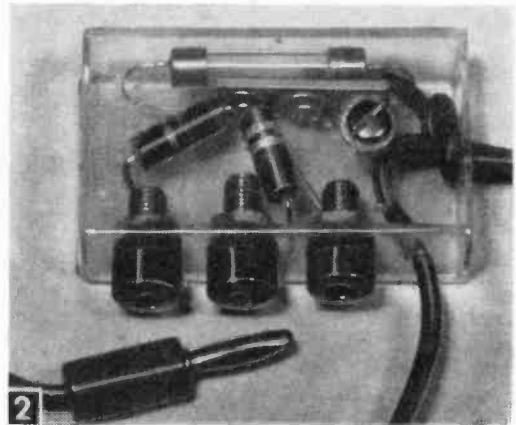

2 Complete adaptor, not including extension wire, fits into $\frac{3}{4} \times 1\frac{3}{8} \times 2\frac{1}{2}$ -in. box and may be stored in car glove compartment.

from an inexpensive trouble light designed to plug into the dash cigaret lighter socket or a suitable length of light fixture cord and fit it with a plug made from the base of a burned-out dash or dome lamp. If you use the latter, break the glass around the lamp base and scrape the base shell clean. Solder the cord leads into the base and fill the base with sealing wax. The wax can be melted by applying a heated soldering iron until wax flows into shell.

In the event that an instrument fuse is not

readily available, get one of the midget fuses your local service station stocks for auto clock circuits. With a little care, pigtail leads can be

soldered to the ends of any regular glass cartridge fuse with a low current rating.


The output leads of the adaptor are fitted with small clips. One clip lead is fitted with either a phone tip or banana type plug for connecting to the desired output jack. Jack #1 should be used for operating either a 6 or 9-volt transistor set from a 6-volt car battery. Jack #2 is used when operating a 6-volt set from a 12-volt car battery. Jack #3 is used for operating a 9-volt set on a 12-volt car battery.

Because of the several variable factors previously mentioned, polarity indications cannot be shown in the wiring plan. To determine which lead is positive, which is negative, attach the adaptor to the dash socket and connect the clip leads into the set. If set fails to work, simply reverse the clips and the radio will play.

However, do not expect to sit in the car and play the radio unless the vehicle has a fabric convertible top. As most experimenters well know, loop radios do not work in hardtop automobiles unless an external antenna is used.


MATERIALS LIST—CAR BATTERY ADAPTOR

No. Req.	Size and Description
1	plastic box $\frac{3}{4}$ x $1\frac{1}{2}$ x $2\frac{1}{2}$ -in. or larger
12 ft	light plastic extension cord
3	phone tip or banana jack
1	phone or banana jack
1	3-lug tie strip
2	small test clips
1	300 ohm, 1-watt composition resistor
1	600 ohm, 1-watt composition resistor
1	25 ma. pigtail instrument fuse
1	plug—see text

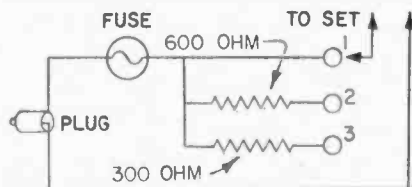

3 SCHEMATIC DIAGRAM

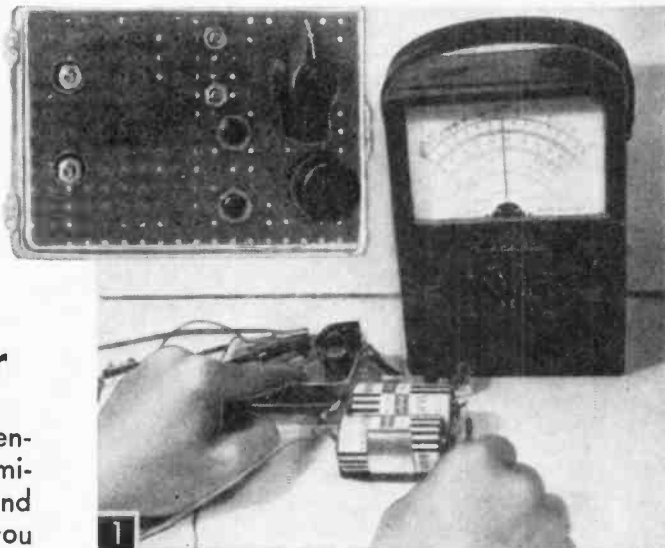Meter amplifier (front panel view shown inset) in use with Heathkit volt-ohm-meter.




Sensitive Direct Current Meter Amplifier

This amplifier increases the sensitivity of a millimeter or microammeter many times! And it can be built from parts you probably have on hand—

By FORREST H. FRANTZ, SR.

TRANSISTORS are basically current amplifiers (in contrast to vacuum tubes which are voltage amplifiers). This characteristic of a transistor makes it a natural as a current amplifier for a meter. With a current amplifier, a low cost milliammeter can be made as sensitive as an expensive microammeter, and microammeters can be made more sensitive. Extremely small currents can be measured; and, if series resistors are employed with the transistor amplifier-meter combination, the result is a sensitive voltmeter which draws very little current from the circuit under measurement. Here is an amplifier unit which can be built from about \$5 worth of parts.

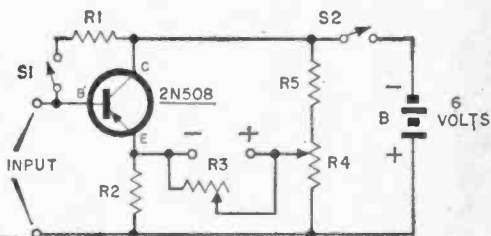

2 SCHEMATIC

Construction. The circuit is shown in Fig. 2. Miniature perforated board layout is shown in Fig. 3. The entire assembly is housed in a plastic case (See Fig. 4).

First, prepare the circuit board. The board on the Materials List is the exact size required, the hole centers coincide with perforations. Drill a $\frac{1}{8}$ -in. hole for each hole position (back the board with a wood block to prevent breakage). The larger holes may be made with a taper reamer or with drills of appropriate size.

Place the finished circuit board against the face of the plastic case for use as a guide in making the case pilot holes. Use a heated ice pick to make pilot center holes, enlarging these to size with a taper reamer. The battery holder holes on the case must be of about $\frac{1}{16}$ in. dia. since the mounting nuts are placed on the front of the circuit board.

Cut the shaft of R3 to a length of $\frac{3}{8}$ in., the shaft of R4 to a length of $\frac{1}{2}$ in. By placing the unwanted end of the shaft in a vise and cutting to desired length with a hacksaw, you do not place any stress on the shaft bushing which could damage the control.

Fasten the battery holder, potentiometers (R3 and R4), switches (S1 and S2), terminals and soldering lugs (plus and minus) on the circuit board. Retaining nuts for all parts (except the battery holder) fasten from the front of the plastic case in the final assembly.

Turn battery holder connection lugs to the side as required to contact adjacent lugs for connecting the cells in series and solder the appropriate lugs together. Then fill the battery contact eyelets on the holder with solder.

Next make connections between the mounted components and wire R1, R2, and R5 into the circuit. (The value of R1 depends on the meter to be used with the amplifier.) Connect the input leads and slip $\frac{1}{4}$ in. lengths of spaghetti on the transistor leads and solder it into the circuit.

Now remove the nuts which retain R3, R4, S1, S2, and the terminals (plus and minus). Place the circuit board in the plastic case and refasten the component retaining nuts on the front side of the case. Fasten the knobs on R3 and R4, and place the penlite cells in the battery.

Operating Principles. The number of times a given base current change appears to be amplified in the collector circuit of a transistor is commonly called the Beta. Another way to say this is: Beta equals change in collector current divided by the change in base current that started the process. The Beta of the 2N508 transistor is better than 100. It would therefore seem that a current of 10 microamperes on the base of this transistor could cause full scale deflection of a 0-1 milliammeter. Actually, however, the Beta of a transistor isn't constant. Generally, meter current amplifiers are operated without a base biasing resistor and the Beta is lower under these conditions than under the test conditions for which a numerical Beta is given. Another factor

DC METER AMPLIFIER

Table A—Sensitivities and Calibration Points for Various Meter-Transistor Combinations

Value of R1 (Megohms)	Meter Range	Meter-Amp Sensitivity (Micro Amperes)	Beta of Transistor	Calibration Point
.58	1 ma.	20 full scale	50 or more	mid-scale
5.8	100 μ a	2 full scale	50 or more	mid-scale
.116	1 ma.	50 full scale	20 or more	full-scale
1.16	100 μ a	5 full scale	20 or more	full-scale
1.16	200 μ a	10 full scale	20 or more	mid-scale

which tends to reduce the amount of useful current amplification the transistor has in a meter amplifier application is the leakage current (I_{co}) which flows although the base is open.


The current in the emitter circuit of a transistor is nearly equal to the collector current. The meter connects into a bridge circuit consisting of the transistor and resistors R2, R4, and R5. R4 functions as a "zero" control. With S2 depressed, R4 is adjusted for zero deflection of the meter. If a current flows through the input leads, the meter deflection is proportional to this current.

The potentiometer R3 which shunts the meter is a scale adjustment; its setting determines the amount the meter will be deflected for a given base input current. It is set in the following manner: First, depress S2 and adjust R4 to zero the meter. Then S1 is depressed (with S2 still depressed) and R3 is adjusted for a predetermined scale meter deflection. This calibrates the meter.

The value of R1 is chosen to provide a calibration current which is equal to the meter current calibration point divided by 50. Thus, for a 1-ma meter, if the predetermined calibration points is to be full-scale reading, the calibration current is 1 ma divided by 50, or 20 microamperes. The voltage difference from base to emitter is approximately 0.2 v. The battery voltage is 6 v. R1 will have a voltage drop of 6 minus 0.2, or 5.8 volts and the current through it is to be 20 microamperes. Its resistance ($R = V/I$) is (5.8/20) Megohms. The computed value is .29 Megohms or 290K. A 270K resistor that is high in value or a 330K resistor that is low in value can be selected from ordinary 10% or 20% tolerance carbon resistors.

An alternate approach is to let the predetermined meter calibration point be mid-scale. The current through R1 should then be 20/2 or 10 microamperes, and $R1 = (5.8/10)$ Megohms = .58 Megohms; 560K is near enough to this value to use. The battery voltage can be expected to be a few tenths of a volt below 6 anyway, so that 560K

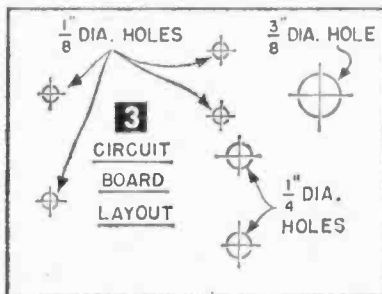should be more correct than the computed value of 580K. Table A shows the value of R1 for various basic meter ranges, the predetermined



meter calibration point and the base current that will cause full-scale meter deflection.

After the meter amplifier has been zeroed (R4) and the scale adjustment (R3) has been made, the amplifier input leads are connected into the circuit in which a measurement is to be made and S2 is depressed. The meter reading divided by 50 is the amplifier input current. The conversion may be performed mentally by multiplying the meter reading by two, taking the proper unit conversion into account.

MATERIALS LIST—DC METER AMPLIFIER


Desig.	Description
R5	470 ohm, 1/2 watt, 10% carbon resistor
R2	2.2K, 1/2 watt, 10% carbon resistor
R1	see text and Table A
R4	100 ohm wirewound potentiometer (Clarostat Series 43-100)
R5	10K dime-size potentiometer (Lafayette VC-34)
T	2N508 transistor (GE)—text gives information for using other transistors
S1, S2	miniature push button switches (Lafayette MS-449)
B	4—1.5 v penlite cells series connected (RCA VS074)
	4-cell Battery Holder (Lafayette MS-170)
	2 7/16 x 3 3/8" miniature perforated bakelite board (Lafayette MS-304)
	1 x 2 5/8 x 3 3/8" plastic case (Lafayette MS-159)
	miniature knob (Lafayette MS-185)
	pointer knob (Lafayette KN-41)

Alternatives. Suppose you want to use a transistor other than the 2N508 which you may have on hand, say a CK722 or a 2N107. They'll work, but their current gains are low and they have appreciable leakage. To use other transistors, use a single 1K pot in place of R4 and R5. The zero adjustment will be more critical since no padding resistor is provided, but you'll be able to zero the meter.

Resistor R1 is computed as described earlier, but the assumptions are different. Assume the input base current to be the meter reading divided by 20. Thus for a 0-1 ma meter, figure 1/20 ma or 50 microamperes of input current for full-scale deflection. Then R1 is (58/50) Megohms or 116K for full-scale deflection (110K is the nearest common value).

If transistors of better quality than the experimenter types are used, current amplification scale factors greater than 20 may be assumed. Even experimenter grade transistors which you might have may have Betas of 50 or more. The reduced values were assumed because Betas vary widely between transistors of a given type. Thus, although some readers may get transistors with low Betas, very few will get transistors with Betas below those assumed for the types covered in this discussion.

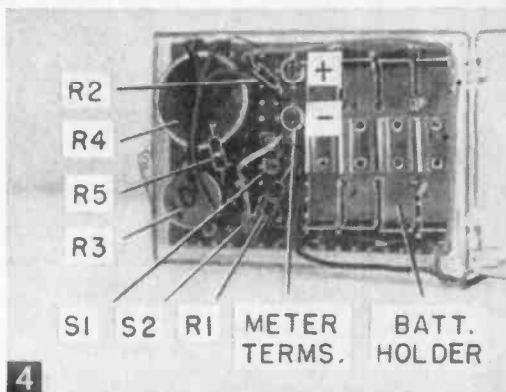The physical construction of the meter amplifier may be varied if you prefer different construction. The amplifier and a basic meter move-



Back view of meter amplifier unit.


ment may be incorporated in a single case, for example. Shunt multipliers may be provided at the amplifier input if several various low current ranges are desired.

Voltmeter. A resistor connected in series with the input lead and the base of the transistor converts the amplifier-meter combination into a high-sensitivity voltmeter. Assume the current sensitivity of the combination is 20 microamperes for full-scale meter deflection (the case for the model described in this article when employed with a 0-1 ma meter), and the meter is to read full-scale when the measured voltage is 50 v. Then the required series resistor is (50/20) Megohms or 2.5 Megohms. The nearest standard values are 2.2 and 2.7 Megohms. However, standard values of 1 and 1.5 Megohms are available. Connect these in series.

Since this voltmeter arrangement only draws 20 microamperes from the circuit under test, it may be used to make measurements in most vacuum tube equipment without upsetting circuits and introducing loading error in measured values.

Nail Clipper Strips Wire

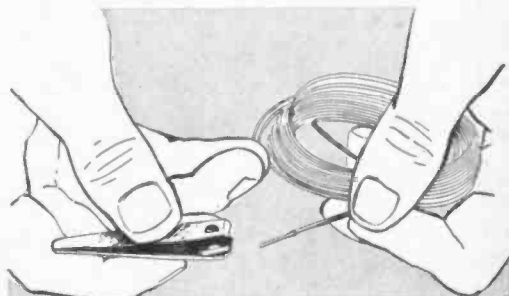- A nail clipper makes an excellent tool for radio and TV hobbyists, to use for removing insulation from small-gage wiring. First, however, remove



the pressure-handle to avoid exerting too much force and cutting right through the wire.—R. J. DECRISTOFORO.

Transistorized Photo-Cell Control

A beam of light can be a handy workman around the home

By THOMAS A. BLANCHARD

WHEN this photoelectric-cell switch is placed so its activating light beam shines across a doorway, hall or porch, a person passing through will break the light beam and cause a door chime to sound, a light to turn on or a burglar alarm to ring.

The switch may be wired across any existing 115-volt switch to control lights, a bell, etc., not exceeding 2 amps., or about 130 watts. It is battery operated and therefore portable and completely independent of the house current which it controls. The entire unit is housed in a $2\frac{1}{8} \times 2\frac{1}{4} \times 2\frac{3}{4}$ -in. radio utility box. All components are mounted on $2\frac{1}{2} \times 2\frac{1}{2}$ -in. perforated plastic panel.

Place the components on the panel and mark and drill holes for mounting the parts as in Fig. 2. Make the battery brackets as in Fig. 3C and bolt them to the panel with 3-48 x $\frac{1}{4}$ -in. screws. Also drill three $\frac{5}{32}$ -in. holes for the 6-32 x 1 in. mounting screws. Make the fiber tube spacers for the mounting screws the same length that the photocell projects through the perforated panel. Transfer the location of these holes and holes for potentiometer and photocell to the front of the box and drill.


The cadmium sulphide photocell is a Clairex CL-2 which is about the size of a small composition resistor. This tiny unit has the general characteristics of a vacuum tube photocell. It is a photo-conductive device like the phototube. It has the unique property of having a very high resistance in darkness, but as it is exposed to light the resistance drops from the megohm range to 10,000 ohms in bright light.


To actuate the control, only a small light change is required so that sufficient current passes

Front and rear views of panel showing placement of parts.




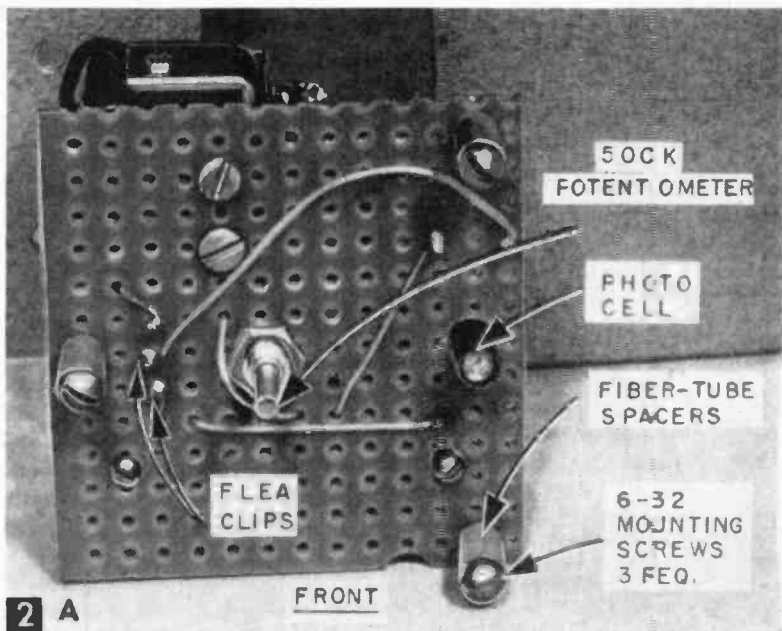Tiny self-contained photoelectronic control being test-actuated at close range with flashlight. Unit is sensitive enough to respond to feeble daylight at surprisingly long distances.



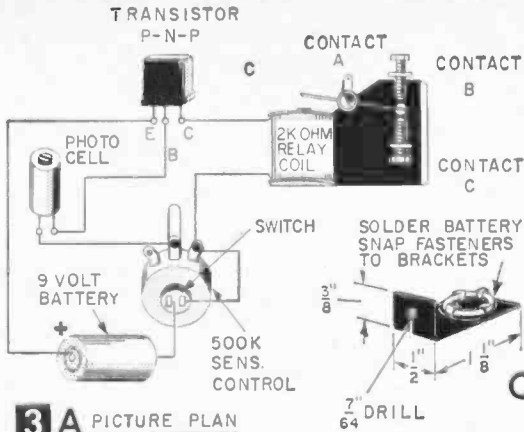

3 A PICTURE PLAN

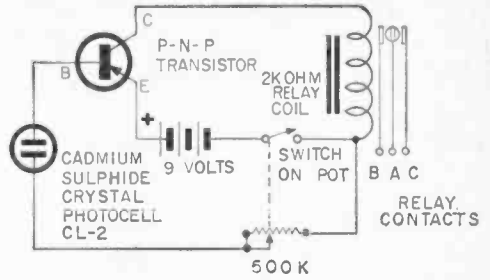

BATTERY BRACKETS
2 REQ. 1/16 BRASS

B SCHEMATIC PLAN

MATERIALS LIST—PHOTOCELL SWITCH

No. Req.	Size and Description
1	2 1/8 x 2 1/2 x 2 3/4" aluminum radio utility box
1	Sigma sensitive relay type 4F with 200 ohm coil
1	Clairex photocell type CL-2
1	2 1/2 x 2 1/2" perforated phenolic (Bakelite) (Lafayette)
1	500K miniature potentiometer with switch
1	P-N-P transistor (type 2N107, 2N34, CK722, etc.)
5	Lafayette "flea clips"
1	1/16 x 1/2 x 3" brass for battery clips
1	9v transistor battery
3	3/16 I.D. x 3" long fiber tube for mounting screw spacers
3	6-32 x 1" rh machine screws for mounting panel
2	3-48 x 1/4" rh machine screws for battery clips
	Hookup wire and misc. hardware

through it to provide a base return negative voltage to the transistor, thus causing a large flow of current through transistor to the relay coil. The cadmium cell should not be confused with the short-lived selenium cell which is a

photovoltaic device.


Connect the leads from the photocell and transistor to flea clips and insert them through the holes in the perforated panel. Solder hookup wire to the flea clips on the other side of the panel as in Figs. 2 and 3.

The use of a sensitive plate relay is most important. Fixed relays are set up at the factory with predetermined pick-up and drop-out relay contact specifications. Altering these adjustments is difficult and sometimes impossible. The relay employed is the fully adjustable Sigma 4F with a variable hairspring armature adjustment and screw gapped contacts. The coil resistance of the unit is 2000 ohms.

In this application we adjusted armature tension and contacts so that relay picked up at 700 microamps and dropped out at 500 uA. The relay coil with photo cell in darkness draws just 200 uA and only 1.6 milliamps in brightest light.

While the life of conventional transistor batteries is limited, those desiring a battery good for 10,000 hours of service may employ the rechargeable nickel-cadmium cells now on the market. Many of these batteries are designed expressly for transistor service and will fit nicely into limited space.

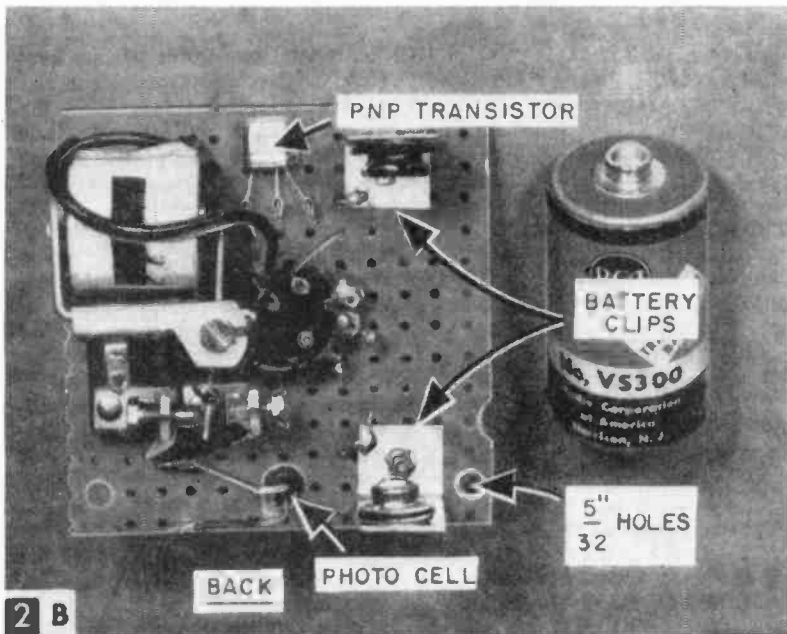Sensitivity of the photo control can be regulated by adjusting the miniature 500,000 ohm linear potentiometer which is wired in series with the photo control so that the desired pick-up and drop-out of relay switch contacts may be adjusted to meet existing light conditions.



2 B

What To Listen For On Short Wave, Spring and Summer, 1960

By C. M. STANBURY II




QSL (verification card) from Radiodifusion Argentina al Exterior. Note that on globe map Argentina includes the Falkland Islands (held by the British) and a large portion of Antarctica. RAE covers South American news from a different point of view. For details on this and other easily received SW broadcasts see Table B.

An international broadcast is worth the expense only if you—the listener—can receive it and—for one reason or another—also enjoy the program. (Admittedly, your interests as a short-wave listener and the interests of a SW broadcaster may not always coincide.) Let's look into the factors that affect reception and then analyze the programs themselves to discover which make for enjoyable listening.

Shortwave signals are weak compared to local broadcasting but this is unimportant, as there is little static on the shortwaves. The serious problems for the broadcaster are finding a clear wavelength, since scores of countries are broadcasting, and choosing a wave length that will be reflected by the ionosphere, a region of ionized air 60 and more miles above the earth upon which all short-wave broadcasting depends. The broadcaster must choose a wave-length which is short enough to escape absorption characteristic of lower frequencies and yet not too short for reflection via the ionosphere. If he's going to stick within the internationally authorized shortwave bands (see Table A), this summer he will be limited to a

TABLE A—
BEST SHORTWAVE BANDS,
SPRING AND SUMMER, 1960

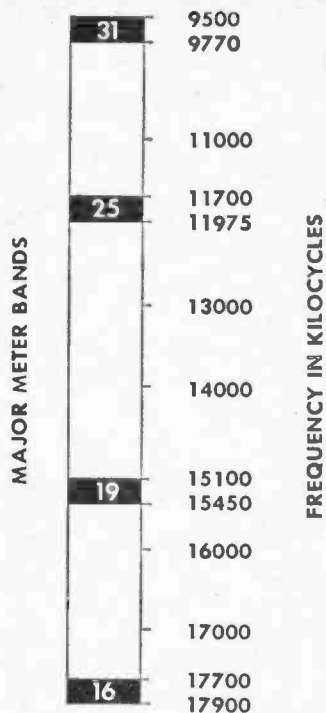

*To convert to megacycles, divide by 1000

total of 1100 kc, a total two-thirds of that covered by the standard broadcast band. The National Bureau of Standards estimates that the average shortwave listener will tolerate four times as much interference as he will on the broadcast band. This compromise is a matter of necessity.

During the summer, every summer, absorption of radio waves by the ionosphere increases, while in the top layer of the ionosphere ionization decreases. This means that the longer 49 and 40 meter waves will not escape absorption (only the Communists use the latter for North America anyway) and therefore will be unsuitable for consistent transoceanic broadcasting, and due to decreased ionization in the top layer of the ionosphere, 13 meters at the top end of the dial will be reflected only sporadically. Which leaves 16, 19, 25 and 31 meters—and of these the 16-meter band is on the doubtful side. During the past few summers 16 meters has been "Open" (reflected) but with a dropping sunspot count (sunspots increase reflection); international broadcasters will be able to count on this one less and less.

Taking it by regions, daytime European signals will be received best on 19 meters with some on 16 meters, especially in the afternoon. Then evenings these signals will be heard on 25 and 31 meters with 19 also open several hours past sunset. Similar conditions hold for Africa except you probably won't hear any on 19 while dark. Asiatics will first appear around sunset or shortly before on 16 and 19 meters and because it is a peak listening period, such stations having North American broadcasts will transmit them during this period. However during the early *am* hours of darkness many Asiatic signals should be audible from 19 thru 31 meters. Pacific islands will also be heard during the *am* hours on 19, 25 and 31 meters.

Latin American stations, with the exception of

Argentina and Chile, can be received much more easily; they will be received in the summertime all the way down to 6 megacycles (49 meters) and—when static permits—even lower.

The Human Element. As international broadcasting is directed by human beings, for human motives, it is of course far from perfect. And as in any other of man's endeavors, these services range from good, such as the quality program put out by the Swiss Broadcasting Corporation, to the absolute lowest as epitomized by Radio Peking. However there is always one constructive way to judge any shortwave station. Does it provide something worthwhile not readily obtainable elsewhere?

In this connection there are two common practices which, in varying degrees, lessen short-

TABLE B—STATIONS TO START WITH

COUNTRY	FREQUENCY OR WAVE-LENGTH	TIME* (EASTERN STANDARD)	BROADCASTER AND DETAILS
SWITZERLAND	11865 and 9535 Kc/s	2030-2215 and 2315-2400	Swiss Broadcasting Corporation. Swiss news (neutrality and more neutrality), commentary from Swiss newspapers (not so neutral). Good source of factual information about this, one of the world's first republics. You might say it was pro-Swiss but then the Voice of America is pro-U. S. and you really wouldn't want anything else. An interesting little touch with S.B.C.: on each broadcast they give the weather for Switzerland. Finally of note are special international features such as rates of exchange for world's currencies.
NETHERLANDS	15220 Kc/s (16 meters) 11730 and 9590 (9715†)	1615-1705 2130-2210	Radio Nederland. International news from a democratic West European viewpoint. Usually concludes program with a topical talk. These probably reflect quite accurately the general Dutch viewpoint.
SPAIN	9363 Kc/s	2215-2250, 2315-2350 and 0015-0050	The Voice of Spain. This one operates off regular broadcast frequencies to avoid interference. Features a reasonable quantity of Spanish folk and popular music. Too bad the entire program doesn't consist of same.
ISRAEL	9009 (11845) Kc/s	1530-1600	The Voice of Zion. Another off-band operation and that time is a little early for 31M but with a clear channel it should get through. Interesting source of Israeli news from a Zionist point of view. Also Israeli folk and popular music, but not enough.
CONGO REPUBLIC	11725 Kc/s	2015-2100	Radio Brazzaville (French government radio). African news from, primarily, a French point of view. Certainly better than none at all.
JAPAN	17855 and 15325 Kc/s	1930-2030	Radio Japan. News from Asia's leading democracy. Some Japanese folk and popular music; as usual, not enough.
ARGENTINA	9690 (15345) Kc/s	2200-2300 and 2400-0100	Radiodifusion Argentina al Exterior. South American news from a different if not unbiased point of view. Rest of program consists of Argentine popular music, more polished than most Latin American music and probably less interesting. Compare with the Voice of Spain.
GREAT BRITAIN	16 thru 31 meters	1600-2200	General Overseas Service, British Broadcasting Corporation. This is general programming intended for the entire English speaking world and not any one specific area. Time given is best for North America, but G.O.S. can usually be heard throughout the day on many frequencies. The G.O.S. is an excellent example of British programming and conservative English thought. Covers international affairs, theatre, literature and music. Also international sports but the latter would be of little interest to the average American.
AUSTRALIA	11810 Kc/s	0714-0845 and 1014-1145	Radio Australia. Australian news—the continent has an area of almost 3,000,000 square miles, remember. Remainder of program is mostly entertainment. These broadcasts have twice been voted most popular by the world's short-wave listeners.
CANADA	15195 (11900 or another 25 meter frequency)	2000-2045	Radio Canada. Good source of international and Canadian news. Because of the nation's proximity, the latter is of special interest to U. S. citizens.

* Time is given on the 24-hour clock. 1200 is 12 noon, 1300 is 1 pm, 2400 is midnight, and so on. In other words, for times past noon subtract 1200 to get Eastern Standard Time.

† Frequencies listed in brackets are alternate possibilities. If you fail to hear a program on the channels listed first, try these.

wave's usefulness. First, many stations play classical music. Of course if the transmission is intended for an area where shortwave is the only kind of broadcasting, such a feature is certainly justified. But when beamed to North America, it is a waste of time and frequency. As explained, shortwave is anything but a hi-fi media and the classical music fan would do far better on FM, or in some areas, even on the standard broadcast band.

Second, most SW broadcasters when attempt-

ing to give a view of their country, tend to over-emphasize institutions and material things, passing by the real human values. While this is a fault common to most governmental undertakings, it is quite understandable here as these values are quite intangible and obviously difficult to put into words.

I have listed in Table B ten broadcasts which I think you'll find interesting. The chart tells which have been picked for all-round excellence and which for only one or two special features.

Easy Transistor Class Identification

• It's almost impossible to determine whether a transistor is of the NPN or PNP variety just by looking at it in a circuit. However, an easy clue to identification lies in the fact that the middle letter of the transistor class designation indicates which terminal of the battery is connected to the collector element. Thus, in the case of the PNP type, the *negative* terminal of the battery is connected to the collector; similarly, the *positive* terminal of a battery is connected to the collector element of a transistor of the NPN variety. Either by checking the polarity of the potential on the collector element, or by tracing out wires to the battery, it is a relatively simple matter to determine correctly the class of a given transistor.—JOHN A. COMSTOCK.

Wire Scraper from Old Blade

• An old piece of hacksaw blade can be used for cleaning wires when soldering. It will not cut the strands as will a knife.—FRANK A. JAVOR.



Transistors Wired in Tandem

• When building direct-coupled amplifiers using transistors, wiring can be simplified and space saved by connecting matched pairs of transistors together. Cement or tape the two transistors together back-to-back, and solder the emitter lead of one unit to the base lead of the other.



Art Huba

"This circuit has a response of 20-20,000 cps—practically no harmonic distortion up to 25 watts . . ."

memorize morse in 20 minutes!

By Dr. BRUNO FURST

THE International Morse Code is a language of sound used for radio-telegraphy communication. In it, short and long pulses of sound (*dits* and *dahs*) are combined to indicate the 26 letters of the alphabet, the 10 numerals, punctuation marks, and other information. Table A gives the phonic sounds of International Morse as well as the written designations of the pulses, a dot for a short pulse (*dit*), a dash for a long pulse (*dah*). Except when it is the final syllable of a character, a dit is contracted to di, the t becoming lost in the d of the following syllable.

A brief depression of the telegraph key sends a dot signal; a depression three times as long, a dash. Between signals forming the same letter, there is a pause equal to one dot; the pause between two letters within a word is equal to three dots (a dash); the pause between two words is equal to seven dots.

If the letter *a* were represented by one dot, *b* by two dots and so, no help in memorizing the code would be necessary. However, the distribution of dots and dashes is completely irregular (except that the most commonly used characters have the simplest signal combinations) and help is necessary. There is no uniformity in sequence. There is no pattern. Taken all in all, the code presents a confusing picture, difficult to memorize. Here then is a method which has been tested over and over again that enables everybody (even those without previous experience) to learn the International Morse Code in 15 to 20 minutes.

Since the code consists of dots and dashes, the dots are replaced by vowels (a-e-i-o-u-y), the dashes by consonants. For each letter of the alphabet, a specific word which begins with the letter that it stands for is substituted. For example, the cue word *Air* is substituted for the letter *a*. The cue words (or cue word combinations) at right above represent the entire alphabet:

A ir	J ust now	S uzie
B ruise	K odak	T ot
C hina	L ydia	U sual
D ray	M onk	V isual:
E sso	N ote	With
F lery	O n top	X-rays
G lobe	P arty	Y okels
H is essay	Q-Club	Z ombie
I ssue	R eno	

In order to make easier the task of remembering which word belongs to which letter, memorize this five-sentence story (in it, the cues are used in consecutive order):

"A shell burst in the *Air*, causing a *Bruise* to a soldier in *China*, who was riding in a *Dray*.

"The soldier, Private *Esso*, wrote about the *Fiery Globe*. His *Essay* is an *Issue Just Now*.

"With his *Kodak* he took pictures of *Lydia* and a *Monk* writing a *Note On Top* of a hill.

"Then he went to a *Party* at the *Q-Club* in *Reno*, taking *Suzie* and her *Tot* along as *Usual*.

"At the club, *Visual With X-rays* were *Yokels* drinking a *Zombie*."

Because of its very oddity, this story—read once or twice—is easy to remember. So also, because of it, are the cue words, since they appear in it in alphabetical order; each cue word acts as an association for the succeeding cue word. Thus each brings the next to mind. (But if you learn the signals mechanically, by rote, and forget one, there is no way in which to recall it.)

Having learned the cue words, apply the following rules: The first letter of each word is used only to indicate the letter of the alphabet being coded. (If the first letter of each word were included in the decoding, many exceptions would be necessary because the Morse Code signs for several consonants start with a dot—F, H, R, etc.—whereas the vowel O starts with a dash.) For the succeeding letters, substitute a dot for each vowel, a dash for each consonant (for example A ir · — or C hina — · — ·).

Because there are no words in the English language consisting *only* of four vowels (as

for an amateur license you must demonstrate ability to send and receive the morse code. here's how you can learn the code - quickly

TABLE A—INTERNATIONAL MORSE CODE

LETTER	SIGNALS	PHONIC SOUND
A	· —	di DAH
B	— · · ·	DAH di di dit
C	— · · · ·	DAH di DAH dit
D	— · · ·	DAH di dit
E	· · · ·	dit
F	· · — ·	di di DAH dit
G	— — ·	DAH DAH dit
H	· · · · ·	di di di dit
I	· ·	di dit
J	· · — —	di DAH DAH DAH
K	— — · ·	DAH di DAH
L	· · · · ·	di DAH di dit
M	— —	DAH DAH
N	— ·	DAH dit
O	— — — —	DAH DAH DAH
P	· · — · ·	di DAH DAH dit
Q	— — · —	DAH DAH di DAH
R	· · · ·	di DAH dit
S	· · ·	di di dit
T	—	DAH
U	· · —	di di DAH
V	· · · —	di di di DAH
W	· — —	di DAH DAH
X	— · · —	DAH di di DAH
Y	— · — —	DAH di DAH DAH
Z	— — · ·	DAH DAH di dit

NUMBER	SIGNALS	PHONIC SOUND
1	· — — — —	di DAH DAH DAH DAH
2	· · — — —	di di DAH DAH DAH
3	· · · — —	di di di DAH DAH
4	· · · · —	di di di di DAH
5	· · · · ·	di di di di dit
6	— · · · ·	DAH di di di dit
7	— · · · · ·	DAH DAH di di dit
8	— — · · ·	DAH DAH DAH di dit
9	— — — · ·	DAH DAH DAH DAH dit
0	— — — — —	DAH DAH DAH DAH DAH

PUNCTUATION MARKS & SIGNS	SIGNALS	PHONIC SOUND
PERIOD	· · · · · —	di DAH di DAH di DAH
COMMA	— · · · · —	DAH DAH di di DAH DAH
QUESTION MARK	· · — · · ·	di di DAH DAH di dit
ERROR	· · · · · ·	di di di di di di dit
DOUBLE DASH	— · · ·	DAH di di di DAH
WAIT	· · · ·	di DAH di di dit
END OF MESSAGE	· · · · ·	di DAH di DAH dit
INVITATION TO TRANSMIT	— — —	DAH di DAH
END OF WORK	· · · · · —	di di di DAH di DAH
FRACTION BAR	— · · · ·	DAH di di DAH dit
EXCLAMATION	— · · · · —	DAH DAH di di DAH DAH
COLON	— — · · · ·	DAH DAH DAH di di dit

the author

Dr. Bruno Furst teaches the art of improving the efficiency of memory. He is director of the School of Memory and Concentration in New York City (the school was 20 years old last fall), professor of law at McGeorge College and instructor at Brooklyn College, Adult Education. His system of memory training has been introduced by many business firms, at the U.S. Army Intelligence School in Washington, and at many Army and Air Force installations.

Aside from his resident classes in New York and other cities in the United States, South America, Africa and Australia, he conducts a correspondence course as well as a self-study course. Readers interested in further developing their memory and powers of concentration can write to Dr. Furst in care of the School of Memory and Concentration at 365 West End Avenue, NYC 24.

Remember this exception by thinking of S.O.S. For example, H is essay and R eno — .

The s in His is ignored because it is not at the end of the cue word combination. The o in Reno has a dot substituted for it because it is at the end of the cue word.

The entire alphabet is thus transposed as follows:

ir	ota
A · —	N — ·
ruise	n top
B — · · ·	O — — —
hina	arty
C — · · · ·	P · — — ·
ray	Club
D — · ·	Q — — · —
sso	eno
E ·	R — · ·
lery	usie
F · · · ·	S · · ·
lobe	ot
G — — ·	T —
is essay	sual
H · · · ·	U · · —
ssue	isual
I · ·	V · · · —
ust now	ith
J — — — —	W — — —
odak	rays
K — — —	X — · · —
ydia	okels
L · · · ·	Y — — · —
onk	ombie
M — —	Z — — · ·

needed for H) or of three consonants (as needed for O), one exception is necessary: For the letters s and o a dot or dash is substituted only when they appear at the end of a cue word or cue word combination. In all other positions they are disregarded.

For learning numbers in the International Morse Code, no memory help is needed. The signs follow a uniform, progressive pattern (see Table A). The numbers from 1 to 5 start with from 1 to 5 dots; the numbers from 6 to 0 start with from 1 to 5 dashes. All are supplemented by the opposite symbol to a total of five.

Besides the International (Continental) Morse Code, there is an American Code which deviates in several instances from the International Code (see Table B). Considerable auditory skill is needed to read this code because of the irregular spacing used within certain letters (irregular in comparison to International Morse spacing). It is therefore rarely used in radio applications. To apply my method to the American Code, simply change some of the cue words and construct a story of your own. With understanding of the method that I suggest, these changes are easily done, and a story that you construct is even easier for you to remember than a story that I or someone else constructs for you.

Of course, knowing the signals will not make you immediately proficient in sending and receiving the Code. Proficiency requires practice. Your ear must grow accustomed to the sound of the Code. But the highest hurdle—the memorization of the Morse Code signals—need not take you more than 20 minutes.

Almost everything that we have to learn and to remember in school, in college and in later life can be made easier and retained longer by using more efficient methods. Whenever you face something new that must be

TABLE B—AMERICAN MORSE CODE

LETTER	SIGNALS	LETTER	SIGNALS	NUMBER	SIGNALS
A	· —	N	— ·	1	· — — ·
B	— · · ·	O	· ·	2	· · — ·
C	· · ·	P	· · · ·	3	· · — ·
D	— · ·	Q	· · — ·	4	· · · —
E	·	R	· · ·	5	— — —
F	· — ·	S	· · ·	6	· · · · ·
G	— — ·	T	—	7	— — — ·
H	· · · ·	U	· · —	8	— · · · ·
I	· ·	V	· · · —	9	— · · —
J	— · · · ·	W	· — —	0	—
K	— · —	X	· — · ·		
L	—	Y	· · · ·		
M	— —	Z	· · · ·		


learned, do not plunge immediately into parrot-like memorization. Give some thought to the question: Can I find a short-cut which simplifies the task and makes learning and remembering more interesting and more exciting? Invariably the answer is yes.



"I don't remember whether I made that change or not, but I do remember making a mental note to do it."

Lifesaver for Components

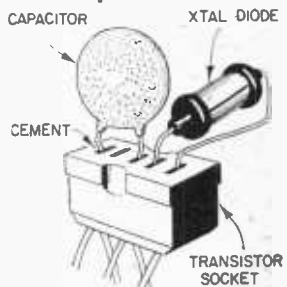● Building a compact transistor circuit? You can save heat-sensitive component parts from being ruined by using transistor sockets not only for transistors, but also for ceramic capacitors, crystal diodes and other parts easily damaged by too much heat from a soldering iron. Just insert the leads into the socket, then add a touch of service cement to the lead where it enters the socket.




Hi-Fi Speaker Improvement

● Where two separate speakers are used in a hi-fi system to reproduce the high and the low frequencies, apply one or two coats of lacquer to the cone of the larger speaker. This will stiffen the cone and improve its response to the lower frequencies.—JOHN A. COMSTOCK.

File Used as Reamer

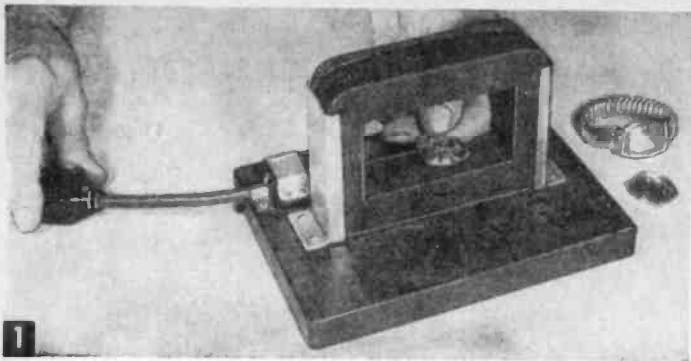● When a rat-tail file breaks, don't throw it away—break it up into a number of 2-in. lengths and use them in your power drill to enlarge radio chassis holes. They cut very rapidly and are ideal for enlarging tube socket holes and for similar radio work.—J. A. C.



Demagnetizer for Watches and Small Tools

By HAROLD P. STRAND

THE next time your watch starts to lose time or stops because it is magnetized, you can save yourself a trip to the jeweler's by using this demagnetizer (Fig. 1). With the 115 volt 60 cycle power turned *On*, the alternating current field, created by passage of current through the wound coil, quickly knocks out all magnetism by simply passing the watch movement through the coil opening. Small screw drivers or punches may also be demagnetized with this device.

The hairspring of the balance wheel of a watch has a tendency to accumulate a permanent magnetism, since it is tempered spring steel. This may happen for no apparent reason, or it may occur while you are wearing the watch around electrical equipment, especially where direct current is used. Magnetized turns of the hair spring will stick together or result in an erratic action of the watch movement.




Remember, when using this device, to turn on the power *before* placing the piece in the opening and turn off the power *after* its removal. Otherwise, the sudden switching off of the power while the watch or tool is in place, may result in increasing rather than removing magnetism.


The demagnetizer consists of a rectangular coil, a base board, line cord and switch. To wind the coil, first make up a wooden form which is a permanent part of the unit (Fig. 2). The coil may be wound on a lathe at slow speed, or on a winding machine equipped with a turn counter, but you can handwind the coil by carefully counting the turns. Press a block into the opening of the form, and use a $\frac{1}{4}$ -20 machine screw, nut and washer in a bored hole in the block to provide a stud that can be held in the chuck for turning (see Fig. 4). Solder a flexible #20 lead wire to both start and finish ends of the coil, and bring

out for connection with the line and the switch.

The resulting coil, when energized with 115-volt alternating current, will have sufficient resistance and inductance so that only a small current will flow. If a small tool is placed in the coil opening, a light pull and vibration will be felt from the effects of the magnetic field produced. Since the current in the coil is reversing constantly through 60 cycles or 120 alternations a second, the magnetic field also is in a constant state of reverse, and this causes a complete elimination of the original magnetic polarity in the piece or neutralizes it to zero.

Fig. 3 shows the start of

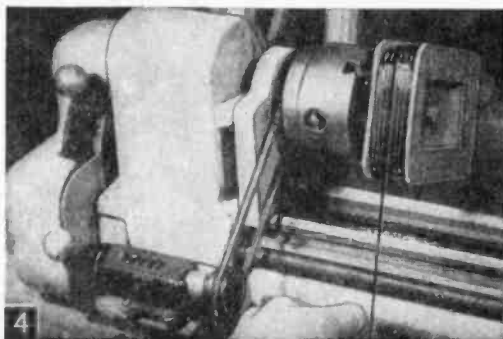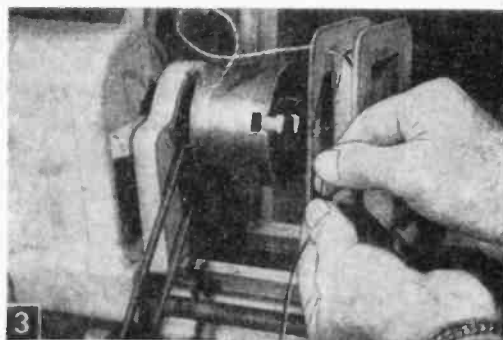
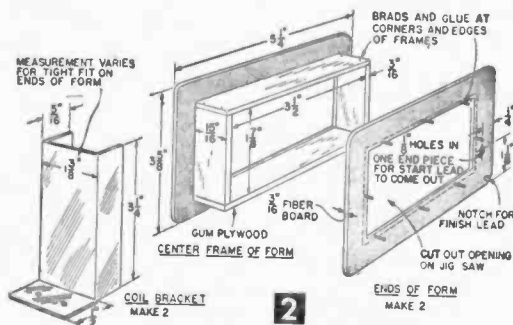


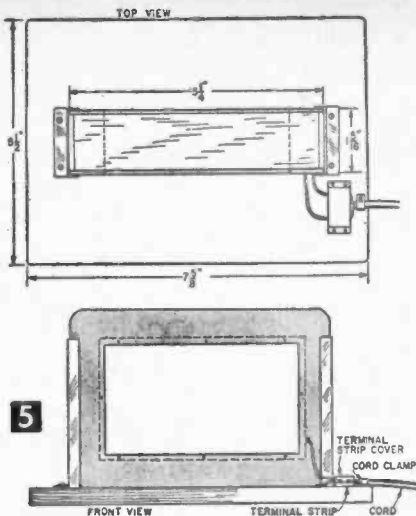

winding the coil in a small lathe, with the flexible lead wire passed through a small hole in the form and soldered to the starting end of the magnet wire. A short piece of plastic tubing will be slipped over the splice to insulate it. A turn counter has been fixed up on this lathe bed, with a rubber vacuum cleaner belt to drive it. Wind 2500 to 2800 turns (Fig. 4) and then solder on the other flexible lead to the finish end. Wrap a turn of electrical or adhesive tape around the winding to bind it in place and then remove the form from the chuck and tap out the block.


Make the base of the demagnetizer from a piece of maple or birch and sand smooth (Fig. 5). The coil is held in position by two side brackets (Fig. 2) which can be made from any soft aluminum or brass sheet stock about 1/32 in. thick. Their width should be such as to tightly grip the sides of the coil form. Use two small round head screws to secure them to the base (Fig. 6).

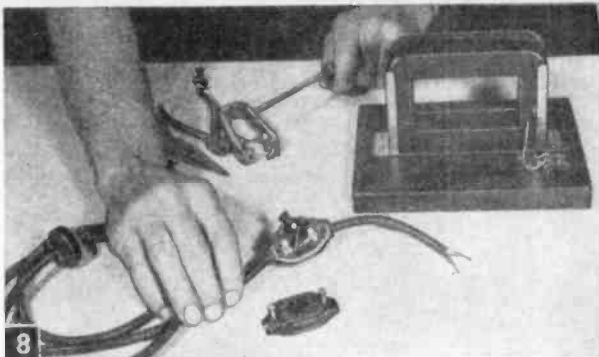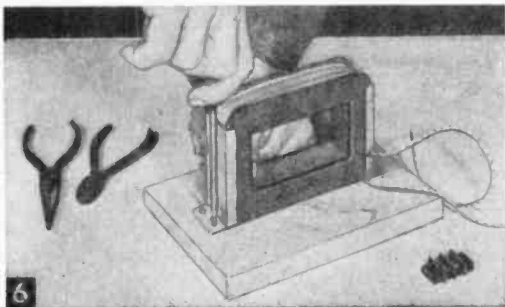The next step is to install a cord switch about 4 in. from one end of a 6 ft. length of rubber line cord (Fig. 8). Connect a regular attachment



MATERIALS LIST—DEMAGNETIZER


Amt. Req'd.	Description	Use
1 pc.	maple or birch 7 7/8 x 5 1/2 x 3/4"	base
1 pc.	3/16" birch or gum plywood, 12 x 15 1/16"	inner frame for coil
1 pc.	3/16" Masonite fiber board, 8 x 6"	sides of coil form
1 pc.	1/32" soft aluminum or brass, 8 x 2"	bracket supports
1 pc.	1/32" soft aluminum or brass, 2 1/2 x 1 1/16"	cover over terminal strip
1	Jones terminal strip, #140, 2 terminal	
1	cord-type toggle switch	
6 ft.	rubber vacuum cleaner cord	
1	attachment plug cap	
1 pc.	sheet brass, 1 x 9/8 x 1/32 thick (bend up to make cord clamp)	
1 lb.	#30 or #29 Formex magnet wire	
	brads, glue, stain, shellac	
4	3/4" #4 rh brass wood screws	
4	1/2" #3 rh brass wood screws	
1	1/2" #5 rh brass wood screw	
2 pcs.	#20 flexible insulated lead wire, 6" long	

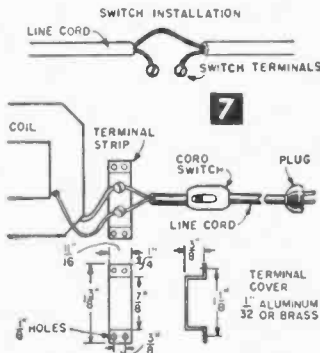

plug cap to the other end. Connect cord to the terminal screws of the terminal strip and make a small clamp to hold cord securely. Place a small cover piece over the live terminals of the terminal strip as protection against accidental shock, screwing through holes in the cover and also down through holes in the terminal strip, to hold the assembly to the base, taking care to

avoid contact between cover and live terminals. Finish the wood base and the coil unit as desired. A coat of mahogany stain was used in the original, and two thin coats of shellac were then applied as final finish. Sand lightly with 6/0 garnet paper and apply one coat of satin varnish which will complete this project.

Dam for Soldering Lug


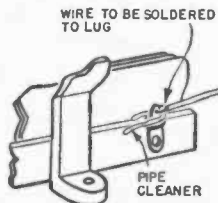


• For a neater job of soldering a wire or cable to a lug, build a dam around it with a pipe cleaner as shown. This idea is particularly good for automotive or radio jobs, where precision is necessary.—V. H. LAMOY.

High-Voltage Traveling Arc

Favorite laboratory background for the movies' "mad scientist" is the Jacob's Ladder or traveling arc. Make your own for about \$25

By HAROLD P. STRAND

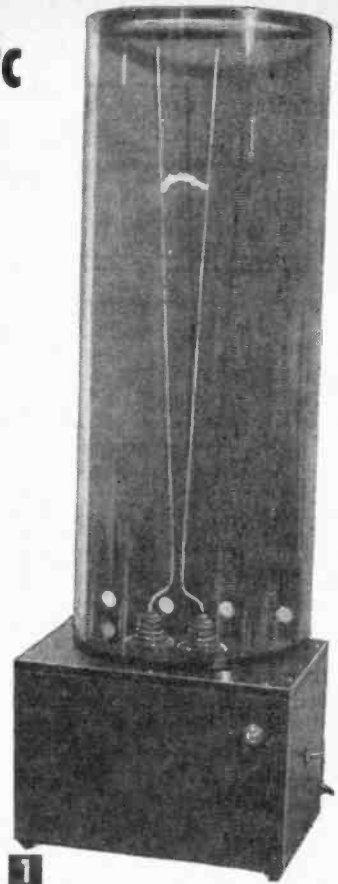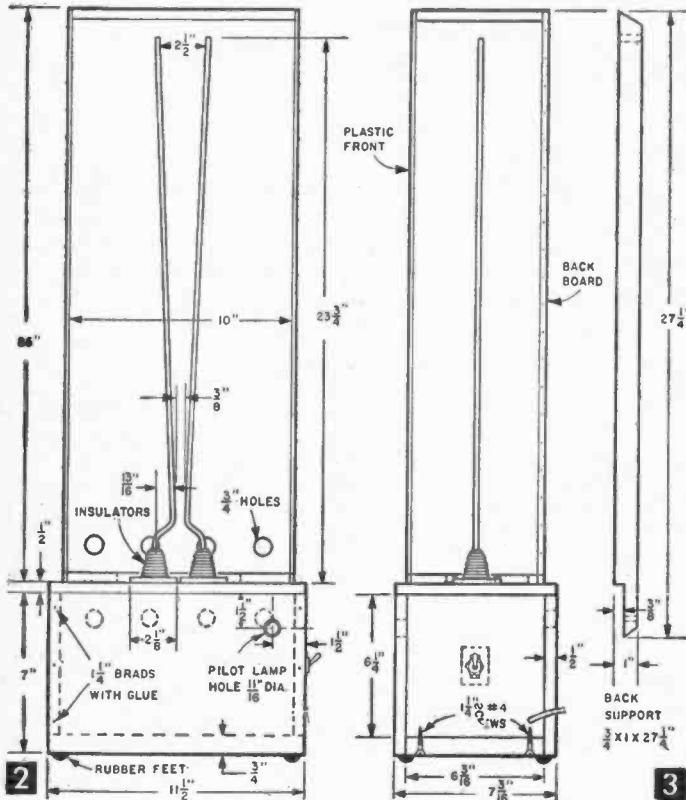

A continuous series of flaming arcs will move up the electrodes of this device, which is similar to one shown at the Boston Museum of Science.


What causes the flaming arc to rise? You might expect the spark to remain at the bottom, where the spacing of the wires is shortest. The explanation is that the air is heated in the

vicinity of the arc and, as heated air naturally rises, it pulls the arc up with it. As a 15,000 volt transformer is used in the base, an arc of considerable intensity results and you need the protection against accidental contact that is provided by the enclosure.


You can amuse yourself and your friends with this high-voltage traveling arc, and it makes a good electrical display at shows and exhibits to attract attention to a particular booth. The transformer, from an obsolete Timken oil burner, was purchased secondhand from an oil burner service shop for \$15. Be sure to have the transformer tested before purchasing, which can be done by arranging two well-insulated wires from the secondary terminals to form a gap for the arc

REMEMBER when you saw a movie scientist working in his laboratory with the powerful crackle of an electrical arc slowly moving upward between two V-shaped rods in the background? These "Jacob's Ladders" pack a lot of drama into usually dull laboratory equipment and are sure-fire attention getters. You can build your own for experimenting and display—like the one in Fig. 1. As you switch it On, a heavy flaming arc jumps between the wires at the short gap above the insulators. Immediately it starts rising to the top getting longer as the distance between rods increases until it dies out near the top. As soon as one arc is extinguished, another one starts. The process is continuous as long as you keep the switch closed.

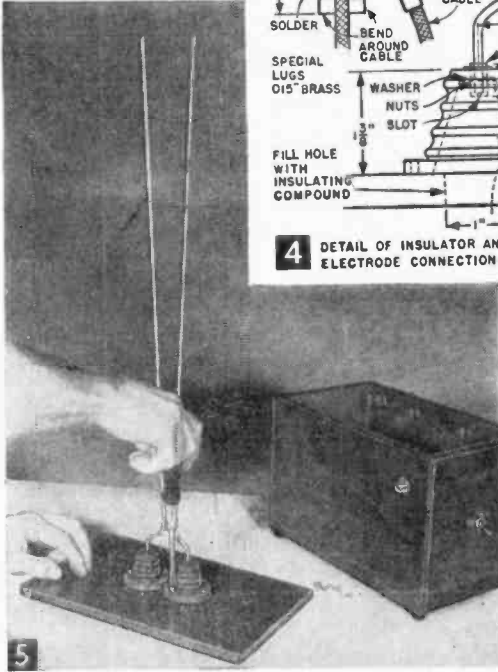Attach the porcelain insulators to the stained and shellacked cover over 1-in. diameter holes provided.




5

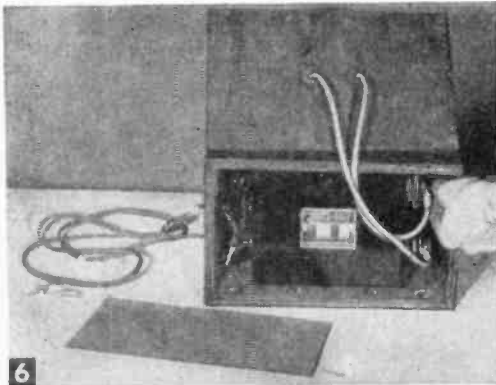

6

With the transformer mounted in the cabinet and the primary connections made with #18 insulated wire, the high-voltage leads of the automotive ignition cable are attached to the secondary terminals. Note that the holes under the insulators on the cover have been sealed with sealing compound.

to jump across. If the unit is in good condition, a heavy arc about 1-in. long should be obtained. Defective windings will produce a weak and short arc, or no arc at all. (CAUTION: Take extreme care in working around such a transformer, as it packs a charge of electricity that can be dangerous or even fatal.) Other makes of oil burner transformers may be used if the rating is about the same, but the dimensions of the box or cabinet given here may have to be modified to suit the size.

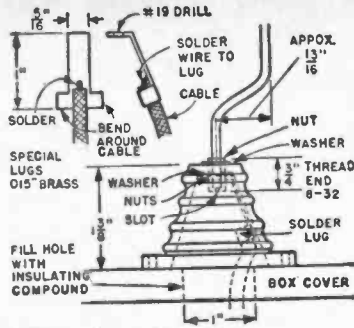

4 DETAIL OF INSULATOR AND ELECTRODE CONNECTION

Start by making the box from 1/2 and 3/4 in. birch plywood, cutting the parts about 1/16 inch oversize to allow for dressing down to final size on the sanding disc.

Bore the required holes in the cabinet, including four 3/4-in. ventilating holes at the back (Fig. 8A). Assemble sides and ends with a good grade of cabinet glue and 1 1/4-in. brads, then screw bottom onto the end pieces. Carefully sand all surfaces by hand, slightly rounding the corners. Set the brads and fill the holes with Plastic Wood.


The box can now receive its finish.

Apply a coat of walnut oil stain and allow this to dry about ten minutes. Wipe off the surplus stain with a cloth, bringing out the grain. Allow the stain to dry for several hours and then apply a coat of shellac which has been thinned somewhat with denatured alcohol. After drying, lightly rub the surface with #4/0 sandpaper and apply a second coat of shellac, a bit heavier than the first, or with less alcohol. Lightly rub this coat with fine steel wool, taking care to avoid rubbing through the finish at the corners. Apply another coat or two if sufficient shellac has not been built up on the surface. Finish the cover in the same way. Equip the cabinet with rubber knobs or feet at the bottom corners and install a pilot lamp to warn that the power is on and a toggle switch to control the flow of power to the primary. However, a push-button switch can be used instead if desired for momentary operation.

Shape the electrode wires from 5/32 or 3/16 in.

MATERIALS LIST—TRAVELING ARC

- | | | |
|----|--------|--|
| | | Birch Plywood |
| 2 | 1/2 | x 7 x 11 1/2", sides, cabinet |
| 2 | 1/2 | x 6 3/4 x 6 3/4", ends, cabinet |
| 1 | 1/2 | x 7 1/4 x 11 1/2", top, cabinet |
| 1 | 1/2 | x 6 3/4 x 11 1/2", bottom, cabinet |
| 1 | 1 | x 10 x 25", back board, enclosure |
| 2 | 1/2 | x 6 x 10", end pieces, enclosure |
| 1 | 1 | x 1 x 27 1/4" (birch or maple), back support, enclosure |
| | | Miscellaneous |
| 1 | 15,000 | volt, 30 milliampere oil burner ignition transformer for 115 volts 60 cycles (Timken Model A-R Spec. #638-291 or equiv.) |
| 2 | | porcelain stand-off insulators, 1 3/8" high, about 2" diameter bases |
| 1 | | S.P.S.T. toggle switch, 6 amperes at 115 volts, with ON-OFF plate |
| 1 | | pilot lamp assembly for 115 volts, clear lens (Dialco #95408-937, Allied Radio #52E507) |
| 1 | | NE-51 neon lamp |
| 8 | ft | #18 or #16 rubber lamp cord for primary connections |
| 1 | | attachment plug cap |
| 1 | sheet | rubber 1/8 x 5 1/2 x 10" (rubber floor tile will do) |
| 2 | | 5/32 or 3/16 dia. x 25" long hard aluminum rod for electrodes, from metal products supply company (see local phone directory). Cut to length after bending |
| 4 | | rubber knobs or cabinet feet with wood screw threaded center studs |
| *1 | sheet | clear rigid vinyl plastic .030 x 17 3/4 x 25" |
| 2 | | solder lugs, .015 x 3/4 x 1 1/2" brass or copper |
| 2 | | solder lugs to fit transformer secondary terminals |
| | | high tension automotive ignition cable |
| | | Misc. stain, shellac, screws, nuts, washers |
- *The Forest Products Co., 131 Portland, Cambridge, Mass., will supply the plastic in a .030 x 20 x 25" piece for \$2.75 ppd in U.S.

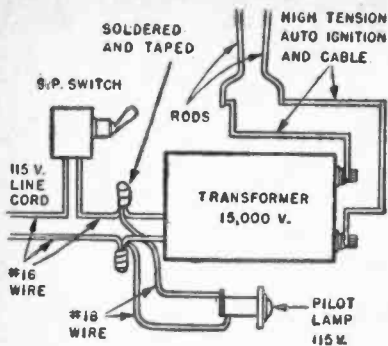

7 PICTORIAL WIRING DIAGRAM

dia. hard aluminum rod stock so they will be about $\frac{3}{8}$ in. apart at the bottom end and about $2\frac{1}{2}$ in. apart at the top (Figs. 2 and 4). The exact spacing will depend on the diameter of the bases of the insulators obtained, since if they are larger than those we used, greater offset will have to be put in wires to get required spacing. Cut #8-32 to 10-32 threads on wires, depending on rod size, so nuts and washers can be used as in Fig. 4.


Attach the porcelain insulators with the attached electrodes to the box cover (Fig. 5).

Secure the transformer to the cabinet bottom, using four wood screws at its base. Complete the primary connections with two soldered and taped joints (Figs. 6 and 7). Connect the high-voltage cables to the secondary terminals, using solder lugs on the cables (Fig. 4). Seal the holes in the cover through which the cables pass with a sealing compound, which can be any insulating type of hard-setting cement capable of being melted and poured in the holes (Figs. 4 and 6). Place a piece of rubber (shown on the bench, Fig. 6) on top of the transformer to prevent possible leakage of current to that metal surface.


Attach the cover, using roundhead brass screws. Give the unit a preliminary test in this condition, standing 3 or 4 feet away for safety. The arc should form at the bottom and rise, but not in a proper manner as it will when the enclosure is provided.

Construct the enclosure from $\frac{3}{8}$ -in. birch plywood (Fig. 8). Make the openings in the two curved end pieces on the jigsaw and attach to the back board with glue and flathead screws. Fit the back brace to the board. Bore four $\frac{3}{4}$ -in. diameter holes through the back board at the lower end to admit air. Apply walnut oil stain and finish exactly the same as the cabinet.

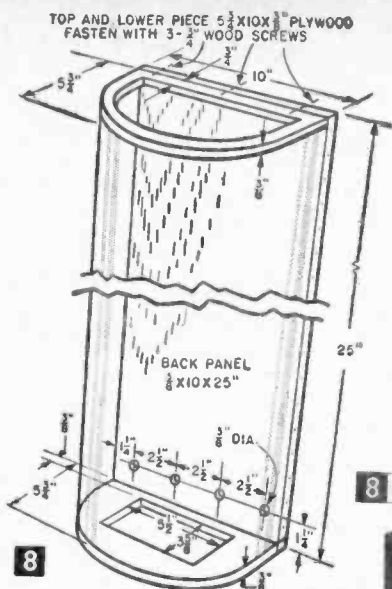Cut the .030-in. clear vinyl plastic front to size with sharp scissors, taking care to avoid cracking, and install to the edges of the unit in a simple manner, using small brads with heads or very small tacks along the two sides



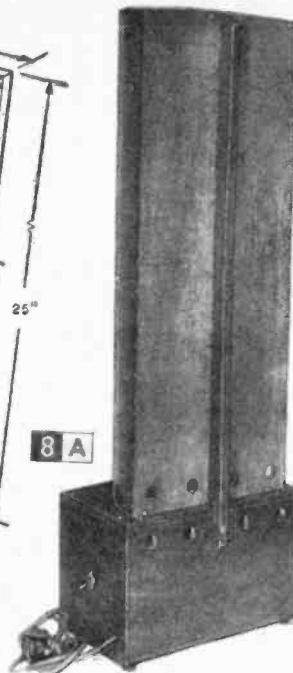8 A view of the finished job from the back side. The author built the device in slightly more than two evenings at a cost of about \$25.



(Figs. 8 and 8A). Apply shellac to the edges first, and allow to dry until tacky. Then place the plastic in position on one edge and secure. Bend the material around the curved end pieces, pull it tight and secure it at the other edge. Be sure to drill a small hole for each brad, since this plastic is quite brittle and may crack if you try to drive a brad through it. Avoid the use of plastic that will support combustion, such as some of the cellulose variety. Vinyl plastic will soften if given too much heat, but will not burn easily.

Long testing has proved that the plastic front was sufficiently far enough away from the arc to keep out of trouble. However, if you want added fire safety, cement or tack a strip of sheet asbestos around the inside edge of the top opening, where the intensity and flame of the arc are the greatest.

Drop the completed enclosure down over the wires and secure to cabinet with a single screw through the supporting brace (Figs. 3 and 8A).

While the unit can probably be operated continuously for quite some time without damage, it is well to use it intermittently or for special demonstrations, since the wire electrodes become quite hot due to the moving arc stream. Print a sign or name plate on the front of the cabinet, reading "CAUTION—15,000 volts," as a general warning to persons who may tend to get careless.

If used properly, however, there should be no danger to anyone.

A Volt-Ohmmeter and Transistor Tester For The Experimenter


By C. F. ROCKEY

If you do much serious radio or electronic experimental work, you will frequently need to make voltage and resistance measurements within your circuitry. And the present intense interest in transistors makes a simple transistor tester increasingly valuable. Why deny yourself these essential measurements when you can build a unit to perform both of these functions in a single Saturday afternoon? One for which the cost will be well below that of currently available, American-made instruments of equivalent utility.

Experience indicates that 99% of all routine electronic circuit tests are those of dc voltage and resistance. While ac voltage and dc current scales would be occasionally useful, the added cost and complexity involved does not justify including them within this device.

The only expensive item is the meter itself. Good meters cost money, poor ones are not worth the little they do cost. But the 0-1 milli-ampere meter used here is one of the most useful of instruments, and it is well worth its approximate \$10 cost. (You will find plenty of future use for it, long after you have electronically outgrown this project.) Surplus 0-1 milliammeters are available, we understand, at something like one-half new-meter price. But be careful. It is easy for the beginner to get stung. Make sure that the meter you use is of the correct current rating, has not been damaged by shock or mishandling, and is of the moving-coil (D'Arsonval) type. The cost of the remaining parts in this project is small.

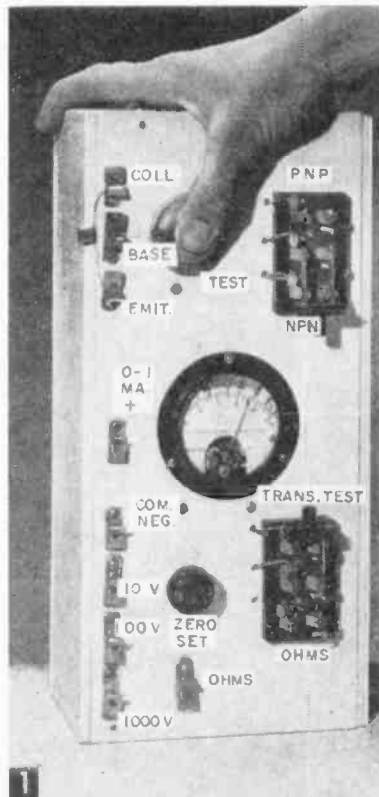This project is big; the writer does not believe in miniaturization in home projects. First, I'm not a jeweler and secondly, miniaturization is costly and subject to difficulties in maintenance. You can redesign this job to fit in a much smaller space. But you will sacrifice ease of construction and maintenance thereby.



Not a "black box," but a white one that is inexpensive and useful.

a 1/2-in. drill. This is the hard way, but it works. The rim of the meter will neatly cover any misses.

Next, drill 1/8-in. holes to mount the two DPDT switches. Use a switch as a template. These switches are available at many chain hardware stores, "dime" stores, etc., throughout the country. Drill a 3/8-in. hole for the zero-set potentiometer. Finish the drilling with the 1/8-in. holes for the Fahnestock clips, the mounting holes for panel, and pushbutton lead holes.

If you consider Fahnestock clips old-fashioned, substitute pin jacks. But you'll find, as the writer did, that they'll lose their grip much sooner, despite their prettier looks.

With all the holes drilled, sand and finish. When finish is dry, mount all parts except the meter. Then wire the circuitry according to Fig. 6. Mount the voltmeter multiplier resistors between two tie-lugs, as shown in Fig. 5. Finally, insert and connect the meter. When the wiring is

Begin by building the case and panel, a simple plywood box 4 x 6 1/2 x 13 1/2 in. Nail the sides and bottom together to form the cabinet, but leave the top loose. This will be the panel (see Figs. 3 and 5) upon which all parts will be mounted. Quarter-inch plywood scraps were used by the author for the panel, sides, and bottom. The ends are three-quarter inch pine stock. Sand the base and panel for a neat job, but do not finish until all holes have been drilled. Then give the panel a final sanding and finish as you prefer. I used some semi-gloss wall paint I had on hand, but orange shellac is acceptable, and dries much faster.

Cut the meter hole squarely in the center of the panel. A hole of 2 3/4 in. dia. will fit most modern meters. (The old Weston, vintage of the thirties, used in the writer's job, took a 2 1/2-in. hole.) If you have a suitable expansion bit, use this to cut the hole. If not, draw a circle in the right place and drill all around its circumference with

MATERIALS LIST—VOLT-OHM-METER AND TRANSISTOR TESTER

No. Req'd	Description
1	0 to 1 ma. milliammeter, 3" size (Weston, Triplett, Simpson, or other good make)
2	DPDT, plastic base knife switches
1	push-button, flush mounting
9	Fahnestock clips
1 set	test leads, ICA
1	1000 ohm potentiometer, (Mallory, IRC, or any other good make)
1	knob for potentiometer
1	flashlight cell, large size
1	single-point tie-lug
1	double-point tie-lug
1	triple-point tie lug
1	1 Megohm, 1-watt carbon 5% resistor
1	100K, 1-watt carbon 5% resistor
1	10K, 1-watt carbon 5% resistor
1	1K, 1-watt carbon resistor
1	47 ohm, 1-watt carbon resistor
1	200K, 1-watt carbon resistor
1	9.1K, 1-watt carbon resistor
	6-32 rh machine screws, 3/4" with nuts, #6 x 3/4" rh wood screws, hookup wire, rosin-core solder, finish
2 pcs	1/4 x 6 x 13 1/2" plywood
2 pcs	1/4 x 3 3/4 x 13 1/2" plywood
2 pcs	3/4 x 3 1/2 x 6" pine stock

transistor's amplifying ability, its "dc beta." The greater the change, the more the potential amplification. One would normally consider a change in current of 0.4 milliamperes to be about the minimum to be expected of a good transistor, as sold today. For a quick check, then, the current should swing up to at least 0.6 ma. when the button is pressed if the transistor is to develop satisfactory gain in the usual circuit.

Experience with this tester will reveal the great variability of characteristics found in transistors of the same type sold on the market today. Even with the tremendous strides being made in semiconductor technology, it is economically impossible to hold the tolerances within the 10% or so, one finds in vacuum tubes. This is especially so in the case of the cheaper units which most of us are economically forced to use. But with a tester like the one described here, you can pick and choose from your stock, selecting the highest-gain units

In-circuit testing of resistors is possible, but watch out for those parallel circuits and make sure circuit is dead.

transistor, but no simple test can definitely assure of a good one, since too many factors are involved. All currently-available types may be significantly checked with it, and the result will be found valid and reliable.



Practically, a transistor has two properties which will determine whether it is usable or not. These are:

1. The open-base, emitter-collector leakage.
2. The grounded-emitter dc voltage gain, or "dc beta."

This device gives a comparative indication of both of these properties.

Place the "PNP—NPN" switch in the appropriate position for the transistor you wish to test. Connect transistor leads to correct terminals. Then throw the "ohms—trans. test" switch into the "trans. test" position. The reading you now observe upon the meter is a function of the open-base, emitter-collector leakage. (This is before the test button is pressed.) The lower the meter reading under these conditions, the better the condition of the transistor. In every case, the meter reading should be less than 0.1 milliamperes, preferably closer to 0.05 milliamperes. If the reading exceeds 0.2 milliamperes it is a sure sign that the transistor has been electrically mistreated, and should be considered questionable, if not downright bad.

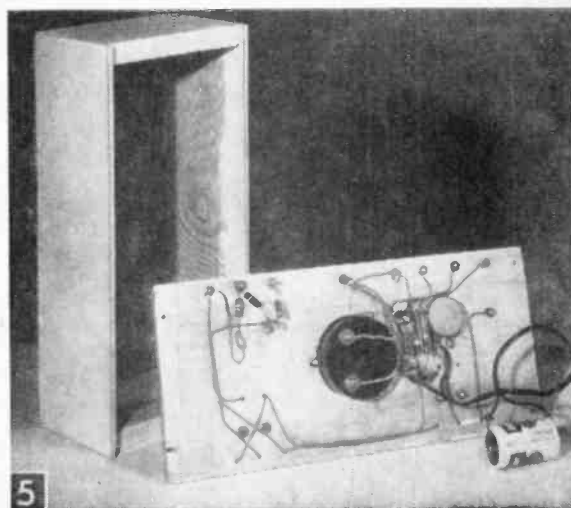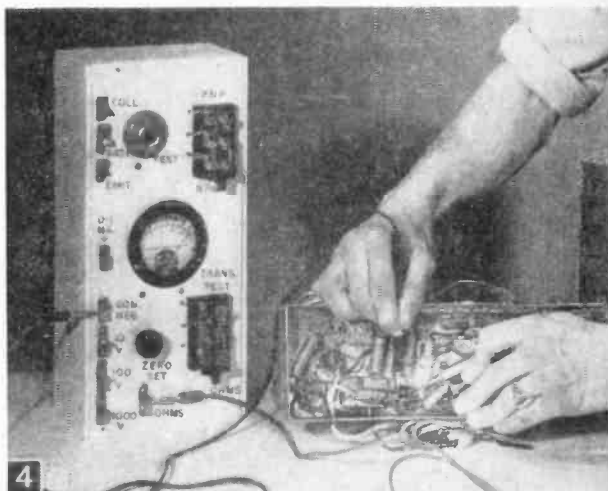
If the transistor passes the above test, press the button. The current indication should increase sharply, at least to 0.6 milliamperes. It is the change in current observed which gives the measure of the



Back view of front panel of case, showing simple wiring.

for the most critical parts of the circuit. If you do this, you will soon see the improvement in performance of the gear you build. (Incidentally, do not leave switch in "trans. test.")

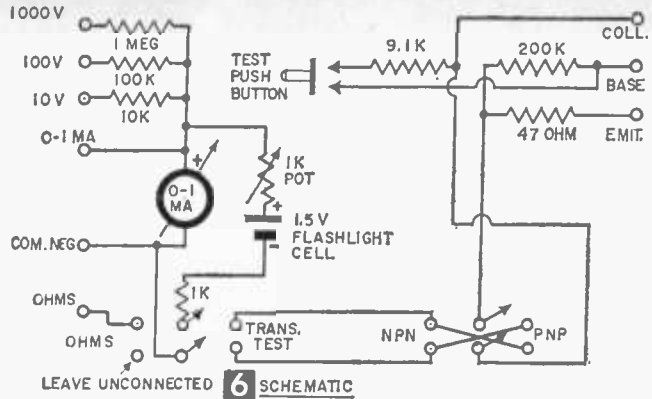You can also use this device for comparative checks of semiconductor, "crystal" diodes. Connect the diode from the "emit" to the "coll" terminals, with the meter switch in "trans. test" position. Switching the "PNP-NPN" switch back and forth slowly should reveal a current difference of at least 0.6 of a milliamperere, if the diode is usable. The greater this difference, the better.



Electronic Black Magic

How does it work? Only two wires connect the switch to the lamps, yet throwing the switch in one direction lights one lamp, throwing it in the opposite direction turns the first lamp off, the second on


By FORREST H. FRANTZ, Sr.

FOR every lamp that is to be controlled separately by a single switch throw, two wires are required from lamp to switch—usually. Here, however, one switch and only two wires control two lamps. Extra conductors in the two wires? Hidden wires? Hair-thin connecting wires? Those you demonstrate this device to will look for all of these possibilities. That's one reason connecting clips are used between the switch and lamp cases: to allow observers to convince themselves that the insulation over each lead covers only one wire.

After the observer is convinced that no hidden wires exist, he may take a guess that wireless radio is involved. This goes out the window when you tell him that the entire outfit costs only about \$2, and at that price radio isn't involved. Magnetic coupling, then? To kill this theory, separate the cases by several feet. Point out that the light bulb intensity remains constant no matter what the physical separation between units.

How does it work then? Electronic black magic.

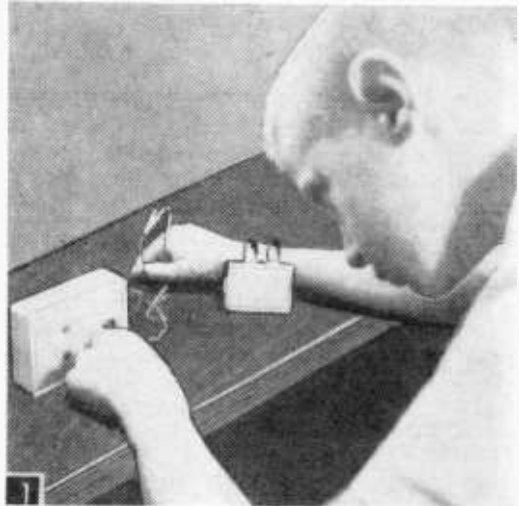Construction. Layouts for switch and lamp cases are shown in Fig. 2. The smaller holes, and pilots for the larger holes, are made with a heated ice pick. Plastic that accumulates around the sides of the holes may be trimmed off with a pocketknife after the material has cooled. Larger holes are finished with a hand taper reamer.



Black magic from white boxes. A single switch and a single pair of wires control two lamps.

MATERIALS LIST—ELECTRONIC BLACK MAGIC

Desig.	Description
SWITCH UNIT	
B	four 1.5-v penlite cells, series connected (RCA VS074)
S	DPDT toggle switch (Carling 316-25)
	battery holder (Lafayette MS-170)
	1 x 2 5/8 x 3 3/8" plastic case (Lafayette MS-159)
LAMP UNIT	
D1, D2	1N54A diode (RCA)
L1, L2	#48 miniature lamp (RCA)
	1 x 1 1/8 x 2 1/8" plastic case (Lafayette MS-156)
	2 Minigator clips (Mueller 30)


Components for this project may be obtained from Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, New York.

When you make the holes for the lamps, work slowly and ream the holes just large enough so that the lamps fit into them tightly.

When all of the holes have been made in the cases, wash them with soap and water, rinse and dry with a lintless cloth. Then paint the insides any color you wish. I used white because this encourages the observer to hold the cases up to the light to try to determine their contents. Although he'll be able to see the switch and battery, he won't be able to see enough to determine the


secret. Use two coats of paint if necessary.

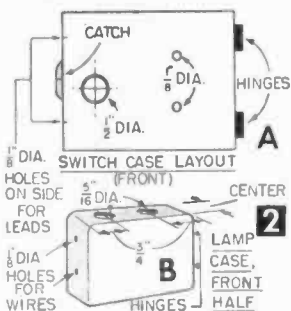Now mount the battery holder and the switch in the switch case (see Fig. 3). Connect the battery holder terminals so that the four penlite cells will be in series. Fill the battery contact holes on the holder with solder. This assures reliable contact. Don't allow the clips to cut the paper covering on the batteries when you insert them. Complete the wiring as shown in Fig. 5.




The inside view of the lamp case is shown in Fig. 4. Wire the lamp case, making sure you observe diode polarities. Don't apply heat to the diodes for a long period of time when you solder them into the circuit. Too much heat will damage them.

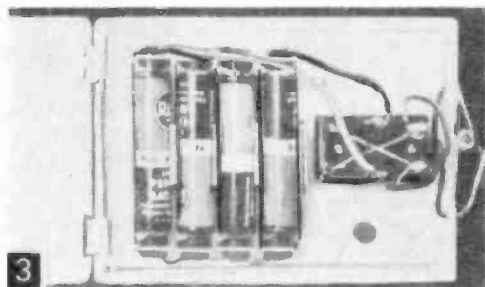
With construction completed, connect the units



Inside view of switch case.

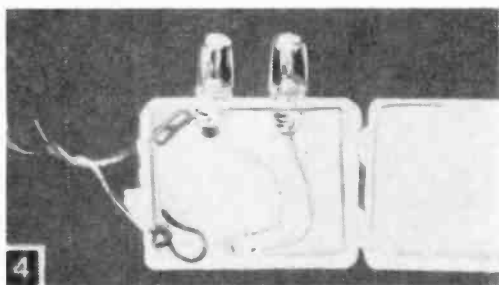

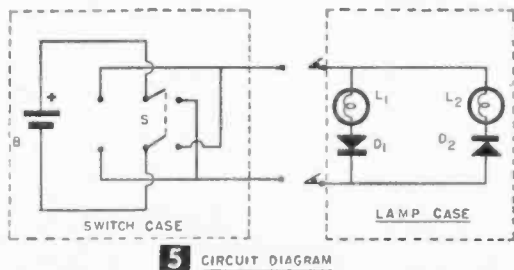
Inside view of lamp case. Disconnect two cases when not in use to prevent unnecessary drain on batteries.



5 CIRCUIT DIAGRAM

together and try your handiwork. By now you probably know the electronic black magic that's involved, but for the gadgeteer without electronic experience, an explanation is in order.

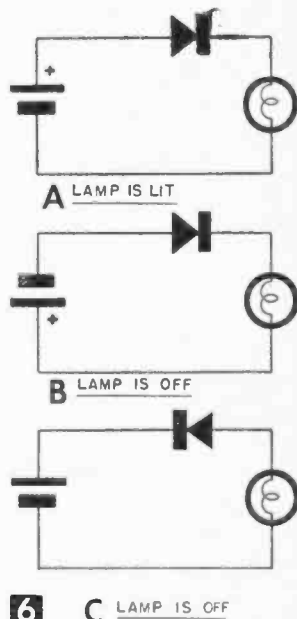A diode will conduct in one direction only. A diode connected in series with a lamp and battery as shown in Fig. 6A will conduct and allow the lamp to light. But if the battery polarity is reversed (Fig. 6B), the diode will not pass current, the lamp will not light. By the same token, if the battery is left as shown in Fig. 6A, but the diode is reversed as in Fig. 6C, the lamp will not light.



6 LAMP IS LIT, LAMP IS OFF, LAMP IS OFF



Now, referring to Fig. 5, it is apparent that throwing the switch causes the battery polarity to be reversed. Since the diodes are oppositely connected to the respective lamp bulbs, one—and only one—of the lamps will light, the position of the switch determining which one will. No black magic after all.

Crystals Like It Cool

• The crystal elements of microphones and phonograph pickups and crystal diodes and transistors are sensitive to high temperatures. All these crystal and semiconductor elements are enclosed in a case or shell. If exposed to strong sunlight, the temperature inside may rise far higher than that outside the case or shell, damaging the elements so they no longer work and may actually melt. To prevent damage, be sure to shade the pickup arm of a portable phono pickup or shelter a transistor radio being carried or used on a picnic during the summer. And never leave a pickup unit in its case in the window.—JAMES A. McROBERTS.

SOLUTION TO
AMATEUR
RADIO
PUZZLE
Page 51

H	A	M	F	E	S	T	E	D	O	S	L
A	E	N	T	F	C	C	W	O			
R	I	G	D	I	T	O	S	C	Q	S	O
M	C	C	P	C	I	V	T				
O	S	W	L	O	G	M	H	O	T		
N	E	T	O	C	T	A	L	N	C	E	
I	U	G	X	H	O	H	M	S			
C	B	K	C	O	B	A	N	D	T		
S	G	E	X	T	R	A	R	E	N	D	
H	Y	S	O	T	R	E	T				
C	U	P	F	L	L	I					
H	A	M	N	O	V	I	C	A	A	C	
O	T	T	E	N	Y	A	G	I	K		
K	W	V	A	A	D	C	E				
E	T	H	E	R	L	O	S	S	W	E	T

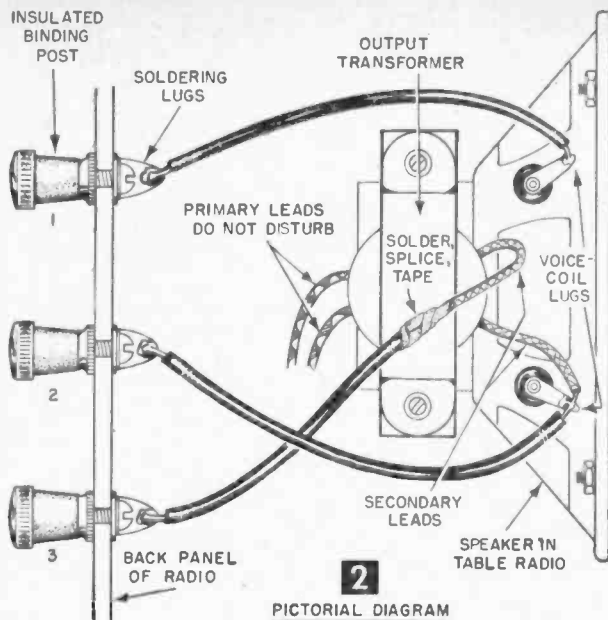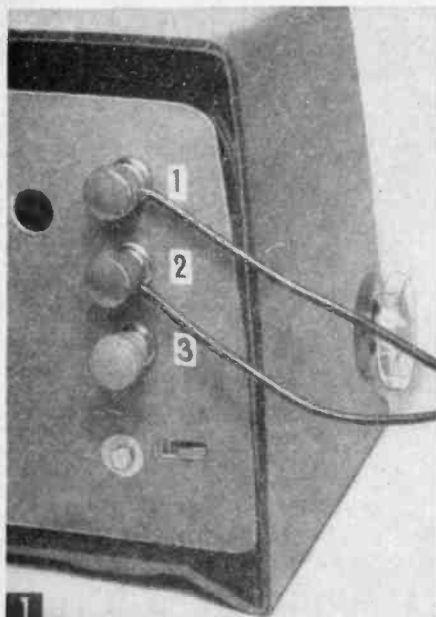

Four Extra Uses for Table Radios

BY making a few wiring changes and adding three insulated binding posts to the back of your table radio as shown in Figs. 1 and 2 you can:


1. Use the speaker only for an experimental dynamic microphone, or speaker can be connected to a code practice set for group instruction or testing a radio you are building by connecting the latter to posts 1 and 2. If the speaker has a permanent magnet, pull out the line cord plug; if it uses a field coil, turn the set on to energize the speaker magnet.

2. Add a small extension PM speaker to the radio for use in other rooms, connecting it to posts 1 and 3 if both speakers are to operate or posts 2 and 3 if only the extension speaker is to be used.

3. Boost the radio fidelity by connecting a large PM speaker housed in a good baffle to posts 2 and 3.

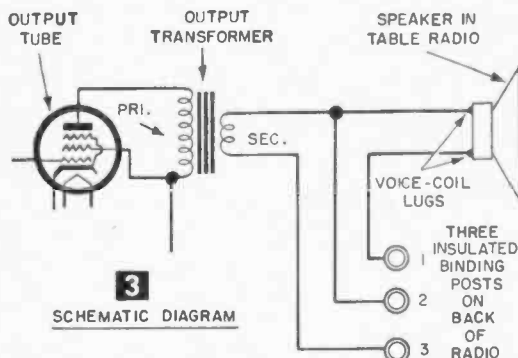4. Use the radio speaker as a "tweeter" and a large PM speaker connected, in series, to posts 1 and 3, as a "woofer." Place the radio on top of the woofer cabinet. If you want the speakers in parallel, connect the woofer to posts 1 and 2 and a wire jumper from post 1 to 3. In either case the speakers should be in phase (their cones moving in the same direction at the same time) to give the best tone quality. If they are out of phase, reverse the woofer connections for better sound.

The radio still can be used as its designer intended by connecting a wire jumper to posts 1-3.



How to Wire. Fig. 1 shows the installation on an FM table radio; Figs. 2 and 3 furnish the wiring info. Do not disturb the two wire leads, usually red and blue, on the primary side of the output transformer. If you cannot find a place for the posts on the rear panel where they won't interfere with the loop antenna, if any, mount the posts on a strip of insulating material and fasten with an angle bracket to the back of the cabinet.

Caution: If one side of the speaker voice-coil and one of the output transformer's secondary leads are grounded to the chassis of an ac-dc radio, remove these leads from the chassis and connect the latter directly to the voice-coil. This will by-pass a possible hot chassis, and there will be no danger when handling the binding posts. If the radio has a power transformer, there is no danger and no change need be made.—ART TRAUFFER.

“Hop-Up” That Small Radio with a Tuned Antenna Coupler



1

You'll be surprised at how well your small receiver performs when coupled to an outdoor antenna with a tuned antenna coupler.

Do you want to listen to that distant 250-watt station despite a 5000-watter blasting away nearby? Do you live so far from the nearest transmitter that even your local reception is weak and full of noise? If so, this simple gadget is for you.

A long, outside antenna seldom proves satisfactory with the usual small broadcast receiver, since it often spoils the selectivity of the front-end. A simple antenna tuner, such as this unit, used with an outside antenna, will restore this selectivity and couple the circuits more effectively. Result: No more “birdies,” or local station smear, and the little ones from far away stick their heads above the mud.


Obtain a cardboard mailing tube, or a core from a bathroom tissue roll about 1½ in. in diameter and at least 3½ in. long. (The dimensions are not critical, and may vary ½ in. either way.) Carefully close-wind on this tube 150 turns of No. 24 copper magnet wire. Cotton-covered wire is best but enamelled wire will do. Arrange for taps on this coil at 50 and 100 turns (see Fig. 2).

Connect this coil in series with a variable capacitor of 360-mmf maximum capacitance. Any variable capacitor having this capacitance will work satisfactorily. (If you use a two-gang unit, salvaged from the junkpile, use only one section.) Mount the capacitor and coil upon a ¾ x 4 x 4 in. softwood board (see Fig. 2), and your antenna tuner is complete.

There are two ways to connect this tuner to

your radio, depending upon the impedance of its input circuit. Try both connections, the one giving the sharpest tuning and the greatest signal boost will be immediately evident. The connection shown in Fig. 3A is for high-impedance, 3B for low impedance inputs.

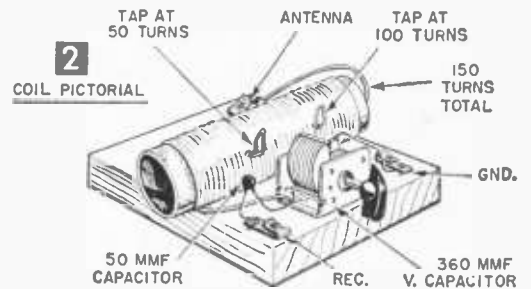
Use a well-insulated outdoor antenna with a total length of 60 to 150 ft. A good cold-water pipe ground should also be used. Set the radio dial to the frequency of the weak station you wish to hear and rotate the variable capacitor knob until it peaks to maximum volume. Then readjust radio tuning for best signal quality. Clip the antenna clip on the coil tap that gives best results.—C. F. ROCKEY.



2
COIL PICTORIAL

MATERIALS LIST—ANTENNA COUPLER

No. Req'd	Description
1	variable capacitor, 360 mmf. max.
1	Mueller spring battery clip, miniature size knob, for variable capacitor
¼ #	No. 24 magnet wire, cotton-covered or enamelled
1	0.01 mfd., 200 w.v. paper capacitor
1	50 mmf., disc-type ceramic capacitor

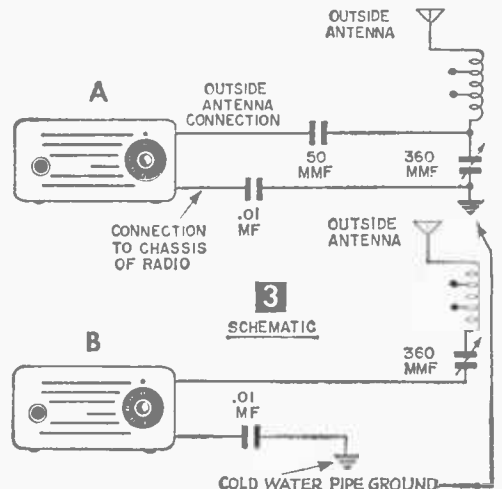

3
SCHEMATIC

Learn By Doodling

By ROBERT W. LUEBKE


HERE'S an easy way to test your knowledge of amateur radio circuits. The six circuits given on these two pages are some of those you'll find it essential to know about when working toward an Amateur Radio Operator's General Class license. We publish them by special permission of The American Radio Relay League, publishers of the *Radio Amateur's License Manual*.

The connecting wires have been removed, but all the components are shown. Cover the

outlines on these pages with onion-skin or any other translucent paper and "doodle" in the missing connecting lines. Check your doodling for errors by comparing with the complete circuit diagrams on page 94.


If you find your first doodle in error, study the circuit carefully and try again. Use a new sheet of paper each time rather than doodling directly on these pages. Soon you will be able to draw the entire circuit without using the outline at all.

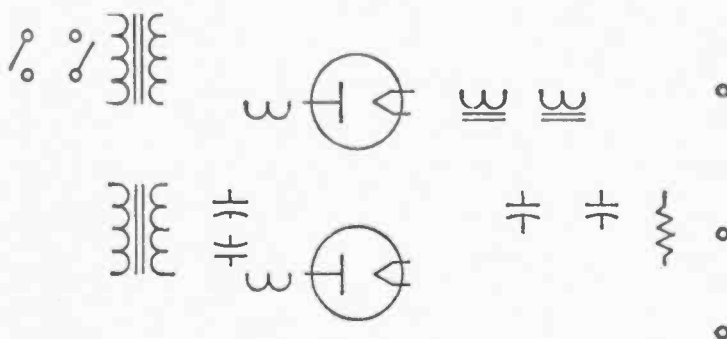1. Draw a schematic diagram of a full-wave single-phase power supply using a center-tapped high-voltage secondary with a filter circuit showing a bleeder resistor providing two different output voltages and a method of suppressing "hash" interference from the mercury-vapor rectifier tubes. Give the names of the component parts and approximate values of filter components suitable for either amateur radiotelephone or radiotelegraph operation.



1

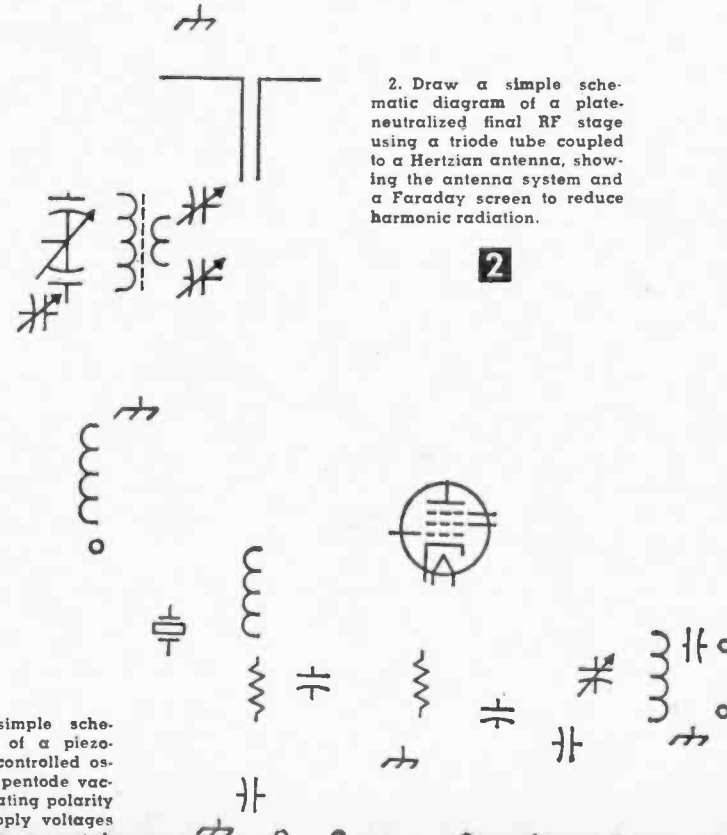2. Draw a simple schematic diagram of a plate-neutralized final RF stage using a triode tube coupled to a Hertzian antenna, showing the antenna system and a Faraday screen to reduce harmonic radiation.




2

3. Draw a simple schematic diagram of a piezoelectric crystal-controlled oscillator using a pentode vacuum tube, indicating polarity of electrode supply voltages where externally connected.

3


4. Draw a simple schematic diagram of a half-wave rectifier with a filter which will furnish pure dc at highest voltage output, showing filter capacitors of unequal capacitance connected in series, with provision for equalizing the dc drop across the different capacitors.

4

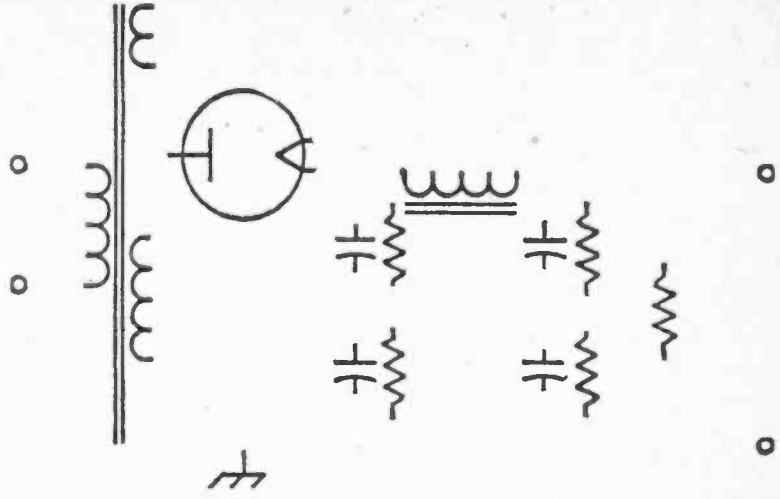


5. Draw a schematic diagram of a pentode audio power-amplifier stage with an output coupling transformer and load resistor, showing suitable instruments connected in the secondary for measurement of the audio-frequency voltage and current, and naming each component part.


5

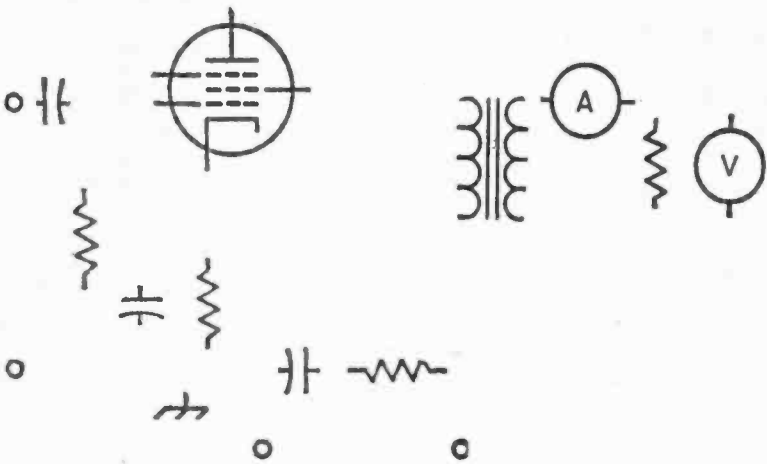

6. Draw a simple schematic diagram of two RF amplifier stages using triode tubes, showing the neutralizing circuits, link coupling between stages and between output and antenna system, and a keying connection in the negative high-voltage lead including a key-click filter.

6

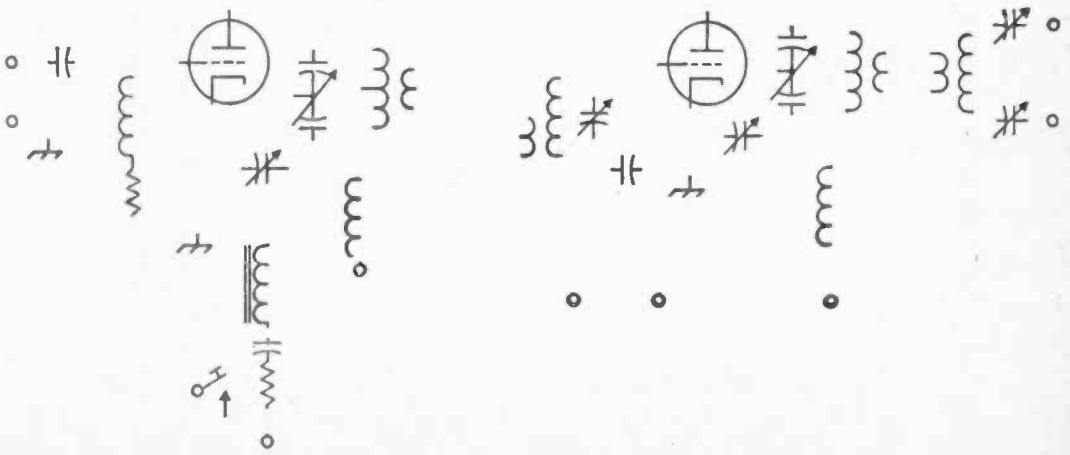

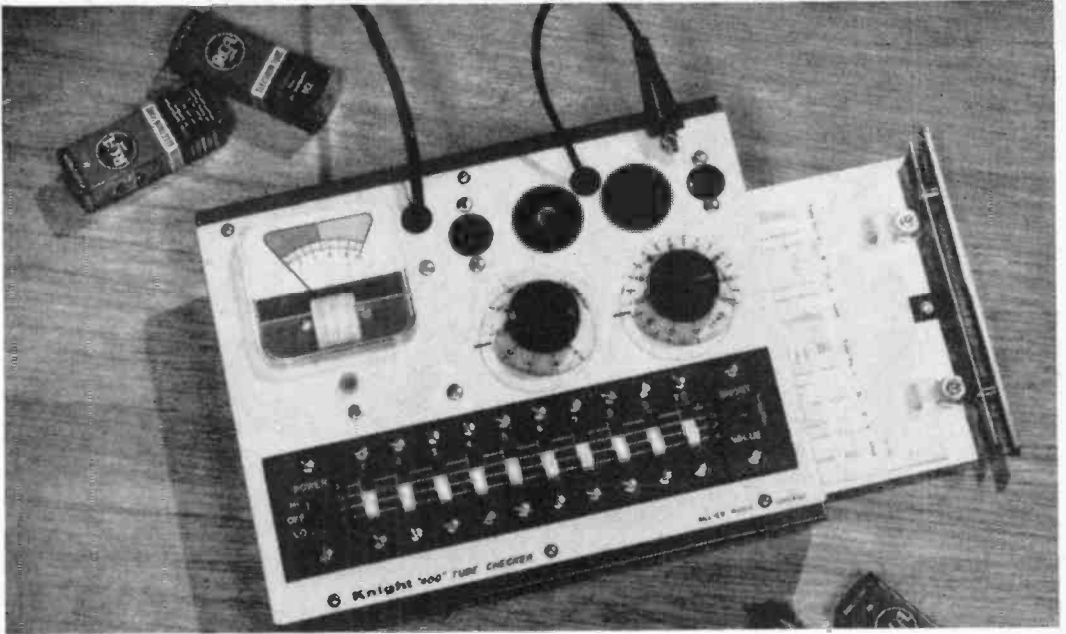

Knight Tube Checker KIT REPORT

THE KNIGHT-KIT 400 tube checker is an excellent construction project—and it is the lowest priced cathode emission checker on the market.

The 400 tests for filament continuity, for short-circuits and for cathode emission. The most important of these tests is the cathode emission test. In this test full line voltage is applied between the control grid of the tube and ground through the meter. The resulting electron emission from heater to grid is measured, and this is assumed to be the same as if current from heater to plate (as occurs in actual tube use) were being measured.

Seven filament voltages are available on the unit, although in actual use a tube would require a specific filament voltage, of which there are at least a dozen in common use. Presumably there is no possibility of damage to the grid as the result of carrying line voltage during this test.


We ordered our test kit by mail. It arrived by parcel post, in a sturdy carton. The parts were well padded with corrugated, and all of the small parts were in polyethylene bags—screws in one bag, washers in another, and so on. Transformer, meter and wafer switch were individually boxed and padded. Resistors were mounted on a card, each of them

designated by a number, keyed to the instruction booklet. All hook-up wire was cut to the lengths required for the project. Instructions call for a certain color wire—that color is pre-cut to the right length, nine different colors, nine corresponding lengths.

Panel and case of the checker were of heavy-gage steel, well constructed, neatly and accurately punched to receive the four tube sockets, meter, load resistor and 13 slide

KNIGHT 400 TUBE CHECKER

- Checks cathode emission, shorted elements, filament continuity of 400 tube types.
- Has sockets for 7-pin miniature, 9-pin miniature, octal and loctal-base tubes.
- Meter has red-green "Replace-Good" Scale, special scale for diodes.
- Slide-out metal drawer has flip-type tube charts in loose-leaf binding.
- For operation from 110-125 v, 50-60 cycle ac; has "Hi-Lo" line-voltage compensator switch.
- Carrying weight: 5¼ lbs.; size: 2¾ x 8 x 9½ in.
- Allied Radio (100 N. Western Ave., Chicago 80) catalog # 83Y707. Price: \$19.95.

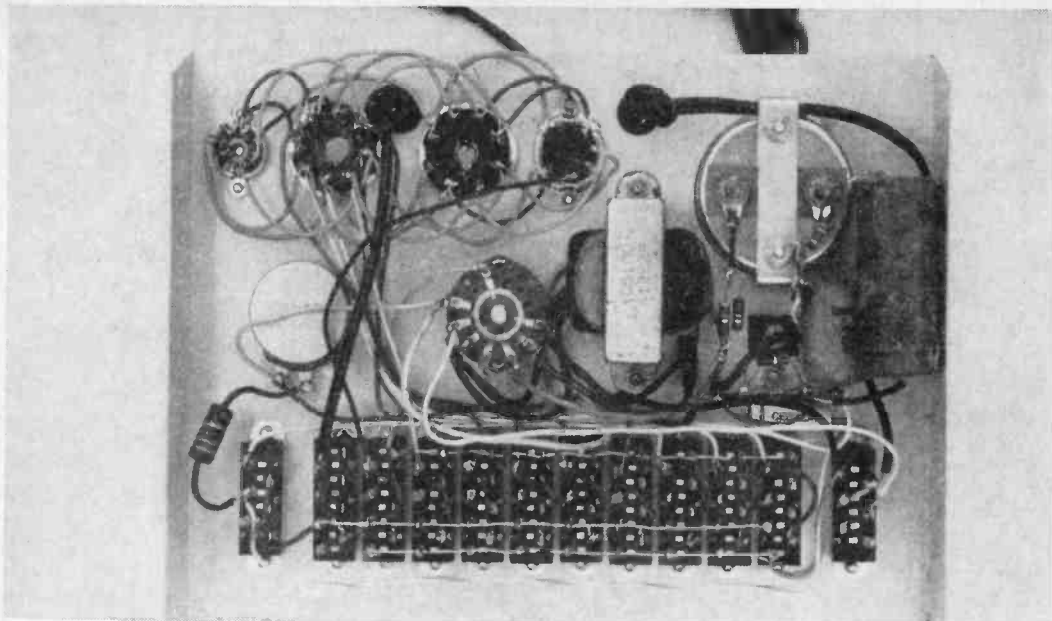


This underside view of the completed panel shows trim parts placement and design.

switches. The panel was handsomely enameled in white, grey and black; all dial markings were clear and distinct. The line cord appeared to be of good quality and plentiful solder was supplied.

Of the 25 tubes that we tested for cathode emission, all but three registered perfect on the meter—so perfect that the needle banged the meter housing in most instances. The tubes tested varied in age from two to 15 years. Of the three that did not register perfect, two registered zero, and were, indeed, burned-out. For one of the tubes that was

tested, an error in the flip-type tube chart data accompanying the checker caused the tube to test *shorted*. In testing for shorts in miniature tubes on this tester—as on all other testers—it is necessary to make each test as brief as possible to avoid the possibility of causing a short in the tube due to the relatively high voltage used in the test.

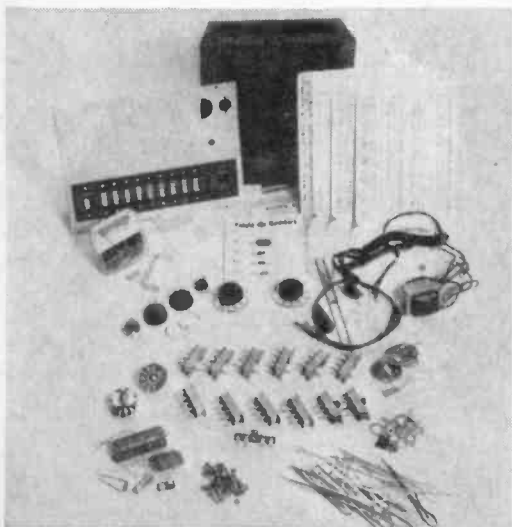
This kit makes an enjoyable construction project, and when used in conjunction with a tube manual, provides a good introduction to some of the ailments that beset tubes and the diagnosis of those ills.—H. SIEGEL.



The components of the tube checker.

Shield Spring for Soldering

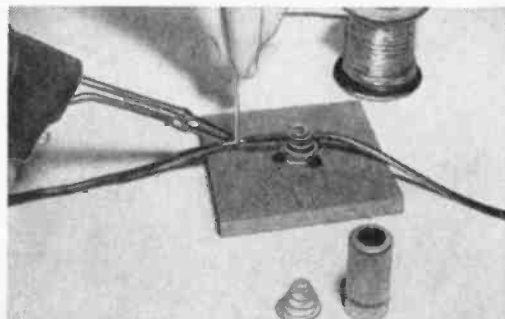• A spring removed from a miniature tube shield makes a handy gadget to hold parts or wires still while you solder them. By tacking the spring down to a scrap piece of wood as shown and clamping the work between the spring's turns, it makes a welcome partner for any electronic hobbyist's bench.—J.A.C.



Loop Crystal Set

Just aim the loop at the station you want, and then enjoy yourself

By ARTHUR TRAUFFER








watt stations, no conventional antenna or ground is needed. The loop crystal set can be carried around playing, and used anywhere in the house; just aim the loop at the desired station.


Interfering stations, which are at right-angles to the desired station, can be greatly reduced in volume simply by pointing the loop at the desired station with the loop broadside to the interfering station. In some cases, a loop crystal set will prove to be more selective

IN THESE days of powerful transmitters, sensitive germanium diodes, and sensitive earphones, a loop crystal set for local stations is practical and sometimes a distinct advantage. For example, for those living within about 4 miles of 5,000 watt stations, and 5 or 6 miles from 50,000

than most crystal sets using a conventional antenna and ground, but don't expect the same sensitivity with a loop that you will get with a long outside antenna and a cold water pipe ground. A binding post on the side of the cabinet provides for an additional antenna for those living outside the range of the loop, and for those desiring to pick up more distant stations after the locals have signed off for the night.

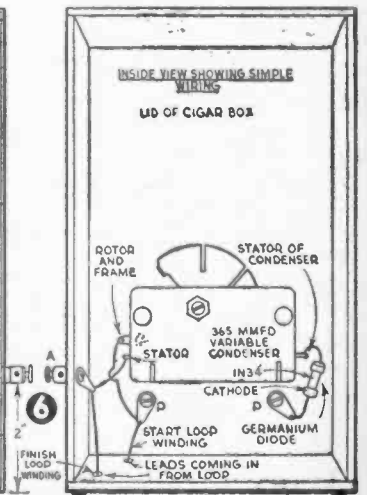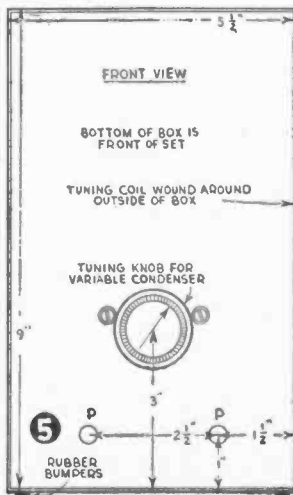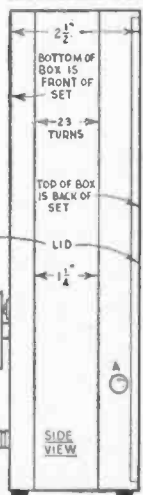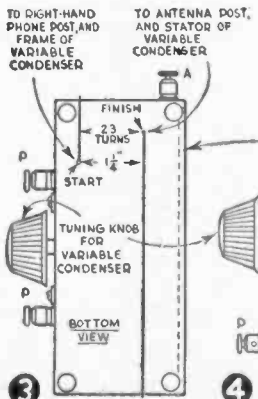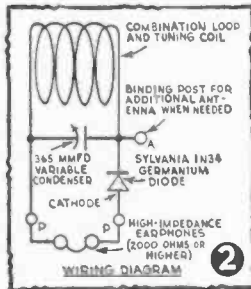
The extreme simplicity of this set is demon-



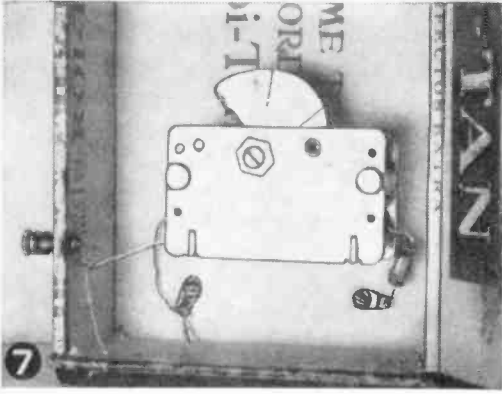

strated by the fact that the set shown (Fig. 1) was assembled and wired by a child under the supervision of the author.

This set differs from other crystal sets in that the tuning coil is wound around the outside of a cigar box to form a loop antenna (Fig. 2), instead of on a small Bakelite or cardboard tube inside the set. Figs. 5 and 6 show the simple layout for the 365 mmfd. variable condenser, the 3 post-type binding posts, or Fahstock clips for the earphones, and the extra antenna connections. Fasten a soldering lug under the head of each binding post screw. Wind the loop, consisting of 23 turns of #24 gage enameled or double-cotton covered magnet wire, around the outside of the cigar box (Figs. 3 and 4). To start loop winding, connect to right-hand phone post (as seen from front view of set) and to variable condenser rotor and frame (Figs. 3 and 6). Then wind 23 turns clockwise around outside of box and connect the other end of loop

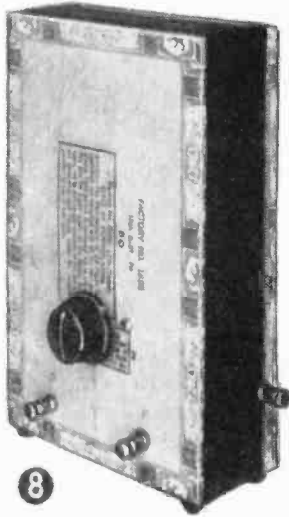

to antenna post and stator of variable condenser. The width of loop winding will be about $1\frac{1}{4}$ in. with the turns spaced the diameter of the wire apart. Connect germanium diode cartridge from another variable condenser stator lug to left-hand phone binding post (Figs. 6 and 7). Mount a pointer knob or a graduated turning dial, on the variable condenser shaft, and tack or glue 4 small rubber bumpers onto the bottom of the cabinet. The set is now completed (Fig. 1).


Wind a few turns of Scotch tape over the loop wires to protect the wires (Fig. 8), or brush a couple of coats of shellac over the loop wires. The writer tried shunting a small by-pass capacitor across the phone terminals, but no improvement was noted. This loop crystal set will give you slightly more volume indoors than outdoors, due to RF energy picked up by induction from the house wiring circuit. There will be some variation in signal strength in different parts of the room and different rooms in the house, due also to the house wiring circuit.

Glue a disc of heavy white paper or thin white cardboard onto the panel under the pointer knob on the tuning condenser so you can log your stations. When an additional antenna is used, however, the log will shift somewhat due to the added capacity introduced into the tuning circuit by the antenna. A water pipe or gas pipe connected directly to the antenna post makes a very efficient antenna for picking up distant stations. To obtain better results on distant stations connect a water pipe to the antenna post and use a bed spring as a counterpoise. Connect the bed spring to the right-hand phone post, which is the other side of the loop.

If you use a variable condenser larger than the one specified, you may have to remove 1 or 2 turns from the loop in order to cover the entire broadcast band. If you use a smaller capacity condenser you may have to add 1 or 2 turns to the loop. It is best to use a condenser not smaller than 365 mmfd., which is a standard size for the broadcast band. A little experimenting will give the desired results.

Auxiliary Auto Aerial

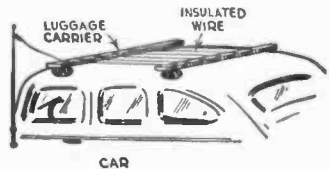• An auxiliary aerial for trips, when you are away from broadcasting stations, can be added to your car radio if you



have a luggage carrier on top of your car. String an insulated wire back and forth between carrier crossbars and attach one end to regular aerial with a small clip.—W. H. McCLAY.

MATERIALS LIST—LOOP CRYSTAL SET

- 1 $5\frac{1}{2}$ " x 9" x $2\frac{1}{2}$ " cigar box
- 1 365 mmfd. variable condenser, single gang, any good make. The one used by the writer was made by Insuline
- 1 Sylvania 1N34 germanium diode, or any other sensitive crystal
- 60 ft. No. 24 or 26 enameled or double-cotton-covered magnet wire
- 3 post-type binding posts or Fahstock clips
- 3 soldering lugs
- 4 small rubber bumpers
- 1 Bakelite knob or tuning dial for $\frac{1}{4}$ " shaft

Draftsman's Tape Holds Tight

• Draftsman's tape makes an excellent "third hand" to hold electronic components together during assembly or soldering. Due to its high insulation, the tape can be left on permanently.

What Every Young Man Should Know—

About Printed Circuits

AS THE radio and TV industry turns more and more to the use of printed circuitry, the experimenter will eventually have to tinker with, or repair, such sets.

Figure 4 shows a popular four-tube superhet table receiver using a circuit that is more or less standard with the industry. Figure 5 shows a hand-wired set which employs the identical circuit. Note the confusion the latter presents compared to the neat underside of the set with the printed circuit board.

A printed circuit starts on the drawing board. First the positions and mounting holes for the individual components are determined, then a drawing resembling a modified peg board is sent to the tool and die maker who creates a punch and die set which will pierce the necessary holes in the panel of phenolic plastic.


Using a copy of the initial drawing, the draftsman next draws in a series of heavy lines connecting the various component holes. This drawing resembles a puzzle maze. Note in Fig. 4 that no paths cross each other on the underside

As more and more manufacturers turn to high-speed production, where radios almost wire themselves, you may wonder how it's done. Or worse—how it can be redone. Despair is changed to easy repair with these tips

By THOMAS A. BLANCHARD



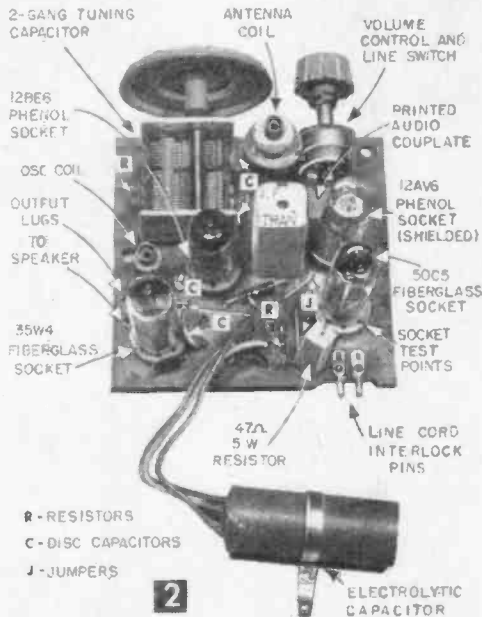Many printed sets are vertically mounted in cabinet and slide out for quick circuit repair. Note that a fine-tip pencil iron, not over 40 watts, is used to prevent wiring damage.




A typical "printed" circuit four-tube superheterodyne showing top of chassis. Note set is complete except for attachment of speaker and line cord. Strap of electrolytic capacitor is secured to a speaker mounting screw in cabinet.

of the board. Where a B- lead must cross a B+ path, a small wire jumper is inserted on the top of the board to complete the circuit.

The drawing is turned over to a photographer for copying. The photographer first produces a regular negative. This film is then printed on another film or reversed in development, to get a positive transparency. This positive copy goes to the silk screen printer.

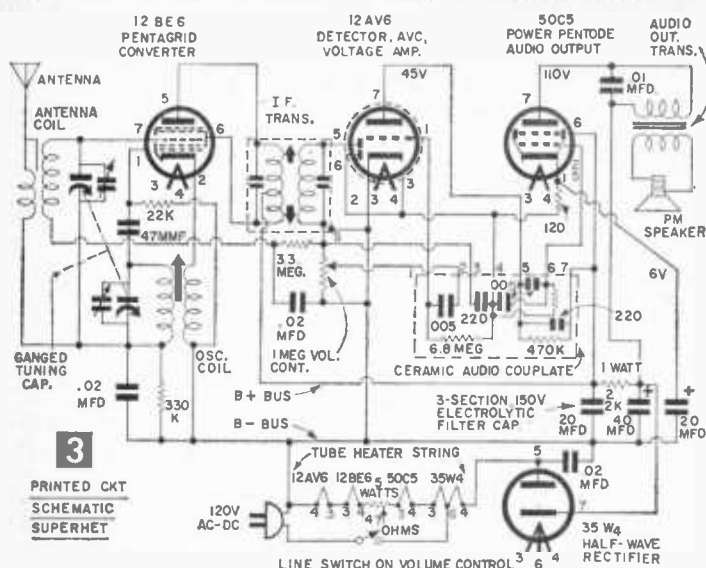The printer mounts a piece of fine Swiss silk in a printing frame, coats the stretched silk with a photographic light sensitive emulsion and al-



lows the silk to dry in the dark. Next the positive film is placed in contact with the sensitized silk and exposure made in a bright light, then the silk is developed just the same as a photograph.

Development creates the printed wiring image on the silk screen. The emulsion has washed out of the silk where maze lines appeared, the background has filled in solid. The silk screen is now mounted in a suitable press and a phenolic wiring board is placed underneath. A squeegee now passes over the silk screen forcing a special conductive paint through the tiny weave openings in the silk. When the silk screen is lifted the plastic panel bears an exact reproduction of the draftsman's original drawing.

The conductive paint is graphite in a suitable vehicle. Experimenters can purchase this paint in any radio parts house under the trademark "Tube Coat" (General Cement Div., Textron, Inc., Rockford, Ill.)

When the phenolic board has dried, it is transferred to a copper electroplating bath. Here a thin film of metal is deposited on the graphite paint, while the rest of the board remains blank. (In some instances the vapor vacuum plating technique is employed to deposit the copper, but the end result is the same.)

The printed circuit is now finished. The plate may be buffed or blast-tumbled with sawdust to

polish the copper image. Next the board is fluxed and protected from damage at the same time by spraying with rosin dissolved in alcohol. The printed boards may now be moved on to the assembly department. The assemblers are sometimes human, but more often automatons.

Resistors and capacitors in printed circuitry are identical to those used in usual radio assembly. Items such as coils are fitted with tubular pins instead of the spade type soldering lugs. Tubular pins replace lugs on IF transformers, tube sockets, etc. Since the wiring board has been punched, assemblers simply push each component into its proper position on the "peg board" layout.

With all components in place, the board is dipped into a tray (soldering pot) of molten solder consisting of 60% tin and 40% lead. It is removed immediately and given a momentary blast with a CO₂ (liquid carbon dioxide) gun which instantly sets the solder. In one fell swoop all parts have been rigidly secured to the wiring board and all connections and conductive paths completed.

There now remains only the matter of sliding the printed chassis into the cabinet, attaching knobs, and hand soldering the output transformer which is mounted on the speaker frame. Because of uniformity of design, tuning capacitor, oscillator coil and IF transformers are often prealigned so that

the receiver is immediately ready for shipment to the dealer.

Servicing a printed circuit is easier than working on the old metal chassis construction. Hidden breaks in hookup wire have been eliminated. All wiring is in clear sight, moreover many circuit boards have voltage measurement points and other identifying data printed along with the circuit. Cold circuit joints are practically unheard of. Failure of the set will be in an easily accessible component located on top of the board.

In regular wiring, wafer sockets carrying rectifier and output tubes often char because of the intense heat such tubes produce. The printed circuits employ wafer sockets fitted with eight supporting pillars. Because the sockets provided for hot tubes such as the 35W4 and 50C5 are a fiberglass laminate, socket charring is eliminated.



A single dipping into molten solder secures all components to wiring board and establishes the printed wiring paths which resemble a puzzle maze.

These pillars serve a dual function, since measurements can be made from the top of the socket without removing the tube from the set (see Fig. 2).

Most printed circuit receivers contain printed circuits within printed circuits. For example the complete resistance/capacitor network for the audio amplifier is contained in a small ceramic plate fitted with seven pigtail leads or soldering pins. A breakdown of a component in such a couplate or audet does not always require replacement of the entire unit unless the trouble is a short circuit. Locating the open capacitor or resistor, you need only jump it with a disc capacitor or small composition resistor as the case may be. Dotted area of schematic Fig. 3 shows the tiny couplate and its built-in components.


To replace a defective part on the circuit board, here is a simple and sure method: If a disc capacitor or composition resistor is involved, clip the pigtail leads as close to the component body as possible. Small diagonal wire cutters are the best tool for this. Because circuit boards may contain unused holes, and since some components contain more than two leads, apply a drop of nail polish or model plane dope to the wiring board prior to cutting out the defective part, to identify the holes from which the bad part is being removed. A toothpick makes a good applicator.

With the defective components removed, apply a pencil type soldering iron to the underside of the circuit board and pull out the clipped pigtail from the top of the board with flat or needle-nose pliers. With all pigtails removed, the next step is to open the clogged solder holes in the printed circuit.

For this you'll need a metal probe to which radio solder will not adhere. One such metal is stainless steel. Now, while you can buy a probe for \$1 from any parts supplier, you can get six probes for a dime at your local hardware or dime store. These bargain probes are "Fowl Lacers" used to keep the stuffing in the Thanksgiving turkey.

Again applying the pencil soldering iron to the underside of the board, insert one of the stainless steel pins into the clogged hole and twist as the solder softens. Remove the iron and slowly remove the pin. A neat open hole is the result.

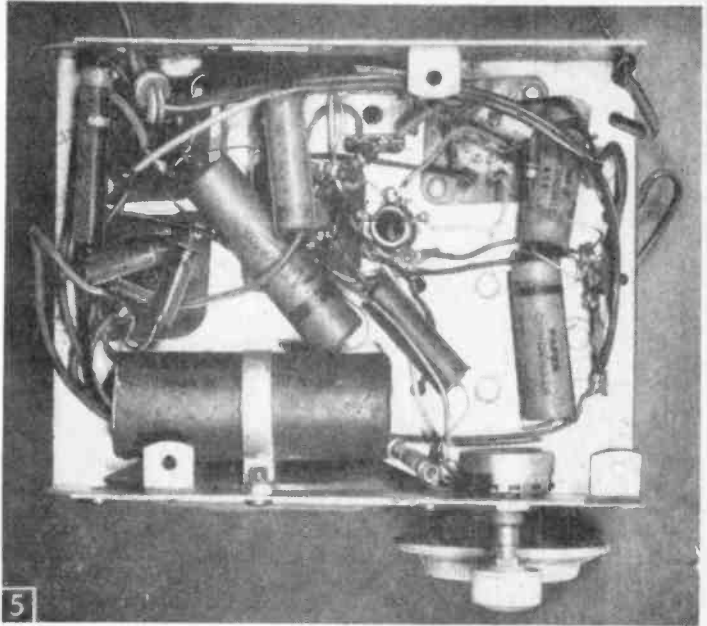With all holes cleared in this manner, you need only insert the new component and resolder the underside of the circuit board. Here a word of caution is in order. Do not use dime store solder, nor use a soldering gun, nor any other heavy-duty iron. You need a 60 tin-40 lead solder alloy



Underside of a four-tube set with hand-wired components and conventional metal chassis. Its circuit is identical to that of the printed set, but note the "jungle" of parts.

such as Kester's "Resin-Five" or Alpha's "Tri-Core." The iron should have a fine tip.

Since solder carries most of the current load in a typical printed radio circuit, you want to melt only the center of the circuit path. When a new part is being installed, hold the iron steady, allowing the solder to form a molten puddle at the joint. At this point, merely lift the iron away from the connection and allow the joint to cool while avoiding any jiggle of the component which could result in a "cold" bond.

Most printed circuits feature interlock cord sets such as are found on TV sets. This is to insure safety since all ground returns may be live except for the tuning capacitor and volume control shafts which are kept at a safe potential through a capacitor/resistor ground return. With so much exposed wiring, plus a direct ground on the IF transformer cans and detector tube shield, never work on line-powered sets on a metal table, or in rooms with concrete floors, since dangerous or fatal shock could result through carelessness.

When chassis is connected to line, be sure the bench or table is clear of small tools, wire, or solder. Such items shorting on the printed circuit can result in its utter ruin before the power line fuse has a chance to blow.

Removing Lock-In Tubes

- To remove a "Lock-In" or octal tube with ease, push against the side of the tube with a thumb while pulling gently upward, so as to un-snap the locking arrangement. Sockets for these tubes have spring catches which prevent tubes from falling out during shipping or rough use in portable receivers.



Tune in on the World

By C. M. STANBURY II

THE development of radio has given us a wonderful medium for vicarious travel. However, the average listener hears only what his local AM, FM and TV stations care to broadcast. Only when you make full use of your equipment and ears does the *magic* dimension of radio come into play. Such application of ears and equipment is known as *DXing*—distant reception.

Via DX you can move throughout the country learning about people and happenings. The only price is patience and a reasonable amount of equipment and know-how. Your table radio will do for a start; once you decide what you want you may purchase or build more.

There is an element of skill in DXing. In 1920 the reception of KDKA Pittsburgh in New York was a feat. A few years later the same listener was shooting for the Pacific Coast and beyond. He didn't stop until the globe was circled, and today this same pioneer is tuning for the moon. There are as many challenges as there are bands. Colombia on the standard broadcast band is DX. On the short-wave band it's routine. If you saw it on your TV, you'd be one tremendous DXer. Table B shows all the bands of the radio spectrum. However, most of the dividing lines are purely arbitrary, one band shading into the next. Major exceptions are the medium-wave broadcast band and the FM and TV broadcast bands. Like conventional means of travel, each band has its own advantages. And for every individual personality, taste and temperament, there is at least one that is "right."

Early Broadcasting. Radio broadcasting became possible when De Forest invented the vacuum tube, although earlier there had been the dots and dashes of *spark-gap* transmitters. It was just one step from the vacuum tube to voice transmissions, broadcasting and KDKA. Both KDKA in Pittsburgh and WWJ Detroit claim the first broadcast, but KDKA was first licensed. With the licensing of these stations in 1920, the dash into broadcasting was on and radio's golden era had begun. The twenties were an era of newness for the sake of newness, and radio was of a piece with the era. It caught the public's fancy, and its continual expansion kept its fans enthusiastic, even rabid. Every radio listener was a DXer—even those with local stations to listen to hunted distant calls. Stations took on the character of their locale. Those like WEAJ New York acquired sophistication, while rural broadcasters took on a neighborly air. A famous rural broadcaster was Henry Field's KFNF Shen-

endoah, Iowa. Field, realizing the great selling power of his battery-operated pioneer, transformed it into a general store of the air. "I don't know if they're any good but you try them out and let me know," he would say, and whether the product was dried prune or automobile tires, the entire shipment would be sold within 48 hours. The DXer was soon able to shoot for the West Coast, for in 1920 California boasted of KNX and KGER; Seattle, of KTW.

Like everything else in the Jazz Age, radio was wild. The Federal Radio Commission licensed, but the stations chose their own frequencies. Many stations tried several channels before settling on one, only to find that some nearby competitor was camping on the same wave-length. Station WHT in Chicago used two channels, switching from one to the other at 9 p.m. Adding to the complexity and confusion of the game were outlaw stations which were hard to trace. In 1928 the chaos was complete as the FRC was declared null and void. During that year every station did as it pleased.

Despite the anarchy, many stations were on the air to stay. In California, KNX, KFI, KGO, KLLX, KYA, KMJ, KXO and KFSD; in Washington, KTW, KHQ, KJR and KGY; in Iowa, KFNF. Some of the eastern pioneers were Baltimore's WCBM, WGY Schenectady, WOR New York, WNAC Boston and WSM Nashville. Also founded in 1927 was the Newark News Radio Club, sponsored by the *Newark Evening News*. In 1928, Irving Potts, president then, as now, of the NNRC,


TABLE A—RADIO CLUBS

American Ionospheric Propagation Association, 360 Zimmerman Blvd., Kenmore 17, N. Y., Covers TV only.
National Radio Club, 325 Shirley Ave., Buffalo 15, N. Y., Covers standard broadcast band only. Publishes <i>DX News</i> which is issued weekly during fall, winter and early spring. Annual dues are \$4.
Newark News Radio Club, 215 Market St., Newark 1, N. J. Monthly bulletin contains sections on all branches of DXing. Annual dues are \$4.
Universal Radio DX Club, 109 Mesa St., Vallejo, California. Devoted primarily to short-wave. Annual dues are \$4. Publishes <i>Universallite</i> , which includes experimental space section.

inaugurated a series of DX programs over WOR attracting widespread attention to the club.

The party was over in 1930. The nation had a king-sized hangover. The effect on radio should have been catastrophic, but it wasn't. Despite the fact that numerous stations went broke, radio hung on. For with a twist of the dial, a man could become top dog, champion. For a few hours the depression ceased to exist.

DXers competed in trying to log the most stations. Of the many radio clubs organized during this period only two remain: the National Radio Club and the Universal Radio DX Club. Normally, standard broadcast band (BCB) stations are not heard at a great distance, but on a morning in 1932 scores of night-owls heard a cricket match. Some logged it as *Poste Parisien* while others claimed it to be Rockhampton, Australia.

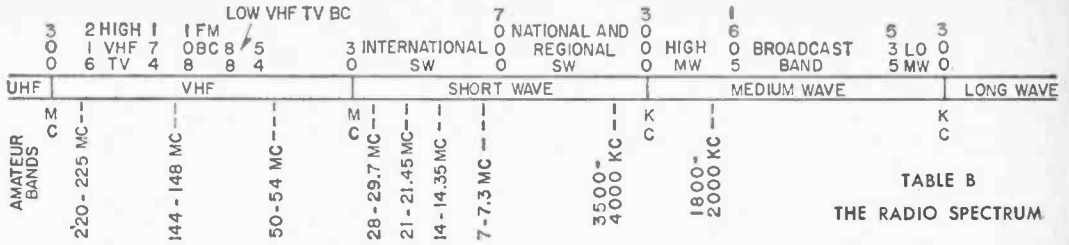

Verifications were received from both stations—at first Poste Parisien had been heard carrying a wire broadcast of the match. Later when the European station had faded out, Australia was heard with an on-the-spot description of the same match. When verification of reception established the validity of both sides' claims, the practice of collecting verification cards and letters became almost universal—the cards evidenced the listener's accomplishments and provided the souvenirs that every "tourist" collects. Completing the winter of 1932-33, DX's greatest season, the NNRC scheduled its second historic DX broadcast, a test from LR5 in Buenos Aires. It was a great success—every listener who tried heard LR5.

The Broadcast Band Today. DX permits you to escape the limits of your local stations. If you're a sports fan, the number of baseball, football and basketball broadcasts available to you will be tripled via DX. Those interested in American folk music will be trying for such stations as WAOK in Atlanta, Georgia. Most of the music played by WAOK is the folk or popular music of the southern Negro, sometimes referred to as rhythm and blues. Similarly, many stations such as WVOK Birmingham specialize in hillbilly tunes. When disasters occur, stations in the disaster area reflect the emergency. DXers are able to listen in.

Examples of broadcast band DX, and others, may be heard on an ordinary radio. Some BCB DX may be had around sunset and during the evening. The first period will produce brief reception from a large number of stations. This is accomplished by tuning to a channel used primarily by daytime stations and catching them as they sign off. Such a procedure will boost total of stations heard and verified, but it doesn't provide very interesting listening.

For best results you should listen between 1 and 6 a.m. Most stations are off during this period leaving four excellent sources of DX: 1) a number of stations operating all night and, because of the comparatively clear channels, easily heard at a distance; 2) stations further west which sign off later; 3) stations conducting equipment tests and frequency checks; 4) and stations which sign on before others of their channel.

A greater challenge is offered by attempting reception of foreign stations on the broadcast-band. BCBers have battled static, interference from U. S. and Canadian stations and ridiculously weak signals, to come up with such faraway locations as French West Africa, Russia and Aus-

This chart shows the frequencies allocated to all the commercial broadcasting media. From right to left, these allocations are: Standard Broadcast, 535-1605 kc.; National and Regional Shortwave, 3000-7000 kc.; International Shortwave, 7000 kc. to 30 megacycles; Very High Frequency Television, 54-88 mc. and 174-216 mc.; Frequency Modulation (FM), 88-108 mc. The Ultra High Frequency Television band begins at 473 mc., off the left side of the chart. Amateur band frequencies are also shown.

tralia. Best listening periods here are the early evening and after midnight. Ordinary receivers will usually not do—a communications type set is needed for best results.

International Broadcasting. Like the pioneer international wireless telegraphy, the first international broadcast stations used long-wave. The first was at Daventry, England on 187 kc. This station might compete with KDKA and WWJ as first broadcaster (however regular transmissions were not scheduled until 1922). The British Broadcasting Corporation attempted a North American service with the Daventry transmitter but reception was unsatisfactory.

Short-wave was known in the twenties but was not considered of practical use. In India and the islands which now comprise Indonesia, frequencies just above 3000 kc were used for local broadcasting. In this part of the world, static renders the broadcast band almost useless. Short-wave was carried on by experimental stations and culminated in a regular service by the BBC. Enhanced by the broadcasts of King George V, interest grew rapidly, enough to make it an unqualified success. Today, stimulated by World War II and world tensions, international short-wave broadcasting has greatly increased in scope. For more on this, see page 74.

International broadcasting plays a part in improving understanding among peoples. However, many short-wave services are carried on for political, religious or economic (sometimes an appeal to the tourist trade) reasons and are thus necessarily limited in depth and frankness. Similar to commercial broadcasting, there are both far-sighted and narrow-minded sponsors. As on the broadcast-band, you may use comparison but there are never two contrasting stations within the same country to compare. Thus, you can

TABLE C—BEST SEASONS FOR THE BANDS	
Long Wave:	Late fall and winter
Medium Wave:	Fall, Winter and early spring
Short Wave:	All year round
Very High Frequency (VHF) and Ultra High Frequency (UHF):	Late spring, summer and fall

TABLE D—VERIFICATIONS

In order for a station to verify your reception, you must give enough broadcast details so that your report can be checked. In reporting to *broadcast* stations, there must be a complete general description of the program heard. Much better than the general description, however, is the definite item system. Commercials, program name and announcer's name would all be definite items. Song titles will usually not do, however, since many stations keep no record of them. In verifying TV stations, visual descriptions are, of course, important. Always enclose return postage.

In reporting to *utility* stations you may *not* repeat specific details of communications heard. Instead, list date/time, frequency, station contacted or called and, in the case of a mobile facility, position if known. Many utility stations require the DXer to submit a prepared card for them to sign and mail back to him.

obtain a general picture of Europe or Asia but only a comparatively stilted view of individual countries and their people. You can get closer to a country by tuning in on programs intended for home consumption (usually below 7000 kc) or for nationals abroad. Unless you have command of a second language, however, you'll be limited to English-speaking countries. Another way of penetrating the gloss is by concentrating on programs featuring folk music. The imperfections of short-wave are countered by its availability—you can hear stations at any hour of the 24.

Police and Other Utilities. Broadcasting stations occupy only a tenth of the short-wave bands and only two-fifths of the medium-waves. With the exception of a few narrow amateur bands, the rest of the bands are assigned to *utility* radio services—ships, aircraft, airports, police and coast guard. This is the most potentially revealing of all radio listening. The authentic bits of life you overhear come straight. These are men going about the business of living, and you are a completely invisible observer. The aeronautical channels are a source of rare countries—8845 kc will produce such places as Kuwait and Bahrain, Arabia. Other faraway countries can be heard via aircraft passing over them.

VHF and UHF. Distant reception on medium-wave and short-wave is made comparatively consistent by the ionosphere, a layer of gases extending from 50 to 250 miles above the earth which are affected by ultra-violet radiation from the sun. The ionosphere reflects and refracts medium and short-waves back to earth thus making distant communications possible. As frequencies above 30 mc aren't normally reflected by the ionosphere, reception over 30 mc does not extend much beyond the horizon. Occasionally, however, DX is made possible via an upward extension of ionospheric effects, or special conditions in the troposphere. The long periods of nothingness punctuated by bursts of exciting reception give this brand of listening a flavor all its own. For high-frequency DX you need the proper antenna—it should be the right length, directional, and mounted on a rotor. To find the proper length

for FM antennas see the article on page 136.

America's pioneer FM station, in Alpine, N. J., went on the air in 1938. The first commercial FM station on the air was WSM-FM in 1941, now off the air. Cultural offerings are standard on FM. FM, a high fidelity sound system, is ideal for the reproduction of classical music and this music is widely broadcast on FM. Because of the audience it attracts, other intellectual features such as literary reviews are made commercially feasible. During a DX opening you will have your choice of many stations.

Television. Almost simultaneous with the discovery of radio itself, men became fascinated by the prospect of transmitting pictures to distant points. The first commercial VHF TV station WNBT (now WRCA-TV) opened in 1941. Because of high production costs, most broadcasters



TABLE E—RECEIVERS

For best results on any band, a communications type receiver should be used. These are priced from \$75 up. The major manufacturers selling to the general public are as follows:


- Hallicrafters Company, 4401 West 5th Ave., Chicago 24, Illinois
- Hammarlund Manufacturing Co., 460 W. 34th St., New York 1, N. Y.
- National Company Inc., Malden 48, Massachusetts

These companies will furnish information upon request. When purchasing a receiver, these features should be considered: Frequencies covered and in how many bands (the more the better), sensitivity and selectivity, including crystal selectivity. (The latter is essential in foreign BCB DXing.)

stick closely to established program formula, as gambling or experimenting is too expensive. A few misses and the broadcaster would be out of business. Thus 95% of American TV stations have similar programming. The polish possessed by the BCB outlet does not compare to that of his video cousin. The DX results of this are unmistakable: In comparison with the other broadcasting forms, the number of DX viewers is small, only FM attracts less. The largest TV DX club has 100 members. While most DXers have at one time or another tried for a distant TV station, usually their interest has been only a passing one.

The European TV scene is in startling contrast to the North American. With numerous different nationalities and national customs in close proximity, DX is very popular and the number of such viewers far exceeds those on this side of the Atlantic. This is surprising when you consider not only the language barrier, but that four different TV systems are used in Europe—which means a DX viewer has to make numerous modifications in his set.

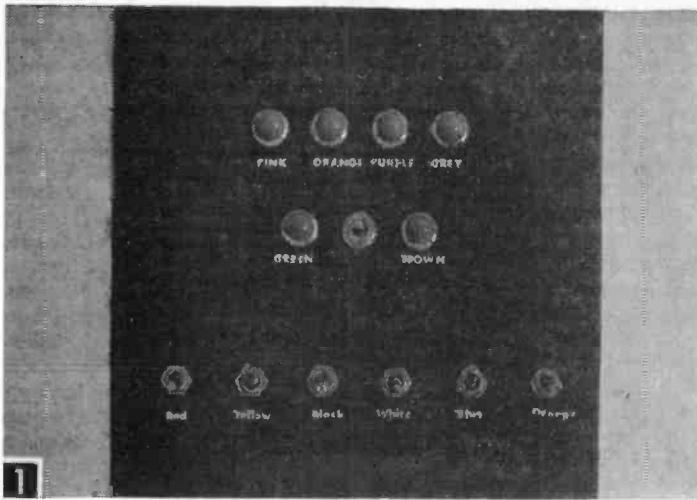Despite its present inadequacies, TV's potentialities are obvious. The possible uses and human benefits are endless. DX-wise, the future holds unlimited promise. As technological advances multiply, such potentialities will convert an increasing number of DX listeners to DX viewers.



Most commercially produced toys are either entertaining or educational, rarely both. Here's a toy you can make that is both, and inexpensive to boot.

- 1) Set On-Off switch to the Off position.
- 2) Set two color switches to the On position.
- 3) Set the On-Off switch to On. If the proper colors have been selected, the mixed color lamp will light.

How to Build. In a piece of 1/4-in. plywood, or other suitable material, bore all the holes necessary to mount the indicator lamp sockets and the toggle switches. Using the Fig. 3 layout as a guide for hole positioning, bore seven 1/2-in. holes to accommodate the toggle switches, and six 1 1/16-in. holes for the indicator lamp sockets.

Mount the indicator lamp sockets in the 1 1/16-in. holes so that all the terminals are aligned horizontally (see Fig. 2).

Electronic Color Wheel

By D. X. FENTEN and J. SCHACHNER



THE Electronic Color Wheel is entertaining, educational, inexpensive, and easily built. To light a lamp, two correct switches must be thrown. The lighted lamp is the color that would result if the colors indicated on the switches were mixed. If, for example, the red and yellow switches were thrown, the orange lamp would light. However, if two color switches are thrown that have no definite color combination, (red and green.) nothing happens.

Single- and double-pole, double-throw toggle switches are used to build the color wheel circuit. The second throw on each switch is used to prevent improper readings in the event that more than two switches are closed. However, despite the fact that the DPDT switches are incorporated to prevent incorrect readings, they are not infallible. Errors can occur. By closing a few select special combinations of three switches, for example, a lamp can be lit.

Consider the situation when the red, yellow, and blue switches are closed. Normally, no lamp should light. However, when the red switch is closed, its "lo" contacts close, (see Fig. 2), applying ground to both wiper arms on the blue switch. In effect, this jumps out the red 2c contacts. If the blue and yellow switches are now closed, the green lamp will light. In this manner, an erroneous indication can be overcome in either of two ways—expensive, complex circuitry, or following a simple set of rules of play. As:


- 4) to facilitate wiring. Mount the SPST switch in the middle row between the two lamps, the remaining switches in the six remaining holes on the bottom row. Reading from right to left, as in Fig. 2, the switches mount in this order:

HOLE	COLOR
1	Red
2	Yellow
3	Black
4	White
5	Blue
6	Orange

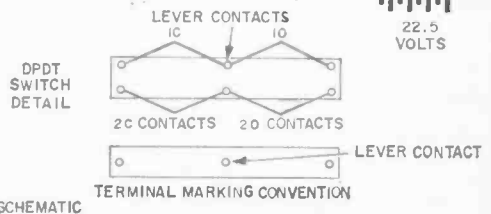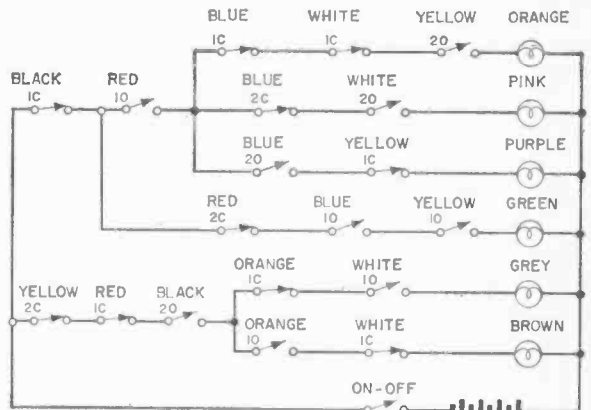

2

SCHMATIC

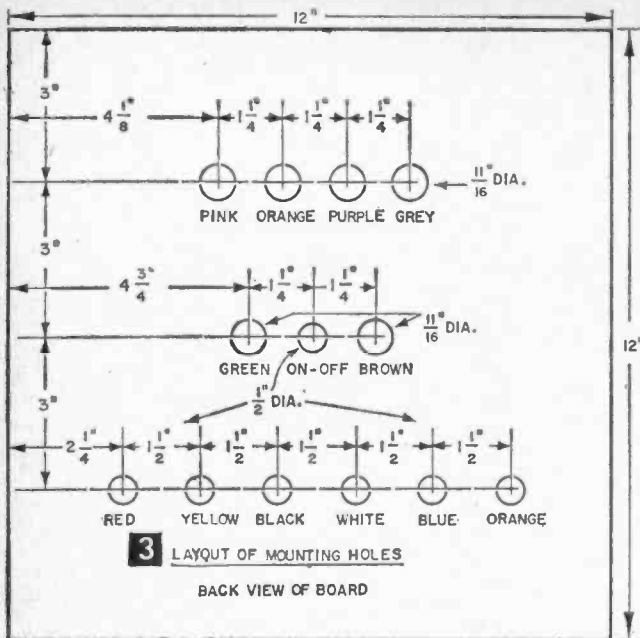

method, so a holder which is most easily installed should be used, or a home-made, improvised version designed and used.

The battery shown in Fig. 4 is a standard 22.5-v hearing aid battery. Simply mounted with two #6-32 x 3/4-in. screws and a strip of friction tape, it is easily replaced if necessary, and the mount is inexpensive and easily fabricated.

Solder the negative side of the battery to the On-Off switch and wire the 2c terminals of the red, yellow and black switches to the other side of the On-Off switch. Solder the common side of all the lamps to the positive side of the battery. The other terminal of each lamp is wired to the correct terminal of the color switches. When this has been completed, the control circuit—the switch terminals—is wired, completing the assembly.

Nothing remains but to turn a youngster loose on the wheel.


The switches, unlike the lamp sockets, mount vertically. This will place the "o" terminals on the top and the "c" terminals on the bottom, the "1" switch on the left, and the "2" switch on the right.


Now mount the battery on the lamp board. The mount will vary according to the size and type of battery used. Each of the many standard size battery holders has its own mounting

MATERIALS LIST—COLOR WHEEL

No. Reqd.	Description
1	1/4" x 1 x 1' plywood
6	DPDT toggle switches, without center Off position
1	SPST toggle switch
7	Indicator lamp sockets and lamps
6	indicator lamp jewels of the following colors: orange, pink, green, purple, grey, brown.
1	battery (can be either of several normally available, but battery voltage and the required lamp voltage must be the same; 6-v. lamps and a 6-v. battery, 22.5-v. lamps and a 22.5 battery, etc.)

Wiring in the switches.

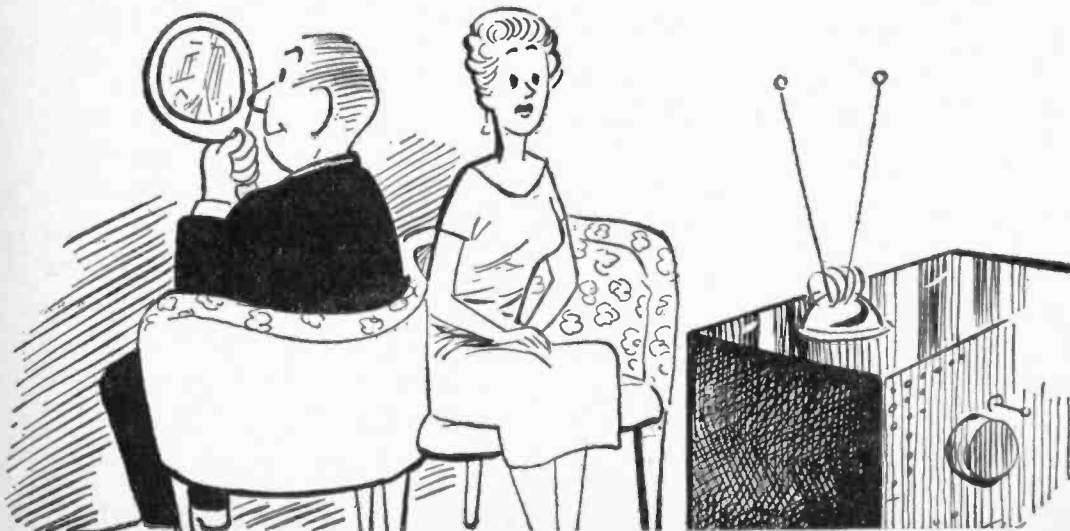

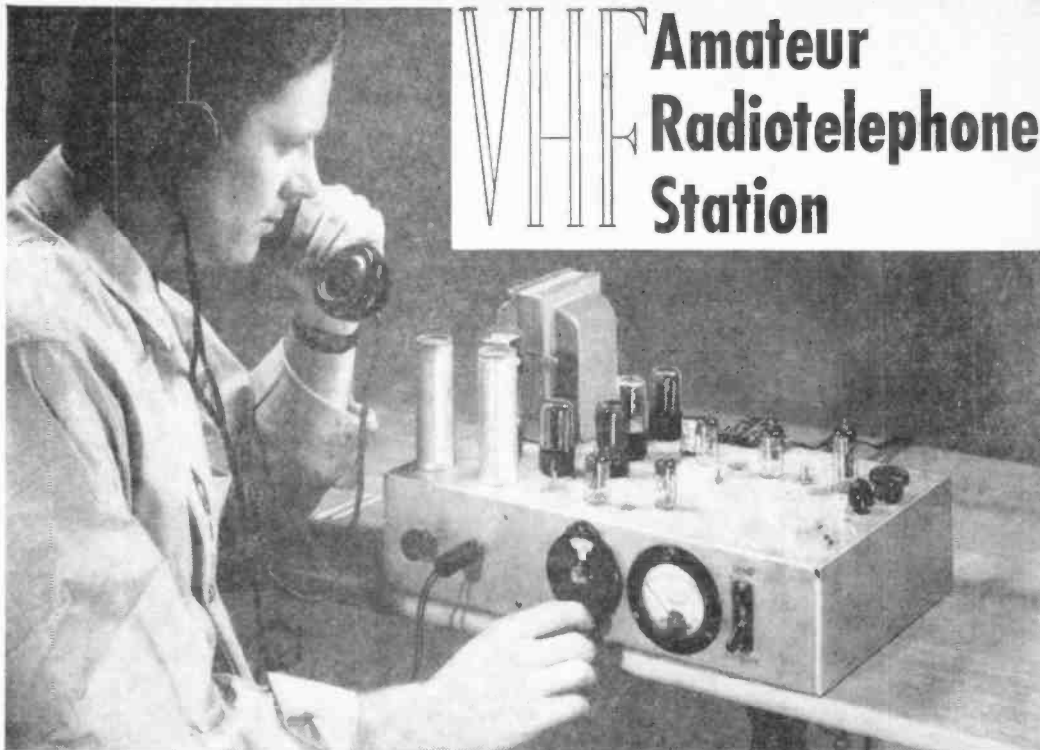

VHF Amateur Radiotelephone Station

The VHF amateur radiotelephone station in action. The operator is listening for an answer to a two-meter CQ.

By C. F. ROCKEY,
W9SCH

SELF-CONTAINED in a single chassis—except, of course, for antenna, microphone and headphones—this Very High Frequency transmitter-receiver operates in the 144 megacycle, two-meter amateur band. Probably as straightforward—and simple to construct—as a VHF station can be, its cost runs under \$60, less than one-fourth the cost of comparable, commercially made equipment. The receiver, tube for tube, develops maximum gain, has maximum sensitivity. It will easily receive signals from within and beyond the range of the transmitter; also, its efficiently engineered R.F. stage greatly reduces signal-radiation interference during reception. And, since all three stages of the transmitter are tuned to a different frequency, self-oscillation of a transmitter stage (with attendant off-frequency operation) is virtually impossible. No tricky “overtone” oscillator circuit, requiring hand-picked crystals, is used; no neutralization is necessary; there is no spurious signal output from the push-push final amplifier.

Construction of Power Supply and Receiver. On the 4 x 10 x 17-in. chassis, punch socket holes (Figs. 1 and 2) with 1 $\frac{1}{16}$ -in. dia. and $\frac{3}{4}$ -in. dia. socket punches (obtainable at electronics supply store) and mount the power trans-


former, rectifier tube socket, filter capacitors, filter choke coil, terminal strip, and volume control-power switch. (Mounting holes for the transformer are drilled from the data supplied by the manufacturer; tube sockets, filter choke and other station circuit components, except where otherwise indicated, are fastened to the chassis with 6-32 x $\frac{3}{8}$ -in. machine screws and nuts.)

Wiring for the power supply is shown in Fig. 3. (Figure 6 gives a pictorial wiring diagram for both receiver and transmitter sections.) Solder all connections with rosin core solder, checking connections at each step. When the wiring has been double-checked, connect a line cord to the proper terminals on the terminal strip (Fig. 1), insert the 5Z3 rectifier tube in its socket, plug the line cord into a power outlet and turn on the power switch. Now connect a d-c voltmeter from B+ to chassis; it should read between 300 and 400 volts. If it doesn't, check for faulty wiring or a defective tube and remedy or replace.

With the power supply working, mount and wire the send-receive switch (mount according to manufacturer's instructions; see Fig. 4 for wiring), the receiver's 6AG5 and 12AT7 sockets (with *rh* 4-36 x $\frac{1}{4}$ -in. screws) and the sockets for the receiver section's two 6SN7's. Then mount and wire the receiver's main tuning capacitor's

6

LEGEND			
A- 10MMF	D- 5000MMF	G- 47K	K- 330K
B- 50MMF	E- 2.2K	H- 100K	L- 1MEG.
C- 1000MMF	F- 22K	J- 220K	

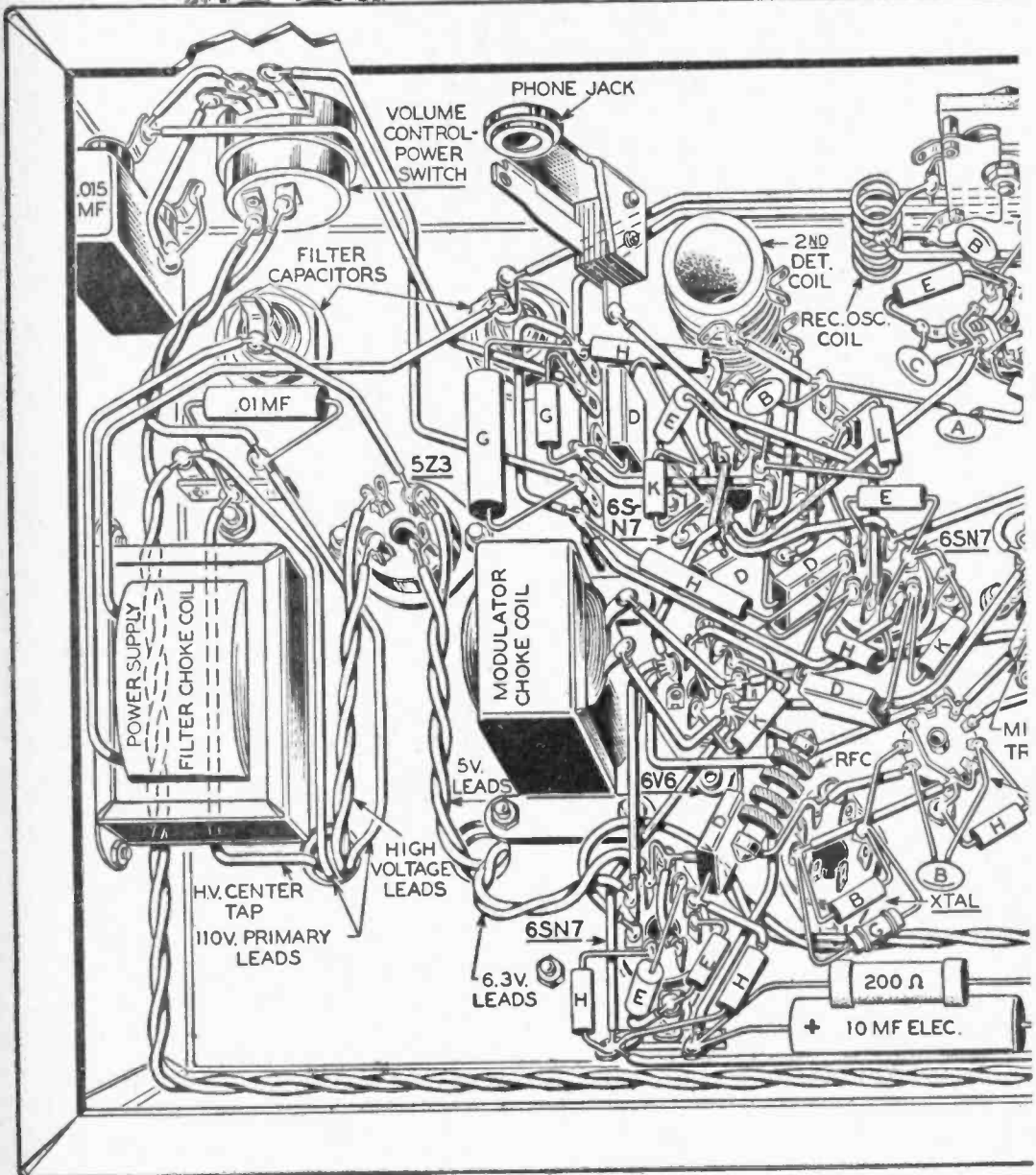


tion of the 12AT7 is soldered to the coil one turn from the ground end. When the R.F. amplifier, mixer and oscillator circuits are completed, apply power and throw the send-receive switch to the receive position. The tuning range for the oscillator, as indicated by a grid-dip meter, should be from within about 115 to about 132 megacycles. If the oscillator is not oscillating, look for shorts between tube pins or try a dif-

ferent 12AT7. If the oscillator's tuning range is incorrect, squeeze or spread the oscillator coil turns slightly until the correct range is obtained.

When the oscillator is working correctly, plug the headphones into their jack, adjust the volume control for a good, strong hiss, set the grid-dip meter for 145 megacycles and place it about 10 ft. from the set. Now tune the main tuning dial on

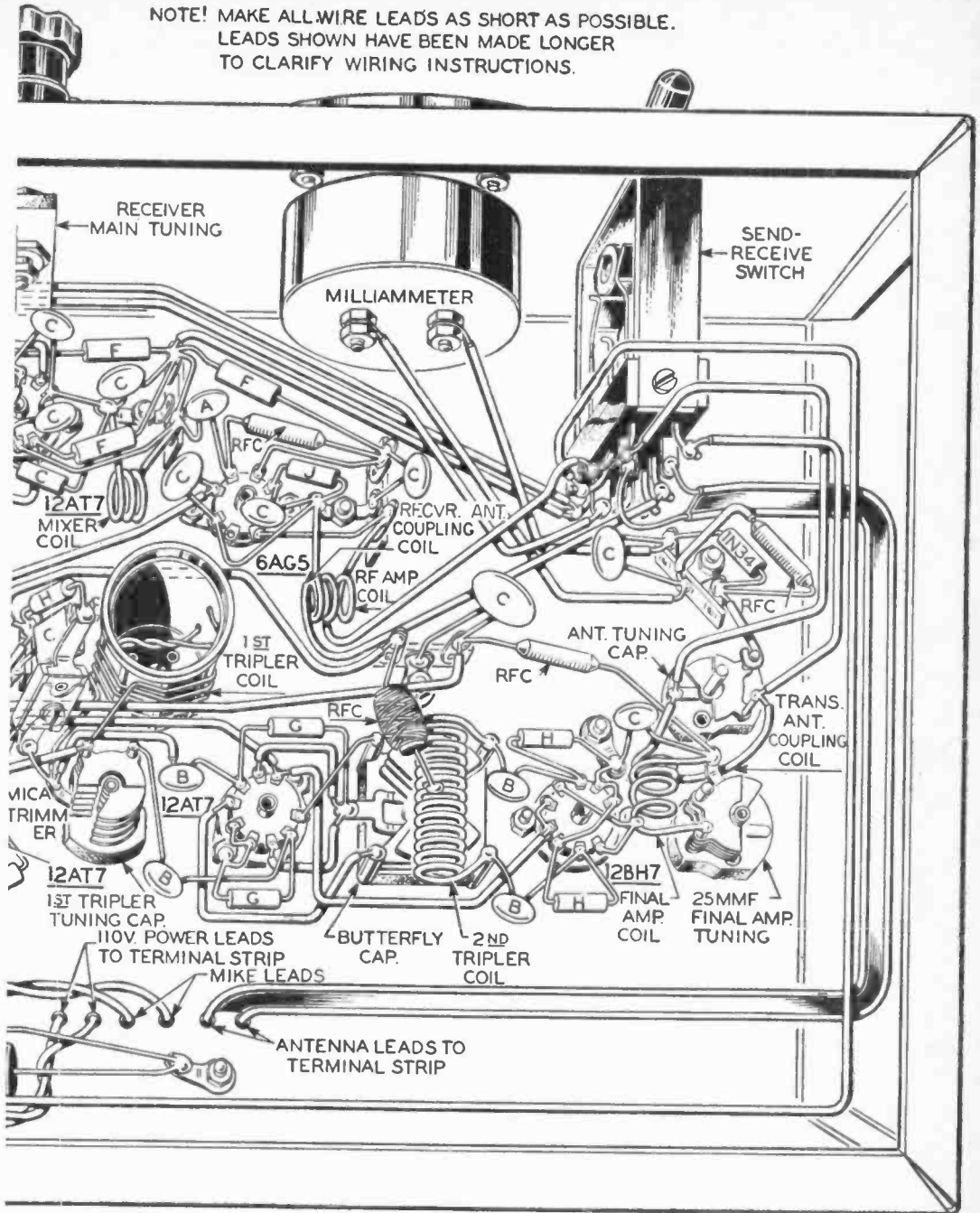NOTE! MAKE ALL WIRE LEADS AS SHORT AS POSSIBLE.
LEADS SHOWN HAVE BEEN MADE LONGER
TO CLARIFY WIRING INSTRUCTIONS.




the receiver throughout its range. At some point on the dial the hiss should disappear. Turning the grid-dip meter off should cause it to reappear. If it does, the receiver is operative. If it doesn't, you'll need to recheck the wiring in the mixer and R.F. amplifier circuits only; the oscillator has been checked.

For test purposes, couple a dipole antenna (see Fig. 8) to the 6AG5 R.F. amplifier grid coil

by means of one turn of wire inserted between the two turns at the ground end of the grid coil. With the volume turned up, tune the main receiver tuning dial through its range. If there are radio-equipped taxicabs, mobile radio telephones, or other 144-megacycle amateurs operating within range of you, you should hear them.

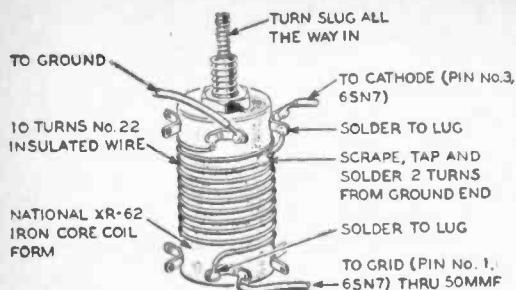Note that when a signal is tuned in, the hiss from the receiver tends to disappear and the



7 SECOND DETECTOR COIL
(WHEN WOUND, COAT WITH POLYSTYRENE CEMENT)

voice signal takes its place. The stronger the signal, the more completely the hiss will disappear. Slight readjustment of the volume control and slight retuning will often do wonders to clear up a weak signal.

Finish work on the receiver section by connecting the antenna coil leads of the 6AG5 directly to the appropriate connections of the send-receive switch (Fig. 4). Then run a short length of 300 ohm "twin-lead" TV lead-in line from the proper switch connections to the antenna terminals on the Jones terminal strip and connect antenna lead-ins to these terminals.

Construction of the Transmitter. Fasten tube sockets for the 12AT7's, 12BH7 and crystal (use 6-32 screws for the crystal socket, 4-36 for tube sockets) and mount the 50 mmf first-tripler tuning capacitor, the "butterfly" second-tripler tuning capacitor, and the 25 mmf final amplifier tuning and antenna tuning capacitors. Be sure that the 50 mmf and the 25 mmf capacitors are mounted with shafts insulated from the chassis. (Drill the shaft hole large enough to give the shaft ample clearance.)

First wire the crystal oscillator (see Figs. 6 and 9), wiring to any two alternate pins desired on the crystal socket. In the oscillator's plate circuit, RFC2 (Fig. 9) designates a National R-100 2½ mh R.F. choke.

Choose your crystal frequency according to the class of amateur license you hold. If you hold a general class license, any crystal frequency between 8.000 and 8.210 megacycles will do. If you are a novice, choose a crystal frequency between 8.032 and 8.132 megacycles.

When the crystal oscillator circuit wiring is completed, plug the crystal into the socket pins that are connected to the oscillator circuit. Apply power and throw the send-receive switch into the send position. Now, holding it by its glass envelope, touch the base of a 2-watt neon bulb to the plate connection (pin #1) of the 12AT7 oscillator tube. A faint but definite bluish-red glow of the neon bulb indicates satisfactory operation of the oscillator circuit. If no glow is observed, recheck the wiring or substitute a different crystal.


Next, wire the first tripler circuit. The first tripler coil is wound as shown in Fig. 10.

With the first tripler wired, apply power and

set grid-dip meter to about 24 megacycles. Hold the grid-dip meter coil near the tripler coil and adjust the 50 mmf capacitor until maximum output from the tripler is observed on the meter. This adjustment must be made with an insulated screwdriver to avoid shocks and to insure accurate tuning.

When a good, strong indication is secured on the grid-dip meter, insert the loop of the transmitter tuning lamp (see Fig. 11) into the first-tripler coil with the loop of the lamp parallel to the turns of the coil. When the lamp is inserted all the way into the coil, and the 50 mmf capacitor is readjusted for maximum tripler output, a noticeable glow of the lamp filament should be observed.

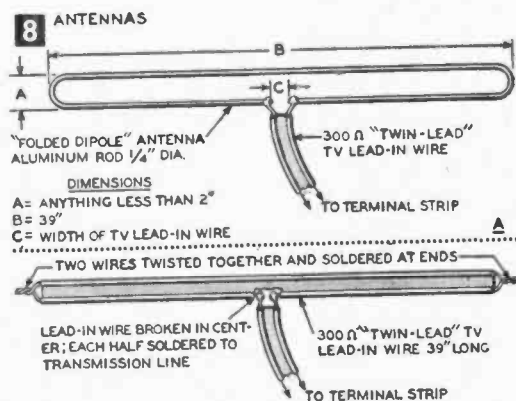Now, wire the second-tripler 12AT7. The second-tripler coil consists of 12 turns of #14 tinned copper wire wound on a ½-in. dia. form. Space the turns carefully to make the entire coil about 1¾-in. long, then remove the form. Connect this



A is superior for outdoor installations.

B is suitable for indoor or temporary use.


RULES FOR ERECTING ANTENNA

- (1) Keep it horizontal.
- (2) Keep it broadside to the directions you wish most to work.
- (3) Erect it as high above ground as possible.

coil between the two stationary sets of plates of the "butterfly" capacitor. Keep leads as short as possible.

The R.F. choke (RFC3) connected to the center tap of the second-tripler coil is made by scramble-winding 100 turns of magnet wire equal to or smaller than #22 around a 1 megohm, 1 watt carbon resistor. Solder the ends of the coil to the resistor leads, dope liberally with polystyrene cement, and solder RFC3 into the circuit.

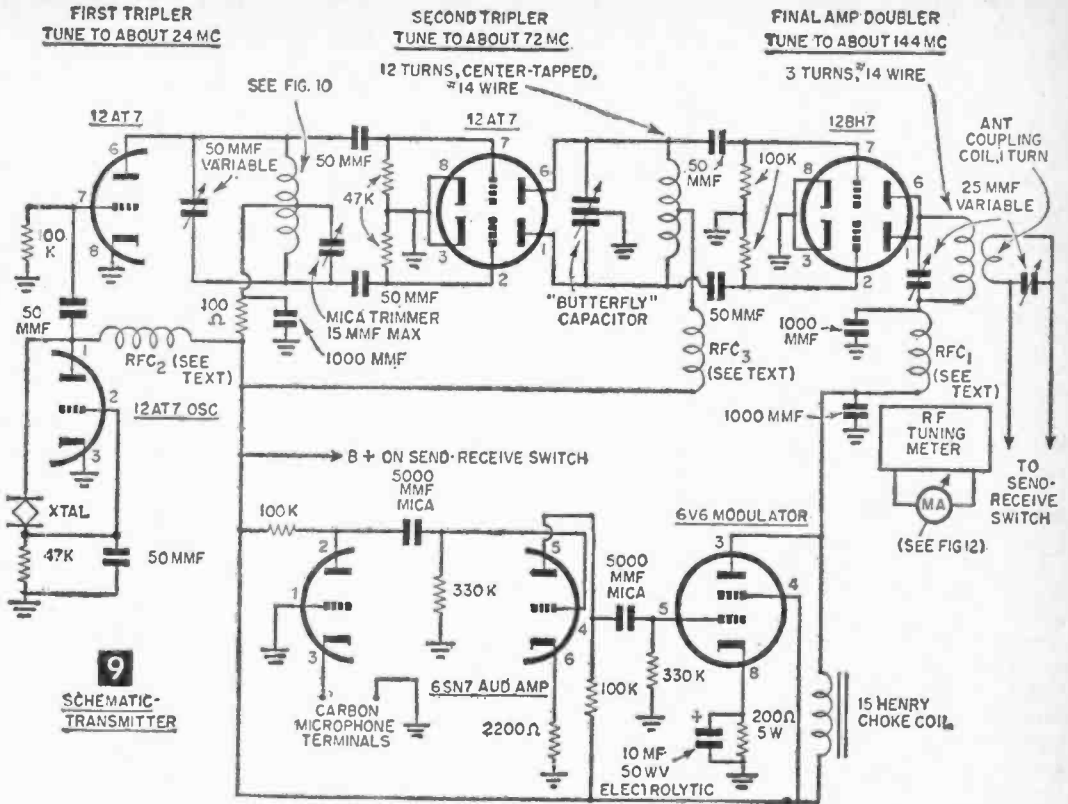Insert the 12AT7 in its socket and apply power. Tune the grid-dip meter to about 72 megacycles and adjust the "butterfly" capacitor for maximum second-tripler output. Then insert the loop of the tuning lamp between the middle turns of the second-tripler coil and readjust the "butterfly" capacitor for maximum second-tripler output. Then, using an insulated screwdriver, read-



9
SCHEMATIC-TRANSMITTER

just the first-tripler 50 mmf tuning capacitor until the tuning lamp (still in the second-tripler circuit) glows brightly. Now, adjust the first-tripler 15 mmf mica trimmer capacitor and the first-tripler 50 mmf tuning capacitor alternately, until the tuning lamp glows at nearly full brilliance.

The final stage of the transmitter's R.F. section to be wired is the push-push doubler final amplifier. It operates at the output frequency of 144 megacycles, so make every lead as short as possible. The final-amplifier tank coil consists of three turns of #14 tinned copper wire 1/2-in. in diameter. Space out the turns until the length of the entire coil is about one in., remove the form, and connect the coil across the final amplifier tuning capacitor. Keep leads to minimum length.


When the final amplifier is completed, tune the grid-dip meter to about 144 megacycles, insert the 12BH7 tube in its socket and, after the tube has heated, apply B+ by throwing the send-receive switch to *send*. Using the insulated screwdriver, adjust the 25 mmf final-tuning capacitor for maximum indication on the grid-dip meter and readjust the "butterfly" capacitor for maximum output at the final amplifier. Then insert the tuning lamp between the turns of the final amplifier coil. It should gleam brilliantly.

Finally, wire the audio amplifier and modulator. (RFC1 designates an Ohmite Z-144 VHF R.F. choke.) To test the audio amplifier-modu-

lator system, temporarily replace the 15 Henry choke coil in the modulator plate circuit with the primary of any loudspeaker output transformer and loudspeaker. With the microphone connected and the send-receive switch in the *send* position, speaking into the microphone should produce a loud, clear signal from the loudspeaker.

Now insert a single-turn antenna coupling coil into the final-amplifier tuning coil at the end farthest from the 12BH7 socket. Push it well down into the final-amplifier coil to obtain tight coupling and run its leads directly to the 25 mmf antenna tuning capacitor. From there, run leads directly to the proper terminals of the send-receive switch (see Fig. 4).

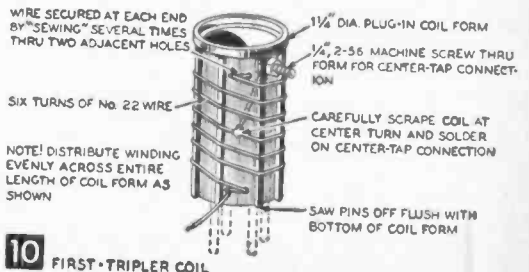Give the entire transmitter a final test by connecting a #48 dial lamp bulb directly across the antenna terminals on the terminal strip. With every component in the circuit and with the




10 FIRST-TRIPLER COIL

send-receive switch in *send* position, the lamp should glow brightly. Touch-up the various tuning adjustments for maximum brilliance of the lamp and then speak clearly and directly into the microphone. The lamp should flicker noticeably, indicating that modulation is taking place.


MATERIALS LIST—AMATEUR RADIOTELEPHONE STATION

Req'd.	Receiver and Power Supply
1	10 x 17 x 4" aluminum chassis
1	knob, 1/4" shaft
1	terminal strip, 6 terminal (Jones barrier 6-140)
6	8-prong sockets (Amphenol type MIP)
4	9-prong sockets (Amphenol, 59-410)
1	7-prong miniature socket (Amphenol, 147-505)
1	power transformer (Stancor type PC-8410 or equivalent)
1	filter choke coil (Stancor type C-1001 or equivalent)
2	can type electrolytic capacitors, 16 MFD 450 v.v. (Cornell-Dubilier, Type KR-516A or equivalent)
1	single circuit phone jack
1	Vernier dial, 0-100-0 scale (National type BM)
1	4PDT anti-capacity switch (Federal #1424)
1	50K linear taper potentiometer, with switch (50,000 ohms)
1	pair 2000 ohm headphones (Trimmi "Dependable" or equiv.)
1	phone plug
5 ft.	power line cord with plug
1	.01 mf, 400 volt paper capacitor
1	Ohmite Z-144 R.F. choke
8	1000 mmf disk type ceramic capacitors
8	50 mmf disk type ceramic capacitors
1	10 mmf disk type ceramic capacitors
1	1000 ohm, 1/2 watt composition resistor
1	220 ohm, 1/2 watt composition resistor
1	100K ohm, 1/2 watt composition resistors (100,000 ohms)
1	47K ohm, 1 watt composition resistor (47,000 ohms)
3	47K, 1/2 watt composition resistors (47,000 ohms)
2	22K, 1/2 watt composition resistors (22,000 ohms)
2	22K, 1 watt composition resistors (22,000 ohms)
5	330K, 1/2 watt composition resistors (330,000 ohms)
3	2200 ohm, 1/2 watt carbon resistors
1	100 ohm, 1/2 watt carbon resistor
1	1 meg., 1 watt carbon resistor
1	0.5 mf paper capacitor
6	5000 mmf mica capacitors, "postage stamp" type ceramic, iron core coil form (National type XR-62)
1	15 mmf midget variable capacitor (Hammarlund type HF15 or equivalent)
1	5Z3 tube
2	6SN7GT8 tubes
1	12AT7 tube
1	6AG5 tube
25'	#14 tinned copper wire
	flock-up wire, solder
	tube polystyrene cement
	tiepoints
	screws
	miscellaneous hardware
10"	300 ohm twin lead TV antenna lead-in wire
12"	#22 insulated magnet wire
	antenna materials, as desired
	Transmitter
2	knobs, 1/4" shaft
1	choke coil (Stancor type C-1002 or equivalent)
1	0-1 milliammeter (Triplet)
1	0.5 mf, 200 v. paper capacitor (Sprague or equivalent)
1	10 mf, 50 v. electrolytic capacitor (Sprague or equivalent)
2	Ohmite type Z-144 VHF RF chokes
1	2 1/2 mh RF choke (National R-100)
1	1 1/4" ribbed plastic coil form (ICA)
3	25 mmf midget variable capacitor (Hammarlund type APC 25 or equivalent)
1	50 mmf midget variable capacitor (Hammarlund type APC 50 or equivalent)
1	"Butterfly" type midget variable capacitor, 10 mmf per section (Johnson 11MB11)
1	1 1/2-15 mmf mica trimmer capacitor
1	1N34 crystal diode
1	quartz transmitting crystal, about 8 megacycles, see text (Petersen radio "PR" type Z2 or Bliley type AX-2)
1	6SN7GT8 tube
2	12AT7 tubes
1	12BH7 tube
1	6V6GT tube
2	#48; 2 v., 60 MA dial lamps
1	2 watt neon bulb
1	single-button, telephone-type microphone
1	2-lug tiepoint

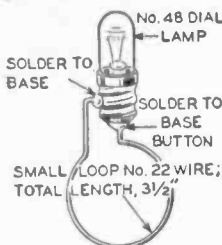The R.F. output meter (Fig. 12) assures proper tuning of the transmitter under all conditions. Fasten the 1N34 crystal diode, the RFC1 choke (an Ohmite Z-144) and the 1000 mmf capacitor to a two-lug tiepoint strip mounted near the transmitter antenna tuning capacitor. The 1 1/2-in. pickup lead should be brought within about 1/2 in.



11 TRANSMITTER TUNING LAMP

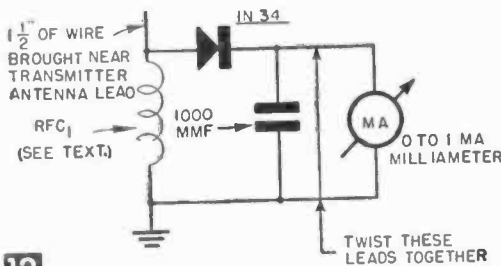

12 RF TUNING METER


of the transmitter 25 mmf antenna tuning capacitor and a twisted pair of wires run to the 0-to-1 milliammeter on the front of the chassis. Apply power, and throw send-receive switch to *send*. If the meter reads backwards, reverse the leads to it. Position the pickup lead so that when

the transmitter is operating and the antenna is properly loaded the meter reads about mid-scale. The transmitter may now be easily adjusted by tuning for the greatest meter reading.

Connect the transmitter to one of the antennas shown in Fig. 8, put the antenna as high and in the clear as possible and you're ready to go on the air. With a dipole antenna 25 ft. high, your range of communication will be around 10 miles; with a dipole antenna 50 ft. high, it will be about 15 miles; 100 ft. high will get you out 20 miles. With a high-gain directional antenna system, you can get out in excess of 100 miles under special atmospheric conditions.

Weatherproofing TV's Lightning Arrestor

• Does your TV picture get snowy nearly every time it rains? If your TV's lightning arrestor is located outdoors where it is exposed to the elements, signal loss may result when the arrestor becomes covered with rain. To prevent this, install arrestor in a plastic box with a tight-fitting lid. Cut holes in the side of the box to accept the lead-in wire; drill holes in the bottom to fit the arrestor's mounting screws.—**JOHN A. COMSTOCK.**

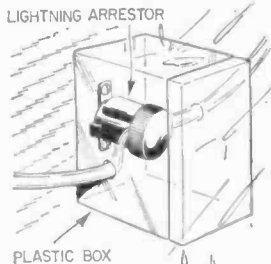



Press the key, and the signal plays through the radio speaker. When plug connecting accessory oscillator is removed (not shown in photo) radio functions normally.

Loudspeaker Code Practice Oscillator

For 50¢

Stealing power from a superhet radio, and playing through the speaker, this unit will also double as a tone generator

ONLY two main parts, a neon lamp and a resistor, plus the key and plug, are all that you need to build this oscillator. Not only is it handy for code practice, it also provides two full octaves of tone, for testing and experimental purposes.

The oscillator's operation is based on the neon glow relaxation circuit, principle of which is shown in Fig. 2. Such a circuit, while it has been popular for years, requires many more parts, and provides only earphone volume and tone. Our circuit (Fig. 3) actually drives a loudspeaker with lusty volume.

The minimum 90 volt d-c current required to excite the neon glow lamp in the oscillator circuit is obtained from the plate lug of the output tube of any small ac-dc radio. The other lead of the oscillator is connected to the first diode of the radio's detector tube. Since this diode is also the input of the voltage amplifier, the weak oscillator signal is therefore automatically amplified by the set's two audio stages and reproduced by the speaker. The wiring plan (Fig. 3) shows how to make the connections to the tube sockets of most popular radio sets. If you want to use an

MATERIALS LIST—CODE PRACTICE OSCILLATOR

No. Reqd.	Description
1	NE-2 Neon Lamp
1	220,000 ohm 1/4 or 1/2-watt composition resistor
1	3 5/8" long, 3/4" wide, 3/8" deep plastic box
1 pc.	spring brass, steel, etc.
1	7/8" dia. plastic garment button
4	3-48 x 3/8" long rh machine screws and nuts
1	subminiature phone plug & Jack (Lafayette MS-281 & 282)

earlier model receiver, simply check the respective diode and plate pins of the input and output tubes on a tube chart, and connect according to the tube base outlines.

The miniature phone plug and jack allow the oscillator to be connected to the radio set at will. When the plug is removed from the jack, the set again functions in normal fashion. Leads from the tube sockets to this jack should be as short as possible, and the jack must be fully insulated from the metal chassis of the radio, or a short circuit will result. On some sets, you may find that the hardboard back, to which the loop antenna is attached, is a convenient place for the jack, or drill a hole in plastic cabinet.

As a novelty, the code practice oscillator shown in Fig. 3, was built into a small plastic box, such as is used to package emery boards. The key was homemade of spring brass. The serious radio amateur practicing code for license examinations is advised to use a conventional type of sending key, since the "feel" of a solid key under the hand is important in learning speed.


Drill a hole in the plastic just large enough to pass the NE-2 neon glow lamp, cementing it in place with Duco cement. Shape the key by bending a strip of spring brass according to the plan.

The knob is a 7/8-in. dia. garment button.


The tone of the oscillator is determined by the setting of the receiver's volume control. If the key is held down, and the volume control rocked back and forth, an electronic siren effect will result.

If, instead, you alternately close the key, and vary the volume control setting, a musical tune will result, much in the manner of the "Uke-A-tron." This is an electronic musical instrument, described in S&M Radio-TV Experimenter, Volume 3 (#538—50 cents). And it demonstrates the basic principle of electronic organs.

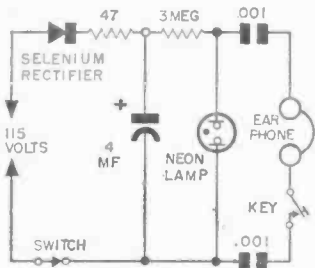Another interesting feature of the relaxation oscillator is that it not only provides an audible signal, but also a visual signal. Every time the key is pressed, the lamp fires with a bright orange glow.—
THOMAS A. BLANCHARD



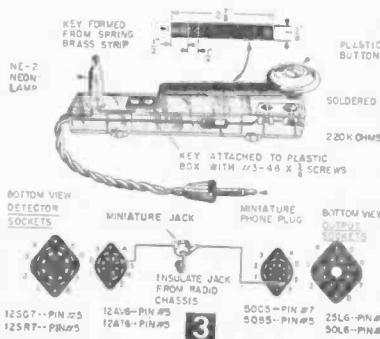
2 SCHEMATIC DIAGRAM (TYPICAL RELAXATION OSCILLATOR CIRCUIT)



3


Sound Down

By BERNARD DICKMAN
and
ALFRED LUCAS

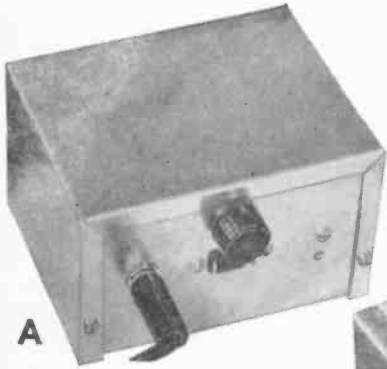

A

1

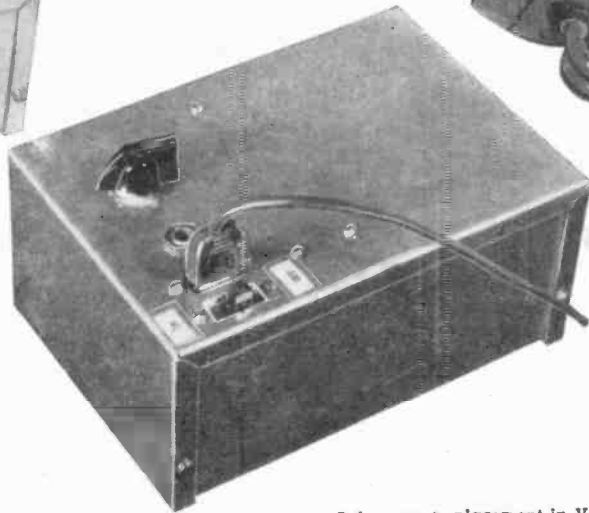

B




Micro-switch mounted at back of phone cradle controls sound dimmer on either version one (A) or two (B) of sound-down unit.

Below, parts placement in Version One.


HERE'S a device which will automatically turn down the sound on your television or radio set when you lift the telephone receiver. There are two versions, one of which can be built for less than \$10, the other for less than \$15. The first version (Fig. 1A), while it is the less expensive of the two, draws current from the battery all the time the telephone is in use. The second version (Fig. 1B), will draw current only the moment the telephone is lifted from or returned to its cradle.

Part layouts for the two versions are shown in Figs. 2 and 3. The value of the potentiometer is not critical; almost any good junk-box unit will do. Schematics are shown in Figs. 4 and 5. Note particularly the wiring of the micro-switch (S2). In both schematics it is shown with the phone in use. Switch S1, on the schematic for the second version (Fig. 5) is shown in position for use in turning the TV or radio completely off.

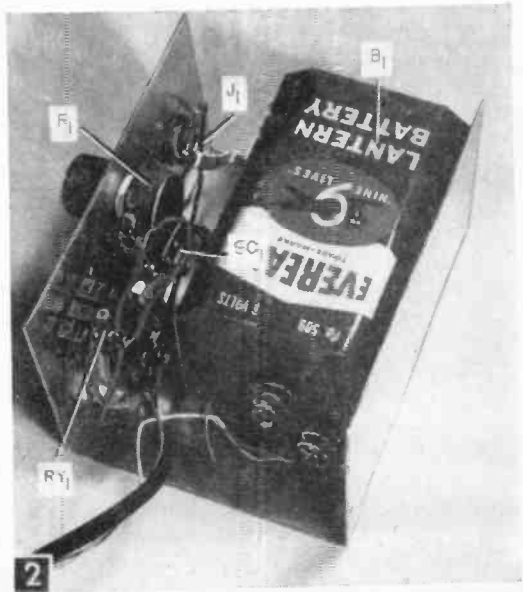After the unit has been wired, connect the micro-switch (Fig. 6) to the telephone. Press it tightly into position under the lip of the handhold of the telephone as is shown in Fig. 1. Pull




2

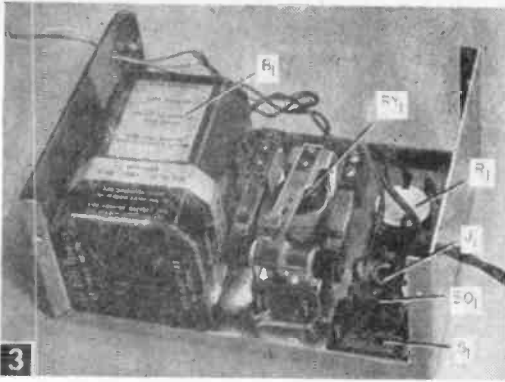


Parts placement in Version Two.

the radio turned on, adjust potentiometer R1 to the desired difference in sound from the TV or radio set. Then, when the telephone receiver is returned to its cradle, the sound will automatically return to normal listening volume. If either unit is plugged into the wall socket with the TV or radio line plug inserted into the ac chassis socket on the unit, the radio or TV will be turned off when the telephone receiver is off the cradle. The first version, in other words, can control a radio and a television set simultaneously; the second version can only be used for one function at a time. The first version controls in these two

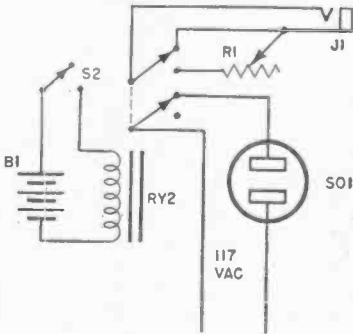ways: 1) with several ac chassis sockets added, several sets can be turned on and off; 2) with one set connected so that sound will be turned down and one set so that sound will be turned off, both radio and TV can be controlled simultaneously.





4 VERSION ONE SCHEMATIC

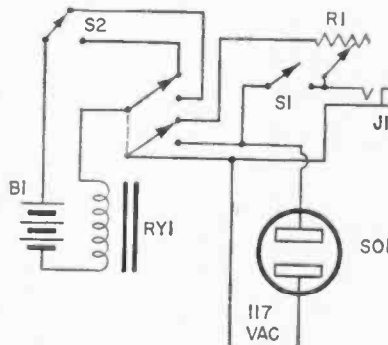

5 VERSION TWO SCHEMATIC

cotter pins tight while holding switch in position. Bend the leaf of the micro-switch around the arm rest. Test to see if switch makes and breaks contact when telephone receiver is lifted from and returned to cradle, then cut cotter pins to suitable length.

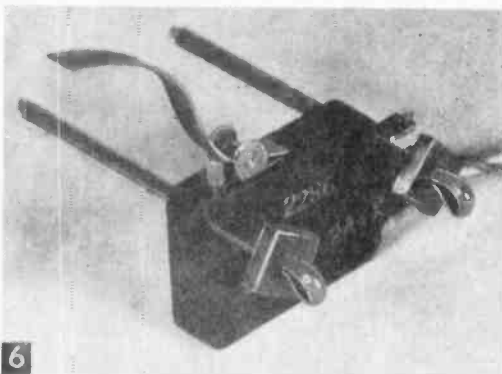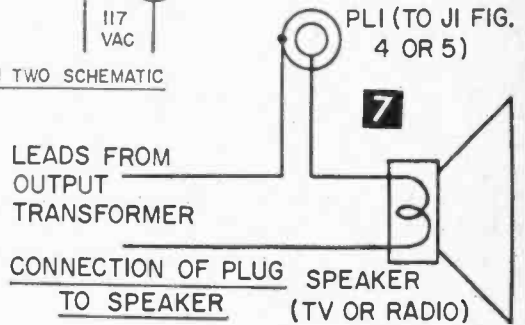To connect either of the versions so that they turn down the sound on a radio or TV, connect the phone plug in series with one of the speaker terminals of the set. The second version must never be plugged into the 117-v wall socket when it is being used with the phone plug. After turning switch S1 on, insert the phone plug into the jack on the unit. With the phone off its cradle and



6 Micro-switch with cotter pins and nuts ready for mounting on phone.

MATERIALS LIST—VERSION ONE	
Desig.	Description
B1	6-v lantern battery
J1	standard phone jack
PL1	standard phone plug
R1	0-100 ohm linear potentiometer (see text)
RY2	6-v dc, DPDT relay (Advance GHA/2C/6VD; Allied Radio 76 P 461)
S2	leaf actuated micro-switch (Acro 2CMD1-2AXX-A24; Allied Radio 35 B 030)
SO1	ac chassis socket aluminum case 3 x 4 x 5" (Bud Minibox CU-3005; Allied Radio 80 P 365) screws, grommet, line cord and plug, cotter pins, nuts (for cotter pins)
VERSION TWO	
B1	6-v lantern battery
J1	standard phone jack
PL1	standard phone plug
R1	0-100 ohm linear potentiometer (see text)
RY1	6-v dc, DPDT ratchet relay (Potter and Brumfield AP11D; Allied Radio 76 P 585)
S1	Single pole, single throw slide switch
SO1	ac chassis socket
S2	leaf actuated micro-switch (Acro 2CMD1-2AXX-A24; Allied Radio 35 B 030) aluminum case 3 x 5 x 7" (Bud Minibox CU-3008; Allied Radio 80 P 368) screws, grommet, line cord and plug, cotter pins, nuts (for cotter pins)



1 Oscillogram pattern of a full-wave, battery charger rectifier showing lower half-cycle, (lost in Fig. 4) inverted and above horizontal centerline, indicating it is being used.

Using an OSCILLOSCOPE

For diagnosing troubles in electronic circuits, the oscilloscope is as useful to the experimenter as the X-ray machine is to a physician

By HAROLD P. STRAND

THE oscilloscope is probably the most useful of all test apparatus commonly employed by electronic technicians and engineers. It can actually give you a moving picture of what is going on in a circuit by means of waveforms and traces on the face of a cathode ray tube. It can be used for many varieties of test, teaching and research work, such as signal tracing, peak-to-peak measurements, frequency measurements, and servicing radio and television receivers. One interesting application is for testing and watching the operation of microphones. The voice produces a varying wave-form on the scope in step with the intensity and type of sounds delivered to the microphone.

It is commonly believed that an oscilloscope is too complex, and too difficult for an experimenter to construct himself. Actually, however, kits are available from electronic supply houses that belie this belief. The scope used for the experiments discussed in this article, for instance, was made from an Allied Radio kit with printed circuit board, that makes the job of building a good, general-purpose oscilloscope quite simple.

This scope is designed for viewing waveforms to 1.5 megacycles. It has built-in regulated cali-

brator to measure exact amplitude of the waveform appearing on the screen, by the flick of a switch. The sweep covers from 15 cycles to 150 kilocycles. These specifications are usually adequate for most general use. The vertical amplifier has a sensitivity of .025 volts (r.m.s) per inch and the input impedance is 3.3 megohms shunted by 45 mmfd. The horizontal amplifier has a sensitivity of .07 volts per inch and an impedance of 2.2 megohms shunted by 30 mmfd. The kit is supplied by Allied Radio, 100-A N. Western Ave., Chicago 80, Ill., under Cat. No. 83YU146, \$44.95 complete. Laced cables, printed circuit board and pre-cut hook-up wires all trimmed, plus easy-to-follow assembly instructions make its construction simple for anyone having some electronic experience.

The wiring of the printed circuit board of this kit especially simplifies its construction.

Those of you who have never used this marvel of circuitry, will be pleasantly surprised at the time saved over conventional wiring. The complex part of the circuit will be already wired for you; it is only necessary to insert the sockets and the resistor and capacitor leads in punched holes and solder them on the back to the silvered copper foil pattern. The top side of the board is lettered and marked to help in quickly identifying the parts to be installed.

Soldering to the printed circuit is not difficult if care is taken to apply just the right amount of heat and all excess solder is eliminated. For use on the connections where small diameter wire is involved, an Ungar soldering pencil was found to be very satisfactory. For use at the other terminals, where larger wire is found, such as with the 1 and 2 watt resistors and large capacitors, you use a 60-watt iron. When you have completed assembly and tests, you can begin your experiments.

The first should be the production of a 60-cycle sine wave on the screen. A 6.3-volt filament transformer mounted on a small piece of board, with insulated line terminals and a terminal strip for the low-voltage secondary leads, is made up

for quick connections to the scope with either 6.3 volts or 3.15 volts. You can obtain either voltage by using the two outside or the center and one outside terminal and many experiments can be conducted at a safe, low voltage. This test unit is shown in Fig. 3, connected to the vertical input terminals of the scope.

Set the V. Input Atten. to .1, the Sync Selector to +INT and the Sweep Selector between 15 and 150. Turn on the power to both the scope and the transformer and after the former warms up a few minutes, you should get a sine waveform on the screen by adjusting the V. Gain, H. Gain and the Sweep Vernier controls. The latter is a vernier on the sweep selector and a point will be found where a single cycle wave will appear and the Sync Lock control will hold the trace stationary. The sine wave is adjusted on the screen so as to be equally divided and below the center horizontal line. This represents a good wave-form




Testing the completed oscilloscope with a small step-down filament transformer. The sine wave shown in the above photograph is one cycle or two alternations of the 60 cycle current.




Tools needed to assemble the kit.

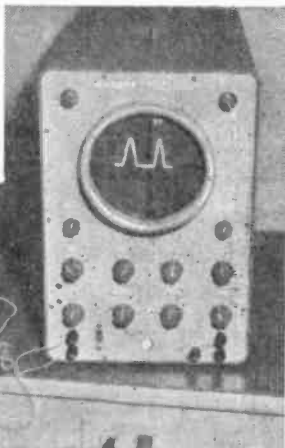Oscilloscope pattern quickly identifies a half-wave rectifier. Note that lower half wave has been cut off and lost.



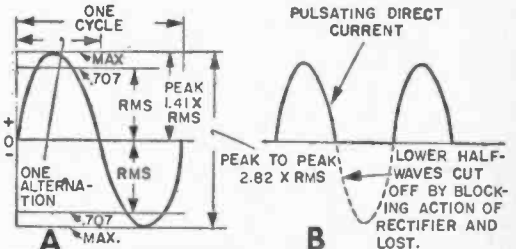which is usually obtainable from the standard 60-cycle line. It shows the rise and fall of the alternating current from 0 to positive maximum, then back to 0 to reach a maximum amplitude in



A SINE WAVE VOLTAGE VALUES
PEAK TO PEAK VALUE IS THE TOTAL AMPLITUDE FROM POSITIVE MAXIMUM TO NEGATIVE MAXIMUM. RMS (ROOT MEAN SQUARE) VALUE IS ORDINARILY READ BY VOLTMETERS.



B HALF-WAVE RECTIFIER WAVE FORM

LOWER HALF-WAVE OF TYPE SHOWN ABOVE IS INVERTED AND USED

5

PLASTIC SCREEN RULED 10 LINES PER INCH

FULL-WAVE RECTIFIER WAVE FORM

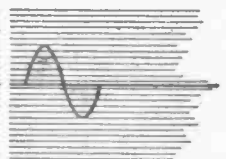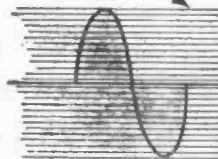


SINE WAVE FROM 18 VOLTS RMS (KNOWN VOLTAGE)

SINE WAVE OF 1/2 AMPLITUDE 9 VOLTS RMS

C

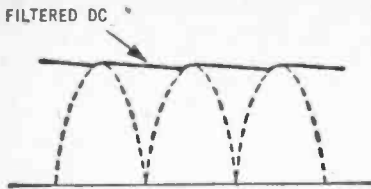VOLTAGE MEASUREMENTS BY COMPARISON WITH KNOWN VOLTAGE



SHOWING THE EFFECT OF FILTERING
A FULL-WAVE RECTIFIER OUTPUT


a negative direction, from where it returns to 0. This is one cycle or two alternations. This sine wave is shown in Fig. 5A for further study and the relation of peak voltage to r.m.s. (root-mean-square) voltage as ordinarily measured by voltmeters, is indicated.

The oscilloscope can be used to measure voltage by comparison of the amplitude of the waveform from a known voltage with an unknown voltage. A plastic screen ruled with 10 lines to the inch (Fig. 5C) and applied to the face of the tube is a convenient method of calibration. The waveform from the known voltage can be adjusted between a certain number of lines and without touching the vertical gain control, the unknown voltage is applied, using the same vertical input terminals of the scope. If the trace has a peak to peak amplitude from the unknown voltage that is twice as great as that from the known voltage, the voltage is twice as great. Knowing the value of one signal applied, is quite easy to calculate other voltages.

To get familiar with the scope controls, turn the Sync Selector to the -INT position and it will be found that the trace is shifted 180 electrical degrees, indicating that synchronization is being effected through the use of the negative half-cycles. If moved to the EXT position, the trace will start to drift, as in this position it requires the use of an external synchronizing source to be connected to the Ext. Sync. terminal.

Further experiments with the controls should include the V. Input Atten. When on the .01 position, the signal voltage connected to the V. Input terminals is divided by a factor of 100 and the trace will be considerably reduced in vertical gain from that shown when the switch is on the 1 position. The .1 marker divides the input signal by 10. This allows some control over the value of the input voltage to the scope and therefore, when applying an unknown voltage or one known to be quite high, always place the attenuator on the .01 position first, advancing the switch later to the other positions if required.

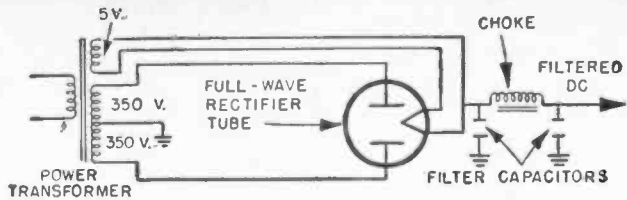
The oscilloscope is useful for indicating either half-wave or full-wave rectification. Such recti-



6

FILTERED POWER SUPPLY

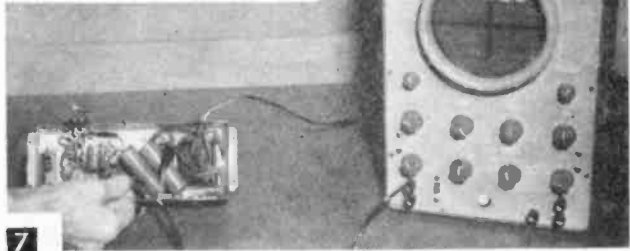Oscilloscope is connected across choke of a phonograph amplifier to show how filtering smooths out the pulsating current of a rectifier.



7

An example of an interesting pattern provided by a microphone.




8

fiers are used in battery chargers, radio and television power supplies and many other types of electrical apparatus.

For the demonstration of half-wave rectification (Fig. 4) a selenium stack has been connected in series with one side of the secondary of the 6.3 volt test transformer and a dummy resistance load connected across the resulting line, with leads to the V. Input scope terminals. A half-wave vacuum tube would show approximately the same waveform.

A half-wave rectifier uses but one of the half-waves of the 60 cycle sine wave shown in Fig. 5A, the other half being lost or wasted. The half-wave that has been cut off is indicated by dotted lines (Fig. 5B) and represents the action of the blocking effect of the rectifier, so that D.C. pulsating current is produced from an alternating current source. An oscillogram of a half-wave rectifier, showing two half-waves above the cen-

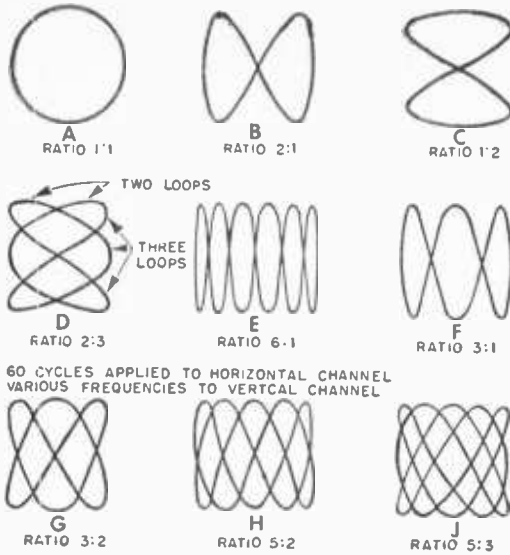

$$\frac{\text{NUMBER OF LOOPS TANGENT TO A HORIZONTAL LINE}}{\text{NUMBER OF LOOPS TANGENT TO A VERTICAL LINE}} = \text{RATIO OF FREQUENCY}$$

9

VARIOUS LISSAJOUS FIGURES FOR DETERMINING FREQUENCY

ter line with a space between is shown in Fig. 4. In full-wave rectifiers, both half-waves are used for better efficiency, the lost half-wave of the first case being inverted and used to pass unidirectional current. Rectifiers may be either of the dry disc or vacuum tube types.


An example of full-wave rectification in a battery charger is shown in Fig. 1. A dummy resistance load, of a value to show a small amount of current on the meter, has been connected across the spring clips, with leads connecting to the scope. It will be seen that the half-wave lost in the first subject has now been inverted to the space between the half-waves above the line and we have a full-wave rectifier. The pattern has been adjusted by the Vertical Position control so its lower points are on the horizontal line of the screen to get the correct picture. Full wave is obtained from either a bridge type rectifier stack or two half-wave stacks in a circuit with a center-tapped transformer. A full-wave vacuum tube rectifier also delivers this type of current.

The rectifiers illustrated produce pulsating direct current which is unidirectional but is not steady enough for some applications such as electronic power supplies. To smooth out the ripple to an extent as required for the purpose, a filter is added. This usually consists of a choke and two electrolytic capacitors (Fig. 6).

An example of a filtered power supply (Fig. 7) shows the scope connected across the choke in a phonograph amplifier. While the trace on the screen is not exactly a straight line, it has far less ripple than would be the case with the unfiltered rectifier shown in Fig. 1 or in other

words, it now takes the peaks of the waves only with just a slight dip between. Such an oscillogram allows the designer to check the effect of more or less inductance and capacitance so as to result in as little ripple as possible. (Care should be taken while working around apparatus employing high voltage, such as power supplies, since such voltage can deliver dangerous shocks if the worker gets careless and comes in contact with live terminals.)

An interesting demonstration of voice modulation on the oscilloscope is possible with a crystal microphone. Connect the microphone leads to the vertical input terminals, attaching the insulated center wire of the shielded cable to the red terminal (V. Input) and the braid to the ground terminal. When connecting any apparatus always connect the lead from the ground to the GND. terminal where one of the leads does represent

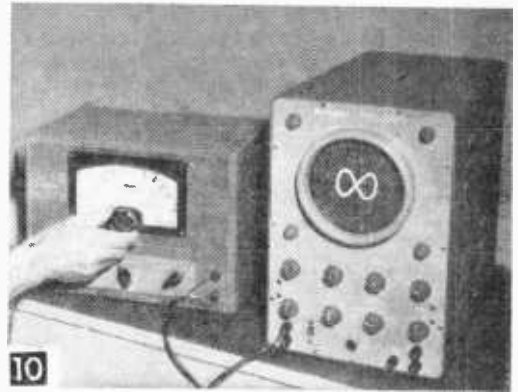


Frequency measurements are made with 60 cycles applied to the horizontal channel, by placing the Sweep Selector on this point and applying the unknown frequency to the vertical channel. Here an audio oscillator is being used to obtain a pattern of 120 cycles.

ground such as with microphones and many radio and TV test connections. Also, use shielded leads to prevent stray pick-up. Various sounded words and letters, as well as whistling will produce a wide variety of interesting patterns one of which is shown in Fig. 8. Musical notes sounded are especially effective. By this means, a good test for the condition or quality of a microphone is provided. A good unit in sensitive condition will respond to very low tones, while a cheap unit or one in bad condition will usually require loud signals in order to get comparable traces or the same gain on the screen. A dead microphone can be quickly identified, since it will have no response.

For use with a crystal microphone, the oscilloscope controls should be set somewhat generally as follows. The V. Input Atten is on 1, the Vertical Gain about 3/4 advanced clockwise, the Horizontal Gain about 1/2 advanced clockwise, the Sweep Selector between 15 and 150, Sync. Selector on +INT. The controls are further adjusted as required in a test.

Frequency measurements are another possi-

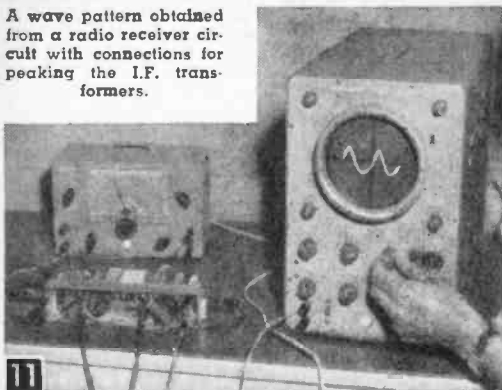A wave pattern obtained from a radio receiver circuit with connections for peaking the I.F. transformers.



bility open to the owner of an oscilloscope. It is often necessary to determine the frequency of some power source and this can be done quite easily by what are known as Lissajous figures. By this method a known frequency is applied to the horizontal channel and the unknown to the vertical channel to produce a variety of patterns that can be interpreted to indicate the frequency of the unknown signal. Fig. 9 shows some of the Lissajous patterns obtained.

The Sweep Selector is set to the 60 cycle position which allows a portion of the 60 cycle line to be applied for the horizontal sweep. For demonstration of various frequencies, which can be taken as the unknown frequency source, an audio oscillator is connected to the vertical input terminals of the scope as in Fig. 10. By adjusting a knob and a range switch, frequencies from 20 to 20,000 cycles are possible; 120 cycles are being delivered to the scope and the pattern shown has two top loops and one side loop. The Sweep Vernier has been adjusted to get the figure shown in Fig. 10. The calculation for frequency of the unknown signal is made by considering the ratio of the loops at the top of the pattern, which represents the unknown frequency, to the loop or loops at the side. In this case the ratio is 2:1. The actual frequency is determined by dividing the loops tangent to an imaginary horizontal line by those tangent to a vertical line or in this case $2/1=2$ and multiplying this ratio by that of the standardizing frequency or 60 cycles to get 120 cycles. If the unknown frequency source happened to be 30 cycles, for another example, there would be one loop at the top to two at the side, as indicated in Fig. 9C. It will be noted that there is but one loop at the top, with two at the side or a ratio of 1:2. Therefore, $1/2=.5$ or the frequency would be $\frac{1}{2}$ that of 60 cycles or 30 cycles. This can be carried out for a great variety of unknown frequency measurements up to a point where it will be difficult to count the number of loops or perhaps up to ratios of 8:1 maximum. In many cases the figures will not remain very stationary due to phase differences in the two signals, but in other cases where they are exactly in phase, the patterns will be quite stationary.

Radio and television service men often use an oscilloscope to get wave patterns in various parts of circuits and also for lining up the I.F. transformers in a superheterodyne radio receiver. For locating trouble in the audio stage the oscilloscope is often connected across the speaker output leads. Where oscillograms are desired in some parts of the I.F. or R.F. sections, an extra accessory is required, called a demodulator probe. In Fig. 11 the Allied oscilloscope is being employed for peaking the I.F. transformers. A signal generator, shown at the left, produces the necessary 456 kc signal to the grid of the mixer tube through a .001 capacitor. The scope is connected across the detector load resistor. The controls on the scope are adjusted to get a pattern showing the frequency response curve of single-peaked I.F. transformers. This output waveform can be used in combination with the tone from the signal generator to make the adjustments at the I.F. transformers. It is usually necessary to shunt out the oscillator section of the variable tuning condenser to accomplish this work.

There are so many possible applications of the oscilloscope in electronics and industry that it would be impossible to try and describe them here. In general the operator should have some background knowledge of electricity and electronics in order to handle the instrument properly. There are several good books on the subject which are suggested for study, among them being the following—


Modern Oscilloscopes and Their Use by Jacob H. Ruiter, Jr., Rinehart & Company, 232 Madison Avenue, New York 16, N. Y.


Obtaining and Interpreting Test Scope Traces by John F. Rider, John F. Rider Publisher, Inc., 480 Canal St., New York 13, N. Y.

The Oscilloscope by George Zwick, Gernsback Publications, Inc., 25 West Broadway, New York 7, N. Y.

Cleaning Fuse Clips

• When tubular fuse-holding clips in electrical equipment become corroded, contact resistance increases and the fuse and its holder effectively become a "resistor," thus impairing the fuse's original purpose. To prevent this, place the fuse in the center of a strip of crocus cloth, with the abrasive side out, and force this into the fuse clip holder. Move the fuse and cloth back and forth several times to burnish the overall insides of the clips and expose fresh metal. This will assure a positive contact when the fuse is replaced. If this process tends to make the fuse fit loosely in the clips, pinch them together slightly, then replace the fuse.—JOHN A. COMSTOCK.

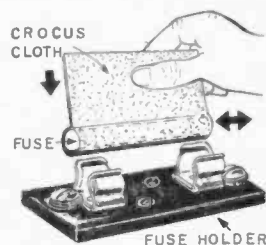

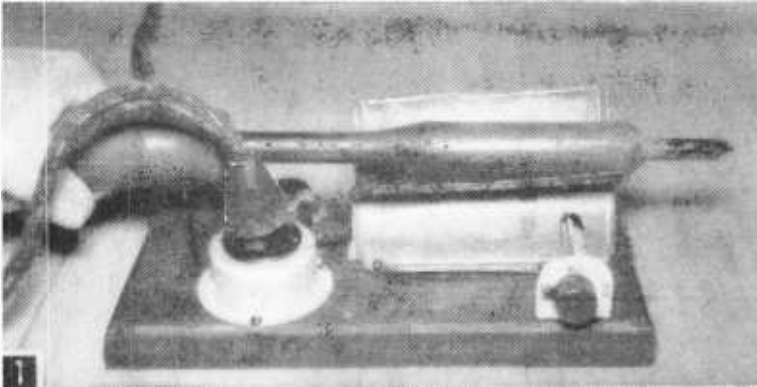

Thermostatically controlled stand regulates heat of iron through three levels—saves on electric bills!

Thermostatically Controlled Soldering Iron Stand

A thermostatically controlled soldering iron stand prolongs element life, prevents "frozen" tips and provides the right iron temperature for a variety of jobs. It is one of the few appliances that saves current while working instead of consuming it

By W. McCORMICK



HERE'S a thermostatically controlled soldering iron stand you can make, mostly of junk, that will control any iron from 80 to 600 watts. The temperature sensing element is a bi-metal thermostat. When two strips of metal having different expansion co-efficients, such as steel and brass, are fastened together and heated, the compound strip will bend, with the more expansive metal, the brass, on the convex side. If one end of the strip is held fast, a swinging motion occurs at the free end. This motion can open and close electrical contacts.



To use this principle to control soldering iron temperature, first make the sheet asbestos thermostat base, Fig. 2. Next, make the brackets shown in Figs. 3A and 3B, and the indicator bracket, Fig. 3C, and indicator dial, Fig. 3D, and cement the dial to the face of the bracket. Do not use material heavier than called

for or the thermostat will regulate poorly.

Now, snip out the thermostat armature blades, one of tin-can steel, the other of brass shim stock (Fig. 4A). Scribe the location of all holes on each blade, center-punch and drill. Deburr blades, flatten them and rivet them together with $\frac{1}{16}$ -in. diameter eyelet rivets *only* at holes "C" and "D." Ream hole "E" and force-fit a $\frac{1}{4}$ -in. x 2-56 rh machine screw into it with the screw head on the armature's brass side. Run a hex nut on the screw, tighten it and snip off the excess screw shank. File screw shank flush with the nut, make sure nut is still tight, and file the screw head flat.

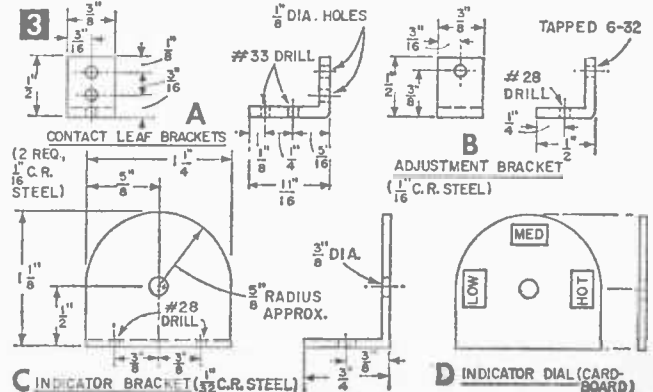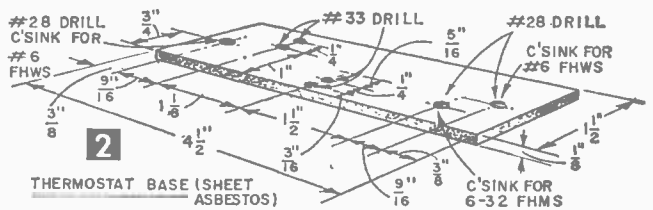Now set one of the brackets (Fig. 3A) before you with its foot behind it and its $\frac{1}{2}$ -in. dimension in the vertical plane. Place the brass side of the armature against the back side of the vertical bracket leg, approaching the bracket



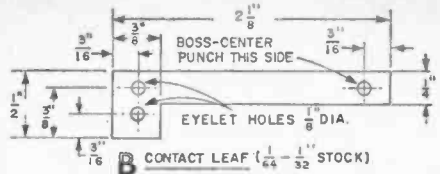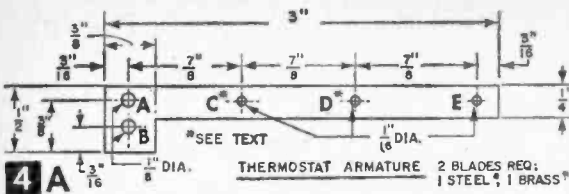


with the brass side of the armature from behind, and rivet the armature and bracket *lightly* together with 1/8-in. diameter eyelets. Mount the armature assembly on the thermostat base with 1/4-in. x 4-40 fh machine screws. Adjust the armature blades parallel with the armature base, and set the eyelets.

Next, make the contact leaf shown in Fig. 4B. Place the second bracket with its foot toward you and its 1/2-in. dimension in the vertical plane. Rivet the contact leaf *lightly* to the far side of the vertical leg, with the leaf's boss facing from you. Use 1/8-in. diameter eyelets.

Check the contact leaf for parallelism with the

thermostat base, and set the eyelets and mount this assembly on the thermostat base with 1/4-in. x 4-40 fh machine screws. The boss on the contact leaf should face the flat screw head in the armature. Center up the contact leaf's boss with the screw head in the armature, leaving about 1/32-in. between the boss and screw head. Spring the armature a little if necessary. Tighten all the bracket mounting screws.

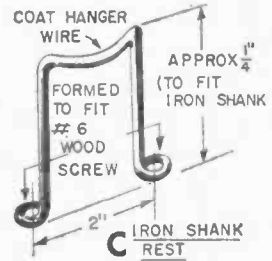



Now mount the adjustment bracket (Fig. 3B) with its tapped hole facing the back side of the contact leaf's boss, and in alignment with the armature's screw-head contact. (Foot of bracket toward you.) Snip the red tip off the fiber aligning tool, and cut the fiber shaft, leaving the tool 3 in. long, overall. Thread 1/2 in. of the fiber shaft with a 6-32 thread. (The bracket hole thread will do this if the fiber shaft is made slightly pointed.) Slip the compression spring on the threaded end of the alignment tool and screw the threaded shaft into the tapered bracket hole one or two turns—*not* enough to force the contact leaf boss against the screw head in the armature. Put a soldering lug and nut on the screw end nearest the upright of both the armature bracket and the contact leaf bracket. Tighten nuts.

Next, make the thermostat cover and iron pan (Fig. 5). Cut both ends out of a #303 tin can and snip cylinder lengthwise into two half-round sections. Form and drill. Rivet finished pieces together with 1/8-in. diameter eyelets and blue over a flame. Form the iron-shank rest (Fig. 4C) from a 6-in. length of coat hanger wire.

Now, chamfer the top edges of the hardwood base 1/4 in., and give it a coat of thinned black enamel. Drill a 5/16-in. hole in the shell of the 110-v outlet and insert the grommet. Then place all the completed parts on the wood base and make a trial layout. The thermostat assembly mounts with #6 x 1/2-in. fh wood screws. The

MATERIALS LIST—SOLDERING IRON STAND

- | No. Req'd. | Description |
|------------|--|
| 1 pc | sheet asbestos, 1/8 x 1 1/2 x 4 1/2" (linen-base Bakelite can be used for irons under 200 watts) |
| 1 pc | cold rolled steel, 1/16 x 3/8 x 5" |
| 1 pc | phosphor bronze, spring steel, spring brass or beryllium copper, 1/2 x 2 1/8 x 1/4 to 1/2" |
| 1 pc | brass shim stock, 1/64 x 1/8 x 3" |
| 1 pc | cold rolled steel, 1/2 x 1 1/4 x 1 7/8" or two thicknesses tin can steel sweated together |
| 6 | 1/8" O.D. x 1/8" eyelet rivet |
| 2 | 1/16" O.D. x 1/8" eyelet rivet |
| 1 | 2-56 x 1/4 rh machine screw and hex nut |
| 4 | 4-40 x 3/4 fh machine screw and hex nut |
| 1 | 6-32 x 1/2 fh machine screw and hex nut |
| 13 | #4 x 1/2" rh wood screws |
| 2 | #6 x 1/2" fh wood screws |
| 2 | #6 x 1/2" rh wood screws |
| 1 | rubber grommet 5/16" mtg. hole (Walsco 7023F) |
| 1 | cable clamp 1/4 to 3/8" cable (Walsco 7505F) |
| 1 | assort. comp. spring 3/32 x 1 1/2" (Walsco 7440F) |
| 1 | instrument knob 1/4" shaft (Burstain Applebee 12A122) |
| 1 | alignment tool (General Cement #8247) |
| 1 | Amphenol 61F receptacle (outlet) |
| 1 | Amphenol 231S receptacle shell |
| 1 | electric iron cord, asbestos wrapped heavy duty |
| 2 | soldering lugs (Walsco 7150F) |
| 1 | compression spring, 3/32" I. D. x 1 1/2" approx. (from old ball point pen or Walsco 7440F) |
| 1 | 2 x 2" piece white-faced cardboard |
| 1 | #303 tin can |
| 1 | tin can (any size) |
| 10' | length #14 ga. stranded hook-up wire |
| 1 | hardwood base 4 x 8 1/2 x 3/4" thick |

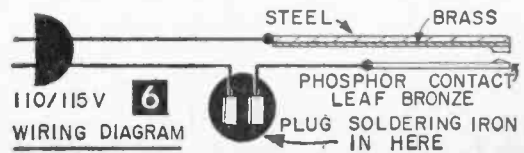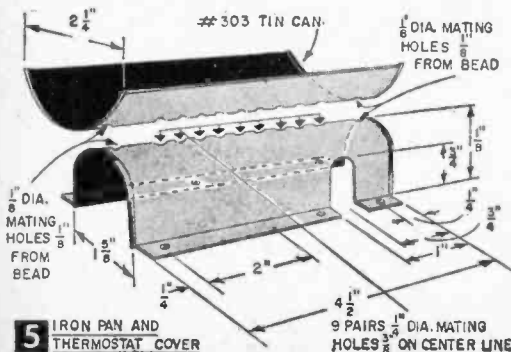


indicator bracket, 110-v outlet and the iron-shank bracket mount with #4 x 1/2-in. rh wood screws. The cord clamp takes a #6 x 1/2-in. rh screw.

Wire as shown in Fig. 6. Wrap solder lugs around the connections to the thermostat, and crush lug loops on the wires. Trim wire ends, and tape the appliance cord where it passes under the cable clamp. Mount the thermostat cover and iron pan assembly over the thermostat.


To calibrate unit, plug a lamp into the solder-

ing iron outlet and plug the iron stand cord into a 110/115-v outlet. Turn the aligning tool clockwise until the bulb just lights without flickering. Put the adjusting knob on the 1/4-in. diameter end of the aligning tool, set it to point to "LOW" on the indicator dial and tighten its set screw. The unit is now fully calibrated and will read "MEDIUM" and "HOT" temperatures correctly. Unplug the lamp, plug in your soldering iron in its place.

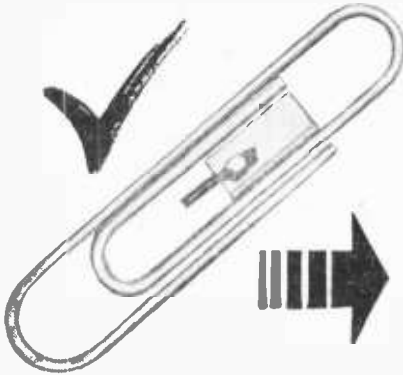Unique Circuit Simplifier the Tunnel Diode



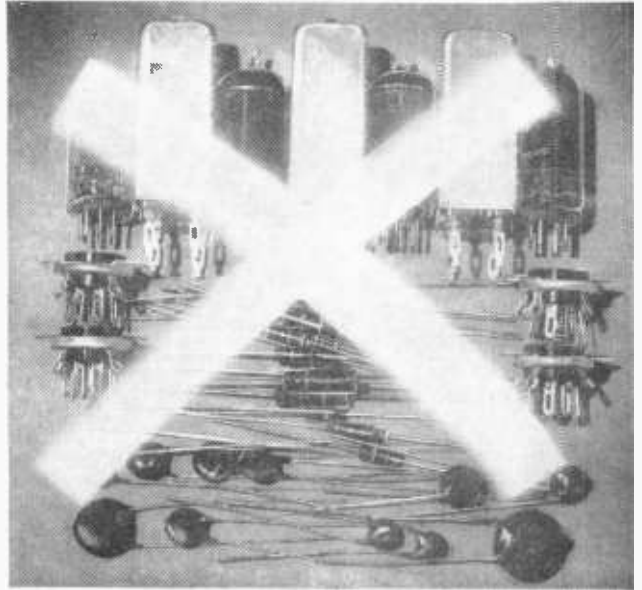Nestled inside this paper clip—with room to spare—is a tunnel diode, one of last year's most startling electronics developments. If an FM receiver were rebuilt using one of the new diodes, all the conventional components shown at the right could be omitted.




THE tunnel diode—newest baby in the fast-growing family of semiconductors—may soon be giving its first cousin, the transistor, an inferiority complex.

So small that a radio transmitter the size of a 50¢ piece has been built with it, the fantastic tunnel diode can perform almost all the functions of a standard low-power transistor and could lead to enormous savings in cost and complexity of electronic circuits.

A few of its features that have electronics engineers most intrigued are: An amplification noise figure of about one decibel, power requirements as low as one millionth of a watt and operation frequencies as high as 10,000 megacycles.

In some instances, the new diode may replace conventional components. In others, it might be used to improve their performance by working with them.

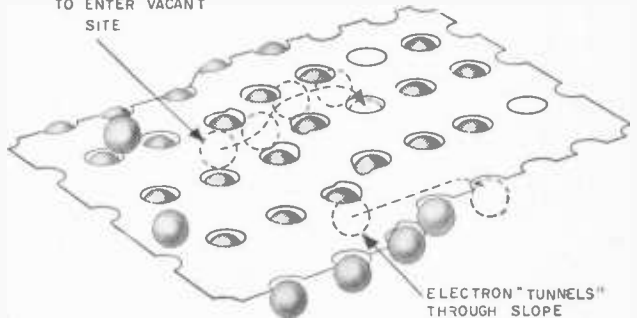ELECTRON "ROLLS UP" SLOPE TO ENTER VACANT SITE



Here—in an extremely simplified diagram—is how the tunnel diode operates. Drawing represents a structure similar to a Chinese checkerboard, with one side slightly raised. Holes on the left side (which represents an n-type semiconductor) are filled with marbles, with a few left over and sitting on top. Right side (representing a p-type semiconductor) has a few holes vacant. The slope represents the potential barrier. A marble (or electron) from the left, can—after being given a push—enter a hole on the right by rolling up the slope and dropping in. Or, without the push, it can miraculously "tunnel" through the board and appear in a hole. The former process is used in conventional diodes and transistors. The latter represents what happens in tunnel diodes.

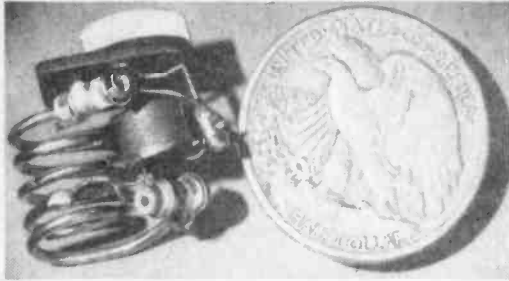


Photo compares transmitter with 50¢ piece. It consists of one variable and two fixed ceramic capacitors, tuning coil and the diode itself—inside can in center of transmitter.

The tunnel diode was first reported by a Japanese scientist—Dr. Leo Esaki—in 1958, and although its construction is very similar to an ordinary rectifying diode's, it works on an entirely different principle.

It takes its name from the phenomenon that makes its operation possible: quantum-mechanical tunneling.

As with transistors, it depends on the transfer of an electrical charge across a p-n junction. This is the region between a p-type semiconductor, which has an excess of positive carriers or "holes" (empty electron states), and an n-type, which has an excess of free electrons.

The opposite sides of this junction take on a charge which resists the movement of the "holes" and electrons across it. In the transistor, a charge carrier must be emitted into a region where its energy can be boosted by an outside voltage. It is then collected on an output electrode. The speed of this process is limited by the time it takes the charge carrier—having left the emitter—to traverse the control region and appear on the collector. This time limits the frequency at which the device can function and is quite long compared to, say, the time needed for a signal to travel an equivalent distance along a copper wire. The reason: in the wire, each electron moves only a microscopic distance, and those coming out the other end aren't the same ones that went in as a signal.

The quantum-mechanical theory says there is another way in which the particles can pass the barrier: an electron has a small, but definite, probability of disappearing from one side of the potential barrier and re-appearing simultaneously on the other—even though it does not have enough energy to surmount the barrier. It is as though the particles "tunnel" under the barrier, setting up almost instantaneous surges of current. Thus, in the tunnel diode, the signal moves with the same speed as it would in a copper wire—the speed of light.

The construction of the amazing device gives it some other interesting characteristics.

Its p-n junction is made of materials more heavily loaded—or doped—with impurities than

conventional diodes (semiconductor materials are doped to form either p-types or n-types), and made so that the barrier between p and n sections is extremely thin, less than a millionth of an inch thick.

So long as no outside voltage is applied across the p-n junction, there is no net current—since the electrons tunnel back and forth easily through the barrier in both directions. Apply a small voltage, however, and current appears. Add still more voltage, and current *decreases*. Add more, and current increases again.

In the range where an increase in voltage results in a fall-off of current, the tunnel diode is said to have "negative" resistance—making it suited for use as an amplifier or oscillator.


This negative resistance quality, combined with speed-of-light operation, makes possible a very high frequency response. Oscillation frequencies higher than 2000 megacycles have already been obtained—matching advanced transistor performance—and engineers confidently expect frequencies of more than 10,000 megacycles in the near future.

Some other outstanding features:

- It is smaller than a transistor and, because of its simplicity, ultimately will be just a fraction of its present size.
- It is affected very little by environment. The tunnel diode can operate at the near-absolute zero temperature of liquid helium or—at the other end of the thermometer—at temperatures up to 650°F, while conventional silicon diodes won't operate above 400°F.
- It has a low noise level, only parametric amplifiers and masers competing closely with it. And of these, only the tunnel diode can operate directly from a battery.
- Because it is less dependent on the structural perfection of its crystal than is the transistor, the tunnel diode is less affected by the damage that nuclear radiation can do to such crystal structures.

Soldering Flux Can Carries Vise

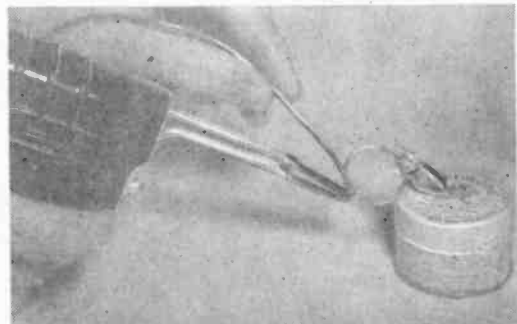- Attach a test-clip to the lid of a can of soldering flux to use as a handy vise for holding small



parts while applying solder. Enlarge hole in clip slightly with a drill and attach to can with a small self-tapping metal screw.—JOHN A. COMSTOCK.


Less bulky than conventional units, complete tachometer clamps to steering column for handy visibility. Instrument can also be installed on dash or used as portable test device.

THE Speed of an engine is the key to its performance. A standard item on the dash panels of many sports cars, the "tach" makes it possible to select the best engine speeds for gas economy. Also it advises the driver when the engine is turning over at just the right speed for shifting—thus cutting down unnecessary clutch and transmission gear wear. And it is essential in making proper carburetor and distributor tune-up adjustments in the garage.

This tachometer is designed to operate on either 6 or 12 volt ignition systems, positive or negative ground. Provided that you change one part, which depends on the number of cylinders, you can use this tachometer on any kind of engine from a "one lung" 2 stroke outboard motor up to an 8 cylinder 4 stroke engine. The photo shows the dial calibrated 0-5000, which is sufficient for most purposes, but it can also be arranged to read the range, 0-10,000 rpm. With an accessory switch, it can even be used to measure the speeds of rotating shafts in appliances and power tools. And unlike conventional tachometers which are bulky and difficult to install, it is compact, and hooks up without costly special cables and switch assemblies. Cost for all parts should be under \$25.

Construction. The meter, M1, shown in Fig. 1, is inexpensive, but has an accurate 50 micro-ampere movement. With the attached circuitry the entire assembly extends only 2 3/8 in. deep behind the panel. Begin construction by cutting Discs A and B (Fig. 2), of 1/32-in. sheet bakelite with either a jig saw or circle cutter. If you use a circle cutter, drill the center hole for a #6 screw, and reverse the cutter blade so that the cutting edge is inside. Rotate the cutter counter-clockwise, and work through from both sides of the bakelite sheet to obtain neat discs. Make the spacer, C, from a piece of 1/4-in. brass bar stock, and thread it through with a 6-32 tap.

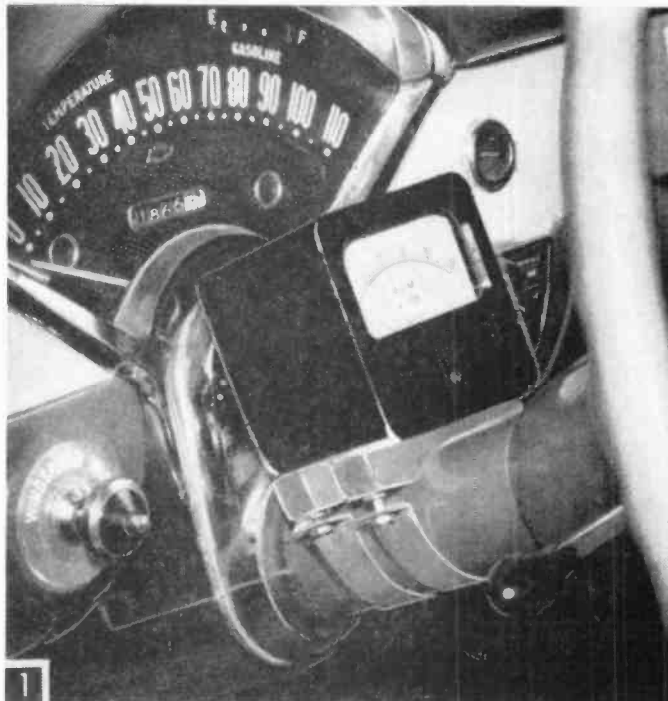Parts layout is not critical, but it is necessary to be careful to avoid crowding the wiring in some spots. Cut out the two templates (Fig. 3), and fasten them to the bakelite sheets with tape or rubber cement. Turret type terminal lugs can be used for easier and neater construction, however if you prefer, you may choose to use 4-40





Electronic Tachometer

Dependable transistor circuit counts ignition pulses. Readings indicate proper speeds for operating and tuneup of cars, outboards, truck, marine and stationary engines

By JAMES E. PUGH JR.

machine screws instead. Either way, drill the holes carefully for a tight fit. Fasten solder lugs to the bottom of disc A for mounting and making connections to the meter. Drill two 5/16-in. holes in this disc for the meter terminal screws. A 6-32 screw fastens disc A to the threaded spacer later and also connects the positive solder lug at the center (Fig. 8), and thus brings the positive terminal through to the back of disc B.

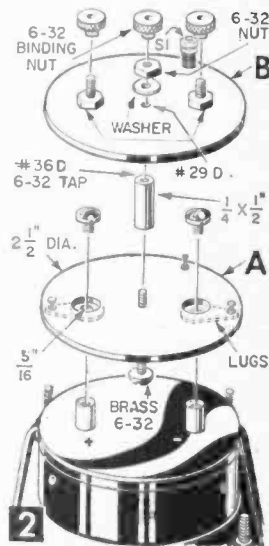

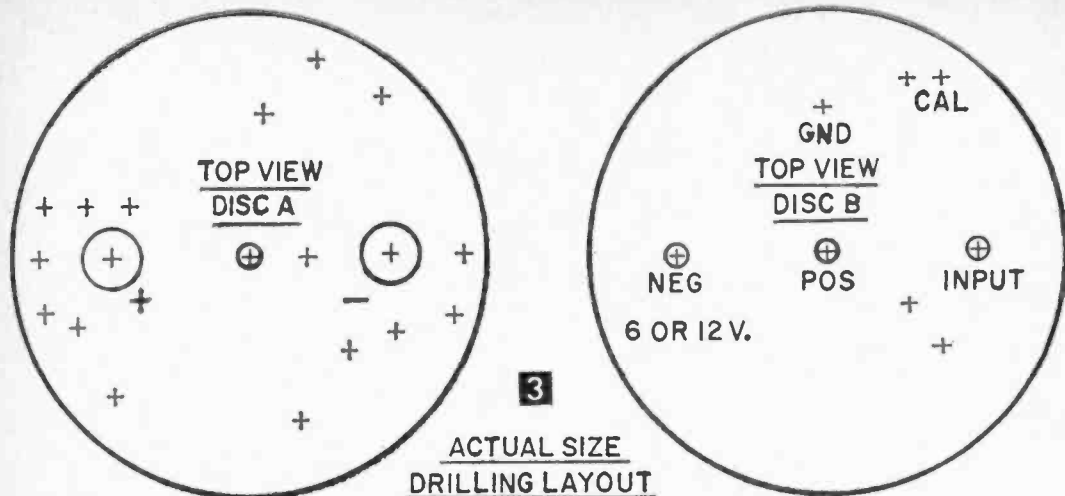

Use a 4-40 screw for the calibration switch S1 (Fig. 3). When all parts are assembled, this switch operates by turning the screw in and out of its threaded hole in Disc B, and it contacts the C4-V1 terminal.

Mount potentiometer R7 with its adjustment screw near the disc edge for ease of adjustment. Note that the wiring will be connected to terminals 1 and 2 on this control, so that clockwise adjustment of the screw will increase reading.

Making the Case. The case and brackets (Fig. 5), are made of utility sheet aluminum, with the corners rounded by means of a wooden forming block. Make the block as in Fig. 4 from two pieces of 2 x 4 glued together. Cut the sheet metal to size, and notch out the slots. Clamp the bottom portion to the block, and use a rubber hammer, or soft wood block to shape the metal


around the form. Bend over the end tabs, and drill the four holes to fit the meter mounting screws. Make the two dust gaskets of cardboard or sheet rubber, and use sheet metal screws to fasten the two halves of the bottom together. Drill the holes for fastening the rear cover to fit sheet metal screws, and install the grommet.


Saw and sand the curve on the two wood blocks, Fig. 5, to fit the diameter of the steering post of your car, and shape the two mounting straps to fit. Fasten to car steering post with four 6-32 x 1 1/4-in. rh machine screws as in Fig. 1.

Wiring. Since the tachometer is designed to operate on any kind of engine, and can also be set up for various speeds you may want later to change part C4, the capacitor which determines the range of the instrument. Select the value of C4, which corresponds to your engine (Table A),

and connect it to the D2-D3 feed-through terminal with a fine wire link, as in Fig. 8. This will reduce the danger of damaging the diodes when soldering C4. Similar links are used at the D2D4 to meter plus, and D3D5 to meter minus connections. Another very important precaution is to hold the terminal wires of the diodes, the transistor, and capacitor C3 with long nosed pliers, between the part and the solder point, to avoid damage from overheating.

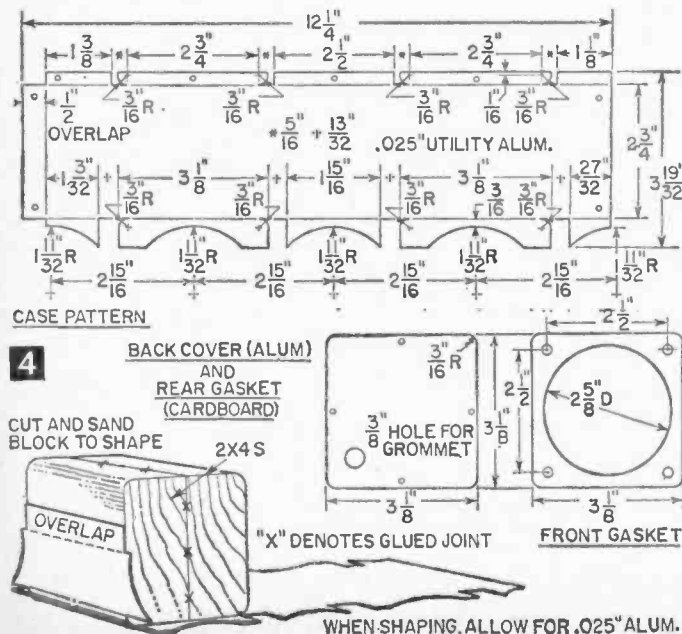
How It Works. This tachometer circuit consists of three main sections; a low pass filter, a clipper and pulse amplifier, and a counting circuit. A low voltage pulse is picked up at the distributor breaker points (see Figs. 9 and 10 for connections to engine) and is fed to the input of the low pass filter circuit, as shown on the schematic. This resistance-capacitance filter circuit is de-



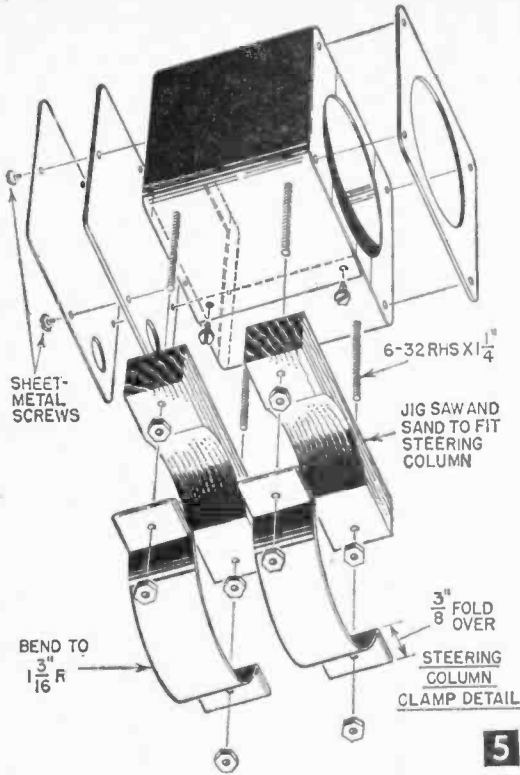

5

CALIBRATION SWITCH (SI) 6

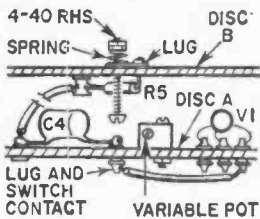

signed to pass the maximum number of pulses from an 8-cylinder engine operating at 10,000 rpm. Frequencies above this range and other "hash" elements are eliminated by the filter, to eliminate the possibility of error in the meter readings.

Then the output of the filter circuit is fed to transistor V1, where the wave shape is clipped

TABLE A. Calibration data for tachometer using 0-50 meter scale, 5000 rpm at full scale reading.

Number of cylinders		Pulses per second	60 cps calibration	optimum C4
2-stroke	4-stroke			
	1	41.7	36+	.20 uf.
1	2	83.3	36	.10 uf.
2	4	166.7	18	.068 uf.
	6	250	12	.04 uf.
4	8	333	9	.03 uf.

+ at 30 cps

and shaped into a square pulse, and amplified. The Zener diode, (D1) is next in the circuit line-up, and it keeps the pulses at a constant level, regardless of changes in battery voltage. It makes it possible to use the tachometer on either 6 or 12 volt systems, without changing any parts, and with only a minor calibration adjustment.


Next in the counting circuit, the capacitor C4 with the resistive part of the rectifier and meter circuit, convert the square pulses into negative and positive spikes. The electronic enthusiast may enjoy observing these wave shapes on an oscilloscope.

Finally, the diodes D2, D3, D4 and D5, wired as a full wave bridge rectifier, change all the spikes to one polarity to produce a meter current that is directly proportional to the number of pulses coming from the engine.

Calibration. When you have finished the wiring of your tachometer, connect the flexible ground link to correspond to whether your car is wired negative (Fig. 9), or positive ground (Fig. 10). Connect the tachometer to the car battery, or to one of corresponding voltage. Next, connect an audio signal generator to the tachometer ground and input terminals, and set it to 60 cycles per second (or to 30 cps for a 1 cylinder 4 stroke engine).

Adjust potentiometer R7 to give the meter reading listed in Table A for your kind of engine. Note that if you set the audio signal generator to multiples of 60 cps, the meter reading will increase proportionately, for example for calibrating a 6-cylinder 4-stroke engine, the reading at 60 cps will be 12; at 120 cps it will be 24; at 180 cps, 36, etc.

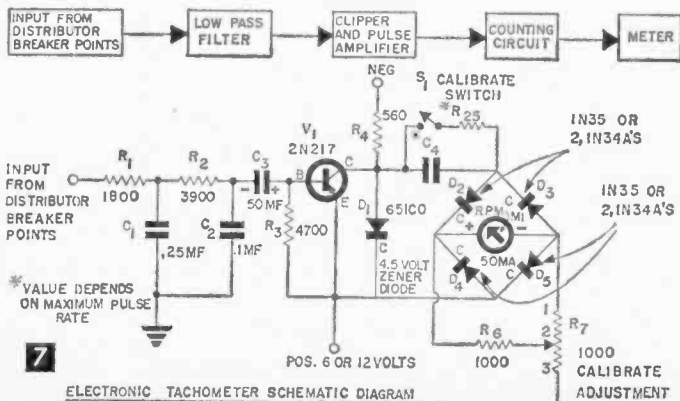If you have no signal generator, you may be able to borrow one from a radio ham, or use one at a radio service shop. Otherwise you can calibrate without it, by using the output from a 6 or 12 volt filament transformer. Connect the transformer to the tachometer ground and input terminals, and adjust the meter reading, by means of trimmer pot R7, to the desired point as listed in Table A.



7

ELECTRONIC TACHOMETER SCHEMATIC DIAGRAM

MATERIALS LIST—ELECTRONIC TACHOMETER

- M1 0-50 DC Microammeter (Lafayette Radio Co., 165 Liberty Ave., Jamaica 33, N. Y. Cat. #TM-70)
- D1 4.5 volt voltage regulator Zener Diode (Texas Instrument 651 C0)
- D2, D3, D4, D5—Two IN35 diodes (paired type) or four IN34A single diodes Sylvania crystal diodes
- V1 2N217 Transistor, RCA

CAPACITORS

- C1 .25 mfd. 200 volt metallized-paper tubular capacitor, Aerovox P 82Z
- C2 .1 mfd. 200 volt metallized-paper tubular capacitor, Aerovox P 82Z
- C3 50 mfd. 25-volt ultra miniature electrolytic capacitor, Barco P25-50 (Lafayette Radio)
- C4 100 volt capacitor Elmenco tubular, Type DP (See table A for value)

RESISTORS

- R1 1800 ohm 1/2 watt 10% Carbon resistor
- R2 3900 ohm 1/2 watt 10% Carbon resistor
- R3 4700 ohm 1/2 watt 10% Carbon resistor
- R4 560 ohm 1/2 watt 10% Carbon resistor
- R5 See Table A 1/2 watt 10% Carbon resistor
- R6 1000 ohm 1/2 watt 10% Carbon resistor
- R7 1000 ohm miniature trimmer potentiometer Bourns Wirewound Trimit 273

HARDWARE

- 1 Threaded bushing, 1/4 inch x 1/2 - 6-32
- 1 dz. ea. Turret terminals, Keystone Electronics Corp. Type 1532 single end; Type 1522 double end (Allied Radio)

MISCELLANEOUS

terminals, screws, nuts, decals, plastic spray, or varnish, 1/16 soft aluminum sheet metal

Next, disconnect the signal generator, close S1, and select a resistor for R5 that will give a convenient reading near the top of the scale. The value of this resistor, will of course, vary for different tachometers. In the one illustrated in this article, a 47,000 ohm resistor gives a reading of 48. Solder the resistor in place and write the meter reading, with S1 switch closed, on a small piece of white tape. By means of this switch, you can easily check the calibration after the tachometer is installed, simply by closing the switch (with the ignition on, but engine off).


Table A lists the pulses per second that are obtained from various engines at 5,000. To calibrate

your tachometer to read 0 to 10,000 maximum, simply double the PPS value, and divide the C4 value and 60 cycle calibration point by two. The formula for calibrating the tachometer for use on any engine is: $PPS = \frac{C \times R}{60 \times N}$

which PPS is the number of pulses per second; C is the number of cylinders, R is the revolutions per minute, and N is the number of revolutions per each cylinder firing.

The value of N will be 1 for a 2 stroke cycle, and 2 for a 4-stroke cycle engine.

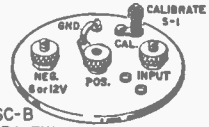The stability of the tachometer circuit is excellent, and your meter readings should be linear with .5% at 70° F.




DISC-B TOP VIEW



DISC-B BOTTOM VIEW



DISC-A TOP VIEW

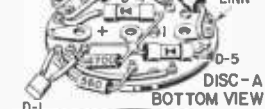

DISC-A BOTTOM VIEW






PICTORIAL 8

Installation. Use small diameter test prod wires for connecting to the engine, and be sure to follow the following precautions to avoid damaging the meter and transistor:

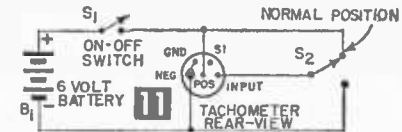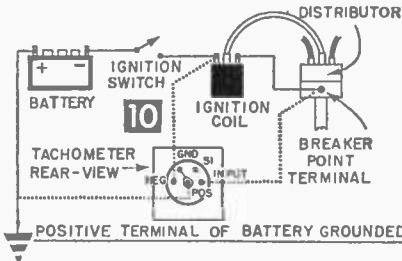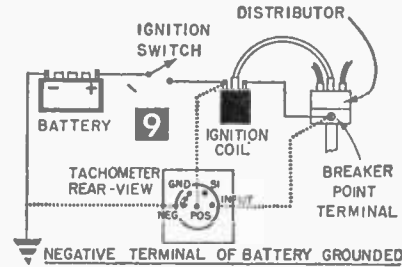1. Make sure that the flexible ground link is connected to the correct ground position for your car, as shown in Figs. 9 or 10.
2. Be sure that the tachometer terminals are connected to the correct battery terminals, with the "hot" tachometer terminal connected to the coil side of the ignition switch.
3. Never start the engine with the calibrate switch (S1) on.

Using Your Tachometer. The tachometer, installed on your car, will not only add to driving pleasure, but will save you money as well. For example, gas consumption is higher at both low and high rpm, therefore, shift and drive with the engine operating in the middle range as much as possible for maximum gas mileage.



CONNECTION FOR MOTORS, DRILL PRESSES, LATHES, ETC. WHERE PULSE IS SUPPLIED BY SHAFT-ACTUATED SWITCH. S.P.D.T. SWITCH ACTUATED BY MOTOR SHAFT

When piston speed exceeds 2500 feet per minute, ring and cylinder wear go up fast. Calculate the engine speed, at which the piston speed is about 2500 fpm, and use your tachometer as a reminder to operate below this range, to minimize wear.

Best gear shifting is obtained when the teeth of the driving and driven transmission gears are moving at about the same speed. Synchromesh transmissions in standard cars reduce some of the strain when the speeds are unequal, but with your tachometer you can practically eliminate this wear. And on trucks etc., which have no synchromesh, the tach is even more useful. Driving and driven gear speeds can easily be calculated. Synchronize your gears, simply by adjusting your motor speed to the best speed while in neutral and then shift.

If you own a sports car, or one of the smaller foreign cars, never start, pull a heavy load, or travel uphill at low rpm. To do so causes heavy wear on the connecting rod and main bearings. The tachometer will remind the driver to avoid such abuse. Since maximum torque is developed over a narrow band of engine speeds, the tachometer will help you to select the best rpm for fast passing and pulling heavy loads.

Tuneup With Tachometer. To adjust your carburetor, set the low speed adjustment (air to gas ratio) for maximum tachometer reading at idle speed. Then set the idle adjustment to the recommended value, usually between 400 and 600 rpm.

Adjust your distributor setting for maximum rpm, and then back it off slightly to compensate for the grade of gas being used. It should be adjusted for highest rpm without ping. Generally, the adjustment that yields the highest rpm gives the highest economy, power and speed.

Checking Tool Speeds. You can use the tool to measure speeds in checking performance and servicing of electric motors, drill presses, etc. Often, the rpm especially of metal working machines, is the guide to selecting or grinding tools that will cut at the proper rate of feed. Figure 11 shows the circuit needed to hook up your tachometer, with a switch to supply the pulses, and a dry cell battery. An old distributor will work fine as a switch, or you can use a snap action leaf switch, equipped with a roller. Make a cam for the shaft, or simply file a flat spot, and use a 6 volt dry cell, or low voltage rectifier for a power supply.

Using the switch as in Fig. 11, will result in the same readings as for a 1 cylinder, 2 stroke engine, since one pulse will be obtained for each revolution.

It should be noted that if you install an ordinary contact switch, as in Fig. 11, for continuous service on a rotating machine, that the life of the switch will be limited. Many makes of roller, leaf and snap switches are available; however, Switch #11-104, offered by Licon Division of Illinois Tool Works, will operate for many hours at up to 3500 rpm, and is available through distributors.


Compass Making

A MAGNETIZED sewing needle, a cork or round wood disc and a small bowl of water form this simple magnetic compass.

Take a fair-sized steel sewing needle and magnetize it by stroking it along its length with the South pole of a small permanent magnet, either horseshoe or bar type as in Fig. 2. You use the South pole of the magnet because a piece receiving induced magnetism from contact with a permanent magnet will assume the opposite polarity when separated. Thus a South pole will leave a North pole at the point of the needle and this end will point towards the North, provided that you end your magnet-rubbing strokes in the direction of the point.

Some permanent magnets are marked N and S for identification. If not, use an ordinary pocket compass to test it; the end which attracts the North pole of the pocket compass will be the South pole of the magnet (unlike poles attract), and you can mark this end with an S.

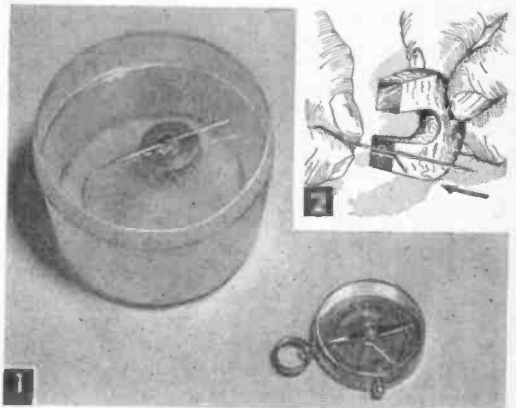The float for the needle is a $\frac{3}{8}$ in. long piece cut off from a hardwood $\frac{3}{4}$ in. diameter dowel. For the water container, use a small plastic, glass or china dish or saucer. Do not use metal. After magnetizing the sewing needle, place it on the



float and melt a drop of wax over it in the approximate center.

Checking the complete magnetic compass with a standard pocket compass (Fig. 1) shows that the needle is pointing due North. The closer you move the two compasses together, the more you will notice a slight interference between the two magnetized needles. Of course, compasses should be kept away from any iron or steel objects which might cause stray magnetic fields and result in an error.

You can arrange a cardboard ring on the top of the dish with N, S, E and W markings.—H.P.S.



Voltmeter accuracy may be checked within reason by dry cell giving 1.5 volt readings.

Repair That Old Meter!

Simple repairs on meters can easily be made by the home craftsman in his own workshop

By J. B. DEVEREAUX

BECAUSE of the delicacy of such instruments, many home shop mechanics, electrical and radio experimenters hesitate to attempt repairs of any sort on electric meters. Such timidity is perhaps justified in many cases where major repairs are required and where extensive dismantling would impose problems that would finally wind up in brushing the parts off the bench and into the waste can.

On the other hand, there are many simple ailments that can be remedied with a little patience and care and many otherwise good meters may often be restored to serviceable condition with a half-hour's tinker-




ing. We are here dealing only with moving coil meters inasmuch as they are by far the most common type in use today for direct current. For A.C. we have the moving iron meter which is also relatively simple and can be easily repaired in many instances. Where major damage has been done, and this is evident by examination, then the owner of the meter had best give up the job or send the meter back to its maker for rehabilitation.


The simple ailments that may be cured at home are frictional retardation, bad balance, overthrow and sticky needles. All other troubles are usually hopelessly beyond home tinkering without the knowledge of design and the special assembly tools and skill available to the manufacturer of the meter only.

The meter that requires tapping with the fingers to bring full reading has frictional trouble of some sort. The needles of such meters move to a certain point depending upon the current and there they stop. Thereafter if agitated by tapping, the needle will move forward for another scale unit or two. Such meters are usually troubled with dull

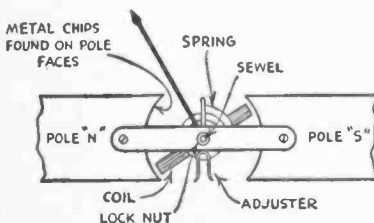Use only very small screw drivers in taking meter out of case.



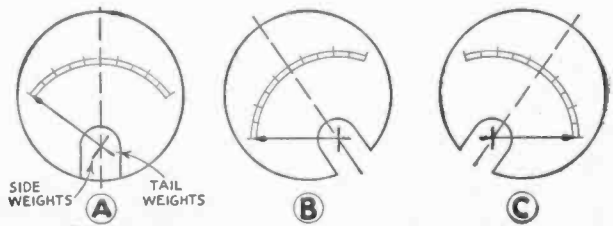1 VITAL PARTS OF MOVING COIL VOLT METERS AND AMMETERS



2 HOW TO BALANCE METER POINTER,

pivots, cracked jewels, dirty points or lint. Cracked jewels may result from dropping or other rough handling and the manufacturer only can remedy such ailments. That also goes for dull pivots. Lint may be removed by the aid of a toothpick or a piece of sharp-pointed wood smeared with a bit of light adhesive material. One must be careful, however, to see that the wood is clean and that he does not deposit more in the meter than is carried away.

Workers on meters of any kind must provide a scrupulously clean bench covered with a piece of glazed cardboard. This should be wiped clean with a moist cloth before the meter case is opened. Lintty clothes on the worker should also be avoided, it being best to roll up the sleeves. Such precautions may sound a bit silly to amateurs until it is recalled that the barest piece of foreign matter in a milliammeter or milli-volt meter can produce readings inaccurate by as much as 50%.



The meter should be uncased using the right sized miniature screw driver so that the screw slots will not be ruined. If a shunt is present, it should be left soldered in place. Removal may interfere with readings. Should the repairman find that the moving coil has been burned out by heavy current, he will know that so far as the home repair is concerned, the meter is beyond recall. The same holds true if the pivots are found to be dull. Special machinery would be required to sharpen them and a manufacturer would prefer to replace them with new ones. If the coil, spring, pivots and jewels appear sound then the meter is simply troubled with friction.

Should an examination under a magnifier reveal lint, then the stick moistened with the light adhesive may be tried. Inasmuch as these meters


have powerful magnets, they often accumulate bits of iron or steel and these often introduce frictional factors. Their removal may usually be effected with the sharpened end of a paper clip. One must make sure, however, that all metal filings are removed from the end of the paper clip wire before it is introduced into the

meter to pry off any metal chips that may already be there adhered to the magnet. Great care should be exercised in the use of this simple tool to make sure that one does not touch the coil of the sensitive spring.

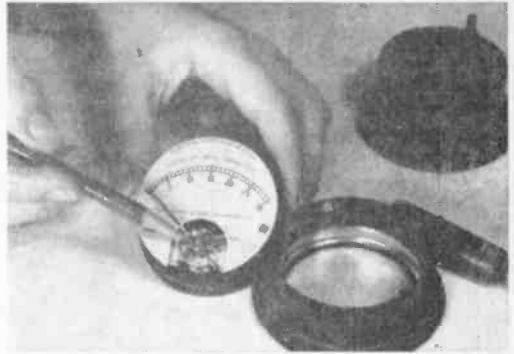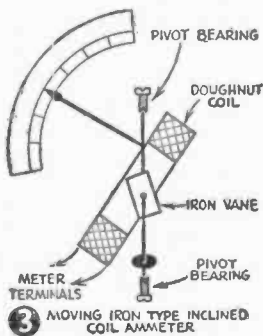If the pointer is found to be touching the dial, often the case with rough usage or dropping, then the pointer may be straightened with a small pair of tweezers but here a very steady hand will be required.



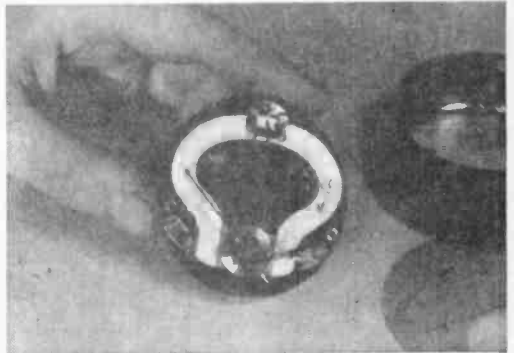Pointing to pivot bearings, which, if broken, makes factory repair imperative.



An ammeter removed from case.

Oftentimes, especially in the case of the cheaper meters, frictional losses are introduced by tight pivots. In such a case, the jewel screw may be given a half turn or so.

The meter is given a final examination before being replaced in the case. One watches especially for a hair which may have dropped in. With a really sensitive meter, this is like introducing a telegraph pole into the works.

An unbalanced meter is brought into balance by means of the simple steps, 1, 2, and 3 shown in drawing number 2. First the pointer or needle is set on zero by means of the zero adjustment screw while the meter is held in a normal or horizontal position. Then the position of the meter is shifted to that shown at B. The tail weight is then adjusted until meter pointer rests on zero. The side weight is then adjusted until pointer is on zero while holding meter in vertical position. This operation is a very delicate one and the meter may be very easily damaged, especially the pointer, if a steady hand is not used. Overthrow is often due to a bent pointer, that is, bent to the right. Sometimes in the cheaper meters a flexible tail weight is used and this must be bent one way or another to restore balance. Daubs of shellac are used at times.

Old meters that have been used near heavy transformers will usually have badly weakened magnets and these are always factors in inaccu-

racy. The only hope here is for re-magnetization or replacement with a new magnet.

A.C. meters with moving iron are treated in much the same manner. In the case of a vane moving in a close fitting chamber, lint or tiny particles of iron may cause great trouble, making the meter practically useless at times.


With such meters, the soft iron vane should not be bent since all meters of this type depend upon proper relationship here for accuracy. Any change in the position of the coil around the vanes will also result in inaccuracy.

The accuracy of small meters runs plus or minus 2% of the full scale deflection. In the case of a small voltmeter of a few volts range, simple tests for ordinary accuracy may be run

by connecting to two or more (depending upon voltage of meter) new dry cells in series, each cell adding 1½ volts. A potentiometer may also be used so that the pointer of the meter may be run up and down the scale.

A multimeter such as is used by radio repairmen may be used to calibrate such meters inasmuch as extreme accuracy can never be had with inexpensive instruments. The multimeter type of check will be quite sufficient. If the repairman does not have such an instrument then he may be asked for assistance. Calibration may be only a matter of a few minutes. In such cases, the multimeter is used with a potentiometer, the former serving as the standard for determining the calibration.

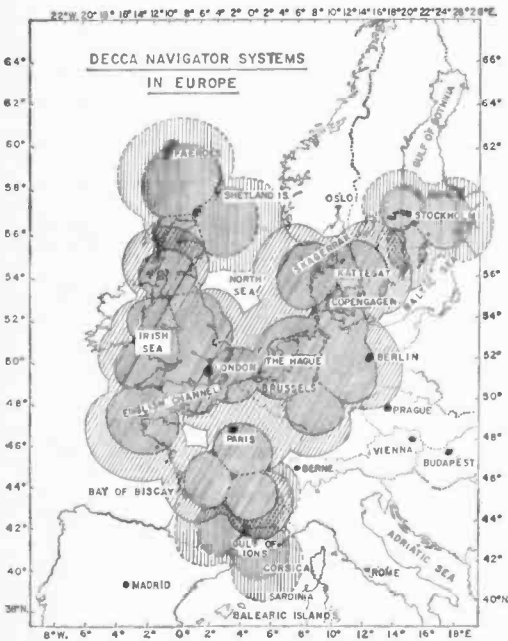Why Wait For Air Safety? By C. M. STANBURY



IS THE U. S. doing anything to improve air safety? Is Washington taking steps to alleviate air traffic congestion? Yes. If you've read any of the magazines in the radio field, you're already familiar with numerous research projects in this field, including radar which, in the future, could increase the effective air space as much as 60 times.

But why wait when the world already has a well established navigational system, a system which in many ways is more effective than even the most advanced radar? This system is DECCA.

DECCA vs. Radar. In the future radar could increase effective air space 60 times. It would do this by dividing the present 10-mile-wide airway

in three, cutting the required vertical separation in half, and reducing the distance between high speed aircraft flying the same course from 100 to 10 miles. It could do all this in the future.

DECCA cuts the width of the airway by only half; vertical separation remains unchanged. But separation between aircraft flying the same course is, within 60 miles of the terminal, cut to a mere two miles. The effective airspace is multiplied 100 times. As the distance increases from the terminal, the Master DECCA station and the congested area around them, the system gradually becomes less effective. But at the same time, the air traffic density and danger of air collisions is also diminished.

So DECCA is usually as accurate as radar will be. More important, DECCA is ready now. It has done all these things in Europe for several years and is now doing them in Eastern Canada which is the western terminus for all major North Atlantic routes.

VOR and DME Systems. The Federal Aviation Agency is not, of course, sitting on its hands waiting for this advanced radar to become operational. The FAA is spending millions of dollars for the construction of these comparatively new VHF and UHF navigation devices. A VOR (VHF Omni Range) automatically indicates the aircraft's bearing in relation to the VOR station. It is accurate to within 4 degrees. DME measures the distance from the plane to the facility. A system such as VORTAC which combines VOR and DME, can indicate for the aircraft its position so long as it is within range. Sounds like a match for DECCA, but let's look beneath the surface.

At a distance of 30 miles, VORTAC has a potential accuracy of 1 mile which would permit a minimum separation between aircraft of 2 miles. That's just what DECCA has already obtained at twice that distance. Further we haven't told you about DECCA's potential accuracy, 10 yards within 50 miles.

ICAO Turns Its Back on DECCA

At a special meeting in Montreal, the International Civil Aviation Organization voted to adopt DME as a standard short range navigational aid to go along with VOR. The action, spearheaded by the FAA, was bitterly opposed by Great Britain, Canada (previously neutral) and Australia. After the resolution had been pushed through, the head of the British delegation indicated that his country would continue to use and develop DECCA. He elaborated: "Our belief is that the need

for a high accuracy, hyperbolic system will arise much more quickly than many here today believe. Before long we will have to get together and adopt such a system." But probably the most telling objection was that of Australia, which has used DME since the war: On the basis of their unequalled length of experience, they concluded that DME, especially DME allied with VOR, could not meet the needs of the jet age. Time will tell who is right.


However, let's be generous and assume both systems to be equally accurate. DECCA can serve any number of aircraft simultaneously, DME only 50. When this number is exceeded, the system automatically accepts the 50 strongest and rejects the rest. How would you like to be riding in the 51st?

Worst of all, VOR and DME systems, because they utilize VHF and UHF frequencies, are limited to line-of-sight reception. DECCA is not. Nor for practical aeronautical purposes is DECCA affected by natural barriers such as hills or mountains. The new U. S. system is. In one month in 1958, some 40 VOR/DME navigation facilities were either inoperative, partially out of order, or in some way operating imperfectly. And this figure does not include those being relocated or re-

Every moment wasted on VOR and DME systems, when the U. S. should be building DECCA chains, costs us money and lives. In 1958 the *Electra* disaster brought this out with sickening emphasis. LaGuardia Field is equipped with the newest VOR/DME system—VORTAC—but Flight 320 still wound up in the East River. Nor was tracking via radar enough.

Speaking conservatively, if there'd been DECCA it might not have happened. The American manufacturer of DECCA, Bendix Aviation, has developed RAILS (Remote Area Instrument Landing System) which can be used where conventional ILS is inadequate. By combining DECCA, the aircraft's own absolute altimeter and a computer, the pilot is furnished with glide path guidance, distance to touch down and ground speed.

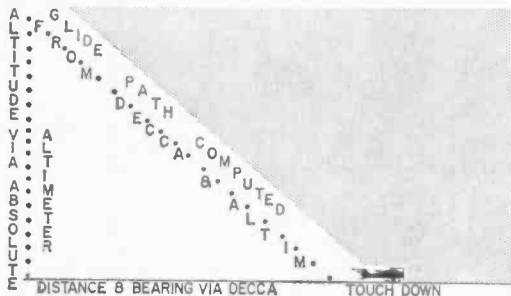Maybe Flight 320 was destined to miss the runway and no amount of technology could have saved her. But DECCA could have made her chances for survival better, while VORTAC was powerless. And there'll be more 320's. How many? That depends upon how much time we waste with VOR/DME, how long we ignore DECCA.



A control system incorporating DECCA—RAILS (Remote Area Instrument Landing System). Although the accuracy of this system is still being evaluated, chances are good it will enhance DECCA's overall superiority. At present it's only commercial use is in conjunction with the Bell helicopter service in the Dallas-Fort Worth area.

constructed. What hope has this system in such mountainous regions as the Rockies or the Alleghenies?

The Handwriting on the Sky. I have no desire to sell radar short. The radar of today, although it does not equal DECCA as a navigational aid, is already an important navigational device. In the future it will be on a par with DECCA. Most probably, they will complement each other. Radar, under those circumstances, would be an airborne system providing data on other nearby aircraft. DECCA would act as the overall, stable ground-based system. They would continually provide a cross-check on each other.


But why wait? Why fool around with VOR and DME which, considering DECCA's obvious superiority, are no better than interim measures when no interim measures are necessary. DECCA is here now.

How DECCA Works


A DECCA chain normally consists of 4 stations, a master and 3 slave stations designated red, green and purple. By measuring the phase difference between radio waves from the master station and any two of the slaves, a navigation fix is obtained and automatically plotted on a gridded chart. Because it utilizes lightweight receiving equipment and is extremely simple to operate, DECCA is suited to all types of aircraft, big or small, commercial or private.

Tape Tube Handle

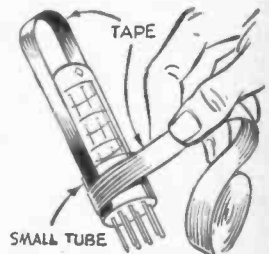• Pulling miniature and sub-miniature tubes from their sockets in crowded electronics hookups will be much easier if you provide each tube with a handle. Use a strip of masking or *Mystik* tape looped over the top of the tube and secured



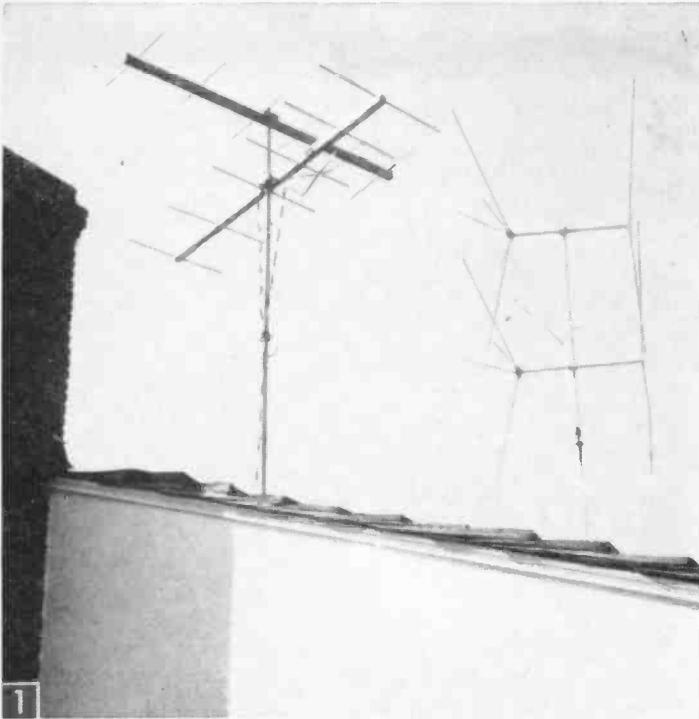around the bottom with another strip of tape. Don't use tape on tubes that heat up excessively, because of the possible danger of fire due to tape igniting. *Never* use plastic tape for this purpose as it ignites easily.—J. A. Comstock.



Completed aerials are turned toward their respective transmitters. These aerials could have been mounted on the same pole as the commercial aerial in the background.

your attic, if you have a non-metallic roof.

When carefully directed toward the desired TV or FM station transmitter, these Yagi, high-gain type aerials will give the best single (or dual) channel reception possible with any conventional antenna and are especially useful in the so-called dead or fringe areas. Though usually used to fill in the weak spots in commercial "all-channel" aerials, these antennas may be used alone or in stacks.

First, calculate the materials needed and the dimensions of the components from the information given in Fig. 2 and Tables A (for TV aerials) and B (for FM aerials).

While there are six cross pieces called for in construction of the aerials in the tables, as many as 10 could be used to improve signal strength. For extreme fringe areas, try adding two to four more directors, cut to the same length and spaced the same distance as the last director (L_6) in the table. If two close TV channels are available locally (other than 6 and 7, since the FM band lies between these channels), an aerial cut for one of these channels usually will work well for the other. One of these aerials, successfully bringing in channels 7 and 9, was dimensioned for TV channel 8, unused in the Seattle area where

Custom-Build Your TV and FM Aerials

By R. W. MONTAGUE


ESPECIALLY tailored to receive tough-to-get channels, one or several of these antennas, cut for the needed channels, can be stacked on your present television mast or mounted in

the antenna is located.

It will be noted from Table A that aerials for channels 2, 3 and 4 would be quite large, and it may be that another type of aerial might be more

TABLE A—TV AERIALS

Band	Channel	Spacing Between Cross Pieces					Total Spar Length	Length of Cross Pieces						
		S_1	S_2	S_3	S_4	S_5		L_1	L_2	L_3	L_4	L_5	L_6	
		(Inches)					S-4"	(Inches)						
Low VHF Band (54 to 88 mc)	2	41 $\frac{1}{2}$	46 $\frac{1}{2}$	38 $\frac{1}{2}$	56 $\frac{1}{2}$	55 $\frac{1}{2}$	243 $\frac{1}{2}$	96 $\frac{1}{2}$	87 $\frac{1}{2}$	83 $\frac{1}{2}$	81 $\frac{1}{2}$	80 $\frac{1}{2}$	80 $\frac{1}{2}$	80 $\frac{1}{2}$
	3	37 $\frac{1}{2}$	42 $\frac{1}{2}$	35 $\frac{1}{2}$	51	50	220 $\frac{1}{2}$	87	79	75 $\frac{1}{2}$	73 $\frac{1}{2}$	73	73	
	4	34 $\frac{1}{2}$	38 $\frac{1}{2}$	32 $\frac{1}{2}$	46 $\frac{1}{2}$	45 $\frac{1}{2}$	201 $\frac{1}{2}$	79 $\frac{1}{2}$	72 $\frac{1}{2}$	69	67 $\frac{1}{2}$	66 $\frac{1}{2}$	66 $\frac{1}{2}$	
	5	30 $\frac{1}{2}$	33 $\frac{1}{2}$	28 $\frac{1}{2}$	40 $\frac{1}{2}$	40	178 $\frac{1}{2}$	69 $\frac{1}{2}$	63 $\frac{1}{2}$	60 $\frac{1}{2}$	59	58 $\frac{1}{2}$	58 $\frac{1}{2}$	
	6	28	31 $\frac{1}{2}$	26 $\frac{1}{2}$	37 $\frac{1}{2}$	37 $\frac{1}{2}$	164 $\frac{1}{2}$	64 $\frac{1}{2}$	58 $\frac{1}{2}$	56	56	54 $\frac{1}{2}$	54	
High VHF Band (174 to 216 mc)	7	13 $\frac{1}{2}$	15 $\frac{1}{2}$	12 $\frac{1}{2}$	18 $\frac{1}{2}$	17 $\frac{1}{2}$	81 $\frac{1}{2}$	31	28 $\frac{1}{2}$	26 $\frac{1}{2}$	26 $\frac{1}{2}$	26 $\frac{1}{2}$	26	
	8	13	14 $\frac{1}{2}$	12 $\frac{1}{2}$	17 $\frac{1}{2}$	17 $\frac{1}{2}$	78 $\frac{1}{2}$	29 $\frac{1}{2}$	27 $\frac{1}{2}$	26	26	25 $\frac{1}{2}$	25 $\frac{1}{2}$	
	9	12 $\frac{1}{2}$	14 $\frac{1}{2}$	11 $\frac{1}{2}$	17	16 $\frac{1}{2}$	76 $\frac{1}{2}$	29	26 $\frac{1}{2}$	25 $\frac{1}{2}$	25 $\frac{1}{2}$	24 $\frac{1}{2}$	24 $\frac{1}{2}$	
	10	12 $\frac{1}{2}$	13 $\frac{1}{2}$	11 $\frac{1}{2}$	16 $\frac{1}{2}$	16 $\frac{1}{2}$	73 $\frac{1}{2}$	28 $\frac{1}{2}$	25 $\frac{1}{2}$	24 $\frac{1}{2}$	24 $\frac{1}{2}$	23 $\frac{1}{2}$	23 $\frac{1}{2}$	
	11	11 $\frac{1}{2}$	13 $\frac{1}{2}$	11	16	15 $\frac{1}{2}$	71 $\frac{1}{2}$	27 $\frac{1}{2}$	24 $\frac{1}{2}$	23 $\frac{1}{2}$	23 $\frac{1}{2}$	22 $\frac{1}{2}$	22 $\frac{1}{2}$	
	12	11 $\frac{1}{2}$	12 $\frac{1}{2}$	10 $\frac{1}{2}$	15 $\frac{1}{2}$	15 $\frac{1}{2}$	69 $\frac{1}{2}$	26 $\frac{1}{2}$	24 $\frac{1}{2}$	23	23	22 $\frac{1}{2}$	22 $\frac{1}{2}$	
	13	11 $\frac{1}{2}$	12 $\frac{1}{2}$	10 $\frac{1}{2}$	15 $\frac{1}{2}$	14 $\frac{1}{2}$	67 $\frac{1}{2}$	25 $\frac{1}{2}$	23 $\frac{1}{2}$	22 $\frac{1}{2}$	22 $\frac{1}{2}$	21 $\frac{1}{2}$	21 $\frac{1}{2}$	
Partial UHF Band	14	5 $\frac{1}{2}$	5 $\frac{1}{2}$	4 $\frac{1}{2}$	6 $\frac{1}{2}$	6 $\frac{1}{2}$	32 $\frac{1}{2}$	11 $\frac{1}{2}$	10 $\frac{1}{2}$	10 $\frac{1}{2}$	9 $\frac{1}{2}$	9 $\frac{1}{2}$	9 $\frac{1}{2}$	
	15	4 $\frac{1}{2}$	5 $\frac{1}{2}$	4 $\frac{1}{2}$	6 $\frac{1}{2}$	6 $\frac{1}{2}$	32 $\frac{1}{2}$	11 $\frac{1}{2}$	10 $\frac{1}{2}$	9 $\frac{1}{2}$	9 $\frac{1}{2}$	9 $\frac{1}{2}$	9 $\frac{1}{2}$	
	16	4 $\frac{1}{2}$	5 $\frac{1}{2}$	4 $\frac{1}{2}$	6 $\frac{1}{2}$	6 $\frac{1}{2}$	32 $\frac{1}{2}$	11 $\frac{1}{2}$	10 $\frac{1}{2}$	9 $\frac{1}{2}$	9 $\frac{1}{2}$	9 $\frac{1}{2}$	9 $\frac{1}{2}$	

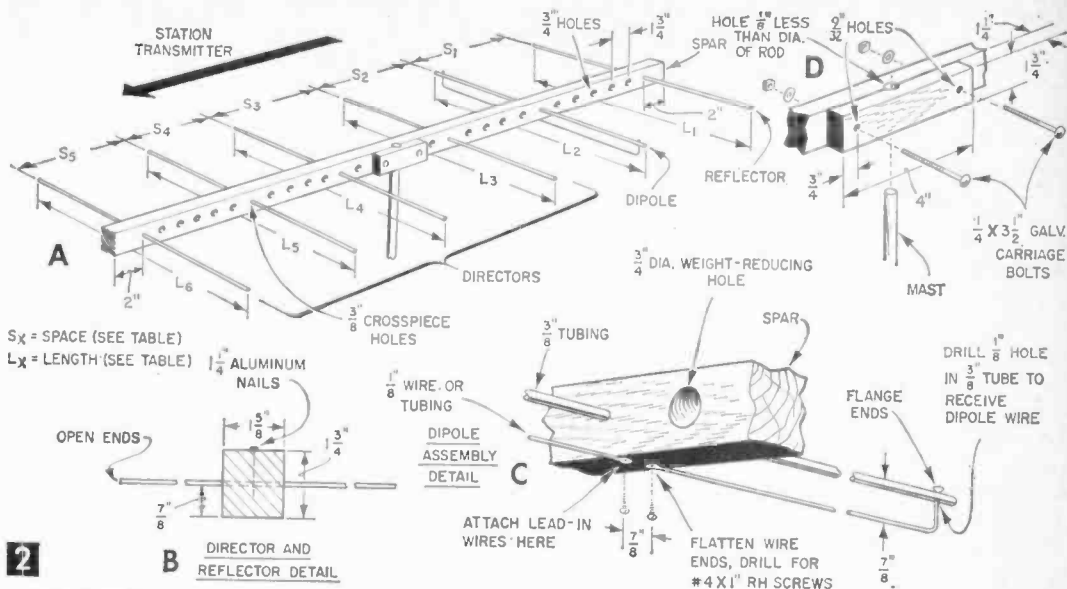

2

TABLE B—FM AERIALS

Calculate FM aerial dimensions as follows:

1. Learn the frequency of the particular FM station desired.
2. Calculate wave length in in. (W_L), using the following formula:

$$W_L = \frac{11,070}{\text{frequency (mc)}}$$

3. Prepare a table for the aerial desired, similar to those in TV aerial Table A:

S_1	S_2	S_3	S_4	S_5	L_1	L_2	L_3	L_4	L_5	L_6
.215 W_L	.240 W_L	.20 W_L	.290 W_L	.285 W_L	.495 W_L	.450 W_L	.430 W_L	.430 W_L	.420 W_L	.415 W_L

EXAMPLE

A station operating on a frequency of 98 mc would have a W_L of: $\frac{11,070}{98}$ or 112.9 (112 $\frac{2}{3}$). Following the formula above would produce these specifications for an antenna:

S_1	S_2	S_3	S_4	S_5	L_1	L_2	L_3	L_4	L_5	L_6
24.2"	27.1	22.6	32.7	32.1	55.8"	50.7	48.5	48.5	47.4	46.8"

desirable. However, the information is included in the table (which covers all VHF channels in the U. S. and Canada and some UHF) because in extremely bad signal areas this type of aerial would give the highest gain and may have to be used. Mounted in the attic these aerials would not be so conspicuous. UHF television channels higher than those given in the table are best received by other types of aerials; an extremely small Yagi would be difficult to build.

MATERIALS LIST—AERIALS

Amt.	Description
1 pc	*1 $\frac{3}{8}$ x 1 $\frac{3}{4}$ " fir, pine or oak
6 pcs	* $\frac{3}{8}$ " O.D. alum. tubing or rod (copper can be substituted)
1 pc	* $\frac{1}{8}$ " (#10) copper or aluminum wire or tubing
1 pc	1 $\frac{3}{4}$ x 1 $\frac{5}{8}$ x 4" fir, pine or oak
6	1 $\frac{1}{4}$ " aluminum nails
2	1 $\frac{1}{4}$ x 3 $\frac{1}{2}$ " galv. carriage bolts, washers and nuts
2	#4 x 1" rh screws and washers
	varnish or paint
	misc. installation hardware and lead-in wire to match individual installation (see text)

* Length determined by specifications of desired aerial.

It also may be possible to select a frequency in the middle of the FM band and get good reception for the whole band with a single aerial. This depends on individual location problems and must be decided by the wearisome method of trial and error.

Start construction by cutting the 1 $\frac{3}{8}$ x 1 $\frac{3}{4}$ -in. wood spar to the length determined as explained above. Drill the $\frac{3}{8}$ -in. cross piece holes as in Fig. 2A, spacing as in Table A or B. Also drill

a number of $\frac{3}{4}$ in. holes as in Fig. 2A to reduce the aerial's weight without loss of strength. Cut cross pieces to length from $\frac{3}{8}$ -in. O.D. aluminum tubing, the size used in commercial TV aerials, and available from aluminum supply houses or salvage yards (occasionally it is obtainable free from TV repair shops). If using salvaged tubing, first clean off with fine sandpaper. If the tubing is not available, substitute $\frac{3}{8}$ -in. O.D. copper tubing or the heavier $\frac{3}{8}$ -in. aluminum rod (available from Sears, Roebuck and Co.).

Insert cross pieces, except the dipole, in the proper holes as in Fig. 2. Use paraffin to ease the metal through the tightly-fitting holes. Center the tubes and from the top of the spar, through the tubing, drill a hole for a 1 $\frac{1}{4}$ -in. aluminum nail as in Fig. 2B and fasten securely.

Complete and assemble the dipole parts as in Fig. 2C, and check for fit. Remove one $\frac{1}{8}$ -in. wire section and insert the dipole into its spar hole. Complete the assembly, then flange the ends of the wires where they pass through the tube. In-

sert #4 x 1-in. *rh* screws with washers through holes drilled in the flattened end of the 1/8-in. tubing. These screws must be the same distance apart as the distance between the upper and lower dipole tubes. Lead-in wires will be attached to these screws.

At the center of your aerial, located by measuring and balancing, clamp a 1 1/8 x 1 1/4 x 4-in. piece of wood stock. Center a 1/4-in. hole 3/4 in. from each end of the block (Fig. 2D), insert 1/4 x 3 1/2-in. galvanized carriage bolts, washers and nuts, and draw up tightly. Center a hole in the top of this assembly, sizing it 1/8 in. under the diameter of the roof or attic aerial mast (usually a 1 1/4-in. dia. pole) and drilling with an expansive bit or hole saw. Apply at least three coats of spar varnish or marine quality paint to the now-finished antenna, allowing plenty of drying time between coats.

Install the aerial as in Fig. 2A, with the directors closest to the transmitter of the station desired. Where two stations will be brought in by the aerial, the latter will probably be best directed between the two transmitters. Try it before fastening permanently in place.


There are so many variables involved in aerial installations that it is impossible to describe one lead-in hookup that will work well in each case.

The trial and error method must usually be resorted to in the end. It sometimes is possible to just tie lead-in wiring for the new aerial almost any place into the existing lead-in wire to the set (using standard 300 ohm double-strand television wire) if the new aerial is being used to supplement another aerial. If this doesn't give a good picture or interferes with other channels received, a hi-lo coupler may be needed. Low-band channels (2 through 6) will probably have to be led in through a coupler if high band channels (7 through 13) are also received. As a last resort, a completely separate lead-in wire may be used by coupling into an antenna switch (available from TV supply stores, Allied Radio, Dept. SM, 100 N. Western Ave., Chicago 80, Illinois or Sears, Roebuck & Co., Chicago) at the back of the television set. However a 40¢ double-throw knife switch available in hardware stores would serve, though less conveniently. When the aerial is installed and hooked up, make fine direction adjustments by turning the aerial slightly in each direction until the best picture is obtained.

These aerials can be stacked on one roof pole about a foot apart, if desired, although aerials pointing in the same general direction should be two feet or more apart, if possible.

Roll-Up Aerial


• Stronger and clearer radio signals from greater distances are possible with an aerial made from a roll-up steel rule. To mount the rule cut a hole in the top of the radio cabinet and bolt a fiber washer to the hole so that the rule will not ground against the cabinet. Insulate rule housing from the set with friction tape, and fasten the housing to the cabinet with a strip of metal bolted to the cabinet. Solder one end of a length of insulated wire to the rule housing, and connect the other end to the aerial terminal of the set as shown in photo below. Range and volume increase as the rule is pulled out and are reduced as the rule is pushed in.—M. A. TIDD.

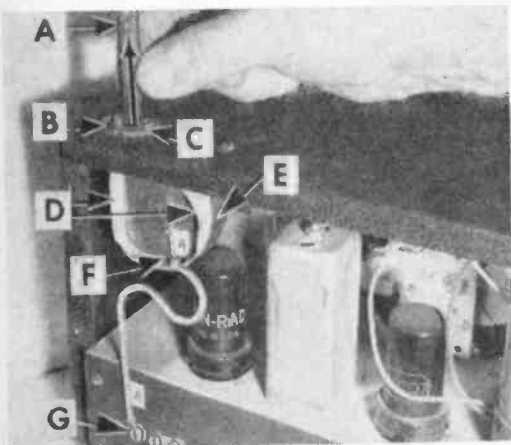

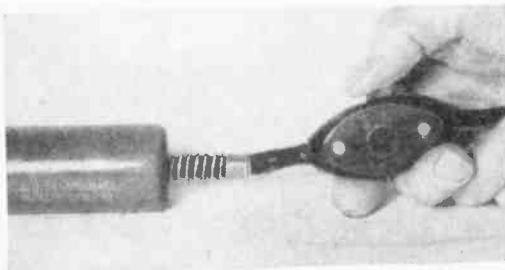
(A) Steel rule, (B) fiber washer, (C) bolts, (D) friction tape, (E) metal strip, (F) solder wire to case, (G) aerial terminal.

Soldering-Iron Switch

• Install a feed-through tumbler switch with "on" and "off" markings on it on the cord of your electric soldering iron close to the handle, as



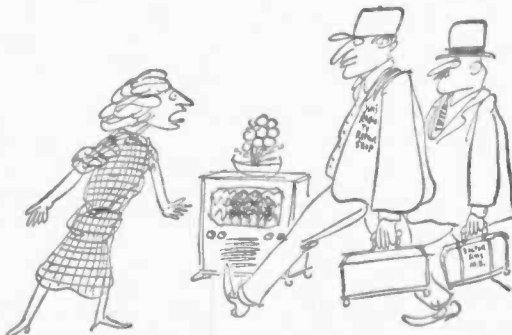shown in the photo. The iron can be kept plugged in while in use and simply turned on or off as needed.—ARTHUR TRAUFFER.



Thank goodness, you're here! My husband is sick in the bedroom—and Jack Paar's all blurry!

Experimenting with a one-stage audio amplifier.

THERE are two possible approaches to follow in obtaining a radio lab kit. One is to acquire the parts yourself and make up your own kit. The second approach, and the approach that I consider best for beginners, is to buy a commercial kit. I tried both approaches.

The home-rolled version was built on a miniature perforated bakelite board. The board layout, component placement and preliminary wiring are shown in Fig. 2 (front) and Fig. 3 (back). Lay out and drill the board first. Shorten the volume control shafts to $\frac{3}{8}$ in. length with a hacksaw. Solder leads about $1\frac{1}{2}$ in. long on the transistor sockets. Mount the parts and complete the wiring to the interconnection lugs (called "flea clips"). Fill the portions of the flea clips that protrude from the front of the board with solder for increased rigidity. The transistor sockets are held in place with Duco cement. Bend the leads tightly against the board as an added precaution.

A separate battery board cut from a piece of perforated Masonite (see Fig. 4) was provided, the batteries held in place with rubber bands. Brackets provided with machine screws make terminal contact. A third bracket provided with a metal spring cut from a tin can makes the connection between the two rows of batteries. The experimental board may be mounted on the battery board with brackets, or it may be used unattached as shown in Fig. 4.

The hook-up of Fig. 4 is the simple one-transistor audio amplifier shown schematically in Fig. 5A. A number of additional, but by no means all of the circuits that can be built with the home-rolled lab kit are also shown in Fig. 5. The resistors and all of the capacitors aren't mounted on the board. They were originally connected by plugging them into the flea clips. However, this wasn't too satisfactory and mini-gator clip leads were adopted for all connections.

The audio one-transistor amplifier of Fig. 5A has very low volume. If another transistor amplifier is connected in front of this amplifier, the two-transistor amplifier of Figure 5B results, with much greater volume. The transistor configuration used is known as the common emitter circuit because the emitters of the transistors are both connected to an input terminal and the common battery terminal. The capacitors between collector of T2 and between the base of T1 and volume control center terminal and base of T2 are provided to allow all audio signals to pass, but to prevent transistor bias voltages from being upset. A capacitor has low impedance for ac voltages, but it has (ideally) infinite impedance




Learning Electronics By Experimenting

"Breadboard" experimentation is a logical way for a beginner to learn electronics, and the approach has considerable merit for the old-timer, too, because it allows him to try his ideas quickly with comparatively conventional parts


By FORREST H. FRANTZ, Sr.

for dc voltages. The resistors in the circuit establish the dc bias voltages on the transistor elements that are required to make the transistors function.

It is apparent then that there are two basic groups of voltages that you are concerned with in any piece of electronic equipment. One is the voltage required to make the transistors or tubes function at all—the dc bias voltages. The other is the signal voltage which is the voltage of interest. The dc bias voltages are somewhat like the gasoline requirement in an automobile and might be thought of as fuel supplied at the right place in the proper amount. The input signal voltage corresponds to the driver's demands of the automobile which he injects at the input in the form of throttle and steering commands. The

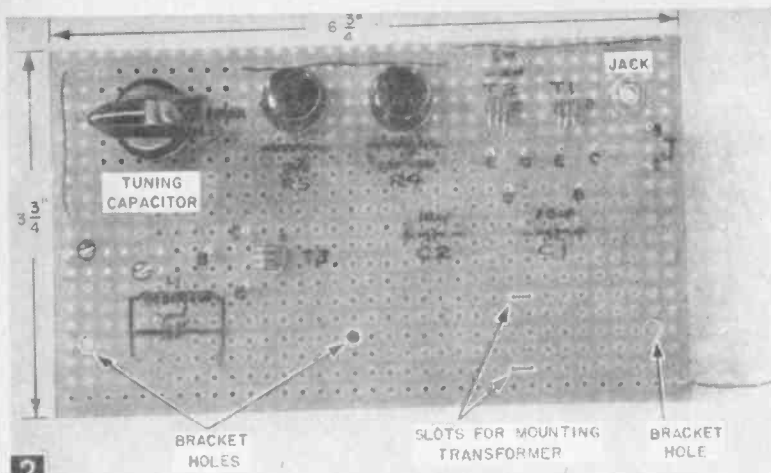

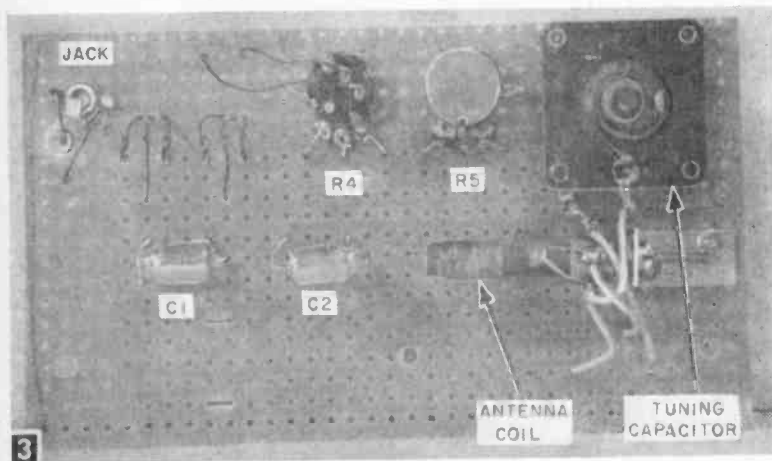2 Front view of home-made lab kit circuit board.



3 Back view of home-made lab kit circuit board.

input signal is handled by the electronic equipment as required (in this case it's amplified) for the desired output. The mechanical, electrical, and pneumatic systems of an automobile operate on the driver's input signals in an analogous way to provide the required energy and direction at

Well, all electronic equipment has an amount of noise associated with it. Although this noise is very low, the amplifier will build it up to a point where the transistor characteristics, part values, and *dc* operating voltage in the circuit limit the output signal size. But at this point, the output signal is high enough to be useful. A key connected in one of the leads from the battery to the amplifier as shown in Fig. 5D would permit quick turn-on and turn-off of the oscillator, and the unit could be used as a code practice set.


Figure 5E is a crystal detector tuner which may be added to the amplifier of Figure 5B to produce a broadcast receiver. The coil-capacitor combination builds up the radio frequency (RF) voltage received from the antenna at a particular frequency determined by the tuning capacitor setting. The tap on the coil permits the signal to be fed to the crystal diode without disturbing the tuning. The crystal diode is a unidirectional device; that is, it passes a signal readily when the anode side is plus, but impedes the signal when it's minus. The waveforms show: A, an RF signal which is the carrier and has the fre-

the wheels. The two-transistor amplifier may be used with the microphone (as shown) or with a phono pick-up, or with a radio tuner.


If the amplifier output is connected to the amplifier input as shown in Fig. 5C, an audio oscillator is created. An oscillator is a device that converts *dc* operating voltage into an *ac* signal. It may be thought of as an *ac* generator driven by a *dc* voltage. The advantage of an electronic generator (oscillator) is that the frequency may be varied and controlled very readily. The frequency of Fig. 5C may be varied by adjusting the control that functioned previously as a volume control for the amplifier.

The principle of the oscillator's operation is that a part of the signal at the output is fed back into the input and is continually recirculated. The amplifier action of the basic unit builds the signal at the input back up to the proper level for the output signal continuously.


How do you start it?

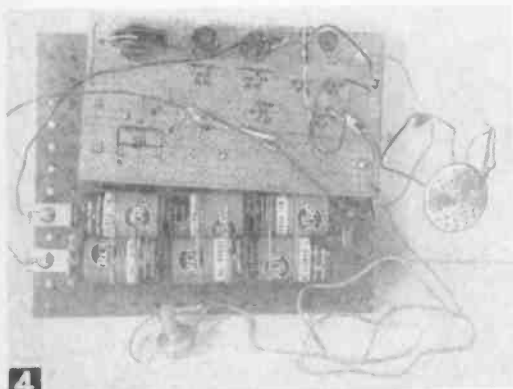


4 One-stage audio amplifier hook-up.

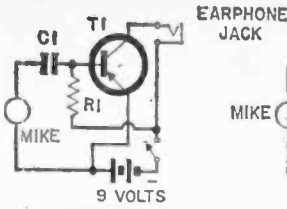


A 1-TRANSISTOR AUDIO AMPLIFIER

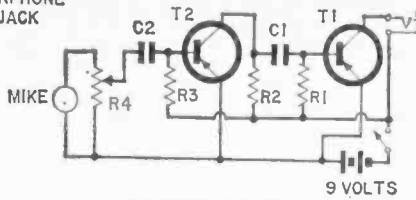


B 2-TRANSISTOR AUDIO AMPLIFIER

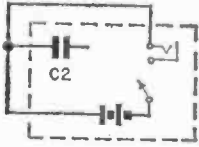

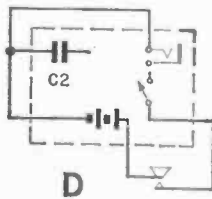C WITH MIKE DISCONNECTED FROM CIRCUIT 5B AND FEEDBACK CONNECTION SHOWN, YOU'VE CREATED AN AUDIO OSCILLATOR




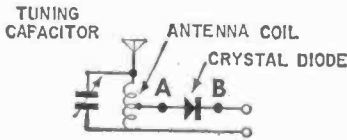D KEY IN SERIES WITH BATTERY LEAD CONVERTS UNIT OF 5C TO CODE PRACTICE OSCILLATOR



E SIMPLE TUNER CONNECTED IN PLACE OF MIKE IN 5B CONVERTS UNIT TO SIMPLE RADIO

WAVE FORMS

 


WITH BY-PASS CAPACITOR FILL-IN

quency of the capacitor-coil tuned combination modulated in height (amplitude) by an audio signal which is the desired signal information; B, the signal rectified (negative excursions chopped off) by the diode as it would appear between the crystal diode cathode and common if no capacitance appeared across these terminals; and C, the audio signal that appears at these terminals due to alternate charging and discharging of a capacitor connected across these terminals. In the case of the simple receiver consisting of this detector and the amplifier of Figure 5B, this fill-in is provided by the capacitance of C2 through the base to emitter circuit of T2 and the stray wiring capacitance of the circuit.

The Commercial Kit. This kit (Knight 10-Circuit Transistor Lab Kit, Allied Radio Catalog No. 83Y299, \$15.75) costs a little more than the basic, home-rolled version just described, but with it you can perform twice as many experiments.


Figure 6 shows the parts and instructions furnished with the kit. There's a preliminary wiring manual which describes the basic assembly in step-by-step and pictorially illustrated detail, and a folder with general soldering and construction information. A set of cards showing how to make plug-in connections between the various parts for each of the 10 circuits is included with the kit. The card for a given circuit fits on the board as shown in Fig. 7, and connections are made with plug leads. There is also a manual of experiments provided in the kit. This manual shows a pictorial and a schematic diagram for each circuit and provides

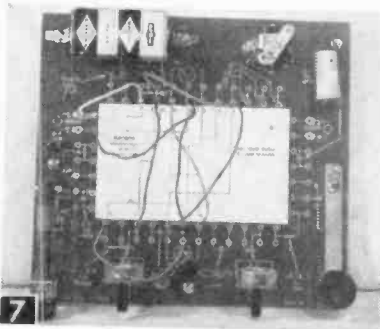

The Knight 10-in-1 Transistor Lab Kit with the Electronic Switch Circuit set up.

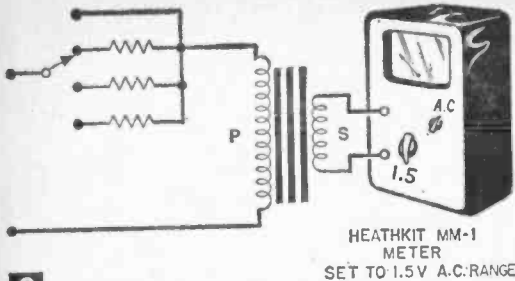Parts and instructions furnished with Knight 10-in-1 Transistor Lab Kit.





8 BASIC ARRANGEMENT

a text explaining how to adjust and use it, how it works, and how to apply the circuit. In addition to this specific information for each circuit, the manual has sections on how radio works, transistors, capacitors and resistor color codes, and electronic symbols.

The 10 circuits which may be built with the Knight Kit are: a two-stage broadcast radio; a photoelectric relay; a wireless broadcaster; a code practice oscillator; an electronic switch; a two-stage audio amplifier; a capacity operated relay, an electronic timer; a voice operated relay; and an electronic flasher.

The Knight Kit may also be used for additional experiments and hook-ups, the only limit being the ingenuity of the builder. For example, with an external multimeter, you can measure voltages across various circuit elements. You're cautioned to use a 20,000 ohm-per-volt meter or vacuum tube voltmeter (VTVM), however, since lower sensitivity meters will upset the circuit seriously and may even damage components. Currents may be measured by replacing connecting leads with a meter. And the number of experiments that can be performed can be increased by using components external to the Lab Kit board. Thus, a supplementary board with two transformers, two transistor sockets, a few resistors and capacitors, and a loudspeaker would allow you to add several kinds of amplifiers to the basic audio amplifier, broadcast receiver, or code practice oscillator. The extra parts and board would permit you to add a one-transistor transformer-coupled Class A output stage, a one-transistor-resistance coupled output stage, a two-transistor Class A transistor-coupled output amplifier, a two-transistor Class A resistance-coupled output amplifier, a two-transistor Class B transformer-coupled output stage, and a two-transistor complimentary symmetry output stage. Thus a parts investment of from \$10 to \$15 adds six circuits—probably more for the ingenious experimenter—and would provide a comparatively thorough lab course in audio amplifier circuits.

Transformer Principles. Since, in amplifiers, the plate load impedance of an output tube is always much greater than the low impedance of the loudspeaker voice coil which it drives, a voltage step-down transformer from output tube to speaker is necessary to make the speaker look like a high impedance to the tube, and the tube

a low impedance to the loudspeaker. The same technique may be used to increase the input impedance, and hence the ohms-per-volt sensitivity of an ac voltmeter. The advantage of using a transformer to increase meter impedance is that no tubes, transistors or operating power are required.

The chief advantage of a high input impedance ac meter is that circuit loading is reduced and circuit measurements for which 1,000 ohms-per-volt or even 5,000 ohms-per-volt ac meter sensitivities would be inadequate are brought within reach. Another advantage is that ac voltmeters employing the higher quality (better frequency response) miniature transformers to increase input impedance are extremely portable, wide frequency instruments. This is particularly true if germanium diodes are used for rectification in the meter.

TABLE A—SIMPLIFIED IRON CORE TRANSFORMER THEORY

P = Power (watts) I = Current (amperes)
 V = Volts Z = Impedance (ohms)
 Subscripts: p = Primary s = Secondary


For an Iron Core Transformer correctly terminated, efficiency approaches 100%. Then,

- (1) $P_p = P_s$ (Z_p and Z_s are assumed resistive)
- (2) (a) $I_p^2 Z_p = I_s^2 Z_s$ (b) $\frac{E_s^2}{Z_s} = \frac{E_p^2}{Z_p}$
- (3) (a) $Z_p = Z_s \frac{I_s^2}{I_p^2}$ (b) $Z_p = Z_s \frac{E_p^2}{E_s^2}$
- (4) (a) $I_p^2 = I_s^2 \frac{Z_s}{Z_p}$ (b) $E_p^2 = E_s^2 \frac{Z_p}{Z_s}$
- (5) (a) $I_p = I_s \sqrt{\frac{Z_s}{Z_p}}$ (b) $E_p = E_s \sqrt{\frac{Z_p}{Z_s}}$

To get a feel for what you can do with transformers in this application, let's take a quick look at some examples. Table A summarizes the applicable formulae and theory used in the examples.

A Heathkit MM-1 Volt-Ohm Milliammeter has an ac sensitivity of 5,000 ohms-per-volt. The lowest ac range is 1.5 v. The meter input impedance for this range is 5,000 x 1.5 or 7,500 ohms. The meter will be set to the 1.5 ac v range for all measurements, and series resistances in the transformer primary circuit (Fig. 8) will be used to increase range. To increase the input impedance from 7,500 ohms by a factor of 100 to 750,000 ohms would require a transformer with a 750,000 ohm primary and a 7,500 ohm secondary.

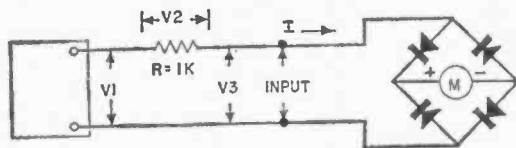But, in changing the meter impedance with the transformer, the input voltage required for full



AUDIO SIGNAL GENERATOR

9

Basic ac meter, consisting of germanium diode bridge and dc mill- or microammeter, plus instrumentation for determining input impedance and sensitivity (see Table B, next page).

scale meter deflection will be changed. The transformer primary voltage for full scale meter deflection is calculated with equation 5b on Table A:

$$E_p = 1.5 \sqrt{\frac{750,000}{7,500}}$$

$$E_p = 15 \text{ volts}$$

The new sensitivity of the meter is 750,000 ohms-per-15 volts or 50,000 ohms-per-volt!

For ranges other than 15-v full scale, the multiplier series resistance will be 50,000 times (Voltage Range minus 15). Thus, for the 50-v scale, the multiplier resistance is 50 x (50 - 15) kilohms, or 1.75 megohms.

This can be improved, however, and approached more practically. The lowest range (15 v) has a low dc resistance in spite of its high ac impedance. This might interfere with circuit op-

TABLE B

In Fig. 9, signal generator output is adjusted for full scale deflection of meter "M" at 1,000 cycles, V_1 and V_2 are measured with an audio voltmeter such as the Heathkit AV-2.

Then:

- a) $V_3 = V_1 - V_2$
- b) $I = \frac{V_2}{R}$
- c) $Z_{in} = \frac{V_3}{I}$

For example 2, measured values are:

$R = 1K, V_1 = .75V, V_2 = .15V.$


Then,

- a) $V_3 = .75 - .15 = .6v$
- b) $I = \frac{.15}{1000} = .15MA$
- c) $Z_{in} = \frac{.6}{.15 \times .001} = 4,000 \Omega$

and $\sim V$ sensitivity = $\frac{4000}{.6} = 6,650 \frac{\Omega}{V}$

eration. A capacitor (0.1 mfd or larger) in series with the primary will eliminate this possible source of trouble. A transformer that has the correct impedance used might be difficult to find at a reasonable price. A considerable reduction in transformer impedance can be tolerated if the impedance ratio is unchanged without changing the final ohms-per-volt sensitivity. For this example an impedance ratio of 50,000 ohms to 500 ohms will be satisfactory if the transformer can handle the input signal level linearly.

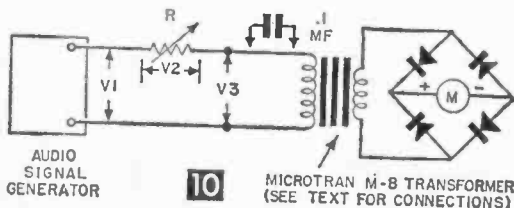If the lowest range of the basic meter in our first example had been 5 v, the new lowest ac range would have been 50 v. This would have



Method used for experimental verification of calculations: $V_1 = 5$ volts; R (60,000 ohms) adjusted for full-scale deflection of M . V_2 was 1.9 volts. Calculated value of Z_{in} is 103 K ohms, sensitivity is 33,400 ohms per volt using the measured values.

MATERIALS LIST—HOME-MADE TRANSISTOR LAB KIT

Design.	Description
R2	10K, $\frac{1}{2}W$ resistor
R1, R3	220K, $\frac{1}{2}W$ resistor
R4	10K miniature volume control with switch (Lafayette VC-28)
R5*	50K miniature volume control (Lafayette VC-36)
C1, C2	10 mfd., 15v. miniature electrolytic capacitors (Lafayette CF-122)
	tuning capacitor (Lafayette MS-215)
	antenna coil (Lafayette MS-299)
T1, T2	transistor (Raytheon CK722 or GE 2N107)
D	diode (GE 1N64)
	three transistor sockets (Lafayette MS-149)
	flea clips (Lafayette MS-263)
	miniature perforated board (Lafayette MS-305)
	two miniature knobs (Lafayette MS-185)
	one pointer knob (Allied 55H074)
	miniature phone jack (Lafayette MS-282)
	minigator clips for connecting leads (Mueller 30)
	perforated Masonite board (Lafayette ML-81)
	brackets
	six batteries (Burgess #1)


* Not used in any of the circuits presented in text, but handy to have for experimental work.

been objectionable. Here's an approach that can be applied to a multimeter or even a basic dc meter movement which overcomes this objection. The Heathkit MM-1 meter cited in example 1 has a 150 microampere lowest current range on the selector switch. Set the meter to this range and connect it to a rectifier bridge consisting of 4 Raytheon 1N66 diodes (see Fig. 9). Instrument the circuit as shown in Table B. The input impedance of the rectifier-meter combination is 4,000 ohms for full scale meter deflection. The sensitivity was 6,650 ohms-per-volt.

Next, the meter-bridge combination was connected in the circuit shown in Fig. 10. The transformer, a Microtran M8, was connected for 15,000 ohms primary impedance (red and blue leads), and 600 ohms secondary impedance matching (brown and violet leads). The impedance ratio is 25, and the square root of this ratio is 5. The transformer primary impedance predicted by the theory is 25 x 4,000 or 100,000 ohms, and the sensitivity is predicted as 5 x 6,650 or 33,200 ohms-per-volt. The voltage input to the transformer primary for full scale deflection should be 100,000 ohms divided by the sensitivity, 33,200 ohms-per-volt. The predicted primary voltage is 3 v. The actual voltages measured in the circuit are given in the caption for Fig. 10. Using the method shown in Table B, these voltages yield the same results as those predicted above within a reasonable percentage of error.

The linearity of the instrument can be improved by setting the meter pointer about 3% to 5% up scale from zero.

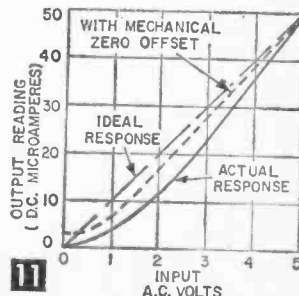The linearity of a transformer-diode-rectifier-meter type ac voltmeter can be improved by off-setting the meter needle from zero and calculating series resistance for exact fit at full scale.



Use the mechanical zero set with zero voltage input to do this. Do it before the measurements shown in Fig. 9 are made. This automatically accounts for the upscale dial position in calculations and adjusts the full scale point. The results of the technique are shown in Fig. 11.

It is apparent that the method of the second

example provided a lower bottom ac voltage range than the first method. This improvement resulted from the increased sensitivity of the rectifier-meter combination and the lower impedance ratio of the transformer windings. The decrease in transformer impedance ratio reduced the sensitivity.

ELECTRONICS ANAGRAM

Here is an anagram puzzle that will challenge your knowledge of electronics. To be absolutely sure you do

not fill in the wrong word or abbreviation, read each clue very carefully. Many are designed to intentionally mislead.—JOHN A. COMSTOCK

(For the solution, see page 154.)

ACROSS:

- 1) A point of maximum current or voltage in a stationary wave system.
- 3) Form of phono turntable drive.
- 5) Done with an insulated tool to avoid detuning effects of body capacitance.
- 8) Volt-ampere (abbr.).
- 9) A concentrated number of these will burn the screen of a cathode-ray tube.
- 10) Unit of loudness.
- 11) Volts times amperes.
- 14) Carries electrons in motion.
- 15) Capacitors block it.
- 17) A type of frequency meter.
- 19) The rms value of an alternating current wave.
- 20) One-millionth of an ampere.
- 21) A radiator of electromagnetic waves.
- 22) Inductive opposition to ac (abbr.).
- 23) Done to locate a microphonic tube.
- 24) A particular type of test instrument widely used (abbr.).
- 25) Potential placed on a certain vacuum tube element (letters symbol).
- 27) Done to improve operating characteristics of electronic components.
- 28) An amplifier that handles power (abbr.).
- 29) A TV station's pic-

- ture signal is put on a carrier wave in this manner (abbr.).
- 30) A circuit that can bite.
- 31) Matching transformer.
- 32) A primary color used in color TV.
- 35) Unit of conductance.
- 36) What a volume, gain, or tone control is.
- 37) A coil that opposes RF currents.
- 39) Connection not made (abbr.).
- 41) Figure of merit (letters symbol).
- 42) Transformer, trimmer (letters symbol).
- 43) EMF unit.
- 44) Capacitance (letters symbol).


- 45) Single side band (abbr.).
- 46) A noise made by electrons in vacuum tubes.
- 49) Modulation similar to frequency modulation (abbr.).
- 50) Term connected with 'scopes.
- 51) Main oscillator (abbr.).
- 54) An inert gas (abbr.).
- 56) What a ham calls his radio outfit.
- 57) Controlled by radio (abbr.).
- 58) An antenna system of two or more vertical radiators.

- 4) A particular type of transducer.
- 5) The electron catcher of a vacuum tube.
- 6) Code that is periodically interrupted.
- 7) Number of interconnected stations.
- 12) The kind of signal ordinarily superimposed on a carrier wave (abbr.).
- 13) Captures certain frequencies and disposes of them.
- 16) A positive ion.
- 18) To eliminate audio echoes.
- 19) Same meaning as #5 down.
- 20) Same as #20 across.
- 26) Plays recordings.
- 33) Voltage drop measured across a resistor (letters symbol).

DOWN:



- 1) An electro-acoustic unit of power.
- 2) Fleming invented the first one.
- 3) To send radio waves into space.

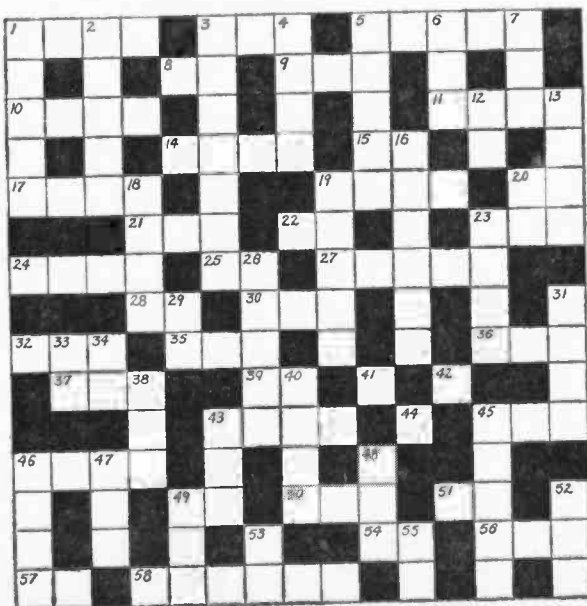- 34) A device that finds directions.
- 38) A tube that utilizes an electron gun (abbr.).
- 40) Temporary connector.
- 43) A meter that measures volts, ohms, and amperes (abbr.).
- 45) Might blow a fuse.
- 46) Emits sound waves (abbr.).
- 47) A meter rating.
- 48) Type of transistor (abbr.).
- 52) A gain compensating circuit (abbr.).
- 53) Output power.
- 55) C-bias (letters symbol).



Portable Earphone Plug Box

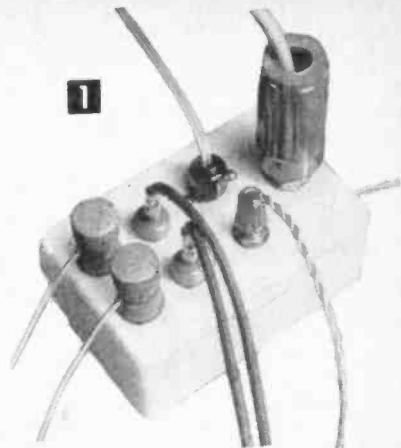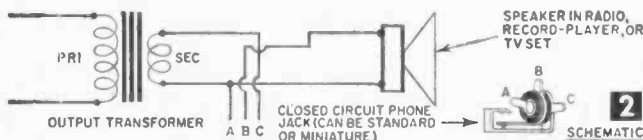You can quickly connect various sizes and types of earphone jacks to your radio, Hi-Fi, recorder or TV set with this versatile "Jack in the Box"



HERE'S an easy project for you Hi-Fi fans and experimenters who are so often annoyed by the fact that earphones as well as radios, record players, recorders, etc. come with non-interchangeable plugs and jacks.


If you want to plug in earphones that fit one piece of equipment, into another, you may have to either cut the wire and put on a new plug, or make a special adapter—by then, the program you wanted to hear is over. Here is an unusual answer to the problem; a plug box (Fig. 1) that accepts every common kind of plug. Also, it can be used to connect several earphones, or speakers at once, and will come in handy for test work and hi-fi experimenting.

Figure 1 shows a 3 x 2 x 1 1/4" deep hinged plastic box. In its lid are mounted two binding posts, a pair of standard phone tip jacks, and three other commonly used phone jacks. You don't need a blueprint giving sizes and locations of holes. In fact, you may want to modify the layout to fit the special needs of your equipment. Just mount the parts where you please, making sure they are not too crowded. All the holes are quickly made by reaming up to size with the small pointed end of a pen-knife blade.

Wire all the plugs in parallel (Fig. 2), with 20 gage solid copper wire soldered at each connection. If the spring prongs on the large phone jack are too long, bend the ends over to fit. Solder a length of light twin lead, or twisted lead wire to the prongs of the phone jack, and bring it out through a hole in the box side.

The phone box is connected to the radio, record player, or TV speaker through a circuit

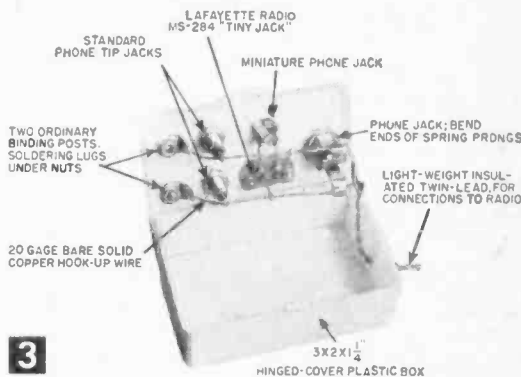Built in less than an hour, this "Jack Box" accommodates five kinds of non-interchangeable earphone and speaker connections, permitting instant hookup of many combinations.



Holes in plastic box lid for mounting parts are reamed up to size with small knife blade. The jacks are wired in parallel, with solid copper hook-up wire.

opening jack. When the phone box is plugged in, the speaker is off; remove the plug, and the speaker is automatically reconnected.

Some ac-dc table radios ground one side of the output transformer, and of the speaker coil, directly to the chassis. If there is a wire leading from one side of the speaker coil directly to the metal chassis, your set is this type. With such a set, your earphones would be "hot" when the power plug of the radio is inserted one way into the power outlet. Eliminate the hazard simply by unsoldering the two chassis connections and wiring them directly together without electrically contacting the chassis.

Before touching any chassis parts, especially of TV sets, pull the power plug, and discharge the high-voltage capacitors, which can cause fatal shock.

If you are a stereo fan, you will easily be able to adapt the plug box to a "twin channel" design. A larger plastic box will provide space for mounting two sets of jacks, and the unit will make it easy to experiment.—ART TRAUFFER

MATERIALS LIST—PHONE PLUG BOX

No. Req.	Size and Description
1	3" long x 2" wide x 1 1/4" plastic box with deep-hinged cover (available in 10-cent stores, etc.)
1	Standard single phone jack, Switchcraft #12B (Allied 41H-632)
2	Miniature phone jacks of the type needed to fit your plugs
2	Standard phone tip jacks
2	Standard binding posts, with soldering lugs to fit
1	Short length lightweight insulated twin-lead, or twisted-lead wire

Misc. Machine screws, nuts, washers as required

Save Over \$90—Build Your Own ELECTRIC GUITAR

By J. EVANS KNAPP

Craft Print Project No. 277



2




1

Perfect formula for serenading a lovely lady: one electric guitar, playing through the phonograph connection of a table-model radio.

VERY few instruments have enjoyed the meteoric rise in popularity the guitar has in recent years. Long established as an ideal portable instrument for accompanying ballads, country and western singers, the guitar of not so many years ago still had its limitations. One was that its music was too soft to be used in orchestras (or at noisy parties).

That's not true today, thanks to the magic of electronics. For, when you hook up an amplifier to a guitar, you automatically give it the same stature as a piano—and far more versatility. You get, not only a full range of volume, but a complete control of tone—everything from throbbing base for rhythm chords to pure, treble melody notes to lead or back up the singer. You find, suddenly that guitars can “talk” sweet or sassy, soft or sharp, boogie beat or ballad strum.

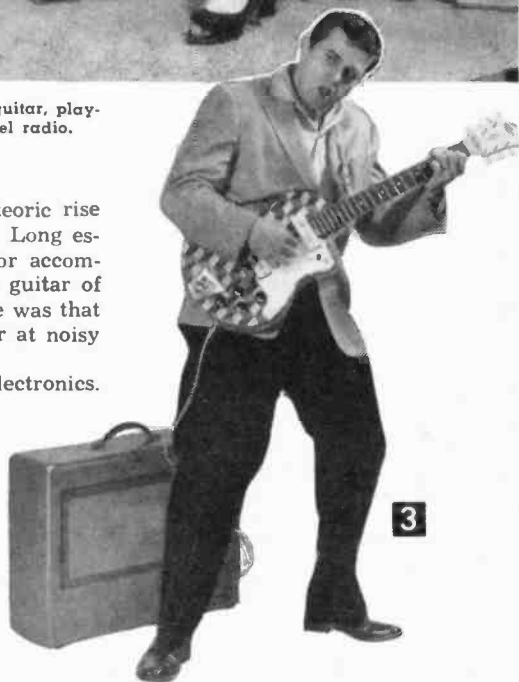A good guitar deserves a good carrying case. Make the box dimensioned in Fig. 20A, using glue and $\frac{3}{4}$ in. nails at all joints. Then, mark a line on the ends and sides 2 in. from the top and saw the box in two parts, making a top and bottom section. Sand all edges, rounding them



3

Electric guitar hooked up to a commercial music amplifier. Looks as if this fellow enjoys his rock-billy crooning.

gage, draw a second line around the pattern $\frac{5}{32}$ in. from the first line. Starting at the top of the body design as indicated in Fig. 5, saw the five bending form pieces to shape on a bandsaw or jigsaw. The material between the two lines is waste, so make your saw cuts in this waste material leaving just a trace of the penciled lines on the center and outside form sections. Two saw cuts will be required. With the center portion cut out, rout out a $\frac{1}{2} \times \frac{1}{2}$ in. rabbet around the top corner as shown in sec. A-A of Fig. 4, to provide clearance for the $\frac{3}{8} \times \frac{3}{8}$ in. beading. Then saw the outside form into four sections.


Make the steam box Fig. 6 next. Set it up on a low bench or box and prop up one end with some house bricks or block of wood. To generate the steam, place a tea kettle on a hot plate and attach a short length of hose over the kettle spout. Insert the other end of the hose into the steam box and stuff some rags around the hose to hold it in place.

You are now ready to start the actual construction of the guitar by steam bending and forming the body sides. For this you will need a $\frac{3}{32} \times 1\frac{1}{8} \times 60$ in. piece of maple. Since this thickness cannot be purchased, rip a $\frac{3}{16}$ in. thick strip with a circular saw from the $\frac{3}{4} \times 2\frac{1}{4} \times 60$ in. piece of stock called for in the materials list. Dress this strip down on a thickness planer to $\frac{3}{32}$ in. If you do not have a planer, you can use a jointer by backing the strip with a length of scrap stock to support it while pushing it through the jointer. A belt sander could also be used. However, in this case rip the stock $\frac{1}{8}$ in. thick and sand to $\frac{3}{32}$ in.


Place the finished piece on edge in the steam box and stuff the top of the box with rags. When the water in the kettle begins to boil steam will fill the box and saturate



8

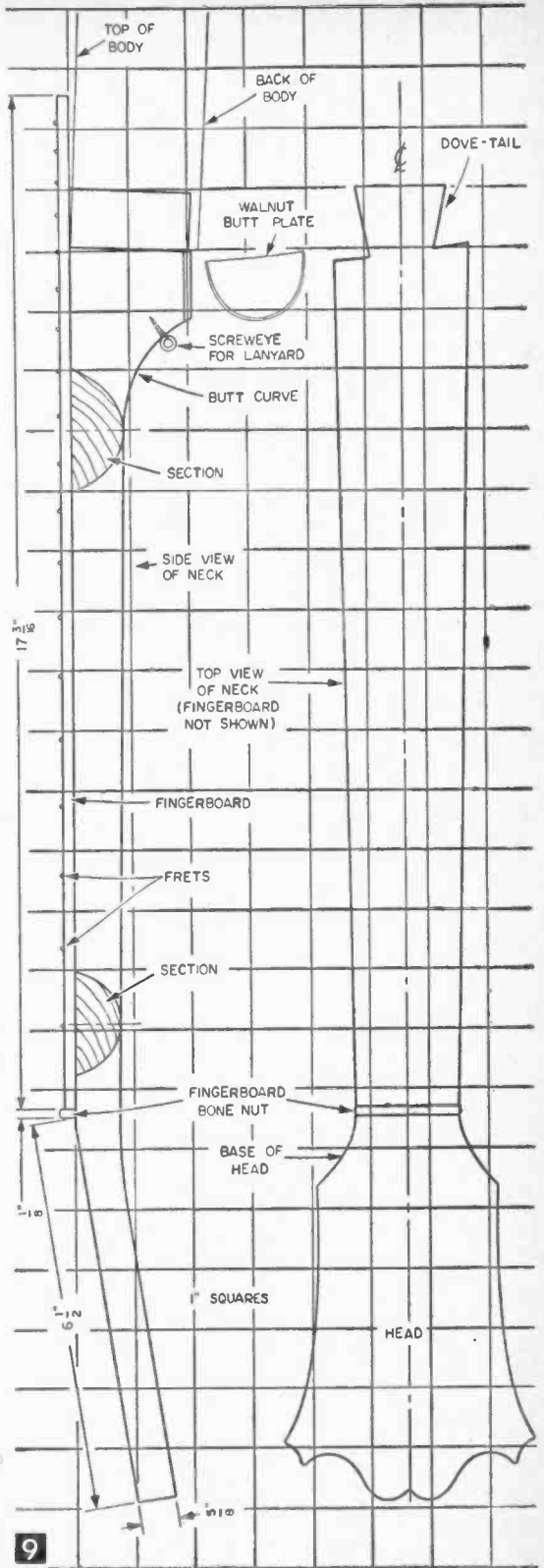

9

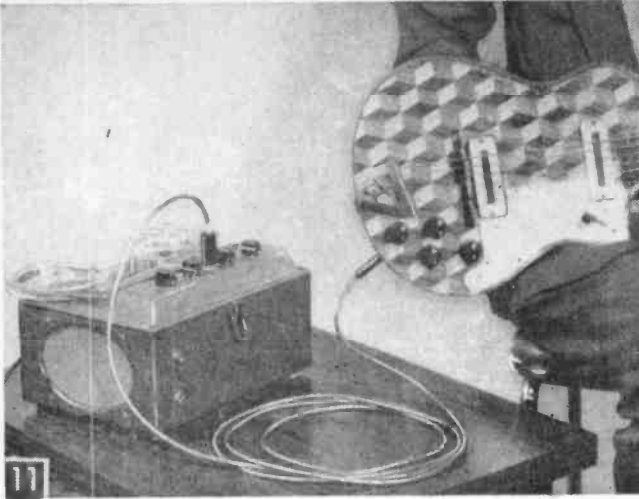

Here a small tape recorder (purchased second-hand for \$40) not only serves as an amplifier for the guitar, but also will record what you play if you want to hear it later—an invaluable method for improving your playing. And, an extension speaker plugged into that jack on the front of the recorder will give you some stereophonic effects.

fitted to the body later. Transfer the shape of the side patterns to the maple stock first and saw from the end of the head to the butt curve at the dovetail end of the neck. Do not cut the scrap piece off, but back it the saw. Then make the other cut, which is the top surface of the head.

Now, using the top pattern of the neck, transfer its shape to the top of the maple stock. Beginning at the dovetail, saw to the location of the nut on both sides, back out the saw on each cut. Then make cuts at right angles to the long cuts you just made at the location of the nut, removing the scrap side pieces. Also cut off the bottom scrap piece. To make the cuts on the sides of the head square with the top surface of the head, turn the neck bottom-side up and transfer the shape of the head on the underside of the neck. When sawing the neck sides, tilt the neck up so that the top surface of the head is flat against the jigsaw table. File the underside of the neck with a coarse wood rasp to the shape of the templates and sand.

Set the neck aside for the moment and remove the center bending form from the guitar body but leave the outside bending form pieces around the body. Then glue the bottom $\frac{3}{8} \times \frac{3}{8}$ in. beading to the lower edge of the body sides. Use masking tape to hold the beading in place. When the glue dries remove the body from the form and carefully sand the edges of the sides and beadings square and flush. Place the sub-top on the body arranging it so the edges of the top project about $\frac{1}{16}$ in. beyond the sides all around. Since the braces on the underside of the sub-top rest against the beading, mark and file the beading to provide clearance for the braces. The underside of sub-top must fit flat against the beading. Glue the sub-top to the body and clamp in gluing clamp (Fig. 7) by tightening all thumb nuts down snug. Remove from clamp when dry

and sand edges flush with body sides. Glue the sub-bottom on later.

Your next step is to overlay the top with contrasting woods as in Figs. 8 and 10. First lay out the centerline from the neck block to the tail block on the sub-top. The three pieces of hardwood (maple or holly, walnut and mahogany) that the overlays are cut from should all be exactly the same width ($\frac{3}{4}$ in.). Using a planer blade in the circular saw, rip the hardwood into $\frac{3}{32} \times \frac{3}{4}$ in. strips. Set the miter gage at 45° and saw 150 diamond-shaped pieces (Fig. 10) from the walnut strips. Then reset the miter gage to $22\frac{1}{2}^\circ$ and cut 150 pieces each from the maple and mahogany strips. Find length A of these pieces (Fig. 10) by measuring length A on the diamond shaped pieces. After cutting six or eight of these pieces make a test assembly with some diamond-shaped pieces to make sure they fit perfectly.


After all the pieces are cut, start the overlay by gluing a line of diamond-shaped walnut pieces on the centerline of the sub-top as in Fig. 10. Ignore the cutouts for the pickups at this time since these openings will be cut later. Continue gluing the other pieces in position, working from center to edges. After the glue dries, trim edges and sand flush with sides. Sand the top.

To install the walnut trim around the outside top edge (Fig. 4), first rout all around the top edge $\frac{3}{32}$ in. deep and to a depth $\frac{1}{16}$ in. below the sub-top (Sec. A-A Fig. 4). Rip saw a strip of $\frac{1}{8} \times \frac{1}{4}$ in. walnut and place it in the steam box. When flexible, bend it around the routed body and secure with masking tape. After the strip has dried, remove the tape and strip, apply glue to the routed edges and again tape the walnut strip in place. When the glue dries, remove the tape and sand the walnut trim strip flush with the top and sides.


Make cutouts in the top for pickups and mixer, and drill the holes for the tone controls. First lay out the cutouts and hole locations as in Fig. 10 and then saw out with a deep-throat coping saw. Use a $\frac{3}{8}$ in. machine drill for the holes.

Now, set this part aside and take up the previously made neck piece. On the top side of the head, lay out the $\frac{7}{32}$ in. holes and the three diamond-shaped walnut inlay pieces (Fig. 14). Drill the holes and rout or chisel out the head to a depth of $\frac{1}{16}$ in. for the walnut inlays. Glue the inlays in place and sand flush.

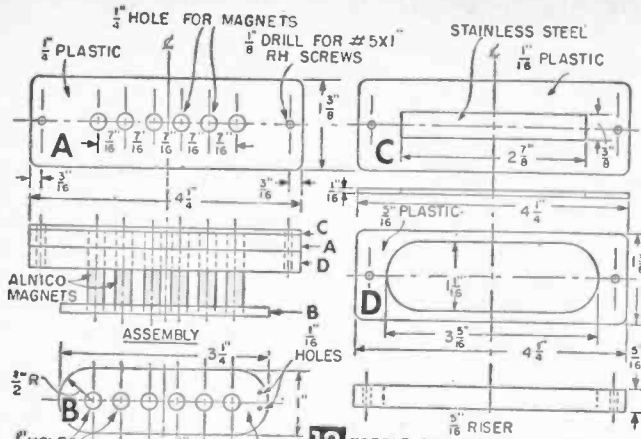Fasten the neck to the body so that the centerline of the neck and the centerline of the body are in perfect alignment. This is very important because a slight discrepancy will throw the strings completely out of alignment and the strings will not come over the fingerboard where they belong. Use a combination coarse and fine rasp to fit the dovetail on the neck to dovetail



12 TREBLE OR MELODY PICK UP

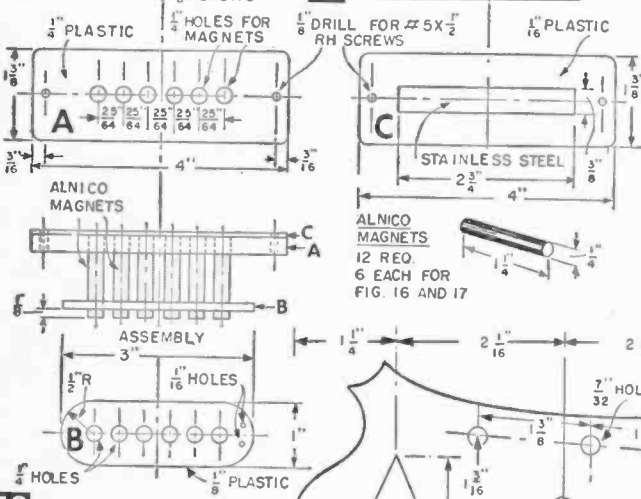


13 BASS OR CHORD PICK UP

of six 1/4 in. dia. magnets 1 1/4 in. long by inserting the magnets through the 1/16 in. holes. Cement magnets in place with household cement.

Now, wrap one turn of Scotch #33 electrical tape around all six magnets forming a core on which to wind a coil. Thread an 8 in. length of #20 shielded grid wire through one of the 1/16 in. holes in piece B and solder the end of a spool of #40 Nylclad heavy magnet wire to the #20 wire. Wind the #40 wire around all of the magnets at once in even layers to form a coil. It will take about 3,500 ft. of magnet wire, or about 6,500 turns on the coil which should test approximately 3,700 ohms on an ohmmeter. If you do not have an ohmmeter, have the coil tested at your local radio repair shop. Complete the coil by soldering the end of the coil to another 8 in. length of #20 shielded grid wire, threaded through the other 1/16 in. hole, and wrap four turns of #33 electrical tape around the entire coil.

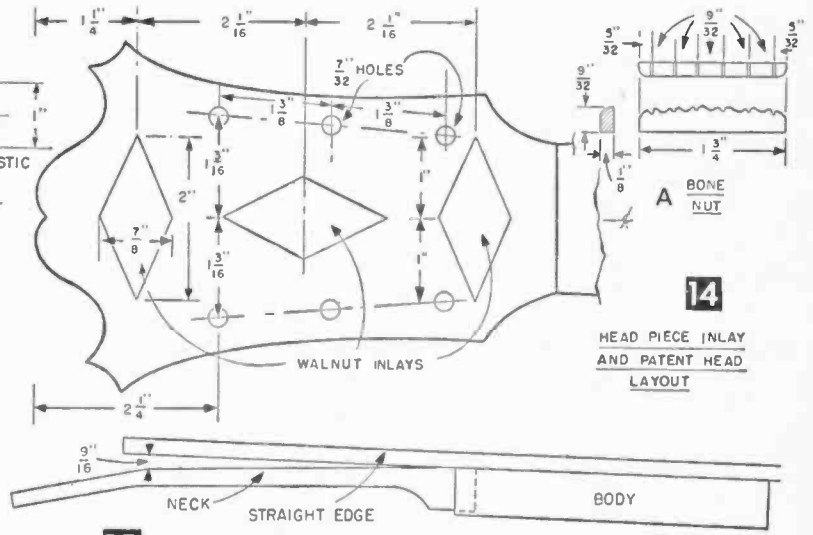Make the top piece (C in Fig. 12) from 1/16 in. thick plastic, cut out the center and tightly fit a piece of stainless steel into the opening. Ce-



14 HEAD PIECE INLAY AND PATENT HEAD LAYOUT

in the body.



The top surface of the neck should be at a slight angle with the top surface of the body when tested with a straightedge as in Fig. 15. If you file away too much stock, use wooden shims to fill in where needed. When you are satisfied with a good fit, glue the neck to the body with Weldwood glue and let dry.

Before fastening the back of the body in place, make and install the electrical parts that go inside the body. Starting with the treble pickup, make piece A from 1/4 in. plastic and piece B from 1/8 in. plastic according to dimensions given in Fig. 16. When drilling the 1/4 in. holes for the Alnico magnets, center piece B on top of piece A, tape together and drill through both pieces at once. Assemble both pieces at opposite ends

ment in place if necessary. Also make up piece D in Fig. 12 and place over the coil under piece A. Place piece C on top of piece A and tape the three pieces together. Then drill the 1/8 in. holes for the #5 x 3/4 in. rh screws.

The bass or chord pickup (Fig. 13) is similar to the treble pickup with the exception that the magnets project 1/8 in. below the bottom piece B and no riser piece is used. Wind the coil with 6,900 turns of #40 Nylclad magnet wire. The

15 ALIGNING GUITAR NECK TO BODY

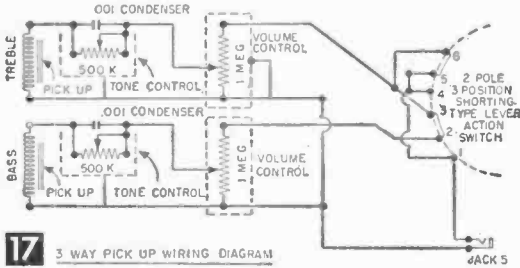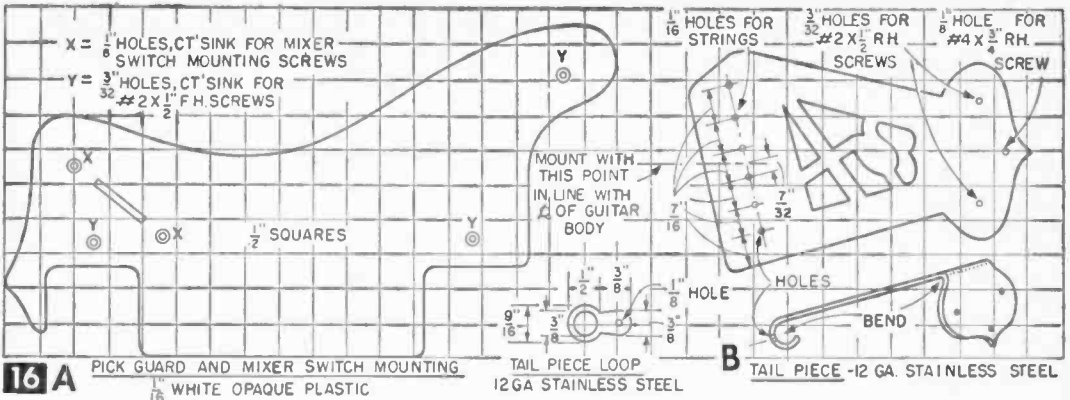

coil should test at about 4,000 ohms. Next sand the top with #8 wet or dry sandpaper using it dry. Then apply natural transparent paste wood filler according to directions on the can. When thoroughly dry, again sand with #8 sandpaper and apply a coat of clear gloss varnish. Only varnish the top at this time, being careful that the varnish does not run down the sides. After the varnish dries, sand with #8 wet or dry sandpaper, using it wet.


Now, mount the pickups, tone and volume controls and mixer switch to the top in their proper places as shown in Fig. 10. Then drill a 3/8 in. hole through the lower, right hand side (shown

in Fig. 4) and mount the phone jack. Although the mixer switch is set into the opening cut in the top, it is actually fastened to the pick guard. Make the pick guard of 1/16 in. thick white opaque plastic as detailed in Fig. 16A. Fasten the mixer switch to the guard and fasten the guard to the body top with three screws.

With all of the electrical parts in place, hook them up with soldered connections using #20 single-strand, shielded grid wire in varnished spaghetti according to the wiring diagram as shown in Fig. 17.

Fitting the back of the body in place is your next step. Use a pad of old blankets to lay the instrument on while you are working on the back. If you do not intend to inlay the back as you did the top, make the back of 1/8 in. maple plywood. If you do intend to inlay the back use the previously cut 1/16 in. thick subback. Lay out the hand hole opening (Fig. 18) on the back piece and saw it out with a fine jeweler's saw blade in a coping saw. This opening will provide access to the electrical wiring in the event servicing is required. Fit braces A, B and C in Fig. 18, trimming the 3/8 x 3/8 in. beading where needed as you did for the top of the body. Be sure to install the 3/8 x 3/8 in. vertical braces between the top and bottom center braces on each side of the pickup hole cut in the body top as in Sec. A-A, Fig. 4.

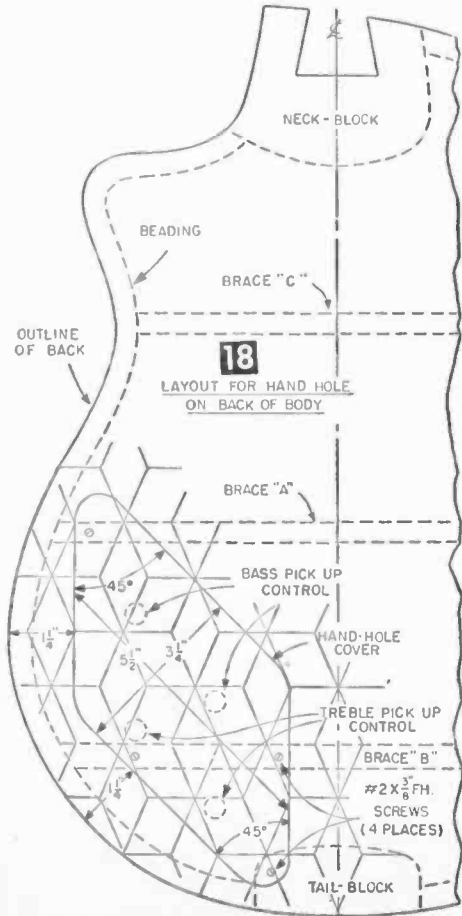Now, glue the back piece to the body and clamp with the gluing clamp as you did when gluing the top. The inside of one piece of the gluing clamp will have to be cut out to clear the pickups and switches protruding on the top of the body. Tape the piece you cut out for the hand hole in place and glue the inlay pieces in position as you did on the top. When you come to the edges of the hand






hole, cut the pieces of inlay to conform to the opening and glue in place. Place a piece of paper between the cut edges of the inlay pieces so that the hand-hole cover will not become glued shut. When finished, fasten cover to body with four #2 x 1/2 in. fh screws, countersunk. Trim and sand the edges of the back flush with the sides and sand the inlay surface flat and smooth. Then rout out the edge for the walnut binding and install the binding as you did around the top.

The fingerboard and bone nut which are purchased parts need only be trimmed to fit as is shown in Fig. 9. The 12th fret should be 12 5/8 in. from the bone nut. Glue in place on the neck. When dry, sand and finish the back, sides and neck as you did the top. Use paste wood filler on the inlay surface only and do not apply any type of finish on the fingerboard or nut. When the first coat of varnish has dried, wet sand the entire instrument, except the fingerboard and nut, and apply two more coats of varnish, sanding between coats. The final coat of varnish can be rubbed down with 2/0 pumice and rottenstone.

You can make the tail piece or purchase one at your local music store. To make one, draw the one shown in Fig. 16B full-size on paper and transfer to 12 gage stainless steel. Saw this out with a metal-cutting blade on a scroll saw. Drill the holes and bend to shape. Also make the tail-piece loop (Fig. 16B). Then mount the tail piece and loop to the guitar body so that the center of the six drilled holes for the strings is exactly in line with the body centerline. The leather lanyard can also be purchased or you can make your own according to the dimensions given in Fig. 19.

Next, install the purchased patent or machine heads to the underside of the neck head as in Fig. 13. To string up your instrument, use *Lektro-Magnetic* strings for the electric Spanish guitar. After stringing, set the rosewood adjustable bridge in place.

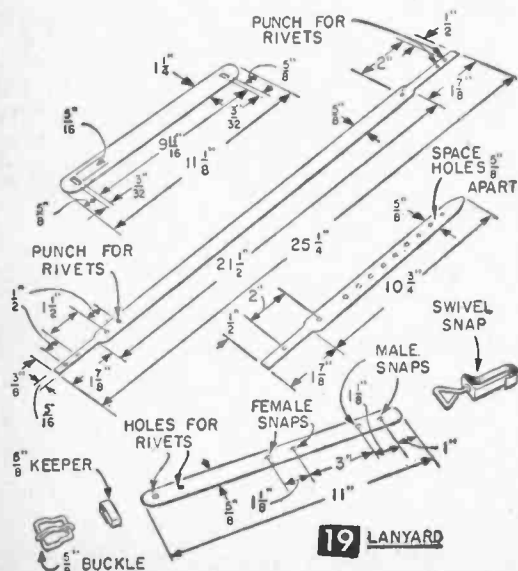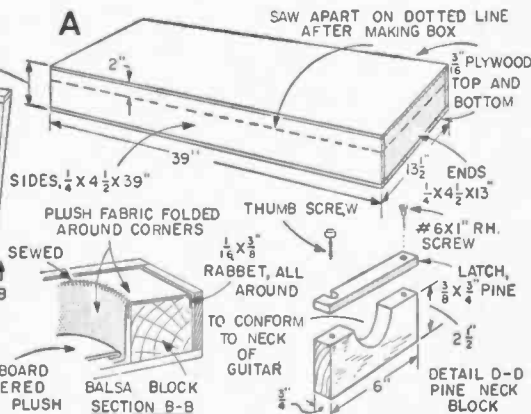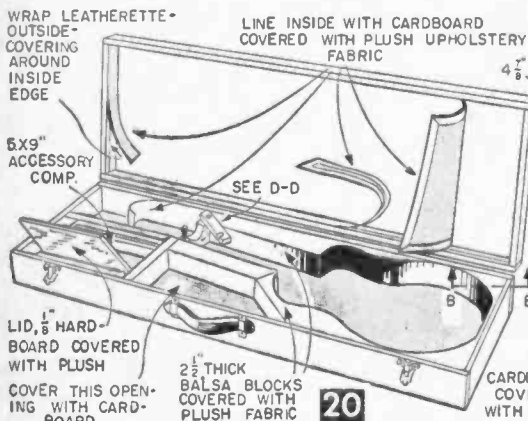Since this instrument is made on the 25-1/4 in. scale, the bridge will be 12 5/8 in. from the 12th fret on the fingerboard. You are now ready to tune your guitar.




● Craft Print No. 277, in enlarged size for building the Electric Guitar is available at \$2. Order by print number. To avoid possible loss of coin or currency in the mails, we suggest you remit by check or money order (no C.O.D.'s or stamps) to Craft Print Dept. 226, SCIENCE AND MECHANICS, 450 East Ohio Street, Chicago 11, Illinois. Please allow three to four weeks for delivery. To obtain our Craft Print Catalog—which contains descriptions of 196 different plans—send us 20¢ (includes 10¢ for postage and handling).

SOLUTION TO ELECTRONICS ANAGRAM
Page 144

N	O	D	E	R	I	M	A	L	I	G	N
E	I	V	A	I	O	N	C	E			
P	H	O	N	D	K	O	W	A	T	T	
E	D	W	I	R	E	D	C	C	R		
R	E	E	A		P	E	A	K		M	A
A	N	T		X	L	T		Y	A	P	
V	T	V	M		E	P		A	G	I	N
		P	A		H	O	T		O	T	S
R	E	D		M	H	O		E	N		P
		R	F	C		N	C		O	T	U
		R		V	O	L	T		C	S	S
S	H	O	T		O	I	N		H		
P	P	P	M		P	I	P		M	O	A
K	V		A		P		N	E	R	I	G
R	C		A	D	C	O	C	K	G	T	C

Why Does the Lamp Light?

• For an interesting electrical experiment, take a paper capacitor of 2 mfd or larger from your junk-box. Do not use an electrolytic capacitor in this setup as it may explode. Paper capacitors were extensively used in the power units of early radios and are still extensively used in modern amateur transmitters, so such a paper capacitor should not be hard to find. Test the capacitor by connecting an ohmmeter across its terminals. If the capacitor is good, the ohmmeter will indicate (after a quick "kick") an open circuit through the unit.

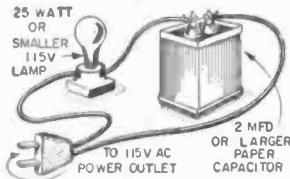

Now connect your capacitor in series with a cleat lamp socket and screw in a 25-watt, or smaller, bulb. When you connect the series combination to the ac power line, you will note that the bulb lights up, although not at full brilliance.

Since the ohmmeter had just shown us that the capacitor is an open circuit, how, then, can the lamp light?

A capacitor is made of two separate conducting sheets with a good insulating substance (such as

oiled paper) between them. Practically, no electrons can move through the paper to complete the circuit between the plates, yet an ac current passes.


Although the ohmmeter indicated an open circuit through the capacitor, the needle did "kick" when the test leads were first applied. This kick is the clue to our apparent paradox; it represents electrical energy flowing in to charge the capacitor. A good capacitor may thus retain a stored charge for hours. The electrical energy in this charge may be nearly completely recovered from the capacitor.

The voltage across the ac power line periodically reverses itself 60 (50 in some parts of the country) times per second. Now, when a capacitor is connected across such a line it is forced to charge and discharge twice during each complete reversal, or 120 times each second. Each time it charges or discharges, electrons move through its connecting wires. Since our lamp is connected in one of these wires, this charge-discharge current causes it to light.

This principle is universally applied to separate ac from dc (unchanging) currents throughout vacuum-tube and transistor circuits.—C. F. ROCKEY.

Get This Valuable Book

FREE

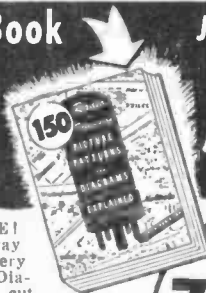

Just For Examining COYNE'S New Set
"Applied Practical Radio-Television"
 on 7 DAY FREE TRIAL!

Yes, you get our big Diagrams book, FREE! It's like a road-map that shows you the way to easier Radio-TV repair. Needed by every serviceman. Complete 11x22" Schematic Diagrams on many Radio and TV sets help cut servicing time. Includes simple instructions on how to use diagrams and picture patterns. This book is yours FREE for asking to see Coyne's great new 7-book set, "Applied Practical Radio-Television!"

AT LAST! MONEY-MAKING "KNOW-HOW" ON TRANSISTORS, COLOR TV AND SERVICING

Coyne's great 7-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that's easy to understand you'll find everything you want in Volumes 1 to 5 on over 5000 practical facts and data. Every step from fundamentals to installing, servicing and trouble-shooting all types of radio and TV sets. So up-to-date it includes the latest on COLOR TV and UHF. All this plus Volume 7—**TRANSISTOR CIRCUITS**—the most complete book ever published on the applications of Transistors in electronics. New! Set has colorful design, washable covers.

EXTRA! 868 Page TV Encyclopedia Included!

For speedy, on-the-job use, you also get Volume 6—famous Coyne CYCLOPEDIA. Answers problems on servicing, alignment, installation etc., in easy ABC order. Use this 7-volume, TV-RADIO LIBRARY FREE for 7 days; get the Servicing Book FREE!

NOW!
7 BIG BOOKS
 IN ONE GREAT SET!



SEND NO MONEY!

Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. (Cash price, only \$24.95.) Or you can return the library at our expense in 7 days and owe nothing. YOU BE THE JUDGE. Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

FREE BOOK—FREE TRIAL COUPON!

Educational Book Publishing Division
 COYNE ELECTRICAL SCHOOL, Dept. 20-RE
 1501 W. Congress Pkwy., Chicago 7, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name Age

Address

City Zone State

Where Employed

Check here if you want library sent C.O.D. You pay postman \$24.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.

Educational Book Publishing Division
COYNE ELECTRICAL SCHOOL
 1501 W. Congress Pkwy., Dept. 20-RE Chicago 7, Ill.

25 Years Ago in Radio

A QUARTER of a century ago, *White's Radio Log* was 12 years old and commercial broadcasting itself was not much older. Yet as these pages reproduced from the March 1934 issue of *White's* show, broadcasting was even then a healthy medium of entertainment. Some of the programs popular in 1934 are still on the air (and most of 1934's sponsors are still going

strong). Indeed, the programming of the Thirties may seem to many to have been radio's golden age, flawed possibly by immaturity, but lusty and vital all the same. Here—for those of you old enough to remember—is what you were listening to 25 years ago. And here—for those of you who missed it—is what your fathers heard, and grow nostalgic about today.

NETWORK RADIO PROGRAMS OF MARCH 1934

C., CBS Network Stations. N.F., WEAf; N.Z., WJZ—both NBC Networks. Eastern Standard Time used exclusively. Sponsors' names appear in parentheses.

A & P Gypsies (Great A & P Tea Co.)	Monday, 9:00 p.m., N.F.
Abe Lyman's Orch.: Frank Munn (Sterling Products)	Friday, 9:00 p.m., N.F.
Adventures of Tom Mix and his Ralston Straight Shooters (Ralston Purina Co.),	Mon.-Wed.-Fri., 5:30 p.m., also Wed.-Fri., 6:30 p.m., N.F.
Albert Payson Terhume (Spratts Ptd., Ltd.)	Sunday, 4:00 p.m., N.Z.
Albert Spalding (Fletcher's Castoria)	Wednesday, 8:30 p.m., C.
American Album of Familiar Music (Bayer Co., Inc.)	Sunday, 9:30 p.m., N.F.
American Revue (American Oil Co.)	Sunday, 7:00 p.m., C.
Amos 'n' Andy (Pepsodent Co.)	Daily except Sat. & Sun., 7 p.m., also western, 11:00 p.m., N.Z.
An Evening in Paris (Bourjois Sales Corp.)	Sunday, 8:00 p.m., C.
Armour Program, featuring Phil Baker (Armour Co.)	Friday, 9:30 p.m., N.Z.
Baby Rose Marie (Tasty Yeast, Inc.)	Sunday, 12:15 p.m., N.Z.
Bar X Days and Nights (Health Products Co.)	Sunday, 2:00 p.m., N.Z.
Ben Bernie's Blue Ribbon Orchestra (Premier-Pabst Sales Co.),	Tues., 9 p.m., 12 midnight, N.F.
Benny Meroff's Review (Plough, Inc.)	Wednesday, 10 p.m., N.Z.
Betty and Bob (General Mills, Inc.)	Daily except Sat. & Sun., 4:00 p.m., N.Z.
Betty Moore, Interior Decorator (Benjamin Moore & Co.)	Wednesday, 11:30 a.m., N.F.
Big Ben Dream Drama (Western Clock Co.)	Sunday, 5:00 p.m., N.F.
Big Hollywood Show (Phillips Dental Magnesia)	Sunday, 2:30 p.m., C.
Big Show (Ex-Lax Co.)	Monday, 9:30 p.m., C.
Bill and Ginger (C. F. Mueller Co.)	Monday, Wednesday, Friday, 10:15 a.m., C.
Billy Bachelor (Wheatena Corp.)	Daily except Saturday, 7:15 p.m., N.F.
Bing Crosby, Gus Arnheim's Orch., Mills Bros. (John Woodbury Co.)	Monday, 8:30 p.m., C.
Boake Carter (Philco Radio & Television Corp.)	Daily except Sat. & Sun., 7:45 p.m., C.
Bobby Benson and Sunny Jim (Hecker H-O Co.)	Daily except Sat. & Sun., 6:15 & 8:15 p.m., C.
Broadway Melodies (American Home Products Corp.)	Sunday, 2:00 p.m., C.
Buck Rogers in the 25th Century (Cocomalt)	Mon., Tues., Wed., Thurs., 6:00 & 7:30 p.m., C.
Buick Presents (Buick Motor Co.)	Monday & Thursday, 9:15 p.m., C.
Byrd Expedition Broadcast (General Foods Corp.)	Saturday, 10:00 p.m., C.
Cadillac Concert (Cadillac Motor Car Co.)	Sunday, 6:00 p.m., N.Z.
Camel Caravan (R. J. Reynolds Tobacco Co.)	Tuesday & Thursday, 10:00 p.m., C.
Capt. Henry's Maxwell House Show Boat (General Foods Corp.)	Thursday, 9:00 p.m., N.F.
Carborundum Band (Carborundum Co.)	Saturday, 9:30 p.m., C.
Charm Secrets (Lavoris Co.)	Tuesday & Thursday, 11:15 a.m., C.
Chase & Sanborn Hour (Standard Brands, Inc.)	Sunday, 8:00 p.m., N.F.
Chevrolet Program (Chevrolet Motor Co.)	Sunday, 10:00 p.m., N.F.
Cities Service Program (Cities Service Co.)	Friday, 8:00 p.m., N.F.
Clara, Lu 'n' Em (Colgate-Palmolive-Peet Co.)	Daily except Sat. & Sun., 10:15 a.m., N.Z.
Climalene Carnival (The Climalene Co.)	Tuesday & Thursday, 11:30 a.m., N.F.
Conoco Travel Adventures (Continental Oil Co.)	Wednesday, 10:30 p.m., N.Z.
Contented Program (Carnation Milk)	Monday, 10:00 p.m., N.F.
Cook Travelogues (Thomas Cook & Son)	Sunday, 2:30 p.m., N.F.
Cooking Close-Ups (Pillsbury Flour Mills)	Monday, Wednesday, Friday, 11:00 a.m., C.
Corn Cob Pipe Club of Virginia (Larus & Brothers Co.)	Wednesday, 10 p.m., N.F.
Cruise of the Seth Parker (Frigidaire Corp.)	Tuesday, 10:00 p.m., N.F.
Dangerous Paradise (John H. Woodbury Co.)	Wednesday and Friday, 8:30 p.m., N.Z.
Death Valley Days (Pacific Coast Borax Co.)	Thursday, 9:00 p.m., N.Z.
Del Monte Ship of Joy (California Packing Corp.)	Monday, 9:30 p.m., N.F.
Djer Klav Recital (Vadsco Sales Corp.)	Monday, 8:30 p.m., N.Z.
Don Quixote Dramatization (Jeddo-Highland Coal Co.)	Thurs., Fri., Sat., 7:15 p.m., N.Z.
Easy Aces (Wyeth Chemical Co.)	Tuesday, Wednesday, Thursday, Friday, 1:30 p.m., C.
Eddie Duchin and his Orchestra (Pepsodent Co.)	Tues., Thurs., Sat., 9:30 p.m., N.Z.
Edwin C. Hill (Barbasol Co.)	Daily except Saturday & Sunday, 8:15 & 11:30 p.m., C.
Eno Crime Clues (Harold S. Ritchie & Co.)	Tuesday & Wednesday, 8 p.m., N.Z.
First Nighter (Campana Corp.)	Friday, 10:00 p.m., N.F.
Fitch Program (F. W. Fitch Co.)	Sunday, 7:45 p.m., N.F.


Fleischmann Hour (Standard Brands, Inc.)	Thursday, 8:00 p.m., N.F.
Forty-five Minutes in Hollywood (Borden Co.)	Saturday, 8:00 p.m., C.
Fox Fur Trappers (I. J. Fox, Inc.)	Tuesday, 7:30 p.m., N.F.
Frank Crummit and Julia Sanderson (General Baking Co.)	Sunday, 5:30 p.m., C.
Fred Allen's Sal Hepatica Revue (Bristol-Myers Co.)	Wednesday, 9:30 p.m., N.F.
Fred Waring's Pennsylvanians (Ford Motor Co.)	Sunday, 8:30 p.m., Thursday, 9:30 p.m., C.
Galaxy of Stars (Red Star Yeast & Products Co.)	Tues., Thurs. & Sat., 11:00 a.m., N.F.
Garden of Tomorrow (Tennessee Corp.)	Sunday, 10:30 a.m., N.F.
Gems of Melody (Carleton & Hovey Co.)	Sun., 2:45 p.m., N.F., Wed., 7:15 p.m., N.Z.
Gene Arnold and the Commodores (Crazy Crystals Water Co.)	Sun., Wed., Fri., 2:00 p.m., N.F., Mon. & Thurs., 12 noon, N.Z.
Goldbergs (Pepsodent Co.)	Daily except Saturday & Sunday, 7:45 p.m., N.F.
Grand Hotel (Campana Corp.)	Sunday, 5:30 p.m., N.Z.
Gulf Headliners (Gulf Refining Co.)	Sunday, 9:00 p.m., N.Z.
Hall of Fame (Lehn & Fink Products Co.)	Sunday, 10:30 p.m., N.F.
Happy Bakers (Continental Baking Co.)	Monday, Wednesday & Friday, 8:00 p.m., C.
Hoover Sentinels Concert (The Hoover Co.)	Sunday, 4:30 p.m., N.F.
Horlick's Adventures in Health (Horlick Malted Milk Co.)	Tuesday & Thursday, 8:30 p.m., Tuesday, 11:45 p.m., N.Z.
Household Musical Memories (Household Finance Corp.)	Tuesday, 9:00 p.m., N.Z.
Ipana Troubadours (Bristol-Myers Co.)	Wednesday, 9:00 p.m., N.F.
Irene Rich in Hollywood (Welch Grape Juice Co.)	Sun., 3:15 p.m., Wed., 7:45 p.m., N.Z.
Jack Armstrong, All American Boy (General Mills, Inc.)	Daily except Sun., 5:30 & 6:30 p.m., C.
Jack Frost's Melody Moments (National Sugar Refining Co.)	Monday, 9:30 p.m., N.Z.
Jane Ellison's Magic Recipes (The Borden Sales Co.)	Wednesday, 11:45 a.m., C.
Jack Pearl (Standard Brands, Inc.)	Wednesday, 8:00 p.m., N.F.
Joan Marrow (J. W. Marrow Mfg. Co.)	Tuesday & Thursday, 1:15 p.m., C.
Jergens Program (Andrew Jergens Co.)	Sunday, 9:30 & 11:15 p.m., N.Z.
Josephine Gibson Hostess Council (H. J. Heinz Co.)	Mon., Wed., Fri., 10:00 a.m., N.Z.
Judy and Jane (J. A. Folger & Co.)	Daily except Saturday & Sunday, 2:30 p.m., N.F.
Just Plain Bill (Kolyons Sales Co.)	Daily except Saturday & Sunday, 2:00 & 7:15 p.m., C.
Lady Esther Serenade (Lady Esther Co.)	Sun., 3:00 p.m., Tues. & Wed., 8:30 p.m., N.F.
Lazy Dan, the Minstrel Man (American Home Products Corp.)	Sunday, 1:30 p.m., C.
Leo Reisman's Orch. with Phil Duey (Philip Morris & Co.)	Tuesday, 8:00 p.m., N.F.
Let's Listen to Harris (Northam Warren Corp.)	Friday, 9:00 p.m., N.Z.
Little Miss Bab-O's Surprise Party (B. T. Babbitt Co., Inc.)	Sunday, 1:00 p.m., N.F.
Little Italy (Delaware, Lack. & Western Coal Co.)	Tuesday & Thursday, 6:45 p.m., C.
Little Orphan Annie (Wander Co.)	Daily except Sunday, 5:45 p.m., 6:45 p.m., N.Z.
Lowell Thomas (Sun Oil Co.)	Daily except Saturday & Sunday, 6:45 p.m., N.Z.
Madam Sylvia of Hollywood (Ralston Purina Co.)	Tuesday, 10:30 p.m., N.F.
Malteser Program (Malted Cereals Co.)	Sunday, 1:30 p.m., N.F.
Manhattan Merry-Go-Round (R. L. Watkins Co.)	Sunday, 9:00 p.m., N.F.
Marie the Little French Princess (Affiliated Prod., Inc.),	Tues., Wed., Thurs., Fri., 1:00 p.m., C.
March of Time (Remington Rand, Inc.)	Friday, 8:30 p.m., C.
Metropolitan Opera Broadcast (American Tobacco Co.)	Saturday, 1:45 p.m., N.F. & N.Z.
Minneapolis Symphony Orchestra (General Household Utility Co.)	Tuesday, 9:30 p.m., C.
Molle Show (The Molle Co.)	Monday, Wednesday, Thursday, 7:30 p.m., N.F.
Music by Gershwin (Health Products Corp.)	Monday & Friday, 7:30 p.m., N.Z.
Music on the Air with Jimmy Kemper (Tide Water Oil Sales Co.),	Mon., Wed., Fri., 7:30 p.m., C.
Myrt & Marge (Wm. Wrigley, Jr., Co.)	Daily except Sat. & Sun., 7:00 & 10:45 p.m., C.
Mystery Chef (R. B. Davis Co.)	Tues. & Thurs., 9:45 a.m., C.; Wed. & Fri., 9:00 a.m., N.Z.
Nat Shilkret and his Salon Orchestra (Smith Bros.)	Sunday, 9:45 p.m., N.Z.
National Barn Dance (Dr. Miles Laboratories)	Saturday, 11:00 p.m., N.Z.
Nestle's Chocolate (Lamont-Corliss & Co.)	Friday, 8:00 p.m., N.Z.
Old Gold Program (P. Lorillard Co.)	Wednesday, 10:00 p.m., C.
Oldsmobile Presents (Old's Motor Works)	Tuesday & Friday, 9:15 p.m., C.
Oxol Feature (J. L. Prescott Co.)	Monday, Tuesday, Wednesday, Friday, 5:45 p.m., C.
Oxydol's Own Ma Perkins (Procter & Gamble Co.)	Daily except Saturday & Sunday, 3:00 & 4:30 p.m., N.F.
Patri's Dramas of Childhood (Cream of Wheat Corp.)	Sunday, 10:00 p.m., C.
Paul Whiteman and his Orchestra (Kraft Phenix Cheese Corp.)	Thursday, 10 p.m., N.F.
Pet Milky Way (Pet Milk Sales Corp.)	Tuesday & Thursday, 11:00 a.m., C.
Philadelphia Orchestra (Liggett & Myers Tobacco Co.)	Daily except Sunday, 9:00 p.m., C.
Playboys (M. J. Breiten-Bach Co.—Pepto Mangan)	Sunday, 10:45 a.m., C.
Plough's Musical Cruiser (Plough, Inc.)	Wednesday, 10:00 p.m., N.Z.
Pond's Program (Lamont-Corliss & Co.)	Friday, 9:30 p.m., N.F.
Pontiac Presents (Buick-Oldsmobile-Pontiac Sales Co.)	Saturday, 9:30 p.m., C.
Princess Pat Players (Princess Pat, Ltd.)	Sunday, 4:30 p.m., Monday, 10:30 p.m., N.Z.
Pure Oil Program (Pure Oil Co.)	Saturday, 9:00 p.m., N.Z.
Real Silk Show (Real Silk Hosiery Mills)	Sunday, 7:00 p.m., N.Z.
Red Davis, Dramatic Sketch (Beech-nut Packing Co.)	Mon., Wed. & Fri., 8:45 p.m., N.Z.
Richard Hudnut Presents Marvelous Melodies (Hudnut Sales Co., Inc.)	Friday, 9:30 p.m., C.
Bin Tin Tin Thriller (Chappel Bros., Inc.—Ken-L-Ration)	Sunday, 7:45 p.m., C.
Rings of Melody (Perfect Circle Co.)	Sunday, 2:30 p.m., N.Z.
Romance of Helen Trent (Edna Wallace Hopper, Inc.)	Daily except Sat. & Sun., 2:15 p.m., C.
Roses and Drums (Union Central Life Ins. Co.)	Sunday, 5:00 p.m., C.
Saturday Night Terraplane Party (Hudson Motor Car Co.)	Saturday, 10:00 p.m., N.F.
Sealed Power Side Show (Sealed Power Corp.)	Monday, 8:00 p.m. & 12 midnight, N.Z.
Seven Star Revue (Corn Products Refining Co.)	Sunday, 9:00 p.m., C.
Silver Dust (Gold Dust Corp.)	Tuesday, Thursday & Saturday, 7:50 p.m., C.

Sinclair Greater Minstrels (Sinclair Refining Co.)	Monday, 9:00 p.m., N.Z.
Singing Lady (Kellogg Co.)	Daily except Saturday & Sunday, 5:30 p.m., 6:30 p.m., N.Z.
Skippy (Phillips Dental Magnesia)	Daily except Saturday & Sunday at 5:00 & 6:00 p.m., C.
Smiling Ed McConnell (Acme White Lead & Color Works)	Sunday, 6:30 p.m., Wednesday & Friday, 12:30 p.m., C.
Soconyland Sketch (Standard Oil Co. of N. Y.)	Monday, 8:00 p.m., N.F.
Songs Your Mother Used to Sing (Wyeth Chemical Co.)	Sunday, 6:00 p.m., C.
Stamp, Adventurer's Club (Louden Packing Co.)	Thursday, 5:45 & 6:45 p.m., C.
Sweetheart Melodies (Manhattan Soap Co.)	Thursday, 11:30 a.m., N.F.
Swift Garden Program (Swift & Co.)	Sunday, 3:30 p.m., N.F.
Swift Review (Swift & Co.)	Friday, 10 p.m., C.
Talkie Picture Time (Luxor, Ltd.)	Sunday, 5:30 p.m., N.F.
Texaco Fire Chief Band; Ed Wynn (Texas Co.)	Tuesday, 9:30 p.m., N.F.
Tito Guizar's Mid-day Serenade (Brillo Mfg. Co.)	Sunday, 12:30 p.m., C.
Today's Children (Pillsbury Flour Mills Co.)	Daily except Sat. & Sun., 10:30 a.m., N.Z.
Today's Children with Keenan & Philips (S. C. Johnson & Son)	Tues. & Thurs., 11:30 a.m., C.
Tower Health Exercises (Metropolitan Life Ins. Co.)	Daily except Sun., 6:45 to 8:00 a.m., N.F.
Trade & Mark (Smith Brothers, Inc.)	Saturday, 8:45 p.m., C.
True Story Court of Human Relations (True Story Pub. Co.)	Sunday, 7:00 p.m., N.F.
Voice of Firestone (Firestone Tire & Rubber Co.)	Monday, 8:30 & 11:30 p.m., N.F.
Voice of Romance (Rieser Co., Inc.)	Saturday, 6:15 p.m., C.
Warden Lawes in "20,000 Years in Sing Sing" (Wm. R. Warner Co.)	Wed., 9 p.m., N.Z.
Ward's Family Theatre (Ward Baking Co.)	Sunday, 6:45 & 7:30 p.m., C.
Waves of Romance (Rieser & Co.)	Sunday, 5:15 p.m., N.F.
Wayne King's Orchestra (Lady Esther Co.)	Monday, 10:00 p.m., C.
White Owl Program (General Cigar Co.)	Wednesday, 9:30 p.m., C.
Wildroot Institute (Wildroot Co.)	Sunday, 4:15 p.m., N.F.
Will Osborne and His Orchestra (Corn Products Refining Co.)	Mon., Wed., Fri., 10:45 a.m., C.
Wizard of Oz (General Food Corp.)	Monday, Wednesday & Friday, 5:45 p.m., N.F.
Vince Program with John McCormack (Wm. R. Warner Co.)	Wednesday, 9:30 p.m., N.Z.
Voice of Experience (Wasey Products, Inc.)	Daily except Sun., 12 noon; also Tues., 8:30 & 11:45 p.m., Thurs., 8:30 p.m., C.
Yeast Foamers (Northwestern Yeast Co.)	Sunday, 3:30 p.m., N.Z.
Ye Happy Minstrel and Tiny Band (Wheatena Corp.)	Mon., Wed., Sat., 6:45 p.m.; Tues. & Thurs., 4:45 p.m., C.
Zoel Parenteau's Orchestra (Worcester Salt Co.)	Friday, 6:45 p.m., C.

For some auditors, listening to a favorite program was a ritual. At 7:00, for example, everyone stopped everything and the country lis-

tened to Amos 'n' Andy. Here are the programs of a typical 1934 weeknight (Wednesday in this instance), and the times you tuned them in.

6:45 to 8:00 a.m. Tower Health Exercises	N.F.	7:00 p.m. Myrt and Marge	C.
9:00 a.m. The Mystery Chef	N.Z.	7:15 p.m. Billy Batchelor	N.F.
10:00 a.m. Josephine Gibson Hostess Council	N.Z.	7:15 p.m. Gems of Melody	N.Z.
10:15 a.m. Bill and Ginger	C.	7:15 p.m. Just Plain Bill	C.
10:15 a.m. Clara, Lu 'n' Em	N.Z.	7:30 p.m. Buck Rogers in the 25th Century	C.
10:30 a.m. Today's Children	N.Z.	7:30 p.m. The Mollie Show	N.F.
10:45 a.m. Will Osborne and his Orch.	C.	7:30 p.m. Music on the Air with Jimmy Kemper	C.
11:00 a.m. Cooking Close-Ups	C.	7:45 p.m. Boake Carter	C.
11:30 a.m. Betty Moore, Interior Decorator	N.F.	7:45 p.m. Goldberg's	N.F.
11:45 a.m. Jane Ellison's Magic Recipes	C.	7:45 p.m. Irene Rich in Hollywood	N.Z.
12:00 noon. Gene Arnold and the Commodores	N.F.	8:00 p.m. Eno Crime Clues	N.Z.
12:00 noon. The Voice of Experience	C.	8:00 p.m. Happy Bakers	C.
12:30 p.m. Smiling Ed McConnell	C.	8:00 p.m. Royal Gelatin Review with Jack Pearl	N.F.
1:00 p.m. Marie, the Little French Princess	C.	8:15 p.m. Bobby Benson and Sunny Jim	C.
1:30 p.m. Easy Aces	C.	8:15 p.m. Edwin C. Hill, "The Human Side of the News"	C.
2:00 p.m. Just Plain Bill	C.	8:30 p.m. Albert Spalding	C.
2:15 p.m. Romance of Helen Trent	C.	8:30 p.m. Dangerous Paradise	N.Z.
2:30 p.m. Judy and Jane	N.F.	8:30 p.m. Lady Esther Serenade	N.F.
3:00 p.m. Oxydol's Program	N.F.	8:45 p.m. "Red Davis" Dramatic Sketch	N.Z.
4:00 p.m. Betty and Bob	N.Z.	9:00 p.m. Ipana Troubadours	N.F.
4:30 p.m. Oxydol's Program	N.F.	9:00 p.m. Philadelphia Orchestra	C.
5:00 p.m. Skippy	C.	9:00 p.m. Warden Lawes in "20,000 Years in Sing Sing"	N.Z.
5:30 p.m. Adventures of Tom Mix	N.F.	9:30 p.m. Fred Allen's Revue	N.F.
5:30 p.m. Jack Armstrong, All American Boy	C.	9:30 p.m. Vince Program with John McCormack	N.Z.
5:30 p.m. Singing Lady	N.Z.	9:30 p.m. White Owl Program	C.
5:45 p.m. Little Orphan Annie	N.Z.	10:00 p.m. Plough's Musical Cruiser	N.Z.
5:45 p.m. The Oxol Feature	C.	10:00 p.m. Corn Cob Pipe Club	N.F.
5:45 p.m. Wizard of Oz	N.F.	10:00 p.m. Old Gold Program	C.
6:00 p.m. Buck Rogers in the 25th Century	C.	10:30 p.m. Conoco Adventures	N.Z.
6:00 p.m. Skippy	C.	10:45 p.m. Myrt and Marge	C.
6:15 p.m. Bobby Benson and Sunny Jim	C.	11:00 p.m. Amos 'n' Andy	N.Z.
6:30 p.m. Adventures of Tom Mix	N.F.	11:30 p.m. Edwin C. Hill, "The Human Side of the News"	C.
6:30 p.m. Household Music Box	C.		
6:30 p.m. Jack Armstrong, All American Boy	C.		
6:30 p.m. Singing Lady	N.Z.		
6:45 p.m. Little Orphan Annie	N.Z.		
6:45 p.m. Lowell Thomas	N.Z.		
6:45 p.m. Ye Happy Minstrel & Tiny Band	C.		
7:00 p.m. Amos 'n' Andy	N.Z.		

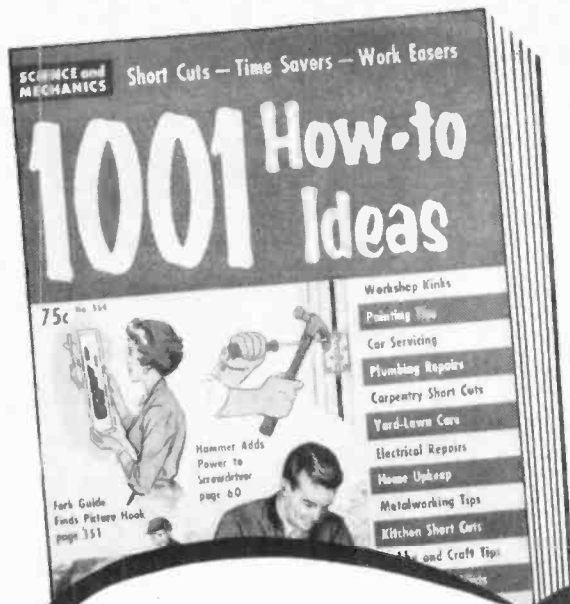

on sale now
get your copy of


1001 How-to Ideas

Kinks like this

on- radio-tv repairs
home decorating
home remodeling
groundskeeping
plumbing repairs
electrical repairs
home maintenance
auto repairs
carpentry
woodworking
masonry
metalworking
power tool use
hand tool use
photography
craft hobbies

Salvaging Flashlights

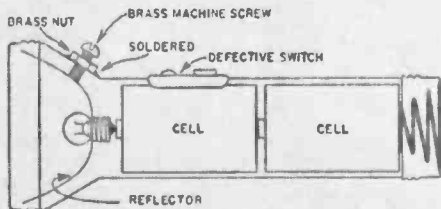• Since a flashlight switch is riveted to the case, and the interior of the case is hard to get at for repairs, it is simpler to ignore the original switch entirely when it is broken or badly worn and install a simple substitute switch. Do this by



drilling a hole in the case close to the reflector, soldering a square or hexagon nut over the hole, and twisting a roundhead machine screw into the nut. To light the lamp, simply turn the screw clockwise until the end of the screw contacts the reflector. This provides the necessary connection from the case to the reflector, as the reflector is usually in contact with the lamp base but not the case. To turn off the lamp, back up the screw.

Only **75¢**

If you do it yourself around the home, you'll want a copy of the 1960 edition of *1001 How-to Ideas* (Vol. 2, No. 564). Compiled by the editors of *Science and Mechanics Magazine*—The Magazine That Shows You How—*1001 How-to Ideas* contains tested tips and shortcuts that will save you

many, many hours on your projects—and dollars, too. Whatever area of do-it- (or make-it-) yourself you're interested in, you'll find at least a score of ideas in this book that will show you faster, easier, thriftier ways to do it.

Get a copy now.

Get your copy of the 1960 edition from your newsdealer, or send 75¢ for a copy to
SCIENCE AND MECHANICS 450 E. Ohio St. Dept. 332 Chicago 11, Illinois

THE FRABIJAN'S BUSTED?

Don't Throw It Away,
Fix It - Subscribe To

SCIENCE and MECHANICS

The Magazine That Shows You How

- Every issue packed with useful, money-saving information on home repairs and upkeep
- Every issue, projects to build—boats, household accessories, workshop and hobby equipment
- Every issue, news on science and industry, car test reports
- Every issue, everything under the sun from satellites to sofas to surfboarding

Science and Mechanics has always been a leader in its field—readers' mail says it's the leader—but the **NEW Science and Mechanics** is bigger and better than ever. Now a Davis Publication, the **NEW Science and Mechanics** has the same solid substance, the same respect for facts it's always had. As before, it publishes the latest news on science and industry (written to relate to your needs and interests), plus completely detailed do-it- and make-it-yourself project articles. But under its new

aegis, *Science and Mechanics* has more editorial content than ever before, and it's presented in new, more entertaining and more attractive ways . . . And in every issue of the **NEW S&M** there's a big **BONUS** feature.

For one of the most interesting experiences of your magazine-reading life, and for one of the most useful and practical magazine purchases you'll ever make, subscribe now to the **NEW S&M**. The first tip you use from the many in each issue will more than repay you.



The April Issue, Now On Sale, Includes:

Fold-Out Blueprints for MINIATURE, BATTERY-POWERED TAPE RECORDER. Can be built for about \$35. Completely portable, compatible—can be played back on ordinary home recorder at 3¾ ips. Equivalent of commercial units costing \$100-\$250.

3-OCTAVE, 120-BASS CHORD ORGAN. Separate balance control for treble and bass. More chord selection (though less tone control) than \$900-plus commercial models. Will cost approximately \$50 to build; easily equivalent of \$250 commercial organs.

Plus Project Articles on ONE-TUBE TIN CAN RECEIVER. Inexpensive broadcast-band receiver pulls in stations 70 miles distant.

TRANSMITTER FOR THE NOVICE. Compact 75-watt transmitter that even a Novice YL can build in a few hours (in fact, one did). The rig puts out a good signal on 40 and 80 meters, features band-switching, and—with suitable power supplies—can be used either at home or in a car.

USE THE COUPON INSERTED OPPOSITE THIS PAGE TO SUBSCRIBE TODAY

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KSJB	Jamestown, N.D.	5000	670-447.5			KUEQ	Phoenix, Ariz.	10000
WFRM	Coudersport, Pa.	10000	WMAQ	Chicago, Ill.	50000	KBIG	Avalon, Calif.	10000
WAEL	Mayerquez, P.R.	1000	680-440.9			KCBS	San Francisco, Calif.	50000
WREC	Memphis, Tenn.	5000	CHFA	Edmonton, Alta.	5000	KSSS	Colorado Springs, Colo.	2500
KROD	El Paso, Tex.	5000	CHLO	St. Thomas, Ont.	1000	KVFC	Cortez, Colo.	10000
KERB	Kermitt, Tex.	10000	CJOB	Winnipeg, Man.	10000	WKLS	Orlando, Fla.	5000
KTBB	Tyler, Tex.	10000	CKGB	Timmins, Ont.	5000	KYMB	Boise, Idaho	2500
610-491.5			CKBC	San Fran., Calif.	50000	WYOL	Olney, Ill.	2500
CHNC	New Carlisle, Que.	5000	WCTT	Corbin, Ky.	1000	KBOE	Oskaloosa, Iowa	2500
CJAT	Trall, B.C.	1000	WCBM	Baltimore, Md.	1000	WNOP	Newport, Ky.	10000
CKL	Thompson, Man.	1000	WNAC	Lawrence, Mass.	50000	WFRB	Frostburg, Md.	2500
CKTB	St. Catharines, Ont.	5000	WDBC	Escanaba, Mich.	10000	WTAO	Cambridge, Mass.	2500
WGSN	Birmingham, Ala.	5000	KFEQ	St. Joseph, Mo.	5000	KPBM	Carlsbad, N. Mex.	10000
KAVL	Lancaster, Calif.	1000	WNRN	Binghamton, N.Y.	1000	WGSN	Huntington, N.Y.	1000
KFRS	San Francisco, Calif.	5000	WRVM	Rochester, N.Y.	2500	KRMB	Montreal, Que.	10000
WCKR	Miami, Fla.	5000	WPTF	Raleigh, N.C.	50000	WPAQ	Mount Airy, N.C.	10000
WCEH	Hawkinsville, Ga.	5000	WISR	Butler, Pa.	2500	KRMG	Tulsa, Okla.	5000
KUAM	Aogana, Guam	5000	WAPA	San Juan, P.Rico.	10000	WVCH	Chester, Pa.	10000
WRUS	Rossville, Ky.	5000	WMP5	Memphis, Tenn.	10000	WBS	Santurce, P.Rico	10000
KDL	Duluth, Minn.	5000	KENS	San Antonio, Tex.	5000	WBAB	Barnwell, S.C.	5000
WDAF	Kansas City, Mo.	5000	KDNW	Omak, Wash.	10000	WIRJ	Humbolt, Tenn.	2500
KOJM	Havra, Mont.	5000	690-434.5			WJIG	Tullahoma, Tenn.	5000
WGR	Manchester, N.H.	5000	CBU	Vancouver, B.C.	10000	KTRH	Houston, Tex.	5000
KGGM	Albuquerque, N.Mex.	5000	CBF	Montreal, Que.	50000	750-399.8		
WTVS	Charlotte, N.C.	5000	WVCK	Birmingham, Ala.	50000	WSB	Atlanta, Ga.	50000
WAYN	Columbus, Ohio	5000	KVNA	Flagstaff, Ariz.	1000	WBMD	Baltimore, Md.	10000
KCP	Philadelphia, Pa.	5000	KEVT	Tucson, Ariz.	2500	KMMJ	Grand Island, Neb.	1000
KILT	Houston, Tex.	5000	KBBA	Benton, Ark.	2500	WHEB	Portsmouth, N.H.	1000
KVNU	Logan, Utah	5000	KAPI	Pueblo, Colo.	2500	KSED	Durant, Okla.	2500
WLSL	Roanoke, Va.	5000	WADS	Ansonia, Conn.	5000	KXL	Portland, Oreg.	10000
KEPR	Kennewick, Wash.	5000	WAVE	Jacksonville, Fla.	25000	WPDX	Clarksburg, W.Va.	10000
620-483.6			KULA	Honolulu, Hawaii	10000	760-394.5		
CKCK	Regina, Sask.	5000	KGGF	Coffeyville, Kans.	10000	KGU	Honolulu, Hawaii	10000
KTAB	Phoenix, Ariz.	5000	WTIX	New Orleans, La.	10000	WJR	Detroit, Mich.	50000
KNGS	Hanford, Calif.	10000	KSTL	St. Louis, Mo.	10000	WPCS	Tarboro, N.C.	1000
KWSD	Mt. Shasta, Calif.	10000	KRCD	Prineville, Oreg.	10000	770-389.4		
KSTR	Grand Junction, Colo.	5000	KUSD	Vermillion, S.Dak.	10000	KUOM	Minneapolis, Minn.	5000
WJUN	St. Petersburg, Fla.	5000	KHCY	San Jose, Tex.	10000	WCAL	Northfield, Minn.	5000
WTRP	LaGrange, Ga.	10000	KPET	Lamesa, Tex.	10000	WEW	St. Louis, Mo.	10000
KWAL	Wallace, Idaho	1000	KEZY	Tyler, Tex.	2500	KQB	Albuquerque, N. Mex.	50000
KMNS	Sioux City, Iowa	5000	WCBY	Bristol, Va.	10000	WABC	New York, N.Y.	50000
WMT	Louisville, Ky.	5000	WNNT	Warsaw, Va.	2500	KXA	Seattle, Wash.	1000
WLBZ	Bangor, Maine	5000	700-428.3			780-384.4		
WJDX	Jackson, Miss.	5000	WLW	Cincinnati, Ohio	50000	WBBM	Chicago, Ill.	50000
WNUJ	Newark, N.J.	5000	710-422.3			WJAG	Norfolk, Neb.	1000
WHEN	Syracuse, N.Y.	5000	CJSP	Leamington, Ont.	2500	WCKB	Dunn, N.C.	10000
WDNC	Durham, N.C.	5000	CFRG	Gravelbourg, Sask.	50000	WBBO	Forest City, N.C.	10000
KGW	Portland, Oreg.	5000	CKVM	Ville Marie, Que.	1000	KSPI	Stillwater, Okla.	2500
WHJB	Greensburg, Pa.	1000	WRKR	Mobile, Ala.	1000	WARL	Arlington, Va.	10000
WCAY	Wayne, S.C.	1000	KMPG	Los Angeles, Calif.	10000	790-379.5		
WATE	Knoxville, Tenn.	5000	KICN	Denver, Colo.	5000	CBY	Corner Brook, N.F.	1000
KWFT	Wichita Falls, Tex.	5000	WGBS	Miami, Fla.	50000	CKMR	Newcastle, N.B.	1000
WCAX	Burlington, Vt.	5000	WRDM	Rome, Ga.	10000	CKSO	Sudbury, Ont.	5000
WYNR	Beeckley, W.Va.	5000	KEEL	Shreveport, La.	10000	WTUG	Tuscaloosa, Ala.	5000
WTMJ	Milwaukee, Wis.	5000	WHB	Kansas City, Mo.	10000	KCEE	Tucson, Ariz.	10000
630-475.9			WDR	New York, N.Y.	50000	KDSE	Texarkana, Ark.	1000
CFCO	Chatham, Ont.	1000	DRRH	Manila, P.I.	10000	KDAN	Eureka, Calif.	1000
CHLT	Sherbrooke, Que.	1000	WKBJ	Mayaguez, P.Rico	1000	CABQ	Los Angeles, Calif.	5000
CFGY	Charlottetown, P.E.I.	1000	WTRP	Paris, Tenn.	2500	WLBE	Leesburg, Fla.	5000
CJET	Smith Falls, Ont.	5000	KGNC	Amarillo, Tex.	10000	WPFA	Pensacola, Fla.	10000
KRC	Wilmington, Man.	1000	KURV	Edinburg, Tex.	250	WQXI	Atlanta, Ga.	5000
CKOV	Kelowna, B.C.	1000	KIRO	Seattle, Wash.	50000	WGXA	Calro, Ga.	10000
CKYL	Peace River, Alta.	1000	WDSM	Superior, Wis.	5000	KXXX	Colby, Kans.	5000
WAVU	Albertville, Ala.	10000	720-416.4			WAKY	Louisville, Ky.	5000
WJDB	Thomasville, Ala.	10000	WGN	Chicago, Ill.	50000	WRUM	Furford, Me.	1000
KJMD	Juneau, Alaska	10000	730-410.7			KGHL	Billings, Mont.	5000
KVMA	Magnolia, Ark.	10000	CJNR	Blind River, Ont.	1000	WNNY	Watertown, N.Y.	10000
KDD	Monterey, Calif.	10000	CKAC	Mississauga, Ont.	50000	WLSV	Wellsville, N.Y.	10000
KHOW	Denver, Colo.	5000	CKDM	Dauphin, Man.	1000	WTNC	Thomasville, N.C.	10000
WNAL	Washington, D.C.	5000	CKLQ	N. Vancouver, B.C.	10000	WKLM	Wilmington, N.C.	5000
WSAV	Savannah, Ga.	5000	KFQD	Anchorage, Alaska	10000	KXGD	Fargo, N.Dak.	5000
KIDO	Boise, Idaho	5000	WJMW	Athens, Ala.	10000	KWIL	Albany, Oreg.	5000
WLAP	Lexington, Ky.	5000	KNBY	Newport, Ark.	10000	WAEB	Allentown, Pa.	500
KTIB	Thibodaux, La.	5000	WKTG	Thomasville, Ga.	10000	WPIC	Sharon, Pa.	10000
WIMS	Ironwood, Mich.	5000	KBLR	Goodland, Kans.	10000	WEAN	Providence, R.I.	5000
KDWB	St. Paul, Minn.	5000	WFHM	Wichita, Kan.	2500	WVBD	Bamberg, S.C.	10000
KXOK	St. Louis, Mo.	10000	WMTG	Vanceville, Ky.	10000	WETB	Johnson City, Tenn.	10000
KGVV	Belgrade, Mont.	10000	KTRY	Bastrop, La.	2500	WNC	Memphis, Tenn.	5000
KOH	Reno, Nev.	5000	WARB	Covington, La.	2500	KTH	Houston, Tex.	5000
KLEA	Livingston, N.Mex.	5000	WMMS	Bath, Maine	5000	KFYD	Lubbock, Tex.	5000
WIRC	Hickory, N.C.	10000	WACE	Chicopee, Mass.	5000	WSIG	Mount Jackson, Va.	10000
WNFD	Wilmington, N.C.	5000	WRE	Warrenton, Me.	10000	WTAR	Norfolk, Va.	5000
KJCL	Scranton, Pa.	5000	KWDA	Worthington, Minn.	10000	KVOS	Bellingham, Wash.	1000
WPRO	Providence, R.I.	5000	KUPA	Billings, Mont.	5000	KNEW	Spokane, Wash.	5000
KGFX	Pierre, S.Dak.	2500	WDS	Ontonagon, N.Y.	10000	WEAU	Washington, Wis.	5000
KMAC	San Antonio, Tex.	5000	WFMC	Goldsboro, N.C.	10000	800-374.8		
KGDN	Edmunds, Wash.	5000	WHS	Shelby, N.C.	10000	CHAB	Moose Jaw, Sask.	10000
KZUN	Opportunity, Wash.	5000	WHRW	Bowling Green, Ohio	2500	CKOK	Penitton, B.C.	10000
640-468.5			KBQY	Medford, Oreg.	10000	CFOB	Ft. Frances, Ont.	1000
CBN	St. John's, N.F.	10000	WNAH	Nanticoke, Pa.	10000	CJBC	Bellefonte, Ont.	1000
KEL	Los Angeles, Calif.	50000	WPIT	Pittsburgh, Pa.	10000	CKRW	Windsor, Ont.	50000
WOI	Ames, Iowa	50000	WPAL	Charleston, S.C.	10000	CLRQ	Quebec, Que.	10000
WHKK	Akron, Ohio	1000	WLLN	Lenoir, Tenn.	10000	CJAD	Montreal, Que.	10000
WNAD	Norman, Okla.	1000	WKSJ	Grand Prairie, Tex.	5000	VOWR	St. Johns, N.F.	1000
650-461.3			KSVN	Ogden, Utah	10000	WHOS	Decatur, Ala.	10000
KPOA	Honolulu, Hawaii	10000	WPIK	Alexandria, Va.	10000	WNGY	Montgomery, Ala.	10000
WSM	Nashville, Tenn.	50000	WMNA	Gretna, Va.	10000	KING	Juneau, Alaska	5000
KRCT	Baytown, Texas	2500	KULE	Ephrata, Wash.	10000	KAGH	Crossett, Ark.	2500
660-454.3			740-405.2			KVON	Norriton, Ark.	2500
KFAR	Fairbanks, Alaska	10000	CBXA	Edmonton, Alta.	250	CKBK	Bakersfield, Calif.	2500
KOWH	Omaha, Nebr.	5000	CBL	Toronto, Ont.	50000	KHIL	Brighton, Colo.	5000
WRCA	New York, N.Y.	50000	WBAM	Montgomery, Ala.	50000	WLAD	Danbury, Conn.	2500
WESC	Greenville, S.C.	50000	780-340.7			WMBM	Miami Beach, Fla.	10000
CKSKY	Dallas, Tex.	1000	WCSB	New York, N.Y.	50000	WSUZ	Palatka, Fla.	10000
						WJAT	Swainsboro, Ga.	10000
						KXIC	Iowa City, Iowa	10000
						WRUS	Russellville, Ky.	10000

Ke.	Wave Length	W.P.	Ke.	Wave Length	W.P.	Ke.	Wave Length	W.P.	Ke.	Wave Length	W.P.
WRZ Clinton, N.C.	10000		WWR Russellville, Ala.	10000		WAGN Presque Isle, Maine	5000		KEAP Fresno, Calif.	5000	
WRFD Worthington, Ohio	50000		KAR Little Rock, Ark.	5000		WOR Boston, Mass.	5000		KEB Los Angeles, Calif.	5000	
890-336.9			KDES Park Springs, Calif.	1000		WBT Detroit, Mich.	1000		KGLN Glenview Spgs., Colo.	1000	
WLS Chicago, Ill.	50000		KVEC San Luis, Ohio	1000		KRSI St. Louis Park, Minn.	10000		WRSC Groton, Conn.	5000	
WHNC Henderson, N.C.	10000		KIUP Durango, Colo.	5000		WBKH Hattiesburg, Miss.	5000		WUB Washington, D.C.	5000	
KBYE Okla. City, Okla.	10000		KREX Grd. Junction, Colo.	5000		KLIK Jefferson City, Mo.	5000		WDVH Gainesville, Fla.	5000	
900-333.1			KLMR Lamar, Colo.	1000		WBBF Rochester, N.Y.	1000		WTO Marianna, Fla.	1000	
CKTS Sherbrooke, Que.	1000		WMEG Eu Galle, Fla.	10000		WBX Utica, N.Y.	5000		WLOB Pensacola, Fla.	5000	
CHML Hamilton, Ont.	5000		WGST Atlanta, Ga.	5000		WPET Greensboro, N.C.	5000		WBOP Pompano Beach, Fla.	10000	
CHNO Sudbury, Ont.	10000		KAHU Waipahu, Hawaii	10000		WNCC Barnesboro, Pa.	5000		WKKY Hartwell, Ga.	10000	
CJBR Rimouski, Que.	10000		WMOK Metropolis, Ill.	10000		WPEN Philadelphia, Pa.	5000		WBBY Perry, Ga.	5000	
CKJL St. Jerome, Que.	10000		WBAW W. Lafayette, Ind.	5000		WSPA Spartanburg, S.C.	5000		WUP Russellville, Ga.	5000	
CJVI Victoria, B.C.	10000		KFNF S.W. Des Moines, Iowa	1000		WWT Waterbury, S.Dak.	10000		KUPI Idaho Falls, Idaho	1000	
CKBJ Yorkton, Sask.	10000		WTGW Whitesburg, Ky.	10000		WGF Franklin, Tenn.	10000		WITY Danville, Ill.	1000	
CJGX Princeton, Sask.	10000		WBOC Bogalusa, La.	10000		KDSX Denton, Tex.	500		KOKA Shreveport, La.	5000	
WATV Birmingham, Ala.	10000		KTCO Jonesboro, La.	5000		KPRC Houston, Tex.	5000		WCAP Lowell, Mass.	1000	
WGOK Mobile, Ala.	10000		WPIX Lexington Pk., Md.	5000		KSEL Lubbock, Tex.	1000		WPBC Minneapolis, Minn.	10000	
WGOK Ozark, Ala.	10000		WMPL Hancock, Mich.	10000		WXGI Richmond, Va.	10000		WAFP MeComb, Miss.	10000	
KPRB Fairbanks, Alaska	10000		KOHL Fairbault, Minn.	10000		KJR Seattle, Wash.	5000		KMBC Kansas City, Mo.	5000	
KWQZ Harrisburg, Pa.	10000		KWAD Wadena, Minn.	1000		WKAZ Charleston, W.Va.	5000		KSGM Ste. Genevieve, Mo.	500	
KBIF Centerville, Calif.	10000		KRAM Las Vegas, Nev.	1000		WKTL Sheboygan, Wis.	5000		KYVR Grants, N.Mex.	1000	
WJWL Georgetown, Del.	10000		KQEO Reno, Nev.	1000		960-312.3			KMIN Grants, N.Mex.	1000	
WSWN Belle Glade, Fla.	10000		KQED Albuquerque, N.Mex.	1000		CFAC Calgary, Alta.	10000		WTRY Troy, N.Y.	5000	
WMOP Ocala, Fla.	10000		WTTM Trenton, N.J.	1000		CHWS Halifax, N.S.	10000		WKLM Wilmington, N.C.	5000	
WCGA Calhoun, Ga.	10000		WKRT Cortland, N.Y.	1000		CKWT Watertown, N.Y.	5000		WAAA Wm.-Salem, N.C.	10000	
WCRY Macon, Ga.	2500		WGHQ Saugerties, N.Y.	10000		WBRC Birmingham, Ala.	5000		WONE Dayton, Ohio	5000	
WJIV Savannah, Ga.	2500		WBBB Burlington, N.C.	5000		WMOZ Mobile, Ala.	1000		WIK Wilkes-Barre, Pa.	5000	
KSIR Wichita, Kan.	1000		WMNI Columbus, Ohio	500		KOOL Phoenix, Ariz.	5000		KDSJ Deadwood, S.Dak.	1000	
WKYV Louisville, Ky.	2500		KGAP Lebanon, Ore.	1000		KAVR Apple Valley, Calif.	5000		KWSJ Nashville, Tenn.	5000	
WLSI Pikeville, Ky.	2500		WJAP Providence, R.I.	5000		KNEZ Lompoc, Calif.	500		KFRD Roseton, Tex.	1000	
KREH Okadale, La.	2500		WTNO Orangeburg, S.C.	1000		KABL Oakland, Calif.	1000		KSCG Richfield, Utah	5000	
WCME Brunswick, Maine	5000		KEZU Rapid City, S.Dak.	1000		WELI New Haven, Conn.	5000		WVHC Bristol, Va.	5000	
WATC Gary, Mich.	1000		WLIV Livingston, Tenn.	10000		WLOL Lake City, Fla.	5000		WMEK Chase City, Va.	500	
KTIS Minneapolis, Minn.	10000		KELP El Paso, Tex.	1000		WJCM Sebring, Fla.	10000		KUTI Yakima, Wash.	5000	
WDDT Greenville, Miss.	10000		KECK Odessa, Tex.	1000		WJCM Sebring, Fla.	10000		WHAW Weston, W.Va.	10000	
KFAL Fulton, Mo.	10000		KTLL Texas City, Tex.	10000		WRFCA Athens, Ga.	5000		WUBC Manitowoc, Wis.	10000	
KJSK Columbus, Neb.	10000		KTIY Olympia, Wash.	10000		KSRA Salmon, Idaho	10000		WPRE Prairie du Chien, Wis.	5000	
WOTV Nashua, N.H.	10000		KXLY Spokane, Wash.	5000		WSBT South Bend, Ind.	5000		990-302.8		
WBRV Boonville, N.Y.	2500		WMMN Fairmont, W.Va.	5000		KMA Shenandoah, Iowa	5000		CBW Winnipeg, Man.	5000	
WSPN Saratoga Spgs., N.Y.	2500		WOKY Milwaukee, Wis.	1000		WPRT Prestonsburg, Ky.	10000		GBT Grand Falls, N.F.	1000	
WAYN Rockingham, N.C.	10000		930-322.4			KROF Abbeville, La.	10000		WBB WFayette, Ala.	10000	
WIAM Williamson, N.C.	10000		CFBC Saint John, N.B.	5000		WBOC Salisbury, Md.	5000		WFGT Ft. Worth, Tex.	5000	
KFNW Fargo, N.Dak.	10000		CJCA Edmonton, Alta.	10000		WGM Fitchburg, Mass.	5000		WHAK Rogers City, Mich.	5000	
WAND Canton, Ohio	5000		CJON St. John's, N.F.	10000		KLTF Little Falls, Minn.	5000		KLTT Tucson, Ariz.	10000	
WFRO Fremont, Ohio	5000		WETO Gadsden, Ala.	10000		WABG Greenwood, Miss.	1000		KKIS Pittsburg, Calif.	5000	
WCFA Clearfield, Pa.	10000		KTKN Ketchikan, Alaska	10000		KFVS Cape Girardeau, Mo.	1000		KLIR Denver, Colo.	10000	
WFLN Philadelphia, Pa.	10000		KAPR Douglas, Ariz.	10000		KNEB Scottsbluff, Neb.	1000		WBZY Torrington, Conn.	10000	
WKXY Knoxville, Tenn.	10000		KHJ Los Angeles, Calif.	5000		KWYK Farmington, N.Mex.	10000		WHOO Orlando, Fla.	10000	
WCOR Lebanon, Tenn.	10000		KTUD Durango, Colo.	5000		WEAN Pittsburg, N.Y.	5000		WDDW Dawson, Ga.	10000	
KALT Atlanta, Tenn.	10000		WCSB Hillford, Del.	5000		WATC Kingston, N.C.	5000		WCAZ Carthage, Ill.	10000	
KMCO Conze, Tex.	5000		WJAX Jacksonville, Fla.	5000		WSTW Wooster, Ohio	10000		WITZ Jasper, Ind.	10000	
KFLD Floydada, Tex.	2500		WKXY Sarasota, Fla.	1000		KGWA Enid, Okla.	1000		KAYL Storm Lake, Iowa	2500	
KCLW Hamilton, Tex.	2500		WNGR Bainbridge, Ga.	5000		KLAD Klamath Falls, Ore.	5000		KRSL Russell, Kans.	2500	
WAFC Staunton, Va.	10000		KSEI Pocatello, Idaho	5000		WHYL Carlisle, Pa.	5000		WJMR New Orleans, La.	2500	
KUEN Wenatchee, Wash.	300		WTAD Quincy, Ill.	5000		WADP Kane, Pa.	10000		KCLP Rayville, La.	5000	
WATK Antigo, Wis.	2500		WKCT Bowling Green, Ky.	1000		WATS Sayre, Pa.	10000		WABO Waynesboro, Miss.	2500	
910-292.5			WFND Frederick, Md.	1000		WELB Beaufort, N.C.	10000		KRMO Monet, Mo.	2500	
CJVD Drumheller, Alta.	1000		WFEB Holyoke, Mass.	5000		WBMC McMinnville, Tenn.	10000		KSPV Artesia, N.Mex.	1000	
CKLY Lindsay, Ont.	1000		WBEK Back Creek, Mich.	5000		KIMP Mt. Pleasant, Tex.	10000		WEEB Southern Pines, N.C.	10000	
CBQ Ottawa, Ont.	5000		WSLJ Jackson, Miss.	5000		KGKL San Angelo, Tex.	5000		WJETH Gallipolis, Ohio	10000	
CFJC Kamloops, B.C.	10000		KWOC Poplar Bluff, Mo.	1000		KDVO Provo, Utah	5000		KABY Albany, N.Y.	2500	
CHRL Roberval, Que.	10000		KOFI Kalispell, Mont.	5000		KRBJ Roanoke, Va.	5000		WIBG Philadelphia, Pa.	5000	
CKHO Phoenix, Ariz.	5000		KOGA Ogallala, Neb.	5000		WALE Richland, Wash.	1000		WVSC Somerset, Pa.	2500	
KLCN Blytheville, Ark.	5000		WPNH Rochester, N.H.	5000		KATH Shawano, Wis.	1000		WPRA Mayaguez, P.R.	1000	
KAMD Camden, Ark.	5000		WPAT Paterson, N.J.	5000		970-309.1			WAKN Aiken, S.C.	1000	
KDEE El Cajon, Calif.	10000		WBEH Buffalo, N.Y.	5000		CKCH Hull, Que.	5000		WNOX Knoxville, Tenn.	10000	
KEWB Oakland, Calif.	10000		WBERH Hamilton, Ala.	5000		WTRH Troy, Ala.	5000		KWAM Memphis, Tenn.	10000	
KOXR Oxnard, Calif.	10000		WBTB Tusculum, N.C.	5000		KNEA Jonesboro, Ark.	10000		KTRM Beaumont, Tex.	100	
KPOF nr. Denver, Colo.	5000		WEOL Elyria, Ohio	5000		KBIS Bakersfield, Calif.	10000		KSVD Wichita Falls, Tex.	10000	
WHAY New Britain, Conn.	5000		WKY Oklahoma City, Okla.	5000		KCHV Coachella, Calif.	10000		KTUT Tooele, Utah	10000	
WPLA Plant City, Fla.	10000		KAGI Grants Pass, Ore.	1000		KBEE Modesto, Calif.	10000		WNRY Narrows, Va.	1000	
WGAF Valdosta, Ga.	5000		WCNR Bloomsburg, Pa.	10000		KFEL Pueblo, Colo.	10000		WANT Richmond, Va.	1000	
WAKO Lawrenceville, Ill.	5000		KSON Aberdeen, S.D.	10000		WFLA Tampa, Fla.	5000		WKLJ Sparta, Wis.	250	
WSUJ Iowa City, Iowa	5000		WSEV Sevierville, Tenn.	5000		WHLB Atlanta, Ga.	5000		1000-299.8		
WCSB Boston, Rhode, La.	5000		KDET Center, Tex.	10000		WVOP Vidalia, Ga.	5000		CKBW Bridgewater, N.S.	1000	
WABI Bangor, Maine	5000		KENY Bellingham-Ferndale Wash.	10000		KHBC Hilo, Hawaii	1000		WCFL Chicago, Ill.	5000	
WDFD Flint, Mich.	5000		WSAZ Huntington, W.Va.	5000		KAYT Rupert, Idaho	10000		KTOK Okla. City, Okla.	5000	
WCOC Meridian, Miss.	5000		WLBL Auburndale, Wis.	5000		WAVE Louisville, Ky.	5000		KSTA Coleman, Tex.	2500	
KOYN Billings, Mont.	10000		940-319.0			KSFL Alexandria, La.	1000		KJAT Haverhill, Vt.	5000	
KYSS Missoula, Mont.	10000		CBM Montreal, Que.	5000		WCSH Portland, Maine	5000		WHWB Richmond, Va.	1000	
KBIM Roswell, N.Mex.	5000		CJGX Yorkton, Sask.	10000		WAND Aberdeen, Md.	5000		KOMO Seattle, Wash.	5000	
WLAS Jacksonville, N.C.	10000		CJIB Vernon, B.C.	10000		WESO Southbridge, Mass.	10000		1010-296.9		
KLJB Miami, N.Dak.	10000		KFRE Fresno, Calif.	5000		WJAN (Shemung, Mich.)	5000		CBX Edmonton, Alta.	5000	
KGIC Miami, Okla.	10000		WINZ Miami, Fla.	5000		KMKT Jackson, Mich.	1000		CFRB Toronto, Ont.	5000	
KURY Brookings, Ore.	500		WMAZ Macon, Ga.	5000		KOOK Billings, Mont.	5000		KVNC Winslow, Ariz.	1000	
WAVL Apollo, Pa.	10000		WNIA New York, N.Y.	5000		KLNT No. Platte, Neb.	5000		KLRA Little Rock, Ark.	10000	
WGBI Seranton, Pa.	10000		KIDA Mt. Vernon, Ill.	1000		WNTA Newark, N.J.	5000		KCHJ Delano, Calif.	5000	
WSBA York, Pa.	10000		WYLD New Orleans, La.	1000		WBRV Buffalo, N.Y.	5000		KCMJ Palm Spgs., Calif.	1000	
WPRP Ponca, P.R.	10000		WESA Charleston, N.C.	250		WCHN Norwich, N.Y.	5000		KSAY San Fran., Calif.	10000	
WDRD Spartanburg, S.C.	5000		WIPR San Juan, P.R.	10000		WBIT Canton, N.C.	10000		WCNU Crestview, Fla.	10000	
WJHL Johnson City, Tenn.	5000		KIXZ Amarillo, Tex.	1000		WDAY Fargo, N.Dak.	5000		WZRO Jacksonville Beach, Fla.	1000	
WEPG S. Pittsburgh, Tenn.	5000		950-315.6			WICA Ashtabula, Ohio	5000		WGUN Deatur, Ga.	5000	
KRIO McAllen, Tex.	1000		CKNB Campbellton, N.B.	1000		WATH Athens, Ohio	10000		WCSI Columbus, Ind.	5000	
KRRV Sherman, Tex.	1000		CKBB Barris, Ont.	5000		KAKC Tulsa, Okla.	10000		KSMN Mason City, Iowa	10000	
KALL Salt Lake City, Utah	10000		WRMA Montgomery, Ala.	10000		KOIN Portland, Ore.	5000		KIND Independence, Kans.-	2500	
WRRJ White River Junction, Vermont	10000		KXJK Forrest City, Ark.	5000		WWSW Pittsburg, Pa.	5000		KDLA DeRider, La.	10000	
WRNL Richmond, Va.	5000		KFSF Ft. Smith, Ark.	1000		WJMX Florence, S.C.	5000		WSD Baltimore, Md.	10000	
WHYE Roanoke, Va.	10000		KABN Auburn, Calif.	1000		KNOK Ft. Worth, Tex.	5000		KCHJ Chillicothe, Mo.	2500	
KORD Paso, Wash.	10000		KIMN Denver, Colo.	5000		KREM Spokane, Wash.	5000		KJC Festus, Mo.	2500	
KODE Renton, Wash.	1000		WFBS Ft. Walton Bch., Fla.	10000		WYD Pineville, W.Va.	1000		KRVN Vicksburg, Neb.	2500	
KISN Vancouver, Wash.	1000		WFO Orlando, Fla.	5000		WHA Madison, Wis.	5000		WINS New York, N.C.	5000	
WHSM Hayward, Wis.	10000		WGTA Summerville, Ga.	10000		980-305.9			WABZ Albermarle, N.C.	1000	
WDR Sturgeon Bay, Wis.	5000		WGOV Valdosta, Ga.	5000		CKNW New Westminster, Brit. Columbia	5000		WELS Kinston, N.C.	1000	
920-325.9			KBOI Boise, Idaho	5000		CFPL London, Ont.	10000		WITT Lewisburg, Pa.	2500	
CJCH Halifax, N.S.	10000		KLER Orofino, Idaho	5000		CFBV Quebec, Que.</					

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KMLW	Marlin, Tex.	2500	KSCO	Santa Cruz, Calif.	5000	WRNO	Orangeburg, S.C.	5000
WELK	Charlottesville, Va.	10000	WTIC	Hartford, Conn.	50000	WTYC	Rock Hill, S.C.	10000
WMEV	Marion, Va.	10000	WKLO	Louisville, Ky.	5000	WSWN	Seneca Townshin. South Carolina	10000
WCST	Berkeley Sprgs., W. Va.	2500	WOAP	Owosso, Mich.	2500	WAPD	Chattanooga, Tenn.	5000
WSPT	Stevens Pt., Wis.	10000	WINE	Kenmore, N.Y.	10000	WCWK	Morristown, Tenn.	1000
1020—293.9			WEWO	Laurinburg, N.C.	10000	WTAW	Bryan, Tex.	10000
KPOP	Los Angeles, Calif.	5000	KWJJ	Portland, Oreg.	10000	KCCO	Corpus Christi, Tex.	10000
WCIL	Carbondale, Ill.	10000	WEFP	Pittsburgh, Pa.	10000	KOYE	El Paso, Tex.	10000
WPEO	Peoria, Ill.	10000	KRLD	Dallas, Tex.	5000	KJBC	Midland, Tex.	10000
KDKA	Pittsburgh, Pa.	50000	1090—275.1			KPNG	Port Neches, Tex.	1150
1030—291.1			CHEC	Lethbridge, Alta.	5000	KOLJ	Quanah, Tex.	5000
WBZ	Boston, Mass.	50000	CHIB	Brampton, Ont.	250	KOFE	Pullman, Wash.	10000
WZZA	Springfield, Mass.	5000	CHR5	St. Jean, Que.	5000	KAYO	Seattle, Wash.	5000
KOB	Albuquerque, N. Mex.	10000	KTHS	Little Rock, Ark.	50000	KKEY	Vancouver, Wash.	10000
KCTA	Corpus Christi, Tex.	50000	WCRA	Effingham, Ill.	2500	WELC	Welch, W. Va.	10000
1040—288.3			KNWS	Waterloo, Iowa	10000	WXKX	Chippewa Falls, Wis.	50000
KHVV	Honolulu, Hawaii	5000	WBAL	Baltimore, Md.	50000	WISN	Milwaukee, Wis.	5000
WHD	Des Moines, Iowa	50000	WILD	Boston, Mass.	10000	1160—258.5		
KTKL	Dallas, Tex.	10000	WJUS	Muskegon, Mich.	10000	WJJD	Chicago, Ill.	50000
WIVI	Christiansted, V.I.	250	KING	Seattle, Wash.	50000	KSL	Salt Lake City, Utah	50000
1050—285.5			1100—272.6			1170—256.3		
CFGP	Grande Prairie, Alta.	10000	KJBS	San Francisco, Calif.	10000	CFNS	Saskatoon, Sask.	1000
CKSB	St. Boniface, Man.	10000	WBBB	Carrollton, Ga.	2500	WCOV	Montgomery, Ala.	10000
CJIC	Sault Ste. Marie, Ont.	250	WHLI	Hempstead, N.Y.	100000	KCBA	San Diego, Calif.	50000
CHUN	Toronto, Ont.	5000	KYW	Cleveland, Ohio	50000	KCJG	San Jose, Calif.	1000
WRFS	Alexander City, Ala.	10000	WGPA	Bethlehem, Pa.	2500	WLBH	Mattoon, Ill.	2500
WCRI	Scottsboro, Ala.	2500	1110—270.1			KSTT	Davenport, Iowa	1000
KVWM	Show Low, Ariz.	5000	CTTJ	Galt, Ont.	250	KVOO	Tulsa, Okla.	50000
KVLC	Little Rock, Ark.	10000	KBLA	Pasadena, Calif.	10000	WLEO	Ponce, P.R.	250
KWFO	San Mateo, Calif.	10000	WALT	Tampa, Fla.	100000	KPUG	Bellingham, Wash.	1000
KOFS	Wasco, Calif.	10000	KIPA	Hilo, Hawaii	1000	WVVA	Wheeling, W. Va.	50000
KLMO	Longmont, Colo.	2500	WMBI	Chicago, Ill.	50000	1180—254.1		
WJSB	Crestview, Fla.	10000	KFAA	Omaha, Neb.	50000	WLDS	Jacksonville, Ill.	10000
WIVY	Jacksonville, Fla.	10000	WBT	Charlotte, N.C.	50000	WHAM	Rochester, N.Y.	50000
WHBD	Tampa, Fla.	2500	KBND	Bend, Oreg.	5000	1190—252.0		
KVMF	Titusville, Fla.	5000	WNAR	Norristown, Pa.	5000	KNBA	Vallejo, Calif.	2500
WJAZ	Albany, Ga.	10000	WVJP	Caguas, P.R.	250	WOWO	Ft. Wayne, Ind.	50000
WAUG	Augusta, Ga.	1000	WHIM	Providence, R.I.	10000	WANN	Annapolis, Md.	10000
WBIE	Marietta, Ga.	5000	1120—267.7			WKOX	Framingham, Mass.	10000
KZIN	Coeur D'Alene, Idaho	2500	WUST	Bethesda, Md.	2500	WLIB	New York, N.Y.	10000
WDZ	Decatur, Ill.	10000	KNOX	St. Louis, Mo.	50000	KEX	Portland, Oreg.	50000
KNCO	Garden City, Kans.	10000	WROL	Buffalo, N.Y.	10000	KLIF	Dallas, Tex.	50000
WZFP	Covington, Ky.	10000	KCLE	Cleburne, Tex.	2500	WDTV	St. John, V.I.	1000
WYTH	Mayfield, Ky.	10000	1130—265.3			1200—249.9		
KLPL	Lake Providence, La.	2500	CKWX	Vancouver, B.C.	50000	WDAI	San Antonio, Tex.	50000
KCIJ	Shreveport, La.	2500	KSDO	San Diego, Calif.	5000	1210—247.8		
WGAY	Silver Sprgs., Md.	10000	KWKH	Shreveport, La.	50000	WCNT	Centralia, Ill.	10000
WPAG	Ann Arbor, Mich.	10000	WCAR	Detroit, Mich.	50000	WKNX	Saginaw, Mich.	10000
KLOH	Pipestone, Minn.	10000	WDGY	Minneapolis, Minn.	50000	WADE	Wadesboro, N.C.	10000
WACR	Columbus, Miss.	10000	WNEW	New York, N.Y.	50000	WADE	Dayton, Ohio	2500
KSIS	Sedalia, Mo.	10000	1140—263.0			WCAU	Philadelphia, Pa.	50000
KRBD	Las Vegas, Nev.	5000	CKXL	Calgary, Alta.	10000	1210—245.8		
WBNC	Conway, N.H.	10000	KRAK	Sloekton, Calif.	5000	CJOC	Lethbridge, Alta.	10000
WSEN	Baldwinsville, N.Y.	2500	WME	Miami, Fla.	10000	CKDA	Victoria, B.C.	10000
WSTS	Massena, N.Y.	10000	KGBM	Boise, Idaho	10000	KVSA	Kenora, Ont.	1000
WNGM	New York, N.Y.	50000	WSIV	Pekin, Ill.	10000	KCEC	New Glasgow, N.S.	10000
WBTL	Farmville, N.C.	2500	KLPR	Oklahoma City, Okla.	10000	KCKW	Moncton, N.B.	10000
WFSC	Franklin, N.C.	5000	WITA	San Juan, P.R.	500	CISS	Cornwall, Ont.	1000
WLDN	Lincolnton, N.C.	10000	KSDO	Sioux Falls, S.Dak.	10000	KCSM	Shawinigan, Quebec	1000
WGBP	Sanford, Fla.	2500	KORC	Mineral Wells, Tex.	250	WEDR	Birmingham, Ala.	10000
KCCO	Clinton, O.K.	2500	WRVA	Richmond, Va.	50000	WPRN	Buiter, Ala.	10000
KFMJ	Tulsa, Okla.	10000	1150—260.7			KIBS	Palo Alto, Calif.	10000
KUBE	Pendleton, Oreg.	10000	CKSA	Lloydminster, Alta.	1000	KFCF	Denver, Colo.	10000
KEED	Springfield, Oreg.	10000	CHSJ	Saint John, N.B.	5000	WTTT	Arlington, Fla.	2500
WBUT	Buttery, Pa.	2500	CKDC	Hamilton, Ont.	5000	WKBX	Kissimmee, Fla.	2500
WLYC	Williamsport, Pa.	10000	CKX	Brandon, Man.	5000	WFEC	Miami, Fla.	2500
WSMT	Sparta, Tenn.	10000	CKTR	Three Rivers, Que.	10000	WCLK	Camilla, Ga.	10000
KLEN	Killeen, Tex.	2500	WBCA	Bay Minnette, Ala.	5000	WRCK	Rockmart, Ga.	2500
WGBT	Gate City, Va.	2500	WGEA	Geneva, Ala.	10000	WSTF	Thomasson, Ga.	2500
WBRG	Lynchburg, Va.	10000	WRO	Okaloosa, Fla.	5000	WFD	LaSalle, Ill.	10000
WCMS	Norfolk, Va.	10000	WCOS	Coolidge, Ariz.	1000	WFRS	Waukegan, Ill.	10000
KNBX	Kirkland, Wash.	10000	KLRL	No. Little Rock, Ark.	5000	WSLM	Salem, Ind.	10000
WCEF	Parkersburg, W. Va.	10000	KJAX	Santa Rosa, Calif.	5000	KJAN	Atlantic, Iowa	2500
WECL	Eau Claire, Wis.	10000	KGMC	Englewood, Colo.	10000	KOFO	Ottawa, Kans.	2500
WLIP	Kenosha, Wis.	2500	KCNX	Midland, Conn.	5000	WFKN	Franklin, Ky.	2500
KWIV	Douglas, Wyo.	2500	WDEL	Wilmington, Del.	5000	KBCL	Bossier City, La.	2500
1060—282.8			WDMB	Daytona Beach, Fla.	10000	WLBH	Dunham Springs, La.	2500
CFCN	Calgary, Alta.	10000	WTMP	Tampa, Fla.	50000	WSME	Sanford, Maine	10000
CJLR	Quebec, Que.	5000	WFPM	Fort Valley, Ga.	10000	WBCH	Hastings, Mich.	2500
KPAY	Chico, Calif.	10000	WJEM	Valdosta, Ga.	10000	WAVN	Stillwater, Minn.	10000
WNOE	New Orleans, La.	50000	KANI	Oahu, Hawaii	1000	WMDC	Hazlehurst, Miss.	2500
WHFB	Benton Harbor, Mich.	10000	WGH	Marion, Ill.	50000	KBHM	Branson, Mo.	10000
WMAF	Montre, N.C.	2500	WKY	Des Moines, Iowa	1000	KGMO	Cape Girardeau, Mo.	2500
WCMW	Canton, Ohio	10000	KSAL	Salina, Kans.	5000	KLPW	Union, Mo.	2500
WRCV	Philadelphia, Pa.	50000	WMST	Mid. Sterling, Ky.	5000	WKBY	Keene, N.H.	10000
1070—280.2			WLOC	Mumfordsville, Ky.	10000	WGNV	Norburgh, N.Y.	10000
CBA	Sackville, N.B.	50000	WJBO	Baton Rouge, La.	5000	WIND	New Syracuse, N.Y.	10000
CHOK	Sarnia, Ont.	50000	WGHM	Skowhegan, Maine	50000	WKMT	Kings Mtn., N.C.	10000
WAPI	Birmingham, Ala.	50000	WCOP	Boston, Mass.	5000	WREJ	Reldsville, N.C.	2500
KNX	Los Angeles, Calif.	50000	WGEN	Mid. Pleasant, Mich.	10000	WENC	Whiteville, N.C.	10000
WVCG	Corral Gables, Fla.	10000	WGEN	Albany, Minn.	5000	KEYD	Oakes, N.Dak.	10000
WIBC	Indianapolis, Ind.	50000	KRNS	Osage Beach, Mo.	10000	WGAR	Cleveland, Ohio	50000
KFB	Wichita, Kans.	10000	KSEN	Sielby, Mont.	1000	WERT	Van Wert, Ohio	2500
KHMO	Hannibal, Mo.	5000	KDEF	Albuquerque, N.Mex.	10000	WGYN	Gwynn, Okla.	10000
WHPE	High Point, N.C.	10000	WRUN	Utica, N.Y.	5000	WJUN	Mexico, Pa.	2500
WDIA	Memphis, Tenn.	50000	WFNS	Burlington, N.C.	10000	WRIB	Providence, R.I.	10000
KOPY	Alice, Tex.	1000	WGBR	Goldboro, N.C.	5000	WALO	Waterboro, S.C.	10000
KWOW	Madison, Wis.	10000	WUE	Aiton, Ohio	10000	WFWL	Cademy, Tenn.	250
1080—277.6			WMA	Lima, Ohio	1000	WPEH	Etowah, Tenn.	10000
CHED	Edmonton, Alta.	10000	KNEC	McAlester, Okla.	1000	WPHY	Millington, Tenn.	250
1090—275.1			KAGD	Klamath Falls, Oreg.	5000	KLBS	Livingston, Tex.	2500
1230—243.8			WHUN	Huntindon, Pa.	10000	1230—243.8		
CFWC	Camrose, Alta.	1000	WKPA	New Kensington, Pa.	10000	CFCW	Camrose, Alta.	1000
CHFC	Churchill, Man.	250	WORA	Mayaguez, P.R.	1000	CFCL	Chesterfield, Que.	250
CFGR	Gravelbourg, Sask.	250	1290—275.1			CFBR	Gravelbourg, Sask.	250
CFYT	Dawson City, Yukon T.	100	CHEC	Lethbridge, Alta.	5000	CFYT	Dawson City, Yukon T.	100
CJBA	Belleville, Ont.	250	CHIB	Brampton, Ont.	250	CJBA	Belleville, Ont.	250
CJFP	Port Arthur, Ont.	1000	CHR5	St. Jean, Que.	5000	CJFP	Port Arthur, Ont.	1000
CJEC	New Glasgow, N.S.	1000	KTHS	Little Rock, Ark.	50000	CJEC	New Glasgow, N.S.	1000
CLLD	Theftord Mines, Que.	250	WCRA	Effingham, Ill.	2500	CLLD	Theftord Mines, Que.	250
CKMP	Midland, Ont.	100	KNWS	Waterloo, Iowa	10000	CKMP	Midland, Ont.	100
VQAR	St. John's, Nfld.	100	WBAL	Baltimore, Md.	50000	VQAR	St. John's, Nfld.	100
KVXD	Val D'Or, Que.	250	WILD	Boston, Mass.	10000	KVXD	Val D'Or, Que.	250
WAUD	Auburn, Ala.	250	WJUS	Muskegon, Mich.	10000	WAUD	Auburn, Ala.	250
WJBB	Haleyville, Ala.	250	KING	Seattle, Wash.	50000	WJBB	Haleyville, Ala.	250
WBHP	Huntsville, Ala.	250	1100—272.6			WBHP	Huntsville, Ala.	250
WNUZ	Talledega, Ala.	250	KJBS	San Francisco, Calif.	10000	WNUZ	Talledega, Ala.	250
WTBC	Tuscaloosa, Ala.	250	WBBB	Carrollton, Ga.	2500	WTBC	Tuscaloosa, Ala.	250
KTFW	Sitka, Alaska	250	WHLI	Hempstead, N.Y.	100000	KTFW	Sitka, Alaska	250
KSUN	Sischo, Ariz.	250	KYW	Cleveland, Ohio	50000	KSUN	Sischo, Ariz.	250
KAAA	Kingman, Ariz.	250	WGPA	Bethlehem, Pa.	2500	KAAA	Kingman, Ariz.	250
KRIZ	Phoenix, Ariz.	250	1110—270.1			KRIZ	Phoenix, Ariz.	250
KCON	Conway, Ark.	250	CTTJ	Galt, Ont.	250	KCON	Conway, Ark.	250
KFPW	Ft. Smith, Ark.	250	KBLA	Pasadena, Calif.	10000	KFPW	Ft. Smith, Ark.	250
KBTM	Bonarboro, Ark.	250	WALT	Tampa, Fla.	100000	KBTM	Bonarboro, Ark.	250
KGBE	Bakersburg, Gaif.	250	KIPA	Hilo, Hawaii	1000	KGBE	Bakersburg, Gaif.	250
KWTC	Barstow, Calif.	250	WMBI	Chicago, Ill.	50000	KWTC	Barstow, Calif.	250
KBS	Bishop, Calif.	250	KFAA	Omaha, Neb.	50000	KBS	Bishop, Calif.	250
XIBO	El Centro, Calif.	250	WBT	Charlotte, N.C.	50000	XIBO	El Centro, Calif.	250
KDAC	Ft. Bragg, Calif.	250	KBND	Bend, Oreg.	5000	KDAC	Ft. Bragg, Calif.	250
KGAF	Los Angeles, Calif.	250	WNAR	Norristown, Pa.	5000	KGAF	Los Angeles, Calif.	250
KRFB	Paso Robles, Calif.	250	WVJP	Caguas, P.R.	250	KRFB	Paso Robles, Calif.	250
KRDG	Redding, Calif.	250	WHIM	Providence, R.I.	10000	KRDG	Redding, Calif.	

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KITO	San Bernardino, Calif.	5000	KOKK	Keokuk, Iowa	1000	GKAK	Gallup, N.Mex.	5000	KNOE	Aztec, N.M.	250
WCCE	Hartford, Conn.	5000	WTTL	Madisonville, Ky.	5000	WEVD	New York, N.Y.	5000	KSIL	Silver City, N.Mex.	250
WTUX	Wilmington, Del.	10000	W00C	Prestonsburg, Ky.	5000	WPOW	New York, N.Y.	5000	WMBO	Auburn, N.Y.	250
WTMG	Ocala, Fla.	5000	KIKS	Sulphur, La.	500	WEBO	Oswego, N.Y.	10000	WENT	Groversville, N.Y.	250
WSCM	Panama City Beach, Florida	5000	KUZM	W. Monroe, La.	10000	WHAZ	Troy, N.Y.	1000	WJOC	Jamesstown, N.Y.	250
WIRK	W. Palm Bch., Fla.	5000	W00B	W. Grand, Mass.	10000	W00B	Portland, Me.	5000	WUSA	Lockport, N.Y.	250
W0EC	Americus, Ga.	10000	W0RC	Worcester, Mass.	5000	WKOV	Wellston, Ohio	5000	WMSA	Albany, N.Y.	250
W0CK	Canton, Ga.	10000	W0RM	Oceanboro, Mich.	5000	KPOJ	Portland, Ore.	5000	WALL	Middletown, N.Y.	250
W0DC	Savannah, Ga.	10000	KRBI	St. Peter, Minn.	10000	WBLF	Bellefonte, Pa.	500	WIRY	Plattsburg, N.Y.	250
KYTE	Pocatello, Idaho	10000	WXXX	Hattiesburg, Miss.	10000	WICU	Erie, Pa.	5000	WJRI	Lenoir, N.C.	250
WIRL	Peoria, Ill.	5000	KFSB	Joplin, Mo.	5000	WLAT	Conway, S.C.	5000	WTSB	Lumberton, N.C.	250
W0BL	Benton, Ky.	10000	KFBF	Great Falls, Mont.	5000	WFCB	Greenville, S.C.	5000	WDXF	Oxford, N.C.	250
KJEF	Jennings, La.	10000	WJLK	Asbury Park, N.J.	250	WAEW	Grossville, Tenn.	10000	W00W	Washington, N.C.	250
W0GR	Houghton Lake, Michigan	5000	W0AN	Camden, N.J.	250	KMRO	Garysburg, Tenn.	1000	W0GN	Waynesville, N.C.	250
WNIL	Niles, Mich.	5000	WVIP	Midvale, N.C.	10000	KML	Camersburg, Pa.	5000	W0AIR	Winston-Salem, N.C.	250
W0IA	Saline, Mich.	5000	WTLB	Utica, N.Y.	1000	KSWA	Graham, Tex.	5000	KGPC	Grafton, N.D.	250
KBMO	Benson, Minn.	5000	W05E	Ashville, N.C.	5000	KINE	Kingsville, Tex.	10000	W0NC	Ashland, Ohio	250
W0LE	Batesville, Miss.	10000	W0TC	Charlotte, N.C.	1000	K00K	Tyler, Tex.	10000	W0UB	Athens, Ohio	250
KALN	Thayer, Mo.	10000	W0TK	Durham, N.C.	1000	W0TM	Danville, Va.	5000	W0ZE	Springfield, Ohio	250
K0VO	Missoula, Mont.	5000	KNOX	Grand Forks, N.Dak.	5000	WESR	Tasley, Va.	10000	W0STY	Steubenville, Ohio	250
K0VL	Orlando, Fla.	5000	WFAH	Alliance, Ohio	10000	KFKF	Bellevue, Wash.	10000	W0HNP	Huntsville, Ala.	250
W0KNE	Keene, N.H.	5000	KNPT	Newport, Ore.	5000	WETZ	New Martinsville, West Virginia	1000	K0CY	Cody, Wyo.	250
KSRC	Soorro, N.M.	10000	W0FD	Ford, Pa.	10000	W0HL	Sheboygan, Wis.	1000	K0OD	Corvallis, Ore.	250
W0GLI	Babylon, N.Y.	1000	W0SA	Ephrata, Pa.	10000	K0VE	Lander, Wyo.	1000	K1HR	Hood River, Ore.	250
W0NBF	Binghamton, N.Y.	5000	W0NAE	Warren, Pa.	5000	K0VE	Lander, Wyo.	1000	K0FR	North Bend, Ore.	250
W0HXY	Hickory, N.C.	5000	W0KID	Kingstree, S.C.	5000	CFGB	Goose Bay, Nfld.	250	W0FBG	Altoona, Pa.	250
W0EYE	Sanford, N.C.	10000	W0DDO	Chattanooga, Tenn.	5000	CFSL	Wayburn, Sask.	250	W0CVI	Connellsville, Pa.	100
K0MP	Bellaire, Ohio	5000	W0DXI	Jackson, Tenn.	5000	CFYK	Yellow Knife, N.W.T.	150	W0SAJ	Grove City, Pa.	250
W0HD	Dayton, Ohio	5000	W0BNT	Onelda, Tenn.	10000	CHAD	Amos, Que.	250	W0HAT	Philadelphla, Pa.	250
K0MA	Pendleton, Ore.	5000	KZIP	Amarillo, Tex.	10000	CHAS	Yarmouth, N.S.	250	W0RAW	Reading, Pa.	250
KLQI	Portland, Ore.	10000	W0RBR	Delias, Tex.	5000	CHRD	Drummondville, Que.	250	W0BRE	Wilkes-Barre, Pa.	250
W0TRN	Tyone, Pa.	10000	K0YLD	Odessa, Tex.	5000	CKAR	Parry Sound, Ont.	250	W0WPA	Williamsport, Pa.	250
W0ICE	Providence, R.I.	5000	K0LBD	San Antonio, Tex.	5000	CKOX	Woodstock, Ont.	250	W0WRI	Aquadilla, P.R.	250
W0F1G	Sumter, S.C.	1000	W0EEL	Fairfax, Va.	5000	W0KUL	Cullman, Ala.	250	W0GRI	Greenville, Tenn.	250
K0TD	Oak Ridge, Tenn.	5000	W0GH	Newport News, Va.	5000	W0JFI	Florence, Ala.	250	W0WHI	Rock Hill, S.C.	250
K0BLT	Big Lake, Tex.	10000	K0ARY	Prosser, Wash.	10000	W0GWC	Selma, Ala.	250	W0WSSJ	Sumter, S.C.	250
K0IYV	Crockett, Tex.	5000	W0IBA	Madison, Wis.	5000	W0FEB	Sylmar, Ala.	250	K0RSD	Rapid City, S.Dak.	250
K0RGV	Weslaco, Tex.	5000			K0KIB	Seward, Alaska	250	W0BAC	Cleveland, Tenn.	250	
K0TRN	Wichita Falls, Tex.	5000	CJSD	Sorel, P.Q.	1000	K0KID	Miami, Ariz.	250	W0KRM	Columbia, Tenn.	250
W0PVA	Wichita Hgts., Va.	5000	CKKK	Kitchener, Ont.	1000	K0KNO	Noogales, Ariz.	250	W0WGS	Waynesville, N.C.	250
W0AGE	Leesburg, Va.	10000	W0AGF	Othman, Ala.	1000	K0KNG	Prescott, Ariz.	250	W0WDM	Memphis, Tenn.	250
W0W0W	Logan, W.Va.	5000	W0WEN	Homewood, Ala.	10000	K0KBT	Batesville, Ark.	250	W0WDT	Winchester, Tenn.	250
W0HIL	Milwaukee, Wis.	10000	K0WNN	Fort Smith, Ark.	5000	K0KBS	Springdale, Ark.	250	W0KWC	Abilene, Tex.	250
W0COW	Sparta, Wis.	10000	K0RLW	Walnut Ridge, Ark.	10000	K0KRS	Springdale, Ark.	250	K0AND	Corsicana, Tex.	250
1300-230.6			K0HSJ	Hemet, Calif.	5000	K0KST	St. Albans, Calif.	250	K0KAF	Fredericksburg, Tex.	250
CBAF	Moncton, N.B.	5000	K0KUD	Oceanside, Calif.	5000	K0KNA	Fresno, Calif.	250	K0DUB	Lubbock, Tex.	250
W0TLS	Tallahassee, Ala.	10000	K0KRA	Rocky Ford, Colo.	10000	K0KATY	San Luis Obispo, Calif.	250	K0KRB	Lufkin, Tex.	250
K0WCB	Searcy, Ark.	10000	W0WATR	Waterbury, Conn.	1000	K0KIST	Santa Barbara, Calif.	250	K0KVM	Monahans, Tex.	250
K0ROP	Brawley, Calif.	1000	W0WGM	Hollywood, Fla.	10000	K0KOMY	Watsonville, Calif.	250	K0PDN	Pampa, Tex.	250
K0YNO	Fresno, Calif.	1000	W0WHIE	Griffin, Ga.	10000	K0KDN	Denver, Colo.	250	K0LEP	Port Arthur, Tex.	250
K0KWK	Pasadena, Calif.	1000	W0WNEA	Toledo, Ga.	10000	K0KSD	Salida, Colo.	250	K0KTL	San Angelo, Tex.	250
K0VOR	Colo. Sprs., Colo.	1000	K0KNAK	Kankakee, Ill.	5000	W0WNC	New Haven, Conn.	250	K0VIC	N. of Victoria, Tex.	250
W0VWZ	New Haven, Conn.	1000	K0KNAQ	Maquoketa, Iowa	5000	W0WDDK	Washington, D.C.	250	W0TWN	St. Johnsburg, Va.	250
W0RKT	Cocoa Beach, Fla.	5000	K0KLWN	Lawrence, Kans.	5000	W0WTAN	Clearwater, Fla.	250	W0STA	Charlotte Amalie, V.I.	250
W0SOL	Tampa, Fla.	5000	W0WRT	Bardstow, Ky.	10000	W0WRD	Daytona Bch., Fla.	250	W0KEY	Covington, Va.	250
W0WMT	Moultrie, Ga.	5000	W0WNG	Wayfield, Ky.	10000	W0WDR	Lake City, Fla.	250	W0HAP	Hopewell, Va.	250
W0WMO	Winder, Ga.	1000	K0KHL	Homer, La.	10000	W0WTS	Marlanna, Fla.	250	W0HJA	Orange, Va.	250
K0WZE	Lawlston, Idaho	5000	W0WICO	Salisbury, Md.	10000	W0WQT	Pan Beach, Fla.	250	K0KPA	Pasco, Wash.	250
W0TAQ	LaGrange, Ind.	5000	W0WARA	Attleboro, Mass.	1000	W0WNSM	Valparaiso-Niceville, Fla.	250	K0KAP	Raymond, Wash.	250
W0TRX	W. Hartford, Ill.	1000	W0WKS	Lawrence, Mo.	5000	W0WGAU	Athens, Ga.	250	K0KME	Wenatche, Wash.	250
W0HNT	Huntington, Ind.	5000	W0WDMJ	Marquette, Mich.	5000	W0WAKE	Atlanta, Ga.	250	W0HAR	Clarksburg, W.Va.	250
W0NFT	Terre Haute, Ind.	5000	W0WGPC	Houston, Miss.	5000	W0WBBQ	Augusta, Ga.	250	W0WEPN	Martinsburg, W.Va.	250
K0GLO	Mason City, Iowa	5000	W0WRJW	Plymouth, Miss.	5000	W0WGA	Cardon, Ga.	250	W0WMDN	Madison, W.Va.	250
W0BLG	Lexington, Ky.	1000	K0KXLW	Clayton, Mo.	10000	W0WKS	Columbus, Ga.	250	W0WVE	Welch, W.Va.	250
W0IBR	Baton Rouge, La.	1000	K0KOLT	Scottsbluff, Neb.	5000	W0WBT	Lyons, Ga.	250	W0WLDY	Ladysmith, Wis.	250
K0LUE	Shreveport, La.	10000	W0WHG	Hornell, N.Y.	5000	W0WTF	Tifton, Ga.	250	W0WRI	Witkauke, Wis.	250
W0WFR	Baltimore, Md.	1000	W0WAGY	Forest City, N.C.	5000	K0KPS	Preston, Idaho	250	W0WFRW	Wis. Rapids, Wis.	250
W0WDA	Gulmry, W.Va.	1000	W0WCGG	Greensboro, N.C.	5000	W0WSDY	Decatur, Ill.	250	K0W0B	Laramie, Wyo.	250
W0WOOD	Grand Rapids, Mich.	5000	K0KDY	Minot, N.Dak.	10000	W0WJPF	Herrin, Ill.	250	K0W0R	Worland, Wyo.	250
W0WRBC	Jackson, Miss.	5000	W0WHOK	Lancaster, Ohio	10000	W0WJDL	Joliet, Ill.	250			
K0MMO	Marshall, Mo.	10000	K0KWDE	Clinton, Okla.	10000	W0WBIW	Bedford, Ind.	250	1350-222.1		
K0KRL	McCook, Neb.	10000	W0WKAP	Allentown, Pa.	10000	W0WTRC	Elkhart, Ind.	250	CH0V	Pembroke, Ont.	1000
K0PTL	Carson City, Nev.	5000	W0WAMP	Pittsburgh, Pa.	5000	W0WLB	Muncie, Ind.	250	CJDC	Dawson Creek, B.C.	1000
W0AAT	Trenton, N.J.	2500	W0WSCR	Seranton, Pa.	1000	K0KROS	Clinton, Iowa	250	CHGB	St. Anne de la Pocatiere, Que.	1000
W0WSC	Fulton, N.Y.	1000	W0WFLS	Bloomingville, N.R.	10000	K0KLLI	Estherville, Iowa	250	K0KLB	Oshawa, Ont.	1000
W0W0L	Goldsboro, N.C.	1000	W0WMS	Columbia, S.C.	1000	K0KKS	Kansas City, Kans.	250	K0KEN	Kentville, N.S.	1000
W0WSDY	Mt. Airy, N.C.	5000	K0KELO	Sloux Falls, S.Dak.	5000	W0WCM	Ashtland, Ky.	250	W0WELB	Elba, Ala.	5000
W0WERE	Cleveland, Ohio	5000	W0WKIN	Kingsport, Tenn.	5000	W0WNB	Murray, Ky.	250	W0WAD	Gadsden, Ala.	5000
W0WVMO	Mt. Vernon, Ohio	500	W0WMSR	Manchester, Tenn.	10000	W0WKEK	Richmond, Ky.	250	K0AAB	Holt Springs, Ark.	1000
K0WME	Tulsa, Okla.	5000	K0KVMZ	Colo. City, Tex.	10000	W0WKEK	Richmond, Ky.	250	W0LKB	Bakersfield, Calif.	1000
K0DOV	Medford, Ore.	5000	K0KXYZ	Houston, Tex.	5000	K0KGAN	Bastrop, La.	250	K0KCC	San Bernardino, Calif.	5000
W0WTL	The Dalles, Ore.	1000	W0WAGY	Forest City, N.C.	5000	K0KRM	Shreveport, La.	250	K0KSR	Santa Rosa, Calif.	1000
W0WCKI	Greer, S.C.	1000	W0WLLY	Richmond, Va.	5000	W0WAG	Gardner, Mass.	250	K0KH	Fueblo, Colo.	5000
K0KOLY	Mobridge, S.Dak.	10000	K0KXRO	Aberdeen, Wash.	10000	W0WNBK	Pittsfield, Mass.	250	W0WPK	Kennewick, Wash.	500
W0WMTN	Morrisstown, Tenn.	5000	K0KXIT	Walla Walla, Wash.	10000	W0WLEW	Bad Axe, Mich.	250	W0WDFP	Dade City, Fla.	1000
W0WNAK	Nashville, Tenn.	5000	W0WQMN	Superior, Wis.	10000	W0WLAN	Grand Rap., Mich.	100	W0WRB	Warner Robins, Ga.	1000
K0VET	Austin, Tex.	1000			W0WCSR	Hillsdale, Mich.	250	K0KRLC	Lewiston, Idaho	5000	
K0TFY	Greenfield, Tex.	1000	CBH	Halifax, N.S.	10000	W0WNT	Manistee, Mich.	250	W0WEEK	Peoria, Ill.	1000
K0KSL	Seattle, Wash.	1000	W0ROS	Scottsboro, Ala.	10000	W0WAG	Menominee, Mich.	250	W0WBD	Salem, Ill.	5000
W0WCLG	Morgantown, W.Va.	1000	K0KMP	Tucson, Ariz.	5000	W0WMBN	Potosky, Mich.	250	K0KRT	Des Moines, Iowa	5000
W0WKL	St. Albans, W.Va.	1000	K0KFA	Los Angeles, Calif.	5000	W0WEXL	Royal Oak, Mich.	250	K0KMAN	Manhattan, Kans.	5000
1310-228.9			W0WARM	Ft. Pierce, Fla.	10000	K0KDLM	Detroit Lakes, Minn.	250	W0WLOU	Louisville, Ky.	5000
CKOY	Ottawa, Ont.	5000	W0WYSE	Lakeland, Fla.	10000	W0WWEV	Evansville, Minn.	250	W0WSMB	New Orleans, La.	5000
CJRH	Richmond Hill, Ont.	5000	W0WBYM	Milton, Fla.	5000	W0WJMB	Brookhaven, Miss.	250	W0WDEA	Ellsworth, Me.	1000
W0HWP	Foley, Ala.	10000	W0WEMN	Tallahassee, Fla.	5000	W0WAML	Laurel, Miss.	250	W0WHH	Howell, Mich.	5000
W0WJM	Marion, Ala.	5000	W0WMLT	Dublin, Ga.	5000	K0KXED	Mexico, Mo.	250	K0KD	Orawville, Minn.	1000
K0KBUZ	Mesa, Ariz.	5000	W0WEAW	Evanston, Ill.	10000	K0KSNM	Salerno, Mo.	250	W0CMP	Pine City, Minn.	1000
K0K0K	Malvern, Ark.	1000	W0WRAM	Newmouth, Ill.	100						

KLFT Golden Meadow, La.	10000	KATZ St. Louis, Mo.	5000	KUSH Cushing, Okla.	10000	KBOR Brownsville, Tex.	1000
KLVI Vivian, La.	5000	KTTN Trenton, Mo.	5000	KASH Eugene, Ore.	1000	KWEL Midland, Tex.	1000
WINX Rockville, Md.	1000	KONG Oneida, N.Y.	10000	WHOL Allentown, Pa.	5000	KCFH Cuero, Tex.	5000
WBOS Brookline, Mass.	5000	WRWL Woodside, N.Y.	5000	WEZN Elizabethtown, Pa.	5000	KHAE McKinney, Tex.	10000
WTYM East Longmeadow, Mass.	5000	WGV Charlotte, N.C.	10000	WFIS Fountain Inn, S.C.	10000	KGT Orange, Tex.	1000
WHR Ann Arbor, Mich.	1000	WIDU Fayetteville, N.C.	10000	WGUS N. Augusta, S.C.	5000	KBCB Centerville, Utah	10000
WTRU Muskegon, Mich.	5000	WFKR Reidsville, N.C.	1000	WHBT Harrison, Tenn.	5000	WBDF Virginia Bch., Va.	10000
WKDL Clarkdale, Miss.	10000	WJSC W. Jefferson, N.C.	10000	WKBJ Milan, Tenn.	10000	WHLL Wheeling, W. Va.	5000
		WBLY Springfield, Ohio	10000	KBBB Berger, Tex.	5000	WCWC Ripon, Wis.	5000

U. S. and Canadian AM Stations by Location

Abbreviations: C.L., call letters; Kc., frequency in kilocycles; N.A., network affiliation—A: American Broadcasting Co., C: Columbia Broadcasting System, Inc.; M: Mutual Broadcasting System; N: National Broadcasting Co., Inc.

Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.
Abbeville, S.C.	KROF	960		Anchorage, Alaska	KBYR	1270		Avon Park, Fla.	WAVP	1390		Bennington, Vt.	WBTN	1370	
Abbeville, S.C.	WABY	1590		Anderson, Ind.	KFQD	730	C-A	Avondale Estates, Ga.	WAVO	1420		Benson, Minn.	KBMO	1290	
Aberdeen, Md.	WAMD	970		Andalusia, Ala.	KENI	550	A-M-N	Axtet, N. Mex.	KNDE	1340		Benton, Ark.	KBBA	690	
Aberdeen, Miss.	WMPA	1240		Anderson, S.C.	WCTA	920		Babylon, N.Y.	WBAB	1440		Benton, Ky.	WCBL	1290	
Aberdeen, S.Dak.	KABR	1220		Anderson, S.C.	WCBC	1470		Bad Axe, Mich.	WGLI	1290		Benton Harbor, Mich.	WVFB	1000	
Aberdeen, Wash.	KSDN	930	A	Andrews, Tex.	WADS	1240		Bainbridge, Ga.	WNGR	930		Berkeley Springs, W. Va.	KRE	1400	
Abilene, Tex.	KWBK	1450		Ann Arbor, Mich.	WANS	1280	M	Baker, Ore.	WAZA	1360		Berlin, N.H.	WCST	1010	
	KXRO	1320	M	Annapolis, Md.	KACT	1360		Bakersfield, Calif.	KBKR	1490		Berryville, Ark.	WKCB	1230	
	KRBC	1470	A		WANN	1190			KAFY	550	M	Berwick, Pa.	WBRK	1280	
	KNIT	1280			WABW	810			KBIS	970		Bessemer, Ala.	WEZB	1450	
	KWKC	1340	M		WNAV	1450	A		KERN	1410	C	Bethesda, Md.	WUST	1120	
Abingdon, Va.	WBBI	1230			WHRV	1600	A		KEE	1230		Bethlehem, Pa.	WGPA	1100	
Ada, Okla.	KADA	1230	A		WRAJ	1440			KMAP	1490		Blanford, Maine	WIDE	1400	M
Adel, Ga.	WAGB	1470			WANA	1490			KLYD	1350		Big Lake, Tex.	KBLT	1290	
Adrian, Mich.	WABJ	1490	A		WDNG	1450	A		KPMK	1560	A	Big Rapids, Mich.	WBRR	1460	
Agua, Guam	KUAM	610	N		WHMA	1390			WSEN	1050	A	Big Spr., Tex.	KBST	1490	A
Aguaadilla, P.R.	WABA	850			KANO	1470			KRBN	1400			KHM	1270	
	WGRF	1340			WATK	900			WBMD	750	N		BYG	1400	M
Ahoskie, N.C.	WRCS	970			WAVL	910			WCAO	600			WLD	1220	
Aiken, S.C.	WAKN	990			KAVR	960			WCBM	680	C		WOWL	1490	M
Akron, Ohio	WAKF	1590	A		WAPL	1570			WFRB	1390			WMI	570	
	WADC	1350	C		WHBY	1230	M		WFTJ	1230			KBMY	1240	M
	WCUE	1150			WHPJ	1470			WFD	1010			730	N	
	WHKK	640	M		WVBD	900	M		WWIN	400	A-M		KOOK	970	C
Alamogordo, N.M.	KALG	1230	M		WVBD	900	M		WVBD	900	A-M		KOYN	910	
Alamosa, Colo.	KRAC	1270			WVBD	900	M		WVBD	900	A-M		KURL	730	
Albany, Ga.	KGIV	1450	M		WVBD	900	M		WVBD	900	A-M		WINR	680	N
	WJAZ	1050			WVBD	900	M		WVBD	900	A-M		WKOP	1390	C
	WJAZ	1050			WVBD	900	M		WVBD	900	A-M		WNB	1290	C
Albany, Ky.	WANY	1390			WVBD	900	M		WVBD	900	A-M		WPI	1370	N
Albany, Minn.	KASM	1150			WVBD	900	M		WVBD	900	A-M		WBRC	960	C
Albany, N.Y.	WABY	1400			WVBD	900	M		WVBD	900	A-M		WCRT	1260	A
	WAFB	1460	M		WVBD	900	M		WVBD	900	A-M		WEDR	1220	
	WPTB	1540	A		WVBD	900	M		WVBD	900	A-M		WATV	900	
	WRDQ	590	C		WVBD	900	M		WVBD	900	A-M		WVGN	610	
Albany, Ore.	KWIL	790	M		WVBD	900	M		WVBD	900	A-M		WDE	850	
	KABY	990			WVBD	900	M		WVBD	900	A-M		WYOK	690	
Albemarle, N.C.	WABZ	1010			WVBD	900	M		WVBD	900	A-M		KSUN	1230	A
	WZKY	1590			WVBD	900	M		WVBD	900	A-M		KIBS	1230	A
Albert Lea, Minn.	KATE	1450	M		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Albertville, Ala.	WAVD	630	A		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Albion, Mich.	WALM	1260			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Albuquerque, N.M.	KABQ	1350			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KDEF	1150			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KGGM	610	C		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KOB	1030	N		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KQD	920	M		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KHBM	1580	A		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	WEAG	1470			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Aleca, Tenn.	WRFS	1050			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alexander City, Ala.	KALB	580	A		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alexandria, La.	KDSE	1410			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KSJL	970	N		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alexandria, Minn.	KXRA	1490	A		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alexandria, Va.	WPIK	730	M		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Algona, Iowa	KLGA	1600			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Aliga, Tex.	KOPY	1070			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Aligan, Mich.	WOWE	1580			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Allentown, Pa.	WHOL	1600			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	WAEB	790			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	WKAP	1320			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	WSAN	1470	C		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alliance, Nebr.	KCOW	1400			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alliance, Ohio	WFAH	1310			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alma, Ga.	WCOB	1400			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alma, Mich.	WFCY	1280			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alpena Township, Mich.	WATZ	1450			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alpine, Tex.	KVLF	1240	M		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alton, Ill.	WOKZ	1570			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alton, Man.	CFAM	1290			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Altoona, Pa.	WFBI	1340	N		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	WRTA	1240	A		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	WYAM	1430	C		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alturas, Calif.	KCND	570			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Altus, Okla.	KWHW	1450			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Alva, Okla.	KALV	1430			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Amarillo, Tex.	KFBI	1010	M		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KGNC	710	N		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KIXZ	940	C		WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KRAY	1360			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	KZIP	1310			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Ambridge, Pa.	WBEA	1460			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Ameritus, Ga.	WDEC	1290			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Ames, Iowa	WOFI	1430			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
	WOFI	640			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Amherst, N.S.	CKDH	1400			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Amite, La.	WABL	1570			WVBD	900	M		WVBD	900	A-M		KWGS	1380	
Amory, Miss.	WAMY	1580			WVBD	900	M		WVBD	900					

Location	C.L. Ke. N.A.	Location	C.L. Ke. N.A.	Location	C.L. Ke. N.A.	Location	C.L. Ke. N.A.
Brampton, Ont.	CHIC 1090	Cartersville, Ga.	WBHF 1450 M	Clanton, Ala.	WSAI 1360	Cornelia, Ga.	WCRR 1330
Brandon, Man.	CKX 1150	Carthage, Ill.	WCAZ 990	Claremore, Okla.	WKLF 980	Corner Brook, Nfld.	WCOR 1450
Branson, Mo.	KBHM 1220	Carthage, Mo.	KDMO 1490	Claremont, N.H.	KWPR 1270	Corning, Ark.	CBY 790 P
Brighton, Vt.	WTSB 1450	Carthage, Tenn.	WRKM 1350	Clarksburg, W.Va.	WTVS 1230	Corning, N.Y.	KCCB 1260
Brawley, Calif.	KROP 1300 A	Carthage, Tex.	KGAS 1590	Clarksburg, W.Va.	WBOY 1400 N	Corning, N.Y.	WCBA 1350
Breckenridge, Minn.	KBMW 1450	Carthagesville, Mo.	KCRV 1370	Clarksburg, W.Va.	WBA 1340 M	Corning, N.Y.	WDL 1450 A
Breckenridge, Tex.	KSTB 1430	Casa Grande, Ariz.	KPFN 1260	Clarksdale, Miss.	WRD 750	Corwall, Ont.	CISS 1220
Bremen, Ga.	WBFB 1440	Casper, Wyo.	KTWO 1470 C	Clarksdale, Miss.	WROX 1450 M	Corona, Calif.	KBUC 1370
Bremerton, Wash.	KBRO 1490		KATI 1400	Clarksdale, Miss.	WKDL 1600	Corpus Christi, Tex.	
Brenham, Tex.	KWHI 1280		KVQD 1230 A-M	Clarksville, Ark.	KLYR 1360		KCTA 1030 M
Brevard, N.C.	WPNF 1240 M-N	Cayce, S.C.	WCAY 620	Clarksville, Tenn.	WJZM 1400 M		KCCT 1150
Brewton, Ala.	WEBJ 1240 M	Cedar City, Utah	KSUB 500 C	Clarksville, Tenn.	WDXN 540		KEYS 1440
Brideport, Conn.	WICC 600 M	Cedar Rapids, Iowa	KCRG 1600 M	Clarksville, Tenn.	KCAR 1350		KRYS 1360 N
	WNAB 1450 A		KPIG 1450	Claxton, Ga.	WLA 1470		KSLK 1230 A-C
	WNSN 1240		WNT 600 C	Claxton, Ga.	KXLW 1320		KUNO 1400
Bridgeton, N.J.	CKSN 1240	Cedartown, Ga.	WGAA 850	Claxton, Ga.	KFUO 850		KRTO 1370
Bridgewater, N.S.	KBUR 800	Center, Tex.	KDET 930	Clayton, N.Mex.	KLMX 1450		KRNC 1340
Brighton, Colo.	KHIL 800	Centerville, Iowa	KCDG 1400	Clearfield, Pa.	WCPA 900		KVFC 740
Bristol, Conn.	WBIS 1440	Centerville, Tenn.	WHLP 1570	Clearwater, Fla.	WTAN 1340		WKRT 920
Bristol, Tenn.	WOPI 1490 N	Centerville, Utah	KBBC 1600	Cleburne, Tex.	KCLE 1120		WOAC 550
Bristol, Va.	WCVB 690 A	Central City, Ky.	WNES 1600	Cleveland, Ga.	WRWH 1580		KFLY 1240
	WFHG 980 M		WNTA 1380	Cleveland, Miss.	KLQ 1340		KFD 1340
Broekton, Mass.	WBET 1450	Centraira, Ill.	WCNT 1210	Cleveland, Ohio	WDSK 1410		WTNS 1560
Brookville, Ont.	WBET 1450	Centraira & Chehalis, Wash.	KELA 1470		KYW 1100		
Broken Bow, Nebr.	KN1 1280	Centreville, Miss.	WGLC 1580		WDDK 1260 M		
Brookfield, Mo.	KGHM 1470	Chadron, Nebr.	KCSR 1450		WERE 1300		
Brookhaven, Miss.	WCHJ 1470	Chambersburg, Pa.	WCHA 800		WGAR 1220 C		
	WJMB 1340 M		WHK 1420		WHK 1420		
Brookings, Oreg.	KURY 910	Champaign, Ill.	WCBG 1590		WABQ 1450		
Brookings, S.Dak.	KBRK 1430	Chanute, Kans.	KDWS 1440		WJW 950 N		
Brookline, Mass.	WBOS 450	Chapel Hill, N.C.	WCHL 1360	Cleveland, Tenn.	WBAC 1340 M		
Brooklyn, N.Y.	WBFB 1330	Charleroi, Pa.	WESA 940		WCLE 1570		
Brooksville, Fla.	WJJB 1450	Charles City, Iowa	KCHA 1580	Cleveland, Tex.	KVLB 1410		
Brownfield, Tex.	KTFY 1300	Charleston, Ill.	WEIC 1270	Cleve. Hgts., Ohio	WJMO 1490 A		
Brownsville, Tex.	KBOR 1600 A	Charleston, Mo.	KCHR 1350	Clifton, Ariz.	KCLF 1400 A		
Brownwood, Tex.	KBWD 1380 M	Charleston, S.C.	WCSC 1390 C	Clifton Forge, Va.	WCFV 1230		
	KEAN 1240		WKE 1340 A-M	Clifton, Ill.	WHW 1520		
	WGIG 1440 A		WQSN 1450	Clinton, Iowa	KRDS 1340 M		
	WCGD 1490		WTMA 1250 N	Clinton, Mo.	KDKD 1280		
Brunswick, Maine	KORA 1240 M	Charleston, W.Va.	WCVA 1400	Clinton, N.C.	WRRZ 880 A		
Bryan, Tex.	WTAW 1150		WCHS 580 C	Clinton, Okla.	KWOE 1320		
	WBEN 930 C		WHNS 1490 A	Clinton, S.C.	WPCC 1400		
	WBNY 1400		WKAZ 950 N	Cloquet, Minn.	WKLK 1230		
	WEBR 970 M		WTL 1240 M	Clovis, N.Mex.	KLW 1240		
	WGR 550 A	Charlotte, Mich.	WGER 1390	Coachella, Calif.	KCHV 970		
	WWS 1520 N	Charlotte, N.C.	WBT 1110 C	Coalinga, Calif.	KBMX 1470		
	WUOL 1120 A		WAYS 610 A	Coatesville, Pa.	WCOJ 1420		
Buffalo, Wyo.	KBBS 1450		WGIV 1600	Cocoa, Fla.	WKKO 860		
Burford, Ga.	WDMF 1460		WKTC 1240	Cocoa Beach, Fla.	WEZY 1480		
Burbank, Calif.	KBLA 1490		WIST 930 M	Cody, Wyo.	KOD 1400 A		
Burley, Idaho	KBAR 1230 A-M		WSDC 1300 N	Coeur d'Alene, Ida.	KVNI 1240 M		
Burlington, Iowa	KBUR 1490 A		WWDK 1480		KZIN 1050		
Burlington, N.C.	WFNS 1150	Charlotte Amalie, V.I.	WSTA 1340	Coffeyville, Kans.	KGGF 690 A		
	WCAX 620 C	Charlottesville, Va.	WCHV 1260 A	Colby, Kans.	KXXX 790		
	WDOT 1230 A		WELK 1010	Coldwater, Mich.	WTVB 1890		
	WJQY 1230 A		WLN 1400 M	Colman, Tex.	KSTA 1000		
Burns, Oreg.	WPRN 1220	Charlottesville, P.E.I.	CFY 630	Colfax, Wash.	KCL 1450		
Butler, Ala.	WBUT 1050	Chase City, Va.	WNEK 980	College Park, Ga.	WCPC 1570		
Butler, Pa.	WFBR 680	Chatham, Ont.	CFCO 630	Colonial Heights, Va.	WPVA 1290		
Butte, Mont.	KBOW 1490 C	Chattanooga, Tenn.	WOGA 1450 M	Colorado City, Tex.	KVMC 1320		
	KOPR 550 M		WAPD 1150 A	Colo. Sprgs., Colo.	KRBD 1240		
	KXLF 1370 N		WDEF 1370 N		KVOR 1000 C		
	WATT 1240 M		WDDO 1310 C		KSSS 740		
Cadillac, Mich.	WNEL 1450	Chesapeake, Va.	WDXB 1490		KYSN 1460 M		
Caguas, P.R.	WRDL 1450	Chesapeake, Wash.	WNT 1260	Columbia, Ky.	WAIN 1270		
	WRF 1450	Chesapeake, Wash.	KITI 1420	Columbia, Miss.	WCJU 1450 M		
	WRF 1450	Chelan, Wash.	KOZI 1220	Columbia, Mo.	KFRU 1400 A		
Cairo, Ga.	WGRA 790	Cheraw, S.C.	WCRE 1420	Columbia, Pa.	KBIA 1580		
Cairo, Ill.	WKRO 1490	Cherokee, Iowa	KCHE 1440	Columbia, S.C.	WCOS 1400 A		
Calais, Maine	WCID 1230	Chester, Pa.	WFE 990		WIS 560 N		
Caldwell, Idaho	WQDY 1490	Chester, Pa.	WVCH 740		WMSC 1320 C		
Calera, Ala.	WBVE 1370	Chester, S.C.	WGOD 1490		WNOK 1230		
Calixco, Calif.	KICG 1490	Cheyenne, Wyo.	KFCB 1240 A		WNOK 1230		
Calgary, Alta.	CFCA 960		KCHF 1590		WOIC 1470		
	CFNC 1060		KYVO 1370 M	Columbia, Tenn.	WJGD 1280		
	CKXL 1140		WAAF 950		WJW 1340		
	WCGA 900	Chicago, Ill.	WBBM 820	Columbus, Ga.	WDAK 540 N		
Camas, Wash.	KPVA 1480		WBFB 1000		WRBL 1420 C		
Cambridge, Md.	WCEN 1240		WCFL 1000		WGBA 1270 M		
Cambridge, Mass.	WTAD 740		WCRW 1240		WCLS 1580		
Cambridge, Ohio	WFB 1270		WEDC 1240		WOKS 1340		
Camden, Ark.	KAMD 910		WGES 1390	Columbus, Ind.	WCSI 1010		
Camden, N.J.	WCAN 1310		WGN 720 M	Columbus, Miss.	WACR 1050		
	WKDN 800		WJJD 1160		WCB 550 M		
	WACA 1590		WLS 890 A	Columbus, Nebr.	KJSK 900		
Camden, Tenn.	WFVL 1220		WMAQ 670 N	Columbus, Ohio	WBNS 1460 C		
Campan, Tex.	KML 1330		WNB1 1110		WCOL 1230 A		
Campan, Tex.	WCLB 1220		WNSB 1240		WNNI 920		
Campbell, Ohio	WHOT 1570		WOBX 1490		WQSU 820		
Campbellsville, Ky.	WTCO 1450		WOC 1290		WTWN 510		
Campbellton, N.B.	CFNB 950		WACE 730		WKVO 1580		
Camrose, Alta.	CCKC 1230		WCBJ 1580	Calville, Wash.	KCVL 1270		
Canon City, Colo.	KRLN 1400 M		CJMT 1420	Commerce, Ga.	WJJC 1270		
Canonburg, Pa.	WCNG 540		KCTA 1510	Concord, N.H.	WKXL 1450		
Canton, Ga.	WCAN 1440		KCHI 1010	Concord, N.C.	WEGD 1410		
Canton, Ill.	WBYS 1560		WCHL 1350	Concordia, Kans.	KNGK 1390		
Canton, Miss.	WDOB 1370		CHWIK 1270		KFRM 550 A		
Canton, N.C.	WWIT 970		WBGC 1240	Connellsville, Pa.	WCVI 1340		
Canton, Ohio	WAND 900		WAXX 1150	Connellsville, Ind.	WCNB 1580		
	WCMW 1060		WBGR 1260	Conroe, Tex.	KMCO 900		
	WHBC 1480 A		WVIV 1040	Conroy, Ark.	KCON 1230		
Cape Girardeau, Mo.	KFVS 960		WNCH 260	Conway, N.H.	WBNC 1050		
	KGMO 1220		WVFC 1230	Conway, S.C.	WLAT 1350 M		
Carbondale, Ill.	WCIL 1020		WHFC 1450	Cooksville, Tenn.	WLB 1400 C		
Carbondale, Pa.	WCIL 1440		WCKY 1530	Coaldale, Ariz.	KCKY 1150 C		
Caribou, Maine	WFST 600		WCIN 1480	Cos Bay, Oreg.	KOOS 1230 M		
Carlisle, Pa.	WHYL 960		WCPD 1230		KYNG 1420		
Carlsbad, N.Mex.	KAVE 1240 C		WKRC 550 C	Copper Hill, Tenn.	KWRO 1450		
	KPBM 740		WLV 700 N-A	Couquille, Oreg.	WVCG 1070		
	KTEE 1410			Coral Gables, Fla.	WDTT 680 M		
Carmel, Calif.	WROY 1460			Corbin, Ky.	WJHM 1490 M		
Carmel, Ill.	WRAY 1460			Cordova, Alaska	KLAM 1450		
Carrizo Springs, Tex.	KBEN 1450			Corinth, Miss.	WCMA 1230		
Carroll, Iowa	KCMI 1380						
Carrollton, Ala.	WRAG 580						
Carrollton, Ga.	WLBB 1100						
Carson City, Nev.	KPTL 1300						

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Del Rio, Tex.	KDLK 1230	Elba, Ala.	WELB 1350	Fayetteville, Tenn.	WEKR 1240 M	Gaffney, S.C.	WFGN 1570
Delta, Colo.	KDTA 1400	Elberton, Ga.	WSGC 1410 A	Fergus Falls, Minn.	WEKR 1240 M	Gainesville, Fla.	WDFW 980
Deming, N.Mex.	KUTS 1230	El Cajon, Calif.	KDEO 910 A	Fernandina Beach, Fla.	KOTE 1250 M		WGGG 1230 A
Demopolis, Ala.	WXAL 1400 M	El Campo, Tex.	KULP 1390				WGGG 1230 A
Denham Sprngs., La.	WLBI 1220	El Centro, Calif.	KXO 1230 M			Gainesville, Ga.	WGGG 1230 A
Denison, Iowa	KDSN 1580		KAMP 1430				WGGG 1230 A
Denison, Tex.	KDSX 950	El Dorado, Ark.	KDMS 1290	Ferriday, La.	WPAP 1570		WGGG 1230 A
Denton, Tex.	KDNT 1440		KELD 1400 A	Festus, Mo.	KXEN 1010	Gainesville, Tex.	WGAF 1580
Denver, Colo.	KDNC 1340	Eldorado, Kans.	KBTO 1360	Findlay, Ohio	WFN 1310	Galax, Va.	WBOB 1360 M
	KFML 1390	Elgin, Ill.	WRMN 1410	Fisher, W.Va.	WEIM 590 A	Galesburg, Ill.	WGIL 1400
	KHOW 630 A	Elizabeth City, N.C.	WCNC 1210	Fitchburg, Mass.	WFGM 960		WGIL 1400
	KIMN 950 M		WGA1 560	Fitzgerald, Ga.	WBHB 1240 M	Gallatin, Tenn.	WHIN 1410
	KLIR 990	Elizabethton, Tenn.	WBEJ 1240	Flagstaff, Ariz.	KCLS 600 N	Gallipolis, Ohio	WJEH 990
	KLZ 580 C	Elizabethtown, N.Y.	WIEL 1400		KVNA 690 A	Gallup, N. Mex.	KGAK 1330 A
	KICN 710				KEOS 1290	Galt, Ont.	CKGR 1110
	KDA 850 N	Elizabethtown, Ky.	WBLA 1450 M	Flat River, Mo.	KFM 1240 M	Galveston, Tex.	KILE 1400
	KPof 910	Elizabethtown, Pa.	WEZN 1240 A	Flin Flon, Man.	CFAR 590		KGCB 1540
	KFSC 1220	Elk City, Okla.	KBEB 1600 A	Flint, Mich.	WDFD 910 N	Gander, Nfld.	KNEO 1050
	KTLN 1280	Elkhart, Ind.	WTRC 1340 N		WTRX 1320 A	Garden City, Kans.	KNEO 1050
De Queen, Ark.	KDQN 1390		WCMR 1270		WAMM 1430 A		KIUL 1240 M
De Ridder, La.	KDLA 1010	Elkin, N.C.	WIFM 1540		WMRP 1570	Gardner, Mass.	WGAW 1340
Des Moines, Iowa	KCBC 1390 A	Elkins, W.Va.	WONE 1240		WKMF 1470	Gary, Ind.	WGCA 1270
	KIDA 940 A	Elko, Nev.	KELK 1240 M		WTAC 600 A		WGRY 1370
	KRAT 1350	Ellensburg, Wash.	KXL 1240	Flomaton, Ala.	WTBC 990	Gaston, N.C.	WGNB 1450 A
	KSO 1480	Ellsworth, Me.	WDEA 1350	Florence, Ala.	WOL 1480 M		WLTC 1370
	KWKY 1150 M	Elmira, N.Y.	WELM 1400 A-C	Florence, S.C.	WJMX 920 A	Gate City, Va.	WATC 900
	WHO 1040 N	Elmira Helghts-Horseheads, N.Y.	WENY 1230 N		WOLS 1230	Gaylord, Mich.	WATC 900
Detroit, Mich.	WCAR 1130			Floydada, Tex.	KFLD 900	Geneva, Ala.	WGEA 1150
	WJBK 1500			Foley, Ala.	WHPE 1310	Geneva, N.Y.	WGVA 1240 A
	WJLB 1400			Fond du Lac, Wis.	KFIZ 1450 M	Georgetown, Del.	WJWL 900
	WJR 760			Forbes, Ark.	KBJT 1570	Georgetown, Ky.	WGOR 1580
	WJW 950 N			Forde, Ark.	KFD 1400 M	Georgetown, S.C.	WGTN 1400 M
	WXYZ 1270 A			Forest, Miss.	KMDD 1600	Gettysburg, Pa.	WGAT 1050
Detroit Lakes, Minn.	KDLM 1340			Forest City, N.C.	WBBO 780	Gillette, Wyo.	KINL 1490
					WAGY 1320	Gilroy, Calif.	KPER 1290
Devils Lake, N.Dak.	KDLR 1240 M			Forest Grove, Oreg.	KGGG 1570	Gladewater, Tex.	KSIJ 1430
	KK 1580			Forrest City, Ark.	KJKK 950	Glasgow, Ky.	WKAY 1490
	KSPL 1580			Ft. Bragg, Calif.	KDAC 1230	Glasgow, Mont.	KLTZ 1240
Dexter, Mo.	KDIX 1230			Ft. Collins, Colo.	KCOL 1410	Glendale, Ariz.	KRUX 1360
Diboll, Tex.	KDIX 1230			Ft. Dodge, Iowa	KWMT 540 M	Glendale, Calif.	WGL 1050
Dickinson, N.Dak.	WDKN 1260			Ft. Frances, Ont.	CFOB 800	Glen Dale, Mont.	KXGN 1400
Dickson, Tenn.	KDBM 800			Ft. Knox, Ky.	WSAC 1470	Glen Falls, N.Y.	WWSG 1450 A
Dillon, Mont.	KDBM 800			Ft. Lauderdale, Fla.	WFTL 1400	Glenwood Sprngs., Colo.	
Dillon, S.C.	WDSC 800 A				WVIL 1580		KGLN 980 M
Dinuba, Calif.	KRDU 1240			Ft. Lupton, Colo.	KHIL 800	Globe, Ariz.	KWJB 1240 A
Dodge City, Kans.	KGND 1370 M			Ft. Madison, Iowa	KXGI 1360	Gloverster, Va.	WDDY 1420
Dothan, Ala.	WDIG 1450 M			Ft. Morgan, Colo.	KMD 1400 M	Gloversville-Johnston	WENT 1340 C
	WOOF 560			Ft. Myers, Fla.	WINK 1240 C		WENT 1340 C
Douglas, Ariz.	KAWT 1450 M				WMYR 1410	Golden, Colo.	KXXI 1250
	KAPR 930			Ft. Payne, Ala.	WFPA 1400	Golden Meadow, La.	KLFT 1600
Douglas, Ga.	WDNG 860				WZOB 1250	Golden Valley, Minn.	
Douglas, Wyo.	KWIV 1050			Ft. Pierce, Fla.	WARN 1330		KEVE 1440 M
Dover, Del.	WKDN 410				WIRA 1490		WFCM 730
	WKEN 1600			Ft. Scott, Idaho	KMD 1600		WGR 150 A
Dover, N.H.	WTSN 1270			Ft. Smith, Ark.	KFPW 1230 C		WGR 150 A
Dover, Ohio	WJER 1450				KFS 950 A		WGR 150 A
Doylestown, Pa.	WBUX 1570				KTC 1410 M		WGR 150 A
Drumheller, Alta.	CJDV 910				KWHN 1320		WGR 150 A
Drummondville, Que.					KWST 1160		WGR 150 A
	CHRD 1340				WFTW 950		WGR 150 A
	WMLT 1330				WGL 1250 A		WGR 150 A
Dubin, Ga.	WXLI 1440				WOW 1190		WGR 150 A
Du Bois, Pa.	WCED 1420 C				WANE 1450 C		WGR 150 A
Dubuque, Iowa	KDTH 1370 A				WKJG 1380 N		WGR 150 A
	WDBQ 1490 M				KKPR 580		WGR 150 A
Duluth, Minn.	KOAL 610 C				KJG 870		WGR 150 A
	WBCB 560				KUL 1540		WGR 150 A
	WBC 1080				KFKJ 1270		WGR 150 A
Dumas, Tex.	KDD 800				WBAP 570 A		WGR 150 A
Duncan, Okla.	KRHD 1350 M				WBP 820 N		WGR 150 A
Dundalk, Md.	WAYE 860				KXDL 1360		WGR 150 A
	WBBB 1360				WFA 430		WGR 150 A
Dundee, N.Y.	WFLR 1570				WFIS 1800		WGR 150 A
Dunkirk, N.Y.	WDD 1410				WKOX 1190		WGR 150 A
Dunn, N.C.	WKCB 780				WIL 1570		WGR 150 A
Du Quoin, Ill.	WQON 1580				WFKY 1490 M		WGR 150 A
Durango, Colo.	KIUP 930				WFRK 1220		WGR 150 A
	KDGO 1240				WFRK 1220		WGR 150 A
	KSF 750				WFRK 1220		WGR 150 A
Durant, Okla.	WSFC 820 C				WFRK 1220		WGR 150 A
Durham, N.C.	WSRC 1410				WFRK 1220		WGR 150 A
	WRSB 1490				WFRK 1220		WGR 150 A
	WTK 1310				WFRK 1220		WGR 150 A
Dyersburg, Tenn.	WDSG 1450				WFRK 1220		WGR 150 A
	WTRD 1330				WFRK 1220		WGR 150 A
Eagle Pass, Tex.	KEPS 1270				WFRK 1220		WGR 150 A
Easley, S.C.	WELP 1360				WFRK 1220		WGR 150 A
E. Grand Forks, Minn.					WFRK 1220		WGR 150 A
	KRAD 1590				WFRK 1220		WGR 150 A
Eastland, Tex.	KERC 1380				WFRK 1220		WGR 150 A
E. Lansing, Mich.	WKAR 870				WFRK 1220		WGR 150 A
E. Liverpool, Ohio	WOHI 1490 A				WFRK 1220		WGR 150 A
East Longmeadow, Mass.					WFRK 1220		WGR 150 A
	WTYM 1600				WFRK 1220		WGR 150 A
E. Point, Ga.	WTJH 1260				WFRK 1220		WGR 150 A
E. St. Louis, Ill.	WAMY 1490				WFRK 1220		WGR 150 A
Easton, Pa.	WEST 1400				WFRK 1220		WGR 150 A
	WEST 1400				WFRK 1220		WGR 150 A
Eatontown, N.J.	WHTG 1410				WFRK 1220		WGR 150 A
Eau Claire, Wis.	WEAQ 790 N				WFRK 1220		WGR 150 A
	WBIZ 1400 M				WFRK 1220		WGR 150 A
	WECL 1050				WFRK 1220		WGR 150 A
Eau Gallie, Fla.	WNEG 920				WFRK 1220		WGR 150 A
Easton, N.C.	WCQJ 1260				WFRK 1220		WGR 150 A
Edinburg, Tex.	KURV 930				WFRK 1220		WGR 150 A
Edmonds, Wash.	KDGN 630				WFRK 1220		WGR 150 A
Edmonton, Alta.	CBX 1010				WFRK 1220		WGR 150 A
	CBXA 740				WFRK 1220		WGR 150 A
	CFRN 1260				WFRK 1220		WGR 150 A
	CHED 1080				WFRK 1220		WGR 150 A
	CHFA 680				WFRK 1220		WGR 150 A
	CJCA 930				WFRK 1220		WGR 150 A
	CKUA 580				WFRK 1220		WGR 150 A
Edmundston, N.C.	CIEM 570				WFRK 1220		WGR 150 A
Effingham, Ill.	WCRA 1090				WFRK 1220		WGR 150 A

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Lewistown, Mont.	WLAM 1470 A	Macon, Miss.	WMBC 1400	Medicine Hat, Alta.	CHAT 1270	Montgomery, Ala.	WBAM 740
Lewistown, Pa.	WKXO 1230 M	Madera, Calif.	KHOT 1250	Melbourne, Fla.	WMWB 1240 M	WCOV 1170 C	
Lexington, Ky.	WKVA 920 M	Madison, Fla.	WMAF 1230	Memphis, Tenn.	WHBQ 560 M	WAPX 1600 A	
	WMLP 630 N	Madison, Ga.	WYD 1250		WHCR 1430	WHHY 1440 N	
	WBLG 1300 A	Madison, Ind.	WORX 1270		WHD 780 N	WHGY 800	
	WVWK 590 M	Madison, Wis.	WHA 970		WDIA 1070	WRMA 950	
Lexington, Mo.	KLEX 1570		WIBA 1310 N		WMPS 680	WMOB 1340 M	
Lexington, Nebr.	KRVN 1010		WISW 1480 A-M		WHHM 1340 A	WNON 1340 M	
Lexington, N.C.	WBUY 1440	Madison, Tenn.	WKOW 1070 C		WLOK 1480	KHBM 1430	
Lexington, Tenn.	WDXL 1490	Madisonville, Ky.	WENO 1430		WREC 600 C	WFLW 1360	
Lexington, Va.	WEL 450 N		WFMW 730		KWAM 990	Monticello, Ky.	WCLM 1430
Lexington Pk., Md.	WPTX 920 M	Magee, Miss.	WTTL 1310	Mena, Ark.	WAGN 1450	Monticello, Va.	CKFB 1290 A
Libby, Mont.	KOLL 1230 M	Magnolia, Ark.	KVMA 630 M	Menominee, Mich.	WMNE 1340 A	Montpelier-Barre, Vt.	CBK 690
Liberal, Kans.	KSCB 1270	Malden, Mo.	KTCB 1470	Menomonee, Wis.	WMNE 1340 A	Montreal, Que.	CSFJ 1240 A
Liberty, N.Y.	WVOS 1240	Malden, N.Y.	WICY 1490 M	Merced, Calif.	KYOS 1480 M		CBM 940 N
Lihue, Hawaii	KTOH 1490	Malvern, Ark.	KBOK 1310		KWIP 1580		CFCC 600 A
Lima, Ohio	WIMA 1150 A	Manassas, Va.	WPRW 1460	Meriden, Conn.	WMMW 1470		CJAD 800
Lincoln, Ill.	WPRC 1370	Manchester, Conn.	WINF 1230	Meridian, Miss.	WCOO 910 C		CJMS 1280
Lincoln, Nebr.	KFLN 1400 A	Manchester, Ga.	WFDR 1370		WDLA 1330		CKAC 730 C
	KLMS 1480	Manchester, Ky.	WVXL 1450		WDOX 1270		CKCB 580
	WLON 1050	Manchester, N.H.	WFEA 1370		WKOK 1450 A		WPEE 1550
Lindsay, Ont.	CKLY 910		WGR 610 C	Mesa, Ariz.	WBIZ 1390		WHIP 1350
Linton, Ind.	WBTO 1600		WKR 1240	Mesa, Ariz.	KWIC 1310		WHIP 1350
Litchfield, Ill.	WSMI 1540	Manchester, Tenn.	WMSR 1320	Metropolis, Ill.	WNOK 920		WHIP 1350
Litchfield, Minn.	KLFD 1410	Manhattan, Kans.	KSAC 580	Mexia, Tex.	KBUS 1950		WHIP 1350
Little Falls, Minn.	KLTF 960		KMAN 1350	Mexico, Mo.	WXED 1340 M		WHIP 1350
Little Falls, N.Y.	WLF 1230	Manila, P.I.	DZPI 1800 M-C	Mexico, Pa.	WJEU 1220		WHIP 1350
Littlefield, Tex.	KUDD 1490		DR 71 N	Miami, Ariz.	WKIC 1340		WHIP 1350
Little Rock, Ark.	KARK 920 N	Manitowish, Wis.	WMTE 1340	Miami, Fla.	WGBS 710 C		WHIP 1350
	KAJI 1250 M	Manitou Springs, Colo.	CMNS 1490		WCKR 910 N		WHIP 1350
	KOKA 1010 A	Manitowoc, Wis.	WCUB 980		WFFC 1220		WHIP 1350
	KLKY 1440		WOMT 1240 M		WAME 1260		WHIP 1350
	KTHS 1090 C	Mankato, Minn.	KYSM 1230 N		WMI 1140		WHIP 1350
	KULC 1050		KTSD 1420 A		WQAM 560		WHIP 1350
	KUDJ 1510	Manning, S.C.	WYMB 1410		WINZ 940		WHIP 1350
	WNER 1250	Mansfield, La.	KDBC 1360	Miami, Okla.	KLGC 910		WHIP 1350
	KPRK 1340 M	Mansfield, Ohio	WMAN 1400 A	Miami Beach, Fla.	WMET 1490		WHIP 1350
	WLIV 920		WCLW 1570		WKAT 1360 M-A		WHIP 1350
	KETX 1440	Maquoketa, Iowa	KMAQ 1320		WIMS 800		WHIP 1350
	KLBS 1220	Marlanna, Fla.	WTYS 1340 M	Melchigay City, Ind.	WMBN 1420		WHIP 1350
	CKSA 1150		WFOI 980	Middlesboro, Ky.	WJBO 560		WHIP 1350
Lloydminster, Alta.	WBFZ 1230 M	Marietta, Ga.	WFON 1230	Middletown, Conn.	WCNX 1150		WHIP 1350
Lock Haven, Pa.	WUSJ 1430		WBIE 1050	Middletown, N.Y.	WALL 1340		WHIP 1350
Lockport, N.Y.	KVCR 1570	Marietta, Ohio	WMOA 1490 M	Middletown, Ohio	WPFB 570		WHIP 1350
Lodi, Calif.	KVNU 610 M	Marine City, Mich.	WDOG 1590	Midland, Mich.	WMDN 1490		WHIP 1350
Logan, Utah	KLGN 1390	Marinette, Wis.	WMAW 570 N	Midland, Tex.	CKRP 1230		WHIP 1350
Logan, W.Va.	WLOG 1230 M	Marion, Ala.	WJAM 1310		CKMS 550 A		WHIP 1350
Logansport, Ind.	WVOW 1290	Marion, Ill.	WGH 1150	Milan, Tenn.	KWEL 1600		WHIP 1350
Lompoc, Calif.	KNEZ 960 M	Marion, Ind.	WMRI 860	Miles City, Mont.	KATL 1340 M		WHIP 1350
London, Ky.	WFL 1400	Marion, N.C.	WBRR 1250	Milford, Del.	WKSB 930		WHIP 1350
London, Ont.	CFPL 980	Marion, Ohio	WMRN 1490 A	Milford, Mass.	WMRC 1490 M		WHIP 1350
	CKSL 1290	Marion, S.C.	WATP 1430	Milledgeville, Ga.	WMVG 1450		WHIP 1350
Long Beach, Calif.	KFOX 1280	Marion, Va.	WMEV 1010 A	Millen, Ga.	WWSR 1570		WHIP 1350
	KGER 1390	Marked Tree, Ark.	KPCA 1580	Millington, Tenn.	WHE 1220		WHIP 1350
Longmont, Colo.	KLMO 1050	Marksville, La.	KAPB 1370	Millville, N.J.	WMYB 1440		WHIP 1350
Longview, Tex.	KFRD 1370 A	Marlborough, Mass.	WSRO 470	Milton, Fla.	WBYE 1330 M		WHIP 1350
	KLUE 1280	Marlin, Tex.	KNLW 1010		WSRA 1490		WHIP 1350
Longview, Wash.	KEDO 1400 A	Marquette, Mich.	WDNJ 1320 M	Milton, Pa.	WMLP 1570		WHIP 1350
	KFB 1270	Marshall, Minn.	KMHL 1400 A	Milwaukee, Wis.	WEMP 1250		WHIP 1350
Lorain, Ohio	WWJZ 1380	Marshall, Mo.	KMMO 1300		WFOX 860 M		WHIP 1350
Loris, S.C.	WLSC 1570	Marshall, N.C.	WMMH 1460		WISN 1150		WHIP 1350
Los Alamitos, N.Mex.	KRSN 1490 A	Marshall, Tex.	KMHT 1450		WAIL 1290		WHIP 1350
Los Angeles, Calif.	KABC 790 A		KDD 1410		WOKY 920		WHIP 1350
	KFI 640 N	Marshalltown, Iowa	KJFB 1230		WTMJ 620 N		WHIP 1350
	KHJ 930 M	Marshfield, Wis.	WDLB 1450	Minden, La.	KASO 1240		WHIP 1350
	KFSB 1150	Martin, Tenn.	WCNT 1410	Minden, La.	KORC 1140		WHIP 1350
	KFB 980	Martinsburg, W.Va.	WEPM 1340	Mineola, N.Y.	WISN 1150		WHIP 1350
	KGFJ 1230	Martinsville, Va.	WHEE 1370	Minneapolis, Minn.	WCCO 830 C		WHIP 1350
	KFAC 1330		WNVA 1450 N		WL0L 1330		WHIP 1350
	KLAC 570	Marysville, Calif.	KMVC 1410		WLMN 1400		WHIP 1350
	KMPC 710	Marysville, Kans.	KNDY 1370		WDGY 1130		WHIP 1350
	KNX 1070 C	Marysville, Mo.	KNIM 1580		WPBC 980		WHIP 1350
	KPOL 1540	Marysville, Tenn.	WGAP 1400		WTCN 1280 A		WHIP 1350
	KPOP 1020	Mason City, Iowa	KGLO 1300 C		WUD 770		WHIP 1350
	KRRD 1150		KRIB 1490	Minot, N.Dak.	KLPM 1390 M		WHIP 1350
Louisburg, N.C.	WYRN 1480		KSMN 1310		KQDY 1320		WHIP 1350
Louisville, Ky.	WAVE 970 N	Massena, N.Y.	WMSA 1040 A		KCJB 910 C		WHIP 1350
	WAKY 790 M		KSMC 1310	Mission, Kans.	KBKC 1480		WHIP 1350
	WHAS 840 C	Massillon, Ohio	WTOS 1050	Mission, Tex.	KIRT 1580		WHIP 1350
	WKLO 1080 A	Matane, Que.	CKBL 990	Missoula, Mont.	KGVD 1290		WHIP 1350
	WINN 1240	Matawan, W.Va.	WHJC 1360		KXLL 1450 N		WHIP 1350
	WKYU 900	Mattoon, Ill.	WLBH 1170		KYSE 1340 M		WHIP 1350
	WLOU 1350	Mayaguez, P.R.	WAE 600		KQSS 910		WHIP 1350
	WMT 620		WKJB 710	Mitchell, S.Dak.	KORN 1490 M		WHIP 1350
Louisville, Miss.	WLSM 1290		WORA 1150	Moab, Utah	KURA 1450		WHIP 1350
Loveland, Colo.	KLOV 1570		WRA 970	Moberly, Mo.	KNCJ 1230		WHIP 1350
Lovington, N.Mex.	KLEA 630		WTIL 1300	Mobile, Ala.	WAL 1410 N		WHIP 1350
Lowell, Mass.	WCAP 980	Mayfield, Ky.	WKTM 1050		WABB 1480 A		WHIP 1350
	WLLH 1400 M		WNGO 1320		WGOK 900		WHIP 1350
Lybbeck, Tex.	KCBD 1590 M-N	Mayodan, N.C.	WMYN 1420		WKAB 840		WHIP 1350
	KDAV 580	Mayon, N.C.	WFTM 1240 M		WKRG 710 C		WHIP 1350
	KDJB 1340	McAlester, Okla.	KTMC 1400		WMOZ 960		WHIP 1350
	KFYB 1390 C		KMG 1150	Moberly, S.Dak.	KOLY 1300		WHIP 1350
	KLLL 1460 M	McAllen, Tex.	KRIO 910 M	Modesto, Calif.	KTRB 890		WHIP 1350
	KSEL 1950 A	McCamey, Tex.	KCMR 1450		WCB 870		WHIP 1350
Ludington, Mich.	WKLA 1450 A	McComb, Miss.	WHNY 1250 A		KFIV 1360 A		WHIP 1350
Lufkin, Tex.	KRBA 1340 A	McCook, Nebr.	KBRL 1300 M	Moline, Ill.	WQUA 1230 A		WHIP 1350
	KTRF 1420 M	McGehee, Ark.	KVSA 1220	Monahans, Tex.	KVKM 1340 M		WHIP 1350
Lumberton, N.C.	WAGR 580	McKeesport, Pa.	WEDO 910	Moneton, N.B.	CBAF 1300		WHIP 1350
	WTSB 1340 M		WPK 1360		CKGW 1220		WHIP 1350
	WLVA 500 A	McKinney, Tenn.	WHDM 1340	Monett, Mo.	KRM 990		WHIP 1350
	WVOD 1390 M-N	McKinney, Tex.	KMAE 1600	Monmouth, Ill.	WRA 1330		WHIP 1350
	WBRG 1050	McMinnville, Oreg.	KMCM 1260	Monroe, Ga.	WMRE 1490		WHIP 1350
Lynn, Mass.	WLYN 1360	McMinnville, Tenn.	WBMC 960	Monroe, La.	KMLB 1440 A-N		WHIP 1350
Lyons, Ga.	WBAT 1340		WMNT 1230 M		KLIC 1230 M		WHIP 1350
Maebomb, Ill.	WKAI 1510	McPherson, Kans.	KNEX 1540		KNOE 1390		WHIP 1350
Macon, Ga.	WBML 1240	McRae, Ga.	WDAX 1410		WQTE 560		WHIP 1350
	WCRY 980	Medford, Mass.	WHD 480	Monroe, N.C.	WMAF 1060		WHIP 1350
	WMAZ 940 C	Medford, Mass.	WHIL 1430	Monroe, Wis.	WRA 1260		WHIP 1350
	WNEX 1400 A-M	Medford, Oreg.	KNED 1440 N	Monroeville, Ala.	WMFB 360		WHIP 1350
			KDOV 1300	Monterey, Calif.	KIDD 630		WHIP 1350
			KBOY 730		KMBY 1240 C		WHIP 1350
			KYJC 1230 A-C	Montevideo, Minn.	KDMA 1450 A		WHIP 1350
			WIGM 1490 M	Monte Vista, Colo.	KSLV 1240		WHIP 1350
							WHIP 1350

Location	C.L. Ke. N.A.	Location	C.L. Ke. N.A.	Location	C.L. Ke. N.A.	Location	C.L. Ke. N.A.
New Bern, N.C.	WNBH 1340 M WHIT 1450 M WRNB 1490	Oceanlake, Oreg.	WHYS 1370 KBCH 1380	Park Falls, Wis.	WTAP 1230 A WFPF 1450	Ponca City, Okla.	WLDQ 980 WPOM 1470
Newberry, S.C.	WRNB 1490 KGNB 1240	Oceanside, Calif.	KUDE 1320 KECK 920	Parry Sound, Ont.	CKAR 1340 KLKC 1540	Ponca, P.R.	WBBS 1230 M WPPP 910 WEUC 1420
New Braunfels, Tex.	WYAY 910 A	Odessa, Tex.	KOSJ 1420 KOYL 1310 KRIG 1410 M	Pasadena, Calif.	KALI 1430 KPPC 1240 KRLA 1110 KWKW 1300		WPAB 550 WLED 1170 WSPD 1260
New Britain, Conn.	WKNB 840		KOEL 950 KOGA 930 KLO 1430 M KSVN 730 KVOG 1490	Pasadena, Tex.	KLVL 1480	Pontiac, Mich.	WPOB 1460
New Brunswick, N.J.	WGTC 1450	Oelwein, Iowa	KOGA 930	Pascagoula, Miss.	WPMP 1580 A	Poplar Bluff, Mo.	KWOC 930
Newburgh, N.Y.	WGNV 1220	Ogallala, Nebr.	KLO 1430 M	Pasco, Wash.	KORD 910 KPKC 1340	Portage, Wis.	WPDR 1350
Newburyport, Mass.	WNBP 1470	Ogden, Utah	KOMA 1520 N		KPRL 1230 M	Portage la Prairie, Man.	CFRY 1570
New Carlisle, Que.	CHNC 610	Ogdensburg, N.Y.	KOWS 1400 M	Paso Robles, Calif.	WALK 1370	Port Alberni, B.C.	CJAV 1240
Newcastle, N.B.	CKMR 790	Oil City, Pa.	WKRZ 1310	Patchogue, L.I., N.Y.	WPAC 1580	Portales, N.Mex.	KENM 1450
New Castle, Pa.	WKST 1280 M	Oklahoma City, Okla.	KBYE 890 A KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Paterson, N.J.	WPAT 930	Port Angeles, Wash.	KOPN 1250
Newcastle, Wyo.	KASL 1240		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pawtucket, R.I.	WPAP 550 A	Port Arthur, Ont.	CFPA 1230
New Glasgow, N.S.	WGLC 1200		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Payette, Idaho	CKYL 630	Port Arthur, Tex.	KOLE 1340 KPAC 1250 M
New Haven, Conn.	WVAV 1300 WELI 960 WNHC 1340 A KANE 1240 KVM 1360		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Peace River, Alta.	KIUN 1400 M	Porterville, Calif.	KTIP 1450 A CHUC 1500
New Iberia, La.	WJMR 950 WJNB 800 WNOE 1060 WSNB 1350 A WNPS 1450 WTIX 690 WWL 870 C WYFE 600 WYLD 940 M		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Peas, Tex.	WLN 1420 WLN 1420 M	Port Hope, Ont.	CHUC 1500
New Kensington, Pa.	WKPA 1150		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Peekskill, N.Y.	WSIV 1140	Port Hueneme, Calif.	KALS 1520
New London, Conn.	WLEC 1490 M		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pekin, Ill.	WFHK 1430	Port Huron, Mich.	WHLG 1490 WTLT 1350 A
New Martinsville, W. Va.	WVET 1330 M WCOH 1400 M WDSU 1280 N WJWB 1230 WJMR 950 WJNB 800 WNOE 1060 WSNB 1350 A WNPS 1450 WTIX 690 WWL 870 C WYFE 600 WYLD 940 M		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pell City, Ala.	CHOV 1350	Port Jervis, N.Y.	WDLC 1490
Newport, Ark.	WNOP 740		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pembroke, Ont.	KUBE 1050	Portland, Ind.	WPGW 1440
Newport, Oreg.	KNPT 1310		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pendleton, Oreg.	KUMA 1290 A	Portland, Maine	WCSH 970 N WGAN 560 C WLOB 1310
Newport, B.I.	WADK 1540		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pennington Gap, Va.	WSWY 1570 WBOP 980 WBRS 1450 C WNVY 1230 A WCOA 1370 N WFA 790 CKOK 800	Portland, Oreg.	KBPS 1430 KJL 1290 KEX 1190 KGW 620 KGIN 970 C KPAM 1410 KPDQ 830 M KPOJ 830 M KWJJ 1080 A KWJP 730 A
Newport, Tenn.	WLIK 1270		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pensacola, Fla.	WSWY 1570 WBOP 980 WBRS 1450 C WNVY 1230 A WCOA 1370 N WFA 790 CKOK 800	Port Neches, Tex.	KPNG 1150
Newport, Vt.	WIKI 1490		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Penticton, B.C.	WIRL 1290 M WPEI 1020 WPY 1400	Portsmouth, N.H.	WHBB 750
Newport News, Va.	WGH 1310 A WYUO 1270		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Peoria, Ill.	WMBD 1470 C WIRL 1290 M WPEI 1020 WPY 1400	Portsmouth, Ohio	WNXT 1400 A WLOW 1400 A
New Rochelle, N.Y.	WVOX 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Perry, Fla.	WPY 1400	Portsmouth, Va.	WLOW 1400 A WAVY 1350 N
New Smyrna Beach, Fla.	WSAB 1230 M WCOB 1280 KJRG 950 WBKN 1410 WNNJ 1360 WNNC 1280 KNJ 860		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Perry, Ga.	WBNN 980	Post, Tex.	KUKK 1000
Newton, Iowa	WCOB 1280		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Perryton, Tex.	KEYE 1400 M	Post, Okla.	KWPC 1280
Newton, Kans.	KJRG 950		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Peru, Ind.	WARU 1000	Post, Mo.	KYRO 1280
Newton, Miss.	WBKN 1410		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Petaluma, Calif.	WFLS 490	Potsdam, N.Y.	WPDW 1470
Newton, N.J.	WNNJ 1360		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Peterborough, Ont.	CHEX 980	Pottstown, Pa.	WPAZ 1370
Newton, N.C.	WNNC 1280		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Petersburg, Va.	WSSV 1240 M	Pottsville, Pa.	WPAW 1450
New Ulm, Minn.	KNJ 860		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Petoskey, Mich.	WMBN 1340	Poughkeepsie, N.Y.	WEDC 1390
New Westminster, B.C.	CKNW 980		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Phenix City, Ala.	WPXN 1460 A	Powell, Wyo.	KPOW 1260 M
New York, N.Y.	WABC 770 A WBXN 1380 WCBS 880 C WEDV 1330 WHOM 1480 WINS 1010 WLIB 1190 WMCA 570 WMGM 1050 WNEW 1130 WNYC 830 WOR 710 M WADO 1280 WPDW 1330 WQXR 1560 WRCR 660		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Philadelphia, Pa.	WCAU 1210 WFLS 490 WDS 1480 WFL 560 A WHAT 1340 WIBG 990 WIP 610 M WJMJ 1540 WJPN 950 WROV 1450 WTEL 860	Poughkeepsie, N.Y.	WEDC 1390
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Philadelphia, Pa.	WCAU 1210 WFLS 490 WDS 1480 WFL 560 A WHAT 1340 WIBG 990 WIP 610 M WJMJ 1540 WJPN 950 WROV 1450 WTEL 860	Powell, Wyo.	KPOW 1260 M
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Phillipsburg, Pa.	WPBH 1260	Poynette, Wis.	WIBU 1240
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Phoenix, Ariz.	KIFN 860 KNAT 1400 KHAT 1480 KHBP 1280 KOP 550 A KDOL 960 C KPHO 910 A KQUE 740 KRIZ 1230 KTAR 620 N KTRF 1320 KWB 1590 KXFX 630 KCCR 1900 KLSI 950 KPEK 1240 M KCLA 1400 M KOTN 1480 M KWB 1590 WCMF 1350 WMLF 1230 WYWO 970 KLOH 1050 WPTW 1570 KKS 910 KOP 550 A KSEK 1340 KDKA 1020 KQV 1410 WCAE 1250 WEEP 1080 WAMP 1320 N WPIT 730 WPSW 1870 WBBA 1580 WBEC 1420 A WBRK 1340 M WPTS 1540 KVDP 1400 M WPLA 910 WSWV 1390 WYR 1340 M WIRY 1340 M WBDP 1380 WOND 1400 WPLM 1390 WPNC 1470 WPLY 1420 KPCD 1420 WKL 440 KWIC 1240 M KYTE 1290 WVDM 540 WVOW 1600	Prairie du Chien, Wis.	WPRE 980 KWSK 1570
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Phoenia, Ariz.	KIFN 860 KNAT 1400 KHAT 1480 KHBP 1280 KOP 550 A KDOL 960 C KPHO 910 A KQUE 740 KRIZ 1230 KTAR 620 N KTRF 1320 KWB 1590 KXFX 630 KCCR 1900 KLSI 950 KPEK 1240 M KCLA 1400 M KOTN 1480 M KWB 1590 WCMF 1350 WMLF 1230 WYWO 970 KLOH 1050 WPTW 1570 KKS 910 KOP 550 A KSEK 1340 KDKA 1020 KQV 1410 WCAE 1250 WEEP 1080 WAMP 1320 N WPIT 730 WPSW 1870 WBBA 1580 WBEC 1420 A WBRK 1340 M WPTS 1540 KVDP 1400 M WPLA 910 WSWV 1390 WYR 1340 M WIRY 1340 M WBDP 1380 WOND 1400 WPLM 1390 WPNC 1470 WPLY 1420 KPCD 1420 WKL 440 KWIC 1240 M KYTE 1290 WVDM 540 WVOW 1600	Pratt, Kans.	KWSK 1570
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pine Bluff, Ark.	KCLA 1400 M KOTN 1480 M KWB 1590 WCMF 1350 WMLF 1230 WYWO 970 KLOH 1050 WPTW 1570 KKS 910 KOP 550 A KSEK 1340 KDKA 1020 KQV 1410 WCAE 1250 WEEP 1080 WAMP 1320 N WPIT 730 WPSW 1870 WBBA 1580 WBEC 1420 A WBRK 1340 M WPTS 1540 KVDP 1400 M WPLA 910 WSWV 1390 WYR 1340 M WIRY 1340 M WBDP 1380 WOND 1400 WPLM 1390 WPNC 1470 WPLY 1420 KPCD 1420 WKL 440 KWIC 1240 M KYTE 1290 WVDM 540 WVOW 1600	Prescott, Ariz.	KYCA 1490 N KXK 1450 A KZDK 1340
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pine City, Minn.	WCMF 1350	Presque Isle, Me.	WAGM 1450
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pineville, Ky.	WMLF 1230	Preston, Idaho	KPST 1340
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Pineville, W. Va.	WYWO 970	Preston, Ky.	WPRT 960 WDOC 1310
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Price, Utah	KOAL 1230 M
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Pricehard, Ala.	WAIP 1270
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Prince Albert, Sask.	KYCA 1490 N
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Prince George, B.C.	CKPG 550
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Prince Rupert, B.C.	CFPR 1240
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Princeton, Ind.	WRAY 1250
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Princeton, Ky.	WPKY 1580
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Princeton, W. Va.	WLOH 1490 A
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Prineville, Oreg.	KROG 890
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Prosser, Wash.	WEAN 790 M
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Providence, R.I.	WHIM 1110 WICE 1290 WJAR 920 N WPRD 630 C WRIB 1220 KIX 1400 A KEYY 1450 KOVO 960 M KOLS 1570 KDZA 1230 KAPI 690 KFEL 970 KGHF 1350 M KCS 590
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Pulaski, Tenn.	WKSJ 1420 A
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Pulaski, Va.	WPUV 1580
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Pullman, Wash.	KWSC 1250 KOFE 1150
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Punxsutawney, Pa.	WPME 1540
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Putnam, Conn.	WCT 1350
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Physiup, Wash.	KAY 1300
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Quannah, Tex.	KOLJ 1150
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Quebec, Que.	CBV 980 CHRC 800 CJLR 1060 CJRC 1340 CKCV 1280 CKW 970 A
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Quincy, B.C.	WGNM 1230 M
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Quincy, Ill.	WTAD 940 C
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Quincy, Mass.	WJDA 1300
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Quincy, Wash.	KPDR 1370
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Quintman, Ga.	WSEB 1490
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Racine, Wis.	WRJN 1400
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Radford, Va.	WRAD 1460
	WVAB 1270 WVOC 1460		KOLR 1140 KOCY 1340 KOMA 1520 N KTOK 1000 C KTOW 800 WKY 930	Piquette, Miss.	WRIF 1320	Raleigh, N.C.	WKIX 850 A
	WVAB 1270 WVOC 14						

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Rapid City, S. Dak.	WPTF 680 N WSHE 570 WRAL 1240 KOTA 1380 C KRSJ 1340 KEZU 920 KRTN 1490 A WMOV 1360 KRAL 1240 M KAPA 1340 KSDX 1240 KCLP 990 KFEU 1240 C WHUM 1240 C WRAP 1340 N KRDG 1230 M KPAP 1270 KSDA 1400 KVCV 600 C KBLF 1490 CKRD 850 CKAL 1410 WCCB 1440 KPRB 1240 KCU 1250 KGRG 1490 WRDB 1400 CBK 540 CKCK 620 CKRM 980 WFRB 1800 A KREY 1220 WREM 1480 KOH 630 N KBET 1340 M KOLO 920 C KONE 1450 KDOT 1230 KQDE 1100 KRXX 1230 WOBT 1240 WJMC 1240 KSCV 980 KALE 980 WTO 1450 WRIC 540 WKBY 1490 A WEKY 1340 M WANT 990 WBBL 1480 WVLI 1590 WLEE 1490 N WEET 1320 WMBG 1380 A WRNL 910 M WRVA 1140 C WKGJ 950 CJRV 1310 WMNF 1280 KRCK 1360 KRKS 1240 CJBR 900 WRIO 1320 WWMV 1520 WTRB 970 WCWC 1600 WRIV 1390 KPRO 1440 KACE 1579 KWRL 1450 M WWEV 1390 CJFP 1400 WELR 1360 WDBJ 960 C WRIS 1410 M WHYE 910 WROV 1240 N WVLS 640 N	Rome, N.Y. Ronceverte, W. Va. Roseburg, Oreg. Rosenberg, Tex. Rosville, Ga. Roswell, N. Mex. Rouyn, Que. Roxboro, N.C. Royal Oak, Mich. Rumford, Me. Rupert, Idaho Rushton, La. Rusk, Texas Russell, Kans. Russellville, Ala. Russellville, Ark. Russellville, Ky. Rutland, Vt. Saanich, B.C. Sackville, N.B. Sacramento, Calif. Safford, Ariz. Saginaw, Mich. St. Albans, Vt. St. Albans, W. Va. Ste. Anne de la Pocatiere, Que. St. Augustine, Fla. St. Boniface, Man. St. Catharines, Ont. St. Charles, Mo. St. Cloud, Minn. St. George, Utah St. Helen, Mich. St. Hyacinthe, Que. St. Jean, Que. St. Jerome, Que. Saint John, N.B. St. John's, Nfld. St. Johnsburg, Vt. St. Joseph, Mich. St. Joseph, Mo. St. Joseph d'Alma, Que. St. Louis, Mo. St. Mary's, Pa. St. Paul, Minn. St. Peter, Minn. St. Petersburg, Fla. St. Petersburg Beach, Fla. St. Thomas, Ont. Ste. Genevieve, Mo. Salamanca, N.Y. Salem, Ill. Salem, Ind. Salem, Mass. Salem, Mo. Salem, Oreg. Salem, Va. Salida, Colo. Salina, Kans. Salinas, Calif. Saline, Mich. Salisbury, Md. Salisbury, N.C. Salmon, Idaho Salt Lake City, Utah	WKAL 1450 A WRDN 1400 KRRR 1490 C KRXL 1240 A KFRD 980 WRIP 980 KSWJ 1230 KGFL 1400 M KBIM 910 CKRN 1400 WRXO 1430 WEXL 1340 WRUM 790 KAYT 970 KRUS 1490 KTLU 1580 KRSL 990 WVWR 920 KXJR 1490 WRUS 1420 WHWV 1000 WSYB 1380 M CFAX 810 CBA 1070 KGRA 1320 N KFBK 1530 A KGBM 1490 M KROY 1240 C KXDA 1470 KGLU 1480 A WKNX 1210 WSAM 1400 N WSGW 790 M WVWV 1420 CHQB 1350 WFOY 1240 C WSTN 1240 CKSB 1500 CTB 610 KADY 1460 KFAM 1450 N WJON 1240 KOKU 1450 KMIC 1590 KBS 1240 CHRS 1090 CKJL 900 CFBC 930 CHSJ 1150 CJBN 640 CJDN 950 VOAR 1230 VDCM 590 VQWR 800 WTWN 1340 WSJM 1400 KFEF 680 KBS 1240 KUSN 1270 CFGT 1270 KATZ 1600 KFUD 850 KMOX 1120 C KSD 550 N KSTL 690 KWK 1580 KXOK 630 WEL 770 M WTW 1430 A KRSI 950 WKB1 1400 KSTP 1500 N KJWB 1590 M KRBI 1310 WFIN 680 WUN 620 A WLCY 1380 M WILZ 1590 CHLD 680 KSGM 980 WNY 1590 WJBD 1590 WSLM 1220 WESX 1230 KSMO 1340 KSLM 1390 A KBYZ 1490 WUN 620 A WBLU 1480 KYRH 1340 M KSAL 1150 M KODN 1460 KSBW 1380 M WLB 1290 WBOC 980 WIDC 1320 WJDY 1470 WSTP 1490 M WSAT 1280 A KSR9 960 KALL 910 M KCPX 1320 N KLUB 570 A KNAK 1280 KSL 1170 C KSLP 1370 KWHO 860 KWIC 1540 KTXL 1340 KGKL 960 A KPEP 1420 KWFR 1269 KCOR 1350	KENS 680 C KUKA 1250 KUBO 1310 KMAC 630 A KQNO 860 KTS5 550 WOAI 1250 KCKC 1350 KFKM 590 KRNO 1240 KITD 1290 M WSNT 1490 KCBQ 1170 KFN 540 KFSO 600 C KGB 1360 A KSDO 1240 KSDO 1130 KSPT 1400 WLEC 1450 M KGIL 1260 WTRR 1400 WIOE 1360 WSME 1220 WWEY 1290 WYFC 1050 KFCR 610 M KCBS 740 C KJBS 1100 KNBC 680 N KQBY 1550 M KSAV 1010 KSAN 1450 KSF 960 KYA 1820 KLOK 1170 KJEO 1590 KEEN 1370 KRRX 1500 KFR 680 M WHOA 400 WIPR 940 KWAP 580 C WKVM 1230 WITA 1140 KATY 1340 KVEC 920 M KCNY 1470 KOFY 1050 KTM 1510 KBA 1410 KWIZ 1480 KOB 1490 KIST 1340 N KTM5 1250 A-M KSCO 1080 KTRC 1400 A KWF 1260 C KCOY 1400 KSM2 1240 KDAY 1580 KSPA 1400 KSRQ 1350 KJK 1150 WKA 580 C WYBZ 1240 A WKXY 930 WSPB 1450 C WIPN 900 WYBZ 1280 CHOK 1070 CFQC 600 CFNS 1170 CKOM 1420 WGHQ 920 WSDO 1250 Ontario CJIC 1050 CKCY 1400 WCCP 1450 M WJIV 900 WSA 630 N WSGA 1400 WTDG 1290 C WSDK 1230 A WDRM 1010 WATS 960 KCA 1330 WGY 810 N WSNY 1240 KNEB 960 M KOLT 1320 C WGR1 1050 WRO 1330 KPD 900 WLCK 1250 WARM 590 A WEJL 630 WGB1 910 C KAWK 1400 WSCR 1320 WSUX 1280 KAYO 1150 KING 1090 A KIRD 710 C KJR 950 KOL 1300 KOMD 1000 N KTIX 1590 KTW 1250 KKA 770 KWCB 1300 WJCM 960 KDRO 1490	Seguin, Tex. Selma, Ala. Seminole, Tex. Seneca Township, S.C. Sevierville, Tenn. Seward, Alaska Seymour, Ind. Seymour, Ind. Shamokin, Pa. Shamrock, Tex. Sharon, Pa. Shawano, Wis. Shawinigan, Que. Shawnee, Okla. Sheboygan, Wis. Shelby, Mont. Shelby, N.C. Shelbyville, Tenn. Shenandoah, Iowa Sherbrooke, Que. Sheridan, Wyo. Sherman, Tex. Show Low, Ariz. Shreveport, La. St. Albans, N.H. St. John's, N.B. St. Joseph, Mo. Sidney, Mont. Sidney, Nebr. Sierra Vista, Ariz. Sikeston, Mo. Siler City, N.C. Siloam Springs, Ark. Silver City, N. Mex. Silver Springs, Md. Simcoe, Ont. Sinton, Tex. Sioux City, Iowa Sioux Falls, S. Dak. Sitka, Alaska Skowhegan, Maine Smithfield, N.C. Smiths Falls, Ont. Snyder, Tex. Socongo, N. Mex. Soda Springs, Idaho Somerset, Ky. Somerset, Pa. Sonora, Calif. Sorel, P.Q. So. Bend, Ind. Southbridge, Mass. So. Boston, Va. South Daytona Beach, Fla. Florida So. Gastonia, N.C. So. Paris, Me. So. Pittsburg, Tenn. So. St. Paul, Minn. So. Williamsport, Pa. Sparta, Ill. Sparta, Tenn. Sparta, Wis. Spartanburg, S.C. Spencer, Iowa Spokane, Wash. Springdale, Ark. Springfield, Ill. Springfield, Mass. Springfield, Mo. Springfield, Ohio Springfield, Oreg. Springfield, Tenn. Springfield, Vt. Springhill, La. Spruce Pine, N.C. Stamford, Conn. Stamford, Tex. Stark, Fla.	KSIS 1050 KWED 1580 WJCH 1340 C WHBB 1480 WRJL 1570 KSMJ 1250 WSNW 1150 WVSE 960 KIBJ 1340 A WJCO 1390 KSEY 1230 WISL 1490 KBYP 1580 WFCP 790 WJCH 960 CKSM 1220 KGF 1450 M WHBL 1330 WKTL 950 KSEN 1150 M WQHS 730 M WJCH 1340 WHAL 1400 KHFAL 920 KMA 960 A CHLT 320 CKTS 900 KWYO 1410 M KRRV 910 M KTXD 1050 KVMW 1050 KANB 1300 KCIJ 1050 KEEL 710 KJEN 1550 M KJDE 1480 KOKA 980 KRNO 1340 A KWIK 1130 C KGGC 1480 M KSH 1340 A KFD 420 A KSN 1400 WNCA 1570 M KUOA 1290 M KSIL 1340 C WGA 1050 OFS 560 KOD 1590 KSCJ 1360 A KMNS 620 KTRI 1470 KISD 1320 KELD 1230 KHO 1270 KSDO 1140 A KFW 1230 C-A KSEW 1400 WGHM 1150 WJPM 1270 CJET 630 KST 1450 M KSCR 1290 KBRV 540 WSPC 1240 M WTL0 1480 WVSC 990 KROG 1450 CJIS 1320 WNU0 1490 A WJVA 1580 M WSBT 960 C WESO 970 WHLF 1400 A WELE 1590 WGS 1420 WTKQ 1450 WEPG 910 WISK 630 M WIFT 1450 WHCO 1230 WSMT 1020 WGDW 1290 WTHE 1400 M WORD 910 N WSP 950 C KID 1240 KGA 1510 A KLYK 1230 KPEG 1380 KHQ 590 N KNEW 790 M KREM 970 KXLY 920 C KBRS 1340 A WCVS 1450 A-M WMAV 970 N WTA 1240 C WVSP 1450 M WHYN 560 C WMA5 1450 M WSPR 1270 KJGB 1260 N KICK 1340 KTT 1400 C KWTO 560 A WIZE 1340 A WBLY 1600 KEED 1050 WDBL 1590 WBRB 1480 KBS 1480 WTOE 1470 WSTC 1400 A KWAT 1400 WGR 1490	

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KGDN	Edmonds, Wash.	630	KIPA	Hilo, Hawaii	1110	KMBC	Kansas City, Mo.	980
KGEE	Bakersfield, Calif.	1230	KIRO	Seattle, Wash.	1450	KMFL	Juneteau, Tex.	1450
KGKX	Stirling, Calif.	1230	KIRT	Mission, Tex.	1580	KMBY	Montelero, Tex.	1420
KGEM	Boise, Idaho	1450	KIRX	Kirksville, Mo.	1450	KMCD	Fairfield, Iowa	1570
KGEN	Tulare, Calif.	1370	KISD	Sioux Falls, S.Dak.	1230	KMCM	McMinville, Oreg.	1260
KGER	Long Beach, Calif.	1390	KISN	Vancouver, Wash.	910	KMCO	Conroe, Tex.	900
KGEZ	Kalspell, Mont.	1600	KIST	Santa Barbara, Calif.	1340	KMDO	Ft. Scott, Kans.	1600
KGFF	Shawnee, Okla.	1450	KIT	Yakima, Wash.	1280	KMED	Medford, Oreg.	1440
KGJJ	Los Angeles, Calif.	1230	KITI	Chehalis, Wash.	1420	KMEL	Wenatchee, Wash.	1300
KGL	Roswell, N.Mex.	1400	KITN	Yakima, Wash.	920	KMHL	Marshall, Minn.	1400
KGFV	Keosau, Colo.	1340	KITD	Sydney, Ontario, Calif.	1290	KMHS	Marshall, Tex.	1400
KGFX	Pierre, S.Dak.	630	KIUL	Garden City, Kans.	1240	KMIL	Camden, Tex.	1330
KGGF	Coffeyville, Kans.	690	KIUP	Pecos, Tex.	1400	KMIN	Grants, N.M.	980
KGGM	Albuquerque, N.Mex.	610	KIUR	Durango, Colo.	930	KMJJ	Fresno, Calif.	1580
KGHH	Pueblo, Colo.	1350	KIVY	Crockett, Tex.	1290	KMLB	Monroe, La.	1440
KGHL	Billings, Mont.	980	KIXL	Dallas, Tex.	1040	KMLW	Marlin, Tex.	1010
KGHM	Brookfield, Mo.	1470	KIXX	Provo, Utah	1400	KMMJ	Grand Island, Nebr.	750
KGIL	San Fernando, Calif.	1260	KIXZ	Amarillo, Tex.	940	KMMS	Marshall, Mo.	1300
KGIW	Alamosa, Colo.	1450	KJAN	Atlantic, Iowa	1000	KMNS	Sioux City, Iowa	1260
KGKB	Tyler, Tex.	960	KJAT	Henderson, Tex.	1400	KMOA	Osceola, Ark.	1360
KGKL	San Angelo, Tex.	1490	KJAX	Santa Rosa, Calif.	1150	KMOM	Great Falls, Mont.	520
KGLC	Miami, Okla.	910	KJAY	Topeka, Kans.	1440	KMOP	Tucson, Ariz.	1320
KGLN	Glenwood Sprngs., Colo.	980	KJBC	Midland, Tex.	1150	KMOX	St. Louis, Mo.	1130
KGLM	Mason City, Iowa	1300	KJBS	San Francisco, Calif.	1100	KMPC	Los Angeles, Calif.	710
KGLU	Safford, Ariz.	1480	KJCK	Junction City, Kans.	1420	KMRC	Morgan City, La.	1480
KGMB	Honolulu, Hawaii	590	KJEF	Jennings, La.	1290	KMRS	Morris, Minn.	1290
KMC	Englewood, Colo.	1150	KJET	Butte, Mont.	1360	KMUS	Muleshoe, Tex.	1370
KMG	Cape Girardeau, Mo.	1220	KJW	Webster City, Iowa	1570	KMUR	Murray, Wash.	960
KGMS	Sacramento, Calif.	1380	KJIM	Ft. Worth, Tex.	870	KMUS	Muskogee, Okla.	1360
KGNB	New Braunfels, Tex.	1420	KJND	North Platte, Nebr.	970	KMVI	Walluku, T. H.	550
KGNC	Amarillo, Tex.	710	KJNU	Juneau, Alaska	630	KMYC	Marysville, Calif.	1410
KGNO	Dodge City, Kans.	1370	KJOE	Shreveport, La.	1480	KNAF	Fredericksburg, Tex.	1340
KGO	San Francisco, Calif.	810	KJOY	Stockton, Calif.	1280	KNAK	Salt Lake City, Utah	1280
KGDN	Oregon City, Oreg.	1520	KJRY	Seattle, Wash.	950	KNAL	Victoria, Tex.	1400
KGDS	Turkey, Wyo.	1480	KJRW	Newton, Kans.	950	KNBA	Vallejo, Calif.	1190
KGPC	Grafton, N.Dak.	1340	KJRK	Clatsop, Nebr.	1500	KNBN	San Francisco, Calif.	580
KGRN	Grinnell, Iowa	1410	KJRE	Vancouver, Wash.	1150	KNBX	Kirkland, Wash.	1050
KGRS	Gresham, Oreg.	1230	KKID	Pendleton, Oreg.	1240	KNBY	Newport, Ark.	1280
KGRT	Las Cruces, N.Mex.	1370	KKIS	Pittsburg, Calif.	990	KNCK	Concordia, Kans.	1390
KGST	Fresno, Calif.	1600	KKOG	Ogden, Utah	730	KNCM	Moberly, Mo.	1230
KGU	Honolulu, Hawaii	760	KKSN	Grand Prairie, Tex.	730	KNCO	Garden City, Kans.	1050
KGVV	Greenville, Tex.	1400	KKAD	Los Angeles, Calif.	570	KNDE	Aztec, N.Mex.	1490
KGVU	Missoula, Mont.	1290	KKAC	Klamath Falls, Oreg.	860	KNDY	Marysville, Kans.	1570
KGVW	Billings, Mont.	630	KKAM	Cordova, Alaska	970	KNEB	Scottsbluff, Nebr.	960
KGW	Portland, Oreg.	620	KKAS	Las Vegas, Nev.	1230	KNEC	Madison, Okla.	1450
KGWA	Enid, Okla.	1240	KKBB	Livingston, Tex.	1220	KNEL	Brady, Tex.	1190
KGYD	Dyalla, Wash.	1220	KKCN	Blue Hill, Ark.	910	KNEM	Nevada, Mo.	1240
KGYN	Guyon, Okla.	1580	KKCO	Poteau, Okla.	1280	KNEP	Palestine, Tex.	1450
KHAM	Albuquerque, N.Mex.	1580	KKCG	Lawton, N.Mex.	630	KNEU	Provo, Utah	1450
KHAS	Abingdon, Nebr.	1230	KKCH	Ottumwa, Iowa	1460	KNEV	Spokane, Wash.	790
KHAT	Phoenix, Ariz.	1470	KKCM	Le Mars, Iowa	1410	KNEW	McPherson, Kans.	1050
KHBC	Hilo, Hawaii	1320	KKCN	Killeen, Tex.	1050	KNEZ	Lompoc, Calif.	920
KHBM	Monticello, Ariz.	1430	KKED	Wichita, Kans.	1480	KNFS	Hanford, Calif.	660
KHBR	Hillsboro, Tex.	1560	KKER	Orofino, Idaho	950	KNIM	Maryville, Mo.	1580
KHEM	Big Springs, Tex.	1270	KKEX	Lexington, Mo.	1570	KNIT	Abilene, Tex.	1520
KHEN	Henryetta, Okla.	1590	KKFD	Litchfield, Minn.	1410	KNOC	Natchitoches, La.	1450
KHEP	Phoenix, Ariz.	1280	KKFT	Golden Meadow, La.	1600	KNOE	Nogales, Ariz.	1390
KHEY	El Paso, Tex.	620	KKGL	Altoona, Iowa	1600	KNOG	Nogales, Ariz.	1600
KHFM	Sierra Vista, Ariz.	1490	KKGN	Logan, Utah	1390	KNOR	Norman, Okla.	1400
KHFW	Pampa, Texas	1230	KKGR	Redwood Falls, Minn.	1490	KNOT	Prescott, Ariz.	1450
KHIL	Brighton-Fort Lupton, Colorado	800	KKLC	Redwood Falls, Minn.	1490	KNOW	Austin, Tex.	1490
KHIT	Walla Walla, Wash.	1320	KKLD	Monroe, La.	1230	KNOX	Grand Forks, N.Dak.	1310
KHJ	Los Angeles, Calif.	930	KKLE	Dallas, Tex.	1190	KNPT	Newport, Ore.	1310
KHMO	Hannibal, Mo.	1070	KKLF	Jefferson City, Mo.	950	KNPJ	New Ulm, Minn.	860
KHMB	Hobbs, N.Mex.	1280	KKLG	Estherville, Iowa	1430	KNQ	Waterloo, Iowa	1090
KHOG	Fay, Ark.	1480	KKLN	Lincoln, Nebr.	1440	KNR	Waterloo, Iowa	1090
KHOT	Madera, Calif.	1250	KKLO	Portland, Oreg.	1230	KNX	Los Angeles, Calif.	1070
KHOW	Denver, Colo.	630	KKLP	Denver, Colo.	990	KOA	Denver, Colo.	1850
KHOZ	Harrison, Ark.	900	KKLR	Twin Falls, Idaho	1310	KOAC	Corvallis, Oreg.	550
KHQ	Spokane, Wash.	590	KKLS	Brainerd, Minn.	1380	KOAL	Provo, Utah	1230
KHSJ	Hemet, Calif.	1320	KKLC	Parsons, Kans.	1540	KOAM	Pittsburg, Kans.	860
KHSL	Chico, Calif.	1390	KKLA	Leesville, La.	1570	KOAB	Albuquerque, N.Mex.	1030
KHUB	Fremont, Nebr.	1340	KKLB	Lubbock, Tex.	1460	KOBE	Las Vegas, N.Mex.	1540
KHUC	Borger, Texas	1490	KKLM	Longmont, Colo.	1050	KOBY	San Francisco, Calif.	1540
KHVV	Honolulu, Hawaii	1040	KKLN	Lincoln, Colo.	1020	KOCA	Kilgore, Tex.	1250
KIBE	Palo Alto, Calif.	1220	KKLO	Lincoln, Nebr.	1480	KOCY	Oklahoma City, Okla.	1340
KIBB	Seward, Alaska	1240	KKLP	Clayton, N.Mex.	1450	KOD	Joplin, Mo.	1230
KIBL	Beville, Tex.	1430	KKLV	Ogden, Utah	1430	KODI	Cody, Wyo.	1440
KIBS	Bishop, Calif.	1290	KKLG	Kelso, Wash.	1490	KODL	The Dalles, Oreg.	1400
KICA	Clovis, N.Mex.	1980	KKLO	Pipestone, Minn.	1050	KODM	North Platte, Nebr.	1240
KICD	Spencer, Iowa	1240	KKLN	San Jose, Calif.	1170	KODN	Delwin, Iowa	850
KICK	Springfield, Mo.	1340	KKLM	Corvallis, Oreg.	1340	KOFA	Yuma, Ariz.	1240
KICN	Denver, Colo.	710	KKLN	Albuquerque, N.Mex.	1580	KOFI	Pullman, Wash.	1150
KICO	Calexico, Calif.	1490	KKLO	Lake Charles, La.	1570	KOFK	Kalspell, Mont.	930
KIDD	Idaho Falls, Idaho	590	KKLP	Loveland, Colo.	1570	KOFM	Ottawa, Kans.	1020
KIDD	Monterey, Calif.	630	KKLP	Lake Providence, La.	1570	KOFS	San Mateo, Calif.	1250
KIDO	Boise, Idaho	630	KKLR	Minot, N.Dak.	1390	KOGA	Ogallala, Nebr.	930
KIEM	Eureka, Calif.	1480	KKLS	Oklahoma City, Okla.	1140	KOGT	Orange, Tex.	1600
KIET	Glendale, Calif.	870	KKLT	Union, Mo.	1010	KOHA	Hammond, La.	1350
KIFI	Idaho Falls, Idaho	1260	KKLU	Little Rock, Ark.	1270	KOHU	Hermiston, Oreg.	1570
KIFN	Phoenix, Ariz.	860	KKLV	Little Rock, Ark.	1270	KOIM	Omaha, Nebr.	1290
KIFW	Sitka, Alaska	1340	KKLN	Little Falls, Minn.	960	KOIN	Portland, Oreg.	970
KIHN	Hugo, Okla.	1230	KKLT	Blackwell, Okla.	1580	KOJM	Havre, Mont.	610
KIHO	Sioux Falls, S.Dak.	1270	KKLT	Glasgow, Mont.	1240	KOKA	Shreveport, La.	980
KIHR	Hood River, Oreg.	1340	KKLB	Salt Lake City, Utah	570	KOKB	Austin, Tex.	1370
KIJJ	Huron, S.Dak.	1340	KKLV	Longview, Tex.	1280	KOKL	Wichita, Okla.	1240
KIKK	Bakersfield, Calif.	800	KKLU	Evanson, Wyo.	1240	KOKO	Warrensburg, Mo.	1450
KIKI	Honolulu, Hawaii	850	KKLV	Wheatland, Wyo.	1580	KOKX	Keokuk, Iowa	1310
KIKM	Miami, Fla.	630	KKLV	Leadville, Colo.	1230	KOKY	Little Rock, Ark.	1440
KIKS	Sulphur, La.	1310	KKLV	Vivian, La.	1600	KOKE	Seattle, Wash.	1300
KILE	Galveston, Tex.	1400	KKLV	Pasadena, Tex.	1480	KOLT	Tucson, Ariz.	1320
KILO	Grand Forks, S.Dak.	1440	KKLV	Levelland, Tex.	1230	KOLE	Port Arthur, Tex.	1450
KILT	Houston, Tex.	610	KKLN	Lawrence, Kans.	1320	KOLJ	Quannah, Tex.	1150
KIMA	Yakima, Wash.	1460	KKLN	Lebanon, Mo.	1230	KOLB	Libby, Mont.	1230
KIMB	Kimbelt, Nebr.	1260	KKLV	Bakersfield, Calif.	1350	KOLR	Reno, Nev.	920
KIML	Gillette, Wyo.	1490	KKLV	Spokane, Wash.	1360	KOLR	Stirling, Colo.	1490
KIMO	Hilo, Hawaii	630	KKLV	Clarksville, Ark.	1360	KOLS	Pryor, Okla.	1570
KIMN	Denver, Colo.	950	KKLV	Denver, Colo.	960	KOLT	Scottsbluff, Nebr.	1320
KIMP	Mt. Pleasant, Tex.	960	KKLV	San Antonio, Tex.	630	KOLY	Mobridge, S.Dak.	1300
KIND	Independence, Kans.	1010	KKMA	McKinney, Tex.	1600	KOMA	Oklahoma City, Okla.	1520
KINE	Kingsville, Tex.	1330	KKMA	Fresno, Calif.	1340	KOMB	Cottage Grove, Oreg.	1400
KINS	Seattle, Wash.	1090	KKMA	Tulosa, N.Mex.	1590	KOMF	Tulsa, Okla.	1300
KINT	Eureka, Calif.	980	KKMA	Manhattan, Kans.	1350	KOMO	Seattle, Wash.	1000
KINY	El Paso, Tex.	1580	KKMA	Manhattan, Kans.	1350	KONW	Omaha, Wash.	680
KIOA	Des Moines, Iowa	800	KKMA	Maquoketa, Iowa	1490	KONY	Watsonville, Calif.	1340
KIOX	Bay City, Tex.	1270	KKMA	Winnsboro, La.	1570			

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KRE	Berkeley, Calif.	1400	KSOX	Raymondville, Tex.	1240	KUGN	Eugene, Oreg.	590	KWKH	Shreveport, La.	1130
KREH	Oakdale, La.	900	KSPA	Santa Paula, Calif.	1400	KUIK	Hillsboro, Oreg.	1360	KWKW	Pasadena, Calif.	1180
KREI	Farmington, Mo.	800	KSPI	Stillwater, Okla.	780	KUJ	Walla Walla, Wash.	1420	KWKY	Des Moines, Iowa	1150
KREM	Spokane, Wash.	970	KSPJ	Diboll, Tex.	1260	KUKI	Ukiah, Calif.	1400	KWLC	Decorah, Iowa	1240
KREO	Indio, Calif.	1400	KSTP	Sandpoint, Idaho	1400	KULO	Post, Tex.	1370	KWLM	Willmar, Minn.	1340
KRES	St. Joseph, Mo.	1500	KSTQ	Salt Lake City, Utah	1400	KUN	Hot Springs, Mo.	1270	KWMT	Fl. Dodge, Iowa	540
KREW	Sunnyvale, Wash.	1230	KSRC	Socorro, N. Mex.	920	KUH	Honolulu, Hawaii	500	KWNT	Winnemucca, Nev.	1400
KREX	Grand Junction, Colo.	920	KSRO	Santa Rosa, Calif.	1350	KULE	Ephrata, Wash.	730	KWNO	Winona, Minn.	1230
KRF0	Owatonna, Minn.	1390	KSRV	Ontario, Oreg.	1380	KULP	El Campo, Tex.	1390	KWOA	Worthington, Minn.	730
KRFS	Superior, Nebr.	1600	KSSS	Colorado Springs, Colo.	740	KUNA	Pendleton, Oreg.	1290	KWOC	Poplar Bluff, Mo.	930
KRGI	Grand Island, Neb.	1430	KSSY	Sulphur Springs, Tex.	1230	KUNO	Corpus Christi, Tex.	1400	KWCE	Clinton, Okla.	1300
KRGV	Weslaco, Tex.	1290	KSTA	Coleman, Tex.	1000	KUOA	Siloam Springs, Ark.	1290	KWON	Bartlesville, Okla.	1400
KRHD	Duncan, Okla.	1350	KSTB	Salem, Ore., Tex.	1430	KUW	Winneaux, Minn.	1270	KWOS	Jordanville, Wyo.	1340
KRIB	Mason City, Iowa	1400	KSTL	St. Louis, Mo.	690	KUPI	Idaho Falls, Idaho	980	KWPS	Jerome, Wyo.	1240
KRIC	Beaumont, Tex.	1450	KSTN	Stockton, Calif.	1420	KURA	Moab, Utah	1450	KWQW	Pomona, Calif.	1600
KRIG	Odessa, Tex.	1410	KSTP	St. Paul, Minn.	1500	KURL	Billings, Mont.	730	KWQF	Muscatine, Iowa	860
KRIO	McAllen, Tex.	910	KSTR	Grand Junction, Colo.	620	KURY	Edinburg, Tex.	710	KWPM	West Plains, Mo.	1450
KRIZ	Phoenix, Ariz.	1230	KSTT	Davenport, Iowa	1170	KURV	Brookings, Oreg.	910	KWRP	Claremore, Okla.	1270
KRKC	King City, Calif.	1570	KSTV	Stephenville, Tex.	1510	KUSD	Vermillion, S. Dak.	690	KWRD	Henderson, Tex.	1470
KRKD	Los Angeles, Calif.	1150	KSTP	Cedar Rapids, Iowa	590	KUSH	Cushing, Okla.	1600	KWRE	Warrenton, Ore.	730
KRKE	Everett, Wash.	1380	KSU0	Susanville, Calif.	1240	USN	Union, Mo.	1270	KWRW	Warren, Ark.	850
KRKF	Ridgely, Calif.	1240	KSUM	Fairmont, Minn.	1370	KUTI	Yakima, Wash.	980	KWRJ	Riverton, Wyo.	1450
KRLA	Pasadena, Calif.	1110	KSUN	Bisbee, Ariz.	1230	KUTY	Palmdale, Calif.	1470	KWRO	Coquille, Oreg.	1450
KRLC	Lewiston, Idaho	1350	KSV0	Richfield, Utah	980	KUVR	Holdrege, Nebr.	1380	KWRT	Boonville, Mo.	1370
KRLD	Dallas, Tex.	1080	KSPV	Artesia, N. Mex.	990	KUZN	W. Monroe, La.	1310	KWRW	Guthrie, Okla.	1490
KRLN	Canon City, Colo.	1400	KSWA	Graham, Tex.	1330	KVCK	Wolf Point, Nebr.	1450	KWSC	Pullman, Wash.	1270
KRLW	Walnut Ridge, Ark.	1320	KSWI	Council Bluffs, Iowa	1500	KVCL	Winfield, La.	1270	KWSD	Mt. Shasta, Calif.	620
KRMD	Shreveport, La.	1340	KSWJ	Keosauqua, Mo.	1380	KVY	Medford, Ore.	1400	KWSH	Wewaka-Seminole, Okla.	1260
KRMG	Tulsa, Okla.	1400	KSWS	Roswell, N. Mex.	1230	KVEC	San Luis Obispo, Calif.	920	KWSK	Pratt, Kans.	1570
KRMO	Monett, Mo.	900	KSY0	Yreka, Calif.	1490	KVEL	Vernal, Utah	1250	KWSD	Wasco, Calif.	1050
KRMS	Osage Beach, Mo.	1150	KSYD	Wichita Falls, Tex.	990	KVEN	Ventura, Calif.	1450	KWTC	Barstow, Calif.	1230
KRNO	San Bernardino, Calif.	1240	KSVL	Alexandria, La.	970	KVET	Austin, Tex.	1300	KWTO	Springfield, Mo.	560
KRNR	Roseburg, Oreg.	1490	KTAC	Tacoma, Wash.	850	KVFC	Cortez, Colo.	740	KWTX	Wax, Tex.	1230
KRNS	Burns, Oreg.	1230	KTAE	Taylor, Tex.	1260	KVFD	Fort Dodge, Iowa	1400	KWVW	Waterloo, Iowa	1330
KRNT	Des Moines, Iowa	1350	KTAP	Taylor City, Tex.	1450	KVHL	Homer, Ark.	1320	KWYK	Farmington, N. Mex.	960
KRNY	Keosauqua, Mo.	1480	KTAR	Phoenix, Ariz.	620	KVIC	Victoria, Tex.	1340	KWYN	Wynne, Ark.	1400
KROC	Rochester, Minn.	1340	KTAT	Frederick, Okla.	1570	KVIN	New Iberia, La.	1360	KWYO	Sherridan, Wyo.	1410
KROD	El Paso, Tex.	600	KTBB	Tyler, Tex.	600	KVIN	Vinita, Okla.	1470	KWYR	Winnier, S. Dak.	1270
KROF	Abbeville, La.	960	KTBC	Austin, Tex.	590	KVPI	Redding, Calif.	540	KXAK	Seattle, Wash.	760
KROG	Sonora, Calif.	1450	KTGB	Malden, Mo.	1470	KVKM	Monroeville, Tex.	1410	KXEL	Atterton, Iowa	1540
KROP	Brawley, Calif.	1300	KTGN	Berkeley, Ark.	1400	KVLC	Cleveland, Tex.	1410	KXEN	Festus, Mo.	1010
KROS	Clinton, Iowa	1340	KTGP	Porter, Okla.	1410	KVLF	Alpine, Tex.	1240	KXEO	Mexico, Mo.	1340
KROX	Crookston, Minn.	1400	KTEE	Carmel, Calif.	1410	KVLG	LaGrange, Tex.	1570	KXGI	Ft. Madison, Iowa	1360
KROY	Sacramento, Calif.	1240	KTEE	Walla Walla, Wash.	1490	KVLH	Pauls Valley, Okla.	1470	KXGN	Glendive, Mont.	1400
KRPL	Moscow, Idaho	1400	KTEM	Tempe, Tex.	1400	KVLL	Fallon, Nev.	1250	KXGO	Fargo, N.D.	790
KRRV	Sherman, Tex.	910	KTER	Terrell, Tex.	1570	KVLM	London, Ark.	1300	KXHK	Low City, Iowa	1410
KRSC	Othello, Wash.	1400	KTFI	Twin Falls, Idaho	1270	KVNC	Colorado City, Tex.	1320	KXJT	Dalhousie, Ark.	950
KRSD	Rapid City, S. Dak.	1340	KTFE	Texarkana, Tex.	1450	KVND	Cowinslow, Ariz.	690	KXLL	Portland, Oreg.	750
KRSI	St. Louis Park, Minn.	950	KTFD	Fort Dodge, Iowa	1400	KVNI	Coeur d'Alene, Idaho	1240	KXLE	Ellensburg, Wash.	1240
KRSJ	Russell, Kans.	980	KTHE	The Thermopilis, Wyo.	1240	KVNU	Logan, Utah	1010	KXLF	Butte, Mont.	1370
KRSK	Los Alamos, N. Mex.	740	KTHS	Little Rock, Ark.	1090	KVOC	Casper, Wyo.	1230	KXLG	Great Falls, Mont.	1400
KRTN	Raton, N. Mex.	1490	KTHT	Houston, Tex.	790	KVOD	Emporia, Kans.	1400	KXLL	Low City, Iowa	1450
KRTR	Thermopilis, Wyo.	1490	KTIB	Thibodaux, La.	620	KVOL	Lafayette, La.	1330	KXLS	Lewistown, Mont.	1230
KRUN	Ballingier, Tex.	1400	KTIL	Tillamook, Oreg.	1510	KVOM	Morrilton, Ark.	800	KXLR	No. Little Rock, Ark.	1150
KRUS	Ruston, La.	1490	KTIM	San Rafael, Calif.	1590	KVON	Napa, Calif.	1440	KXLL	Clayton, Mo.	1320
KRUX	Glendale, Ariz.	1360	KTIP	Porter, Okla.	1410	KVOT	Pulsaski, Okla.	1170	KXLY	Spokane, Wash.	920
KRVN	Lexington, Nebr.	1010	KTIS	Minneapolis, Minn.	900	KVOP	Plainview, Tex.	1400	KXO	El Centro, Calif.	1230
KRWC	Forest Grove, Oreg.	1570	KTIX	Seattle, Wash.	1590	KVOR	Old Springs, Colo.	1300	KXOA	Sacramento, Calif.	1470
KRXK	Rexburg, Idaho	1230	KTJ0	Hobart, Okla.	1420	KVOS	Birmingham, Wash.	780	KXOL	Ft. Worth, Tex.	630
KRXL	Roseburg, Oreg.	1240	KTKN	Ketchikan, Alaska	930	KVOU	Uvalde, Tex.	1490	KXOX	Sweetwater, Tex.	1240
KRYS	Corpus Christi, Tex.	1360	KTKR	Taft, Calif.	990	KVOX	Moorhead, Minn.	1280	KXRA	Alexandria, Minn.	1490
KSAC	Manhattan, Kans.	580	KTKT	Tucson, Ariz.	980	KVOY	Yuma, Ariz.	1400	KXRI	Russellville, Ark.	1490
KSAL	Salina, Kans.	1150	KTKU	Tululula, La.	1360	KVZO	Laredo, Tex.	1490	KXRO	Aberdeen, Wash.	1320
KSAM	Huntsville, Tex.	1490	KTLN	Denver, Colo.	1280	KVZL	Ville Platte, La.	1050	KXRV	Rockwell, Calif.	1250
KSAN	San Francisco, Calif.	1450	KTLQ	Mtn. Home, Ark.	1490	KVRC	Arkadelphia, Ark.	1230	KXSL	Golden, Colo.	1250
KSBY	San Francisco, Calif.	1010	KTLQ	Tahlequah, Okla.	1350	KVRH	Salida, Colo.	1430	KXXX	Bozeman, Mont.	1450
KSBW	Salinas, Calif.	1380	KTLU	Rusk, Tex.	1580	KVRS	Rock Springs, Wyo.	1360	KXXX	Coiby, Kans.	790
KSCB	Liberal, Kans.	1270	KTLW	Texas City, Tex.	920	KVSA	McGehee, Ark.	1220	KYAN	San Francisco, Calif.	1260
KSCJ	Sioux City, Iowa	1360	KTMC	McAlester, Okla.	1400	KVSF	Santa Fe, N. Mex.	1240	KYCA	Prescott, Ariz.	1490
KSCO	Santa Cruz, Calif.	1080	KTMS	San Marcos, Calif.	1250	KVSG	Yonkers, N.Y.	1490	KYCE	Boise, Idaho	740
KSD	St. Louis, Mo.	550	KTN0	Falls City, Nebr.	1230	KVVO	Show Low, Ariz.	1370	KYNE	Fresno, Calif.	1300
KSEA	Redding, Calif.	1400	KTNM	Tucumcari, N. Mex.	1400	KWAD	Wadena, Minn.	920	KYNT	Coos Bay, Oreg.	1420
KSEB	Aberdeen, S. Dak.	930	KTNT	Tacoma, Wash.	1400	KWAK	Stuttgart, Ark.	1240	KYNG	Yankton, S. Dak.	1450
KSD0	San Diego, Calif.	1130	KT0C	Jonesboro, La.	920	KWAL	Wallace, Idaho	860	KYDK	Houston, Tex.	1590
KSEI	Pocatello, Idaho	930	KTOD	Sinton, Tex.	1420	KWAM	Memphis, Tenn.	990	KYDQ	Blythe, Calif.	1450
KSEJ	Pittsburg, Kans.	1340	KT0E	Mankato, Minn.	1590	KWAT	Watertown, S. Dak.	950	KYOS	Mered, Calif.	1480
KSEL	Lubbock, Tex.	950	KT0F	Lufkin, Tex.	1420	KWBA	Baytown, Tex.	1360	KYRD	Greely, Colo.	1450
KSEM	Moses Lake, Wash.	1470	KTRF	The River Falls, Minn.	1230	KWBB	Wichita, Kans.	1410	KYRU	Potosi, Mo.	1280
KSE0	Shelby, Mont.	1150	KTRH	Houston, Tex.	740	KWBE	Beatrice, Nebr.	1450	KYSN	Mankato, Minn.	1230
KSEO	Durham, N.C.	750	KTRI	Sioux City, Iowa	1470	KWBG	Bopne, Iowa	1590	KYSO	Colorado Sprgs., Colo.	1460
KSET	El Paso, Tex.	1340	KTRN	Beaumont, Tex.	990	KWBU	Hutchinson, Kans.	1450	KYSS	Pocatello, Idaho	910
KSEW	Sitka, Alaska	1400	KTRM	Wichita Falls, Tex.	1290	KWCB	Searcy, Ark.	1300	KYTT	Pocatello, Idaho	1290
KSEY	Seymour, Tex.	1230	KTRP	Sastrop, La.	730	KWCL	Oak Grove, La.	1280	KYUM	Yuma, Ariz.	560
KSFA	Nacogdoches, Tex.	860	KTRQ	San Antonio, Tex.	530	KWCT	Chickasha, Okla.	1560	KYVJ	Yonkers, N.Y.	1470
KSFE	Needles, Calif.	1340	KTRS	Rolla, Mo.	1490	KWEB	Rochester, Minn.	1270	KYVW	Cleveland, Ohio	1100
KSFD	San Francisco, Calif.	560	KTRS	Springfield, Mo.	1400	KWED	Seguin, Tex.	1580	KZEE	Weatherford, Tex.	1220
KSFB	St. Genevieve, Mo.	980	KTUS	Tucson, Ariz.	1400	KWEI	Weiser, Idaho	1260	KZFY	Tyler, Tex.	690
KSIB	Creston, Iowa	1520	KTUL	Tulsa, Okla.	1530	KWEL	Midland, Tex.	1600	KZIN	Coeur d'Alene, Idaho	1050
KSID	Sidney, Nebr.	1340	KTV0	Tulsa, Okla.	1530	KWEW	Hobbs, N. Mex.	1480	KZIO	Prescott, Ariz.	1340
KSIG	Crowley, La.	1450	KTUR	Turlock, Calif.	1390	KWFR	San Angelo, Tex.	1260	KZJF	Hunter, Tex.	1470
KSIJ	Gladewater, Tex.	1430	KTUT	Tooele, Utah	990	KWFS	Stockton, Calif.	1230	KZJM	Farmington, N. Mex.	1280
KSIL	Silver City, N. Mex.	1340	KTW0	Seattle, Wash.	1250	KWHI	Brenham, Tex.	1280	KZUN	Opportunity, Wash.	630
KSIM	Sikeston, Mo.	1400	KTW1	Casper, Wyo.	1470	KWHK	Hutchinson, Kans.	1280	WAAA	Winston-Salem, N.C.	980
KSIN	Wichita, Kans.	900	KTWJ	Jasper, Tex.	1350	KWHN	Fort Smith, Ark.	1320	WAAF	Worcester, Mass.	1440
KSID	Sedalia, Mo.	1050	KTKL	Salt Lake City, Utah	1340	KWHD	Salt Lake City, Utah	860	WAAB	Chicago, Ill.	950
KSIW	Woodward, Okla.	1450	KTKM	Sherman, Okla.	1530	KWHK	Altus, Okla.	1450	WAAG	Adel, Ga.	1470
KSIX	Corpus Christi, Tex.	1230	KTKN	Sherman, Okla.	1530	KWIC	Salt Lake City, Utah	1570	WAAT	Winton, N.J.	1300
KSJB	Jamestown, N. Dak.	600	KTKO	Turlock, Calif.	1390	KWIK	Pocatello, Idaho	1240	WAAY	Huntsville, Ala.	1550
KSJO	San Jose, Calif.	1590	KTKP	Tulsa, Okla.	1530	KWIL	Albany, Oreg.	790	WABA	Aquadilla, P.Rico	850
KSKY	Dallas, Tex.	660	KTKR	Rolla, Mo.	1490	KWIN	Ashland, Oreg.	1400	WABB	Mobile, Ala.	1480
KSL	Salt Lake City, Utah	1390	KTKS	Springfield, Mo.	1400	KWIV	Douglas, Wyo.	1050	WABC	New York, N.Y.	770
KSL0	Salem, Oreg.	1390	KTKT	Tucson, Ariz.	1400	KWIZ	Santa Ana, Calif.	1480	WABG	Greenwood, Miss.	960
KSLM	Opelousas, La.	1230	KTKU	Tulsa, Okla.	1530	KWJB	Bogalusa, La.	1240	WABI	Bangor, Maine	910
KSLV	Monte Vista, Colo.	1240	KTKV	Tulsa, Okla.	1530	KWJC	Wichita, Okla.	1450	WABJ	Wichita, Okla.	1470
KSMA	Santa Maria, Calif.	1240	KTKW	Turlock, Calif.	1390	KWJD	Portland, Oreg.	1080	WABL	Amite, La.	1570
KSMI	Seminola, Tex.	1250	KTKX	Tulsa, Okla.	1530	KWJP	Merced, Calif.	1580	WABQ	Waynesboro, Miss.	990
KSMN	Mason City, Iowa	1010	KTKY	Wendover, Calif.	1460	KWKI	Moses Lake, Wash.	1260	WABW	Cleveland, Ohio	1540
KSMO	Salem, Mo.	1340	KKUBA	Yuba City, Calif.	1600	KWKK	St. Louis, Mo.	1380	WABT	Winter Park, Fla.	1440
KSMY	Snyder, Tex.	1450	KKUBC	Montrose, Colo.	580	KWKC	Abilene, Tex.	1340	WABU	Tuskegee, Ala.	580
KSD	Des Moines, Iowa	1460	KKUBE	Pendleton, Oreg.	1050						
KSDK	Arkansas City, Kans.	1280	KKUBD	San Antonio, Tex.	1310						
KSDN	San Diego, Calif.	1240	KKUBE	Oceanside, Calif.	1320						
KSD0	Sioux Falls, S. Dak.	1140	KKUDL	Kansas City, Mo.	1450						
KSP0	Salt Lake City, Utah	1370	KKUDU	Ventura, Calif.	1590						
			KKUDY	Littleton, Colo.	1510						
			KKUEN	Wenatchee, Wash.	900						
			KKUEQ	Phoenix, Ariz.	740						

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WABV	Abbeville, S.C.	1590	WAVE	Louisville, Ky.	970	WBRM	Marion, N.C.	1250	WCNT	Centrailla, Ill.	1210
WABW	Annapolis, Md.	810	WAVI	Dayton, Ohio	1210	WBRN	Big Rapids, Mich.	1480	WCNU	Crestview, Fla.	1010
WABY	Albany, N.Y.	1400	WAVL	Apollis, Pa.	920	WBRO	Waynesboro, Ga.	1310	WCNX	Middletown, Conn.	1150
WABZ	Albany, N.Y.	1010	WAVM	Avondale, Minn.	1210	WBRT	Bardonia, Ky.	1320	WCOP	Pensacola, Fla.	1370
WACA	Camden, S.C.	1590	WAVO	Avondale Estates, Ga.	1420	WBRY	Valhalla, N.Y.	910	WCOC	Meridian, Miss.	910
WACB	Kittanning, Pa.	1380	WAVP	Avon Park, Fla.	1390	WBXX	Berwick, Pa.	1280	WCOD	Greensboro, N.C.	1320
WACE	Chicopee, Mass.	730	WAVV	Albertville, Ala.	630	WBRY	Waterbury, Conn.	1580	WCOH	Newnan, Ga.	1400
WACK	Newark, N.Y.	1420	WAVY	Portsmouth, Va.	1350	WBSC	Bennetsville, S.C.	1550	WCOD	Coatesville, Pa.	1420
WACL	Waycross, Ga.	570	WAVZ	New Haven, Conn.	1500	WBSS	New Bedford, Mass.	1420	WCOL	Columbus, Ohio	1230
WACO	Waco, Tex.	1480	WAWK	Kendallville, Ind.	1570	WBSS	Pensacola, Fla.	1450	WCOR	Cornelia, Ga.	1450
WAGR	Columbus, Miss.	1420	WAWZ	Zarephath, N.J.	1380	WBT	Charlotte, N.C.	1110	WCOP	Boston, Mass.	1150
WACT	Tuscaloosa, Miss.	1420	WAXE	Wright Beach, Fla.	1370	WBT	Barfield, N.Y.	1490	WCOR	Lebanon, Tenn.	1900
WADA	Shelby, N.C.	1390	WAXF	Chippewa Falls, Wis.	1470	WBT	Williamsville, W.Va.	1510	WCPS	Clinton, Miss.	1410
WADC	Akron, Ohio	1350	WAWB	Waynesboro, Va.	1490	WBTL	Farmville, N.C.	1050	WCPU	Lewistown, Maine	1240
WADE	Wadesboro, N.C.	1210	WAYE	Dundak, Md.	860	WBTM	Oanville, Va.	1330	WCPU	Montgomery, Ala.	1170
WADK	Newport, R.I.	1540	WAYN	Rockingham, N.C.	900	WBTN	Bannington, Vt.	1370	WCOW	Sparta, Wis.	1290
WADP	New York, N.Y.	1280	WAYS	Charlotte, N.C.	610	WBTO	Linton, Ind.	1600	WCOW	Columbia, Pa.	1580
WADD	Kane, Pa.	960	WAYX	Waycross, Ga.	1230	WBUD	Trenton, N.J.	1260	WCPA	Clearfield, Pa.	900
WADS	Ansonia, Conn.	690	WAYZ	Waynesboro, Pa.	1380	WBUT	Butler, Pa.	1570	WCPH	Houston, Miss.	1320
WAEB	Allentown, Pa.	1490	WAZA	Bainbridge, Ga.	1360	WBUX	Doylestown, Pa.	1570	WCPH	Etowah, Tenn.	1220
WAEL	Mayaguez, P.R.	600	WAZF	Yazoo City, Miss.	1230	WBUX	Lexington, N.C.	1440	WCPK	College Park, Ga.	1570
WAEM	Crossville, Tenn.	1330	WAZL	Hazleton, Pa.	1490	WBUX	Fredonia, Pa.	1570	WCPM	Cumberland, Ky.	1260
WAFC	Staunton, Va.	900	WABA	West Lafayette, Ind.	920	WBVL	Bourbonville, Ky.	950	WCPO	Cincinnati, Ohio	1230
WAGC	Chattanooga, Tenn.	1450	WABC	Babylon, N.Y.	1440	WBVP	Beaver Falls, Pa.	1230	WCPS	Tarboro, N.C.	760
WAGE	Leesburg, Va.	1290	WABE	Cleveland, Tenn.	1340	WBVE	Calera, Ala.	1370	WCRA	Emphingham, Ill.	1090
WAGF	Dothan, Ala.	1320	WABF	Baltimore, Md.	1090	WBYS	Canton, Ill.	1500	WCRA	Waltham, Mass.	1330
WAGG	Franklin, Tenn.	950	WABM	Montgomery, Ala.	740	WBZ	Boston, Mass.	1030	WCRE	Cheraw, S.C.	1420
WAGM	Presque Isle, Maine	1450	WABN	Wichita, Tex.	570	WBZ	Springfield, Mass.	1030	WCRI	Scottsboro, Ala.	1050
WAGN	Memnonie, Mich.	1340	WBAR	Barton, Fla.	1420	WBZ	Torington, Conn.	980	WCRI	Horseshoe, Tenn.	1150
WAGR	Lumberton, N.C.	580	WBAT	Marion, Ind.	1400	WCAE	Pittsburgh, Pa.	1250	WCRI	Owensboro, Ky.	1570
WAGS	Bishopville, S.C.	1380	WBAW	Wilkes-Barre, Pa.	1240	WCAL	Northfield, Minn.	770	WCRO	Johnstown, Pa.	1230
WAGY	Forest City, N.C.	1320	WBAW	Barnwell, S.C.	740	WCAM	Camden, N.J.	1310	WCRR	Corinth, Miss.	1330
WAIK	Galesburg, Ill.	1590	WBAW	Green Bay, Wis.	1360	WCAP	Baltimore, Md.	900	WCRR	Greenwood, S.C.	1450
WAIL	Baton Rouge, La.	1460	WBBA	Pittsfield, Ill.	1580	WCAP	Lowell, Mass.	980	WCRT	Birmingham, Ala.	1260
WAIM	Anderson, S.C.	1230	WBBC	Burlington, N.C.	920	WCAR	Detroit, Mich.	1130	WCRT	Washington, N.J.	1580
WAIN	Columbia, S.C.	1270	WBFB	Rochester, N.Y.	950	WCAS	Gadsden, Ala.	570	WCRT	Chicago, Ill.	1240
WAIP	Pritchard, Ala.	1270	WBBI	Airport, Va.	1230	WCAT	Lexington, Mass.	1290	WCSC	Macon, Ga.	1900
WAIR	Winston-Salem, N.C.	1340	WBBL	Richmond, Va.	1480	WCAU	Philadelphia, Pa.	1210	WCSP	Portland, Maine	970
WAIT	Chicago, Ill.	820	WBMM	Chicago, Ill.	780	WCAX	Charleston, W.Va.	1300	WCSP	Portland, Maine	970
WAJF	Decatur, Ala.	1490	WBBN	Perry, Ga.	980	WCAX	Burlington, Vt.	620	WCSP	Indianapolis, Ind.	1010
WAJR	Morristown, W.Va.	1440	WBBO	Forest City, N.C.	780	WCAY	Cayce, S.C.	620	WCSP	Hillsdale, Mich.	1340
WAKE	Atlanta, Ga.	1340	WBQQ	Augusta, Ga.	1340	WCAY	Carthage, Ill.	1390	WCSS	Amsterdam, N.Y.	1490
WAKN	Alken, S.C.	990	WBRT	Lyons, Ga.	1340	WCBA	Corning, N.Y.	1470	WCST	Berkeley Springs, W.Va.	1010
WAKD	Lowmooch, Ill.	910	WBRT	Youngstown, Ohio	1240	WCBC	Anderson, Ind.	1470	WCST	New Brunswick, N.J.	920
WAKR	Akron, Ohio	1590	WBCT	Pataskala, Ohio	1460	WCBC	Chattanooga, Tenn.	580	WCCT	Corbin, Ky.	680
WAKU	Lafayette, Pa.	1570	WBCE	Bay Minette, Ala.	1150	WCBI	Columbus, Miss.	1290	WCCT	Manitowoc, Wis.	980
WAKY	Louisville, Ky.	790	WBCE	Levittown, Pa.	1490	WCBL	Benton, Ky.	1490	WCUE	Akron, Ohio	1150
WALA	Mobile, Ala.	1410	WBCH	Hastings, Mich.	1220	WCBM	Baltimore, Md.	680	WCUM	Cumberland, Md.	1230
WALB	Albany, Ga.	1590	WBCK	Battle Creek, Mich.	930	WCBS	Fremont, Mich.	1490	WCVA	Culpeper, Va.	1490
WALD	Waterboro, S.C.	1220	WBGM	Bay City, Mich.	1440	WCBS	New York, N.Y.	880	WCVI	Coneliasville, Pa.	1340
WALE	Fall River, Mass.	1400	WBCR	Christiansburg, Va.	1260	WCBT	Roanoke Rapids, N.C.	1240	WCVI	Greensboro, N.C.	1450
WALK	Patterson, N.Y.	1470	WBCS	Christfield, Mass.	1460	WCBY	Chesapeake, Mich.	1240	WCVI	Springfield, Ill.	1450
WALL	Middletown, N.Y.	1340	WBEC	Pittsfield, Mass.	1420	WCCL	Lawrence, Mass.	800	WCVS	Springfield, Ill.	1450
WALM	Albion, Mich.	1260	WBEE	Harvey, Ill.	1570	WCEN	Nellisville, Wis.	1370	WCVS	Ripon, Wis.	1600
WALD	Humacao, P.R.	1240	WBEE	Elizabethton, Tenn.	1240	WCEN	Minneapolis, Minn.	830	WCYB	Bristol, Va.	690
WALT	Tampa, Fla.	1110	WBEL	Beloit, Wis.	1380	WCEN	Savannah, Ga.	1450	WCYN	Cynthiana, Ky.	1400
WALY	Herkimer, N.Y.	1420	WBEN	Buffalo, N.Y.	930	WCEN	Savannah, Ga.	1450	WCYN	Cynthiana, Ky.	1400
WAMD	Aberdeen, Md.	970	WBET	Brockton, Mass.	1460	WCEN	Cambridge, Md.	1240	WCYN	Cynthiana, Ky.	1400
WAME	Miami, Fla.	1260	WBEU	Beaufort, S.C.	960	WCEN	Mt. Pleasant, Mich.	1150	WCYN	Cynthiana, Ky.	1400
WAMI	Opp, Ala.	850	WBFB	Wilmington, N.C.	1430	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAML	Laurel, Miss.	1340	WBFC	Chillicothe, Ohio	1410	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAMM	Flint, Mich.	1420	WBFD	Bedford, Pa.	1300	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAMD	Homestead, Pa.	860	WBGR	Chilpey, Fla.	1240	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAMP	Pittsburgh, Pa.	1320	WBGS	Jesup, Ga.	1370	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAMS	Wilmington, Del.	1380	WBHB	Fitzgerald, Ga.	1240	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAMY	E. St. Louis, Ill.	1480	WBHC	Hampden, S.C.	1270	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAMW	Washington, Ind.	1450	WBHF	Cartersville, Ga.	1450	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAMY	Amerus, Ky.	1480	WBHY	Windsor, Wis.	1230	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WANA	Anniston, Ala.	1490	WBIA	Austria, Ga.	1230	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WANB	Waynesburg, Pa.	1580	WBIE	Marletta, Ga.	1050	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAND	Canton, Ohio	900	WBIG	Greensboro, N.C.	1470	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WANE	Ft. Wayne, Ind.	1450	WBIL	Leesburg, Fla.	1410	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WANN	Annapolis, Md.	1190	WBIP	Booneville, Miss.	1400	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WANS	Anderson, S.C.	1280	WBIR	Knoxville, Tenn.	1240	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WANT	Richton, Miss.	990	WBIS	Clinton, Miss.	1440	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WANV	Albany, Ky.	1390	WBIV	Bedford, Ind.	1340	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAOK	Atlanta, Ga.	1380	WBIZ	Eau Claire, Wis.	1400	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WADV	Vincennes, Ind.	1450	WBKH	Hattiesburg, Miss.	950	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAPA	San Juan, P.R.	680	WBKN	Newton, Miss.	1470	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAPE	Jacksonville, Fla.	690	WBKV	West Bend, Wis.	1410	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAPF	McComb, Miss.	980	WBLA	Elizabethton, N.C.	1450	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAPG	Patuxent, Ala.	1070	WBLC	Celina, Miss.	1240	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAPI	Birmingham, Ala.	1070	WBLE	Bellevue, Pa.	1330	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAPL	Appleton, Wis.	1570	WBLL	Lexington, Ky.	1900	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAPD	Chattanooga, Tenn.	1150	WBLO	Dalton, Ga.	1230	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAPX	Montgomery, Ala.	1600	WBLO	Evergreen, Ala.	1470	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAQE	Towson, Md.	1570	WBLS	Batesburg, S.C.	1430	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARA	Attleboro, Mass.	1320	WBLS	Bedford, Va.	1350	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARB	Covington, La.	730	WBLS	Salem, Va.	1480	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARC	Altoona, Pa.	1490	WBLY	Windsor, Ohio	1600	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARE	Ware, Mass.	1250	WBNA	Beaufort, N.C.	1400	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARF	Jasper, Pa.	1240	WBNC	McMinville, Tenn.	960	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARK	Hagerstown, Md.	1490	WBND	Baltimore, Md.	750	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARR	Arlington, Va.	780	WBNE	West Point, Ga.	1310	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARR	Seranton, Pa.	590	WBNI	Macon, Ga.	1240	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARN	Ft. Pierce, Fla.	1330	WBNC	Conway, N.H.	1050	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WARO	Peru, Ind.	1600	WBND	Boonville, Ind.	1540	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WASA	Havre, Grace, Md.	1330	WBNS	Celina, Miss.	1240	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WASK	Lafayette, Ind.	1450	WBNT	Ontida, Tenn.	1410	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATA	Boone, N.C.	1400	WBNX	New York, N.Y.	1380	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATC	Gaylord, Mich.	950	WBNY	Buffalo, N.Y.	1400	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATE	Knoxville, Tenn.	620	WBOD	Galax, Va.	1360	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATH	Athens, Ohio	970	WBOS	Salisbury, Md.	960	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATK	Antigo, Wis.	900	WBOT	Virginia Beach, Va.	1600	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATM	Atlanta, Ga.	1230	WBOK	New Orleans, La.	800	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATN	Waterdown, N.Y.	1290	WBOS	Brookline, Mass.	1600	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATO	Oak Ridge, Tenn.	1290	WBOS	Terra Haute, Ind.	1290	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATP	Marion, S.C.	1430	WBOW	Bozalusa, La.	920	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATR	Waterbury, Conn.	1320	WBOW	Clarksburg, W.Va.	1400	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATS	Sayre, Pa.	960	WBPD	Orangeburg, S.C.	1580	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATT	Cadillac, Mich.	1240	WBPF	Lock Haven, Pa.	1230	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATW	Birmingham, Ala.	1490	WBPG	Lock Haven, Pa.	1230	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATX	Ashland, Miss.	1490	WBPH	Chickasaw, Miss.	1430	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WATZ	Alpena, Mich.	1450	WBRC	Birmingham, Ala.	960	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAUC	Wauchula, Fla.	1310	WBRO	Bradenton, Fla.	1420	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	1400
WAUD	Auburn, Ala.	1230	WBRE	Wilkes-Barre, Pa.	1340	WCEN	Charlotte, Mich.	1390	WCYN	Cynthiana, Ky.	

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WDOV	Dover, Del.	1410	WETZ	New Martinsville, West Virginia	1330	WGEE	Indianapolis, Ind.	1590	WHIM	E. Providence, R.I.	1110
WDOV	DuQuoin, Ill.	1580	WEUC	Ponce, P.R.	1420	WGEN	Quincy, Ill.	1440	WHIN	Gallatin, Tenn.	1010
WDRC	Hartford, Conn.	1360	WEUP	Huntsville, Ala.	1600	WGES	Chicago, Ill.	1390	WHIO	Dighton, Ohio	1290
WDRF	Chester, Pa.	1590	WEVD	Emporia, Va.	860	WGET	Gettysburg, Pa.	1450	WHIP	Moorestville, N.C.	1350
WDSC	Dillon, S.C.	800	WEVE	New York, N.Y.	1330	WGEZ	Beloit, Wis.	1490	WHIR	Danville, Ky.	1230
WDSG	Dyersburg, Tenn.	1450	WEVW	Eveleveth, Minn.	1340	WGFS	Covington, Ga.	1430	WHIS	Bluefield, W.Va.	1440
WDSK	Cleveland, Miss.	740	WEVY	St. Louis, Mo.	770	WGGA	Gainesville, Ga.	550	WHIT	New Bern, N.C.	1450
WDSM	Superior, Wis.	1110	WEWJ	Laurin, N.C.	1080	WGGG	Gainesville, Fla.	1230	WHIY	Orlando, Fla.	1270
WDSP	DeFuniak Springs, Florida	1280	WEXL	Royal Oak, Mich.	1340	WGH	Marion, Ill.	1150	WHJB	Zanesville, Ohio	1240
WDSR	Lake City, Fla.	1340	WEYF	Sanford, N.C.	1290	WGH	Salamancan, N.Y.	1310	WHJC	Greensburg, Pa.	620
WDSU	New Orleans, La.	1190	WEZB	Bessemer, Ala.	1450	WGHM	Newport News, Va.	1310	WHIC	Waco, Tex.	1360
WDTV	St. John, V.I.	1280	WEZE	Boston, Mass.	1260	WGHM	Skowegan, Maine	1150	WHLD	Cleveland, Ohio	1420
WDUN	Gainesville, Ga.	1200	WEZZ	Williamsburg, Ky.	1440	WGHN	Grd. Haven, Mich.	1370	WHLE	Hempstead, N.Y.	1160
WDUX	Waupaca, Wis.	840	WEZZ	Richmond, Va.	1590	WGHQ	Sauperties, N.Y.	920	WHKK	Akron, Ohio	640
WDUZ	Green Bay, Wis.	1400	WEZZ	Elizabethtown, Pa.	1600	WGHQ	Brunswick, N.Y.	1440	WHKP	Hendersonville, N.C.	1450
WDVA	Danville, Va.	1250	WEZZ	Coon, Fla.	1450	WGHG	Galesburg, N.H.	1400	WHKY	Hickory, N.C.	1290
WDVH	Gainesville, Fla.	1480	WEZZ	Dallas, Tex.	570, 820	WGHG	Charlottesville, N.C.	1600	WHLB	Niagara Falls, N.Y.	1270
WDVL	Vincland, N.J.	1270	WFAC	Alliance, Ohio	1310	WGHK	Atlanta, Ga.	1600	WHLL	South Boston, Va.	1400
WDM	Pocomoke City, Md.	540	WFAR	Farrall, Pa.	1470	WGHK	Charleston, W.Va.	1300	WHLM	Wheeling, W.Va.	1600
WDWD	Dawson, Ga.	990	WFAS	White Plains, N.Y.	1230	WGL	Fort Wayne, Ind.	1250	WHLN	Blommsburg, Pa.	550
WDWS	Champaign, Ill.	1400	WFAU	Augusta, Me.	1340	WGLC	Centerville, Miss.	1580	WHLO	Harlan, Ky.	1410
WDXB	Chattanooga, Tenn.	1470	WFAX	Falls Church, Va.	1220	WGLI	Babylon, N.Y.	1290	WHLP	Centerville, Tenn.	1570
WDXE	Lawrenceburg, Tenn.	1390	WFBC	Greenville, S.C.	1330	WGLM	Hollywood, Fla.	1320	WHLS	Port Huron, Mich.	1450
WDXI	Jackson, Tenn.	1350	WFBC	Altoona, Pa.	1390	WGLM	Washington, D.C.	570	WHLT	Huntington, Ind.	1300
WDXL	Lexington, Tenn.	1490	WFBL	Syracuse, N.Y.	1490	WGLM	Chicago, Ill.	720	WHMA	Anniston, Ala.	1390
WDXN	Clarksville, Tenn.	540	WFBM	Indianapolis, Ind.	1260	WGLM	Wilmington, N.C.	1450	WHMB	Northampton, Mass.	1400
WDXR	Paducah, Ky.	1560	WFBR	Baltimore, Md.	1300	WGLM	Murfreesboro, Tenn.	1450	WHMP	Charleston, W.Va.	1490
WDXZ	Decatur, Ill.	1050	WFBZ	Ft. Walton Bch., Fla.	950	WGN	Newburgh, N.Y.	1220	WHMS	Henderson, N.C.	890
WEAB	Greer, S.C.	800	WFDF	Flint, Mich.	910	WGO	Walhalla, S.C.	1460	WHNC	McComb, Miss.	1250
WEAG	Alcoa, Tenn.	1470	WFDR	Manchester, Ga.	1370	WGOH	Grayson, Ky.	1370	WHND	Des Moines, Iowa	1040
WEAN	Arlington, Va.	1390	WFDT	St. Helen, Mich.	1590	WGOH	Goldsboro, N.C.	1300	WHOA	San Juan, P.R.	1400
WEAN	Providence, R.I.	1350	WFEE	Manchester, N.Y.	1340	WGOH	Georgetown, Ky.	1580	WHOC	Philadelphia, Miss.	1490
WEAQ	Eau Claire, Wis.	790	WFEB	Sylacauga, Ala.	1220	WGOV	Valdosta, Ga.	950	WHOD	Hempstead, Ohio	600
WEAT	W. Palm Beach, Fla.	860	WFEC	Miami, Fla.	1220	WGOV	Walpole, Pa.	1100	WHOM	New York, N.Y.	1480
WEAV	Plattsburg, N.Y.	950	WFGM	Fitchburg, Mass.	960	WGPC	Albany, Ga.	1450	WHOO	Orlando, Fla.	990
WEAW	Evanson, Ill.	1330	WFGN	Gaffney, S.C.	1570	WGR	Calro, Ga.	790	WHOP	Hopkinsville, Ky.	1230
WEBB	Baltimore, Md.	1360	WFHG	Bristol, Va.	980	WGR	Green Cove Springs, Fla.	1580	WHOS	Decatur, Ala.	800
WEBC	Duluth, Minn.	560	WFHK	Ellet City, Ala.	1430	WGR	Grand Rapids, Mich.	1410	WHDT	Campbell, Ohio	1570
WEBJ	Brewton, Ala.	1240	WFHR	W. Va. Springs, W.Va.	1340	WGRF	Agua delia, P.R.	340	WHDU	Union, Maine	1340
WEBO	Owensboro, Ky.	1240	WFHS	Sumter, S.C.	1290	WGRM	Greenwood, Miss.	1240	WHOW	Clinton, Pa.	580
WEBO	Harrisburg, Ill.	1240	WFIL	Philadelphia, Pa.	560	WGRM	Lake City, Fla.	1260	WHPP	Harrisburg, Pa.	580
WEBR	Buffalo, N.Y.	970	WFIN	Findlay, Ohio	1330	WGRV	Greenville, Tenn.	1340	WHPE	High Point, N.C.	1070
WEBS	Milton, Fla.	1330	WFIS	Fountain Inn, S.C.	1600	WGRY	Kearny, Ind.	1370	WHRT	Hartselle, Ala.	860
WECL	Eau Claire, Wis.	1050	WFIV	Fairfield, Ill.	1390	WGSA	Savannah, Ga.	1400	WHRV	Ann Arbor, Mich.	1600
WEDC	Chicago, Ill.	1240	WFKN	Franklin, Ky.	1220	WGSM	Huntington, N.Y.	740	WHRW	Bowling Green, Ohio	730
WEDO	McKeesport, Pa.	810	WFKY	Franklin, Ky.	970	WGSB	Millen, Ga.	1260	WHSC	Hartsville, S.C.	1420
WEDR	Birmingham, Ala.	1220	WFLA	Tampa, Fla.	970	WGST	Atlanta, Ga.	920	WHSN	Hayward, Wis.	910
WEDS	Southern Pines, N.C.	980	WFLB	Fayetteville, N.C.	1490	WGST	Guntersville, Ala.	1270	WHSS	Hattiesburg, Miss.	1230
WEEK	Boston, Mass.	590	WFLN	Philadelphia, Pa.	900	WGSW	Greenwood, S.C.	1350	WHTC	Holland, Mich.	1410
WEEK	Peoria, Ill.	1350	WFLR	Dundee, N.Y.	1570	WGTA	Summerville, Ga.	950	WHUD	Eatontown, N.J.	1450
WEEL	Fairfax, Va.	1310	WFLW	Mt. Airy, N.C.	730	WGTC	Greenville, N.C.	1590	WHUC	Cookeville, Tenn.	1400
WEEN	Lafayette, Tenn.	1460	WFLM	Goldsboro, N.C.	930	WGTL	Kannapolis, N.C.	870	WHUB	Hudson, N.Y.	1230
WEPP	Pittsburgh, Pa.	1080	WFM	Frederick, Md.	1460	WGTM	Wilson, N.C.	590	WHUM	Reading, Pa.	1150
WEER	Warrenton, Va.	1570	WFMM	Cullman, Ala.	1480	WGTM	York, S.C.	1450	WHUN	Washington, Pa.	1240
WEU	Reading, Pa.	850	WFMJ	Youngstown, Ohio	1390	WGTD	Georgetown, S.C.	1450	WHVF	Wausau, Wis.	1230
WEEX	Easton, Pa.	1490	WFMO	Fairmont, N.C.	860	WGUN	Cypress Gardens, Fla.	540	WHVH	Henderson, N.C.	1450
WEGD	Concord, N.C.	1410	WFMW	Madisonville, Ky.	730	WGUS	North Augusta, S.C.	1600	WHVR	Hanover, Pa.	1280
WEHH	Elmira Heights, Horseheads, N.Y.	1590	WFNC	Fayetteville, N.C.	1130	WGUY	Bangor, Maine	1250	WHWB	Rutland, Vt.	1000
WEIC	Charleston, Ill.	1270	WFNS	Burlington, N.C.	1150	WGYA	Geneva, N.Y.	1240	WHY	Roanoke, Va.	910
WEIM	Fitchburg, Mass.	1280	WFNB	Fosters, Ohio	1430	WGYM	Greenville, Miss.	1260	WHYL	Carlisle, Pa.	960
WEIN	Weirton, W.Va.	1430	WFOD	Marletta, Ga.	1230	WGW	Selma, Ala.	1450	WHYN	Springfield, Mass.	560
WEJL	Seranton, Pa.	630	WFOM	Hattiesburg, Miss.	1400	WGW	Asheboro, N.C.	1260	WHYR	Seale, Va.	570
WEKR	Fayetteville, Tenn.	1490	WFOS	St. Augustine, Fla.	1260	WGY	Schenectady, N.Y.	810	WIAC	Williamston, S.C.	1380
WEKY	Richmond, Ky.	1470	WFPA	Port Payne, Ala.	1450	WGYV	Greenville, Ala.	1380	WIAM	Williamston, N.C.	900
WEKZ	Monroe, Wis.	1260	WFGP	Atlantic City, N.J.	1400	WHA	Madison, Wis.	970	WIBA	Madison, Wis.	1310
WELB	Elba, Ala.	1350	WFGM	Fort Valley, Ga.	1150	WHAB	Baxley, Ga.	1260	WIBB	Macon, Ga.	1280
WELC	Welch, W.Va.	1150	WFPA	Hammer, La.	1400	WHAK	Greenfield, Mass.	1240	WIBG	Indianapolis, Ind.	1070
WELD	Fisher, W.Va.	890	WFRA	Franklin, Pa.	1430	WHAK	Rogers City, Mich.	960	WIBC	Philadelphia, Pa.	990
WELS	S. Dayton, Ga.	1590	WFRB	Frostburg, Md.	740	WHAL	Shelbyville, Tenn.	1400	WIBM	Jackson, Mich.	1450
WELI	New Haven, Conn.	1390	WFRD	Reidsville, N.C.	1600	WHAM	Rochester, N.Y.	1180	WIBR	Birmingham, Ala.	1300
WELK	Charlottesville, Va.	1010	WFRL	Frederick, Pa.	1570	WHAP	Hopewell, Va.	1340	WIBY	Poyette, W.Va.	1240
WELL	Battle Creek, Mich.	1410	WFRM	Coopersport, Pa.	900	WHAR	Clarksburg, W.Va.	1340	WIBV	Belleville, Ill.	1260
WELM	Elmira, N.Y.	1400	WFRP	Franklin, Ohio	1050	WHAS	Louisville, Ky.	840	WIBW	Topeka, Kans.	580
WELU	Tupelo, Miss.	580	WFRS	Frederick, Md.	1430	WHAT	Philadelphia, Pa.	1340	WIBX	Utica, N.Y.	950
WELP	Easley, S.C.	1360	WFSC	Caribou, Maine	660	WHAY	Haverhill, Mass.	1490	WIBY	Ashtabula, Ohio	970
WELR	Roanoke, Ala.	1360	WFST	Clinton, N.C.	960	WHAZ	Weston, Conn.	980	WICE	Bridgeport, Conn.	600
WELS	Kinston, N.C.	1010	WFTC	Kinston, N.C.	960	WHB	Troy, Va.	1330	WIC	Providence, R.I.	1290
WELY	Ely, Minn.	450	WFTG	London, Ky.	1400	WHB	Kansas City, Mo.	710	WICB	Seranton, Pa.	1400
WELZ	Belzoni, Miss.	1460	WFTL	Ft. Lauderdale, Fla.	1400	WHB	Selma, Ala.	1490	WICK	Salisbury, Md.	1320
WEMB	Erwin, Tenn.	1420	WFTN	Maysville, Ky.	1240	WHBC	Canton, Ohio	1480	WICU	Erle, Pa.	1330
WEMP	Millwaukee, Wis.	1250	WFTS	Front Royal, Va.	1450	WHBF	Rock Island, Ill.	1270	WICV	Malone, N.Y.	1490
WENA	Bayamon, P.R.	1560	WFTW	Ft. Walton Beach, Florida	1260	WHBG	Harrisonburg, Va.	1360	WIDE	Bliddeford, Maine	1400
WENC	Whiteville, N.C.	1220	WFUL	Fulton, Ky.	1270	WHBI	Newark, N.J.	1280	WIE	Fayetteville, N.C.	1600
WEND	Baton Rouge, La.	1380	WFUN	Huntsville, Ala.	1450	WHBJ	Shelbyville, Tenn.	1330	WIE	Elizabethtown, Pa.	1400
WENE	Endon, N.Y.	1430	WFUR	Grand Rapids, Mich.	1570	WHBN	Harrisburg, Ky.	1420	WIG	Clinton, Mo.	1340
WENK	Union City, Tenn.	1240	WFVA	Fredericksburg, Va.	1230	WHBO	Tampa, Fla.	1070	WIGM	Medford, Wis.	1490
WENN	Homewood, Ala.	1320	WFW	Fuquay Sprgs., N.C.	1450	WHBQ	Memphis, Tenn.	560	WIIN	Atlanta, Ga.	970
WEND	Madison, Tenn.	1430	WFWL	Hammer, Tenn.	1400	WHBT	Harrison, Tenn.	1600	WIKB	Iron River, Mich.	1230
WENT	Gloversville, N.Y.	1340	WFYC	Aimea, Mich.	1280	WHBU	Anderson, Ind.	1340	WIKC	Bogalusa, La.	1490
WENY	Elmira, N.Y.	1230	WFYI	Mineola, N.Y.	1520	WHBY	Appleton, Wis.	1230	WIKY	Newport, Vt.	1490
WEOA	Evanhville, Ind.	1490	WGAA	Cedartown, Ga.	1340	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WEOK	Poughkeepsie, N.Y.	1390	WGAC	Augusta, Ga.	580	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WEOL	Elyria, Ohio	930	WGAD	Gadsden, Ala.	1350	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WEPG	S. Pittsburgh, Tenn.	910	WGAE	Elizabeth City, N.C.	910	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WEPM	Martinsburg, W.Va.	1340	WGAL	Lancaster, Pa.	1490	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WERC	Erle, Pa.	1260	WGAN	Portland, Maine	560	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WERD	Atlanta, Ga.	860	WGAP	Marville, Tenn.	1400	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WERE	Cleveland, Ohio	1300	WGAR	Cleveland, Ohio	1220	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WERH	Hamilton, Ala.	970	WGAS	S. Gastonia, N.C.	1020	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WERI	Westerly, R.I.	1230	WGAT	Gate City, Va.	1050	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WERT	Van Alstyne, Ohio	1220	WGAU	Wheaton, Pa.	1340	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WESA	Charleroi, Pa.	940	WGAW	Gardner, Mass.	1340	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WESB	Brauford, Pa.	1490	WGAY	Silver Spring, Md.	1050	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WESC	Greenville, S.C.	660	WGBA	Columbus, Ga.	1270	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WESD	Southbridge, Mass.	970	WGBB	Freeport, N.Y.	1240	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WESR	Tasley, Va.	1330	WGBF	Evansville, Ind.	1200	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WEST	Easton, Pa.	1400	WGBG	Greensboro, N.C.	1480	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WESX	Salem, Mass.	1230	WGBI	Wheaton, Pa.	1340	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WET	Wetumpka, Ala.	1250	WGBR	Goldsboro, N.C.	910	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WETA	Wetumpka, Ala.	1250	WGBS	Miami, Fla.	710	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WETD	Gadsden, Ala.	930	WGBL	Red Lion, Pa.	1440	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
WETU	Wetumpka, Ala.	1250	WGBD	Chesler, S.C.	1490	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
			WGBE	Gulfport, Miss.	1240	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400
			WGBF	Geneva, Ala.	1150	WHBY	Appleton, Wis.	1230	WIKY	Evansville, Ind.	1400

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WINK	Fort Myers, Fla.	1240	WJPS	Evansville, Ind.	1330	WKWF	Key West, Fla.	1600	WMBG	Richmond, Va.	1380
WINN	Louisville, Ky.	1240	WJQJ	Jackson, Miss.	1400	WKWK	Wheeling, W.Va.	1400	WMBH	Joplin, Mo.	1450
WINR	Tampa, Fla.	1010	WJR	Detroit, Mich.	760	WKXL	Concord, N.H.	1400	WMBI	Chicago, Ill.	1110
WING	Binghamton, N.Y.	680	WJR	Tuscaloosa, Ala.	1150	WKXV	Knoxville, Tenn.	950	WMBL	Morehead City, N.C.	740
WINS	New York, N.Y.	1010	WJRI	Lenoir, N.C.	1030	WKXY	Sarasota, Fla.	930	WMBN	Miami Beach, Fla.	800
WINT	Winter Haven, Fla.	1360	WJSB	Crestview, Fla.	1050	WKYB	Oklahoma City, Okla.	950	WMBP	Petalosky, Mich.	1340
WINX	Rockville, Md.	1600	WJSD	Jonesboro, Tenn.	1590	WKYB	Paducah, Ky.	1240	WMBR	Jacksonville, Fla.	1460
WINZ	Miami, Fla.	940	WJTB	Atlanta, N.Y.	1220	WKYV	Kaysers, W.Va.	1270	WMBT	Uniontown, Pa.	590
WIO	Sanford, Fla.	1360	WJUN	Mexico, Pa.	1220	WKZD	Kalamazoo, Mich.	590	WMC	Memphis, Tenn.	570
WION	Ionia, Mich.	1430	WJVA	South Bend, Ind.	1580	WLAC	Nashville, Tenn.	1510	WMCA	New York, N.Y.	750
WIDS	Tawas City, Mich.	1490	WJWC	Cleveland, Ohio	850	WLAD	Danbury, Conn.	800	WMCH	Church Hill, Tenn.	1260
WIGU	Kokomo, Ind.	1350	WJWL	Georgetown, Del.	900	WLAF	LaFollette, Tenn.	1450	WMCK	McKeesport, Pa.	1360
WIP	Philadelphia, Pa.	610	WJWS	South Hill, Va.	1370	WLAK	La Grange, Ga.	1240	WMCO	Harvard, Ill.	1600
WIPR	Lake Wales, Fla.	1280	WJXN	Jackson, Miss.	1450	WLAL	Lakeland, Fla.	1430	WMDC	Hazletch, Miss.	1270
WIPR	San Juan, P.R.	940	WJZN	Clarksville, Tenn.	1400	WLAM	Lakeston, Mdne	1470	WMDF	Mount Dora, Fla.	1580
WIPS	Ticonderoga, N.Y.	1250	WKAB	Hot Springs, Ark.	840	WLAN	Lancaster, Pa.	1390	WDM	Midland, Mich.	1490
WIRA	Fort Pierce, Fla.	1400	WKAL	Macomb, Ill.	1510	WLAP	Lancaster, Ky.	630	WDMG	Eau Gallie, Fla.	920
WIRB	Enterprise, Ala.	600	WKAL	Rome, N.Y.	1450	WLAR	Rome, Ga.	1410	WMEK	Chase City, Va.	980
WIRC	Hickory, N.C.	630	WKAM	Goshen, Ind.	1460	WLAT	Conway, S.C.	1300	WMEN	Tallahassee, Fla.	1330
WIRE	Indianapolis, Ind.	1430	WKAN	Kankakee, Ill.	1320	WLAU	Laurel, Miss.	1600	WMET	Miami Beach, Fla.	1490
WIRJ	Humboldt, Tenn.	740	WKAP	Allentown, Pa.	1320	WLAV	Grand Rapids, Mich.	1340	WMFY	Marion, Va.	1010
WIRK	W. Palm Beach, Fla.	1290	WKAQ	San Juan, P.R.	580	WLAW	Lawrenceville, Ga.	1360	WMFX	Boston, Mass.	1310
WIRL	Peoria, Ill.	1230	WKAR	East Lansing, Mich.	870	WLBY	Blue Springs, Mo.	1450	WMFG	New York, N.Y.	1350
WIRO	Ironton, Ohio	1290	WKAT	Miami Beach, Fla.	1360	WLBB	Carrollton, Ga.	1100	WMFH	Hibbing, Minn.	1240
WIRY	Plattsburg, N.Y.	1450	WKAT	Hot Springs, Ark.	840	WLBC	Muncie, Ind.	1340	WMFJ	Daytona Beach, Fla.	1450
WIS	Columbus, Miss.	560	WKAZ	Charleston, W.Va.	950	WLBE	Leesburg, Fla.	790	WMFG	High Point, N.C.	1230
WISE	Asheville, N.C.	1310	WKB	N. Wilkesboro, N.C.	810	WLBG	Laurens, S.C.	860	WMF	Chattanooga, Tenn.	1260
WISL	Indianapolis, Ind.	1310	WKBH	La Crosse, Wis.	1410	WLBI	Mattoon, Ill.	1170	WMF	Terre Haute, Ind.	1500
WISH	Shamokin, Pa.	1480	WKB	St. Mary's, Pa.	1400	WLBJ	Denham Springs, La.	1220	WMGA	Moultrie, Ga.	1400
WISM	Madison, Wis.	1480	WKB	Millan, Tenn.	1600	WLBJ	Bowling Green, Ky.	1410	WMGN	New York, N.Y.	1050
WISN	Milwaukee, Wis.	1150	WKBK	Keene, N.H.	1220	WLBR	Bangor, Maine	1360	WMGR	Bainbridge, Ga.	930
WISD	Ponce, P.R.	1260	WKB	Covington, Tenn.	1250	WLBU	Auburndale, Wis.	930	WMGW	Meadville, Pa.	1490
WISR	Kinston, N.C.	1230	WKB	Youngstown, Ohio	520	WLBY	Lebanon, Ky.	1590	WMGY	Montgomery, Ala.	800
WISB	Butler, Pa.	1380	WKB	Harrisburg, Pa.	1230	WLBY	Lebanon, Pa.	1270	WMIC	St. Helen, Mich.	1590
WIST	Charlotte, N.C.	930	WKB	Manchester, N.H.	1240	WLBY	Bangor, Maine	620	WMID	Atlantic City, N.J.	1340
WISV	Virouqua, Wis.	1360	WKBV	Richmond, Ind.	1490	WLBY	Lebanon, Pa.	1270	WMIE	Miami, Fla.	1140
WITA	San Juan, P.R.	1140	WKB	Buffalo, N. Y.	1520	WLBY	Lebanon, Pa.	1270	WMIF	Middleboro, Ky.	560
WITB	Baltimore, Md.	1230	WKB	Kissimmee, Fla.	1220	WLBY	Bangor, Maine	620	WMIL	Milwaukee, Wis.	1290
WITC	Lewinsburg, Pa.	1010	WKB	Muskegon, Mich.	850	WLBY	Lebanon, Pa.	1270	WMIN	Mpls. St. Paul, Minn.	1400
WITZ	Danville, Ill.	980	WKB	Berlin, N.H.	1230	WLBY	Lebanon, Pa.	1270	WMIO	Iron Mountain, Mich.	1450
WITZ	Jasper, Ind.	890	WKB	Bowling Green, Ky.	520	WLBY	Lebanon, Pa.	1270	WMIS	Natchez, Miss.	1240
WIX	Christiansburg, Va.	1010	WKDA	Nashville, Tenn.	1240	WLBY	Lebanon, Pa.	1270	WMIX	St. Vernon, Ill.	940
WIX	Knoxville, Tenn.	860	WKDA	Newberry, S.C.	1240	WLBY	Lebanon, Pa.	1270	WMJF	Cordele, Ga.	1490
WIV	Vaquos, P.R.	1370	WKDC	Clarkdale, Miss.	800	WLBY	Lebanon, Pa.	1270	WMJL	Pineville, Ky.	1230
WIVY	Jacksonville, Fla.	1050	WKDC	Camden, N.J.	1600	WLBY	Lebanon, Pa.	1270	WMML	Milton, Pa.	1570
WIZE	Springfield, Ohio	1340	WKDC	Hamlet, N.C.	1400	WLBY	Lebanon, Pa.	1270	WMNL	Waukegan, Ill.	1290
WIZZ	Streator, Ill.	1250	WKE	Huntington, W. Va.	800	WLBY	Lebanon, Pa.	1270	WMNU	Urbain, Ga.	1430
WJAC	Johnstown, Pa.	1400	WKE	Keewanee, Ill.	1450	WLBY	Lebanon, Pa.	1270	WMNV	Milville, N.J.	1440
WJAG	Norfolk, Nebr.	780	WKE	Bower, Del.	1600	WLBY	Lebanon, Pa.	1270	WMNB	Melbourne, Fla.	1240
WJAK	Jackson, Tenn.	1460	WKE	Griffin, Ga.	1450	WLBY	Lebanon, Pa.	1270	WMNH	Marshall, N.C.	1460
WJAM	Marion, Ala.	1310	WKE	Covington, Va.	1340	WLBY	Lebanon, Pa.	1270	WMNI	Fairmont, W.Va.	920
WJAN	Ishpeming, Mich.	970	WKE	Knoxville, Tenn.	1340	WLBY	Lebanon, Pa.	1270	WMNJ	Bath, Maine	730
WJAR	Providence, R.I.	920	WKM	Hazard, Ky.	1390	WLBY	Lebanon, Pa.	1270	WMNT	McMinville, Tenn.	1290
WJAS	Pittsburgh, Pa.	1320	WKID	Urbana, Ill.	1580	WLBY	Lebanon, Pa.	1270	WMNW	Glean, N.Y.	850
WJAT	Swainsboro, Ga.	800	WKIK	Leardstown, Md.	1370	WLBY	Lebanon, Pa.	1270	WMOD	Moundsville, W.Va.	1370
WJAX	Jacksonville, Fla.	930	WKIN	Kingsport, Tenn.	1320	WLBY	Lebanon, Pa.	1270	WMOG	Brunswick, Ga.	1490
WJAY	Mullins, S.C.	1280	WKIP	Poughkeepsie, N.Y.	1450	WLBY	Lebanon, Pa.	1270	WMOH	Hamilton, Ohio	1450
WJAZ	Albany, Ga.	1460	WKIS	Orlando, Fla.	740	WLBY	Lebanon, Pa.	1270	WMOK	Metropolis, Ill.	920
WJBC	Halesite, Ala.	1230	WKIS	Raleigh, N.C.	850	WLBY	Lebanon, Pa.	1270	WMON	Montgomery, W.Va.	1340
WJBD	Bloomington, Ill.	1230	WKIZ	Key West, Fla.	1500	WLBY	Lebanon, Pa.	1270	WMOP	Ocala, Fla.	900
WJBE	Salem, Ill.	1350	WKJB	Mayaque, P.R.	710	WLBY	Lebanon, Pa.	1270	WMOR	Marion, Ohio	1490
WJBF	Detroit, Mich.	1500	WKJF	Fort Wayne, Ind.	1380	WLBY	Lebanon, Pa.	1270	WMOS	Moundsville, W.Va.	1370
WJBL	Holland, Mich.	1260	WKLC	Cocoa, Fla.	860	WLBY	Lebanon, Pa.	1270	WMOT	Brunswick, Ga.	1490
WJBO	Baton Rouge, La.	1150	WKLD	Ludington, Mich.	1450	WLBY	Lebanon, Pa.	1270	WMOH	Hamilton, Ohio	1450
WJBS	DeLand, Fla.	1490	WKLE	Washington, Ga.	1370	WLBY	Lebanon, Pa.	1270	WMOK	Metropolis, Ill.	920
WJBW	New Orleans, La.	1230	WKLF	Clanton, Ala.	980	WLBY	Lebanon, Pa.	1270	WMON	Montgomery, W.Va.	1340
WJCD	Seymour, Ind.	1390	WKLK	Cloquet, Minn.	1230	WLBY	Lebanon, Pa.	1270	WMOP	Ocala, Fla.	900
WJCM	Sebrina, Ind.	960	WKLM	Winnington, N.C.	980	WLBY	Lebanon, Pa.	1270	WMOR	Marion, Ohio	1490
WJDA	Quincy, Mass.	1300	WKLO	Louisville, Ky.	1080	WLBY	Lebanon, Pa.	1270	WMOS	Moundsville, W.Va.	1370
WJDB	Thomasville, Ala.	630	WKLV	Lebanon, Va.	1440	WLBY	Lebanon, Pa.	1270	WMOT	Brunswick, Ga.	1490
WJDX	Jackson, Miss.	620	WKLY	Park, Ky.	1440	WLBY	Lebanon, Pa.	1270	WMOH	Hamilton, Ohio	1450
WJDY	Salisbury, Md.	1470	WKLY	Hartwell, Ga.	980	WLBY	Lebanon, Pa.	1270	WMOK	Metropolis, Ill.	920
WJEF	Grand Rapids, Mich.	1230	WKLZ	Kalamazoo, Mich.	1470	WLBY	Lebanon, Pa.	1270	WMON	Montgomery, W.Va.	1340
WJEM	Gallatin, Miss.	910	WKMC	Royal Springs, Pa.	1370	WLBY	Lebanon, Pa.	1270	WMOP	Ocala, Fla.	900
WJEN	Hagerstown, Md.	1240	WKMF	Flint, Mich.	1470	WLBY	Lebanon, Pa.	1270	WMOR	Marion, Ohio	1490
WJEM	Valdosta, Ga.	1150	WKMH	Dearborn, Mich.	1310	WLBY	Lebanon, Pa.	1270	WMOS	Moundsville, W.Va.	1370
WJER	Dover, Ohio	1450	WKMI	Minneapolis, Minn.	1330	WLBY	Lebanon, Pa.	1270	WMOT	Brunswick, Ga.	1490
WJET	Erie, Pa.	1400	WKML	King, Minn.	1220	WLBY	Lebanon, Pa.	1270	WMOH	Hamilton, Ohio	1450
WJGD	Columbia, Tenn.	1280	WKMN	New Britain, Conn.	840	WLBY	Lebanon, Pa.	1270	WMOK	Metropolis, Ill.	920
WJHB	Talladega, Ala.	1580	WKNE	Keene, N.H.	1290	WLBY	Lebanon, Pa.	1270	WMON	Montgomery, W.Va.	1340
WJHC	Johnston City, Tenn.	910	WKNX	Saginaw, Mich.	1210	WLBY	Lebanon, Pa.	1270	WMOP	Ocala, Fla.	900
WJHO	Orehta, N.C.	1400	WKNY	Kingston, N.Y.	1490	WLBY	Lebanon, Pa.	1270	WMOR	Marion, Ohio	1490
WJIG	Tullahoma, Tenn.	740	WKOP	Hopkinston, Ky.	1480	WLBY	Lebanon, Pa.	1270	WMOS	Moundsville, W.Va.	1370
WJIM	Lansing, Mich.	1240	WKOP	Kingsport, Pa.	1240	WLBY	Lebanon, Pa.	1270	WMOT	Brunswick, Ga.	1490
WJIV	Savannah, Ga.	900	WKOP	Binghamton, N.Y.	1360	WLBY	Lebanon, Pa.	1270	WMOH	Hamilton, Ohio	1450
WJJC	Commerce, Ga.	1270	WKOW	Wellston, Ohio	1330	WLBY	Lebanon, Pa.	1270	WMOK	Metropolis, Ill.	920
WJJD	Chicago, Ill.	1160	WKOW	Madison, Wis.	1070	WLBY	Lebanon, Pa.	1270	WMON	Montgomery, W.Va.	1340
WJJE	Niagara Falls, N.Y.	1160	WKOX	Framingham, Mass.	1190	WLBY	Lebanon, Pa.	1270	WMOP	Ocala, Fla.	900
WJJK	Lewinsburg, Tenn.	1490	WKOY	Bluefield, W.Va.	1240	WLBY	Lebanon, Pa.	1270	WMOR	Marion, Ohio	1490
WJKO	Springfield, Mass.	1600	WKOZ	Kosciusko, Miss.	1350	WLBY	Lebanon, Pa.	1270	WMOS	Moundsville, W.Va.	1370
WJLB	Detroit, Mich.	1400	WKPA	New Kensington, Pa.	1150	WLBY	Lebanon, Pa.	1270	WMOT	Brunswick, Ga.	1490
WJLD	Homewood, Ala.	1400	WKRC	Cincinnati, Ohio	550	WLBY	Lebanon, Pa.	1270	WMOH	Hamilton, Ohio	1450
WJLK	Asbury Park, N.J.	1310	WKRR	Murphy, N.C.	1390	WLBY	Lebanon, Pa.	1270	WMOK	Metropolis, Ill.	920
WJLS	Beckley, W.Va.	560	WKRG	Mobile, Ala.	710	WLBY	Lebanon, Pa.	1270	WMON	Montgomery, W.Va.	1340
WJMA	Orange, Va.	1340	WKRM	Columbia, Tenn.	1340	WLBY	Lebanon, Pa.	1270	WMOP	Ocala, Fla.	900
WJMB	Brooklyn, Miss.	920	WKRO	Cairo, Ill.	1490	WLBY	Lebanon, Pa.	1270	WMOR	Marion, Ohio	1490
WJMC	Rice Lake, Wis.	1240	WKRS	Waukegan, Ill.	1220	WLBY	Lebanon, Pa.	1270	WMOS	Moundsville, W.Va.	1370
WJMJ	Philadelphia, Pa.	1540	WKRT	Cortland, N.Y.	920	WLBY	Lebanon, Pa.	1270	WMOT	Brunswick, Ga.	1490
WJMO	Cleveland Hgts., Ohio	1490	WKRT	York, Pa.	1340	WLBY	Lebanon, Pa.	1270	WMOH	Hamilton, Ohio	1450
WJMR	New Orleans, La.	990	WKSB	Milford, Del.	930	WLBY	Lebanon, Pa.	1270	WMOK	Metropolis, Ill.	920
WJMS	Ironwood, Mich.	630	WKSK	W. Jefferson, N.C.	1600	WLBY	Lebanon, Pa.	1270	WMON	Montgomery, W.Va.	1340
WJMX	Athens, Ala.	730	WKSR	Pulaski, Tenn.	1420	WLBY	Lebanon, Pa.	1270	WMOP	Ocala, Fla.	900
WJMK	Florence, S.C.	970	WKST	New Castle, Pa.	1280	WLBY	Lebanon, Pa.	1270	WMOR	Marion, Ohio	1490
WJNC	Jacksonville, N.C.	910	WKTC	Charlotte, N.C.	1310	WLBY	Lebanon, Pa.	1270	WMOS	Moundsville, W.Va.	1370
WJNO	W. Palm Beach, Fla.	1230	WKTF	Warrenton, Va.	1420	WLBY	Lebanon, Pa.	1270	WMOT	Brunswick, Ga.	1490
WJOB	Hammond, Ind.	1230	WKTG	Thomasville, Ga.	750	WLBY	Lebanon, Pa.	1270	WMOH	Hamilton, Ohio	1450
WJOC	Jamestown, N.Y.	1340	WKTH	Chattanooga, Tenn.	1340	WLBY	Lebanon, Pa.	1270	WMOK	Metropolis, Ill.	920
WJOE	Ward Ridge, Fla.	1570	WKTM	Mayfield, Ky.	950	WLBY	Lebanon, Pa.	1270	WMON	Montgomery, W.Va.	1340
WJOI	Florence, Ala.	1340	WKTP	South Paris, Maine	1450	WLBY	Lebanon, Pa.	1270	WMOP	Ocala, Fla.	900
WJOL	Joliet, Ill.	1340	WKTY	Atlantic Beach, Fla.	1600	WLBY	Lebanon, Pa.	1270	WMOR	Marion, Ohio	1490
WJON	St. Cloud, Minn.	1240	WKUL	Cullman, Ala.	1340	WLBY	Lebanon, Pa.	1270	WMOS	Moundsville, W.Va.	1370
WJOP	Lake Superior, N.Y.	1280	WKVA	Lewistown, Pa.	820	WLBY	Lebanon, Pa.	1270	WMOT	Brunswick, Ga.	1490
WJOY	Burlington, Vt.	1230	WKVM	San Juan, P.R.	910	WLBY	Lebanon, Pa.	1270	WMOH	Hamilton, Ohio	1450
WJPA	Washington, Pa.	1450				WLBY	Lebanon, Pa.	1270	WMOK	Metropolis, Ill.	920
WJPF	Ishpeming, Mich.	1240				WLBY	Lebanon, Pa.				

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WNAD	Norman, Okla.	640	WOSU	Columbus, Ohio	820	WRCD	Dalton, Ga.	1430	WSKY	Asheville, N.C.	1230
WNAE	Warren, Pa.	1310	WOTR	Corry, Pa.	1370	WRCO	Richland, Wis.	1450	WSLB	Ogdensburg, N.Y.	1400
WNAJ	Grenada, Miss.	1400	WOTW	Nashua, N.H.	900	WRCS	Ashokle, N.C.	970	WSLJ	Jackson, Miss.	930
WNAH	Nashville, Tenn.	1360	WOUB	Athens, Ohio	1340	WRCY	Philadelphia, Pa.	1060	WSLM	Salem, Ind.	1220
WNAK	Natick, Pa.	730	WOWE	Weech, W.Va.	1340	WRDB	Reedsburg, Wis.	1400	WSLS	Roanoke, Va.	610
WNAW	Neenah, Wis.	1280	WOWM	Omaha, Neb.	590	WRDP	Auburn, Maine	1400	WSM1	Nashville, Tenn.	1500
WNAZ	Norristown, Pa.	1110	WOWE	Alleghen. Mich.	1580	WRDW	Augusta, Ga.	240	WSM2	Northfield, La.	1510
WNAZ	Natchez, Miss.	1450	WOWI	New Albany, Ind.	1570	WRFB	Holyoke, Mass.	930	WSM3	Sanford, Maine	1220
WNAU	New Albany, Miss.	1470	WOWL	Florence, Ala.	1240	WRFC	Memphis, Tenn.	600	WSM4	Litchfield, Ill.	1540
WNAV	Annapolis, Md.	1430	WOWD	Ft. Wayne, Ind.	1190	WRFD	Lexington, Va.	1450	WSM5	Nashua, N.H.	1590
WNAW	Yankton, S. Dak.	570	WDXF	Oxford, N.C.	1340	WRFM	Renssen, N.Y.	1480	WSMT	Sparta, Tenn.	1050
WNEF	Binghamton, N.Y.	1290	WDXZ	Ozark, Ala.	900	WRFN	Topeka, Kans.	1250	WSNJ	Nor. Bridgeton, N.J.	1240
WNEB	New Bedford, Mass.	1470	WOPK	Porter, Pa.	530	WRFB	Reidsville, N.C.	1230	WSNT	Sandersville, Ga.	1490
WNEP	Newburyport, Mass.	1470	WOPX	Pathogen, N.Y.	1580	WRFB	Tallahassee, Fla.	240	WSNY	Schenectady, N.Y.	1150
WNEB	Murray, Ky.	1340	WPAD	Paducah, Ky.	1450	WRFC	Athens, Ga.	960	WSNY	Schenectady, N.Y.	1150
WNEB	Wellsboro, Pa.	1490	WPAG	Ann Arbor, Mich.	1050	WRFD	Worthington, Ohio	880	WSOC	Charlotte, N.C.	1240
WNEB	Saranac Lake, N.Y.	1240	WPAL	Charleston, S.C.	730	WRFS	Alexander City, Ala.	1050	WSOK	Savannah, Ga.	1230
WNEA	Siler City, N.C.	1570	WPAM	Pottsville, Pa.	1450	WRGA	Rome, Ga.	1470	WSOL	Tampa, Fla.	1300
WNEC	Barnesboro, Pa.	950	WPAP	Fernandina Beach, Fla.	1570	WRGR	Starks, Fla.	1470	WSON	Henderson, Ky.	860
WNEC	Ashland, Ohio	1340	WPAQ	Mount Airy, N.C.	1450	WRGS	Jacksonville, Tenn.	1370	WSOO	Sit. Ste. Marie, Mich.	1320
WNEB	Daytona Beach, Fla.	1150	WPAR	Parkersburg, W.Va.	740	WRHI	Rock Hill, S.C.	1340	WSPT	Deatur, Ill.	1340
WNEB	Syracuse, N.Y.	1260	WPAT	Paterson, N.J.	930	WRHI	Providence, R.I.	1450	WSPT	Spartanburg, S.C.	950
WNEB	South Bend, Ind.	1490	WPAT	Pawtucket, R.I.	550	WRIC	Richlands, Va.	540	WSPB	Sarasota, Fla.	1410
WNEB	Worcester, Mass.	1230	WPAX	Thomasville, Ga.	1240	WRIC	Wausau, Wis.	1400	WSPD	Toledo, Ohio	1370
WNEG	Taccoa, Ga.	1320	WPAY	Portsmouth, Ohio	1400	WRIG	Pahokee, Fla.	1400	WSPN	Saratoga Sprrgs., N.Y.	900
WNER	Live Oak, Fla.	1250	WPAY	Pottstown, Pa.	1370	WRIM	Rio Piedras, P.R.	1320	WSPR	Springfield, Mass.	1270
WNEF	Central Ky., Ky.	1600	WPBZ	Minneapolis, Minn.	980	WRIO	Rio Piedras, P.R.	1320	WSPR	Stevens Pt., Wis.	1010
WNEF	New York, N.Y.	1130	WPCC	Minneapolis, Minn.	1400	WRIS	Roselle, Ga.	980	WSR1	York, Pa.	1490
WNEK	Macon, Ga.	1400	WPCC	Minneapolis, Minn.	1400	WRIS	Roselle, Ga.	980	WSR2	Durham, N.C.	1410
WNGO	Mayfield, Ky.	1320	WPCC	Minneapolis, Minn.	1400	WRIT	Milwaukee, Wis.	1310	WSR3	Durham, N.C.	1410
WNGC	New Haven, Conn.	1340	WPCC	Minneapolis, Minn.	1400	WRIV	Riverhead, N.Y.	1390	WSR4	Hillsboro, Ohio	1590
WNEA	Cheekowaga, N.Y.	1230	WPCT	Putnam, Conn.	1350	WRJN	Racine, Wis.	1400	WSR5	Durham, N.C.	1590
WNIA	Arcadio, P.R.	1230	WPDM	Potsdam, N.Y.	1470	WRJW	Pleasanton, Miss.	1320	WSSC	Sumter, S.C.	1340
WNIA	Niles, Mich.	1290	WPDJ	Jacksonville, Fla.	600	WRKJ	Rockland, Maine	1430	WSSO	Starkville, Miss.	1230
WNJR	Newark, N.J.	1480	WPRR	Portage, Wis.	1350	WRKH	Rockwell, Tenn.	1400	WSSR	Starkville, Miss.	1230
WNKY	Neon, Ky.	1480	WPXK	Clarkston, W.Va.	1430	WRKM	Carthage, Tenn.	1350	WSTA	Charlotte, Amalie, V.I.	1400
WNLC	New London, Conn.	1440	WPEL	Philadelphia, Pa.	950	WRKO	Cocoa Beach, Fla.	1300	WSTC	Stamford, Conn.	1400
WNLK	Norwalk, Conn.	1350	WPEL	Philadelphia, Pa.	950	WRLO	Lanitt, Ala.	1470	WSTK	Woodstock, Va.	1230
WNMP	Evansville, Ill.	1590	WPEL	Peoria, Ill.	1020	WRMA	Montgomery, Ala.	950	WSTL	Eminence, Ky.	1600
WNNT	Newton, N.C.	1230	WPEP	Taunton, Mass.	1570	WRMT	Titusville, Fla.	1470	WSTN	St. Augustine, Fla.	1420
WNNT	Newton, N.J.	690	WPEP	Taunton, Mass.	1570	WRMT	Titusville, Fla.	1470	WSTP	Salisbury, N.C.	1490
WNNT	Warsaw, Ind.	890	WPEP	Greensboro, N.C.	950	WRMT	Titusville, Fla.	1470	WSTP	Salisbury, N.C.	1490
WNNE	New Orleans, La.	1060	WPEP	Greensboro, N.C.	950	WRNB	New Bern, N.C.	910	WSTS	Massena, N.Y.	1050
WNOG	Naples, Fla.	1270	WPEP	Greensboro, N.C.	950	WRNL	Richmond, Va.	1490	WSTU	Suart, Fla.	1450
WNOK	Columbia, S.C.	1230	WPEP	Greensboro, N.C.	950	WROA	Gulfport, Miss.	1390	WSTV	Staubenville, Ohio	1340
WNOP	Newport, Ky.	740	WPEP	Greensboro, N.C.	950	WROB	West Point, Miss.	1450	WSUB	Groton, Conn.	980
WNOR	Norfolk, Va.	1230	WPEP	Greensboro, N.C.	950	WROD	Daytona Beach, Fla.	1340	WSUH	Oxford, Miss.	1420
WNOR	High Point, N.C.	1230	WPEP	Greensboro, N.C.	950	WROK	Rockford, Ill.	1440	WSUJ	Iowa City, Iowa	910
WNOW	York, Pa.	1250	WPEP	Greensboro, N.C.	950	WROK	Rockford, Ill.	1440	WSUR	St. Petersburg, Fla.	620
WNXX	Knoxville, Tenn.	990	WPEP	Greensboro, N.C.	950	WRON	Ronoverce, W.Va.	1400	WSUX	Seaford, Del.	1280
WNPS	New Orleans, La.	1450	WPEP	Greensboro, N.C.	950	WROS	Scottsboro, Ala.	1330	WSUZ	Patakat, Fla.	800
WNPT	Tuscaloosa, Ala.	1280	WPEP	Greensboro, N.C.	950	WROW	Ronoke, Va.	1240	WSVA	Harrisonburg, Va.	550
WNRG	Grundy, Va.	1250	WPEP	Greensboro, N.C.	950	WROW	Ronoke, Va.	1240	WSVS	Crews, Va.	600
WNRV	Woodscock, R.I.	1380	WPEP	Greensboro, N.C.	950	WROX	Clarksville, Miss.	1450	WSWN	Belle Glade, Fla.	900
WNRV	Narrows, Va.	930	WPEP	Greensboro, N.C.	950	WRPM	Rocky Mount, N.C.	1050	WSWV	Winston Gap, Va.	1570
WNSL	Laurel, Miss.	1260	WPEP	Greensboro, N.C.	950	WRPB	Warner Robbins, Ga.	1350	WSWW	Platteville, Wis.	1590
WNSM	Valparaiso, N. Carolina	1340	WPEP	Greensboro, N.C.	950	WRR	Dallas, Tex.	1310	WSYB	Rutland, Vt.	1380
WNTA	Newark, N.J.	970	WPEP	Greensboro, N.C.	950	WRRF	Washington, N.C.	930	WSYD	Mt. Airy, N.C.	1300
WNUZ	Talladega, Ala.	1230	WPEP	Greensboro, N.C.	950	WRRR	Rockford, Ill.	1330	WSYL	Sylvania, Ga.	1490
WNVN	Norton, Va.	1230	WPEP	Greensboro, N.C.	950	WRRZ	Clinton, N.C.	880	WSYR	Syracuse, N.Y.	570
WNVY	Pensacola, Fla.	1350	WPEP	Greensboro, N.C.	950	WRSA	Saratoga Sprrgs., N.Y.	1280	WTAB	Tabor City, N.C.	1370
WNYC	New York, N.Y.	830	WPEP	Greensboro, N.C.	950	WRSA	Saratoga Sprrgs., N.Y.	1280	WTAC	Ft. Hunt, Mich.	600
WNYX	Salamanca, N.Y.	1590	WPEP	Greensboro, N.C.	950	WRTA	Altoona, Pa.	1240	WTAD	Quincy, Ill.	930
WNXT	Portsmouth, Ohio	1260	WPEP	Greensboro, N.C.	950	WRUF	Gainesville, Fla.	850	WTAG	Worcester, Mass.	580
WDAI	San Antonio, Tex.	1200	WPEP	Greensboro, N.C.	950	WRUM	Rumford, Maine	790	WTAL	Tallahassee, Fla.	1270
WDAF	Owosso, Mich.	1080	WPEP	Greensboro, N.C.	950	WRUN	Utica, N.Y.	1150	WTAN	Clearwater, Fla.	1340
WDAF	Oak Hill, W. Va.	860	WPEP	Greensboro, N.C.	950	WRUS	Russellville, Ky.	610	WTAD	Cambridge, Mass.	740
WDBS	Jacksonville, Fla.	1340	WPEP	Greensboro, N.C.	950	WRVA	Richmond, Va.	1140	WTAP	Parkersburg, W.Va.	1280
WDBT	Rhineland, Wis.	1240	WPEP	Greensboro, N.C.	950	WRVC	Vienna, Ky.	1060	WTAR	Norfolk, Ill.	1560
WDC	Davenport, Iowa	1420	WPEP	Greensboro, N.C.	950	WRVA	Richmond, Va.	1140	WTAR	Norfolk, Va.	790
WDCB	W. Yarmouth, Mass.	1240	WPEP	Greensboro, N.C.	950	WRWH	Cleveland, Ga.	1380	WTAW	Bryn, Tex.	1150
WDCB	North Vernon, Ind.	1460	WPEP	Greensboro, N.C.	950	WRWJ	Seima, Ala.	1570	WTAX	Springfield, Ill.	1220
WDCB	E. Liverpool, Ohio	1490	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTAY	Robinson, Ill.	1570
WDCB	London, Ohio	1470	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTBC	Tuscaloosa, Ala.	1230
WDCB	Bellefontaine, Ohio	1330	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTBF	Troy, Ala.	970
WDCB	Shelby, N.C.	730	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCH	Chillicothe, Md.	1450
WDCB	Ames, Iowa	640	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCH	Shawano, Wis.	960
WDCB	Saline, Mich.	1290	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Tell City, Ind.	1230
WDCB	Columbia, S.C.	1470	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Winter Garden, Fla.	1600	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Charleston, S.C.	1340	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Meridian, Miss.	1450	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Jackson, Miss.	1590	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Albany, N.Y.	1460	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Columbus, Ga.	1340	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Milwaukee, Wis.	920	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Alton, Ill.	1570	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Washington, D.C.	1450	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Syracuse, N.Y.	1490	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Florence, S.C.	1230	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Owensboro, Ky.	1430	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Bellaire, Ohio	1290	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Manitowoc, Wis.	1240	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Winona, Miss.	1570	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Pleasantville, N.J.	1400	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Durham, N.C.	980	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Oneida, N.Y.	1600	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Lakeland, Fla.	1230	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Defiance, Ohio	1280	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Grand Rapids, Mich.	1300	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Dothan, Ala.	560	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Washington, D.C.	1340	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Dallas, Tex.	1310	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Washington, N.C.	1340	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Oak Park, Ill.	1490	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Bristol, Tenn.	1490	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	New York, N.Y.	710	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Mayaguez, P.R.	1150	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Worcester, Mass.	1310	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Spartanburg, S.C.	930	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	York, Pa.	1350	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	1400
WDCB	Boston, Mass.	950	WPEP	Greensboro, N.C.	950	WRXO	Roxboro, N.C.	1430	WTCT	Traverse City, Mich.	

World-Wide Short-Wave Stations

Most international broadcasting is done within frequency limits agreed upon at international conventions. These frequency ranges are listed here, at the right, expressed both in frequency and by meter bands (wave-length).

Not all of the bands are employed at once. In fact, only one or two are usable at any one time. The time of the day and the season for seasons, since the season is opposite in the southern hemisphere) are the two chief determining factors. Broadcasters beaming programs to the U.S. use the best band for the time. Broadcasts not beamed to the U.S., if heard here at all, will be scattered over the bands. Low frequencies are better heard at night than by day. High frequencies are better heard in summer than in winter.

- 5950 to 6200 kc/s (49 meter band)
- 7100 to 7300 kc/s (41 meter band)
- 9500 to 9775 kc/s (31 meter band)
- 11700 to 11975 kc/s (25 meter band)
- 15100 to 15450 kc/s (19 meter band)
- 17700 to 17900 kc/s (16 meter band)
- 21450 to 21750 kc/s (13 meter band)

The symbol • denotes stations beaming regular evening broadcasts to the United States.

Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	
4768	HJEF	Call, Colombia	6035	GWS	London, England	6405	TGQA	Quezaltenango, Guat.	9531	COGO	Havana, Cuba	
4775	HJGB	Bucaramanga, Col.	6035	Monte Carlo, Monaco	6450	COCY	Santa Clara, Cuba	9535	HER4	Bern, Switzerland		
4783	HJAB	Barranquilla, Col.	6035	XYZ	Rangoon, Burma	6632	HC2RL	Guayaquil, Ecu.	9535	SEBU	Stockholm, Sweden	
4790	YVQC	Ciudad Bolívar, Vz.	6037	San Jose, Costa Rica	6660	HROW	Tegucigalpa, Hond.	9540	Munich	Germany		
4797	HJFU	Armenia, Colombia	6040	GSY	London, England	6758	YNVP	Managua, Nic.	9540	VLG9	Melbourne, Aus.	
4800	YVME	Maracaibo, Venez.	6040	KCBR	Delano, Calif.	6790	ZJM6	Limassol, Cyprus	9540	ZL2	Wellington, N. Zeal.	
4805	ZY58	Manaos, Brazil	6040	Tangler	Tangler	6830	4XB21	Tel Aviv, Israel	9543	XYZ	Rangoon, Burma	
4810	YVMG	Caracas, Venez.	6040	WFO	Cincinnati, U.S.A.	6870	HC4EB	Manta, Ecuador	9548	XEFT	Vera Cruz, Mex.	
4815	HJBB	Cucuta, Col.	6045	YDF	Djakarta, Indonesia	7105	Paris, France	9550	HVJ	Vatican City		
4820	XEJG	Guadalajara, Mex.	6050	H1IN	Ciudad Trujillo, D.R.	7112	CR4AA	Prata, Cape V. Isls.	9550	Paris, France		
4820	YVNB	Coro, Venez.	6050	GSA	London, England	7120	GRM	London, England	9550	OLR3A	Prague, Czechoslovakia	
4830	YVOA	San Cristobal, Vez.	6054	HJEX	Call, Colombia	7135	BER7	Taipei, Formosa	9550	Gronada	Windward Is.	
4835	HJKE	Bogota, Colombia	6055	HER2	Bern, Switzerland	7135	MCM	London, England	9555	DXZ2	Pori, Finland	
4840	YVOI	Valera, Venez.	6055	GSX	London, England	7145	Radio Free Europe	London, England	9555	XETT	Mexico, Mex.	
4845	CSA93	Punta Delgada, Az.	6060	H101	San Francisco, Calif.	7150	GRT	London, England	9560	JBD2	Kawachi, Japan	
4848	HJGF	Bucaramanga, Col.	6060	Tangler I	Tangler	7150	Moscov, U.S.S.R.	9560	London, England			
4850	YVMS	Barquisimeto, Vz.	6060	WDSI	New York, U.S.A.	7165	VOU	Delhi, India	9560	Paris, France		
4855	HJFN	Nelva, Colombia	6065	SB0	Motala, Sweden	7175	YUD	Delhi, India	9560	WLWO	Cincinnati, U.S.A.	
4860	JKL	Tokyo, Japan	6065	XEXE	Mexico City, Mex.	7180	JOA	Tokyo, Japan	9560	WRCA	New York, U.S.A.	
4860	YVFA	San Felipe, Venez.	6069	JOB	Tokyo, Japan	7185	GRK	London, England	9565	Komsomolsk, U.S.S.R.		
4865	PRCS	Belem, Para, Brazil	6070	GRB	London, England	7200	GWZ	London, England	9565	ZYK3	Recife, Brazil	
4865	HJFA	Perella, Colombia	6075	WPA	Sa Fran, U.S.A.	7205	Warsaw, Poland	9570	Aiglers	Algeria		
4871	HJBG	Cucuta, Colombia	6080	Munich III	Germany	7210	GWL	London, England	9570	GWX	London, England	
4880	YVKF	Caracas, Venez.	6081	OAX4Z	Lima, Peru	7210	HEI3	Bern, Switzerland	9570	KCBR(VOA)	Delano, Calif.	
4892	YVKB	Caracas, Venez.	6085	ORU	Brussels, Belgium	7222	Budapest	Hungary	9570	Warsaw	Poland	
4895	HJCH	Bogota, Col.	6085	VP4RD	Port-of-Spain, Trinidad	7230	GSW	London, England	9570	Bucharest	Rumania	
4895	PRF6	Manaos, Brazil	6095	ZYK2	Recife, Brazil	7240	Moscov, U.S.S.R.	9570	Rome	Italy		
4900	YVLA	Caracas, Venez.	6095	GMW	London, England	7240	Paris, France	9580	GSC	London, England		
4900	YVQE	Ciudad Bolívar, Vz.	6099	VL16	Sydney, Australia	7250	GW	London, England	9580	VLB9	Shepparton, Aus.	
4903	HJAG	Barranquilla, Col.	6092	Radio Luxemburg	9595	Horby, Sweden	7255	Prague	Czechoslovakia	9585	Madrid	Spain
4907	YVMM	Coro, Venez.	6095	Radio Free Europe	9595	Munich, Germany	7257	JKH	Tokyo, Japan	9590	Hilversum	Neth.
4910	JKI	Nazaki, Japan	6095	HJFK	Perella, Colombia	7260	GSU	London, England	9590	WABC	New York, U.S.A.	
4910	YDB2	Djakarta, Indon.	6100	Belgrade	Yugoslavia	7260	Moscov, U.S.S.R.	9590	GRY	London, England		
4915	Accra	Ghana	6100	WRCA	New York, U.S.A.	7260	GWN	London, England	9600	KCBR	Delano, Calif.	
4915	YVKR	Caracas, Venez.	6100	GSL	London, England	7285	JKJ	Tokyo, Japan	9600	KRCA	San Francisco, U.S.A.	
4917	H19B	Santiago, Dom. Rep.	6112	H1IZ	Ciudad Trujillo, D.R.	7290	Hamburg	Germany	9600	Leninград	U.S.S.R.	
4917	VL44	Brisbane, Aus.	6112	Berlin	Germany	7290	VUD	Delhi, India	9605	HPJ5	Panama, Pan.	
4930	HJAP	Cartagena, Col.	6120	Y214	Limassol, Cyprus	7290	WFO	Delhi, India	9605	JKL2	Tokyo, Japan	
4940	JKM	Kawachi, Japan	6120	Tangler	Tangler	7295	Moscov, U.S.S.R.	9605	KCLO	Frac Europe, Lisbon, Portugal		
4940	YVMQ	Barquisimeto, Vz.	6120	WRCR	New York, U.S.A.	7300	Radio Free Europe	9607	Athens	Greece		
4945	HJCV	Bogota, Col.	6122	HP5P	Panama, Pan.	7300	SV2D	Athens, Greece	9610	PR3	Sydney, Australia	
4945	ZQ1	Kinshasa, Jamaica	6124	HRQ	San Pedro Sula, Hond.	7315	YSA	San Salvador, Salv.	9610	ZYCR	Rio de Janeiro, Brazil	
4951	Dakar	Senegal	6124	GWA	London, England	7320	GRJ	London, England	9610	LERQ	Oslo, Norway	
4960	YVQA	Cumana, Venez.	6130	XEUZ	Mexico, Mex.	7335	BEC36	Taipei, Formosa	9610	XRG	Mexico, Mex.	
4967	HJAE	Cartagena, Col.	6130	COCD	Havana, Cuba	7360	Moscov, U.S.S.R.	9615	Voice of Amer.	Tangler		
4970	YVVK	Caracas, Venez.	6130	Port Moresby	New Guinea	7670	Soňa, Bulgaria	9615	VLB9	Shepparton, Aus.		
4985	YVMO	Barquisimeto, Vz.	6130	HJED	Call, Colombia	7800	ZAA	Tirana, Albania	9615	WFO	New York, U.S.A.	
4995	H1IA	Santiago, D. Rep.	6145	HJDE	Medellin, Col.	7863	SUX	Cairo, Egypt	9615	TIDCR	San Jose, C.Rica	
5010	Gronada	Windward Is.	6147	PRL9	Rio de Janeiro, Br.	7933	HLKA	Pusan, S. Korca	9620	Horby, Sweden		
5014	PJ3C	Willmstid, Curac.	6150	GW	London, England	7951	Alicante	Spain	9620	Paris, France		
5020	HJFW	Manizales, Col.	6150	TGAZ	Guatemala, Guat.	8036	FXE	Beirut, Lebanon	9620	ZL8	Wellington, N.Z.	
5023	H18Z	Santiago, D. Rep.	6160	H1KJ	Bogota, Colombia	8664	COJK	Camaguey, Cuba	9625	XEBT	Mexico, Mex.	
5030	YVPK	Caracas, Venez.	6160	Honolulu	Hawaii	8825	COKG	Santiago, Cuba	9625	GWQ	London, England	
5045	ZY23	Petropolis, Brazil	6160	Munich, Germany	9236	COBZ	Havana, Cuba	9625	VP4RD	Port-au-Spain, Trinidad		
5050	YVKD	Caracas, Venez.	6165	GWK	London, England	9252	Bucharest	Rumania	9630	HJKC	Bogota, Colombia	
5053	H1ZL	Ciudad Trujillo, D.R.	6165	HER3	Bern, Switzerland	9290	PRN9	Rio de Janeiro, Brazil	9630	VD4/10	Delhi, India	
5055	H1DW	Medellin, Col.	6167	4VCM	Port-au-Prince, H.	9316	LRS	Buenos Aires, Arg.	9630	Rome	Italy	
5075	HJKH	Sutatenza, Colom.	6170	Munich	Germany	9340	OAX4J	Lima, Peru	9630	Munich	Germany	
5078	PZH5	Paramaribo, Surinam	6170	GSZ	London, England	9363	COBC	Havana, Cuba	9635	Voice of Amer.		
5880	HRN	Tegucigalpa, Hond.	6170	KCBR	Delano, Calif.	9369	Madrid	Spain	9640	Colono		
5940	Khabarovsk	U.S.S.R.	6170	KCBR(VOA)	Delano, Calif.	9380	Khabarovsk	U.S.S.R.	9640	DZH2	Manila, P.I.	
5940	Moscov, U.S.S.R.		6170	NYKO	Manaos, Venez.	9400	OTM2	Leopoldville, Congo	9640	GVZ	London, England	
5952	TGNA	Guatemala, Guat.	6172	ZJM5	Limassol, Cyprus	9410	GRJ	London, England	9645	LLH	Oslo, Norway	
5960	HJCF	Bogota, Colombia	6175	XEXA	Mexico, Mex.	9452	LYR1	Buenos Aires, Arg.	9645	TIFC	San Jose, C.Rica	
5965	Shanghai, China		6180	LRM	Mendoza, Argentina	9463	TAP	Ankara, Turkey	9646	HVJ9	Vatican City	
5969	HVJ	Vatican City	6180	Ashkabad	U.S.S.R.	9480	Moscov, U.S.S.R.	9650	Honolulu	Hawaii		
5970	H14T	Ciudad Trujillo, D.R.	6180	GRQ	London, England	9500	XEWX	Mexico, Mex.	9650	Moscov, U.S.S.R.		
5985	YVZ	San Pedro, Br.Gul.	6182	TGWB	Guatemala, Guat.	9504	OLR3B	Prague, Czechoslovakia	9650	Tangler		
5985	Radio Free Europe		6182	HJCT	Bogota, Colombia	9505	HOLA	Colon, Panama	9650	WDSI(VOA)		
			6185	Frankfurt	Germany	9505	JBD	Kawachi, Japan	9650	N. Y.		
			6190	H19T	Puerto Plata, D.R.	9510	YVHJ	Barquisimeto, Ven.	9652	ZJM8		
			6190	WLWO	Cincinnati, U.S.A.	9510	GSB	London, England	9654	OTC2		
			6190	WRCA	New York, U.S.A.	9515	KNB	VOA, Dixon, Calif.	9655	JKI2		
			6195	GRN	London, England	9515	TAP	Ankara, Turkey	9655	AVEH		
			6200	Paris, France		9520	HJFM	Bogota, Colombia	9660	EQG		
			6215	SP13	Warsaw, Poland	9520	OZF	Skamlebak, Denmark	9660	GW		
			6235	HR02	La Ceiba, Hond.	9520	VL9	Port Moresby, Brit. New Guinea	9660	VLQ9		
			6235	Karachi	Pakistan	9520	WJWO	Cincinnati, U.S.A.	9665	HEU3		
			6248	Budapest	Hungary	9525	GWJ	London, England	9668	TGNB		
			6285	TGTQ	Guatemala, Guat.	9525	ZB3W	Victoria, Hong Kong	9668	Munich		
			6295	OTM1	Leopoldville, Congo	9527	Warsaw	Poland	9670	Voice of Amer.		
			6295	TGLA	Guatemala, Guat.	9530	Honolulu	Hawaii	9670	Moscov		
			6320	Baden	Baden, Germany	9530	Manila	Philippines	9675	WNT		
			6322	COCW	Havana, Cuba	9530	Delano	Calif., U.S.A.	9675	JOB3		
			6335	TGTA	Guatemala, Guat.	9530	Honolulu	Hawaii	9680	XEQQ		
			6351	HPRD	Madrid, Hond.	9530	WABC	New York, U.S.A.	9680	VUD		
			6374	CSA21	Lisbon, Port.	9530			9680	Moscov, U.S.S.R.		
									9680	Voice of America, Tangier		

Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location
9680	VLR9/VLH9	Melbourne, Australia	11795	W5T	West Germany Radio, Cologne	15120	Rome, Italy		15405	DMQ15	Cologne, W. Germany
9685	Paris, France		11795	YDF3	Djakarta, Indonesia	15120	Warsaw, Poland		15405	P2C	Paramaribo, Surinam
9685	WLWO	Cincinnati, U.S.A.	11795	WRUL	Boston, U.S.A.	15130	SA36	Lisbon, Portugal	15410	Moscow, U.S.S.R.	
9690	LRA	Buenos Aires, Arg.	11795	Radio	Pakistan, Karachi	15130	Voice of America,	Tangier	15420	Paris, France	
9690	GRX	London, England	11795	ELWA	Monrovia, Liberia	15130	WABC	New York, U.S.A.	15420	Brazzaville, Fr. Equat. Africa	
9690	Moscow, U.S.S.R.		11800	JK14	Tokyo, Japan	15130	KLWB	Cincinnati, U.S.A.	15425	Radio Netherlands	
9690	Singapore, Malaya		11800	GWH	London, England	15130	WBOU	Bound Brook, N. J., U.S.A.	15435	GWE	London, England
9695	JKM2	Kawachi, Japan	11800	Brussels, Belgium		15135	PRR33	Japan, Tokyo	15440	Moscow, U.S.S.R.	
9700	GWY	London, England	11810	Moscow, U.S.S.R.		15135	PR33	Sao Paulo, Brazil	15440	Radio Netherlands	
9700	WDS1	New York, U.S.A.	11810	Radio Sweden, (except—Nov. to Febr.)		15140	GSF	London, England	15450	GRD	London, England
9700	Sofia, Bulgaria		11810	Rome, Italy		15150	YDC	Djakarta, Indonesia	15455	Brazzaville, Fr. Eq. Africa	
9700	WLVO	of America, Tangier	11810	VLA11	Shepparton, Aus. (Morning program)	15150	ZK2	Recife, Brazil	15620	Madrid, Spain	
9700	WLVO	Cincinnati, U.S.A.	11815	Warsaw, Poland		15150	OAX4R	Lima, Peru	15880	Peking, China	
9700	KCBR	Delano, Cal., U.S.A.	11820	GSN	London, England	15150	CE1515	Santiago, Chile	17200	GVP	London, England
9700	FZ6	Ft. de France, Mart. Moscov, U.S.S.R.	11820	XEBR	Hermosillo, Mex.	15155	SBT	Motala, Sweden	17215	GRA	London, England
9710	Dakar, Fr. W. Africa		11825	JK16	Tokyo, Japan	15155	ZY89	Sao Paulo, Brazil	17220	LRA5	Buenos Aires, Arg.
9710	YDF6	Djakarta, Indonesia	11825	Moscow, U.S.S.R.		15160	VUD5/7	Delhi, India	17230	GVQ	London, England
9710	Rome, Italy		11825	ZYK3	Recife, Brazil	15160	VLB15	Shepparton, Aus.	17250	WRUL	Boston, U.S.A.
9715	Cairo, Egypt		11830	FZ54	Salgon, Fr. Indo-C.	15160	TAU	Ankara, Turkey	17500	Rome, Italy	
9716	Moscow, U.S.S.R.		11830	Moscow, U.S.S.R.		15165	WLVO	Cincinnati, U.S.A.	17780	WGEO	Schenectady, U.S.A.
9717	Radio Free Europe, Ger.		11830	Voice of America, Tangier		15165	ZYN7	Fortaleza, Brazil	17780	VUD	Delhi, India
9720	PRL7	Rio de Janeiro, Brazil	11830	WBOU(VOA)	New York, U.S.A.	15170	LKV	Oslo, Norway	17770	KCBR	Delano, Cal., U.S.A.
9730	French Equatorial Africa		11830	WDSI(VOA)	New York, U.S.A.	15170	TGWA	Guatemala, Guat.	17770	Rome, Italy	
9730	Nanking, China		11835	CXA19	Montevideo, Uru.	15170	Moscow, U.S.S.R.		17770	Voice of America, Tangier	
9730	DZ17	Manila, P.I.	11835	PRAGUE, Czechoslovakia		15175	LNI	Oslo, Norway	17770	Radio Sweden, Stockholm	
9730	Leipzig, Germany		11840	VLW11	Perth, Australia	15180	GSO	London, England	17775	Hilversum, Netherlands	
9735	H12T	Ciudad, Trujillo, D.R.	11840	OLR4A	Prague, Czech.	15180	Moscow, U.S.S.R.		17780	VUD/10/11	Delhi, India
9741	CSA23	Lisbon, Portugal	11840	LRT	Tucuman, Argentina	15180	OZH2	Shamlebak, Den.	17780	WBOU	New York, U.S.A.
9745	HCBJ	(Missionary Station), Quito, Ecuador	11845	Karachi, Pakistan		15190	VUD5/11	Delhi, India	17780	Voice of Amer., Manila, P.I.	
9745	ORU	Brussels, Belgium	11847	Paris, France		15190	OIX4	Porl, Finland	17784	HERZ	Bern, Switzerland
9750	CR7BE	Lourenco Marques, Moz.	11850	VLB11	Shepparton, Aus.	15195	TAQ	Ankara, Turkey	17785	JOA	Tokyo, Japan
9765	TGWA	Guatemala, Guat.	11850	ORU	Brussels, Belgium	15200	Moscow, U.S.S.R.		17790	GS6	London, England
9770	London, England		11850	TGNC	Guatemala, Guat.	15200	VLA15/VLJL	Shepparton, Aus.	17795	WRUL	Boston, U.S.A.
9770	ORU	Brussels, Belgium	11850	VUD11	Delhi, India	15205	XESC	Mexico	17800	WLVO	Cincinnati, U.S.A.
9770	PRL4	Rio de Jan., Brazil	11850	LKX	Oslo, Norway	15205	Voice of America, Tangier		17800	Radio Australia, Melbourne	
9780	Rome, Italy		11855	DZH9	Manila, Philippines	15210	Munich, Germany		17800	Radio Poland	
9785	Monte Carlo, Monaco		11855	Radio Free Europe, Lisbon, Portugal		15210	GWU	London, England	17800	KRHO	Honolulu, Hawaii
9825	GRH	London, England	11860	GSE	London, England	15210	WBOU(VOA)	New York, U.S.A.	17800	Stockholm, Sweden	
9830	Budapest, Hungary		11860	KWID	San Fran., U.S.A.	15210	VLG15	Melbourne, Aus.	17800	OIX5	Porl, Finland
9833	COBL	Havana, Cuba	11865	CR6RA	Luanda, Angola	15220	ZL10	Wellington, N.Z.	17805	DZ16	Manila, P.I.
9865	YDF8	Djakarta, Indonesia	11865	HER5	Bern, Switzerland	15225	JB03	Kawachi, Japan	17810	Forma	Radio
9915	GRU	London, England	11870	Munich, Germany		15228	Komsomolsk, U.S.S.R.		17810	GSV	London, England
9966	Brazzaville, Fr. Eq. Africa		11870	KNBN	San Fran., U.S.A.	15230	GWD	London, England	17810	Moscow, U.S.S.R.	
10058	SUV	Cairo, Egypt	11870	KNBN	San Fran., U.S.A.	15230	Moscow, U.S.S.R.		17815	WRUL	Boston, U.S.A.
10195	Paris, France		11870	Voice of America, Tangier		15230	LSA	Prague, Czech.	17820	Colombo, Ceylon	
10225	PSM	Rio de Janeiro, Brazil	11870	WRUL	Boston, U.S.A.	15230	VLB15	Melbourne, Aus.	17825	LLN	Dal, Norway
10258	XRR4	Peiping, China	11875	OLR4C	Prague, Czech.	15230	WRUL	Boston, U.S.A.	17825	LAK	Ankara, Turkey
10780	SDB2	Motala, Sweden	11875	Radio Portugal		15230	WRUL	Boston, U.S.A.	17825	Radio Japan, Tokyo	
11027	CSA29	Lisbon, Portugal	11880	Moscow, U.S.S.R.		15235	BED3	Taipei, Formosa	17830	Moscow, U.S.S.R.	
11090	CSA92	Ponta Delgada, Azores	11880	LRS	Buenos Aires, Arg.	15235	JOBS	Tokyo, Japan	17830	WDSI(VOA)	New York, U.S.A.
11455	Peking, China		11880	VLL11/VLH11		15240	Belgrade, Yugoslavia		17835	Karachi, Pakistan	
11475	ZNX52	Barbadoes, B.W.I.	11880	Horby, Sweden		15240	KRCA	San Fran., U.S.A.	17840	Radio Sweden	
11513	Tangier, Morocco		11880	XEHM	Mexico, Mex.	15240	Paris, France		17840	Brazzaville, Fr. Eq. Africa	
11515	Peking, China		11880	GRE	London, England	15240	WLD	Melbourne, Aus.	17840	Moscow, U.S.S.R.	
11630	Leningrad, U.S.S.R.		11880	SPK	Stockholm, Sweden	15250	Bucharest, Rumania		17840	VL17	Shepparton, U.S.A.
11640	All India Radio, Delhi		11885	APK3	Karachi, Pakistan	15250	Voice of Amer., Manila, P.I.		17840	HVJ	Vatican City
11650	Peking, China		11890	Moscow, U.S.S.R.		15250	WLVO	Cincinnati, U.S.A.	17850	Paris, France	
11670	Bangkok, Thailand		11890	GWV	London, England	15250	Voice of Amer., Tangier		17860	ORU3	Brussels, Belgium
11680	HJCQ	Bogota, Colombia	11890	KZJ1	Manila, P.I.	15250	Voice of Amer., Tangier		17865	Damascus, Syria	
11680	GRG	London, England	11890	WQU	New York, U.S.A.	15260	GS1	London, England	17870	CSA4	Lisbon, Portugal
11685	Peking, China		11895	FHE3	Dakar, Fr. W. Af.	15270	KCBR	Delano, Cal., U.S.A.	17890	HCBJ	(Missionary Station), Quito, Ecuador
11695	HP5A	Panama, Panama	11895	Radio Portugal		15270	Munich, Germany		17910	Grenada, Windward Is.	
11700	GWV	London, England	11895	Manila, Philippines		15270	WBDU(VOA)	New York, U.S.A.	18250	TFTO	Paris, France
11702	Paris, France		11900	CE1190	Valparaiso, Chile	15270	Sverdlovsk, U.S.S.R.		18450	Moscow, U.S.S.R.	
11705	JOA4	Tokyo, Japan	11900	CXA10	Montevideo, Uru.	15280	Munich, Germany		20088	Geneva, Switzerland	
11705	SBP	Motala, Sweden	11900	HC1B	Calvary Road, Ministry	15280	ZL4	Wellington, N.Z.	21420	KNBN	(V.D.), San Fran., Calif.
11710	Moscow, U.S.S.R.		11900	EXEX	Mexico City, Mex.	15280	Moscow, U.S.S.R.		21460	GSV	London, England
11710	Voice of America, Tangier		11900	Rome, Italy		15280	Voice of Amer., Tangier		21480	Hilversum, Netherlands	
11710	VUD5/7	Delhi, India	11910	Budapest, Hungary		15285	CR7BG	Lourenco Marques, Mozambique	21490	Paris, France	
11714	ZJM7	Limassol, Cyprus	11910	Karachi, Pakistan		15285	WBOU(VOA)	New York, U.S.A.	21500	WRCA	New York, U.S.A.
11715	HE15	Bern, Switzerland	11915	Radio Netherlands		15290	WRU	Boston, U.S.A.	21510	VUD5	Delhi, India
11718	Athens, Greece		11915	Damascus, Syria		15290	LRU	Buenos Aires, Arg.	21520	HER8	Bern, Switzerland
11720	PRL8	Rio de Janeiro, Brazil	11915	Radio Quito, Ecuador		15290	VUD5/9	Delhi, India	21530	GS1	London, England
11720	Radio Poland		11915	Radio Portugal		15295	Voice of Amer., Tangier		21540	VL2	Shepparton, Aus.
11720	DTM4	Leopoldville, Belgium Congo	11915	BED4	Taipei, Formosa	15300	DZH8	Manila, P.I.	21550	GST	London, England
11720	ORY2	Brussels, Belgium	11924	FZ54	Salgon, Vietnam	15300	GWR	London, England	21560	Moscow, U.S.S.R.	
11724	HNG	Baghdad, Iraq	11930	GVX	London, England	15300	Singapore, Malaya		21560	Rome, Italy	
11725	COCY	Havana, Cuba	11935	Warsaw, Poland		15305	HARB	Bern, Switzerland	21570	WDSI(VDA)	New York, U.S.A.
11730	GVV	London, England	11937	Bucharest, Rumania		15305	K97	Manitoba, U.S.S.R.	21580	Horby, Sweden	
11730	KGE1	San Fran., U.S.A.	11950	YSA	X San Salvador, Salv.	15310	KCBR	Delano, Calif.	21590	WGEO	Schenectady, N.Y.
11730	CE1173	Santiago, Chile	11955	GVY	London, England	15310	GSP	London, England	21600	WLVO(VOA)	Cincinnati, U.S.A.
11735	BED6	Taipei, Formosa	11960	Moscow, U.S.S.R.		15320	VLG15	Melbourne, Aus.	21620	Colombo, Ceylon	
11735	LKQ	Frederikstad, Nor.	11964	Lisbon, Portugal		15320	Moscow, U.S.S.R.		21640	GRZ	London, England
11735	Radio Free Europe, Ger.		11970	Brazzaville, Fr. Eq. Africa		15325	Rome, Italy		21650	WRUL	Cincinnati, U.S.A.
11740	Moscow, U.S.S.R.		11972	TIH	San Jose, C.Rica	15330	KGE1	San Fran., U.S.A.	21670	LIP	Dal, Norway
11740	Warsaw, Poland		11980	Moscow, U.S.S.R.		15330	SOE	Bulgaria	21675	GVP	London, England
11742	WRUL	Boston, U.S.A.	11995	CSA32	Lisbon, Portugal	15335	Brussels, Belgium		21680	VL2C1	Shepparton, Aus.
11742	CE1174	Santiago, Chile	11998	CE1180	Santiago, Chile	15335	Karachi, Pakistan		21690	Voice of America, Tangier	
11750	GSD	London, England	12040	GRV	London, England	15340	Moscow, U.S.S.R.		21700	VUD10	Delhi, India
11755	Radio Portugal		12095	GRF	London, England	15340	KCBR	Delano, Cal., U.S.A.	21710	GV5	London, England
11740	Moscow, U.S.S.R.		12175	TFJ	Reykjavik, Iceland	15345	Athens, Greece		21730	WBOU(VOA)	New York, U.S.A.
11760	VLCA11/VLBI	Shepparton, Aus.	14492	Radio Moscow		15345	Formosa Radio		21740	KCBR	Delano, Cal., U.S.A.
11760	VUD7/11	Delhi, India	14690	PSA	Rio de Janeiro, Brazil	15347	LRA	Buenos Aires, Arg.	21740	KGE1	San Fran., U.S.A.
11764	CR7BH	Lourenco Marques, Mozambique	15050	ETA	Addis Ababa, Eth.	15350	Paris, France		21740	GVV	London, England
11770	GVU	London, England	15050	V3USE	Forest Side, Mauritius	15350	WRUL	Boston, U.S.A.	21750	GVT	London, England
11770	YDE/YDF7	Djakarta, Indonesia	15060	Peking, China		15350	WRUL	Boston, U.S.A.	21815	DE138	Linz, Austria
11775	Radio Poland		15070	GWG	London, England	15350	WLWD	Cincinnati, U.S.A.	25640	HER9	Bern, Switzerland
11780	BBC	London, England	15085	HVJ	Vatican City	15350	UO8	Delhi, India	25650	DMQ25	Cologne, West Germany
11780	Moscow, U.S.S.R.		15100	Moscow, U.S.S.R.		15360	London, England		25670	Sweden	Radio, Stockholm
11780	XEQH	Mexico, D.F.	15100	EPB	Teheran, Iran	15360	Moscow, U.S.S.R.		25675	Radio Australia, Melbourne	
11780	ZL3	Wellington, N.Z.	15105								

United States FM Stations

Abbreviations: Mc., megacycles, asterisk (*) indicates educational station

Location C.L. Mc. Location C.L. Mc. Location C.L. Mc.

ALABAMA

Albertville WAVU-FM 105.1
 Alexander City WRFS-FM 106.1
 Andalusia WCTA-FM 98.1
 Anniston WHMA-FM 100.5
 Athens WJOF 104.3
 Birmingham WAFI-FM 99.3
 WBRG-FM 106.9
 WSMF 93.7
 Clanton WKLF-FM 100.9
 Cullman WFMH-FM 101.1
 Decatur WHOS-FM 102.1
 Homewood WJLN 104.7
 Lanett WRLD-FM 102.9
 Mobile WKRG-FM 99.9
 Tuscaloosa WTBC-FM 95.7
 WUOA *91.7

ARIZONA

Globe KWJB-FM 100.3
 Mesa KBUZ-FM 104.7
 Phoenix KELE 95.3
 Tucson KFGA *88.5
 KFMM 99.5

ARKANSAS

Blytheville KLCN-FM 96.1
 Ft. Smith KFPW-FM 94.9
 Jonesboro KBTM-FM 101.9
 KASU 91.9
 Mammoth Springs KAMS 103.9
 Pine Bluff KOTN-FM 92.3
 Siloam Springs KUOA-FM 105.7

CALIFORNIA

Atherton KPEN 101.3
 Bakersfield KERN-FM 94.1
 KQXR 101.5
 KPTA 94.1
 Berkeley KPFJ *89.3
 KRE-FM 102.9
 KSPC *88.9
 Claremont KRED-FM 96.3
 Eureka KARM-FM 101.9
 Fresno KMJ-FM 97.9
 KRFM 93.7
 Glendale KFMU 97.1
 KUTE 101.9
 Long Beach KFOX-FM 102.3
 KLON *88.1
 KNOB 97.9
 Los Angeles KABC-FM 95.5
 KBCA 105.9
 KBMS 105.9
 KCBH 98.7
 KFAC-FM 92.3
 KGLA *103.5
 KHJ 101.1
 KMLA 100.3
 KNX-FM 93.1
 KBIQ 104.3
 KPOL-FM 93.9
 KRHM 94.7
 KRKK-FM 96.3
 KUSC *91.5
 KXLU *88.7
 KHOF 99.5
 Marysville KMYC-FM 99.9
 Modesto KBEE-FM 103.3
 Oakland KTRB-FM 104.1
 KAFE 98.1
 Ontario KASK-FM 93.5
 Oxnard KAAR 104.7
 Pasadena KPCC 89.3
 KPLI 99.1
 KDUO 97.5
 Sacramento KCRA-FM 96.1
 KFBK-FM 96.9
 KGMS-FM 100.5
 KJML 95.3
 KXOA-FM 107.9
 KVCB *91.9
 San Bernardino KFSD-FM 94.1
 San Diego KGB-FM 101.5
 KITT 105.9
 KSDS *88.3
 San Francisco KALW *91.7
 KCBS-FM 98.9
 KDFC 102.1
 KEAR 97.3
 KGD 103.7
 KNBC-FM 99.7
 Kron-FM 96.5
 KSRF 94.9
 KSJD-FM 92.3
 KCSM *90.9
 Santa Ana KWIZ-FM 96.7
 Santa Barbara KKWV 97.5
 Santa Clara KSCU *90.1
 Santa Maria KEYM 99.1
 KSMA-FM 102.5
 Santa Monica KCRW *89.9
 Stockton KCVN *91.3
 West Covina KOWC 98.3

COLORADO

Boulder KRNV 97.3
 Colorado Springs KRCC *91.3
 KFHM 96.5
 KSHS *90.5
 Denver KFML-FM 98.5
 KDEN-FM 99.5
 KLIR-FM 100.3
 KTCM 105.1
 Manitou Springs KCMS-FM 102.7

CONNECTICUT

Brookfield WGHF 95.1
 Danbury WLAD-FM 98.3
 Hartford WHCN 105.9
 WRTC-FM 98.3
 WTRC-FM 96.5
 Meriden WMNW-FM 95.7
 New Haven WNHCFM 99.1
 Stamford WSTC-FM 96.7
 Storrs WHUS *90.5

DELAWARE

Dover WDDV-FM 94.7
 Wilmington WDEL-FM 93.7
 WJBR 99.5

D. C.

Washington WASH-FM 97.1
 WFAN 100.3
 WGMS-FM 103.5
 WMAL-FM 107.9
 WOL-FM 98.7
 WRC-FM 93.9
 WTOP-FM 96.3
 WWDC-FM 101.1

FLORIDA

Coral Gables WVCG-FM 105.1
 Daytona Beach WNDV-FM 94.5
 Gainesville WRUF-FM *104.1
 Jacksonville WJAX-FM 95.1
 WZFN 96.9
 WMBR-FM 96.1
 WCKR-FM 97.3
 WGBS-FM 96.3
 WTHS *91.7
 WWPB-FM 101.5
 WKAT-FM 93.1
 WMET-FM 93.9
 WDBO-FM 92.3
 WDDU-FM 96.5
 WKIS-FM 100.3
 WXQT-FM 97.9
 WFSU-FM *91.9
 WDTN-FM 100.7
 WFLA-FM 93.3
 WPKM 104.7
 WTUN *88.9
 WPRK *91.5
 Winter Park

GEORGIA

Athens WGAU-FM 102.5
 Atlanta WABE *90.1
 WPLD-FM 103.3
 WGKA-FM 92.9
 WSB-FM 98.5
 Augusta WAUG-FM 105.7
 WBBQ-FM 103.7
 WRBL-FM 93.3
 Gainesville WDUK-FM 103.9
 Lagrange WLAG-FM 104.1
 Macon WMAZ-FM 99.1
 Newnan WCOH-FM 96.7
 Savannah WTCC-FM 97.3
 Swainsboro WJAT-FM 101.7
 Toccoa WLET-FM 106.1

HAWAII

Honolulu KAIM-FM 95.5
 KUOH *90.3
 KVOK *88.1

ILLINOIS

Anna WRAJ-FM 92.7
 Bloomington WJBC-FM 101.5
 Carmi WROY-FM 97.3
 WDWB-FM 97.5
 WBEZ *96.3
 WBEZ *91.5
 WCLM 101.9
 WDFH 95.9
 WEBB 93.9
 WEFM 99.5
 WEHS 97.9
 WENR-FM 94.7
 WFMF 100.3
 WFMQ 107.3
 WFMT 98.7
 WKFM 103.5

Location C.L. Mc. Location C.L. Mc. Location C.L. Mc.

INDIANA

WMAQ-FM 101.1
 WNIW 97.1
 WSEL 104.3
 WSOY-FM 102.1
 WNIC *91.1
 WSEI 95.7
 WEPS *88.1
 WXFV 103.9
 WYOS 105.1
 WNUJ *89.3
 WBEQ-FM 99.9
 WLDV-FM 100.5
 WWKS *91.3
 WLBH-FM 96.9
 WMIK-FM 94.1
 Oak Park WOPV-FM 102.3
 WVLN-FM 92.9
 WPRS-FM 98.3
 WMBD-FM 92.5
 WGEN-FM 105.1
 WTAD-FM 99.5
 WRDK-FM 97.5
 WBFV-FM 98.9
 WTAQ-FM 103.7
 WILL-FM *90.9

INDIANA

Bloomington WFIU *103.7
 Columbus WCSI-FM 98.8
 Crawfordsville WCNB-FM 100.3
 WBSB-FM 106.3
 Elkhart WCBN-FM 95.1
 WTRC-FM 100.7
 WIKY-FM 104.1
 WEVC *91.5
 WPSR 90.7
 WGVE *88.1
 WGSJ 91.1
 WRE *91.7
 Hammond WJOB-FM 92.3
 Hartford City WHCI *91.9
 Huntington WVSH *91.9
 Indianapolis WAJC *104.5
 WFFS 95.5
 WIAN 104.1
 WITZ-FM 90.7
 WORX-FM 96.7
 WMRI-FM 106.9
 WMUN 104.1
 WWHI *91.5
 WNAS *88.1
 WCTW 102.5
 WYSN *91.1
 WETL *91.9
 WTHI-FM 99.9
 WWSK *91.3
 WRSW-FM 107.3
 WFML 106.5

IOWA

Ames WOI-FM *90.1
 Boone KFGQ *99.3
 Clinton KRCS-FM 96.1
 Des Moines WOC-FM 103.7
 KOPB *88.1
 WHD-FM 100.3
 WOBQ 103.3
 KSIU *91.7
 Iowa City KGLD-FM 101.1
 Muscatine KWPC-FM 96.7
 Storm Lake KAYL-FM 101.5
 Waverly KWAR 89.1

KANSAS

Emporia KSTE *88.7
 KANU *91.5
 Manhattan KSDB-FM *88.1
 Newhall KJRG-FM 92.1
 Ottawa KTJO-FM *88.1
 Wichita KFHF-FM 100.3
 KNUW *89.1

KENTUCKY

Ashland WCMJ-FM 93.7
 Central City WNES-FM 101.9
 Fulton WFL-FM 104.9
 Hazard WKIC-FM 96.5
 Henderson WSDN-FM 99.5
 Hopkinsville WHDP-FM 98.7
 Lexington WBKY *91.3
 WLFAP-FM 94.5
 WFPK *91.9
 Louisville WFPL *89.3
 WLVL 97.5
 Madisonville WFMW-FM 93.9
 WNGD-FM 94.7
 Owensboro WQMI-FM 92.3
 WWSF-FM 96.1
 Paducah WPAD-FM 96.9
 WKYB-FM 93.3

LOUISIANA

Alexandria KALB-FM 96.9
 Baton Rouge WJBO-FM 98.1

Location C.L. Mc. Location C.L. Mc.

MAINE

Monroe KMBL-FM 104.1
 New Orleans WBEB 89.3
 WDSU-FM 105.3
 WRCM 97.1
 WMMT 95.7
 Shreveport KRMD-FM 101.1
 KBCL-FM 96.5
 KWKK-FM 94.5

MARYLAND

Annapolis WNAV-FM 99.1
 Baltimore WCAO-FM 102.2
 WFSO-FM 97.9
 WITR-FM 104.3
 WUST-FM 106.3
 Bethesda WPGC 95.5
 Brabury Heights WCUW-FM 102.9
 Cumberland WJAZ-FM 94.7
 Hagerstown WARK-FM 106.9
 Oakland WBUZ 95.5

MASSACHUSETTS

Amherst WAMF *88.1
 WUFA *86.1
 WUOA *91.9
 Boston WBCN 104.1
 WBUZ-FM 106.7
 WCOF-FM 100.7
 WEEI-FM 103.3
 WERS *88.9
 WHDH-FM 94.5
 WRKO-FM 95.5
 WXHR 96.9
 WBET-FM 97.7
 WBSO-FM 92.9
 WGBH-FM *89.7
 WHRB-FM 107.1
 WMAI-FM 98.3
 Lowell WLLH-FM 99.5
 WBSM-FM 97.3
 WNBH-FM 98.1
 S. Hadley WMHC 88.5
 Springfield WHYN-FM 98.1
 WEDK 91.7
 WMAA-FM 104.5
 WCRB-FM 92.7
 WYZZ-FM 94.3
 Williamstown WCFM *90.1
 Winchester WHSR-FM *91.9
 Worcester WTAG-FM 96.1

MICHIGAN

Ann Arbor WUOM *91.7
 Benton Hbr. WHFF-FM 99.9
 Coldwater WTVB-FM 98.3
 Dearborn WKMH-FM 100.3
 Detroit WDET-FM *101.9
 WDR 90.9
 WFI 94.7
 WJBK-FM 93.1
 WNUZ 103.5
 WMZK 97.9
 WJR-FM 96.3
 WWJ-FM 97.1
 WKYZ-FM 101.1
 WKR-FM *90.5
 E. Lansing WSWM 99.1
 Flint WBE 95.1
 Grand Rapids WFRS 92.5
 WJEF-FM 93.7
 WLAJ-FM 96.9
 WHPR *86.1
 WMKZ 94.1
 WMCB *91.1
 WDM 95.5
 WQAK *89.3
 WQMC 104.3
 Saginaw WSAM-FM 98.1
 Sturte WSTR-FM 103.1

MINNESOTA

Mankato KYSM-FM 103.5
 Minneapolis KTIS-FM *98.5
 KWFM 97.5
 WLOL-FM 99.5
 KFAM-FM 104.7

MISSISSIPPI

Jackson WJDX-FM 102.9
 Meridian WMMI *88.1

MISSOURI

Jayton KFUD-FM 99.1
 Joplin WMBH-FM 96.1
 Kansas City KCMQ-FM 94.9
 CKMK 93.3
 KCUR-FM 89.8

How to CRACK the education barrier



Is there an "education barrier" between you and promotion? Are young college graduates being brought in to fill positions above you?

You can break down that barrier . . . gain real security, responsibility, prestige . . . *surprise fellow employees and win their respect.* You can match yourself against the smartest of the college boys and come out a WINNER. Here's how!

AN HOUR A DAY THE I.C.S. WAY!

If you can spare an hour a day, if you have the determination to make good, if you're willing to invest pennies now for dollars later on—then I.C.S. can help you. You can be a man or woman, young or old, skilled or unskilled. So long as you

can understand simple language and illustrated training manuals, you need have no doubts. The I.C.S. hour-a-day plan is SUCCESS-PROVED. You learn while you earn—anywhere, any time.

Just pick the subject you want!

Only I.C.S. offers you such a wide range of subjects to choose from. Drafting. Engineering. Television. Aeronautics. Business. High School. 258 courses in all. *I.C.S. is the oldest, largest home-study school. It is also the best known in business and industry.*

Free catalog plus free books!

When you mail the coupon below, you get a complete catalog on the subject you check with information about employment opportunities, training requirements, etc. And you get "How to Succeed"—36 pages of valuable tips on winning recognition, pay raises, success. Also, a free sample lesson in basic mathematics.

For Real Job Security—Get an I. C. S. Diploma!

I. C. S., Scranton 15, Penna.

Accredited Member,
National Home Study Council

INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX 62248A, SCRANTON 15, PENNA.

Without cost or obligation, send me "HOW TO SUCCEED" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):

- ARCHITECTURE and BUILDING CONSTRUCTION**
 - Air Conditioning
 - Architecture
 - Arch. Drawing and Designing
 - Building Contractor
 - Building Estimator
 - Carpenter Builder
 - Carpentry and Millwork
 - Carpenter Foreman
 - Heating
 - Painting Contractor
 - Plumbing
 - Reading Arch. Blueprints
- ART**
 - Commercial Art
 - Magazine Illus.
 - Show Card and Sign Lettering
 - Sketching and Painting
- AUTOMOTIVE**
 - Automobile
 - Auto Body Rebuilding and Refinishing
 - Auto Engine Tuncup
 - Auto Technician

- AVIATION**
 - Aero-Engineering Technology
 - Aircraft & Engine Mechanic
- BUSINESS**
 - Accounting
 - Advertising
 - Business Administration
 - Business Management
 - Cost Accounting
 - Creative Salesmanship
 - Managing a Small Business
 - Professional Secretary
 - Public Accounting
 - Purchasing Agent
 - Salesmanship
 - Salesmanship and Management
 - Traffic Management
- CHEMICAL**
 - Analytical Chemistry
 - Chemical Engineering
 - Chem. Lab. Technician
 - Elements of Nuclear Energy
 - General Chemistry
 - Natural Gas Prod. and Trans.
 - Petroleum Prod. and Engr.
 - Professional Engineer (Chem)
 - Pulp and Paper Making

- CIVIL ENGINEERING**
 - Civil Engineering
 - Construction Engineering
 - Highway Engineering
 - Professional Engineer (Civil)
 - Reading Struc. Blueprints
 - Sanitary Engineer
 - Structural Engineering
 - Surveying and Mapping
- DRAFTING**
 - Aircraft Drafting
 - Architectural Drafting
 - Drafting & Machine Design
 - Electrical Drafting
 - Mechanical Drafting
 - Sheet Metal Drafting
 - Structural Drafting
- ELECTRICAL**
 - Electrical Engineering
 - Elec. Engr. Technician
 - Elec. Light and Power
 - Practical Electrician
 - Practical Lineman
 - Professional Engineer (Elec)
- HIGH SCHOOL**
 - High School Diploma

- Good English
- High School Mathematics
- High School Science
- Short Story Writing
- LEADERSHIP**
 - Industrial Foremanship
 - Industrial Supervision
 - Personnel-Labor Relations
 - Supervision
- MECHANICAL and SHOP**
 - Diesel Engines
 - Gas-Elec. Welding
 - Industrial Engineering
 - Industrial Instrumentation
 - Industrial Metallurgy
 - Industrial Safety
 - Machine Shop Practice
 - Mechanical Engineering
 - Professional Engineer (Mech)
 - Quality Control
 - Reading Shop Blueprints
 - Refrigeration and Air Conditioning
 - Tool Design
 - Tool Making
- RADIO, TELEVISION**
 - General Electronics Tech.

- Industrial Electronics
- Practical Radio-TV Eng'g
- Practical Telephony
- Radio-TV Servicing
- RAILROAD**
 - Car Inspector and Air Brake
 - Diesel Electrician
 - Diesel Engr. and Fireman
 - Diesel Locomotive
- STEAM and DIESEL POWER**
 - Combustion Engineering
 - Power Plant Engineer
 - Locom Fizing Technician
 - Stationary Diesel Engr.
 - Stationary Fireman
- TEXTILE**
 - Carding and Spinning
 - Cotton Manufacture
 - Cotton Warping and Weaving
 - Loom Fizing Technician
 - Textile Designing
 - Textile Finishing & Dyeing
 - Throwing
 - Warping and Weaving
 - Worsted Manufacturing

Name _____ Age _____ Home Address _____

City _____ Zone _____ State _____ Working Hours _____ A.M. to P.M. _____

Occupation _____ Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special low monthly tuition rates to members of the U. S. Armed Forces.



J. E. SMITH
Founder, National Radio Institute, Washington D.C.
Over 40 years' experience training men at home.

Mail Postage-Free Card for **SAMPLE LESSON FREE** *Shows you how easy, practical it is to* **Train at Home for RADIO TELEVISION ELECTRONICS**

Oldest and Largest Home Study Radio-Television Training School. N.R.I. has Trained Thousands for Good Pay Jobs

Since 1914 . . . for more than 40 years—N.R.I. has been training ambitious men at home in spare time for Radio-TV. Let us send you a sample lesson to help prove you can keep your job and TRAIN AT HOME in your spare time for better pay and a brighter future. We will also send N.R.I.'s 64-page catalog to show you that Radio-Television is today's field of OPPORTUNITY for properly trained men.


Television Making Good Jobs, Prosperity

The technical man is looked up to. He should be. He does important work, is respected for what he knows, gets good pay for it. There are splendid opportunities for the man well trained in Radio-Television Servicing or Broadcasting. Government, Aviation, Police, Ship, Micro-Wave Relay, Two-Way Communications for buses, taxis, trucks are growing Radio-TV fields, making more good jobs.


N.R.I. is the Tested Way to Better Pay

N.R.I. Training is practical, thorough. You get the benefit of N.R.I.'s 40 years' experience. Many successful N.R.I. men start without any knowledge of Radio, many without high school education. Find out what Radio-Television training can mean to you. Make the first move today toward becoming one of that select group—a Radio-TV Technician. Send postage-free card for Actual Lesson and 64-page Catalog, both FREE. NATIONAL RADIO INSTITUTE, Dept. DB83, Washington 16, D. C.

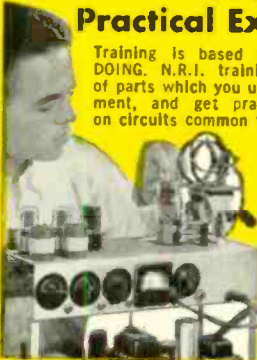Without Extra Charge NRI Sends Equipment for Practical Experience



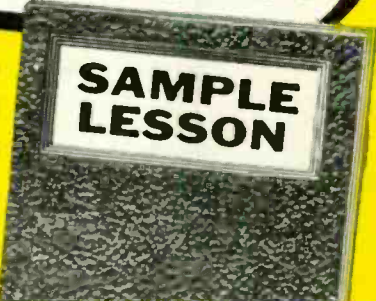Training is based on LEARNING-BY-DOING. N.R.I. training includes kits of parts which you use to build equipment, and get practical experience on circuits common to both Radio and Television. Shown at left is low-power Broadcasting Transmitter you build as part of N.R.I. Communications Course. FREE Catalog shows other equipment you get, things you learn.



WHAT N.R.I. GRADUATES DO AND SAY



Has Own Radio-TV Business

"We have an appliance store with Radio-TV servicing. During Army service, NRI training helped me get top rated job!"—W. M. WEIDNER, Fairfax, S. D.



Chief Engineer with KGGU

"I am Chief Engineer with station and also have my own spare time servicing business."—R. BARNETTE, Bismarck, N. D.



Paid for Instruments from Earnings

"I am doing very well in spare time. Sometimes have three TV jobs waiting, also fix car radios."—E. F. SEAMAN, N. Y., N. Y.

See Other Side

FIRST CLASS
Permit No. 20-R
(Sec. 34.9, P.L. & RJ)
Washington, D. C.

BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed In The United States

POSTAGE WILL BE PAID BY

NATIONAL RADIO INSTITUTE

Washington 16, D. C.





Learn Radio Television Electronics

by Practicing at Home

N.R.I. SENDS KITS with which you practice building circuits, common to Radio and Television. You LEARN-BY-DOING. As part of N.R.I. Servicing Course, you build Vacuum Tube Voltmeter and AC-DC Receiver shown here.

2 BOOKS FREE

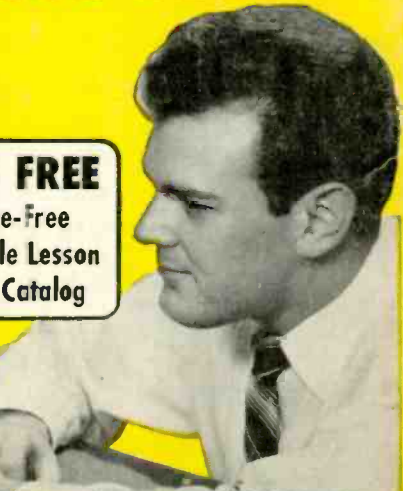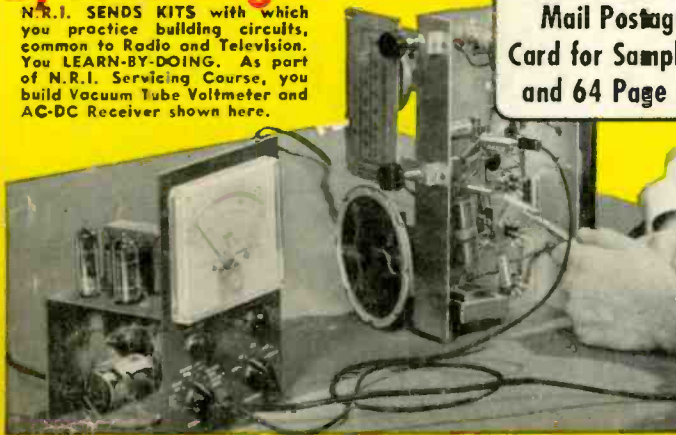Mail Postage-Free Card for Sample Lesson and 64 Page Catalog



Fast Growing Field Offers You Good Pay, Success, Bright Future

Bigger than ever and still growing. That's why Radio-Television has special appeal to ambitious men not satisfied with their future prospects. More than 4,000 Radio and TV Stations use trained technicians. 150 million home and auto Radios and 40 million TV sets must be kept in service. Color TV promises added opportunities. There are good jobs, bright futures in Radio-TV Servicing or Communications. Training PLUS Opportunity is the ideal combination for success. Plan now to get into Radio-TV. The technical man is looked up to, does important work, gets good pay. Keep your job while training. With N.R.I. you learn at home in spare time. N.R.I. is the OLDEST and LARGEST home study Radio-TV school. Its methods have proved successful for more than 40 years.



J. E. SMITH, Founder, N.R.I.

Many Good Jobs in Radio-TV Servicing and Communications for Trained Men



See Other Side

CUT OUT AND MAIL THIS CARD NOW

Sample Lesson & 64-Page Catalog

Both FREE

NO STAMP NEEDED—WE PAY POSTAGE

NATIONAL RADIO INSTITUTE
Dept. 0883, Washington 16, D. C.

Mail me Sample Lesson and 64-page Catalog. (No salesman will call. Please write plainly.)

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____

ACCREDITED MEMBER, NATIONAL HOME STUDY COUNCIL



Start Soon to Make \$10—\$15 a Week Extra in Your Spare Time

Soon after enrolling, many N.R.I. students start to earn \$10, \$15 a week in spare time fixing sets for friends and neighbors. Some make enough to start their own full time Radio-TV shops. Easy-to-understand lessons teach you basic principles. You LEARN-BY-DOING on N.R.I. equipment which "brings to life" things you study.

Find out what N.R.I. offers. Study fast or slow—as you like. Diploma when you graduate. Mail postage-free postcard now. **ACTUAL LESSON FREE.** Also 64-page catalog that shows opportunities, equipment you get. Cost of N.R.I. courses low. Easy terms. NATIONAL RADIO INSTITUTE, Dept. 0883, Washington 16, D. C.