

September

# SHORT WAVE ★ CRAFT

Edited by  
**HUGO**



**BEGINNING:**  
*A New Series*  
HOW TO BUILD and OPERATE  
**AMATEUR**  
TRANSMITTERS  
*for*  
**The BEGINNER**



*"Her Slave's Voice"*

NOW  
**25¢**  
IN CANADA  
30¢

IT IS always the well-trained man who wins out over the horde of thousands of superficially trained and incompetent men. You are reading this magazine because you are interested in radio. Sooner or later, the time will come when you will wish to cash in on your knowledge. Your chance may come over night, and then the big and vital question will be, "How well equipped am I to fill the job?" You are in radio because you like it. You also realize that, at the present time, there are many branches of the radio art which you do not know as thoroughly as you should. Knowledge, these days, can be gotten cheaper than ever before. It isn't necessary

# CUT PRICES ON RADIO BOOKS

for you to go to college to become proficient in radio. Start today, to build a REAL radio library and become acquainted with all branches of this great and growing art. In this page are listed the world's best radio books. We have combed the market for the really important books in radio; so that, no matter what branch you are interested in, you can pick out the best books that are now printed. Start, now, to build a complete radio library. You do not have to get all the books at once, but make up your mind to get one book a month; so that, when your chance comes, you will be fully equipped to win out over the others not so well equipped.

**IMPORTANT.—All prices have been drastically reduced—take advantage of it.**

**SHORT WAVE WIRELESS COMMUNICATION.** by A. W. Lader and C. R. Stoner. Cloth covers, size 6x9", 348 pages, 200 illustrations, 12 plates. Price..... **\$3.46**

Short wave experimenters who have grown out of 1-tube sets will revel in this book, which tells the "how come" of short-wave operation. A good portion of the volume is devoted to the amateur and commercial aspects of S. W. transmission.

**RADIO FREQUENCY ELECTRICAL REQUIREMENTS.** by Hugh A. Brown. Cloth covers, size 6x9", 386 pages, 235 illustrations. Price..... **\$3.90**

One of the few great books on this important subject. Everything from thermionic-tube coefficients to piezo-electric measurements.

**PRACTICAL TELEVISION.** by E. T. Lerner. Cloth covers, size 5 1/2 x 8 1/2", 223 pages. Price..... **\$3.69**

This book explains television in full, including elementary principles, photo-electric cells, and all important types of television sets as well as basic principles of optics, images, mirrors, lenses, etc.

**MAGNETIC PHENOMENA.** by Samuel Robinson Williams. Cloth covers, size 6x9", 230 pages, 150 illustrations, and numerous tables. Price..... **\$2.98**

All electric motors, coupling coils, magnetic and dynamic loud speakers, transformers, choke coils, etc., are dependent on magnetic phenomena. This fine book is complete on the subject.

**CINEMATOGRAPHY.** by James H. Cameron. Stiff covers, size 7 1/2 x 15", 240 pages, 150 illustrations. Price..... **\$3.90**

Everything on the subject from "silent" and "talkie" 16 mm. film to its manufacture and to the final projection is in this marvelous volume.

**AUDELS RADIOMAN'S GUIDE.** by Frank D. Graham. Cloth covers (flexible), size 5 1/2 x 8 1/2", 220 pages, 300 illustrations. Price..... **\$ .89**

A practical, concise book presenting the theoretical and practical information for the proper operation, maintenance and service as applied to modern radio practice.

**THE RADIO AMATEUR'S HANDBOOK.** (New Revised Edition), by A. Frederick Collins. Cloth covers, size 5 1/2 x 7 1/2", 394 pages, 116 illustrations. Price..... **\$1.97**

If you wish to become a radio amateur (radio ham) this book tells you how. Everything in re-receiving and transmitter sets and how to build them.

**EXPERIMENTAL RADIO.** by R. H. Ramsey, Prof. of Physics, Indiana University. Cloth covers, size 7 1/2 x 5 1/2", 256 pages, 168 illustrations. Price..... **\$2.69**

A marvelous book for the experimenter. Experiments follow in easy comprehensible language.

**RADIO THEORY AND OPERATION.** by M. T. Loomis. 5th revised edition. Cloth-bound; size 5 1/2 x 8 1/2", thick; 1,000 pages; over 800 illus.; 450 review questions and answers. Price..... **\$4.38**

Written in textbook style, a tremendous amount of useful information has been crammed into this thin-paper, compact reference work. Radio transmission and reception have been covered, "from soup to nuts." A truly great book.

**S. GERNSBACK'S RADIO ENCYCLOPEDIA** (Second Edition). 8th Morocco Flexible Binder, 352 pages, 2201 radio definitions, 1253 illustrations, 34 tables. Price..... **\$3.19**

The most comprehensive encyclopedia of its kind in print. Remarkably up-to-date in every way, with marvelous illustrations.

**DRAKE'S CYCLOPEDIA OF RADIO AND ELECTRONICS.** by H. P. Manly. Cloth covers, size 6x9", 1050 pages, 1080 illustrations. New 1932 Edition. Price..... **\$4.88**

The largest work of its kind ever put between two covers. New and up-to-date; a standby for every radio man.

**FUNDAMENTALS OF RADIO.** by R. R. Ramsey, Professor of Physics, Indiana University. Cloth covers, size 9 1/2 x 6", 372 pages, illustrated. Price prepaid..... **\$3.46**

The backbone of the radio art. This book gives you the foundation on radio from A to Z.

**RADIO OPERATING QUESTIONS AND ANSWERS.** (Revised Fifth Edition) by Nilson and Hornung. Cloth covers, size 5 1/2 x 8", 390 pages, 96 illustrations. Price..... **\$2.47**

Contains over 600 questions and answers covering all phases of licensed radio operation. Revised to contain much new material. Nothing better in print for the transmitting and receiving amateur.

**OFFICIAL RADIO SERVICE MANUAL.** Volume 1, by Hugo Gernsback and Clyde Fitch. Flexible loose-leaf binder, size 9 1/2 x 8", over 2,000 illustrations, 650 pages. COMPLETE WITH SIX SUPPLEMENTS. Price prepaid..... **\$4.38**

The Service Man's Bible. Greatest book ever published on the subject. Contains all old circuits of every inamenable commercial radio set up to 1931.

**THE RADIO MANUAL.** by George E. Sterling and Robt. S. Kruse. E.E. 2nd enlarged edition. Flexible fabrikoid covers. Size 5 1/2 x 8", 805 pages, 348 illustrations. Price..... **\$5.88**

A complete Radio Course for the operator, the technician, the amateur, the student and experimenter. Everything imaginable in the whole radio art is covered in this great book—the "radio Bible" of the amateur. DON'T MISS THIS.

**PRACTICAL RADIO CONSTRUCTION AND REPAIRING.** by J. A. Moyer, S.B., A.M., and J. F. Wostrel. Cloth covers, size 8x5", 354 pages, 163 illustrations. Price..... **\$2.47**

A handbook that every radio set tester and general student must have. The diagrams alone are worth the price of the book.

**THEORY OF VACUUM TUBE CIRCUITS.** by Leo James Peters. Cloth covers, size 6x9", 226 illustrations, 226 pages. Price..... **\$2.98**

It is one thing to "connect green lead No. 1 to pink lead No. 4," but it is another to know why the connections are made. Read this book and learn the design factors in tube circuits.

**PRINCIPLES OF RADIO COMMUNICATION.** by J. H. Morecroft, Prof. of Electrical Engineering, Columbia University. Cloth covers, size 9 1/2 x 6", 988 pages, profusely illustrated. Price..... **\$7.35**

THE radio classic, by the dean of radio. Covers entire radio art as does no other book.

**RADIO ENGINEERING HANDBOOK.** by Keith Henney. Flexible Leatherette, size 4 1/2 x 7 1/2", 581 pages, 482 illustrations. Price..... **\$4.88**

Each of the 23 sections has been written by a specialist! Includes valuable data on talkies and short waves.

**RADIO SERVICE MAN'S HANDBOOK WITH ADDENDA DATA SHEETS.** Flexible covers, size 9 1/2 x 12", 200 pages, 400 illustrations. Price prepaid..... **\$1.49**

The Service Man's standby. Contains the latest practical information on radio servicing.

**HOW TO PASS U.S. GOVERNMENT RADIO LICENSE EXAMINATIONS.** by R. L. Duncan and C. E. Drew. Flexible covers, size 9 1/2 x 7", 170 pages, 92 illustrations, appendix. Price..... **\$1.89**

The most important book on the subject ever published. Gives every conceivable angle which will help you to pass a radio license examination successfully.

**RADIO MOVIES AND TELEVISION.** by C. Francis Jenkins. Cloth covers, size 9 1/2 x 6", 144 pages, profusely illustrated. Price..... **\$.98**

A complete volume by the master of television, giving everything in detail for building your own television sets.

**RADIO PHYSICS COURSE** (2nd enlarged edition), by Alfred A. Ghirardi. Cloth covers, size 7 1/2 x 9 1/2", 392 pages, 510 illustrations, numerous tables. Price..... **\$3.46**

The finest and most popular book on electricity and radio. Each subject is clearly discussed, with the aid of dozens of excellent drawings. Chapters on talkies, television, electronics and service work, etc. Biggest buy in radio books.

**RADIO VISION.** by C. Francis Jenkins. Cloth covers, size 9 1/2 x 6", 144 pages, profusely illustrated. Price prepaid..... **89c**

An excellent book. The Jenkins television system, as well as many other modern television systems fully described.

We herewith present the most complete collection of recent important radio books. We have, after an exhaustive study, selected these volumes because they represent the foremost radio books of their kind in print today. There is such a great variety that we are sure it will satisfy any taste as well as any requirement that the student of radio might have. We publish no catalog and ask you to be kind enough to order direct from this page. Prompt shipments will be made to you direct from the publishers. We merely act as a clearing house for a number of radio publishers and OUR PRICES ARE AS LOW OR LOWER THAN WILL BE FOUND ANYWHERE. Remit by money order or certified check. Register all cash.

**SHORT WAVES.** by C. R. Leutz and R. H. Gable. Stiff covers. Size 6x9", 384 pages, 258 illustrations. Price..... **\$2.98**

The biggest and most complete book on short waves. Covers every imaginable phase, including S. W. Superheterodynes. The authors are famous S. W. authorities.

**FIRST PRINCIPLES OF TELEVISION.** by A. Dinsdale. Cloth covers, size 6x9", 212 pages, 130 illustrations, 38 plates. Price..... **\$3.46**

A real review of television in design, construction and operation. This amazingly comprehensive book contains many heretofore unpublished facts on this absorbing topic.

**ELECTRICITY AT HIGH PRESSURES AND FREQUENCIES.** by Henry L. Transtrom. Cloth covers, size 7 1/2 x 5 1/2", 248 pages, 141 illustrations. Price prepaid..... **\$2.33**

A marvelous book for the student in electricity and radio. General fundamentals lead up to a complete discussion of every type of Tesla and Oudin high-frequency coils, Geissler tubes, etc.; construction details of Tesla coils are given in great profusion. THE ONLY BOOK OF ITS KIND.

**OFFICIAL RADIO SERVICE MANUAL.** Volume II, by Hugo Gernsback, C. E. Denton and C. H. W. Nason, with 1932 Free Supplements, 1000 pages, 2000 illustrations, Flexible Loose-leaf Binder, size 9 1/2 x 12". Price..... **\$4.00**

The talk of the radio industry. This marvelous volume contains everything in radio, circuits and radio developments for 1932. Not a line of duplication between 1931 and 1932 volumes. (Vol. I and Vol. 2.)

**RADIO RECEIVING TUBES.** by Moyer and Wostrel. Cloth covers, size 7 1/2 x 5 1/2", 298 pages, 181 illustrations. Price..... **\$2.47**

One of the finest books on vacuum tubes. Everything worthwhile on the subject treated in a masterful manner.

**PHOTOCELLS AND THEIR APPLICATION.** (Second Edition), by V. K. Zworykin and E. D. Wilson. Cloth covers, size 5 1/2 x 8", 332 pages, 180 illustrations. Price..... **\$2.88**

Does this book tell you why and how to use light-sensitive cells? The answer is that the first edition was a "sell out," and the second edition brought right up to date, is even a better volume. Enough said.

**ELECTRONICS.** by R. C. Hudson. Cloth covers, size 6x9", 134 pages, 45 illustrations. Price..... **\$1.95**

"This book is written for the reader who may wish to know something about what is going on and who has not heretofore given the matter much attention," says the author. Read it and learn how dry rectifiers, vacuum tubes, batteries, television tubes, and other apparatus work; get the "low down" on electrons and atoms.

**RADIO SERVICING COURSE.** by Ghirardi and Freed. Cloth covers, size 5 1/2 x 7 1/2", 192 pages, 124 illustrations; 114 test Questions; 28 test-instrument circuit diagrams. Price..... **\$1.48**

A practical book beginners and old-timers in radio service will find useful. Nine chapters discuss measuring instruments and tests, and trouble-shooting; the chapter "Useful Information for Servicemen," closes the book.

**RADIO ENGINEERING.** by Frederick Emmons Terman. Cloth covers, size 6x9", 700 pages, 425 illustrations. Price..... **\$4.88**

Not a book for the beginner in radio, but a reference volume for the technician who wants modern information on the design and use of band-selectors, automatic volume control, diode detectors, and the thousand-and-one units and circuit arrangements which have been recently developed.

**PRINCIPLES OF RADIO.** by Keith Henney, M. A. Cloth covers, size 8 1/2 x 6", 478 pages, 396 illustrations. Price..... **\$3.46**

A marvelously written textbook with the latest radio principles including screen grid and pentode, amplifiers, etc.

## NEW LOW PRICE RADIO BOOKS

Here are 12 new, up-to-date books on every conceivable radio subject, just published. Modern in every sense. ALL BOOKS UNIFORM from 64 to 72 pages; 50 to 120 illustrations. All books written by well-known radio authors. Order by Number.

- No. 1 RADIO SET ANALYZERS, by I. Van Der Merwe
- No. 2 MODERN RADIO VACUUM TUBES, by Robert Hertzberg
- No. 3 THE SUPERHETERODYNE BOOK, by Clyde Fitch
- No. 4 MODERN RADIO HOOK-UPS, by R. D. Washburne
- No. 5 HOW TO BECOME A RADIO SERVICE MAN, by Louis Martin
- No. 6 BRINGING ELECTRIC (RADIO) SETS UP TO DATE, by Clifford E. Denton
- No. 7 RADIO KINKS & WRINKLES (for Experimenters) by C. W. Palmer
- No. 8 RADIO QUESTIONS & ANSWERS, by R. D. Washburne
- No. 9 AUTOMOBILE RADIO & SERVICING, by Louis Martin
- No. 10 HOME RECORDING AND ALL ABOUT IT, by Geo. J. Saliba
- No. 12 HOW TO BUILD AND OPERATE SHORT-WAVE RECEIVERS, by the Editors of SHORT WAVE CHART
- No. 13 HOW TO BECOME AN AMATEUR RADIO OPERATOR, by M. F. Eddy

PRICE PREPAID EACH BOOK..... **\$ .45**  
PRICE PREPAID FOR ALL 13 BOOKS..... **\$4.85**

### HOW TO ORDER

We cannot ship C. O. D. Our prices are net, as shown. Some of the books sent prepaid (in U. S. only). Those that are not thus listed will be shipped by express collect if sufficient postage is not included by you.

**FOUNDATIONS OF RADIO.** by Rudolph L. Duncan. Cloth covers, size 5 1/2 x 8", 216 pages, 145 illustrations. Numerous tables. Price..... **\$2.47**

This textbook gives you the fundamentals of electricity as applied to radio. It equips you for further study in the field of radio.

**EXPERIMENTAL RADIO ENGINEERING.** by John H. Morecroft. Cloth covers, size 6x9", 346 pages, 250 illustrations. Price..... **\$3.46**

A student's book; devoted to the principles of radio apparatus; intended to accompany a course in electricity. The best of its kind.

# I will train you at home

to fill a

# BIG PAY Radio Job!



**Here's Proof**



**\$50 to \$75 a Week**

"The National Radio Institute put me in a position to make more money than I ever made in good times. I am in the Radio service business for myself, where it is possible for me to make from \$50 to \$75 a week. Service work has increased because people who in normal times would buy a new Radio, now are contented to have the old one 'pepped up'."

Bernard Costa,  
150 Franklin Street,  
Brooklyn, N. Y.



**Runs Successful Radio Business**

"I am a member of the firm of South Grand Radio & Appliance Co., which runs a very successful business. The greater part of my success I owe to N.R.I. Without your training, I could never have been successful in Radio."

J. A. Vaughn,  
Grand Radio & App. Co.,  
3107 S. Grand Blvd.,  
St. Louis, Mo.



**Does Radio Work In Spare Time**

"I am operating a 120-acre farm. Three nights a week I teach a Radio class. On the other nights I make service calls. Words cannot express my gratitude to N.R.I. Your training prepared me to earn nice sums of cash in spare time."

Hoyt Moore,  
R.R. No. 3, Box 919,  
Indianapolis, Ind.



**Our Own Home**  
Pioneer and World's Largest Home-Study Radio training organization devoted entirely to training men and young men for good jobs in the Radio Industry. Our growth has paralleled Radio's growth. We occupy three hundred times as much floor space now as we did when organized in 1914.

If you are dissatisfied with your present job, if you are struggling along in a rut with little or no prospect of anything better than a skinny pay envelope—clip the coupon NOW. Get my big FREE book on the opportunities in Radio. Read how quickly you can learn at home in your spare time to be a Radio Expert—what good jobs my graduates have been getting—real jobs with real futures.

**Free Book Tells How Mail Coupon!**

**Many Radio Experts Make \$40, \$60, \$75 a Week**

In less than 15 years the Radio Industry has grown from a few million to hundreds of millions of dollars in business a year. Over 300,000 jobs have been created by this growth, and thousands more will be created by its continued development. Many men and young men with the right training—the kind of training I give you through N.R.I. method—have stepped into Radio at two and three times their former salaries.

**Get Ready Now for Jobs Like These**

Broadcasting stations use engineers, operators, station managers and pay up to \$5,000 a year. Manufacturers continually employ testers, inspectors, foremen, engineers, service men, buyers, for jobs paying up to \$7,500 a year. Radio operators on ships enjoy life, see the world, with board and lodging free, and get good pay besides. Dealers and jobbers employ service men, salesmen, buyers, managers, and pay up to \$100 a week. My book tells you about these and many other interesting Radio jobs.

**Many Make \$5, \$10, \$15 a Week Extra in Spare Time Almost at Once**

The day you enroll with me, I send you Instructions, which you should master quickly, for doing 28 Radio jobs common in most every neighborhood, for spare-time money. Throughout your training I send you information on servicing popular makes of sets. I give you the plans and ideas that have made \$200 to \$1,000 a year for N. R. I. men in their spare time. My Course is famous as the Course that pays for itself.


**Talking Movies, Television, Short Wave Money-Back Agreement Included**

Special training in Talking Movies, Television and Home Television experiments. Short Wave Radio, Radio's use in Aviation, Servicing and merchandising home and auto sets, Broadcasting, Commercial and Ship Stations are included. I am so sure that N. R. I. can train you satisfactorily that I will agree in writing to refund every Penny of your tuition if you are not satisfied with my Lessons and Instruction Service upon completion.

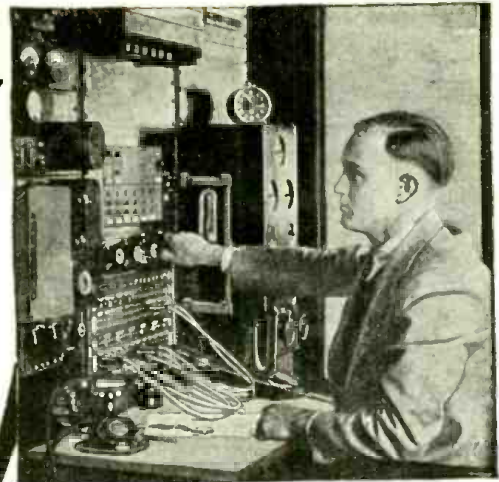**64-page Book of Information FREE**

Get your copy today. It's free to any ambitious fellow over 15 years old. It tells you about the opportunities in Radio; about my Course; what others who have taken it are doing and making. Find out what Radio offers you without the slightest obligation. ACT NOW!

**J. E. SMITH, President**  
National Radio Institute, Dept. 3JB3  
Washington, D. C.




**Special Free Offer**



Act now and receive in addition to my big free book, "Rich Rewards in Radio," this Service Manual on D.C., A.C., and Battery operated sets. Only my students could have this book in the past. Now readers of this magazine who mail the coupon will receive it free. Overcoming hum, noises of all kinds, fading signals, broad tuning, howls and oscillations, poor distance reception, distorted or muffled signals, poor Audio and Radio Frequency amplification and other vital information is contained in it. Get a free copy by mailing the coupon below.

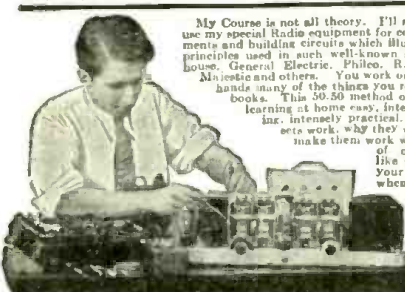**SPECIAL Radio Equipment for Broad Practical Experience Given Without Extra Charge**



My Course is not all theory. I'll show you how to use my special Radio equipment for conducting experiments and building circuits which illustrate important principles used in such well-known sets as Westinghouse, General Electric, Philco, R. C. A., Victor, Alnic and others. You work out with your own hands many of the things you read in our lesson books. This 60-50 method of training makes learning at home easy, interesting, fascinating, intensely practical. You learn how sets work, why they work, and how to make them work when they are out of order. Training like this shows up in your pay envelope—when you graduate you have had training and experience—You're not simply looking for a job where you can get extra per cent.

**I have doubled and tripled the salaries of many. Find out about this tested way to BIGGER PAY**



**FILL OUT AND MAIL THIS COUPON TODAY**



**J. E. SMITH, President**  
National Radio Institute, Dept. 3JB3  
Washington, D. C.

Dear Mr. Smith: I want to take advantage of your Special Free Offer. Send me your manual "Trouble Shooting in D.C., A.C. and Battery Sets" and your book "Rich Rewards in Radio," which explains Radio's Opportunities for bigger pay and your method of training men at home in spare time. I understand this request does not obligate me. (Please print plainly)

Name.....ge.....

Address.....

City.....State....."M"

**The Famous Course That Pays For Itself**

**IN THIS ISSUE: PROMINENT SHORT-WAVE AUTHORS**  
**Mouromtseff • Worcester • Victor • Shuart • Denton • Palmer**



**HUGO GERNSBACK**  
 Editor

**H. WINFIELD SECOR**  
 Managing Editor

**Contents for September, 1933**

Editorial—The Short Wave Amateur, by Hugo Gernsback .....	265
3 ½ Inch Waves Now Practical, by I. E. Mouromtseff, Research Department, Westinghouse Electric & Mfg. Co. ....	266
The "PENTAFLEX"—In Which 1-Tube Equals 2, by J. A. Worcester, Jr. ....	268
AMATEUR TRANSMITTERS—How To Build, Install, and Operate Them, by Leonard Victor, W2DHN ....	270
The "Monitor"—How To Build and Use It .....	273
This 3-Tube SUPERHET Has "IT", by George W. Shuart, W2AMN, W2CBC .....	274
The Acratone DISCOVERER S-W Receiver, by Clifford E. Denton .....	276
Leotone 2-Volt Set Has "Pep" .....	278
2-Tube A.C. Receiver Works on Your B.C. Audio, by Henry J. Wagner .....	279
Attention! All Squads! By Fred E. Ebel, W9CZU ....	280
World-Wide Short-Wave Review, edited by C. W. Palmer .....	282
An Ultra Short-Wave Converter .....	284
Hats Off To Catharine Martin! Builder of 200 Sets ....	285
What's New In Short-Wave Apparatus .....	286
Letters From S-W Fans .....	288
SHORT WAVE STATIONS OF THE WORLD—"Up-to-date" List .....	290
\$5.00 For Best S-W Kink Monthly .....	293
SHORT WAVE LEAGUE—New Amateur Regulations.....	294
Making An Automatic Key .....	295
Short-Wave QUESTION BOX .....	296
"When To Listen In," by Robert Hertzberg.....	313
Swappers .....	318

**FEATURES IN NEXT ISSUE**

- Second of the series—AMATEUR TRANSMITTERS—"How To Build the Power Amplifier" and also "How To Calibrate the Monitor," by Leonard Victor, W2DHN.
- The "53 Twinplex," by J. E. Worcester, Jr.
- The Miller 7-Tube Short-Wave Superhet.
- The RT Low-Cost 15 to 30 Watt Phone & C. W. Transmitter (For All Amateur Bands), by George W. Shuart, W2AMN, W2CBC.
- The Measurement of Ultra Short Waves, by C. C. Whitehead.
- Results of Test With Empire State Building U. S. W. Transmitter.
- The 5-Tube Portable S-W Superhet, by Clifford E. Denton.



**Certified Circuits**

● **SHORT WAVE CRAFT** goes to a large expense in verifying new circuits published in this magazine. Whenever you see the seal shown here in connection with any of the sets published in this and future issues of **SHORT WAVE CRAFT**, this will be your guarantee that this set has been tested in our laboratories, as well as privately, in different parts of the country to make sure that the circuit and selected parts are right. Only "Constructional-Experimental" circuits are certified by us.

When you see our certificate seal on any set described you need not hesitate in spending money for parts, because you are assured in advance that the set and circuit are bona fide and that this magazine stands behind it.

**SHORT WAVE CRAFT** is the only magazine that thus certifies circuits and sets.

**OUR COVER**

● **OUR** cover picture illustrates "Her Slave's Voice," a paraphrase on the famous Victor slogan, "His Master's Voice." We don't know who the fortunate young lady is who has for her beau the radio amateur who is throwing kisses to her over his radiophone transmitter, but we imagine that this scene would be oft repeated if the young lady in question happened to be as comely as the one whose likeness appears in the picture, who happens to be Miss Jane Froman, "N.B.C." radio star, who has been called the "most beautiful star on the air."

COPYRIGHT, 1933, BY H. GERNSBACK


Published by **POPULAR BOOK CORPORATION**

**HUGO GERNSBACK**, President - - **H. W. SECOR**, Vice-President  
**EMIL GROSSMAN** - - - - - Director of Advertising  
 Chicago Adv. Office - - - **L. F. McCLURE**, 737 No. Michigan Blvd.  
 Publication Office - - - 404 N. Wesley Avenue, Mount Morris, Ill.  
 Editorial and General Offices - - 96-98 Park Place, New York, N. Y.  
 London Agent: **HACHETTE & CIE.**, 16-17 King William St., Charing Cross, W.C.2

Paris Agent: **HACHETTE & CIE.**, 111 Rue Reaumur  
 Australian Agents: **McGILL'S AGENCY**, 179 Elizabeth St., Melbourne

**SHORT-WAVE CRAFT**—Monthly. Entered as second class matter May 7, 1930, at the post office at Mount Morris, Illinois, under the act of March 3, 1879. Trademarks and copyrights by permission of H. Gernsback, 98 Park Place, N. Y. C. Text and illustrations of this magazine are copyrighted and must not be reproduced without permission. **SHORT WAVE CRAFT** is published on the 15th of every month. Twelve numbers per year. Subscription price is \$2.50 a year in the United States and possessions. Canada and foreign countries, \$3.00 a year. Single copies 25c. Address all contributions for publication to Editor, **SHORT WAVE CRAFT**, 96-98 Park Place, New York, N. Y. Publishers are not responsible for lost manuscripts. Contributions cannot be returned unless authors remit full postage. **SHORT WAVE CRAFT** is for sale at all principal newsstands in the United States and Canada. European agents: Brentano's, London and Paris. Printed in U. S. A. Make all subscription checks payable to Popular Book Corporation.
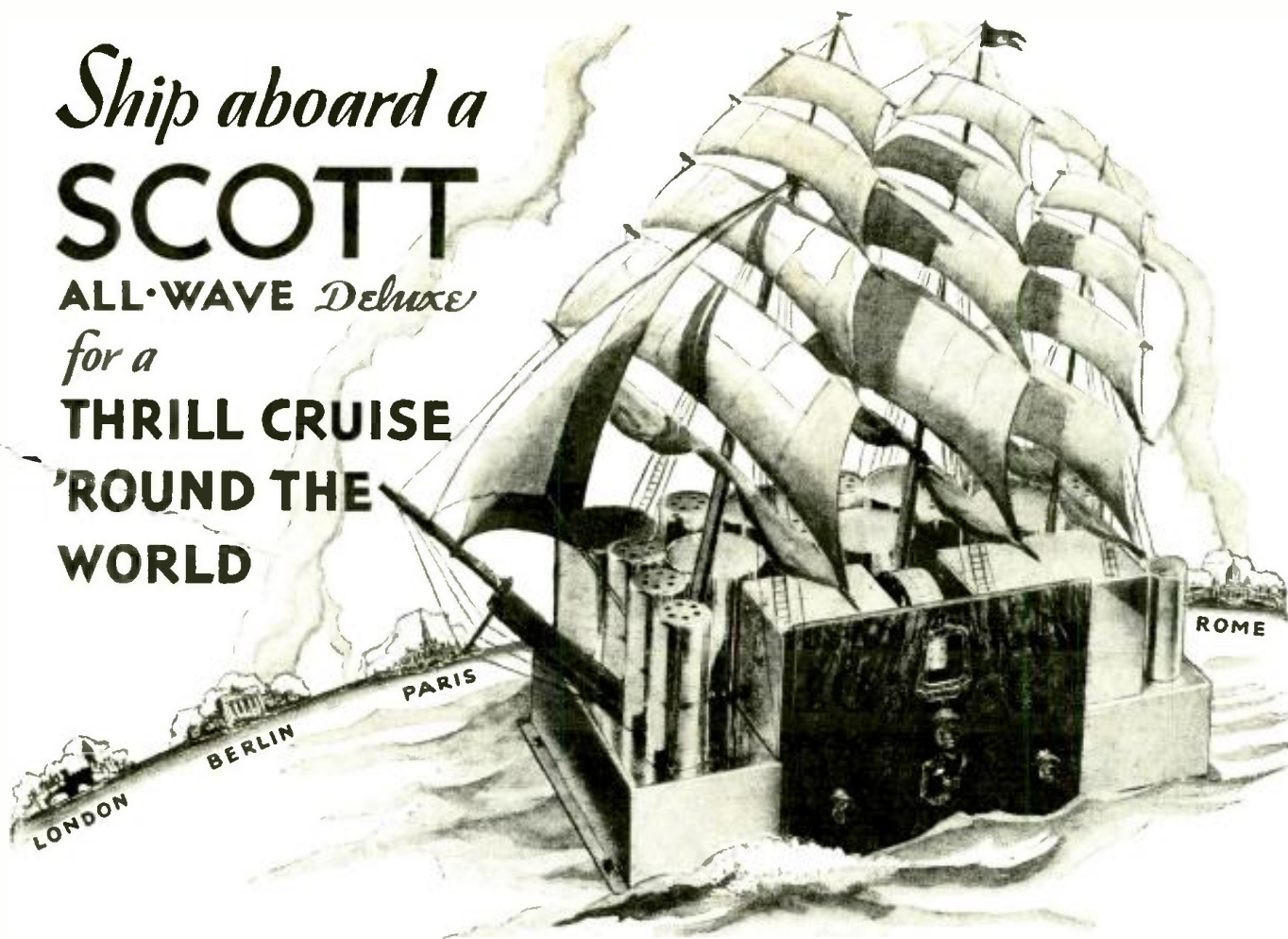
# Ship aboard a SCOTT ALL-WAVE *Deluxe* for a THRILL CRUISE 'ROUND THE WORLD



If you're an adventurer at heart (and aren't we all!) you'll glory in the thrills of cruising the ether-waves via a SCOTT ALL-WAVE *Deluxe* Radio.

Sit right in your own comfortable living room . . . there's no sea-bag to pack, no dunnage to stow, no passports to secure. Just the twist of a single, simple tuning dial and it's "Ho! You're off for strange lands of romance and allure!"

### Supreme for Stay-at-Home Listeners

First a shake-down cruise in home waters. Listen in on American broadcast stations near and far—coast-to-coast is an easy jaunt. Discover the marvelous capability of this dream ship to carry you anywhere at your will . . . with a delightful fidelity of tone that puts you right into the sending studio, giving you every word of speech and every note of music with a glorious perfection that transcends all previous heights of mechanical sound reproduction. Your own ears will tell you so . . . and the evidence is backed up by scientific laboratory findings that prove SCOTT radio reproduction to be the closest to perfection yet attained.

As a first venture in short wave reception listen-in on the crime wave as reported by police calls from one end of the land to the other . . . eavesdrop on gossipy amateur wireless telephony "hams", and hear the air-planes and their ground stations talk back and forth.

### Hear Canada and Mexico

Now venture farther! Roam the air-waves to Canada and Mexico. Hear something different . . . something typical of these near-by foreign lands broadcast on wave bands from 15 to 550 meters. Don't fret about the rumors you may have heard that these countries are soon to change wave-lengths . . . your SCOTT can be equipped to receive on all bands between 15 and 4,000 meters at a small extra charge.

### Listen-in On All of Europe

And now you've "got the feel of your ship." Head out into the open . . . start on a fascinating exploration cruise for radio joys that are new and different.

Here's England, first! GSB, at Daventry, is sending out the news of the day for the benefit of Colonial

listeners-in . . . there's peppy music from a famous London hotel . . . and at signing off time (midnight in London, but only 6 P.M. Central Standard Time) the chimes of Big Ben, atop the Houses of Parliament, clang sonorously as though you were actually there to hear them in person.

Slip your moorings once again. Cross the Channel and lend an ear to Radio Colonial, Pointoise, France. It's bringing you Parisian music and typically French entertainment.

### Varied Programs from Far Countries

Distance still lures you? Then set your course for Germany . . . in a jiffy you're listening to Zeesen, with programs of glorious symphony orchestras, and perhaps a speech by "Handsome Adolph" that will give you a different viewpoint on Hitlerism.

Make port at Madrid, in sunny Spain, and hear EAQ broadcasting typical National music. Announcements from this station are considerably made in English as well as Spanish.

Then swing south to Rome and hear the voice of 12RO's woman announcer tell you it's "Radio Roma, Napoli," that's on the air. Most likely the following musical program will be opera direct from LaScala, in Milan, or some other musical treat worth going actual miles to hear—and you'll be listening to it, with purity of tone and richness of reproduction that's truly amazing, without stirring from your easy chair at home.

And now for an adventure-trek that holds a supreme "kick" for the radio sensation-seeker! Sail away "down under." Listen in to VK2ME or VK3ME, in Sydney and Melbourne, Australia. Hear the call of that famous Kookaburra bird, listen with delight to an interesting and varied program of music and talks on the commercial and scenic attractions of the Antipodes.

### Owners' Reports Show Real Ability

And these are but a few of the interesting places to be visited by means of your SCOTT ALL-WAVE *Deluxe* Receiver . . . F. L. Stitzinger, for instance, is a Scott owner who in a six-month's period received 1588 programs from 41 stations in 22 foreign lands. A. G. Luoma got 1261 programs from 75 different stations in 26 countries, and some 200 other SCOTT owners reported reception of 16,439 programs from 320 stations in 46 countries during the same time.

"Can such startling radio performance be true?"

you ask. Do you doubt that any but radio professionals can enjoy the delights of exploring the air-waves the world over, far from the too-familiar programs of broadcast stations here at home? Do you think that it may be possible, but feel that the cost of sufficiently able equipment is more than you can afford for entertainment?

### New Value at Moderate Cost!

Then set your mind at ease! For such performance is actually possible . . . we gladly prove it to you, and back the proof by an iron-clad guarantee of consistent foreign reception.

Laboratory technique, employing the world's most skillful, specially trained engineers and craftsmen in custom-building a receiver constructed to the highest standards of perfection known in radio, makes possible the super-performance of the SCOTT ALL-WAVE *Deluxe* for any radio-user, regardless of his experience or skill in operating. In this set top efficiency is coupled with absolute simplicity of tuning.

Prohibitively high priced? Not at all! You can have a SCOTT, and enjoy the supreme thrill of mastering the air-waves of all the world, at moderate cost.

### Get Complete Details—Mail Coupon!

Because the SCOTT ALL-WAVE *Deluxe* is one of the truly fine things of the world, custom-built for those discriminating people who demand the best, it is not distributed broadcast, to be casually picked up here, there, or anywhere. To get full particulars regarding it, absolute PROOF of its performance, and all the information you require, simply send the coupon below direct to the modern scientific laboratories where it is built.

E. H. SCOTT RADIO LABORATORIES, INC.  
4450 Ravenswood Ave., Dept. S.W.C.-93, Chicago, Ill.


Tell me how I can have a SCOTT ALL-WAVE *Deluxe* to take me radio world-cruising. Include all technical details, proofs of performance, and complete information.

Name.....  
Address.....  
City..... State.....

# NEW!

## SUPER *Deluxe* 16-TUBE ALL-WAVE RADIO

### WORLD-WIDE RECEPTION ...

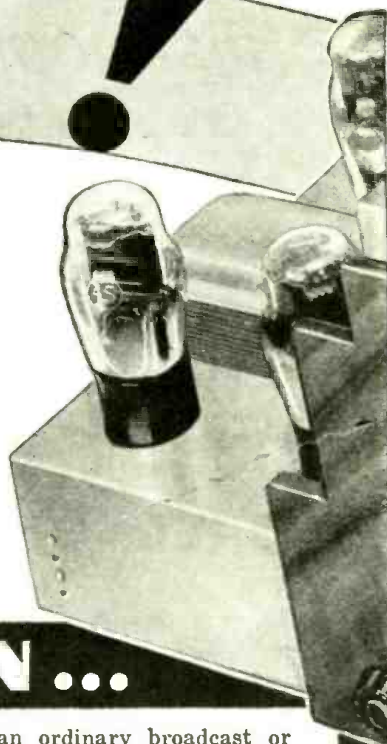

**BUY** your radio direct from the Midwest Laboratories and save from 30% to 50%. This Super, Deluxe 16-Tube ALL-WAVE Radio makes it easy to secure clear, loud-speaker reception from stations 10,000 miles and more distant. It gives you complete wave length coverage of 9 to 2000 meters (33 megacycles to 150 KC)—enabling you to secure almost magical radio performance! Midwest users regularly log such stations as: GSC, London—VK2ME, Sydney, Australia—JIAA, Tokio, Japan—RW50, Moscow Russia—DJB, Berlin, etc. Never before so much radio for so little money! Send coupon today!

Why be satisfied with an ordinary broadcast or "dual" wave set when you can have this super-powerful 16-Tube Deluxe ALL-WAVE Midwest radio? It puts the whole world of radio at your finger tips. It has FIVE distinct wave bands—ultra short, short, medium, broadcast and long—all tuned with a single dial! You can switch instantly from U. S. programs—Canadian, police, amateur, commercial airplane and ship broadcasts—to the finest short wave programs from Australia, Japan, Russia, Italy, Germany, France, England, South America, etc.

### 40 New 1934 Features

These sensational new features give you amazing performance, perfect realism, new beauty of tone, new wealth of power, fractional microvolt sensitivity, better than 7 KC selectivity. For example—Automatic SELECT-O-BAND (exclusive with Midwest) simplifies short wave tuning by instantly pointing out wave length of station. Amplified AUTOMATIC VOLUME CONTROL keeps volume at pre-determined level over wide range of signal inputs, prevents "fading" and interstation "blasting." Some of the other features include:


Automatic Select-O-Band Indicator  
All-wave 9 to 2,000 meter tuning range  
(33 megacycles to 150 KC)  
Five Full Wave Bands  
Illuminated Frequency Indicator  
Station Group Locator  
Dial Frequency Calibration in Kilocycles and Megacycles  
Balanced Unit Super Heterodyne Circuit  
Slow Motion, Velvety action Tuning  
Positive Amplified Automatic Volume Control, Fully Delayed

New and Improved Electro-dynamic Auditorium Speaker  
Latest Type, Higher Efficiency Tubes  
7 KC Selectivity, Automatically Adjusted Scientifically Shielded (Coils and Switch Catacombed)  
Positive Signal Control  
Litzendraught I.F. Transformers, R.F. Coils, and Oscillators  
Stat-O-Mit Interstation Silencer  
Super Power Class "A" Audio Amplifier  
29 Tuned Circuits . . . 10 in Cascade—3 Variable  
All Police and Airplane Bands  
New Duplex—Diode—High Mu Pentode

All short and Ultra Short American and European Bands.  
Fractional Microvolt Sensitivity  
Perfect Tone Quality . . . at low volume levels (Low Volume Compensator)  
16-Tubes . . . Equivalent to 18 tubes  
New Thermionic Rectifier  
Simplified, Centralized Tuning—No Vernier, No Auxiliary Tuning.  
Absolute Minimum of Background Noises  
Low Operating Cost
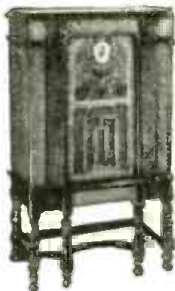
#### New Style Consoles

The new, big Midwest 1934 catalog shows a complete line of beautiful artistic, de luxe consoles . . . in the new modernistic designs. Hand made by Master Craftsmen, they lend distinction and dignity to any home. Save 30% to 50% by ordering direct from Midwest Laboratories. Mail the coupon today.




The new Super Deluxe 16-Tube Midwest ALL-WAVE radio positively gives you more features and more advantages than sets selling in stores at two to three times Midwest's sensationally low price! Don't try any radio until you get all the facts! Write for the new Midwest 1934 catalog. You'll be amazed at the unbelievably low direct-from-Midwest Laboratories Prices. They save you from 30% to 50%.



#### "OUT-PERFORMS \$200.00 SET"

"Am writing this unsolicited letter in regard to my Midwest radio. It is more than you claim for it in many regards. It is more selective than any radio that I have come in contact with. It will whip or out-perform any set even above the \$200.00 class and it must be great when your competitor owns up that it is superior to any machine that he sells. I have received South American stations and European stations during the short time that I have had the set. I consider that the Radio is worth three times what you ask for it."—L. E. Wallace (Member I.R.E.), 1521 S. W. 7th St., Miami, Fla.

# MIDWEST RADIO CORP.

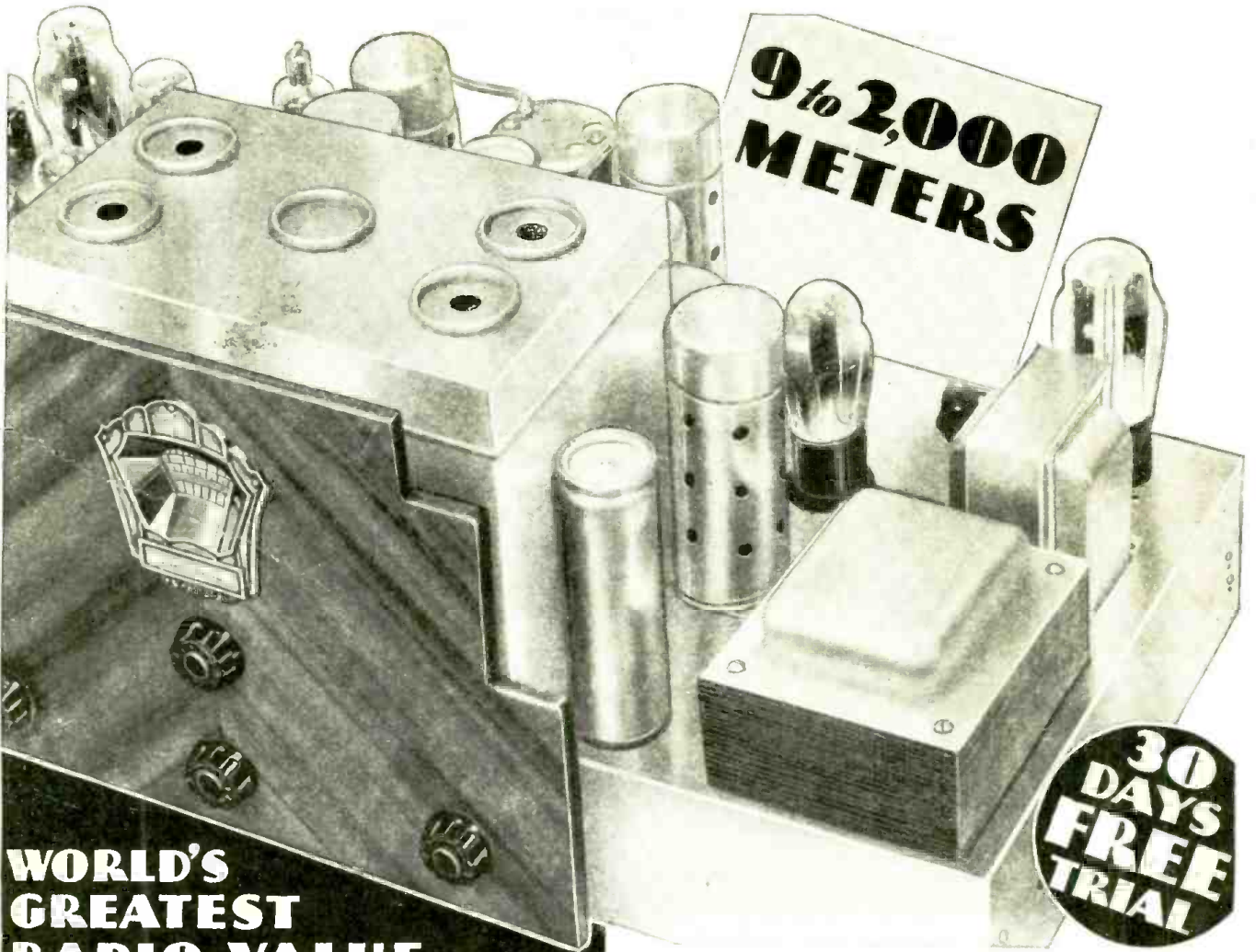

**WORLD'S  
GREATEST  
RADIO VALUE ...**

**\$49.50** \*  
*with New  
Deluxe  
Auditorium Type  
SPEAKER*

*Deal Direct with Laboratories*

**SAVE  
UP TO 50%**

Get a bigger, better, more powerful, clearer-toned radio—at a positive saving of from 30% to 50%. Buy now while you can take advantage of the tremendous values Midwest offers you. No middlemen's profits to pay. Present inflationary legislation is sure to result in higher prices. Try any Midwest Radio for 30 days—FREE—before you decide. As little as \$5.00 puts a set in your home. Satisfaction guaranteed or money back! Just sign and mail coupon—or send name and address on postcard.

(\*Canadian Prices Slightly Higher.)

Midwest guarantees your satisfaction by permitting you to try any Midwest set—right in your own home—on 30 days FREE trial. Thousands upon thousands of delighted Midwest owners all over the U. S. and in many foreign countries are daily enjoying the world's finest radio programs because of Midwest's revolutionary policy of selling direct from the laboratory at rock-bottom prices—and on easy terms. But don't judge quality by price. Even though we offer unbelievably low prices, Midwest Radios are of the very highest quality and positively guaranteed. When you buy from Midwest, you deal with one of the old-established, pioneer radio builders who has been selling quality sets all over the world for more than fourteen years. Mail the coupon or write us a postal for new 1934 catalog, easy terms and low laboratory prices.

**Terms  
AS LOW AS  
\$5.00  
DOWN**

**Get All the Facts  
NOW!**

**RUSH THIS COUPON FOR  
AMAZING 30-DAY FREE TRIAL  
OFFER AND NEW 1934 CATALOG**

Midwest Radio Corp.,  
Dept. 239,  
Cincinnati, Ohio.  
Without obligation on my part send me your  
new FREE 1934 catalog, and complete details  
of your liberal 30-day FREE trial offer. This  
is NOT an order.

Name.....  
Address.....  
City.....  
State.....

**AGENTS! Make Easy Extra Money.  
Check Here For Details ( )**

**DEPT. 239 — CINCINNATI, OHIO, U. S. A.**  
Established 1920 Cable Address Miraco. ABC 5th Edition





# OPPORTUNITIES *are many* for the Radio Trained Man



Don't spend your life slaving away in some dull, hopeless job! Don't be satisfied to work for a mere \$20 or \$30 a week. Let me show you how to get your start in Radio—the fastest-growing, biggest money-making game on earth.

## Jobs Leading to Salaries of \$50 a Week and Up

Prepare for jobs as Designer, Inspector and Tester—as Radio Salesman and in Service and Installation Work—as Operator or Manager of a Broadcasting Station—as Wireless Operator on a Ship or Airplane, or in Talking Picture or Sound Work—HUNDREDS OF OPPORTUNITIES for a real future in Radio!

## Ten Weeks of Shop Training Pay Your Tuition After Graduation

We don't teach by book study. We train you on a great outlay of Radio, Television and Sound equipment—on scores of modern Radio Receivers, huge Broadcasting equipment, the very latest and newest Television apparatus, Talking Picture and Sound Reproduction equipment, Code Practice equipment, etc. You don't need advanced education or previous experience. We give you—RIGHT HERE IN THE COYNE SHOPS—the actual practice and experience you'll need for your start in this great field. And because we cut out all useless theory and only give that which is necessary you get a practical training in 10 weeks.

# TELEVISION *and* TALKING PICTURES

And Television is already here! Soon there'll be a demand for THOUSANDS of TELEVISION EXPERTS! The man who learns Television now can have a great future in this great new field. Get in on the ground-floor of this amazing new Radio development! Come to COYNE and learn Television on the very latest, newest Television equipment. Talking Picture and Public Address Systems offer opportunities to the Trained Radio Man. Here is a great new Radio field just beginning to grow! Prepare NOW for these wonderful opportunities! Learn Radio Sound Work at COYNE on actual Talking Picture and Sound Reproduction equipment.

## PAY FOR YOUR TRAINING After You Graduate

I am making an offer that no other school has dared to do. I'll take you here in my shops and give you this training and you pay your tuition after you have graduated. Two months after you complete my course you make your first payment, and then you have ten months to complete your payments. There are no strings to this offer. I know a lot of honest fellows haven't got a lot of money these days, but still want to prepare themselves for a real job so they won't have to worry about hard times or lay offs.

I've got enough confidence in these fellows and in my training to give them the training they need and pay me back after they have their training.

If you who read this advertisement are really interested in your future here is the chance of a life time. Mail the coupon today and I'll give you all the facts.

## ALL PRACTICAL WORK At COYNE in Chicago

ALL ACTUAL, PRACTICAL WORK. You build radio sets, install and service them. You actually operate great Broadcasting equipment. You construct Television Receiving Sets and actually transmit your own Television programs over our modern Television equipment. You work on real Talking Picture machines and Sound equipment. You learn Wireless Operating on actual Code Practice apparatus. We

don't waste time on useless theory. We give you the practical training you'll need—in 10 short, pleasant weeks.

## MANY EARN WHILE LEARNING

You get Free Employment Service for Life. And don't let lack of money stop you. Many of our students make all or a good part of their living expenses while going to school and if you should need this help just write to me. Coyne is 33 years old. Coyne Training is tested—proven beyond all doubt. You can find out everything absolutely free. Just mail coupon for my big free book!

H. C. Lewis, Pres. RADIO DIVISION Founded 1899

## COYNE Electrical School

500 S. Paulina St., Dept. 63-2K, Chicago, Ill.

Mail Coupon Today for All the Facts

H. C. LEWIS, President

Radio Division, Coyne Electrical School  
500 S. Paulina St., Dept. 63-2K, Chicago, Ill.

Dear Mr. Lewis:— Send me your Big Free Radio Book, and all details of your Special Offer.

Name.....


Address.....

City.....State.....

**NOW  
READY**

**The Two NEW SHORT WAVE BOOKS**


**Here is Great News!**

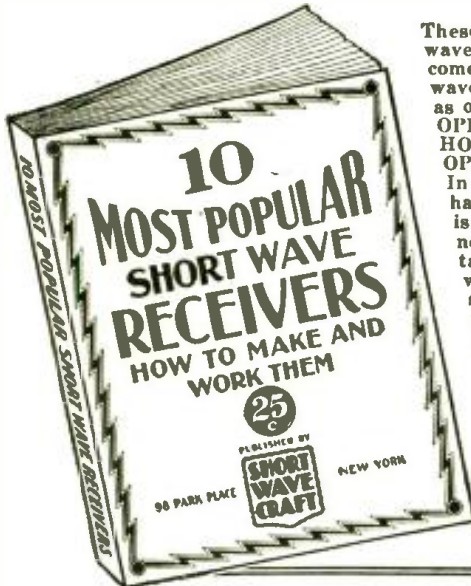

These new books contain everything on short waves worth knowing and the books will be welcomed by all short wave experimenters, short wave fans and short wave enthusiasts, the same as our former two books HOW TO BUILD AND OPERATE SHORT WAVE RECEIVERS, and HOW TO BECOME AN AMATEUR RADIO OPERATOR.

In conformity with the times these books have been priced at 25c instead of 50c, which is the price of our other books. Yet the two new 25c volumes that we are offering, contain a tremendous amount of information, with the type and illustrations chosen in such a manner as to give you almost as much for your 25c as you received for your 50c before. Only by increasing the press run enormously and making other printing economies has it been possible to price these books at such a low, popular price.

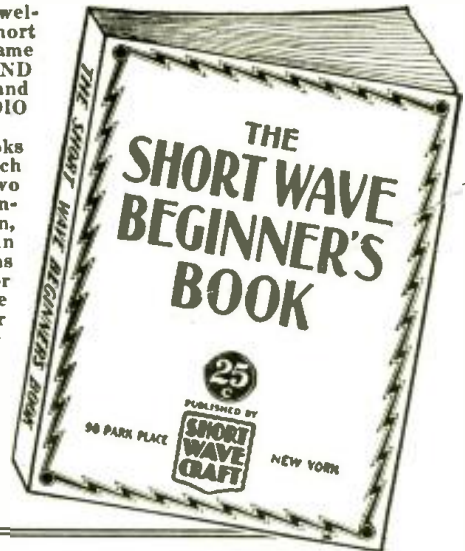You make no mistake in getting either or both of these new and popular books and we know from our many years of experience with short wave enthusiasts that you will thank us for having made these books possible.



**Ten Most Popular Short Wave Receivers. How to Make and Work Them**

This new volume is a revelation to those who wish to build their own short wave receivers. The editors of SHORT WAVE CRAFT over a period of years have learned to know what short wave experimenters and set builders want. They have selected ten outstanding short wave receivers and these are described in the new volume. Everything worthwhile about every one of the ten receivers is described in the text. Each receiver is fully illustrated with a complete layout, pictorial representation, photographs of the set complete, hookup and all worthwhile specifications. Everything from the simplest one tube set to a 5-tube T. R. F. receiver is presented. Complete lists of parts are given to make each set complete. Select any or all receivers and know beforehand that you will be able to successfully build and operate such a receiver and not waste your money. You are shown how to operate the receiver to its maximum efficiency.

**CONTENTS**

- The Doerle 2-Tube Receiver That Reaches the 12,500 Mile Mark. by Walter C. Doerle.
- 2-R.F. Pentode SW Receiver having two stages of Tuned Radio Frequency, by Clifford E. Denton and H. W. Secor.
- My de Luxe S-W Receiver, by Edward G. Ingram.
- The Binneweg 2-Tube 12,000 Mile DX Receiver, by A. Binneweg, Jr.
- Build a Short Wave Receiver in your "Brief-Case," by Hugo Gernsback and Clifford E. Denton.
- The Denton 2-Tube All-Wave Receiver, by Clifford E. Denton.
- The Denton "Stand-By," by Clifford E. Denton.
- The "Stand-By" Electrified.
- The Short Wave MEGADYNE, by Hugo Gernsback.
- A COAT-POCKET Short Wave Receiver, by Hugo Gernsback and Clifford E. Denton.
- Boy, Do They Roll In on this One Tube! By C. E. Denton.
- The S-W PENTODE-4, by H. G. Cisin, M. E.
- Louis Martin's Idea of A GOOD S-W RECEIVER, by Louis Martin.

**IMPORTANT**

THERE IS NO DUPLICATION BETWEEN THIS BOOK AND OUR OTHER VOLUME—"HOW TO BUILD AND OPERATE SHORT WAVE RECEIVERS." ALL THE MATERIAL PUBLISHED IN THE NEW BOOK HAS NEVER APPEARED IN ANY BOOK BEFORE.

**PRICE 25c PREPAID 40 PAGES OVER 75 ILLUSTRATIONS**

**The Short Wave Beginner's Book**

Here is a book that will solve your short wave problems. It contains everything that you would wish to know in connection with short waves, leading you in easy stages from the simplest fundamentals to the present stage of the art as it is known today. It is the only low-priced reference book on short waves for the beginner.

The book is profusely illustrated with all sorts of photos, explanations and everything worthwhile knowing about short waves—the book is not "technical." It has no mathematics, no "high-faluting" language and no technical jargon. Wherever technical words are used, explanations are given. You are shown how to interpret a diagram and a few simple sets are also given to show you how to go about it in making them. Everything has been done to make it possible to give you a complete, fundamental understanding of short waves.

After reading this book, you will never be at a loss for short wave terms, or will have to consult other text-books or dictionaries. The editors of SHORT WAVE CRAFT who have edited this book have seen to it that everything has been done to make this volume an important one that will be used as reference for years to come.

It abounds with many illustrations, photographs, simple charts, hookups, etc., all in simple language. It also gives you a tremendous amount of very important information which you usually do not find in other books, such as time conversion tables, all about aeriels, noise elimination, how to get verification cards from foreign stations, all about radio tubes, data on coil winding and dozens of other subjects.

**Partial List of Contents**

- Getting Started in Short Waves—the fundamentals of electricity.
- Symbols, the Short Hand of Radio—how to read schematic diagrams.
- Short Wave Coils—various types and kinks in making them.
- Short Wave Aeriels—the points that determine a good aerial from an inefficient one.
- The Transposed Lead-in for reducing Man Made Static.
- The Beginner's Short-Wave Receiver—a simple one tube set that anyone can build.
- The Beginner's Set Gets an Amplifier—how the volume may be increased by adding an amplifier.
- How to Tune the Short-Wave Set—telling the important points to get good results.
- Regeneration Control in Short Wave Receivers.
- Audio Amplifiers for S. W. Receivers.
- How to Couple the Speaker to the set.
- Learning the Code—for greater enjoyment with the S-W set.
- Wave length to Kilocycle Chart.
- Wire Chart—to assist in the construction of coils.
- Kinks in the construction of S-W Receivers.

**PRICE 25c PREPAID 40 PAGES OVER 75 ILLUSTRATIONS**

**Mail Coupon Today!**

SHORT WAVE CRAFT SW-9-33  
96-98 Park Place, New York City.  
Gentlemen:

I enclose herewith 25c. for which please send me prepaid, a copy of your new book "Ten Most Popular Short Wave Receivers. How to Make and Work Them."

I enclose herewith 25c for which please send me prepaid, a copy of your new book "The Short Wave Beginner's Book."

I enclose 50c for which please send me, prepaid, your two books, "Ten Most Popular Short Wave Receivers. How to Make and Work Them," and "The Short Wave Beginner's Book."

(Send money order, check, cash or new U. S. stamps. Register letter if it contains currency or stamps).

Name .....

Address .....

City ..... State.....



## The Short-Wave Amateur

An Editorial by HUGO GERNSBACK

● SHORT-WAVE amateurism originally started in the United States away back in the old days, long before the word "radio" was known; it was "wireless" in those days, and there was no "broadcasting." Wireless enthusiasts conversed with each other exclusively by means of the dash and dot method. Experimenters transmitted on any wavelengths they felt like using, as there was no law restricting them in any way. At that time—in 1908—I published the world's first radio magazine, MODERN ELECTRICS, which was the mouthpiece of the transmitting amateurs.

Soon it was found necessary to promulgate laws to regulate all radio transmission, and the United States, along with other countries, began to formulate such laws. All the bills introduced into Congress were antagonistic to the amateur, and either completely ignored him or made no provision for him remaining in radio at all. The writer, almost single-handedly, fought the cause for the amateur by making many trips to Washington and talking to various Senators and other lawmakers in order to uphold the rights of the amateur. This was particularly the case with the Alexander Bill, which made its appearance on December 11, 1911. The rights of the amateur, as outlined in that bill, were not acceptable to the writer, and steps were taken to bring about a satisfactory amendment. This was clearly stated in the writer's editorial in the February, 1912, issue of MODERN ELECTRICS. In that editorial is also to be found the first recommendation that if a wireless law were framed it should restrict the amateur from using a higher power than one kilowatt and his wavelength should be kept below 200 meters. When finally Congress passed the "Wireless Act of 1912," which was in force 15 years, the writer's recommendations were accepted in full, and thus the radio amateur came into his own.

It was thought at that time by the lawmakers, as well as by technical experts, that wavelengths below 200 meters were unfit for use, and that is perhaps the reason why the provision was made at all! Strange to say, the wavelengths below 200 meters are now the world's most important ones, because in the bands below 200 meters all the short-wave stations of the world are grouped.

Since that time (1912), wireless amateurism, all over the world and particularly in the United States, has shown constant progress. At this time of writing, there are actually 40,000 licensed transmitting amateurs in the United States alone. By the end of this year, it is conservatively estimated that there will be at least 44,000 U. S. amateurs, who are more popularly called "hams."

Amateurs are licensed by the Federal Radio Commission. Under the present law, the Radio Act of 1927, they must take an examination showing that they can transmit and receive Continental Code at the rate of 10 words per minute. They must, of course, know something about the tech-

nical side of radio as well. They can transmit by code or by voice.

Amateurs, as the word applies, cannot take commercial business. No business concern can send messages between two amateur stations for pay. If, however, you wish to get a message to your aunt 2,000 miles away, and you know a transmitting amateur, he will gladly take your message, transmitting it for nothing. Then, the "ham" in the distant city who receives the message will deliver it free of charge to your aunt. Amateurs communicate with each other at all times of the day and night. Distances all around the world are covered daily.

Nor do amateurs use a great deal of power to so converse half way around the globe. It is frequently done with less energy than is consumed by a single small electric light bulb! Most amateur transmitting tubes consume not more than 5 to 10 watts, unbelievable as this sounds. Nor is the apparatus expensive. Frequently, the "ham" who has only modest means will build his transmitter from so-called "junk" and cover respectable distances with such apparatus.

It is of considerable interest to note that under new government regulations, which will go into effect at once, new channels are set aside for amateur radio phone use. These channels will embrace 1800 to 2000 kilocycles (166.7 to 150 meters), 28,000 to 28,500 kilocycles (10.53 to 10.71 meters) and 400,000 to 401,000 kilocycles (74.81 to 75 centimeters). This is in line with a recommendation which the writer outlined in his editorial entitled, "Wanted, a Short Wave Phone League" in the December-January, 1931-1932 issue of SHORT-WAVE CRAFT.

At that time he pointed out that there were thousands of amateurs who wished to converse with each other without the necessity of taking a code examination. While the new regulations, as yet, have not dropped the code requirements, it is to be hoped that such regulations will come about in the ultra-short wave field sooner or later.

At the time the writer made the recommendation, a number of amateurs evidently did not read it right through, because they had an idea that the writer favored unlimited phone transmission in the higher wave bands, which, of course, he did not, as a perusal of that editorial will quickly reveal. The point is that in the ultra short wave regions, below 6 meters, you cannot transmit phone emissions beyond the horizon. In other words, 20 or 30 miles is as far as the wave will reach before going out into space. Therefore, there will not be a tremendous amount of congestion or confusion because the phone transmission will only be used *locally*. It will be impossible to accomplish, at least at this stage of the art, long distance transmission. There will, therefore, be no confusion.

Contrary to the opinion of many "dyed-in-the-wool" radio amateurs, there are quite a large percentage of experimenters who, try as they will, can never learn the code.

---

**SHORT-WAVE CRAFT IS PUBLISHED ON THE 15th OF EVERY MONTH**

This is the September, 1933, Issue - Vol. IV, No. 5. The next Issue Comes out September 15th

---

*Editorial and Advertising Offices - 96-98 Park Place, New York City*

# 3 1/2 Inch Waves

Twenty miles on a wavelength of 9cm., or about 3 1/2 inches, is predicted by Dr. Mouromtseff and repeated tests have been made where phone and other signals have been clearly received over distances more than a mile apart. Phone conversation on 3 1/2 inch waves is being demonstrated at A "Century of Progress."

**I. E. MOUROMTSEFF, Electronic Division Elec.**



3 1/2 inch (9 cm.) receiving apparatus, with reflector to concentrate the signals, set up for test. These 3 1/2 inch wavelength signals are not disturbed by atmospheric noises, fogs, sleet, or rain.

### Vital Uses for Ultra Short Waves

From the basic properties of quasi-optical waves, it is clear that they cannot be used for "long distance" communication. But whenever communication, or signalling must be established between the points "directly seen" to each other, quasi-optical waves possess considerable advantage, both over visual light signals and over regular radio waves. When used instead of, or parallel with, light beacons, they surpass them in the ability of penetrating through fog, mist, rain and similar atmospheric obstacles, because they are neither absorbed, nor scattered even by the heaviest cloudhurst. In addition, quasi-optical waves allow voice and sound communication. Also, unlike light signals, the same apparatus can be used day and night with equal convenience. In contrast to the longer radio waves, quasi-optical waves can be efficiently projected in narrow beams without building costly directive antenna arrays; require insignificant power; are not disturbed by atmospheric noises; and bring about a considerable degree of secrecy of communication. In addition, being sharply limited in range by the curvature of the earth, quasi-optical waves allow for sharply defined regional broadcasting. They are also very suitable for television carrier, because they can easily be modulated by frequencies of several hundred kilocycles; this also allows for simultaneous modulation by several broadcast frequencies, thus increasing the efficiency of communication on a quasi-optical beam. Generally quasi-optical beams are very suitable in numerous cases of sea and air navigation and for military purposes, even to their use on the battlefield, in trenches.

● RADIO waves of various lengths are transmitted in quite different manners. Those ranging from extremely long ones of 20,000 meters, down to the ordinary broadcast range around 300 meters, fill out and travel through the space between this world and an upper layer of "ionized" air high above the earth. Radio "short waves," from 100 to 7 meters, such as used by police and radio amateurs, are reflected back and forth between the earth and the upper ionized strata like a beam of light between two long parallel mirrors. Ultra-short waves, or those under 7 meters, travel only in straight lines, their range being essentially limited by the curvature of the earth.

like ordinary "short-waves", be reflected back and forth between the surface of the earth and the mysterious "Heavyside layer" which hangs like a giant reflector, miles up in the sky. Instead, like a runaway locomotive, the ultra-short waves "jump the track," and leave the earth entirely at the first curve, and go shooting off, who knows where, into interplanetary space.

For the present, investigators are aiming at targets closer than radio power; use like a searchlight beam for communication in fog; to signal the approach of icebergs; to project radio paths for aviators to follow. And more interesting still; the use of high frequency to treat disease, for which Westinghouse has supplied a 35-centimeter apparatus. And perhaps, sometime, will come radio power.

Since ultra-short waves travel in straight lines, together with the possibility of focussing and projecting them at a distance in narrow beams by means of parabolic reflectors, similar to those used for searchlights, suggested for them the name "quasi-optical," which signifies "like-optical."

### 9 Centimeter Waves Demonstrated

In the Westinghouse exhibit at Chicago's "Century of Progress" is probably the first practical equipment ever built for ultra-short wave or "beam" transmission on such a short wavelength as 9 cm (9/100 of 1 meter). Never before, outside of small technical groups, has this scientific advance been demonstrated to the public at

### Increasing the Range of U. S. W's.

Due to the rectilinear propagation, quasi-optical waves, as has already been mentioned, have a very small range limited by the distance of "direct vision," or essentially by the geographical horizon. This usually does not exceed a few miles. However, one can increase the reach of a beam if the transmitter, or the receiver, or both, be raised above the ground, the higher the better. This simultaneously contributes to the elimination of absorption and field distortion due to the proximity of the ground. Therefore, the tops of high buildings, towers, the hilltops, or an elevated seashore will be the most suitable locations for quasi-optical beam stations. Houses, trees and other intervening objects between a transmitting and receiving station can absorb and dissipate en-

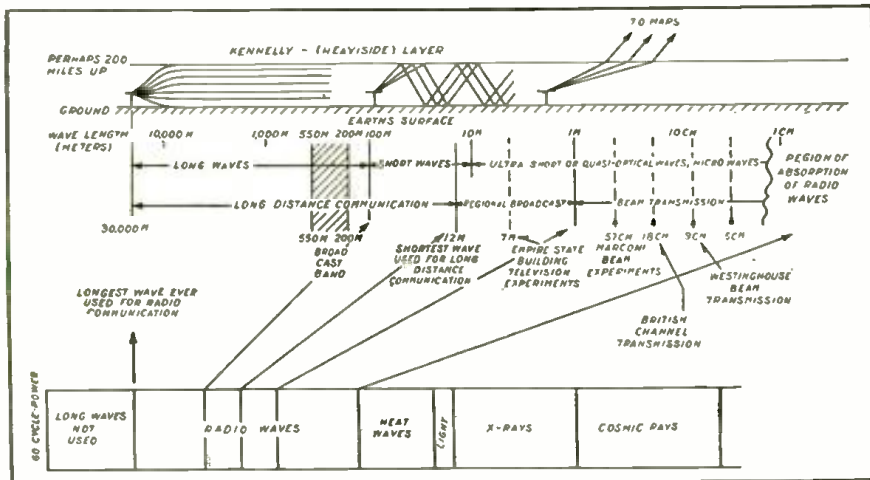


Chart showing graphically the various wavelengths.

# Now Practical

Wherever signalling must be established between two points "directly seen" to each other, these quasi-optical waves show considerable advantage over light signals and radio waves of ordinary length; the ultra short-waves surpass these older mediums in their ability to penetrate through fog, mist or rain.

## Research Laboratories, Westinghouse Mfg. Co.

ergy of a beam, and therefore, must be avoided.

### 3 1/2 Inch Waves Pierce Rain and Fog

A very important factor, emphasizing the usefulness of quasi-optical waves, is their ability to pierce such obstacles as fog, rain, and so on, which are sometimes completely opaque to the most powerful beams of light. In this respect, some calculations show that radio waves about 5 cm actually are not in the least affected by the atmospheric barriers; however, below this limit, absorption increases very rapidly, so that waves of two or three centimeters cannot be used at all for practical purposes. On the other hand, the shorter the waves, the easier and more efficient is the construction of the optical part of the beam transmission equipment, because the smaller are the reflectors and the sharper is the beam. The problem is: how to generate such extremely short waves. Fortunately, the absorption limit, 5 cm, almost coincides with the shortest waves which actually can be generated by means of vacuum tubes.

### 20 Mile Range

At the *Century of Progress*, the "beamcasting" demonstration is made from one end of the Westinghouse exhibit's long curved balcony to the other end, a distance of several hundred feet. However, the apparatus has been successfully tested many times at Pittsburgh between points more than a mile apart. There is every indication that it can be successfully

"Beamcasting" on 3 1/2 inch waves. During trials of this apparatus at East Pittsburgh, speech and music were transmitted over one mile and reception is believed possible over 20 miles.

used between points located 20 miles and more apart!

That the radio waves have the straight line characteristics of light rays was shown in the demonstration in which the radio waves from the sender are reflected off a flat sheet of material to the beamcaster's receiver, just as light rays are reflected by a flat mirror or shiny surface.

The rays can be deflected by any flat material placed directly in the path of the beam. Metals reflect the radio beams almost completely, while non-metallic substances absorb part of the energy. Part of the demonstration was devoted to showing the degree of absorption of various materials such as asbestos board, wood and cardboard.

Our engineers have so developed their transmitter that the radio waves are polarized horizontally. A screen, consisting of wires, about three to the inch and running parallel to the direction of polarization, when placed in front of the beam, does not allow the waves to pass through it, but reflects them just as a solid sheet of metal does. However, when the wires are placed at right angles to the direction of polarization, the rays pass through unhindered.



### Direct Measurement of the Wave

One of the most interesting points in the demonstration was a direct measurement of the wavelength. A metal sheet, placed in front of the transmitter, combined the direct and reflected waves into standing waves. At certain points along the beam, no oscillation can be detected while other points have a maximum oscillation, or the distance between two adjacent points of minimum oscillation or between two adjacent maximum points is exactly half the wave length—or four and one-half centimeters, slightly less than two inches. A metric rule is used to show this measurement.

Power generated in the "beamcaster" at the nine-centimeter wavelength approximates one watt and has never been approached by any other generator at such a low wavelength. It even exceeds the power used in short-wave transmission at 18 centimeter (7 inch) wavelength across the English channel.

(Continued on page 299)


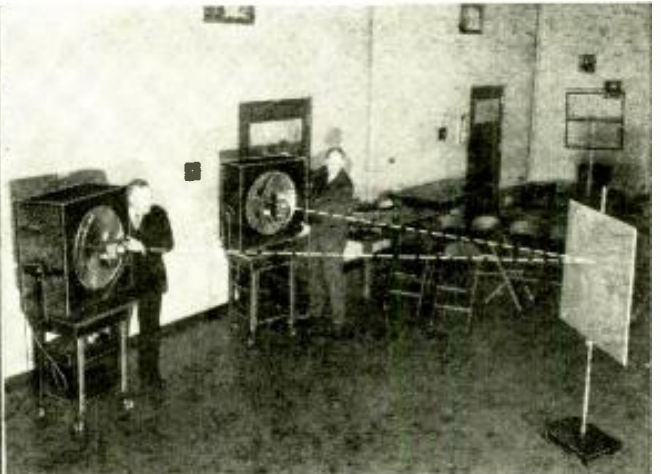


Illustration above at left shows S. M. Kintner, vice-president of the Westinghouse Company, in charge of engineering, actually measuring the length of a 9.1 cm. wave on a rule. Photo at right shows how these ultra short-waves can be deflected like light by flat material. Metal reflects the beam almost completely, while other material like asbestos board, wood, etc., absorb some of the energy.
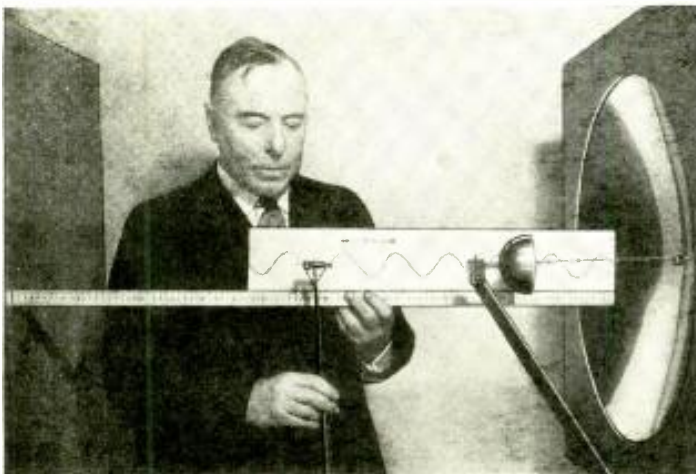
# The PENTAFLEX

By J. A. WORCESTER, Jr.

"Two tubes for one"—that's what you actually achieve with this newest concoction of Mr. Worcester's, who is well-known to our readers for his "Oscillodyne" receivers. By utilizing the new 6A7 (or 2A7) pentagrid-converter tube in a reflex circuit, the author has indeed discovered a very remarkable combination. George Shuart, W2AMN, took a whirl at the dial and admitted that this was the "greatest" one-tuber yet.



Words fail us when it comes to telling about the results the editors obtained and which you can also obtain, without a doubt, with the "Pentaflex"—the latest brain-child of J. A. Worcester, Jr., originator of the Oscillodyne receivers described in previous numbers. By exercising great ingenuity Mr. Worcester combined the many new features of the new 6A7 tube with a reflex circuit—and is it a wow?!

● THE receiver described in this article is so named because it utilizes the new 6A7 pentagrid converter tube in a reflex circuit. With this connection it is possible to obtain the equivalent of a two tube receiver employing a screen grid detector and one stage audio with only one tube; thus enabling an appreciable saving in space, equipment and power consumed.

In actual practice, this circuit has even proved superior in regard to volume to the conventional two tube circuit. This is probably due to the construction of the tube for its intended purpose whereby there exists a certain amount of electron coupling between the two circuits, thus producing a small amount of audio frequency feedback and a consequent increase in signal strength. The writer has tuned in GSA, Daventry, and DJC, Germany, every night for more than a week with this small set and although the volume appeared to fluctuate considerably from night to night, it was possible on all occasions to bring these stations in with sufficient volume to readily understand the announcement. On some occasions the volume was actually too great for comfortable earphone reception.

#### Description of the Circuit

Referring to the schematic wiring diagram, it will be noted that the input circuit is of a conventional nature. Inspection of the plate circuit, however, will reveal that the R. F. currents after passing through the tickler winding are by-passed to ground through the condenser C6. The audio frequency component of the plate current passes through the resistor R5, causing an audio frequency voltage drop across this resistor. This voltage is impressed on the first grid through

the blocking condenser C5. The resistor R4 prevents a negative charge from accumulating and blocking the grid. The amplified currents flowing in the second grid circuit, which becomes the plate of the triode amplifier, pass through the earphones as shown.


Regeneration is controlled in the usual manner by varying the screen grid voltage with a 50,000 ohm potentiometer.

The resistor R2 provides bias for the triode grid, while the return of the control grid is made directly to the cathode.

The heater current is turned on and off by a double-pole, single-throw switch which also breaks the potentiometer return, thus preventing plate current drain through the potentiometer winding when set is not being used.
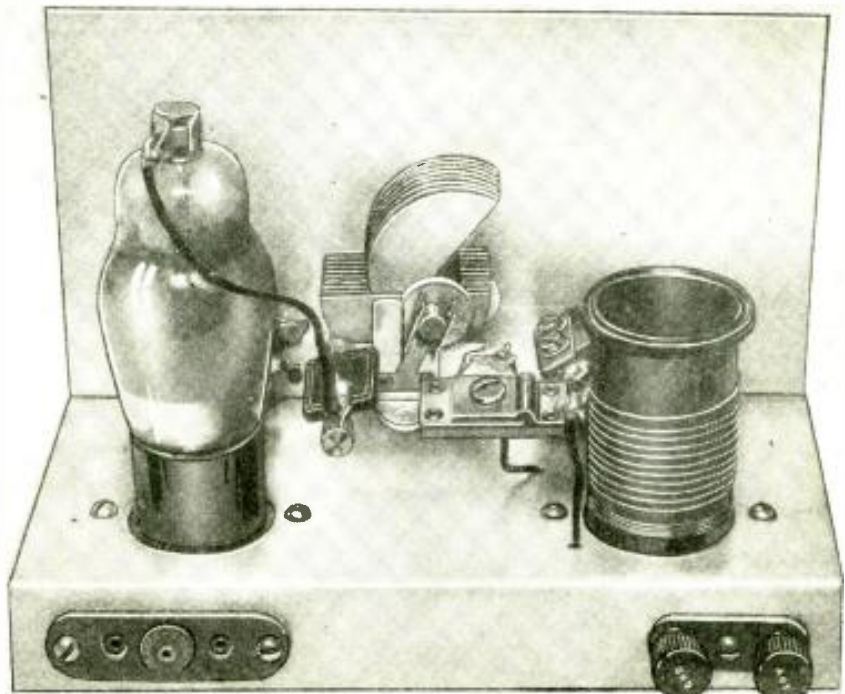
#### Batteries or A. C. Can be Used

Either a 6A7 or 2A7 tube may be used, which are identical except for the heater characteristics. The 6A7 requires a heater voltage of 6.3 volts at .3 amperes, while the 2A7 requires 2.5 volts at 1 ampere. Both tubes are designed for either A. C. or D. C. operation. If it is desired to use dry cells, it will probably be found more convenient to use the 6A7 with four dry cells connected in series, while if a 2½ volt A. C. source is available,



Yep! Only one tube to buy, a 6A7 or a 2A7 pentagrid-converter, plus a little simple wiring, and you have a sensitive receiver which has an output equivalent to "two" tubes—thanks to the reflexing.

# In Which 1 Tube=2



the sturdy 2A7 tube can be used. The front panel consists of a 5" x 7" piece of 14 gauge aluminum while the subpanel is formed by bending a 7"x5" sheet to a depth back of the panel of 3 inches and a height of 1 inch. The panel is fastened to the subpanel by three machine screws.

Mounted on the front panel are the Hammarlund variable condensers, the switch and the potentiometer.

Underneath the subpanel are mounted the bypass condensers, the .0005 mf. by-pass and the resistors. All of these parts are mounted by their pigtails and wherever it becomes necessary to expose any appreciable length of same, they are covered with spaghetti tubing for insulation purposes. The sockets are also mounted under the subpanel, although there is no objection to mounting them above if facilities for cutting the holes required are not available. It might be pointed out, in this connection, that there are two sizes of 7 prong sockets, having different pin circle diameters. The smaller size, having a .75" pin circle diameter, is the one that takes the 6A7 tube.

The twin binding post strip and the twin speaker jack assembly are mounted at the rear. Battery connections are made by connecting a five conductor cable directly to the required points.

The equalizing condenser and the

grid condenser and leak are mounted directly on the Hammarlund variable condenser, as shown.

### Coil Data

The coils can be obtained ready-wound, but specifications are furnished below for winding the coils on blank forms, if desired. The data furnished are for the manufactured Alden coils, but if these coils are constructed it is recommended that about fifty to a hundred per cent more tickler turns than those specified be employed. This is because this tube when used in this circuit requires more feedback than that required for the usual screen-grid tube.

Although all the manufactured coils will oscillate by decreasing the capacity of the antenna condenser sufficiently, the use of more tickler turns is recommended in that it permits closer antenna coupling with consequently increased input.

Coil specifications:

### Coil Winding Data

Band Meters	Grid Coil Turns	Tickler Coil Turns	Space between Coils
10-20	4 1/4 T. No. 22 Wound 6 T. per inch	4 T. No. 31 Close wound	3/32"
20-40	10 3/4 T. No. 22 Wound 12 T. per inch	6 T. No. 31 Close wound	3/16"
40-80	22 3/4 T. No. 22 Wound 16 T. per inch	7 T. No. 31 Close wound	3/32"

80-200	51 1/4 T. No. 22 Wound 40 T. per inch	15 T. No. 31 Close wound	3/8"
200-350	68 3/4 T. No. 28 Close wound	28 T. No. 36 Close wound	3/8"
350-500	131 1/4 T. No. 32 Bank wound in 2 layers	32 T. No. 36 Close wound	3/8"

Data for Na-Ald coils form 1 1/4 inches dia. by 2 1/4 inches long (4 pin).


### Operating Features

The operation of this receiver is no different from the usual screen grid detector and one step with the following exception. As the feedback is increased to a point where oscillation begins, a series of regular clicks will sometimes be heard which vary slightly in frequency with the feedback employed. As these interfere with reception when receiving C. W., it is necessary to increase the feedback still further until the clicks stop. Outside of this one eccentricity at some positions of the tuning condenser, it will be found that the regeneration control is generally not as critical as in the usual regenerative receiver.

### PARTS REQUIRED FOR THE "PENTAFLEX"

- C1—Hammarlund Equalizer EC-35 (3-35 mmf.)
- C2—Hammarlund 140 mmf. midget condenser (MC-140-M)
- C3, C5—.5 mf. tubular condenser, 200 D. C. W. V.
- C4—.01 mf. mica condenser, 200 D. C. W. V.
- C6—.0001 mf. pigtail mica condenser
- C7—.0005 mf. pigtail mica condenser

(Continued on page 306)

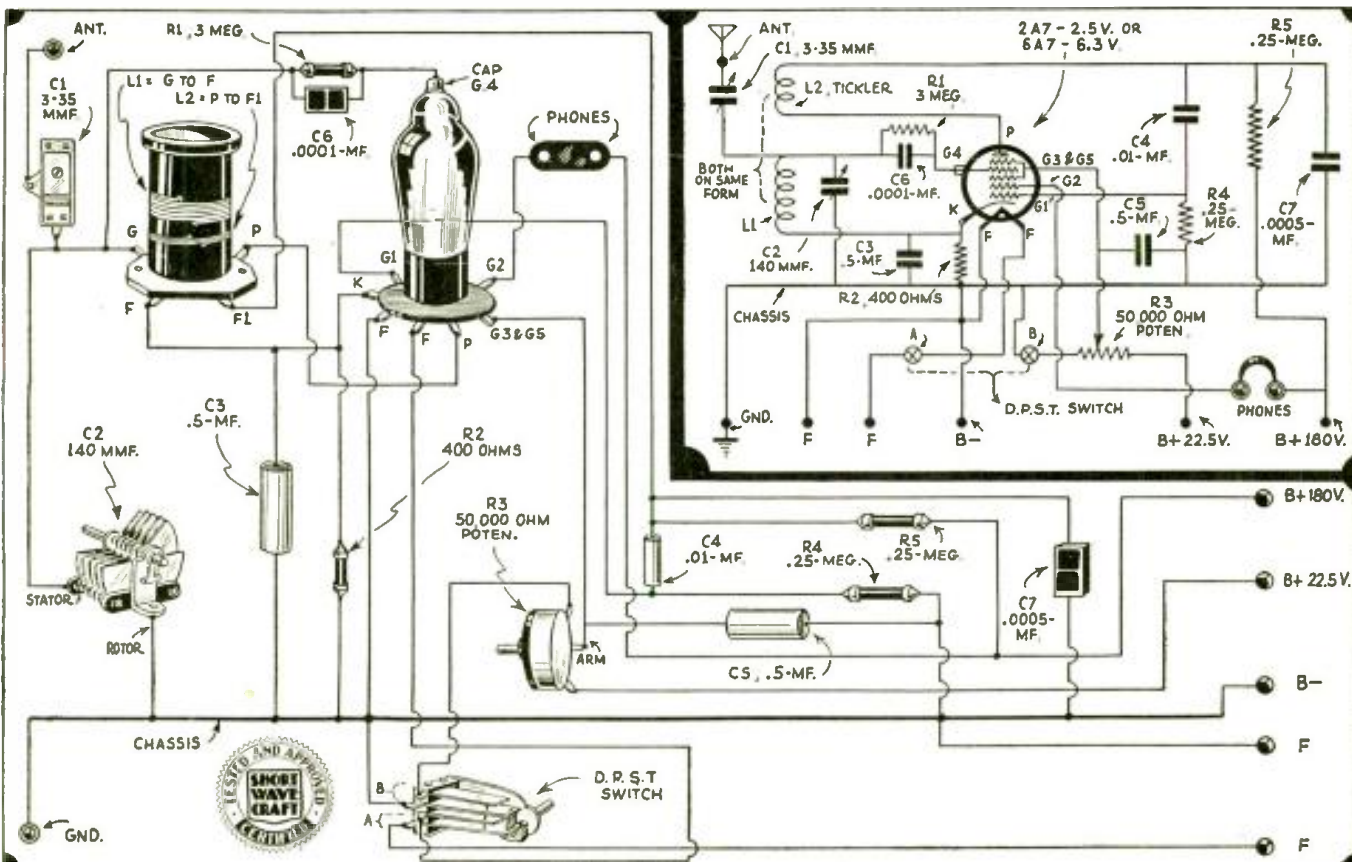

One tube does all the work—either a 6A7 or a 2A7, plus the really few and inexpensive parts shown in the above picture diagram. Anyone can build this "one-tuber," which really gives the same output as a "2-tube receiver," due to the reflex circuit used, as verified by Mr. Shuart, well known to our readers.



Front view of the C.W. (code) amateur transmitter, which is here described in detail by Mr. Victor, together with its power supply unit.

# Amateur Transmitters

## How to Build, Install, and Operate Them

● THIS transmitter was designed and constructed with three objects in view. First, it had to be an *all-band* outfit, very easy to build and operate, because it is intended as a "first transmitter" for the chap who has just obtained his "ham ticket," or who hopes to get it in the near future. Secondly, the cost of the outfit had to be very low, and last, but not least, despite the simplicity of the "rig," it had to be highly efficient and capable of working some real DX (distance).

As a test of its constructional simplicity, a friend of the author's, who had never built a set before in his life, was given all the parts, plain instructions, and shown the transmitter. He completed a perfect working duplicate, unaided, in an hour and a half! The cost is slightly less than that of a two-tube regenerative receiver, and will vary according to how much material can be found in the junk box.

As far as DX is concerned, during the week the set was under test (which was poor, owing to summer conditions) more than two dozen perfect contacts were made from New York, with England and Brazil as the furthest worked.

The outfit is divided into three parts, the tube transmitter, the power supply, and the antenna. This trans-

By LEONARD VICTOR, W2DHN



The editors have been fairly deluged with requests for more articles on the subject of amateur short-wave *transmitters*. We are pleased, therefore, to present herewith the first of a series of articles by Leonard Victor, well-known licensed owner and operator of an amateur short-wave station. Mr. Victor also explains, in an accompanying article, how to build and use a *monitor* for checking the frequency of the transmitter after it has been built. In the articles which are to follow in future numbers of SHORT WAVE CRAFT, Mr. Victor will explain, in easily understood fashion, just how to add *phone* to the transmitter.

mitter can be used with any four-prong tube, from a 30 with 90 volts of "B" battery up to a 10 with 500 volts from an A.C. power pack. For battery operation a 71A or an 01A with 180 volts will give very good results. The model illustrated uses a 45 tube for the oscillator and an 80 for the rectifier; because both of these are receiving type tubes which can be purchased very cheaply, but still will put out a very healthy, respectable signal.

Briefly, the transmitter operates as follows. The power transformer steps up the alternating current, which is rectified by the 80 tube and changed to a pulsating direct current. This current is then led through the filter, which consists of the filter choke coil and the two filter condensers, where the

remaining pulsations are smoothed out so that the current becomes smooth *direct current*. This *direct current* then goes on to the tube transmitter proper, which converts it into *radio-frequency power*. The feed line which will be described later in the article, take the radio frequency and puts it into the antenna where it can be radiated throughout the world, depending upon conditions.

The circuit of this transmitter is a modification of the widely-used tuned-grid, tuned-plate arrangement, having only one variable control. Oscillation is caused by feed-back, as in a receiver, but due to the power applied to the tube it oscillates well with only the feed-back affected by the capacity between the grid and the plate of the tube.

The frequency on which a signal is sent is determined by the tank circuit L-1, C-1 (diagram). The grid circuit must be approximately in resonance with the plate circuit for feed-back and oscillation to take place.

It is possible to use a fixed grid coil for each amateur band, since one adjustment is adequate over a considerable range of the plate tank tuning. The need for an antenna control is eliminated by use of a single-wire, untuned feeder connecting the plate cir-



cuit and the antenna. The antenna, or "flat-top" as it is called, is tuned to the desired transmission frequency by cutting it to a predetermined length.

### TRANSMITTER SPECIFICATIONS

L1 and L2, plate and grid coils. Specifications given under the illustration of the coils.

C1, 350 mmf. (.00035 m.f.) variable tank condenser. Any good receiving condenser will do.

C2, 2000 mmf. (.002 m.f.) fixed plate blocking condenser, mica, receiving type.

C3, 2 2000 mmf. (.002 m.f.) filament by-pass condensers. Same as C2.

C4, 250 mmf. (.00025 m.f.) grid by-pass condenser, mica, receiving type.

R.F.C., low resistance, high quality radio frequency choke, capable of passing 100 ma. The one used is a Hammarlund.

R1, 150 ohm center-tapped filament resistor, anything over 40 ohms can be used.

R2, 50,000 ohm, 5 watt wire-wound resistor.

S1, 4-prong socket to which filament, plate, and negative leads are lead. Cable from power supply plug into this socket.

### CONSTRUCTING THE SET

There should be no difficulty about constructing the set, using the wiring diagram and the pictures shown with the story.

The base of the transmitter is a board 12 inches long by 7 inches wide. This should be sand-papered and given a coat of varnish so that its appearance is neat and workman-like. The board is mounted on four rubber or metal tacks, one in each corner, such as are used under the legs of chairs, to allow clearance for the two filament wires and prevent scratching of the table on which the transmitter is placed.

The grid coils are wound with No. 30 double cotton covered wire on regular coil forms. After the proper number

of turns has been determined, the coils should be given a coat of collodion or clear varnish so they will retain their characteristics.

The plate coils are wound of  $\frac{1}{4}$ " diameter soft copper tubing. Wind the coil around a pipe or dry cell approximately  $2\frac{3}{8}$ " diameter. Flatten the ends and drill them to fit over the machine screws on the stand-off insulators. The stand-offs behind the tank condenser should be mounted 5" apart between centers.

The lay-out of the apparatus is self-explanatory. The right-hand socket is for the grid coil and just behind is the grid leak and grid condenser (R2, C4).

The socket next to the tank condenser is for the tube. Behind the tube, the three condensers in a row are the two .002 mf. filament by-pass condensers, C2, C3. The plate lead of the tube is connected to one side of the condenser stator and the other side of the stator goes to the insulator at the extreme left. The right-hand stand-off is connected to the rotor of the condenser, the plate blocking condenser and the R.F. choke. The socket at the back is for the plug from the power supply cable. The Fahnestock clips at the right are for connection to the key. All the parts are wired with regular square bus-bar, covered with spaghetti. The connections to the plate of the tube and the tank connections are made of very heavy bus-bar to carry the high current flowing in that circuit. The filament leads from the tube to the power supply socket are run under the board. The 0-100 millimeter should be connected in the *keying leads*. It is usually most convenient to have it right by the key.

The power supply is mounted on a varnished board, 12" x 9". It is a conventional unit of the same type as is used on receivers, supplying 350 volts direct current and  $2\frac{1}{2}$  volts A.C. for the filament of the 45 transmitting tube. A standard "brute force" filter

is used, consisting of two 16-mf., 450 volt peak electrolytic condensers and a 30-henry, 150 milliampere choke coil. Any suitable arrangement adaptable to the parts at hand may be used for the power supply unit and the plate voltage may be anything available from the transformer from 250 volts up to 400.

A regular 80 tube is used as the rectifier. The filament and the high voltage plus and minus leads are connected to the cable that runs to the transmitter. A 10,000-ohm bleeder resistor is used between plus and minus of the high voltage to afford good regulation and prevent a chirping note.


### THE ANTENNA

The type antenna to be used with this transmitter is known as a single-wire, matched impedance, voltage feed Hertz, but don't let that scare you; it is one of the simplest types of aerials and very efficient in operation.

The size of the antenna will be largely dependent on the location and the frequency to be used. For *all-band* operation an antenna between 3500 and 3600 kc. must be used. These antennas work perfectly for doubling, i.e., an 80 meter antenna will work on 40 and 20 meters.


The specifications for the antenna can be taken right from the table given and if the wire is very accurately measured and the feeder carefully placed, the antenna will work perfectly the first time, without any trouble. The feeder may be any length at all, up to 1000 ft., which makes it possible to set up an excellent antenna with this system. However, the feeder must run at right-angles to the flat-top, for at least the first 30% of its length. The specifications call for No. 14 enameled wire, solid. The feeder can be any heavy rubber-covered, copper, lead-in wire that may be handy.

(Continued on page 311)

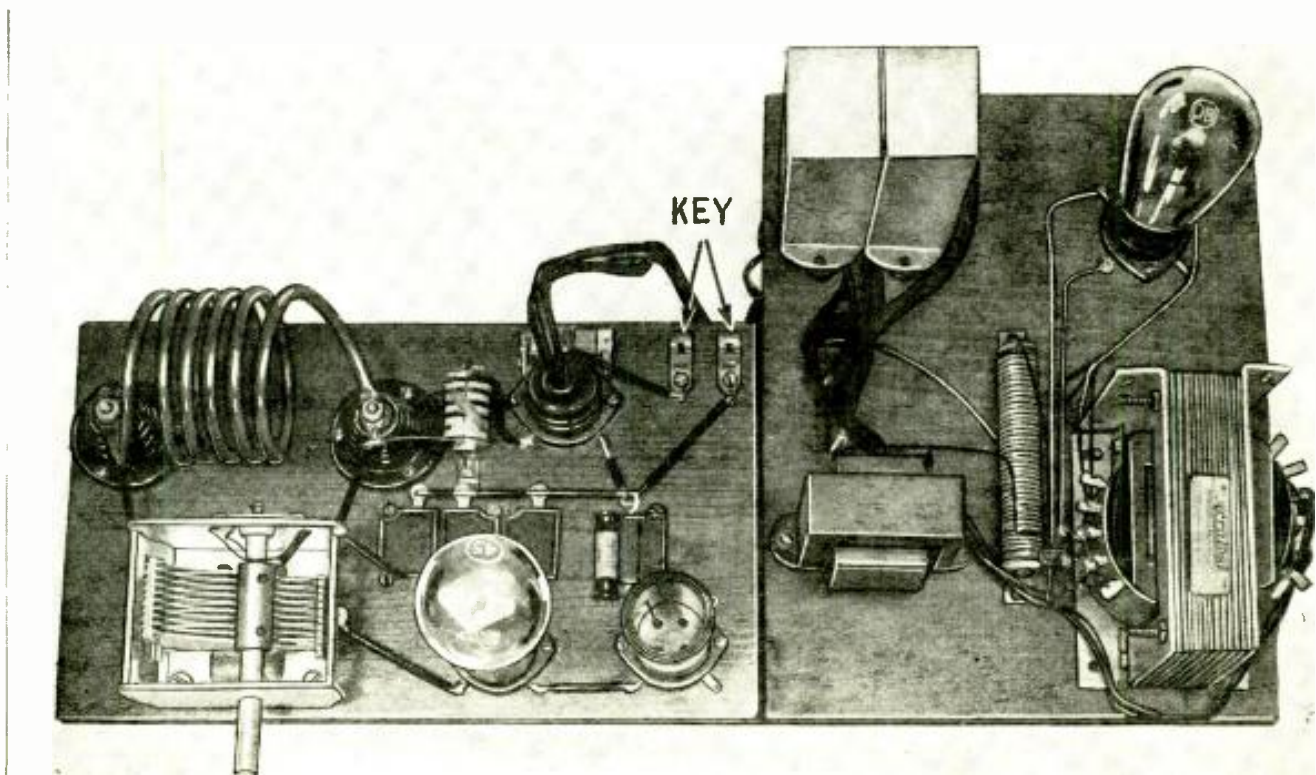


Top view of the C.W. transmitter, the construction of which is fully described in the accompanying article by Mr. Victor. The set illustrated uses a 45 tube for the oscillator and an 80 for the rectifier.

# Details of C.W. "Code" Transmitter

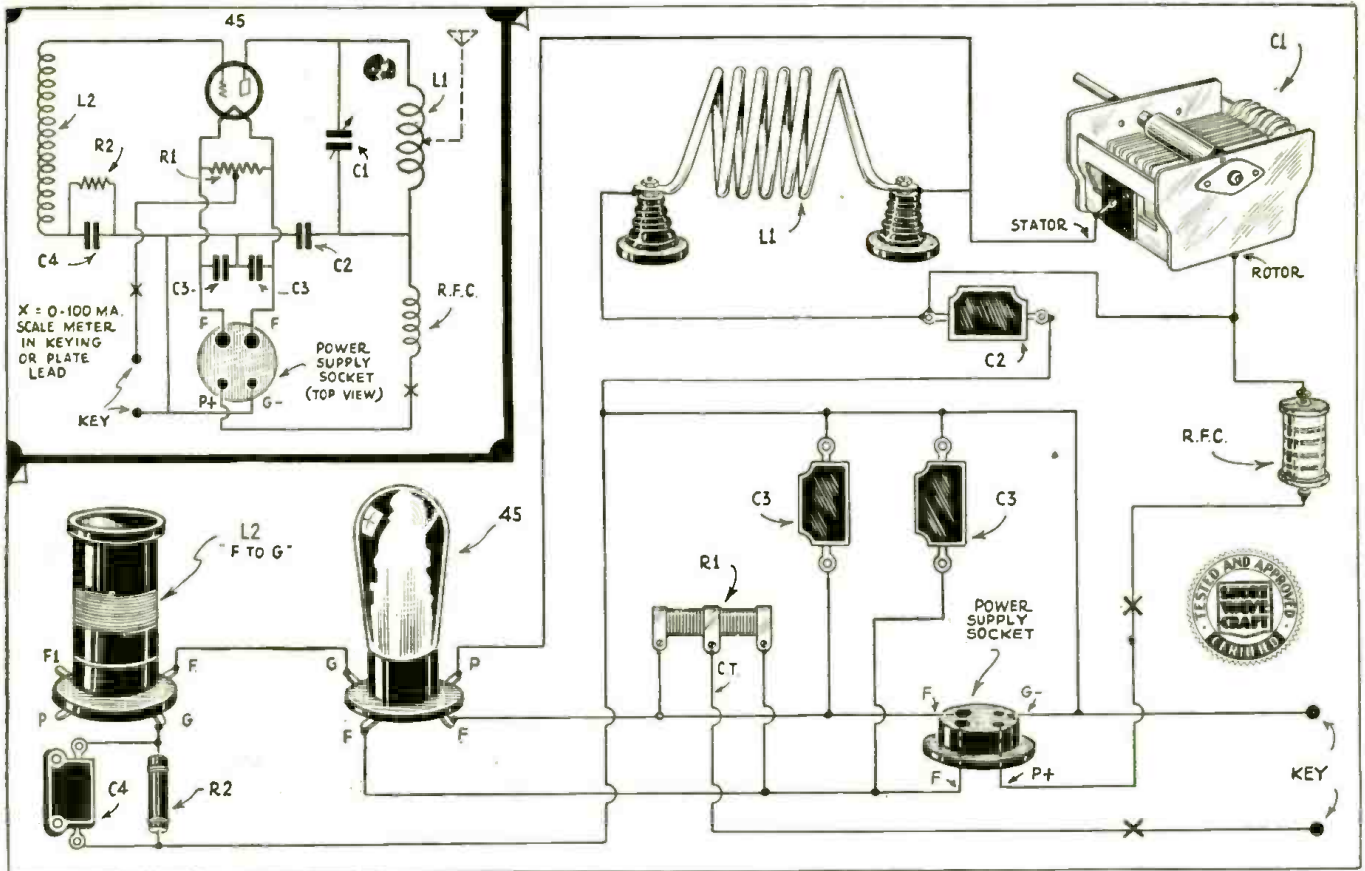

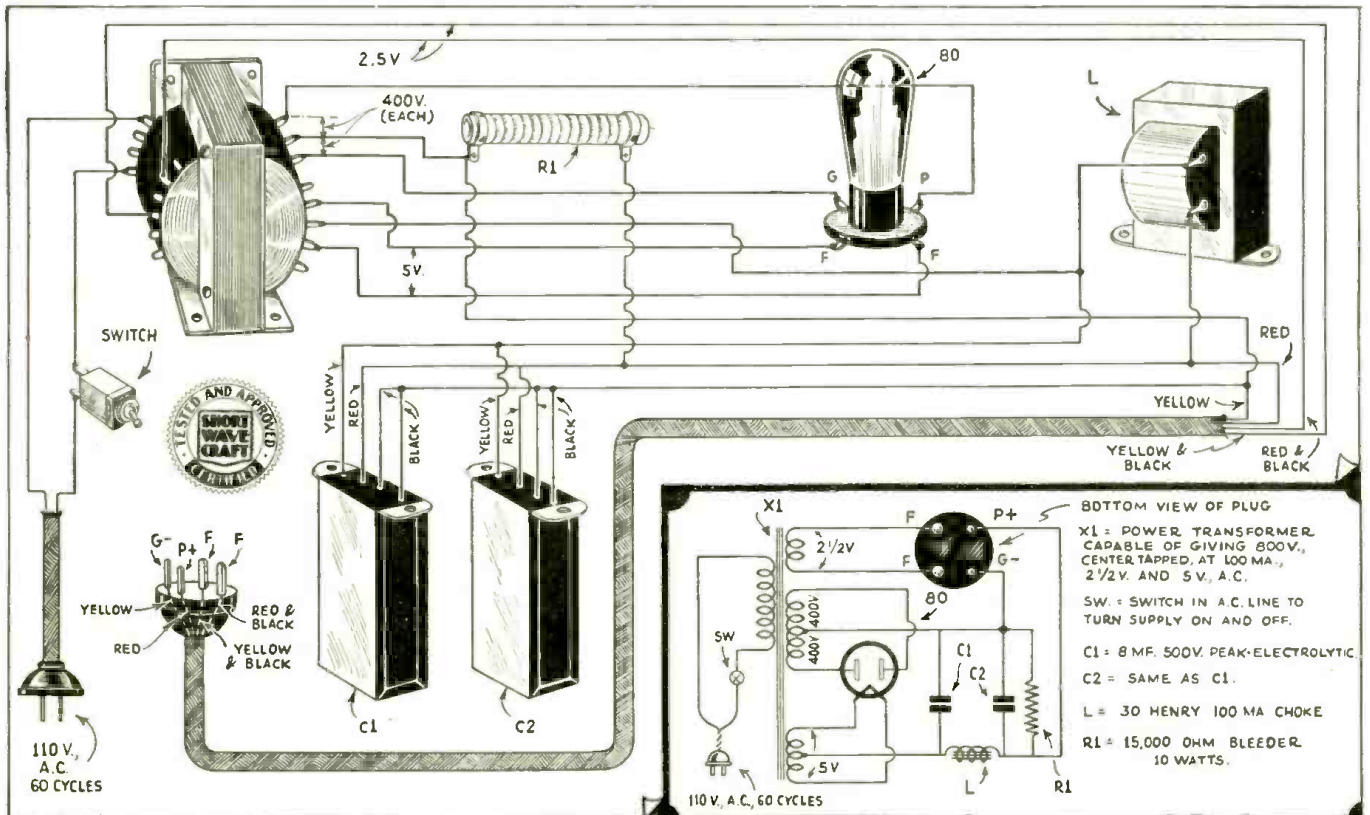The diagrams above show in schematic and also physical form how to wire the simple lay-out of parts comprising the C.W. transmitter for amateur use, as here described by Mr. Victor. A 45 or a smaller tube may be used as the oscillator.



The "power-supply" unit, using an 80 type tube for the rectifier, is shown in diagrammatic form above. It supplies 350 volts D.C. for the plate and 2 1/2 volts A.C. for the filament of the 45 transmitting tube.

# The MONITOR—How to Build and Use It

By LEONARD VICTOR, W2DHN



The author of the article on the C. W. transmitter here describes the next most important adjunct to every "ham" station—the *monitor* and how to use it. Next month, Mr. Victor will describe in clear style how to calibrate the monitor.

...dispensable items in the monitor. This is a one-tube, is used to note and is it is the whether the transmitter of the ham band. The due to its great too strong a transmitter, all necessity for a the monitor. oscillating tube weak note of its determined by the ing condenser and the used in the grid circuit.

It is possible to find the transmitter is working in the band by tuning it in on the monitor and then tuning the monitor whistle in on the receiver. Obviously the procedure can be reversed for placing the transmitter in any desired part of the band.

The unit is simplicity itself and almost any changes necessary can be made to adapt the monitor to the parts available. All of the components should be solidly placed so that the monitor will hold calibration, i. e., return to the same frequency at a given point on the dial. This is a mechanical detail and should be given great consideration on the part of the constructor.

The monitor shown in the picture uses a 2-volt, 30 type tube, but any of the small size tubes, such as the 99 type, may be used, by supplying the proper filament voltage. A little experimentation will determine the best spot to place the monitor, both to give

a healthy signal in the receiver and have a fairly loud note from the transmitter. The coils may have to be changed by the "cut and try" method in some cases so that adequate band coverage can be obtained.


After the monitor has been calibrated try not to jar its mechanical setup. Be careful of the coils and see that the position of the turns is not changed, as this will affect the operation of the unit as far as accuracy is concerned.

If an extra pair of earphones is not available to use with the monitor at all times, a resistance having approximately the same value as the phones should be used in the monitor, when tuning it in on the receiver. This will minimize the unbalancing effect due to the changing of the voltage on the plate of the tube, which in turn shows up in the grid tuning circuit.

In next month's issue, simple, detailed instructions will be given as to the accurate calibration of the monitor.




Front view of the monitor.

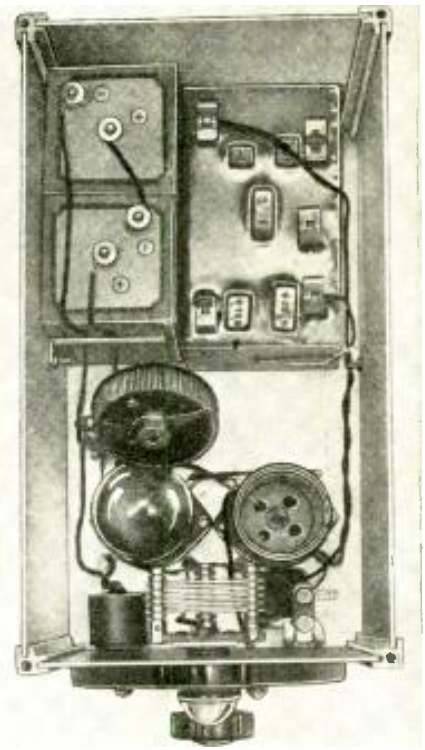

What the innards of the monitor looks like! The batteries for operating the 1-tube receiver are included in the shield box and a phone jack is provided.

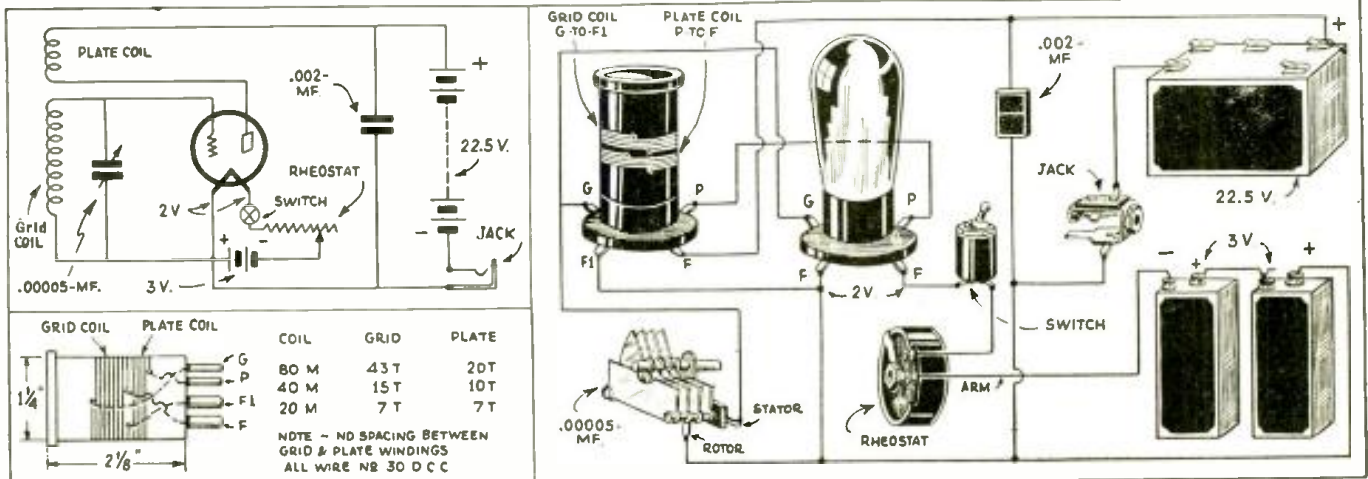
**—NEW—**  
**"All-Amateur Band"**  
**Transmitter**  
 for  
 Phone and C. W.  
 15 to 30 watts output  
 —and Low Cost . . .  
 Described by George W. Shuart,  
 W2AMN, W2CBC  
 In Next Issue!



Both schematic and picture wiring diagrams are given for the construction of the monitor—a one-tube receiver built in a shield box, so as not to pick up too strong a signal from the local transmitter. A 2-volt tube is used and no antenna is required.



# This 3-TUBE "SUPER"

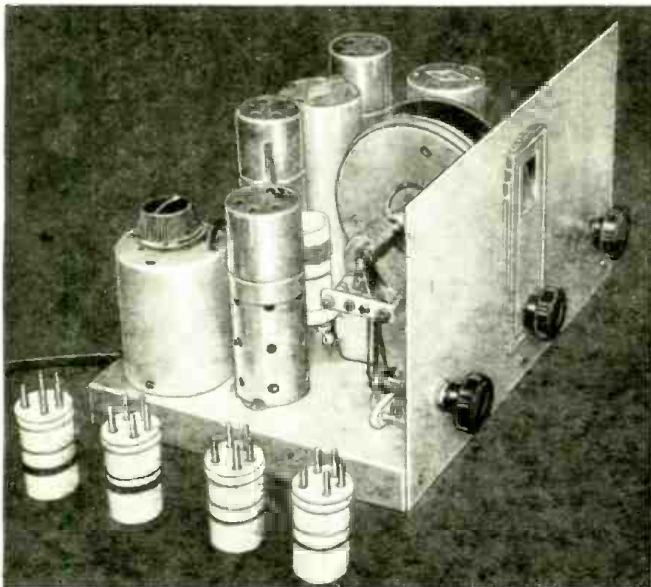

Very "professional looking" indeed is this easy-to-build, 3-tube Superhet which brings in the "foreign" and other DX short-wave stations with marvelous ease—and on a loud speaker!

● THE new type tubes now on the market have paved the way for many changes in our short-wave receivers. Among these is the much discussed *Pentagrid Converter*, the type 2A7 or 6A7, which works very nicely on the "High Frequency" bands.

The receiver presented in this article employs one of these tubes as the high frequency *first detector and local oscillator*, and this tube is partly responsible for the minimum number of tubes used to make up a very simple and efficient short-wave superheterodyne receiver, which can be built by the average short wave "Fan" at very nominal cost. The receiver described here, provides all that any one could want for general short-wave reception, including various amateur activities. Although no provision is made for band-spread, and would be necessary should one wish to use it for amateur work.

## Separate Beat Oscillator for "Code"

This receiver is really a three tube set, so far as ordinary reception is concerned; the fourth tube is provided to allow "CW" reception on code and also provide an easy method of locating the various short-wave broadcast (phone) stations; after the modulated signal has been located the beat oscillator is no longer needed and is turned off.

The line-up of tubes is as follows: the 2A7, as stated before, is used as the frequency converter, a type 58 for the intermediate frequency amplifier, and a type 2A5 as the second detector tube. The type 2A5 used as the second detector gives sufficient audio amplification to operate a speaker, either magnetic or dynamic, at regular speaker volume. That is, any of the major foreign short-wave stations can be heard all over the house and one does not have to stand with one's ear in the speaker either. The fourth tube, the type 57, is the *beat oscillator* tube and plays no part in the reception of broadcast (phone) reception, other than to aid in tuning or locating the station.

The coils used in this receiver are very easy to construct; they are all close-wound and the two sets, that is,

Loud-speaker reception of "foreign" short-wave stations is a regular performance for this 3-tube Superhet, designed by Mr. Shuart who gave us the very excellent "band-spread" S-W converter in the July and August issues. This Superhet has an extra tube which acts as a C. W. oscillator for code reception; one of the new pentagrid-converter tubes acts as first detector and oscillator for "phone" reception. You'll be delighted beyond words with this set.


the first detector and oscillator coils are identical in number of turns. The coils used in the set shown are wound on small isolantite forms. Complete coil data is given in the appended "Coil table."

In designing this set, size and simplicity were among the main considerations. The front panel is made of 1/16th inch aluminum and is 12 inches long by 7 inches high. The base or chassis is made of the same stock and is 8 inches wide by 12 inches in length and 1 inch deep. All bypass condensers and resistors are mounted in this space under the set. The layout of parts in this receiver cannot be changed very much without the necessary addition to the size of the chassis.

A drum type dial is used in order that the two tuning condensers can be mounted on either side, allowing short leads to the two coils and the frequency-converter tube. The 2A7 converter tube is mounted directly behind the drum dial. If the 2A7 were put in any other position, the length of the connecting leads to one set of coils and condenser would be much too long. The layout used in a set using separate tubes for the oscillator and first detector cannot be used with the new tube with any great success, if simplicity of wiring and short leads are taken into consideration. Many other layouts were tried with very little success—in fact it made a very awkward looking job.
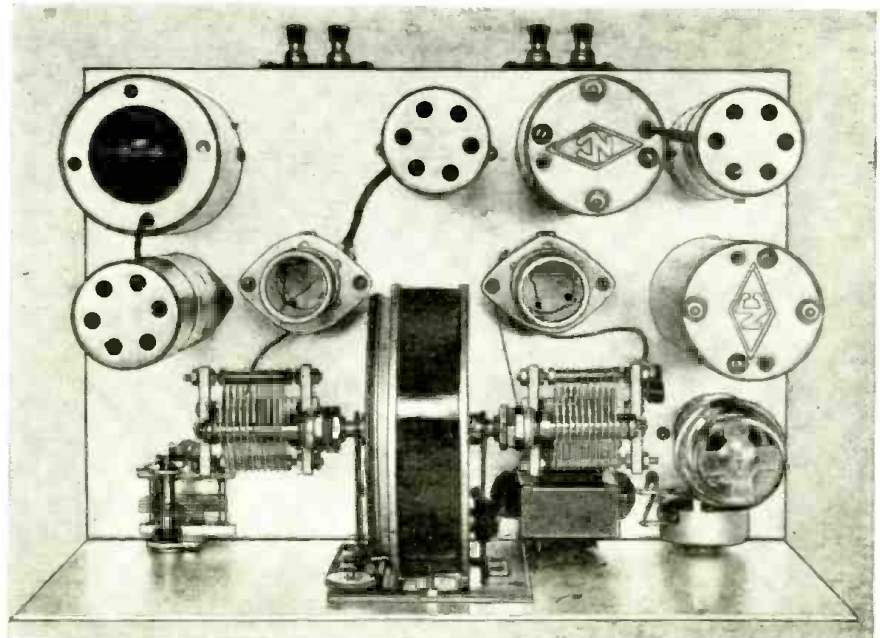
## Description of the Circuit


In describing the circuit we will start with the high frequency end of the receiver first. Many different circuits were tried in the high frequency unit and that shown in the diagram proved to be the most stable in oscillation. The circuit as can be seen in the diagram, permits the current from the plate and the anode-grid to return through



This top view of George Shuart's latest set—the 3-tube Superhet, shows the excellent layout of the parts.

# Has "IT"

By **GEORGE W. SHUART**  
(W2AMN-W2CBC)

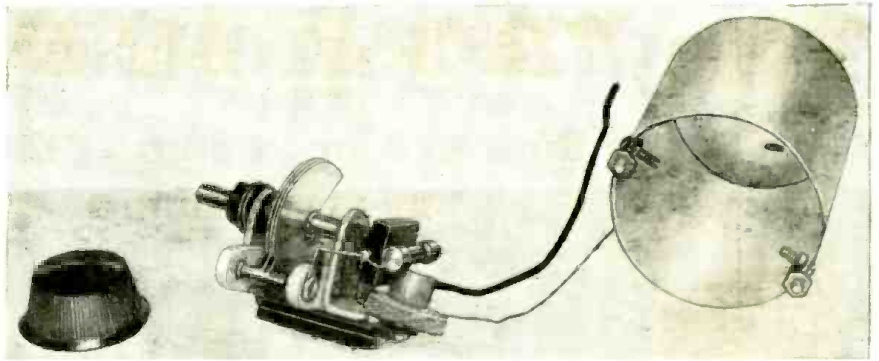

The parts used, together with shield can, in building the CW oscillator for "code" reception.

the oscillator plate coil. In this circuit it is surprising how uniform the output of the oscillator circuit is; with only the few tickler turns shown in the coil table, there is no change in oscillator output over the entire tuning range of the oscillator grid coil, and it shows no tendencies of going out of oscillation as the capacity of the grid circuit is either increased or decreased. No increase in stability could be noticed when the oscillator grid circuit was changed to a high capacity with lower inductance. Even with the grid condenser turned to minimum capacity, there are no signs of instability. The values of resistances shown in the diagram of the converter circuit are those that work best with 250 volts applied to the plate. If a lower voltage is used, it is suggested that a change in the values be made, if the full gain of the 2A7 is to be had. This is mentioned because there is very little pickup in the first detector and the "over-all" gain in the converter circuit is very small.


When using *single-control* in a superheterodyne some sort of provision is necessary to get the two circuits to track. With the coil data given and the use of a 1000 MMF. condenser in series with the oscillator grid-tuning condenser, the two circuits were made to track very evenly, the 35 mmf. variable condenser used in the detector circuit is for compensating for small changes which may occur in the antenna circuit. The tuning condensers used in this receiver are of the 270 degree type. These condensers aid in tuning considerably because of the added 90 degrees in the tuning range giving less cramped tuning than the

regular 180 type, a very worthwhile feature indeed.

### Air-tuned I. F. Transformers Used

Referring to the diagram it can be seen that the intermediate frequency amplifier stage is of conventional style using a pentode tube. The I.F. transformers are the new style having *air-dielectric* tuning condensers. These transformers represent a decided improvement in that they can be adjusted and will hold their calibration indefinitely. If the builder wishes to build his own IF. transformers this can be done quite easily. The coils for the primary and secondary should have an inductance of from 1 to 1.3 millihenries and should be tuned with a 100 mmf. midget variable condensers. The above values are for frequencies between 550 and 465 kc. The regular universal-wound inductances are used and should not be coupled too close or the selectivity of the transformer will be destroyed; about one and one quarter inches is a good degree of coupling. The volume is controlled by a 20,000 ohm variable resistor inserted in series with the 300 ohm cathode bias resistor of the type 58 IF. amplifier tube. The .01 cathode bypass condenser is large enough to render the volume control quiet in operation. The set is equipped with a voltage

(Continued on page 307)

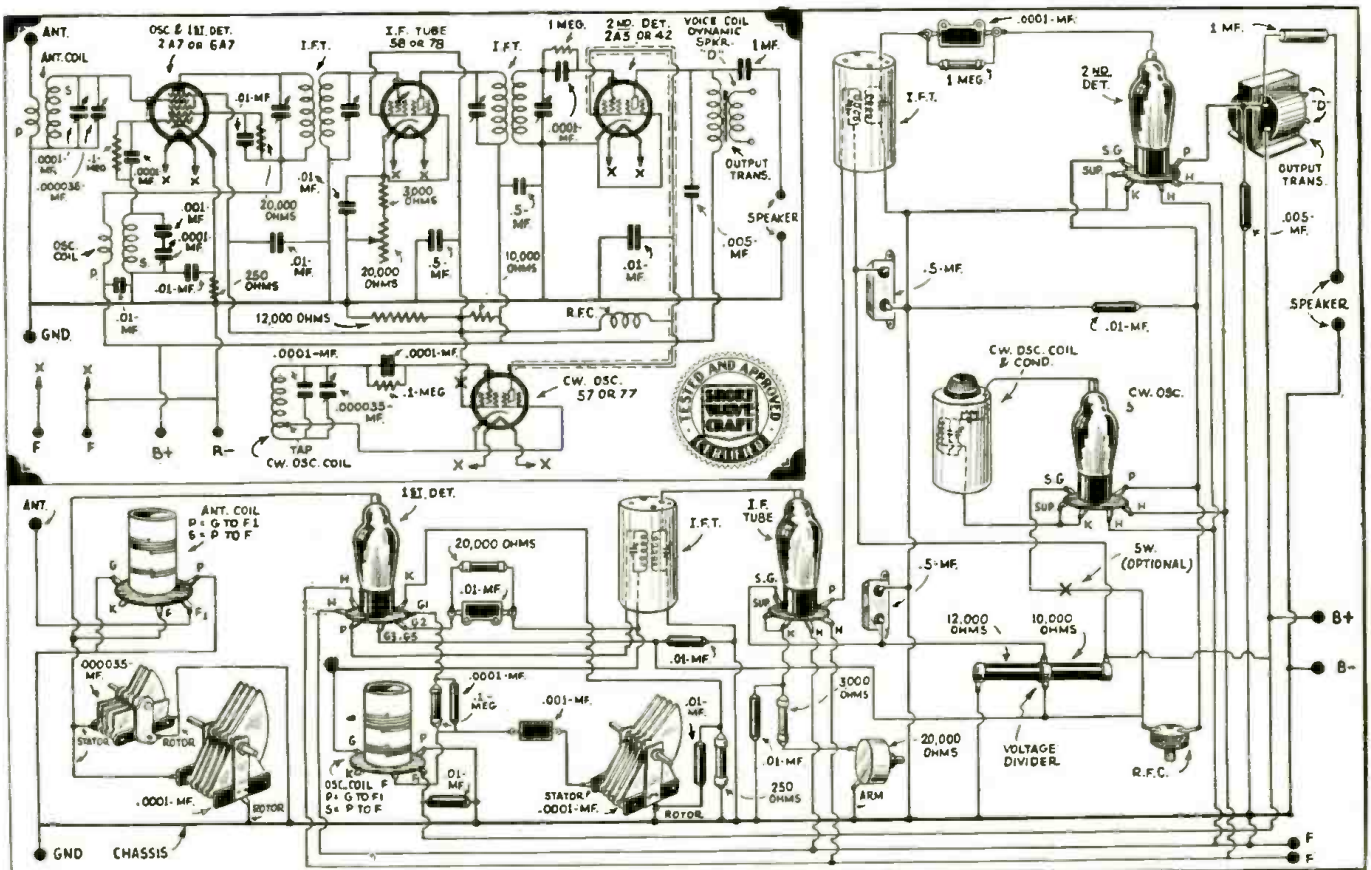


Schematic and also picture wiring diagrams are given above for the 3-tube superheterodyne short-wave receiver, the fourth tube being used as an extra oscillator for CW or "code" reception.

# The "ACRATONE DISCOVERER"

## An Easily Built 5-Tube "DeLuxe" Short-Wave Receiver

By CLIFFORD E. DENTON\*

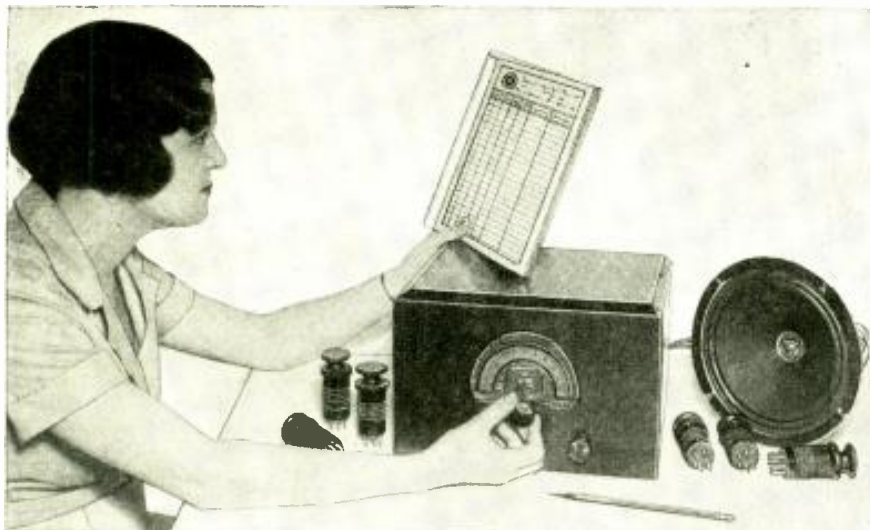

Yes, you will need a good-sized, well-arranged "log" book in which to record the many stations you are sure to hear with this receiver—and they come bouncing in on the loudspeaker!

● IN designing the "Acratone Discoverer," my purpose was to produce a de luxe short-wave kit that could be relied upon to "deliver the goods" consistently. I am happy to state that I have succeeded 100 per cent in doing this. Furthermore, the design is so well-balanced that every "Discoverer" set built in accordance with the directions will give the same splendid results. Everything has been simplified to the last degree, so that the novice at set building will have no more difficulty with this receiver than with a beginner's "two-tube" job.

Before starting to tell you about the "Discoverer," I spent several months experimenting with the circuit. That's a really peculiar thing about radio. Any radio engineer can sit down and design a new radio circuit on paper in fifteen minutes. But when such a set is actually built up for the first time, many "bugs" must be removed before it becomes a practical proposition. The value of a resistor must be increased at one point or decreased at another, condensers may have to be added to eliminate hum, regeneration may not be smooth enough. These and many other small but important points must be ironed out.

In presenting the "Discoverer" you can rest assured that all this experimenting has been completed in my laboratory. The circuit and the parts are finished products, certain to work and give you the kind of results you want. Even the smallest details have been worked out for you. The chassis has all mounting holes drilled, thus eliminating all laborious work. Every component fits into its designated place. And the kit itself contains every part specified, from the largest item down to the small hardware.


The "Acratone Discoverer" employs five of the new type tubes in a highly

improved tuned R.F. circuit. A single R.F. stage using the 58 variable mu R.F. pentode fulfills every requirement of sensitivity. A 58 tube is also used as the detector. Electron coupling regeneration is obtained by connecting the cathode of the detector tube to a tapped point in the secondary of the R.F. transformer L2. The regenera-

This particular short-wave receiver presents not only a handsome appearance in its beautifully finished metal case, but it represents the very newest ideas in short-wave engineering. The "proof of the pudding" lies, of course, in the actual results obtained, and this receiver certainly "steps out" and proves that it has the goods! The tubes used are 58 R.F., 58 detector, with 56 and 59 first and second A.F.'s.

tive action obtained is very powerful and changing the position of the regeneration control does not detune the set. A variable resistor controls regeneration by changing the detector screen grid voltage. In this way, well-regulated, even control is obtained.

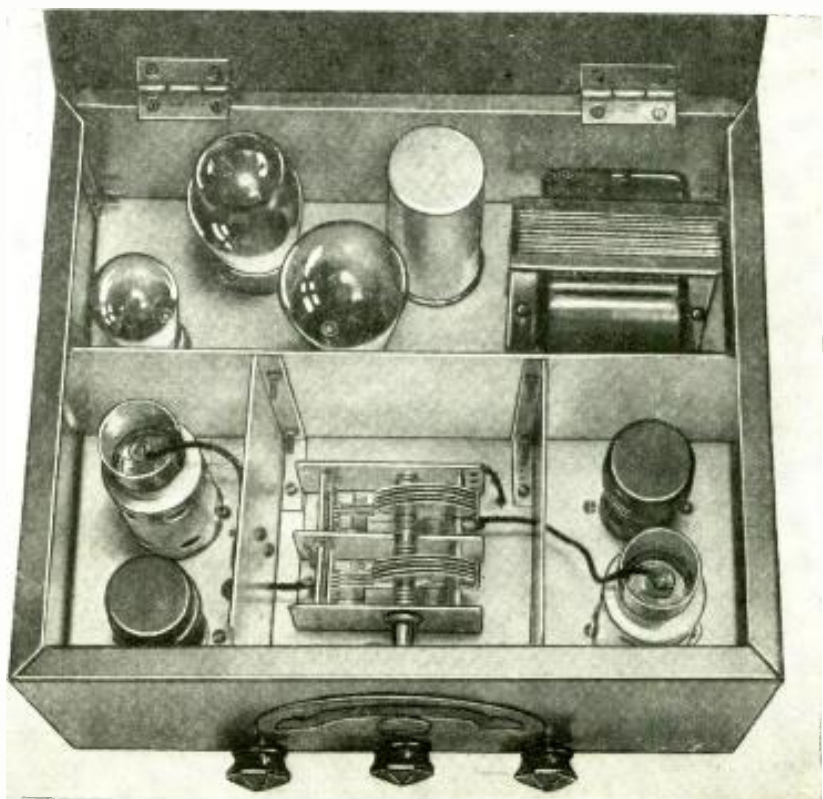A general purpose 56 tube is used in the first audio stage. This is fol-



Looking down into the "Acratone Discoverer" 5 tube S-W receiver, showing the careful layout of the shielding partitions.

\*Chief Engineer Federated Purchaser

lowed by a 59 power output tube of high-power sensitivity. The phone jack is connected so that the grid bias on the 59 is not disturbed when using the phones. No direct current flows in the jack terminals, so that there is no chance of getting a shock at this point.


A full wave type 80 rectifier is used, with conventional power supply. The filter system consists of the dynamic speaker field, by-passed at either end by 8 mf. electrolytic condensers. These are combined in a single case.

The plug-in coils specified with the "Acratone Discoverer" are of special design and add considerably to the effectiveness of the circuit. Four coils are used to cover the short-wave bands from 15 to 200 meters. Two sets of these are required, one to be plugged in at L1 and the other at L2, making a total of eight coils in all. The "Discoverer" is well shielded and is furnished with a handsome gun-metal finished cabinet.

All in all, I can highly recommend this receiver because it is basically correct from every standpoint. It is easy to assemble and wire, comparatively inexpensive, good-looking and most important of all, it will bring in the DX stations.

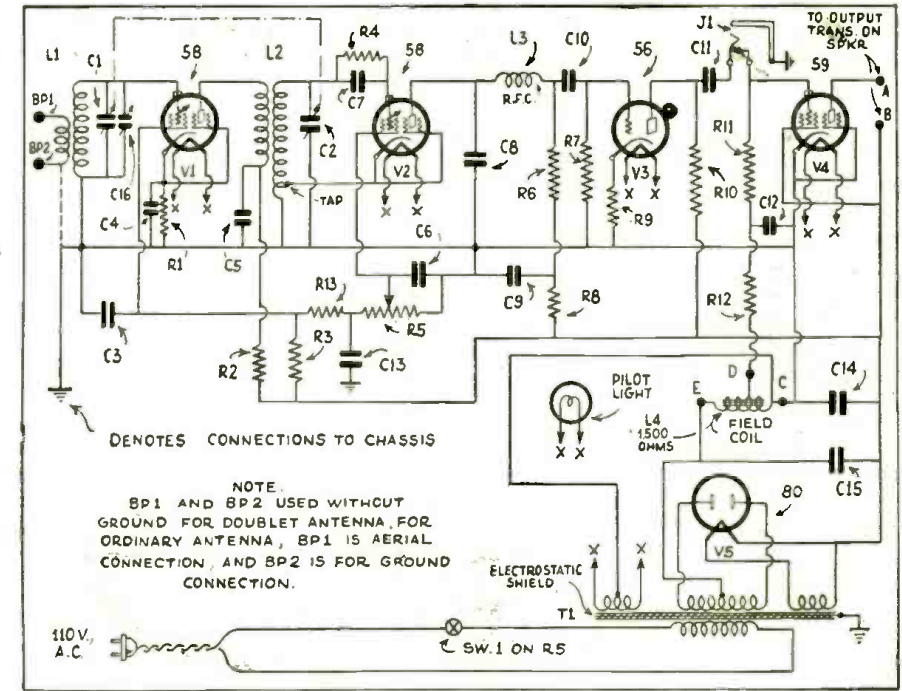**Constructing the "Discoverer" 5 Tuber**

The metal chassis is furnished bent to shape and with the wafer sockets V3, V4, V5, speaker connection socket and binding post strip riveted in place. The four Isolantite sockets V1, L1, V2, L2 are fastened in place. The tube shield bases for V1 and V2 are also fastened in position at this time. The dual variable tuning condenser




Schematic wiring diagram of the "Acratone Discoverer," showing the disposition of the five tubes.

C1, C2 is equipped with stay bolts, so that the bolts can be slipped into the holes provided for them in the chassis and fastened securely. The condenser is mounted and then the dial. A single bolt on the front chassis wall holds the dial in place.

The small variable condenser C16 is mounted at the right of the front

chassis wall. The regeneration control R5 is at the left. The phone jack J1 is mounted on the rear chassis wall as shown in the sketch.

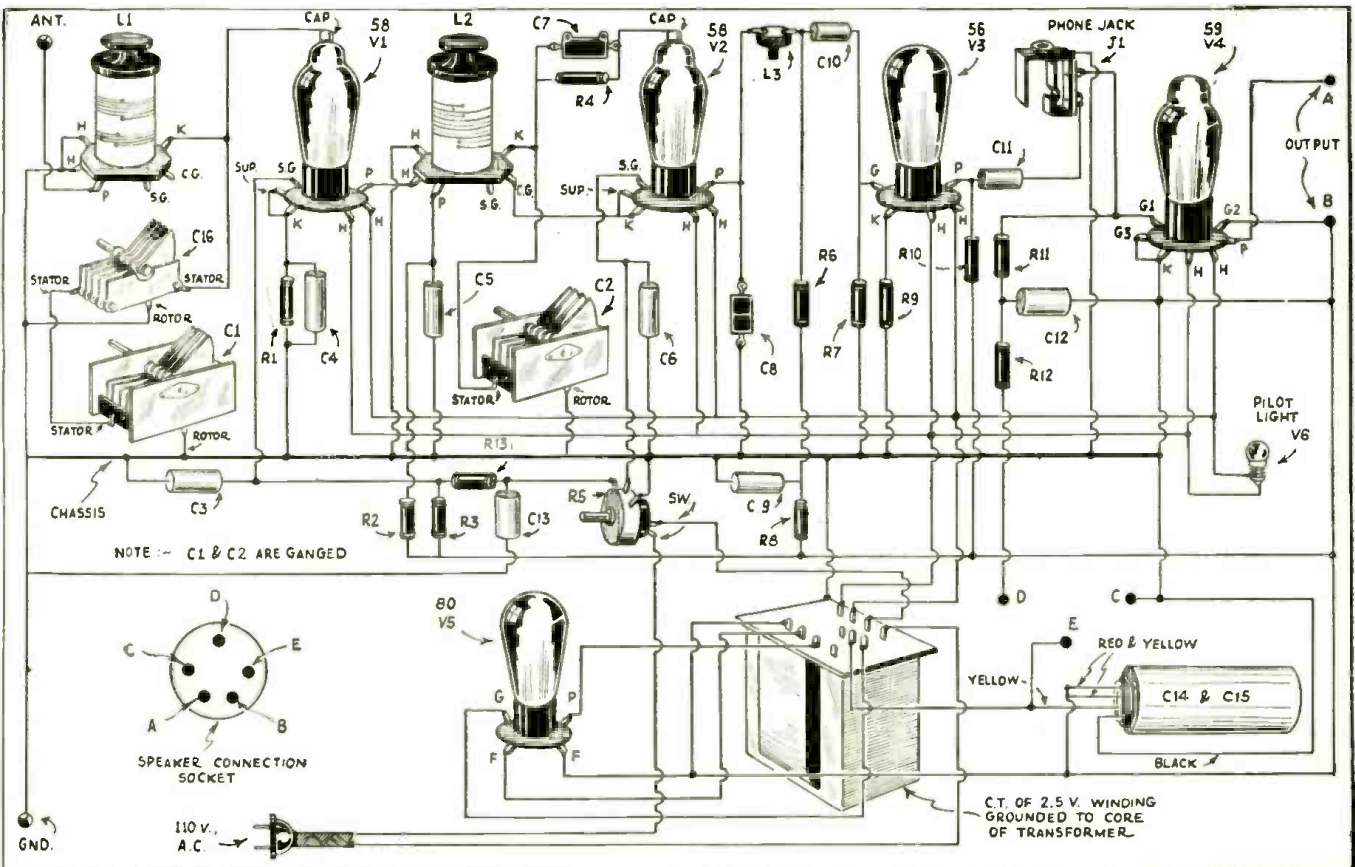The power transformer T1 is mounted next, being so placed that the 110-volt lugs are towards the rear of the chassis. A small bakelite termin- (Continued on page 297)



This picture wiring diagram shows how simple a matter it is to construct a strictly up-to-date short-wave receiver of the highest engineering design—and it becomes all the simpler when one realizes that this set is available in "kit" form, with the exact parts as specified by the engineer who designed the set.

# Leotone 2-Volt Set Has "Pep"!

This receiver possesses high selectivity, due to careful shielding; strong signals are produced in the loud-speaker by the judicious selection of the proper tubes. Four 2-volt dry-cell type tubes are used and standard plug-in coils are employed. A receiver that many readers have asked for data on.



It's "dead easy" to change the plug-in coils in the Leotone receiver, thanks to the diagonally opening metal cabinet. This 4-tube, 2-volt receiver operates a loud speaker nicely.

● THE carefully shielded 4-tube short-wave receiver shown in the accompanying illustrations embodies several new features. In the first place, the designers of the Leotone receiver have refreshingly departed from the usual mechanical arrangement of the tuning condensers found in the average receiver, and in this receiver we find them mounted vertically instead of horizontally. By this means, the engineers were permitted to mount the dial so that the graduations are read horizontally through a window at the bottom of the cabinet. Another excellent feature is the diagonal separation of the metal shielding cabinet, which exposes the plug-in coil sockets in a jiffy by simply flipping up the lid of the cabinet, which is a very desirable feature whenever the plug-in coils have to be changed. Improved selectivity is afforded by providing a well-designed tuned radio frequency stage. The plug-in coils used in the antenna circuit are of the same 4-pin type as those used for coupling the plate circuit of the R.F. tube with the grid of the detector tube. These plug-in coils may be of any standard make, data for winding which are given herewith, and designed for use with .00014 mf. tuning condensers. The two tuning condensers are ganged and a small variable trimming condenser of about 30 to 50 mmf. is connected across the second tuning condenser in the plate circuit of the R.F. tube.

To prevent the possibility of short-circuiting the B battery should the

plates of the second tuning condenser accidentally touch, a small fixed condenser of .01 mf. is connected in series with the plate of the second R.F. tube and the stator of the second tuning condenser as the diagram clearly shows. Due to the high value of this series blocking condenser there is no appreciable reduction in the tuning capacity.

Any average size antenna system may be used with this short-wave receiver or approximately the same size antenna as that used for broadcast reception. Instead of using a series trimming condenser in the antenna circuit the trimmer in this case is connected across the second tuning condenser in the plate circuit of the R.F. tube, as indicated in the diagram.

### Detector Circuit Features


In this particular receiver grid-leak detection is employed, which provides high sensitivity and also smooth operation of the regeneration characteristic,

the detector operating approximately on the square law. Regeneration is controlled in this detector circuit by means of the 100,000 ohm rheostat (potentiometer) which is connected in series with the 22.5 volt B plus feed, as illustrated in the diagram.

A volume control is also provided in this interesting circuit. In series with a 15-ohm filament resistor in the positive wire feeding the R.F. tube, we find a 20 ohm variable resistance, which is used as a *volume control*. This 20 ohm variable resistor also serves the purpose of checking any oscillations which might be set up in the R.F. circuit.

As in all other short-wave receivers, the radio frequency choke, RFC, is an important item and it should have low distributed capacity with a maximum of inductance, the value of the R.F. choke in this case being about 30 mh. One may try R.F. chokes having induct-

(Continued on page 300)

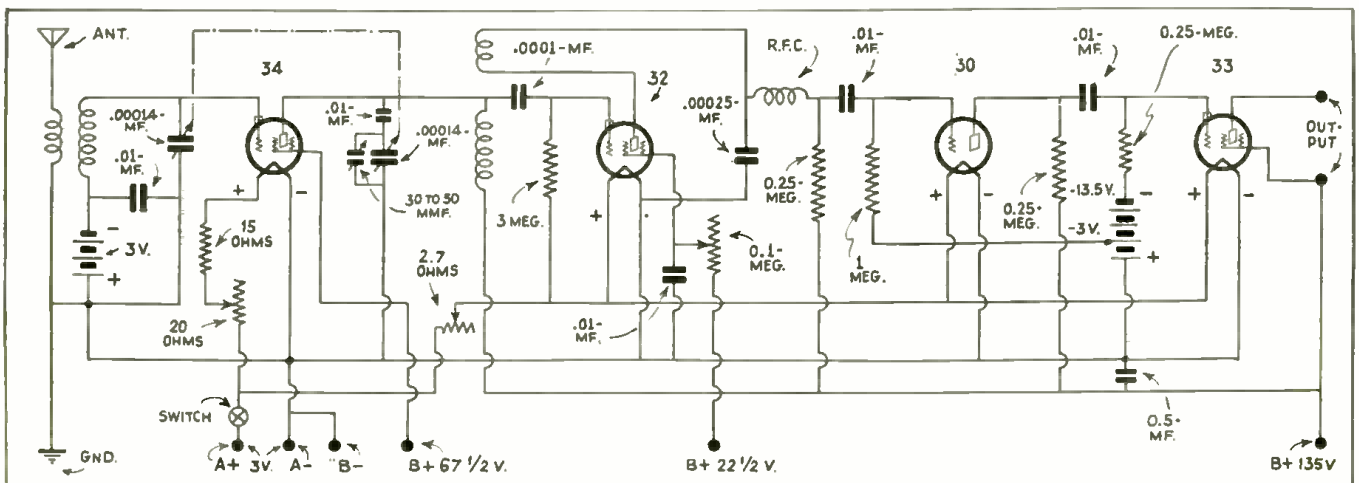

The interesting hook-up devised by the Leotone engineers, whereby maximum strength of signal is obtained, with a minimum of battery consumption. An A. C. model is also available.



# 2-TUBE A. C. Receiver To Work on Your B. C. Audio



By HENRY J. WAGNER

\$20.00 June Prize-Winner

Mr. Wagner has tried out many different types of short-wave receivers; the one he here describes represents his final selection, with which he hears the "Europeans" in fine shape.



Photo at left above shows Zenith 200-550 it. Front and rear "close-ups" of the S-W

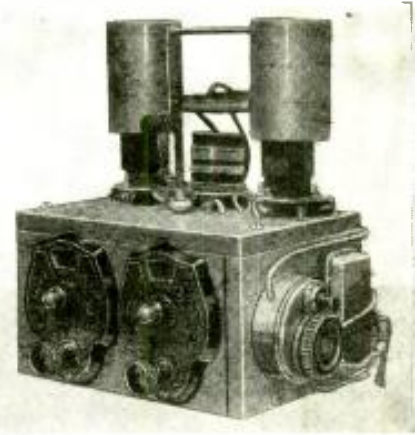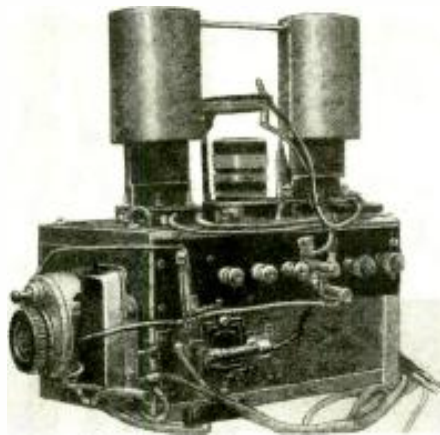

meter "broadcast" receiver with Mr. Wagner's short-wave receiver perched on top of receiver unit appear at the center and right; the S-W signals are passed through the audio amplifier of the Zenith "B.C." set.

● I BELIEVE that short-wave fans will be interested in my reception of short-wave international broadcasting stations, whose programs are being heard directly from the loud speaker of a Zenith broadcast set. This model, 9 type 52, is equipped with a phono. pick-up connection at the rear of the chassis, which is coupled to its audio system. A two tube A.C. type short-wave receiver, which is placed on the top of the Zenith console, feeds its audio output into the phono. jack connection of the broadcast receiver, and with a combined power amplification of seven tubes, drives its 12 inch dynamic speaker.

For regular broadcast reception, the Zenith receiver is switched on in the regular way. To change to the short-wave band requires three operations that can be performed in five seconds. When the tubes heat up, the short-wave converter is ready to function. A selector switch connects the aerial

lead-in from Zenith to converter, or vice versa. Another switch closes the connecting lead from converter to Zenith phone jack; another switch snaps on the house lighting current to the converter power supply. This describes the short wave change-over.

### "Foreign" Stations Heard Nightly


To swing back to broadcast reception (1500 to 550 kc.) move selector switch arm and open switch to phono. jack lead. The set receives, nightly, GSA, Daventry; EAQ, Madrid, and DJC, Berlin, with full loud speaker volume, and has remarkable stability. Placing the hands near the coils does not effect them. The American short-wave transmitters W1XAZ, W8XK, W2XE, W3XAL, etc., came in like "locals," and the regeneration must be cut down in most cases.

The original filament resistor wire was removed and a two-point contact was substituted in its receptacle by in-

serting two fine circular wound wires, over which slides the antenna lead-in contactor. Right-hand (clockwise turn of the knurled knob) connects antenna to short-wave receiver; the other way connects the Zenith broadcast receiver to the antenna.

Tubes in detector and audio amplifier stage are 27's. Filament current supply is from a separate filament transformer, placed within the Zenith cabinet. Plate supply is furnished by a Majestic type Raytheon "B" Eliminator, minimum output, 135 volts. Only two voltage taps are used, the 45 and 90 volt taps, respectively. However, this voltage is previously regulated by means of the resistor controls of the eliminator. Experience will determine which voltage is best for the detector and first amplifier—which is done by turning the knurled knobs on the eliminator.

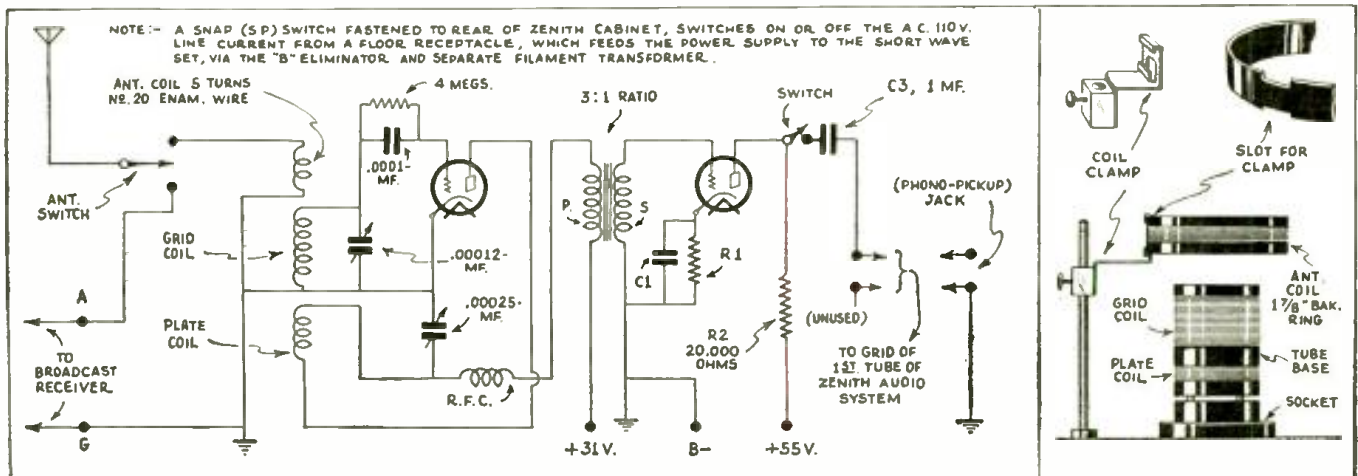You will note there is no cathode (Continued on page 317)



Connections between the few pieces of apparatus required for building the 2-tube A.C. receiver, which Mr. Wagner finally found the best after many trials, are given in the diagram above.



"Aching all over, Bill connected up the dynatron frequency meter and set the dial reading to 10.1, the position that corresponded to the frequency of the police transmitter. . . Doc, standing behind the amateur, allowed nothing to escape his eagle eye and acute ear. . ."

# ATTENTION! All Squads!

● **THOUGH** Bill heard the door of his radio shack open and close, he did not turn around to welcome the visitor—a peculiarity which never failed to offend those who did not know the amateur well, and again, never failed to amuse those who were fortunate enough to be called friends. Though the latter chaffed the amateur on this apparent unsociability, they knew it was not bad manners that caused this eccentric behavior, but on the contrary, complete attention to the ham who was being worked.

Accordingly Bill, oblivious to his visitor, went on chewing the rag with the 160-meter fone down in Aurora, Illinois, three hundred miles away; a no mean distance what with a pair of overloaded '10's as oscillators and skip-distance being by no means great on 160 meters even allowing for nightfall.

"Glad to hook up with you, old boy," chatted Bill. "I was just going to pull the switch when I heard you calling CQ. Never heard such a dead night!"

## An Unwelcome Visitor!

Had Bill eyes in the back of his head, they would have blinked in surprise at the sight "before" them. For they would have seen not the clean-cut youth that distinguishes most amateurs, but instead, a repulsive, sallow, hawk-faced individual.

And were the mythical eyes critical they would have detected a slight droop

By **FRED E. EBEL**  
W9CZU

of the man's shoulders indicative of many years of hunching over pool tables.

Yet with all his repellent mien, Bill's visitor showed in his pinched features a high intelligence, or, considering the man's reputation, a misguided intelligence.

For the "uninvited guest" was none other than the notorious gang leader, "Doc" Turk, the same man who, years ago, had won a scholarship for his brilliant essay "The Prevention of Crime." The same man, too, whose abrupt departure from the university caused considerable concern. Even more concern when the school treasurer reported a deficit of two thousand dollars from the school safe. But at the time of this startling revelation, the versatile Mr. Turk had already forged commercial operator's papers, and, though his knowledge of the code was no greater than the average lid's, was pounding brass two thousand miles at sea on a dirty fruit vessel.

At this occupation of "Sparks" he engaged himself for five years, until, growing old enough to recognize the possibilities of capitalizing on his evil genius, Mr. Turk struck out for the Big City, not however without first relieving the captain of his life's savings.

Here he established himself as a ring leader and acquired the appellation of "Doc" undoubtedly because of his erudition.

From that time on Doc Turk's unsavory adventures have been almost daily chronicled in the papers. Even now he was making crime history. . . .

## The Fight!

Doc Turk smiling mirthlessly over the statement that it was a dead night, strode over to the 110-volt line-switch and threw off the current.

"Hey!" exclaimed Bill noticing the meter needles falling to zero. "Hey!" again, this time more as a gasp as he beheld his unusual guest.

"Sorry, young fellow," Doc said matter-of-factly, "but I'll have to use your station for about fifteen minutes. Just do as I say and you won't get hurt. Now follow me: tune your transmitter to the police station's frequency."

Bill, bewildered and numb of brain just stared at the man. Doc's features tightened; he pulled out a vicious looking Colt. "I'm not fooling," he rasped, "get going!"

The amateur collected some of his wits; he resorted to guile.

"I can't," he lied. "I'm down on 40 meters. The police station's on 122 meters. I couldn't. . . ."

"Doc laughed. "That's one for the book! So you're on 40—indeed! Well, listen here punk"—he wagged the automatic under Bill's nose—"I know you're on the 160-meter band; heard you! I'm an ex-commercial op, kid.

"I could tune this rig in my sleep, but tuning means fingerprints. Now get going—time's valuable and it's just

about time for my boys to pay a little visit at the bank."

Bill saw the futility of argument. He, a mere amateur and this man an ex-commercial operator—no, he could not fool him. But he could lick him! Bill saw that immediately. He, lanky and wiry; his adversary, stunted and dissipated. A short scuffle and it would be all over. Bill would call the police and . . . but that gun!

He had it. He would direct the gang leader's attention off his person and then . . .

"Okay," sighed Bill in mock resignation, "hand me that wavemeter behind you."

The amateur held his breath. Would the gangster turn? He did. Viciously Bill struck out. The Colt went spinning and clattering across the floor, finally coming to rest in a corner. Bill lost no time pinning his light assailant to the floor. Now for the police. For once he regretted that his shack was practically sound proof; shouting would be of no avail.

But he had a transmitter! One that thousands of amateurs and short-wave fans could hear. Right in his block was a BCL with a short-wave converter. . . .

It was laborious lunging and pulling the gangster toward the 110-volt line-switch which Doc had just a few moments ago shut off. But, finally, with one knee pressing unceremoniously on the raging crook's chest, Bill threw the

switch. He waited for the tubes to heat.

And now the unhappy amateur had cause for further regret; the speech amplifier's pickup was crude. One had to speak directly into the "mike" and the latter was behind him on the table, five feet away! And that which would have simplified matters—the automatic—lay in the opposite corner of the shack. Bill was upon further thought glad of this. He did not want to fight for the gun's possession. One would probably be killed. The radio was safer.

The tubes were warm now. Bill, inwardly cursing his procrastination in building a more efficient speech amplifier, turned his head toward the "mike" and yelled: "Hel . . ."

But he got no further. In that brief unguarded moment Doc had twisted his head and sunk his teeth into the amateur's arm. Instead of "Help" an agonizing cry of pain was broadcast.

Instinctively Bill's good arm pressed the wound. Doc took advantage of this. He sprang up and kicked the amateur in the stomach. Then throwing off the switch, he propped the gasping youth into a chair.

"Why, you—" Doc was inarticulate with rage, while Bill, fighting for air, felt like dying.

"One more slip like that, chump, and out you go!" warned Doc, the gun once more giving him the courage he desired. "Now will you get going, or should I let you have it?"

Cold steel pressed on to Bill's forehead. He did not want to die; he would do it.

●What would you do if you were the owner of an amateur transmitting station and was suddenly confronted by a gangster with a drawn gun, who ordered you to tune your station so as to interfere with police radio waves? This was the unusual experience through which Bill Jensen passed, and whether you agree with the way he reacted or not, we are sure that you will admire the clever bit of radio science which Bill brought to bear on the situation. How did the police learn of the situation in Bill's shack?

**Heterodyning with the Police Radio**

Aching all over, Bill connected up the dynatron frequency meter and set the dial reading to 10.1, a position that corresponded to 122 meters, or 2,458 kilocycles, the frequency of the police transmitter.

Doc, bending over the amateur's shoulders, allowed nothing to escape his eagle eye and acute ear. He checked every detail, even adjusting the condensers of the transmitter to zero beat with the monitor's note. Bill could hardly help admiring the fellow's thoroughness.

"We didn't allow the tube of the frequency meter to warm up," observed the ex-commercial operator. "That means 'frequency drift' which suits me just fine. Our frequency will be slightly off of the cop's wavelength and won't those signals sing a sweet heterodyne!"

Bill did not appreciate the gang chief's humor. He simply sat nursing his aches and unhappily wondering if his friends would visit him in jail. From the latter, Bill's active imagina-

tion took a more grim and morbid turn. He saw the gang chief's hoodlums breaking open banks, killing objecting watchmen, and, in general, running the gamut of crime, while the police radio—an impotent array of shiny expensive apparatus less useful than a peanut tube oscillator with loop modulation! Into these unpleasant meditations Doc's voice barked:

"How do you test the tone quality of your rig?"

"Phonograph records," replied the amateur listlessly.

"Fine! Put one on the turntable. If the heterodyne squeal doesn't mess up enough this will."

"No records," from Bill.

"No records? What do you call this?"

Doc held up a small aluminum home recording disc.

Bill's eyes flashed; he tried to answer calmly:

"Oh, that? That's one of those home recording records. My little brother made it during the Christmas holidays.



(Continued on page 315)



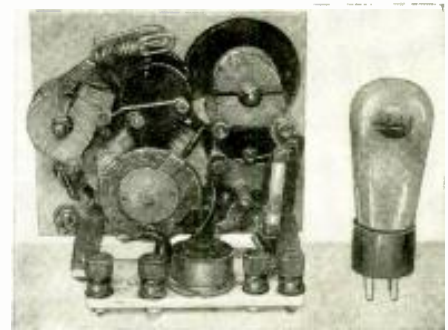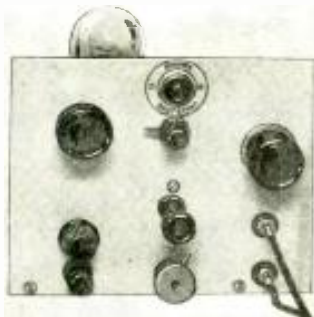**The "Tinymite" 1-Tuber Rolls 'em In**



All ready for action—the "Tinymite" 1-tube S-W Receiver and phones.



Rear view of the "Tinymite."

● THE tickler switch of the *Tinymite* receiver rotates from the bottom to the top for higher waves, so that when the tickler switch is set on the third point from the bottom and the secondary switch is set on the third point from the top, they are on 160 meters and one should be able to hear amateurs, phone, police calls and airplanes. If the set refuses to oscillate on the lower waves, keep moving the tickler switch toward the top. If broadcast waves are desired, turn the secondary switch to the bottom point and leave tickler switch on the 160 meter or third point from the top, or move up to the top point.

The author has a confirmation on duplex speech between W3KL and Sandy Hook, N. J., and other "DX" records, which he can swear to if necessary. He has received (at Tionesta,

Pa.) amateurs, phone, police calls, pilots in planes, plane stations and broadcast, all on a sixty-five foot aerial, one 45 "B" battery and 4 1/2 volts "A" battery on a 99 tube, which seems to work best in the set. You might try a 30 type tube.

The author has heard police calls from Lansing, Pittsburgh, Cincinnati, Chicago; plane stations such as Toledo, Indianapolis, St. Louis, Cleveland and New York. The regeneration slide is critical on airplanes. If the set fails to oscillate pull the coils together, if too much, push apart, slowly turning the tuning condenser.

The aerial condenser is critical and seems to work good when set close; try adjusting it for different wavelengths. Give the set a critical test on a real aerial. If too much oscillation

occurs shorten the aerial or adjust aerial condenser slowly.

The author's original reception check shows:

WRDS	W1BCR	W1DFF
WKDN	W3KL	W3XK
WPDC	W8DHT	W8ATM
W8FCL	W8HN	W8KFF
W8ACI	W8AGE	WBCW

**Parts List for "Tinymite"**

- 1—celluloid panel—bakelite may be used, 4 3/4 x 5 3/4
- L1—The secondary is a coil taken from old Crosley "pup." It was tapped at four evenly divided places.
- L2 is the tickler, a coil taken from RCA old type superhet. It is tapped at four evenly divided points.
- C1—.0001 mf. midget condenser, Hammarlund (National)
- C2—vernier condenser, 10 to 20 mmf. capacity. —Hammarlund (National)
- C3—.0001 mf. midget regeneration control condenser.

(Continued on page 306)


# WORLD-WIDE SHORT-

## Automatic Volume Control

(From *Wireless Magazine*—London, England)

● AUTOMATIC volume control is in great favor at the moment. In the author's experience this refinement is only about 50 per cent effective and decreases the volume on weak signals, increasing the background noise between adjacent stations. Of all the systems tried, a detector limiting device was to be preferred as it helps to stabilize the output more than others.

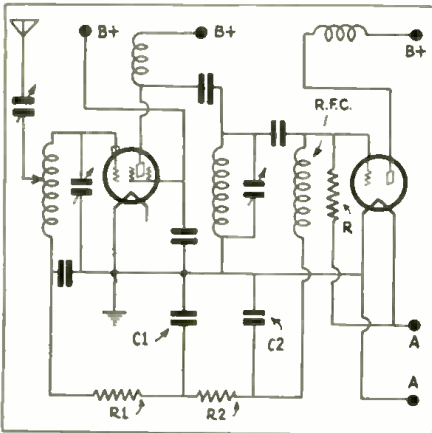"The arrangement is very simple and in operation, all you need do is push up the reaction (regeneration) to give the maxi-




A new English circuit providing automatic volume control for short-wave reception.

mum amplification on a moderately weak signal; when a local or other powerful transmitter is tuned in, the output limiter will come into operation, keeping the volume at the same level all the time.

"The diagram shows the principle of the idea. Unless two high-frequency stages or high magnification A. C. valves (high amplification A. C. tubes) are used, the normal methods of automatic volume control are not to be recommended."

"I have not tried a double-diode triode or the simple double diodes in a short-wave—perhaps this may prove a solution to successful volume control," says the English writer of the article mentioned.

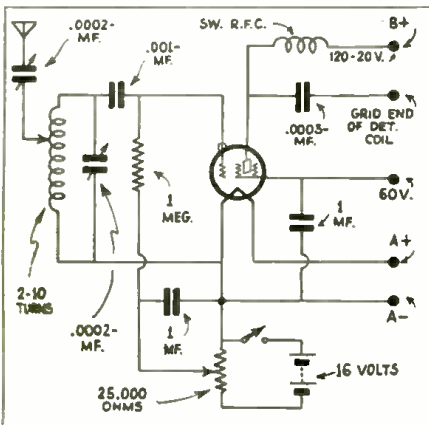The diagram of the detector limiting device is shown here. Unfortunately no data were given, so the experimenter who is interested will have to find the correct values by trial.



Improved screen-grid radio-frequency amplifier hook-up.

● The editors have endeavored to review the more important foreign magazines covering short-wave developments, for the benefit of the thousands of readers of this magazine who do not have the opportunity of seeing these magazines first-hand. The circuits shown are for the most part self-explanatory to the radio student, and wherever possible the constants or values of various condensers, coils, etc., are given. Please do not write to us asking for further data, picture-diagrams or lists of parts for these foreign circuits, as we do not have any further specific information other than that given. If the reader will remember that wherever a tuned circuit is shown, for instance, he may use any short wave coil and the appropriate corresponding tuning condenser, data for which are given dozens of times in each issue of this magazine, he will have no difficulty in reconstructing these foreign circuits to try them out.

## Improved Screen-Grid R. F. Stage

(From *Amateur Wireless*—London, England)

● MANY English "fans" who have built short-wave receivers of the usual regenerative type are finding that the addition of a tuned R. F. stage is quite worthwhile. This unit can be made separate from the main set and be connected to it.

For normal short-wave working the straight high frequency (English term for radio frequency) set has commanded wide support, for in spite of the general belief about the loss of amplification below 100 meters, experience shows that down to about 20 meters real high frequency gain is obtained with a good H. F. stage.

Even down to the lowest of the normal wavebands, that is to say, 14 meters, a stage of screen-grid has proved an advantage in maintaining the smoothness of reaction (English term for regeneration). Moreover, the resulting stabilization of the detector and its segregation from the aerial tuning means that the detector tuning can be calibrated accurately.

For most listeners a stage of tuned-grid coupling should be very useful. The diagram shows how such a stage can be added. There is the usual aerial tuning coil, from 2 to 10 turns, according to the waveband wanted. (It would be better to use another coil identical with the coil in the regular set, so that the tuning would be more or less the same on both the set and amplifier.—*Editor.*) The negative bias is applied to the screen-grid tube by a potentiometer across a 16 volt grid battery (commonly called a "C" battery in the U. S.). The grid-leak and condenser method of applying this bias is strongly recommended.


In the anode (plate) circuit there is a good short-wave R. F. choke, with a .0003 mf. coupling condenser connecting from the

plate to the aerial terminal of the set, that is to the grid tuning coil of the detector.
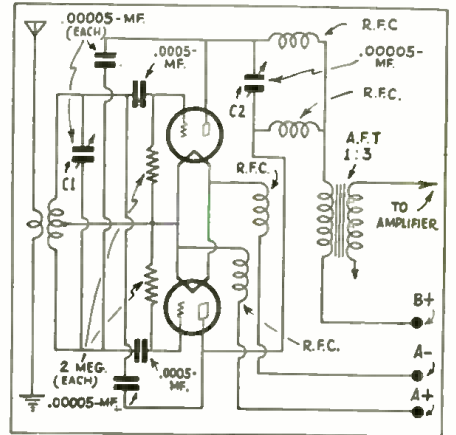
## A Push-Pull Ultra-Short-Wave Receiver

(From *Funk-Technische Monatshefte*—Berlin, Germany)

● IN the field of ultra short waves, the receivers that have become almost universal are certain forms of the super-regenerative circuit and superheterodynes. While these sets are proving their worth, they are often erratic in operation and are very difficult to control.




Superior stability and other features are claimed for this "push-pull" short-wave detector circuit

A different type of ultra-short-wave set is described in the above magazine. The author claims much greater stability with the arrangement shown, with sufficient sensitivity and amplification to compare favorably with the ordinary super-regenerative circuits. The set employs two triodes arranged in phase opposition, so that a push-pull action is obtained.

The circuit shows the values of the capacities required in the various parts of the circuit. The coil data were not given in the article, but the experimenter will find that coil constants supplied for other sets appearing in *SHORT-WAVE CRAFT* may be applied, by changing the value of C1 to suit the coil requirements. The only change necessary is the addition of a center-tap on the grid winding.

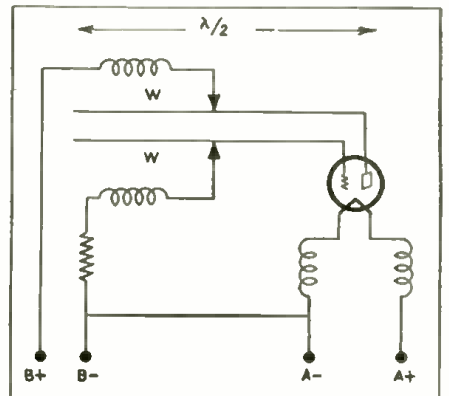While no exact details are available for this circuit, it seems to have merit. The editors will be glad to hear from any experimenter who constructs one of these



With the ultra short-wave system shown, wave lengths as low as 2.8 meters were obtained with high power.

# WAVE REVIEW

Edited by  
C. W. PALMER

sets, as to its stability and also how it compares to other systems for the wavelengths below 10 meters.

## Ultra-Short-Wave Oscillator


(From *World-Radio—London, England*)  
 • DURING attempts which have been made to generate considerable amounts of power at very high frequencies, an entirely new form of circuit has appeared. The new circuit would seem to be a logical development of the Hartley and the Gutton-Touly circuits, which have become the standard circuits for ultra-short waves. It consists of a pair of Lecher wires attached to the tube electrodes (W and W), the difference between this and previous circuits being that L and C are distributed instead of lumped as in the two circuits mentioned above. The tube thus forms an integral part of the Lecher system.

The advantage of this is that the L/C ratio is kept as high as is physically possible, so that much shorter wavelengths may be generated with the same tube. Using a large (30 kw.) power tube, the shortest wavelength obtainable with circuits of conventional form was 6 meters, and then only with low efficiency. With the new system a wavelength of 2.8 meters was obtained and with quite good efficiency (over 20 per cent).

There are, however, apparently two snags in the method. First, the mechanical difficulty of tuning; secondly, on account of the fact that the tube forms part of the transmission line it must be so constructed or joined to the latter that its characteristic impedance is the same as that of the line. Since one cannot insert a transformer between the valve and the line, it is necessary to design the valve mechanically to form part of the line. The most efficient construction appears to be that of cylindrical electrodes of normal form, the line being formed of concentric tubes in continuation of the electrodes. The tubes form the line, of course, and may, in the case of very short waves, form the aerial—since their length is nearly a half-wavelength.
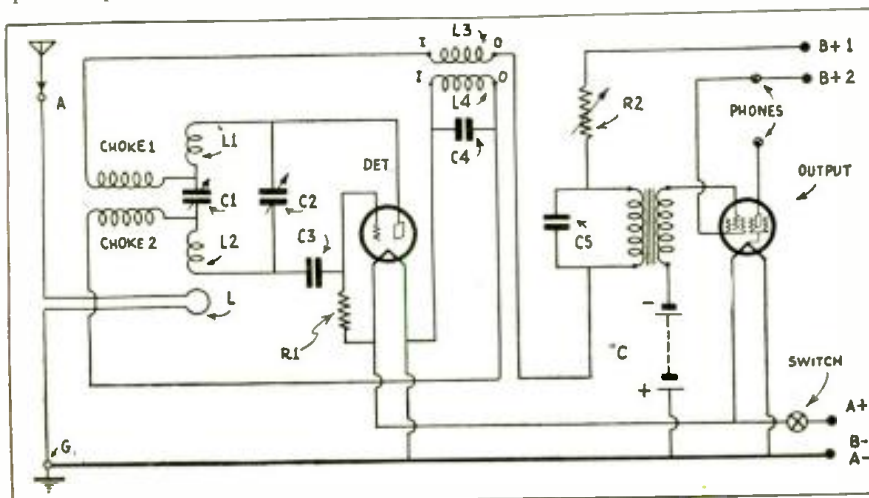
## A 5 to 7 Meter Super-Regenerative Set


(From *Wireless World—London, England*)  
 • THIS set is a simple two-valve (tube) super-regenerative receiver intended for headphone reception; but as its sensitivity is of a very high order, there is every reason to believe that in many cases signals will attain an intensity suitable for loud-speaker reproduction. A single valve (tube)



5 to 7 meter super-regenerative receiver diagram. C1=50 mmf. max., C2=35 mmf. max., C3=.0001 mf., C4=.01 mf., C5=.001mf., R1=2 megohms, R2=50,000 ohms variable.

## U. S. W. Transmitter and Receiver

(From *World-Radio—London, England*)

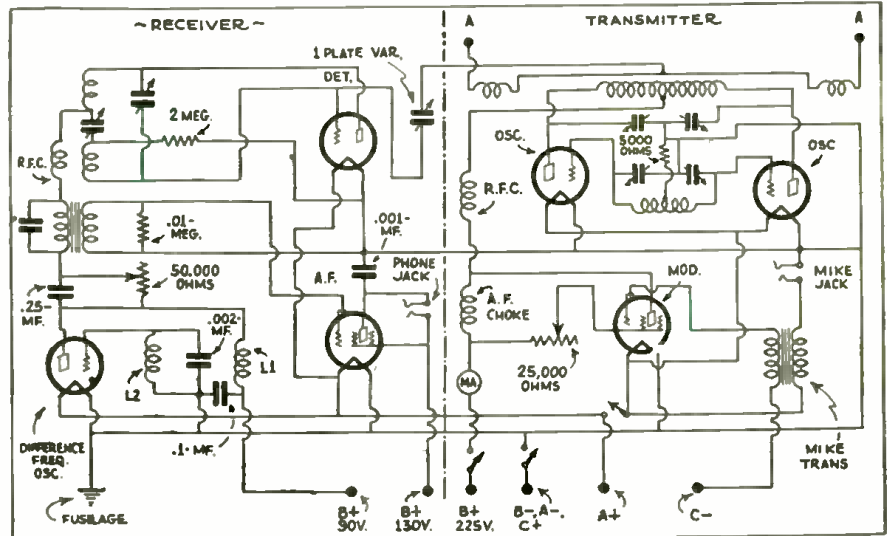

The circuit diagram used in the combined airplane transmitter and receiver here described.

• IN this article there was described a portable transmitter and receiver arranged for duplex telephony on a single aerial for use between an airplane and its airdrome. This transmitter and receiver

is made to serve the dual function of quenching oscillator (better known in U. S. as difference frequency oscillator) and detector, its sensitivity being controlled by a 50,000 ohm resistance R2 in the H. T. ("B" battery) supply lead. A single low frequency (audio) amplifier is employed and coupled to the detector by a step-up transformer. In the last stage either a triode or pentode valve may be used; the latter is recommended as it affords greater amplification.

A few special components (parts) are necessary including one small variable condenser C2, having a very low minimum capacity and a maximum value of not more than 35 mmf. This is used to tune a circuit consisting of two small coils L1 and L2 joined in series with a semi-variable condenser C1. This has a maximum value

(Continued on page 319)

were designed and constructed in the Straits Settlements.

Duplex communication can be obtained by tuning the receiver and transmitter to slightly different frequencies. In this particular case, the wavelengths used were separated by 0.1 meter, being 7.1 and 7.2 meters respectively. Using a push-pull circuit for the transmitter with half-wave Hertzian aeriels, one finds a point in the aerial coupling-coil circuit which is a point of low or zero potential for the transmitted wave. To the received wave, which is of slightly different frequency, however, it offers sufficient potential to allow the transfer of received signals from aerial to receiver. Reception is therefore carried on without interference from the transmitter.

The combined transmitter and receiver was fitted into the front cockpit of a Moth airplane, and the requisite batteries which were housed in the luggage locker in the fuselage were connected to it by means of a multiple cable, with a plug and socket to make easy removal possible. During tests of the range it was found that a maximum for the power used was approximately 10 miles at 5,000 feet altitude.

The weight of the combined unit is approximately 25 lbs. The batteries used weighed 80 lbs., but it is hoped by the use of a wind-screw (air-propelled) generator to reduce the total weight to 50 lbs.


The complete circuit diagram of the transmitter and receiver as operated from the common batteries is shown in the accompanying illustration. It was found advisable to fit a variable resistance of 25,000 ohms in the auxiliary grid circuit of the modulator, to give a control of the modulation as various observers use the microphone in different ways, the tendency for anyone wearing headphones being to shout. The total power input to the transmitter was approximately 3½ watts.

As already stated, the aeriels used were half-wave Hertzian and were simply attached to the wings at a point about 3 feet from the ends of the folding lower wings. Ordinary rubber insulated flexible wire was used and no trouble was experienced.

(No other details about the construction of the units were given than those shown on the diagram. The interested experimenter can easily substitute parts for those not specified. The coils L1 and L2 are the variation frequency coils of the super-regenerative receiver, while the two coils

(Continued on page 317)

# AN ULTRA Short-Wave Converter

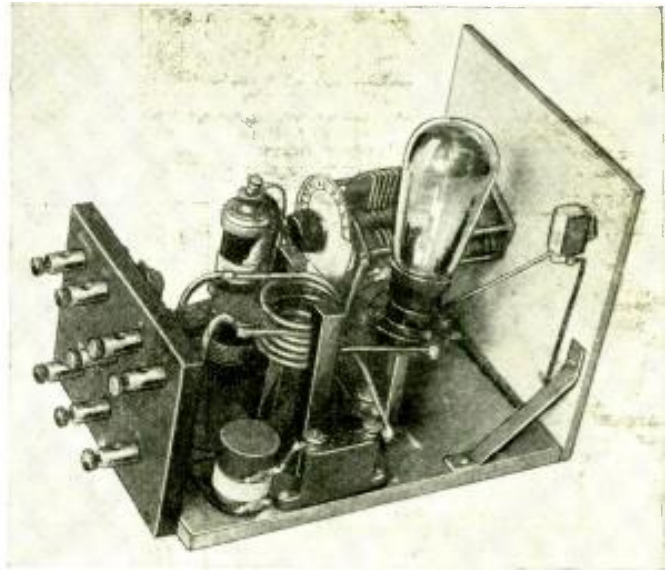

The ultra short-wave converter which uses but one tube; it permits you to tune in waves of from 5 to 10 meters length with your broadcast receiver.

Details for building an ultra short-wave converter to be used with any broadcast receiver, for tuning in waves in the 5 to 10 meter region. It uses but one tube which acts as an oscillator and detector or "frequency changer," forming a superheterodyne when connected to your B. C. set.

● IN some recent experiments conducted by the B.B.C. (British Broadcasting Corp.) in which programs were broadcast on a wavelength of about seven meters, a number of sets were designed to pick up the signals. Preliminary tests made it obvious that receiver technique on seven meters is very different from that of the normal broadcast bands. The length of the aerial, for example, may be no more than the battery leads and much less than the usual ground wire. It is generally better, therefore, to replace the usual ground connection by a counterpoise and couple the aerial to the grid magnetically, so that there is no direct connection. Again, as the tuning inductance for this wavelength consists of about 10 inches of wire, great care must be taken with the layout of parts to avoid long leads.

This receiver is an adapter, consisting simply of an oscillating tube which acts as a frequency changer. By this means, any existing broadcast set can

be converted into an ultra short-wave superheterodyne receiver. The circuit of the adapter is shown in the diagram. The tuning circuit is very simple. An aerial coil L1 is coupled to the grid coil L2, which is tuned by a variable condenser C1, having .0001 mf. capacity. This condenser is made up of two parts, a main section and a vernier section. The main portion is adjusted by a small knob in the rear of the set and the vernier only is operated by the dial on the front panel. This makes the tuning sufficiently stable for ordinary purposes, and still allows the set to cover a reasonably wide wave band.

Regeneration is provided by coil L3 and the plate bypass condenser C2. A plate resistor of 25,000 ohms is used with an output coupling condenser of .001 mf. Four ultra-short-wave chokes are inserted in the battery supply leads.

from the form, the turns will spring and the diameter of the coil increase to about 1 3/4 in. which is the required size. The direction of the winding is important and the sketches of the coils should be referred to in order to ensure the correct result.

The R.F. chokes are of the single-layer type, made by winding 24 turns of number 18 B & S gauge insulated copper wire, with adjacent turns touching, on a form one inch in diameter and 1 1/4 inches long. They may be supported by a machine screw inserted from beneath the baseboard into a threaded hole in the form.

(While the tube recommended for this set cannot, of course, be obtained in the U. S., it can be substituted by any triode with similar characteristics. The original type has an impedance of 4,000 ohms.)

### Tuning Coils

The coils are wound with No. 8 B & S gauge bare copper wire. The aerial, grid and feedback windings each consist of about 1 3/4 turns. They are made by winding the wire as tightly as possible around a wooden form 1 1/4 inches in diameter, spacing the turns 1/16 inch. When the wire is released

### Methods of Operation

To tune in the ultra-short-wave transmission, the first step is to adjust the broadcast receiver to maximum sensitivity with the tuning dial set to a point where *no interference* is produced from the broadcast band. The vernier condenser should then be set to the middle of its scale and the main section of the tuning condenser should be set approximately to tune in the desired transmission. Final adjustments can then be made quite satisfactorily with the vernier condenser. It will be found that there are two tuning points at which signals come in with equal clarity; this is the usual result with this type of adapter. There may also be found two other points at which signals are received, but at which they are much weaker and of poorer quality than the real tuning points.—*World-Radio, London, England.*

### Preventing "Tuning Holes"

● SHORT wave receiving sets, particularly those sets designed for CW code reception on wavelengths below 100 meters, will stop oscillating when they are tuned to the same frequency  
(Continued on page 319)


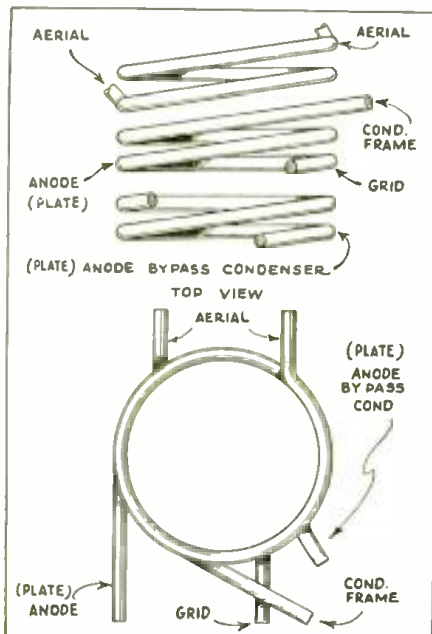


Diagram at left shows details of the ultra short-wave converter coils, while wiring diagram showing how to build this extremely simple converter appears below.

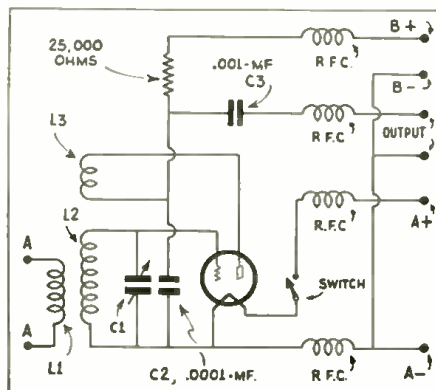



Miss Catherine Martin of Altadena, California, (Call W6JDQ) who has been an enthusiastic "short-wave fan" for several years and who is now one of Uncle Sam's licensed amateur radio operators.

## HATS OFF TO Catherine Martin— Builder of 200 Sets! And She Has An Amateur License Too

Miss Catherine Martin is one of the outstanding, if indeed she is not the outstanding, young lady "ham" station owner and operator of all time. Miss Martin who hails from the sunbathed city of Altadena, California, has had a lot of experience in building and operating short-wave sets in the four years since she first "listened in" on a crystal set. Miss Martin has built around 200 sets, some "broadcast," but mostly "short-wave". She recently passed successfully Uncle Sam's examination for an Amateur Operator's License and her station call letters are W6JDQ.

● ABOUT four years ago, this past Mother's Day, my brother made me a "crystal" set, the first set I ever had. I could only get one station, KFI, on the set at first, but later, when I could just barely hear another station, KHJ, I was thrilled beyond expression. True, I could get all the stations on the family radio, but to be able to receive two stations on my very own set was practically beyond comprehension. Thus, I started in radio.

I had played around with many hobbies previous to this time and I had always been interested in science and mechanics. When I began to experiment with that crystal set I knew I had found my future field.

I was not contented with the crystal set, to make a one or two tube battery set, was at that time my highest ambition. I made that set—and it worked! Wonder of wonders, my head began to swell. At that time A.C. sets were becoming especially popular so I procured a few old D.C. sets. At first I made only broadcast sets and played with them, then my desire for DX took me into the short-wave field.

As a short-wave builder I wasn't so "hot". I did make a set that would bring in the local hams, and even reached up to San Francisco. In the basement of the house I fixed up a room that served very nicely as a workshop.

A little later I got enough money to buy an A.C. Pilot Super-Wasp, and my work in short waves really began. With the Super-Wasp I could easily reach out for the DX I had been wishing for.

### She Has Made 200 Sets!

I guess I've made around two hundred sets, some broadcast or long wave, but mostly S.W. I learned all I knew up to about two months ago just by reading books and magazines, picking it out by myself, and learning much through sad experience.

Two months ago I decided I must begin to really get busy, so I began the Radio and Television Institute course. I have enjoyed it immensely and find it excellent.


Although I have never had an amateur station, I have wanted one and have all the parts for the transmitter. Code work has held me back. Now, however, I have started, with the help of my physics teacher who is an old army operator, a class in code after school. I hope to have a real "ham" station soon.

I am really a disgrace to the feminine population, because instead of having a nice girlish bedroom and closet, I have radio sets in the bedroom, and the closet—horrors!—the shelves are

"chuck full" of old sets and parts. My clothes, instead of being the main articles, are shoved into the corner, and radio things fill every available space.

Everything I have, with the exception of the Super-Wasp, I have made myself, cabinet and radios. In the cabinet, as you can see from the picture, I have three radio sets. On the lower left-hand panel is the Super-Wasp. The panel above the Super-Wasp is on hinges, opening so as to change the coils on the set. In the upper left hand panel is a short wave set I made a short time ago, however I am making another set now to take

(Continued on page 300)

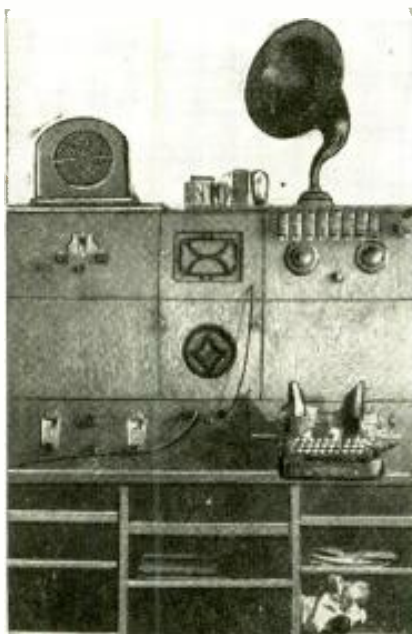

The "operating" desk in Miss Martin's station at Altadena, Calif. Yes, she has a "mill"—and some switchboard, what!



Miss Martin with one of her numerous receiving sets. It has screen-grid tubes 'n'everything.

# WHAT'S NEW

# In Short-Wave Apparatus

The short-wave apparatus here shown has been carefully selected for description by the editors after a rigid investigation of its merits.

## Universal A.C.-D.C. Portable S.W. Receiver

● A HEADPHONE portable receiver for short-wave reception, operating from either the A.C. or D.C. line, requiring few parts, being simple to construct and assuring good performance, is especially attractive to the set builder at this time of the year when week-end traveling is popular.

The fact that good results can be obtained on short waves with the simplest equipment has often been pointed out in SHORT WAVE CRAFT. This fact is substantiated by this receiver which uses but two tubes and a rectifier, yet has a record of having received several European stations in the short time that it was tried out.

The flexibility of this little receiver is of course due to the use of the 25Z5 as a rectifier when A.C. is the supply; the tube being floated otherwise on the D.C. line. For D.C. operation the only use of the tube is for the resistance of its heater, as you can see by referring to the circuit diagram. The filament of this tube in addition to the 200 ohm, 20 watt series resistor serves to reduce the line voltage to the correct value for the two other tubes.

Of these two others, one, the 78 is the detector. While this tube is ordinarily classed as a super-control radio frequency amplifier, it lends itself well to the grid-leak type of detection, with the cathode connected to ground. Since the "B" current of the entire set is only about 16 milliamperes, the three separate chokes in the positive "B" lead drop the voltage only 7 volts, part of which is counteracted by the voltage-lifting effect of the filter condensers.

### The Circuit

As an examination of the diagram will show, the set uses a standard regenerative detector fed into a power pentode audio stage, coupled by the resistance-condenser method. One varia-

tion from the standard type of circuit is in the aerial series condenser. Instead of placing a semi-variable capacity in the set, a variable condenser of 60 mmf. is mounted directly on the panel. The adjustment of this condenser is extremely important in a short-wave receiver, as many of you know.

By correctly adjusting this condenser, the natural wavelength of the aerial is shifted and this often results in an unconscious selection of half-wave and quarter-wave aerial conditions. Whatever the merits of the "measured" aerials may be, at least it is true that the regenerative effect in the detector is increased by decreasing the series capacity which assures satisfactory oscillation on even the highest frequencies.

The actual construction of the receiver is very simple—as explained before. The layout of the parts can be readily seen from the panel view. The values of the parts used are important, however, and it is suggested the original parts be used wherever possible.

### List of Parts

- 1—Set of Powertone short-wave plug-in coils.
- 1—Powertone 50 millihenry R.F. Choke.
- 3—Powertone 30 henry chokes (special low resistance type).
- 2—Hammarlund 140 mmf. variable condensers.
- 1—Hammarlund 60 mmf. variable condensers.
- 1—Powertone .0001 mf. condenser.
- 1—Powertone .01 mf. condenser.
- 1—Powertone 10 mf. condenser.
- 1—Powertone three-section dry electrolytic condenser (16—16—8 mf.)
- 1—Powertone 3 megohm grid-leak.
- 1—Powertone 250,000 ohm resistor.
- 1—Powertone 500,000 ohm resistor.
- 1—Powertone 750 ohm resistor (1 watt).
- 1—Powertone 200 ohm resistor (20 watt).
- 3—Six contact sockets, Alden, (National, Hammarlund).
- 1—Four contact sockets, Alden, (National, Hammarlund).
- 1—Grid clip.

- 2—Pairs of Binding Posts; Eby.
- 1—Line Switch.
- 2—Dials—Vernier Type.
- 1—Knob.
- 1—Powertone metal chassis.
- 1—Six-foot cord with plug.
- 1—Tube shield for 78 tube.
- 1—Powertone metal panel.
- 1—Powertone Carrying Case.
- 1—78 Tube, Gold Seal.
- 1—43 Tube, Gold Seal.
- 1—25Z5 Tube, Gold Seal.

—C. W. Palmer.

## New Glass H. T. Condensers

● WITH the increasing use of high frequencies for transmitting purposes, the need for electrically and mechanically perfect equipment is apparent. With this thought in mind, one radio manufacturer offers a new line of electrostatic capacitors, in




A novel new type of guaranteed high tension condenser for transmitting and similar equipment, the dielectric of which is composed of selected flint glass (No. 117)

which a high quality of flint glass is used for the dielectric medium, instead of paper or other materials.

By using flint glass for the dielectric (Continued on page 299)



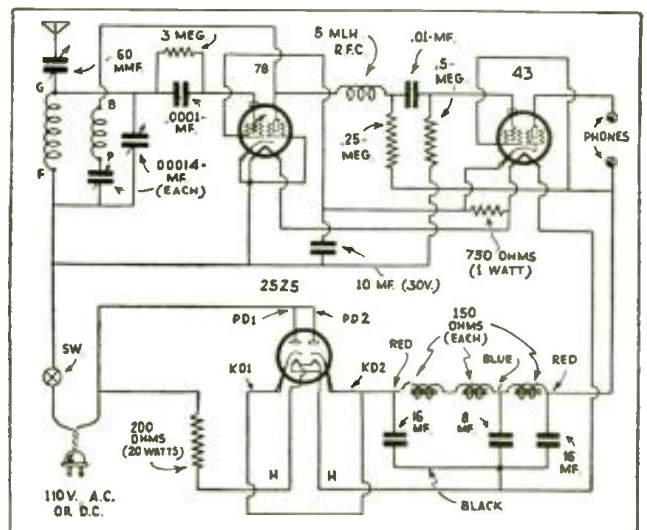Above—C. W. Palmer, author of the accompanying article making actual test with the Powertone portable 110-volt, A.C.-D.C. Receiver. (No. 116)



Simple wiring diagram used in the 110-volt A.C.-D.C. portable illustrated above. The plate current is rectified by a 25Z5 tube. The whole outfit is very light.

(Names and addresses of manufacturers furnished upon receipt of stamped envelope; mention No. of article.)



# VELOCITY... The Latest Microphone

● WHEN Bell invented the telephone, he could not visualize what demand would be made of his invention only half a century later. For fifty years the carbon microphone reigned supreme, but when radio ceased to be an

**By A. Barbieri, E.E.**  
Research Engineer of Bruno Laboratories

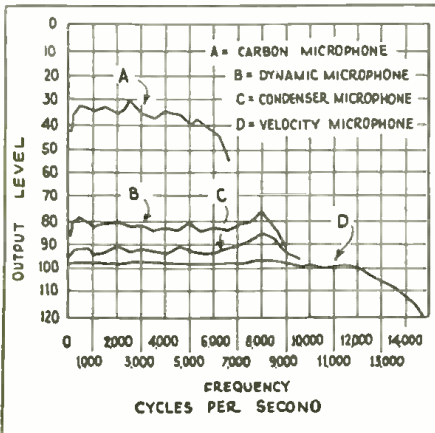


Fig. 1. Graphs showing output level and frequency response of four different types of microphones.

experiment, the first and most important link in the chain of electro-mechanical apparatus used in the transmission of sound was made the object of an enormous amount of research.

The first improvement to appear was the *condenser* microphone. This device consists of two electrodes spaced one thousandth of an inch or more. One electrode is a very thin diaphragm of aluminum, the other a relatively mas-

The velocity microphone has the "whole world by the ears," to use the popular expression, and the editors are glad to present herewith a description of a "mike" of this type, intended for the amateur.

sive disk. The sound waves striking the diaphragm will cause very minute changes in the spacing between electrodes, thus changing the capacity of the device, which in turn, amplified by two or more stages, produces variation in the electrical circuit to which it is connected.

The *condenser* microphone, when properly constructed, is absolutely quiet in operation. There is no possibility of hissing, as this microphone is essentially an open-circuit device—nor is it possible to "blast" it. However, its *output level* is very much lower than that of the carbon microphone and it is for this reason that at least two stages of amplification are necessary before a condenser microphone can be of any practical use.

The *frequency response* of a typical condenser microphone, however, is far superior to that of an average carbon. Figure 1 shows a comparative set of curves taken with four commonly used microphones.

Figure 2 shows a typical wiring diagram exceptionally well suited for a *condenser* microphone *pre-amplifier*.


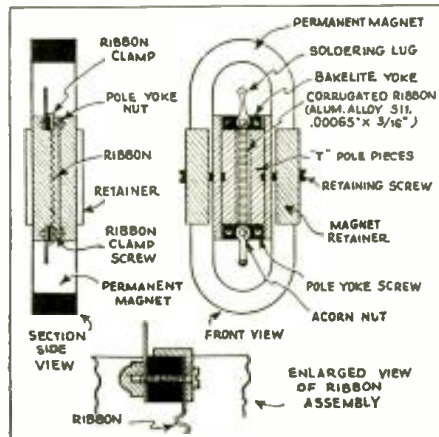


Fig. 4—Sectional view of the Bruno Velocity Mike.

The type 864 tubes are recommended as they are not as microphonic as others. With the proper changes in "A" battery supply, the 30 type tubes can be used satisfactorily.

Next on the list of recent microphone developments is the *dynamic*. Its construction is very similar to the dynamic speaker. It consists of very delicate movable parts, capable of being operated by the very minute energy of the sound waves exerted on the dia-

(Continued on page 309)

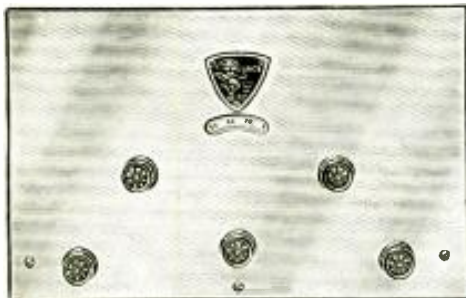


Front view of the Powertone-Wallace S-W receiver.

● MANY short-wave enthusiasts prefer to purchase a completely built, wired and tested receiver from a radio supply house. Others like to "roll their own"; that is, assemble a receiver from a standard kit of approved and specified parts. So that the fancies of all can be satisfied, a well-known radio manufacturer is building Wallace receivers, wired or unwired, or in kit form with complete constructional and wiring information.

One of the obstacles to enjoyable short-wave reception is the difficulty encountered in finding DX stations. This task is simplified in the Wallace receiver by use of a specially manufactured Hammarlund combination band-spread tank-tuning condenser. This condenser is built in two sections; one ("band-spread") of two plates, a stator and a rotor, the other ("tank")
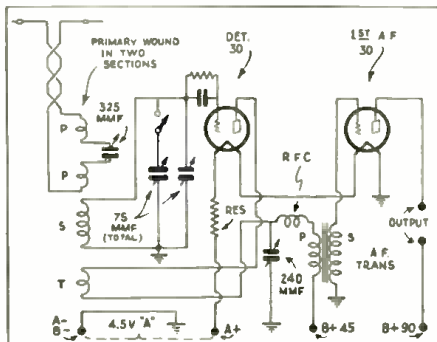
## Powertone-Wallace S-W Receiver

This short-wave receiver represents a new departure, particularly in the design of the antenna coil, which is arranged in two sections with a variable tuning capacity connected between them. This set is especially suited for transposition lead-ins.



Connections used in the new receiver here described; note split antenna coil.



Rear view of the receiver, showing the new type tuning coil.

of nine plates, five stators and four rotors. When a plug-in coil is inserted in its socket, it "band-spread-tunes" the beginning of the band for which the coil is wound. A unique switching arrangement, controlled from the front of the receiver panel, automatically enables the band of the coil to be spread out for that portion to which the coil first responds in wavelength or frequency. Another snap of the control switch on the receiver panel and the *band-spread* section of the condenser is automatically "paralleled" with the larger condenser section and tuning is then accomplished with 11 plates—6 rotors and 5 stators. When used in this manner, the tuning of the receiver is no longer of the band-

(Continued on page 313)

# LETTERS FROM S-W FANS

## Give Us More Station Photos!



Rex Brooks' Amateur Transmitting and Receiving Station

### REX BROOKS' STATION

Editor, SHORT WAVE CRAFT:

I made contact with your "mag." about a year ago and have kept regular schedule ever since. (nuff sed) Thanks for some "FB" dope. Don't care for all the stuff but guess everybody can't be suited all the time.

Have been on the air about four months with a "junk" station, consisting entirely of old receiver parts. The rig, including transmitter, receiver, power supplies, monitor, etc., cost about fifteen bucks to construct, and have sure had plenty of qso with it.

Am inclosing a snap of the "om" and "rig," in answer to your requests for pictures of stations. Hoping that if published it may bring in some "dx" schedules, missing qsis, ham correspondence or "what have you."

REX BROOKS, W7CSI,  
121 West Works St., Sheridan, Wyo.

*(Fine business, Rex and we are glad to publish the interesting picture of your transmitting and receiving station herewith. We bet you thoroughly enjoy this outfit and we note also that you built it at a very reasonable figure. It just shows what a lot of "real fun," packed with many "thrills," you can really get out of short waves, especially when one has the courage and persistence to master the telegraphic code and take the government examination so as to go "on the air" with their transmitter. We hope many more of the "brothers in that great short-wave fraternity," will kick in with some good photos of their stations, including the "OM" himself.—Editor.)*

### THE 1-TUBE OSCILLODYNE A "PIP"

Editor, SHORT WAVE CRAFT:

I receive the SHORT WAVE CRAFT magazine every month and I think it is the best radio magazine out. I built the one-tube Oscillydne set described in the April issue and I think it's a "pip."

I have picked up stations all over the

United States and other parts of the world. Here are some of the stations, in the U. S. I have heard—W8XK Pittsburgh, W2XAF Schenectady, W1XAL Boston, W9XAA Chicago, W3XL Boundbrook, N. J., W1XAZ Springfield, Mass., WEA Rocky Point, W9XF Chicago, W8XL Dayton, Ohio, WOO Deal, N. J., and a few ships at sea.

I will let you know again some time how your set is working. Foreign—VK3ME Melbourne, VE3BW Bowmanville, Ont., VE9GW Bowmanville, Ont., VK3ME Sydney, Australia, GSB Daventry, Eng.

JIMMIE LEES,  
Excelsior, Minn.

*(Fine business, Jimmy, and we shall be glad to hear from you again with another list of stations that you pick up on the "Oscillydne."—Editor.)*

### Oscillydne "Greatest Yet"

Editor, SHORT WAVE CRAFT:

I sure have good news for you! I completed the "Oscillydne" this afternoon and it is the greatest yet. I believe it will be as famous as the "Doerle"—maybe! It sure beats my 2-tube "junk pile" and I don't mean maybe.

I haven't had time to bring in a good list of stations yet, but there are about ten I have got and you will get a lot more later even if you don't want them!

Two days ago I received my SHORT WAVE LEAGUE certificate, so guess I belong to the "gang." I would like to know if there are any other SHORT WAVE LEAGUE members in my town, or in cities near by.

RAYMOND E. HARRIMAN,  
53 Howland Ave.,  
Jamestown, R. I.

*(Your experience, Raymond, was similar to the editors', who have experienced exceptionally fine results with the "Oscillydne." One thing about the Oscillydne that you have undoubtedly noticed is that the dial is "alive" with stations on practically every band, or at least whenever you listen in at the right time, so that there are stations on the air transmitting at the wavelengths you are tuning to at that particular time of the day. Another point in favor of the Oscillydne is that it does seem to get the most out of whichever tube you happen to be using with it. The editors have tried the Oscillydne with both battery and A.C. tubes and it has invariably shown uniformly fine results—plenty of sensitivity and volume.—Editor.)*

### NEWS FROM SHANGHAI!

Editor, SHORT WAVE CRAFT:

I read with great interest, the article "Short-Wave Record Set by League Report," written by H. Winfield Secor, in the May issue of SHORT WAVE CRAFT, in which it was described how the radio operators of the New York Times station received the "League of Nations Report and Recommendations" which was sent by the Geneva station, "HBP," on February 18, 1933.

Perhaps your readers would be interested in another radio operator's point of view, regarding the reception of that "memorable" report.

A Russian radio operator, assisted by the writer, received the above mentioned report on that date, for Reuters, Limited, an English News-Agency here in Shanghai.

We received notice from our office that the Geneva station, HBP, would send the "League of Nations Report and Recommendations" on that date. Due to a mix up in time, about 1,000 words of the beginning of the report, was lost, and also because of QRM from harmonics of a broadcast station, which is very close to our station. We actually began copying the report, from about 10:45 p.m. (Shanghai time). The entire reception, was by means of headphones and a typewriter, no tape recorder was had or was used. So the speed of about 25 words or so a minute, which was maintained by the Geneva station throughout the report, suited us admirably.

The "Report" lasted from about 10 p.m. to about 8:30 a.m. (Shanghai time). Signals were very good and steady, about QSA 5 R 6-7, with slight traces of fading.

The receiver used, and which has been in use in this station for more than two years and which is still "going strong," is a "Marconi China Receiver, Type S.W. 32." This receiver, built in China, consists of three tubes of English make. They are 4 volt tubes and 135 volts of "B" battery is used. The "C" battery is a 4½ volt type with tappings for 3 volts. Filament supply is from a 4 volt storage battery.

The receiver is at the present moment being used for the bulk of our press work in this receiving station, since the long wave receiver, which we use for 18,500 meters, is now useless, owing to weather conditions. The long wave receiver is used during the winter months for press from Great Britain.

The antenna which we use all the time for short wave work, is about 50 feet long, in an East-West direction, with the lead-in connected in the eastern direction. The lead-in is about 20 feet long. No ground was used or is used for all receptions.

The circuit of the above mentioned receiver, is of the conventional regenerative detector and two stages of audio amplification. Compare this one with the elaborate receiver employed by the NEW YORK TIMES station.

Besides receiving the 15,000 word "report" from Geneva, it was our duty to receive the daily presses from Japan and Great Britain, so anyone can imagine how busy the two of us were on that day.

The "Reuters" receiving station is located on the ground floor of a four story apartment house. The antenna, which is on the roof, is supported by two bamboo poles about 30 feet high, each. We, the two of us, have received from Japan and Great Britain and several other countries, more than 101,000 words in one month!

I wish also to mention that the reception of the "report" from Geneva was entirely on 38.47 meters.

The main idea of this letter is to bring out the lack of elaborateness or preparedness on our part and the care and preparation indulged in by the operators of the NEW YORK TIMES station.

I also wish to mention that this station is not the station in Shanghai, which was mentioned in Mr. Secor's article.

FRANK M. LEE,  
Seymour Road,  
Lane 643, House No. 8,  
Shanghai, China.

## IF

YOU have built one of the S-W Receivers described in this magazine and you obtain good results with it—write the Editor and tell him about it. He will also welcome constructive criticism.

*(F.B. (fine business) O.M., you and your buddy certainly did a fine piece of work in the reception of the Geneva report over such a vast distance and with just a 3-tube receiver. Sounds almost impossible, but just shows what a "good 3-tuber" can do when it is expertly handled. This should be great news for all S-W fans, especially in these days when 3 tubes is about the limit for many pocket-books. We salute you!—Editor.)*

# Bouquets and Brickbats from Our Readers

## CHANGES OSCILLODYNE TO S-W ADAPTER

Editor, SHORT WAVE CRAFT:


I just can't resist from writing to you about the 1-tube Oscillodyne, which I think might be of interest to the ones who have made this set. I have changed it into an adapter, on which I receive these stations regular, with good volume and clearness—IJJD, Germany; EAQ, Madrid, Spain; FYA, France I2RO, Rome, Italy; GSB, England, and many others.

There is no change in the Oscillodyne receiver; this makes it possible to use it as an adapter or receiver. To change it into an adapter get a 5 prong tube base, solder a piece of wire about three feet long to prong P, and another piece to C, one to F minus and another to F plus. The leads F minus and F plus are twisted to reduce hum. Connect the wire from P to output of the Oscillodyne, C to the ground, F minus and F plus to the filament of the Oscillodyne. Remove the '27 (det.) tube from the broadcast receiver, and put the adapter plug in its place. Place the '27 tube in the Oscillodyne. Remove the Ant. and Gnd. from the broadcast receiver, and connect them to the Oscillodyne. Turn on the set and it will be ready for operation in about a minute.

Some experimenting might be necessary on the condenser marked X in the hook-up, and on grid leak R. I am using a .0005 mf. and .00025 mf. for condenser X and a 6 meg. grid-leak for R. Here's hoping anyone trying this adapter has as much luck with it as I am having. I would be glad to hear from anyone that does try it; I will also answer any questions concerning the Oscillodyne Adapter.

SAUL KORNEKE, Jr.,  
2032 Lautner St.,  
N. S. Pittsburgh, Pa.

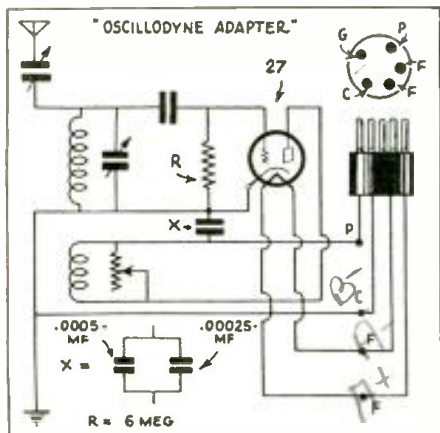(Great idea, Saul, and we are publishing your diagram herewith, for the benefit of other short-wave "fans" who may like to try out this improved short-wave adapter.—Editor.)



How Mr. Korneke, Jr., wired his Oscillodyne for use as a S-W Adapter.

## WHOLE WORLD ON THE DOERLE

Editor, SHORT WAVE CRAFT:

I have had a "Doerle" set for two months and I would like to tell you of the results. Here they are:

- |         |   |           |                          |
|---------|---|-----------|--------------------------|
| Canada  | VE9GW<br>VE9DR<br>VE9JR<br>VE9CS<br>CGA | Two waves | VEX<br>CFA<br>CCD        |
| England | GSA<br>GSB<br>GBS<br>GBK                |           |                          |
| Germany | DJA<br>DJB<br>DJC                       |           | Australia VK3ME<br>VK2ME |

## William Wolf's "Listening Post" Is a Corker!



The photo above shows the short-wave Receiving Station of William Wolf, 265 E. 176 Street, Bronx, New York City. Mr. Wolf has been a prolific reader of Short Wave Craft and he has built a number of sets described in various issues. No. 1 is the "Globe Trotter"; 2, is a 3-tube receiver with 2 shield-grid tubes, detector and 2 A.F. stages; 3, is the "2 R.F. Set" described in a previous issue of this magazine, and comprising two shield-grid T.R.F. stages, with a detector and two audio stages; 4, is a self-contained "1-tube" battery set, with a filament voltmeter on the panel, all batteries being included inside the cabinet; 5, is a general "test switchboard" fitted with numerous meters for testing, also jacks which provide the various plate potentials for operating the different receivers as desired; a power amplifier as well as loud-speaker are also mounted in this cabinet. No. 6 indicates a 3-tube receiver of the fully shielded type and comprising 1 S.G., R.F. stage—1 S.G. detector and 2 A.F. stages.

- |             |       |           |  |
|-------------|-------|-----------|--|
| Spain       | EAQ   | U. S.     | W8XK<br>W1XAZ<br>W2XAF<br>W3XAU<br>W3XE<br>W4XAA<br>W5XF<br>WZNAL<br>WOO |
| France      | FYA   | Two waves |  |
| Italy       | I2RO  |           |  |
| Switzerland | HBL   |           |  |
| Venezuela   | YV1BC |           |  |
| Columbia    | HKD   |           |  |
- Also two ships, the *Majestic* and the *Empress of Britain*, besides many amateurs, police and air port stations.
- KENNETH PRATT,  
514 Eliot St., Mattapan, Mass.

(Well, well, Kenneth, you seem "to take the cake"—some dandy list of "foreigners"—and all on a little "Doerle" receiver. You do not state whether it is the two or three-tube Doerle that you hung up this fine reception record with, but we know, from the hundreds of letters reporting great success with the Doerle receiver, that either the two or three-tube Doerle will "bring home the bacon." The reason why the Doerle brings in the DX stations in such wonderful fashion, is undoubtedly due to the fact that it is basically sound and does not employ a "freak" circuit. Some of the results that builders and owners of the Doerle sets write the editor about, seem almost unbelievable but we know that they are undoubtedly genuine, from the fact that so many readers have attested to the reception of the same stations over and over again. Here's wishing you plenty of thrills with the Doerle.—Editor.)

## WELCOME CRITICISM

Editor, SHORT WAVE CRAFT:  
I have just bought the June number of SHORT WAVE CRAFT and read Mr. R. G. Hunt's comments, page 104.

While I certainly agree with the first paragraph, I would like to say my "But" to the rest.

I am a reader of this splendid magazine and RADIO-CRAFT since 1930 and have not missed a single number, and when I get my copy I look for the big set and not the small "Junk Box Two." I was tickled to see the "pet stenographer" with the nine

tube "super-hot," rather than with the silly earphones and the one tube "Gogriphem-signalifyoucan."

May be it will occur to some of the boys that other fellows are pretty far away and the next station you care to hear is about 6,000 miles from here! In this case there is only one thing, and that is the all-wave "super," 10 tubes and up, if your "family" is to enjoy it too.

It is the big set which inspires the man who wants it, more than anything else and I trust SHORT WAVE CRAFT will soon bring out one again.

C. H. MIRTLE,  
São Paulo, Brazil.

(Blaze away, Brother Mirtle! We like it! Constructive criticism is always valuable and welcome. Yes, we agree that many of the "boys" like yourself, are far from home and the editors have not forgotten this fact either. Nowadays, with a depression still within our memory and money not so plentiful, we know that thousands of our readers are not interested in sets using more than 3-tubes, perhaps. However, you will note a number of sets described right along, especially those of the "super-heterodyne" type, which we believe you will find thoroughly reliable for reception of stations all over the world, even in your location. The "band-spread" Short Wave Superhet, described in the July and August issues, by George W. Shuart, is particularly recommended as this set has "high gain" and it also enables you to spread the stations over the dial "on any band"! It is one of the very best short-wave receivers that the editors have ever had the pleasure of operating.—Editor.)

## FROM ITALY! AND HE LIKES S.W.C.

Editor, SHORT WAVE CRAFT:  
Only a few months ago I have "discovered" your magazine and from that time I did not leave off buying it. I can state that every issue is full of news and descriptions the amateur is looking for.  
(Continued on page 303)

# SHORT WAVE STATIONS OF THE WORLD

## SECTION TWO

The lists that appear here-with comprise Section Two of the SHORT WAVE CRAFT index of the world's short wave stations, which has proved very popular with S. W. fans everywhere. As compared with Section Two published in the July, 1933, number, it represents many additions and corrections. A member of the staff of SHORT WAVE CRAFT

Section One of this list, which appeared in the August, 1933 number, contained a "grand" list of short wave relay broadcasting, experimental and commercial radiophone stations. It will appear in the October, 1933 number, with further additions and last minute corrections.

made a special trip to Washington, D. C., to obtain authentic data directly from the Federal Radio Commission. Please write to us about

any new stations, changes in schedules or other important data that you learn through announcements over the air or correspondence with the stations themselves. A post card will be sufficient. We will safely return to you any verifications that you send in to us. Communications of this kind are a big help in tracking down new stations.

## AIRPORT RADIO STATIONS

The airport stations do not follow any fixed schedules, and are likely to be heard any time of the day or night. The airplane transmitters are usually heard on the same wavelengths. The little "boxes" are for your dial settings.

<p><b>Group One</b> <input type="text"/></p> <p>94.86 m.-3160 kc. 53.83 m.-5570 kc.                  94.56 m.-3170 kc. 53.74 m.-5580 kc.                  93.29 m.-3215 kc. 53.64 m.-5590 kc.                  52.98 m.-5680 kc.</p> <p>Bakersfield, Calif. <b>KQK</b>                  Bellefonte, Pa. <b>WNAM</b>                  Boise, Idaho <b>KRA</b>                  Brooksville, Pa. <b>WNAL</b>                  Burbank, Calif. <b>KEU</b>                  Cheyenne, Wyo. <b>KOE</b>                  Chicago, Ill. <b>WUCG</b>                  Cleveland, Ohio <b>WNAK</b>                  Dallas, Tex. <b>KNAT</b>                  Des Moines, Iowa <b>KQM</b>                  Elko, Nevada <b>KKO</b>                  Fort Worth, Tex. <b>KGUC</b>                  Fresno, Calif. <b>KGT</b>                  Iowa City, Iowa <b>KQQ</b>                  Kansas City, Mo. <b>KNAS</b>                  Lincoln, Neb. <b>KRF</b>                  Medford, Ore. <b>KGE</b>                  Moline, Ill. <b>WNAU</b>                  Newark, N. J. <b>WNAO</b>                  North Platte, Nebr. <b>KMR</b>                  Oakland, Calif. <b>KFO</b>                  Okla. City, Okla. <b>KNAV</b>                  Omaha, Nebr. <b>KMP</b>                  Orlando Twsp., Ill. <b>WNAT</b>                  Paseo, Wash. <b>KRD</b>                  Ponca City, Okla. <b>KGUZ</b>                  Portland, Ore. <b>KVO</b>                  Redding, Calif. <b>KUT</b>                  Rock Springs, Wyo. <b>KQC</b>                  Sacramento, Calif. <b>KFM</b>                  Salt Lake City, Utah <b>KQD</b>                  San Diego, Calif. <b>KGQZ</b>                  Seattle, Wash. <b>KZJ</b>                  Spokane, Wash. <b>KGTZ</b>                  Tulsa, Okla. <b>KNAU</b>                  Wichita, Kans. <b>KGTE</b></p> <p><b>Group Two</b> <input type="text"/></p> <p>103.23 m.-2905 kc. 60.15 m.-4990 kc.                  97.63 m.-3070 kc. 54.45 m.-5510 kc.                  97.15 m.-3090 kc. 52.88 m.-5680 kc.</p>	<p>60.39 m.-4970 kc. 52.7 m.-5690 kc.                  52.45 m.-5720 kc.</p> <p>Alameda, Calif. <b>KGSB</b>                  Albuquerque, N. M. <b>KSX</b>                  Burbank, Calif. <b>KSI</b>                  Butte, Mont. <b>KBTY</b>                  Camden, N. J. <b>WAEE</b>                  Columbus, Ohio <b>WHG</b>                  Cresson, Pa. <b>WAEG</b>                  Harrisburg, Pa. <b>WAED</b>                  Indianapolis, Ind. <b>WHM</b>                  Kansas City, Mo. <b>KST</b>                  Kingman, Ariz. <b>KGTL</b>                  Las Vegas, Nev. <b>KGTN</b>                  Newark, N. J. <b>WAEF</b>                  Pittsburgh, Pa. <b>WAEC</b>                  Pocatello, Idaho <b>KGTX</b>                  Robertson, Mo. <b>KGTR</b>                  Springfield, Mo. <b>KGTO</b>                  Tulsa, Okla. <b>KSY</b>                  Wichita, Kans. <b>KGTD</b>                  Winslow, Ariz. <b>KGTA</b></p> <p><b>Group Three</b> <input type="text"/></p> <p>103.23 m.-2905 kc. 60.15 m.-4990 kc.                  97.63 m.-3075 kc. 54.45 m.-5510 kc.                  97.15 m.-3090 kc. 53.83 m.-5570 kc.                  94.86 m.-3160 kc. 53.74 m.-5580 kc.                  94.56 m.-3170 kc. 53.64 m.-5590 kc.                  94.26 m.-3180 kc. 52.98 m.-5660 kc.                  93.29 m.-3215 kc. 52.88 m.-5670 kc.                  60.39 m.-4970 kc. 52.7 m.-5690 kc.</p> <p>Denver, Colo. <b>KGSP</b>                  Las Vegas, Nev. <b>KGTS</b>                  Pueblo, Colo. <b>KGSR</b>                  Salt Lake City, Utah <b>KGTH</b></p> <p><b>Group Four</b> <input type="text"/></p> <p>93.09 m.-3220 kc. 86.52 m.-3470 kc.                  92.8 m.-3230 kc. 86.08 m.-3490 kc.                  92.52 m.-3240 kc. 61.00 m.-4920 kc.                  92.09 m.-3250 kc. 53.55 m.-5600 kc.                  87.02 m.-3450 kc. 53.45 m.-5610 kc.                  86.77 m.-3460 kc. 53.26 m.-5630 kc.</p> <p>Abilene, Tex. <b>KGUL</b>                  Beaumont, Tex. <b>KGTV</b>                  Birmingham, Ala. <b>WSDE</b>                  Boston, Mass. <b>WSDD</b>                  Mobile, Ala. <b>WAEK</b></p>	<p>Newark, N. J. <b>WSDC</b>                  Tuscon, Ariz. <b>KGUO</b></p> <p><b>Group Five</b> <input type="text"/></p> <p>129.63 m.-2315 kc. 86.08 m.-3490 kc.                  127.33 m.-2355 kc. 63.29 m.-4740 kc.                  93.09 m.-3220 kc. 61.00 m.-4920 kc.                  92.8 m.-3230 kc. 53.55 m.-5600 kc.                  92.52 m.-3240 kc. 53.45 m.-5610 kc.                  92.09 m.-3260 kc. 53.26 m.-5630 kc.                  87.02 m.-3450 kc. 45.87 m.-6540 kc.                  86.77 m.-3460 kc. 45.8 m.-6550 kc.                  86.52 m.-3470 kc. 37.43 m.-8015 kc.</p> <p>Albany, N. Y. <b>WSDM</b>                  Atlanta, Ga. <b>WQPD</b>                  Bera, Ohio <b>WSDQ</b>                  Big Spring, Tex. <b>KGUG</b>                  Brownsville, Tex. <b>KGUE</b>                  Burbank, Calif. <b>KGUR</b>                  Chicago, Ill. <b>WSDG</b>                  Cincinnati, Ohio <b>WSDI</b>                  Columbus, Ohio <b>WSDP</b>                  Dallas, Tex. <b>KGUF</b>                  Douglas, Ariz. <b>KGUN</b>                  El Paso, Tex. <b>KGUA</b>                  Frijole, Tex. <b>KGUM</b>                  Indianapolis, Ind. <b>WSDZ</b>                  Indio, Calif. <b>KGUQ</b>                  Jackson, Miss. <b>KSDB</b>                  Little Rock, Ark. <b>KQUU</b>                  Louisville, Ky. <b>WSDF</b>                  Memphis, Tenn. <b>WSDK</b>                  Nashville, Tenn. <b>WSDT</b>                  New Orleans, La. <b>WQDQ</b>                  Omaha, Nebr. <b>KGTS</b>                  Phoenix, Ariz. <b>KGUP</b>                  Robertson, Mo. <b>KGUT</b>                  San Antonio, Tex. <b>KGUD</b>                  Shreveport, La. <b>KGUK</b>                  Springfield, Ill. <b>WAEJ</b>                  Waco, Tex. <b>KGUH</b></p> <p><b>Group Six</b> <input type="text"/></p> <p>112.44 m.-2670 kc. 98.83 m.-3040 kc.                  112.27 m.-2675 kc. 55.79 m.-5380 kc.                  105.11 m.-2850 kc.</p> <p>Chicago, Ill. <b>WSDS</b></p>	<p>Duluth, Minn. <b>WSDL</b>                  Fargo, N. D. <b>KNWB</b>                  Madison, Wis. <b>WSDR</b>                  Milwaukee, Wis. <b>WAEH</b>                  Pembia, N. D. <b>KNWC</b>                  St. Paul, Minn. <b>KNWA</b></p> <p><b>Group Seven</b> <input type="text"/></p> <p>111.19 m.-2680 kc. 51.5 m.-5820 kc.                  102.1 m.-2935 kc.</p> <p>Detroit, Mich. <b>WAEI</b></p> <p><b>Group Eight</b> <input type="text"/></p> <p>129.63 m.-2310 kc. 45.87 m.-6540 kc.                  127.33 m.-2355 kc. 45.8 m.-6550 kc.                  86.52 m.-3470 kc. 45.73 m.-6560 kc.                  63.29 m.-4740 kc. 37.45 m.-8010 kc.</p> <p>Blythe, Calif. <b>KGUS</b>                  Buffalo, N. Y. <b>WSDO</b>                  Houston, Tex. <b>KGUB</b></p> <p><b>Group Nine</b> <input type="text"/></p> <p>126.1 m.-2380 kc. 63.22 m.-4740 kc.                  101.83 m.-2950 kc. 53.07 m.-5650 kc.                  100.46 m.-2990 kc. 45.52 m.-6590 kc.                  72.11 m.-4160 kc. 45.45 m.-6600 kc.</p> <p>Atlantic City, N. J. <b>WEEQ</b>                  Baltimore, Md. <b>WEEB</b>                  Charleston, S. Car. <b>WEEC</b>                  Greensboro, N. Car. <b>WEEG</b>                  Jacksonville, Fla. <b>WEEJ</b>                  Linden, N. J. <b>WEEN</b>                  McRae, Ga. <b>WEEH</b>                  Miami, Fla. <b>WEEM</b>                  Orlando, Fla. <b>WEEO</b>                  Richmond, Va. <b>WEER</b>                  Spartanburg, S. Car. <b>WEEF</b></p> <p><b>Group Ten</b> <input type="text"/></p> <p>113.29 m.-2650 kc. 45.59 m.-6580 kc.                  104.53 m.-2870 kc. 37.43 m.-8010 kc.                  97.32 m.-3080 kc. 36.5 m.-8220 kc.                  55.5 m.-5400 kc. 24.33 m.-12,330 kc.                  53.64 m.-5700 kc. 18.47 m.-16,240 kc.                  45.66 m.-6570 kc. 18.24 m.-16,450 kc.</p> <p>Brownsville, Tex. <b>KGJW</b>                  Miami, Fla. <b>WKDL</b>                  San Juan, P. R. <b>WMDV</b></p>
---	--	--	--

## AIRPORT RADIO STATIONS—Alphabetically by Call Letters

The number in parenthesis following the location indicates the frequency group in which the station operates.

<p><b>KBTY</b> Butte, Mont. (2)  <b>KEU</b> Burbank, Calif. (1)  <b>KFM</b> Sacramento, Calif. (1)  <b>KFO</b> Oakland, Calif. (1)  <b>KGE</b> Medford, Ore. (1)  <b>KGGUC</b> Ft. Worth, Tex. (1)  <b>KGJW</b> Brownsville, Tex. (10)  <b>KGQZ</b> San Diego, Calif.  <b>KGSB</b> Alameda, Calif. (2)  <b>KGSP</b> Denver, Colo. (3)  <b>KGSR</b> Pueblo, Colo. (3)  <b>KGT</b> Fresno, Calif. (1)  <b>KGTA</b> Winslow, Ariz. (2)  <b>KGTD</b> Wichita, Kans. (2)  <b>KGTE</b> Wichita, Kans. (1)  <b>KGTH</b> Salt Lake City, U. (3)  <b>KG TJ</b> Las Vegas, Nev. (3)  <b>KGTL</b> Kingman, Ariz. (2)  <b>KGTN</b> Las Vegas, Nev. (2)  <b>KG TQ</b> Springfield, Mo. (2)  <b>KGTR</b> Robertson, Mo. (2)  <b>KGTS</b> Omaha, Neb. (5)  <b>KGTV</b> Beaumont, Tex. (4)  <b>KGTX</b> Pocatella, Idaho (2)  <b>KGTZ</b> Spokane, Wash. (1)  <b>KGUA</b> El Paso, Tex. (5)</p>	<p><b>KGUB</b> Houston, Tex. (8)  <b>KGUD</b> San Antonio, Tex. (5)  <b>KGUE</b> Brownsville, Tex. (5)  <b>KGUF</b> Dallas, Tex. (5)  <b>KGUG</b> Big Spring, Tex. (5)  <b>KGUH</b> Waco, Tex. (5)  <b>KGUK</b> Shreveport, La. (5)  <b>KGUL</b> Abilene, Tex. (4)  <b>KGUM</b> Frijole, Tex. (5)  <b>KGUN</b> Douglas, Ariz. (5)  <b>KGUO</b> Tucson, Ariz. (4)  <b>KGUP</b> Phoenix, Ariz. (5)  <b>KGUQ</b> Indio, Calif. (5)  <b>KGUR</b> Burbank, Calif. (5)  <b>KGUS</b> Blythe, Calif. (8)  <b>KGUT</b> Robertson, Mo. (5)  <b>KGUZ</b> Ponca City, Okla. (1)  <b>KKO</b> Elko, Neva. (1)  <b>KMP</b> Omaha, Neb. (1)  <b>KMR</b> No. Platte, Nebr. (1)  <b>KNAS</b> Kansas City, Mo. (1)  <b>KNAT</b> Dallas, Tex. (1)  <b>KNAU</b> Tulsa, Okla. (1)  <b>KNAV</b> Okla. City, Okla. (1)  <b>KNWA</b> St. Paul, Minn. (6)  <b>KNWB</b> Fargo, N. D. (6)</p>	<p><b>KNWC</b> Pembina, N. D. (6)  <b>KOE</b> Cheyenne, Wyo. (1)  <b>WAEC</b> Pittsburgh, Pa. (2)  <b>WAED</b> Harrisburg, Pa. (2)  <b>WAEF</b> Camden, N. J. (2)  <b>WAEF</b> Newark, N. J. (2)  <b>WAEF</b> Cresson, Pa. (2)  <b>WAEH</b> Milwaukee, Wis. (6)  <b>WAEI</b> Detroit, Mich. (7)  <b>WAEJ</b> Springfield, Ill. (5)  <b>WAEK</b> Mobile, Ala. (4)  <b>WEEB</b> Baltimore, Md. (9)  <b>WEEC</b> Charleston, S. C. (9)  <b>WEEF</b> Spartanburg, S. C. (9)  <b>WEEG</b> Greensboro, N. C. (9)  <b>WEEH</b> McRae, Ga. (9)  <b>WEEJ</b> Jacksonville, Fla. (9)  <b>WEEM</b> Miami, Fla. (9)  <b>WEEN</b> Linden, N. J. (9)  <b>WEEQ</b> Orlando, Fla. (9)  <b>WEEQ</b> Atlantic City, N. J. (9)  <b>WEER</b> Richmond, Va. (9)  <b>WHG</b> Columbus, Ohio (2)  <b>WHM</b> Indianapolis, Ind. (2)  <b>WKDL</b> Miami, Fla. (10)</p>	<p><b>WMDV</b> San Juan, P. R. (10)  <b>WNAO</b> Newark, N. J. (1)  <b>WNAK</b> Cleveland, Ohio (1)  <b>WNAL</b> Brookville, Pa. (1)  <b>WNAM</b> Bellefont, Pa. (1)  <b>WNAT</b> Orlando Twntshp., Ill. (1)  <b>WNAU</b> Moline, Ill. (1)  <b>WQDQ</b> New Orleans, La. (5)  <b>WQPD</b> Atlanta, Ga. (5)  <b>WSDC</b> Newark, N. J. (4)  <b>WSDD</b> Boston, Mass. (4)  <b>WSD E</b> Birmingham, Ala. (4)  <b>WSD F</b> Louisville, Ky. (5)  <b>WSDG</b> Chicago, Ill. (5)  <b>WSDK</b> Memphis, Tenn. (5)  <b>WSDL</b> Duluth, Minn. (6)  <b>WSDM</b> Albany, N. Y. (5)  <b>WSDO</b> Buffalo, N. Y. (8)  <b>WSDP</b> Columbus, Ohio (5)  <b>WSDQ</b> Berea, Ohio (5)  <b>WSDS</b> Chicago, Ill. (6)  <b>WSDT</b> Nashville, Tenn. (5)  <b>WSDZ</b> Indianapolis, Ind. (5)  <b>WSID</b> Cincinnati, Ohio (5)  <b>WUCG</b> Chicago, Ill. (1)</p>
---	---	--	---

## TELEVISION STATIONS

Television transmission at the present time is highly experimental in nature, and for this reason it is difficult to give operating hours, scanning speeds, lines per second, etc., with any degree of accuracy.

<p style="text-align: center;"><b>According to frequency and wavelength</b></p> <hr/> <p>1600-1700 kc.      176.5-187.5 m.</p> <p style="text-align: center;">Dial:</p> <p><b>W2XR</b>—Radio Pictures, Inc. Long Island City, N. Y. 1000 watts. 60 lines</p> <hr/> <p><b>W1XAV</b>—Short Wave &amp; Television Co. Boston, Mass. 1000 watts. 60 lines</p> <hr/> <p><b>W8XN</b>—Sparks-Withington Co. Jackson, Mich.</p> <hr/> <p>200-2100 kc.      142.9-150 m.</p> <p style="text-align: center;">Dial:</p> <p><b>W9XAO</b>—Western Television Corp. Chicago, Ill. 500 watts. 45 lines</p> <hr/> <p><b>W6XAH</b>—Pioneer Mercantile Co. Bakersfield, Cal. 1000 watts. 60 lines</p> <hr/> <p><b>W9XK</b>—Iowa State University Iowa City, Iowa 100 watts. 60 lines</p>	<p><b>W8XF</b>—Goodwill Station Pontiac, Mich. 1000 watts</p> <hr/> <p>2100-2200 kc.      136.4-142.9 m.</p> <p style="text-align: center;">Dial:</p> <p><b>W3XAK</b>—National Broadcasting Co. 5000 watts. Portable</p> <hr/> <p><b>W2XBS</b>—National Broadcasting Co. New York, N. Y. 5000 watts</p> <hr/> <p><b>W6XS</b>—Don Lee Broadcasting Corp. Gardena, Calif. 1000 watts</p> <hr/> <p><b>W9XAP</b>—National Broadcasting Co. Chicago, Ill. 2,500 watts</p> <hr/> <p><b>W9XAK</b>—Kansas State College, Manhattan, Kans. 125 watts</p> <hr/> <p>2200-2300 kc.      130.4-1364 m.</p> <p style="text-align: center;">Dial:</p> <p><b>W9XAL</b>—First National Television Corp. Kansas City, Mo.</p> <hr/> <p>2750-2850 kc.      105.3-109.1 m.</p> <p style="text-align: center;">Dial:</p> <p><b>W9XG</b>—Purdue University W. Lafayette, Ind. 1500 watts. 60 lines</p>	<p><b>W2XAB</b>—Atlantic Broadcasting Corp. New York, N. Y. 500 watts</p> <hr/> <p>43,000-46,000 kc.      6.52-6.98 m.  48,500-50,300 kc.      6.00-6.20 m.  60,000-80,000 kc.      3.75-5.00 m.</p> <p style="text-align: center;">Dial:</p> <p><b>W9XD</b>—The Journal Co. Milwaukee, Wis. 500 watts</p> <hr/> <p><b>W9XE</b>—U. S. Radio &amp; Tele. Corp. Marion, Ind. 1000 watts</p> <hr/> <p><b>W8XF</b>—Goodwill Station, Pontiac, Mich.</p> <hr/> <p><b>W3XAD</b>—RCA-Victor Co., Camden, N. J. 2000 watts</p> <hr/> <p><b>W2XBT</b>—National Broadcasting Co. Portable 750 watts</p> <hr/> <p><b>W1XG</b>—Short Wave &amp; Television Co. Boston, Mass. 200 watts</p> <hr/> <p><b>W2XR</b>—Radio Pictures, Inc. Long Island City, N. Y. 1000 watts</p>	<p><b>W2XF</b>—National Broadcasting Co. New York, N. Y. 5000 watts</p> <hr/> <p><b>W6XAO</b>—Don Lee Broadcasting System Los Angeles, Calif. 150 watts</p> <hr/> <p><b>W3XE</b>—Philadelphia Storage Battery Co. Philadelphia, Pa. 1500 watts</p> <hr/> <p><b>W2XAK</b>—Atlantic Broadcasting Corp., New York, N. Y. 50 watts</p> <hr/> <p><b>W10XX</b>—RCA-Victor Co., Portable and Mobile. 50 watts</p> <hr/> <p><b>W8XAN</b>—Sparks-Withington Co., Jackson, Mich. 100 watts</p> <hr/> <p><b>W8XL</b>—WGAR Broad-casting Co., Cuyahoga Hts., Ohio. 200 watts</p>
--	--	---	--

# POLICE RADIO ALARM STATIONS

By Frequency and Wavelength

## 2506 kc.-120 m.

Dial:

KGZE San Antonio, Tex.

## 2470 kc.-121.5 m.

Dial:

KGOZ Cedar Rapids, Ia.  
 KGPV Davenport, Ia.  
 WPDZ Fort Wayne, Ind.  
 WPDY Kokomo, Ind.  
 WPEC Memphis, Tenn.  
 KGPI Omaha, Neb.  
 WPDY Philadelphia, Pa.  
 KGPV San Francisco, Cal.  
 KGPV San Jose, Cal.  
 KGPW Salt Lake City, U.  
 WRDQ Toledo, Ohio  
 WPFJ Gary, Ind.  
 WPFJ Swathmore, Pa.  
 WPFJ Knoxville, Tenn.  
 WPFJ Johnson City, Tenn.

## 2458 kc.-122.0 m.

Dial:

WPDO Akron, Ohio  
 WPDV Auburn, N. Y.  
 WPDV Charlotte, N. C.  
 WRDH Cleveland, Ohio  
 WPDV Rochester, N. Y.  
 WPEA Syracuse, N. Y.  
 WPEA Asheville, N. C.

## 2450 kc.-122.4 m.

Dial:

WPDK Milwaukee, Wis.  
 WPEE New York, N. Y.  
 WPEF New York, N. Y.

WPEG New York, N. Y.  
 KGPH Okla. City, Okla.  
 KGPO Tulsa, Okla.  
 KGPZ Wichita, Kans.  
 KGZF Chanute, Kans.  
 KGZP Coffeyville, Kans.  
 KGPQ Honolulu, T. H.

## 2442 kc.-122.8 m.

Dial:

KGPX Denver, Col.  
 WPDF Flint, Mich.  
 WPEB Grd. Rapids, Mich.  
 WMDZ Indianapolis, Ind.  
 WPDY Lansing, Mich.  
 WPEE Louisville, Ky.  
 KGPV Portland, Ore.  
 WPDH Richmond, Ind.  
 KGZH Klamath Falls, Ore.  
 WPFJ Muskegon, Mich.  
 WPFJ Reading, Pa.  
 KGZR Salem, Ore.

## 2430 kc.-123.4 m.

Dial:

WPDY Columbus, Ohio  
 KGPV Portland, Ore.  
 WPDY Dayton, Ohio  
 KGZD San Diego, Cal.  
 WPFJ Highland Park, Ill.  
 WPFJ Toms River, N. J.  
 WPFK Hackensack, N. J.

## 2422 kc.-123.8 m.

Dial:

WMJ Buffalo, N. Y.  
 KGPE Kansas City, Mo.

KGPG Vallejo, Cal.  
 WPEK New Orleans, La.  
 WPDW Washington, D. C.  
 WPFJ Jacksonville, Fla.

## 2416 kc.-124.1 m.

Dial:

KGPV Minneapolis, Minn.  
 WPDY St. Paul, Minn.

## 2414 kc.-124.2 m.

Dial:

WPDY Atlanta, Ga.  
 KGPS Bakersfield, Cal.  
 WCK Belle Island, Mich.  
 WPDY Detroit, Mich.  
 WRDR Grosse Pt. Vil. Mich.  
 WMO Highland Pk., Mich.  
 KGPA Seattle, Wash.  
 WPDY Tulare, Cal.  
 KGZM El Paso, Tex.  
 WPFH Baltimore, Md.  
 KGZM Tacoma, Wash.  
 WPFJ Columbus, Ga.  
 WPFM Birmingham, Ala.  
 WPFJ Clarksburg, W. Va.  
 WPFJ Santa Barbara, Cal.  
 WPFJ Mount Pleasant, N. Y.

## 1712 kc.-175.15 m.

Dial:

KGPJ Beaumont, Tex.  
 KSW Berkeley, Cal.  
 WPDY Chicago, Ill.  
 WPDY Chicago, Ill.  
 WPDY Chicago, Ill.  
 WKDU Cincinnati, Ohio

KVP Dallas, Tex.  
 KGPL Los Angeles, Cal.  
 KGJX Pasadena, Cal.  
 WPDY Pittsburgh, Pa.  
 KGPC St. Louis, Mo.  
 KGZI Wichita Falls, Tex.  
 WPFJ Newton, Mass.  
 KGZL Shreveport, La.  
 WPEH Somerville, Mass.  
 WPEP Arlington, Mass.  
 KGZB Houston, Tex.  
 WPFJ Hammond, Ind.  
 WPFN Fairhaven, Mass.  
 KGZQ Waco, Tex.  
 WPET Lexington, Mass.  
 WPEI E. Providence, R. I.  
 WPFJ Portland, Me.

## 1574 kc.-189.5 m.

Dial:

WRDS E. Lansing, Mich.  
 WMP Fram'gham, Mass.  
 WPEW North'pton, Mass.  
 KGPY Shreveport, La.  
 WPEL W. B'dgew'r, Mass.  
 WPEV Portable, Mass.

## 1534 kc.-196.1 m.

Dial:

KGHO Des Moines, Ia.

## 257 kc.-1123 m.

Dial:


WBR Butler, Pa.  
 WJL Greensburg, Pa.  
 WBA Harrisburg, Pa.  
 WMB W. Reading, Pa.  
 WDX Wyoming, Pa.

## Alphabetically By Call Letters

KGHO Des Moines, Iowa	1534 kc.	KSW Berkeley, Cal.	1712 kc.	WPDZ Fort Wayne, Ind.	2470 kc.
KGJX Pasadena, Cal.	1712 kc.	KVP Dallas, Tex.	1712 kc.	WPEA Syracuse, N. Y.	2458 kc.
KGOZ Cedar Rapids, Iowa	2470 kc.	WBA Harrisburg, Pa.	257 kc.	WPEB Grand Rapids, Mich.	2442 kc.
KGPA Seattle, Wash.	2414 kc.	WBR Butler, Pa.	257 kc.	WPEC Memphis, Tenn.	2470 kc.
KGPB Minneapolis, Minn.	2416 kc.	WCK Belle Island, Mich.	2414 kc.	WPEE New York, N. Y.	2450 kc.
KGPC St. Louis, Mo.	1712 kc.	WDX Wyoming, Pa.	257 kc.	WPEF New York, N. Y.	2450 kc.
KCPD San Francisco, Cal.	2470 kc.	WJL Greensburg, Pa.	257 kc.	WPEG New York, N. Y.	2450 kc.
KGPE Kansas City, Mo.	2422 kc.	WKDU Cincinnati, Ohio	1712 kc.	WPEH Somerville, Mass.	1712 kc.
KGPG Vallejo, Cal.	2422 kc.	WMB W. Reading, Pa.	257 kc.	WPEI E. Providence, R. I.	1712 kc.
KGPH Oklahoma City, Okla.	2450 kc.	WMDZ Indianapolis, Ind.	2442 kc.	WPEK New Orleans, La.	2422 kc.
KGPI Omaha, Neb.	2470 kc.	WMJ Buffalo, N. Y.	2422 kc.	WPEL W. Bridgewater, Mass.	1574 kc.
KGPI Beaumont, Tex.	1712 kc.	WMO Highland Park, Mich.	2414 kc.	WPEP Arlington, Mass.	1712 kc.
KGPL Los Angeles, Cal.	1712 kc.	WMP Framingham, Mass.	1574 kc.	WPET Lexington, Mass.	1712 kc.
KGPM San Jose, Cal.	2470 kc.	WPDY Tulare, Cal.	2414 kc.	WPEV Portable, Mass.	1574 kc.
KGPN Davenport, Iowa	2470 kc.	WPDY Chicago, Ill.	1712 kc.	WPFJ Reading, Pa.	2442 kc.
KGPO Tulsa, Okla.	2450 kc.	WPDY Chicago, Ill.	1712 kc.	WPFJ Columbus, Ga.	2414 kc.
KGPP Portland, Ore.	2442 kc.	WPDY Chicago, Ill.	1712 kc.	WPFJ Hammond, Ind.	1712 kc.
KGPP Honolulu, T. H.	2450 kc.	WPEE Louisville, Ky.	2442 kc.	WPFJ Hackensack, N. J.	2430 kc.
KGPS Bakersfield, Cal.	2414 kc.	WPDF Flint, Mich.	2442 kc.	WPFJ Gary, Ind.	2470 kc.
KGPW Salt Lake City, Utah	2470 kc.	WPDH Richmond, Ind.	2442 kc.	WPFM Birmingham, Ala.	2414 kc.
KGPX Denver, Colo.	2442 kc.	WPDY Columbus, Ohio	2430 kc.	WPFN Fairhaven, Mass.	1712 kc.
KGZB Houston, Tex.	1712 kc.	WPDK Milwaukee, Wis.	2450 kc.	WPFJ Knoxville, Tenn.	2470 kc.
KGZD San Diego, Cal.	2430 kc.	WPDY Lansing, Mich.	2442 kc.	WPFJ Clarksburgh, W. Va.	2414 kc.
KGZE San Antonio, Tex.	2506 kc.	WPDY Dayton, Ohio	2430 kc.	WPFJ Johnson City, Tenn.	2470 kc.
KGZF Chanute, Kans.	2450 kc.	WPDY Auburn, N. Y.	2458 kc.	WRDH Cleveland, Ohio	2458 kc.
KGZH Klamath Falls, Ore.	2442 kc.	WPDY Akron, Ohio	2458 kc.	WRDR Grosse Pt. Village, Mich.	2414 kc.
KGZI Wichita Falls, Tex.	1712 kc.	WPDY Philadelphia, Pa.	2470 kc.	WRDQ Toledo, Ohio	2470 kc.
KGZL Shreveport, La.	1712 kc.	WPDY Rochester, N. Y.	2458 kc.		
KGZM El Paso, Tex.	2414 kc.	WPDY St. Paul, Minn.	2416 kc.		
KGZN Tacoma, Wash.	2414 kc.	WPDY Kokomo, Ind.	2470 kc.		
KGZP Coffeyville, Kans.	2450 kc.	WPDY Pittsburgh, Pa.	1712 kc.		
KGZQ Waco, Tex.	1712 kc.	WPDY Charlotte, N. C.	2458 kc.		
KGZR Salem, Ore.	2442 kc.	WPDY Washington, D. C.	2422 kc.		
		WPDY Detroit, Mich.	2414 kc.		
		WPDY Atlanta, Ga.	2414 kc.		

**ELIMINATING "FRINGE HOWL"**

\$5.00 Prize Winner.

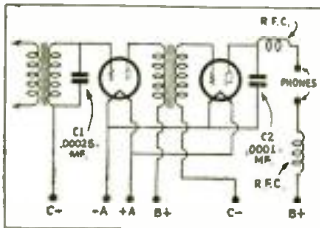


Many receivers are cursed with a condition known as "fringe howl." That is one reason why S-W receivers are so often placed on the "shelf" by disgusted fans. This condition may be eliminated entirely by the proper circuit arrangements. Many fans shunt the secondary of the first A.F. transformer by means of a resistor; but there is a better solution.

The first A.F. transformer is shunted by a .00025 mf. by-pass condenser, indicated in the diagram as C1. In some cases it might have to be increased, but it should be kept as small as possible, since a large capacitance will decrease the volume. C2, which is shunted from the plate of the last tube to the filament, has a value of .0001 mf. This capacity should not exceed this value, since an increase in capacitance would tend to cut off the higher notes of the musical scale.

The radio frequency chokes prevent body capacity troubles in the phone cord. If they are not employed, touching the phone cord will detune the set or knock it out of oscillation. When by-passed in this way the set is entirely freed from "fringe howl," and very stable regeneration is obtained.—Fred H. Williams.

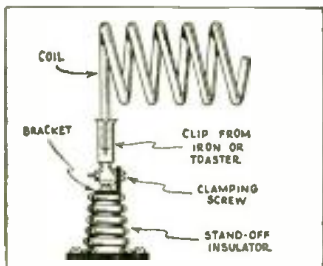**PLUG-IN TRANSMITTER COILS**


From the junk-box several contact clips such as used in the plug connection on irons, toasters, etc., were obtained. These clips are the ones that are used to fit over the male contact pins, and normally



have an opening of about one-eighth inch. If you haven't them, any electric dealer can supply them at very low cost. These were mounted on small stand-off insulators as shown in the figure. By bending a short length of the inductance perpendicular to its axis, the arrangement was completed. The coils in my case are of one-eighth inch copper tubing, but by spreading the clips slightly, larger sizes may be accommodated. Contact surfaces on both the coils and the clips should be kept clean and bright, of course. Any good metal polish or burnishing paste will take care of this.—Frederick Grimwood, (Station WPTW).

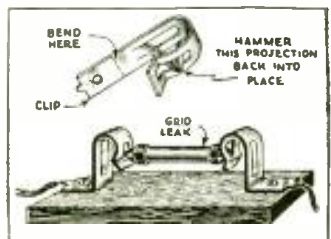**GRID-LEAK CLIPS**


The accompanying illustration shows how to improve very effective grid-leak spring clips. To make this grid-leak shunt one needs two Fabronite spring clips. Next, the center tongue on each spring clip is hammered back into place, so as to leave no obstruction under the curved springy part of the clip. Next, the ends of the clips are bent at right angles, as shown, by means of a pair of pliers or a vise and they are mounted with the two curved members facing towards each other. The distance between the two clips will depend on the size of the grid-leak cartridge to be accommodated.—Paul Kornke, Jr.



**\$5.00 For Best Short Wave Kink**

The Editor will award a five dollar prize each month for the best short-wave kink submitted by our readers. All other kinks accepted and published will be paid for at regular space rates. Look over these "kinks" and they will give you some idea of what the editors are looking for. Send a typewritten or ink description, with sketch, of your favorite short-wave kink to the "Kink" Editor, SHORT WAVE CRAFT.


**TAPPED-COIL SWITCH**

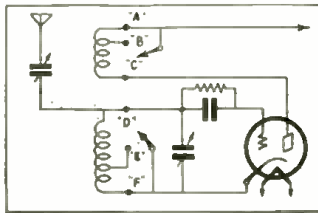

This coil switch layout is very convenient for the fan or "ham" who works two bands; for instance, 20 meters before nightfall and 40 meters after dark. It is bothersome to change plug-in coils every time you change from one band to another. The coil can be wound on six-prong forms and used with six-prong sockets. Likewise many sets of coils can be made; for instance 160 meter amateur band and the 80 meter amateur band, 49 meter and 30 meter relay stations, etc.

From "D" to "E" are the number of turns required for the lowest (in wavelength) band on the grid coil. Then from "E" to "F" is the difference between the higher and lower band's number of turns. Likewise on the tickler from "C" to "D" is the tickler number of the lowest band and from "D" to "A" is the difference between the tickler on the lowest band and the tickler on the highest band. For instance, if 40 turns on the secondary respectively tune the 80 meter band. From "D" to "E" equals 30t., from "E" to "F" equals 10t., from "C" to "B" equals 10t., and from "B" to "A" equals five turns. Toggle switches may be used.—R. C. Amundsen.

**CHOKE COIL MOUNTING**

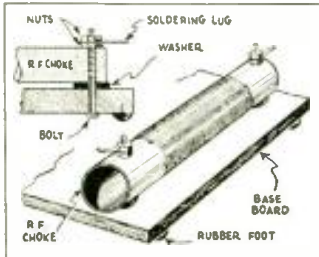


After laboriously winding 300 turns of No. 36 D.S.C. wire on a 1/2" dowel, the next job is to mount it. Here is a simple and efficient method. Drill two holes through the baseboard which coincide with two holes that are drilled through the choke near its ends. Separate the choke from the baseboard by means of a washer. Fasten the assembly thus far with a nut. Then insert a soldering lug which is held in place by another nut. (A lock washer may also be inserted if desired.) The same assembly is mounted on the other side of the choke. The soldering lug provides a terminal for the end of the choke. This makes an easy compact mounting for the choke; it can be mounted in the same manner on the under-side of a subpanel. The diagram makes the assembly clear.—Theodore Ulmer, W8HMO, W8HMR.

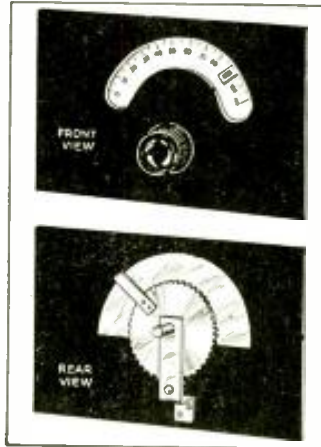**NEW DIALS FOR OLD**


This dial is easily constructed from material found in most workshops, and when finished presents a very neat appearance. Select an old type dial that is not too badly scratched and with a hack-saw remove the original knob and cut the dial in two a little below the center. Then from an old alarm clock remove a large gear, preferably the one connected to the main spring, and also a small pinion, that will mesh with the large wheel teeth; a suitable indicator needle should be secured to the large wheel, and bent so that it will follow the dial figures. A mounting

bracket for the wheel and pinion can be made from a piece of iron sufficiently heavy to prevent bending under ordinary operating conditions. After selecting the position for the dial on the panel cut a semi-circular aperture the same diameter as the dial, mount the dial to center with the aperture and secure with machine screws. A suitable knob is then mounted on the end of the pinion shaft, and the dial is ready for use. If desired a pilot lamp may be mounted above the dial so that the light will strike the figures.—Lincoln A. Williams.



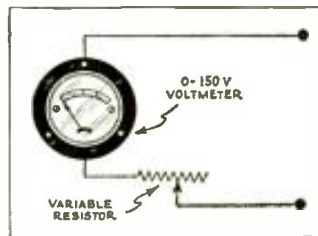**EXTENDING METER'S RANGE**


Here is a simple scheme I use to temporarily extend the range of a voltmeter. I had a voltmeter with a 150 volt scale and desired to read voltages in excess of 150 volts. The voltage from some stable source of potential, such as B batteries is read with the voltmeter, let us say it amounts to 94 volts. A variable resistor whose range will include a resistance equal to the meter's resistance is placed in series with the meter as shown in the



sketch. This combination is again placed across the B batteries and the resistance of the resistor varied until the meter reads half of what it did before, or 47 divisions on the scale. The combination may then be used to measure unknown voltages and the meter is calibrated to read 0 to 300 volts. By adjusting the resistor till the meter reads 1/2 or 1/4 of its normal deflection its range can be increased 3 times or 4 times instead of doubled. This scheme can of course be used on any range voltmeter.—Lawrence W. Hale.

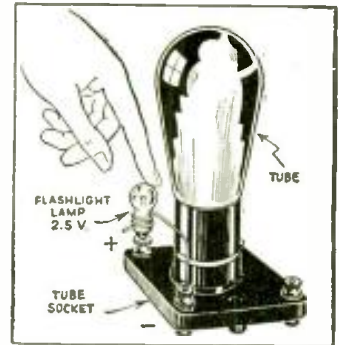
**TUBE PROTECTOR**

After "blowing out" several costly tubes, I devised a scheme that has saved me much grief and dollars too. Here 'tis: I procured a 10c flashlight bulb removed the radio tubes from the sockets, mounted it as in sketch. Turn on rheostat; if bulb burns "O.K." then it is safe to plug-in the tubes. The bulb should have




The same voltage rating as the tube or tubes used.—Clinton Parker.

**AMMETER SWITCH**

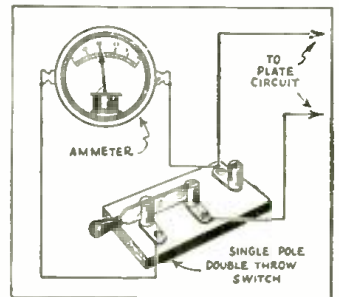


Here's how to lengthen the life of the transmitter plate ammeter. When keying, the ammeter has to swing at a tremendous speed and there are continuous surges of current through it. By putting in a single-pole, double-throw switch, as illustrated I can switch the meter in or out as desired. For adjustment, I switch the meter in; then I cut it out when I am ready to send; thereby adding a great deal to the life of the ammeter.—Geo. J. Crossland, W6SRW.

**TRANSPOSITION INSULATORS**

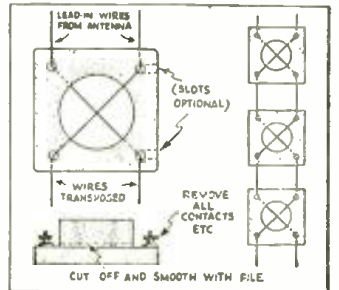

The spreaders for a transposed lead-in for S. W. aerials can be made out of old bakelite sockets found in your old "junk box." First remove all the nuts, bolts and contact points from the socket. Then saw off the top part, leaving a square with four holes for the wire.—J. Vlcek.

**TIGHTENING LOOSE COILS**

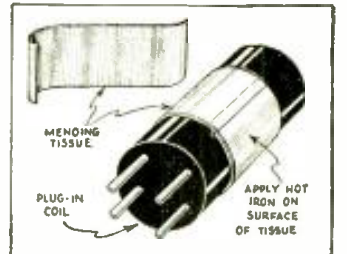

Many fans make it a practice of winding their own coils. Sometimes when the wire is wound and soldered in the prongs, the wire works loose and makes the whole coil a failure. Here is a kink that will solve the trouble. Procure mending tissue that can be bought at any store and wind around the coil. Then apply a warm iron on the surface of the tissue. This will make it a neat and lasting job.—Alfonso Slemianowski.

# SHORT WAVE LEAGUE



## HONORARY MEMBERS

Dr. Lee de Forest  
 John L. Reinartz  
 D. E. Replogle  
 Hollis Baird  
 E. T. Somerset  
 Baron Manfred von Ardenne  
 Hugo Gernsback  
*Executive Secretary*

# New Amateur Regulations

NEW governmental regulations governing the "hams" and formulated with their approval will go into effect on October 1, affecting about 40,000 amateur transmitting stations. The new rules largely concern routine and technical operation, but one of the most important, which went into effect on June 23, widens the channels set aside for *amateur radiophone* use. These channels now embrace 1,800-2,000 kilocycles, 28,000 to 28,500 kilocycles, and 400,000 to 401,000 kilocycles.

### Summary of Regulations

The October regulations may be summarized as follows:

1. Combined operator-station licenses are to be issued hereafter to individual "hams" instead of requiring two separate licenses. The licenses will stipulate three classes of privileges: (a) unlimited, (b) unlimited radio telegraph but limited radio telephone, and (c) same as Class B, but with special examinations and practical code tests required on demand.

2. Applicants residing more than 125 miles from Washington or from any one of the twenty district offices of the Radio Commission are to be examined by mail hereafter, and their papers will be graded in Washington. In addition to the district inspection offices, Federal inspectors will visit the following cities quarterly for personal examinations: St. Louis, Pittsburgh, Nashville, Oklahoma City, San Antonio, Columbus, Des Moines, Cincinnati, Cleveland, Schenectady and Winston-Salem, S. C. Applicants residing within 125 miles of Washington, a district office or an examining city will be given a personal supervisory examination.

3. Amateur portable stations will not be licensed as such, but portables may be operated away from specified locations with the usual call letters on condition advance notice of all locations is filed with the district inspector. Amateur mobile stations will not be permitted, except aboard aircraft and capable of operating in the 56,000-60,000 and 400,000-401,000 kilocycle bands.

4. Station licenses will be issued only to licensed amateur operators who have made satisfactory showing of ownership or control of proper transmitting apparatus. Rigid technical efficiency must be maintained as specified by the commission, including pure Type A-1, or continuous wave transmission in radio telegraphing below 14,400 kilocycles.

5. Corporations, associations or organizations cannot secure amateur sta-

THE new amateur regulations recently promulgated by the Federal Radio Commission are given herewith in full, because they are of the utmost importance to every "ham" or would-be ham. We advise all LEAGUE members to cut them out and to paste them inside their "log" books or in some other reliable place where they will not be lost.

tions, though bona fide amateur societies can secure them through a licensed "ham" acting as trustee. This is in keeping with the plan never to commercialize amateur radio or permit commercial interests to encroach on the "ham" wave lengths.

For the most part, the changes were made to expedite the handling of amateur radio matters within the commission, which has suffered a severe budget cut and accordingly has reduced its field force considerably. They are also designed to increase the efficiency of "hamdom" and thus somewhat relieve the congestion existing on the amateur waves due to the growing number of "hams."

If rule number 4 doesn't sound clear, we will elucidate. It means simply that raw A.C. for plate supply is OUT, and that respectable D.C. must be employed to insure the "pure Type

A-1 transmission" specified. Intentional tone modulation becomes a serious offense. CLEAN, WHISTLE-LIKE NOTES ARE NOW THE ORDER OF THE DAY.

Just why mobile amateur stations will be permitted in airplanes and not in other types of vehicles is something of a mystery. As one of our readers aptly puts it, not one ham in ten thousand owns an airplane, but plenty of them have motorboats, in which short-wave transmitters really would be valuable from the standpoint of safety of life.

## Readers' Opinions A Good Idea!

Editor, SHORT WAVE CRAFT:

I find it hard to understand why some "hams" seemingly satisfied to pound brass and fill the air with their own ear splitting code, should object to the LEAGUE'S proposal of putting a new class of experimenters in the five meter band, experimenters with new ideas, experimenters more eager for research and control of experiment than for futile babbling over the air. These objectors should have more of the fellowship, tolerance, patient disinterestedness of the "old-timers" who have obtained for them the privileges they now enjoy.

We need more research on *modulation*, and I foresee, that in the near future, through the use of the new cathodic jet relay (see SHORT WAVE CRAFT page 606 Feb., 1933), we will have a carrier wave phone modulation "chopped" to audio frequencies as neatly as it is done in code signalling. Great distance and clearness should be obtained. Quit the squabbling and bucking, you hams and get going on this

Yours sincerely,  
 Arthur J. Pelletier,  
 34 Hancock Street,  
 Boston, Mass.

## Favors "Code-less" Phone License

Editor, SHORT WAVE CRAFT:

I am in favor of code-less phone licenses on 5 meters. I have learned my code but on account of sickness I haven't been financially able to purchase a set of batteries for my "two-lunger," and at the present time don't just know when I will be able to purchase any more batteries.

I will not promise to answer all letters I receive, but will appreciate any and all letters received from anyone who wishes to write. If three cents is

(Continued on page 306)

## Get Your Button!

The illustration herewith shows the beautiful design of the "Official" Short Wave League button, which is available to everyone who becomes a member of the Short Wave League.

The requirements for joining the League are explained in a booklet, copies of which will be mailed upon request. The button measures 3/4 inch in diameter and is inlaid in enamel—3 colors—red, white, and blue.

Please note that you can order your button AT ONCE—SHORT WAVE LEAGUE supplies it at cost, the price, including the mailing, being 35 cents. A solid gold button is furnished for \$2.00 prepaid. Address all communications to SHORT WAVE LEAGUE, 96-98 Park Place, New York.







# Making An AUTOMATIC KEY

● MANY an amateur operator has heard the familiar rhythm of an automatic key on the air and remarked at the snappy operating that such a key affords. However, all amateurs cannot afford the ten to twenty dollars necessary to purchase one of these convenient instruments. But one can be put together for practically nothing plus a little patience and skill.

The key to be described cost nothing. Every piece of hardware and hard rubber was in the junk-box, where for several years all sorts of hardware had been placed for future use. Prac-

Right: side view and details of the parts used in building the automatic "speed" key.

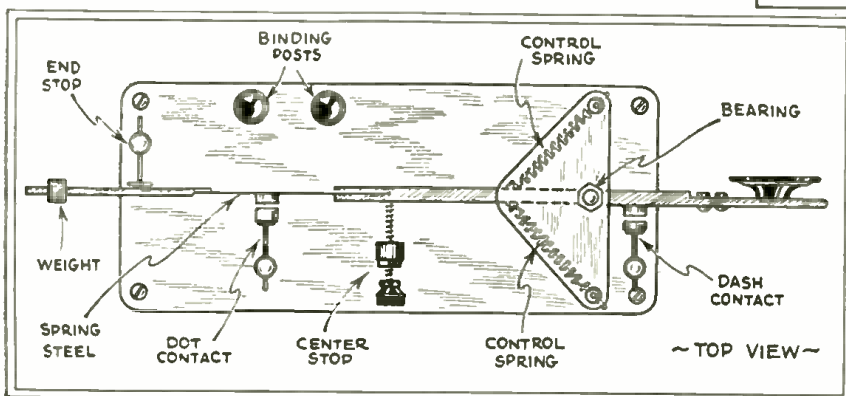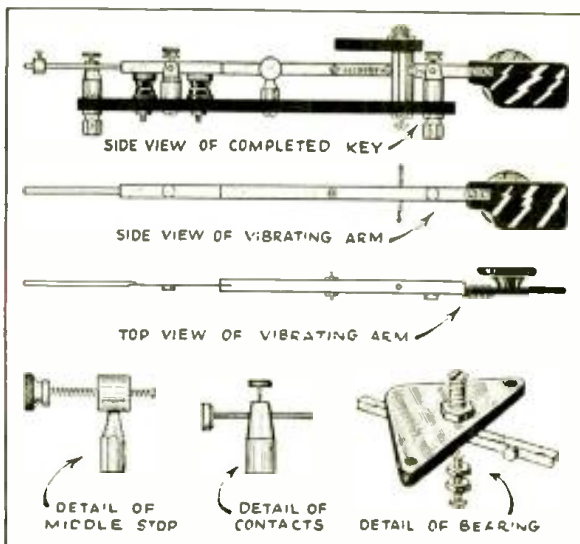Below: top view of the assembled automatic "speed" key here described. You can make dots and dashes like a "streak of lightning" with it.



1 1/4 inches from the handle end of the rod (the contacts, 4 of them, are sawed from brass rod the same size as the arm). One inch farther on a hole is drilled for the pivot. This pivot is a one-eighth inch bolt filed to a point at both ends after the head has been sawed off and is seven-eighths of an inch long. It is soldered to the arm. One inch from the pivot a hole is drilled to accommodate a very small bolt which fastens the control springs to the arm. At the end of the rod (opposite the handle end) a small slit is sawed lengthwise for 1/4 of an inch. The piece of spring steel (out of an old clock and bent straight) is soldered into this slit. At the other end of the spring steel, the two-inch piece of brass rod is soldered. This rod came from an old bakelite-end condenser. A brass dot contact is soldered in the middle of the spring steel and on the same side as the dash contact. This completes the vibrating arm.

### Laying Out the Base

The base is then laid out. At each corner is placed a mounting foot. These happened to be half-inch hexagonal binding-post nuts. Holes are then drilled in the base for the two stops, the two pillar posts, the two binding-

(Continued on page 316)

tically all amateurs have such a collection of odds and ends so that there should be no trouble in obtaining the parts. Besides, size and dimensions can be altered as well as materials without impairing the operation of the key. However, as this key was the result of experimentation, it will be described specifically. The parts are:

- 1 brass rod, round or square, 5 inches long, 1/4 inch thick
- 1 hard rubber base, 7 x 3 ins.
- 2 pieces of hard rubber, 3 x 3 in. and 2 x 1 in.
- 2 binding posts (Eby)
- 4 mounting feet


- 1 old condenser bearing (end)
- 1 spring, 3/8 inch dia. and about 2 in. long
- 2 pillar posts, one inch high
- 1 strip of flat steel spring, 3/4 in. wide, 2 1/4 in. long
- 1 brass rod 2 in. long, 3/8 in. dia.
- Miscellaneous bushings, bolts, nuts, solder, nails, etc.

### Making the Vibrating Arm

The first step is to construct the vibrating arm. Take the quarter-inch brass rod and attach the handle to it by two small nuts and bolts. Next solder the dash contact to the arm
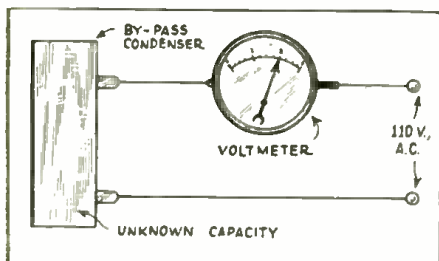
## Measuring Condenser Capacities

● THE drawing herewith shows how I connected a low-resistance battery-type voltmeter, having a ten volt scale, in series with an A.C. circuit and a condenser; it would be the safest to connect a 110 volt lamp in series with the meter. With the particular meter I used, the needle gave a deflection of



With a suitable meter connected in series with a source of A.C. and a condenser, proportional scale readings are obtained with various capacities.

## Automatic Regeneration Control

about one volt for every microfarad of condenser capacity. If the meter has a high resistance it will be necessary to try it on a condenser of known capacity and then compute the percentage of difference.—Clark Waage.

● THE desirability of a detector with self regeneration control is, of course, evident. Here is a good way to accomplish this most desirable feature. The circuit at right is that of a dynatron similar to one used very successfully by me some seven months ago. The regeneration scheme is, however, new. One condenser, C2, increases the regeneration as the frequency increases; the other, C3 decreases it at the same time. Thus, if the condensers are properly adjusted, these two effects neutralize each other and regeneration is ever constant. No power supply is shown, as that is not important and none that could be shown would please even a majority of the readers.


The constants are standard save for the following:

C2—140 mmf. equalizer.

C3—140 mmf. equalizer.

R1—50,000 ohms adjustable.

—Roger Geffen.

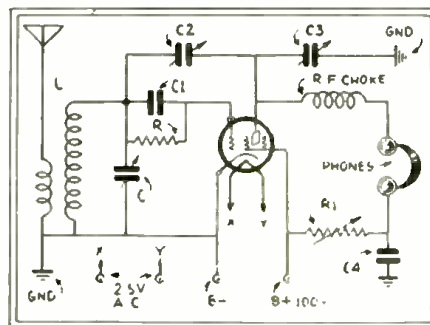

By means of this circuit an attempt is made to accomplish automatic regeneration control.

# SHORT WAVE QUESTION BOX

## LEAD-IN BLOCKS

F. G. Hall, Indianapolis, Ind.

(Q) I have quite a number of old bakelite panels on hand and would like to know if I could cut these up into square little blocks, for use as separators on a transposed wire lead-in.

(A) It is perfectly practical to use bakelite for this purpose. Of course, you have to be careful to cut the bakelite in such a manner that the wires will cross over properly without touching each other.

## WIRE FOR COILS

Paul Hogg, Shaker Heights, Ohio.

(Q) Before ordering some spools of magnet wire, I wish your advice in regard to the correct sizes for short-wave plug-in coils. I understand that the heavier the wire, the better the results. What is your advice?

(A) For all practical purposes No. 18 wire is quite heavy enough for use as the secondary winding on any short-wave coils. Wire as thin as No. 26 may also be used for the same purpose, without any appreciable difference in results. It is advantageous to use the heavier wire because it will hold better on the coil form.

For coils requiring more than 15 or 18 turns, No. 20 or 22 may be used. Primary and tickler coils in all cases need not be heavier than No. 24.

In the heavy size the wire may have enameled insulation, as the turns are separated. Coils that are close-wound should have double-cotton or double-silk insulation.

## SOUNDER OPERATION

M. L. P., Kansas City, Mo., asks.

(Q) I have been trying, rather unsuccessfully, to operate an ordinary telegraph relay in the plate circuit of the output tube of my short-wave receiver. Although the signals with earphones or loud speaker are unbearably loud, and I am positive the current is flowing through the relay windings, I cannot make the relay armature kick over enough to work a local circuit with a telegraph sounder in it. I am an old Morse wire man and get a great deal of fun out of listening to amateur and commercial stations, but would like to have the dots and dashes come in over the sounder. A diagram of my set is enclosed.

(A) The better your audio amplifier is, the less chance it has of working the relay-sounder combination you describe. The reason is simple. Your amplifier (consisting of two ordinary transformer coupled stages with 01A and 71A tubes) is of the regular class "A" variety, and the actual plate current remains at a fairly steady value, as indicated by a D.C. plate milliammeter, whether signals are being

● Because of the amount of work involved in the drawing of diagrams and the compilation of data, we are forced to charge 25c each for letters that are answered directly through the mail. This fee includes only hand-drawn schematic drawings. We cannot furnish "picture-layouts" or "full-sized" working drawings. Letters not accompanied by 25c will be answered in turn on this page. The 25c remittance may be made in the form of stamps or coin.

Special problems involving considerable research will be quoted upon request. We cannot offer opinions as to the relative merits of commercial instruments.

Correspondents are requested to write or print their names and addresses clearly. Hundreds of letters remain unanswered because of incomplete or illegible addresses.

received or not. In fact, movement of the milliammeter needle during signal reception indicates very definitely that the amplifier is distorting.

What you need for the operation of a telegraph relay or sounder is very sharp direct current pulses. The loud signals you hear in phones or loud speaker are due to the audio-frequency component of the plate current. The phones or speaker respond to them because the vibrating diaphragm is thin and light and can follow the rapid fluctuations. A telegraph relay is an enormously slower device, and will respond only to violent plate current changes.

Our suggestion is that you add a third stage of amplification, and that you adjust the grid bias, by means of a potentiometer, as shown in Fig. 1, until this stage acts more as a detector than as an amplifier and distorts voice or music so badly it is hardly recognizable. A sensitive relay should then respond properly to code signals.

## INSTALLING NEW TUBES

Arthur H., New York, asks,

(Q) I have an old three-tube short-wave receiver using type 01A tubes. This has always worked well, but recently two of the tubes went bad and I thought I might as well replace them by newer tubes. What do you recommend?

(A) This depends on your source of filament current. If you intend to use dry cells, your best bet is the type 30 tube, which draws only .06 ampere at two volts and is therefore very economical. If you have a six-volt storage battery, by all means use the type 37, which is one of the so-called automobile series. These are particularly desirable for short-wave work because of their complete freedom from "microphonics," which can sometimes be extremely annoying with tubes of the two-

volt series, unless resilient sockets are used.

The 30's will fit in the same sockets as the old 01A's; the 37's being of the heater-cathode variety, will require new five-prong sockets. The filament consumption of the 37 is .6 ampere at 6.3 volts, which is only a fraction of an ampere more than the drain of the 01A.

## SHORT-WAVE NETWORKS

Quite a number of people have inquired about diagrams of transmitters and receivers for special purposes, such as a calling system for cruising taxicabs, communication between the scattered forest camps of lumber firms, motorboat and yacht installations, etc.

(A) The main thing that all these people do not realize is that transmitting stations of any kind, power or location in the United States must be licensed by the Federal Radio Commission, and that the rules concerning various classes of service are very clear and specific. Furthermore, amateur licenses are not valid for commercial communication, except, of course, under emergency conditions. Amateur licenses are not issued to corporations or firms or to cover stations in motorboats. Any business organization contemplating the use of private radio stations should communicate directly with the Federal Radio Commission, Washington, D. C., before it spends a cent on equipment.

This information is given in SHORT WAVE CRAFT because we know for a fact that amateurs are always being approached by firms that want to avoid telephone and telegraph tolls between various cities. It is a good idea for both amateur and business man to know the situation.

## SIMPLEST POSSIBLE SET

R. G. Washburne, Bogota, N. J., asks.

(Q) Will you please publish a diagram of the very simplest possible short-wave receiver, using the absolute minimum of parts, and working, of course, on dry cells?

(A) The accompanying diagram, Fig. 2, is what you want. The set as shown uses one type 30 tube, which requires either two No. 4 or No. 6 dry cells in series for filament supply and one 22½-volt "B" battery for plate supply. The plug-in coils are wound on old tube bases. With a good pair of ear phones and a lot of patience, this set will actually bring in foreign broadcasting stations, and certainly hundreds of code stations. You should be able to build the thing in about one hour flat.

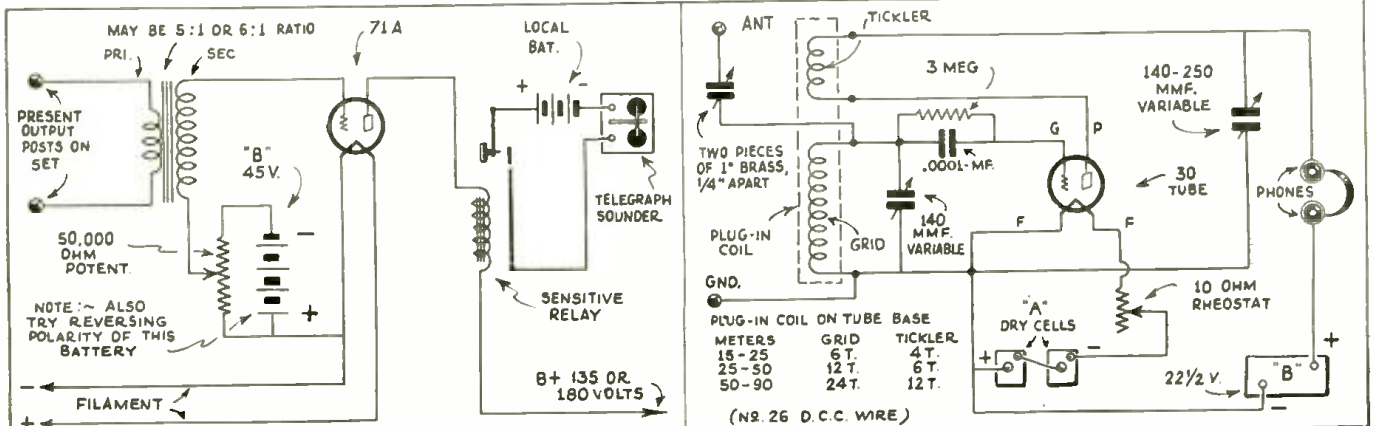


Diagram showing how to arrange special biasing adjustment in output audio stage to work a relay and telegraph sounder.

The "simplest" short-wave receiver circuit, using a vacuum tube, is presented in the above diagram.

## The "Acratone Discoverer"

(Continued from page 277)

al strip is mounted beneath the chassis  $\frac{3}{4}$ " from the under side, near the outlet hole provided for the 110-volt supply cable. The cable is firmly anchored to this strip. The dual electrolytic condenser C14, C15 is mounted next.

The long metal shield plate "C" is fastened to the top of the chassis as indicated and the two smaller shield strips are then fastened at right angles to this and to the chassis.

Fixed resistor R4 is soldered to the terminals of mica condenser C7 and the latter is then fastened to the side of shield plate "A" as shown. The R.F. choke L3 is fastened underneath the chassis using a  $2\frac{1}{4}$ " bolt which also serves to fasten the socket V2. All other parts are soldered in position during wiring.

### Wiring Details

Flexible hookup wiring is recommended. The usual order of procedure should be followed. Filament circuit first, then grid circuit, plates, cathodes, by-pass condensers and negative returns, filter system and power supply. Special care should be taken to make connections to socket terminals exactly as shown in the sketches.

Do not depend on the chassis as a return circuit for the tuning circuit. Run wires to all points in the high frequency circuit. This is necessary if maximum results are to be obtained.

In wiring to the tube sockets, study the diagrams of sockets carefully, before starting the wiring. Note that the control grid connections are made to the caps of tubes V1 and V2.

### Operating the Set

The "Discoverer" uses a simple tuned R.F. circuit where the only required adjustment is that of the trimmer condenser on C1. This adjusting condenser is designated on the diagrams as C16. After all the wiring and preliminary testing have been accomplished, the set should be fastened in the metal cabinet furnished with the kit. The antenna and ground should then be connected and the tubes and coils inserted in the proper sockets. The speaker should

# WHEN YOU BUILD SHORT-WAVE USE THIS PRECISION EQUIPMENT

### NATIONAL SOCKETS

Isolantite coil and tube sockets, glazed upper surface for sub-panel or base mounting in 4, 5, 6 or 7 prong types. Exclusive locator-groove makes tube insertion easy.



### MIDGET CONDENSERS

NATIONAL makes a full line of midget condensers for short and ultra shortwave work. Send for special Bulletin giving specifications and prices.




### BX VELVET VERNIER DIAL WITH VERNIER INDEX

Has standard NATIONAL Velvet Vernier B-Dial drive, variable ratio, 6-1 to 20-1,—and with new Vernier Index reading accurately to 1/10th division. Ideal for service men's oscillators, etc.


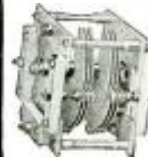
### EMP CONDENSER

A split-stator condenser for receivers and low power push-pull transmitters. Isolantite stator insulators, 1200 v. Single spaced. Standard size 100 mmf. per sect. Available up to 350 mmf. per sect.



### TYPE R-100 R. F. CHOKE

Isolantite mounting, continuous universal winding in four sections. For pigtail connections or standard resistor mountings. Ind.  $2\frac{1}{2}$  mh., distributed cap., 1 mmf., DC resistance 50 ohms. Current rating, 125 M.A. for low powered transmitters and all types of high frequency receivers.



### TYPE R-152 RADIO FREQUENCY CHOKE

Isolantite insulation on metal base, —10,000 v. insulation, continuous universal winding in 5 tapered sections, inductance 4 m.h., distrib. cap. 1 mmf., DC resistance 10 ohms, current ratings,—continuous 0.6 amp., intermittent 0.8 amp. For both high and low powered transmitters and laboratory oscillators.




### NATIONAL SW-3 AMATEUR RECEIVER

The famous NATIONAL Thrill Box, made for amateurs. High signal-to-noise ratio. . . . High R. F. gain through use of '58 tubes. . . . Genuine single control. Because original tooling and engineering cost is now written off, the SW-3 is offered at the low list of \$24.50, less coils. Band spread coils, \$4.75 per pair. Full line of standard R-39 coils for complete coverage from 9 to 2000 meters. (Usual trade discounts apply.)


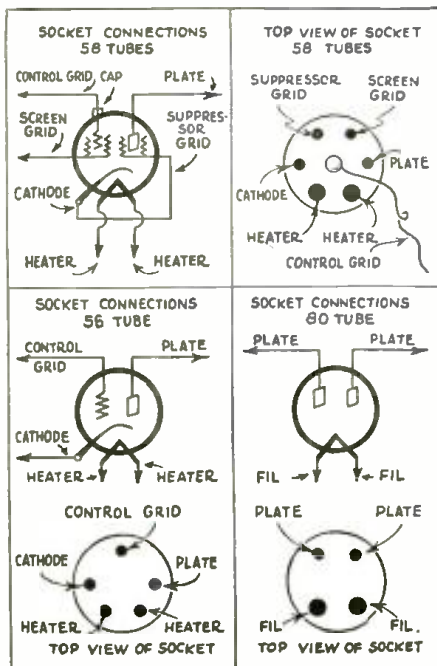
### AIR-DIELECTRIC TUNED I. F. TRANSFORMERS

Designed with Velvet Vernier micrometer tuning. . . . All peaking adjustments from top of shield, self-locking rotors, isolantite insulation. . . . New type Litz coils. . . . 450 to 550 kc. range. . . . U. S. pats. Nos. 1,656,532, 1,713,146. Others pending.



Drawing Showing Tube Socket Connections.

## NATIONAL PRECISION SHORT-WAVE PARTS AND RECEIVERS

NATIONAL COMPANY, INC.,  
61 Sherman Street,  
Malden, Massachusetts

Gentlemen:  
Please send me your latest 16-page catalogue. I enclose 6 cents to cover mailing costs.

NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_ S.W.C. 9-33

be plugged into the 5-prong wafer socket mounted on the rear of the receiver chassis before the power supply is turned on.

The regeneration control knob should be turned to the right to place the receiver in operation, as this closes the A.C. power switch. Time should then be allowed for the tubes to heat up. The regeneration control should be advanced about one-quarter of the way until a squeal is heard in the speaker. If this is not heard, rotate the small antenna trimmer condenser slowly until the two main tuning circuits are in exact resonance. As the trimmer condenser is turned and the antenna circuit is placed into resonance with the detector tuning circuit, it should be necessary to turn the regeneration control to the left, due to the excess of oscillation or regenerative action present in the circuit. If the regeneration control is advanced too far, it becomes impossible to obtain the re-

generative action and as this condition varies with the different bands, it is necessary to have a regeneration control which is capable of covering all the variations due to the difference in coil characteristics for the various bands.

The antenna trimmer condenser C16 should be adjusted constantly to exact resonance with condensers C1, C2 when tuning for weak or distant signals. The operator will note that the smoothest control of regeneration will occur when the antenna and the detector circuits are tuned to exact resonance and the regeneration control is backed off a trifle from the point of maximum regeneration.

### Special Regenerative Action

Actually, this receiver works in a slightly different way than that ordinarily ascribed to regenerative circuits. This action can be described as follows:

# NEW POWERTONE WALLACE

Hoover Cup Prize Winner

## SHORT WAVE RECEIVER



Designed by Don C. Wallace, W6AM, W6ZZA, internationally known short wave expert and amateur



Tested and approved by SHORT WAVE CRAFT



A famous set for its uncanny ability to receive a horde of D.X. Stations. Proper circuit design and layout is the result of much painstaking labor. Each part has a definitely set purpose—and functions at peak efficiency at all times. Band spread tuning of the important

amateur bands, 160, 80, 40 and 20 meters, is controlled by a single panel switch. Produces an extremely high ratio of signal to noise. A control is provided for each important circuit, resulting in peak efficiency under all conditions. Heavily cadmium plated sub-base with black crackle front panel. Plug-in coils are specially wound of flat silvered ribbon to produce the highest possible circuit efficiency. The use of HAMMARLUND parts add to its professional performance. Employs two 230 tubes. Requires two volts D.C. for filament operation, 45-90 volts of "B" battery.

Kit of parts, blueprint and choice of one coil..... **\$14.70**  
 Completely wired and tested, \$3.20 extra.  
 No. 1 Coil—20-30 meters No. 2 Coil—40-60 meters  
 No. 3 Coil—75-150 meters No. 4 Coil—150-200 meters

Each Coil..... **\$1.18**  
**3 TUBE PORTABLE AC-DC SHORT WAVE RECEIVER**  
 Tested and approved by Short Wave Craft Magazine.

Price of complete Kit, with blueprint..... **\$8.95**  
**TRY-MO RADIO CO., Inc.**  
 Dept. S-9 85 Cortlandt St., N. Y., N. Y.  
 Our new Servicemen's Manual will be ready by September, 1st. Send in 50c now and be sure to get your copy. Quantity is limited. Send For New 108 Page Catalog FREE

The detector is constantly oscillating and is pulled out of oscillation by means of the regeneration control. There are two factors which govern this action; one is the power absorbed from the detector circuit by the preceding stage. This absorption is considerable due to the close coupling between the R.F. stage and the detector. Further, the reduction of the applied voltage to the screen grid of the detector tube will tend to pull the tube out of oscillation.




In the ordinary regenerative receiver, the tube is pushed into oscillation by means of energy feed-back from the plate circuit to the grid circuit or by some other means. The fundamental action is that of a stable tube and the tube is actually forced into oscillation by means of any one of the commonly known methods. In this receiver, we use the opposite method, whereby the tube is constantly oscillating and has to be pulled out of oscillation for voice reception or music.

Therefore, keep the antenna trimmer condenser C16 constantly in step with the main tuning condenser C1, C2, so that exact resonance is obtained in both of these tuned circuits. Turn the regeneration control dial and after the whistle of the incoming carrier has been heard, carefully tune C1, C2, which are on a common shaft, and adjust C16 for absolute resonance. Then you will find at this time that you can advance C16 control with greater signal output.
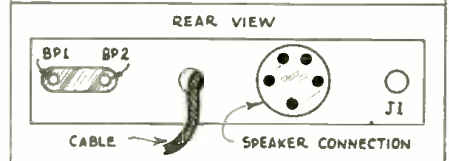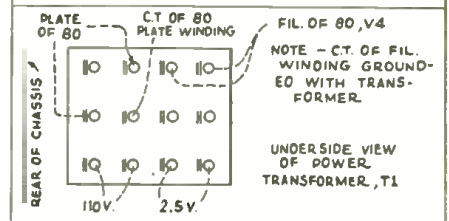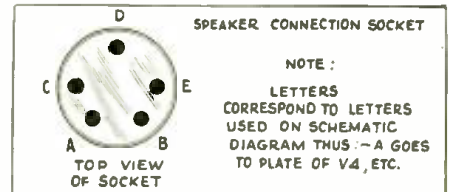
### Parts List Acratone "Discoverer" 5 Tube Set

- 1—Acratest Two-Gang variable condenser, .00014 mf. each section, (C1, C2)
- 5—.02 mf. 300 volt Acratest cartridge condensers, (C3, C4, C5, C10, C11)
- 1—.1 mf., 200 volts Acratest condenser, (C12)
- 1—.5 mf., 200 volts Acratest condenser, (C6)
- 2—.0001 mf. Micamold Mica Condensers, (C7, C8)
- 2—2 mf., 400 volts Acratest Electrolytic Condenser, (C9) (C13)
- 1—Acratest Dual 8 mf. (ea. section) Electrolytic condenser (C14, C15)
- 1—25 mmf. USL Midget variable condenser, (C16)
- 1—800 ohm 1/2 watt Acratest resistor, (R1)
- 2—2000 ohm, 1/2 watt Acratest resistors, (R2, R9)
- 1—25,000 ohm, 1/2 watt Acratest resistor, (R8)
- 1—8 meg., 1/2 watt Acratest resistor, (R4)
- 1—25,000 ohm potentiometer (R5) and switch (Sw1)
- 2—.25 meg., 1/2 watt Acratest resistors, (R6, R12)
- 2—.5 meg., 1/2 watt Acratest resistors, (R7, R11)
- 1—.1 meg., 1/2 watt Acratest resistor, (R8)
- 1—50,000 ohm, 1/2 watt Acratest resistor, (R10)
- 1—25,000 ohm, 1/2 watt Acratest resistor, (R13)
- 1—Full-Vision vernier tuning dial and escutcheon with pilot light V6
- 4—Acratest 6 prong wafer type isolantite sockets, (V1, V2, L1, L2)
- 1—Acratest 5-prong wafer type socket (for speaker connection) riveted to chassis.
- 1—Acratest 5-prong wafer type socket, marked for 56 tube (V3)
- 1—Acratest 7 prong wafer type socket, marked for 59 tube (V4)
- 1—Acratest 4 prong wafer type socket, marked for 80 tube (V5)
- 1—Acratest power transformer, (T1)
- 2—Acratest tube shields, for tubes V1 and V2
- 1—Acratest short-wave R.F. choke (L3)
- 1—Dual antenna-ground binding post, (BP1, BP2)
- 1—Drilled metal chassis, cadmium plated, 1 1/2"x9 3/4"x2" high
- 1—Metal shield plate 11 3/4"x5" No. 20 gauge (Plate "C")

- 2—.5 meg., 1/2 watt Acratest resistors, (R7, R11)
- 1—.1 meg., 1/2 watt Acratest resistor, (R8)
- 1—50,000 ohm, 1/2 watt Acratest resistor, (R10)
- 1—25,000 ohm, 1/2 watt Acratest resistor, (R13)
- 1—Full-Vision vernier tuning dial and escutcheon with pilot light V6
- 4—Acratest 6 prong wafer type isolantite sockets, (V1, V2, L1, L2)
- 1—Acratest 5-prong wafer type socket (for speaker connection) riveted to chassis.
- 1—Acratest 5-prong wafer type socket, marked for 56 tube (V3)
- 1—Acratest 7 prong wafer type socket, marked for 59 tube (V4)
- 1—Acratest 4 prong wafer type socket, marked for 80 tube (V5)
- 1—Acratest power transformer, (T1)
- 2—Acratest tube shields, for tubes V1 and V2
- 1—Acratest short-wave R.F. choke (L3)
- 1—Dual antenna-ground binding post, (BP1, BP2)
- 1—Drilled metal chassis, cadmium plated, 1 1/2"x9 3/4"x2" high
- 1—Metal shield plate 11 3/4"x5" No. 20 gauge (Plate "C")



Wiring of Power Transformer, Speaker Connections, etc.

FREE—C. S. Code Guild Sked. Daily C. S. practice programmes on amateur bands.



**You Can Become a Fast, Capable RADIO OPERATOR at Home**


With the Famous **CANDLER Scientific System**

FREE short wave press schedules. Learn to copy px from Candler trained ops, sending out of principal px stations. Amazing results in short time. **FREE ADVICE IF "STUCK."** Write Candler. No obligation. Junior Course for beginners. Advanced Course for ops with speed of 10 wpm or over who want to get in 30 to 45 wpm class and copy behind. Also Radio Typing Course. Save time and money by sending for **FREE BOOK** today. **CANDLER SYSTEM CO., Dept. 2E, 6343 S. Kedzie Ave., Chicago**


"Candler training enabled me to copy 56 1/2 wpm for the all-time record."—T. R. McElroy, Official Champion Radio Operator of the World, 46 Everdean St., Boston, Mass.



**World's Only Code Specialist**

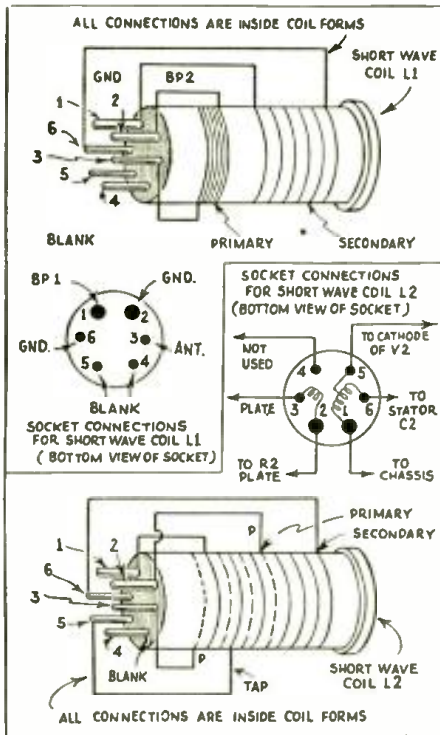

Details of Plug-in Coils and Sockets.

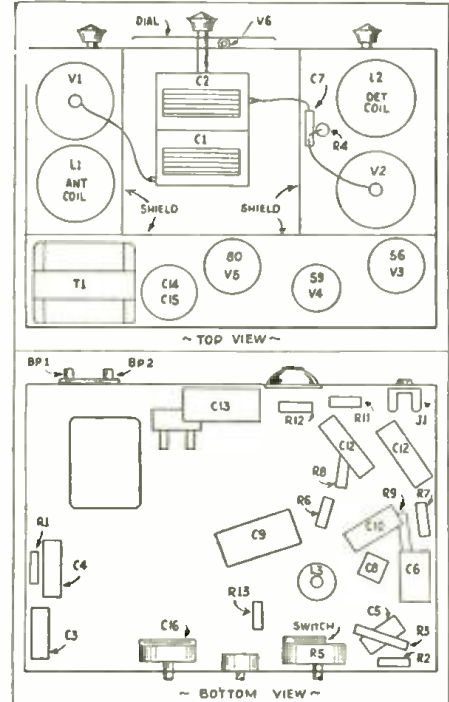

Plan Views of Apparatus Layouts.

- 2—Metal shield plates, 5"x5" No. 20 gauge (Plates "A" & "B")
- 1—Power supply cord and plug
- 2—Screen grid clips
- 3—Small knobs
- 1—Earphone Jack (J1)
- 1—Set 8 Special short-wave coils, covering 10 to 200 meters (L1, L2)
- 1—5-prong speaker plug
- 1—Dynamic Speaker, 8 1/2" Dia. with 1800 ohm field tapped at 300 ohms; matched to output of 59 tube
- 1—Ornamental metal cabinet; gun-metal finish, hinged cover, 11 1/2"x9 1/2"
- 2—58 Variable-mu tubes (V1, V2)—Gold Seal
- 1—56 General purpose tube (V3)—Gold Seal
- 1—59 Output pentode tube (V4)—Gold Seal
- 1—80 Rectifier tube (V5)—Gold Seal

### New Glass H. T. Condensers

(Continued from page 286)

the makers of these condensers have introduced a phase angle of 10 minutes which means that only .00291% of the total power flowing through the capacitor is lost.

By way of comparison, some solid dielectric capacitors have a phase angle in excess of one degree, which means that the losses in this type of capacitor are 1000% greater than those employing flint glass for the dielectric, the sponsors of the new glass insulated units point out.

Another important feature in favor of a glass dielectric is its very low coefficient of expansion. In the majority of cases where wave shifting or creeping is experienced, it has been found that this was directly caused by the expansion of the dielectric material used in the blocking or bypass condensers, causing a change in capacity of the unit. The glass dielectric overcomes this trouble.

A very serious handicap in the construction of a capacitor is the trapping of tiny air bubbles between the plates. This permits corona discharge, which means a decrease in efficiency; in addition, if the corona is great enough it will cause a subsequent rise in temperature, and eventual failure of the unit. By a special method of impregnation this danger is entirely overcome in the new glass insulated condensers. These new type condensers are guaranteed to be free from all defects in both material and workmanship for a period of one year from date of purchase.

### 3 1-2 Inch Waves Now Practical

(Continued from page 267)

The equipment for the *Century of Progress* exhibition consists of a transmitter and receiver, each mounted in an iron-screen rack, 30"x30"x12". Oscillations, corresponding to 9.1 cm. waves, are generated by the small magneto-static tube already mentioned. By means of two-wire transmission line, magnetically coupled to the oscillating circuit, the power is fed into an antenna-dipole located at the focal point of a 24" parabolic metal reflector, which projects the radiated waves in a very narrow beam. The beam is intercepted by another similar mirror on the receiving end, and is focussed by it on a receiving dipole with a crystal detector, by which the 9 cm. oscillations are rectified.

In order to make the transmission audible, the quasi-optical radiation is modulated in the transmitter. A direct audio-modulation is quite feasible, but it is preferable to apply a broadcast-frequency modulation by means of a local oscillator, which can be, for instance, a single 27 type tube. In its turn, the intermediate frequency is modulated in a regular manner by audio frequencies of speech or music. This enables one to receive signals, voice and music directly on a standard broadcast receiver, which gives a greater gain in volume, as compared to the case of a direct audio modulation. All necessary potentials for filaments and plates, both in the transmitter and receiver, are supplied by power-packs from 110 volts A. C. The whole equipment is portable and very simple to handle.

## Look!

APRIL, 1933

**FEATURING -**  
**The Outstanding**  
**Short Wave Receiver**  
**of the Year!**

Shattering all records for consistent, sensational performance...  
**THE NEW IMPROVED ROYAL OLYMPIC**  
establishes a higher standard of Short Wave reception. Verified, load  
sprayed reception from every continental section a new conception of true  
"round the world" reliability.

**THESE FEATURES GUARANTEE**  
**REAL PROFESSIONAL**  
**PERFORMANCE**

THE ROYAL OLYMPIC  
\$29.40

## The ROYAL "OLYMPIC"

SPECIALLY PRICED!

**\$22.00**

COMPLETE with Coils, Tubes, Power Pack & Loud Speaker

The famous ROYAL OLYMPIC SHORT WAVE RECEIVER that is giving consistent, reliable performance in all parts of the world! Time tried and acknowledged to be the most sensational performer in Short Wave History! Never before sold for less than \$33, we are offering these brand new, fully guaranteed, latest model all AC operated genuine ROYAL OLYMPIC RECEIVERS for a short time at the amazing price of \$22.00 COMPLETE! Power pack, tubes, loud speaker, and coils to cover from 14 to 200 meters or amateur band spaced coils are included.

The battery model with tubes, coils and speaker is offered at only \$17.50, a saving to you of over \$7.00.

For a Limited Time Only! ORDER NOW!

### The "FULTONE II" SCREEN GRID POWER PENTODE

This is the same design two tube receiver that has made such a sensational success at prices up to \$25.00. The Fultone II uses a 232 screen-grid high gain detector and a 233 power pentode as an output tube thus giving greater volume than otherwise obtainable! It has an attractive metal cabinet with hinged cover and the entire kit, with every necessary part, includes metal chassis, cabinet, all coils to cover from 15 to 200 meters, and a set of matched, tested tubes.

**COMPLETE WITH TUBES. \$6.85**

Complete as above, assembled, wired and tested—\$8.50

Complete as above, assembled, wired and tested—\$8.50

### ORIGINAL 12,500 Mile Two Tube Receiver

We've sold thousands of these remarkable kits and reports from builders read "Letters from S-W Fans" in Short Wave Craft indicate that they are the best little DX getters ever! Don't let the price fool you! Only the highest grade parts are used and we guarantee the quality to be equal to sets selling for twice as much. These sets are carefully designed and they really work! Getting foreign stations is an every day occurrence!

Clear simple instructions and easy operating make them the ideal beginner's set. Uses 2-230 or 2-201A tubes. Tunes 15 to 200 meters. Crystal finished chassis supplied with all holes drilled.

**COMPLETE KIT \$4.75**  
AC MODEL \$4.95  
ORDER NOW! Satisfaction Guaranteed!  
All prices F. O. B. New York. Deposit required.  
SEND FOR FREE CIRCULAR!

**HARRISON RADIO CO.** Dept. C-23 New York City  
142 Liberty Street  
★ ★ THE HOME OF FOUR STAR SERVICE ★ ★

## Acratone DISCOVERER

### A FIVE TUBE SHORT WAVE SET

DESIGNED BY CLIFFORD E. DENTON



#### THE DISCOVERER KIT

Model 20-A

Complete with all parts. A set of Coils, 15 to 200 meters. Instructions. 8 1/2 inch Dynamic Speaker. Power Supply, and a set of Raytheon 4-Pillar Tubes..... **\$32.50**

#### THE DISCOVERER RECEIVER

Model 20-W

Completely wired and tested on Foreign Stations. With 8 1/2 inch Dynamic Speaker. Power Supply. A set of Coils, 15 to 500 meters and a set of Raytheon 4-Pillar Tubes..... **\$37.50**

All our branches carry a complete line of short wave sets and parts. Replacement Parts, Broadcast receivers, tubes, Public Address equipment, meters and

#### A Real Distance Getter

Sensitive and selective. Brings in hundreds of short wave stations with clarity and brilliance of tone. Every station may be brought in on the loud speaker. Best of all it is available for the set builder in kit form and for the fan completely wired.

The Discoverer is an entirely new Receiver designed primarily for long distance short wave loud speaker reception. During the various tests that Mr. Denton put this receiver through, stations as far away as 10,000 miles were received on the loud speaker with more than sufficient volume.

The Discoverer is a 5-tube T.R.F. receiver having one stage of T.R.F. using a 58 tube, an electron coupled regenerative detector using a 58 tube, and two stages of audio, the first using a 56 tube and the second a 59 power output pentode and a rectifier stage using a 280 tube. The receiver is equipped with a self-contained power supply for 110 to 125 volts A.C. 50 to 60 cycles. A phone Jack is provided for those who prefer phones. An extremely sensitive 8 1/2 inch dynamic speaker is furnished as standard equipment. Provisions are made for the noiseless doublet type antenna. A set of eight space wound coils are supplied. Four are for the R.F. stage and four for the detector. These coils cover from 15 to 200 meters.

other radio supplies. Send for our complete 108-page catalog.

20% WITH ORDER—BALANCE C. O. D.

25 PARK PLACE **Federated Purchaser Inc** NEW YORK CITY

- CHICAGO, ILL. 1331 S. MICHIGAN AV.
- ATLANTA, GA. 431 SPRING ST. NW.
- PHILA. PA. 2209 N. BROAD ST.
- JAMAICA, LI. 3226 MERRICK RD.
- BRONX, N.Y. 534 E. FORDHAM RD.
- NEWARK, N.J. 273 CENTRAL AV.
- PITTSBURGH, PA. 343 BLDG. 5, ALLIES

# "HAM" ADS

Advertisements in this section are inserted at 5c per word to strictly amateurs, or 10c a word (8 words to the line) to manufacturers or dealers for each insertion. Name, initial and address each count as a word. Cash should accompany "Ham" advertisements. Advertising for the October issue should reach us not later than August 17.

MIDGET TRANSMITTERS \$2.00 UP. GUARANTEED tone transmitters \$9.50 complete. Code transmitters using any receiving tube, \$4.00 complete. Range over 1500 miles. The Burks Radio Company, 1448 W. Decatur, Decatur, Illinois.

SW3 COMPLETE \$10.00, SW45 COMPLETE \$12.00, transceiver \$15.00, 30 watt phone transmitter \$15.00. A. Adams, 236 Landis Ave., Vineland, N. J.

QSL's 75c A HUNDRED, 2 COLORS, W9DGH, 1816 Fifth Ave., N., Minneapolis, Minn.

PLUG-IN COILS, 15-210 METERS. SET OF four \$.50. Noel, 809 Alder, Scranton, Penna. QUITTING AMATEUR GAME. TUBES, ETC. 5c up. 453 North Third Street, San Jose, Calif.

CODE MACHINES, TAPES AND COMPLETE instructions for beginners or advanced students, both codes, for sale or rent reasonable. Rental may apply on purchase price. Extra tapes for all machines. Instructograph, 912 Lakeside Place, Chicago.

FOR SALE PRACTICALLY NEW PILOT Universal Wasp, using 1-58, 1-57, 1-56, 2-45's. Excellent Dx. Beautiful cabinet, \$25.00. Raymond Thayer, Gassaway, W. Va.

CRYSTALS, AGAIN AT 95c. HUSKY SIZE. Scientifically ground for maximum power and stability. Calibrated to within 0.05%. Your approximate frequency in 80 and 160 meter bands. Also 525 kc filter crystals for receivers. Same price. 40 meter crystals \$2.00. Inch blanks, 3 for \$1.00. Fully guaranteed. White Radio Laboratory, Sandpoint, Idaho.

SHORT WAVE SETS AT SPECIAL PRICES. Alcoa Aluminum cans, 5x6x9, \$1.45. Bargain sheets upon request. Edbern Radio Co., 2156 Cruzer Avenue, New York City.

SELL MY CURRIE DELUXE 6, SW RECEIVER (January issue) power, speaker, cabinet, \$32.00, or nearest offer. Need cash. E. Baltzley, 1711 Riverside Ave., Muncie, Ind.

CRYSTAL SET. SOMETHING NEW. Separates all stations, operates speaker, blueprint, 6 others, 25c coin. Modern Radiolabs, 151 Liberty, San Francisco, Calif.

ASTOUNDING BARGAINS IN SHORT WAVE apparatus. Receivers from \$3.75 up. Make money building and selling. I furnish kits from \$2.75 up. Write for my free bargain bulletin. Albert Freeman, Main St., South Hanson, Mass.

MAKE BIG MONEY, BE A SAFE EXPERT. Wayne Strong, 735 W. Fairmont, Glendale, Calif.

MICROPHONES, AMPLIFIERS, SOUND heads, speakers. What do you need? Bargains. Wells-Smith Radio Corp., 24 N. Wells St., Chicago.

QSL CARDS, NEAT, ATTRACTIVE. Reasonably priced, samples free. MILLER, Printer, Ambler, Pa.

ANSWER FACTORY CAN HELP YOU WITH that receiver, transmitter, antenna. Send problem and ask for quotation. All work supervised by Robert S. Kruse, RFD No. 2, North Guilford, Conn.

DIZZY CARTOON FOR QSL OR SHACK. Send \$2 with your rough idea for large original pen drawing. WIAFQ, Harwich, Mass.

## IN 1936

You will be interested in tracing the early developments of Short Waves. Your best source of information will be SHORT WAVE CRAFT. Back numbers may be had at 25c per copy. Address: SHORT WAVE CRAFT, 96 Park Pl., New York.

# Hats Off to Catherine Martin

(Continued from page 285)

the place of it. The two upper middle panels contain two magnetic speakers, the bottom panel contains the switches for changing over the aerial on the different radios, the phone jacks, etc. The upper right hand panel holds the long wave set, the Super-Wasp coils hanging just above. The other two right-hand panels are for the transmitter. The two speakers are self-explanatory, I guess. In between them, on top, is a power-pack I made some time ago. The paneling on the cabinet is three-ply wood, walnut stained.


As you can imagine I am rather busy with my school work, the R. T. I. course, making sets, servicing radios, and code practice. I have two ambitions, one I will probably never achieve—the other may some day be realized. The first, to work in the General Electric Laboratories—"The House of Magic"; the other to be a technician of some sort in a broadcast studio. Having picked out radio as my career, I certainly hope to make good in spite of being one of the so-called weaker sex.

### Miss Martin Waxes Technical

You asked for more technical data which is included under the set diagrams. The picture is a 5x8 which is the best I shall be able to send. It was taken by Robert Ande whom you know as he received second prize in the set builders contest some time ago. He has helped me much with set construction.

Now for the set under construction. This set employs the new -57 and -47. Since the -57 gives an amplification factor of 1500, and the -47 pentode a factor of 150, the signals are well amplified.

Tracing through the diagram—the 5-plate antenna condenser works very well on a short-wave set, often helping to tune the distant stations in better. The 13-plate tuning condenser is the usual type employed, the potentiometer helps as the regeneration control as well as the 23-plate condenser. The resistance-coupled stage does not serve to amplify as the transformer stage does, but it produces a steady signal and serves to "hold down" the signal. The -27 acts as an intermediate stage to feed into the transformer

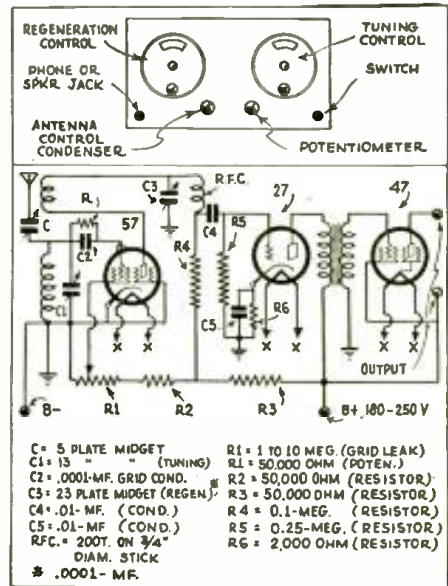

Front Panel and Circuit Diagram of Miss Martin's Receiver.

and -47. The resistances R2 and R3 give the right voltages so that only two "B" leads are necessary, the B- and the B+, 180 to 250 volts. No special tricks are needed in the construction, but the set should be so planned that the grid and plate leads are as short and separated as possible. My set has a 3-ply panel and subpanel. It is not a bread-board layout as the leads can be planned to better advantage if a non-bread-board type is used.

Before this set is finally done, a stage of radio frequency will probably be added. The r.f. stage will employ a -58, and will be very much like that in Mr. Myer's set described in the April, 1933, SHORT WAVE CRAFT. This set, by the way, is a very good one, especially for code.

## Leotone 2-Volt Set Has "Pep"!

(Continued from page 278)

ances from anywhere from 20 to 100 mh. A by-pass condenser of .00025 mf. is connected from the tickler to the filament circuit; the plate load resistor for the detector is 0.25 megohm, which is coupled through a .01-mf. fixed condenser to the 1-megohm grid resistor of the first audio amplifier, a 30 type tube. The plate load resistor for this first audio tube has a value of 0.25 megohm. This couples through another 0.01-mf. condenser to the 0.25-megohm grid resistor of the second audio or output tube, also of the 30 type.

### Receiver Very Economical

This receiver is extremely economical, especially when the great strength of signal produced in the loud speaker is considered; the first three tubes in the set drawing but .18 ampere and the output pentode requiring but 0.26 ampere, the total filament current therefore being only 0.44 ampere. The "B" battery drain is also very low, the total plate current approximating 20 milliamperes. The designers of this receiver

therefore figure that two No. 6 type dry cells, series connected, together with three medium-sized 45 volt "B" batteries, should operate the set for about five months with the average daily use. It is, of course, recommended to try and obtain the large sized "B" battery units if the "old wallet" will stand it, which should provide approximately a year's service.

The Leotone receiver has a wave-length range of 17 to 200 meters; possesses, as we have seen, a very low current drain on both the "A" and "B" batteries; uses four inexpensive tubes of the desirable 2-volt dry-cell type, and may be purchased if desired in kit or fully assembled and wired form. A foundation kit, including one metal case, one chassis, and one shielded compartment, is also available.

### List of Parts for Leotone Receiver

- COILS:  
 2 sets of short-wave plug-in coils for 0.00014 mf. capacity. Alden, (Bruno).  
 1—30 millihenry honeycomb R.F. choke coil.

# WATCH NEXT ISSUES

of Short Wave Craft

for "10 METER" Phone & C. W. Transmitters

Full Constructional Data

and Receivers.

**CONDENSERS:**

- 1—two-gang 0.00014 mf. tuning condenser.
- 5—0.01 mf. mica condensers.
- 1—0.5 mf. bypass condenser.
- 1—0.00025 mf., mica condenser.
- 1—0.0001 mf. mica condenser.

**RESISTORS:**

- 1—15 ohm fixed filament resistor.
- 1—20 ohm rheostat.
- 1—2.7 ohm fixed resistor (may be improvised from a 6 ohm rheostat set to apply 2 volts on filament, when the 20 ohm rheostat is set at zero resistance).
- 1—3 meg. pigtail resistor.
- 1—100,000 potentiometer, with switch attached.
- 3—0.25 meg. (250,000 ohm) pigtail resistors.
- 1—1.0 meg. pigtail resistor.

**OTHER REQUIREMENTS:**

- 3 UX and one UY sockets.
- 1 antenna-ground connector.
- 1 speaker connector.
- 1 six-lead outlead cable.
- 1 drum dial, scale, escutcheon.
- 1 shielded box with hinge cover, overall 9 3/4" wide x 8 3/4" high x 8 3/4".
- 1 chassis with shield compartments, to fit inside shield cover.
- 2—"C" batteries; 1—3 volt, 1—22 1/2 volt (small "B" unit).

**LEOTONE-ALDEN PLUG-IN COIL DATA**

Meters Wave-length	Grid coil turns	Tickler turns	Distance between 2 coils
200-80	52 T. No. 28 En. Wound 32 T. per inch	19 T. No. 30 En. Close wound (CW)	3/8"
80-40	23 T. No. 28 En. Wound 16 T. per inch	11 T. No. 30 En. C. W.	3/8"
40-20	11 T. No. 28 En. 3-32" between turns	9 T. No. 30 En. C. W.	3/8"
20-10	5 T. No. 28 En. 3-16" between turns	7 T. No. 30 En. C. W.	3/8"

Coil form—2 1/8" long by 1 1/4" dia. 4-pin base.

**Do's and Don'ts for Short-Wave Fans**

Edgar Messing

- DON'T use junk; use good material for a good set.
- Don't use an R.F. choke where you can use a resistor.
- Don't wind coils on cardboard tubing; use something that won't absorb moisture.
- Don't try to eliminate unwanted oscillation by reducing gain; look for the cause first.
- Don't put coils too near metal shields or chassis; keep them at least .7 the coil diameter distant from the nearest metal.
- Don't run leads across the chassis to bypass condensers; use roll type condensers and solder them right at the point where they are to work.
- Ditto for R.F. chokes, whether they are resistors or coils.
- Don't use the '82 unless you have to; the '80 will give less trouble.
- Don't trust the chassis as an R.F. ground at the shorter wavelengths; run wires from the variable condenser rotors.
- Don't run long ground leads in the set but try to make all R.F. grounds at one spot.
- Don't run the leads between the high side of the variable condenser and the high side of the coil too close to a metal chassis. Use bare wire if possible. Tests have shown that the elimination of poor condensers and the use of bare wire may increase selectivity as much as 30%.
- Don't use wire larger than No. 18 nor smaller than No. 26 for tuned circuit coils operating below 100 meters.
- Don't use large ticklers spaced far from the coil they are tickling; use No. 30 to 34 wire and wind the coils as close to the tickled coil as possible.
- Don't space the turns on a space wound coil more than the diameter of the wire; the gain is not noticeable for greater spacing and it becomes harder to couple to the coil.
- Don't guess; if you have a meter, measure.

**VALUE • AND • ECONOMY**  
*The Lowest-Priced*  
**COMPLETE**  
*Short-Wave*  
**Superheterodyne**



**COMET**  
**"PRO"**  
*Professional*  
**Short-Wave Receiver**

**T**O own a short-wave receiver comparable with the COMET "PRO", you must buy or build a perfect tuner, an adequate power supply, a complete set of coils, special transformers, etc. These will make your receiver cost more than if you bought the "PRO" complete, with all "accessories" built-in and scientifically matched to the receiver.

The list price of the COMET "PRO" is \$150 (less tubes). But it won't cost you that much! As a recognized amateur you are entitled to a discount of 40 and 2 per cent, which reduces the price to \$88.20, plus a small Federal Excise Tax. That price includes not only a tuner, world-famous for its sensitivity and selectivity, but also a built-in power pack, air-tuned transformers, and all coils needed to cover a range of 15 to 250 meters, with band-spread tuning at all frequencies.

Think it over and you'll buy the COMET "PRO" for its unexcelled performance, plus its unequalled value and economy.

*Mail Coupon for Details*



**HAMMARLUND MANUFACTURING CO.,**  
424-438 33rd Street, New York, N. Y.

.....Check here for folder describing the COMET "PRO" in detail.

.....Check here for General Catalog "33."

Name .....

Address .....


SW-9

**OCTOCOILS**

*A Standard for Short Wave Set Builders Since 1928*

Now in Use in More Than  
**60 Foreign Countries**

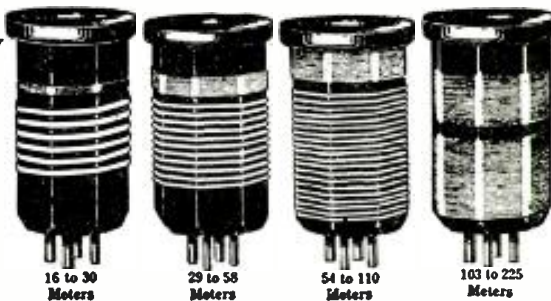The New  
Price  
is now  
**\$2.25**  
per  
set of  
four



Wave-length  
Range  
**15 to 225**  
meters

Increased production has enabled us to tremendously reduce the price of OCTOCOILS always listing at \$5.00 per set. Wave length range 15 to 225 meters with .00015 variable condenser—wound on perfect dielectric bakelite forms in attractive colors—Ask the Hams—they know OCTOCOILS—At your dealer or all Kresge \$1.00 Stores—or sent pre-paid anywhere on receipt of price.

**SHORTWAVE AND TELEVISION CORPORATION**

Division of General Electronics Corporation, 70 Brookline Ave., Boston, Mass. Pioneer manufacturers of Television and short wave apparatus. Owners and/or operators of television and sound stations W1XAV, W1XAU, W1XG and W1XAL.

**Remarkable Freedom  
from NOISE... by use of  
LYNCH**  
Short Wave Antenna System

*Mark Isaacs Co.*  
NEW ORLEANS, LA.  
110 PINE STREET

New Orleans June 14, 1933

Mr. Arthur H. Lynch, Pres.,  
Lynch Mfg. Co., Inc.,  
51 Vesey Street, New York, N. Y.

Dear Mr. Lynch:

Since my letter to you of June third I have spoken to several jobbers as well as servicemen with reference to your short wave antenna equipment. I have also demonstrated a Lynch Short Wave Antenna which I have constructed on the Philco Building, in one of the noisiest spots in our city. All who have seen this antenna and heard the marvelous results that have been obtained, are highly enthusiastic.

I am greatly interested in the advancement of Short Wave Receivers and Antenna equipment, and know from experience that the LYNCH Antenna System actually does, even in extreme cases, eliminate all disturbing noises.

You may be interested to know that I am installing Short Wave Sets and LYNCH Antenna Systems for such concerns as Maison Blanche Radio Department, Barnett Furniture Company, Marks Isaacs Company, Waiter Bros., Inc., Godeaux Clothing Co., and D. E. Holmes Co., Ltd.

Yours very truly,  
(Signed) GENE MORRIS.


Complete Kit ..... \$5.00  
At ALL LYNCH Jobbers and Dealers

If your Jobber, Dealer or Serviceman cannot supply you, order direct from us. Sent post-paid, with instruction booklet, for \$5.00.

Free Descriptive Folder Upon Request  
LYNCH MANUFACTURING CO., Inc.  
51 Vesey Street, New York, N. Y.  
Makers of the Famous Metallized Resistors

**Here  
It Is!**

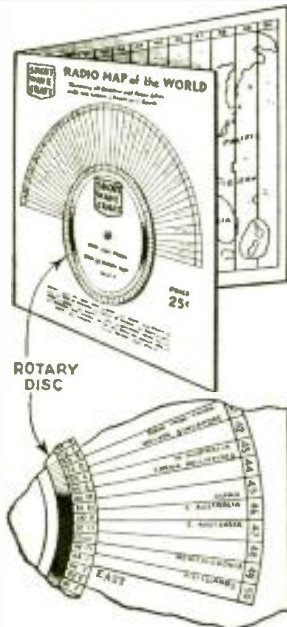The  
finest  
and most  
ingenious  
STATION  
FINDER  
and  
RADIO  
MAP  
of the  
World



Here is a device that no radio man should do without. It lends that professional dignity to your den. It instantly shows you the exact time in any foreign country.

Professional short wave listeners are never without this station finder because they do not twiddle the dials needlessly in trying to fish for stations which may not be on the air due to time differences.

This handy device is printed on heavy yellow board; on the front there is the automatic time converter, which rotates, you can set it for any time of the day in fifty different zones in the world. On the inside are illustrated the fifty zones showing the principal countries of the world. All the important cities are shown, and inasmuch as they are all zoned, the exact time can be converted within a few seconds.

The size of the station finder and radio map of the world is 11x22. The price of this handy device is 25c prepaid.

However, it is sold only to members of the Short Wave League. Outsiders cannot buy it.

We refer you to page 262 for order blank. Take advantage of this opportunity at once, and get rid of your present annoyance in calculating the time for the different countries.

**SHORT WAVE LEAGUE**

38 Park Place

New York, N. Y.

Don't think a set is good because it gives a loud signal; it is the signal to noise ratio that counts.

Don't use switches where you can avoid it; the more switch sections the greater the possibilities of trouble.

Don't use the '24 or '35; use '57's or '58's. The new tubes have lower output capacities and will give greater gain.

Don't swear at fading; use a.v.c. The '55 accomplishes a.v.c. very simply; try it.

Don't use class "B" amplification in your first set; use a single pentode as the output tube.

Don't use resistors larger than 1/2 megohm anywhere throughout the set; higher values are never accurate and often troublesome. In resistance coupling the grid to ground resistor if larger than 1/2 megohm makes the grid too sensitive to stray pick-up.

Don't use resistors larger than 1/4 megohm for detector plate loads; use 100,000 ohms when a '27 or a '56 is the detector, and 1/4 megohm when a '24 or a '57 is used.

Don't make detector cathode resistors too small; use 5,000 to 10,000 ohms in first detector cathodes (5000 ohms will be a bit more sensitive), use 50,000 ohms in the cathode of a second detector '57 or '24, use 30,000 to 40,000 ohms with a '56 or '27.

Don't use an R.F. choke in the plate circuit of the second detector; use a resistor of at least 30,000 ohms.

Don't rely too strongly on carbon resistors below 10 meters; their R.F. resistance and the marked value are two entirely different animals.

Don't use a condenser larger than 4 mikes as the first section of the power pack filter; it isn't good engineering because it isn't economical (Class B expected).

Don't lay out the chassis for beauty; follow the diagram for straight line wiring.

Don't spoil your set by putting too little power in the field of a dynamic speaker; use about 8 watts (square of D.C. through the field times field resistance.) for good quality, six watts for fair quality, and 4 watts for midget set quality.

Don't use a large variable condenser for tuning when you can use a smaller one; the smaller condenser will give greater gain.

Don't expect the smaller condenser to cover as large a range as the larger; a regular .000365 mf. standard broadcast variable will cover from 18 to about 55 meters with a good coil and careful wiring, a .00015 will cover from 18 to 38 meters.

Don't use inductive type condensers; you might just as well use a choke and stop trying to fool the R.F.

Don't put bypass condensers in a block; they may bypass in the wrong direction.

Don't use a transformer without an electrostatic shield if you can help it; the hardest-to-trace kind of hums will originate from that kind of transformer. If you must use a transformer without a shield put .1 mf. high voltage non-inductive condensers from each plate of the rectifier to center tap and put an R.F. choke in series with the first filter section.

Don't use a shielded lead-in with the shield grounded to prevent noise pick-up; you may not hear noise but you will not hear many short wave signals.

Don't overlook the tone control; on short waves it may really be worth its salt (for the first time!). Use a .01 mf. in series with a 30,000 ohm variable resistor from plate to ground of the output tube if it is a '47. These values will also serve to straighten out the response of the '47 and tend to give better quality.

Don't leave out a plate to screen condenser for the '47 if you eliminate the tone control; use a .004 to .006 mf. If this condenser is connected between plate and screen instead of plate to ground it will be just as effective, may have a lower voltage rating, and will be cheaper.

Don't bypass a 400 ohm resistor in an audio circuit with a 1/2 mike condenser; it just won't work. Incidentally, the easiest way to calculate condenser react-

ances is to remember one simple set of figures—1 mf. has a reactance of 1600 ohms at 100 cycles. From this value any condenser reactance at any frequency can be calculated; for example 1 mf. at 1000 cycles has a reactance of 160 ohms, One-half mf. at 100 cycles has a reactance of 3200 ohms, one-half mf. at 2000 cycles—160 ohms. The value of reactance of the bypasser to the thing by-passed should be at least 1:20.

Don't shield grid wires except as a last resort; the additional capacity lowers gain, and decreases range.

Don't let a regenerative set squawk or squeal at the point of regeneration; it makes tuning a nuisance and hurts the ears! The point of regeneration should distinguish itself by a soft "shush." Incorrect values of grid leak and condenser are the usual sources of trouble. Remember that at the higher frequencies it is easier for the grid condenser to "choke" and cause a squeal. A .0001 mf. condenser and 2 megohm leak usually compose a safe combination.

Don't use a variable condenser for controlling oscillation; a variable screen grid bias arrangement controls as satisfactorily and does not react on the tuned circuit as the capacity control does. Use a 50,000 ohm potentiometer connected between 90 volts and B—, the arm going to the screen and by-passed to ground by a 1 mf. condenser to eliminate any audio noise caused by movement of the arm over the resistance strip.

Don't forget the sure and simple test for oscillation; touching the grid terminal of the tube or variable condenser. If the tube is oscillating a sharp click will be heard when either of these terminals is touched and another when the finger is removed.

Don't use a condenser larger than 15 mmf. if a tuned circuit is to be capacity coupled to the antenna; a larger condenser gives too close coupling, a smaller condenser decreases gain at the 200 meter end of the range.

Don't use a trimmer as vernier across the main tuning condenser that has more than 1/6th the capacity of the larger condenser; a large trimmer makes it difficult to pick up stations, adds to reaction effects, and gives a "false" sharp tuning effect.

Don't make grid or plate wires any longer than necessary; the shorter they are the more stable the set.

Don't control volume by varying either bias alone or antenna input alone; a combination of both gives a smoother control with better quality.

Don't forget that a 58 when used as a detector may take the same screen bias as the R.F. or I.F. tubes.

Don't solder to nuts or screws; fasten a soldering lug under the nut and solder to the lug.

Don't use anything but rosin core solder for soldering; some of these so-called non-corrosive soldering pastes can do very funny things to coils at the shorter wavelengths.

Don't apply heat to carbon resistors; make soldered connections to the pigtailed distant at least 1/2 inch from the end of the resistor. The same applies to roll type condensers.

Don't allow solder to fall on coils or in socket prongs; one can search for hours for trouble causes and overlook these very common and annoying reasons.

Don't rely on carbon resistors (or any other type for that matter) to be exactly the values marked; the usual manufacturing tolerance is 10%. Remember, however, that few resistors in a set have to be exact and that 10% tolerance is usually perfectly all right.

Don't forget that oscillator grid condenser and resistor combinations can cause whistles in a super-heterodyne as well as in a regenerative receiver. The author forgot once and spent a night and a day wondering why the I.F. persisted in squealing when there was every sort of by-pass and filter on it.

Don't plug in the juice in a new set before testing for shorts across the high potential supply.



## Letters from S-W Fans

(Continued from page 289)

It is the only magazine really useful to the builder and to everybody that wishes to learn the secrets of short waves. I am afraid I am going to have to subscribe, as I don't want to lose one number.

I am glad to tell you that very often (every night that I keep up studying, as I am a student) I receive very well your stations W8XK and W2XAF. The last one is better and stronger on 31.48 meters. I use an antenna 38 meters long. I can hear clearly your speaker announcing the station during the transmission of music (a thing that never happens in European stations).

I would be glad if I could be of some use to you.

Let me congratulate you on the success of your magazine and believe me,

VITTORIO TURETTI,  
Via Crana 15,  
Turin (11 F),  
Italy.

(Greetings, Vittorio, and we are mighty glad that you took time to write us from Italy. We are tickled to note that you find the descriptions of short-wave sets as presented in SHORT WAVE CRAFT not only pleasing but useful as well. You state that you will be glad if you can be of any service to us and we can only state that the more readers SHORT WAVE CRAFT can obtain, the greater and bigger the magazine can be made. So you can do yourself and short-wave fans everywhere a great favor by telling them about SHORT WAVE CRAFT whenever you have the opportunity. Thanks again for your welcome letter.—Editor.)

### HE LIKES S-W FICTION!

Editor, SHORT WAVE CRAFT:

Some time ago I read a story in SHORT WAVE CRAFT by A. D. Middleton and it was a corker but "Ham" Radio Foils Ransom Plot" in the June issue is the best yet.

Not only is this story thrilling fiction for the S-W fan, but it suggests forcibly to the would-be brass pounder the advantages of better operating.

Keep QSO with this W8UC-W4CA and let's have more of these stories.

J. E. FAW, W2BYX,  
122 Archbold Place,  
Westfield, N. J.

(We try to pick out the best possible short-wave fiction, J.E.F., and we were glad to hear from you to the effect that you liked Mr. Middleton's story in the June number. You will find another interesting and thrilling short-wave tale in this number of SHORT WAVE CRAFT.—Editor.)

### LIKES THE "GLOBE TROTTER"!

Editor, SHORT WAVE CRAFT:

I wish to compliment you on the wonderful magazine which you are publishing. I have been a reader of SHORT WAVE CRAFT, since the April, 1932, issue.

I think the "Globe Trotter" which was described in the November, 1932, issue is a very good receiver. I added one stage of audio and a band-spread" condenser. I have worked many amateurs on the loud speaker. I have received "hams" from nearly every district; I also get short wave broadcast stations of the U. S. and Police Calls. I am hoping you will keep up the good work.

CURTIS SMALL,  
206 E. Broadway,  
Fulton, N. Y.

(Glad you liked the "Globe Trotter," Curtis, and we have received several thousand letters since the publication of the article describing how to build it and telling of the fine results which various readers of SHORT WAVE CRAFT have achieved with it. Many of our readers have heard their first "foreign" short-wave stations on the Globe Trotter. Thanks and let us hear from you again.—Editor.)

### BEGINNERS CAN UNDERSTAND OUR ARTICLES!

Editor, SHORT WAVE CRAFT:

I wish to tell you how we appreciate your magazine down in this little part of the continent.

It is the only magazine we can obtain from our newsstands that a beginner can understand. Your sets are good and yet are described in such simple terms that anyone can understand them.

From our location any short wave station is "DX" to us. That is from seven hundred miles up, so when we build a set to pull your stations in regularly, we are quite pleased.

To give you some idea of how the set "perks" I am listening to GSA, England, at present. Also get Holland, Germany, France, Spain, Italy, Argentina, Ecuador, Columbia and Venezuela. Get practically all your stations over there including "hams," police, airport, ship-to-shore, etc.

HADDON B. MARTIN,  
113 Hawthorne Street,  
Dartmouth, Nova Scotia.

(Tickled pink to hear from you, Haddon, and we are pleased to hear you say that the articles in SHORT WAVE CRAFT are described in simple terms so that practically anyone can understand them. We make a special effort each month to make the various articles we publish clearer than ever before, and we go to a lot of editorial trouble and expense in our Drafting Department in order to make the "picture" diagrams which we feel most anyone, even a rank layman, can follow. Let's hear from you folks down "Nova Scotia way again —and right soon.—Editor.)

### AMLIE CIRCUIT GETS AUSTRALIA!

Editor, SHORT WAVE CRAFT:

As I am a reader of SHORT WAVE CRAFT I would like to tell you that I am very pleased with your fine magazine, and shall always be a reader of it. After looking through the "Letters From S.W. Fans" page in the December issue, I came across a letter from Mr. Ned Chestnutt. I agree with him on Mr. Oliver Amlie's circuit. To prove this circuit is O.K., here is my record! I have heard G5SW, FYA, six days a week on the speaker. I have also heard VK3ME, VK2ME, HRB, GBS, HKD, T14, HV2, 200 amateurs, 25 police stations, all on the loud speaker!

Best of luck to SHORT WAVE CRAFT and staff.

BILL SMITH,  
58th N. 60 St.,  
Philadelphia, Pa.

(Hot-cha-cha, Bill!—My! but you boys are certainly doing wonders with Amlie's circuit which we published in the May, 1932, issue. All we've got to say is that the circuit is certainly "simplification" itself, and anyone can easily build it—that's one thing to be sure of. Here's hoping that many more short-wave "fans" have the fine success with the Amlie circuit that you and many others have experienced with it already.—Editor.)

### THAT "DOERLE" AGAIN!

Editor, SHORT WAVE CRAFT:

Talk about petting a radio! My set is the talk of the neighborhood. I am a kind of a "hobbyist." Before I started tinkering with short-wave sets I was a builder of model airplanes.

I first set my eyes on your magazine last December. From then on airplanes were forgotten! The "Doerle" regenerative circuit was the first radio I built, although, I know plenty of radio through reading books on the subject.

At first the set didn't satisfy me. I had built it in a hurry because I was anxious to hear "foreign" broadcasts. All I ever did hear was W3XAL, W8XK, W8XAL, W4XA, VE9DR, VE9GW, VE9JR, W9XAA, all in the 49 meter band. I also heard

(Continued on page 306)



Now Available—

## AN EASILY ASSEMBLED ALL-WAVE SUPERHETERODYNE COIL KIT

By Miller

Scientific design, high grade workmanship and outstanding performance are assured with every MILLER ALL-WAVE INDUCTANCE KIT.

Blue print of circuit showing all values makes it a simple easy job to build a 7 tube ALL-WAVE Superheterodyne receiver with outstanding performance as proved by present users.

Kit includes 5 inductances wound on bakelite forms, 3 intermediate transformers (456 KC), rectifier plate filter chokes, 3 padding condensers and 2 variable coupling condensers—securely packed for safe shipment anywhere.

LIST PRICE **\$15.00** POST PAID

Standard discounts to Dealers and Amateurs. A deposit of 20% required with order.

### J.W. MILLER COMPANY

5917 So. Main St.  
Los Angeles, California

## LEARN AT HOME TO BE A

## Good Radio Operator

It's Easy

with The NEW MASTER

Teleplex

Code Teaching Machine

Pleasant, interesting work. No experience necessary. We guide you step by step—furnish you Complete Code Course and lend you The New Master Teleplex. Teleplex has instructed more students in the code in the past ten years, than all other systems combined. It is the only instrument ever produced that will record your own sending in visible dots and dashes, and then repeat it to you audibly on headphones. Used by U. S. Army and Navy, R. C. A., A. T. & T. Co. and others. Get started NOW. Low cost, easy terms. Write for folder SW-9 giving full details.

TELEPLEX COMPANY  
76 Cortlandt St. New York, N. Y.

*Skeptical of Short Waves? We actually Guarantee Results*



# BUY GUARANTEED

## These Are Fool-Proof Short-Wave Sets READ WHY WE CAN GUARANTEE RESULTS

When a manufacturer offers such a broad guarantee—a guarantee which is almost unconditional—he must have a lot of confidence in his products. We have that faith in our short-wave receivers, because they are fool-proof. They are fool-proof because they are simple. EACH RECEIVER EMPLOYS A MINIMUM NUMBER OF PARTS TO MAKE ITS RESPECTIVE CIRCUIT OPERATIVE. ALL FANCY EMBELLISHMENTS, USUALLY FOUND ON "EXPENSIVE" SETS, HAVE BEEN ELIMINATED. If properly adjusted and carefully tuned, they will bring in most anything on short waves worth hearing, not only in this country, but anywhere.

Furthermore, only first-class parts have been used throughout. We realize that the separate parts for our sets can be obtained elsewhere, at a lower price, but we do not manufacture and sell sets employing cheap parts; for such receivers are not reliable; they may work, but erratically. We feel, therefore, quite safe in guaranteeing these wonderful sets to perform fully as represented.

And here are letters from those who have actually tried these Short-Wave sets:

### THE OSCILLODYNE

#### HOW IT WORKS

I have constructed the OSCILLODYNE RECEIVER and boy! how it works!

The first day without any trouble I received Spain, England, France, and other foreign countries. Amateurs! why I never knew there was that many until now. With the one tube Oscillodyne, I bring in more stations on one plug-in coil than with a set of coils on different short-wave sets.

IF ANY ONE IS TRYING HIS LUCK ON SHORT-WAVE SETS, IT WILL BE WORTH WHILE TO CONSTRUCT THE ONE TUBE OSCILLODYNE.

PAUL KORNEKE, JR., N. S. Pittsburgh, Pa.

#### A PEACH

The oscillodyne receiver, believe me is a "peach." I get short-wave stations from Germany, France, Spain and Italy—not to mention the American stations, including amateurs all over the United States.

I heartily recommend this set to any Short-Wave fan.

HENRY TOWNSEND, Ramsey, N. J.

### THE DOERLE RECEIVERS SOME LIST!

I have just completed your Doerle two-tube. I received the following on the loudspeaker: XDA, LQA, GMB, VE9DI, VEGW, KKG, WIXAZ, WZXF, W3XAL, W3XAL, W3XK, W3XAL, W3XF, W3XAA, Bermuda, Honolulu, Budapest, Hungary, and "hams" in 38 states.

MAURICE KRAAY, R. F. D. 1, Hammond, Ind.

#### THIS IS GOING SOME!

Today is my third day for working the Doerle set, and to date I have received over fifty stations. Some of the more distant ones I shall list. From my home in Maplewood, N. J., I received the following: WVR, Atlanta, Ga.; W6K, Ohio; W9HIM, Ft. Wayne, Ind.; W9AYS, Elgin, Ill.; W8BERK, Girard, Ohio; and best of all, XDA, Mexico; PZA, Surinam, South America; TIR, Cartago, Costa Rica; G2WM, Leicester, England. I have also received stations WDC and PJQ, which I have not found listed in the call book.

JACK PRIOR, 9 Mosswood Terrace, Maplewood, N. J.

#### A DOERLE ENTHUSIAST

I have just completed my two-tube Doerle, and it surely is a great receiver! It works fine on all the wavebands. Nobody could wish for any better job than this one. I can get W8XK and W3XAA to work on the loudspeaker at night, and the code stations come in with a wall-to behind them.

NAMUEL E. SMITH, Lock Box 241, Graviton, Mich.

#### FRANCE, SPAIN, ETC., ON LOUDSPEAKER

I hooked up my two tube Doerle Kit and I received France, Rome, Spain, Germany and England on the loudspeaker as well as over 100 amateur phone stations. I am very pleased with the receiver and would not part with it for anything. I have listened to many factory built short-wave receivers, but believe me, my DOERLE is the set for me.

ARTHUR W. SMITH, Springfield, Mass.

#### REGULAR FOREIGN RECEPTION

A few days ago, I purchased one of your TWO TUBE DOERLE WORLD WIDE SHORT WAVE RECEIVERS. I just want to tell you that this set does all you claim. In the short time I have had the set, I have brought in stations in England, Germany, France and South America, Davenport, England, and Nauen, Germany can be picked up daily with very strong volume. THE DOERLE IS A FINE SET.

ARTHUR G. GLUCK, Brooklyn, N. Y.

#### THRILLED BY DOERLE PERFORMANCE

I am very much pleased with the DOERLE S-W radio I received; the local amateur stations come in loud and clear. The first foreign station I received was DJA, Zeesoon, Germany. I certainly received this station with a thrill. Your for success.

RANDOLPH GRAY, Quincy, Mass.

## Order From This Page

Send money order or certified check. C. O. D. only, if 20% remittance accompanies all orders. Order NOW—TODAY.



## The Oscillodyne 1 Tube Wonder Set Latest Short-Wave Development This Is The Ideal Beginner's Set

Rear View

Here, then, is a set which brings in stations thousands of miles away; a set which frequently brings in Australia, loud enough to rattle your phones, and with power to spare; a set which, if you do not wish extreme distance, will bring in stations several thousand miles away without aerial or ground.

In our estimation, the Oscillodyne is one of the greatest recent developments in radio circuits, and the editors recommend it warmly to all readers.

### ABSOLUTELY FOOL-PROOF

This set, as we sell it, may be had either completely wired, or in kit form. There is absolutely nothing to go wrong with the Oscillodyne. Simple directions and blueprints show you how to build and operate the set for best results. It may be used either on A. C. or with power pack (such as the one listed on the opposite page.) 2 1/2 volts will be required for the filament of the tube, and 90 volts for the plate. If batteries are employed, a 237 tube should be used in conjunction with either a storage battery or four No 6 dry cells and two 45 volt B batteries.

Only first-class parts are used throughout. The panel is of aluminum, and the sub-base of Bakelite. There is no guess-work with this receiver—no disappointment.

#### Oscillodyne Wonder Set

The set is exactly as illustrated here, size of aluminum panel is 6" high by 4 1/4" wide, base 5 1/4" long by 4 3/4" wide. List of materials used:  
No. 2146. Official One-Tube Wonder Set, completely wired and tested as per above specifications. **\$6.18**  
YOUR PRICE  
No. 2147. Official One-Tube Wonder Set, but not wired; with blueprints and instructions included. **\$5.33**  
No. 2148. COMPLETE ACCESSORIES, including the following: one 6 month guaranteed Neontron No. 237 tube, one set No. 1678 Brandis matched headhones, four No. 6 Standard dry cells; two standard 45-volt "B" batteries, complete shipping weight 22 lbs. YOUR PRICE **\$5.08**



Front View

## The Oscillodyne 2 Tube Loudspeaker Set NO PLUG-IN COILS




Rear View

The principle of the Oscillodyne circuit is a new one. It is of the regenerative variety, yet acts like a super-regenerative set, although it does not belong in this class. Its sensitivity and selectivity are tremendous. The special band-selector switch affords complete hand coverage in four over-lapping stages.

Only parts of the highest quality, such as Hammond condensers, Yasley switches, Kurz Kaech vernier dial, etc., have been used. These parts are mounted on a sturdy cast-iron-plated metal chassis which measures 9" long x 6 1/4" wide x 4" high. Complete set of blueprints and instructions included.

No. 2197. 2-Tube Oscillodyne Loudspeaker Set, Completely wired and tested. Ship. wt. 9 lbs. **\$10.83**  
YOUR PRICE  
No. 2198. 2-Tube Oscillodyne Loudspeaker Set in kit form. Ship. wt. 9 lbs. **\$9.83**  
YOUR PRICE  
No. 2199. Complete accessories for this receiver, including 1—type 56 tube, 1—type 47, 1—special short-wave hmv-free AC power pack, No. 2149; 1—type 280 rectifier tube for the power pack; 1—B. B. L. magnetic loudspeaker. Ship. wt. 14 lbs. **\$11.18**  
YOUR PRICE

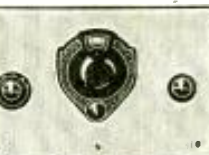

Front View

**RADIO TRADING COMPANY, 100A Park Place, New York City**


# SHORT WAVE SETS

Sets Which Work At Your Command

And NOW The Electrified Official Doerle

2 And 3 Tube Receivers

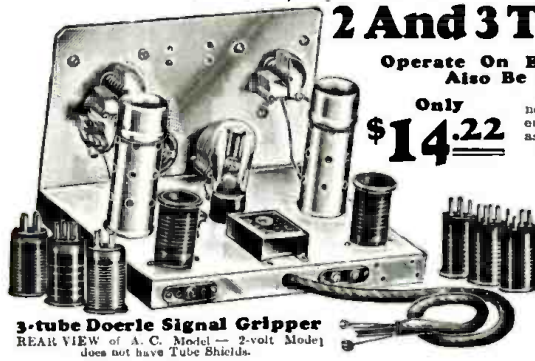Operate On Either A. C. or Batteries—May Also Be Had For 2-Volt Operation



**3-tube Doerle Signal Gripper**  
REAR VIEW OF A. C. Model—2-volt Model does not have Tube Shields.

Only **\$14.22**

Short-wave receivers have come and gone, but never have there been produced short-wave receivers which have taken the entire country by storm as have the famous Doerle Receivers.

**And Now These Doerle Sets Have Been Completely Electrified**

Mr. Doerle described his first receiver, the now famous 2 TUBE 12,500 MILE RECEIVER in the Dec-Jan issue of *Short Wave Craft*, and his 3 TUBE SIGNAL GRIPPER in the Nov. 1932 issue.

If you are a reader of this magazine, you have undoubtedly been surprised at the great number of fan letters published in *Short Wave Craft*, praising these receivers to the skies—and for good reason! We have sold many hundreds of these sets, and they are still going strong.

They are low-priced, yet pull in short-wave stations from all over the world REGULARLY. In practically ANY LOCATION, not only in this country, but anywhere! These two receivers EMPLOY THE 2-VOLT, LOW-CURRENT CONSUMPTION TUBES, and are, therefore, most popular with people living in rural districts where electric service is scarce.

For the thousands of fans however, who enjoy the benefits of electric service, we have developed the 2 and 3 Tube A. C. Doerle sets. These sets, employing the latest type triple-grid tubes, are naturally more selective and infinitely more sensitive than the original Doerle receivers.

Furthermore, not only can they be used on alternating current, but with batteries as well. The 2 tube 12,500 Mile Electrified Doerle Receiver employs a Type 57 triple-grid detector tube, which is resistance-coupled to the type 58 output tube. For operation on batteries the 57 is replaced with a 77-tube and the 58 with a 37. This set actually works a loudspeaker on all local and many distant stations. The 3 Tube Electrified Doerle Signal Gripper employs a 58 triple grid tube as a radio-frequency amplifier, followed by a type 57 detector, and finally, a 58 output tube. For battery operation the Type 78, 77 and 37 tubes are used. This receiver, in its sensitivity and DX ability, equals many expensive 5 and 6 tube short-wave sets.

**Improved Circuit and Design**

Despite the remarkable performance of the Doerle receivers, our technical staff felt that they could obtain better results by making slight modifications of the circuit. This is especially true of the 3 Tube Signal Gripper, both the new A. C. and 2-volt models. In the 2-volt model, the first Type 30 R. F. tube was replaced by a type 34, which is a special-purpose screen-grid R. F. amplifier. In the A. C. model, a type 58 triple-grid, high-gain R. F. tube is employed. Furthermore, in this latter model the Antenna trimmer condenser has been eliminated through the use of inductive coupling. The detector plug-in coils are of the six-prong type, each having three separate windings. This means that the R. F. Stage is inductively coupled to the detector. Yet, despite these various changes, we have not increased the price of these receivers, to you.

By special arrangements with the publishers of *Short Wave Craft*, we have been given the exclusive right to manufacture and sell the Official Doerle Receivers, both the earlier 2-volt and the latest A. C. models—so that now, all short-wave enthusiasts who have ever wished to own any of these fine sets can buy them without the slightest doubt in their mind but what they will perform 100%. This means that all the usual "bugs" have been ironed out by us in such a way that in practically every location, anywhere, they will "do their stuff."


**Only First-Class Parts Are Used**

It may be possible to buy the parts or completed sets at a lower price—we admit this at once—but without concern. For we have used only the best parts available in the construction of our sets. We have done away with all usual "losses" which are incidental to the use of poor components. In these receivers, only the best tuning condensers, and that means Hammarlund—are used! These sets could be produced for a considerably less amount if we used cheaper condensers. We refrained from doing so, however, because they are **COULD NOT GUARANTEE RESULTS!** And this goes for everything else in these sets.

If you are skeptical of the results obtainable with these receivers, read the letters from our many short-wave fans and friends printed on the opposite page.

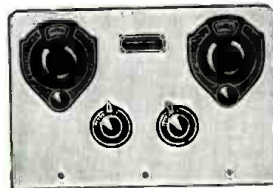**Our Own Tests**

Every one of these Doerle receivers, without exception, is tested in our laboratory under actual operating conditions. We refrain from giving you the astonishing list of stations which we, ourselves, have logged during the course of our tests; for we do not wish to let our enthusiasm run away with us! We would much rather have you and our many other short-wave friends talk about the results. Incidentally, we have yet to receive a single complaint on any of these sets although we have sold many hundreds of them. Each receiver is accompanied by schematic diagram and wiring blueprint, as well as a pamphlet of detailed instructions.



FRONT VIEW Showing general appearance of all Doerle receivers



2-Tube 12,500 Mile Doerle Set Rear View—Both A. C. and 2-Volt Models look alike

Only **\$8.88**

**SPECIFICATIONS**

- No. 2174. Electrified 2 Tube 12,500 Mile Doerle Receiver, completely wired and tested, less tubes. Measures 9" long x 6" high x 6 1/2" wide. Shipping wt. 5 lbs. **YOUR PRICE \$9.43**
- No. 2175. Electrified 2 Tube 12,500 Mile Doerle Receiver in kit form, less tubes, but including blueprints and instructions. Ship. wt. 5 lbs. **YOUR PRICE \$8.23**
- No. 2176. Complete set of tubes for above; either one—57 and one—58 for A. C. operation, or one—77 and one—37 for battery operation. **YOUR PRICE \$1.78**
- No. 2177. Electrified 3 Tube Doerle Signal Gripper, completely wired and tested, less tubes. Measures 10 1/2" long x 7" high x 8 3/4" wide. Shipping wt. 7 lbs. **YOUR PRICE \$14.18**
- No. 2178. Electrified 3 Tube Doerle Signal Gripper in kit form, including blueprints and instructions; less tubes. Ship. wt. 7 lbs. **YOUR PRICE \$12.73**
- No. 2179. Complete set of tubes; either one—58, one—57 and one—56 for A. C. operation or one—78, one 77—and one—37 for battery operation. **YOUR PRICE \$2.68**

**BATTERY SETS**

- No. 2140. TWO TUBE 12,500 MILE 2-VOLT DOERLE SHORT WAVE RECEIVER, completely wired and tested. Ship. wt. 5 lbs. **YOUR PRICE \$8.88**
- No. 2141. TWO TUBE 12,500 MILE 2-VOLT DOERLE SHORT WAVE RECEIVER KIT, with blueprint connections and instructions. Ship. wt. 5 lbs. **YOUR PRICE \$7.68**
- No. 2142. COMPLETE ACCESSORIES, including 2 No. 230 tubes; one set of Brandes Headphones; 2 No. 6 dry cells; 2 standard 45-volt "B" batteries complete, ship. wt. 22 lbs. **YOUR PRICE \$5.38**
- No. 2143. THREE TUBE 2-VOLT DOERLE SET, completely wired, ready to use. **YOUR PRICE \$11.83**
- No. 2144. THREE TUBE 2-VOLT DOERLE SET IN KIT FORM, with blueprint connections and instructions. Ship. wt. 7 lbs. **YOUR PRICE \$10.48**
- No. 2145. COMPLETE ACCESSORIES, including 2 No. 230 tubes; and one type 34, one set of Brandes Headphones; 2 No. 6 dry cells; 3 standard 45-volt "B" batteries; 1 B. B. L. 9 inch Magnetic Loudspeaker. Shipping weight 32 lbs. **YOUR PRICE \$10.98**


## FREE Short-Wave BOOKS YOUR CHOICE

of either one of books illustrated herewith—**FREE OF CHARGE**—with the purchase of any of the short-wave receivers listed in this advertisement.

Book No. 866 explains in a most thorough-going manner the ways and means of obtaining an amateur transmitting license. Furthermore, all government rules regulating amateur transmissions are reviewed. Book 830 is a comprehensive and thorough compilation of the most prominent short-wave receiver circuits published during a period of two years. Build up your radio library with one of these books.



Book No. 830

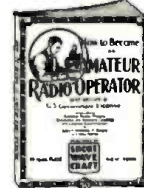

Book No. 866

**FREE** 116 page Summer Edition of Radio and Short Wave Treatise, 100 hook-ups, 1,000 illustrations. Enclose 4c for postage. Treatise sent by return mail.

### Special Short-Wave Hum-Free A. C. Power Pack

Designed Especially For The Doerle Receivers



**\$6.23**

Everyone knows that an A. C. short-wave set is no better than the power pack which supplies its power! A power supply for short-wave use must be constructed with extreme care. It must be absolutely free from hum or other disturbances caused by insufficient filtering, poor wiring, or faulty equipment.

This unit has a two-section filter circuit, employing two-heavy duty 30 Henry chokes and a tremendous amount of capacity. This assures PURE D. C. with practically no ripple at all.

The power pack supplies 250 volts at 50 ma. for the plates of the tubes, 22 1/2 volts for the screens, and 24 1/2 volts at 5 amperes for the filaments. These various voltages are obtained from convenient binding posts on the side of the pack. Furthermore, provisions are made for energizing the field of a dynamic speaker. Any speaker having a field resistance of from 1500 to 2500 ohms may be thus energized. All the component parts of this pack are built into a sturdy metal base which is black, crackle finished. The power transformer and one of the chokes are the only units which are mounted on top of the chassis. The pack employs a type 280 full-wave rectifier which is inserted in a socket on top of the base. A convenient on-off switch is mounted on the side. The pack is sold complete with four feet of connecting cord, terminating in a special Heiden soft rubber plug. Measures 7 1/4" long x 4" wide x 4 1/4" high overall. Sold complete with 280 tube. Ship wt. 10 lbs.

No. 2149 Special Short-Wave Hum-Free A. C. Power Pack, including 280 tube. **YOUR PRICE \$6.23**

**RADIO TRADING COMPANY, 100A Park Place, New York City**

# FREE

This Regular 50c Manual



Here is your chance to read up on ultra short wave radio! "Below Ten Meters" is by far the best compilation of technical data on the very short waves, which are now becoming increasingly popular and important. There are 98 pages, chock full of practical "do-it" diagrams and photos—all clearly presented in understandable form. Compiled and edited by those famous short wave experts, James Millen and Robert S. Kruse.

● **Given FREE** ●

This book is given to you absolutely free with a One Year Subscription to **SHORT WAVE CRAFT**. Twelve big issues which bring you an entire year's information on the latest developments in short wave radio. Your first copy of **SHORT WAVE CRAFT** will reach you in a day or two.

Send \$2.50 in check or money order for a year's subscription to **SHORT WAVE CRAFT**. Register letter if it contains stamps or currency. (Canadian and foreign 50c extra.)

**SHORT WAVE CRAFT**

96-98 Park Place New York, N. Y.

**HOT CHA!**

**1** WINDS LIKE A WATCH

**2** provides quick, easy filling by positive mechanical action.

**1,** reveals the ink supply at all times. Both conveniences no other pen affords. Ask to see—compare—the Nozac\* (no sack) when you shop for a sackless pen... \$5.00 and more.

**2,** reveals the ink supply at all times. Both conveniences no other pen affords. Ask to see—compare—the Nozac\* (no sack) when you shop for a sackless pen... \$5.00 and more.

Other Conklins \$2.75, \$3.50 and more. Pencils \$1 and more.

**THE CONKLIN PEN CO., Toledo Chicago San Francisco**

\*Proved by over 2 years of general public use.

**Conklin NOZAC**

REG. U.S. PAT. OFF.

**SATISFACTION GUARANTEED**

## Letters from S-W Fans

(Continued from page 303)

hundreds of "amateurs." The trouble was that I couldn't get any lower than forty meters. (This was probably due to the losses.)

I made up my mind to rebuild it. I got hold of a metal panel which helped to stop the "hand capacity." (I don't use the "Doerle extension bakelite shafts.") I made very short "leads," having learned my lesson that long connections don't pay. I built the set in two parts; one section containing the detector stage and first audio stage; the second is a second and third audio stage, *carefully matched and shielded!*

And boy, oh boy! Do the foreign stations come in now! I have held EAQ, Madrid, Spain, for two hours (5:00 to 7:00 EST) almost every day for about two months. G5SW and I2RO come in pretty fair (all loudspeaker reception). I am more than "satisfied" with the "Doerle circuit!" I am a 100% **SHORT WAVE CRAFT** booster. I haven't missed any of your magazines, since December.

I guess I have said enough (hi! hi!) so I'll say the best 73's to you and "diddle-de-bump-de-bump" as W9ARK says.

JOSEPH W. SEMKOW,  
3433 Seyburn Ave.,  
Detroit, Mich.

(Hi! Hi! yourself, Joseph. You've certainly dressed the "Doerle" up pretty and get mighty fine results too—we'll say. As becomes apparent from your letter, and as many other readers have found the Doerle regenerative tuning and detector circuit can sure "roll them in" up to 12,000 miles, and after that—well, as Ethel Barrymore puts it—"that's all there is, there ain't no more." So-o-o-o-o-o-o, the thing to do seems to be to use the "Doerle hook-up" and tune stations in; then with the addition of an extra audio stage as you have done, it's a cinch to put stations on the "loud speaker"—Editor.)

If the "Code test" were eliminated on phone transmission below six meters I would apply for such a license. I have tried to learn code about two years ago and became disgusted with it. About four months ago I tried it again but in vain. I can learn code and no doubt anyone can learn it, providing they devote enough time on that one subject, but who wants to spend all that time on something that is not used on phone transmission.

Many readers will agree with me when I say that everyone cannot master code in two months just as M. R. Rofajko claims he did (in the Feb. 1933 issue of **SHORT WAVE CRAFT**). Rofajko also states that if code were eliminated, inexperienced fellows would build transmitters and get on the air. If his statement were true inexperienced fellows would learn code, then build transmitters and get on the air. He probably does not know that if code were eliminated a person would still have to pass a test to prove his knowledge of the transmitting apparatus and as a person can prove that knowledge it will be proof enough he can operate a transmitter efficiently.

In my opinion it is easier to build a transmitter than it is to learn code.

The least that could be done about it is give it a tryout to see how things work out, and if things do not prove satisfactory the license may automatically become void after a certain date.

Joseph Zielinski,  
1637 Blackhawk Street,  
Chicago, Illinois

## The Tynmite

(Continued from page 281)

- C4—midget vernier—2 plate condenser; about 10 to 20 mmf.—Hammarlund (National).
  - C5—80 mmf. trimmer (Hammarlund) aerial condenser.
  - C6—.0002 mf. grid condenser; .0001 or .00015 may be used instead.
  - R1—2½ megohm grid-leak. Lynch (International).
  - R2—10 ohm fixed rheostat.
- L. S. Hoover, Tionesta, Pa.

## Short Wave League

(Continued from page 294)

enclosed I will promise to answer all that contains three cents.

Anyone keeping touch with F. R. C., I will certainly appreciate it if they will keep me posted as to when code-less phone licenses are legal on five meters and below. I would like to see more "fiction" articles. The December story sure was a dandy!

After I have read all the articles on receivers and transmitters, I like to rest my brain on a good short wave "fiction" story. I would like to see more letters from Texas hams; I am hoping some day to be on the air with a 5 meter phone transmitter. I will close hoping to hear from anyone who wishes to write.


Vivian D. Kinard,  
Big Spring, Texas

## Disgusted With Code

Editor, **SHORT WAVE CRAFT**:

Dear sir:

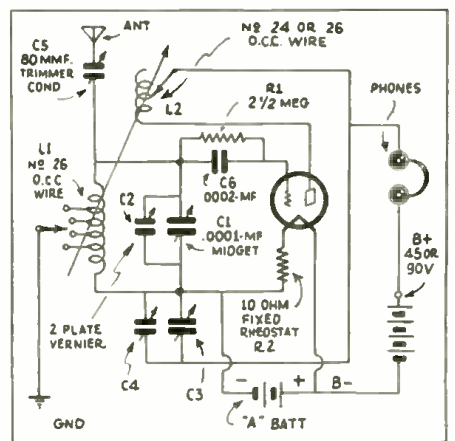Being a subscriber to *Radio Craft* and a newsstand buyer of **SHORT WAVE CRAFT**, I can readily state that you have the most interesting magazine for the experimenter and short-wave enthusiast.



Hook-up for the "Tynmite."

## The Pentaflex

(Continued from page 269)

- R1—Lynch 3 meg. metallized grid leak ½ watt
- R2—400 ohm tubular wire-wound pigtail resistor
- R3—50,000 ohm potentiometer
- R4, R5—Lynch .25 meg. metallized resistor. ½ watt
- L1, L2—Alden (Na-ald) plug-in coils (see text for details)
- 1—National type "BM" 3" dial (0-100-0)
- 1—National grid-clip, type 24
- 1—D. P. S. T. switch
- 1—Eby twin binding post assembly (laminated)

- 1—Eby twin speaker jack assembly (laminated)
  - 1—Eby laminated 7 prong socket, small (.75" pin circle diameter)
  - 1—Hammarlund 4 prong isolantite socket (S-4)
  - 1—6A7 or 2A7 tube
  - 3—FT, 5-conductor cable
  - 1—Roll Hook-up Wire
  - 1—Blau Aluminum panel, 14 Ga. 5"x7"
  - 1—Blau Aluminum panel, 14 Ga. 5"x5", bent to form 3"x5"x1" subpanel.
  - 1—Length varnished cambric tubing (spaghetti)
- Miscellaneous nuts, bolts, solder, etc.

## This 3-Tube Superhet Has "IT"

(Continued from page 275)

divider of 22,000 ohms, tapped at 12,000 ohms for the various screen voltages. The screen voltages are taken off the divider at a point 12,000 ohms from the high potential side of the resistor.

### Grid-leak Detection

Grid-leak detection is used in the 2A5 second detector tube because this method gave by far the greater audio output, a one megohm leak seems to be about right and can be of the one-half watt variety.

Modulation of the second detector for CW reception is obtained by hooking the detector screen-grid in parallel with the oscillator plate and fed through an R.F. choke from the 100 volt tap on the voltage divider. In order to get full audio output from the 2A5 detector, it is necessary to bypass the screen with a .01 mf. condenser. To prevent the output of the oscillator from getting into the radio frequency stage, the connection from the plate of the oscillator to the screen of the detector is run through flexible shielding; this shield should be grounded to the base of the receiver at several points to hold it firm. Should this shield be left loose and rub against the chassis, it would cause considerable scratching noise in the speaker.

The power from the output tube is fed to the speaker by an output transformer or a choke and condenser arrangement, according to the type of speaker used. The output transformer is an affair used to work on a pair of pentodes and has a 12 ohm secondary for use with a dynamic speaker, the center tap on the primary is unused; the plate is connected to one side and the B plus is connected to the other. If it is desired to use a magnetic speaker this can be done by connecting one side of the speaker through a 1 mf. condenser to the plate of the tube, and the other speaker lead to the chassis; this keeps the high plate current of the tube out of the speaker or phones, should one wish to use them.

### Beat Oscillator Details

Last but not least, is the beat oscillator, used mostly for code reception and this unit can be left out of the set if the builder is interested only in short wave broadcast (phone) reception. The tuning unit of the


beat oscillator is a home-made affair and can be constructed very easily. The entire unit is inclosed in a shield-can measuring 2½ inches in diameter and 3 inches high. A general idea of the construction and assembly of this can be seen by glancing at the photograph. It is not advised to try and wind the coil because it could not be made small enough to fit in the shield with all the other parts. The easiest way is to "buy, beg or borrow" a universal-wound coil of the same value as that used in the "IF." transformers; unwind about twenty or twenty-five turns and tie a loop in the wire and start to rewind, or, wind back the turns removed, keeping the loop which forms the cathode tap "out in the clear." The tap should be about five or six inches long. This coil, the 100 mmf. fixed tank condenser and the 100 mmf. grid condenser and grid-leak are all mounted on a Hammarlund 35 mmf. midget tuning condenser. The whole assembly is then mounted in the shield can, with the shaft of the tuning condenser projecting through the shield; in fact the condenser is mounted in a hole in the center of the can, being a single-hole mounting condenser.

Bring the grid lead out the top of the can on the rim, so that the operation of the knob will not interfere with or disturb it. This lead by the way should be shielded and the shield can grounded also. No switch is shown for shutting off the oscillator, but can be added if desired. The operation in the receiver shown is to turn the oscillator out of resonance with the IF. frequency when the oscillator is not desired, and back again when needed.
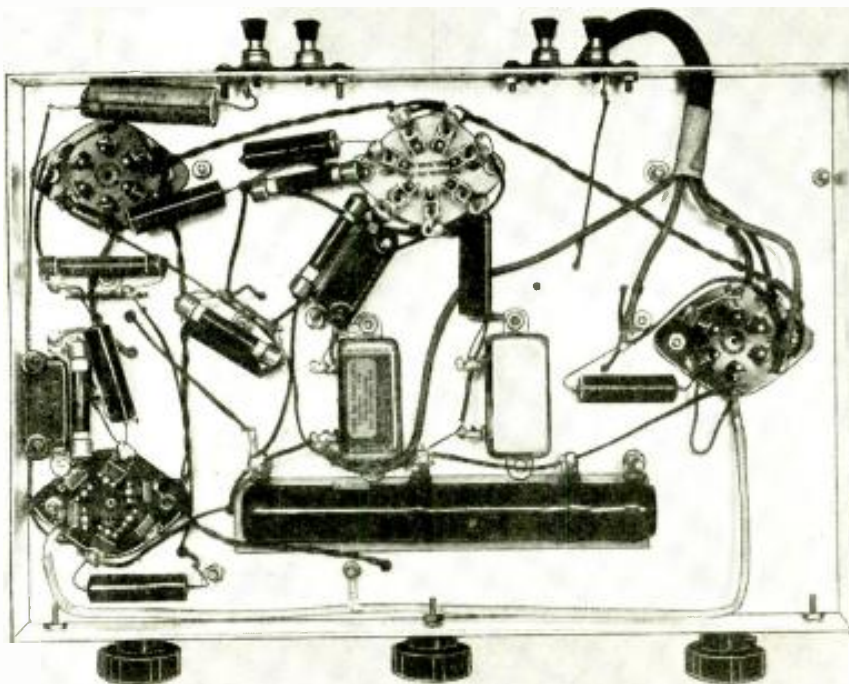
### Hints On Operating Set

Operation and adjustment of this little set is very simple and requires very little experience. If the following explanation is followed carefully no difficulty should be had in getting the set to "perk" right off.

Check all wiring before any voltages are applied, to make certain no error has been



Bottom View of Mr. Shuart's 3-Tube Superhet.

## WORLD'S FINEST PHOTO-INSTRUMENT



In all the  
WORLD  
No Other  
CAMERA  
Like This!

The only Quick-Acting, Automatic Winding, Ground Glass Focusing Camera using Standard Roll Film. Good for all purposes. No Separate Parts or Attachments are Necessary!

No Double Exposures with "PAL KO!"  
It THINKS and COUNTS for you.

Used by Government Educational Experts and leading Publications. Simple! Positive! Dependable!  
3 Cameras in One! "PAL KO" takes full postcard 3A, or ½ or ¼ this size—19 pictures on a 6 exposure film!

SAVINGS ON FILMS ALONE WILL SOON PAY FOR "PAL KO"

SATISFACTORY PERFORMANCE GUARANTEED OR MONEY REFUNDED!

SOLD DIRECT "FROM MANUFACTURER TO YOU."

WRITE TODAY FOR FREE CATALOG.

**PAL KO Inc.**

819 Wash. Blvd. CHICAGO Dept. S-C

## SLIDE RULES • •

### Midget 5in1 Circular Type:



Metal 4" Dia.  
Price \$1.50  
Case 50c extra

1.23<sup>3</sup> = ? √50.41 = ?  
1.24<sup>5</sup> = ?  
Tan 8°5' = ?  
Cot 79½° = ?  
4½ × ⅓ = ?  
Log 56.25 = ?  
6% of 145.9 = ?  
5.16 - ⅔ + 1.78 = ?

Solve easily all these and dozens of other mathematical problems without pencil and paper—by means of the Midget Slide Rule. This rule solves any problem in multiplication, division, addition, subtraction, and proportion. It also gives roots and powers of numbers. The "Tig" scales give the sines, cosines, tangents and cotangents of all angles; also logs of numbers. Adds and subtracts fractions. Approved by colleges.

### RADIO Slide Rule Short Wave Type

Price 75 cts.

Printed on white bristol board. Size 7¼". Every short wave and radio student must have this inductance, capacity, and "coil-timeness" slide rule. It will answer such questions as: What is inductance of coil one inch in diameter, winding two inches long and having 20 turns per inch? What winding length of No. 24 S. C. C. wire must be put on a form two inches in diameter, to obtain an inductance of 100 microhenries? To what frequency and wavelength will 35 microhenry coil tune with a 50 mmf. condenser?



Dataprint Co., Box 322, Ramsey, N. J.

## SEXOLOGY

MAGAZINE

SEXOLOGY, foremost educational sex magazine, is written in simple language and can be read by every member of the family. It is instructive, enlightening—not a risqué book—contains no jargon. Devoted to Science of Health Hygiene. Contains 18 important articles, Questions and Answers, Book Review—68 pages with attractive two-colored cover. Here are a few articles: Neuter Approach to Sex Discussion; Sexual Misadjustment of Life and Marriage; Fidelity and Impotence. Get a copy of SEXOLOGY at any news-stand or send 25c in stamps for copy of current issue. SEXOLOGY 23 West Broadway New York, N. Y.

# 89¢ SALE!

of VALUABLE REFERENCES for HOME, OFFICE and SCHOOL

Postage 11c per book. Postage FREE if 5 books are ordered. (Formerly \$1.50 to \$7.85)

**A Genuine Friend in Need!**  
**89¢**  
Special



Right at your finger-tips are instant answers to every question. Get the book! . . . Look up in the index! A bad cold? Feel bad all over? Stomach upset? Feel tired, run down? Here you find out what's the matter, what to do in ordinary illness; how to treat until Doctor gets there in serious cases. In half a million American homes this New Home Medical Adviser is a daily guide, counsellor and friend. It is kept handy beside atlas, dictionary, almanac, Bible and other references so everyone can quickly refer, read, learn, understand and KNOW. Sixteen medical specialists here in 1 handy book. The leading home medical authority for 25 years. Authentic, proven, newly revised and up-to-date on latest medical practice.

### How to Diagnose and Treat:

Anemia, Heart Trouble, Diarrhea, Billiousness, Indigestion, Worms, Nervous Debility, Gout, Delirium Tremens, Nervous Collapse, Insanity, Apoplexy, Colds, Toothache, Diphtheria, Heat Stroke, Food Poisoning, Earache, Rheumatism, Lumbago, Stiff Neck, Hives, Itching, Rupture, Piles, Tumors, Typhoid Fever, Malaria, Smallpox, Vaccination, Erysipelas, "Pink Eye," Deafness, Earache, Measles, Sex Hygiene, Gonorrhea, Syphilis, Sexual Functions, Abuse, Duties of Parents, Marriage Relations, Bright's Disease, Puberty, Menstruation, Leucorrhoea,

Childbirth, Children's Diseases, Croup, Bowlegs, St. Vitus' Dance, Personal Hygiene, Skin, Hair, Teeth, Diet, Home Exercises, Rest, Weight and Height, Emergency Treatment for Burns, Fractures, Bites; Lightning Stroke, Sunstroke, Poisons and all Accidents.

**1. NEW HOME MEDICAL ADVISER.** 472 pages. Fully illustrated, many in color. Full-page body charts. Well bound gold stamped, size 5 1/2 x 7 1/2. Complete in 1 handy vol. (Formerly in 4 vols., \$6.) **89¢**  
Our Bargain Price (postage 11c extra).....

**2. FAMOUS WOMEN.** When Cleopatra bore Caesar a son! Curious and hitherto unknown facts at last revealed in these 498 short biographies of famous (and infamous) women, Semiramis to Mary Pickford. 328 pages. 32 full-page portrait illustrations. (Formerly \$3.) Our Bargain Price **89¢**  
Price (postage 11c extra).....

**3. GRAPHOLOGY, or, Character Analysis** through Caesar a son! Curious and hitherto unknown facts at last revealed in these 498 short biographies of famous (and infamous) women, Semiramis to Mary Pickford. 328 pages. 32 full-page portrait illustrations. (Formerly \$3.) Our Bargain Price **89¢**  
Price (postage 11c extra).....

**4. THE SECRET OF GOLD,** By Robert Collier, world-renowned writer and teacher of practical psychology. How to realize Money by easy psychology methods. Anyone can read, use, learn and benefit. (Formerly 7 vols., \$7.85.) Same text now in 1 vol. Bright red artcraft, handsomely embossed. Our Bargain Price (postage 11c extra)..... **89¢**

### FREE BOOK WITH EVERY ORDER

While our 236 copies last, we will include in your shipment without extra charge 1 copy of "The Winning Principle of Success" (value \$1). Rush order to make sure of getting this free book. POSTAGE FREE if you order 5 books (\$4.45 worth). Stock up NOW for season's entertainment and study. Mail this coupon TODAY!

SCIENCE PUBLICATIONS, 94 S. PARK PLACE, NEW YORK, N. Y.

Please send me the books I have circled below for which I enclose \$..... to cover purchase price and postage. I understand that my money is to be refunded on any unsatisfactory purchase.

1    2    3    4    5    6    7    8    9    10

Name.....

Address..... City..... State.....  
(POSTAGE FREE if 5 or more books are ordered. Otherwise include 11c per book postage with remittance.)

# The Mayflower

PLYMOUTH



On the Ocean at Manomet Point  
One of New England's Finest Resort Hotels

## Surprisingly Inexpensive

Special Vacation Tour 9 days \$60.00 up including transportation, Hotel accommodations, sight seeing, etc. Smooth Sandy Beach . . . Surf Bathing . . . Warm Sea Water . . . Swimming Pool

Tennis Courts . . . Golf Course . . . On Hotel Grounds

UNDER SAME MANAGEMENT  
MAYFLOWER HOTEL  
HYANNIS

CAPE COD'S NEWEST HOTEL  
CHARLES A. DOOLEY, MGR.

# CAPE COD

in MASSACHUSETTS



made in connections and that all have been soldered firmly. Then apply filament and "B" voltages and connect a pair of phones to the out-put terminals; all adjustments should be made using phones. Set the condenser across the plate coil of the first IF transformer at about half capacity. Then start up some "noise-producing" electrical instrument such as a buzzer or vacuum cleaner, near the set and proceed to adjust the other IF tuning condensers for maximum volume. When this stage has been reached, tune the beat oscillator condenser until a slight hissing sound is heard in the phones, this indicates that the oscillator is in tune with the IF frequency; then proceed to locate some kind of short-wave station. Of course the noise-generator has to be shut off at this point. When a station is once located then adjust the IF trimmers until full efficiency or loudest signal has been reached. During this adjustment however, the condenser in the plate circuit of the first IF transformer should not be touched unless the frequency of the IF unit is to be changed. This is mentioned because the adjustment of this primary tuning condenser has a decided effect on the high frequency oscillator frequency, and will most certainly result in maladjustment. Therefore do all adjusting with the other three IF condensers unless the intermediate frequency is to be changed.

### Coil Winding Table

Make two of the following

COIL	Tickler or antenna	GRID
No. 1	4 turns No. 34 wire	5 turns No. 28 wire
No. 2	5 turns No. 34 wire	10 turns No. 28 wire
No. 3	8 turns No. 34 wire	24 turns No. 28 wire
No. 4	10 turns No. 34 wire	45 turns No. 28 wire

All coils close-wound, Diameter of form 1 1/2 inch. The above coils cover all of the popular S. W.-broadcast and Amateur bands.

Any standard commercial SW coils will work if designed for 100 mmf. condensers. Otherwise change tuning condensers to match coils that are designed to work with 150 mmf. condensers.

Spacing between grid coils and tickler or antenna coil is 3/4 inch.

### Parts List—Shuart 3-Tube Superhet

- 1—8x12x1 Inch Chassis 1/16 in. Blan.
- 1—7x12 Inch Panel 1/16 in. Blan.
- 1—drum dial—National.
- 1—100 mmf. Variable Condenser, Clockwise, National—270°
- 1—100 mmf. Variable Condenser, Counter Clockwise, National—270°.
- 2—35 mmf. Variable Condensers, Hammarlund.
- 8—5 Prong coil forms, small Hammarlund.
- 2—National Isolantite sockets (5 prong).
- 1—National Isolantite sockets (7 prong).
- 2—National "Airtuned" IF. Transformers.
- 3—Tube shields, Hammarlund.
- 3—6 prong tube sockets, wafer, Eby.
- 2—.5 MF. Bypass condensers.
- 1—.5 MF. Bypass condensers.
- 7—.01 MF. Bypass condensers.
- 3—.0001 MF. Mica grid cond.
- 1—22,000 ohm voltage divider, tapped at 12,000.
- 2—100,000 resistors—1 watt, Lynch (International).
- 1—20,000 resistors—1 watt, Lynch, (International).
- 1—300 ohm resistors— 1 watt, Lynch (International).
- 1—250 ohm resistors—1 watt, Lynch (International).
- 1—1 meg. resistor—1 watt, Lynch (International).
- 1—20,000 Volume control, Acratest.
- 1—Antenna-Ground binding post strip, Eby.
- 1—Speaker binding post strip, Eby.
- 1—4 wire cable.
- For "Beat Oscillator tuning unit, see text."
- 1—2A7 or 6A7 tube, Gold Seal.
- 1—2A5 or 42 tube, Gold Seal.
- 1—58 or 78 tube, Gold Seal.
- 1—57 or 77 tube, Gold Seal.

# Velocity . . . The Latest Microphone

(Continued from page 287)

phragm. When these waves strike the diaphragm the voice coil attached to it vibrates in a strong magnetic field, supplied by permanent or electro-magnets, and generates a very small E. M. F. This current is suitably amplified much in the same manner as in the case of the condenser microphone, previously described, by two or more stages of amplification.

Referring to Fig. 1, the output level of the average dynamic microphone is greater than that of the condenser, but lower than that of the carbon. The pre-amplifier is therefore necessary to bring it up to the output level of the carbon. Its frequency response does not differ very much from that of the condenser, inasmuch as this microphone belongs to the same group, namely the pressure type, which employs a diaphragm as the varying element.

The main advantage over the other type is the fact that the dynamic is impervious to average climatic conditions and does not have to be placed in proximity to the pre-amplifier; in fact, if the proper transformers are used, it can be placed even one hundred feet away.

Its construction, however, requires such precision as to render it far out of the reach of the amateur.

## The Velocity Mike

The velocity type, the latest addition to the microphone family, embodies a different principle, which while not new in itself, has been only recently introduced in America.

The velocity or ribbon microphone is essentially an electro-dynamic device. It consists of a very thin corrugated aluminum ribbon suspended in a strongly magnetic field produced by electro- or permanent magnets. The sound waves striking the ribbon will cause it to vibrate, thus generating a small E. M. F., which when properly amplified, will perform as previously described.

The absence of a stretched diaphragm makes this microphone respond very faithfully to frequencies varying from 30 to 16,000 c. p. s. (cycles per second.)

By referring to Fig. 1, it will be noted that the curve is remarkably flat, sloping in a gradual way down to 16,000 c. p. s., and is free of any resonance peak. Its output is far below that of the carbon "mike"; in fact it ranks last, yet no more than two stages of amplification are necessary to bring it up to the necessary sound level.

Its sensitivity is controlled by the thickness, width and length of the ribbon. Another factor is the intensity of the magnetic field. Its remarkable frequency response is due to the proper corrugation, tension, and texture of the ribbon, which

requires various temperature treatments. Commercial velocity microphones employ ribbons two-tenths of one thousandth of one inch thick (.0002"). If you stop to consider that the average human hair is fifteen times as thick, you will realize that an aluminum ribbon of this thickness would be almost impossible to handle, unless it was hardened by some process. Good results, however, are obtained with ribbon .0006" thick, which is the standard size of an excellent ribbon microphone recently placed on the market for amateur use.

Thicker ribbons make the microphone sluggish and insensitive. Soft aluminum ribbons will soon lose their elasticity and become useless.

Figure 4 illustrates a typical velocity microphone of excellent design which is fast becoming popular in the amateur and public address fields.

## Velocity Mike Is Directional

The velocity microphone is decidedly a directional one. Its pick-up range is much narrower than the other three types. As a matter of fact, it is absolutely insensitive to sound generated 90 degrees to either face. This quality is very desirable in motion-picture work, where the noise of a camera located in the same plane of the microphone will not be picked up by the microphone.

Another very important feature produced by the inherent directional quality of the ribbon microphone is the absence of feedback, so troublesome in public address work.

These microphones require the use of a special low-impedance transformer to match the impedance of the ribbon. The design of this transformer is as important as the microphone itself and inasmuch as the impedance varies with the size of the ribbon, it is essential—for a perfect match—to determine the exact impedance of the ribbon before purchasing a transformer; or it is advisable to obtain at least the assurance of the manufacturer that a certain transformer will match a particular type of velocity microphone.

By the use of another transformer at the amplifier, it is possible to place the pre-amplifier away from the microphone. This distance can be over one hundred feet without serious losses. If it is desired to have the pre-amplifier near the microphone, a different type of transformer is to be used. Figure 5 shows the two methods of connecting a velocity microphone to a standard pre-amplifier.

A careful analysis of the facts stated above should not give the impression that any one of the microphones described is, in a general way, better than the other.

Each one will perform better than the

(Continued on page 311)

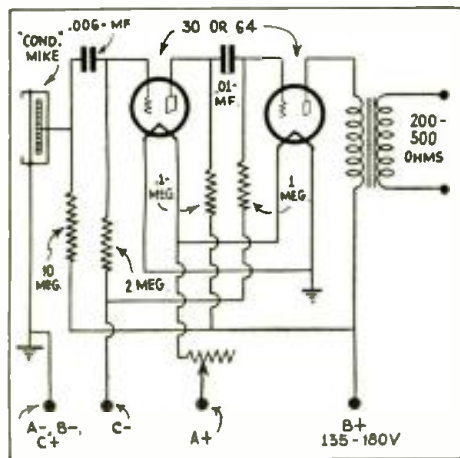


Fig. 2  
Condenser "mike" pre-amplifier

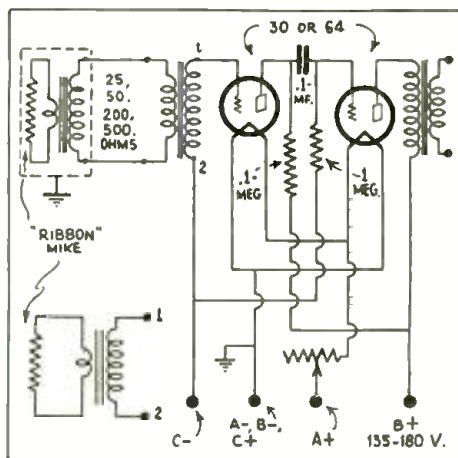


Fig. 3  
Ribbon "mike" pre-amplifier

**BARGAINS ON ARMY and NAVY RADIO SURPLUS**

An ideal combination for the experimenter and Amateur learning the code. This head-phone receiver and Transmitting Key.

**ARMY HEADPHONE RECEIVER**  
100 ohm ..... \$7.75  
Transmitting key, army air corps. Silver & " contacts, with blinker light. Reduced to ..... \$1.50

**EDISON STORAGE BATTERIES**  
All Types—1.2 Volts per Cell

A-4	Amps. 175	Per cell	\$3.00
A-6	Amps. 225	Per cell	4.00
A-8	Amps. 300	Per cell	5.00
B-4	Amps. 90	Per cell	2.50
M-8	Amps. 11	Per cell	1.00
L-40	Amps. 25	Per cell	1.50
J-3	Amps. 37	Per cell	1.00

Special Buy on Western Electric's Army with adjustable telephone contacts. (Capable of controlling a local circuit with a very low primary consumption (6-volt battery), only a few left. Special \$3.50 WHITE FOR OUR BARGAIN BULLETIN

**MANHATTAN ELECTRIC BARGAIN HOUSE**  
105 Fulton St. Dept. 5 N. Y. City

**FORDSON presents**  
**RADIO'S BIG VALUE**

Nothing like it! 6-tube  
**Goldentone**

Gets police calls has automatic volume control with new duplex diode, triode 55 tube; has tremendous power, no hum or distortion, with Class A type 2A5 tubes; full range tone control; full size dynamic speaker; full vision spotlight control. Fully selective and sensitive—easiest to coast reception. A full-size radio in every way. "Outperformed 12-tube set in every way."—J. L. A. Adkins, W. Va. Complete with beautiful midget cabinet and 6 Raytheon tubes \$13.85. GUARANTEED. Send today for free circular. (Know the newest in auto radio—the "FORDSON" sensation!)

**30 DAYS FREE TRIAL**  
6-tube chassis & Dynamic Speaker  
**\$9.95**

**FORDSON RADIO MFG. CORP.**  
11703 Livernois Ave. Detroit, Mich.

**YOU GET THERE!**  
with **RCA Institutes** radio training

No matter what you want to learn in practical radio . . . whether you desire elementary or advanced knowledge . . . RCA Institutes is fully prepared to give you the training.

**RESIDENT SCHOOLS NEW YORK AND CHICAGO**  
Illustrated Catalog on Request  
**EXTENSION COURSES FOR HOME STUDY**  
under convenient "no obligation" plan.

**R.C.A. INSTITUTES, INC.** Dept. SW-9  
75 Varick Street, New York  
1154 Merchandise Mart, Chicago

**REAL RED HOT BARGAINS!**

Slightly used 845's and 211's, guaranteed, each ..... \$7.95  
25-WATT tubes, with new thoriated filament ..... 4.25  
Have 18 watt 210, 90-day guaranteed ..... 1.30  
CG-1162, New Navy 5-wattors, 25c each, per dozen ..... 1.00  
New SUPREME Model 45 tube tester, our special ..... 29.50  
New SUPREME Model 233 set analyzer, our net ..... 39.50  
Weston Model 301 milliammeter, almost like new, all ranges, special for this month only, each ..... 3.75  
Licensed LOFTIN WHITE Portable Public Address Amplifier—have output of about 4 watts ..... 6.95  
Sonicorde "d" dynamic speaker, matched, for above ..... 3.95  
Output transformer for above amplifier, only ..... .95  
NATION AL SW145, complete with 4 sets of coils, tubes and power pack, our net special ..... 43.75  
GYPSY Auto Radio, 6-tube, uses latest type tubes with mounting brackets and cables (less accessories and speaker) WHILE THEY LAST ..... 9.95

LET US GIVE YOU OUR CONFIDENTIAL PRICES ON THE NATIONAL PB-7, SW-3, and the HAMMARLIND COMET PRO RECEIVERS. BARGAINS GALORE! SEND FOR OUR FREE HAM SHEET!

**UNCONDITIONAL GUARANTEE ON ALL OUR RADIO SUPPLIES**  
**UNCLE DAVE'S**  
RADIO SNACK  
135 BROADWAY-ALBANY, N. Y., U.S.A.

# CAMERA and COMPLETE OUTFIT 35¢

(Add 10c for postage and packing)


Take and make your own pictures

Brilliant View Finder  
Good Quality Lens

Developing and Fixing Chemicals  
4 Films

1 Package Printing Paper  
1 Printing Frame

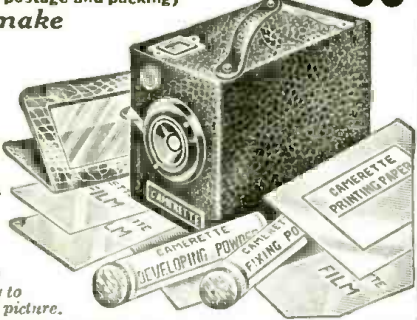Everything necessary to turn out the finished picture.



**ALSO HOW MARVELOUSLY CHEAP.** It is quite efficient, and will take **SPLENDID PICTURES.** Just the thing for beginners in photography. It takes pictures not quite 2 x 1 1/4 inches with clearness, sharpness and distinctness. Loads and unloads in daylight. Has a **VERY GOOD LENS.** **BRILLIANT VIEW FINDER.** A simple yet effective **SHUTTER,** time and instantaneous, leatherette handle. Comes complete with **4 FILMS.** 1 package of **PRINTING PAPER,** a neat little **PRINTING FRAME** with glass top, and **SUPPLY OF CHEMICALS** for developing, fixing and turning out the finished picture. Full printed instructions so plainly written that a child cannot fail to understand. Never before has such an inexpensive opportunity been offered of indulging in the fascinating art of photography. With this outfit you can take portraits of your friends, views of places of interest you may visit, and snapshots of curious events and quaint characters. **CAMERA AND COMPLETE OUTFIT ONLY 35¢** with 10¢ extra for postage. **EXTRA FILM 10¢** per package of 5 Films. **EXTRA PRINTING PAPER 10¢** per package.

# BOYS! THROW YOUR VOICE

Into a trunk, under the bed or anywhere. Lots of fun fooling teacher, policeman or friends.



# THE VENTRILO

a little instrument, fits in the mouth out of sight, used with above for Bird Calls, etc. Anyone can use it. Never fails. A 16-page course on Ventriloquism and the Ventrilo. All for 10¢ postpaid.

# LUMINOUS PAINT

**Make Your Watches, Clocks, Etc., Visible by Night**

The very latest discovery in the scientific world. Hitherto, practically unobtainable. **LUMINOUS PAINT,** which, applied to the surface of any article, emits rays of white light, rendering it perfectly visible in the dark. **THE DARKER THE NIGHT, THE MORE BRILLIANT IT SHINES.** Quite simple to use. Anyone can do it. A little applied to the dial of your watch or clock will enable you to tell the time by night. You can coat the push buttons or switch plates of your electric lights, match boxes, and innumerable other articles; make your own Luminous Crochets, Luminous Rows, etc. Full instructions sufficient to make several small articles. Price 25¢. Larger size 50¢ and \$1.00 postpaid.

# BIG ENTERTAINER


180 Jokes and Riddles. 34 Magic Tricks, 15 Parlor Games, 73 Toasts, 15 Tricks with Cards, 50 Money-making Secrets, 10 Funny Readings, 3 Monologues, 21 Puzzles and Problems, 5 Comic Recitations. Cut-outs for Checkers and Chess, Dominoes, Fox and Geese, 9 Men Morris, Spanish Prison Puzzle, Game of Anagrams, etc. All for 15¢ postpaid.

ONLY 10c Per Pair


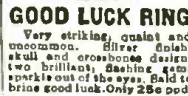
# Fighting Roosters

With very little practice you can make these miniature models of Game Roosters imitate in the most life-like manner the evolutions of a FIERCE COCK-FIGHT. Endless amusement. Well made, with real feathers. Pair 10c. 3 prs. 25c. Postpaid.



# GOOD LUCK RING

Very striking, quaint and uncommon. Silver finish; two brilliant, sparkling stones; sparkles out of the eyes. Said to bring good luck. Only 25¢ postpaid.



# PLAY PIANO IN ONE HOUR

With this new **VAMPING BOARD.** No teacher needed. Surprisingly simple. Place the **Vamping Board** upright over the piano keys, and vamp away to thousands of songs, ballads, waltzes, fox trots, rag-time, etc. No knowledge of music required. After using a few hours, the Board may be disposed of with entirely. Price 15¢ Postpaid.



# LEARN TO HYPNOTIZE

This book tells how. Explains all about Hypnotism, how to hypnotize, how to produce sleep, how to awaken a subject, how to hypnotize animals, hypnotism in diseases, etc. ONLY 10c postpaid.



# TELL YOUR OWN FORTUNE

With the aid of this dream book and fortune-teller. Will you be lucky in love? Successful in business? Will you be wealthy? Complete with dictionary of dreams with descriptions and correct interpretations, with lucky numbers, fortunate days, oracles, divination, palmistry, etc. Price 10c p. pd.



# FORTUNE TELLING BY CARDS

64 page book tells how. Gives the meaning of each and every card, how to deal and lay them out. Everything explained in simple language. 10c postpaid.




# PERFORMING SKELETON

A jointed figure of a skeleton 14 in. in height, will dance to music and perform various gyrations and movements while the operator may be some distance from it. Price 10c. 3 for 25c. pd.


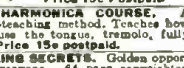
# HOW TO PITCH

Book contains lessons by leading pitchers, written in simple language. 56 illustrations. 25c postpaid.



# 125 CARD TRICKS

and sleight of hand. Contains all the latest and best card tricks as performed by celebrated magicians, with exposure of card tricks used by professional gamblers. Price 25c postpaid.

# SOLAR TELESCOPE—\$1.25 NEARLY 3 FEET LONG



The new Excelsior Solar Telescope is a large and serviceable instrument, nicely made and accurately fitted. When extended it is almost three feet in length, and when closed measures not quite twelve inches in length. Telescopes of this size usually sell for many times this price, but by importing them direct from a large European manufacturer, we are enabled to offer them to our customers for **ONLY \$1.25 each**, at which price they ought to sell readily. The lenses are well made, the sides are brass bound, and the four sections are perfectly fitted. Here is your chance to obtain a Telescope for a nominal sum. It will be sent postpaid to any address upon receipt of \$1.25 in any convenient form. Postage stamps accepted if more convenient. **770 page Catalog of novelties, tricks, jokes, sporting goods, firearms, jewelry, novelties in seeds and plants, etc., 10c.**

# BLANK CARTRIDGE PISTOL

Protection against Burglars, Tramps & Dogs



Well-made and effective; modelled on latest type of revolver; appearance alone is enough to scare a burglar. When loaded it may be as effective as a real revolver without danger to life. It takes standard 22 Cal. Blank Cartridges obtainable every where. Price 50¢. Superior quality, \$1.00. Blank Cartridges, 60¢ per 100. Holster (Cowboy type) for Blank Cartridge Pistol, 50¢. Shipped by Express only.

# LOOK 35¢ LOOK WONDERFUL INSTRUMENT

Greatest thing yet. Nine separate articles in one. Everybody delighted with it. Odd, Curious and interesting. Lots of pleasure as well as very useful. It is a double microscope for examining the wonders of nature. It is also an Opera Glass, a Spectacles, a Burning Glass, a pocket Mirror, and a LARYNGOSCOPE for examining eye, ear, nose and throat. It is worth all the cost to locate even one painful cinder in the eye. Folds flat and fits the pocket. Something great—you need one. Don't miss it. Sent by mail. Only 35¢ or 3 for \$1.

# Electric Telegraph Set 15c

Here you are boys! A private electric telegraph set of your own for 15¢! Lots of fun sending messages to your friends. Get two sets, hook them up as shown in the directions, for two-way messages for sending and receiving. No trouble at all to operate with the simple instructions that accompany each set. Operates on any standard dry battery obtainable everywhere. With this outfit you can learn to transmit and receive messages by the Morse International Code, and in a very short time become an expert operator. Mounted on wooden base measuring 4 1/2 inches. First class construction throughout, complete with key, sounder magnet, miniature Western Union blank, packed in a neat box with all illustrated instructions—ALL FOR 15¢ POSTPAID.

# PISTOL CIGARETTE CASE

It looks like a deadly weapon, but it is merely a novel Cigarette Case. This clever contrivance has proved itself better than the real thing in many an awkward encounter. Great fun "sticking up" your friends. They squirm and protest it might be loaded. Pull the trigger and the slide flies open disclosing the cigarettes. Well made, light and compact. Weight only 2 ounces. Price 25c Postpaid.

# NOVELTY FRENCH PHOTO RING

A classy looking ring, with imitation platinum finish, set with large imitation diamond. In the Shank of the ring is a small microscopic picture, almost invisible to the naked eye, yet is magnified to an almost incredible degree and with astonishing clearness. There are pictures that should suit all tastes, such as bathing girl beauties, pretty French actresses in interesting poses, also views of places of interest in France, Panama Canal and elsewhere; others show Lord's Prayer or Ten Commandments in type. State wishes and we will try and please you. PRICES 25c, 3 for 65c, or \$2.25 per doz. postpaid. Add 10c for 770 page catalog. Shows many other photo novelties. The world's greatest assortment of novelties, jokes, tricks, puzzles, etc. No other catalog like it anywhere.

# MAKE YOUR OWN RADIO



Enjoy the concerts, baseball games, market reports, latest news, etc. This copy-righted book "EFFICIENT RADIO SETS" shows how to make and operate inexpensive Radio Sets, the materials for which can be purchased for a mere trifle. Also tells how to build a short-wave Receiver for bringing in foreign stations, police calls, ships at sea, etc. Only 15¢. postpaid.

# SILENT DEFENDER

Used by police officers, detectives, sheriffs, night watchmen and others as a means of self-protection. Very effective. Easily fits the hand, the fingers being grasped in the four holes. Very useful in an emergency. Made of aluminum they are very light, weighing less than 2 ounces. Handy pocket size always ready for instant use. PRICE 25¢ each, 2 for 45¢ postpaid. Catalog 10¢.

# WONDERFUL X-RAY TUBE

A wonderful little instrument producing optical illusions both surprising and startling. With it you can see what is apparently the bones of your fingers; the lead in a lead pencil, the interior opening in a pipe stem, and many other similar illusions. Price 10c, 3 for 25c.

# Expanding Matches

More fun than fighting with your fists. They look just like ordinary matches but explode with a loud bang when lit. 22 matches in a box. PRICE 10c per box, 3 boxes 25c, or 75¢ per doz. boxes. Not available. Shipped by Express only.

# ITCHING Powder

This is another good practical joke the intense discomfort of your victims is thoroughly enjoyable. All that is necessary to start the itching is to deposit a little of the powder on a person's hand and the powder can be applied upon to do the rest. The result is a vigorous scratch, then some more scratch, and still more. 20 boxes, 3 boxes for 25c or 75¢ per doz. Shipped by Express.

# ANARCHIST BOMBS

One of these glass vials dropped in a room full of people will cause more consternation than a hamburger cheese. The small entirely disappears in a short time. 20 boxes, 3 boxes for 25c, 75¢ per doz. Boxes, or 75¢ per doz. Boxes. Shipped by Express. Not Prepaid.

# SNEEZING POWDER

Place a very small amount of this powder on the back of your hand and blow it into the air, and watch them sneeze without knowing the reason why. It is most amusing to hear their remarks, as they never suspect the real source, but think they have caught it one from another. Between the laughing and sneezing you yourself will be having the time of your life. For parties, political meetings, car rides, or any place at all where there is a gathering of people, it is the greatest joke out there. Price 10c, 3 for 25c, 75¢ per doz. Shipped by Express. Not Prepaid. 770 page Novelty Catalog 10c.

# COMICAL MOTTO RINGS

Lots of harmless fun and amusement wearing these rings. Made in platinum finish (to resemble platinum) with wording on enamel, as illustrated. Price 25c. ea. Postpaid.

# MAGIC MADE 250 EASY TRICKS

An excellent little book containing 250 easy magic tricks, tricks with beads, coins, handkerchiefs, eggs, rings, etc. So simple that a child can perform them. Profusely illustrated. Sent postpaid to any address for only 10c. 3 copies for 25c. Postpaid.

**LATEST CATALOG**  
**JOHNSON SMITH & CO.,** Dept. 989, Racine, Wis.  
A copy of our NEW CATALOG mailed on receipt of 10c, or the De Luxe Edition with cloth binding 25c. Bigger and better than ever. Only book of its kind in existence. Nearly 800 pages of all the latest tricks in magic, the newest novelties, puzzles, games, sporting goods, rubber stamps, unusual and interesting books, curiosities in seeds and plants, etc., unobtainable elsewhere. Remit by Cash, Money Order, Check or unused U. S. Postage Stamps, for all articles listed above. Canadian money-stamps and Postal Notes accepted if 10% added for Exchange.

**ADDRESS ORDERS FOR ALL GOODS ON THIS PAGE TO**  
**JOHNSON SMITH & CO. DEPT. 989 Racine, Wis.**



# Velocity . . . The Latest Microphone

(Continued from page 309)

other under certain conditions; in fact at times one type cannot be substituted for another.

When in need of a microphone, therefore, it would be advisable to determine first which one is best suited for the work. The cost of installation is a very important factor. The need of pre-amplification, with the necessary extra power supply necessary to operate the condenser-dynamic and ribbon types, makes the carbon microphone the choice of the moderately priced installation.

The condenser and dynamic microphones are employed to cover large areas, such as orchestras, stages and far away "pick-ups." One is to be kept indoors, preferably, while the other can be taken outdoors without much worry.

The ribbon-velocity "mike," however, is the all-around microphone. Its fidelity of reproduction is unsurpassed. It is rugged, yet sensitive; it is unaffected by climatic condition and when used outdoors needs only to be protected from strong winds.

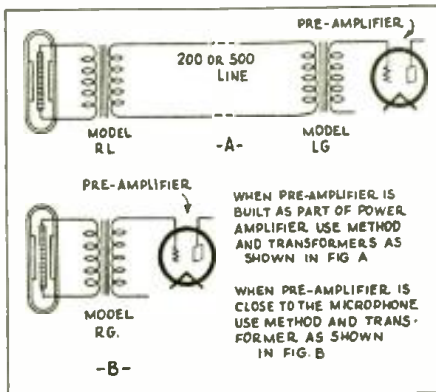


Fig. 5 How to couple "mike" over short and long circuits

## Amateur Transmitters

(Continued from page 271)

### TUNING UP

After the transmitter is wired and the antenna is up, the monitor is called into play. Suppose we intend to work in the 80-meter band, on 3,575 kilocycles. We have already cut our antenna according to the measurement in the table for that particular frequency. Put the 80-meter coil on your receiver and set your monitor just inside the low frequency edge. Usually there are some stations operating right on the edge of the band, but always to be on the safe side, unless your monitor is already accurately calibrated, set it inside the first ten stations you hear. Plug your earphones in on the monitor and then press the key on the transmitter. Turn the transmitter dial until the current goes down to its lowest point, about 30 (milliamperes). Somewhere in the portion of the dial where the transmitter draws minimum current, a whistle should be heard in the earphones, signifying that the set is operating O.K. The grid coils will probably be all right, but it may be necessary to add on or take off a few turns until the transmitter draws least current (without the antenna) at the low frequency end of the band.

Now clip the antenna on the tank coil, one turn for 20, two for 40 and five for 80 meters, from the "cold" or plate blocking condenser end.

As the dial is turned through the frequency of the antenna, there should be a sharp rise in plate current, as shown on the milliammeter. The antenna should be clipped as far up to the "hot end" of the tank coil as is possible, without spoiling the note, because for good reliable operation the note must be pure D.C. The transmitter will work only on the frequency to which the antenna is cut, hence if a frequency well in the band has been chosen, there will be no worry about off frequency operation. Always operate right on the peak of the antenna, although in case of interference a shift can be made up to 15 kc. each side of the peak. When doubling the antenna, say using an 80 meter antenna on 40 meters, the peak will be much broader. Always keep the note pure d.c.

### CONCLUSION

This set has been built to operate on the three most popular amateur bands, 20, 40 and 80 meters. Twenty is the big daylight DX band. Forty is usually good for about fifteen hundred miles, although in the early morning it is possible to work Australia and New Zealand.

However, the best band for the fellow just breaking in the game is the 80-meter

band. There are plenty of stations on all day and all night, and hundreds of good operators who will "pull up" and send slow for a newcomer. After experience has been obtained on the 80 meter band, the outfit can be put down on 40 and 20 for a try at some big DX.

This is the first of a series of articles dealing with C.W. and phone transmitters of all types. In subsequent articles we will show you how to enlarge and improve your transmitter easily and how to add phone to it.

### ANTENNA DATA

Frequency	Antenna Length	Feeder Length from center of aerial
3575 KC	134 ft.	18' 8"
3600 KC	132 ft.	18' 5"
3700 KC	129 ft.	18'
3800 KC	125' 9"	17' 6"
3900 KC	122' 7"	17'

For 40 meter aeriels multiply the frequency by 2 and divide the aerial and feeder placement lengths by 2. For 20 meters multiply and divide by four. The bands are as follows:

80 m.	3500 to 1000 kc.
40 m.	7000 to 7300 kc.
20 m.	14000 to 14400 kc.

Use good insulators, measure carefully, and solder the feeder on tightly.

### Power Supply Parts List

- 1 Acratest power transformer (T)
- 2 Eby socket 4 prong (S)
- 2 Dual 8-mf. Acratest electrolytic cond. (C)
- 1 30-henry, 150 ma. choke (S)
- 1 10,000-ohm Bleeder resistor 50 watts (R)
- 1 Wooden base board
- 1 4 wire cable
- 1 4 wire socket plug

### Grid and Plate Coil Specifications

Grid Coils No. 30 d.c.c. wire	80 m.—50 turns	Wound on coil form— 1 1/4" diam. 3/4" copper tubing
	40 m.—15 turns	
	20 m.—6 turns	
Plate Coils	80 m.—14 turns	3/4" copper tubing
	40 m.—6 turns	
	20 m.—4 turns	

### TRANSMITTER PARTS

- 1 set of grid coils (See specs.) L-2
- 1 set of plate coils (See specs.) L1
- 1 Acratest .00035 mf. tuning cond., C1
- 3 .002 mf. mica C2, C3
- 1 .00025 mf. mica C4
- 1 Hammarlund R.F. Choke R.F.C.
- 1 Acratest 150 ohm CT Resistor R1
- 1 Acratest 5 watt resistor 50,000 ohms R2
- 3 Eby Sockets
- 1 Wooden base board 7"x13"
- 1 O-100 Readrite milliammeter



Diagram of typical antenna for 3575 kc. Ant. of No. 14 solid enamelled copper feeder of heavy rubber covered lead-in wire. Use good insulators. Solder feeder on carefully. Feeder at right angles to flat top for first 30% of distance.

## AMERICA'S OUTSTANDING MICROPHONE VALUE!



Lifetime Model No. 88

is the most remarkable value in a microphone ever offered! It is ruggedly constructed—precisely machined—beautifully chrome plated—3/4" diameter—2" thick overall—and weighs 1 1/2 pounds. It has a durable in diaphragm .002" thick—gold spots—special stretch ring arrangement—gold contact buttons of 200 ohms each—is scientifically dampened and possesses a practically flat curve response over the entire voice and musical range. Unconditionally GUARANTEED for more than 10 years!

**Our Special Introductory Offer**  
A \$35.00 Value Double Button Microphone for only **\$6.95**

- Sent postpaid on receipt of remittance—or C.O.D. plus charges.
- Chrome Plated Desk Stand—8 in. High—Complete with Springs...\$1.95
- Stately Bronze Banquet Stand—15 in. High—Complete with Springs...\$2.95
- Stately Bronze Floor Stand—Adjustable 4 to 7 Feet—Complete with Springs...\$4.95
- Transformer to Match Model 88 Mike Unshielded 89c—Shielded...\$1.45
- Your Call Letters—Name—or any five letter word can be placed on the DESK STAND ONLY for 25c additional. Write for descriptive literature of our Electro-Dynamic Speaker Unit—Aluminum Trumpets, etc., offered at lowest prices in America.

### SPECIAL OFFER

- Model No. 6 Double Button Microphone—for amateurs—public addresses, etc. A \$10 Mike for only...\$1.95
- Model No. 6 is a bright aluminum finish, precisely machined Mike—3/4 in. diameter—1 in. thick—weighs 8 oz. Has gold plated diaphragm of special construction—gold plated buttons—200 ohms each—frequency 40 to 3500 cycles within 4 Db. Stand with call letters to match...\$1.50

The LIFETIME CORP. 1302 Dear St. Toledo, Ohio

# 1933 SHORT WAVE MANUAL

BY DON C. WALLACE  
Winner of The Hoover Cup



ONE DOLLAR

—Tells you hundreds of things you never knew before about short-waves.

This Manual with more than 156 pages of short-wave data shows you how to build models of the internationally famous Wallace sets. This famous Wallace Cup Set Winner costs approximately twenty dollars to build.

Here is something entirely new in short-waves. A complete receiving and transmitting system that uses no grounds. The Wallace System is the accepted method for greatest long-distance reception with least interference. It is the winner of the Hoover Cup for best short-wave communication.

What a surprise you will get when you receive your Manual. Acclaimed everywhere as the new authority on the subject. Only \$1.00 per copy, postpaid, in U. S.

Over 156 Pages—Over 200 Illustrations—Size 6x9 Inches—Flexible Covers—Attractive Colored Front Cover.


Mail This Coupon Today!

RADIO PUBLICATIONS  
245-S Greenwich St.,  
New York, N. Y.

Here is \$1.00. Rush a copy of the Wallace Short Wave Manual to

Name.....  
Address.....  
City..... State.....

ORDER DIRECT FROM THIS PAGE

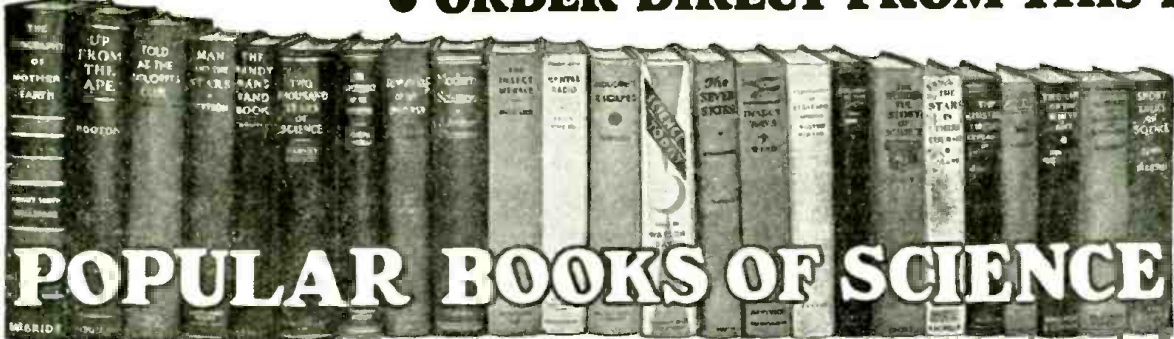

We herewith present the most complete collection of recent important popular science books. We have, after an exhaustive study, selected these volumes because they represent the foremost books of their kind in print today. There is such a great variety that we are sure it will satisfy any taste as well as any requirement of the student of science. We publish an catalogue and ask you to be kind enough to order direct from this page. Prompt shipment will be made to you direct from the publishers. We are ready to act as clearing house for a number of publishers and our prices are ALWAYS LOWER THAN ANYWHERE. Remit by money order or certified check.

POPULAR BOOKS OF SCIENCE

THIS LIST CHANGED MONTHLY. NOTE NEW LOW PRICES

**ASTRONOMY**  
**MAN AND THE STARS**, by Harlan T. Steason. Cloth covers, size 5 1/2 x 8 1/4, 221 pages illustrated. Price \$2.50  
The story of the adventure of astronomy, from the days when primitive man began wondering about the meaning of the heavens, through the work of the great pioneers of the science to the present day. Profoundly exciting.

**THE UNIVERSE AROUND US**, by Sir James Jeans. Cloth covers, size 5 1/2 x 8 1/4, 251 pages, 24 illustrations. Price \$4.50  
A non-technical book which roves through the mysteries of modern physics and astronomy, opening up new vistas for the imagination. The very latest word in physical science. A marvelous work.

**THE STARS IN THEIR COURSES**, by Sir James Jeans. Cloth covers, size 5 1/2 x 8 1/4, 172 pages, 50 illustrations and maps. Price \$2.50  
Modern astronomy and the wonders of the universe as seen through the giant telescope of today. An informal conversational style, and simple language has been retained.

**POPULAR ASTRONOMY**, by Camille Flammarion. Cloth covers, size 5 1/2 x 8 1/4, 696 pages, 291 illustrations. Price \$6.00  
A general description of the heavens written in an interesting and lucid manner for those who wish to acquire a knowledge of astronomy without technicalities.

**AVIATION**  
**WINGS OF TOMORROW**, by de la Cierva. Cloth covers, size 8 1/2 x 5 1/4, 284 pages, 21 illustrations. Price \$2.50  
When the inventor of the most revolutionary aircraft—the autogyro—speaks, we listen with respect. This book is a notable contribution to air transport set forth interestingly and convincingly.

**CHEMISTRY**  
**THE AMATEUR CHEMIST**, by A. Frederick Collins. Cloth covers, size 5 1/2 x 8 1/4, 216 pages, 77 illustrations. Price \$1.50  
An extremely simple but thoroughly practical chemistry book. A vast amount of practical information is given, also how to make and do things which will save time and money.

**EXPERIMENTAL CHEMISTRY**, by A. Fred Collins. Cloth covers, size 5 1/2 x 8 1/4, 276 pages, 108 illustrations. Price \$2.00  
Here is a book that approaches the fascinations of chemistry in a new way. Contains a vast store of interesting and unusual material. THE book for experimenters.

**HOW TO UNDERSTAND CHEMISTRY**, by A. Frederick Collins. Cloth covers, size 5 1/2 x 8 1/4, 322 pages, numerous illustrations. Price \$2.00  
A clear, simple but entertaining book on the wonders of modern chemistry. It explains matter and its make-up, discusses common elements, shows what the symbols of chemistry are and how they are used and gives countless other interesting information.

**POPULAR CHEMISTRY EXPERIMENTS**, by John H. Winn. Cloth covers, size 10 1/2 x 8, 80 pages, 323 experiments, 100 illustrations. Price \$1.50  
Absolutely the book for Junior Chemists. Contains over 300 experiments, all explained clearly and simply. How to make safe fire

works, inks and paints, glass blowing, food analyses and electroplating are but a few of the experiments. The cleverest and newest book on the subject.

**ELECTRICITY**  
**THE BOOK OF ELECTRICITY**, by A. Frederick Collins. Cloth covers, size 5 1/2 x 8 1/4, 185 pages. Price \$1.50  
With the aid of this book, anyone may enjoy the fascination of conducting electrical experiments and learn the fundamental principles of electricity. Contains an abundance of useful information.

**PRACTICAL ELECTRICS**. Cloth covers, size 7 1/2 x 5, 135 pages, 126 illustrations. Price \$0.75  
A universal handy book on every-day electrical subjects. Covers numerous subjects: alarms, batteries, bells, induction, intensity and resistance coils, microphones, motors, phonophones, dynamo electric machines, telephones and storage batteries. All written in a clear and simple manner. Just the book for the young electrician.

**THE WIMSHURST MACHINE**, by A. W. Marshall. Cloth covers, size 5 1/2 x 11, 112 pages, 30 illustrations and drawings. Price \$0.75  
A Practical Handbook on the Construction and Working of the Wimshurst (Static) Machine, including Radiography, Wireless Telegraphy, and many Static Electrical Apparatus. Written in simple language for the experimenter. Only book of this kind.

**INDUCTION COILS**, by H. S. Norris. Cloth covers, size 7 1/2 x 5 1/4, 269 pages, 79 illustrations. Price \$1.50  
Practical handbook on the construction and use of medical and spark coils. Also includes construction data on Ruhmkorff, Tesla coils, etc. Roentgen radiography, wireless telegraphy, and practical information on primary and secondary batteries. An excellent experimenter's volume.

**HOW TO INSTALL ELECTRIC BELLS, ANNUNCIATORS AND ALARMS**, by N. H. Schneider. Cloth covers, size 7 1/2 x 5, 83 pages, 70 illustrations. Price \$0.75  
This book was written to explain in practical language how an electric bell operates and how they are installed. Includes such subjects as batteries, wires and wiring, burglar alarms, fire alarms, interphone house sets, etc. Worth its weight in gold.

**GENERAL SCIENCE**  
**TWO THOUSAND YEARS OF SCIENCE**, by R. J. Harvey-Gibson. Cloth covers, size 5 1/2 x 8 1/4, 322 pages, fully illustrated. Price \$3.50  
This authoritative work is meeting one of the greatest Science needs of the general reader. Fascinating histories of the great inventors and discoveries with lucid explanations of their work.

**EXPERIMENTAL SCIENCE**, by A. Frederick Collins. Cloth covers, size 5 1/2 x 8 1/4, 280 pages, 152 illustrations. Price \$2.00  
A wealth of outstanding and surprising experiments are to be found in this book. Not only vastly entertaining, but also highly instructive. The book for amateurs.

**SCIENCE TODAY**, by Watson Davis. Cloth cover, size 5 1/2 x 8 1/4, 310 pages. Price \$2.50  
48 brief talks about the latest things

Science has found out—about the sun, moon, stars, the earth, light, electricity, the weather, germs, the past of man, and dozens of other absorbing topics.

**INVENTION**  
**THE PSYCHOLOGY OF THE INVENTOR**, by Joseph Rowman. Ph. D. Cloth covers, size 5 1/2 x 8 1/4, 252 pages, 13 illustrations. Price \$3.00  
A comprehensive picture of the inside of the inventor's mind. Observations from 710 prominent inventors are quoted. Many absorbing topics discussed, also facts never before in print. No inventor should miss it.

**PATENTS, INVENTIONS**, by F. B. Wright. Paper covers, size 7 1/2 x 5, 108 pages, 1 plate. Price \$0.35  
A practical and up to date guide for inventors and patentees. How to protect, sell and buy inventions is also thoroughly discussed. Discusses all patent questions and shows you the pitfalls of most inventors.

**MECHANICS**  
**EXPERIMENTAL MECHANICS**, by A. Frederick Collins. Cloth covers, size 5 1/2 x 8 1/4, 302 pages, 167 illustrations. Price \$2.00  
The most cheap and best book on mechanics. Chuck full with experiments you can make: all mechanical work and clock movements, as well as perpetual motion in profusion.

**THE HANDY MAN'S BOOK**, by C. T. Schaefer, M. E. Cloth covers, size 6 1/2 x 9, 341 pages, 14 illustrations and diagrams. Price \$4.00  
A complete manual covering every phase of repair and maintenance work in the home, factory, office and farm, readily understood and applied by the non-professional worker. A fine book.

**THE HOME HANDBOOK**, by A. Frederick Collins. Cloth covers, size 5 1/2 x 8 1/4, 165 pages, illustrated. Price \$1.50  
This book tells with many illustrations, diagrams, how to do the thousand and one odd jobs around the house which need to be done.

**MISCELLANEOUS**  
**HOUDINI'S ESCAPES**, by Walter Gibson. Cloth covers, size 6 1/2 x 8 1/4, 315 pages, illustrated. Price \$3.00  
The first and only authentic record of the actual methods devised and used by Houdini. Explains his modern miracles in non-technical language. Learn how this master accomplished the impossible!

**NEW AND ORIGINAL MAGIC** by Edward M. Massey. Cloth covers, size 8 1/2 x 5 1/4, 205 pages, 39 illustrations. Price \$3.00  
A fund of information for the professional artist and his younger brother, the amateur. It comprises numerous novel and entertaining magic effects. A permanent text and guide for the worker in magic and mystery. Don't miss this.

**How to order**  
We cannot ship C.O.D. Our prices are net, as shown. Please include sufficient postage, for Parcel Post, otherwise books must be shipped by express collect.

**MICROSCOPY AND PHOTOGRAPHY**  
**SCIENCE AND PRACTICE OF PHOTOGRAPHY**, by John R. Roebuck. Cloth covers, size 6 1/2 x 8 1/4, 298 pages, 52 illustrations. Price \$2.50  
A practical book for the professional and amateur. Covers thoroughly and logically the entire elementary ground of photography. Invaluable information and suggestions.

**SEXOLOGY**  
**THE SEXUAL SIDE OF MARRIAGE**, by M. J. Emer, M. D. Cloth covers, size 5 1/2 x 8 1/4, 252 pages, illustrated. Price \$2.50  
An understandable book free from sentiment or hypocrisy, for those whose marriage is the best. Deals frankly with intimate marriage relationships, especially at crucial points where ignorance and misinformation are often disastrous.

**SEXUAL IMPOTENCE**, by Dr. Wm. I. Robinson. Cloth covers, size 5 1/2 x 8 1/4, 502 pages, 18 illustrations. Price \$3.00  
The most complete book obtainable on this important subject. Explains symptoms and cause of impotence, sterility, and frigidity. Gives practical advice for treatment and cure with other valuable sex knowledge.

**COMPLETE BOOK OF SEX KNOWLEDGE**, by Dr. Bernard H. Bernard. Cloth covers, size 7 1/2 x 5, 331 pages. Price \$2.75  
At last here is the book which dispenses with conventionalism in the discussion in detail of the whole sex problem. Not a single one of the sex questions that has not been fully treated.

**SEX CONDUCT IN MARRIAGE**, by Dr. Bernard H. Bernard. Cloth covers, size 7 1/2 x 5 1/4, 218 pages. Price \$1.75  
Answers simply and directly intimate questions which the author has been called upon innumerable times to answer. A sound understanding of sex conduct is gained by simple, straight-forward explanations. A most valuable book.

**WOMEN, HER SEX AND LOVE LIFE**, by Dr. William J. Robinson. Cloth covers, size 5 1/2 x 8 1/4, 411 pages, numerous anatomical illustrations. Price \$3.00  
A real book dealing with intimate relations of woman's sex and love life. Full of practical information on the importance to every woman, and through her to every man.

**SANE SEX LIFE AND SANE SEX LIVING**, by Dr. H. W. Lenz. Cloth covers, size 5 1/2 x 7 1/4, 181 pages. Price \$2.00  
Absolutely the plainest book ever written on the sexual intimacies of marriage. Ignores no details, goes into every subject frankly and gives the most complete and practical information ever contained between two covers. Endorsed by such men as Havelock Ellis, Geo. S. Wilson and Dr. W. F. Robie.

**MARRIED LOVE**, by Dr. Marie C. Stopes. Cloth covers, size 6 1/2 x 7 1/4, 190 pages. Price \$1.00  
Over 800,000 copies of this famous book have been sold already. It is the most complete and most delicate and most helpful books ever written on the vital subject of the intimate contacts of love in marriage. In lifting the ban on this book Judge Woolsey has given the people a great work.

**THE BOOK OF THE MICROSCOPE**, by A. Frederick Collins. Cloth covers, size 5 1/2 x 8 1/4, 245 pages, 71 illustrations. Price \$1.50  
Simple but vivid descriptions of all the wonderfully fascinating uses of the microscope. Plant and animal life, curious hygiene facts, the microscope in criminal investigation are but a few of the subjects discussed. Splendid for experimenters. The only book of its kind in print.

**LOVE. A TREATISE ON THE SCIENCE OF SEX ATTRACTION**, by Dr. Bernard S. Bismey. Cloth covers, size 5 1/2 x 8 1/4, 438 pages, 131 illustrations. Price \$3.00  
Because of the thoroughness and completeness of its contents the sale of this volume was restricted to physicians. It is now available to men and women who desire the real truth and the intimate details about sex and love.

**SEXUAL TRUTHS**, by Dr. William J. Robinson. Cloth covers, size 5 1/2 x 8 1/4, 400 pages. Price \$3.00  
One of the most unique books ever printed. It is an answer to the requests from sane, sensible people for the best, straight-forward information they cannot find elsewhere. Don't be without a copy of this fascinating and daring book.

**BIRTH CONTROL OR THE LIMITATION OF OFFSPRING**, by Dr. William J. Robinson. Cloth covers, size 5 1/2 x 8, 262 pages. Price \$2.00  
This book on the burning question of the day has been written by a pioneer in Birth Control. It is he who advocated the movement to permit husbands and wives to decide for themselves how large their families should be.

**SEX KNOWLEDGE FOR MEN AND BOYS**, by Dr. William J. Robinson. Cloth covers, size 5 1/2 x 7, 262 pages. Price \$2.50  
This is a book that every man and youth, conscious of his responsibilities and health should read. An excellent program for the sex education of the boy makes it a doubly valuable book to parents.

**SEX, LOVE AND MORALITY**, by Dr. William J. Robinson. Cloth covers, size 5 1/2 x 8, 157 pages. Price \$3.00  
Here is the book which dares to be different. After a quarter of a century of daily experiences, this author concludes that the present-day conception of love, sex and morality is wrong. In this pioneer book he outlines a rational code of sexual ethics which liberal and intelligent people will be eager to accept.

**MARRIED LIFE AND HAPPINESS**, by Dr. William J. Robinson. Cloth covers, size 5 1/2 x 8, 250 pages. Price \$3.00  
Here is a book that every husband should read and see that his wife reads it too. For genuine lasting happiness, a better book for women has never been written than this fascinating volume. Every page is crowded with advice and information.

**AMERICA'S SEX AND MARRIAGE PROBLEMS**, by Dr. William J. Robinson. Cloth covers, size 5 1/2 x 8, 500 pages. Price \$3.00  
Never before have you read any book so daring and so outspoken. Facts proved by over 200 cases taken from actual experience.

SCIENCE PUBLICATIONS 94SW Park Place New York, N.Y.

We can get ANY book in Science or Mechanics, Radio, etc. Just furnish us with Title and Author or tell us in which topic you are interested.

## When to Listen

By Robert Hertzberg

### New Mexican Station

● THE sensation of the last month undoubtedly is station XETE, in Mexico City, which has been providing short-wave fans with interesting reception. We wish to thank all the SHORT WAVE CRAFT readers who were kind enough to send us reports on this new outfit.

In regard to XETE, Jerry Pilgrim, 5744 Kingsly Circle, Oakland, Cal., writes:

"XETE is on 31.25 meters from 11:30 a. m. to 2:30 p. m. and from 4:00 to 9:00 p. m., Pacific Standard Time, and later on Saturdays. It comes in with excellent volume after sunset, louder than W1XAZ and W2XAF.

"DUOK in Shanghai, China, is on 49.2 meters and is heard from 3:00 to 5:30 a. m. irregularly.

"YVQ in Maracay, Venezuela, has changed its wavelength to 22.48 meters and VK2ME has changed its schedule to 9:00 to 11:00 p. m. on Saturdays and 2:00 to 7:00 a. m. on Sundays, Pacific Standard Time.

"The short-wave stations that I have received on my two-tube set are W8XK on 48.25 and 19 meters; W1XAL on 25 and 48.25 meters; W2XE, W3XAL, W8XAL, YV1BC, W4XB, W3XAU, VE9CS, all on 49 meters; XETE, W2XAF, W1XAZ and VK2ME on 31 meters. I would like to hear from other short-wave fans."

### German Stations Very Strong

The political upset in Germany has had one good feature, at least as far as short-wave listeners are concerned. The short-wave stations at Konigswusterhausen, which formerly transmitted only at irregular intervals, are now exceedingly busy broadcasting Hitler propaganda in both German and English, and can be heard in the East with roaring loud speaker strength. During the early evening DJC, on 49.83 meters, is without doubt one of the best stations on the air. It may be recognized quite easily by its between-program interval signals, which consists of a few bars of music on the piano. The announcer speaks excellent if somewhat accented English.

### Bowmanville, Canada

Station VE9GW, located in Bowmanville, Ont., Canada, on 49.17 meters, is now operating on the following schedule:

Monday and Tuesday, 8:00 to 12:00 noon, Eastern Daylight Saving Time.

Thursday and Friday, 4:00 to 8:00 p. m.

Saturday, 4:00 to 12:00 p. m.; Sunday, 11:00 a. m. to 9:00 p. m.

The transmissions on 25.42 meters have been discontinued.

### "Leviathan" Laid Up

Some short-wave fans must be classed

with fishermen when it comes to recounting their achievements. One way of checking up their lists of received stations is to note what ships are listed. The favorite stumbling block is the much publicized *S.S. Leviathan*, which has been tied up at a New York dock and virtually abandoned since June. Although the main occupants of the vessel are a couple of escaped monkeys, we continued to see the *Leviathan's* call, WBSN, included in many logs!

### He Hears Germany!

Harry V. Miner, 52 Pratt Street, Allston, Massachusetts, has kindly sent us a verification he received from the German Post Office stations. He has been able to hear DJD on 25.51 meters from 3:00 to 7:00 p. m., and DJC on 49.83 meters as late as 8:00 p. m., E.S.T. We have had this verification translated and are presenting it herewith because it contains specific data.

"The German Postal Administration thanks you for the report of reception of the German around-the-world radio transmitters. The transmitter is located in Zeesen, near Berlin. It operates daily between the hours of 2:00 to 6:00 p. m., Middle European Time (8:00 to noon E.S.T.) on the wavelength of 19.73 meters; from 6:30 p. m. to 12:30 a. m., M.E.T. (12:30 to 6:30 p. m. E.S.T.) and in some instances also up to 1:30 a. m. M.E.T. on 31.38 meters. Mainly it transmits the programs of the Deutschlandsenders, 1534.9 meters, i. e., the programs of the Berlin station. The antenna capacity of the carrier wave is 5 kw. The call letters of the transmitter on 31.38 meters is DJA, and those on 19.737 meters, DJB.

When transmitting to North America, the transmitter in each instance takes advantage of the most favorable conditions for transmission on the wavelengths of 19.737, 25.51, or 49.83 meters. In the two latter instances the transmitter has the call letters DJD and DJC. Every day at 4:00 p. m., M.E.T. (11:00 a. m., E.S.T.) the program of the following day is announced on 19.737 meters in both German and English.

"Just now the operation of the German around-the-world transmitter is being improved by the construction of new antennas and the erection of a second transmitter on a larger scale. After the completion of the whole installation, either one or two transmitters may operate on different wavelengths and antennas as may be desired. It is expected that the German around-the-world transmitter will always be heard in overseas service. We shall be grateful for further observations on the receptions every now and then."

This letter was written on the stationery of the Reichspostzentralamt, Berlin-Tempelhof, and is dated March 22, 1933.

## Powertone-Wallace S-W Receiver


(Continued from page 287)

spread method, but such that an infinitely greater wavelength or frequency range is covered.

This new method of short-wave tuning makes station finding a relatively simple matter. It is particularly advantageous when the receiver is used for amateur code or voice reception. Special plug-in coils can be wound so that any narrow band in the short-wave spectrum can be "spread" at will by simply adding a turn of wire to the secondary winding of the coil, or by removing a turn or two of wire from it. The 75-85.7 meter amateur phone and code band, for example, can be tuned in two ways by means of this condenser switching arrangement. The 75-150 meter coil is first plugged in; the switch on the receiver panel is thrown to the band-spreading position. Almost over the entire sweep of the dial will be found

many amateur phone signals, many stations widely separated from others, no crowding of stations. Contrast this method with that found in other receivers, in which the entire amateur phone band is crowded into a relatively few degrees on the tuning dial. Another snap of the condenser change-over switch and both amateur phone and code bands are tuned with one sweep of the dial, in addition to tuning in the airplane and ground stations, police calls and commercial signals on the upper portion of the dial.

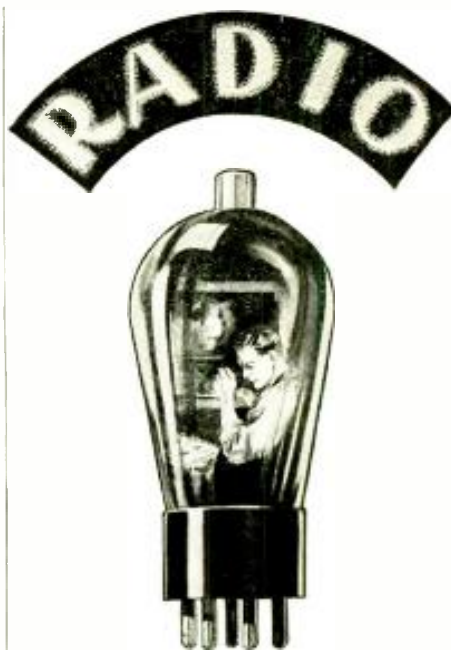However, when this method of tuning is used the stations are not widely separated, because the full capacity of the condenser does not permit band-spread tuning. If, for example, the coil in use covers the amateur phones with band-spread tuning, and it is then desired to band-spread amateur code signals or airplane or police calls, it is merely necessary to add



No ONE can yet say how far-reaching will be the effect of radio on modern living and business—but every one is agreed the industry is still in its infancy . . . that its possibilities are unlimited!

This is why the wisest counselors are advising young men to acquire the fundamentals of radio . . . to prepare themselves for the opportunities ahead. The future is exceedingly bright.

Thousands are finding exactly what they need in the International Correspondence Schools' Radio Course. So can you! Prepared by experts, and frequently revised by them, this course has the enthusiastic approval of the industry.

There is a consistent demand for radio mechanics, assemblers, testers, inspectors, draftsmen, service men, installers and salesmen; also, for operators and attendants on board ship and at commercial radio stations, government police stations and aviation stations. The field of opportunity is unlimited. Let us send you complete information—absolutely free. Use the coupon. Mail it today—Radio beckons you.

### INTERNATIONAL CORRESPONDENCE SCHOOLS

"The Universal University"

BOX 2878-B, SCRANTON, PENNA.

Without cost or obligation, please send me a copy of your booklet, "Who Wins and Why," and full particulars about the subject before which I have marked X:

- RADIO OPERATING
- RADIO SERVICING
- ELECTRICAL ENGINEER
- Electric Wiring
- Electric Lighting
- Welding, Electric and Gas
- Telegraph Engineer
- Telephone Work
- Mechanical Engineer
- Mechanical Draftsman
- Machinist
- Gas Engines
- Diesel Engines
- Aviation Engines
- Civil Engineer
- Refrigeration

Name .....

Age .....

Address .....

City ..... State .....

Occupation .....

If you reside in Canada, send this coupon to the International Correspondence Schools Canadian, Limited, Montreal, Canada.

# an old timer says—

San Francisco, Calif.

Gentlemen:  
 Allow me to congratulate you on Myron F. Eddy's "How to Become an Amateur Radio Operator." I have been a "ham" since 1909 and have worked up from the open crashing sparks of "Old Betsy's" and took sullenly to these new fangled gadgets and had to park "Betsy" in the junk heap under the eaves to go in for tubes. I'm too old now to dabble in the game very much but in my teaching a bunch of ether disturbing young squirts here—all Boy Scouts, I still get a certain "kick" out of it. I purchased nine copies for my gang and I suppose five or six others got them because they saw ours—had to send to Oakland for three additional copies. They're GREAT!

One of the "Old Men" of Radio  
 Ex. Lieut. Al. A. Weber (Retired)  
 1153 Capp St., San Francisco, Calif.



**50c EACH**



THERE is not a radio man in the field, experimenter, service man or dealer who will not want to read these two books. Right up to the minute with outstanding developments in short-wave radio—new methods and apparatus for quickly learning how to become a practical radio operator. Each book is authoritative, completely illustrated and not too highly technical. The text is easily and quickly grasped.

**How to Become an Amateur Radio Operator**  
 We chose Lieut. Myron F. Eddy to write this book because his long years of experience in the amateur field have made him pre-eminent in this line. For many years he was instructor of radio telegraphy at the R.C.A. Institute. He is a member of the I.R.E. (Institute of Radio Engineers), also the Veteran Wireless Operators' Association.

If you intend to become a licensed code operator, if you wish to take up phone work eventually, if you wish to prepare yourself for this important subject—this is the book you must get.

**Partial List of Contents**

Ways of learning the code. A system of sending and receiving with necessary drill words is supplied so that you may work with approved methods. Concise, authoritative definitions of radio terms, units and laws, brief descriptions of commonly used pieces of radio equipment. This chapter gives the working terminology of the radio operator. Graphic symbols are used to indicate the various parts of radio circuits. General radio theory particularly as it applies to the beginner. The electron theory is briefly given, then waves—their creation, propagation and reception. Fundamental laws of electric circuits, particularly those used in radio are explained next and typical basic circuits are analyzed. Descriptions of modern receivers that are being used with success by amateurs. You are told how to build and operate these sets. Amateur transmitters. Diagrams with specifications are furnished so construction is made easy. Power equipment that may be used with transmitters and receivers, rectifiers, filters, batteries, etc. Regulations that apply to amateur operators. Appendix, which contains the International "Q" signals, conversion tables for reference purposes, etc.

**How to Build and Operate Short Wave Receivers**

is the best and most up-to-date book on the subject. It is edited and prepared by the editors of SHORT WAVE CRAFT, and contains a wealth of material on the building and operation, not only of typical short-wave receivers, but short-wave converters as well. Dozens of short-wave sets are found in this book, which contains hundreds of illustrations; actual photographs of sets built, hook-ups and diagrams galore. The book comes with a heavy colored cover, and is printed throughout on first-class paper. No expense has been spared to make this the outstanding volume of its kind. The book measures 7 1/2 x 10 inches.

This book is sold only at such a ridiculously low price because it is our aim to put this valuable work into the hands of every short-wave enthusiast.

We know that if you are at all interested in short waves you will not wish to do without this book. It is a most important and timely new radio publication.

**Over 150 Illustrations in Each Book**

**72 Pages 7x10 Inches Heavy Colored Covers**

**Not Sold on Newsstands**

**SHORT WAVE CRAFT**  
 96-98 Park Place, New York, N. Y.

a few turns of wire to the secondary winding of the plug-in coil, a turn at a time being added, until the minimum indication of the condenser tuning dial brings in the beginning of the wavelength or frequency band that is to be band-spread. Or the commercial short-wave broadcasts, likewise, can be tuned in *band-spread* manner. Those who desire to use the Wallace receiver for listening to a predetermined band can secure a coil for that particular band from the manufacturer of the receiver, or a coil can be wound by any experimenter by referring to the coil winding data given elsewhere in this article.

The two-tube Wallace receiver, illustrated herewith, can be operated with type 30 tubes and dry cells. The extremely low filament drain of the type 30 tubes enables the user to operate the receiver from an ordinary 4 1/2 volt "C" battery for filament lighting and a single 22 1/2-45 volt "B" battery for plate current. A reasonable amount of volume is secured when this method is used but the receiver will still bring in all stations that are otherwise heard when a larger number of tubes is used. In fact, a one-tube receiver will bring in as many stations as a 3- or 4-tube receiver, but the signals are not received with sufficient volume to make reception enjoyable. The two-tube receiver, with the special antenna coupler winding on the coil form, the band-spread system of tuning and the use of a Wallace antenna of specified size, has brought in stations from 26 countries when headphones were used.

The coil winding data are as follows:

- 15 to 40 meter coil, antenna coupler—16 turns (2 windings of 8 turns each). Secondary coil, 6 1/2 turns, double space wound, No. 14 DCC wire. Regeneration coil 6 1/2 turns, closely wound, spaced 1/2" from secondary winding. Use No. 14 DCC wire.
- 40 to 75 meter coil. Antenna coupler—Same for all coils. Secondary coil—16 turns, closely wound. Use No. 22 DCC wire. Regeneration coil—15 turns, closely wound, spaced about 1 1/4" from secondary coil. Use No. 22 DCC wire.
- 75 to 150 meter coil. Antenna coupler—Same for all coils. Secondary coil—28 turns, closely wound. Use No. 22 DCC wire. Regeneration coil—26 turns, closely wound. Use No. 22 DCC wire. Space as far as possible from secondary coil (about 1").
- 150 to 200 meter coil—Antenna coupler—same for all coils. Secondary coil—70 turns No. 26 DCC wire, closely wound. Regeneration coil—20 turns, No. 26 DCC wire, spaced about 1/2" from secondary coil. Coil forms 1 3/8" diameter.

**Powertone-Wallace Two-Tube Short Wave Set Parts List**

- 1—Hammarlund 43-plate midget condenser, 325 mmf.
- 1—Hammarlund special "Wallace" band-spread condenser, 75 mmf. total.
- 1—Hammarlund 84-plate midget condenser, 240 mfd.
- Fixed condenser, .00025 mf.
- Special filament resistor, 8 ohms
- 10-megohm grid-leak, Lynch (International)
- 40 mmf. midget condenser
- .0001 mf. mica condenser
- .0002 mf. mica condenser
- .5 mf. condenser. Pigtail type.
- .01 mf. condensers, Pigtail type
- 10 mf. electrolytic condenser
- 8 mf. each electrolytic condenser
- 16 mf. electrolytic condenser
- Set of four plug-in coils (15-200 meter-).
- Bruno
- 1—Audio impedance
- 25 henry choke
- 15 henry choke
- 5 megohm resistor
- 50,000 ohm Potentiometer
- 60,000 ohm resistor, Lynch (or International)
- 250,000 ohm resistor, Lynch (or International)
- 625 ohm resistor Lynch (or International)
- 175 ohm resistor, Lynch (or International)
- 1—power switch
- 3—wafer sockets, 6 prong, Eby (National, Hammarlund, Na-ald.)
- 1—wafer socket, 4 prong, Eby (National, Hammarlund, Na-ald.)
- 1—Vernier illuminated dial
- 1—Stamped metal chassis
- 1—metal cabinet
- 1—terminal strip, Eby (or other make)
- 1—dual antenna and ground binding post strip. Eby (or other make)

SHORT WAVE CRAFT  
 96-98 SWC Park Place,  
 New York, N. Y.

Gentlemen: I enclose herewith \$.....  
 for which please send me, prepaid a copy  
 of the book checked.

( ) HOW TO BUILD AND OPERATE  
 SHORT WAVE RECEIVERS—50c

( ) HOW TO BECOME AN AMATEUR  
 RADIO OPERATOR—50c.

Send money order, check, cash or new  
 U. S. stamps. Register letter if it con-  
 tains stamps or currency.

Name .....

Address .....

City..... State.....

## Attention! All Squads!

(Continued from page 281)

His weak little voice couldn't do much," disparaged Bill.

"Oh yeah!" Doc put the record on the turntable, turned on the motor and connected the pickup leads to the speech input.

The record scratched badly; occasionally the shrill but unintelligible voice of a child sounded through. Doc grinned evilly as he watched the milliammeter needle dance back and forth in step with the youngster's voice.

"That kid's doing his good turn for today," bantered Doc.

Bill, sullen and motionless, had all to do to disguise his rapid breathing. Inside, his heart beat like a trip-hammer.

Doc, manipulating the record, became talkative, almost friendly.

"Have a smoke," he offered, handing the amateur an expensive brand of cigaret.

"No!" "Okay," he laughed amiably, "maybe it's for the best. I've got to see a politician tonight yet and I'll have to feed plenty of these costly babies to that bird to get what I want."

Bill's expression of contempt did not escape the crook's eye.

"Look here," he said, laughing for the express purpose of irritating the amateur, "this will put you in a pretty bad light. I'd hate"—ironically—"to see you take the rap for operating off-frequency and interfering with police work. Say, you ought to get a cut out of this haul. I'll speak to the boys about it when they meet me here."

Then, for some reason or other, Doc was seized with a fit of laughter. It ended only when the door of the shack opened.

### Capture!

"Drop that gat, Mr. Doc Turk," came from the uniformed man obstructing the doorway.

But the order was unnecessary; Bill, smiling triumphantly, had in a flash knocked the automatic from the gang chief's hand.

It was only a matter of a few seconds and the speechless Mr. Turk was just another handcuffed criminal. His bewilderment was not lessened when he saw his entire gang herded into the shack, all like himself—handcuffed.

"We caught them on the way up here," explained Captain of Police, Carlsen, to the smiling amateur. "I got to hand it to you, son," went on the officer admiringly, "that was a neat trick you pulled. And such a tough bunch of . . ."

The captain stopped, interrupted by the raucous guffawing of one of his men. "Clancy!"

"I . . . I can't help it, Captain," choked Clancy, "just . . . just look at him!"

He pointed to Doc, and indeed, that one wore a ludicrous expression. Taken, as he was, unawares, Doc looked like an African native shown for the first time the Empire State Building.

Captain Carlsen fought back laughter but so did this unnatural repression strain and ache his diaphragm that the good man threw decorum to the winds and enjoyed a hearty laugh.

"Better tell him, boy, I can't stand that funny-looking face much longer!"

Bill nodded and addressed the perplexed gang chief.

"You made a big mistake," he began sarcastically. "In fact, for an ex-commercial operator, I'm surprised at you. Why I wonder with all your superior technical knowledge, did you put that record of my small brother's voice on the air? Don't you know that a child's voice is of higher frequency or pitch than an adult's?"

"Don't you remember," Bill continued patronizingly, "that a pure DC. note pierces through the air much easier than a low-frequency R.A.C. note? The same applies to voices. My little brother's voice pierced through the heterodyne squeal while the deeper-pitched rougher voices of the police did not. Yes, Mr. Turk, the kid did do his good turn for today!"

Doc Turk was still in a daze. He understood how a child's voice could pierce interference, but what of it? How . . . ?

Bill smiled.

"I think I can clear up all you'll want to ask by turning on the record that you, by your own hand, broadcast to the police!"

Bill pushed the pickup plug into a receiver jack labelled "phono" and the following piping voice of a child came through the loudspeaker.

"Dear Sanny Claus, bring me a great big elephant, a rockin' horsey, a . . . a . . . (here the mother prompted the child) . . . Oh yes, Sanny Claus, and I want a whole big box of chochits. My name is Tommy Jensen and I live at 346 Grant Street . . ."

"That's enough," interrupted Captain Carlsen hearing the siren of the "Black Maria." Then turning genially to Bill: "To tell you the truth, son, I'm more interested in another kind of record—these hoodlum's police records!"

## SHIELDED SHORT WAVE BATTERY SET

17 to 200 Meters

USING  
1-'30, 1-'32,  
1-'33, 1-'34  
LOW  
CURRENT  
DRAIN  
INEX-  
PENSIVE  
TUBES



COMPLETE KIT of parts with 2 sets of coils (8 coils) **\$8.95**  
With Tubes ..... **\$10.95**  
Completely Wired ..... **\$10.95**  
With Tubes ..... **\$12.95**

Tubes Guaranteed 3 Months

Foundation Kit, includes 1 Metal Case, 1 Chassis and 1 Shielded Compartment **\$2.45**

A REAL THRILL IN STORE FOR SHORT WAVE RECEPTION. Get Police reports, Ship-to-Ship and Amateur Conversations, also Short Wave Broadcast Stations.

LEOTONE RADIO COMPANY  
63 DEY STREET, NEW YORK CITY



1 WINDS LIKE A WATCH  
2 VISIBLE INK SUPPLY  
1+2= The Nozac\* (no sack). You know when it's filled, when to refill it. Demand the quick, easy, positive mechanical Nozac filling action. See the Nozac before you buy... Compare... \$5 and more. Other Conklin \$2.75, \$3.50 and more. Pencils \$1.00 and more... Ask your dealer.

THE CONKLIN PEN COMPANY  
Toledo  
Chicago San Francisco  
\*Proved by over 2 years of general public use.

Conklin  
NOZAC  
REG. U.S. PAT. OFF.  
SATISFACTION GUARANTEED

## \$20.00 Prize Monthly For Best Set

● THE editors offer a \$20.00 monthly prize for the best short-wave receiver submitted. If your set does not receive the monthly prize you still have a chance to win cash money, as the editors will be glad to pay space rates for any articles accepted and published in SHORT WAVE CRAFT.

You had better write the "S-W Contest Editor," giving him a short description of the set and a diagram. BEFORE SHIPPING THE ACTUAL SET, as it will save time and expense all around. A \$20.00 prize will be paid each month for an article describing the best short-wave receiver, converter, or adapter. Sets should not have more than five tubes and those adapted to the wants of the average beginner are much in demand.

Sets must be sent PREPAID and should be CAREFULLY PACKED in a WOODEN box!


The closing date for each contest is sixty days preceding date of issue (September 1 for the November issue, etc.)

The judges will be the editors of SHORT WAVE CRAFT, and George Shuart and Clifford E. Denton, who will also serve on the examining board. Their findings will be final.

Articles with complete coil, resistor and condenser values, together with diagram, must accompany each entry. All sets will be returned prepaid after publication.

REQUIREMENTS: Good workmanship always commands prize-winning attention on the part of the judges; neat wiring is practically imperative. Other important features the judges will note are: COMPACTNESS, NEW CIRCUIT FEATURES, and PORTABILITY. The sets may be A.C. or battery-operated. Straight Short-Wave Receivers, Short-Wave Converters, or Short-Wave Adapters. No manufactured sets will be considered; EVERY SET MUST BE BUILT BY THE ENTRANT. Tubes, batteries, etc., may be submitted with the set if desired, but this is not essential. NO THEORETICAL DESIGNS WILL BE CONSIDERED! The set must be actually built and in working order. Employees and their families of SHORT WAVE CRAFT are excluded. Address letters and packages to the SHORT WAVE CONTEST EDITOR, care of SHORT WAVE CRAFT Magazine, 96-98 Park Place, New York, N. Y.

# DATAPRINTS

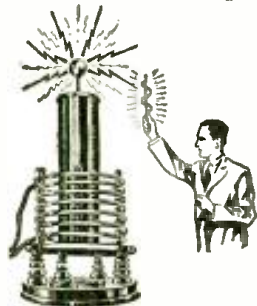

**Just the Technical Information You Need To Build Electrical Apparatus**

Dataprint containing data for constructing this 3 ft. spark Oudin-Tesla coil. Requires 1 K. W. 20,000 volt transformer as "exciter"; see list below.

..... \$0.75  
Includes condenser data.

## OTHER "DATAPRINTS" TESLA OR OUDIN COILS

- 80 inch spark, data for building, including condenser data.....\$0.75
- 8 inch spark, data for building, including condenser data; requires 1/4 K. W. 15,000 volt transformer; see list below..... 0.75
- Violetta type, high frequency coil data; 110 volt A.C. or D.C. type; 1" spark; used for "violet ray" treatments and "Experiments"..... 0.50
- How to operate Oudin coil from a vacuum tube oscillator..... 0.50
- 3 inch spark Tesla coil; operates on Ford ignition coil..... 0.50
- 3 inch spark Oudin coil; 110 volt A. C. "Kick-Coil"..... 0.50

### TRANSFORMER DATA

- Any size, 200 to 5000 watts. (1 Primary and 1 secondary voltage data supplied—specify watts and voltage desired).....\$0.60
- 1 k.w. 20,000-volt transformer data, 110-volt, 60-cycle primary. Suitable for operating 3 ft. Oudin coil..... 0.50
- 1/4 k.w. 15,000-volt transformer data, 110-volt, 60-cycle primary. Suitable for operating 8-inch Oudin coil..... 0.50
- Electric Welding Transformer (State secondary voltage)..... 0.50
- Induction Coils—1 to 12 inch spark data..... 0.50

### MAGNET COIL DATA

- Powerful battery electro-magnet; lifts 40 lbs.....\$0.50
- 110 Volt D.C. magnet to lift 25 lbs..... 0.50
- 110 Volt D.C. 300 lb. lift electromagnet..... 0.50
- 110 Volt D.C. solenoid; lifts 2 lb. through 1 inch..... 0.50
- 110 Volt D.C. solenoid; lifts 6 lb. through 1 inch..... 0.50
- 12 Volt D.C. solenoid; lifts 2 lb. through 1 inch..... 0.50
- A. C. Solenoid, powerful, 110-volt, 60-cycle..... 0.50
- MOTOR—1/10 H.P., 110 volt A.C. 60 cycle (suitable for driving 12" fan or light apparatus), constructional data..... 0.50
- 1200 cycle Synchronous motor..... 0.50
- 60 cycle Synchronous motor..... 0.50

**TELEGRAPHONE—Records Voices or "Code" signals on steel wire by magnetism. Code can be recorded "fast" and translated "slow". Construction data (special).....\$0.50**

**CLOCKS—Electric chime ringer. How to make one to fit on any ordinary clock..... 0.50**

### MISCELLANEOUS DATAPRINTS—

- Electric Ice Scales—How to make..... 0.50
- How to Thaw Pipes by Electricity (including 2 K. W. 110 vt. to 18 vt. transformer data)..... 0.50
- 20 motor circuits—hook-ups..... 0.35
- 20 practical telephone hook-ups..... 0.35
- Treasure Locator..... 0.50
- 100 mechanical movements for inventors..... 0.50
- Polarized Relay—(Ultra Sensitive)..... 0.50
- Electro-medical coil (shocking coil)..... 0.50

### REFRIGERATION MACHINE — Dataprint —

- How to Make Data..... 0.50
- Water-Wheels—How to build, and Light your house..... 0.50
- Model Ship Plans..... 0.50
- Public Address System..... 0.50
- Condenser Microphone..... 0.50

**20 "Electrical Tricks" for LODGES and PARTIES.....\$0.50**

How to Fry Eggs on Cake of Ice Electrically..... 0.50  
"Rewinding" Small Motor Armatures..... 0.50

Other DATAPRINTS on—Centrifugal Pump for Small Fountains, etc; Model Electric Train—will carry child; Compressed Air power plant for model planes; etc. Write for prices.

(20% Discount on all orders for \$3.00 or more. No. C.O.D.)

**The DATAPRINT COMPANY**  
Look Box 322 RAMSEY, N. J.

## Making An Automatic Key

(Continued from page 295)

posts, the two contact posts, and the lower bearing. Drill these holes in corresponding places to the diagram. Since the locations are not critical no dimensions are given. However, care should be taken to place the contact points exactly opposite the contact posts respectively and the lower bearing directly opposite the upper, i. e., in a perfectly vertical line.

The contact posts are adjustable binding-posts set on half-inch high bushings. A nail forms the contact arm. The point is sawed off and a brass contact is soldered on the head. Two of these are made, one for the dot and the other for the dash contact. The end stop is made the same with the contact omitted. As the middle stop requires precise adjustment and must hold its adjustment, it is constructed differently. A tapped bushing is the support. On this is soldered a quarter-inch bushing, threaded, with the hole in a horizontal plane. A 1 1/2-inch bolt is screwed into the horizontal bushing with a nut to lock the adjustment. With this arrangement precise adjusting can be accomplished. The lower bearing is simply a short bolt and two nuts. The end is drilled so as to give a cone-shaped hollow in which the pivot can rest. The two nuts (one above, the other below the base) lock this bearing into place. The pillar posts support the upper bearing plate. Through each of them is drilled a hole to accommodate a one-eighth inch bolt, one inch long, which holds the spring connected to the vibrating arm.


The upper bearing plate is triangular in shape and cut from the 3x3 piece of hard rubber. An old end bearing from a defunct Cardwell condenser is mounted in this piece. This provides a good top bearing. This plate is then mounted on the pillar posts. Next, the spring is cut in half and each half is connected between the arm and the pillar posts on each side.

### Wiring the Key

The key is wired by running a wire from the lower bearing to one binding-post; the other binding-post is wired to both contact posts. After wiring, the key can be connected to an audio oscillator and the final adjustments can be made. The bearings are adjusted until good electrical connection is obtained as well as a flexible but not too loose movement of the arm. The dash contact arm is set between 1/32 to 1/64 of an inch from the dash contact on the vibrating arm. The springs are adjusted so that the contacts do not touch when the arm is in a neutral position. The center stop keeps the dot contact from resting permanently against the dot contact post. It also regulates the speed of the dots to some extent. The end stop is so set as to prevent the dash contact from touching when the arm assumes the neutral position. A small weight on the end of the arm controls the rate of keying as it is adjustable. Though not essential, a knob may be placed on the side of the handle. This knob may be either a standard telegraph key knob or a replica moulded from plastic wood, painted black, and glued on. The knob adds both to the appearance and the ease of operation of the key.

This automatic key, if constructed with care, is very smooth in operation and neat in appearance. The speed can be regulated up to about thirty words a minute. As to operating such a key, dots are made by pressing the handle to the right, dashes to the left. The number of dots made is determined by the length of time that the handle is pressed to the right. For "e" only a very quick touch will suffice; for "i" a little longer, etc. A loose wrist motion is good with the hand resting on the small finger side. The hand is then swung from left to right, the thumb on the left side of the handle and the first two fingers on the other side.

# NEW

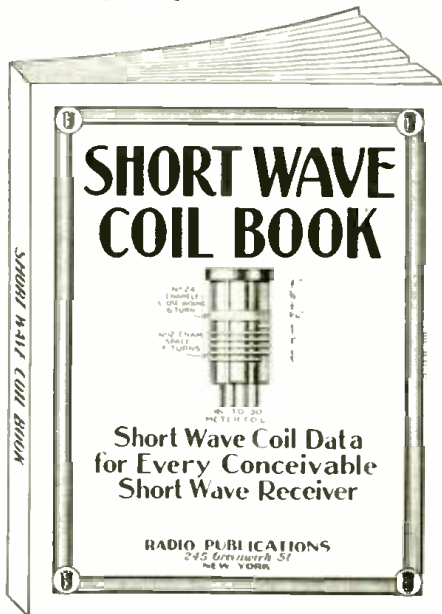

**FOR** the first time, it is now possible for the experimenter and short wave enthusiast to obtain the most exhaustive data on short wave coil winding information that has ever appeared in print.

As every experimenter who has ever tried to build a short wave set knows only too well by experience, the difference between a good and a poor receiver is usually found in the short wave coils. Very often you have to hunt through copies of magazines, books, etc., to find the information you require. The present data has been gotten up to obviate all these difficulties.

Between the two covers of this book you now find every possible bit of information on coil winding that has appeared in print during the past two years. Only the most modern "dope" has been published here.

No duplication. Illustrations galore, giving not only full instructions how to wind coils, but dimensions, sizes of wire, curves, how to plot them, by means of which any coil for any particular short wave set can be figured in advance, as to number of turns, size of wire, spacing, etc.

There has never been such data published in such easy accessible form as this.

Take advantage of the special offer we are making today, as due to increasing costs, there is no question that the price will increase soon.

**RADIO PUBLICATIONS**  
245 Greenwich Street  
NEW YORK, N. Y.

Radio Publications,  
245 Greenwich Street,  
New York, N. Y.

Please send immediately upon publication, your Short Wave Coil Book, for which I enclose 20c herewith (cash, U. S. stamps or money order acceptable). Book is to be sent prepaid to me.

Name.....

Address.....

City and State.....

## 2-Tube A.C. Receiver

(Continued from page 279)

resistor used with the detector tube, but this method is used in obtaining the bias for the second tube. The cathode of the detector connects direct to ground.

Tests made with a Weston 547 type testing outfit, under normal operating conditions as I use the outfit, reveal the following characteristics: detector tube, fil. voltage, 1.50; plate current, 1.3 milliamperes, plate voltage 37 volts; amplifier stage, fil. voltage, 1.65; plate current, .7 milliamperes.

### Circuit Found Very Stable

I find that it is rarely necessary to vary the coupling between antenna coil and grid coil—but if regeneration can be controlled to the point of maximum sensitivity (point of oscillation), it is best to bring down the antenna coil to the closest possible coupling, so as to secure the strongest input signal. The circuit is remarkably stable in operation, possibly because of a happy chance in the location of the various circuit-assembly layouts. I find that despite the theory that placing the tuning coil assembly directly between the grounded tube caps should, in a sense, introduce losses—it seems to result in greater stability. I can adjust the oscillation condenser to a point of greatest regeneration, without going off into "sudden oscillation." In fact, there is a leeway of ten points on the dial, in the case of receiving broadcasting. For a fellow who has made such outfits before, and has found that his oscillation condenser had to be worked to a "hair," as it were, he will appreciate such stability. The only shielding I have on the set is at the tube caps. I found it necessary to have at least one of them, on the detector, or the tube started to "howl." The other one on the second stage was put on merely for the sake of better symmetry of appearance. During the past weeks, I tried other and additional methods of shielding, copper sheathing the outside of the wooden case, etc., but found it "pulled down" my signal strength, and provided no better stability than it had before. Where the wiring penetrates up from the top of the base to tubes, coils, etc., I still have a layer of copper sheathing, which is ungrounded; to remove this would have necessitated unsoldering the various connections, which I declined to do. Perhaps it helps, but I know it doesn't hinder,—so it stays on. All other shielding has been purposely removed—for I find I do not need it.

### No "Dead-Spots"!

Here is another thing I appreciate on this receiver—there are no "dead spots" in tuning, and again I hit the nail on the head "right smack," the first time I wound the various coils on the tube-bases. The turns were about right—a little overlapping between coils, which is desirable, and when capacity for oscillation was needed, the 17 plate condenser had it on hand. It is possible I could dispense with some of its plates, but it is better to let well enough alone. Using an antenna tuning coil was nothing new to me, but the happy part of this particular layout is that the set "perks" and uses the antenna coupling—you don't have to move it a mile away from the grid tuning coil, for fear the set can't be made to oscillate, if you want it to. Close coupling is helpful, instead of detrimental, as some amateur set-builders have so frequently found in the past, to their amazement!

The point of my story is, that this set "perks" better than any I have ever made before. Daventry, England, GSA, is received nightly at will, and its next door neighbor, DJC, Germany, is always there when you want it. In fact, I just tune 'em in and sit back and relax. Sometimes I have to get up and reduce the volume a bit, for the Zenith 12 inch speaker can deliver plenty of output, and you don't have to sit close to the speaker to hear it. EAQ, Madrid, is a "regular," as well as some Latin station, (not XDA, Mexico

City,) who fails to announce in English. Have heard France, and of course, the usual number of "foreign" code stations.

If any owner of a Zenith radio receiver desires to build a set of this type, I shall be glad to hear from him and give him further information, if he so desires it. Of course it is entirely possible that the power supply can be taken direct from the Zenith receiver, but it will involve some difficulties. Off-hand, I would advise a separate power supply.

The value of the grid tuning condenser is .00012 mf.; oscillation control condenser .00025 mf. Detector grid-leak value is 4 megohms and its by-pass condenser capacity .0001 mf.

### Parts List

Antenna coil—5 turns of No. 20 enameled wire, wound on 1 1/2" diameter bakelite ring.  
Coil No. 1 (grid-filament) 6 turns, No. 24 enameled wire, close wound, on tube base. (Plate) 6 turns, No. 24 En. wire. Spacing between both windings approx. 3/16".

Coil No. 2 (grid-filament) 14 turns, No. 24, En. wire, close wound. Plate coil, 8 turns, same wire. (Spacing between grid and plate coils, 3/16".

Coil No. 3 (grid-filament) 30 turns, No. 24, En. wire. (Would advise adding about 4 to 6 turns additional). Tunes short of 200 meters. Plate coil 10 turns, No. 24 En. wire, close wound. Spacing between grid and plate coils, 1/16" to 1/8".

Grid-coil tuning condenser, 8 plates, 2 1/2" circular rotor, obtained from old style TRF receiver. Capacity .00012 mf. (Removed 9 plates for better tuning control.)

Plate-Grid coil variable condenser, (regeneration and oscillation control) a 17 plate type, same specifications as that above, but use all of the plates. Capacity, .00025 mf.

R.F. Choke—80 MH. inductance.  
Audio Transformer; 3:1 ratio.  
Cathode resistor, R1, (audio stage,) 1000 ohms, 2 watt metallic type. Cathode by-pass condenser C1 same stage, .0001 mf.  
Plate resistor, R2, (audio stage) 20,000 ohms.

Coupling condenser, C3, to input jack of Zenith "Phono" connection; 1 mf. (fixed).

Aerial selector switch—home-made; used assembly of old type battery-operated Atwater-Kent 1 dial TRF receiver, consisting of mounting for filament toggle switch and filament resistor, (variable). The switch (toggle) opens or closes connector lead between phone jack and output from plate of 2nd tube.

## U. S. W. Transmitter and Receiver

(Continued from page 283)

in the grid and plate circuits of the detector are the usual tuning and regenerative coils of the tuned circuit. The values of these coils as well as those for the tuned grid and tuned plate of the push-pull transmitter can be found by experiment, depending on the wavelengths to be used.)

**A Lot  
of New S-W  
Circuits  
In the October  
Issue!  
Don't Miss IT!**

## NEW ALDEN S. W. COILS

Precision wound coils with the convenient gripping-rim for easy insertion and removal from socket.

Set of four precision wound short-wave coils—20 to 200 meters with .00014 mfd. condenser.

704SWS List Price \$2.00 net

NEW! 706SWS Set of four 6-prong wound coils with pri., sec. and tickler windings. 20-200 meters with 140 mfd. condenser. Use standard tube socket.

706SWS. List price. Set..... \$3.00

Set of two coils to cover 100 to 540 meters with .00014 mfd. condenser.

704SWS and 704SWO. List Price..... \$1.50

Genuine Maklot Coil Forms with color-coded easy-grip rim. 1 1/2 in. dia. x 2 in. winding space. Red, Yellow, Green or Blue.

704—4-pin coil form. List... 25c  
705—5-pin coil form. List... 25c  
706—6-pin coil form. List... 30c

Send for latest S. W. Sheets showing coils, sockets, plugs, etc. Send for new Analyzer Rewiring Dope Sheet and data on using new tubes in place of old types.

**ALDEN PRODUCTS CO.**  
Dept. SW9 715 Center St.  
BROCKTON, MASS.

## THE "PRIZEWINNER"

As described in June Issue

**AC-DC Short Wave Receiver**



Completely Self-Powered Latest Type 77, 43, 2525 Tubes 15 to 200 Meters

THE PRIZEWINNER is complete. No extras, such as power supply, coils, etc., to buy. Power supply is built-in and will operate on EITHER AC (117 DC) (Four coils included), cover all bands. 20,000 KC to 1,500 KC!

Complete kit of PRIZE WINNER parts identical in every respect with those used in built-up models, complete in every detail including hardware, hookup wire, solder, coils, etc., and also includes the cabinet and dial. Price..... \$8.95

Set of Genuine RCA or Ataturk tubes for prize winner... \$3.75  
Assembled, wired, tested and enclosed in beautiful crackle finish or Cadmium Plated metal cabinet ready to plug into your power line. Complete with four coils... \$10.95

Send for full particulars and Diagram  
**ALAN RADIO CORP., 83 S. Cortlandt St.**  
New York City

## THE NEW AND IMPROVED

## VELOCITY MICROPHONE KIT

Excellent fidelity characteristics. Frequency response 30 to 14000 cycles per second. Not subject to variations with humidity and temperature. Substantially free from resonance peaks. Easy to assemble, not critical in adjustment.

**DEALER'S PRICE \$5.88 Net**

**TRANSFORMERS TO MATCH**  
R. L. Ribbon to 200-500 ohm line \$4.50 Net  
R. G. Ribbon to Grid \$4.50 Net  
L. G. 200 ohm Line to Grid \$4.50 Net

Model R. V. Velocity Microphone assembled with extra sensitive dual ribbon. Factory tested and guaranteed.

**DEALER'S PRICE \$11.76 Net**

**BRUNO LABORATORIES, 20 W. 22nd St., New York**

## SHORT WAVE PARTS AT LOWER PRICES!

Lynch "No-Stat" Broadcast Antenna Kits, complete... \$ 2.50  
Filterformer Antenna Kits, eliminates noises, complete... 1.98  
866 M.V., guaranteed... 1.39  
210's, guaranteed... 1.19  
281's, guaranteed... 1.19  
National SW-3 Short Wave Receivers, less tubes... 14.25  
PYREX INSULATORS stocked... Write for prices!  
Cardwell Transmitting Condensers stocked.  
National Distributors of Chokes, Power, Transmitting, Filament and Plate Transformers. Any Transformer made to order. Send in specifications for our quotation. Write for Free Bulletin full of bargains. 20% with C. O. D. orders, include postage.

**Maurice Schwartz & Son**  
710-712 Broadway Schenectady, N. Y.

**FREE RADIO CATALOG**  
**1934 RADIO CATALOG**  
Write for our new catalog now on the press... most complete line of latest radio sets, service men's supplies, replacement parts at lowest wholesale prices.  
**ALLIED RADIO CORP.**  
837 W. Jackson Blvd. CHICAGO

# A REAL S. W. GLOBE



## A Man's-Sized Globe for Short-Wave Fans

Here, at last, is the most marvelous globe bargain of the world. It's a big fellow, as you can see in comparison with the standard telephone set. The globe measures 12 inches in diameter, and the total height, with pedestal, is 16 inches. The globe is printed in some fourteen different colors, and is waterproof, so that it can be washed without trouble. The "Meridian" in which the globe moves is made of highly polished and nickel-plated metal, while the base is a beautiful dull black. A simple lock "A," makes it possible for you to change the angle of inclination, for easier inspection and measurement. Only the best of material is used in the making of this globe, and this is the first time that a large globe of this kind has been sold at such an extremely low price.

Only with a world globe of this kind is it possible to get a true picture of the relation of countries to each other, air-line distances, etc. For instance, which is nearer to New York—Moscow, Russia, or Rio De Janeiro, Brazil? Capetown, South Africa, or Tokio, Japan? Honolulu, Hawaii, or Lima, Peru? You will be amazed when you actually come to measure the distances. This is best done by stretching a string over the globe. In such a way that it passes directly over the two cities or two points in question. Not only is a flat map deceptive but, when it comes to distance, it is all wrong. The true measurements can be made only on a globe. This globe is big enough to give your den or room a professional appearance; and those who own them would not part with theirs. The low price we are quoting is for introductory purposes; it must be increased in a short time.

The World Short-Wave Globe, as illustrated, 12-inch diameter, 16 inches high. Authentic, up-to-date (published late 1932); over 7,500 names and places—there have been 1362 official changes in the past ten years. Spelling conforms to rulings of U. S. Department of Commerce, and Royal Geographic Society, London, England. Names as they are spelled by

### HOW TO ORDER

Send money order, certified check or check (be sure to register letter). Enclose sufficient money for parcel post otherwise must ship express collect. Shipping weight 8 lbs.

their local broadcasters. Washable lacquer finish; movable-meridian style of mounting. Smart modern base design in black, polished nickel meridian. All globes are packed in a carton for safe shipment, and we guarantee delivery in perfect condition to you. List price, **\$3.75**. Your Special Price.....

**SHORT WAVE CRAFT 98 Park Place New York City**

## THE "HAM" SECTION OF SHORT WAVE CRAFT

is now recognized as a market place where goods can be disposed of in the quickest and most economical way. Its rapid growth is the best evidence of this and the many letters that we receive monthly testify to the faith that the amateurs, experimenters and dealers have in this advertising medium.

### SWAPPERS

SWAPPERS are swappers of correspondence. During the past few years we have noted that Short-Wave enthusiasts love to get acquainted with each other by mail in order to swap experiences.

Use a postcard only. Never write a letter. Address postcard as follows: SWAPPERS, c/o SHORT WAVE CRAFT, 96-98 PARK PLACE, NEW YORK, N. Y.

On the blank side of the postal PRINT clearly your name, address, city and State; nothing else! No charge for this service.—EDITOR.

- ROGER C. AMUNDSEN  
4 Broadview Ave., East Norwalk, Conn.
- ROBERT L. ANDERSON, W8ALZ  
501 North Miami St., West Milton, Ohio
- WILMER ANDERSON  
152 W. Water St., Rockland, Mass.
- JEAN M. ANDRAUD, USNR (Ex. Op.)  
42 Morton St., New York City
- ALBERT C. ARTERBURN  
30 Crescent Place, Yonkers, N. Y.
- JDHN BAK  
2801 W. 2nd St., Chester, Pa.
- JIM BAKOGEORGE  
Barrie, Ont., Canada
- WILLIAM BANYAI  
36 Blossom St., Fitchburg, Mass.
- JOSEPH BARMACKI  
34 W. 16 St., Linden, N. J.
- GEORGE BAYLIN  
210 Aisquith St., Baltimore, Md.
- ROBERT H. BENNETT  
227 Greylock P'kway, Belleville, N. J.
- RAYMOND BENT  
623 W. Wash. St., Hagerstown, Md.
- RAY BIRREN, W9MSG  
5733 Wilson Ave., Chicago, Ill.
- MICHAEL J. BLACKWELL  
1355 Agnes Place, Memphis, Tenn.
- MICHAEL L. BLASKI, JR.  
221 N. Penna. Ave., Wilkes-Barre, Pa.
- GEORGE W. BONIN  
736 Pine St., Central Falls, R. I.
- TED BOSWORTH  
182 Marmion St., East Fremantle, Western Australia
- BILL BOTTRILL  
Box 58, Cass City, Mich.
- WILLIAM E. BRENTLINGER, W9NTS  
1625 S. 11 St., Terre Haute, Ind.
- GEORGE W. BROWN  
155 Holland Street, Fremantle, West Australia
- ROBERT BUEHN  
1411 Jefferson Dr., Mt. Lebanon, Pittsburgh, Pa.
- WILLIAM F. BUHL  
600 Bergen St., Clinton Hill Station, Newark, N. J.
- CAPT. JOHN D. BUSHELL  
95-30-A 89 St., Ozone Park, Long Island, N. Y.
- GODFREY CASSAR  
330 8th Ave., New York City
- FRANK CERNEY  
13214 Svec Ave., Cleveland, Ohio
- FRED CHADWICK  
616 Main St., Southbridge, Mass.
- DONALD E. CHESSER  
223 Meek Ave., Byesville, Ohio
- H. D. CHING  
P. O. B. 873, Hilo, Hawaii
- EDWARD W. CLARKE  
335 Rehner Street, Greensburg, Pa.
- TRUMAN CRAINE  
37 North Fourth St., Meriden, Conn.
- HENRY CLOUD  
81 Hanley Street, Memphis, Tenn.
- DONALD CONNER  
Box 65, Fullerton, Nebraska
- SGT. SALVATORE CRACOLINI  
520 Rutland Road, Brooklyn, N. Y.
- DEANS CPUMLER  
Bidea-Wacc, Latta, S. C.
- W. H. CURRY  
Rt. 2, Box 62, San Jose, Calif.
- ULY DAPARMA  
2138 Belmont Ave., Bronx, N. Y.
- JOSEPH I. DE BETTENCOURT, W3CXJ  
3905 13th St. N. E., Washington, D. C.
- O. J. DEMAREST  
1314-8th Ave., Watervliet, N. Y.
- STEHAN DOBISZ  
35 Sterling St., East Orange, N. J.
- JULIUS W. FANTASKI  
853 High Street, Verona, Pa.
- EDWIN M. FARMER  
309 Court St., Portsmouth, Ohio
- C. M. FEAY, W6EJZ  
4322 E. 58 St., Maywood, Calif.
- HOWARD R. FIELDING  
36 Haines Ave., Lowell, Mass.
- BILLY FIELDS  
422 Third St., Albany, Ga.
- FERRIS JAMES FINNERTY  
Lock Box 3, Twining, Mich.
- ARTHUR FLINT  
19 Nelson Rd., Ellesmere Port, Wirral, Cheshire, England
- JOHN FOLEY, W2EUN  
619 Leland Ave., New York City
- SANFORD FOSHOLDT  
Rudd, Ia.
- CHARLES W. FRAME  
1404 Edgmont Ave., Chester, Pa.
- ALBERT FRIESE, JR.  
446 N. Main Ave., Scranton, Pa.
- A. L. FULGINITI  
328 W. Main St., Girardville, Pa.
- RALPH R. GARRICK  
844 Homestead Ave., Beechwood, Upper Darby, Pa.
- RALPH GARRISON  
Metamora, Ind.
- JOHN S. GAYDOSH  
75 Wesley St., Clifton, N. J.
- I. GERSTENFELD  
2410 Pacific Ave., Atlantic City, N. J.
- C. H. GERE  
714 S. Joe St., Rapid City, S. Dak.
- ALBERT GOLDMAN, W3CUG  
107 Wood St., Bristol, Pa.
- P. J. GOTZSCH  
Lain vun Eil en Duinen 171, Hague, Holland
- JAIIME GREEN  
131 Cantera Street, Ponce, Porto Rico



WILLIAM C. GREENE  
123 S. Central Ave., Somerset, Ky.

MARVIN GURLIN  
R. 1, Box 149, Berlin, N. J.

ROBERT BAAS  
49 Grand View Ave., Ft. Thomas, Ky.

ELLIS K. HAMER, W7BQG  
2705—2nd Ave., No., Great Falls, Mont.

WILLIAM HASLETT  
216 E. Wishart Street, Philadelphia, Pa.

MAX HELLMAN  
205 Powell Street, Brooklyn, N. Y.

JOHN L. HUNTER  
Route 4, Greensburg, Ind.

CHAS. R. HUTCHCROFT  
Box 58, Indianola, Ia.

RICHARD HYDE  
F. O. B. 347, Arvada, Colo.

G. C. HUNT, JR.  
Rockmart, Ga.

CLINTON HURD  
Arvada, Colo.

WELTON JACKSON  
Route 4, Boaz, Ala.

ARDELL JOHNSON  
Company 645 C. C., Reforestation Camp, Scott  
Lake Camp, Three Lakes, Wisc.

ROBERT JONES  
1360 Crescent Rd., S.W., Canton, Ohio

HARRY E. KENTZEL  
Averill Park, Rens. Co., N. Y.

EDWARD T. KLASH  
823 Lex. St. W. Phila., Pa.

OLIVER F. KLEIN  
2235-N. 39 St., Milwaukee, Wisc.

STANLEY M. LADAGE, W3BYK  
923 N. 27 St., Camden, N. J.

CHARLES LAFKOFF  
35 Hinsdale St., Brooklyn, N. Y.

MAC LESTER  
39 Sweetland Ave., Ottawa, Ont., Can.

GEORGE LINDNER  
209 Avenue F., Brooklyn, N. Y.

BEN F. LOCKE  
Marthaville, La.

JOSEPH M. LOEFFLER  
327 S. 7th St., Saginaw, Mich.

AL LONDEMA  
940 Dresden Ave., Salt Lake City, Utah

ROBERT LOSSE  
1820 N. 40th St., Milwaukee, Wisc.

RICHARD K. LYONS  
133 S. 4th Ave., Coatesville, Pa.

WARREN MALLORY  
915-15th St., Boulder, Colo.

MICHAEL MALYSKO  
3098 Playfair Street, Hamtramck, Mich.

JOHN V. MANSHEIM  
R. F. D. 3, Fort Madison, Ia.

BERNARD MIDDENDORF  
1000 South Crescent Ave., Park Ridge, Ill.

H. C. MILES  
221 Sherman Ave., New York City

ALWYNE MILLER  
22 Steiner St., Lawrence, Mass.

LLOYD S. MILLER  
202 Hickory Ave., Tenafly, N. J.

JAMES A. MONTIOR  
229 Summit Ave., Bogota, N. J.

JOSEPH MOORE  
Ayer Rd., R. F. D. No. 2, Williamsville, N. Y.

GUSTAVUS A. MORGAN, JR.  
Box 355, Santa Ana, Texas

ELMER NEUMAN  
224 Woodstock Ave., Swissvale, Pa.

THEODORE R. ODENATH  
169 St. Charles Place, Atlantic City, N. J.

H. OESTERLE  
118 E. 116 St., New York City

ELBURN OXNER  
Route 8, Waco, Texas

ROY OZAWA, W6FOJ  
Rt. 1, Box 303, Cupertino, Calif.

GEORGE PASQUALE  
100 N. Main St., Wellsville, N. Y.

JERRY PILGRIM  
5743 Kingsley Circle, Oakland, Calif.

RADIO-RAVALICO  
Casella 100, Trieste, Via Imbriani, 16, Italy

FRANK RANCE  
120 Bowling St., Cedar Rapids, Ia.

EDMUND D. REGAN  
29 Overhill Rd., Stonehurst, Pa.

HERBERT E. RILEY, W6ZZBC  
919 E. Madison St., Phoenix, Ariz.

FRED H. ROBERTS  
488 Briar Hill Ave., Toronto, Ont., Can.

J. H. ROSENFELDER  
102 E. Vine St., Oxford, Ohio

ARTHUR ROUSE, JR.  
44N Mulberry St., Richmond, Va.

SOL RUBIN  
2086 Blaine Ave., Detroit, Mich.

CHARLES E. RUSSELL  
1006 E. 5th St., Coffeyville, Kans.

AL SANTMIER, JR., W8AKX  
150 South Main St., Doigeville, N. Y.

EDW. SAUNDERS  
P. O. B. 346, Glenview, Ill.

FRANK J. SCHRAMMEYER  
1510 N. 26 St., Philadelphia, Pa.

PAUL E. SEAWARD  
1140 S. Eleanor St., Pomona, Calif.

HOWARD STILL  
Box 553, Ontario, Ore.

NED A. SOSEMAN  
R. 5, Bloomfield, Ia.

CHARLES SOVATSKY  
169 W. Ridge St., Nanticoke, Pa.

LESLIE E. STILES, USNR, WIDUC  
Lebanon, Conn.

EDWARD SUNDIN  
820 Cass Ave., Iron Mountain, Mich.

LELAND TANGEN  
1517 Ave. N., Grand Forks, N. Dak.

HAROLD TEAR  
1517 Thomas Ave., Roanoke, Va.

RUSSELL TWIST  
R. No. 1, Bonner Springs, Kansas

JOHN UNBAN  
3016 Jacob St., Hamtramck, Mich.

UNCLE JOE'S RADIO SHACK  
1 Joseph Whalley, 401 Springdale St., Cumberland, Md.

R. P. VAN BUREN  
2701 A Floyd Ave., Richmond, Va.

GEMINIANO F. VICTA  
10 Yacal St., Manila, P. I.

KEN VOGT  
321 N. Front St., Fremont, Ohio

DOUGLAS WAGNER  
2744 Market Ave., E. St. Louis, Ill.

LEO WALLACE  
47 Lockwood Ave., Yonkers, N. Y.

BENNY WALTERS  
Lloyd, Pa.

DAVID M. WALTERS  
202 Aisquith St., Baltimore, Md.

CHARLES WEBSTER  
1155 North Prairie St., Galesburg, Ill.

D. W. WEIR  
327 S. Humphreys Ave., Los Angeles, Calif.

FRANK WENCEL  
2614 Evalina St., Hamtramck, Mich.

ELLIS E. WOOD, JR.  
878 E. 28 St., Oakland, Calif.


GEORGE WOOD  
4, Elmfield Road, Davenport, Stockport, Cheshire, England

ELBERT E. WOODIS, JR.  
71 North Main St., Webster, Mass.

JOE B. ZAVATKY  
6310 Hamman St., Houston, Texas

E. ZIMMERMAN  
377 Madison St., Passaic, N. J.

**FREE** 116 Page **RADIO** and **SHORT WAVE** **TREATISE**



Avail yourself now of the opportunity to receive the free 1933 summer edition of our Radio and Short Wave Treatise, No. 26. It is a splendid package of useful information, radio stems, diagrams, illustrations, etc. Considerably larger and more instructive than our No. 25 issue. If you had our treatise No. 25 and incidentally all our previous issues, you are familiar with the type of book we publish; but the new No. 26—what a book! The entire editorial section is new from beginning to end—not an old word remains. Considerable space has been devoted to articles for the radio beginner. This alone is worth its weight in gold. The Superheterodyne principle is thoroughly explained in this issue in clear, simple language. No. 26 is not just another catalog. It contains more valuable and up-to-date information than can be found in any radio text book on the subject.


**Over 100 New Hook-Ups, Etc. 1000 Illustrations.**

**PARTIAL LIST OF CONTENTS**  
Fundamental Principles of Radio—Ohm's Law—Discussion of New Tubes—Constructing a Triple Tuning Amplifier—Constructing a Tiny A.C.-D.C. Portable Receiver—All About Superheterodynes—Eliminating Man-made Static—Constructing a Two-tube Short Wave "Globetrotter" Receiver—Completely revised and up-to-date Radio Tube Chart—\$5.00 Prize Suggestions—Radio Kinks, Etc., Etc.

**WRITE TODAY. Enclose 4 cents for postage. Treatise sent by return mail.**

**RADIO TRADING CO.**  
100A Park Place New York City

**•DID YOU GET YOUR COPY?**



Thousands of amateur radio items, at the lowest prices, are contained in this FREE Big Book.

Contains articles by McMurdo Silver, Arthur H. Lynch, I. A. Mitchell, Henry McArthur, and many others.

**AMERICAN SALES CO.**  
Wholesale Radio Distributors  
44 W. 18th St., N. Y., N. Y.  
The Oldest Amateur Supply House, Est. 1919

**SEND FOR YOUR FREE 1933 RADIO CATALOG**

COAST TO COAST RADIO CORPORATION  
123 E. WEST 17th STREET NEW YORK, N. Y.

WE WILL NOT BE UNDERSOLD!

**Patents—Trade-Marks**

All cases submitted given personal attention by members of the firm.

Form "Evidence of Conception" and instructions "How to Establish Your Rights"—Free

**LANCASTER, ALLWINE & ROMMEL**  
Patent Law Offices  
434 Bowen Bldg. Washington, D. C.

**BEGINNERS TRANSMITTER**

Complete with coils and tube \$5.45. Every transmitter tested on at least 500 mile QSO! POWER SUPPLY, complete with tube \$4.95. MONITOR, coils, tube, batteries, fully tested \$5.15. For full information write

**RADIO FREQUENCY LABORATORIES**  
854D-152 St., Jamaica, N. Y.

**Preventing "Tuning Holes"**

(Continued from page 284)

as the fundamental of the open circuit, or to any one of the harmonics of that fundamental frequency. This does not apply to those receiving sets employing a screen-grid buffer tube between the detector tube and the open circuit. By the open circuit is meant that circuit to which the aerial and ground leads are connected. The trouble is caused by the open circuit absorbing so much energy from the receiving set at those particular frequencies that there is not enough energy remaining to keep the set oscillating; and it seems that this always happens at a point on the scale where some station whose reception is particularly desired is transmitting.

A simple remedy for this condition is to connect a winding of about two turns of heavy wire, with a diameter of approximately two inches, in series with the antenna and primary coil. This winding should be placed far enough away from the secondary circuit so that no coupling will exist between them. This two-turn winding is normally short circuited by a switch; but when the receiving set is tuned to one of the frequencies at which it normally stops oscillating, the switch is opened, putting the coil in circuit. This changes the fundamental frequency of the open circuit which now allows the set to oscillate at all of those frequencies which were harmonics of the former open circuit frequency.—Charles Felstead.

**5 to 7 Meter Super-Regenerative Set**

(Continued from page 283)

of 50 mmf. (0.00005 mf.) and is of the type usually employed for trimming purposes. The two H. F. (R. F.) chokes, Choke 1 and Choke 2, come within the category of special components and can, if desired, be home-made. A coil consisting of 50 turns of fine gauge wire spaced to occupy 1" and wound on a ½ inch former would do.

The quenching coils, L3 and L4, are wound on a two-section bobbin built up from thin plywood ½ inch thick. The outside diameter is 2¼ inches, while spacers of the same wood, 1 inch in diameter, separate the three larger discs, thus forming two adjacent spools of wood. A machine screw through the center secures the wooden discs. Each slot contains 500 turns of No. 34 enamel wire, and both the coils are wound in the same direction. Their respective inner and outer ends are connected as marked on the circuit diagram.

For the small tuning coils, L1 and L2, three turns only of No. 14 B&S tinned copper wire are required in each case. They are wound on a ¾ inch former, and the turns spaced to occupy ½ inch in length. Both coils are wound in the same direction and when assembled this relation must be maintained. That is to say, ignoring the presence of C1, coils L1 and L2 may be regarded as one continuous winding. The aerial coupling coil L is a single turn having the same diameter as the others, and all three coils are spaced ¾ inch apart.

# At Last!


## OFFICIAL SHORT WAVE LEAGUE LOG AND CALL BOOK

WE ARE happy to present to the thousands of short wave fans this new Log and Call Book, which enthusiastic readers of Short Wave Craft have been urging us to publish. Here is a book that you will feel proud to possess because it reflects your patience and perseverance in logging distant stations. It is a record you will be proud of in days to come. That, however, is not all. The Log and Call Book is the finest and most complete book of its kind ever published. There is nothing like it on the market now, nor was there ever a book published like it before.

Published Quarterly\*

### PARTIAL CONTENTS

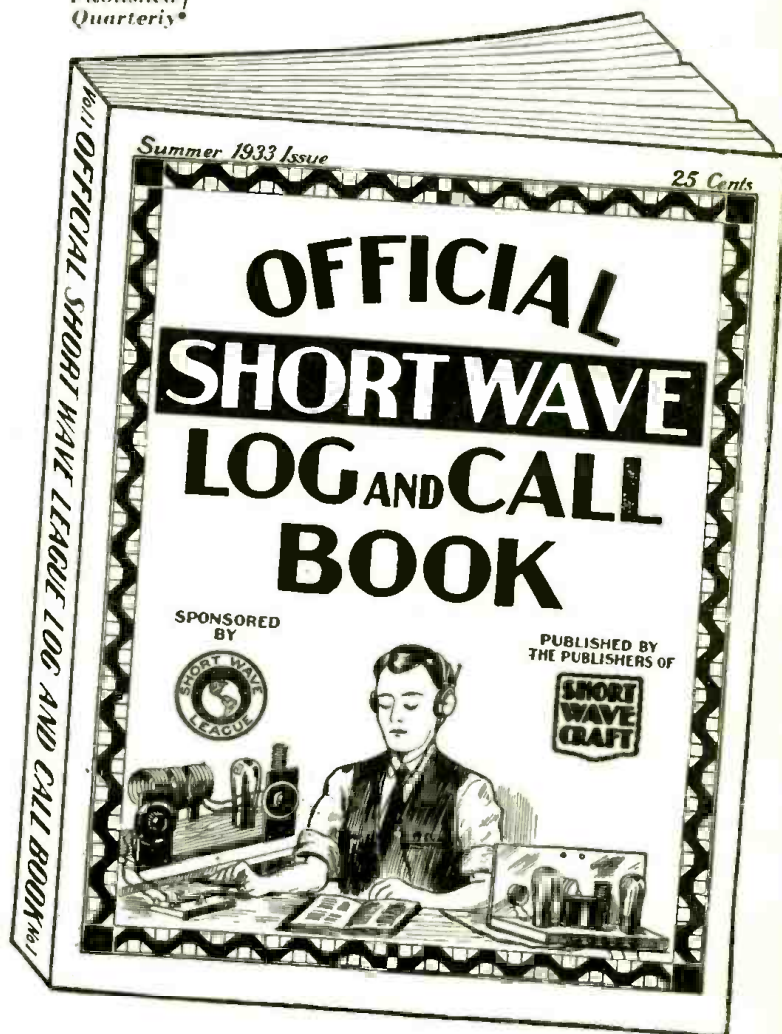1. It contains the largest listing of short wave stations in the world, a much larger list in fact than the list published in SHORT WAVE CRAFT, or any other magazine. Due to space limitations, no regular magazine can publish all the world stations. There are so many short wave stations, such as telegraph stations, experimental stations, ship stations, and others, which normally cannot be included in any monthly magazine list, but frequently you hear these calls and then you wish to know from where they originate. The OFFICIAL LOG AND CALL BOOK gives you this information, besides a lot of other information which you must have.
2. A large section of the book is set aside where the calls can be listed in a proper manner. This log section gives the dial settings, time, date, call letters, location, and other information. Thus, when you hear a station, you make a permanent record which is invaluable.
3. Another section has squared-paper pages on which you can fill in your own frequency (wave-length) curve for your particular receiver. This helps you to find stations which otherwise could never be logged by you.
4. A distance chart showing the approximate distances between the principal cities of the world.
5. A meter to kilocycle conversion chart. Many of the short-wave broadcasters announce their frequency in the latter scale when signing off and many listeners do not know the relation between them.
6. A list of international abbreviations used in radio transmission.
7. The complete Continental code used in all radio work.
8. A list of International Call Letter Assignments; Around the Clock Listing Guide.
9. In addition to this, you will find included a map of the world, with time indications and a host of other useful information which aids you in logging distant stations thousands of miles away.



This is one of the finest books that the publishers of SHORT WAVE CRAFT have ever turned out. You will be proud to possess it.

The size of this book is 9x12 inches, same size as SHORT WAVE CRAFT magazine. It is printed on a good grade of paper, and has a heavy durable cover.

### Mail this Coupon Today!

SHORT WAVE CRAFT  
96-98 Park Place,  
New York, N. Y.

Gentlemen: I enclose herewith 25c for which send to me prepaid, immediately upon publication a copy of your new book OFFICIAL SHORT WAVE LEAGUE LOG AND CALL BOOK. (Send money order, check, cash or new U. S. Stamps. Register letter if it contains stamps or currency.)

Name.....

Address.....

City..... State.....

SW-933

**FOR SALE ON ALL PRINCIPAL NEWSSTANDS**

PRICE  
**25c**

As only a limited quantity was printed for the first issue, it is possible that your newsdealer sold out his supply. Should you not be able to secure a copy at your newsstand, use the handy coupon.

**SHORT WAVE CRAFT**

96-98 PARK PLACE

NEW YORK, N. Y.

The  
NATIONAL  
Seven-Tube  
Short Wave  
Superheterodyne



Incorporating many features usually found only in commercial receivers, the FB-7 anticipates the requirements of even the most advanced enthusiast. Tremendous sensitivity is taken for granted in modern short-wave receivers, but such vital features as stability, high signal-to-noise ratio, true-tracking and strictly single control tuning make the FB-7 outstanding. Write for a complete description of this remarkable receiver, then go to your dealers and compare it with any other receiver.

**NATIONAL COMPANY, Inc., Malden, Mass.**

**FB.7**

# CHOICE OF THE EXPERT

THE SUPER QUALITY RADIO TUBE



Licensed Under RCA Patents — Guaranteed

*Van Dyke*  
RADIO TUBES  
*for*  
SHORT WAVE  
TELEVISION  
TRANSMITTING

*Now!* Ninety-two types of tubes under the famous VAN DYKE trade mark. Visit your nearest S. S. KRESGE CO., green front store for your tube requirements.

Manufactured and Sold Exclusively  
S. S. KRESGE — 25c to \$1.00 — GREEN FRONT STORES

Van Dyke Laboratories  
E. Newark, N. J.