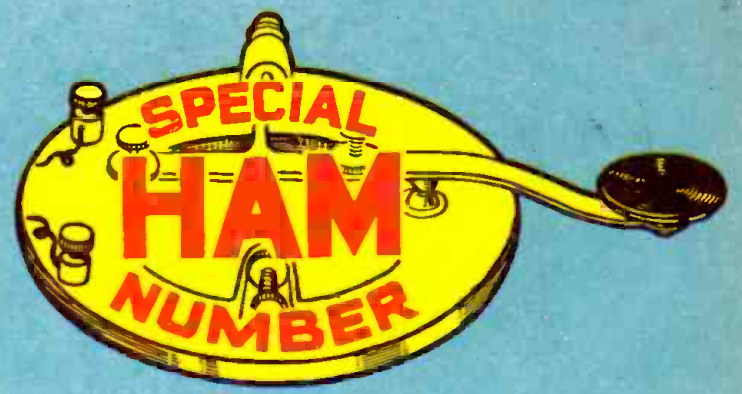


HUGO GERNSBACK
Editor

SHORT WAVE CRAFT

May



WORLD'S
LARGEST
SHORT WAVE
CIRCULATION




World-wide
10 Meter Converter
See Page 12

25¢

IN U. S. AND
CANADA

THE RADIO EXPERIMENTER'S MAGAZINE

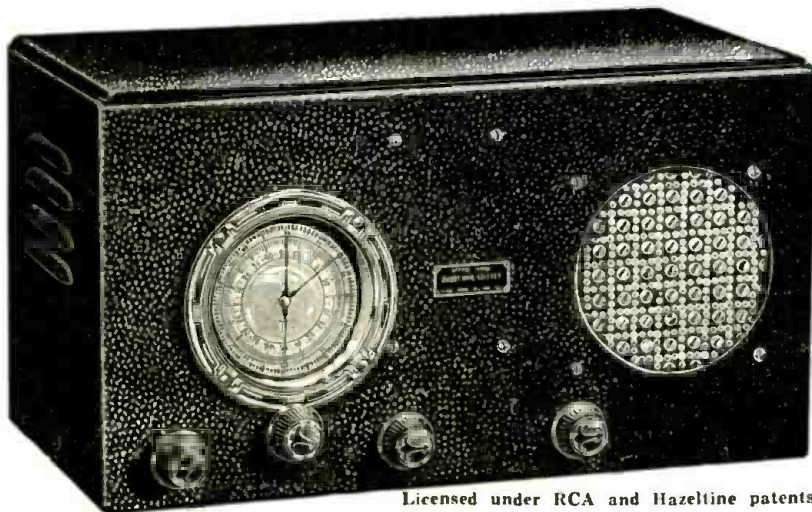Introducing the NEW DOERLE 6-TUBE BANDSPREAD RECEIVER



Licensed under RCA and Hazeltine patents

- ★ Continuous bandspread tuning from 9½ to 625 meters.
- ★ An ideal DX receiver for the long distance SW fan or communications receiver for the transmitting amateur.
- ★ Beautiful, large, illuminated, dual pointer, multi-colored, airplane type dial of great beauty.
- ★ Operates from either single wire type aerial or noise-free doublet.
- ★ Volume control—stage aligning trimmer—and tone controls.
- ★ Unusually smooth acting regeneration control.
- ★ Headphone jack with speaker cut-off switch.
- ★ Highly efficient, low loss ribbed plug-in coils, are a large factor in the amazing sensitivity and selectivity of this receiver. Coils are of the large 3 winding variety and are color coded for easy identification.

The famous Doerle line of receivers are now equipped with the new Octal sockets in which glass and metal tubes are interchangeable. For the first time this quality receiver is available in KIT form for the short wave experimenter who prefers to "build his own."

Uses 6 of the latest hi-gain tubes (6K7G, 6K7G, 6C5G, 6C5G, 6F6G and 5Y3) in a highly efficient and selective circuit, using two tuned stages—electron coupled regenerative detector—POWERFUL 3 stage resistance capacity coupled audio frequency amplifier with power pentode output stage—full wave high voltage rectifier and self contained hum-free power supply. Built-in High Fidelity dynamic speaker capable of handling the entire 3 watts of audio frequency power output of the receiver.

Continuous bandspread over the entire range of 9½ to 625 meters is obtainable due to the use of a special type, multi-colored, airplane dial having a 125 to 1 ratio and two

pointers. Two knobs are provided and make possible either fast or slow motion tuning. ALL of the AMATEUR and FOREIGN SW BANDS are spread over a generous portion of the tuning dial, thereby simplifying tuning so that even a beginner can operate it to the utmost satisfaction. Entirely free from all traces of backlash.

The entire unit is contained in a large, black crackle finished metal chassis and cabinet of extreme beauty. All controls are mounted on the front panel and all parts are readily accessible. No adjustments whatever are necessary. Nothing to get out of order. Simply plug into your electric light socket and enjoy an evening of short wave thrills and entertainment such as you have never before experienced.

Mechanical specifications: Dimensions are 17½"x8"x8¾". Net weight 23 lbs. Shipping weight 33 lbs. Designed to operate entirely from 100-130 volts, 50 to 60 cycles AC house current. Shipment made same day as order is received. Complete satisfaction guaranteed.

If you wish to preserve the front cover, COPY the coupon below and mail at once.

G S RADIO CORPORATION
126 Liberty St., New York City

Dept. S-5

Gentlemen: Please mail without expense or obligation your catalog of the famous Doerle Receiving Sets, illustrating and fully describing All Electric and Battery models, also reproduction of letters from users in all parts of the country.

I enclose \$..... for which please send me.....
(On C.O.D. orders, send 20% deposit.)

Name.....

Street Address.....

City..... State.....

DOERLE 6-tube AC BANDSPREAD RECEIVER, completely wired and tested, with set of 6 matched Arcturus tubes, 8 coils for 9½ to 200 meters, cabinet, instructions, and READY TO OPERATE. Licensed under RCA and Hazeltine patents.....

Specify whether metal or glass tubes desired.

DOERLE 6-tube AC SW KIT, containing all necessary parts, including 8 low loss ribbed coils for 9½ to 200 meters, full size hi-fidelity dynamic speaker, beautiful cabinet, and 4 page instruction booklet, (less tubes, Broadcast coils, and unwired.....

6 Arcturus matched tubes.....\$3.12
Broadcast band coils (2)..... 1.45

LIST PRICE \$34.95.
Discount to Hams,
Fans & Experimenters,
20%.

YOUR NET COST

\$27.96

less 2 Broadcast band
coils, extending the
range up to 625
meters, extra \$1.45.

GS

**RADIO CORPORATION, Dept. S-5
126 Liberty St., New York City**

How a "Tip" got Tom a Good Job

GEE, THERE'S D.J.C. IN BERLIN. THAT'S THE TENTH FOREIGN STATION TONIGHT. RADIO IS SURELY FUN.

HELLO, TOM. HOW'S EVERYTHING?

OH, NOT SO GOOD BILL, BUT I'M STILL HAVING FUN PLAYING WITH RADIO. HADD J.C. LAST NIGHT ON A LITTLE SET I BUILT. IS RADIO STILL YOUR HOBBY TOO?

NO, TOM. I'VE BEEN TOO BUSY MAKING GOOD MONEY OUT OF RADIO TO SPEND TIME "PLAYING" WITH IT.

GOSH, BILL, YOU'RE SURE LUCKY. I NOTICED YOUR SWELL CLOTHES AND SNAPPY CAR. I THOUGHT YOU HAD INHERITED A MILLION. TELL ME ABOUT IT.

I AM LUCKY, TOM, BUT YOU HAD THE SAME CHANCE. REMEMBER ABOUT A YEAR AGO I SHOWED YOU A BOOK FROM NATIONAL RADIO INSTITUTE THAT TOLD ABOUT THE OPPORTUNITIES AND BIG FUTURE IN RADIO, AND HOW OTHERS HAD SUCCEEDED THROUGH THEIR HOME TRAINING? REMEMBER, I TRIED TO GET YOU TO ENROLL FOR THEIR COURSE WHEN I DID.

WELL, IT WAS THE SMARTEST MOVE I EVER MADE. I'M DOING SWELL. MARY AND I ARE TO BE MARRIED NEXT MONTH. TOM, WHY DON'T YOU SNAP OUT OF IT? DON'T STAY IN THAT OREARY LOW PAY JOB ALL YOUR LIFE. RADIO IS MORE THAN A PLAYTHING. IT'S A BIG BUSINESS. IT'S YOUR OPPORTUNITY. TAKE MY TIP. IT ISN'T TOO LATE. RADIO IS STILL YOUNG AND GROWING.

IF BILL SUCCEEDED, I CAN TOO!

THEN I CAN MAKE REAL MONEY SERVICING RADIO SETS

OR GET A JOB IN A BROADCASTING STATION

OR MAKE GOOD MONEY IN ANY ONE OF THE MANY OTHER NEW AND GROWING BRANCHES OF RADIO. THERE'S NO END OF GOOD JOBS FOR A TRAINED RADIO MAN! YES, SIR, I'M GOING TO SEND FOR THAT FREE BOOK AND GET THE DOPE RIGHT NOW!

OR INSTALL AND SERVICE LOUD SPEAKER SYSTEMS

YOU CERTAINLY KNOW RADIO. MINE NEVER SOUNDED BETTER

N.R.I. TRAINING CERTAINLY PAYS. I JUST STARTED A FEW MONTHS AGO AND I'M MAKING GOOD MONEY ALREADY. THIS SPARE TIME WORK IS SWELL FUN, AND SOON I'LL BE ALL SET FOR A GOOD FULL TIME JOB

THANKS!

OH, TOM IT'S WONDERFUL—TO THINK HOW FAST YOU'VE GONE AHEAD SINCE YOU WENT INTO RADIO. WE NEVER COULD HAVE GOTTEN MARRIED ON WHAT YOU WERE GETTING BEFORE.

OUR WORRIES ARE OVER. I'M MAKING GOOD MONEY NOW, AND THERE'S A BIG FUTURE AHEAD FOR US IN THIS LIVE WIRE RADIO FIELD.

..... I will help you start a spare time or full time **Radio service business Without Capital**



Many Radio Experts Make \$30, \$50, \$75 a Week

HERE'S PROOF THAT N.R.I. MEN MAKE GOOD MONEY

BUSINESS PAYS \$300 A MONTH

"I now have my own Radio business which shows three hundred dollars a month profit—thanks again to N. R. I.—FRANK REESE, 222 S. 60th St., Philadelphia, Penna.

\$40 to \$100 MONTH SPARE TIME

"I am servicing broadcast, auto Radios and electrical appliances in spare time. I have run from \$10 as high as \$100 a month. My Radio work equals and often exceeds my regular salary." JOHN J. REID, 536 Dayton Ave., St. Paul, Minnesota.

The world-wide use of Radio receivers has made hundreds of opportunities for good spare time or full time Radio businesses. Many of the twenty million Radio sets are only 25% to 40% efficient. I will show you how to cash in on this condition. I will train you to install and service all types of receiving sets in spare time. I'll show you how to make enough money while learning Radio to start your own service business. Clip the coupon. Get my free book, "High Rewards in Radio." Read how hundreds of N. R. I. men have made good money in spare time or full time businesses.

Many Make \$5, \$10, \$15 a Week Extra in Spare Time While Learning

The day you enroll I start sending you Extra Money Job Sheets which quickly show you how to do Radio repair jobs common in most every neighborhood. I give you plans and ideas that have made good spare time money for hundreds of fellows. My Course is famous as "the Course that pays for itself."

Get Ready Now for a Business of Your Own and for Jobs Like These

In just about 15 years, Radio's growth has created over 300,000 jobs. Thousands of opportunities will be opened by new Radio developments. Broadcasting stations use engineers, operators, station managers and pay up to \$6,000 a year. Manufacturers employ testers, inspectors, foremen, engineers, servicemen, buyers, for jobs paying up to \$7,500 a year. Dealers and jobbers employ servicemen, salesmen, buyers, managers, and pay up to \$75 a week. My Free Book tells about these and other opportunities.


Television, Short Wave, Loud Speaker Systems, Included

There is opportunity for you in Radio. Its future is certain. Television, short wave, loud speaker systems, ship Radio, police Radio, automobile Radio, aviation Radio—in every branch, developments and improvements are taking place. Here is a real future for thousands of men who really know Radio—men with N. R. I. Training. Get the training that fits you for good pay opportunities and success in this growing industry.

Find Out What Radio Offers You

I am so sure N. R. I. can train you satisfactorily that I agree in writing to refund every penny of your tuition if you are not satisfied with my Lesson and Instruction Service upon completion. Get my 64-page book of facts. It's free to any ambitious fellow over 15 years of age. It tells you about Radio's opportunities; about my Course; what others are doing and earning. Find out what Radio offers you. No obligation! ACT NOW! Mail coupon in an envelope, or paste it on a 1c postcard.

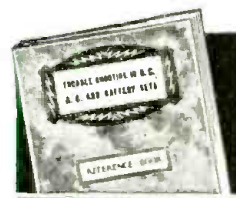J. E. SMITH, President Nat'l Radio Institute, Dept. 6EB3 Washington, D. C.



I'll prove that my training is practical, money-making information, that it is easy to understand—that it is just what you need to master Radio. My sample lesson text, "Radio Receiver Troubles—the Cause and Remedy" covers a long list of Radio receiver troubles in A. C., D. C., battery, universal, auto, T. R. F., super-heterodyne, all-wave, and other types of sets. And a cross reference system shows you the possible cause and a quick way to locate and remedy those set troubles. A special section is devoted to receiver check-up, alignment, balancing, neutralizing and testing. Get this lesson free. No obligation. Just mail coupon.

MAIL THIS for FREE 64 page book

I want to take advantage of your offer. Without obligating me, send me your Free Sample Lesson and your book. "High Rewards in Radio." (No lesson print plainly.)

NAME.....
 ADDRESS.....
 CITY.....
 STATE.....
 ZIP.....

IN THIS ISSUE: PROMINENT SHORT-WAVE AUTHORS

Sprayberry • Shuart • Schrage • McEntee • Doerle • Hooton • Lynch

HUGO GERNSBACK
Editor



H. WINFIELD SECOR
Managing Editor

GEORGE W. SHUART,
W2AMN
Associate Editor

Contents for May, 1936

Editorial—New Short-Wave Interference, by Hugo Gernsback	4
How 5-Mega-cycle Waves Bridged Hurricane Break, by F. B. Woodworth, Bell Telephone Laboratories.....	6
“Ham” Applications of the Cathode-Ray Oscillograph, by F. L. Sprayberry.....	7
B.C. Programs Now on 10 Meters—How to Build a Converter or Superhet to Pick Them Up.....	8
W2AMN’s All-Band Transmitter, by G. W. Shuart, W2AMN	10
World-Wide 10-Meter Converter (Cover Feature), by G. W. Shuart, W2AMN.....	12
The A-B-C of Frequency Modulation, by Wilhelm Schrage.....	13
A Modern 5-Meter Transmitter, by Howard G. McEntee, W2FHP	14
A Neon Tube Oscilloscope, by Arthur Stansfield, W1COL.....	15
A 5-Meter Super-Regenerator, by H. G. Cisin, M.E.....	16
The LAMB “Noise Silencer”.....	16
A “Loop Aerial” S-W Receiver, Walter C. Doerle.....	17
“Silver Trophy” Award for Best S-W Log.....	18
World-Wide Short-Wave Review, Edited by C. W. Palmer	19
\$5.00 for Best Short Wave “Kink”.....	20
Oh! For a “Ham” Shack Like One of These.....	21
A Sensitive 4-Tube “Regen.” Superhet, by H. D. Hooton, W8KPX	22
What’s New in Short-Wave Apparatus.....	23
The Radio Amateur Course, Conducted by G. W. Shuart, W2AMN	26
Short-Wave Stations of the World, by M. Harvey Gernsback	29
Short Wave League and Scout News.....	33
Short-Wave Question Box.....	34
Little-Known Facts About Short and All-Wave Aerials, by Arthur H. Lynch.....	36
When to Listen In, Edited by M. Harvey Gernsback.....	32

Features in the June FAN Issue

A 3 band short-wave receiver for the S-W “Fan,” by George W. Shuart, W2AMN.

A De-Luxe A.F. Amplifier for use with any S-W receiver.

An Improved “low-cost” Transmitter using the new R.C.A. 830 B tubes, having an output of 200 watts.

A 5-meter Transmitter-Receiver—uses metal tubes, by Henry B. Plant, W6DKZ.

3½ Waves Transmitted 16 miles, by Dr. Irving Wolf and Dr. E. G. Linder.

A modulator for Mr. McEntee’s 5-Meter Transmitter described in the present issue—described in detail by Howard McEntee, W2FHP.



Certified Circuits

● SHORT WAVE CRAFT goes to a large expense in verifying new circuits. When you see this seal it is your guarantee that such sets have been tested in our laboratories, as well as privately, in different parts of

the country. Only “Constructional-Experimental” circuits are certified by us.

When you see our certified seal on any set described, you need not hesitate to spend money for parts, because you are assured in advance that the set and circuit are bona fide and that this magazine stands behind them.

SHORT WAVE CRAFT is the only magazine that certifies circuits and sets.

OUR COVER


● This month’s cover painting depicts a very interesting new 10-meter Short-Wave Converter. It was designed and built by G. W. Shuart and brought in stations from all parts of the world on 10 meters, when used with a standard receiver. Full details for constructing this 10-meter World-Wide Converter are given on page 12.

COPYRIGHT, 1936, BY H. GERNSBACK

Published by POPULAR BOOK CORPORATION

HUGO GERNSBACK, President - - - - H. W. SECOR, Vice-President
EMIL GROSSMAN - - - - - Director of Advertising
Chicago Adv. Office - - - - - L. F. McCLURE, 919 No. Michigan Ave.
Los Angeles Adv. Office - - - - - J. A. Kendall, Box 176, Arcade Annex
Publication Office - - - - - 404 N. Wesley Avenue, Mount Morris, Ill.
Editorial and General Offices - - - - - 99-101 Hudson St., New York, N. Y.
European Agent: Gorrings’s American News Agency, 9A Green St.,
Leicester Square, London W. C. 2
Australian Agents: MCGILL’S AGENCY, 179 Elizabeth St., Melbourne

SHORT WAVE CRAFT—Monthly. Entered as second class matter May 7, 1930, at the post office at Mount Morris, Illinois, under the act of March 3, 1879. Trademarks and copyrights by permission of H. Gernsback, 99-101 Hudson St., N. Y. C. Text and illustrations of this magazine are copyrighted and must not be reproduced without permission. SHORT WAVE CRAFT is published on the 1st of every month. Twelve numbers per year. Subscription price is \$2.50 a year in the United States and possessions. Canada and foreign countries, \$3.00 a year. Single copies 25c. Address all contributions for publication to Editor, SHORT WAVE CRAFT, 99-101 Hudson St., New York, N. Y. Publishers are not responsible for lost manuscripts. Contributions cannot be returned unless authors remit full postage. SHORT WAVE CRAFT is for sale at all principal newsstands in the United States and Canada. European agents: Brentano’s, London and Paris. Printed in U. S. A. Make all subscription checks payable to Popular Book Corporation.

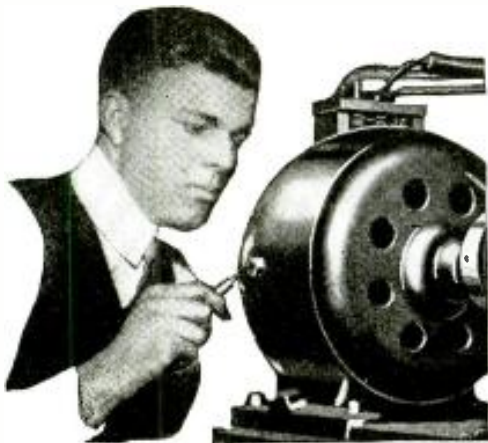

AMAZING EASY WAY TO LIFE-SUCCESS in ELECTRICITY

LEARN THE GREATEST INDUSTRY OF THE AGE—TRAIN NOW FOR A BIG-PAY JOB I'll Finance Your Training!

Are you dissatisfied with your job? Are you out of a job because you lack Specialized Training for a LIVE industry? Is your future uncertain? Then let me show you an amazing, easy way to get into Electricity, where TRAINED MEN are needed . . . Where hundreds of Coyne Graduates are drawing Good Pay every week. Coyne has been training ambitious fellows for the Electrical Industry since 1899 . . . at Coyne you do not need previous experience or a lot of book learning. It makes no difference if you are 16 or 40 years old, Electricity thru Coyne training offers you a big future . . . and you can start any time.

Many make \$30, \$40, \$50 and up, every week

Here is YOUR life opportunity. Every day brings news of new developments in this fascinating, big-pay field, with more jobs and a greater future for the trained man than ever before. If you are ambitious to get ahead, I want to help you. MAIL THE COUPON BELOW and I'll tell you about my finance plan, which has enabled thousands to get Coyne Training with very little money. Get training first, then take 18 months to complete small monthly tuition payments starting FIVE MONTHS after you begin your training, or 2 months after your required training period is over. This is NOT a correspondence course. *H. C. Lewis*



Learn By Doing In 90 Days

The great Coyne Shops are famous the world over for their unusual Learn-by-Doing method of practical, individual instruction. There is no book study, no reciting—you learn quickly and thoroughly by doing actual jobs under the personal guidance of trained instructors, on a great outlay of machinery and equipment assembled strictly for training purposes. That is why, in 12 short weeks, we are able to take fellows without previous experience or a lot of book learning, and train them for jobs leading to good pay.

Many Earn While Learning

If you need part-time work to help pay living expenses while at school, tell us your problems and we may be able to help you as we have hundreds of other students. Then, after you graduate, our FREE EMPLOYMENT DEPARTMENT will give you LIFE-TIME Employment Service. Every Coyne Graduate also receives a Life Scholarship, with free technical and business service and privilege of review at any time without additional tuition charge.

HOME OF COYNE SHOPS



THIS IS our fire-proof modern home wherein is installed thousands of dollars worth of ELECTRICAL EQUIPMENT. Every comfort and convenience has been arranged to make you happy and contented during your training.

PREPARE For JOBS Like These

- DIESEL OPERATOR
- ARMATURE EXPERT
- SUBSTATION OPERATOR
- AUTO ELECTRICIAN
- INVENTOR
- MAINTENANCE ENGINEER
- SERVICE STATION OWNER

and many other money-making opportunities in the Electrical field. Learn by actual work on real dynamos, engines, power plants, autos, switchboards—everything from door bells to full-sized power and lighting plants, in full operation every day.

DIESEL ENGINES REFRIGERATION AIR CONDITIONING

Trained men are needed in these rapidly expanding fields—the fastest growing industries in America today. RIGHT NOW I am including instruction in DIESEL ENGINES, Electric Refrigeration and Air Conditioning AT NO EXTRA COST.

PROOF that Coyne Training Gets QUICK Results

"I owe my electrical success to your 12-week shop course," says R. B. Umbarger of Tennessee. "Two weeks after leaving school I took a wiring job," reports E. O. Berndt of Illinois, "and the profits from this one job alone more than paid for the entire course." A. C. Hoehnle of Ohio says, "Received several raises in pay, due to the training I received at Coyne." And I could quote from hundreds of similar letters from successful Coyne-trained men. WHAT THEY HAVE DONE, YOU SHOULD BE ABLE TO DO!

GET THE FACTS . . . NOW

Coyne is your one great chance to get into this big-pay field. This school is 37 years old . . . Coyne training is tested . . . endorsed by large concerns. And IT COSTS YOU NOTHING to find out about this amazingly easy, practical way to life success. Simply mail the coupon below and I'll send you the big, free Coyne book, with photographs, facts, jobs, salaries, opportunities. THERE'S NO OBLIGATION, SO ACT AT ONCE.



Send Today for this FREE Book!

H. C. LEWIS, President
Coyne Electrical School,
500 S. Paulina St., Dept. 56-82, Chicago, Ill.

Without obligating me, send full details of your "PAY-TUITION-AFTER-GRADUATION" Plan and Big Free Illustrated Catalog.

NAME-----

ADDRESS-----

CITY-----STATE-----

Mail in envelope or paste on postcard.

COYNE H. C. LEWIS, President Founded 1899
ELECTRICAL SCHOOL
500 South Paulina Street Dept. 56-82 Chicago, Illinois

Please mention SHORT WAVE CRAFT when writing advertisers



New Short-Wave Interference

An editorial by HUGO GERNSBACK

● BEFORE the broadcasting era, no one was much concerned with electrical wave effects which were set loose in space, for the simple reason that there was no one who could have objected to stray waves.

But with the advent of ultra-sensitive radio receivers of all types, the situation changed immediately. The public has a right to complain when radio reception is marred by all sorts of man-made static. It is bad enough to listen to natural static about which, so far, not much has been done, but when it comes to the other kind, the public expects that the authorities will take some sort of cognizance of the situation, and put in effect adequate remedies.

This has been the case with a good deal of man-made static, and now-a-days municipalities and electric light companies cooperate to do away with the nuisance. The public utility companies also do this from a purely selfish viewpoint, because they realize that when radio programs are continuously marred by man-made static, the public will not use their radio sets and consequently no electric current will be used. In turn, the electric light corporations suffer thereby, and it is thus to their interest to see that the nuisance is done away with. It is usually not very difficult to do this, particularly when we have to do with leaking transformers, leaking insulators, and various automatic, contact arrangements which include even the harmless-looking electric heating pad and many others. There are, however, several other instrumentalities which have lately created a great deal of havoc. These are: 1—X-ray machines of all types; 2—short-wave *fever* apparatus, or the so-called diathermic machines, used in an ever-increasing number by physicians in the treatment of various diseases.

During the past year, it was found that particularly on the short-wave bands, there was quite a good deal of a mysterious short-wave interference which baffled the "scouts" no end, and incidentally created a tremendous amount of interference.

The emissions were mysterious because they kept popping up all over the country in the most unexpected places. There was no regularity about the transmissions, not only in the intensity, but the frequency (wave lengths) changed continuously. This was particularly true on frequencies from 30 meters downwards. The effect seemed to be a carrier, very broad and loud. It not only bothered individuals who had short-wave sets, but annoyed amateurs, the United States Navy Department, R.C.A. Communications, and The American Telegraph and Telephone Company, where it interfered with communication between ships and land. Not only was interference noted in the United States, but it extended to foreign countries as far as Australia.

The Naval Communication's Reserve undertook to clear the mystery which became popularly known under the term "The Shadow." It took a good deal of sleuthing to run down the interference, and finally it was found that the

problem had its origin, particularly, in the short-wave field of therapeutic machines which are used by physicians more and more of late.

These machines are complete radio transmitters in miniature form. They have the regulation transmitting type power tubes and usually have an intensity of from 100 to 300 watts. These machines are used to cure various afflictions, particularly boils and all conditions in which we have to do with pus. Such machines are remarkable in clearing up boils, carbuncles and the like in short order.

But, while these machines are curing one ill, they also give rise to thousands of others, namely, *interference in the various radio bands!* The machine may operate on one frequency, but as adjustments are made of the electrodes between which the patient is placed, the frequency changes. This is what makes for additional mischief. It can readily be seen why a number of machines of this type can raise untold havoc with radio sets all over the country, because short-wave transmissions of this type do not necessarily cause interference in the locality in which they operate, but can create a most powerful disturbance a thousand, or even three thousand, miles away!

It is curious that the Federal Communications Commission did not immediately take steps to remedy the situation. In the first place we actually have in these machines, real radio transmitters, and it is against the radio law to operate a transmitter without a license. It can be seen that if no steps are taken to remedy the situation, in time there will be so much interference on the short-wave bands that it will be impossible to listen to any transmission. The sensible thing to do would be to have all owners of such machines licensed by the Commission. Secondly, anyone operating such a machine should be required to operate it inside of an electrical shield, so that no radio waves could penetrate to the outside. This is a rather simple thing to do, and the only point is that it may prove somewhat inconvenient and make for additional expense. The electrical shield to which I refer is simply a room completely screened by means of a metal screen. This would have to include ceiling, flooring, as well as doors and windows. This shield would have to be grounded. Then any machine operating in such a room would create no outside disturbance at all, and there would, therefore, be no more interference from that particular machine. If too costly to build such a shield, it is even possible to have a collapsible portable shield which would inclose the machine and the patient; this would be a cage, measuring about six feet on each side and six feet high. Again this cage would have to be grounded so that no waves should pass to the outside. There will, of course, be other solutions which might even be simpler, and which I am sure will be evolved before long.

The main thing at the present time is that the Federal Communications Commission will find it necessary to act promptly, if chaos is not to overtake the short-wave bands.


SHORT WAVE CRAFT IS PUBLISHED ON THE 1st OF EVERY MONTH

This is the May, 1936 Issue—Vol. VII, No. 1. The Next Issue Comes Out May 1

I'LL TRAIN YOU *Quickly* FOR SPARE-TIME AND FULL-TIME JOBS IN **ELECTRICITY**



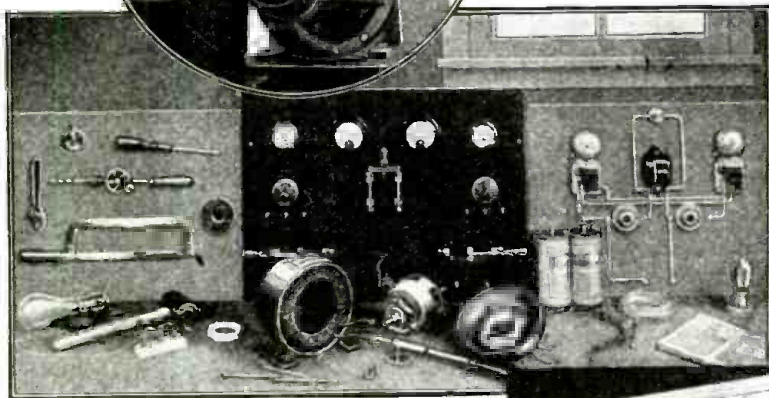BY PRACTICAL SHOP METHODS
in your spare time
RIGHT IN YOUR OWN HOME



Learn to earn up to \$50 a week or more in a real money-making field. Electricity today offers opportunities undreamed-of a few years ago...steady jobs...interesting work...good pay...a real future. And now Electric Institute brings — to your very door — the practical training necessary to qualify for the rich rewards that are waiting. There is no need to give up your present job... no need to leave home, family and friends... no need to travel hundreds, perhaps thousands, of miles to some distant city; pay out large sums of money for traveling and living expenses. Now, you can learn Electricity by a simple, easy, practical method... right at home... at a fraction of the cost of going away to school... and with full assurance of your money back if you're not entirely satisfied.

LEARN BY DOING ACTUAL JOBS IN YOUR OWN ELECTRICAL WORK SHOP... WE FURNISH EQUIPMENT

Electricity is a practical subject which must be taught in a practical way. That's why we furnish each of our students with dozens of items of real electrical equipment and apparatus in addition to his course of study... so you can do the actual work on real electrical jobs... make tests... perform your own experiments. This equipment is furnished without extra cost, not only to aid your training, but to be used to go out and do real jobs... real installations and repairs that you can get real money for. In fact, by doing only two or three such jobs a month your training should actually pay for itself... and the opportunities for extra spare-time earnings are simply amazing!

YOU DON'T NEED PREVIOUS EXPERIENCE OR A LOT OF BOOK LEARNING TO PREPARE FOR JOBS LIKE THESE:

New electrical projects, constantly increasing use of electric power, means more jobs for men with practical training. There is scarcely a large industry today that does not use trained electrical men in some part of their work. Maintenance work, lighting and illumination, automotive electricity, manufacturing, service and repairs, power plant work, switch-board operation, sub-station operation... all offer real opportunities to trained men who can qualify. Or, if you prefer to own and operate an electrical business of your own, Electric Institute training and the equipment furnished will give you a start.



H. W. PETERSON
President, Electric Institute

**THIS
FREE BOOK
TELLS YOU HOW**

**DIESEL ELECTRIC
POWER, RADIO and
REFRIGERATION**

Complete course includes practical training in Diesel Electric Power, Radio, Electric Refrigeration and Air Conditioning. Start NOW and prepare to take advantage of the opportunities that are waiting for trained men in these fields and many other branches of Electricity. It's easy to get all the facts about Electric Institute Training... it takes only a postage stamp to mail the coupon... and that little coupon may be the turning point in your life, if you'll give it a chance.

**—EARN EXTRA MONEY
BY DOING PART TIME
JOBS WHILE LEARNING!**

Opportunities to make \$5, \$10, or more a week while training.

By the most practical, most amazingly easy method of home shop training, the fascinating mystery of electricity is unfolded to you step by step in a way that anyone can quickly understand and which is intended to make you a real practical trained man and not a theoretical engineer. I have designed this course so that it is possible for my students to start earning money almost at once. Do not confuse Electric Institute Training with a theoretical course, with dry text books and tiresome theories. By this new method, you are told—in plain, simple words—exactly what to do, and why... then you do the actual jobs, with real, full-size electrical equipment which we furnish without extra cost as a regular part of your training. That's the modern, easy Electric Institute way to become a practical skilled electrician in your spare time without leaving your present job until you are ready to step into a real electrical job.

**GET INTO A GROWING FIELD
FOR BIG PAY AND A FUTURE**

There is no better way to succeed in life than to train for specialized work in an industry that is expanding. Such opportunities are waiting in the great and growing field of Electricity, where trained men are always needed. And Electric Institute is ready to show you the way. Mail the coupon now—TODAY—for Big, New, Free Book and all facts about this revolutionary plan of home shop training. There is no obligation, and no salesman will call on you. The book costs nothing... but it may be worth a fortune to YOU!

RUSH THE COUPON...TODAY!

H. W. Peterson, President
ELECTRIC INSTITUTE, INC.,
5840 Addison St., Dept. 166E, Chicago, Ill.
Send Free Book with all facts about E. I. Home Shop Training.

Name..... Age.....
Address.....
City..... State.....

ELECTRIC INSTITUTE, Inc. H.W.PETERSON
PRESIDENT

5840 ADDISON STREET, Dept. 166E, CHICAGO, ILLINOIS

Please mention SHORT WAVE CRAFT when writing advertisers

How 5-Megacycle Waves Bridged Hurricane Break



By F. B. Woodworth

Radio Development Department, Bell Telephone Laboratories

Short Waves have indeed performed some very unusual services in an emergency—read how 5 mc. waves carried telephone traffic over a 40-mile "break" in the New York-Havana circuit.

nier to Vaca Key. The telephone pole line runs along the railroad right-of-way between Miami and Key West, where it connects to the Havana cables, thus forming part of the route between the United States and Cuba. In some places the railroad fills were washed away, allowing the poles to topple over. In other places, high water lifted the rails and ties from the roadbed, and the wind blew them against the poles, knocking them down. Where the poles were on the windward side of the railroad, they remained standing. The damage to all communication and transportation services in the vicinity was so severe that it was several days before the true extent of the devastation could be determined. It then became apparent that it would be advantageous to postpone plans for the restoration of the telephone lines until more information could be obtained regarding the plans for restoring the railroad and highway, and until different methods of taking care of the telephone service could be studied. It was, therefore, decided to bridge the gap temporarily by radio, and applications for station licenses were rushed to Washington.


Within eighteen hours after this decision had been reached all equipment was on board a train bound for Florida, and B. L. Dayton of the Long Lines Department and the author were on their way to supervise the installation of the two terminals, assisted by J. F. Andrews of the Long Lines Department who was already in Florida. One of the terminals was to be located near Tavernier and the other at Big Pine Key, thirty-five miles east of Key West. Two line gangs were sent from Alabama and Louisiana by boat to Key

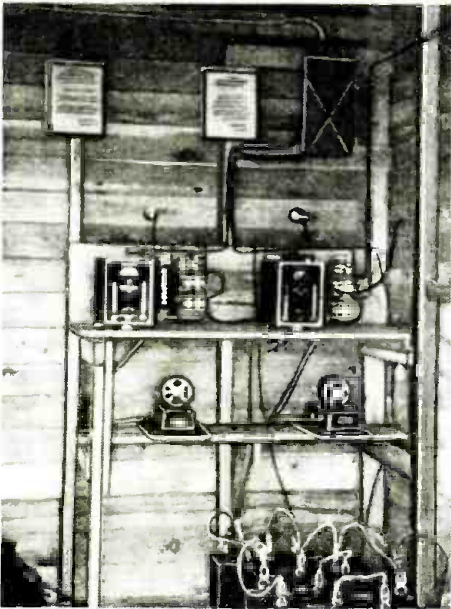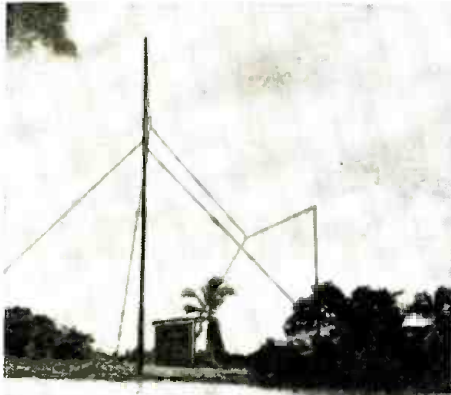

The vertical quarter-wave transmitting antennas were suspended from a messenger wire supported by two poles.

In the transmitter shack, two 19A transmitters are mounted on a shelf with their dynamotors immediately beneath them.

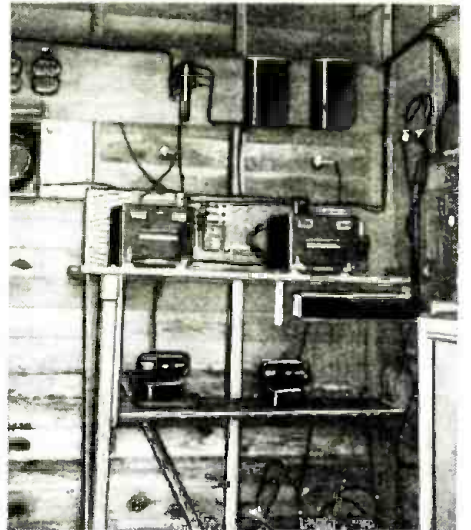● EARLY this winter a tropical hurricane swept across the Florida Keys, completely demolishing large sections of the Florida East Coast Railway along a forty-mile stretch from Taver-




Photos Bell Telephone Laboratories.

Only a single pole was used for the receiving antennas—one being attached to each end of a cross-arm.

Mounting arrangements for the 12A type receiver, in the receiver shack, are similar to those for the transmitters.

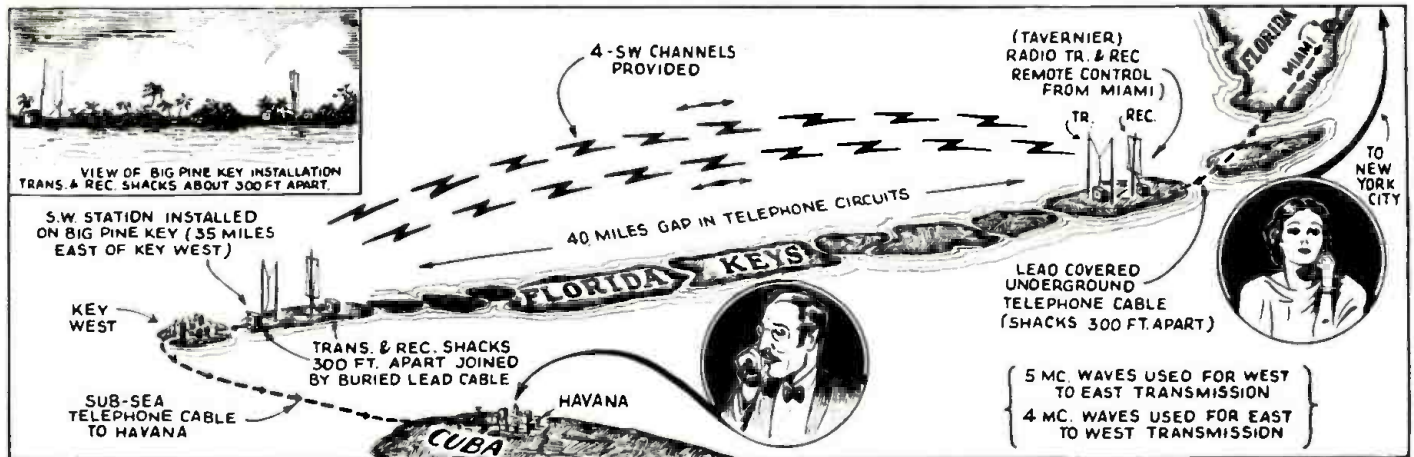West and thence by automobile to Big Pine Key. Here they immediately set to work clearing away the underbrush, dynamiting in (Continued on page 38)



Picture diagram above shows how telephone experts used 5 mc. waves to provide four telephone channels over a 40-mile "break" in the New York-Havana telephone circuit, the break having been caused by a hurricane.

"HAM" Applications of the Cathode-Ray Oscillograph


By F. L. Sprayberry

Are you obtaining the proper percentage modulation from your transmitter? How much audio distortion do you have? How much "ripple" voltage is present in your power supply output? These and other important and perplexing problems which are forever confronting the "Ham" are quickly and easily checked up by means of the cathode-ray oscillograph, as clearly explained by Mr. Sprayberry.

● IT IS indeed hard to imagine anything in the way of auxiliary equipment for use by the "Ham" which could have more value than *Cathode Ray Oscillograph* equipment. Factors which have in the past been difficult to solve in connection with transmitter adjustments are made a matter of routine by this equipment. Adjustments such as amplifier


minimum distortion, operating class, modulation percentage, prevention of overloading, neutralization coupling requirements and numberless other problems bearing directly on the success of the transmitter, may be made quickly and effectively.

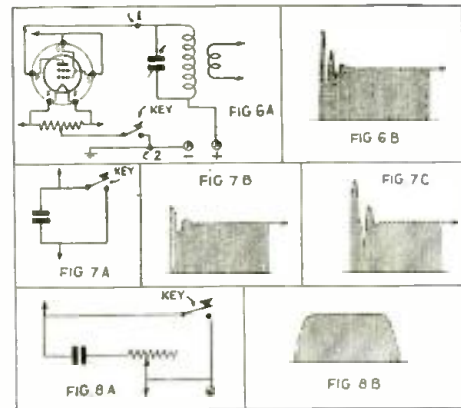Many of the "high-lights" typical of what the Ham can do with Cathode Ray apparatus are pointed out in the following paragraphs. Numerous other tests will suggest themselves at



One of the greatest problems the Ham has to contend with is to establish smooth "keying"; the cathode ray oscillograph, as the diagrams above indicate, help to solve this problem nicely.

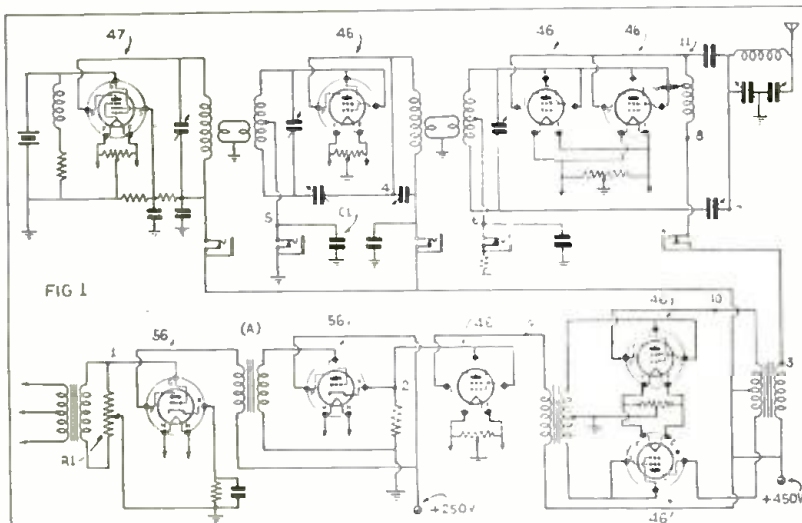every turn. It is no longer necessary to wait for a report from some remote point in order to know whether or not signals are being sent properly. With the aid of Cathode Ray equipment the "ham" can determine this himself at the transmitter.



The RCA cathode-ray oscillograph, a typical model of this newest scientific instrument for analyzing conditions in a radio or an electrical circuit.



Tests on Typical Low-Power Transmitter

A low-powered transmitter has been chosen for the purpose of these tests, which is typical with the average amateur. The problems solved here, moreover are largely general, applying as well to broadcast and commercial equipment.


Detecting Audio Distortion

Audio distortion is best tested one stage at a time. This avoids the necessity of an audio signal generator and quickly localizes the stage where the distortion exists. Turn on the power of the transmitter and the oscillograph, and focus the beam for a 1 mm. (1 millimeter is about 1/25 inch) spot on the center of the target or screen of the oscillograph. Connect the left horizontal and lower vertical plates to the transmitter ground. Now connect both the top vertical plate and the right horizontal plate to the amplifier input within the instrument, one for each set of plates, and adjust the vertical plate bias so that the beam will rest at the center of the screen. Connect the right horizontal free plate to the 56 tube grid (1) on the transmitter voice amplifier and the vertical plate lead to the cathode (2) of the second 56 tube (output). Excite the amplifier with some sound (voice, phonograph record, etc.) and adjust the gain of both oscillo-

(Continued on page 52)

Diagram at left shows typical Ham transmitter circuit, and the numbers at various points indicate where test connections are made to the cathode ray oscillograph.

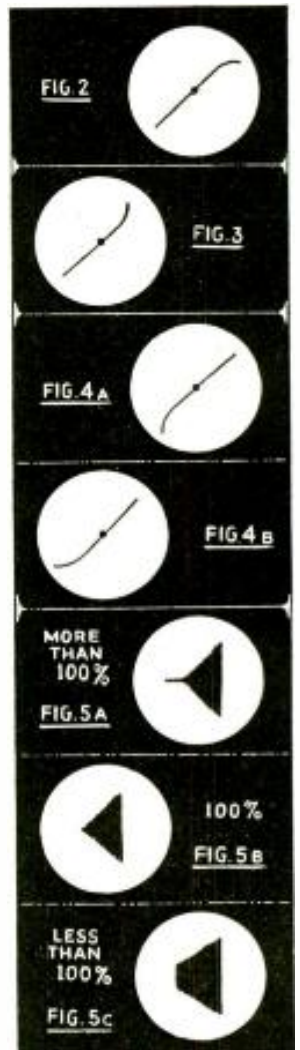Typical "oscillograms," showing percentage of modulation and also indicating degree of distortion.



B. C. Programs Now on

How to Build a Converter or



Penobscot Tower, Detroit, home of the new 10-meter broadcast station W8XWJ (9.488 meters or 31.6 mc. to be exact).

W8XWJ, the ultra high-frequency experimental broadcast station of the Detroit News, and "little brother" of WWJ, made its initial appearance on the air January 29 with a special dedicatory program depicting the advancement of radio broadcasting and the early days of short wave transmission.

A great field has recently been opened in this little explored portion of the short-wave spectrum, from which—no doubt—many advances in the art of radio communication will be made in the near future; and like WWJ, pioneer on the broadcast band, W8XWJ is one of the first few on the "ultra short-waves."

Located atop the Penobscot Building, Detroit's tallest skyscraper, 650 feet above ground,

W8XWJ will command an "optical range" of many miles, which to date appears to be of advantage on these frequencies.

The transmitter itself, as well as the associated audio equipment, is of the most modern "high-fidelity" design and was built by RCA. It consists of a crystal-controlled oscillator using an AT cut crystal, operating on 3950 kc, followed by three frequency-doubler R.F. amplifier stages, in order to raise the frequency to the operating wavelength of 9.488 meters, on 31.6 megacycles. Following the third doubler-stage is a straight-amplifier or buffer-stage. This buffer-stage in turn is coupled to the final modulated class "C" amplifier which employs four high frequency type 800 tubes, connected in a push-pull parallel circuit.

The audio system consists of the standard RCA high fidelity speech amplifier driving a push-pull class "B" modulator employing a pair of 203-A's, which effectively fully modulates the 100 watts of carrier.

During the first few weeks the station will only be on the air between 2 and 5 and 7 and 10 p. m. EST daily and Sundays from 2:30 to 7:30 p.m., carrying the programs regularly broadcast by WWJ. However, after the necessary adjustments are made and the testing completed, W8XWJ will inaugurate a more elaborate schedule of transmission and broadcast many unusual and interesting programs not heard on the regular broadcast channels.

Realizing that only a comparatively few would be able to hear the station due to the fact that only a small percentage of even the latest model all-wave receivers are capable of tuning to this extremely high frequency, it was decided to furnish those who cared to build their own receivers or "converters" with diagrams and instructions. Thus the potential audience would grow much more rapidly.

In designing the converter many things had to be taken into consideration in order to make it applicable to practically all receivers and at the same time keep the cost low and retain ease of construction for those whose fundamental knowledge of such devices is somewhat limited. It consists of one of the new high efficiency metal tubes as a converter, a type 6L7, with a separate triode as an oscillator. A plate coil tuned to approximately 1500 kc. was found to materially increase the conversation gain over the choke and condenser method of coupling. The secondary of this coupling transformer provides a fairly good "match" to the antenna coil of most "broadcast" receivers. A separate

power supply is incorporated in the converter design, thus eliminating the necessity of bringing out the high voltage lead from the B.C. set.

The receiver described was designed by J. L. Murray, prominent consulting radio engineer of Detroit, and is of the super-heterodyne type having broadly-tuned "resistance-coupled" I.F. stages. The converter tube is of the metal type, as are all the tubes in this receiver with the exception of the rectifier, and is used in an "autodyne" circuit. Provision was made, however, to replace the resistance I.F. with broad-tuned high frequency intermediate transformers; and add a separate oscillator tube at a later date. Both the receiver and converter have proven very satisfactory.




W8XWJ's 9.48 meter transmitter; the speech amplifier and control panel appear at right of photo.

DRILL the chassis and mount all tube sockets, transformers, tuning condensers and coils as shown in the picture. Connect the high voltage leads of the power transformer, one to each plate of the 80 tube socket, the plate connections being the contacts in which the smaller pins of the tube fit. To the larger terminals of this socket connect the 5-volt winding of the power transformer. One end of the 6.3 volt wind-

Directions for Building the 10-Meter Converter . . .

ing connects to terminal 2 of each of the other two tube sockets, the other end of the winding connecting terminal 7 of these sockets. These connections

should be made with twisted insulated wire. Attach 110-volt cord with switch in series. From the center tap of the high voltage winding attach a wire to the chassis at the nearest point. From one side of the 5-volt winding, a wire is run to the choke coil and to the red wire of one of the 8 mf. electrolytic condensers. The other end of this choke coil connects to the point marked X and to the red wire (Continued on page 45)

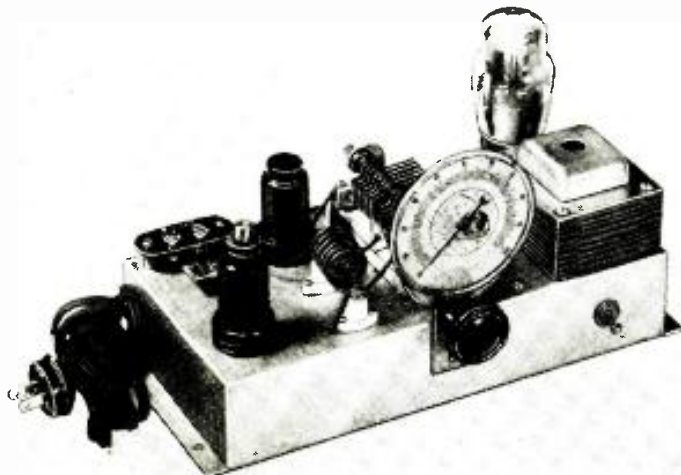

The "Converter" for receiving 9.48 meter waves on your present B.C. receiver.

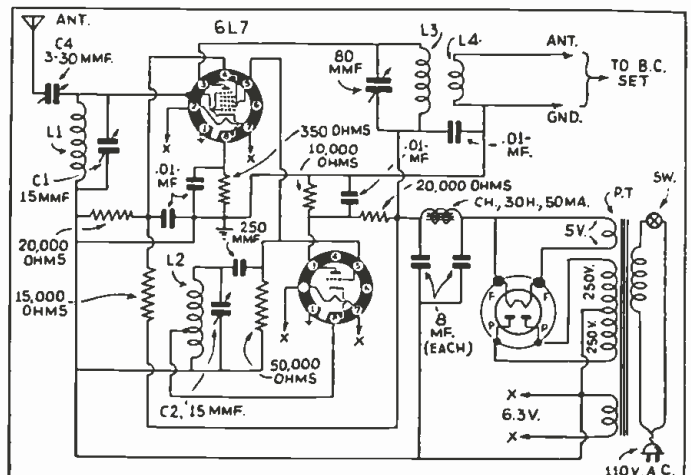


Diagram of S-W converter of simple design.



10 Meters—How to Receive Them

Superheterodyne to Pick Up 10-Meter Stations

• THE receiver is assembled on a 9x12 base, 3 inches deep. It consists of a 6K7R.F. amplifier, 6J7 as a combination detector and oscillator, 2-6K7 tubes as resistance coupled intermediate fre-

The High Frequency Superheterodyne Receiver

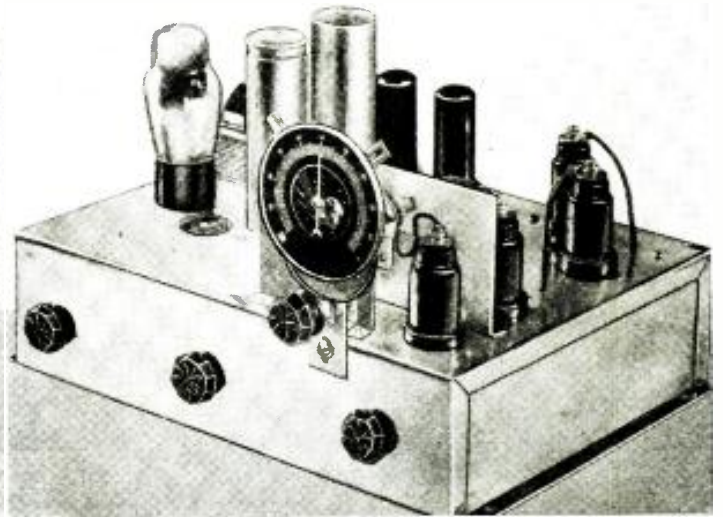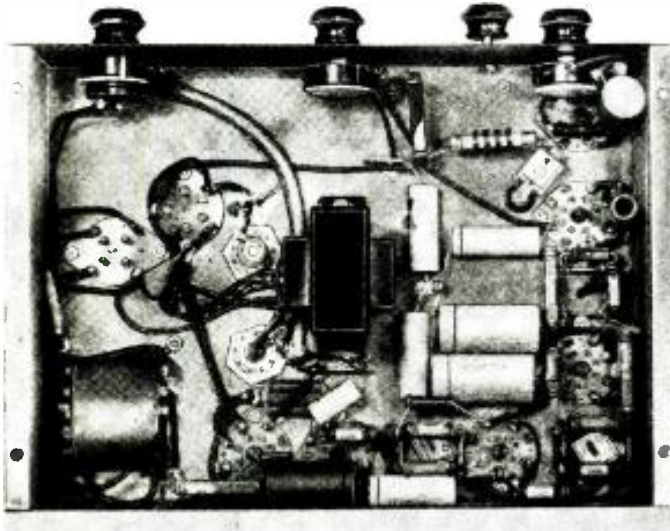The value of the screen and suppressor voltage and the size of grid condenser and leak are chosen so as to obtain oscillation, but not super-regeneration. The detector heterodynes the high



Front and bottom views of 10-meter "super-het" receiver. For the more ambitious, this super-het will prove very interesting.

quency amplifier, a 6F6 connected as a hi mu triode as second detector and a 6F6 as pentode output.

The R.F. stage is similar to those used in an elaborate super-regenerative receiver. It adds more gain, eliminates receiver radiation and eliminates antenna resonance from the detector circuit. The suppressor screen voltage on the detector should be adjusted so that it oscillates mildly over the tuning range, and at this setting the receiver is most sensitive. A semi-variable coupling condenser is used to couple the R.F.

stage to the detector. It is connected about midpoint of the detector coil to prevent overload of this circuit and to allow for greater gain in the detector stage. The detector uses a grid leak for obtaining smooth oscillation and detection. The I.F. frequency is low enough that a grid leak detector is quite efficient. An R.F. choke is used in the detector cathode instead of a tap on the grid coil. This forms a common grid and plate impedance so that the tube oscillates at the frequency determined by the tuned grid circuit.

frequency signals into the I.F. amplifier—a form of the Dow oscillator. The I.F. amplifier uses two stages of moderate gain. The values of resistors and capacities are selected so that the amplifier peaks at about 50 kc. with a bandwidth of approximately 50 kc., allowing for true hi fidelity reception. The values of capacities and grid leaks are selected so as to prevent amplification of audio frequencies in the I.F. amplifier.

Eliminating tuned circuits in the I.F. stages results (Continued on page 44)


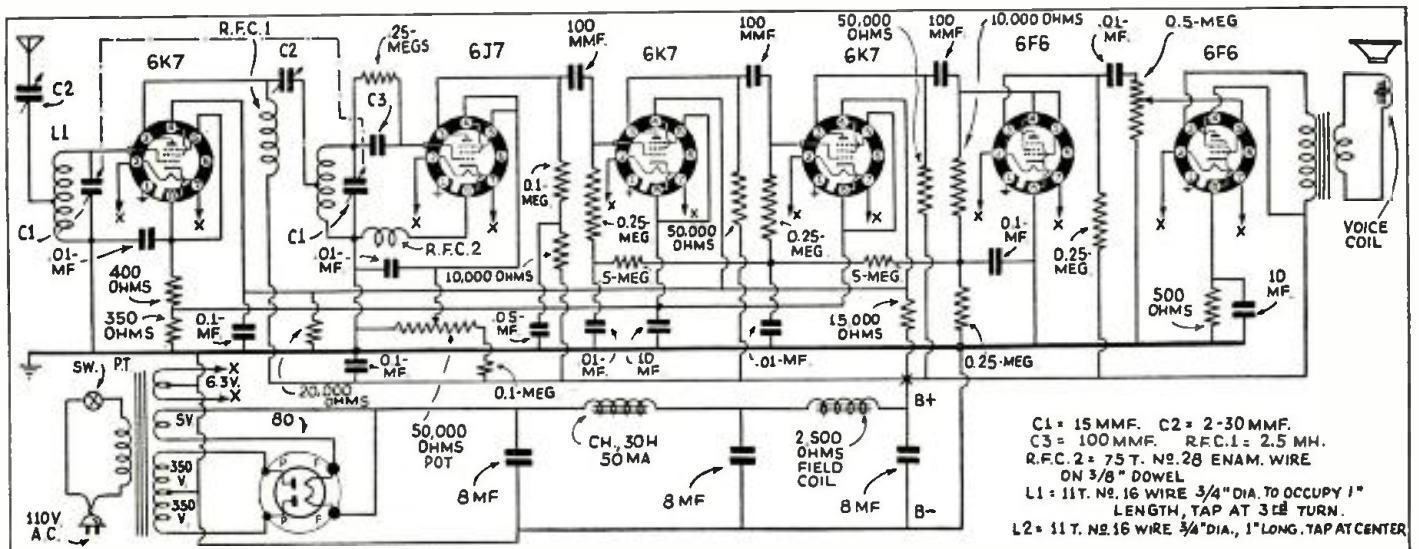


Diagram for the complete 10-meter "super-het". For those who may not be satisfied to tie the "Converter" to their "present" receiver, this complete "super-het" will provide the answer to their 10-meter reception problems.

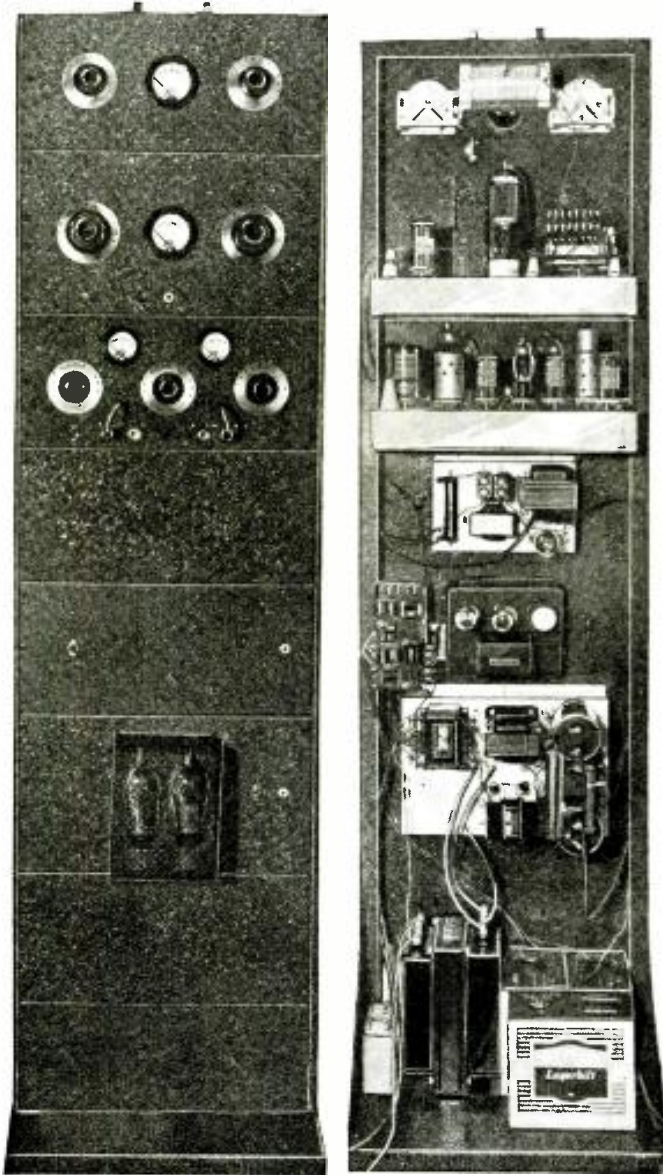

W2AMN's All-Band



Photos at left—close-up, showing front view of the rack and panel transmitter, also rear view in the photo to the right.

watts; with 200 watts on modulation peaks. For CW the output is well over 200 watts. Not a low-power tube by any means.

Rack Stands
6 Feet High

The entire transmitter as can be seen in the photos, is built on a standard 19 inch steel rack and stands six feet high. Looking at the front view we see that the antenna impedance - matching network and the antenna meter occupy the top panel. This panel is 8 3/4 inches high. Next below this is the final amplifier and the plate milliammeter for that stage on a 10 3/4 inch panel. The dial on the right

is the grid tuning and the one on the left is for plate tuning. The jack under the meter is for reading the grid current of this stage. One of the lower small-size meters is used for this purpose. The next two lower panels are the exciter and the power supply for it and which were described last month. Then below the exciter power supply is the modulator for the suppressor grid mounted on an 8 3/4 inch panel. The next panel is for the high voltage power supply and the 866 rectifiers can be seen mounted on the front. For safety we have constructed a wire cage to cover the tubes. This is made of 1/4 inch mesh wire netting and given a coat of black enamel. The panel is the same size as the final. The panels below this are blank and behind them are the high voltage transformer and the bias batteries.

In order to facilitate movement of the transmitter a cradle with ball bearing casters was made to fit under it.

Shunt Feed Used in Plate Circuit


In the diagram of the final amplifier stage, we find that series feed is used in the grid circuit and parallel feed in the plate circuit. There was a good reason for using parallel or shunt feed, in the plate circuit. There is liable to be some slight loss of efficiency with this method, but remember we are using some 2,000 volts on the plate of the final and with series feed we would have high voltage on the coil and tuning condenser. The fact that we have to change the coil leaves us liable to serious consequences, should we fail to remember to pull the high voltage switch. With parallel feed the coil and condenser is at the same D.C. potential as the frame of the transmitter and there is no danger when coming in contact with both at the same time, even if the "B" plus is on.

It is advisable to be extremely careful when working around a transmitter of this type. 2000 volts can cause serious trouble as many past experiences have shown.

● LAST month we described the low power stages of the new transmitter at W2AMN. In this article we will discuss the remaining equipment including the final amplifier, the power-supply and the modulation unit.

CW Output Is Over 200 Watts

As explained previously the final amplifier employs one of the new high-power pentodes. This tube was chosen because of its many excellent features. First it is a screen-grid tube, which means that no neutralizing is necessary. This alone is a distinct advantage. The second remarkable feature is its very modest excitation requirements. Two or three watts is more than sufficient for full output. Then, the third feature is the low audio power requirements when the suppressor grid is modulated; only a few watts are required. Of course for phone, the carrier output is considerably reduced, but even then the transmitter is capable of working plenty of "DX." The carrier output for phone is around 50

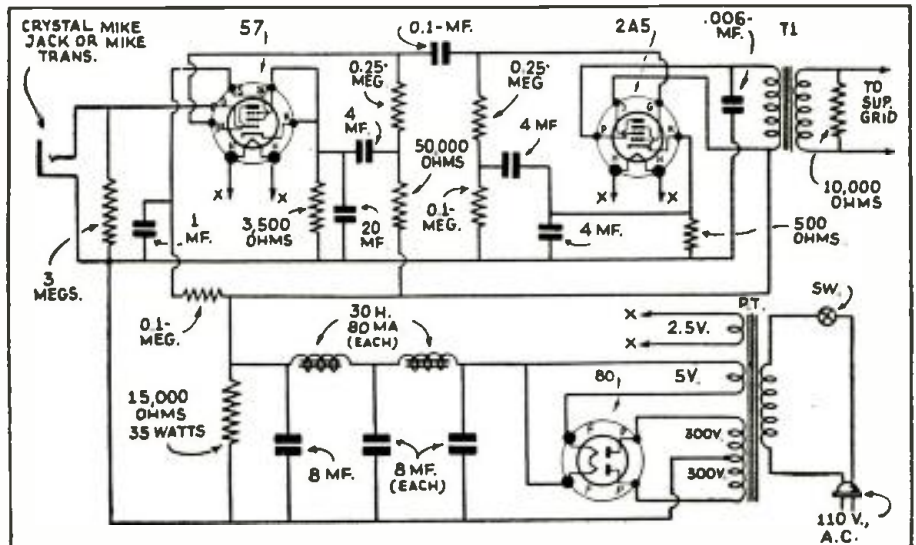

Modulator diagram for suppressor grid modulation.

Transmitter

By George W. Shuart, W2AMN

Part 2—In this article Mr. Shuart describes his modern all pentode transmitter in detail. Complete information is given on the power supplies, modulators, R.F. power amplifier, and antenna system. This transmitter will operate on all amateur bands down to 10 meters using either phone or code. Remarkable results have been obtained on 10 meter phone with this transmitter, which has "worked" Europe, Asia and Africa! It features the new "high-power" pentode transmitter tube.



The complete transmitter in operation. The operating room of W2AMN, showing Mr. Shuart at the controls.

Link Coupling Used Between Buffer and Final Stages

Link coupling was used between the last *buffer* and the *final* stage because of its simplicity and efficiency. In the output circuit we have used the matching network to facilitate the use of a single wire end-fed antenna, which was the best one that could be erected at the writer's QRA. Any other method of course may be used. As the diagram shows plenty of by-pass condensers were used and the reward is absolute stability, even with no tube shield and with no partition between the *input* and *output* circuits. They are of course well separated but should they not be so separated, the shielding would be recommended.

Power Supply

In the power supply diagram we find that for the high voltage a 2,300 volt Thordarson split primary transformer is used. With choke input and under full load this transformer will deliver a full 2,000 volts. When the two Primaries are connected in series the out-

put voltage is 1,000 and this connection should be used while tuning adjustments are being made, in order that no serious damage will be done in case of a m a l a d j u s t m e n t. After all adjustments have been made, save the antenna connection, the primaries are connected in parallel and the antenna connected and necessary coupling and tuning adjustments are made.

Control Relays

We also see that there are relays for controlling the circuits which are to be switched "on" and "off" during operation of the transmitter. These relays are of the *self-locking* type and only a slight touch of a push-button is necessary to perform the operation required.

In parallel with the relay contacts are toggle switches so that the trans-

mitter may be located at a distance from the button board and still, if adjustments are necessary, the transmitter may be operated right from the switches on the panel. One relay opens the B-minus of the exciter and the primary of the high voltage transformer for standby during operation. This is a double-pole, single-throw affair. The other relay turns on all filaments and heaters as well as the primary of the low voltage power supply.

Throughout the parts list and diagrams the values and voltage ratings of the parts are given. These should be followed closely for proper results. Especially the (Continued on page 62)


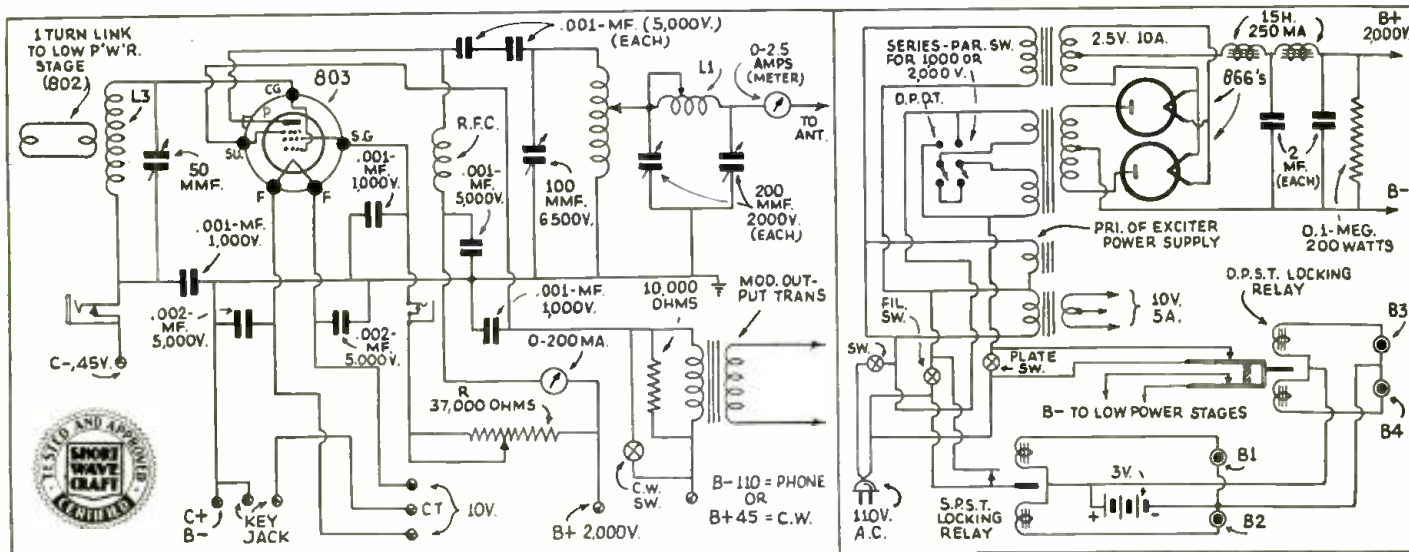


Diagram of the R.F. power amplifier and the high-voltage power-supply, together with the push-button "relay" switching arrangement.

WORLD-WIDE 10-Meter Converter

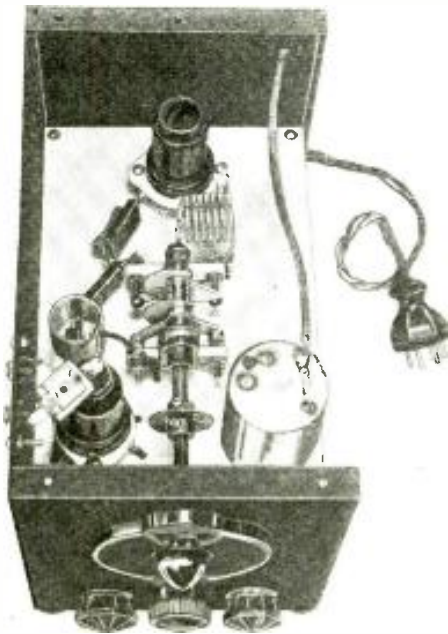

By George W. Shuart, W2AMN



Front view of 10-meter S-W converter. It brings in 10-meter stations "Red-Hot" on your present receiver, if it tunes down to 2,000 kc.

● THE ten meter amateur band is now at its peak, in so far as performance is concerned. Almost any morning one can hear European, Asian and African stations. And not R1 or R2, but from R6 to R8! For the Ham who wants to have an interesting time and work plenty of DX this band offers a wonderful opportunity.

One of the most important parts of the ten meter "gear" is the receiver, most of the older "ham" receivers do not take in the ten meter band, and it is for these that this converter was designed. This converter will work with any fairly sensitive superheterodyne and its performance will be more than gratifying. There is nothing complicated in the construction or operation of the converter and its constructional cost is very nominal indeed.


Only 2 Tubes Required

Only two tubes are used and by glancing at the diagram and remem-

bering that only "DX" with a vengeance! And how! This 10-meter converter rolls the "foreigners" in like "locals"! Simply connect it up with your present receiver and hear "R8" signals from the other side of the world—on 10 meters!

bering that only two tubes are used, one will naturally ask—where is there anything unusual in this arrangement? Well, to be frank, it does not "look" exceptional. But—contrary to expectations, there is tremendous gain in this converter. Yes, we said gain! And experience has proved it.

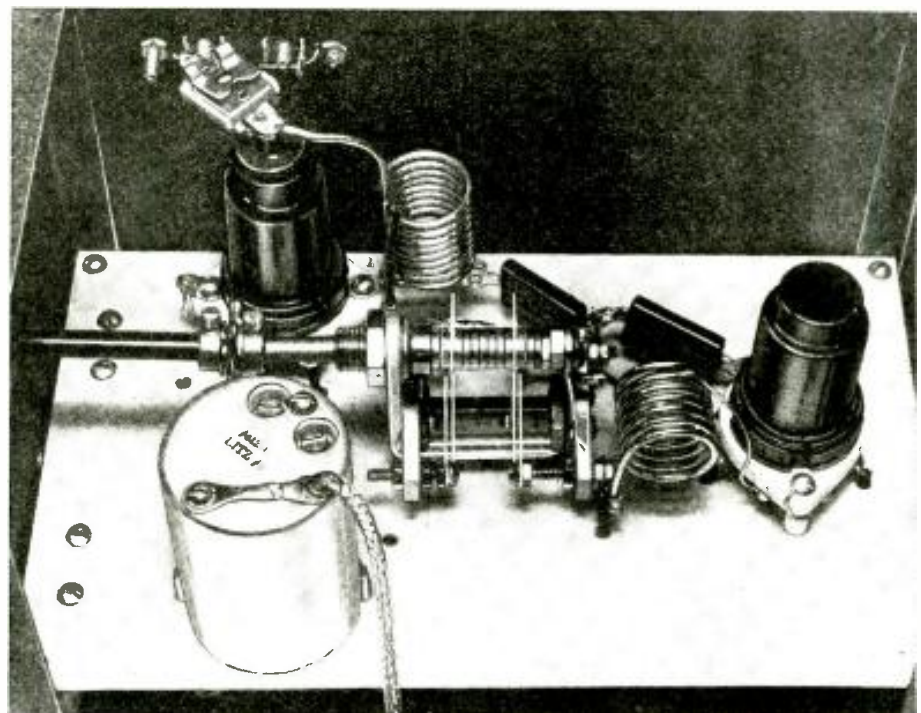The most unusual point is that we have regeneration in this converter and it presents no unusual problem. It just naturally comes about of its own accord here in the first detector circuit. This regeneration makes the detector very sensitive and selective. So selective in fact that



Close-up side view, with cover removed, of the 10-meter converter—it uses but 2 tubes.

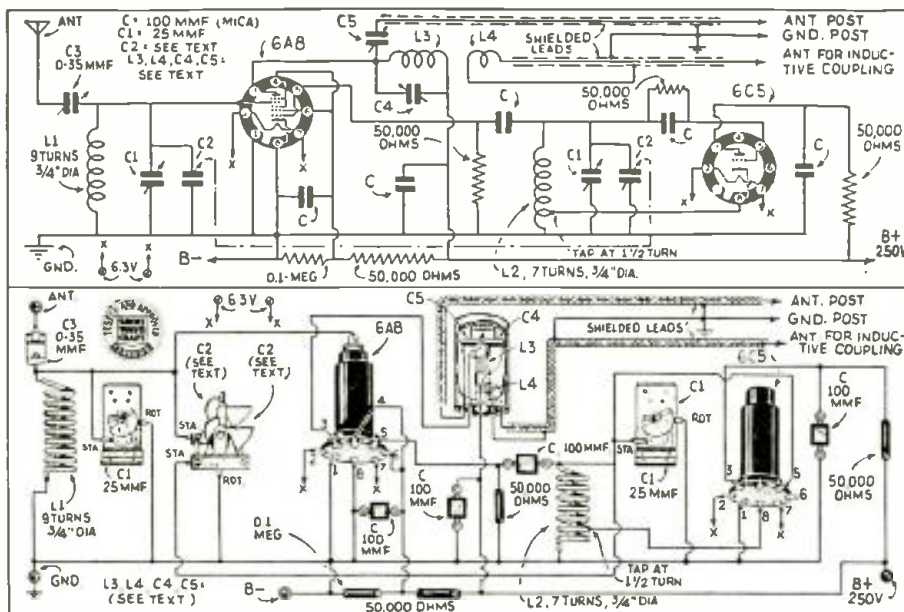


Diagram for building the 10-meter S-W converter.

tuning presented a real problem. At first we expected that the oscillator and detector circuits could be ganged and would "track" with slight difficulty, due to the detector being exceptionally broad on the high frequencies. But operation showed that there was an "Ethiopian in the woodpile" that we had not expected to find.

Feed-back Put to Work

The rule in this case is—if you can't get rid of it, then put it to work! We found that the detector circuit, when unloaded, would oscillate with the oscillator grid coil in its circuit even when the oscillator tube was removed. With the connections employed enough feed-back took place to cause oscillation, but with the antenna coupled to the grid of the detector it stopped. The antenna coupling thus has a control upon this feed-back and this means that for maximum sensitivity, loose coupling should be employed. A peculiar thing this, when the coupling is tightened—the sensitivity decreases and naturally the (Continued on page 51)

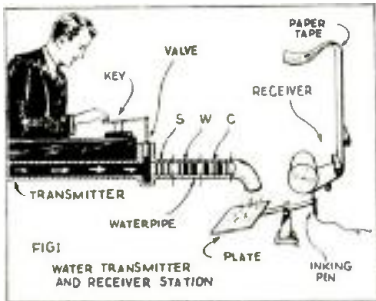


Fig. 1 above shows simple "water jet" analogy of modulation, the signals being transmitted over one water pipe in this instance.

The A-B-C of Frequency Modulation

By Wilhelm E. Schrage


Professor Edwin H. Armstrong, well-known to every short-wave enthusiast, for his numerous contributions to the radio art, recently demonstrated his very latest development—"Frequency Modulation." Mr. Schrage has endeavored with the aid of suitable analogies, to explain in a simple manner just how the Armstrong system of "frequency modulation" works.

● FROM the time radio made its debut up to the present a tremendous amount of work has been done in the research laboratories of many countries to effect a decrease of radio interference. So far as the disturbing noise are concerned, which frequently are created by various electrical appliances actual remedies and circuit tricks have been found which can eliminate all interference of this kind. If the radio listeners are still bothered by a con-

motorized army.

Strange as it may seem, a similar situation to that between the strong Italian and the weak Ethiopian armies now exists between the power radiated by the radio stations and the lightning flashes which are constantly being discharged into the atmosphere around the world.

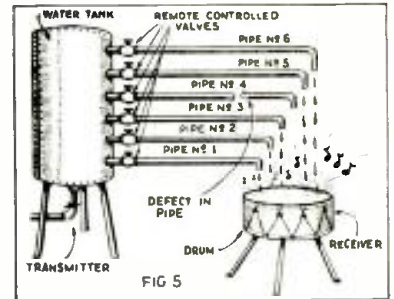Until recently radio waves and lightning flashes had to "march" upon the same broad road, but thanks to a new invention perfected by the famous radio pioneer, Major Edwin H. Armstrong, there are made available tiny roads for the radio waves which cannot be



In Fig. 5, above, an analogy is shown of the new "frequency modulation" system, the signal being carried by numerous channels or pipes.

frequency modulation." This method of modulating a radio transmitter has been known as long as has modern radio communication, but it has been redesigned and improved by Major Armstrong in the last ten years to such an extent that it can now be used for radio transmission.

Signal Transmission by Means of Water


Before we go into the technique of frequency modulation it may be of value to demonstrate by means of an easily understandable experiment the function of amplitude modulation, which is exclusively used for all kinds of radio transmitters now in operation. But since radio waves are invisible we shall take a visible medium to demonstrate amplitude modulation. The best suitable medium for comparison with radio waves is water, and that it is quite possible to use water as a means of communication will be demonstrated by Fig. 1, which shows at the left side a "water-transmitter" and at the right side a "water-receiver."

Code Signal Transmission

To transmit code signals from the transmitter to the receiver the operator uses a valve which interrupts the flowing water into long and short periods, actually consisting of dot and dash impulses. These water impulses are directed against a disc, at the receiving end the disc having an inking pen or stylus which is moved by the incoming code impulses over long or short periods against a paper-tape, where the message is written down as code signals. Experienced readers have recognized already that this communication system by means of water operates in about the same manner as a radio transmitter sending out code signals.

But music transmission: In case music or speech is to be radiated by a trans-

(Continued on page 49)

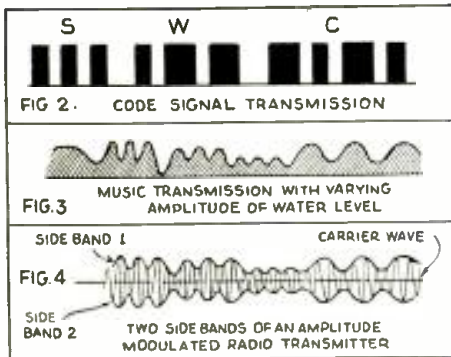

Diagrams above show graphically various aspects of modulation.


siderable amount of these disturbances, despite the fact that all necessary remedies are well-known and ready to be applied, it is not a technical problem, but rather, a financial one.

Lightning Streak vs. Radio Signal

However, so far as atmospheric interference is concerned, even optimistic scientists had discarded all hope that somewhere, some inventor would find a remedy. The main reason for this quite pessimistic opinion was the actual fact, that all radio transmitters in use at present do not radiate as much power into the air as is discharged by one single streak of lightning illuminating the skies for a single split-second.

This argument obviously hits the mark, and indicates impressively that all the tremendous work done by mankind to master the powers of nature may be likened to the effect of a mosquito biting an elephant. However, experience has shown that in a fight between a weak antagonist and a strong one, the strong one may not always win—if the weak one knows how to take advantage of his peculiar abilities.

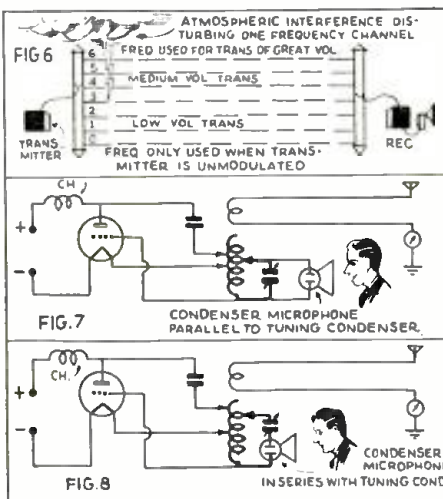One road only to march upon: An interesting example is the present conflict between Ethiopia and Italy. A well-trained army equipped with all the weapons modern science could provide is apparently blocked by an enemy which has the ability to march barefoot over roads not usable by a modern




These diagrams show the principle of radio transmission by means of "frequency modulation," operating with several sets of frequency bands (Fig. 6). Figs. 7 and 8 show how a simple condenser-type microphone may establish simplest form of "frequency modulation."

used by the powerful lightning. Radio waves may now "march" unmolested towards their destination without the danger of being pressed against the "embankments" by a powerful lightning streak, rushing with all its fury over this "common road."

Armstrong's Frequency Modulation

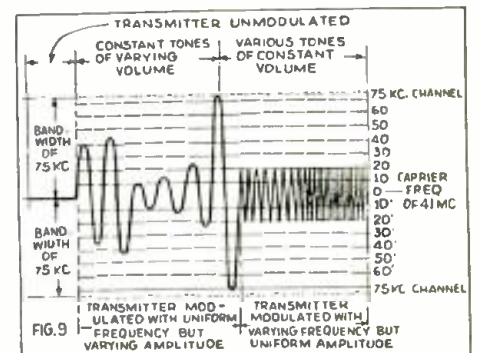The method by which this remarkable progress in radio communication has been accomplished is called "fre-



What the actual frequency band employed by Major Armstrong looks like, when modulated.




A Modern

By Howard G. McEntee, W2FHP

This Month's \$20.00 Prize Winner

Mr. McEntee describes a real "hot" M.O.P.A. transmitter in which a pair of 801's have been added to the well-known "89" transmitter described by W2AMN in a past issue. Excellent performance has been obtained from this transmitter and in order to "clean-up" the 5-meter band, we strongly recommend the MOPA. True, the modulated oscillator has served as a "key" to the ultra-high frequencies, but it is high time it is laid aside for the more up-to-date transmitter, such as the one here described.

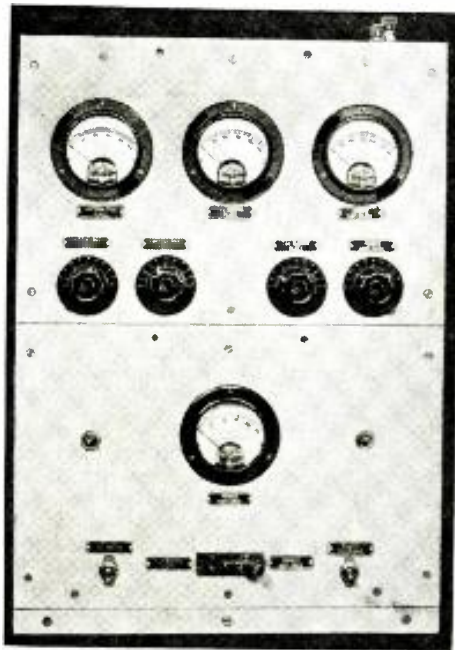

Front view of Mr. McEntee's excellent 5-meter transmitter—she sure packs a mean wallop!

● AFTER working for several years with various types of modulated oscillators, finally ending up with about the most advanced and efficient type of all, the "long lines" transmitter, a hankering was felt for something still more stable, and one that could be received on the best of "superhets" with no trouble. The logical choice, of course, was the M.O.P.A. and it remained only to settle upon the *tube line-up*. The "89" transmitter* described by George Shuart seemed to offer great possibilities, since low cost receiving tubes are used, and it was assumed that two 89's in push-pull would drive any medium low-power final stage. Since highest efficiency for the power used was the aim, two 801's, which are generally conceded to be "tops" for 5 meter transmission, were chosen. Though they cost a little more than ordinary 10's, their smoothness of operation and high output leaves little to be desired.

"Presswood" Rack and Panel Used

Now that the tube line-up was selected, matters proceeded at a fast pace.

*See Feb. 1936 Issue; Page 602.


A rack had to be planned and this was built from 3/4" pine throughout, with top and panels of 1/4" presswood. The panels are each 14"x9 1/4". A strip 14"x3/4" is placed along the bottom front wooden frame member. The frame and the top are enamelled black, and the panels and two chassis, French gray.

As we had no desire to see the 801's "go up in smoke" if excitation failed for any reason, fixed bias was used on them, as well as on the 89 buffers. Two sliders on the C bias voltage divider allow any bias from zero to around minus 200V. The bias runs about 30V for the 89's and 125V for the 801's, with the 475 and 550V, respectively, on the plates. The bias filter choke is a small midget type, as was the bias supply transformer T1. The latter should be capable of supplying 250V and 50 ma., with a 6.3V, 3 A. heater winding, which is used for the 89's and all the meter lighting bulbs. The transformer in the original had no 6.3V winding so a separate filament transformer was needed.

Power Transformer "Specs"

The power transformer is rated at 600V at 200 ma. It has a 7 1/2 V. wind-

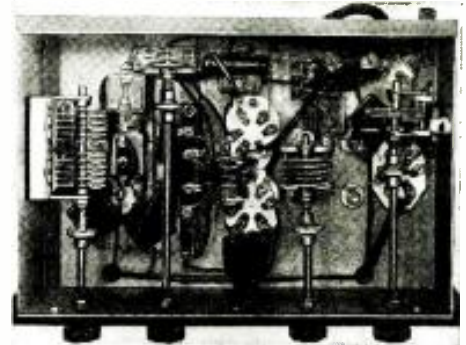
ing, and a heavy 2 1/2 V. winding, besides those for high voltage and rectifier. There was no use for the 2 1/2 V. winding except to light all pilot lamps in the power supply unit. The heavy filter choke is a 250 ma., 15 H. unit, while CH2 gives added filtering for the



Bottom view of the Radio Frequency unit of the transmitter.


89's and drops the voltage somewhat, which is desirable.

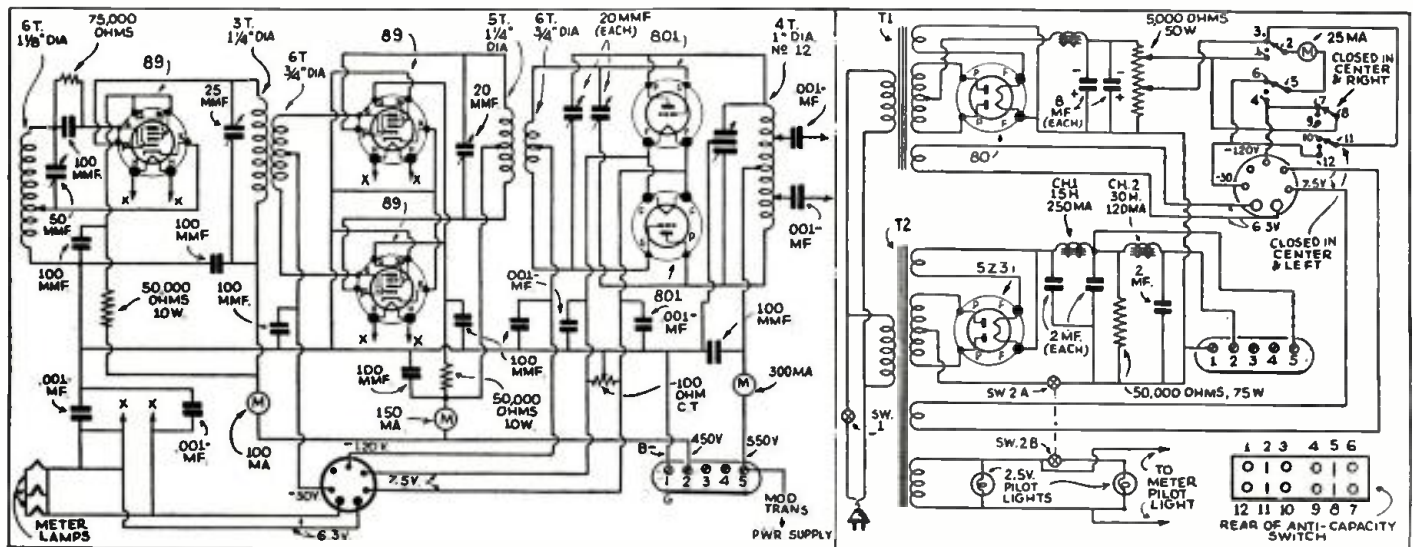The 25 ma. grid current meter is fitted with a switch SW3 to change it from the buffer to P.A. grid circuit. How-



Complete wiring diagram showing how to build Mr. McEntee's 5-meter modern type trans

5-Meter Transmitter

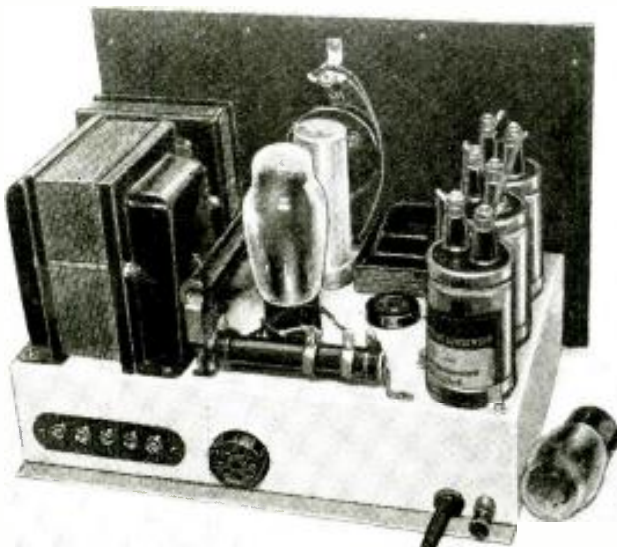

The two photos above show the R.F. amplifier at the right and the power supply unit at the left.


ever, it is hardly ever used for the buffers so this switch may be omitted and the meter left in the P.A. grid lead.

All the meters have small slots cut in

the top of the case so that a pilot lamp can shine through to give indirect lighting. The slot is covered with celluloid to keep out dust. While this lighting doesn't add any efficiency to the

transmitter, it certainly improves the appearance. The pilot lamp connected to SW 2B lights only when the high voltage is on.

(Continued on page 42)

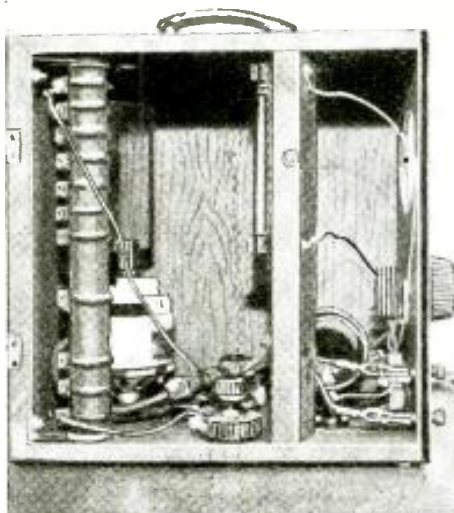


Front view of the Neon tube oscilloscope, which, at slight cost provides the "Ham" with an instrument for checking his modulation.

● HOW many conscientious radio Amateurs have wanted to own an oscilloscope or oscillograph to actually see how their transmitted signals appeared? The cost of such an instrument has probably been more than the average amateur pocketbook could stand, reaching upward from \$50. Most Amateurs, having this amount to spend, would probably decide that \$50 worth of additional transmitting watts would be mere to advantage. Yet, the oscilloscope is just as essential a piece of apparatus as the monitor—and who would be without a monitor—particu-

A NEON Tube Oscilloscope

A Low-Cost Instrument for Checking Modulation

By A. C. Stansfield, W1COL

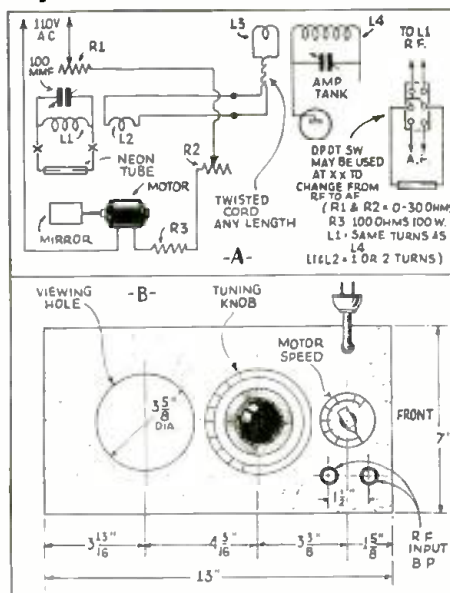

The drawing above shows a front panel lay-out and also diagram of connections of the Neon tube oscilloscope.



A peek at the inside of the Neon tube oscilloscope.


larly the Amateurs operating phone stations. That a phone signal—even correctly modulated—occupies far more space in the radio spectrum than its C.W. brother, is a known fact. If this same phone signal is overmodulated—frequency modulated—it is not only emitting a distorted signal, but is widening its band of frequency occupancy, so that it is "hogging the air"—to put it bluntly!

There is no question but that the true American Amateur is desirous of doing his part in keeping within the Federal limitations and respecting the right of the (Continued on page 55)

5-Meter Super-Regenerator

By H. G. Cisin, M. E.

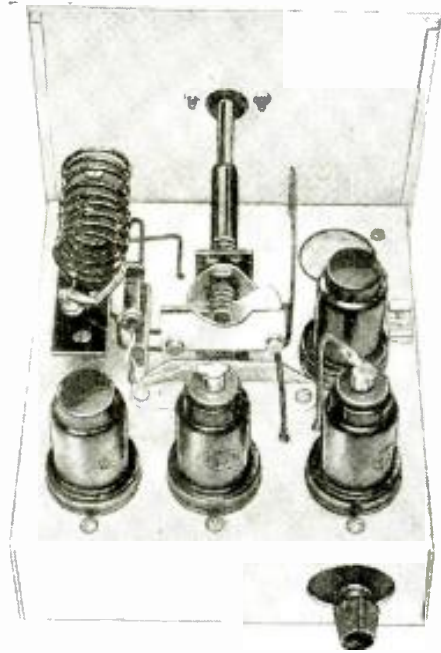This Four Metal-Tube Set Ideal for Amateur and Experimental Reception



Rear view of 5-meter super-regenerative metal-tube receiver.



Front panel view of 5-meter super-regenerative receiver.

average moderate intensity signals and hence this circuit is the writer's choice for *ultra high frequency* reception.

When using this type of super-regenerative circuit, however, it is necessary to guard against extreme radiation, by employing an R.F. stage ahead of the detector. This R.F. stage does not increase the "gain" to any extent, but it does serve to prevent receiver radiation.

The 6K7 R.F. tube is coupled to the 6J7 detector as shown in the schematic diagram. This method allows an adjustment of coupling and therefore does not load the detector input circuit too much. The R.F. signal completes its circuit through the internal capacities of the 6J7 tube, and external circuit to ground capacities. An R.F. choke input is used with tuned receiving antenna.

The super-regenerative detector circuit is of the type known as the blocking grid-leak system. It will be noted that the grid leak return is to a high positive potential. While it would be possible to use the ordinary type of blocking-grid leak with ground return, and still obtain equal sensitivity, the high voltage return prevents detector overloading on strong signals and also results in improved tone quality. The effect is somewhat similar to A.V.C. since signals are all received at approximately the same volume. Hence the manual control in the audio circuit is more than ample.

The standard Colpitts oscillator circuit is employed in the detector. The internal capacities of the 6J7 tube act as the voltage-divider elements, producing the desired oscillation. By using a high value grid-leak, a negative voltage is built up due to the grid current. The decrement of the circuit and the values of the constants includ-

(Continued on page 40)

● EXPERIENCE has demonstrated that the properly designed super-regenerative circuit is superior to a super-heterodyne for *ultra-short wave* reception. This is not because the super can not be made sensitive enough, nor because it cannot be made broad enough for stand-by reception. As a matter of fact, if these were the only requirements, the super-heterodyne would undoubtedly be preferable. However, on five to ten meters, the super-heterodyne circuit—if sensitive enough for amateur requirements—is disqualified for such use, due to the fact that it picks up too much auto-ignition and similar noise interference. A super-regenerative circuit, if designed so that the detector is super-regenerating quite strongly, has a much better *signal-to-voice* ratio for

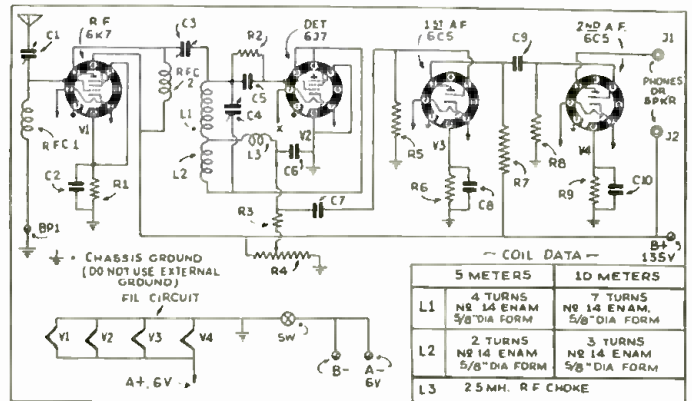


Diagram of Mr. Cisin's 5-meter receiver.

COIL DATA	
5 METERS	10 METERS
L1 4 TURNS NR 14 ENAM 5/8" DIA FORM	7 TURNS NR 12 ENAM 5/8" DIA FORM
L2 2 TURNS NR 14 ENAM 5/8" DIA FORM	3 TURNS NR 14 ENAM 5/8" DIA FORM
L3 25 MH. R.F. CHOKE	

The LAMB "Noise Silencer"

● WHILE there has been much talk about eliminating or reducing man-made interference, it remained for James J. Lamb, technical editor of Q.S.T. to really solve the problem.

So far as we have been able to determine, this is really the only successful method that has ever been proposed or introduced, insofar as the elimination or reduction of noise is concerned. After a great amount of research and study of the character of the various types of noises picked up on the average short-wave set, Mr. Lamb decided that this noise was of such a nature that even if the receiver was inoperative at each impulse of the interfering noise, material alteration of the received signals would not be noticed by the ear. The "pistol shot" or "machine-gun" variety of noise heard in the average short-wave set has actually been caused to "commit

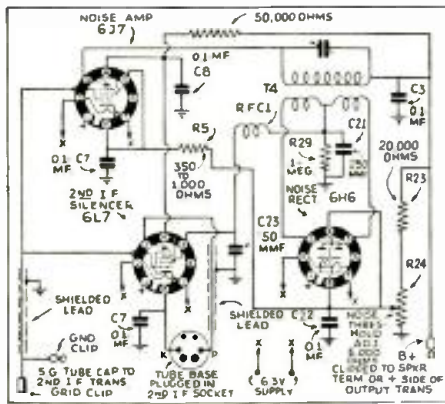


Diagram above shows the relatively simple circuit devised by Mr. James Lamb for noise suppression; the device as shown in the diagram above is connected to the I.F. stages of a good super-set receiver.

suicide" in a very ingenious manner. By referring to the circuit diagram, we find that this noise—as well as the signal—is taken from the grid of the second I.F. stage which uses a 6L7 tube. The noise is then amplified through a 6J7 metal tube and it is then rectified by a 6H6 full-wave rectifier. The resulting D.C. is then applied to the injector grid of the 6L7 second I.F. amplifier tube, from which the signal and noise were originally taken. It can be readily seen that as the strength of the noise increases, the quenching voltage applied to the injector grid as a result of this noise also increases. Thus, the noise is used to cut down the "gain" of the receiver, and the real result is that the noise is cancelled. Through the use of a control indicated as a "noise threshold adjustment" in the diagram, the limits

(Continued on page 39)

A "LOOP AERIAL" S-W Receiver

By Walter C. Doerle

Mr. Doerle this month describes a very interesting 2-tube receiver, using ordinary type 30 battery tubes, the principal feature being a Loop Antenna, which combines a regeneration feature also.


No doubt Frank Buck is without a peer in "bringing 'em back alive" and considering the human elements, human growth and limitations of one desirous of owning a short-wave receiver, a challenge is put to you to build this set, which will bring radio stations in "alive" from the darkest corners of the short-wave globe. And we didn't say "knock 'em cold," but "bring 'em in alive." So here goes.

Guidance Facts For Constructors


The parts for the tuning panel and subpanel have been spread apart a bit



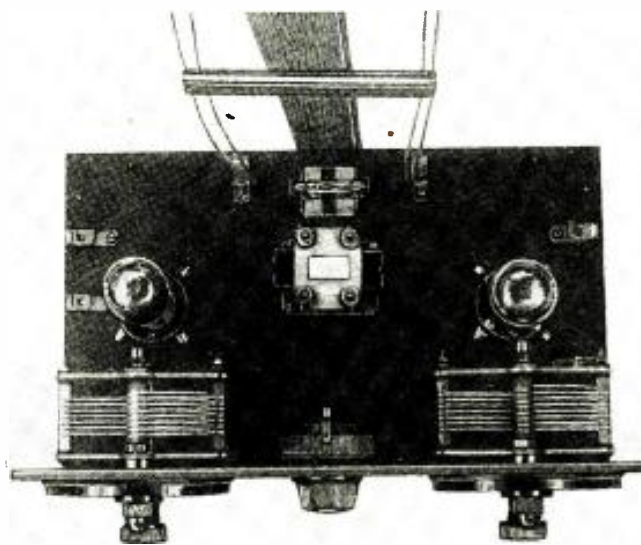A view of the novel receiver here described with its loop aerial.



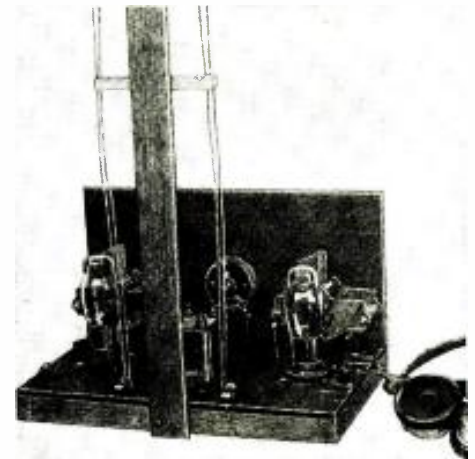
Top or plan view of the "loop aerial" short-wave receiver here described. It uses two type 30 tubes.



Rear view of the 2-tube "loop antenna" S-W receiver.

● BY golly it seems strange that short-wave materials are so sparse among the many radio listeners today and stranger still when one considers the many available opportunities in the short-wave field of activity. For instance, there exists many short-wave publications and one of the best as rated by a college professor known to the author puts *Short Wave Craft* as the "tops." Here you find versatile and

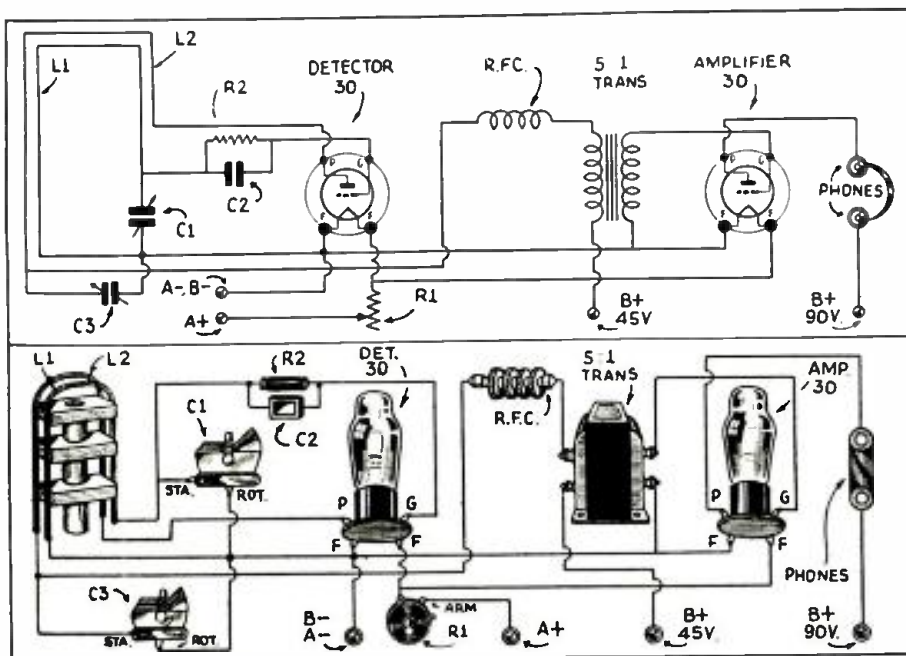"dated" doings in short-wave radio, but when social contacts are made, you don't even find at least a very simple short-wave set in your friends' homes. To fathom this lack of short-wave materials will require some time for solution. However the problem is brought to a conclusion by offering you the description and photos of a short-wave receiving set that can be built at "popular-prices" cost.



Hook-up for the loop aerial receiver.

so as to impress the fact on you that this set is very simple and the number of pieces which comprise it have been reduced to minimum essentials—still retaining the conventional 7"x12" size of panels.

The control panel has mounted on it the two vernier dials, each with its .00035 mf. variable condenser and in the center of this panel is the 10-ohm rheostat and knob which permits controlling the filament voltage for the two type-'30 tubes. Then on the left hand is the station-tuning condenser C1, across which is connected the "loop" L1 (and incidentally the so-called secondary winding of plug-in coils of other receivers). While on the right-hand side is the regeneration condenser C3 connected in series with the loop L2 (so-called tickler coil in usual set) between the plate of the detector and its filament negative side. Why this method of loops—will be given more consideration in the last few paragraphs of this article. At present we have more constructional matters to elaborate upon so that you are not detained with items labelled as "advantages" and "disadvantages."

(Continued on page 59)

SHORT

TWENTY-SIXTH "TROPHY CUP"

Presented to
SHORT WAVE SCOUT

C. T. SCRIMSHER
New Britain, Conn.

For his contribution toward the
advancement of the art of Radio

by



Magazine

26th TROPHY WINNER

62 Stations—45 Foreign

● THE 26th trophy is awarded to Short-Wave Scout, C. T. Scrimsher, New Britain, Conn. Mr. Scrimsher had a total of 62 veris, 45 of which were located outside of the United States.

The receiver used by the winner was a 1936 Philco, model 116 B employing 11 tubes. With this receiver was used a Philco all-wave antenna
(Continued on page 50)

United States Stations

- W1XAL—6040 kc.—University Club. Boston, Mass.
- W1XK—9570 kc.—Relays WBZ. Westinghouse Elect. & Mfg. Co., Boston, Mass.
- W2XAF—9530 kc.—Relays WGY. General Electric Co., Schenectady, N.Y.
- W2XAD—15330 kc.—Same as above.
- W3XAU—6060 kc.—Relays WCAU. Newton Square, Pa.
- W3XAU—9590 kc.—Same as above.
- W3XAL—6100 kc.—Relays WJZ. National Broadcasting Co., Bound Brook, N.J.
- W3XAL—17780 kc.—Same as above.
- W4XB—6040 kc.—Relays WIOD. Miami Beach, Fla.
- W8XK—6140 kc.—Relays KDKA. Westinghouse Elect. & Mfg. Co., Pittsburgh, Pa.
- W8XK—11870 kc.—Same as above.
- W8XK—15210 kc.—Same as above.
- W8XK—21540 kc.—Same as above.
- W8XAL—6060 kc.—Relays WLW. Crosley Radio Corp., Cincinnati, Ohio.



WAVE . SCOUTS

Honorable Mention Awards

L. Lachort, University, Ala.
Melbourne O. Sharpe, Knoxville, Tenn.
C. G. Hurtads, Curacao, P.W.I.

- W9XF—6100 kc.—Relays WENR. National Broadcasting Co., Chicago, Ill.
- W9XAA—6080 kc.—Relays WCFL. Chicago Fed. of Labor, Chicago, Ill.
- W9XBS—6425 kc.—Relays WMAQ. National Broadcasting Co., Chicago, Ill.

Foreign Stations

- CRCX—6090 kc.—Canadian Radio Broadcasting Commission. Bowmanville, Canada.
- CJRO—6150 kc.—James Richardson & Co., Winnipeg, Canada.
- COCD—6130 kc.—"La Voz de Aire." Havana, Cuba.
- COC—6010 kc.—Now COCO. Havana, Cuba.
- XEBT—5990 kc.—Relays XEB. Mexico City, Mexico.

(Continued on page 50)

● ON this page is illustrated the handsome trophy which was designed by one of New York's leading silversmiths. It is made of metal throughout, except the base, which is made of handsome black Bakelite. The metal itself is quadruple silver-plated, in the usual manner of all trophies today.

It is a most imposing piece of work, and stands from tip to base 22 1/2". The diameter of the base is 7 3/4". The diameter of the globe is 5 1/4". The work throughout is first-class, and no money has been spared in its execution. It will enhance any home, and will be admired by everyone who sees it.

The trophy will be awarded every month, and the winner will be announced in the following issue of SHORT WAVE CRAFT. The winner's name will be hand engraved on the trophy.

The purpose of this contest is to advance the art of radio by "logging" as many short-wave phone stations, amateurs excluded, in a period not exceeding 30 days, as possible by any one contestant. The trophy will be awarded to that SHORT WAVE SCOUT who has logged the greatest number of short-wave stations during any 30-day period.

Trophy Contest Entry Rules

● THE rules for entries in the SHORT WAVE SCOUT Trophy Contest have been amended and 50 per cent of your list of stations submitted must be "foreign." The trophy will be awarded to the SHORT WAVE SCOUT who has logged the greatest number of short-wave stations during any 30 day period; (he must have at least 50 per cent "foreign" stations). This period need not be for the immediate month preceding the closing date. The complete list of rules appeared in the September issue of this magazine.

In the event of a tie between two or more contestants, each logging the same number of stations (each accompanied by the required minimum of 50 per cent "foreigns") the judges will award a similar trophy to each contestant so tying. Each list of stations heard and submitted in the contest must be sworn to before a Notary Public and testify to the fact that the list of stations heard were "logged" over a given 30 day period, that reception was verified and that the contestant personally listened to the station announcements as given in the list.

Only commercial "phone" stations should be entered in your list, no "amateur transmitters" or "commercial code" stations. This contest will close every month on the 25th day of the

month, by which time all entries must be in the editors' hands in New York City. Entries received after this date will be held over for the next month's contest. The next contest will close in New York City March 25th; any entries received after that date will be held over till the next month.

The winner each month will be the person sending in the greatest number of verifications. Unverified stations should not be sent in, as they will not count in the selection of the winner. At least 50 percent of the verifications sent in by each listener must be for stations located outside of the country in which he resides! In other words, if the contestant lives in the United States at least 50 percent of his "veries" must be from stations outside of the United States. Letters or cards which do not specifically verify reception, such as those sent by the Daventry stations and, also by commercial telephone stations, will not be accepted as verifications. Only letters or cards which "specifically" verify reception of a "given station," on a given wave length and on a given day, will be accepted! In other words it is useless to send in cards from commercial telephone stations or the Daventry stations, which state that specific verifications will not be given. Therefore do not put such

stations on your list for entry in the trophy contest!

SHORT WAVE SCOUTS are allowed the use of any receiving set, from a one-tuber up to one of sixteen tubes or upwards, if they so desire.

When sending in entries, note the following few simple instructions: Type your list, or write in ink, pencilled matter is not allowed. Send verification cards, letters and the list all in one package, either by mail or by express prepaid; do not split up the package. Verification cards and letters will be returned, at the end of the contest, to their owners; the expense to be borne by SHORT WAVE CRAFT magazine.

In order to have uniformity of the entries, when writing or typing your list, observe the following routine: USE A SINGLE LINE FOR EACH STATION; type or write the entries IN THE FOLLOWING ORDER: Station call letters; frequency station transmits at; schedule of transmission, if known (all time should be reduced to Eastern Standard which is five hours behind Greenwich Meridian Time); name of station, city, country; identification signal if any. Sign your name at the bottom of the list and furthermore state the type of set used by you to receive these stations. State total No. stations.

WORLD-WIDE SHORT-WAVE REVIEW

-Edited By C. W. PALMER

The Fly-Wheel Dial



● A NEW dial has appeared in several new French sets, known as the gyroscopic dial—from its similarity in operation to the gyroscopic compass with its rapidly spinning fly-wheel.

This dial is meant to facilitate tuning on the short-wave bands. When you tune the set, the reduction ratio slows down the movement of the tuning condenser to make station location easy. But when, as is often the case on the short waves, you desire to shift to another part of the band, you simply give the knob a "spin," and the heavy flywheel keeps it moving. Then, at the desired point, a touch stops the dial for close tuning.

This spinning dial is also useful in locating stations, as a spin will carry the condenser across the band, sufficiently slow so that a carrier will usually be heard. Then, a slight turning back is all that is needed to find the station.

This dial was shown in *Science et la Vie* (Paris).

A 5-Meter Super-Regenerative Set


● AN unusual use of the American 2A6 tube was mentioned in the latest issue of *Radio-Ref* (Paris).

The owner and constructor of amateur radio station F8VS has found that this tube has desirable characteristics for use as an ultra-high-frequency detector in a super-regenerative set, when used as a triode.

When used in this way, the diode plates and the cathode are tied together. This leaves the tube as a straightforward triode. The arrangement of the circuit is shown here. The second tube is the suppressor frequency generator, with the large honeycomb coils S4 and S5.

The coils S1, S2 and S3 are the usual tuning coils used for 5-meter regenerative or super-regenerative sets. The other values are indicated on the circuit.

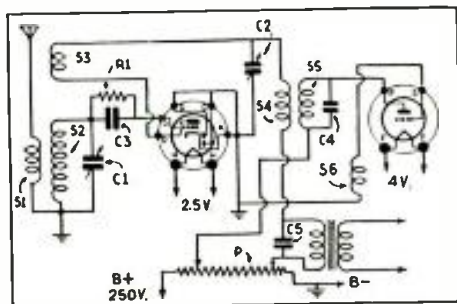Experimenters, who like to try new circuit hints might try the 2A6 in this new and unusual way. (This type of tube was advocated in George Shuart's "Hiss-less" superregenerator; see Nov. 1935 issue S.W.C.—Editor.)




"Hams" will find of interest the 5-meter Super-regenerative receiver hook-up shown in the accompanying diagram; it was devised by a French amateur.

● The Editors have endeavored to review the more important foreign magazines covering short-wave developments, for the benefit of the thousands of readers of this magazine who do not have the opportunity of seeing these magazines firsthand. The circuits shown are for the most part self-explanatory to the radio student, and wherever possible the constants or values of various condensers, coils, etc., are given. Please do not write to us asking for further data, picture-diagrams or lists of parts for these foreign circuits, as we do not have any further specific information other than that given. If the reader will remember that wherever a tuned circuit is shown, for instance, he may use any short-wave coil and the appropriate corresponding tuning condenser, data for which are given dozens of times in each issue of this magazine, he will have no difficulty in reconstructing these foreign circuits to try them out.

A S.W. Reflex Set

● A RECENT issue of *CQ-MB* (Berlin) a magazine published for radio amateurs, contained the circuit of a short-wave set which experimenters in this country will find interesting.

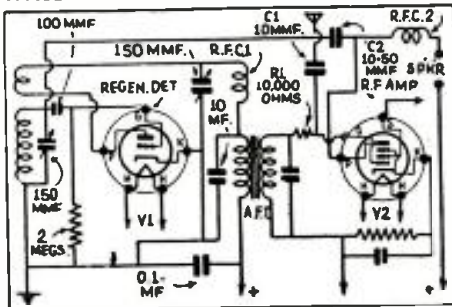It is a reflex of two tubes, in which the pentode acts as an untuned R.F. amplifier; the triode acts as regenerative detector and the pentode serves a second purpose of A.F. amplifier. The signal is fed to the grid of the pentode through C1. It is amplified and then passed through condenser C2 to the grid of the detector. It is detected and then fed through the A.F. trans-



A clever Reflex circuit; the triode is the detector.

former to the pentode control grid and is amplified at audio frequencies.

The values of the parts in this experimental circuit are given. With a few changes, many short-wave sets can be converted to use this ingenious stunt. Why not try it, fellows?


A Novelty in Cabinets

● EVERY once in a while, a really new and original idea is brought out in such an inauspicious way that we are inclined to accept it in a matter-of-fact manner, instead of giving it the attention it deserves.

Such an idea appeared recently in *Practical and Amateur Wireless*, (London).

It has been the practice of set builders in that country to make their sets on wooden or metal subpanels, with upright panels on the front, similar to the sets made in the U.S. by home set-builders.

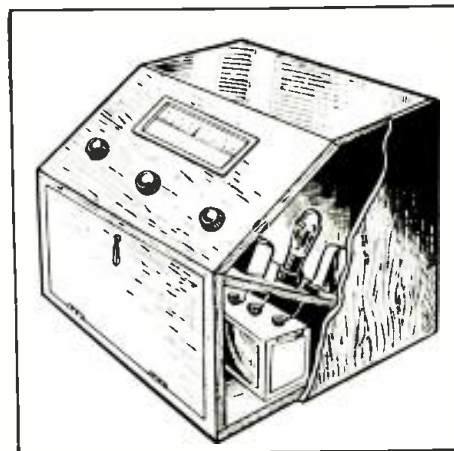But it has become almost universal in that country to use slanting panels in commercial sets, to facilitate reading the tuning dials. In order to permit a home-built set of the type described above to look like a commercially made one, an ingenious experimenter mounted his set as shown in the illustration. This gave the desired result, as well as permitting him



The slanting control panel for receivers is, without a doubt, gaining in popularity daily in this country. One method of accomplishing this effect is shown above.

to use his favorite set without having to rebuild it.

Incidentally, the front panel can be used to mount the dynamic speaker as well as conceal the batteries (if it happens to be a battery set).

The advantage of the sloping panel is obvious—American short-wave fans will find it a distinct advantage in tuning.

S.W. Coil Making


● A NOVEL and efficient way to make ultra-short-wave coils is by the method shown in the illustration here. It consists of four glass tubes, such as test tubes, around which is wound the wire forming the actual coil.

The use of such small tubes makes the coils almost self-supporting, that is, they have the least possible amount of insulating material to cause losses.

The coils with their glass supports are mounted by means of clips made from sheet metal, bent as shown. The metal supports also form coil connections, by soldering the ends of the coil wire to them. Stand-off insulators can be used to mount the coils, or other methods can be devised.

The glass tubes on which the coils are wound can be small bottles, such as the type in which aspirin is sold, for larger coils, test tubes will serve nicely. Celluloid cement will serve to hold the four tubes together for winding.

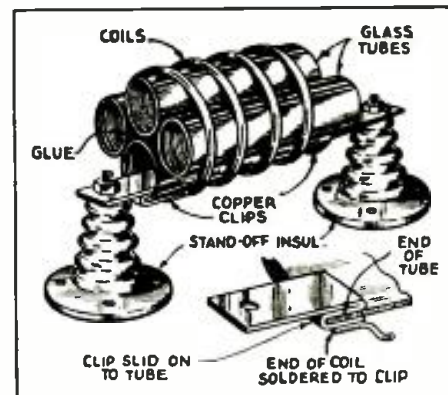This novel coil winding hint was shown in an issue of *Practical and Amateur Wireless* (London) recently.




Above—A novel method of constructing an insulating form on which to wind short-wave coils—it is made from several glass tubes; even test tubes may be used.

\$5.00 Prize


\$5.00 FOR BEST SHORT-WAVE KINK

The Editor will award a five dollar prize each month for the best short-wave kink submitted by our readers. All other kinks accepted and published will be awarded eight months' subscription to **SHORT WAVE CRAFT**. Look over these "kinks" and they will give you some idea of what the editors are looking for. Send a typewritten or ink description, with sketch, of your favorite short-wave kink to the "Kink" Editor, **SHORT WAVE CRAFT**.

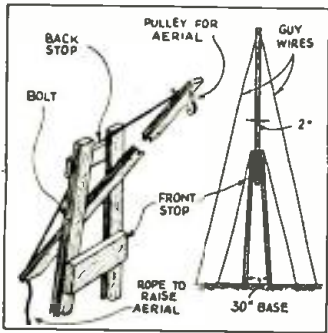


"ONE-MAN" AERIAL MAST

Here is an idea for a "one-man" aerial mast; I erected one 50 ft. high. I do a lot of aerial work and I find this to be the easiest way to get them up and down. I take two pieces 2" x 3" and spread one end about 30" and the other 2", and nail these in position with a 1" x 2" board. Next I drill a hole about 3" from the top; this is where the upper portion of the mast is fastened. The top piece is usually a 24 ft., 2" x 2" piece. A hole is drilled about 6 ft. from one end. This piece fits between the other two and is bolted. You will notice that the top piece is now on a pivot. The guy wires are all attached and the lower section of the mast can be raised by pushing up with the top portion. A rope should be attached to the short end of the top piece.—C. R. Vogler.

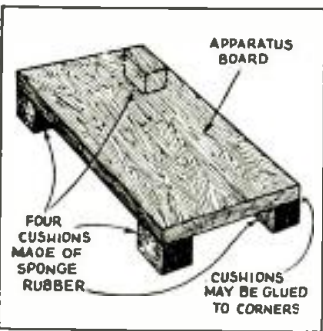

ELIMINATING TRANSMITTER VIBRATIONS


The frequency stability of a breadboard transmitter, employing the much used Hartley or pushpull circuits, can be greatly improved by mounting the board on sponge rubber cushions, of the same width, length and thickness, placed under each of the four corners of the board. The sponge rubber cushions compensate for shifts in frequency due to jarring the instruments. W8STJ used this method with considerable success. Most "ham" stations worked reported remarkable stability of signals, upon learning that the circuit employed was the single 210 Hartley using two 81's in the rectifier supply with 500 volts in the plate circuit.—Justin M. Walker.

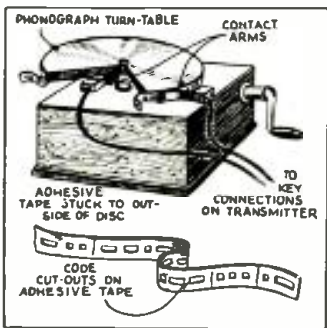

AUTOMATIC KEY


When this key is hooked to the transmitter it will send what you desire endlessly. The arm was made of scrap tin and hooked to a suitable base. (Note—make your cuts in the tape wide enough so that the point of the arm fits into them.) Of course you will have to experiment with the slots to suit your own taste.

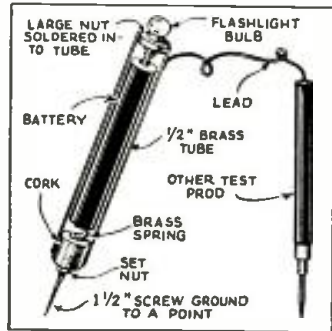For beginners who are learning the code, this is a valuable instrument when connected to an audio oscillator.—Charles Simmons, Jr.




NOVEL TEST PROD

I hope the rest of the fellows can find as many uses for this "kink" as I have. One will find first a brass or metal tube, which is 5 1/2 inches long by 1/2 inch inside diameter. Next solder into one end a nut which a flashlight bulb will screw into. After this find a plain cork which will fit into the tube, and punch a small 1/2 inch screw, that has been filed to a point through it. Then take a small brass strip, drill a hole in one end, and bend into a "U" shape for a spring. Next slip the bolt through this, then through the cork and fasten with a set-screw. Then solder an 18 inch wire, which is fastened to an ordinary test prod, to the top of the brass tube, slip a pen-light battery in and insert the cork. The test prod is now complete and ready for use.—Dave McGuire.

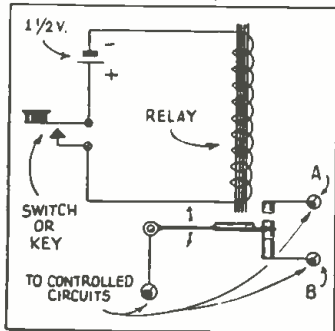


ALL PURPOSE RELAYS

Here is a useful kink which will put some of that "junk box" material to work. On many of the old "B" eliminators and trickle chargers, a small relay is used to throw the A.C. line to charger or eliminator. These relays are very sensitive, and require only a 1 1/2 volt dry cell to operate. They may be used as a START or STOP relay. The writer is using two of these units in a remote-controlled transmitter. One is used as a "standby" switch, while the other is used as a "keying" relay. The keying relay responds perfectly up to 25 wpm, which happens to be the writer's limit.—W. C. Bellheimer.

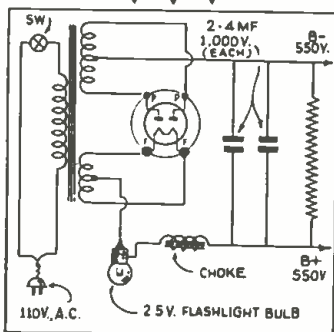


BULB AS FUSE

Herewith is a kink that I believe would help a lot of "hams" in the positive high voltage lead between the filament center tap of the rectifying tube. I use a 2 1/2 volt bulb before the "HV" goes into the choke. Now if you should happen to blow a filter condenser or a plate blocking condenser or if anything should happen to cause a direct "short" on the power supply, this bulb will burn out and not do any harm to the rectifier tube of the 81 type, which won't stand a lot of "shorting." In case you draw an excessive amount of milli (M.A.) caused by overload the bulb will light up and warn you.—N. M. J'erson.

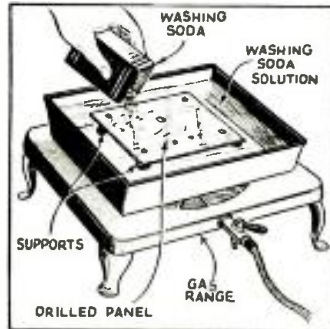

PROF. FINISH FOR PANELS

There is a solution to the problem of having a professional like finish on aluminum panels without the use of lye. After the panel is all drilled, make a solution of two handfuls of washing soda and two quarts of water. Lay the panel "face-up" in a pan that will hold the panel when it is supported by four supports. These supports may be made of stone or other like substances. The panel must be completely covered with this solution. It is now only necessary to boil the panel in the solution until all traces of dirt and scratches disappear. Then rinse the panel in cold water and dry it.—Edward Koch.

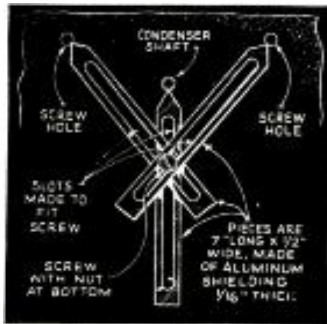


DRILLING GAUGE


While this kink is not new or original with me, I pass it along to the readers of Short Wave Craft. It is rather difficult at times to mount condensers requiring two or more mounting holes. By slotting three strips, as shown in the drawing, and holding them together with a screw, the mounting holes can be drilled accurately.—Melvin E. Conwell.

IRON HOLDER

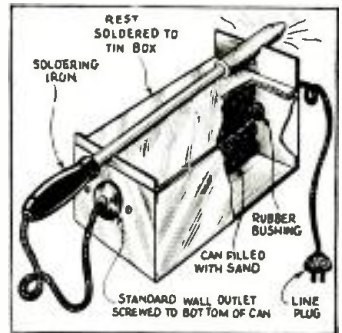After having much trouble with the soldering iron stand sliding all over the bench, I hit upon the following idea: I filled a square tin can with sand and




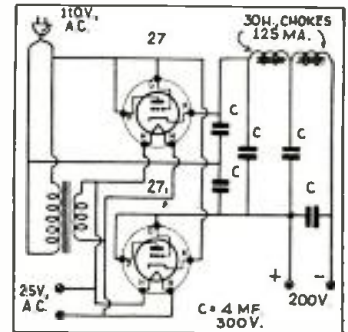wired it over the soldering iron as shown in the diagram. This provides a relatively heavy stand, and is more convenient in every respect than manufactured ones.—H. F. Dunn.



HANDY POWER SUPPLY

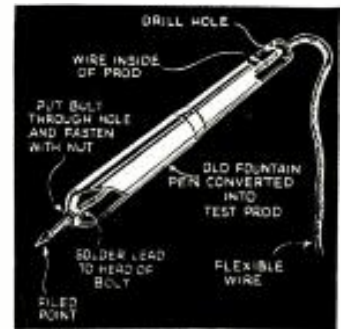Recently, when in need of a power supply, I constructed one with parts found in my junk box and it gave very satisfactory results. Therefore, I am passing this along to the readers of Short Wave Craft as a "Kink." Although it is not original by any means, I feel that a great many readers will be interested in it.—Robert Lyon.




NEW USE FOR OLD FOUNTAIN PEN

I built a testing instrument and needed a pair of test prods, and the following idea was carried out. Two old fountain pens, which were of no particular value, were procured and remodeled as shown in the sketch. A screw projects from one end forms the point or tip, while the cord or test-lead runs up through the fountain pen and out the other end.—Jim Morris.

PAPER CLIP CONNECTOR

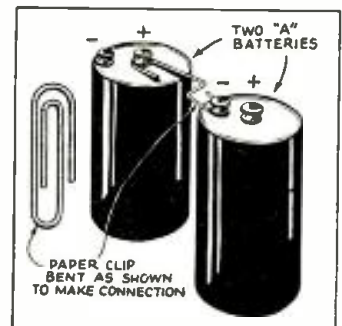Here is a "Kink" for Short Wave Craft. I used a bent paper clip as a connector between two dry cells. This is quite a time-saver, especially as many connections are to be made. The forming of the paper clip is clearly shown in the drawing.—Harry Wrasko.



Oh! for a Ham "Shack" Like One of These

Prize Winner--Lieut. W. W. Johler

Editor, SHORT WAVE CRAFT:

Short Wave Craft has formed part of my technical library for the past number of years. I would be interested in having the picture of my "rig" published in this popular magazine.

The "rig" shown in the photo is located at Kemper Military School, Boonville, Missouri. It is operated by licensed cadets and faculty officers. It enables cadets who have their license to continue with the fascinating hobby and stimulates interest in radio in many others.

The "rig" as shown is of metal chassis construction in a wooden rack. The bottom three racks contain a 1,250 volt power supply, with a pair of 66's for the final plate, 800 volt power-supply, with two 83's in parallel for the oscillator and buffer, separate filament transformers for each stage, and bias for the final. Above that are a 59 tri-tet crystal (Continued on page 61)

W9NTP Has Efficient "Ham" Station



Ambitious array of Transmitters and Receivers in Billy Brentlinger's Ham "Shack."

Editor, SHORT WAVE CRAFT:

I sure get a big kick out of Short Wave Craft with all the interesting circuits and ideas etc. I started reading Short Wave Craft when it was published just every two months. I enjoy looking over the pictures of the "ham" stations, several of whom I have talked to several times, but I didn't know how they looked.

The outfit on the left side belongs to W9NBZ, my radio pal. It is a 47 xtal osc. 2-46's buffer or doubler, a 203A in the final amp. with about 200 watts input which is modulated by four 46's in class "B."

The outfit on the right is my old "ether pusher." It is a 47 xtal osc., 46 buffer or doubler, a pair of 46's in parallel in the final amp. with about 40 to 50 watts (Continued on page 61)



Prize this month goes to Lt. W. W. Johler's "rig."

Paul Bauerle's Station at Lansing, Mich.

Editor, SHORT WAVE CRAFT:

I have been a reader of your radio magazine for some time. The tubes used in my transmitter are 47 crystal, 210 doubler, 211 buffer, 204A final amplifier with 400 (Continued on page 61)



Paul Bauerle's "Ham" Shack at Lansing, Mich.

Amateur Radio Station VU2FY, India

Editor, SHORT WAVE CRAFT:

This magnificent amateur radio station is located in tropical south India, eleven degrees from the Equator. It is owned and operated by Mr. O. A. F. Spindler, a leading Amateur of International fame.

On the right of the photo may be seen the crystal-controlled Xmitter, which is built in three tiers. The bottom tier houses the power supply, which is from A.C. mains, stepped up and rectified. The center tier houses the modulator, and the upper tier the high-frequency components. Two crystals are used, the use of either being controlled by a change over switch, giving four frequencies, one on 14 mc., two on 7 mc. and one on 3.5 mc.

To the left of the transmitter may be seen the General Radio wavemeter and the loud-speaker which is used when signals are too strong for phones.

At the right of the operating table may be seen the speech amplifier, which is built in a steel cabinet, and connected to the modulator by shielded cable to avoid pick-up from transformers.

In the center of the table may be seen the monitor with the change-over switch from receiver to monitor just in front.

At the left of the table are two receivers, the Eddystone Amateur Bands Two, and the Eddystone Screened Grid Scientific Three, which is used for DX fone work. Both receivers are connected to the power supply in parallel, (Continued on page 61)



From India! Amateur Transmitting and Receiving Station of O. A. F. Spindler, call VU2FY.

A Sensitive 4-Tube "Regen." Superhet

By Harry D. Hooton, W8KPX



Front view of Mr. Hooton's regenerative superhet.

● THE super-heterodyne, long considered a luxury by the average short wave fan, is now almost a necessity for use on the crowded *amateur* and *short-wave broadcast* bands. The author has for some time desired a "really good" superhet, with plenty of gain and selectivity, for general DX (distance) work but, since he is limited to the use of batteries for receiver power supply, the cost and upkeep of an "eight" or "ten" tube set would be considerable.


The use of regenerative circuits offer many interesting possibilities for simplifying superheterodyne design and construction. As pointed out in the "Super-Gainer" article on page 470, December 1935 *Short Wave Craft*, a single regenerative first detector provides almost as much gain and image selectivity as can be obtained from two or more R.F. stages using the most expensive construction. The author's own experience with the new all metal tubes has convinced him that these, because of their ease of oscillation, extreme quietness and self-shielding qualities, are ideal for use in regenerative R.F. and mixer circuits. Therefore, it was decided to design a high-gain superhet around a regenerative first detector, metal tubes and the new *iron-core* I.F. transformers. The finished receiver is described in this article.

We are glad to present this article by Mr. Hooton describing his new 4-tube superheterodyne. By using multi-purpose tubes and employing regeneration in the first detector, very good sensitivity is obtained. This set also features the new iron-core I.F. transformers. Complete details are given by Mr. Hooton in the accompanying text.


First Detector Is Electron-Coupled

As shown in Fig. 1, the first detector is of the familiar electron-coupled type, almost identical with the detector circuit of the average regenerative receiver. The *oscillator* is of the conventional variety, the tickler being placed in the cathode circuit for increased stability. The output of the oscillator is coupled to the first detector by the suppressor-injection method. The new high efficiency all-metal tubes are used in both circuits—a 6J7 as first detector and a 6C5 as oscillator. The output of the 6J7 is fed to one of the new iron-core I.F. transformers which is tuned to a frequency of about 456 kc. This is in turn connected to the pentode section of a 6F7 triode-pentode tube where the I.F. signal is amplified and then fed through another iron-core I.F. transformer to the triode portion of the 6F7 which acts as a *second detector*.

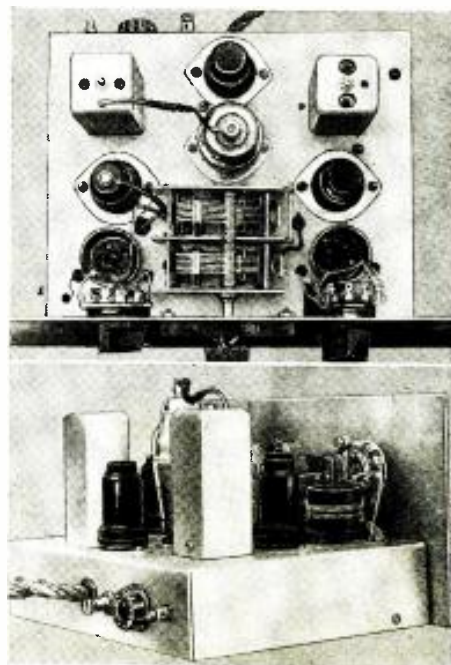The overall gain of the iron-core transformers and the 6F7 tube is about equal to that obtained from the usual two stages of I.F. and detector using the ordinary air-core I.F. transformers. This receiver (Continued on page 54)



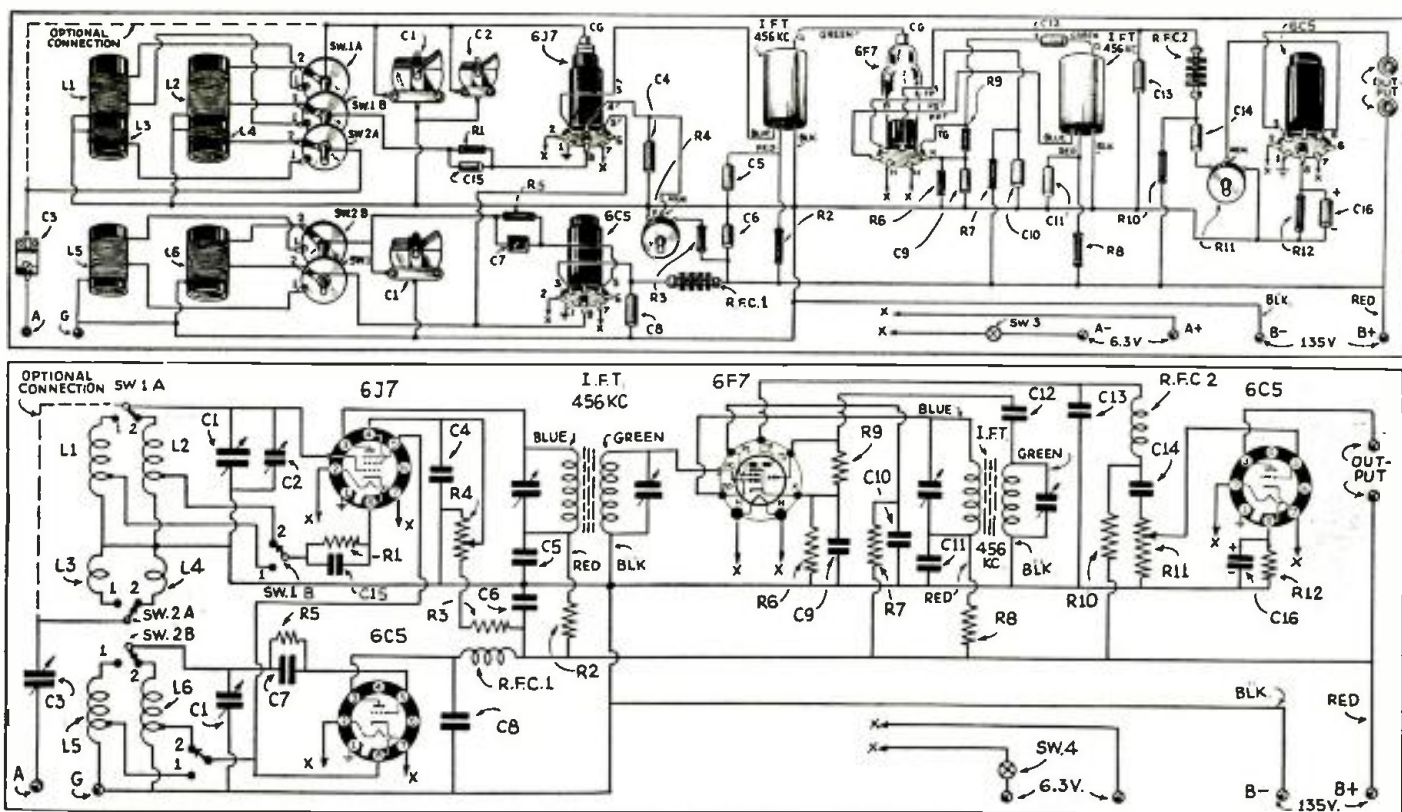Rear view, showing the placement of the parts.




Schematic and physical diagram for the complete superheterodyne short-wave receiver, which employs a regenerative detector.

WHAT'S NEW

The short-wave apparatus here shown has been carefully selected for description by the editors after a rigid investigation of its merits

In Short-Wave Apparatus

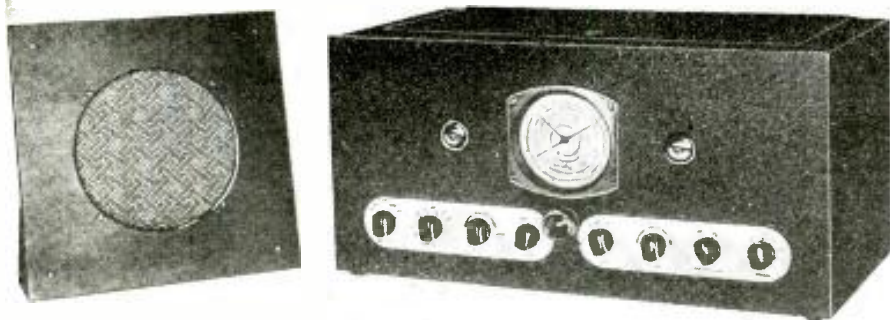New ACR-175 Amateur Communication Receiver Has Range of 5 to 600 Meters Continuous



Complete ACR-175 Amateur Communications Receiver with loud-speaker furnished with the set.

ed and ready for immediate operation. Headphones and speaker, or headphones only, may be used.


Ease of tuning and band-spread are provided by two large diameter knobs mounted concentrically on the tuning shaft. The inner knob operates at a low ratio (20 to 1) and permits any range to be traversed rapidly. The outer knob operates at a higher ratio (100 to 1) and permits extremely fine tuning. A unique dial permits the positive logging of stations of any frequency without resetting to a reference point. The main scales are calibrated in megacycles and are traversed by a double-ended pointer, one end of which also covers a coarse scale of nine equidistant divisions serving as a vernier index. A slightly longer
(Continued on page 61)

● THE ACR-175 Amateur Communication Receiver presents a combination of advanced features not found in receivers selling at considerably higher prices. The ACR-175 has been designed to meet the rigorous requirements of receiver performance necessary to maintain communication in the crowded popular amateur bands. An advanced degree of selectivity, sensitivity and ease of operation is now available.

A superheterodyne circuit is employed with one tuned R.F. stage for ranges A, B and C (500 kc. to 15,500 kc.), thus assuring low image-frequency response and high signal-to-noise ratio. A separate rejection filter is placed in the antenna circuit to minimize interference from powerful commercial stations operating near the I.F. frequency. Iron-core transformers in the I.F. amplifier provide unusually high gain and added selectivity. A quartz crystal, having special orientation and dimensions, assures unusual single-signal response heretofore unattainable. An electron-ray tube serves the dual function of tuning meter and indicator for measuring the strength of incoming signals.


All the controls on the ACR-175 are conveniently located on the front panel.

The coils are fixed and selected by a switch. The sensitivity control is calibrated logarithmically in terms of microvolts of signal input to the receiver. The value of signal-input voltage is read when a deflection just begins to occur on the face of the electron-ray tube. This method of signal measurement in units of absolute value is more accurate and dependable than the arbitrary values now in vogue. A "stand-by" switch removes the plate voltage from the tubes and illuminates a green pilot light, but leaves the heaters light-

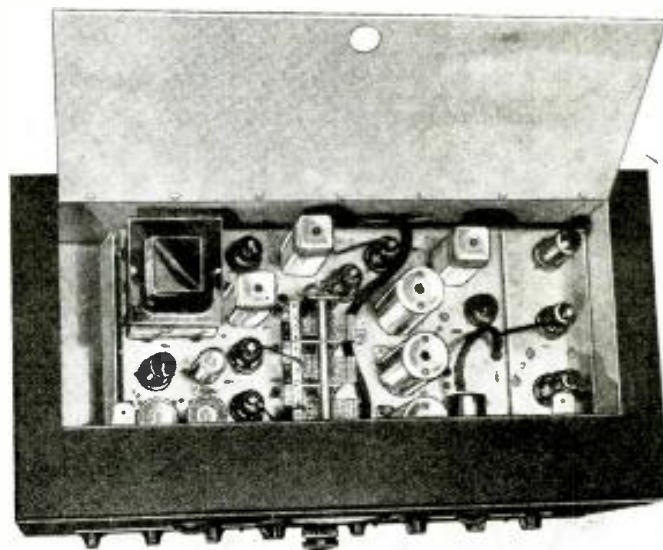

Interior view of the ACR-175, showing neat arrangement and accessibility of the parts and tubes. (No. 539.)

AN AUTOMATIC ANTENNA SWITCH

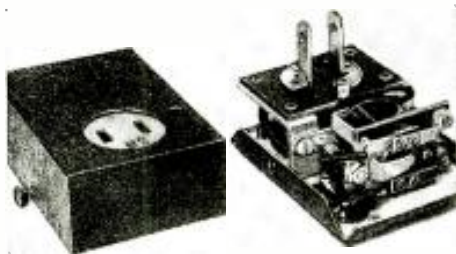

An automatic antenna switch fitted with a relay which connects the aerial and ground to the particular set plugged into the 110-volt socket on the box. (No. 537).


● FOR those desiring to operate more than one receiver from an antenna system, such as for demonstration pur-

poses in sales rooms, this automatic antenna switch is an extremely valuable piece of apparatus. It is not designed to permit the operation of a number of receivers simultaneously from a single antenna, but so connects the circuit that when the A.C. switch of the receiver is turned "on", the antenna and ground are automatically connected to the receiver.

For the benefit of those interested in the circuit, a schematic diagram is given and it can be seen that the field of the relay is in series with the 110-volt lead going to the set. The relay is a double-pole, single-throw affair having fairly heavy contacts. Amateurs, experimenters and Hams may adapt this relay or the principle involved to perform some very novel operations. For instance, if connected properly this relay can be made to turn on the "transmitter" automatically, when the receiver is turned "on." Many other uses, of course, will suggest them-

selves to the average experimenter.

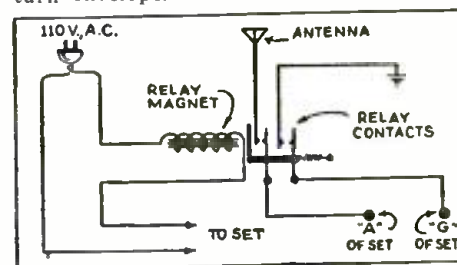Our Information Bureau will gladly supply manufacturers' names and addresses of any items mentioned in *Short Wave Craft*. Please enclose stamped return envelope.



Hook-up of the new automatic antenna device, showing relay magnet connection and armature contacts.

Names and addresses of manufacturers of apparatus described on this and following pages furnished upon receipt of 3-cent stamp; mention No. of article.

The HF-20 S.-W. Transmitter

By Guy Stokely, E.E.



Note the neat and business-like appearance of the HF20 S-W Transmitter designed by Mr. Stokely, who is well-known to the short-wave fraternity. (No. 530)

● THE latest contribution of Eilen Radio Laboratories to the transmitting amateur is model HF-20 amateur band short-wave transmitter. Using the popular and low-priced 2A5 tubes, crystal control, and of an unusually lost cost and efficient design, this makes an ideal low-powered radio telegraph and phone transmitter for the beginner as well as the old timer. It is capable of supplying 20 watts of crystal-controlled power on the 40-80-160 meter bands and a good 15 watts of power on the 20 meter band. For the phone enthusiast, model HV-500 power supply and model M-10 modulator is available, allowing a carrier of 15 watts to be obtained. Referring to the electrical circuit diagram we find the 2A5 tube to be used as an R.F. pentode crystal controlled oscillator, the output of which is capacity coupled to the grids of a type 2A5 power amplifier. Crystal control is used in preference to the older self-excited circuits, due to the high order of frequency stability obtainable (a factor of prime importance in the present day crowded amateur bands). Shunt feed is used in the plate circuit of

the oscillator in order to simplify mechanical construction. The screen-grid is operated at a positive potential of approximately 200 volts and is adequately bypassed by the condenser C1. The plate, fed through the RF choke is operated at about 400 volts. It is essential that a good R.F. choke be used in order to avoid R.F. leakage back into the power supply and the resulting neutralizing difficulties. The oscillator plate tuning circuit is located in the grid circuit of the 2A5 amplifier and results in an exceptionally efficient energy transfer. Grid leak bias is used on the R. F. stage and shunt feed is used in its plate circuit for the same reasons as previously outlined. The antenna coupling coil L3 is wound upon the same form as L2, due attention being paid to proper spacing for maximum energy transfer in designing the coils. The use of plug-in crystals and coils throughout, allows full output to be obtained on any of the amateur bands in common use.


In the lower section of the circuit diagram is shown the power supply. Full-wave rectification using the popular 83 mercury vapor tube is used. A two-section filter with swinging choke input is used and insures absolutely pure D.C. carrier free from

all traces of A.C. hum. A tapped voltage divider allows the proper voltages for the screens and oscillator to be obtained.

The modulator consists of a type 53 tube with both of its grids tied together, and both plates tied together. It operates as a class A driver for the class "B" modulator, also using a type 53 tube. When used with a single button microphone this speech amplifier is ample for exciting the class "B" modulator to its full 10 watts output.


R1—50,000 ohms. R2—200 ohms. R3—50,000 ohms. R4—50,000 ohms, 25 watt divider. C1—C8—C9—.0005 mf. mica. C2—C4—C6—.0001 mf. mica. C3—C7—.00014 mf. variable. C5—.00005 mf. neut. cond.

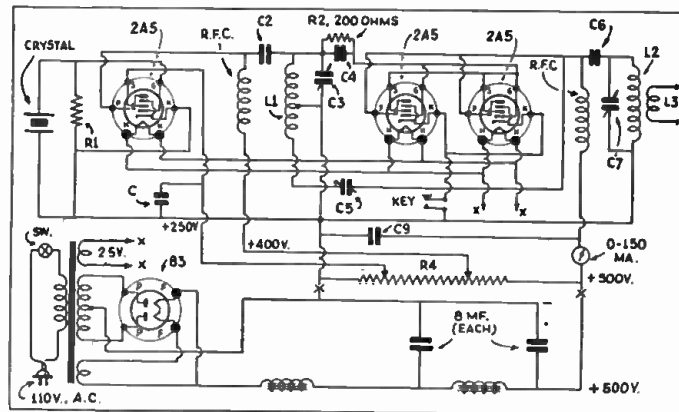This article has been prepared from data supplied by courtesy of Eilen Radio Laboratories.




Wiring diagram of the HF20 S-W transmitter which is capable of supplying 20 watts power on the 40-80-160 meter bands, and 15 watts on the 20-meter band.

New Doublet for All-Wave Reception

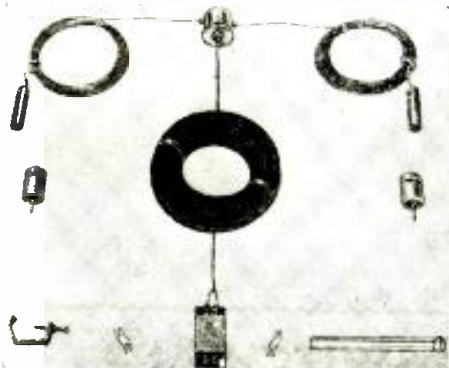

New all-wave R.C.A. doublet antenna "kit," which comes already to install with all joints made for insulators attached. (No. 531).

● THE accompanying diagram and photo show the new R.K. 40 antenna which has been designed for all-wave reception. It comes complete, ready to install and no assembly of parts is required for its installation. It is merely necessary to attach each end of the doublet to circuits such as poles, trees, etc., and make a simple connection to the receiver. The cost of this antenna is very nominal and it should markedly improve reception on any all-wave receiver, which is not already connected to a doublet of good design. The transmission line designed for this antenna is designed to efficiently convey the electric wave energy picked up by the doublet antenna proper, down to the receiver. The receiver coupling unit or transformer matches the impedance of the transmission line to the input receiver circuits. This greatly simplified antenna system provides adequate coverage on both short and long-wave broadcast bands, with a minimum of installation work. The trans-

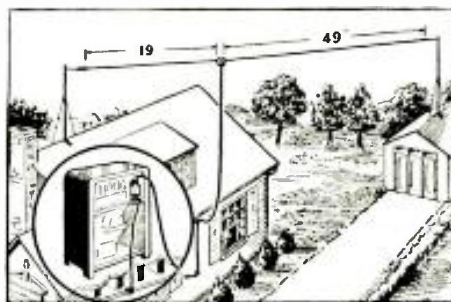


Typical installation of new R.C.A. all-wave doublet antenna.

mission line is of the transposed or twisted type. The antenna comes complete with strain insulators attached and the transmission line cable is 75 feet long. Any one can install an antenna of this type in a very short time. This article has been prepared from data supplied by the courtesy of the R.C.A. Manufacturing Company.

"Mystic-Eye" Tuning Unit

● EVERY one today is looking for some easier and more accurate way of tuning in stations on their receiver. One of the newest and nominally-priced tuning or resonance indicators is the "Mystic Eye" tuning unit here illustrated. It can be mounted on practically any receiver and it resembles a modified cathode-ray tube which causes a variable band of light to appear on the target at the end of the tube, the band widening out as the station is tuned farther away from the resonance point, and narrowing down to a thin line, as the station is tuned into perfect resonance.

Your old set can now be brought up-to-date by adding one of these simple tuning units. Any one at all handy with tools can install the device, and it is very simple to connect, full instructions accompanying the tube and the circuit diagram which comes with it. All you have to do is to drill a small hole in the panel of the cabinet, mount the tuning unit and escutcheon plate, connect the colored wires according to the diagram accompanying the device and your set is right up-to-date, so far as a tuning indicator is concerned. This article has been prepared from data supplied

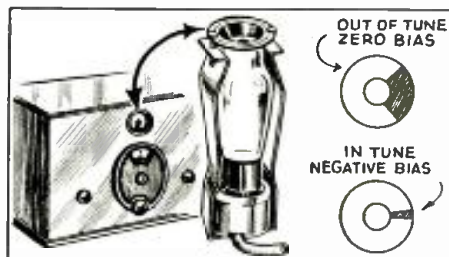

The "Mystic-Eye" tuning unit adaptable to any type receiver. (No. 532.) by the courtesy of the Empire Radio Corp.

NEW APPARATUS FOR THE "HAM"



● TWO new tubes have recently been introduced. One is the type 830B which can be used as a modulator, R.F. amplifier or oscillator.

This tube has a rated plate dissipation of 60 watts. The outstanding feature is that the plate connection is brought out through a cap at the top of the bulb.

Another new tube which should interest those amateurs working on the ultra-high frequency is the 834. This tube can be operated on frequencies as high as 350 megas., 100 megas. at rated input, and above this frequency a slight reduction in input power is necessary.

For the benefit of those interested in these tubes we are re-printing data obtained from the R.C.A. Manufacturing Co. covering the characteristics and operating conditions of both these tubes. Watch for articles in the coming issues of *Short Wave Craft* in which these tubes will be employed.

830 B TENTATIVE CHARACTERISTICS

Filament Voltage (A.C. or D.C.)—10 volts.
 Filament Current—2 amperes.
 Amplification Factor—25.
 Direct Interelectrode Capacitances (Approx.):
 Grid-plate—11 mmf.; Grid-filament—5 mmf.;
 Plate-filament—1.8 mmf.

Two New Tubes the "Ham" Will Like

Bulb—T-16.
 Cap—Small Metal.
 Base—Medium 4-1/2" in Bayonet.

MAXIMUM RATINGS AND TYPICAL OPERATING CONDITIONS

As A-F Power Amplifier and Modulator—Class B.
 D.C. Plate Voltage—1000 max. Volts.
 Max-Signal D.C. Plate Current—150 max. Milliamperes.
 Max-Signal Plate Input—150 max. Watts.
 Plate Dissipation—60 max. Watts.

Typical Operation—2 Tubes:

Unless otherwise specified, values are for 2 tubes
 Filament Voltage (A.C.)—10—10 Volts.
 D.C. Plate Voltage—800—1000 Volts.
 D.C. Grid Voltage (Approx.)—-27—-35 Volts.
 Peak A-F Grid-to-Grid Voltage (Approx.)—250—270—Volts.
 Zero-Sig. D.C. Plate Current—20—20 Milliamperes.
 Max-Sig. D.C. Plate Current—280—280 Milliamperes.
 Load Resistance (per tube)—1500—1900 ohms.
 Effective Load Res. (Plate-to-plate)—6000—7600 Ohms.
 Max-Sig. Driving Power (Approx.)—5—6 Watts.
 Max-Sig. Power Output (Approx.) 135—175 Watts.

As R-F Power Amplifier—Class B Telephony

Carrier conditions per tube for use with a max. modulation fact. of 1.0

D.C. Plate Voltage—1000 max. Volts.
 D.C. Plate Current—100 max. Milliamperes.
 Plate Input—30 max. Watts.
 Plate Dissipation—60 max. Watts.

Typical Operation:

Filament Voltage (A.C.)—10—10 Volts.
 D.C. Plate Voltage—800—1000 Volts.
 D.C. Grid Voltage (Approx.)—-27—-35 Volts.
 Peak R-F Grid Voltage (Approx.)—85—85 Volts.

D.C. Plate Current—95—85 Milliamperes.
 D.C. Grid Current (Approx.)—7—6 Milliamperes.
 Driving Power (Approx.)—9—6—Watts.
 Power Output (Approx.) 23—26 Watts.

As Plate-Modulated R.F. Power Amplifier—Class C Telephony

Carrier conditions per tube for use with max. modulation fact. of 1.0

D.C. Plate Voltage—800 max. Volts.
 D.C. Grid Voltage—-300 max. Volts.
 D.C. Plate Current—100 max. Milliamperes.
 D.C. Grid Current—30 max. Milliamperes.
 Plate Input—80 max. Milliamperes.
 Plate Dissipation—40 max. Watts.

Typical Operation:

Filament Voltage (A.C.)—10—10 Volts.
 D.C. Plate Voltage—600—800 Volts.
 D.C. Grid Voltage (Approx.)—-140—-150 Volts.
 Peak R.F. Grid Voltage (Approx.)—255—265 Volts.
 D.C. Plate Current—95—95—Milliamperes.
 D.C. Grid Current (Approx.)—30—20 Milliamperes.
 Driving Power (Approx.)—7—5 Watts.
 Power Output (Approx.)—38—50 Watts.

As R.F. Power Amplifier and Oscillator—Class C Telegraphy

Key-down conditions per tube without modulation

D.C. Plate Voltage—1000 max. Volts.
 D.C. Grid Voltage—-300 max. Volts.
 (Continued on page 57)



3-Tube Set Equals Five

By William Green



Front view of the new "Fulltone V" A.C.-D.C. receiver, in which three tubes do the work of five. (No. 528.)

operate, easy to build, and low in cost.

It's already beginning to sound like a description of the perfect receiver, but these are only the more important essentials. Here are some additional features in our receiver: It must be hum-free, have continuous band-spread, easy reading dial, good shielding and be portable, trouble free and fool-proof.

The circuit diagram shown on this page is that of the final job built by the author and incorporating every feature mentioned above. A full five-tube circuit is used by means of dual-purpose tubes—6D6, 6F7, 12A7, providing R.F., detector, two audio stages and rectifier. The 6D6 is the "high-gain" R.F. tube, through which the antenna is coupled to the detector. This is inductively coupled by means of a three-winding coil to the pentode section of the 6F7 tube.

The detector is remarkably smooth operating. This has been accomplished by the proper use of sufficient by-pass condensers, and control of regeneration by a potentiometer varying the screen voltage. This same tube has a triode section, which is utilized as the first audio stage. Its output couples into the next duplex tube, the 12A7. The pentode section of the 12A7 is the audio output tube, while the diode section serves as the power supply rectifier. A 350 ohm line resistor, filter choke, and a 12,12,5,5, mf.


This photo shows a view of the chassis and also the metal cabinet for the "Fulltone V."



electrolytic condenser complete the power supply. A good filter circuit makes reception free of all hum and tunable hum on all frequencies. The coil ranges are:

Color	Range in Meters	Range in Kc.
Blue	9 to 15	20 to 33 mc.
Green	15 to 37	8100 to 20 mc.
Yellow	37 to 92	3250 to 8100 mc.
Red	92 to 205	1450 to 3250 mc.
Brown	192 to 425	700 to 1550 mc.
Black	300 to 625	480 to 1000 mc.

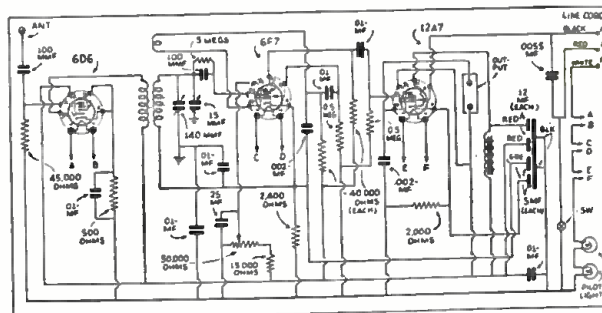This article has been prepared from data supplied by courtesy of Harrison Radio Co.



Wiring diagram of the latest Harrison "Fulltone V."

● WHAT does the amateur and short wave fan really want in a short wave receiver?

The following brief outline indicates what the great majority want, as compiled from numerous suggestions. The receiver must have as few tubes as is consistent with good reception and operation. This eliminates the tiny one-tube "midget," as well as the enormous multi-tube monster. It must be completely self-contained as well as light and compact. The day of the external amplifier, power supply and speaker are definitely over. Universal operation on either A.C. or D.C. is important. The receiver must really bring in those distant "elusive" foreign stations with ease and volume, and in addition must be sufficiently selective for local reception. The speaker should operate with good volume on all stations, with good tone and clarity. A high signal-to-noise ratio is essential. Above all it must be simple to

Names and addresses of manufacturers of apparatus described on this and following pages furnished upon receipt of 3-cent stamp; mention No. of article.

THE RADIO AMATEUR

Conducted by Geo. W. Stuart

Radio Amateur Course





9th lesson—Many points are given here for the selection of tubes used in low-power exciter stages

● THE choice of tubes for the oscillator, buffer, or multiplier stages of a transmitter is always quite a problem to the amateur. Also the circuits to use are numerous, especially with the recent tube developments. In Fig. 1, we have the conventional triode crystal oscillator circuit; with this tube the crystal is used in the grid circuit and oscillation is brought about when the plate circuit is tuned to approximately the crystal frequency. This circuit was the first to be used among amateurs when crystals were still a luxury. Either series or parallel plate feed may be used in this circuit. Fig. 1 shows the *series* method, while Fig. 2 is the same set-up but with *parallel* feed. Number 2 allows the rotor plate tuning condenser to be independent of the high voltage, and it can be mounted on a metal panel or chassis with no insulation.





The next popular crystal circuit was that using the 47 pentode; this was a considerable improvement over the former circuits. In Fig. 3, we find the conventional 47 pentode, which proved to be an excellent crystal controlled oscillator and allowed less R.F. crystal current; thus lightening the load on the crystal. In Fig. 4 we have the same circuit except that the heater-cathode type tube is used; such as the 59, 2A5, etc. There is little advantage in this circuit over the 47 aside from the fact that the heater is separate and no filament by-pass condensers are necessary.

Tritet Oscillator


Later developments in pentode circuits brought forth the well-known Tritet oscillator is shown; this is a modification of the Dow oscillator. In this circuit we can multiply the crystal frequency in the plate tuned circuit, independent of the crystal oscillatory circuit. However, the plate circuit can not be tuned to the crystal frequency because of insufficient internal shielding in the tube. This circuit is shown in Fig. 5, and a number of different type of tubes may be used as is indicated. A more flexible adaption of this same circuit is shown in Fig. 6 where the screen grid pentode tubes are used, the shielding in these tubes is sufficient to allow plate circuit to be tuned to the crystal frequency or an harmonic of it. Here the power pentodes such as the 802, RK23, etc., may be used, or the pentode receiving type tubes where only low-power

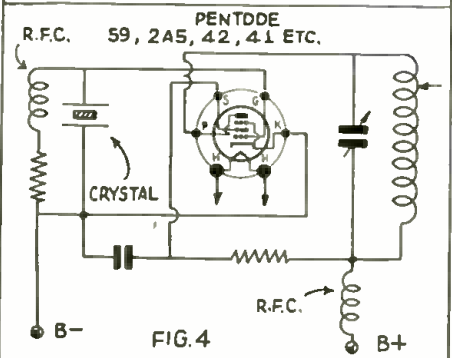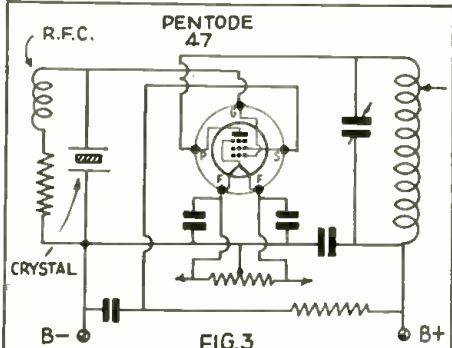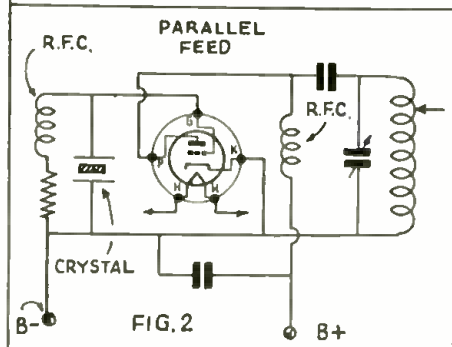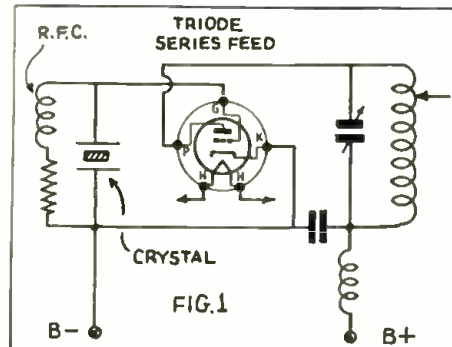

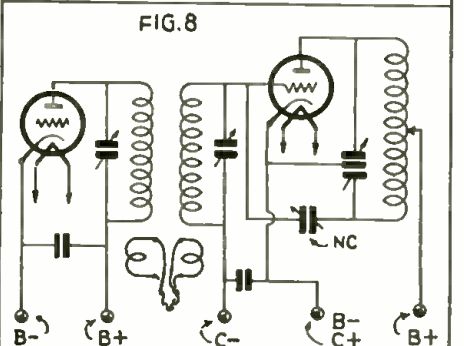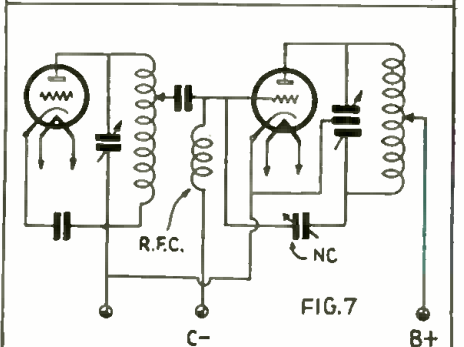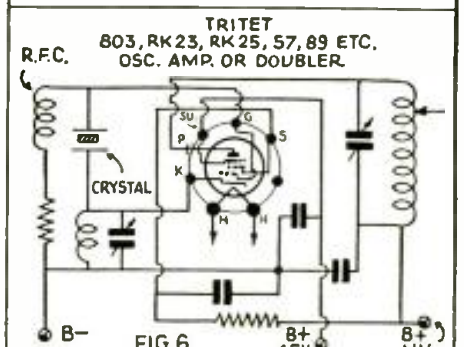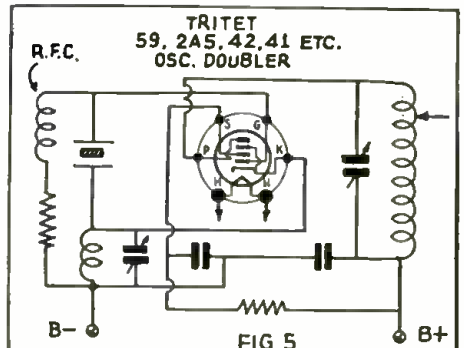Above we have the triode and pentode crystal oscillator, using conventional circuits.



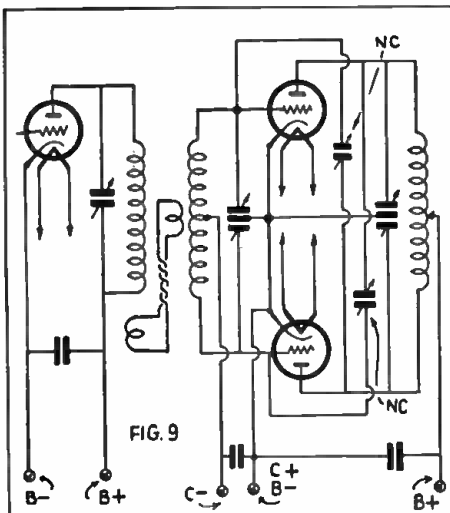Here we have the oscillator—multiplier and also neutralized amplifier and doubler.



OSC-MULTIPLIER

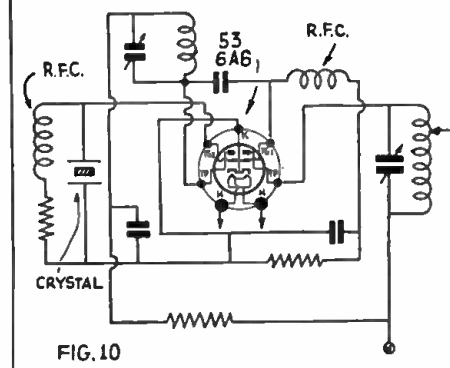


FIG. 10

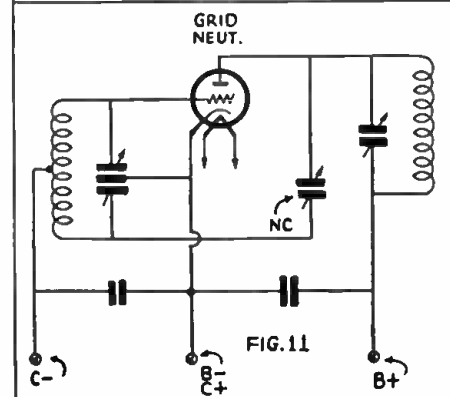


FIG. 11

Many suggestions are given in this lesson regarding the type of tubes which may be used in the low-power stages of a transmitter, where "frequency multiplication" is necessary.

stages are required. Where a number of multiplications are necessary, the receiving type tubes, such as the 57 and 58, are recommended, because of their low cost, and very respectable power "out-put." In the receiving type tubes, though there seems to be little advantage in applying a positive potential to the suppressor, while in the power-type tubes this does increase the out-put appreciably.

Neutralization

So much for the oscillator circuits. We now consider Fig. 7 in which an amplifier tube is added to the oscillator. Here we have a triode neutralized amplifier when operating on a crystal frequency. For a frequency multiplication neutralization is not absolutely necessary, although the neutralizing condenser and the tapped coil arrangement should be employed, because a certain amount of regeneration may be obtained by the proper adjustment of this condenser N.C. and thus increase the harmonic out-put considerably. Those who have not tried this method of frequency doubling will be well rewarded with a considerable increase in "out-put," through the use of the neutralizing condenser, which then becomes merely a feedback control. The coupling between the two stages in this instance is capacitive.

Link Coupling

In Fig. 8 we have both the grid and plate circuits of the amplifier tuned and link coupled to the preceding stage. This link coupling may consist of one or two turns connected with a twisted pair of insulated wires coupled to both tank circuits. This is a recommended method where the extra coil and condenser can be incorporated conveniently in the set-up, although where a great many multiple stages are used, as pointed out (Continued on page 46)

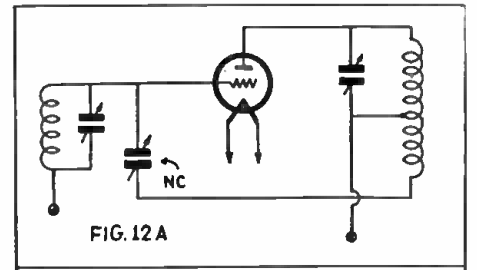


FIG. 12A

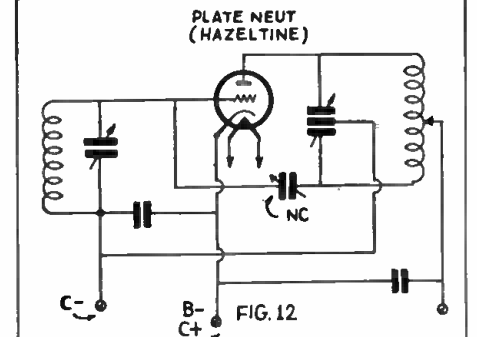


FIG. 12

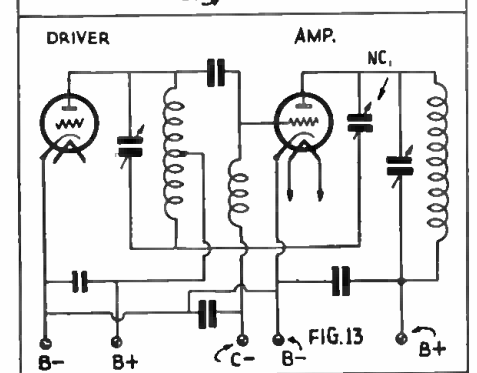


FIG. 13

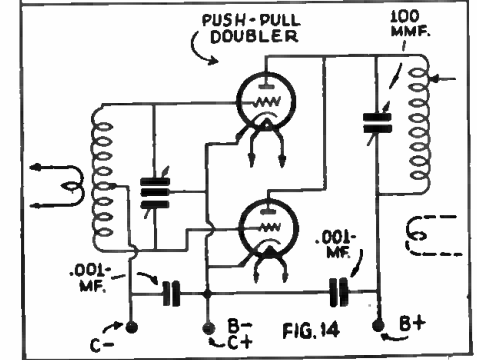


FIG. 14

Here we have various types of multiplier and buffer stages.

Different methods of neutralizing and also push-pull doubler.

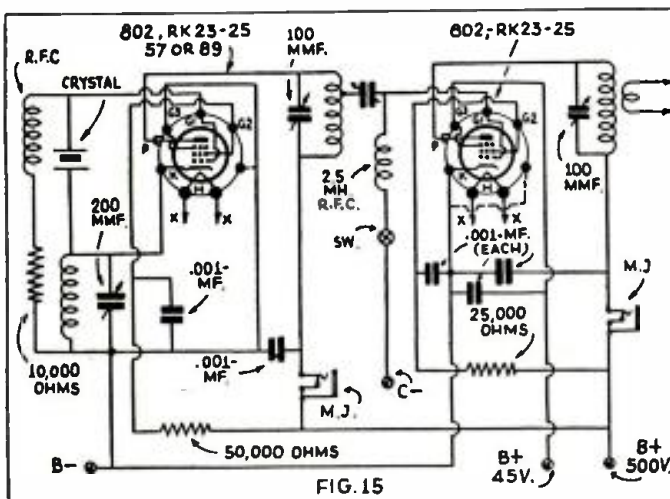


FIG. 15


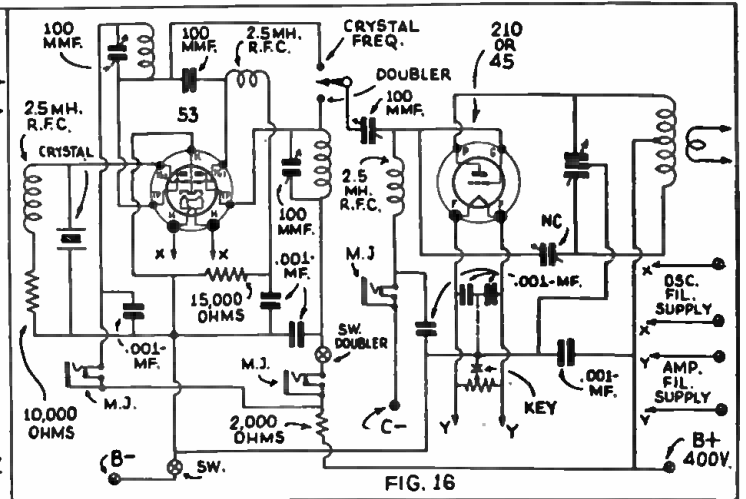


FIG. 16

The dual pentode exciter unit, which will operate on any one of three bands, with one crystal and drive the average medium-power amplifier.

Above: The 53 twin triode is used as an oscillator and multiplier. This will also excite the average medium-power "final" amplifier.

A Long-Lines Oscillator and Modulator


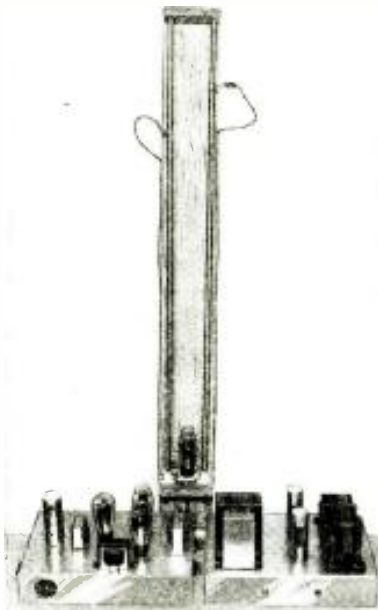


● The long-lines oscillator introduced by *Short Wave Craft* in the latter part of 1934, is now available in commercial form. In this particular one, which is shown in the photograph, a number of different tubes may be used. For instance, if the Ham wishes to start out with a relatively low power a pair of 45's may be employed as oscillators, while for higher power a pair of 210's or 801's with from five to six hundred volts on the plates. The one-half inch copper tubes which form the long-lines circuit are four feet long, and at the high R.F. potential ends are mounted on small stand-off insulators. A wooden frame is also used to increase the mechanical rigidity. This solves the problem of supporting the rather awkward four foot metal tubes. Clips to these vertical rods are in the form of copper ground-clamps which wrap around the copper tubing and make a real low-resistance connection. For changing frequency "shorting bars" are used; these bars either increase or de-

Photo at the left shows the new Eagle "Long-Lines" oscillator with modulator and power supply. Diagram at right shows connections. (No. 533.)

crease the effective length of the circuits and thus decrease or increase the frequency. As a companion unit to this oscillator, there is available a modulator which employs a pair of 46's in class B in the output stage. As a driver a single 46 connected as a triode is used. For amplification into this circuit, a 57 is employed in a triode connection. There is sufficient gain in this circuit for the av-

(Continued on page 61)

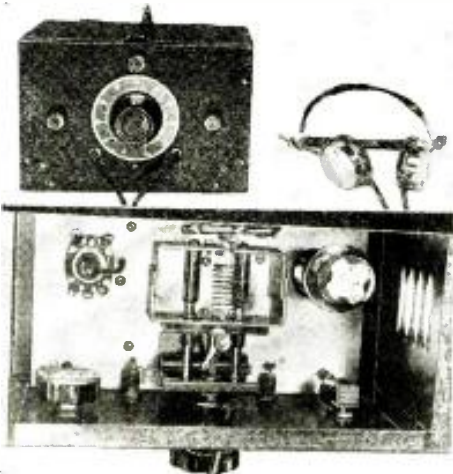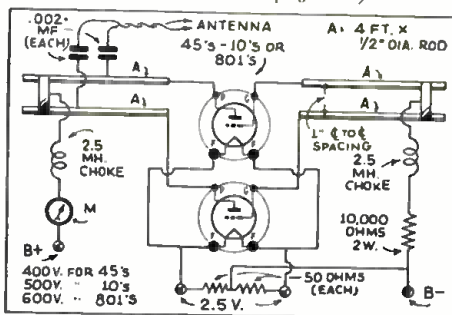

Photos above show front and top views of the new constant "High-Q" 2.5 to 10-meter receiver. (No. 534.)

Constant Hi-"Q" 2.5 to 10 Meter Set

By A. G. Heller

should be as constant as possible over the entire tuning range, with a given tuning capacity.

This novel unit is so constructed that for any rotation of the tuning shaft the condenser plates engage or disengage on a sliding principle. Simultaneously with this action, the tuning coil which is mounted as shown in the illustration, expands or contracts (depending upon whether the capacity is increased or decreased) and consequently the coil undergoes a change in inductance which is related to the change made in capacity and frequency. At the same time the effective distributed capacity (which is a potent figure in high frequency work) is varied inversely with the frequency. Thus we have in effect a tuning coil, and condenser combination whose "Q" factor remains practically constant as the condenser and frequency range is varied. Two separate coils are employed for the 10.5 and 2 1/2 to 1 1/2 meter ranges. Each is of space-wound construction, so that even the normal distributed capacity of each is at a minimum. The 5 and 2 1/2 to 1 1/2 meter coil is of edge-wise wound ribbon wire, in accordance

with theoretical and practical engineering rules which govern the design of such coils. The insulation material employed consists of Vietron in all important positions. This article has been prepared from data supplied by courtesy of Insuline Corp. of America.

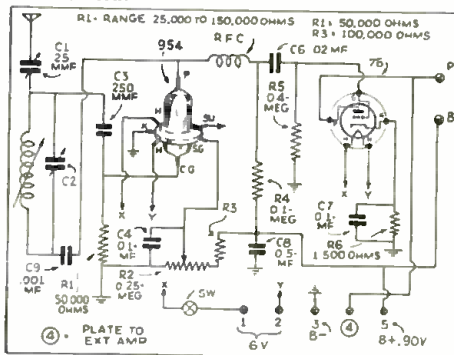


Diagram showing connections of the simple parts used in the constant "High-Q" receiver.

● ONE of the first essentials for successful short-wave receiver design, or for that matter any type of receiver, is the use of an efficient coil for the tuned circuit. The primary requisite for this unit is a high "Q" factor, and this factor

Noise Silencer

● THE famous noise suppressor recently introduced by Jim Lamb of Q.S.T. is now commercially available. The unit shown in the photograph can be used with any sensitive superheterodyne receiver and is very simple to attach to your present set.

The noise silencer is furnished with an



A nominally-priced "noise silencer" now available on the market. (No. 535).

adapter which is plugged into the last I.F. amplifier tube socket of the receiver. The very simple manner in which this can be attached to your receiver permits even the most inexperienced short-wave "Fan" to avail himself of the excellent qualities of the instrument; no technical knowledge is necessary. The noise silencer measures 7 1/2 x 5 1/2 x 3 inches and no external power-supply is necessary. An A.C.-D.C. heater circuit arrangement is employed, which permits the tubes to be run directly from the 110-volt line. Repeated tests have proven that this silencer will overcome the difficulties experienced by a great majority of the noises picked up on the short-wave bands. By means of a manual control a pre-adjustment is made which limits the maximum strength of the interfering noise. In other words, the average noise will never exceed the strength of the desired signal.


This article prepared from data supplied by courtesy of United Radio and Tel. Co.

5-Meter "Long-Lines" Xmitter

By C. A. Wyeth

● THE great popularity of the so-called "long lines" 5-meter oscillator presented

in *Short Wave Craft* one and one-half years ago, has induced several manufacturers to market them. The oscillator shown in the photo is designed to operate with various types of tubes, such as the 45's, 10's, or 801's. The vertical bars are chromeplated and the various fittings are finished in jet black. Needless to say, this presents an extremely pleasing appearance. A number of other features have been incorporated in this instrument, such as specially designed, "shorting" clips, which can be slid up and down the vertical tubes, and also for the antenna connections. Each of these are provided with insulated handles, permitting adjustment of the transmitter to be made. (Continued on page 62)

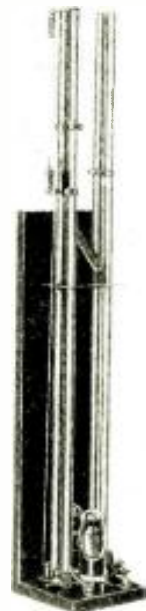

Efficiently built and handsomely finished "Long-Lines" Oscillator. (No. 536.)



Short-Wave Stations of the World

Complete List of Broadcast and Telephone Stations

We present herewith a revised list of the short-wave broadcasting, experimental and commercial radiophone stations of the world. This is arranged by frequency, but the wavelength figures are also given for the benefit of readers who are more accustomed to working with "meters." All the stations in this list use tele-

phone transmission of some kind and can be identified by the average listener. Note: Stations marked with a star ★ are the most active and easily heard stations and transmit at fairly regular times. Please write to us about any new stations or other important data that you learn through announcements over the air

or correspondence with the stations themselves. A post card will be sufficient. We will safely return to you any verifications that you send in to us. Communications of this kind are a big help. Stations are classified as follows: C—Commercial phone. B—Broadcast service. X—Experimental transmissions.

Around-the-Clock Listening Guide

Although short-wave reception is notorious for its irregularity and seeming inconsistency (wherein lies its greatest appeal to the sporting listener), it is a good idea to follow a general schedule as far as wavelength in relation to the time of the day is concerned. The observ-

ance of these simple rules will save time. From daybreak till 3 p.m., and particularly during bright daylight, listen between 13 and 19 meters (21540 to 15800 kc.). To the east of the listener, from about 1 p.m.-8 p.m., the 25-35 meter will be found very pro-

ductive. To the west of the listener this same band is generally found best from about 8 p.m. until 9 a.m. (After dark, results above 35 meters are usually much better than during daylight.) These general rules hold for any location in the Northern Hemisphere.

Short-Wave Broadcasting, Experimental and Commercial Radiophone Stations

NOTE: To convert kc. to megacycles (mc.) shift decimal point 3 places to left: Thus, read 21540 kc. as 21.540 mc.

21540 kc. W8XK -B- 13.93 meters WESTINGHOUSE ELECTRIC PITTSBURGH, PA. 7-9 a.m.; relays KDKA	19355 kc. FTM -C- 15.50 meters ST. ASSISE, FRANCE Calls Argentina, mornings	18115 kc. LSY3 -C- 16.56 meters MONTE GRANDE, ARGENTINA Tests irregularly	16270 kc. WOG -C- 18.44 meters OCEAN GATE, N. J. Calls England, mornings and early afternoon	15330kc.★W2XAD -B- 19.56 meters GENERAL ELECTRIC CO. SCHENECTADY, N. Y. Relays WGY 10 a.m.-2 p.m.
21530 kc. ★GSJ -B- 13.93 meters DAVENTRY B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 6-8:45 a.m.	19345 kc. PMA -B.C- 15.51 meters BANDOENG, JAVA Calls Holland early a.m. Broadcasts Tues., Thur., Sat., 10:00-10:30 a.m. Irregular	18040 kc. GAB -C- 16.63 meters RUGBY ENGLAND Calls Canada, morn. and early aftn.	16240 kc. KTO -C- 18.47 meters MANILLA, P. I. Calls Cal., Tokio and ships 8-11:30 a.m.	15310 kc. GSP -B- 19.6 meters DAVENTRY B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND Irregular
21520 kc. W2XE -B- 13.94 meters ATLANTIC BROADCASTING CORP. 485 Madison Ave., N.Y.C. Relays WABC 7:30-11 a.m.	19220 kc. WKF -C- 15.60 meters LAWRENCEVILLE, N. J. Calls England, daytime	17810 kc. PCV -C- 16.84 meters KOOTWIJK, HOLLAND Calls Java, 6-9 a. m.	16233 kc. FZR3 -C- 18.48 meters SAIGON, INDO-CHINA Calls Paris and Pacific Isles	15290 kc. LRU -B- 19.62 meters "EL MUNDO" BUENOS AIRES, ARGEN- TINA, S. A. Testing 6-7:45 and 11-11:45 p.m. Soon on regular daily schedule.
21420 kc. WKK -C- 14.01 meters A. T. & T. CO. LAWRENCEVILLE, N. J. Calls Argentina, Brazil and Peru, daytime	19160 kc. GAP -C- 15.68 meters RUGBY ENGLAND Calls Australia, early a.m.	17790 kc. ★GSG -B- 16.86 meters DAVENTRY B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 6-8:45 a.m., 9 a.m.-12 n.	15880 kc. FTK -C- 18.90 meters ST. ASSISE, FRANCE Phones Saigón, mornings	15280 kc. DJQ -B- 19.63 meters BROADCASTING HOUSE BERLIN, GERMANY 12:30-3, 8:05-11 a.m.
21080 kc. PSA -C- 14.23 meters RIO DE JANEIRO, BRAZIL Works WKK Daytime	18970 kc. GAQ -C- 15.91 meters RUGBY ENGLAND Calls S. Africa, mornings	17780 kc ★W3XAL -B- 16.87 meters NATIONAL BROAD. CO. BOUND BROOK, N. J. Relays WJZ, Daily exc. Sun. 9 a.m.-1 p.m.	15810 kc. LSL -C- 18.98 meters HURLINGHAM, ARGENTINA Calls Brazil and Europe, daytime	15270 kc. ★W2XE -B- 19.65 meters ATLANTIC BROADCASTING CORP. 485 Madison Ave., N.Y.C. Relays WABC daily, 1-6 p.m.
21060 kc. WKA -C- 14.25 meters LAWRENCEVILLE, N. J. Calls England noon	18890 kc. ZSS -C- 15.88 meters KLIPHEUVEL, S. AFRICA Works Rugby 6:30 a.m.-12 n	17775 kc. PHI -B- 16.88 meters HUIZEN, HOLLAND Used irregularly	15760 kc. JYT -X- 19.04 meters KEMIKWA-CHO, CHIBA- KEN, JAPAN Irregular in late afternoon and early morning	15260 kc. GSI -B- 19.66 meters DAVENTRY B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 12:15-2:15 p.m.
21020 kc. LSN6 -C- 14.27 meters HURLINGHAM, ARG. Calls N. Y. C. 6 a. m.-5 p. m.	18830 kc. PLE -C- 15.93 meters BANDOENG, JAVA Calls Holland, early a. m.	17760 kc. ★W2XE -B- 16.89 meters ATLANTIC BROADCASTING CORP. 485 Madison Ave., N.Y.C. Relays WABC 11 a.m.-1 p.m.	15660 kc. JVE -C- 19.16 meters NAZAKI, JAPAN Phones Java 3-5 a.m.	15250 kc. W1XAL -B- 19.67 meters BOSTON, MASS. Irregular, in morning
20700 kc. LSY -C- 14.48 meters MONTE GRANDE ARGENTINA Tests irregularly	18620 kc. GAU -C- 16.11 meters RUGBY ENGLAND Calls N. Y., daytime	17760 kc. DJE -B- 16.89 meters BROADCASTING HOUSE BERLIN, GERMANY 8:05-11 a.m.	15620 kc. JVF -C- 19.2 meters NAZAKI, JAPAN Phones U.S., 5 a.m. & 4 p.m.	15245 kc. ★TPA2 -B- 19.68 meters "RADIO COLONIAL" PARIS, FRANCE Service de la Radiodiffusion 98, bis, Blvd. Haussmann 6.55-11 a.m.
20380 kc. GAA -C- 14.72 meters RUGBY ENGLAND Calls Argentina, Brazil, mornings	18345 kc. FZS -C- 16.35 meters SAIGON, INDO-CHINA Phones Paris, early morning	17760 kc. IAC -C- 16.89 meters PISA, ITALY Calls ships, 6:30-7:30 a. m.	15415 kc. KWO -C- 19.46 meters DIXON, CAL. Phones Hawaii 2-7 p.m.	15220 kc. ★PCJ -B- 19.71 meters N.V. PHILIPS' RADIO EINDHOVEN, HOLLAND Tues. 3-6 a.m. Wed. 7-11 a.m.
19900 kc. LSG -C- 15.08 meters MONTE GRANDE, ARGENTINA Tests irregularly, daytime	18340 kc. WLA -C- 16.38 meters LAWRENCEVILLE, N. J. Calls England, daytime	17310 kc. W3XL -X- 17.33 meters NATIONAL BROAD. CO. BOUND BROOK, N. J. Tests irregularly	15370 kc. ★HAS3 -B- 19.52 meters BUDAPEST, HUNGARY Broadcasts Sundays, 9-10 a.m.	15210 kc. ★W8XK -B- 19.72 meters WESTINGHOUSE ELECTRIC & MFG. CO. PITTSBURGH, PA. 9 a.m.-7 p.m. Relays KDKA
19820 kc. WKN -C- 15.14 meters LAWRENCEVILLE, N. J. Calls England, daytime	18310 kc. GAS -C- 16.38 meters RUGBY ENGLAND Calls N. Y., daytime	17120 kc. WOO -C- 17.52 meters A. T. & T. CO., OCEAN GATE, N. J. Calls ships	15360 kc. DJT -X.C- 19.53 meters REICHSPOSTZENSTRALAMT. ZESEN, GERMANY Works with Africa and broad- casts 11 p.m.-1 a.m.	15200 kc. DJB -B- 19.74 meters BROADCASTING HOUSE BERLIN, GERMANY 3:50-11 a.m.
19650 kc. LSN5 -C- 15.27 meters HURLINGHAM, ARGENTINA Calls Europe, daytime	18270 kc. ETA -C- 16.42 meters CHIEF ENGINEER P. O. Box 283, ADDIS ABABA, ETHIOPIA Irregularly	17080 kc. GBC -C- 17.56 meters RUGBY ENGLAND Calls Ships	15355 kc. KWU -C- 19.53 meters DIXON, CAL. Phones Pacific Isles and Japan	
19600 kc. LSF -C- 15.31 meters MONTE GRANDE, ARGENTINA Tests irregularly, daytime	18250 kc. FTO -C- 16.45 meters ST. ASSISE, FRANCE Calls S. America, daytime	16270 kc. WLK -C- 18.44 meters LAWRENCEVILLE, N. J. Phones Arg., Braz., Peru, daytime		

(All Schedules Eastern Standard Time)

<p>15180 kc. GSO -B- 19.76 meters DAVENTRY B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 4-5:45 p.m.</p> <p>15140 kc. GSF -B- 19.82 meters DAVENTRY. B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 9 a.m.-12 n.</p> <p>15120 kc. HVJ -B- 19.85 meters VATICAN CITY ROME, ITALY 10:30 to 10:45 a.m., except Sunday Sat. 10-10:45 a.m.</p> <p>15110 kc. DJL -B.X- 19.85 meters BROADCASTING HOUSE, BERLIN, GERMANY 6:30-8 a.m.</p> <p>15090 kc. RKI -C- 19.88 meters MOSCOW, U.S.S.R. Phone Tashkent near 7 a.m. and relay RNE on Sundays Irregularly</p> <p>15070 kc. PSD -C- 19.91 meters RIO DE JANEIRO, BRAZIL Calls N.Y., Buenos Aires and Europe, daytime</p> <p>15055 kc. WNC -C- 19.92 meters HIALEAH, FLORIDA Calls Central America, daytime</p> <p>14980 kc. KAY -D- 20.03 meters MANILA, P. I. Phone Pacific Isles</p> <p>14950 kc. HJB -C- 20.07 meters BOGOTA, COL. Calls WNC, daytime</p> <p>14600 kc. JVH -B.C- 20.55 meters NAZAKI, JAPAN Phone Europe 4-8 a.m. Irregular 12 m-1 a.m. Mon. and Thurs. 4-5 p.m.</p> <p>14590 kc. WMN -C- 20.58 meters LAWRENCEVILLE, N. J. Phone England morning and afternoon</p> <p>14535 kc. HBJ -B- 20.64 meters RADIO NATIONS, GENEVA, SWITZERLAND Broadcasts Irregularly</p> <p>14530 kc. LSN -C- 20.65 meters HURLINGHAM, ARGENTINA Calls N.Y.C., afternoons</p> <p>14500 kc. LSM2 -C- 20.69 meters HURLINGHAM, ARGENTINA Calls Rio and Europe daytime</p> <p>14485 kc. TIR -C- 20.71 meters CARTAGO, COSTA RICA Phone Cen. Amer. & U.S.A. Daytime</p> <p>14485 kc. HPF -C- 20.71 meters PANAMA CITY, PAN. Phone WNC daytime</p> <p>14485 kc. TGF -C- 20.71 meters GUATEMALA CITY, QUAT Phone WNC daytime</p> <p>14485 kc. YNA -C- 20.71 meters MANAGUA, NICARAGUA Phone WNC daytime</p> <p>14470 kc. WMF -C- 20.73 meters LAWRENCEVILLE, N. J. Phone England morning and afternoon</p> <p>14460 kc. DZH -C.X- 20.75 meters REICHSPOSTZENSTRALAMT, ZEESEN, GERMANY Works on telephony and broad- casts 12 n.-2 p.m.</p> <p>14440 kc. GBW -C- 20.76 meters RUGBY, ENGLAND Calls U.S.A., afternoon</p> <p>13990 kc. GBA -C- 21.44 meters RUGBY, ENGLAND Calls Buenos Aires, late afternoon</p>	<p>13820 kc. SUZ -C- 21.71 meters ABOU ZABAL, EGYPT Works with Europe 11 a.m.- 2 p.m.</p> <p>13635 kc. SPW -B- 22 meters WARSAW, POLAND Mon., Wed., Fri. 11:30 a.m.- 12:30 p.m. Irregular at other times</p> <p>13610 kc. JYK -C- 22.04 meters KEMIKAWA-CHO, CHIBA- KEN, JAPAN Phone California till 11 p. m.</p> <p>13585 kc. GBB -C- 22.08 meters RUGBY, ENGLAND Calls Egypt & Canada, afternoons</p> <p>13415 kc. GCJ -C- 22.36 meters RUGBY, ENGLAND Calls Japan & China early morning</p> <p>13390 kc. WMA -C- 22.40 meters LAWRENCEVILLE, N. J. Phone England morning and afternoon</p> <p>13345 kc. YVC -C- 22.48 meters MARACAY, VENEZUELA Calls Hialeah daytime</p> <p>13075 kc. VPD -X- 22.94 meters SUVA, FIJI ISLANDS Daily exc. Sun. 12:30-1:30 a.m.</p> <p>12840 kc. WOO -C- 23.38 meters OCEAN GATE, N. J. Calls ships</p> <p>12825 kc. CNR -B- 23.50 meters DIRECTOR GENERAL Telegraph and Telephone Stations, Rabat, Morocco Broadcasts, Sunday, 7:30-9 a. m.</p> <p>12800 kc. IAC -C- 23.45 meters PISA, ITALY Calls Italian ships, mornings</p> <p>12780 kc. GBC -C- 23.47 meters RUGBY, ENGLAND Calls ships</p> <p>12396 kc. CT1G0 -B- 24.2 meters PAREDE, PORTUGAL Sun. 10-11:30 a.m., Tues., Thurs., Fri. 1:00-2:15 p.m.</p> <p>12290 kc. GBU -C- 24.41 meters RUGBY, ENGLAND Calls N.Y.C., afternoon</p> <p>12235 kc. TFJ -B.C- 24.52 meters REYKJAVIK, ICELAND Phone England mornings, Broadcasts Sun. 1:40-2 p.m.</p> <p>12150 kc. GBS -C- 24.69 meters RUGBY, ENGLAND Calls N.Y.C., afternoon</p> <p>12130 kc. DJS -C.X- 24.73 meters REICHSPOSTZENSTRALAMT, ZEESEN, GERMANY Works phone and broadcasts 7-9 p.m.</p> <p>12000 kc. RNE -B- 25 meters MOSCOW, U. S. S. R. Sun. 6-9, 10-11 a.m., 12:30- 6 p.m. 9-10 p.m., Wed. 6-7 a.m. Daily 12:30-6 p.m.</p> <p>11991 kc. FZS2 -C- 25.02 meters SAIGON, INDO-CHINA Phone Paris, morning</p> <p>11955 kc. ETB -C- 25.09 meters ADDIS ABABA, ETHIOPIA See 18270 kc.</p> <p>11950 kc. KKQ -X- 25.10 meters BOLINAS, CALIF. Tests, Irregularly, evenings</p> <p>11940 kc. FTA -C- 25.13 meters STE. ASSISE, FRANCE Phone CNR morning, Hurlingham, Aree., nights</p>	<p>11880 kc. TPA3 -B- 25.23 meters "RADIO COLONIAL" PARIS, FRANCE 4-5 a.m., 11:15 a.m.-6:05 p.m.</p> <p>11870 kc. W8XK -B- 25.26 meters WESTINGHOUSE ELECTRIC & MFG. CO. PITTSBURGH, PA. 5-10:30 p.m. Fri. till 12 m Relays KDKA</p> <p>11860 kc. GSE -B- 25.29 meters DAVENTRY. B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND</p> <p>11855 kc. DJP -B.X- 25.31 meters BROADCASTING HOUSE, BERLIN, GERMANY 12 n.-2 p.m.</p> <p>11830 kc. W2XE -B- 25.36 meters ATLANTIC BROADCASTING CORP. 485 MADISON AVE., N. Y. C. Relays WABC 6-10 p.m.</p> <p>11820 kc. GSN -B- 25.38 meters DAVENTRY B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 12:15-2:15 a.m.</p> <p>11810 kc. HJ4BA -B- 25.4 meters P. O. BOX 50, MEDELLIN, COLOMBIA 11:30 a.m.-1 p.m., 6:30-10:30 p.m.</p> <p>11810 kc. 2RO -B- 25.4 meters E.I.A.R., Via Montello 5 ROME ITALY 8:15-9 a.m., 9:15-11 a.m., 11:30 a.m.-12:15 p.m.</p> <p>11800 kc. CO9WR -X- 25.42 meters P. O. Box 85 SANCTI SPIRITUS, CUBA 4-8, 9-11 p.m. 9 a.m.-12 n.</p> <p>11795 kc. DJO -B.X- 25.43 meters BROADCASTING HOUSE, BERLIN, GERMANY 3-4:55 p.m.</p> <p>11790 kc. W1XAL -B- 25.45 meters BOSTON, MASS. Sun. 5-7 p.m.</p> <p>11770 kc. DJD -B- 25.49 meters BROADCASTING HOUSE, BERLIN, GERMANY 11:35 a.m.-4:35 p.m.; 4:55, 10:45 p.m.</p> <p>11750 kc. GSD -B- 25.53 meters DAVENTRY. B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND 12:15-5:45 p.m., 6-8, 10-11 p.m.</p> <p>11730 kc. PHI -B- 25.57 meters HUIZEN, HOLLAND Daily exc. Tues. and Wed. 8-10 a.m., Sat. and Sun. 8-11 a.m.</p> <p>11720 kc. CJRX -B- 25.6 meters WINNIPEG, CANADA Daily, 8 p. m.-12 m.</p> <p>11715 kc. TPA4 -B- 25.61 meters "RADIO COLONIAL" PARIS, FRANCE 8:15-9 p.m., 11 p.m.-1 a. m.</p> <p>11680 kc. KIO -X- 25.68 meters KAHUKU, HAWAII Tests in the evening</p> <p>11560 kc. VIZ3 -X- 25.95 meters AMALGAMATED WIRELESS OF AUSTRALASIA FISKVILLE, AUSTRALIA Calls Canada evening and early a.m.</p> <p>11413 kc. CJA4 -C- 26.28 meters DRUMMONDVILLE, QUE., CAN. Tests with Australia Irregularly in evening</p>	<p>11200 kc. XBJQ -X- 26.79 meters BOX 2825, MEXICO CITY, MEX. Irregular</p> <p>11050 kc. ZLT4 -C- 27.15 meters WELLINGTON, N. ZEALAND Phone Australia and England early a.m. Also broadcasts Ir- regularly on Sunday, 9-10 a.m.</p> <p>11000 kc. PLP -B.C- 27.27 meters BANDOEANG, JAVA Relays NIROM programs 5:30 -10 a.m. Irregular on Sundays</p> <p>10770 kc. GBP -C- 27.85 meters RUGBY, ENGLAND Calls Sydney, Austral. early a. m.</p> <p>10740 kc. JVM -B.C- 27.93 meters NAZAKI, JAPAN Tues. and Fri. 2-3 p.m.</p> <p>10675 kc. WNB -C- 28.1 meters LAWRENCEVILLE, N. J. Calls Bermuda, daytime</p> <p>10670 kc. CEC -C- 28.12 meters SANTIAGO, CHILE Broadcasts Thurs., Sun, 8:30-9 p.m., Daily 7-7:15 p.m.</p> <p>10660 kc. JVN -B.C- 28.14 meters NAZAKI, JAPAN Phone Europe 3-8 a.m. Mon. and Thurs. 4-5 p.m. Daily 4-8 a.m.</p> <p>10550 kc. WOK -C- 28.44 meters LAWRENCEVILLE, N. J. Phone Arge., Braz., Peru, nights</p> <p>10520 kc. VLK -C- 28.51 meters SYDNEY, AUSTRALIA Calls Rugby, early a. m.</p> <p>10430 kc. YBG -C- 28.78 meters MEDAN, SUMATRA 5:30-6:30 a. m., 7:30-8:30 p. m.</p> <p>10420 kc. XGW -C- 28.79 meters SHANGHAI, CHINA Calls Manila and England, 8-9 a. m. and California late evening</p> <p>10410 kc. PDK -C- 28.80 meters KOOTWIJK, HOLLAND Calls Java 7:30-9:40 a. m.</p> <p>10410 kc. KES -X- 28.80 meters BOLINAS, CALIF. Tests evenings</p> <p>10350 kc. LSX -C- 28.98 meters MONTE GRANDE, ARGENTINA Tests Irregularly 8 p.m.-12 mid- night.</p> <p>10330 kc. IRK -B.C- 29.04 meters RUYSELEDE, BELGIUM Broadcasts 2:30-4 p.m.</p> <p>10300 kc. LSL2 -C- 29.13 meters HURLINGHAM, ARGENTINA Calls Europe, evenings</p> <p>10290 kc. DZC -X- 29.16 meters KONIGSWUSTERHAUSEN, GERMANY Broadcasts Irregularly</p> <p>10260 kc. PMN -B.C- 29.74 meters BANDOEANG, JAVA Calls Australia 5 a.m. Broadcasts Sun. 5:30-10 a.m.</p> <p>10250 kc. LSK3 -C- 29.27 meters HURLINGHAM, ARGENTINA Calls Europe and U. S., after- noon and evening</p> <p>10220 kc. PSH -C- 29.35 meters RIO DE JANEIRO, BRAZIL</p> <p>10140 kc. OPM -C- 29.59 meters LEDPOLDVILLE, BELGIAN CONGO Phone around 3 a.m. and 1- 4 p.m.</p> <p>10055 kc. ZFB -C- 29.84 meters HAMILTON, BERMUDA Phone N. Y. C. daytime</p>	<p>10055 kc. SUV -C- 29.84 meters ABOU ZABAL, EGYPT Works with Europe 1-6 p.m.</p> <p>10042 kc. DZB -C- 29.87 meters ZEESEN, GERMANY Works with Central America and broadcasts 2-4 p.m.</p> <p>9950 kc. GCU -C- 30.15 meters RUGBY, ENGLAND Calls N.Y.C., evening</p> <p>9890 kc. LSN -C- 30.33 meters HURLINGHAM, ARGENTINA Calls New York, evenings</p> <p>9870 kc. WON -C- 30.4 meters LAWRENCEVILLE, N. J. Phone England, evening</p> <p>9860 kc. EAQ -B- 30.43 meters P. O. Box 951 MADRID, SPAIN Daily 5:15-9:30 p.m.; Saturday also 12 n.-2 p.m.</p> <p>9840 kc. JYS -X- 30.49 meters KEMIKAWA-CHO, CHIBA- KEN, JAPAN Irregular, 4-7 a. m.</p> <p>9800 kc. LSE -D- 30.61 meters MONTE GRANDE, ARGENTINA Tests Irregularly</p> <p>9790 kc. GCW -D- 30.84 meters RUGBY, ENGLAND Calls N.Y.C., evening</p> <p>9760 kc. VLJ-VLZ2 -C- 30.74 meters AMALGAMATED WIRELESS OF AUSTRALIA SYDNEY, AUSTRALIA Phone Java and N. Zealand early a.m.</p> <p>9750 kc. WOF -D- 30.77 meters LAWRENCEVILLE, N. J. Phone England, evening</p> <p>9710 kc. GCA -C- 30.89 meters RUGBY, ENGLAND Calls Arge. & Brazil, evenings</p> <p>9675 kc. DZA -C- 31.01 meters ZEESEN, GERMANY Works with Africa and broad- casts 5-7 p.m.</p> <p>9635 kc. 2RO -B- 31.13 meters E.I.A.R., ROME, ITALY M., W., F., 6-7:30 p.m. Tues., Thurs., Sat. 6-7:45 p.m. Daily 1:30-5 p.m.</p> <p>9625 kc. CT1A1 -B- 31.17 meters LISBON, PORTUGAL Tues., Thurs., Sat. 4:30-7 p.m.</p> <p>9620 kc. YDB -B- 31.19 meters N.I.R.O.M., SOERABAJA, JAVA 5:30-10 a.m.</p> <p>9595 kc. HBL -B- 31.27 meters LEAGUE OF NATIONS GENEVA, SWITZERLAND Saturdays, 5:30-8:15 p. m. Mon. at 1:45 a.m.</p> <p>9595 kc. HH3W -B- 31.27 meters P. O. BOX 117, PORT-AU-PRINCE, HAITI 1-2, 7-8 p.m.</p> <p>9590 kc. HP5J -B- 31.28 meters APARTADO 867, PANAMA CITY, PANAMA 11:45 a.m.-1 p.m., 7:30-10 p.m.</p> <p>9590 kc. PCJ -B- 31.28 meters N. V. PHILIPS RADIO EINDHOVEN, HOLLAND Sun. 7:30-8:30 a.m., 1-2, 7-8 p.m.</p> <p>9590 kc. VK2ME -B- 31.28 meters AMALGAMATED WIRELESS, LTD., 47 YORK ST. SYDNEY, AUSTRALIA Sun. 1-3, 5-9, 9:30-11:30 a.m.</p> <p>9590 kc. W3XAU -B- 31.28 meters NEWTOWN SQUARE, PA. Relays WCAU Daily 12 n.-7:50 p.m. Sun. 12 n.-7 p.m.</p>
------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

(All Schedules Eastern Standard Time)

9580 kc. LRX
-B- 31.32 meters
"EL MUNDO"
BUENOS AIRES, ARGENTINA
Testing

9580 kc. GSC
-B- 31.32 meters
DAVENTRY,
B.B.C., BROADCASTING
HOUSE, LONDON, ENGLAND
4:15-5:45, 6-8, 10-11 p.m.

9580 kc. VK3LR
-B- 31.32 meters
Research Section,
Postmaster Gen'l's. Dept.,
61 Little Collins St.,
MELBOURNE, AUSTRALIA
3:15-7:30 a.m., except Sun.
also Fr. 10 p.m.-2 a.m.

9570 kc. W1XK
-B- 31.35 meters
WESTINGHOUSE ELECTRIC
& MFG. CO.
SPRINGFIELD, MASS.
Relays WBZ, 7 a.m.-1 a.m.
Sun. 8 a.m.-1 a.m.

9565 kc. VUB
-B- 31.36 meters
BOMBAY, INDIA
11 a.m.-12:30 p.m., Wed.,
Thurs., Sat.

9560 kc. DJA
-B- 31.38 meters
BROADCASTING HOUSE,
BERLIN
8.05-11 a.m., 4:55-10:45 p.m.

9540 kc. DJN
-B- 31.45 meters
BROADCASTING HOUSE
BERLIN, GERMANY
12:30-3, 3:50-11 a.m., 4:55-
10:45 p.m.

9530 kc. W2XAF
-B- 31.48 meters
GENERAL ELECTRIC CO.
SCHENECTADY, N. Y.
Relays WGY 4 p.m.-12 m.
Sat. 12 n.-12 m.

9525 kc. LKJ1
-B- 31.49 meters
JELOY, NORWAY
5-8 a.m., 11 a.m.-8 p.m.

9510 kc. VK3ME
-B- 31.55 meters
AMALGAMATED WIRELESS,
Ltd.
167 Queen St.,
MELBOURNE, AUSTRALIA
Daily exs. Sun. 4-7 a.m.

9510 kc. GSB
-B- 31.55 meters
DAVENTRY,
B.B.C., BROADCASTING
HOUSE, LONDON, ENGLAND
12:15-2:15 a.m., 12:15-5:45 p.m.
6-8 p.m.

9501 kc. PRF5
-B- 31.58 meters
RIO DE JANEIRO, BRAZIL
Irregularly 4:45-5:45 p.m.

9500 kc. HJU
-B- 31.59 meters
NATI. RAILWAYS,
BUENAVENTURA, COLOMBIA
Heard between 6 and 11:30 p.m.

9450 kc. TG1X
-B- 31.75 meters
MINISTRE DE FOMENTO
GUATEMALA CITY,
GUATEMALA
Irregularly 6-11 p.m.

9428 kc. COCH
-B- 31.8 meters
2 B ST., VEDADO,
HAVANA, CUBA
Daily 8 a.m.-7 p.m.,
Sun. 11 a.m.-12 n.,
8:30-9:30 p.m.

9415 kc. PLV
-C- 31.87 meters
BANDONG, JAVA
Phones Holland around 9:45 a.m.

9330 kc. CJA2
-C- 32.15 meters
DRUMMONDVILLE, CANADA
Phone England Irregularly

9280 kc. GCB
-C- 32.33 meters
RUGBY, ENGLAND
Calle Can. & Egypt, evening

9170 kc. WNA
-C- 32.72 meters
LAWRENCEVILLE, N. J.
Phone England, evening

9125 kc. HAT4
-B- 32.86 meters
"RADIALABOR,"
GYALI-UT, 22
BUDAPEST, HUNGARY
Sunday 6-7 p.m.

9060 kc. TFK
-C- 33.11 meters
REYKJAVIK, ICELAND
Phone London afternoons.
Broadcasts Irregularly.

9020 kc. GCS
-C- 33.28 meters
RUGBY, ENGLAND
Calle N.Y.C., evenings

9010 kc. KEJ
-C- 33.3 meters
BOLINAS, CAL.
Relays NBC & CBS
Programs in evening Irregularly

8795 kc. HKV
-B- 34.09 meters
BOGOTA, COLOMBIA
Irregular; 6:30 p.m.-12 m.

8775 kc. PNI
-C- 34.19 meters
MAKASSER, CELEBES,
N.I.
Phones Java around 4 a. m.

8760 kc. GCQ
-C- 34.25 meters
RUGBY, ENGLAND
Calle S. Africa, afternoon

8750 kc. ZCK
-B- 34.29 meters
HONGKONG, CHINA
Relays ZBW
Daily 11:30 p.m.-1:15 a.m.
Mon. and Thurs. 3-7 a.m.
Tues., Wed., Fri. 6-10 a.m.
Sat. 6-11 a.m.

8730 kc. GCI
-C- 34.36 meters
RUGBY, ENGLAND
Calle India, 8 a. m.

8680 kc. GBC
-C- 34.56 meters
RUGBY, ENGLAND
Calle ships

8665 kc. CO9JQ
-X- 34.62 meters
CAMAQUEY, CUBA
5:30-6:30, 8-9 p.m. daily
except Sat. and Sun.

8590 kc. YNVA
-B- 34.92 meters
MANAGUA, NICARAGUA
7:30-9:30 p. m.

8560 kc. WOO
-C- 35.05 meters
OCEAN GATE, N. J.
Calle ships Irregular

8400 kc. HC2AT
-B- 35.71 meters
CASSILLA 877
GUAYAQUIL, ECUADOR
8-11 p.m.

8380 kc. IAC
-C- 35.9 meters
Pisa, Italy

8220 kc. ZP10
-B- 36.4 meters
ASUNCION, PARAGUAY
7-9 p.m.

8214 kc. HCJB
-B- 36.5 meters
QUITO, ECUADOR
7-11 p.m., except Monday
Sun. 11 a.m.-12 n.; 4-10 p.m.

8190 kc. XEME
-B- 36.63 meters
CALLE 59, No. 517
MERIDA, YUCATAN
"LA VOZ DE YUCATAN desde
MERIDA
10 a.m.-12 n., 6 p.m.-12 m.

8185 kc. PSK
-C- 36.85 meters
RIO DE JANEIRO, BRAZIL
Irregularly

8036 kc. CNR
-B- 37.33 meters
RABAT, MOROCCO
Sunday, 2:30-5 p. m.

7975 kc. HC2TC
-B- 37.62 meters
QUITO, ECUADOR
Thurs., Sun. at 8 p.m.

7901 kc. LSL
-C- 37.67 meters
HURLINGHAM, ARGENTINA
Calle Brazil, night

7880 kc. JYR
-B- 38.07 meters
KEMIKAWA-CHO, CHIBA-
KEN, JAPAN
4-7:40 a. m.

7860 kc. SUX
-C- 38.17 meters
ABOU ZABAL, EGYPT
Works with Europe 4-6 p.m.

7854 kc. HC2JSB
-B- 38.2 meters
GUAYAQUIL, ECUADOR
8:15-11:15 p.m.

7830 kc. YV9RC
-B- 38.31 meters
CARACAS, VENEZUELA
7-11 p.m.

7799 kc. HBP
-B- 38.47 meters
LEAGUE OF NATIONS,
GENEVA, SWITZERLAND
5:30-6:15 p. m., Saturday

7715 kc. KEE
-C- 38.89 meters
BOLINAS, CAL.
Relays NBC & CBS
Programs in evening Irregularly

7630 kc. ZHJ
-B- 39.32 meters
PENANG, MALAYA
Daily 7-9 a.m.,
also Sat. 11 p.m.-1 A.M. (Sun.)

7620 kc. ETD
-C- 39.37 meters
ADDIS ABABA, ETHIOPIA
Sec 18270 kc.

7550 kc. TI8WS
-B- 39.74 meters
"ECOS DEL PACIFICO"
P. O. BOX 75 PUNTA
ARENAS, COSTA RICA
6 p.m.-12 m.

7510 kc. JVP
-B.-C- 39.95 meters
NAZAKI, JAPAN

7380 kc. XECR
-B- 40.65 meters
FOREIGN OFFICE,
MEXICO CITY, MEX.
Sun. 6-7 p.m.

7281 kc. HJ1ABD
-B- 41.04 meters
CARTAGENA, COLO.
Irregularly, evenings

7100 kc. HKE
-B- 42.25 meters
BOGOTA, COLO., S. A.
Tue. and Sat. 8-9 p. m.; Mon. &
Thurs. 6:30-7 p. m.

7080 kc. VP3MR
-B- 42.68 meters
GEORGETOWN, BRI. GUI-
ANA, S. A.
Sun. 7:45-10:15 a.m.
Mon. 3:45-4:45 p.m.
Tues. 4:45-6:45 p.m.
Wed. 4:45-7:45 p.m.
Thurs. 5-6:45 p.m.
Sat. 4:45-7:45 p.m.

7074 kc. HJ1ABK
-B- 42.69 meters
CALLE BOLIVIA,
PROGRESO-IGUALDAD
BARRANQUILLA, COLOMBIA
Sun. 3-6 p.m.

7030 kc. HRP1
-B- 42.67 meters
SAN PEDRO SULA,
HONDURAS
Reported on this and other waves
irregularly in evening

6996 kc. PZH
-B- 42.88 meters
P. O. BOX 18,
PARAMARIBO, DUTCH
GUIAN
Sun. 9:36-11:36 a.m.
Mon. and Fri. 5:36-9:36 p.m.
Tues. and Thur. 8:36-10:36 a.m.
2:36-4:36 p.m.
Wed. 3:36-4:36, 5:36-9:36 p.m.
Sat. 2:36-4:36 p.m.

6976 kc. HCETC
-B- 43 meters
TEATRO BOLIVAR
QUITO, ECUADOR
Thurs. till 9:30 p.m.

6905 kc. GDS
-C- 43.43 meters
RUGBY, ENGLAND
Calle N.Y.C. evening

6900 kc. HI3C
-B- 43.48 meters
LA RAMONA, DOM. REP.
LA VOZ de RIO DULCE.
7:30-9:30 p.m.

6860 kc. KEL
-X- 43.70 meters
BOLINAS, CALIF.
Tests Irregularly
11 a. m.-12 n.; 6-9 p. m.

6814 kc. HIH
-B- 44.03 meters
SAN PEDRO DE MACORIS
DOMINICAN REP.
12:10-1:40 p.m., 7:30-9 p.m.,
Sun. 3-4 a.m. 4:15-6 p.m.

6755 kc. WOA
-C- 44.41 meters
LAWRENCEVILLE, N. J.
Phone England, evening

6750 kc. JVT
-B.-C- 44.44 meters
NAZAKI, JAPAN
KOKUBAI-DENWA KAISHA,
LTD., TOKIO

6710 kc. TIEP
-B- 44.71 meters
LA-VOZ DEL TROPICO
SAN JOSE, COSTA RICA
APARTADO 257, Daily 7-10
p.m.

6672 kc. YVQ
-C- 44.95 meters
MARACAY, VENEZUELA
Broadcasts Sat. 8-9 p.m.

6660 kc. HC2RLL
-B- 45.05 meters
P. O. BOX 759, GUAYAQUIL,
ECUADOR, S. A.
Sunday, 5:45-7:45 p. m.
Tues., 9:15-11:15 p. m.

6650 kc. IAC
-C- 45.11 meters
PISA, ITALY
Calle ships, evenings

6618 kc. PRADO
-B- 45.33 meters
RIOBAMBA, ECUADOR
Thurs. 9-11:45 p.m.

6611 kc. RV72
-B- 45.38 meters
MOSCOW, U. S. S. R.
1-6 p. m.

6600 kc. HI4D
-B- 45.45 meters
CIUDAD TRUJILLO, DOM-
INICAN REPUBLIC
Except Sun. 11:55 a.m.-1:40
p.m.; 4:40-7:40 p.m.

6560 kc. HI4V
-B- 45.73 meters
CIUDAD TRUJILLO, D.R.
LA VOZ de LA MARINA
5:10-6:40 p.m.

6550 kc. TIRCC
-B- 45.77 meters
RADIOEMISORA CATOLICA
COSTARRICENSE
SAN JOSE, COSTA RICA
Sun. 12:45-2:30, 6-7, 8-9 p.m.

6528 kc. HIL
-B- 45.95 meters
CIUDAD TRUJILLO, D.R.
Sat., 8-10 p.m.

6520 kc. YV6RV
-B- 46.01 meters
VALENCIA, VENEZUELA
12 n.-1 p.m., 6-10 p.m.

6500 kc. HJ5ABD
-B- 46.15 meters
MANIZALES, COL.
12-1:30 p. m., 7-10 p. m.

6450 kc. HJ4ABC
-B- 46.51 meters
"LA VOZ de CAMBEBE,"
APARTADO 39
IBAQUE, COLOMBIA
7:30-11 p.m.

6447 kc. HJ1ABB
-B- 46.53 meters
BARRANQUILLA, COL., S. A.
P. O. BOX 715,
11:30 a.m.-1 p.m.; 4:30-10 p.m.

6425 kc. W9XBS
-X- 46.7 meters
NATL. BROAD. CD.
CHICAGO, ILL.
Relays WMAQ, Irregular

6420 kc. HI1S
-B- 46.73 meters
PUERTO PLATA, DOM. REP.
11:40 a.m.-1:40 p.m., 5:40-
7:40, 9:40-11:40 p.m.

6410 kc. TIPG
-B- 46.8 meters
APARTADO 225,
SAN JOSE, COSTA RICA
"LA VOZ de LA VICTOR"
12 n.-2 p.m., 6-11:30 p.m.

6380 kc. HI3U
-B- 47.02 meters
SANTIAGO de los CABAL-
LEROS, DOM. REP.
Irregular in evening

6375 kc. YV4RC
-B- 47.06 meters
CARACAS VENEZUELA
6:45-9:30 p.m.

6316 kc. HIZ
-B- 47.5 meters
CIUDAD TRUJILLO
DOMINICAN REPUBLIC
Daily except Sat. and Sun.
4:40-5:40 p. m.; Sat. 9:40-
11:40 p. m.; Sun., 11:40 a.
m.-1:40 p. m.

6300 kc. YV12RM
-B- 47.62 meters
MARACAY, VENEZUELA
8-10:30 p.m.

6230 kc. OAX4G
-B- 48 meters
Apartado 1242
LIMA, PERU
Daily 7-10:30 p.m.
Wed. 6-10:30 p.m.

6185 kc. HI1A
-B- 48.5 meters
P. D. BOX 423, SANTIAGO,
DOMINICAN REP.
11:40 a. m.-1:40 p. m.
7:40-9:40 p. m.

6180 kc. XEXA
-B- 48.54 meters
DEPT. OF EDUCATION
MEXICO CITY, MEX.
8-11:30 a.m.

6175 kc. HJ2ABA
-B- 48.58 meters
TUNJA, COLOMBIA
1-2; 7:30-8:30 p.m.

6170 kc. HJ3ABF
-B- 48.62 meters
BOGOTA, COLOMBIA
7-11:15 p. m.

6160 kc. YV3RC
-B- 48.7 meters
CARACAS, VENEZUELA
11 a.m.-2 p.m., 4-10:30 p.m.

6155 kc. COKG
-B- 48.74 meters
BOX 137, SANTIAGO, CUBA
9-10 a.m., 11:30 a.m.-1:30 p.m.,
3:4-3:30 p.m., 10-11 p.m., 12 m.-
2 a.m.

6150 kc. CSL
-B- 48.78 meters
LISBON, PORTUGAL
7-8:30 a.m., 2-7 p.m.

6150 kc. CJRO
-B- 48.78 meters
WINNIEPEG, MAN., CANADA
8 p. m.-12 m.
Sun. 3-10:30 p. m.

6150 kc. HJ5ABC
-B- 48.78 meters
CALI, COLOMBIA
Daily 11 a.m.-12 n., Sun. 12 n.-
2 p.m., Daily except Sat. and
Sun. 7-10 p.m.

6140 kc. W8XK
-B- 48.86 meters
WESTINGHOUSE ELECTRIC
& MFG. CO.
PITTSBURGH, PA.
Relays KDKA
9 p.m.-1 a.m.

6135 kc. HISN
-B- 48.9 meters
SANTIAGO, D.R.
6:40-9:10 p.m.

6130 kc. TGXA
-B- 48.94 meters
GIORNAL LIBERAL PRO-
GRESSISTA, GAUTEMALA
CITY, GUAT.
Heard in the evening.

6130 kc. COCD
-B- 48.92 meters
"La Voz del Aire"
CALLE 6 y 25, VEDADO,
HAVANA, CUBA
Relays CMCD 11 a.m.-12 n., 7-
10 p.m., Sun. 12 n.-4 p.m.

6130 kc. ZGE
-B- 48.92 meters
KUALA LUMPUR,
FED. MALAY STATES
Sun., Tue., and Fri.,
6:40-9:40 a. m.

6120 kc. W2XE
-B- 48.92 meters
ATLANTIC BROADCASTING
CORP.
485 MADISON AVE., N. Y. C.
Relays WABC, 10-11 p.m.

6120 kc. XEFT
-B- 49.02 meters
AV. INDEPENDENCIA 28,
VERA CRUZ, MEX.
11 a.m.-4 p.m., 7:30 p.m.-12 m.
Sat. also 6:30-7:30 p.m.
Sun. 11 a.m.-4 p.m., 9 p.m.-12
Relays XEFT

6115 kc. HJ1ABE
-B- 49.05 meters
CARTAGENA, COL.
P. O. Box 91
Mon. 10 p.m.-12 m.
Daily 7:30-9 p.m.

(All Schedules Eastern Standard Time)

<p>6110 kc. ★CHNX -B- 49.1 meters P. O. BOX 998 HALIFAX, N.S., CANADA Daily 9 a.m.-12:30 p.m., 4-10 p.m. Relays CHNS</p> <p>6110 kc. GSL -B- 49.10 meters DAVENTRY, B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND</p> <p>6110 kc. VUC -B- 49.1 meters CALCUTTA, INDIA Daily except Sat., 3-5:30 a. m., 9:30 a. m.-noon; Sat., 11:45 a. m.-3 p. m.</p> <p>6105 kc. HJ4AB -B- 49.14 meters MANIZALES, COL., S. A. P. O. Box 175 Mon. to Fri. 12:15-1 p. m.; Tues. & Fri. 7:30-10 p. m.; Sun. 2:30-5 p. m.</p> <p>6100 kc. ★W3XAL -B- 49.18 meters NATIONAL BROADCASTING CO. BOUND BROOK, N. J. Relays WJZ Monday, Wednesday, Saturday, 5-8 p. m.; Sun. 12 m-1 a. m.</p> <p>6100 kc. ★W9XF -B- 49.18 meters NATL BROADCAST CO. Relays WENR, Chicago Sun., Tues., Thur., Fri. 9 p. m.- 2 a. m.; W., Sat., 1-2 a. m.</p> <p>6097 kc. ZTJ -B- 49.2 meters AFRICAN BROADCASTING CO. JOHANNESBURG, SOUTH AFRICA. Sun.-Fri. 11:45 p. m., 12:30 a. m. (next day) Mon.-Sat. 3:30-7 a. m., 9 a. m.-4 p. m., Sun. 8:10:15 a. m.; 12:30-3 p. m.</p> <p>6090 kc. ★CRCX -B- 49.28 meters TORONTO, CANADA Daily 5:30-11:30 p. m. Sun. 11:45 a. m.-11:45 p. m.</p> <p>6090 kc. VE9BJ -B- 49.28 meters SAINT JOHN, N. B., CAN. 7-6:30 p. m.</p> <p>6085 kc. 2R0 -B- 49.3 meters E.I.A.R. ROME, ITALY</p> <p>6083 kc. VQ7LO -B- 49.31 meters NAIROBI, KENYA, AFRICA Mon.-Fri. 5:45-6:15 a. m., 11:30 a. m.-2:30 p. m. Also 8:30-9:30 a. m. on Tues. and Thurs.; Sat. 11:30 a. m.-3:30 p. m.; Sun. 11 a. m.-2 p. m.</p> <p>6080 kc. CP5 -B- 49.34 meters LAPAZ, BOLIVIA 7-10:30 p. m.</p> <p>6080 kc. HP5F -B- 49.34 meters Carlton Hotel CDLON, PANAMA 11:45 a. m.-1:15 p. m.; 7:45-10 p. m.</p> <p>6080 kc. W9XAA -B- 49.34 meters CHICAGO FEDERATION OF LABOR CHICAGO, ILL. Relays WCFL Sunday 11:30 a. m.-9 p. m. and Tues., Thurs., Sat., 4 p. m.-12 m.</p>	<p>6079 kc. DJM -B,X- 49.34 meters BROADCASTING HOUSE, BERLIN, GERMANY 3-5 p. m.</p> <p>6072 kc. OER2 -B- 49.41 meters VIENNA, AUSTRIA 9 a. m.-5 p. m.</p> <p>6070 kc. HJ4ABC -B- 49.42 meters PERIERA, COL. 9:30-11:30 a. m., 7-8 or 9 p. m.</p> <p>6070 kc. VE9CS -B- 49.42 meters VANCOUVER, B. C., CANADA Sun. 1:45-9 p. m., 10:30 p. m.- 1 a. m.; Tues. 6-7:30 p. m., 11:30 p. m.-1:30 a. m. Daily 6-7:30 p. m.</p> <p>6065 kc. HJ4ABL -B- 49.46 meters MANIZALES, COL. Daily 11 a. m.-12 n., 5:30-7:30 p. m. Sat. 5:30-10:30 p. m.</p> <p>6060 kc. ★W8XAL -B- 49.50 meters CROSBY RADIO CORP. CINCINNATI, OHIO 6:30 a. m.-8 p. m.; 11 p. m.-1 a. m. Relays WLW</p> <p>6060 kc. W3XAU -B- 49.50 meters NEWTON SQUARE, PA. Relays WCAU, Philadelphia 8 p. m.-11 p. m.</p> <p>6060 kc. OXY -B- 49.50 meters SKAMLEBOAEK, DENMARK 1-6:30 p. m.</p> <p>6050 kc. HJ3ABD -B- 49.59 meters BOX 509, BOGOTA, Col. COLOMBIA BROADCASTING 12 n.-2 p. m., 7-11 p. m.; Sun. 5-9 p. m.</p> <p>6050 kc. HI9B -B- 49.59 meters SANTIAGO DOM. REP. Irregular 6 p. m.-11 p. m.</p> <p>6050 kc. GSA -B- 49.59 meters DAVENTRY, B.B.C., BROADCASTING HOUSE, LONDON, ENGLAND</p> <p>6042 kc. HJ1ABG -B- 49.65 meters EMISORA ATLANTICO BARRANQUILLA, COLO. 12 n.-1 p. m., 6-10:30 p. m. Sun. 1-8 p. m.</p> <p>6040 kc. W4XB -B- 49.67 meters MIAMI BEACH, FLA. Relays WIOD 12 n.-2 p. m., 5:30 p. m.-12 m.</p> <p>6040 kc. PRA8 -B- 49.67 meters RADIO CLUB OF PERNAMBUCO PERNAMBUCO, BRAZIL 1-3 p. m., 4-7:30 p. m. daily</p> <p>6040 kc. ★W1XAL -B- 49.67 meters BOSTON, MASS. Tues., Thurs., 7:15-9:15 p. m. Sun 5-7 p. m.</p> <p>6040 kc. YDA -B- 49.67 meters N.I.R.O.M. TANDJONGPURIK, JAVA 5:45-6:45 p. m., 10:30 p. m.-1:30 a. m.</p>	<p>6030 kc. ★HP5B -B- 49.75 meters P. O. BOX 910 PANAMA CITY, PAN. 12 n.-1 p. m., 7-10:30 p. m.</p> <p>6030 kc. VE9CA -B- 49.75 meters CALGARY, ALBERTA, CAN. Thurs. 9 a. m.-2 a. m. (Fri.); Sun. 12 n.-12 m. Irregularly on other days from 9 a. m.-12 m.</p> <p>6020 kc. CQN -B- 49.83 meters MACAO, CHINA Mon. and Fri. 3-5 a. m.</p> <p>6020 kc. ★DJC -B- 49.83 meters BROADCASTING HOUSE, BERLIN 11:35 a. m.-4:25 p. m., 4:55- 10:45 p. m.</p> <p>6020 kc. XEUW -B- 49.82 meters AV. INDEPENDENCIA, 98, VERA CRUZ, MEX. 8 p. m.-12:30 a. m.</p> <p>6018 kc. ZHI -B- 49.9 meters RADIO SERVICE CO., 20 ORCHARD RD., SINGAPORE, MALAYA Mon., Wed. and Thurs 5:40-8:10 a. m. Sat. 10:40 p. m.-1:10 a. m. (Sun.) Every other Sunday 5:10- 6:40 a. m.</p> <p>6012 kc. HJ3ABH -B- 49.91 meters BOGOTA, COLO. APARTADO 565 6-11 p. m. Sun. 12 n.-2 p. m., 4-11 p. m.</p> <p>6010 kc. ★COCO -B- 49.92 meters P.O. BOX 98 HAVANA, CUBA Daily 9:30 a. m.-1 p. m., 4-7 p. m., Sun. 8-10 p. m. Sat. also 11 p. m.-12 m.</p> <p>6005 kc. HJ1ABJ -B- 49.96 meters SANTA MARTA, COLO. 6-11 p. m. except Wed.</p> <p>6005 kc. VE9DN -B- 49.96 meters CANADIAN MARCONI CO., MONTREAL, QUE. CANADA Saturdays at 11:30 p. m.</p> <p>6000 kc. HJ1ABC -B- 50 meters QUIBDO, COLOMBIA 5-6 p. m., Sun. 9-11 p. m.</p> <p>6000 kc. TGWA -B- 50 meters GUATEMALA CITY, GUAT. 12 n.-1 p. m., 6:30-7:30 p. m. 10-11 p. m. Sat. also from 12 m.- 6 a. m. (Sun.)</p> <p>6000 kc. RV59 -B- 50 meters MOSCOW, U. S. S. R. Daily 12:30-6 p. m.</p> <p>5990 kc. ★XEBT -B- 50.08 meters MEXICO CITY, MEX. P. O. Box 79-44 8 a. m.-1 a. m.</p> <p>5985 kc. HJ2ABC -B- 50.13 meters CUCUTA, COLOMBIA 6-9:30 p. m.</p> <p>5980 kc. HJ2ABD -B- 50.17 meters BUCARAMANGA, COL. 6-10 p. m.</p>	<p>5980 kc. XEVI -B- 50.17 meters MEXICO CITY, MEX. Mon., Wed., Fri., 3-4 p. m. Tues., Fri. 7:30-8:45, 10 p. m.- 12 m.; Sat. 9-10 p. m.; Sun. 1- 2:15 p. m.</p> <p>5980 kc. HIX -B- 50.17 meters CIUDAD TRUJILLO, DOMINICAN REP. Sun. 7:40-10:10. Daily 11:40 a. m.-12:40 p. m., 4:40-5:40 p. m.; Tues. and Fri. 8:10-10:10 p. m.</p> <p>5970 kc. HJN -B- 50.26 meters BOGOTA, COL. 6-11 p. m.</p> <p>5968 kc. HVJ -B- 50.27 meters VATICAN CITY (ROME) 2-2:15 p. m., daily, Sun., 5-5:30 a. m.</p> <p>5950 kc. HJ4ABE -B- 50.42 meters MEDELLIN, COLO. Daily 11 a. m.-12 n., 6-10:30 p. m.</p> <p>5940 kc. TG2X -B- 50.5 meters GUATEMALA CITY, GUAT. 4-8, 9-11 p. m.</p> <p>5910 kc. HRN -B- 50.76 meters TEGUCIGALPA, HONDURAS 12:30-2 p. m., 6-7:30, 8-9:30 p. m.; Sun. 3-5 p. m., 8 p. m.-12 m.</p> <p>5900 kc. HH2S -B- 50.85 meters PORT-au-PRINCE, HAITI 7:30-10:30 p. m.</p> <p>5885 kc. HCK -B- 50.98 meters QUITO, ECUADOR, S. A. 8-11 p. m.</p> <p>5880 kc. YV8RB -B- 51.02 meters "LA VOZ de LARA" BARQUISIMETO, VENEZUELA 6-10 p. m.</p> <p>5860 kc. HI1J -B- 51.19 meters SAN PEDRO de MACORIS, DOM. REP. 6:30-9 p. m.</p> <p>5853 kc. WOB -C- 51.26 meters LAWRENCEVILLE, N. J. Calls Bermuda, nights</p> <p>5850 kc. ★YV5RMO -B- 51.28 meters CALLE REGISTRÓ, LAS DE- LICIAS APARTADO DE COR- RES 214 MARACAIBO, VENEZUELA 11 a. m.-12:30 p. m., 5-9:30 p. m.</p> <p>5825 kc. TIGPH -B- 51.5 meters SAN JOSE, COSTA RICA 7-10 p. m.</p> <p>5800 kc. ★YV2RC -B- 51.72 meters RADIO CARACAS CARACAS, VENEZUELA Sun. 8:30 a. m.-10:30 p. m. Daily 11 a. m.-1:30 p. m., 4-9:30 p. m.</p>	<p>5790 kc. JVU -C- 51.81 meters NAZAKI, JAPAN</p> <p>5780 kc. OAX4D -B- 51.9 meters P.O. Box 853 LIMA, PERU Mon., Wed. & Sat. 9-11:30 a. m.</p> <p>5720 kc. YV10RSC -B- 52.45 meters "LA VOZ de TACHIRA," SAN CRISTOBAL, VENEZUELA 6-11:30 p. m.</p> <p>5713 kc. TGS -B- 52.51 meters GAUTEMALA CITY, GUAT. Wed., Thurs. and Sun. 6-9 p. m.</p> <p>5500 kc. TI5HH -B- 54.55 meters SAN RAMON, COSTA RICA Irregularly 3:30-4, 8-11:30 a. m.</p> <p>5077 kc. WCN -C- 58.08 meters LAWRENCEVILLE, N. J. Phones England irregularly</p> <p>5025 kc. ZFA -C- 59.7 meters HAMILTON, BERMUDA Calls U.S.A., nights</p> <p>5000 kc. TFL -C- 60 meters REYKJAVIK, ICELAND Calls London at night, Also broadcasts irregularly</p> <p>4975 kc. GBC -C- 60.30 meters RUGBY, ENGLAND Calls Ships, late at night</p> <p>4820 kc. GDW -C- 62.24 meters RUGBY, ENGLAND Calls N.Y.C., late at night</p> <p>4752 kc. WOO -C- 63.1 meters OCEAN GATE, N. J. Calls ships irregularly</p> <p>4600 kc. HC2ET -B- 65.22 meters Apartado 249 GUAYAGUIL, ECUADOR Wed., Sat., 9:15-11 p. m.</p> <p>4320 kc. GDB -C- 69.44 meters RUGBY, ENGLAND Tests, 8-11 p. m.</p> <p>4273 kc. RV15 -B- 70.20 meters KHABAROVSK, SIBERIA, U. S. S. R. Daily, 3-9 a. m.</p> <p>4272 kc. WOO -C- 70.22 meters OCEAN GATE, N. J. Calls ships irregularly</p> <p>4098 kc. WND -C- 73.21 meters HIALEAH, FLORIDA Calls Bahama Isles</p> <p>4002 kc. CT2AJ -B- 74.95 meters PONTA DELGADA, SAO MIGUEL, AZORES Wed. and Sat. 5-7 p. m.</p> <p>3040 kc. YDA -B- 98.88 meters N.I.R.O.M. TANDJONGPURIK, JAVA 5:30-11 a. m.</p>
-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

(All Schedules Eastern Standard Time)

All Schedules Eastern Standard Time

ENGLAND

● DAVENTRY operates approximately as follows in April. Trans. 1—12:15-2:15 a. m. on GSN (11.82 mc.) and GSB (9.51 mc.); Trans. 2—6-8:45 a. m. on GSJ (21.53 mc.) and GSG (17.79 mc.). A third transmitter may be used on GSF; Trans. 3—9:10:15 a. m. on GSG and GSF (15.14 mc.), 10:15 a. m.-12 n. on GSF and either GSG or GSE (11.86 mc.); Trans. 4—12:15-2:15 p. m. on GSI (15.26 mc.), GSD (11.75 mc.) and GSB; 2:15-4 p. m. on GSD, GSB and either GSL (6.11 mc.) or GSC (9.58 mc.), 4-5:45 p. m. on GSB, GSD and either GSC or GSO (15.18 mc.); Trans. 5—6-8 p. m. on GSD. GSC and either GSB or a 19 meter wavelength (GSF, GSO or GSP, (15.31 mc.); Trans. 6—10-11 p. m. on GSD and GSC.

When to Listen In By M. Harvey Gernsback

GERMANY

The latest schedule available on the German short wave stations follows: Stations marked (*) are experimental. For South Asia DJN 12:30-3 a. m., 3:50-11 a. m., DJR* 1:30-3:30 a. m., DJB 3:50-11 a. m., DJL* 6:30-8 a. m. For East Asia DJA 12:30-3:50, 8:05-11 a. m., DJQ 12:30-3, DJE 8:05-11 a. m. For Africa 11:35 a. m.-4:25 p. m. on DJD and DJC., on DJP* 12 N-2 p. m.; DJO* 3-4:55 p. m. For S. America. DJA 4:55-10:45 p. m. For Central America DJN, 4:55-10:45 p. m. For N. America DJD and DJC 4:55-10:45 p. m., DJM* 7:30-9:30 p. m.

CZECHOSLOVAKIA

According to a letter received from the directors, the new 34 kw. short wave broadcaster being erected near Prague by the government, should be ready for tests by May of this year. It has wavelengths in all the s-w broadcast bands except the 16 and 11 meter bands.

ITALY

The schedule of the Italian 2R0 has not been changed at the time of writing but it is expected that the afternoon transmission will be shifted to 11.81 mc. shortly. 2R0 has 2.19 meter waves (15.23 and 15.29 mc.), one 16 meter wave (17.77 mc.), one 13 meter wave (21.51 mc.) and one 11 meter wave (25.65 mc.). These will probably be employed during the coming summer, especially during the morning transmissions.

(Continued on page 43)

SHORT WAVE LEAGUE

Here's Your Button

The illustration here shows the beautiful design of the "Official" Short Wave League button, which is available to everyone who becomes a member of the Short Wave League.



The requirements for joining the League are explained in a booklet, copies of which will be mailed upon request. The button measures 3/4 inch in diameter and is inlaid in enamel—3 colors—red, white, and blue.

Please note that you can order your button AT ONCE—SHORT WAVE LEAGUE supplies it at cost, the price, including the mailing, being 35 cents. A solid gold button is furnished for \$2.00 prepaid. Address all communications to SHORT WAVE LEAGUE, 99-101 Hudson St., New York.



HONORARY MEMBERS

- Dr. Lee de Forest
- John L. Reinartz
- D. E. Replogle
- Hollis Baird
- E. T. Somerset
- Baron Manfred von Ardenne
- Hugo Gernsback
- Executive Secretary*

SHORT WAVE SCOUT NEWS

Brecksville, Ohio, O.L.P. Short Wave "Log"

KKP—16030 kc., Hawaii, very loud.
 HH3W—9595 kc., Haiti, very loud, clear and steady.
 VK2ME—9590 kc., Australia, fair, rather choppy; calling W2XAF.
 HRN—5875 kc., Honduras, very good.
 DJC—6020 kc., Germany, very loud and clear.
 HRN—5875 kc., Honduras, very loud.
 HC2RL—6660 kc., Ecuador, very good.
 KEE—7715 kc., U.S., very loud.
 GSC—9580 kc., England, very good, steady.
 DJC—6020 kc., Germany, very loud.
 GSI—6110 kc., England, loud but QRM.
 KEE—7715 kc., U.S., very loud.
 TIEP—6710 kc., Costa Rica, loud, but QRM.
 HH3W is a new station located in Port Au Prince, Haiti. P.O. Box A117.
 Xmitter 42-46-46s Mod. Grid A. 30 watts output. Schedule—1 to 2 P.M., and 7 to 8:30 P.M., E.S.T.

C. Ricardo Widmaier, Opr.

The above is from a veri received from HH3W. HH3W is the call used for broadcasting, while HH2W is the amateur call. (Eastern Standard Time.)

EDWARD M. HEISER,
 Route 2, Box 124
 Brecksville, Ohio.

Official Listening Post Report from Hiram Muxo, 765 Trinity Ave., Bronx, New York.

● GLAD to be of service to Short Wave Craft. My report: These new stations have not verified.
 HRP1—El Eco de Honduras, 6360 kc., R7.
 TGS—Radiotransmisora de la Casa Presidencial, 5713 kc., R8.
 T18WS—Ecos del Pacifico, Punta Arenas, Costa Rica, 7550 kc., bad fading.
 YV8RB—From Barquisimeto, Venezuela, 5880 kc., R9 at times.
 YV5RMO—Ecos del Caribe, Maracaibo, Venezuela, 5850 kc., R9 plus. I heard this station on Feb. 18, about 9:30 P.M., E.S.T.
 The following stations have verified:
 DJE, DJA, DJB—Germany. These stations come in R9.
 EAQ—Spain, 9860 kc., 22:30 to 02:30, G.M.T.; 17:00 to 19:00 G.M.T., Sat.
 2RO—Italy, 6:00 to 7:30 P.M., Mon., Wed., Fri., 6085kc.; 2:30 to 5 P.M., every day on 9780 kc.
 HJ4ABE—La Voz de Antioquia, 50.6 meters, near 5950 kc. Daily 11 A.M., 12 noon; 6 to 10:30 P.M.
 HJ4ABB—Manizales, Columbia. Mon., to Fri., 12:15 to 1 P.M.
 T1PG—La Voz de la Victor, frq. 6410 kc., 1000 watts.
 COCD—La Voz del Aire, 6130 kc.
 COCO—6010 kc., Havana, Cuba.
 CJRX, 11720 kc.; W8XK, 21.50 mc., 1521

mc.; W9XF, 6100 kc., 10 k.w.; W1XAL, 11790 kc.; W2XAF, 9530 kc.; CJRO, 6150 kc.; W2XAD, 15330 kc.; W3XAL, 17780 kc.
 HIRAM MUXO.

Report from F. W. Hartmann, South Amboy, N.J.

● OVER 100 stations were heard in the past month.
 W1XK in Boston and W8XK in Pittsburgh do not verify reports any more. YV1ORSC mentioned in last month's report is in San Cristobal, Venezuela and not Colombia, as was stated.

Among stations heard the past month were:

HP5F—6080 kc., 10:05 P.M., Colon, Panama, fair to good.
 HJ4ABA appears to have raised its frequency slightly.
 HRN—5875 kc., Honduras, very good, best heard Sundays 9-10 P.M.
 YV12RM—6300 kc., 6:45 P.M., Maracay, Venezuela, fair.
 CEC—10670 kc., 8:30 P.M., Chile, heard best around 9 P.M.
 HI1S—Dominican Republic, 6420 kc., heard 8 to 10:30 P.M., calls U.S. amateurs at times.
 DJM—6079 kc., 4:17 P.M., Berlin, Germany, on 12 noon to 4:30 P.M., best heard around 4 to 4:30 P.M.
 CO9GC—6155 kc., 6:28 P.M., Santiago, Cuha, very good.
 TIRCC—6550 kc., 7:48 P.M., San Jose, Costa Rico, fair to good.
 DZB—10042 kc., 2:50 P.M., Berlin, Germany, broadcasts 2 to 4 P.M.
 JVM—10746 kc., Japan, strong code interference on its Monday and Thursday broadcasts, signal strength fair to good.
 DZA—9675 kc., 5:05 P.M., Germany, good.
 W9XAA—11830 kc., Chicago, Ill., heard 8 to 10 A.M.
 VK3ME—9518 kc., Melbourne, Australia, is poor to fair.
 VK3LR—9580 kc., Melbourne, Australia, heard best 7 to 7:30 A. M.
 VE9DN—6005 kc., Montreal, Canada, very good,

heard 11:40 A.M. to noon on Saturdays.
 VK2ME—9590 kc., Sydney, Australia, heard good on Sundays, 7 to 8 A.M.

PMN—10260 kc., 7:25 A.M., Bandoeng, Java, very poor.

HJ3ABD—6050 kc., 10:38 P.M., Bogota, Colombia, very good; HJ3ABD Colombia Broadcasting moved to 6050 kc. from 7400 kc., its old frequency.


HC2JSB—Guayaquil, Ecuador, heard at different times.

HJN—5970 kc., 10:08 P.M., Bogota, Colombia, very good.

JVN—10660 kc., Tokio, Japan, was heard 7:53 to 9:05 A.M.

Verifications received from HAS3. TPA2 for 15 meg. 11890 kc., 11715 kc., DZB, W4XB, W1XAL, 6.04 meg. and W1XAL, 11 meg.

FLETCHER W. HARTMAN,
 365 John Street, South Amboy, N.J.



Short Wave League

At a Directors Meeting held in New York City, New York, in the United States of America the Short Wave League has elected

John F. Müller

a member of this League


In Witness whereof, this certificate has been officially signed and presented to the above.

H. W. Safford
Genl. Secretary

This is the handsome certificate that is presented FREE to all members of the SHORT WAVE LEAGUE. The full size is 7 1/4" x 9 1/2".

See page 58 how to obtain certificate.

Short Wave

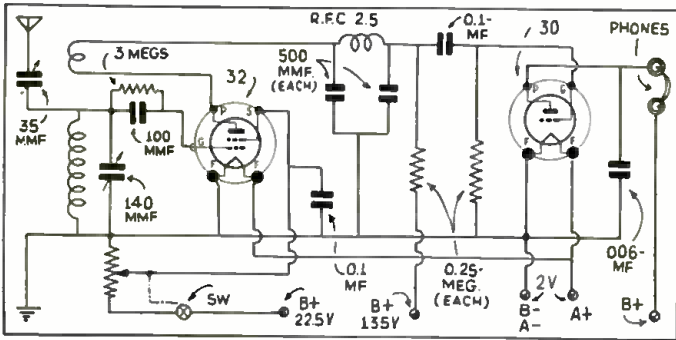

2-tube battery-operated receiver.

REGENERATIVE BATTERY SET

Robert Jones, Westerpont, Md.

(Q) I would like to build a battery set using a type 32 as a regenerative detector, resistance-coupled to a type 30 audio frequency amplifier. Regeneration should be controlled with a potentiometer and the coils should have two windings.

(A) For a battery-operated receiver this one should be the most efficient of the simpler sets. Coil


(A) We see no reason why either the 2-tube set or the Oscillodyne should cause interference in a broadcast receiver providing the smaller sets were tuned to wavelengths below 200 meters.

5 METER RECEIVER

Michael DeFonce, White Plains, N.Y.

(Q) Would you be kind enough to print a diagram of a 5 meter receiver which uses a 37 and a 41.

(A) The 5 meter receiver here

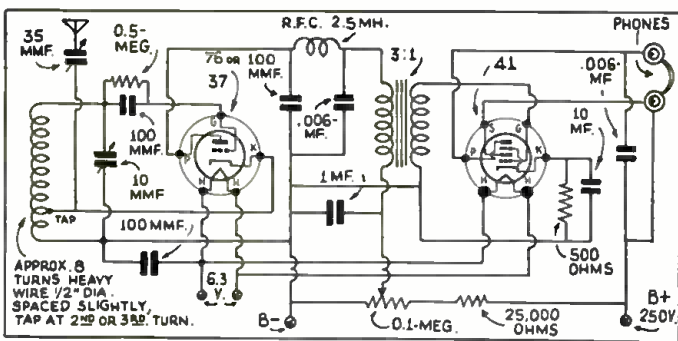

5-meter receiver using 6.3 volt tubes.

data can be obtained from the January 1936 Question Box.

2-TUBE DIAGRAM

C. Drane, Jr., Marshfield, Ore.

(Q) Please print a diagram of a receiver using a 57 and 56 with no R.F. stage.

(A) You will find such a diagram reprinted herewith.


(Q) Will this receiver cause interference in a regular broadcast receiver, when the short wave set is tuned below 200 meters. Also would a 1-tube super-regenerator, such as the 1-tube Oscillodyne, cause interference under similar conditions?

printed is of the self-quenching type and should give excellent results. It is practically the same as the famous 2-tube receiver originated in the November, 1934 issue of *Short Wave Craft* and which is used by nearly 50% of the 5-meter "bugs."

AMPLIFIER FOR BAT. SET

S. Platkin, Brooklyn, N.Y.

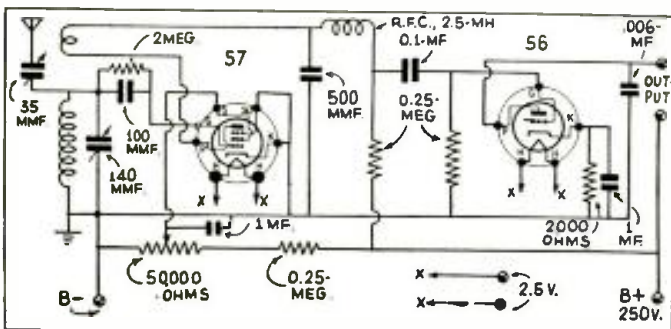(Q) I have built the "Prof. Doerle" and have had excellent results with it. Now I would like to add an amplifier to it, in order that I may obtain full loud-speaker volume. Would you kindly print the diagram and indicate a suitable tube.




The old "standby"; 57 detector and 56 A.F. amplifier.

(A) Undoubtedly the best suited tube is the type 33 pentode. This will provide plenty of volume for the speaker. The input connections as shown in the diagram should be connected to the present phone posts of your receiver.

PHONE-JACK FOR ALL-STAR JUNIOR

M. J. Schaffer, Vallejo, Calif.

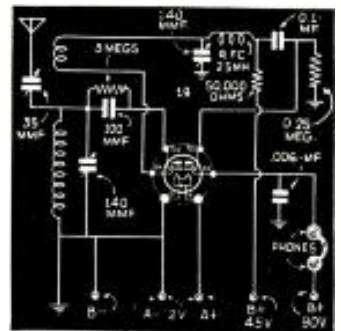(Q) Would you please tell me how I may connect a pair of ear-phones to the All-Star Junior 5-tube Super? If possible I would like to use a jack which would cut out the speaker, while the phones were being used.




"Two-in-one" receiver using a type 19 tube.

2 IN 1 RECEIVER

Harry W. Lewis, Quakertown, Pa.

(Q) Please show a diagram in the Question Box of a 1-tube battery operated receiver using a type 19 tube, one section for the regenerative detector and the other as a resistance-coupled audio amplifier.

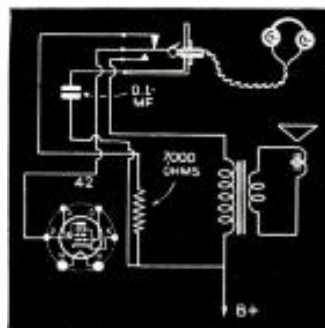(A) This 1-tube receiver which actually performs the same as a 2-tube set, was originally the "Twinplex" which took short-wave "Fandom" by storm several years ago. Excellent results can be expected and it is an ideal beginner's set.



Phone jack for "All-Star" receiver.

(A) We have shown in the diagram a method by which you may connect phones to the 42 amplifier and disconnect the speaker at the same time. The 7000 ohm resistor is brought into the circuit when the primary of the output transformer is disconnected in order to provide a suitable load for the pentode. The Jack has three plates, forming a single-pole double-throw switch and also the output connections for the earphones.

NEED LICENSE FOR FIVE METERS?

Harry Retales, Ipswich, Mass.

(Q) Please give me complete details and information regarding the use of the five meter band. For experimental purposes is a license necessary?


(A) Absolutely! A license is necessary, regardless of what wavelength you are operating on. Many experimenters are under the impression that for the very short waves, no license is needed. This of course is not true.

3-TUBE A.C., T.R.F. RECEIVER


William Danson, Sussex, Can.

(Q) Would you please publish a diagram of a short-wave receiver using a 58 tuned R.F. amplifier, a 57 regenerative detector and a 2A5 audio amplifier? Could another 2A5 be added to this at a later date?

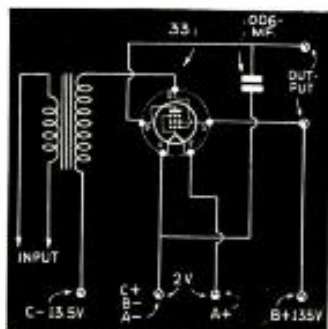(A) The diagram you requested will be found on this page and it should make an excellent short-wave receiver. However, we do not recommend that you add another pentode to the line-up already shown. Better results will be obtained by adding a 56 between the 57 and the 2A5. This will give additional audio volume.



Pentode amplifier for any battery set.

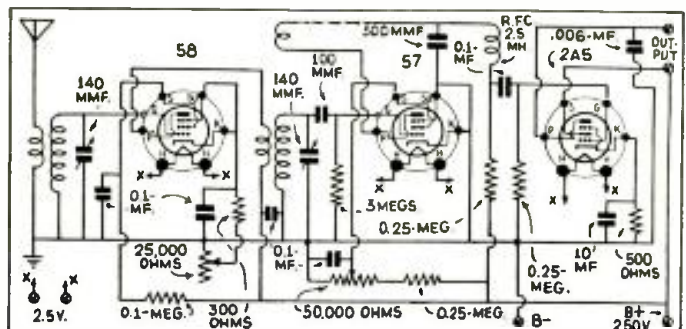

T.R.F. regenerative receiver with pentode A.F. amplifier.

QUESTION BOX


EDITED BY GEORGE W. SHUART, W2AMN

Because the amount of work involved in the drawing of diagrams and the compilation of data, we are forced to charge 25c each for letters that are answered directly through the mail. This fee includes only hand-drawn schematic drawings. We cannot furnish "picture-layouts" or "full-sized" working drawings. Letters not accompanied by 25c will be answered in turn on this page. The 25c remittance may be made in

the form of stamps, coin or money order.

Special problems involving considerable research will be quoted upon request. We cannot offer opinions as to the relative merits of commercial instruments.

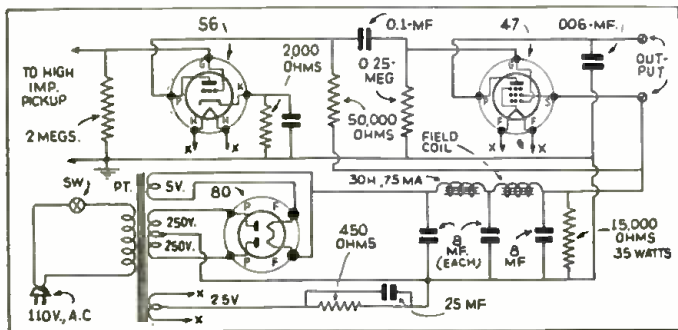Correspondents are requested to write or print their names and addresses clearly. Hundreds of letters remain unanswered because of incomplete or illegible addresses.




Amplifier for phonograph pick-up.

AMPLIFIER FOR PHONOGRAPH PICK-UP

Stuart G. Patterson, Phila., Pa. (Q) I intend to build an amplifier for an electric phonograph using a 56 and a 47 together with an 80 rectifier. Would you please print the necessary diagram and state the impedance of the pick-up head. Also what field-coil resistance should be used in the power-supply.

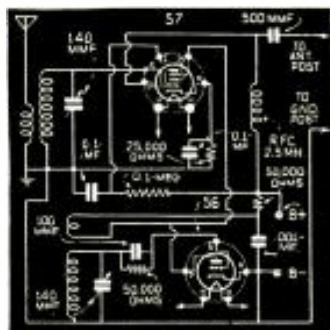(A) The complete diagram is shown and we recommend that a high impedance pick-up be used and coupled directly to the grid circuit. For the field coil we suggest something around 1500 to 2000 ohms. This should be used in place of one of the filter chokes as shown in the diagram.

coil data for this receiver may be found in the January Question Box.



2-tube converter.

3-TUBE E.C. RECEIVER

Arthur Woolf, Johannesburg, S. Africa.

(Q) Would you please be so kind as to publish in one of your coming Question Boxes a circuit diagram showing the connections of an electron-coupled 3-tube receiver. I would like to use a 57 transformer, coupled to a 56 and another transformer coupled to a 2A5. Also furnish the coil data.


(A) We are printing the diagram you request but are not showing transformer coupling. The 57 does not work well through a transformer and we believe better stability and results would be obtained by using resistance coupling. The antenna should be coupled through a 35 mmf. variable condenser. The

2-TUBE CONVERTER


Edward Cole, Cape Girardeau, Mo.

(Q) I have an RCA super-heterodyne receiver which does not cover the short-wave bands and I would like to construct some sort of converter which would give me satisfactory results. Would you be kind enough to print a diagram in your Question Box?

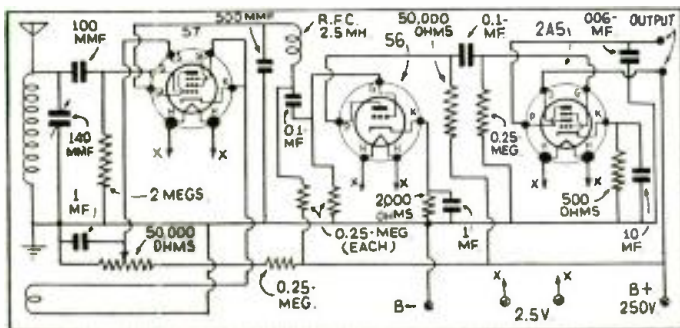(A) We are pleased to print the diagram of a converter using a 56 and a 57. Standard four prong coils are used, data for which may be found in the January Question Box. This should give satisfactory results in conjunction with your receiver. If your set happens to use 6.3 volt tubes, then you will, of course, substitute a 6C6 and a 76 in place of those shown in the diagram.



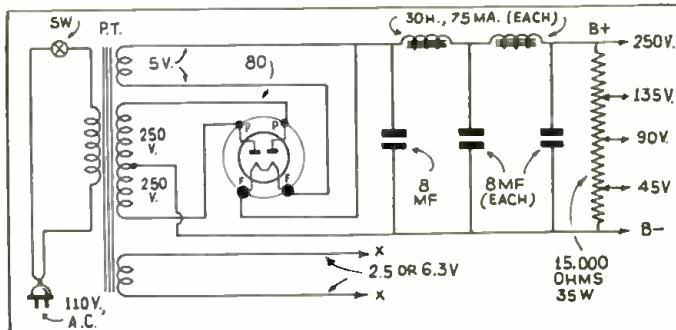Regenerative detector and two A.F. amplifiers.



Power-supply for any A.C. operated receiver.

DIAGRAM OF TWO TYPE 30's


L. Edwards Jr., Shelbyville, Tenn. (Q) Would you be so kind as to publish a diagram of a battery-operated receiver using two type 30 tubes? This should have a regenerative detector with a regeneration condenser and one stage of transformer-coupled audio amplification. The plate supply should consist of 45 volts from a "B" battery.

power supply which will deliver the following voltages: 3 volts, 45, 90, and 145 volts.

(A) The power supply diagram shown will deliver the necessary voltages. However, we do not know why you specify 3 volts, unless this were for the filament supply. Transformers usually have 2.5 or 6.3 volt filament windings.

2-TUBE A.C.-D.C. SET

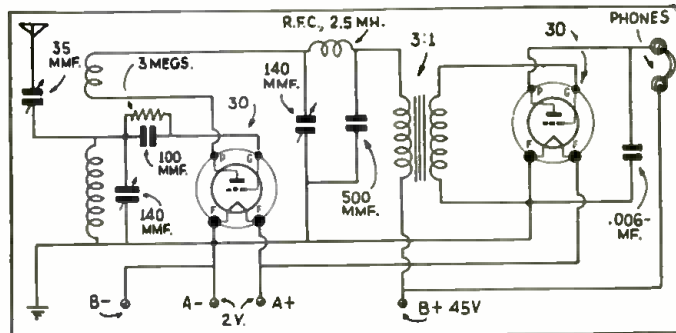(A) This combination provides Boh Feik, Sioux City, Iowa.



Battery set using two type 30's.

a very sensitive and economical receiver and is ideally suited to the needs of the new-comer to the ranks of short waves.


(Q) Would you please print a diagram in your next Question Box. of an A.C.-D.C. receiver.

(A) The 6F7 is used as the detector and audio amplifier; the pentode section as the detector and the triode section as the audio stage. The heaters are operated directly from the 110 volt line through a voltage-dropping resistor.

POWER SUPPLY DIAGRAM

H. V. Calkins, Toledo, Ohio.

(Q) I would like to construct a

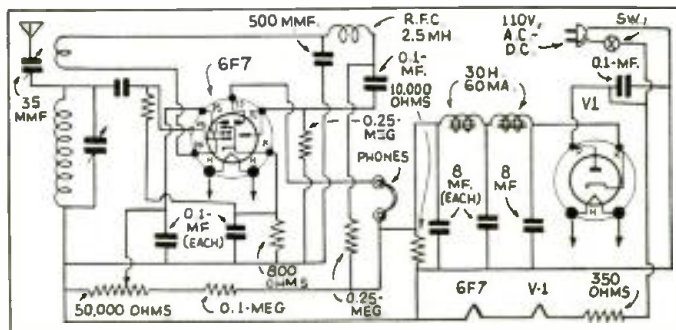

A.C.-D.C. receiver with a 6F7 and a V1.

Some Little-Known Facts About Short and All-Wave Aerials

— By Arthur H. Lynch

Long-Distance Reception

● LONG-DISTANCE radio reception depends upon several important factors. The power used at the transmitter is very important. No less important is the transmitting antenna. Such eminent authorities as Paul F. Godley, have been able to increase the service areas of many of our broadcasting stations by making no changes in power, but simply by improving the design of the antenna systems. We have been attempting to cover long distances by radio for a long time, but it has only been during the past couple of years that the importance of the antenna system has been recognized.

Another important factor to be considered in our long distance work is the location of the receiver itself! Then, too, the design of the receiver and its overall sensitivity, selectivity, and so forth, must be considered.

We are then in just about the position of the person who has a new receiver and wants to install it in a manner which will bring about the most satisfactory reception. There is one drawback to long distance radio reception which is greater than all others—and that is *man-made static!* It makes itself evident to us by producing raucous groans and hisses along with the speech and music we desire. It is much more prevalent in some localities than others, and there are a very few locations where this nuisance does not seem to exist at all. It is this noise, produced by the radiations from the circuits in which electrical machinery is incorporated, therefore, from which we must free ourselves, if we are to get the best possible performance from our receivers.

Installing a Modern Radio Receiver

Radio receivers, as they are being manufactured today, are very satisfactory devices and they are, as a general thing, sensitive enough to cover very long distances for us, if we only give them *half a chance!* It must be remembered from the very start, that we can only use the full sensitivity which the manufacturer has provided in our receiver, if its use does not bring in a lot of noise to "hash up" our desired programs. Most receivers are so sensitive that they will actually bring in stations a thousand miles or more away when attached to a wire just a few feet long, in a location which is free from noise. Therefore, the first thing to do in placing a receiver in operation is to set it up in the most convenient part of the house and attach ordinary pieces of wire to the antenna and ground posts. If the volume control can be run up to the limit, without having the loudspeaker imitate the "battle of the Marne," you may consider yourself very lucky and you need concern yourself but little with the antenna and noise problem which is very much the concern of us less fortunate folk.

If a small amount of noise is observed, it may be eliminated in a great many instances by the very simple expedient of moving the receiver to another part of the same room, or by increasing the length of the antenna wire. The increase in length results in a better signal pickup and has the apparent effect of cutting down the interference. Moving the receiver is a remedy which is frequently effective but is little tried.

If you are, like most of us, still bothered by an undesirable din from your loudspeaker, it may be that a good line filter inserted between your electric light outlet and the receiver will do the trick for you. It will be observed that what we are attempting to do is provide satisfactory reception with the least possible effort and expense. This desirable result is not always possible but it is worth striving for.

With a special discussion of the best location for an antenna; "long distance" reception in noisy locations.


There is a definite relation between the energy picked up by our receiver from the station we desire to hear and the energy it picks up from those circuits which radiate parasitic electrical impulses which create noise. This relationship is known as the *signal-to-noise* ratio. For satisfactory reception we must have a ratio which is in favor of the signal.

Contrary to general belief, there is not much inherent noise in the radio receiver itself. This may be proved very easily by simply disconnecting the antenna and turning the volume control up to the limit. There is a lot of "loose conversation" going on at present about *tube noise*. Such noise is of no practical consequence in the ordinary receiver and, therefore, need have no consideration here at all.

The ideal situation is one where we may have complete freedom from noise and an antenna of reasonable length, let us say from forty up to a hundred or more feet from the antenna post on the receiver to the far end of the antenna. The length, for ordinary reception is not very important.

Fortunately, the noise which most interferes with our reception is confined to an area of a few feet around the wiring which carries it into our location. Interference from a neighbor's vacuum cleaner or oil-burner may be carried along the electric light or the telephone wires and radiated in our house and may then be picked up by our antenna.

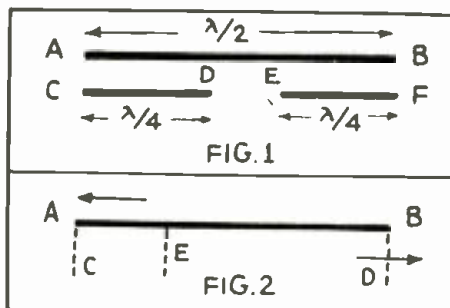Therefore, when we happen to be in a location where interference of the "man-made" variety prevails, it is necessary for us to set up our antenna in a manner which will enable us to pick up the *greatest amount* of energy from the desired stations and the *least possible energy* from radiators of interference. We must, in other words, improve the *signal-to-noise* ratio.



Diagrams showing relation of $\frac{1}{4}$ and $\frac{1}{2}$ wave-length aerials; also impedance-match diagram.

What we need is a means of placing our antenna far enough away from the sources of interference to prevent it being affected by them, and then a means of getting the energy picked up by the antenna to our receiver, without being contaminated by the local parasitic radiations.

Solving the "Noise Pick-up" Problem

The whole matter is not very complicated and may be thoroughly understood by reference to the accompanying figures. Suppose we go over them in rotation, considering each problem and its solution as we go. In Fig. 1 we have represented two different types of antennas. The upper line, between A and B, may be considered to represent the portion of any antenna which is the "flat-top" and which is gen-

erally in a horizontal or semi-horizontal plane. We have represented the length as being $\lambda/2$, ($\lambda =$ wavelength) or approximately one-half the wavelength to which it will respond most readily. The relation of wavelength to the antenna length is an important consideration for either transmitting or receiving, when the service is to be maintained upon a single wavelength. It loses its significance when we attempt to use the antenna to cover a broad band of wavelengths or frequencies, as is the case when we are using a modern, multi-band or all-wave receiver.

An antenna of similar length is represented in the lower portion of the figure by C-D and E-F, though it is broken in the center, and each section is half as long as A-B, or one-quarter wavelength, for some particular frequency. While there has been a great deal said and written about the importance of the length of the antenna and the manner in which it should be erected, it is not generally understood that most of the information which has been published has been based upon the performance of antennas for *specific*, rather than *general* purposes.

For instance, much has been made of the *directional properties* of various forms of antennas. While the *directional properties* may be demonstrated on certain wavelengths with a particular antenna, we can not assume that the same characteristics will be found to exist when the antenna is used on other wavelengths. It should be remembered that we are much more concerned with *reducing noise* than we are with the increasing of signal strength, because the *average, modern receiver*, as we have mentioned, *does not require very much of an antenna to produce plenty of signal from the desired station, if we are able to keep the noise down to a reasonable level.*

Let us assume, then, that either of the forms we have illustrated will do the job, as far as "pick-up" is concerned. Would there be any advantage in selecting one over the other? Progressing to Fig. 2, we have shown three possible connections from A-B, by the dotted lines C, D and E, which represent the ordinary lead-in which is used to connect the antenna to the receiver. If the lead C is employed we may consider that the antenna will receive best from the direction to the left, while the reverse will be true, if the lead-in is taken off in the position indicated by D. However, this statement may be taken with a "grain of salt" in connection with the *average person's receiving antenna*. It is true that antennas having their leads taken off from one end will receive best in the direction opposite the free end, but it is only true to any marked degree, when the horizontal portion of the antenna is several times as long as the wavelength we desire to receive. To have any noticeable *directional properties*, in the regular broadcast band, therefore, the antenna would have to be *several blocks long!* If the connection is made at E, no noticeable directional effects will be observed but another point is raised which has come in for its share of misconception.

If the point at which E is connected is carefully chosen with relation to the total length of the antenna—that is the horizontal portion, A-B—we provide ourselves with what is termed a single-wire, *matched-impedance* lead-in. That is, we will accomplish such a result if we consider that the antenna will respond to a particular frequency or wavelength, rather than a whole group of wave lengths, which is more in line with what we require. Therefore, for the purpose of general reception, we may just as well forget about all the ballyhoo with which such lines have been adorned. We may just as well forget about *impedance matching*, for the moment.

(To be concluded)

WE GUARANTEE SATISFACTORY RESULTS ON ALL OF OUR PRODUCTS



**Eilen
RX-14
6-tube Band-spread Receiver**

BIGGER, BETTER, AND MORE POWERFUL THAN EVER! OUR LARGEST, FINEST, AND MOST SENSITIVE SW RECEIVER — just released after

months of painstaking development in order to produce an efficient, selective, and really good short wave model which WILL satisfy even the most discriminating SW fan.

Uses 6D6-6D4-76-76-42-5Z4 hi-gain tubes as TUNED RF amplifier, TUNED screen-grid regenerative detector, POWERFUL 3 stage resistance-capacity coupled audio frequency amplifier, high voltage full wave rectifier and H.V.-FREE power supply. Operates entirely from 105 to 130 volt AC current. Entirely self contained. No external accessories required.

Large, beautiful, illuminated, airplane tuning control—BANDSPREAD TUNING, continuous from 9½ to 625 meters using the electrical bandspread method.

POWERFUL hi-quality audio system delivering 3 watts of power to the built-in hi-fidelity dynamic loudspeaker—automatic headphone jack—extremely smooth regeneration control and volume control—no fringe howl effects—positively hum free—connections for either doublet or single wire type of antenna—black shrivel finished heavy metal chassis, shielding, and cabinet of extreme beauty—must be seen to be appreciated—selectivity, sensitivity and tonal qualities that will amaze you.

EILEN RX-14 KIT, \$15.95
assembled and ready to wire, of all necessary parts, 8 large low-loss coils for 9½-200 meters, and simple detailed instructions (less cabinet, tubes, and BC coils)
Beautiful, heavy steel cabinet \$2.50
6 MATCHED tubes..... 3.30
SPECIAL: Complete kit, cabinet, and 6 tubes unwired, less BC coils..... **\$19.95**
Labor for wiring and testing, extra.....\$2.00
Broadcast band coils (2), extra..... 1.25

IF METAL TUBES (6K7, 7-6K7, 6D6-5Z4) are preferred, add \$1 to price.

RX-14B:
Battery model. Subtract \$1 from above price. (Less batteries.)

AMATEURS:
MODEL RX-14-AB 6 Tube COMMUNICATIONS RECEIVER has same specifications as RX-14 except that it is equipped with special coils for 20-40-80-160 M bands which spread these bands over 80 to 90% of tuning dial. Also equipped with plate voltage cut-off switch for use during transmitting periods. An ideal receiver for amateur work. Add \$1 to price of RX-14.

**Eilen 6A SHORT WAVE
4-TUBE RECEIVER**
A Giant in Performance

The new, sensational, 1935 Eilen 6A receiver is truly a masterpiece. See article P. 604-628 Dec. issue of S.W.C. Its unusual design, conforming to the best in modern engineering theory, has all the latest up-to-the-minute features. **FULL 6 TUBE PERFORMANCE.—POWERFUL 3 STAGE AUDIO AMPLIFIER** which takes the guesswork out of so-called "loudspeaker reception."

Uses 6K7 (metal) 6F7 (twin 2 in 1) 6A3 (metal)—12A7 (twin 2 in 1) hi-gain tubes as RF amplifier, screen grid regenerative detector, POWERFUL 3 stage audio amplifier with pentode output stage, rectifier and built-in hum-free power supply. Completely self-contained. Nothing else required. Operates entirely from 105 to 130 volt AC or 100 light socket. **BAND SPREAD TUNING—smooth regeneration control free from fringe howl effects—new metal tubes or glass tubes if preferred—built in high quality loudspeaker—automatic headphone jack—large, illuminated airplane type vernier dial—large 3 winding low-loss inductances—selectivity, sensitivity, and volume that will amaze you. Heavy black shrivel finish metal chassis and cabinet. Must be seen to be appreciated. Satisfied owners report dozens of foreign stations on loudspeaker—You may do the same under the proper conditions. ORDER YOURS TODAY! YOU'LL NEVER REGRET IT!**



AMATEURS:
Model 6A-AB has same specifications as 6A except that it has special tuning circuit and coils for spreading out the 20-40-80-160 M bands over 80% of dial scale—plate voltage cut-off switch. Add \$1 to price of 6A.

EILEN 6B or 6B-AB battery model of 6A using 34-19-30-33 tubes. Subtract \$1 from price of 6A or 6A-AB.

6A KIT (unwired), of all necessary parts, 4 coils for 9½ to 200 meters and instructions (less cabinet, tubes, speaker, and B.C. coil)..... **\$7.45**
Beautiful cabinet..... \$1.25
4 matched Arcturus tubes..... 3.15
Special loudspeaker..... 1.45
Broadcast band coils (2)..... 1.25
SPECIAL: Complete kit, cabinet, 4 tubes, loudspeaker, and one B.C. coil, (unwired)..... **\$12.45**
Labor for wiring and testing, extra..... \$1.50

**EILEN
XN-12 4-Tube
BANDSPREAD RECEIVER**

An extremely powerful TUNED RADIO FREQUENCY regenerative receiver designed for the SW fan who wishes a high grade instrument of the highest calibre. Uses 6D6-6D6-2A5-30 tubes as TRF amplifier. Tuned regenerative detector, pentode audio frequency amplifier, rectifier and built-in power supply. HUM-FREE. Operates from 105 to 130 volt AC house current.

Illuminated, airplane dial—smooth regeneration control—effective volume control—BANDSPREAD TUNING—SELECTIVE—SENSITIVE—ENORMOUS HEADPHONE VOLUME—will operate speaker on majority of stations—an unusually efficient DX receiver—heavy, black shrivel finished metal chassis and cabinet. Covers 9½ to 600 meters.



XN-12 KIT of necessary parts, 8 coils, and simple instructions (unwired, less cabinet, tubes and BC coils)..... **\$9.95**
Beautiful metal cabinet, extra..... \$2.00
Set of matched tubes..... **\$1.90**
SPECIAL: Complete kit, cabinet and 4 tubes (less BC coils furnished)..... **\$12.95**
Labor for wiring and testing, extra..... 1.50
Broadcast band coils (2), extra..... 1.25

AMATEURS
Model XN-12-AB is same as above except that it is equipped with plate voltage cut-off switch and has special bandspread coils for the 20-40-80-160 M bands. Add \$1 to price.

Eilen HF-35 3-Tube SW Transmitter

A powerful and well engineered amateur band transmitter of great beauty and efficiency—AT A PRICE WITHIN THE AMATEUR'S REACH. Uses 50-46-16 tubes as TRI-TET CRYSTAL CONTROLLED OSCILLATOR—CLASS C RF POWER AMPLIFIER—built-in antenna tuning system—beautiful, black shrivel metal case and shielding—Triplet meters—Eilen transmitting dials—highest quality constructions—35 watts of power output on 20-40-80-160 M bands. A transmitter that you can be proud to own. An excellent exciter unit for high power stages to be added later. 3 coils for any 1 band and instructions included.



HF-35, assembled, and ready to wire (less tubes, power supply, crystal, holder and additional coils) \$12.95
Matched Arcturus tubes (3).....\$2.15
Eilen quartz crystal (80 or 160)..... 1.95
Eilen crystal holder..... 1.00
Coils for additional bands, per set..... 1.45

HV-475 1-Tube power supply for use with HF-35 (less tube) ready to wire..... **\$12.95**
Labor for wiring extra \$1.00
23 tube for HV-475, extra 65 cents

FREE
Large, illustrated catalogue of SW receiving and transmitting apparatus, kits, parts, and accessories. Send for YOUR copy.
SPECIAL
EILEN 2 section 1200 volt xmitting var. condensers (65 mmf. per section)..... \$0.98
RCA 3011-150 MA filter chokes..... .39

HF-20 KIT of all necessary parts and instructions (unwired less tube, power supply, crystal and crystal holder)..... **\$15.95**
Arcturus tubes (3), extra..... \$1.75
Eilen quartz crystal, 80 or 160 M band..... 1.55
or 40 M band..... 2.35
Eilen crystal holder..... 1.00



MODEL HV-475 power supply for use with above. (Unwired, less 83 tube) Wired—\$1 extra..... **\$12.95**
83 tube 65c

EILEN RADIO LABORATORIES Dept. SC 5, 136 LIBERTY STREET, NEW YORK, N. Y.

HIRAM PERCY MAXIM

● SHORT-WAVE "Hams" throughout the country mourn the passing of Hiram Percy Maxim who passed away on February 17 at La Junta, Colorado. His home was in Hartford, Connecticut, from which point his far reaching activities in short-wave Hamdom emanated. Mr. Maxim was well-known throughout the world, particularly as the inventor of the Maxim silencer and numerous implements of warfare. Mr. Maxim was the president and founder of the American Radio Relay League with headquarters at Hartford, and he was responsible for the rapid growth of the League and its membership, which numbers thousands of short-wave "hams" throughout the country.

Hiram Percy Maxim was the son of Sir Hiram Stevens Maxim, inventor of the Maxim automatic gun, and he was a nephew of Hudson Maxim, inventor of smokeless powder.



For many years, Mr. Maxim was president of the Amateur Cinema League and he was also president of the International Radio Union. Mr. Maxim was born in Brooklyn, New York, September 2, 1869, and in 1886 he graduated from the School of Mechanic Arts of the Massachusetts Institute of Technology. He also held an honorary degree of Doctor of Science from Colgate University. At the start of his career, Mr. Maxim was an electrical engineer with the Fort Wayne (Indiana) Jenny Electrical Company. He was also associated at one time with the Thomson Electric Welding Company of Lynn, Massachusetts. Later he was associated with the American Projectile Company of Lynn, and still later he was chief engineer for the Electric Vehicle Company of Hartford, Connecticut. He was a member of numerous scientific societies and held a commission as Lieut. Commander in the United States Naval Reserve Corps. In 1933, he published a book entitled—"Life's Place in the Cosmos."

Please mention SHORT WAVE CRAFT when writing advertisers

LEARN CODE

Or Increase Your SPEED With The Exclusive SOUND Method That Developed The CHAMPIONS!

Get Your Code Training and Technique Where They Got Theirs!

THE CANDLER SYSTEM
For Years The Dominant Source of Code Training and Telegraph Technique!

This famous SYSTEM is backed by a Quarter Century of Success in training Amateurs and Commercial Operators who could be satisfied only with the best!

You Can Learn Code RIGHT, from the Beginning or obtain your commercial license and qualify for a good job by taking CANDLER TRAINING in your own home, as McElroy, Jean Hudson and many others have done and are doing. It is surprisingly easy and inexpensive.



TED R. McELROY, Official Champion of the World, Class A. Speed 69 wpm.

CANDLER SYSTEM taught at HARVARD and Massachusetts Institute of Technology in their course "The Art of Radio Communication," conducted by our famous student, Champion McElroy.



JEAN HUDSON, W3BAK, Official Champion of the World in Class E.


Jean obtained her ham license at the age of 8, and two months after she began Candler SCIENTIFIC CODE and Touch Typewriting Courses, could copy 30 wpm on her "mill." At the age of 9 she won official championship in Class E, against rigid competition.

FREE—1936 Book of FACTS

Contains McElroy's own story, "How I Learned to Read Code, and What Candler Training Has Meant to Me," also little Jean's story and other valuable information. Whether you want to learn code or increase your speed, this book will help you. A card will bring it. No obligation.

CANDLER SYSTEM CO.

Dept. S-5, Asheville, North Carolina

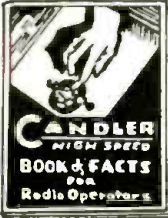

How 5-Megacycle Waves Bridged Hurricane Break

(Continued from page 6)

masts for the antennas, and erecting two shacks, each about eight by twelve feet, for the radio transmitters and receivers. The second day after work started in the field, radio contact was established on a temporary basis. In the meantime the linemen were bringing in connections from the open-wire circuit to Key West, and on September 21 the first circuit was formally turned over for service.

12 Volt Storage Batteries Supplied Power

In the preliminary conferences held to decide the type of apparatus to be employed, it was recognized that a considerable amount of electric power would be required for the operation of the radio apparatus. Since no commercial power was available anywhere near the sites of the radio terminals, it was desirable to use the most efficient and the lowest-power radio equipment available. This led to the decision to use some of the low-power equipment developed for airplane and ship-to-shore communication. To meet these requirements the five-watt 19A transmitter and a 12-type receiver were finally selected. Both of these units have very moderate power requirements, and 12-volt storage batteries could be used as a primary source of power. Complete radio equipment for four channels, two in each direction, including batteries and dynamotors, was shipped from New York to Miami, where it was taken by truck to the site of the eastern terminal just outside of Tavernier. Here half of it was unloaded and the rest put on a fishing boat for the fifty-five-mile water trip to Big Pine Key.

The equipment and arrangement at the two terminals are practically identical. The two radio shacks and antenna poles at Big Pine Key are shown in the photograph at the head of this article. The shacks are about 300 feet apart and each has its antenna poles located adjacent to it and as near the water as practicable. The transmitter antennas are single-wire verticals approximately a quarter-wavelength long. One antenna is fed by a concentric transmission line and the other runs directly to the radio transmitter. Vertical wires were also used for the receiving antennas.

Simplicity and Small Size of Apparatus Outstanding

The simplicity and small size of the apparatus within the shacks are evident from the photographs. In the transmitter shack the two 19A transmitters are mounted on a shelf and the two dynamotors, supplying 500 volts for the plate, are on another shelf directly beneath them. On the floor are the storage batteries supplying power for the filaments and the dynamotors. Sufficient B-battery capacity is also available for emergencies. The box on the wall above the transmitters terminates the lead cable running underground to the receiver shack. The arrangement of the receiver shack is similar. On the upper shelf are the two 12-type receivers, while beneath them are the dynamotors and batteries. A 3000-cycle cut-off filter is connected in the output of each receiver to eliminate carrier hiss and other extraneous high-frequency noises.

To conserve power, the receivers and transmitters at both ends were provided with a remote control on-off circuit, the Big Pine Key terminal being controlled from Key West, and the Tavernier terminal, from Miami. This enabled the testboard men at Key West and Miami to shut down the radio apparatus whenever there is no traffic and thus to save considerable power. Such an arrangement is particularly desirable at Big Pine Key where the batteries have to be carried all the way to Key West for recharging. The batteries for Tavernier were hauled to Homestead for charging.

Every precaution was taken during the installation to prevent cross-talk or any form of interaction between the various circuits at each terminal. Frequencies of about

ASTATIC

The D-104



Ask the Ham Who Owns One

For truthness of tone, dependability in use, ruggedness in construction and quality of performance the Astatic D-104 has proven itself to expert amateurs all over the world as the microphone giving professional value at amateur's price. Ask your jobber to show you this fully guaranteed graffol crystal microphone. List price \$22.50.

Licensed Under Brush Development Company Patents



QUALITY PICKUP

For true fidelity of recordings and minimum wear on records the S-type Astatic Pickup is also the favorite of the veteran amateur.

ASTATIC MICROPHONE LABORATORY, Inc.
YOUNGSTOWN, O., U. S. A.

Manufacturers of

VITREOUS TRANSMITTING GRID LEAKS
VOLUME CONTROLS • POWER RHEOSTATS

Write for Complete Free Catalog

ELECTRAD, Inc.

175 Varick Street, New York

BEGINNER OR OLD TIMER

be a GOOD opr. with: MAC KEY @ \$7.95, finest "speed key" built; JUNIOR MODEL @ \$4.95 a low priced GOOD key; MAC OSCILLATOR @ \$3.95 AC/DC 1,000 cycle practice; "Mac" items sold with positive money back guarantee.

T. R. McElroy, 23 Bayside St., Boston, Mass.

If u hv a Mac Key wrt me now for 25¢ 1st 10 - Mac

NEW! BIRNBACH No. 375 ALL-WAVE ANTENNA



Assembled and Soldered \$4.25
List Price \$4

Easy to install, durable and efficient in every detail. Factory connected and soldered assembly insures correct, perfect connections. No switching required for short wave or broadcast reception. Noise reducing transmission cable conveys signal without loss to receiver coupler, which automatically adjusts to frequency tuned in.

Write Dept. SW 5 for complete Catalog
BIRNBACH RADIO CO., Inc.
145 Hudson St., New York City



1910-1936

THE FINEST IN CONDENSERS—WRITE FOR CATALOG

CORNELL-DUBILIER
CORPORATION

4376 BRONX BOULEVARD
NEW YORK

five megacycles were employed for transmitting from west to east and of about four megacycles, from east to west. This gave a separation of approximately a million cycles between transmitter and receiver frequencies at either terminal, and combined with the 300-foot separation between transmitters and receivers, greatly helped to eliminate interference. In addition all speech wires near the radio receivers, and the composite coils in the connecting telephone lines, were carefully shielded and grounded. The use of underground lead cable to connect the two shacks was another precaution against such interference. With these precautions, and the inherently high quality of the radio apparatus employed, transmission is exceptionally good considering the small amount of power used. During the day a user talking from New York to Havana would not be aware that a radio link was included in the circuit. Sometimes bad static conditions are encountered at night. More than 80 per cent of the calls normally originate during the daytime, however, and the circuit during the first few weeks, was kept in operation only during daylight hours.

Not only was the installation completed in a remarkably short time, but it was carried out under adverse conditions. The sites were covered with a dense mangrove jungle, with mosquitoes and sand flies in droves. Some conception of the appearance of the country may be obtained from the illustration which shows one of the sites during an early stage in the construction. Smudges were kept going continuously in a more or less vain effort to beat back the mosquitoes. Although the shacks were screened, so that the installation inside the shack could proceed without too much annoyance from mosquitoes, the screening proved of little value in barring the sand flies, which readily passed through its meshes. In addition, there were the transportation difficulties caused by the remoteness of the radio terminal sites and the disruption of normal transportation services. In spite of all obstacles, however, the work proceeded rapidly, and the second channel was turned over on September 28. For the first time a radio link had been used in this way as an emergency means of restoring service in an important telephone line.—*Courtesy Bell Laboratories Record.*

The LAMB "Noise Silencer"

(Continued from page 16)

of this operation can be maintained. This adjustment can be so set that the signal will maintain itself at any pre-determined level. Thus when the noise increases above the signal-level, the "gain" of the receiver is cut down, permitting the noise to be cancelled out.

It will thus be seen that the noise can never rise to a greater amplitude than the signal. The diagram given is for an adapter unit which may be applied to any superhet receiver having two I.F. stages. Experience and actual tests have proven that those who try this very ingenious idea will be well rewarded for their efforts.

WAKE UP! FELLOWS!

\$20.00 Prize Monthly for Best Set

● THE editors are looking for "new" receiving circuits—from 1 to 5 tubes preferably. A \$20.00 monthly prize will be awarded to the best short-wave receiver submitted. The closing date for each contest is 75 days preceding date of issue (April 15 for the July issue, etc.). In the event of a tie, an equal prize will be given to each contestant so tying. Address all entries to: Editor, SHORT WAVE CRAFT, 99 Hudson St., New York City.

1936 FULTONE V 3-TUBE RECEIVER

(Stands head and shoulders above all competition)

• Five-In-Three—6D6-6F7-12A7

• All Electric

• REAL Bandsread

• Built-In Speaker

• Consistent Foreign Reception

Screen grid RF stage—Screen grid regenerative detector—High gain first audio tube—Power pentode output—Voltage rectifier—FIVE tube performance from THREE new tube tubes! Self contained humless power supply—operates on 110 volts AC or DC—Triple winding coils—Velvet smooth, large airplane vernier dial—Full loud speaker volume—Tuning range—93.5 to 92.5 meters.

We're proud of it—and we know you will be too! Order your 1936 Fultone V today and enjoy real reception. Try it yourself for five days—full cash refund if you want it.

COMPLETE FULTONE V THREE TUBE RECEIVER KIT of all necessary parts including large airplane dial, crystal finished metal chassis and panel with all holes, four coils 93.5 to 200 meters, and complete easily followed wiring and tuning instructions.

(Not wired, less tubes, cabinet, loud speaker and broadcast coils) **\$7.45**

Three matched guaranteed tubes \$2.20

Metal cabinet for above 1.25

Loudspeaker to fit in set 1.45


200 to 625 meter Broadcast and Long Wave Coils, Two Coils 1.25

Laboratory wired and tested 1.50



SPECIAL COMBINATION OFFER

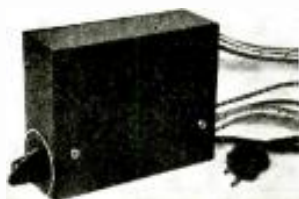Complete Fultone V 3-Tube receiver kit not wired, but with 3 tubes, Two Broadcast band coils, Loudspeaker and Cabinet, Laboratory wired and Tested. **\$11.45** \$1.50 extra



COMPLETE KIT \$3.85

of all necessary first grade parts, crystal finished cabinet with all holes drilled and complete instructions, less tubes, unwired. Threesylvania metal tubes, \$2.50 Completely wired, ready to attach and operate, with tubes \$8.55

• "NOISE SILENCER" ELIMINATES "MAN-MADE" STATIC!

The noise "Check Valve", a development of James J. Lamb, editor of QST, has been acclaimed as one of the greatest discoveries in radio! Attached to any superheterodyne receiver, it eliminates noises caused by any sparking motors (oil burners, vacuum cleaners, fans, etc.) automobile ignition, high tension lines, dial telephones, etc. Reduction of noise as high as 1000 to 1 in power on sharp interference!


Just attach the noise silencer unit to rear or side of your receiver and make three simple clip connections. A few minor adjustments as outlined in the instructions and you enjoy real noise free reception. Works on all wavelengths. The louder the interferer the easier it is to completely cut it out!

HARRISON presents a very compact version of this amazing invention as described in QST and other magazines. A neat metal case measuring only 2"x5½"x1½" houses all necessary parts and the three tubes. Draws only negligible current from receiver.

For SUPERHETERODYNE Receivers only. (Both RCL, SWL, and Amatour). Mention make and model of set when ordering so we may supply the correct pronged attachment plug.

• The ROYAL PR-SIX SIX STEEL TUBE COMMUNICATIONS RECEIVER

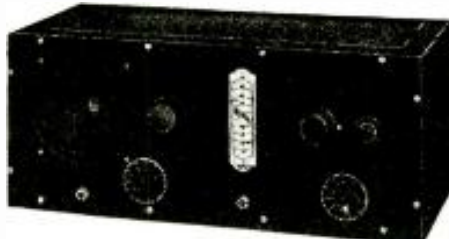IS FULLY DESCRIBED IN THE NEW HARRISON 1936 SHORT WAVE RECEIVER CATALOG



The World Famous Royal PR-SIX \$31.45

with built-in power supply and large dynamic speaker. Complete with SIX real STEEL Tubes, all coils 93.5 to 625 meters, and attractively finished heavy steel cabinet. Laboratory wired and tested, ready to plug in and operate! All the well known makes—from the new Hammarlund "Super-Pro" down to the \$3.45 Harrison "Multi-Kit"—are illustrated and fully described in this NEW Harrison Receiver Catalog.



FREE!

SEND FOR YOUR COPY TODAY!

HARRISON 12 WEST BROADWAY
RADIO COMPANY NEW YORK Dept. C-5 N. Y.

NEW VERNIER INSTRUMENT CONTROLS



No. 525

No. 525 "Front-O-Panel" illuminated airplane type at left has slow speed ratio about 165 to 1 and fast ratio 30 to 1 in 360°. Real silver-plated scale with sun-ray finish. Surface mounting for easy installation.

No. 296 "Plan-O-Vernier" transmitter style at right with built-in Crowe planetary and micrometer indicator. Ratio about 5½ to 1 in 360°. No backlash. Genuine spun-chrome finish.




No. 296

For complete description and other items ask for Bulletin No. 75

Carried in stock by leading jobbers and dealers.

CROWE NAME PLATE & MANUFACTURING CO.
1743 Grace St., Chicago, U. S. A. Cable Address: CRONAME—CHICAGO

Hammarlund "Super-Pro"

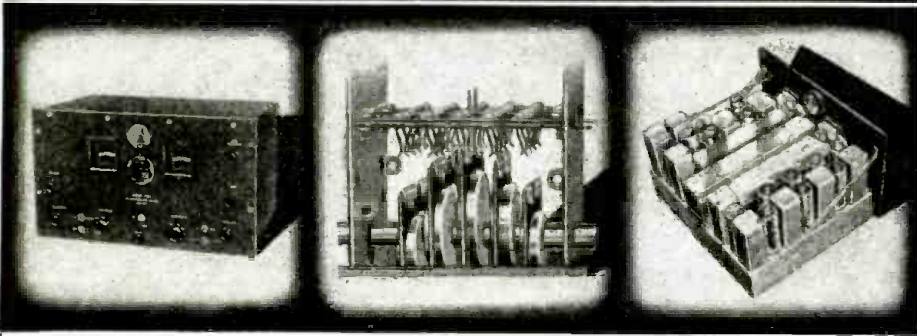

THE Hammarlund "Super Pro," the new amateur—professional receiver is a model unit, designed to meet every rigid precision specification of the professional operator and advanced amateur. It is replete with striking features, such as electrostatically shielded input; selectivity continuously variable from front panel; main dial accurately calibrated in megacycles from 2.5 to 20, and in kilocycles from 540 to 2500; band spread dial (both illuminated); exclusive five-band, silver plated switch (cutaway view illustrated at center above); two tuned R.F. stages on all bands; four air tuned I.F. transformers; three A.F. stages, and separate power supply.

Write department SW-5 for further details!

THE HAMMARLUND MFG. CO., INC.

424-438 W. 33rd St.

New York City

5-Meter Super-Regenerator

(Continued from page 16)

ing grid-leak and condenser and plate return by-pass to cathode, are chosen so that blocking action is attained, thus causing super-regeneration. The circuit as shown functions as a usual oscillator, in which the grid-leak is too high to allow the grid electrons to leak off at a rate which would give a constant value of grid voltage. As a result, there is a variation of average bias which stops oscillation because the plate current is decreased and the mutual conductance of the tube drops.

The circuit constants (values of grid-leak and condenser and circuit decrement) determine the cycles per second this occurs; in this instance, an inaudible rate. Evidently, the plate circuit must constitute a comparatively low impedance path to cathode at such an inaudible frequency, since the plate by-pass must be not lower than .006 mf.

Resistive coupling is used to the first audio (6C5) tube. The plate-to-cathode return by-pass condenser must be quite large to permit super-regeneration. This condenser has no effect on the radio frequency, since it is on the low R.F. voltage side of the R.F. choke.

The super-regenerative circuit is extremely desirable for stand-by operation when receiving modulated oscillator transmitters, due to the fact that it tunes quite broadly. This is due to the fact that the detector circuit oscillates periodically over a band of frequencies often from 50 to 195 k.c. in width. As the plate or grid voltage of the super-regenerative detector is varied over wide limits, it goes in and out of oscillation at extremely high frequency, thus varying its oscillation period and resulting in the desired broad tuning.

Through the use of two stages of audio amplification sufficient volume is obtained to assure satisfactory reception under practically all conditions. The circuit shown will give excellent results even in locations where local interference is abnormally high. For earphone reception, the 6C5 tube in the output stage is very satisfactory. For loud speaker operation, a 6F6 tube is recommended. In changing from the former to the latter, cathode bias remains the same and it is simply necessary to connect the screen-grid terminal of the 6F6 tube to "B" plus.

For power supply, a six volt storage battery may be used with standard "B" batteries or for A.C. operation, the filaments may be supplied directly from a six volt transformer and the "B" supply from a "B" eliminator. Of course, a standard power supply may be constructed for this set using an 80 type rectifier. In this case, especially, care should be taken to have sufficient filtering.

The circuit above described is suitable either for five or ten meter reception. Coil constants are given with the diagram. An important feature of this receiver is the use of metal tubes throughout. These tubes, due to their inherent qualities produce superior results even in ordinary short wave sets. On ultra-short waves, the improvement over the glass tubes is still greater.

Construction Details

The set is constructed on a metal chassis 5 3/4" x 6" x 2" high. An aluminum panel 5 3/4" x 6" high is used.

The small variable condenser is mounted on a thin bakelite strip 2 3/8" above the chassis deck. This is held in place by a small right angle bracket. The coils L1 and L2 are mounted on a thin bakelite coil shelf which is held about 1 3/4" from the chassis deck by means of two pieces of bakelite tubing. The variable condenser is set back about 3" from the panel, being connected to the tuning knob or vernier dial by means of a bakelite rod. If the set is to be used interchangeably for five and ten meter reception, lugs should be soldered to the ends of coils L1 and L2 so



The Breakers

ATLANTIC CITY, NEW JERSEY
On the Boardwalk



SITUATED DIRECTLY ON THE OCEANFRONT AND CONVENIENT TO ALL PIERS AND AMUSEMENTS

\$5 WITH MEALS *Daily* WITHOUT MEALS **\$2.50**
PRIVATE BATH *Per Person* PRIVATE BATH

Hot and Cold Sea Water in all Baths

EXCELLENT FOOD

GARAGE ATTACHED

BEGIN RIGHT

with
**BLILEY
CRYSTAL
UNITS**



20-40-80-160
Meter Bands

- Type LD2—for the 40, 80, 160 meter bands. Drift under 4 cycles/megacycle/°C. \$4.80
- Type HF2—for the 20 meter band. Excellent for multiplying to 10 and 5 meters. \$7.50
- Type BC3—for the 40 and 80 meter bands. Uses a powerful X cut crystal. \$3.95

Your dealer has a copy of the 1936 Bliley catalog for you. Ask for it.

**BLILEY ELECTRIC CO.,
ERIE, PA.**

New Hammarlund Super-Pro 16-Tube

Super Heterodyne

540 to 20,000 Kc. No plug-in coils. Continuous band spread. Tuning meter. 18 watts of audio. Complete.

Write for Descriptive Circular

M & H Sporting Goods Co.
512 MARKET ST. PHILADELPHIA
1709 Atlantic Ave. Atlantic City

ECONOMY CODE MACHINE — \$12

Learn code easily, at your convenience and economically. Famous Instructograph principle. Complete with choice of 5 tapes, and Book of Instructions. Delivered postpaid anywhere in U.S.A. Send postcard for full details.

**INSTRUCTOGRAPH
COMPANY, Dept. W-5
Chicago, Ill.**

912 Lakeside Place

Please mention SHORT WAVE CRAFT when writing advertisers

that the desired coils can be fastened to three binding posts by means of locking nuts.

Having mounted the four tube sockets on the chassis and fastened the panel to the chassis, the volume control is mounted on the front chassis wall, halfway from either side. The variable condenser and coils are mounted next. The other parts are mounted beneath the chassis. Most of them can be soldered in place while the wiring is being completed. A Fahnestock clip should be attached to the top of the chassis to provide a ground connection.

The wiring can be completed in a very short time. If unaccustomed to the new metal tubes, work from a socket diagram to avoid any chance for mistakes. Naturally, all leads should be made as short and direct as possible. Use spaghetti to avoid possibility of short circuits. Be sure to mount coil L3 at least an inch from the bottom side of the chassis deck. A resistor mounting strip may be used for this purpose.

Complete List of Parts

- C1—Hammarlund Antenna Trimmer Condenser, type 1BT-70 (70 mmf.)
- C2—.1 mfd. Cornell-Dubilier Cartridge Condenser.
- C3—Hammarlund Trimmer Condenser, type MICS-70. (70 mmf.)
- C4—Hammarlund Midget Variable Condenser, type SM-15. (15 mmf.)
- C5—.00025 mfd. Cornell-Dubilier Fixed Mica Condenser.
- C6—.006 to .1 Cornell-Dubilier Cartridge Condenser.
- C7—.01 mfd. Cornell-Dubilier Cartridge Condenser.
- C8—.1 mfd. Cornell-Dubilier Cartridge Condenser.
- C9—.01 mf. Cornell-Dubilier Cartridge Condenser.
- C10—.1 mf. Cornell-Dubilier Cartridge Condenser.
- R1—600 ohm 10 watt Electrad Vitreous Enamelled Resistor.
- R2—1 meg. ½ watt I.R.C. Metallized Resistor.
- R3—170,000 ohm, ½ watt, I.R.C. Metallized Resistor.
- R4—75,000 ohm Electrad Potentiometer with Switch, type 202.
- R5—1 meg., ½ watt I.R.C. Metallized Resistor.
- R6—1000 ohm, ½ watt I.R.C. Metallized Resistor.
- R7—170,000 ohm, ½ watt I.R.C. Metallized Resistor.
- R8—1 meg., ½ watt, I.R.C. Metallized Resistor.
- R9—1000 ohm, 10 watt Electrad Vitreous Enamelled Resistor.
- RFC—1 Hammarlund Midget R.F. Choke, type CH-X. (2.1 mh.)
- RFC—2 Hammarlund Midget R.F. Choke, type CH-X.
- L1—See Winding Directions.
- L2—See Winding Directions.
- L3—Hammarlund Midget R.F. Choke, type CH-X.
- J1 and J2—Earphone Jacks.
- BP1—Ground Post.
- V1—Tube, type 6K7 R.C.A. Radiotron.
- V2—Tube, type 6J7, R.C.A. Radiotron.
- V3—Tube, type 6C5, R.C.A. Radiotron.
- V4—Tube, type 6C5 or 6F6 R.C.A. Radiotron.
- 1—Calibrated Dial, I.C.A.
- 1—Bakelite Pointer Knob, I.C.A.
- 1—Small Knob for Volume Control.
- 1—Metal Chassis, Blan, 5 ¾" x 6" x 2" high.
- 1—Blan Aluminum Panel, 5 ¾" by 6" high.
- 1—Bakelite Strip, 1/8" thick, 3 ½" x ¾" for mounting L1, L2.
- 1—Bakelite Strip, 1/8" thick, 2 ¾" x ¾" for mounting variable condenser.
- 1—Bakelite Rod Shaft Extension.
- 2—Pieces of Bakelite Tubing, 1 ¼" high for coil shelf.
- 2—Metal Tube type Screen Grid Clips.

Girl Operators, Attention!

Listen "YL's" and "XYL's"! Why not send the Editor a good photo of your "Rig"—and don't forget yourself. A separate photo of yourself will do, with a "clear" photo of that station! \$5.00 for best "YL" photo.—Editor. See page 649 March issue for details.

**IT'S HERE
hallicrafters
ULTRA SKYRIDER**

5-10 METERS ☆
ACTUALLY 3.9 TO 46 METERS



**THE ULTRA HIGH
FREQUENCY JOB YOU'VE
BEEN WAITING FOR ●**

**A M A Z I N G
F E A T U R E S**

After months of work and experiment, the Hallicrafter engineers are finally satisfied. The Ultra Skyrider is complete—an entirely new approach to ultra high frequency reception. It's a super-sensitive Superheterodyne, with the new Lamb Noise Silencer to reduce the man-made noises so annoying at high frequencies. This new device, described in Q. S. T. will ensure practically noise-free reception.

The Ultra Skyrider fulfills the amateurs dream for 5-10 meter reception—it tunes up to 46 meters with the same high efficiency. In spite of its advantages, it's extremely moderate in price.

The Ultra Skyrider is the finest Hallicrafter product to date with more exclusive features than we can list here—you've got to see it and operate it for full appreciation of its marvelous efficiency.


See the new Ultra Skyrider at your jobbers on April 20, or write for full particulars now.

- Fractional Micro-Volt Sensitivity
- 3.6 to 46 meters tuning on 4 bands
- Lamb Noise Silencer, first time used on any commercial receiver, cuts out 60% of the noise prevalent on ultra high frequency bands.
- No Plug-In Coils
- Individual Coils for each band
- 10 All-Metal Tubes
- Generous Isolantite and Steatite Insulator
- Continuous Electro-Mechanical Band Dial
- Antenna Compensator
- Moderate Price

the hallicrafters

THE HALLICRAFTERS, INC.

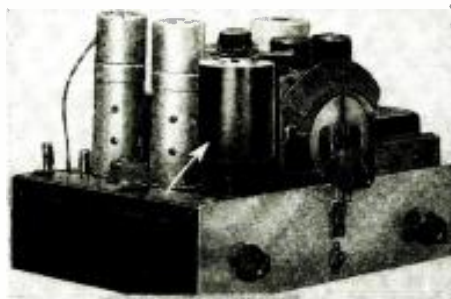3001-U Southport Ave., Chicago, Ill.—Cable Address LIKEX, New York City



ARROW POINTS TO UNO ALL-WAVE COIL.

AT LAST!
The dream of millions has been
REALIZED

This unit alone will take the place of *all the necessary coils required to cover all amateur bands.*

No switches, no soldering and no alteration to your present receiver is required to make use of this unit.

ECONOMICAL — EFFICIENT — ATTRACTIVE

We guarantee satisfactory performance or your money will be refunded by your dealer. Write for our circular, "How to use it and how it works." **\$10.00**

UNO ALL-WAVE COIL CO. Discounts to Amateurs and Experimenters
11 Mollineaux Place Dept. S-5 Roosevelt, N. Y., U. S. A.

Please mention SHORT WAVE CRAFT when writing advertisers

TRY SPRAGUES

and note the difference

DON'T MISS THIS!

Hot off the press comes the new 1936 Sprague Catalog brimful of new condensers, new ideas, new low prices, new service helps. Write for yours today! Save time by making duplicate replacements the Sprague Way! Get the new dope on Interference Elimination! See the complete new line of 450 volt condensers—the finest ever! Learn about the new Sprague mounting flange—and countless other features you can't afford to miss!

Remember: No need to check surges when you use Sprague's. You know they're right.

SPRAGUE PRODUCTS CO.
North Adams, Mass.

SPRAGUE 600 LINE CONDENSERS

AMERICA'S FINEST LINE OF QUALITY UNITS

A Modern 5-Meter Transmitter

(Continued from page 15)

Coils

The R. F. unit is as simple as possible. The oscillator grid coil is wound on an isolantite form, with a clip for changing the cathode tap. The grid condenser and leak are mounted on the top of the coil form. The coils between the 89 oscillator and 89 buffers are mounted on 1" feed through insulators, with the plate coil on the outside. The tuning condenser for the plate coil is directly under it, beneath the chassis.

The coils for the plates of the 89 buffers and the 801 grids are under the chassis and are mounted on a victron strip for efficient insulation. The buffer plate tuning condenser is at the rear of the chassis. It is made by cutting the rear bearing and one rotor and stator plate from a standard 35 mmf. double spaced unit. It would probably be better to move it forward about an inch or more, thus shortening the leads, and there would be no need to cut it up.

The 801 tank condenser is a double-spaced, split-stator unit and is mounted directly under its respective coil. A strip of Victron was placed under it since some of the screws came very near to the steel chassis wall. All the condensers are coupled by Insulex flexible couplings and 1/4" bakelite rods to the knobs. These turn very easily and there is no hand capacity whatsoever.

Neutralizing and By-pass Condensers

The neutralizing condensers are 35 mmf. double spaced Star units. Since this capacity was rather high, they are cut down to 4 stator and 3 rotor plates and are both mounted on a 6" x 1" Victron strip supported on bushings. The neutralizing connections to the 801 sockets are all made above the chassis.

All by-pass condensers in the set are mounted as close to their respective elements as possible, and the ground ends fastened to a piece of No. 12 wire which runs all the way across the chassis in the rear. All other ground connections are, of course, made to the same wire.

When ready to put the outfit into operation, the power supply should first be checked for correct voltages, then all heater and filament circuits should be tested. Set the C bias voltage divider at about the values mentioned previously and check to see that the voltage arrives intact at the grid terminals. It is a good plan to remove the filter input condenser when first trying out the set, as this drops the voltage somewhat.

Tuning Up!

Since the procedure of tuning is exactly the same as in other M.O.P.A. jobs, it will be necessary to go into it but briefly. The oscillator grid condenser should be set about mid scale and the cathode tap at about the 4th turn from the bottom. Then rotate the plate condenser until a large dip occurs in the oscillator plate current. Next tune the buffer plate condenser till the buffer plate current drops sharply. The plate voltage to the 801's should not be connected for this preliminary tuning. Next comes neutralization, which, contrary to expectations, proved to be exceptionally easy. A one-turn loop of insulated wire with a flashlight bulb across it is placed in inductive relation to the plate tank of the 801's and the two neutralizing condensers turned until no setting of the plate tank condenser or of the buffer plate condenser will cause a glow. This point should occur when the neutralizing condensers are about 2/3 open. The plate voltage to the P. A. may now be put on and its plate condenser, and also the other 2 plate condensers tuned for maximum grid current and minimum plate current. Next the antenna should be clipped on and the set tuned to resonance with the plate current on the final amplifier standing at about 100 to 130 ma. For those who want a rough check of cur-

ONE TUBE RADIO ONLY \$1.25 POST PAID

1 TUBE KIT

Have you always wanted a Real Powerful Radio Receiver all your own? A Short and Long Wave set that will actually bring in many foreign stations from all parts of the World. Police calls, airplanes, amateurs, etc., as well as your local stations. ACE Radios give GUARANTEED RESULTS! Thousands now in use. Amazing performance!

Now, the world famous ACE Construction Kits are priced so low that anyone can afford one! For only \$1.25 we send you, postpaid, every part needed to build a powerful one tube receiver with heavy, attractive metal chassis. Not a feeble crystal set! Works on two inexpensive dry batteries. Later, you can change your set into the Two Tube Battery or All-Electric set at special low cost! You get a valuable radio education by wiring it yourself from our clear diagrams. It's easy for even a child! Just a few simple connections. Wavelength range 15 to 600 meters. For more power and volume buy the TWO TUBE receiver Kit—Not wired. Less tubes, Batteries and Phones. \$2.00

ALL ELECTRIC Two tube house current set. No battery needed. Complete construction kit. Not wired. Less Tubes and Kits wired—75c extra. \$3.00

ORDER NOW! Not a toy or an attachment!!

ACE RADIO LABORATORIES
1619 Broadway Dept. C-5 New York City

MYSTIC EYE TUNING UNIT

Will operate on any set with A.V.C. Install it yourself in five minutes!

When signal is strongest the aperture closes, insuring VISUAL hairline tuning as in the highest priced receivers.

This is a COMPLETE unit with new cathode ray tube, 1 meg. resistor, special socket and mounting bracket, 24" of 5 wire cable, and attractive panel escutcheon.

Modernize Your Receiver!

Specify 2 1/2 or 6 volt tube. \$2.97

Send your order now. Postage Prepaid.....

COMMONWEALTH PRODUCTS COMPANY
819 N. Michigan Blvd. Chicago, Ill.

Mail us your order for the world's most reliable and accurate Balancing or Grid Condenser

X L VARIO DENSER in 4 ranges

Mod. N. Cap. 1.2 to 20 MMF
Mod. G1. Cap. 20 to 100 MMF
Mod. G5. Cap. 100 to 500 MMF
Mod. G10. Cap. 500 to 1000 MMF

and the **XL PUSH POST** (best spring type Binding Post)

Mod. N \$1.00 ea.
Mod. G \$1.50 ea.

Non-Corrosive—Navy Type—Bat. Top 20c ea.
Type B1 (Aluminum Base. Bakelite Insulated Top) 15c.
Type M (All Aluminum Body) at 10c each.
For quick connections and positive contact at all times.

X. L. RADIO LABORATORIES
Dept. S.W. S. 1224 Belmont Ave., Chicago, USA.

MORE IS EXPECTED OF... TRIMM Featherweight HEADSETS

There is a definite reason why most discriminating amateurs prefer them.

Write for information.

TRIMM
Radio Manufacturing Co.
1770 W. Berteau Av. Chicago

You cannot make a better investment than to have in your home a **GOLD SHIELD PROFESSIONAL MODEL Carbon Sun Lamp SAVES DOCTOR'S BILLS**

Everyone in your family needs the health giving VIOLET RAYS. This is a large CHROMICUM plated lamp using standard carbons, emitting rays of ultra violet and infra red.

Complete with screen and goggles... \$7.50

WONDERFUL VALUE!
Gold Shield Products Co.
17 W. 60th St. N. Y. City

Size 18" high, 7" wide, 5" deep. Weight 12 pounds.

UNCONDITIONAL GUARANTEE ON ALL OUR RADIO SUPPLIES

UNCLE DAVE'S RADIO SHACK

336 BROADWAY-ALBANY, N. Y., U.S.A.

PEERLESS 3-TUBE HIGH GAIN AMPLIFIER
3 1/2 watts output . . . 5 watts peak . . . 75 DB gain
Field supply for 2500 ohm speaker . . . high impedance input . . . uses 57, 2A5 and 80 tubes
microphone and tubes . . . 3-tube amplifier . . . less speaker . . . \$3.20

SPEAKER with matching xformer for above . . . \$1.40

MICROPHONE, double button, for above . . . 3.75

KIT of 3 matched tubes for above . . . 1.40

DONGAN POWER TRANSFORMERS

1400 v. (T-16) ma—2 1/2 @ 3a; 2 1/2 @ 5a . . . 2.35
1000 v. (T-150) ma—7 1/2 @ 3a; 2 1/2 @ 5a . . . 1.85

PEERLESS 1-Tube Breadboard Power Supply 250 volt DC . . . 2 1/2 volt @ 5a, less tube . . . 2.95

Cable Address "UncleDave"
Long Distance Phone 4-5746
Include 20% deposit with e.o.d. orders
Prices F.O.B. Albany Foreign Trade Solicited
Send for new Ham Catalogue—just out!

Please mention SHORT WAVE CRAFT when writing advertisers

rents, the following are approximately correct for 550V. on the P. A., 500 on the 89's and no load; oscillator plate, 35 ma.; buffer plates, 60 ma.; P. A. plate 50 ma.; and P. A. grid, 10 ma. This holds true for bias voltages as given. On load, the final amp. plate current will rise to about 100 to 130 ma.

Results!

Now for results. About 50 contacts have been made since the outfit was completed. Invariably, the more distant stations gave better reports than with the old transmitter. The signals are more steady, sharper, and there is virtually no drift. Also, the tone quality is almost always commented upon as being improved. The best DX to date is W1AVV and W1EER, who are about 40 miles away and who give reports up to R7 and 8 depending upon conditions.

So here you have a strictly modern transmitter, fitted to work in our increasingly crowded 5 meter bands. Why not build one and give yourself and the "5 meter gang" a real break?

List of Parts

- 3—Hammarlund 6 prong isolantite sockets
 - 2—Hammarlund 4 prong isolantite sockets
 - 1—Hammarlund 5 prong isolantite socket
 - 1—Hammarlund 5 prong isolantite coil form
 - 1—Hammarlund double spaced split stator condenser
 - 1—Hammarlund 50 mmf. midget condenser
 - 2—Hammarlund 25 mmf. double spaced midget condenser
 - 2—Hammarlund "Star" double spaced midget condenser (35 mmf.)
 - 1—300 Ma. meter*
 - 1—150 Ma. meter
 - 1—100 Ma. meter
 - 1—25 Ma. meter
 - 2—R.C.A. 801's
 - 3—R.C.A. 89's
 - 1—R.C.A. 523
 - 1—R.C.A. 80
 - 6—Pilot lamps with sockets
 - 12—I.C.A. name plates
 - 4—I.C.A. 2" dials with knobs
 - 4—I.C.A. insulex flexible couplings
 - 2—I.C.A. 5 post terminal strips
 - 1—I.C.A. 7 prong plug and socket
 - 1—4-pole double throw switch
 - 1—I.C.A. SPST switch
 - 1—I.C.A. DPDT switch
 - 3—I.C.A. grid clips
 - 2—I.C.A. 4-prong sockets
 - 10—I.C.A. 1" feed through insulators
 - 3—strips Victron 1" x 6" x 1/8"
 - 3—Aerovox 2 mf. 1000 V. condensers
 - 10—Aerovox .0001 mf. 1000 V. mica condensers
 - 4—Aerovox .001 mf. 400 V. mica condensers
 - 1—Aerovox dual 8 mf. electrolytic (wire leads)
 - 1—Aerovox 50,000 ohm 75 W. wire resistor
 - 1—Aerovox 5000 ohm 50 W. wire resistor
 - 2—Aerovox 50,000 ohm 10 W. wire resistor
 - 1—Aerovox 75,000 ohm 1 W. carbon resistor
 - 2 feet 7 wire cable
 - 1—Power transformer, Thordarson
 - 1—250 ma. choke, Thordarson
 - 1—midget transformer, Thordarson (200 V., D.C.)
 - 1—midget choke, Thordarson (30H.)
 - 1—120 ma. 30H. choke, Thordarson
 - 2—8" x 12" steel chassis
 - 1—rack
- Wire, hardware, etc. (*Triplett meters specified.)

When To Listen In

(Continued from page 32)

MOSCOW

The short wave programmes from Russia now take place exclusively on 25 meters. From March 1 50 meters was closed for the summer. The schedule is as follows. Daily (and Sun.) 12:30-1:30 and 3-6 p.m. Also 6-7 a.m. on Wednesdays and 6-9, 10-11 a.m. and 9-10 p.m. on Sundays. RNE is being heard fairly well from 4-6 p.m. and on Sunday from 9-10 p.m. Broadcasts in English occur on Sundays, Mondays, Wednesdays and Fridays from 4-5 p.m. Also on Wednesdays from 6-7 a.m. and on Sundays from 10-11 a.m.

CHINA

XGO at Nanking now broadcasts news, etc. daily at 12 noon on 7.53 mc. CQN at Macao, Portuguese China, formerly of the 49 meter band is now on 9.525 mc. (31.49 m.) on Mondays and Fridays from 7-8:30 a.m.

"Police Call" list, greatly enlarged, will appear in the June number.

EVEREADY PLUG-IN RADIO BATTERIES



Simplifies Battery Connections. Socket firmly embedded in the battery seal. Can't come loose.

Adapter furnished with each battery. Connect up once to adapter. When replacing batteries, remove adapter from old battery and place in socket of new battery. Prevents mistakes in connecting up.

"Sealed Socket" construction now available on all popular types of Eveready "B" and "C" batteries.


Headquarters for Battery Information

NATIONAL CARBON COMPANY, INC.

General Offices: New York, N.Y. • Branches: Chicago, San Francisco



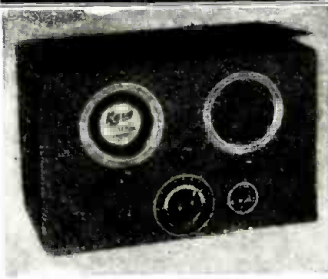Unit of Union Carbide and Carbon Corporation



HAYNES R-S-R- 5-TUBE RECEIVER

2 1/2-555 METERS

Regeneration plus super-regeneration

Combined for the first time in a single A.C.-D.C. receiver having the greatest tuning range ever incorporated in one set. A. J. Haynes, who designed the first regenerative kit (1922) and the first superheterodyne kit set (1924) chose RACO to build the final model of his new R-S-R receiver—another first AND DOES IT PERFORM! The R-S-R is not only a remarkably fine DX receiver for all of the short wave and broadcast bands but it is the smoothest super-regenerator we have ever seen, giving exceptionally efficient reception on the 5 and 10 meter bands.

Complete Kit, unwired, including dynamic speaker, power supply and wired switch-coil assembly (less cabinet and tubes)..... **\$14.95** Complete R-S-R set, with 5 tubes (2-MG-6K7-1 MG 43, 1 MG-25Z5, 1-76), matched dynamic speaker, cabinet, all wired and laboratory tested. READY TO PLUG IN AND OPERATE..... **\$24.65**

**RADIO CONSTRUCTORS
LABORATORIES**



**136 LIBERTY ST., N. Y. C.
DEPT. H-1 EXPORT DEPT. 105 Hudson St.**

Please mention SHORT WAVE CRAFT when writing advertisers

Pilot

ALL-WAVE RADIO SUPER-DRAGON

MODEL XI14

The newest all-wave Pilot radio of the long line of Super Dragon and Super Wasp models, used in 92 countries of the world for extreme DX on short waves and broadcast. Described in the Pilot 1936 circular, sent on request.

PILOT CLIPPER

MODEL 364

Pilot's high-power, metal-tube, all-wave model, with 12 tubes including the Tuning Beacon. This set has unlimited receiving range and power such as you have never experienced. Specially designed for doublet antenna. Write for descriptive circular.



"The Standard of Excellence"

Radio Builders Since 1908

PILOT RADIO CORPORATION

3701-36th St., Long Island City, N. Y.

"RESONANT LINE" TRANSMITTER KITS

56-60 Megacycles



BETTER QSO's—Less frequency modulation. Better coverage with less interference. All parts designed for highest efficiency.

Deluxe Model—All components finished in chromium and black. Complete kit of oscillator parts, less tubes.

Standard Model—Equally efficient as Deluxe but finished in natural color throughout. All oscillator parts complete, less tubes.

Ask your Jobber or dealer. If they cannot supply it, write for catalog and full information.

American Radio Hardware Co., Inc.
Dept. S-5, 476 Broadway, New York City, N. Y.
(Manufacturers of quality products since 1923)

High Frequency Superhet

(Continued from page 9)

in greater simplicity, ease of construction and lower cost. NOTE: (The base on the model receiver is drilled to accommodate a separate high frequency oscillator and 2,000 kc. I.F. transformers when they are available.)

The second detector uses a 6F6 pentode with the grid and screen tied together, causing the tube to function as a hi mu triode. The absence of a cathode resistor in this circuit causes the tube to draw grid current through the grid resistor network when a signal is received. This rectified grid current is fed to the grids of the I.F. amplifier through the filter network shown. This prevents overloading of the second detector and provides automatic volume control.

The output stage is a 6F6 connected as a pentode and coupled to the speaker through the socket provided in the receiver base. The speaker is a 6-inch dynamic with a 2,500-ohm field, the field being a part of the filter system. The speaker should be mounted on a baffle board two or three feet square for good fidelity.

Directions for Building Receiver

Drill the chassis and mount all tube sockets, transformers, resistors and condensers as shown in the picture.

Connect the high voltage leads of the power transformer, one to each plate of the 80 tube socket; the plate connections being the contacts in which the smaller pins of the tube fit.

To the two larger terminals of this socket connect the 5-volt winding of the power transformer.

One end of the 6.3 volt winding connects to terminal 2 of each of the other tubes; the other end of the winding connecting terminal 7 of all of the other tubes. These connections should be made with twisted insulated wire.

Attach 110 volt cord with switch, which is a part of the volume control, in series. From the center tap of the high voltage winding connect a lead to the chassis at the nearest point.

From one side of the 5-volt winding a wire is run to the choke coil and the other end of this choke coil connects to the field winding of the loud speaker. The other side of the field winding supplies all of the high voltage to the receiver and will be referred to hereafter as point X.

The red lead of one of the 8 mfd. electrolytic condensers is attached to the wire which connects the choke coil with the filament wire or the lead which connects

to the 5-volt winding of the power transformer. The other end of choke coil connects to one terminal of the loud speaker field coil and to the red lead of another electrolytic condenser. The other lead from this field coil being connected to the red lead of the third electrolytic condenser and is terminated on a small insulator designated as point X.

Both black leads of the electrolytic condensers are attached to the chassis.

Coils L-1 and L-2 are mounted, one on each of the C-1 (variable) condensers. The end of coil L-1 which connects to the stator plates of front C-1 connects to the grid cap on top of the 6K7 tube which is mounted toward the front of the chassis.

The other end of this coil is mounted to the chassis.

From terminal 8 of this first tube, connect one end of a 400-ohm resistor; the other end of this resistor connects with one end of a 350-ohm resistor and also is attached to terminal 8 of the other two 6K7 tube sockets. The other end of this 350-ohm resistor is attached to the chassis as is one end of a .01 condenser; the other wire from this condenser going to terminal 8 of this first 6K7 tube.

The number 4 terminals of all of the 6K7 tubes are connected together and attached to the high voltage lead of the speaker field, or point X, through a 15,000-ohm resistor and a 20,000-ohm is connected from terminal 4 to ground.

Terminals 5 of the 6K7 tubes are connected to the number 8 terminals of their respective tube sockets.


From terminal number 3 of the first 6K7 socket attach R.F. C-1 and C-2. The other end of R.F. C-1 connects to point X. The other terminal of C-2 is attached to the tap on L-2. The end of L-2 which is attached to the stator connection of the rear C-1 goes to one end of a .25 megohm resistor and to one terminal of C-3.

The other end of this resistor and the other terminal of this condenser is attached to the grid connection on top of the 6J7 tube.

The end of L-2 which is connected with the rotor plates of rear C-1 is grounded to the chassis and runs to R.F. C-2; the other end of R.F. C-2 being connected to terminal 8 of the 6J7 tube.

Terminal 4 of the 6J7 tube is connected to the middle terminal of the 50,000-ohm potentiometer and also has a .1 mf. condenser connected between it and ground; the ground in all cases being the chassis.

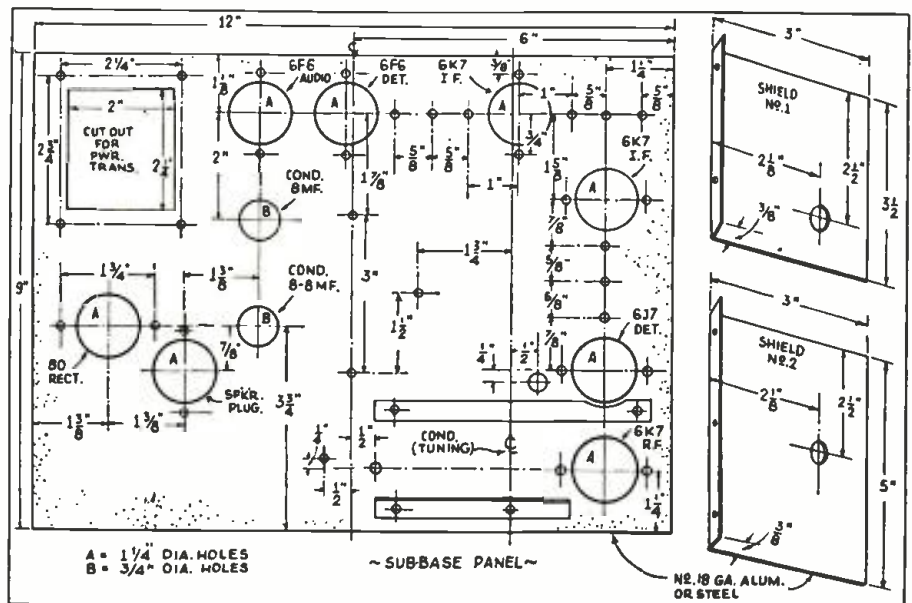From terminal 3 of the 6J7 tube, connect one end of one 100,000-ohm resistor



Details of Superhet Chassis

Please mention SHORT WAVE CRAFT when writing advertisers

and one terminal of .0001 mf. condenser. From the other end of the 100,000-ohm resistor a .5 mf. condenser is attached to ground and also one end of a 10,000-ohm resistor, the other end of which connects with point X. The other end of this condenser connects to the grid cap on top of the second 6K7 tube and also to one end of a 250,000-ohm resistor. The other end of this resistor connects to another 250,000-ohm resistor and these in turn connect to a third 250,000-ohm resistor. The points where each of these three resistors connect with each other are also attached to the bottom end of the respective 250,000-ohm grid resistors.

From terminal 3 of the second 6K7 socket connect one end of a 50,000-ohm resistor and also one terminal of a .0001 mf. condenser; the other end of this resistor going to point X.

The grid connection on top of the third 6K7 tube connects with the other terminals of this .0001 mf. condenser and one end of a 250,000-ohm resistor.

From terminal 3 of the third 6K7 tube, connect one end of another 50,000-ohm resistor and one terminal of another .0001 mf. condenser; the other end of this resistor being connected to point X.

From the other end of this .0001 mf. condenser, run a wire to terminals 4 and 5 of the first 6F6 tube.

One end of a 250,000-ohm resistor is connected to terminal 3 of the 6F6 tube and one end of a .01 mf. condenser. The other end of this 250,000-ohm resistor goes to point X.

The other terminal on the .01 mf. condenser is connected with the outside terminal on the 500,000-ohm volume control; the center terminal of this volume control is connected with terminal 5 on the second 6F6 tube socket; the remaining connection on the volume control going to ground.

From terminal 3 of the last 6F6 tube a lead is run to one terminal on the transformer which is mounted on the loud-speaker; the other terminal of this transformer being connected to terminal 4 of the last 6F6 tube and point X, connections being made by means of the tube socket provided for loud-speaker plug.

Connect a 500-ohm resistor between terminal 8 on the last 6F6 socket and ground. Attach the red wire from a 10 mf. electrolytic condenser to terminal 8 of the last 6F6 socket; the black wire being connected to ground.


One end of the 50,000-ohm potentiometer referred to earlier, connects to ground; the other terminal having a 100,000-ohm resistor in series with it and point X. Terminal No. 1 on each of the tube sockets is attached to ground (chassis) at the nearest point.

Directions for Building the 10-Meter Converter..

(Continued from page 8)

of the other 8 mf. electrolytic condensers. The black wires on both of these condensers are attached to the chassis.

Coil L-1 which consists of six turns of No. 10 copper wire wound to occupy a space of one inch is three-quarters of an inch in diameter. It is mounted upon the small standoff insulators on top of the chassis as shown. From the end of the coil nearest the front of the chassis, a wire one and three-quarter inches in length is connected to the rotor plates of the front section of the tuning condenser (C-1). The other end of this coil is connected by means of a wire one and one-quarter inches in length to the stator plates of this same condenser and also to the grid cap on top of the 6L7 tube which is mounted to the left of this coil. Also from this same end of the coil the wire is attached to one terminal of a 35 mmf. adjustable condenser. The other terminal of this condenser being connected to the antenna terminal. Also from the end of (Continued on page 47)

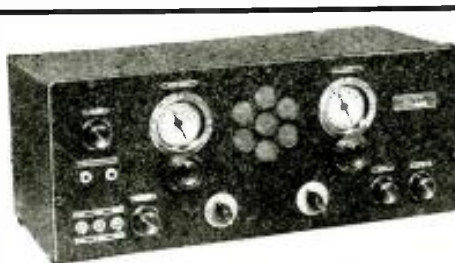

Sargent Model 12

TUNING RANGE. Eight wave bands giving continuous tuning from 15 to 9000 meters without skips or dead spots. Highest I.C. ratio, maximum sensitivity, on 18, 21, 36 and 600 meter ship bands.

MAIN TUNING DIAL. Calibrated in M.C. from 15 to 200 meters, in K.C. from 200 to 9000 meters. Shaded areas mark short wave ship bands.

BAND SPREADER. Uses Sargent mechanical band spreader. This dial is calibrated in M.C. for 18, 21, 36, 48 and 54 meter ship bands.

VARIABLE ANTENNA COUPLING. Variable in 5 steps to match differing interference conditions, wavelengths, etc.

ANCHOR GAP. Located right at the antenna input to the receiver. This gap protects the set against lightning and heavy static.

TWO AUDIO JACKS. Jacks located in first and second audio stages.

AUDIO GAIN CONTROL. Can be set to limit the background noise to suit receiving conditions.

POWER SUPPLY. Heaters wired in parallel for operation from 6 volt supply. "B" supply

Marine Type Communication Receiver

15 to 9000 Meters

from 110 volt ship's lines or auxiliary B Batteries. Toggle switch makes the change. Both sides of line filtered, can be used on lines having positive, negative or neutral ground. For operation ashore, A.C. power pack (separate unit) supplies all voltages. **CIRCUIT.** Tuned R.F. type circuit with regenerative detector. Complete isolation, careful shielding make for high stability and extremely low noise level.

OTHER CONTROLS. R.F. Gain control, Regeneration, R.F. Trimmer, Speaker ON-OFF Switch, Power Switch.

BREAK-IN CONNECTIONS. Terminals in the rear for connection to break-in relay. With contacts open, R.F. biased to cut-off, detector undisturbed permits monitoring own transmission and gives break-in without lag.

CABINET DESIGN. New "tray type" construction permits immediate accessibility for tube changing or servicing. Remove 5 thumb screws and panel and chassis can be drawn out the front of the cabinet, with power connections undisturbed.

Sargent Model 12 has been most thoroughly engineered with exhaustive tests at sea under actual operating conditions on both Atlantic and Pacific coasts. The final design is, without question, the nearest to an ideal receiver that can be developed for work aboard ship. It is built to standards upon which human lives can depend.

Write for complete description and prices. E. M. Sargent Co., 212 9th St., Oakland, Calif.

SPRAYER OUTFIT

ELECTRICAL—PORTABLE **\$32.50** Complete with Gun, ready for Service



This is the ideal Outfit for all around spraying work wherever Current is available. Sprays everything: Lacquers, Oil, Cold Water Paints, Enamels, Varnish, Insecticides, Disinfectants, Shoe Dyes, etc. The Unit is compact, completely self-contained.

Ideal for spraying Furniture, Radiators, Screens, Machinery, and other maintenance paintings in Homes, Schools, Clubs, Hospitals, Stores, Factories, and office Buildings.

The Gun furnished with this Unit is of Pressure Cup type; requires but 2 cu. ft. of Air per minute. Has Bleeder type construction which assures uniform pressure at all times without clogging the Air Passage which is easily cleaned. Furnished with 3 Nozzles which produce Fan, Round, and Right Angle Spray respectively.

Complete Unit consists of Air-cooled Compressor with machined Fan-cooling Pulley, V-Belt Drive; Pressure type Gun with 1 quart Aluminum Paint Cup; 3 Tips; ¼ H.P., Heavy Duty Motor, 110/120 volt, 60 cycle, AC; 15 ft. rubber covered 2 Ply Air Hose; 8 ft. Cord & Plug; Filter Tank; Entire Unit mounted on Base with Ball Bearing Casters.

A low priced Power Sprayer; the kind of Machine that usually sells for \$50.00 to \$60.00.

Price of complete outfit, shipping weight, 60 lbs.	\$32.50
Price of outfit complete, less Motor, shipping weight—35 lbs.	\$25.50
Price of Gun only with 3 nozzles, shipping weight, 7 lbs.	\$7.50
Price of Compressor only, shipping weight 15 lbs.	\$9.50

Our Old Customers Know That Our Merchandise Is Sold on a Strict Money-Back Guarantee

All Shipments will be forwarded by Express Collect if not sufficient postage included with your order.

WELLWORTH TRADING CO.

560 W. Washington Bd. Dept. SW-536, Chicago, Ill

• MORE HARRISON VALUES! — FILTER CONDENSERS —

FARADON 5½ Mfd. Filter Condensers. 4 Mfd. 600 volt and 1½ Mfd. 800 volt DC working. In a neat fibre case. Every one tested at 2000 volts! A real buy! 600 each. Four for \$1.75.

TOBE oil filter condensers. 2000 volt working. Tested at 6000 volts. 1 Mfd.—\$1.70. 2 Mfd.—\$2.50.

Mini Condensers
Most sizes from .00005 up—10c each. .01—27c. Carbon Resistors. Any value. Color coded. ¼, ½, or 1 Watt—65c per doz. 2 Watt—10c each.

THORDARSON Plate Transformer. Type T-2385. Conservatively rated at 100 watts. Delivers 750-550-0-550-750 volts AC. List price \$14.00.

Our Special Price—\$2.95.
Thordarson filament transformer for 50 watters. Delivers 10 volts at 4 Amps with heavy duty contact rheostat. Complete \$1.10.

Jefferson 2½ volt, 12 Amp. (T for 866's. 7500 volt insulation. Excellent value at only \$1.18.

RELAYS: Excellent for keying, remote control, etc. Work on one dry cell. Good silver contacts. Fast action; Midget size. Breaks two and makes one contact. 30c. Larger size. Enclosed in metal case with slip cover. Bakelite terminal panel. Spring tension adjustment. Two pole, double throw—65c.

Samson 85 millihenry RF chokes. 11c, uncased. In neat bakelite case with terminal lugs—27c.
DUOVAC 295-D. A well known tube similar in rating to the 216. Rated plate dissipation 20 watts. Regular price \$1.50. Harrison Special—89c.

Good grade 48's. FB for Xmitting. Three for \$1.00. Heavy Duty 866 mercury vapor rectifiers. FB Value! 96c. Heavy Duty 70's. Home built. Large plate. Extra heavy internal supports and insulation. Every tube tested on high voltage before shipment. Excellent value at only \$1.15.

Columbia 250 tubes. Fully guaranteed. Special—55c.
VALPEY CRYSTALS—Good, powerful oscillators! X Cut. Accuracy to better than .03%. Fully guaranteed. Mounted in dustproof plug-in bakelite holder.

160, 80 or 40 meter band. \$3.00
Unmounted 160 or 80 meter bands—\$1.50
(From stock, within 10 KC)

New Hill all brass adjustable holder. Really one of the best holders made. Will increase output of any xtal! \$1.65.

160 or 80 meter AT CUT Crystals. Very low drift! \$2.75

SEND YOUR MAIL ORDER TODAY!—OR VISIT OUR NEW LARGE STORE!!

(See our Receiver Catalog Advertisement on page 39)
OUR QSL CARD PUTS YOUR NAME ON OUR FREE MAILING LIST FOR OUR "HAM BULLETIN"
SEND IT TODAY, OMI!

HARRISON RADIO COMPANY

12 West Broadway-C5-New York City

Send today for your copy of new 16-page booklet crammed full of valuable and vital information on

"AERIALS AND HOW TO USE THEM"

Contains diagrams and complete information for eliminating noise on all bands, improving foreign reception, use of antenna couplers, balanced line filters, ultra high frequency transmission and reception, ham operation, and multiple installations for apartment houses and store demonstration hook-ups.

Sent postpaid for a dime

Arthur M. Lynch, Inc., Dept. S, 227 Fulton St., N.Y.C.

RADIO INSTRUCTION

THE PERFECT CODE TEACHER! NEW MASTER TELEPLEX

For beginners, experienced operators, and schoolroom. The sure easy way to learn code and to step up your speed. This amazing new instrument will record your own sending on double row perforated paper and repeat it back to you at any speed you desire. 10,000 words can be recorded on one tape.

**NO BATTERIES
NO WINDING
ALL ELECTRIC**

**BUY IT OR
RENT IT**

It is the same in principle and in operation as equal to the Wheatstone Perforator and Transmitter, which cost over \$1,000.

Send for Folder \$5 which tells you how to get the use of this instrument without buying it. No obligation. We furnish complete course and personal instruction with a money back guarantee. Low cost, easy terms. Write today for information.

TELEPLEX CO.

72 Cortland St. New York City
The New Master Teleplex—"The Choice of Those Who Know"

INSTRUCTOGRAPH

**THE PRACTICAL
CODE TEACHER**

Radio Or Morse

It's easy to learn code with this sturdy, well-made machine. Book of Instructions shows you how to study to best advantage; you practice at your convenience, and at the speed you want. For Rent—on attractive terms. Rental paid may be applied toward purchase price if desired. For Sale—cash or terms. A descriptive folder and price list are yours for the asking—no obligation. Just send post-card to—



INSTRUCTOGRAPH COMPANY, Dept. SW-5
912 Lakeside Place, Chicago, Ill.
Canadian Representatives
Radio College of Canada, Ltd., 863 Bay St. Toronto

RADIO ENGINEERING



RCA Institutes offers an intensive course of high standard embracing all phases of Radio. Practical training with modern equipment at New York and Chicago schools. Also specialized courses and Home Study Courses under "No obligation" plan. Catalog, Dept. SW-36.

RCA INSTITUTES, Inc.

76 Verick St., New York. 1154 Merchandise Mart, Chicago
Recognized Standard in Radio Instruction Since 1909

RADIO ENGINEERING,

broadcasting, aviation and police radio, servicing, marine radio telegraphy and telephony, Morse telegraphy and railway accounting taught thoroughly. Engineering course of nine months' duration equivalent to three years of college radio work. All expenses low. Catalog free. School established 1874.
Dodge's Institute, Turner St., Valparaiso, Ind.

RADIO biggest opportunities still ahead

ALMOST in a decade radio has become a giant industry. The opportunities created will be enjoyed by trained men. The International Correspondence Schools Radio Course, prepared by leading authorities and constantly revised, will make you a trained man! A fascinating book—free.

INTERNATIONAL CORRESPONDENCE SCHOOLS

Box 2881-C, Scranton, Penna.
Send me—free—information on subject checked:
 Radio
 Radio Operator
 Radio Service Man
 Electrical Engineer

Name.....
Address.....

Radio Amateur Course

(Continued from page 27)

previously, employing receiving type tubes, this method would be entirely too complicated and the advantages would probably be slight. It is only in the last buffer or between the last buffer and the final amplifier stages where this method is really a distinct advantage.


In Fig. 9 we have the same circuit except that we use two tubes in push-pull. In this case, one link coil is coupled to the B plus end of the driver tube, and the other coupled to the center of the grid tuned circuit, while in Fig. 8, both coupling coils were coupled to the low potential end of the tuned circuits. The push-pull circuit, of course, is not suited for frequency doubling although it is recommended for tripling. However, frequency tripling is not commonly used in the amateur bands.

We can also obtain frequency multiplication with a single tube in another manner as shown in Fig. 10. This is the twin triode type tube, such as the 53 and 6A6, where one section is used as a plate-tuned crystal oscillator and the other triode section capacitively coupled to it, is used as a harmonic amplifier. Choosing the proper method of neutralizing amplifiers is another problem which very often confronts the amateur. Either grid neutralization, as shown in Fig. 11, or plate neutralization (Hazeltine) may be used. There is really no difference in the two circuits where adequate driving power is employed. However, in some instances the plate neutralization method may be slightly superior. In both of these circuits we have used a center-tapped coil, with the tuning capacity shunted across the entire inductance. Another method of accomplishing this is shown in Fig. 12A, where the tuning condenser is only shunted across the plate section of the coil. If the plate coils are well constructed and tapped in the exact electrical center, the method shown in Figs. 11 and 12 are more convenient, because coils may be changed without requiring a resetting of the neutralizing condenser. Neutralization voltage may be also obtained as shown in Fig. 13; that is, directly from the driver-stage tank coil.

If push-pull circuits are to be used for frequency doubling, then the connections, as shown in Fig. 14, must be employed. In this case, the grids are connected in the usual push-pull manner, while the plates are connected in parallel. This is a very efficient frequency doubler although it employs two tubes instead of one, and unless the increased power obtained in this manner is really necessary, the complication does not warrant the use of this type of multiplier. The most versatile and efficient oscillator and multiplier circuits where low-powered exciters with an out-put of around 10 or 15 watts is required, are shown in Figs. 15 and 16. In 15 we have the pentode Tritet "oscillator buffer" or multiplier, which in turn drives another screen-grid tube. This arrangement will provide 10 to 15 watts out-put, when the amplifier tube is operating as a straight amplifier and not a multiplier, and around 5 to 10 watts when doubling takes place in the plate circuit of the amplifier.

In Fig. 16 we have used the combination oscillator and multiplier with the 53 tube, using a two-point switch for operation either at the crystal frequencies or the second harmonic of it, and a 210 or type 45 tube is used as an amplifier. The out-put of this will vary widely, depending upon the excitation. A full 15 watts may be obtained when the triode operates as a straight neutralized amplifier, and in the so-called neutralized doubler arrangement, approximately 10 watts could be obtained. In the diagrams, Figs. 15 and 16, the values of these parts are given and can be used in constructing either of these exciter units.

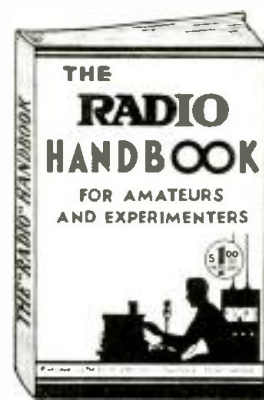A NEW BOOK for AMATEURS and EXPERIMENTERS



ENTIRELY NEW!

A RADIO Handbook prepared by a great technical radio staff. More than 300 pages and over 400 illustrations.

And then, there are 64 pages of new detector data, with details for building any kind of short-wave receiver from a one-tube to a 12-tube crystal superheterodyne. 48 pages of latest 5-meter data, including the design of four new, 5-meter superheterodynes. Also data on building one-tube beginner's transmitters. 32 pages of new Antenna data, directional antennas, etc. 64 pages of Radio-telephone data, including Controlled Carrier Modulation. Tells how and operate any kind of a C.W. or phone transmitter from 10 watts to a kilowatt. Many chapters on radio theory, transformer and choke design, all the new sound system design facts. Many tables, charts, curves, etc. Most complete and authoritative book of its kind.

\$1.00

STIFF BINDING

Order today! Send remittance of One Dollar, plus sufficient money for postage (weight 2 lbs.), check or money order accepted. Register letter if you send cash or unused U.S. postage stamps.

RADIO PUBLICATIONS
101 Hudson Street New York



RADIO'S LIVEST MAGAZINE

Edited by HUGO GERNSBACK

RADIO-CRAFT is devoted to general Radio in all its phases. To Radio Servicing and to the advanced set builder and Radio Technician. Kinks show simple ways out of difficult problems. The latest radio equipment is illustrated and described.

**8
Months for
\$1.00**

RADIO-CRAFT is fully illustrated with photographs, diagrams and sketches. Each issue contains over 150 illustrations. Sample copy—15c.

RADIO-CRAFT

99C Hudson Street New York, N. Y.



Earn While Learning at Home!

**TELEVISION, PHOTO
ELECTRIC CELLS,
PUBLIC ADDRESS**
Many Home Trained Men
make up to \$75 a week and
more in full-time radio
job—\$5-\$15 in spare time
alone. More trained men
needed. Learn at home by
quick, easy, R-T-I WAY.
Endorsed by 50 big concerns.
Write for big Opportunity Book FREE.

**PHILCO
CROSLLEY
ZENITH
GRUNOW
and 46
other
mfgs.
endorse
R-T-I**

RADIO AND TELEVISION INSTITUTE, Inc.
2150 Lawrence Ave., Dept. 215, CHICAGO, ILL.

Be a TELEVISION EXPERT

LEARN TELEVISION WITH RADIO NOW!

Here's opportunity! Get ready for the best paid jobs in Radio as Television sweeps the country. Train at big-time broadcasting station. Get actual experience over our Television Station W9XAI and commercial station W9XBY. Write today for free folder and literature showing actual photos of Television broadcasting, opportunities, etc.

FIRST NATIONAL TELEVISION, INC.
Dept. B-S, Power & Light Bldg., Kansas City, Mo.

QUICK WAY to make money in RADIO



Modern receivers are demanding men with modern training for service work. New training method and service equipment offer starts you earning almost at once. Up to \$3 an hour easy in a short time. Write today for FREE book of details.
Radio Training Association of America
Dept. S.W.C.-65
4525 Ravenswood Ave., Chicago

Please mention SHORT WAVE CRAFT when writing advertisers

IMMEDIATE DELIVERY!

The New RCA

ACR-175 11 Tube Superhet



5 to 600 meters

This new RCA amateur receiver incorporates every desirable feature of design, construction and operation, including several remarkable new developments.

(More fully described in this issue)

\$119.50
NET

Complete, with 11 tubes

Also available on the "MARINE"
NO DOWN PAYMENT
20 Months to Pay Plan

Write for Details

MARINE RADIO COMPANY

124-11 101st AVE., RICHMOND HILL, N. Y.

**Have You Seen the
New Magazine**

Jobs & Careers
THE VOCATIONAL DIGEST

Telling you how to go about:

- When You are Tackling the Job of Finding a Job;
- When You are Planning a Career;
- When You Want to Better Your Position.

The new magazine giving you every month a digest of articles from magazines and newspapers all over the country.

HOW AND WHERE, TODAY

alert, resourceful men and women have succeeded, where others, WHO DID NOT KNOW, have failed.

PRESENT-DAY JOB COMPETITION IS INTENSE. ONLY THE INFORMED MAN OR WOMAN CAN STAY IN THE RACE AND WIN.

"JOBS & CAREERS"

IS YOUR GUIDEBOOK OF OPPORTUNITY

On all newsstands 25c

If your dealer cannot supply you, send a quarter and we will forward a copy at once.

JOBS & CAREERS

520 N. Michigan Avenue, SW5, Chicago, Illinois

10 Meter Converter

(Continued from page 45)


the coil which connects with the rotor plates of the condenser, a wire is also run down through the chassis and soldered to a point beside the tube on the chassis. Terminal 3 of the 6L7 socket is connected to one end of the L-3 winding. The other end of this winding being connected to point X and also to one terminal of a .01 mf. condenser. The other terminal of this condenser being connected to ground or chassis. An 80 mmf. adjustable condenser is connected across this L-3 winding. One terminal of a 20,000-ohm resistor and one terminal of a 15,000-ohm resistor are connected together and a wire is run from this point to terminal 4 of the 6L7 socket which also has one lead from a .01 mf. condenser connected to it. The other end of this condenser goes to ground. Terminal 5 of this same socket is connected to terminal 5 of the 6C5 socket. Terminal 8 of the 6L7 socket is connected to one end of a 350-ohm resistor and also to one connection of a .01 mf. condenser. The other end of the resistor and condenser are connected to ground. Terminal 1 of this socket is also connected to ground as is terminal 1 of the 6C5 socket. A 100,000-ohm and a 20,000 resistor are connected together and from this point a wire is run to terminal 3 of the 6C5 socket. Also from this terminal one end of a .01 mf. condenser is connected. The other end of this condenser goes to ground. Terminal 5 has a connection to one terminal of a .00025 mf. mica condenser and also one end to a 50,000-ohm resistor, the other end of this resistor connects with ground. The other end of this mica condenser is attached to the stator plate connection on the rear of the tuning condenser C-2 and also to one end of the coil L-2. The other end of this L-2 coil is connected with the rotor plates of this same tuning condenser and ground. The tap on L-2 is connected to terminal 8 of the 6C5 socket.

All connections to the L-2 coil must be as short as possible. The remaining connections on the 20,000-ohm resistor and the 100,000-ohm resistor are connected to ground and the remaining connections on the 15,000 and 20,000-ohm resistors are connected with terminal X. The end of the winding L-4 nearest the end of the winding which is connected with terminal 3 of the 6L7 socket is attached to the binding post to the rear of the chassis marked antenna. The other end of the L-4 winding is brought to the binding post marked ground and to chassis. Coil L-2 is wound upon a piece of insulating material one and seven-eighth inches long and three-quarter inches in diameter. It has five turns of No. 22 D.C.C. wire and the winding is spaced to occupy eleven-sixteenths of an inch. The tap is made at a point one-half turn from the end of the winding which connects to ground. The shield can encloses this coil. This winding specification is very critical and must be adhered to in all details.

Coil L-3 is wound upon a one-inch diameter tube which is one and three-quarter inches in length. The winding of this coil consists of No. 28 enamelled wire with turns closely wound to occupy a space of one and three-eighths inches. Over this winding a thin piece of paper is placed and L-4, which consists of 25 turns of the same wire closely wound, is placed near the end of L-3 which connects to point X.

After all connections have been checked, turn the switch on and attach the antenna to the antenna binding post on top of the chassis and ground on the ground post. From the binding post on the rear of the chassis marked antenna, attach a lead to the antenna connection on the broadcast receiver. Likewise from the ground binding post, attach a wire to the ground connection on the broadcast receiver. Tune the broadcast receiver to a point somewhere between 1,400 and 1,500 kilocycles. Adjust condenser C-3 with an insulated screw driver until maximum noise is

**RCA proudly
presents the
ACR-175**

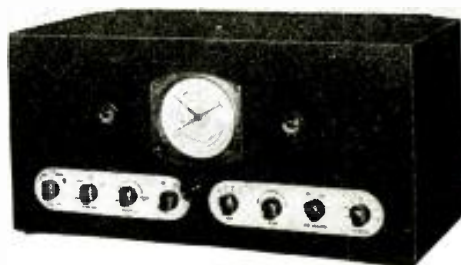

\$119.50
NET—f.o.b. factory

This new RCA amateur receiver incorporates every desirable feature of design, construction and operation, including several remarkable new developments. Translate the following into performance advantages in your station:

1. 5 to 600 meters, continuous
2. Ultra-selective crystal filter
3. "Magic Eye" tuning and signal strength indicator
4. Actual signal input read directly in microvolts
5. Iron Core i. f. Transformers (permanent alignment, high gain)
6. Metal Tubes
7. 11 tubes, 2 i. f. stages
8. Increased sensitivity
9. Greater selectivity with or without crystal
10. Improved signal-to-noise ratio
11. Improved a. v. c.
12. Greater band spread
13. Separate dynamic speaker
14. Pre-selection
15. Band change by switch
16. Individual coils for each band
17. Unusual stability
18. Iron-core heterodyne oscillator calibrated in cycles
19. Audio tone control
20. Unique stand-by pilot light
21. Handsome, rugged metal cabinet
22. Improved velvet drive tuning control—no backlash
23. Direct-reading, calibrated dial
24. Single-control tuning
25. Convenient and accurate logging
26. Two-speed, positive dial drive
27. All controls on front panel
28. Controls conveniently located low on panel
29. Headphone jack
30. Built-in power supply
31. Power transformer operates on 25 to 60 cycles
32. And the price, complete with tubes, crystal, speaker—only \$119.50 net, f. o. b. factory

Available for immediate delivery



AMATEUR RADIO SECTION

RCA Manufacturing Co., Inc.
CAMDEN, N. J.

A Service of the Radio Corporation of America



**W2AMN's
All-Band
Transmitter
Powered by
THORDARSON**

GEORGE W. SHUART, W2AMN, used the THORDARSON equipment here listed and secured excellent results with his modern all-band phone CW Transmitter as described in Short Wave Craft:

Power Supply

- 1—T6283 Plate Transformer
- 1—T6433—866 Filament Transformer
- 1—T6414—803 Filament Transformer
- 1—T6315 Input Choke
- 1—T6408 Filter Choke

Modulator

- 1—T5602 Power Transformer
- 2—T4707 Filter Chokes
- 1—T6773 Suppressor Grid Modulation Transformer

See Your Parts Dealer

Utmost satisfaction is assured if you insist on THORDARSON, supplied by your local dealer.



500 W. Huron St., CHICAGO, ILL.

"CHI-RAD"

Has the New All Star Transmitter Kit

Send for details and prices.

Trade in your old S. W. receiver for a new one at Chi-Rad's liberal terms.

CHICAGO RADIO APPARATUS COMPANY, Inc.

Headquarters for "Hams" for 15 years
W9RA—W9PST
415 S. Dearborn St. Chicago, Ill.

Love thy neighbor!
Avoid criticism by using



CANNONBALL HEADSETS

The favorite set of "Hams"
The phones are built with very heavy bar magnets which greatly increase their efficiency.

instead of the loud-speaker when you want to get any foreign stations any time after 10 p.m. Besides pleasing your neighbors, you will receive clearer reception.

Write for illustrated circular S-5
C. F. CANNON COMPANY
SPRINGWATER, N.Y.

OXFORD NEW SPEAKERS

—give you ALL there is in radio. High piccolo, low organ: Pure tones, no distortion. And they're durable. Write for prices.

OXFORD-TARTAK RADIO CORP.
917 W. VAN BUREN ST., CHICAGO, U.S.A.

heard in the receiver. Also adjust C-4 until greatest noise is obtained, then slowly tune condenser until a station is heard.

Parts for 10-Meter Converter

- 1 adjustable 30 mmf. condenser
- 1 adjustable 80 mmf. condenser
- 1 two-gang tuning condenser, Midget type—having a maximum capacity of 35 mmf.
- 4 .01 mf. fixed condensers
- 2 electrolytic 8 mf. condensers
- 2 20,000-ohm, 1-watt resistors
- 1 15,000-ohm, 1-watt resistor
- 1 50,000-ohm, 1-watt resistor
- 1 100,000-ohm resistor
- 1 350-ohm, 1-watt resistor
- 2 8-contact tube sockets for metal tubes
- 1 30 Henry 50-m.a. choke coil
- 1 4-contact tube socket for 80 type rectifier tube
- 1 power transformer having 250-volt high voltage winding
- 1 5-volt winding
- 1 6.3-volt winding
- 1 dial for tuning condenser
- 3 small Standoff insulators
- 1 piece 3/4-inch diameter insulating material, 1 1/4 inches in length
- 1 shield can, 2 1/2 inches in diameter
- 2 binding posts
- 1 mounting strip with two terminals for antenna and ground.
- 1 piece 3/4-inch tubing 1 1/8 inches long
- 1 6L7 tube
- 1 80 tube
- 1 .00025 mf. fixed mica condenser
- 1 110-volt switch
- 1 110-volt cord and plug
- Small spool of No. 36 enameled covered wire
- 10 feet Pushback wire
- 1 grid cap for metal tube

Champion Radio "Op" Advises You

● IF you as a "Ham" had to put your finger on the weakest spot in the average radio operator's makeup, you would probably wind up by specifying his "style" of sending the code signals. Not only does the average "Ham" or commercial operator frequently become careless and clip off his dots and dashes, or the time-space between them, so that they no longer resemble the theoretically correct time spacing for the length of each signal and the space between them, but a number of other idiosyncrasies creep in.

You may not believe it, but Ted R. McElroy, who holds the imposing title of "Official Champion Radio Telegraph Operator of the World," recently had the following to say regarding the code and how to learn it properly:

"My own experiences in learning to telegraph were about the same as those of any embryo "Ham." Believing that I could develop speed and technique by practice, I did a lot of sending and receiving. After many months of this tiresome routine, I became very much discouraged and, in fact, utterly disgusted. I was hopelessly stuck and despite long hours of practice, I could not raise my speed beyond a certain point.

"The operators in the office where I worked as a messenger recommended various methods. I tried them all, but without results, and I was just about to give it up as a bad job when one day "Chick" Stiles, one of the speediest operators in the office, told me about his favorite system of training for skill and speed and the splendid results he, himself, had received from it. Within a few days after I had decided to try this system, my first lessons came, with a personal instruction letter advising me just what to do and what not to do. I remember particularly well the caution against too much practice, and he outlined certain daily practice procedure which, surprisingly enough, required only 30 minutes to one hour!"

As Mr. McElroy states:
"This was so vastly different from the four to six hours practice I had been indulging in previously, that I was both amazed and skeptical. But I determined to follow the instructions for at least a week or two, and if results were not forthcoming I would stop. I adhered to his advice by studying and practicing as directed, and to my great surprise and delight, I found that the system really worked."

This article has been prepared from data supplied by courtesy of the Candler System Co.

Short Wave League Letter-heads

Designed for Members



This is the official letterhead

It is invaluable when it becomes necessary to deal with the radio industry, mail order houses, radio manufacturers. It can be used in many ways and gives you a professional standing. No member of the LEAGUE can afford to be without this letterhead.

This can only be used by members of the LEAGUE. No one else can purchase it.

Take advantage of this opportunity to handle your LEAGUE correspondence in a business-like manner.
See Page 58 for order blank.

SHORT WAVE LEAGUE

99-101 Hudson St., New York, N. Y.

6 Copies of SHORT WAVE CRAFT 70c PREPAID

For a limited time only, and as long as they last, we will send you six back numbers of SHORT WAVE CRAFT assorted, your choice, for 70 cents.

The usual price for six copies would be \$1.50 and most publishers charge a higher price for back numbers over one year old.

We can supply all copies except the following: June-July, Aug.-Sept., Oct.-Nov., 1930; Dec.-Jan., 1931; Dec.-Jan., May, June, Sept., Nov., 1932; Jan., Feb., March, May, June, July, 1933; Nov., Dec., 1934.

If you do not specify copies we will use our own judgment in sending assorted numbers to fill your order. Note we cannot exchange the copies for ones that have been sent to you.

Practically every copy of SHORT WAVE CRAFT contains important information that you should have. Here is a chance to get those copies.

As we have only a small supply of back numbers on hand, this offer will be withdrawn as soon as they have been sold.

We accept U.S. stamps, U.S. coin, or money order. Rush your order today.

SHORT WAVE CRAFT

99-101 Hudson Street New York, N. Y.

SHORT WAVE CRAFT 5-36
99-101 Hudson Street, New York, N. Y.

Gentlemen: I enclose herewith 70c, for which you are to send me six back number copies of SHORT

WAVE CRAFT as follows:.....

Name

Address

City..... State.....

PATENTS — TRADE MARKS

All inventions submitted held confidential and given personal attention by members of the firm.

Form "Evidence of Conception" and instructions

"How to Establish Your Rights"—Free

LANCASTER, ALLWINE & ROMMEL
PATENT LAW OFFICES
475 Bowen Bldg. Washington, D. C.

The A-B-C of Frequency Modulation

(Continued from page 13)

mitter not only impulses of varying length and equal power need to be sent, but the signals must also be transmitted with dynamic variations. Described in other words—"Since music consists very often of a succession of one and the same tone but reproduced with varying power—the signals to be transmitted have to be sent out with varied volume—or 'amplitude' as the technicians call it."

Amplitude Modulation = Amplitude Variations

Therefore, when music is to be transmitted it is necessary to apply the so-called amplitude modulation. Fig. 3 shows how this is done. The water beam is not only cut off into parts each of different length, as in the case of code transmission (compare Fig. 2), but the single "water cuts" are sent out with varying heights of the water level, or as the radio engineer would call it—"with varying amplitude." This effect is easy to obtain through the use of proper fitting valves of special design. The re-creation of these water amplitudes into sound of different tone volume can easily be obtained by means of a drum as demonstrated by Fig. 5. The principle of this transmission system, expressed in a few words, is as follows: *At all occasions where a particular audio frequency has to be transmitted with greater volume, the amplitude (the water level) must be increased and vice versa.*

If we compare Fig. 3 which shows music transmission with varying amplitude of the water-level, with the curve presented in Fig. 4, which shows the two side-bands of an "amplitude modulated" radio transmitter, we shall easily recognize that our water transmitter actually produces amplitude modulation.

Frequency Modulation = Frequency Variation

Many amateurs become frightened if they merely hear the name frequency modulation. This attitude towards the latest progress in radio communication is not reasonable; if we understand amplitude modulation there is no reason why we should not understand frequency modulation. That this opinion is correct will be demonstrated by means of another water transmitter analog of slightly different design.

Instead of one water pipe (used in Fig. 1 as the signal carrier), a great many are employed in the system shown by Fig. 5. Each of these several pipes is furnished with a valve operated by "remote control" to cut off the water beam or jet into parts of varying length but there is one great difference between the system shown in Fig. 1 and Fig. 5.

Series of pipelines for each particular amplitude: In the system shown in Fig. 1 the various "water cut-offs" are transmitted over one and the same pipe, regardless of whether they have a small or large amplitude. In the transmission system of Fig. 5, signals with a small amplitude are transmitted over pipeline No. 1, but signals of medium amplitude require 3 or 4 pipelines, and consequently signals of large amplitude require all the pipelines.

How the signals of various amplitude which are to be received, are transformed into sounds of equivalent volume, is easy to understand from Fig. 5, showing a drum placed below the various pipe openings.

Broken line does not interrupt transmission: This kind of transmission has of course the disadvantage that considerably more space is needed to install the many pipelines. However, it has the marked advantage that in case one pipe has become defective during reconstruction work (for example excavation in a city street) the transmission will not be affected to a great extent, since the broken pipe is used only during a part of the entire transmission time. During the period of use it is employed to transmit only a particular volume of the tone to be transmitted, or as the technicians say—a particular amplitude.

One transmitter radiates a great many frequencies: In radio transmission by means of frequency modulation the same condition exists as in multiplex water pipeline transmission. The principles of radio communication are shown by Fig. 6. We see that the transmitter at the left radiates not only a single frequency band, (as in the case when "amplitude modulation" is used), but a great many different frequency bands.

In case a tone of small volume is to be transmitted it will be sent over channel No. 1, for example. For a tone of medium volume, channels No. 2, 3 and 4 will be employed, and if a tone of very great volume is to be transmitted, then all six channels will be used.

Atmospheric Interference Does Not Affect Transmission

That atmospheric interference cannot disturb a frequency modulated transmission is explained by Fig. 6. We know from experiments that atmospheric electricity has a frequency band which is rather broad, and which moreover actually covers a considerable part of all radio frequencies in use at present. And we also know that a few of these many frequencies contained in atmospheric electricity are especially powerful.

When atmospheric electricity disturbs our reception it is mostly due to such a powerful frequency. The disturbance which we meet is due to the fact that such a powerful interference has collided with the frequency of the station we wish to receive.

Only One Channel May Be Disturbed

As long as only one channel is available (as in amplitude modulation), and this channel is disturbed, the entire communication is cut off, or at least, considerably disturbed—in other words, we hear plenty of "static!" However, if we have many channels, as in the case frequency modulation, we obtain an effect similar to the one demonstrated in Fig. 5.

The system presented in Fig. 5 shows that though one pipe or even two may be put out of order, all the other ones will remain unaffected! About the same thing will happen in radio communication, if many frequency channels (as in the case of frequency modulation) are used. One particular channel may be affected, but since this particular channel is used only for a part of the entire transmission time, the disturbance will have no considerable effect; sometimes it will not be recognizable at all.

How Frequency Modulation Is Produced

After we have studied the principal facts about frequency modulation, and its advantages in effecting radio communication—"without interference"—there remains only to explain how this new kind of modulation may be obtained. This is also quite easy to understand and will be demonstrated by the aid of Fig. 7, which shows the principal diagram of a transmitter. Parallel to the condenser of the tuning circuit, an additional small condenser (in the form of a condenser microphone) has been connected. This condenser microphone acts in about the same manner as a "trimmer" or band-spread condenser; an auxiliary of radio reception which is often applied in receivers of modern design.

We know from the operation of our receivers that in case we vary the additional small condenser, the frequency tuning of our receiver changes. Exactly the same variation of frequency tuning is obtained when the announcer shown in Fig. 7 speaks into the condenser microphone. The sound waves hit the plates of the condenser microphone, and make them vibrate, or, described in other words—"the distance between the plates of the condenser microphone changes." We know that by changing the distance between the condenser plates, the capacity value of a condenser changes. Therefore it is easy to under-

Send for Your Copy



IT'S GREAT!
FREE

Everyone in Radio is talking about the new ALLIED catalog. It will pay you to send for YOUR copy of the most complete Radio Supply Guide ever published. A full-sized 136 page catalog completely covering everything you need in radio equipment. The most complete, accurate and thorough Profit Guide available today—a real directory to radio progress. Packed with full-size sections on every field in radio. Up-to-the-minute on newest developments. Filled with outstanding values. This new book is Radio's Leading Supply Guide—geared to everything new in radio. It will still be up-to-date months from now.

136 PAGES All value-packed. Not a short-lived skimpy seasonal circular which constantly needs supplements and is soon discarded. Here is a solid 136 page luxuriously printed book. Covers everything in radio. Logically arranged for quick reference. Features big new sections in beautiful Rotogravure. Every page is loaded with outstanding new values.

A Full Sized Catalog

The new Spring and Summer ALLIED Catalog is full-sized in every way. Has complete sections on every radio field. Offers you full-sized listings, full-sized values and fuller profits.

NEW The fullest, finest array of new, improved 1936 radio receivers. Modern in every detail. Models from 4 to 11 tubes housed in rich, artistic cabinets. Sets featuring the miraculous "Televe" visual tuner; perfected metal tube sets. De luxe radio-phonograph combinations. Auto sets using all metal tubes. And for the rural areas—latest 6 volt battery sets. Also—exclusive—the startling new Farmpower units.

NEW An elaborate section on Public Address—page after page of new Sound developments. Mobile and portable systems of high versatility to meet every need. Amplifiers and complete P.A. systems ranging in size from 4 to 50 watts. Nothing has been overlooked. Your Sound problem can be solved easily, thoroughly, economically with ALLIED's entirely new equipment. And prices are excitingly low!

NEW Greatly enlarged Amateur Section—a diversified selection of receivers and transmitters for every Ham need. Dozens of newest set-building kits for the experimenter and home-builder. Complete lines of standard, first class testing equipment for Serviceman and laboratory. Famous brands on every page. Thousands of replacement parts, padgets, accessories. Tools, books, manuals. A truly endless directory to absolutely everything in radio.

Allied Radio

833 W. Jackson Blvd., Dept. E.
Chicago, Ill.

Send me your FREE 1936 Spring and Summer Catalog.

Name _____

Address _____

City _____ State _____


SERVICEMEN, DEALERS, AMATEURS, RADIO BUILDERS

Please mention SHORT WAVE CRAFT when writing advertisers

THE ONE AND ONLY

Encyclopedia on Short Waves

By C. R. Leutz and R. B. Gable

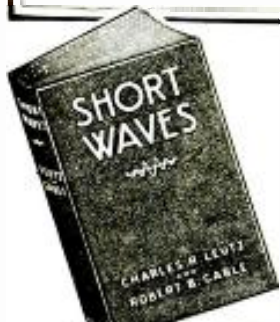

NOW \$1.00

384 Pages—Over 345 Illustrations Bound hand-somely in red linen, stiff covers. Size 6x9"

"SHORT WAVES" is written by Leutz and Gable, two foremost radio authorities. You will remember Charles R. Leutz as one of the pioneers in radio, also designer and manufacturer of the famous LEUTZ Transoceanic Receivers. Mr. Robert Gable owned and operated one of the finest low power broadcasting stations in the country. He is well known as an experimenter and research worker in scientific fields. Considering the value of this book for data alone, its cost should really be more than originally asked. But when you see the illustrations in the book you will marvel at how this book could be sold for ONE DOLLAR. It originally sold for \$2.98. The book is printed on a very expensive super-calendered paper. It contains 384 pages with over 345 photographic illustrations and diagrams. The supply of these books is not expected to last long. Once they are gone no additional copies will be available. ORDER NOW—be sure to tell your friends about this remarkable book value. Send the coupon today for your copy of "SHORT WAVES" by Leutz and Gable.

YOU SAVE \$1.98 JUST AS LONG AS THE SUPPLY OF THIS BOOK LASTS! THIS BOOK ORIGINALLY SOLD FOR \$2.98

"SHORT WAVES" is the most important and comprehensive volume of short-waves ever published. This book has EVERYTHING on short-waves—it literally contains a complete education on short-waves.

Short Wave Scouts

(Continued from page 18)

system running in the direction north and south.

Mr. Scrimsher states that more recently he has erected a Zeppelin antenna which has increased his volume some 30 per cent. This new antenna, however, is running in an east and westerly direction and is 50 feet above the ground.

Congratulations, Mr. Scrimsher!

We would like to point out to the many readers interested in this contest that recently we have received a number of entries in which there is great evidence of forgery. On many of these the dates on the veri cards were changed so that they came within the 30-day period selected in order to bring up the grand total. This is quite a serious offense, inasmuch as an affidavit is taken that the stations were all received within a certain period.

Needless to say, if there are any signs of changing dates the entry is immediately disqualified regardless of its total.

In one or two cases the entrant has lost the trophy merely because he was dishonest in submitting his list.

MAIL COUPON TODAY!

RADIO PUBLICATIONS, Dept. SWC-5-36
103 Hudson Street, New York, N. Y.

Gentlemen: Enclosed you will find my remittance of One Dollar (\$1) (cash, money order or new U. S. stamps) for which send me One Copy of "SHORT WAVES" by Leutz and Gable. I understand this book may be returned to you within three days if I am not completely satisfied and my money refunded.

NAME

ADDRESS

CITY STATE

(include 15c extra to cover mailing charges) (25c foreign countries)

• Partial Contents of "Short Waves" •

- HISTORICAL REVIEW
- SHORT WAVE PROPAGATION
- COMMERCIAL RADIO TELEPHONY AND TELEGRAPHY
- SHIP TO SHORE RADIO TELEPHONY
- DIRECTIONAL ANTENNAE
- TELEVISION
- AIRCRAFT RADIO EQUIPMENT
- SHORT WAVE BROADCAST RECEIVERS
- ULTRA SHORT WAVES (Medical and Surgical Applications)
- AMATEUR SHORT-WAVE EQUIPMENT

Don't forget that this comprehensive volume is sold on a MONEY-BACK GUARANTEE. If you are not satisfied with it, return it within three days for refund. Use the coupon at the left for ordering your copy of "SHORT WAVES" by Leutz and Gable.

RADIO PUBLICATIONS
103 Hudson St. New York, N. Y.

stand that the vibrating plates of the condenser microphone must affect the frequency radiated by the transmitter.

As long as the announcer speaks softly the frequency fluctuations of the transmitter will be small. But in case he raises his voice very much, the plates of the condenser microphone will vibrate to a larger extent, and consequently the frequency of the transmitter will vary greatly; or, more technically expressed—the frequency of the transmitter "swings out" to a larger extent.

Something About the "Frequency Swing"

The expression "swings out" describes much better what actually happens when frequency modulation is applied, than the expression we have used until now: "the frequency varies!" In reality the transmitter varies its frequency not only in one direction (as demonstrated by the simplified diagram of Fig. 6) but the frequency swings to both sides of the "carrier frequency" (marked Q in Fig. 9). This "swing effect" is easy to understand if we keep in mind that the condenser microphone is not always compressed by the sound impulses, but also expands—in a reversed direction—and in the same degree as it was compressed.

That means, as Fig. 9 indicates, the "carrier frequency" not only increases in its frequency value, but also decreases.

The "Band-Width" Necessary

As Fig. 9 shows, the frequency marked as No. 0 (carrier frequency) swings for example not only to channel 40 in a specific case, but also back to channel 40' etc. In practice, the width of the swing is considerably larger as it is possible to recognize from Fig. 9. Major Armstrong, for example, who uses the two kilowatt transmitter located atop the Empire State Building, in New York City, operates this ultra short-wave transmitter on a frequency of 41 mc. (Megacycles). The carrier frequency of 41 mc. swings to both sides to such

an extent that the entire band-width of the transmitter covers a frequency range of 150 kc.

Percentage "Band-Width" Quite Small

The required frequency range of 150 kc. for a single transmitter appears, at first glance, quite large, but we have to keep in mind that a transmitter operating with such a band-width in the ultra short-wave range (between 1 and 10 meters) occupies (by percentage) much less space than a transmitter operating with the usual band-width of 10 kc. in the "broadcast" band.

The wave range between 5 and 10 meters appears, at first, quite small. However, if we express the width of this wave range in frequencies or cycles, we find that it actually involves a frequency band of 30,000 kc. (30,000,000 cycles).

If we figure out how much this band-width is expressed in frequencies of all short wave channels above 10 meters; together with all broadcasting and long wave channels, we will ascertain that this tremendous wave range involves not more than 30,000 kc. Again, if we try to find the percentage of space required by a single transmitter, figured on the frequency basis in relation to the meter basis, we will find that a single transmitter operating with 10 kc. band-width in the broadcast band, requires 2 per cent of the entire space of the broadcast band. A frequency-modulated transmitter with a band-width of 150 kc. operated in the ultra short-wave range requires (figured on a similar basis) 0.5 per cent only.


The modulation system actually employed: Before closing this description it seems necessary to remark that the modulation system shown in Fig. 7 and 8 are the more simple methods of frequency modulation. Since the microphone must be mobile, to give the broadcast studios the necessary freedom to move it (far way from the transmitter) to any place desired, Major Armstrong has developed a similar modulation system, but of different design.

- TIPG—6410 kc.—"La Voz de Victor." San Jose, Costa Rica.
- HP5J—9590 kc.—"La Voz de La Panama." Panama City, Panama.
- HP5B—6030 kc.—"Radiodifusora de La Miramar." Panama City, Panama.
- TG2X—5940 kc.—"La Voz de La Policia." Guatemala, C.A.
- HIH—6814 kc.—"La Voz Del Higuamo." San Pedro de Macoris, Dominican Republic.
- HC2RL—6658 kc.—"Quinta Piedad." Quayquil, Ecuador.
- PRADO—6620 kc.—"El Prado." Riobamba, Ecuador.
- YVQ—6672 kc.—"Estacion Nacional de Radio." Maracay, Venezuela.
- YV2RC—5800 kc.—"Broadcasting Caracas." Caracas, Venezuela.
- YV3RC—6160 kc.—"Radiodifusora Venezuela." Caracas, Venezuela.
- YV6RV—6520 kc.—"La Voz de Carabobo." Valencia, Venezuela.
- YV1ORSC—5720 kc.—"La Voz del Tachira." San Cristobal, Venezuela.
- HJ3ABH—6012 kc.—"La Voz de La Victor." Bogota, Colombia.
- HJ4ABA—11710 kc.—"Ecos de La Montana." Medellin, Colombia.
- CEC—10670 kc.—"Compania Internacional de Radio S.A." Santiago, Chile.
- EAQ—9860 kc.—"Radiodifusion Ibero-Americana." Madrid, Spain.
- 2RO—9635 kc.—Radio E.I.A.R. Rome, Italy.
- 2RO—11810 kc.—Same as above.
- HVJ—15120 kc.—Vatican City, Rome, Italy.
- PHI—11730 kc.—The PHOHI. station. Hilversum, Holland.
- PCJ—15220 kc.—Philips Radio Laboratories. Eindhoven, Holland.
- HAT4—9125 kc.—Radio Labor. Budapest, Hungary.
- HAS3—15370 kc.—Same as above.
- HBL—9595 kc.—Societe des Nations. Geneva, Switzerland.
- DJA—9560 kc.—Der Deutsche Kurzwellensender. Zeesen, Germany.
- DJB—15200 kc.—Der Deutsche Kurzwellensender. Zeesen, Germany.
- DJC—6020 kc.—Der Deutsche Kurzwellensender. Zeesen, Germany.
- DJD—11770 kc.—Der Deutsche Kurzwellensender. Zeesen, Germany.
- DJE—17760 kc.—Der Deutsche Kurzwellensender. Zeesen, Germany.
- DJN—9540 kc.—Der Deutsche Kurzwellensender. Zeesen, Germany.
- DJQ—15280 kc.—Der Deutsche Kurzwellensender. Zeesen, Germany.
- 11715 kc.—Radio Colonial, Paris, France.
- 11890 kc.—Radio Colonial, Paris, France.
- 15245 kc.—Radio Colonial, Paris, France.
- RNE—12000 kc.—Radio Center, Moscow, U.S.S.R.
- CT1AA—9600 kc.—Estacao Radio. "Radio Colonial." Lisbon, Portugal.
- PMA—19345 kc.—Java Wireless Stations. Bandung, Java.
- PLP—11000 kc.—Java Wireless Stations. Bandung, Java.
- VK2ME—9590 kc.—"The Voice of Australia." Sydney, Australia.
- VK3ME—9518 kc.—Melbourne, Australia.
- VK3LR—9580 kc.—National Broadcasting Service. Lyndhurst, Australia.

Please mention SHORT WAVE CRAFT when writing advertisers

TWO GREAT S-W

10c BOOKS

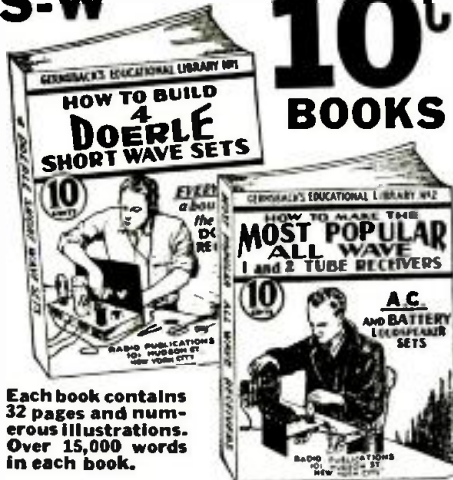

Each book contains 32 pages and numerous illustrations. Over 15,000 words in each book.

HOW TO MAKE FOUR DOERLE SHORT WAVE SETS

- ★ LITERALLY thousands of radio fans have built the famous DOERLE Short Wave Radio Receivers. So insistent has been the demand for these receivers, as well as construction details, that this book has been specially published.
- ★ Contains EVERYTHING that has ever been printed on these famous receivers. These are the famous sets that appeared in the following issues of SHORT WAVE CRAFT: "A 2-Tube Receiver that Reaches the 12,500 Mile Mark," by Walter C. Doerle (Dec., 1931-Jan., 1932). "A 3-Tube 'Signal Gripper,'" by Walter C. Doerle (November 1932). "Doerle '2-Tube' Adapted to A. C. Operation" (July 1933). "The Doerle 3-Tube 'Signal-Gripper' Electrified," (August 1933) and "The Doerle Goes 'Band-Spread'" (May, 1934).

Due to a special arrangement with SHORT WAVE CRAFT, we present a complete 32-page book with stiff covers, printed on an extra heavy grade of paper with numerous illustrations. Nothing has been left out. Not only are all the DOERLE sets in this book, but an excellent power pack if you wish to electrify any of the DOERLE sets, is also described.

HOW TO MAKE THE MOST POPULAR ALL-WAVE 1- and 2-TUBE RECEIVERS

- ★ THERE has been a continuous demand right along for a low-priced book for the radio experimenter, radio fan, radio Service Man, etc., who wishes to build 1- and 2-tube all-wave sets powerful enough to operate a loudspeaker.
- ★ This book contains a number of excellent sets, some of which have appeared in past issues of RADIO-CRAFT. These sets are not toys but have been carefully engineered. They are not experiments. To mention only a few of the sets the following will give you an idea.
- The Megadyne 1-Tube Pentode Loudspeaker Set, by Hugo Gernsback.
- Electrifying The Megadyne.
- How To Make a 1-Tube Loud-speaker Set, by W. P. Chesney.
- How To Make a Simple 1-Tube All-Wave Electric Set, by F. W. Harris.
- How To Build A Four-In-Two All-Wave Electric Set, by J. T. Bernsley, and others.

Not only are all of these sets described in this book, but it contains all of the illustrations, lookups, etc.—and believe it or not, each book contains over 15,000 words of new legible type. Each book is thoroughly modern and up-to-date. All the latest improvements have been incorporated into the sets.

Remember, these books sell at the extraordinary low price of ten cents; you can not possibly go wrong in buying them. Despite its low cost, our usual guarantee goes with this book as well!

IF YOU DO NOT THINK THAT THESE BOOKS ARE WORTH THE MONEY ASKED FOR THEM RETURN THEM WITHIN TWENTY-FOUR HOURS AND YOUR MONEY WILL BE INSTANTLY REFUNDED.

There has never been such a wealth of data published in low-priced radio books of this type in the history of the radio publishing business.

Take advantage of the special offer we are making and use the coupon below.

RADIO PUBLICATIONS
101 Hudson Street
New York, N. Y.

RADIO PUBLICATIONS SW 5-36
101 Hudson Street
New York, N. Y.

Please send immediately books checked:
 How to Build Four Doerle Short-Wave Sets.....10c
 How to Make the Most Popular All-Wave 1- and 2-Tube Receivers.....10c
 I am enclosing.....c; the price of each book is 10c. (Coin or U.S. Stamps acceptable.) Books are sent post-paid.

Name
 Address
 City..... State.....

Please mention SHORT WAVE CRAFT when writing advertisers

World-Wide 10-Meter Converter

(Continued from page 12)

selectivity decreases. When once adjusted though, regeneration is constant over the entire ten meter band! There we have the reason for the unusual performance of the converter. When operated with a superhet tuned to approximately 2000 kc. the ten meter sensitivity is many times greater than the sensitivity of the super at 2000 kc. That is of course for a given setting of the volume control of the super. We mention this because the noise-level is higher on ten than on 2000 kc. The super on 2000 kc. can be run "wide open," whereas the gain control can be run only halfway open with the converter operating on ten. Part of the "background" is of course due to tube noise especially encouraged by regeneration.

The tubes used are a 6A8 as the detector and a 6C5 as the oscillator. The 6A8 seems to be the best tube for the detector, because we tried the 6L7, which is no doubt a good tube, but there were no signs of regeneration and believe us when we say this converter was not at all adequate without the regenerative feature. And for this reason we recommend that those who build it should duplicate it—part for part in value and make. Also the various voltages indicated should be employed.

Tuning Condensers—How Built

The tuning condensers for the two circuits are constructed from a National SE90, 270 degree condenser. All plates were removed and the stator reassembled in two sections, with a single plate in each. The spacing between these two is slightly over one-half inch. Two rotor plates are also used, making two 2-plate tuning capacities operated by a single shaft. No shielding was used between these two stators, but let no one assume that the coupling thus permitted accounts for the regeneration. This split-stator condenser was put in nearly a month after the converter was first placed into operation; the original one was too large (too high capacity). With the two UM25, 25 mmf. National condensers used for band-setting and the coil specifications given, the ten meter band is spread over nearly the entire dial and even this is none too great a spread. Getting the two circuits to track, even with these very small condensers, required that the plates of the split-stator condenser be bent and spaced in a manner to allow perfect "tracking."

Coupling Converter to Receiver

Coupling the converter to the receiver is another very important part of the job. For this purpose we have used an old or discarded I.F. transformer. The can was removed and the windings removed from the wood dowel. Then we used some of the wire removed and wound a single layer of it three-quarters of an inch long. This is close wound and given a coat of coil lacquer. One of the padding condensers (C4) of the old transformer is used to tune the coil and the other (C5) condenser is used to couple the converter output circuit to the antenna post of the superhet receiver. This condenser (C5) is used only when the converter is used with a receiver employing a capacitive input circuit. If your receiver uses an antenna coupling coil, then you will need a small coil (L4) having a similar number of turns and coupled to L3 as shown in the drawing.

Some experimenting may be necessary with this winding in order to obtain the greatest amount of effective coupling. Using an I.F. transformer for this part of the converter provides the necessary mounting; the tuning condensers and the whole unit is also well shielded.

The coupling leads to the receiver should also be shielded to minimize "pickup" on the frequency to which the superhet is tuned. The frequency of the super is not critical, but should be higher than 2000 kc. in order to prevent "images" from appearing in the ten meter band. Although with the selectivity provided in the first detec-

BRUSH Spherical Microphone



For remote pickup, "P. A.," commercial interstation and amateur use. Low in price...but built to Brush's traditionally high mechanical and electrical standards. Wide frequency response. Non-directional. No diaphragms. No distortion from close speaking. Trouble-free operation. No button current and no input transformer to cause hum. Beautifully finished in dull chromium. Size only 2 1/2 inches in diameter. Weight 5 oz. Output level minus 66 D. B. Locking type plug and socket connector for either suspension or stand mounting at no extra cost. Full details, Data Sheet No. 13. Free. Send for one.

BRUSH Lapel Microphone



For after dinner and convention speakers, lecturers, etc. Gives great mobility. The smallest, lightest microphone on the market. Size 1 1/2 x 1 1/4 x 3/8. Weight with coat attachment less than 1 oz. Special internal construction and rubber jacketed outer case insure quiet operation. No interference from breathing noises, etc. Typical Brush sound cell response and trouble-free operation. Details on request.



MICROPHONES • MIRE STANDS • TWEETERS • HEAD PHONES • LOUD SPEAKERS

BUD PLUG-IN COIL FORMS



For every purpose where plug-in inductances are required in S.W. Receivers and Transmitters. Made of Special High Grade Low Loss Bakelite in natural brown color, and in the following three sizes. Ribbed for air space windings.

2 1/2 inch diameter—3 1/2 inch winding space	
No. 734—1 Prong—List	\$1.00
No. 735—5 Prong—List	\$1.65
No. 736—6 Prong—List	\$1.70
1 1/2 inch diameter—2 1/2 inch winding space	
No. 125—4 Prong—List	\$1.30
No. 126—5 Prong—List	\$1.35
No. 310—6 Prong—List	\$1.40
1 1/4 inch diameter—2 1/4 inch winding space	
No. 591—4 Prong—List	\$1.20
No. 592—5 Prong—List	\$1.25
No. 593—6 Prong—List	\$1.30
40% Discount to Radio Dealers and Amateurs	

BUD RADIO, INC.
1937 E. 55th St. CLEVELAND, OHIO


Two-Tube SW Receiver Only \$3.00



Best tubes, phones, unwired. A REAL power. Full 2 tube short wave set that brings in foreign stations, police calls amateurs & broadcast stations under good conditions. The world at your fingertips. Inexpensive, simple and easy to operate. Requires no batteries. Works entirely from 110 volt house current. Large, easy to follow wiring diagram and instructions. WE GUARANTEE RESULTS. 2 Tubes, extra...\$1.50 Double Headphones, extra...\$1.15 Wired, extra...\$0.75

Centrallion Engineering Co.
136-A Liberty, New York City

New! - GREATEST

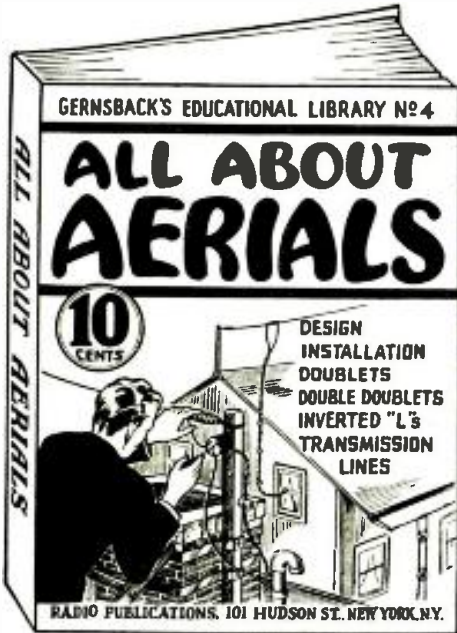

IN recent months the radio public has been made aerial-conscious by virtue of the many articles and advertisements on Aerial Equipment which have appeared in many radio magazines and literature. These articles have been so diversified, and in many cases so conflicting, that the radio experimenter, fan and Service Man are beginning to scratch their heads and ask: "What's it all about?" As a consequence, the demand for a low-priced book explaining in a clear, lucid manner the principles underlying the design and installation of efficient aerials has become a crying need. Furthermore, the steadily increasing nuisance of man-made static, resulting in noisy radio reception—particularly in connection with short-wave receivers—has made the importance of a good antenna a paramount issue. For the thousands of radio fans, both short-wave and broadcast, who wish to know just what type of antenna they should use and why, this book has been especially published.

ALL ABOUT AERIALS

In simple, understandable language this book explains the theory underlying the various types of aerials; the inverted "L," the Doublet, the Doublet, etc. It explains how noise-free reception can be obtained, how low-impedance transmission lines work, why transposed leads are used. It goes into detail on the construction of aerials suitable for long-wave broadcast receivers, for short-wave receivers, and for all-wave receivers. The book is profusely illustrated in a manner which will appeal to the most inexperienced in radio; clear, self-explanatory; it is written in so simple a style that it will clear up the aerial situation in your mind, once and for all. Such a wealth of information is presented in this book that you will wonder how it can be done at this low price.

Believe it or not, the book contains over 15,000 words of clear, legible type. It is thoroughly modern and up-to-date.

Remember that this book sells at the extraordinary low price of 10c; you cannot possibly go wrong in buying it. Despite its low cost, our usual guarantee goes with this book.

IF YOU DO NOT THINK THAT THIS BOOK IS WORTH THE MONEY ASKED FOR IT, RETURN IT WITHIN 24 HOURS AND YOUR MONEY WILL BE INSTANTLY REFUNDED.

There has never been such a wealth of data published in a low-priced radio book at this price in the history of radio business. Take advantage of this special offer we are making and use the coupon below.

RADIO PUBLICATIONS
101 Hudson Street
New York, N. Y.



RADIO PUBLICATIONS (No. 4) SW-5-36
101 Hudson Street
New York, N. Y.

Please send immediately your book "ALL ABOUT AERIALS," for which I enclose 10c (coin or U. S. stamps, acceptable). Book is to be sent prepaid to me.

Name

Address

City..... State.....

tor, there was no trouble with images. The main trouble seemed to be the picking up of harmonics of 20 meter stations and commercial stations operating close to that band.

Well, there's the story fellows, and we hope that those who read this article will give the "rig" a try and see how efficient it really is and also help to populate the ten meter band.

Parts List for 10-Meter Converter

- 3—50,000 ohm resistors (insulated) ½ watt, I.R.C.
- 1—50,000 ohm resistor (insulated) 1 watt, I.R.C.
- 1—100,000 ohm resistor (insulated) 1 watt, I.R.C.
- 5—.0001 mf. mica condensers, Cornell-Dubilier.
- 2—25 mmf. UM-25 National Var. condensers.
- 1—Remodeled National SE-90 condenser, (see text).
- 2—National Octal sockets.
- 1—Double tuned I.F. transformer, remodeled as per text. (C4, C5, are approximately 70 mmf.) Padders.
- 1—3 inch National Dial.
- 1—30 mmf. padding condenser (C3) National M30.
- 1—6A8 metal tube, RCA Radiotron.
- 1—6C5 metal tube, RCA Radiotron.

COIL DATA:

Detector coil has 9 turns of No. 12 tinned copper wire, with an inside diameter of ¾ inch, spaced to a length of 1¼". The "oscillator" coil has 7 turns of the same size wire, wound to the same diameter, and spaced to an over-all length of 1½ inches.

"Ham" Applications of the Cathode-Ray Oscillograph

(Continued from page 7)

graph amplifiers, until the maximum vertical deflection is equal to the maximum horizontal deflection.

Now if the stage has good fidelity a 45 degree diagonal straight line pattern will be formed. If the line bends toward the horizontal (see Fig. 2) at the upper right end, it indicates that the apparatus is non-linear. Overloaded transformer (A) due to saturation, not enough bias on the second 56, too much grid signal input or insufficient plate voltage or a combination of these effects may be responsible. If the line bends up (see Fig. 3) look for audio regeneration (rather rare) or incorrect filtering of the signal voltage.

For any tendency toward bending in the lower section of the line, such as in Fig. 4A or B, look for inadequate grid filtering or poor ground connections and tendencies toward regeneration. For an effect like Fig. 4B, abnormal bias on the second tube will be the most probable offender. A straight line indicates linear relationship between the signal voltages in all parts of the circuit between the two test points. With a constant external sweep frequency applied to the grid of the saw-tooth oscillator, actual pictures of the voice currents may be obtained, but these are no good for distortion analysis as we cannot always detect distortion by the shape or form of a wave. Most waves are far too complicated for this.


The other stages can be tested in the same way, and finally the entire amplifier can be tested by connecting 1 to the right hand horizontal plate and the top vertical plate to point 3.

You must expect a little curvature of the line as in Fig. 4B, because of the characteristic of class B amplifiers. However, with the proper plate voltage and associated apparatus this can be minimized.

Testing Power Supply

Next we may test the power supply ripple voltage, either for exact voltage value or for relative value as compared to the D.C. available. Connect an A.C. source, say between 15 and 50 volts to both horizontal and vertical deflector plates, and adjust the straight line resulting to a

Just Out! 10c BOOKS

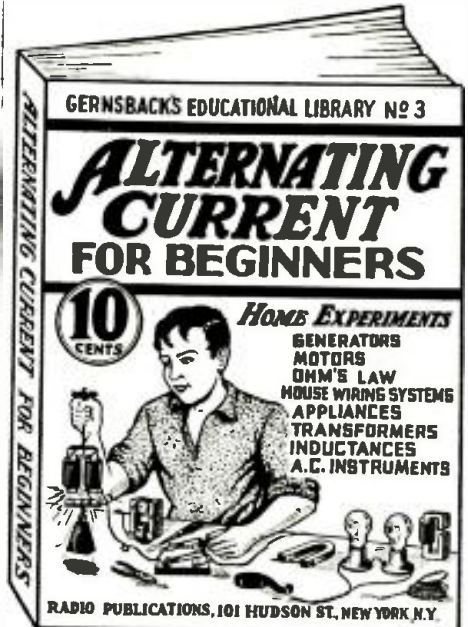

LITERALLY thousands of beginners each year ask the question "HOW CAN I GET STARTED IN RADIO?" In order to understand the theory of radio, it is necessary, first of all, to have a fundamental knowledge of electricity and, particularly of alternating currents. We stress this point because radio is a study of alternating currents of a very high frequency nature.

In this book, which is prepared especially for new beginners, we explain in a simple, lucid manner: How Alternating Current is Generated; What its Properties Are; What The Laws Governing It Are, and How It is Applied to Everyday Household Use. Furthermore, we give in simple language detailed instructions on how to perform practical experiments with alternating current in the home.

ALTERNATING CURRENT FOR BEGINNERS This book contains everything necessary to give the beginner his first foothold in the study of electricity and Radio. Electric circuits are explained with simple analogies to hydraulic systems. Ohm's Law, one of the fundamental laws of radio, is thoroughly explained; the generation of alternating current; sine waves; the units—volts, amperes, and watts are explained. Condensers, transformers, A.C. instruments, inductors and generators—all these are thoroughly discussed. House-wiring systems, electric appliances and electric lamps—nothing has been left out.

Here are some of the practical experiments which you can perform at home. Simple tests for differentiating between alternating and direct current; how to light a lamp by induction; how to make a simple electric horn; how to demagnetize a watch; how to test motor armatures; how to charge storage batteries from A.C. outlet; how to test condensers with A.C.; how to make A.C. electro magnets; how to fry eggs on a cake of ice; how to make simple A.C. motors and many others.

The book contains 32 pages, profusely illustrated with clear, self-explanatory diagrams. It contains over 15,000 words of clear, legible type. It is an education in itself and lays the groundwork for a complete study of radio and electricity.

At the extraordinary price of 10c, you cannot possibly go wrong. Despite its low cost, however, our usual guarantee goes with this book.

IF YOU DO NOT THINK THAT THIS BOOK IS WORTH THE MONEY ASKED FOR IT, RETURN IT WITHIN 24 HOURS AND YOUR MONEY WILL BE INSTANTLY REFUNDED.

There never has been such a wealth of data published in a low-priced radio book at this price in the history of the radio publication business. Take advantage of this special offer we are making and use the coupon below.

RADIO PUBLICATIONS
101 Hudson Street
New York, N. Y.



RADIO PUBLICATIONS (No. 3) SW-5-36
101 Hudson Street
New York, N. Y.

Please send immediately your book "ALTERNATING CURRENT FOR THE BEGINNER," for which I enclose 10c (coin or U. S. stamps, acceptable). Book is to be sent prepaid to me.


Name

Address

City..... State.....

Please mention SHORT WAVE CRAFT when writing advertisers

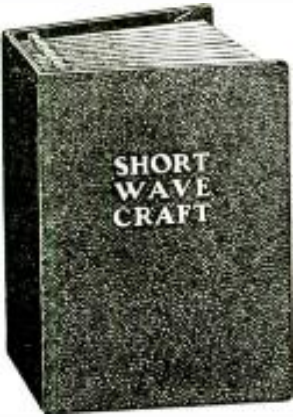NO ONE READS AND THEN DISCARDS SHORT WAVE CRAFT



Readers keep their copies for years as a steady reference and thousands of letters attest to this.

It is now possible to save your copies and for this purpose we designed a splendid binder for you which holds twelve copies. It is made of heavy substantial material and is covered with black grain leatherette. The name of the magazine is stamped in gold on the cover.

An ingenious mechanical arrangement is provided which makes it possible to hold the copies flat when reading from the binder.

SHORT WAVE CRAFT Binder as described, prepaid in the United States **\$1.25**

Canada and foreign countries 25c extra. We accept money order, check, stamps or cash.

SHORT WAVE CRAFT
99-101 HUDSON ST., NEW YORK, N. Y.

45 degree angle (estimated) on the screen. Now with the horizontal plates left connected and the input voltage known, the ripple at either side of the power choke may be connected to the vertical plates. Obviously, if the angle remains the same the ripple voltage is equal to the timing voltage. If the angle is more vertical, the ripple voltage is higher being equal to $(\frac{1}{\cos \theta}) = E_r$. This, of course, means that all phase differences between the two are eliminated without changing their values otherwise. Any phase difference between voltage applied to the horizontal and vertical plates will result in an ellipse or circular pattern. The exact angle will then be indeterminate. Instead of being from lower-left to upper-right as shown in the diagram, they may be from lower-right to upper-left where the phase is 180 degrees instead of zero degrees. Analysis can be made as easily in this case as otherwise. Voltage may also be read as a vertical deflection with any sweep frequency or no sweep voltage at all if calibrated for voltage readings.

Neutralization Tests

For a very accurate neutralization adjustment, connect the top vertical plate amplifier input to point 4 on the circuit of Fig. 1. Break the plate circuit of the 46 buffer stage and adjust for no vertical deflection. A high frequency sweep saw-tooth voltage on the horizontal plates is recommended here although not essential. By means of it, transients may be segregated from recurrent forms. At point 5 there should be no R.F. even with the by-pass condenser C-1 disconnected. Some negative D.C. may form here, but this is normal due to excitation of the grid and rectification.

At points 6 and 7, the same considerations may be tested for the power stage. The effectiveness of the R.F. choke in the power output plates may be ascertained by touching the top vertical plate to point 8, being sure to use a range appropriate for the high voltage at this point.

Determining Per Cent of Modulation

Now for 100% modulation, the voltage at point 8 of Fig. 1 will vary from zero to double that at 450 volts (or 900 volts). With a constant audio input provided by a simple audio oscillator (preferably around 400 cycles) and point 9 or 10 of the audio amplifier fed to the saw-tooth wave generator so as to "lock-in" to this frequency or a multiple of it, connect the top vertical plate to 11. A hazy pattern of the voice envelope should appear, from which the modulation percentage may be determined by inspection. Adjustment of R-1 and the output plate voltage may be made for maximum percentage modulation. If this cannot be attained in your particular set-up, changes in design will be necessary.

Another method of measuring modulation percentage with the Cathode Ray Oscilloscope is by means of the triangle pattern.

Place the audio wave on the horizontal plates in such a manner that increased amplitude will deflect the beam to the right. Bias the beam in the center of the target, and attach the vertical plate to 11 or the modulated R.F. output. Now as an audio signal is fed in the input of the A.F. system a triangle will be formed. If the audio voltage sweeps the spot to the left in a straight line any distance after it converges into a point, it is an indication that the modulation is over 100%! On the other hand, if the pattern does not converge into a point, due to R.F. still remaining at the minimum part of the audio cycle to the left, the modulation is less than 100%. Since there is negligible audio loss across the R.F. choke, the two free plates may be placed across it at points 8 and 11, with 11 vertical and 8 horizontal.

Analyzing "Transients"

Almost without question, the greatest value of this instrument is in the analysis and study of transients. Alteration of the circuit for eliminating these non-recurrent disturbing factors may be made while the Cathode Ray test equipment is connected (Continued on page 63)

EXCLUSIVELY FOR HAMERS!

A Ham Catalog That Beats Them All

This is the world's greatest exclusive ham catalog because:

1. It has more pages and lists more items than any other.
2. More nationally known manufacturers are represented.
3. It has been compiled BY amateurs FOR amateurs.
4. It contains diagrams, questions and answers and other valuable information.
5. It is the first catalog to describe the new RCA ACR-175 Receiver, the new UTC and Thordarson Transmitters!

IT'S FREE!

But the supply is limited so you'll have to hurry. Ask for Catalog No. 60 on your QSL cards. Address Dept. SW-56



It takes SIZE to make rapid service possible.

WHOLESALE RADIO SERVICE CO.
NEW YORK, N.Y. 100 SIXTH AVE.
CHICAGO, ILL. 301 W. JACKSON BLVD.
ATLANTA, GA. 410 W. PEACHTREE ST. N.W.
BRONX, N.Y. 442 E. FORDHAM RD.
NEWARK, N.J. 219 CENTRAL AVE.

SHORT WAVE LISTENER
the leading short-wave fan magazine
NOW 15c on all newsstands




It contains the largest listing of short wave stations in the world.

4600 SHORT WAVE STATIONS and many feature articles of interest to the short-wave fan.

If you cannot get the magazine at your newsstand due to sell-out, send 15c in cash, stamps, or money order, and we will send the magazine to you direct, prepaid.

OFFICIAL SHORT WAVE LISTENER MAGAZINE
99 HUDSON STREET NEW YORK, N. Y.

VEST POCKET SOLDERING IRON



Smallest good iron now on the market. Will do the work of irons twice its size. Only 10 inches long, 1/2 inch in diameter. By using the highest grade elements, it heats up in half the time of ordinary irons. Guaranteed to give satisfaction or money back. We issue no catalog on this item. Enclose \$1.20 and iron will be sent prepaid in U.S. 10c extra in Canada.

GOLD SHIELD PRODUCTS CO.
17 West 60th St., N. Y. City

QUALITY PARTS FOR HAMERS SERVICEMEN RADIO INDUSTRY

Complete facilities to meet every requirement in drilling and engraving of panels, and on all insulating materials and metals. Write today for complete descriptive catalog on parts of standard manufacture. Send 10c in stamps or coins to cover cost of mailing and mailing.

INSULINE CORP. OF AMERICA
25 PARK PLACE NEW YORK, N. Y.

Make This OSCILLOSCOPE

Low cost, easily constructed kit for amateurs and experimenters. With it view and demonstrate wave form! Use it for making resonance and r.f. indicators and audio oscillators. Comes with an improved brilliant tube having unexcelled fidelity response and long life. NOW BETTER ADAPTED TO R.F. OPERATION. Nothing like it for accuracy and performance.

Definition of wave form clear-cut and clear. See it Improved at your job. Tube, clips, lens or order Mirror and direct at this Motor Shaft Adapter low price.

\$2.00 Net

Prepaid with Improved at your job. Tube, clips, lens or order Mirror and direct at this Motor Shaft Adapter low price.




Oscilloscope Kit

The Finished Job

SUNDT ENGINEERING COMPANY
4262 Lincoln Ave. Chicago, Ill.

(Affiliate of Littelfuse Labs., Makers of Instrument Fuses—Radio and Aut. Fuses—High Voltage Fuses—Aircraft Fuses—Fuse Mountings—Neon Potential Fuses and Indicators.)


GOOD RESULTS Demand GOOD INSTRUMENTS



Model 421
0.1 Milliammeter
2% Accuracy

Triplett Electrical Instrument Co.
285 Harmon Drive Bluffton, Ohio

TRIPLETT manufactures a complete line of electrical instruments for radio, electrical and general industrial purposes both standard and custom built—For better short wave work, write for catalogue.



A Sensitive 4-Tube "Regen." Superhet.

(Continued from page 22)

was designed for use with headphones, so only one A.-F. stage is used—a 6C5 all-metal tube, resistance-capacity coupled to the output of the second detector. The grid resistor of the 6C5 output stage is a 250,000 ohm potentiometer connected in the conventional volume control circuit. An A.-F. volume control is desirable since it allows the volume to be regulated to any desired degree without disturbing the setting of the regeneration control in any way.

Coil Positions



Proceeding with our description, the detector coils are at the left of the tuning condenser; the oscillator coils are at the right. In each circuit the highest frequency coil is placed above the chassis and close enough to the wave-band switches to insure short direct wiring between them; the lower frequency coils are mounted underneath the chassis and are placed at right angles to each other to prevent the inter-coupling mentioned above. The socket for the 6J7 tube is at the left of the tuning condenser; that of the 6C5 is at the right. The 6F7 socket is at the center of the chassis just behind the tuning condenser. The socket at the rear and center of the chassis is for the 6C5 audio output tube. The iron-core I.-F. transformers are mounted at the rear corners close enough to the 6J7 and 6F7 sockets to keep the plate and grid leads fairly short. The antenna and ground connections are at the left rear of the chassis; the two tip jacks connect the headphones or speaker into the plate circuit of the 6C5 audio stage.

This layout is the result of considerable experimental work with this particular circuit and should not be changed if our results are to be duplicated. The various bypass and fixed condensers, resistors, etc., that are placed underneath the chassis are supported by the wiring and are merely mounted in the position that gives the shortest leads.

Lining Up the Set

Tune in a weak station, preferably a broadcasting station, back down the regeneration control until the voice or music clears up and readjust the padding condenser for maximum volume. If the signal becomes very loud, tune to a weaker station or reduce the input by turning out the antenna-series condenser. Do not reduce the volume by turning down the A.F. volume control! Now with an insulated screw driver or neutralizing tool, turn the trimmer of the grid section of the output I.F. transformer until the signal is loudest. Repeat the process with each trimmer in turn, working away from the second detector. If the signal becomes loud it will be necessary to reduce the input again as I.F. circuits cannot be sharply peaked with strong signals from either an oscillator or broadcast stations. It is best to leave the trimmer across the primary of the input transformer alone as it is extremely critical and if it is changed, all of the trimmers, including the "padder," will have to be readjusted. Adjust the antenna-series condenser until there are no "dead-spots" in the tuning scale and set the regeneration control for best reception in exactly the same manner as in the ordinary regenerative receiver.

If the detector and oscillator circuits do not track properly, i.e., produce the correct I.F., remove or add turns to either the detector or oscillator grid coils until the difference between their tuned circuits is equal to the I.F. or 456 kc. The oscillator must operate on a frequency 456 kc. higher than that to which the detector is tuned. In case either the first detector or the oscillator does not oscillate normally this may be due to insufficient turns in the tickler circuit or the inter-coupling mentioned above. Keep the "hot" R.F. leads as far apart as possible and, if the trouble still persists, these leads may be shielded with

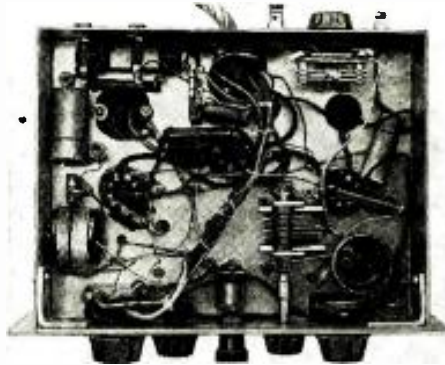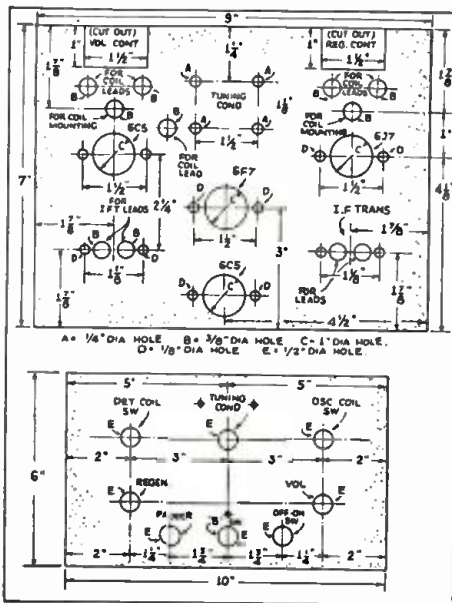

Chassis Data and Bottom View

the usual braided copper sleeving which is then grounded to the chassis. If the lack of oscillation is due to insufficient tickler turns, simply move the cathode tap up one or two turns toward the grid end of the coil until satisfactory oscillation is obtained.

This particular model uses only two sets of coils and tunes from about 15 to 65 meters in two positions of the coil switches. This arrangement effectively covers most of the frequencies used in present-day short-wave activities, excluding the 80 and 160 meter "amateur" bands. It is possible to add a third set of coils which will include the 80 meter amateur band on position "three" of the switches. However, great care must be used to prevent absorption losses and inter-coupling. The author does not recommend the use of more than three sets of coils; if a greater range is desired, use plug-in coils instead of those shown here. The four coils in this receiver are wound on the 1 1/2 inch bases taken from discarded tubes of the 201a type.

Loud Speaker Worked on Strong "Sigs"

As mentioned above, this receiver was not designed for loud-speaker operation. However, we have used a sensitive speaker at times when conditions are very good. Several foreign stations have been brought in at good loud-speaker volume with the

6C5 stage alone. If regular use of a loud-speaker is desired, it is advisable to add an output stage to the circuit shown in Fig. 1. A 6.3 volt pentode such as the 38 will give plenty of volume and the darin on the "B" batteries is quite small. Speakers can be obtained with windings of the proper impedance to match this or any other output tube, no output transformer being required.

If the above instructions have been carefully followed, it is not likely that any serious trouble will be encountered. It must be remembered that this circuit is new to most experimenters and the author asks that the constructor be patient if he does not get results at once. A careful adjustment of the padding condenser or a trimmer may make a great deal of difference in the signal strength or selectivity. If any difficulty is experienced, however, the author will be glad to give further advice or information if a self-addressed and stamped envelope is enclosed for reply. Letters should be sent in care of *Short Wave Craft*.

List of Parts

CONDENSERS

- C1 Tuning condenser, 2 gang, 140 mmf. per section.—Hammarlund.
- C2 Midget tuning condensers, 50 mmf. Hammarlund.
- C3 Midget tuning condenser, 35 mmf. Hammarlund.
- C4, C5, C11 Paper cartridge condensers, 0.1 mf. 400 volts. Cornell-Dubilier.
- C6 Paper cartridge condenser, 0.25 mf. 400 volts. Cornell-Dubilier.
- C7 Mica fixed condenser, .00025 mf. Cornell-Dubilier.
- C8 Mica fixed condenser, .003 mf. Cornell-Dubilier.
- C9, C10 Paper cartridge condensers, 0.05 mf. 400 volts. Cornell-Dubilier.
- C12 Mica fixed condenser, .0001 to .00025 mf. Cornell-Dubilier.
- C13 Mica fixed condenser, .001 mf. Cornell-Dubilier.
- C14 Paper cartridge condenser, .01 mf. 400 volts. Cornell-Dubilier.
- C15 Paper or Mica fixed condenser, .01 mf. (see text). Cornell-Dubilier
- C16 Electrolytic condenser, 25 mf. 25 volts. Cornell-Dubilier.

RESISTORS

- R1 Metallized resistor, 1/4 watt, 15,000 ohms. I.R.C.
- R2 Metallized resistor, 1/2 watt, 1,000 ohms. I.R.C.
- R3 Metallized resistor, 1/4 watt, 25,000 ohms. I.R.C.
- R4 Potentiometer, wire wound, 50,000 ohms. I.R.C.
- R5 Metallized resistor, 1 watt, 35,000 ohms. I.R.C.
- R6 Metallized resistor, 2 watts, 300 ohms. I.R.C.
- R7 Metallized resistor, 10,000 ohms, 1/4 watt. I.R.C.
- R8 Metallized resistor, 1 watt, 1,000 ohms. I.R.C.
- R9 Metallized resistor, 1/4 watt, 500,000 ohms. I.R.C.
- R10 Metallized resistor, 1 watt, 100,000 ohms. I.R.C.
- R11 Potentiometer, carbon type, 250,000 ohms.
- R12 Metallized resistor, 2 watts, 1,000 ohms. I.R.C.

COILS

- L1, L2, L3, L4, L5, L6 Detector, oscillator and antenna coils (see coil table below).
- I.F.T. Iron-core I.F. transformer. One input and one output, Miller. (456 kc. pre-tuned.)
- RFC1 R.F. choke, 2 1/2 millihenry. Hammarlund.
- RFC2 R.F. choke, 10 or 12 millihenry. Hammarlund.

OTHER PARTS

- 1 Electralloy chassis, 7x9x2 inches in size. I.C.A.
- 1 Aluminum or electralloy panel, 6x10 1/2 inches. I.C.A.
- 2 Wave-band switches, 3 pole, 3 position (SW1, SW2).
- 2 Off-on switches (SW3, SW4).
- 3 "Octal" sockets for metal tubes. Isolantite.
- 1 7 prong socket for 6F7 tube (small).
- 1 tube shield.
- Miscellaneous knobs, jacks, binding posts, dial, etc.

COIL TABLE

Range in Meters	Grid Turns	Tap at (Turns)	Antenna Turns	Size Wire (D.C.C.)
15-35	7 1/4	3	2 1/2	No. 24
35-65	12	5	4 3/4	No. 24
65-150	30	9	7	No. 28

All coils are close wound on 1 1/2 inch forms; antenna coils are coupled to the grid end of the coils.

Awards in the \$50.00 Prize Letter Contest which closed March 31, will be published in the July number.

Westinghouse Power Generator

Manufactured for U. S. Signal Corps

200 Watt 110 V. AC



A. C. ELECTRICAL POWER

from a Windmill, from available Waterpower, from your Automobile, from your Motorcycle, from your Bicycle, Foot-pedals or Handcrank (for transportable Radio Transmitters, Strong Floodlights, Advertising Signs); do you want to operate AC Radio sets from 32 V. DC farm light systems; operate two generators in series to get 200 V AC; obtain two phase and three phase AC, etc., etc.

There Are Over 25 Applications Some of which are:

A.C. Dynamo Lighting from eight to ten 20 Watt 110 Volt lamps. Short Wave Transmitter supplying 110 Volts AC for operating "Ham" transmitter. Operating 110 V. AC 60 Cycle Radio Receiver in DC districts. Motor Generator. Public Address Systems. Electric Sirens on motor boats, yachts, etc. Camp Lighting. Short Wave artificial "fever" apparatus. Television. Pelton Waterwheel for lighting or other purposes. Airplane: for lighting strong search light or electric signs. Laboratory work, etc., etc.

1/4 to 1/2 H.P. needed to run generator
BLUE-PRINT 22 x 28 in. and Four-Page 8 1/2 x 12 in. INSTRUCTION SHEETS FREE with Generator.

Generator, as described, including four replacement carbon brushes. **\$7.90**
 Instructions


Send \$2.00 deposit balance C.O.D. Shipping weight 18 lbs.

(Replacement carbon brushes bought separate \$1.50 per set of four. Set of instructions bought separate \$1.00.)
MONEY-BACK GUARANTEE

WELLWORTH TRADING COMPANY
 560 West Washington Blvd., Dept. SW536, Chicago, Illinois

Internationally popular for its many scientific and technical articles—

EVERYDAY SCIENCE AND MECHANICS

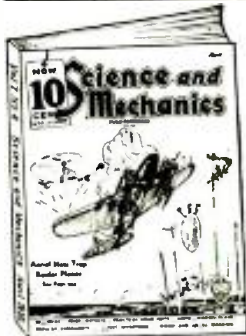

Over 150 illustrations

EVERYDAY SCIENCE AND MECHANICS is the finest scientific-technical—mechanical—construction magazine in the field. Up-to-the-minute with news flashes of scientific events. Dozens of constructional articles and many popular experiments. Ideas from which you can make things to sell.

Edited by **HUGO GERNSBACK**

A Host of Interesting Subjects Covered

Woodworking—Photography—Magic—Patents and Inventions—Book Reviews—Metal-Working—Chemistry—Engineering—Microscopy—Electrical Experiments—Household Hints—Astronomy—Prize Contests—and other subjects.


10c the copy **Everyday Science and Mechanics**
 Get your copy today! On all newsstands

99-C Hudson St., New York, N. Y.

A Neon Tube Oscilloscope

(Continued from page 15)

next fellow to share the air in true Amateur fashion. That many Amateurs offend is a matter of common knowledge and yet the offences committed in 98% of the cases are unintentional. They are due to either lack of suitable measuring devices, or insufficient knowledge. Discounting the latter instances, how many phones on the air today are noticeably imperfect in some respect. "Pretty good quality, but a broad signal," you say. In defense it might be said that this particular station is equipped with a few excellent meters. Of course meters are of great value, and we could not get along without them, but meters do not always tell the true story, particularly on registering voice frequencies. Thermocouple meters are often sluggish, and always sluggish enough not to read the peaks dwelt momentarily upon by the vast and complicated range of the human voice. The oscilloscope is perhaps the most accurate means of recording these instantaneous peaks, that, out of control, constitute the major offense committed by phone transmitters. Much campaigning has been done on the matter of over-modulation, and while the results have been noticeable, lack of equipment has been the chief reason for not clearing up the situation. The oscilloscope data here furnished is the layout used in the one constructed and put into operation by WICOL.

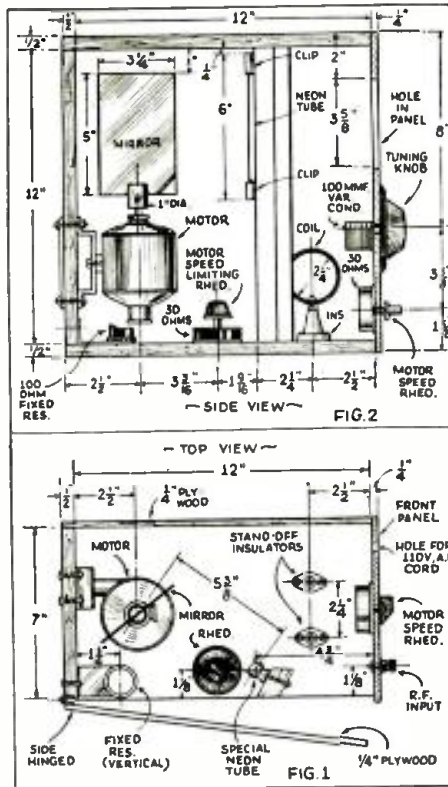

Side and Top Views of Oscilloscope.

The wiring diagram is simple and self-explanatory as portrayed in Fig. 3. Figure 3 also shows the front panel on which are mounted the Hammarlund Star .0001 midget variable condenser, the motor speed rheostat, and the binding posts to which the radio frequency input is connected. Fig. 1 is a view looking down on the floor of the instrument. The inside cabinet dimensions are height 12 inches; depth 12 inches; width 7 inches. The top, back, and bottom are of 1/2 inch stock for rigid construction to withstand motor vibration. The sides and front panel are of 1/4 inch plywood, and the left side is hinged so as to get to the parts without disturbing wiring, etc., and to be able to shift coils (L1 Fig. 3) for various bands. The cabinet is painted flat black—inside to reduce the ef-

Save!



LOWER PRICE—HIGHER QUALITY



Mass production economies ploughed back into lower prices! Our regular labelled, voltage-rated, guaranteed oil-filled transmitting condensers now available at these new prices:

Type 1005—1000 V.			
Cap.	Old List	New List	Your Cost
1	\$3.20	\$2.70	\$1.62
2	4.25	3.35	2.01
4	6.00	4.85	2.91
Type 1505—1500 V.			
1	4.00	2.85	1.71
2	5.25	3.90	2.31
Type 2005—2000 V.			
1	4.75	3.55	2.13
2	6.50	4.75	2.85

Positively the best value ever offered. Quality condensers at bargain prices. Compare features as well as costs!

DATA Send for new 1936 catalog covering condensers and resistors. Also sample copy of Research Worker.

AEROVOX CORPORATION

72 Washington St. Brooklyn, N. Y.

"COSMAN 4" 5-Band 4-Tube Receiver



The year's outstanding inexpensive short-wave receiver. Provides Band Spread tuning of any signal; Uses two of the new Metal tubes; Built-in Dynamic Speaker; 15-550 meter tuning range; 5-Band switch coil assembly—no plug-in coils; 4" Airplane Dial; Hammarlund Tuning condenser; Built-in power supply and numerous other features found only in higher priced receivers. Uses four tubes: 2-6K7's; 1-43 and 1-25Z5. A.C.-D.C. operation.
 Complete kit of parts and instructions. **\$10.50**
 Not wired, less tubes and cabinet.....\$2.50
 Wired and tested, Extra.....\$2.50
 4 Matched Sylvania tubes.....2.25
 All Metal Crystallized Cabinet for "Cosman 4".....2.25

Send For Our New 1936 Catalogue.
TRY-MO RADIO CO., INC.
 85 CORTLAND ST. NEW YORK CITY
 Distributor: Powerline Electric Corp., 179 Greenwich St., N.Y.C.

AMERICAN CRYSTAL MICROPHONE

(Licensed)

Attractive Design
 Standard accessories. Engineered for flexibility.

Request catalogue from your jobber or direct from factory.




AMERICAN MICROPHONE CO.
 A California Corporation
 1915 South Western Avenue. Los Angeles, Calif.

SPRING SALE HURRY! LIMITED QUANTITY

ASTONISHING VALUES

The items described below are priced low for immediate clearance. Those with a star (*) are available only in limited quantity. Once sold out, no more can be had at any price. They are all big bargains—these low prices. Order direct from this page. 100% satisfaction guaranteed on every transaction. We are a wholesale house and cannot accept orders for less than \$1.00. If C.O.D. shipment is desired, please remit 20% of the total amount of the order, balance will go forward C.O.D. Send money order, certified check or new U.S. stamps. Include sufficient extra remittance with order if to be shipped via parcel post. Excess remittance will be refunded.

★ Thordarson 1100 Volt Power Transformer



Specifications: 7.5 V.—3 A.; 7.5 V.—3 A. center tapped; 3 V.—8 A. center tapped; 1100 V.—150 mils. center tapped. For 107-120 volts, 60 cycles, A.C. operation. Excellent for 250 or 210 transmitters. Size: 5 x 3 3/4 x 4" deep. Ship. wt. 11 lbs. No. A-3773

YOUR PRICE **\$2.95**


★ Heavy Duty 30-Henry Filter Choke



Will handle 150 mils. without getting warm. Has D.C. resistance of 500 ohms. Excellent for public address power amplifiers and low-powered transmitters. Measures 3 3/4" x 2 1/4" x 3 3/4" overall. Ship. wt. 10 lbs. No. A-116

YOUR PRICE **80c**

Air Scout 1-Tube Short-Wave Receiver Kit



One of the lowest priced short-wave kits on the market. Although compact, it is sensitive and simple to build. A one tube battery-operated receiver which is capable of bringing in police signals, amateurs, broadcast stations and lots of distant stations. All terminals are color-coded—easily assembled by anyone. Has an attractive modernistic black wood base with a red pedestal. Uses a type 30 low drain tube. Complete kit includes all parts, base, hardware, wire, 1 1/2" type 30 tube, earphone and clear instructions.


No. A-214, less tube but including 1 plug-in coil and earphone. YOUR PRICE **\$4.75**

40-80 meter coil: 11-15 meter coil: Each.....34c extra

EXTRA COILS

40-80 meter coil: 11-15 meter coil: Each.....45c

★ Thordarson 210 Push-Pull Output Transformer



For coupling push-pull 210's, to voice coil of dynamic speaker. A heavy-duty unit in a shielded metal case. Size 3 1/2 x 3 x 3 3/4" high. Genuine Thordarson product. Ship. wt. 4 1/2 lbs. No. A-T2629

YOUR PRICE **75c**

3-Inch Magnetic Speaker



Excellent for use with 2 and 3 tube short-wave receivers and portable sets. Used with type 30, 33, 38, 201A, 71 and 112A tubes. Resistance 1000 ohms. Ship. wt. 3 1/2 lbs. No. A-3

YOUR PRICE **\$1.15**

★ Kolster Heavy Duty Filter Choke



Handles 110 mils. Replaces models for Kolster 20, 21, 22, 23, 30 heavy chokes. 500-ohm size: 1 1/2 x 2 1/4 x 1 1/4" Ship. wt. 3 lbs. No. A-1488

YOUR PRICE **75c**

★ Genuine Kolster 12 in. Dynamic Speaker




Known as the speaker with perfect tone. Has a free edge cone. The voice coil of which is mounted on chamois leather. Will handle an enormous amount of power without distortion. Has extra heavy duty field coil having resistance of 6000 ohms and mounted in a heavy cast-iron housing. Output transformer not included. Measures 12" in diameter and 7" deep. Net wt., 20 1/2 lbs. Ship. wt., 23 1/2 lbs. Big Bargain.

No. A-502

YOUR PRICE **\$3.95**


★ Universal Push-Pull Input Transformer



For use with all type tubes arranged in push-pull class "A" or "A prime." Measures 3 1/4 x 1 5/8 x 2" high overall. Ship. wt., 2 lbs. No. A-F1000

YOUR PRICE **75c**

HUDSON 4-TUBE A.C.-D.C. RECEIVER



Lowest priced R.C.A. licensed set on the market! Nothing else to buy—ready to operate. Employs 4 tubes, viz. 1-38, 1-76, 1-78 and 1-40. Operates on any 110 volt outlet, either A.C. or D.C. Uses sensitive magnetic speaker. Large illuminated airplane dial calibrated in kilocycles and meters. Tunes from 550 to 1750 K.C. (175-545 meters). Power consumption 30 watts. Size: 9 1/2 x 6 3/4 x 4 1/2" overall. Ship. wt., 6 lbs. No. A-42

YOUR PRICE Complete with 4 tubes cabinet, dial, wired, ready to operate. **\$6.95**

★ Thordarson Audio Transformer



Ratio 3 to 1. Excellent for interstage coupling. Totally shielded in black enamel case. Convenient soldering lugs for sub-chassis wiring. High efficiency. Ship. wt., 2 lbs. No. A-31

YOUR PRICE **50c**

★ Thordarson 15-Volt Filament Transformer



Delivers 3 amps. Fully shielded. Operates on 110-20 volts, 60 cycles. A.C. Ship. wt., 6 lbs. No. A-2610

YOUR PRICE **\$1.35**

"PIED PIPER" Crystal Set



Requires no tubes or batteries to operate. Adjustable crystal control. Merely needs aerial, ground and headphones to operate. Range 150 to 550 meters. Ship. wt., 5 lbs. No. A-5

YOUR PRICE **\$2.60**


"FEATHERWEIGHT" Headphones



Extremely light weight. Can be worn for a long time without fatigue. Standard 2000 ohms. Ship. wt., 1 lb. No. A-1679

YOUR PRICE **98c**

HUDSON DUAL-WAVE 5-TUBE A.C.-D.C. SET



Tunes from 540 to 4500 K.C. covering standard broadcast band as well as the police and amateur bands. Works on any 110 volt circuit, either A.C. or D.C. Tubes: 1-25Z5, 1-33, 1-78, 1-77 and 1-50B2. Large illuminated airplane dial. Two-band switch. Dynamic speaker. Phonograph provision. Measures 10" wide x 7 1/2" high x 5" deep. Complete with cabinet 5 tubes, speaker, dial, wired, ready to operate. Ship. wt., 7 1/2 lbs. No. A-5CT—YOUR PRICE **\$11.46**

Add 59c for 220 volt model

ORDER DIRECTLY FROM THIS PAGE

We buy and sell for cash only, which explains our exceptionally low prices. Send money via money order, certified check or new U.S. stamps. Send 20% deposit for C.O.D. shipments. Include extra remittance for parcel post charges (any excess will be refunded) otherwise shipment will be made by air express, charges collect. 100% satisfaction guaranteed on every transaction.

Standard Aerial Kit



Contains 70 ft. rubber covered lead-in wire, 70 ft. standard aerial wire, lightning arrester and all necessary insulators and lead-in strips for an inverted "L" aerial. Two such kits plus twisted lamp cord make a very nice doublet antenna system. Ship. wt., 3 lbs. No. A-1633

YOUR PRICE **65c**

RADIO TRADING CO., 101A Hudson St., New York City

fect of reflected light rays. The motor—in this case a sewing machine motor—is mounted vertically and to the back of the cabinet so that its shaft is 2 1/2 inches from the inside rear, and centrally with relation to either side. Other types of motors will, of necessity, be mounted as best adapts them. Two 30 ohm filament type rheostats and a hundred ohm, 100 watt fixed resistance, are connected in series with the motor in the 110 volt line. The motor should be of universal type, having a commutator, with ability to run on both A.C. and D.C. One of the rheostats is shown on the panel and controls the motor speed manually.

Too great a motor speed will bend the mirror due to centrifugal force as most inexpensive motors are apt to be slightly out of true or wobbly in the bearings. Once the mirror is bent it will be difficult to flatten it out perfectly again, and the picture will not be true. Do not put the mirror on the motor until you have it sufficiently slowed down or you will probably ruin it! A good practice is to set R2 (Fig. 3) so that with all of R1 in the circuit, the motor runs at its slowest speed without stalling. Slow speeds are most desirable, but the motor must run smoothly

and evenly. As stated before, the fixed resistor R3 will of course vary depending on the current drawn by your particular make of motor but it will not be difficult to determine the correct value. Resistors capable of carrying the motor current without heating should be used, otherwise the motor speed will pick up as the resistors heat. The neon tube is now mounted on the vertical brace which is of 3/4 inch stock and which is set at an angle, so the neon tube faces the center of the mirror. The tube is mounted at a height so that it is opposite the mirror.


If a metal cabinet is used, it may be necessary to mount the tube more than the stipulated 1 1/8th inches from the side to eliminate the effect of the metal on the neon tube. The coil L1 Fig. 3, should have about the same number of turns as the tank coil of the transmitter's amplifier tank. The coils in this case have plugs and plug into stand-off insulators to make "band-changing" easy. The coupling coil L2 is 2 turns of rubber insulated wire wound over L1 and terminated with small clips which clip to the rear of the rf binding posts. Figs. 1, 2 and 3 give complete layout and wiring.

In using the oscilloscope for audio (voice current) viewing, it may be necessary to step up the last audio stage through a small "step-up" audio transformer, if the output voltage of the audio amplifier is not great enough to light the tube. Of course, when using the scope for audio work, coil L1 and condenser have no part in the process.

To put the oscilloscope into operation (radio frequency) and assuming that the correct coil L1 is in place, attach a pair of twisted wires to the binding posts on the panel (connected internally to L2) and connect the other end of the twisted cord to a 1 or 2 turn coil (L3) which coil should be very loosely coupled to the tank of the final stage of the transmitter. The transmitter should be under load, or on the air when making tests. Now rotate the tuning condenser of the scope over the band. If the coil L1 is in band the tube will glow as the condenser is tuned to resonance. Now adjust the coupling of L3 to the transmitter tank so that the neon tube, which glows from the center toward either end, glows for a distance of 3/4 of an inch on each electrode. (Total length of glow 1 1/2 inches).

Please mention SHORT WAVE CRAFT when writing advertisers

INVALUABLE

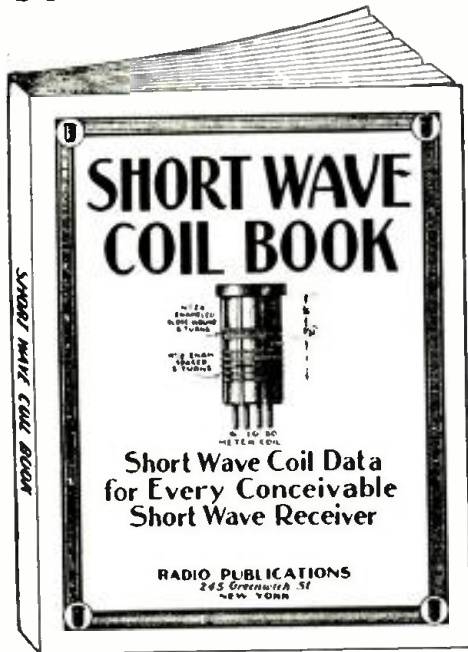

SHORT WAVE SET BUILDERS MUST HAVE THIS BOOK

It is now possible for the experimenter and short wave enthusiast to obtain the most exhaustive data on short wave coil winding information that has ever appeared in print.

As every experimenter who has ever tried to build a short wave set knows only too well by experience, the difference between a good and a poor receiver is usually found in the short wave coils. Very often you have to hunt through copies of magazines, books, etc., to find the information you require.

Between the two covers of this book you now find every possible bit of information on coil winding that has appeared in print during the past two years. Only the most modern "dope" has been published here.

No duplication. Illustrations galore, giving not only full instructions how to wind coils, but dimensions, sizes, of wire, curves, how to plot them, by means of which any coil for any particular short wave set can be figured in advance, as to number of turns, size of wire, spacing, etc.

There has never been such data published in such easy accessible form as this.

FRIENDS PESTER HIM

Dear Sirs:

I received your Short Wave Coil Book and am very well pleased. I showed it to my radio friends and now they are always pestering me for coil data, hi hi!

BERNARD A. DECKELMANN,
11348 So. State St.,
Chicago, Ill.

RADIO PUBLICATIONS
97 HUDSON STREET
NEW YORK, N. Y.

Radio Publications
97 Hudson Street,
New York, N. Y.

Please send immediately, your Short Wave Coil Book, for which I enclose 25c herewith (coin, U. S. stamps or money order acceptable). Book is to be sent prepaid to me.

Name

Address

City and State.....

Checking Modulation

Now start the motor and through the viewing hole there should be a steady even ribbon 1½ inches wide on the mirror. (So far only the unmodulated rf is used). Vary the motor speed, and if any series of lumps appear on both sides of the ribbon at any motor speed, there is ac present which is modulating the rf carrier. (Of course this should be located and eliminated). The next step is to turn on the speech and modulator stages and speak into the microphone. The ribbon should vary in width from zero to twice its unmodulated amplitude IF YOU ARE MODULATING 100%. Over-modulation will show a greater amplitude than under-modulation. No peaks should exceed the 100% amplitude limit! Adjust your transmitter accordingly. Distortion will show a higher cycle peak on one side of the ribbon than the other. Under-modulation will be evident because the peaks will not reach the 100% line. The speed of the motor should be varied for best results. A pure sinusoidal signal—one of unvarying frequency—applied through the modulator should appear in the scope as a symmetrical pattern. Voice frequencies, of course, being a complication of many frequencies will show as numerous peaks and valleys on both edges of the ribbon.

The kit mentioned above is supplied by the Sundt Engineering Co.

Two New Tubes

(Continued on page 25)

D.C. Plate Current—150 max. Milliampers.
D.C. Grid Current—30 max. Milliampers.
Plate Input—150 max. Watts.
Plate Dissipation—60 max. Watts.

Typical Operation:

Filament Voltage (A.C.)—10—10—10 Volts.
D.C. Plate Voltage—600—800—1000 Volts.
D.C. Grid Voltage (Approx.)—95—105—110 Volts.
Peak R.F. Grid Voltage (Approx.)—235—245—250 Volts.
D.C. Plate Current—140—140—140—Milliampers.
D.C. Grid Current (Approx.)—30—30—30 Milliampers.
Driving Power (Approx.)—7—7—7 Watts.
Power Output (Approx.)—45—70—90 Watts.

FREQUENCY	15	30	60	MEGACYCLES
Percentage of Max. Rated Plate Voltage and Plate Input max. max. max.	100	75	50	Per Cent

834 TENTATIVE CHARACTERISTICS

Filament Voltage (A.C. or D.C.)—7.5 Volts.
Filament Current—3.25 Amperes.
Amplification Factor—10.5.
Direct Inter-electrode Capacitances (Approx.):
Grid-plate—2.6 mmf.
Grid-filament—2.2 mmf.
Plate-filament—0.6 mmf.
Bulb—S-21.
Base—Medium 4-pin, Bayonet.

MAXIMUM RATINGS AND TYPICAL OPERATING CONDITIONS

As R.F. Power Amplifier—Class B Telephony
Carrier conditions per tube for use with a max. modulation fact. of 1.0
D.C. Plate Voltage—1250 max. Volts.
D.C. Plate Current—100 max. Milliampers.
Plate Input—75 max. Watts.
Plate Dissipation—50 max. Watts.

Typical Operation:

Filament Voltage (A.C.)—7.5—7.5—7.5 Vols.
D.C. Plate Voltage—750—1000—1250 Volts.
D.C. Grid Voltage (Approx.)—70—90—115 Volts.
Peak R.F. Grid Voltage (Approx.)—90—100—115 Volts.
D.C. Plate Current—50—50—50 Milliampers.
D.C. Grid Current (Approx.)—1—0.5—0 Milliampers.
Driving Power (Approx.)—3.3—3.1—3 Watts.
Power Output (Approx.)—11—16—20 Watts.

As Plate-Modulated R.F. Power Amplifier—Class C Telephony

Carrier conditions per tube for use with a max. modulation fact. of 1.0
D.C. Plate Voltage—1000 max. Volts.
D.C. Plate Current—100 max. Milliampers.
D.C. Grid Current—20 max. Milliampers.
Plate Input 100 max. Watts.
Plate Dissipation—35 max. Watts.

Typical Operation:

Filament Voltage (A.C.)—7.5—7.5 Volts.

(Continued on page 63)



Model 750

Multi-Purpose Model For Amateurs

The demand for a high quality, high efficiency separate speaker for "Hams," Amateurs, Experimentors and Engineers resulted in the design of the above Wright-DeCoster Multi-Purpose Model.

Model 750 cabinet complete with 6" Hiflux Magnetic Speaker. Standard Impedances. 7000 ohms or 10,000 ohms, center tapped. **\$7.50** List Price

Model 880 Cabinet complete with 6" Electro Dynamic Speaker with Universal Transformer to match all output tubes. **\$8.80** List Price

Model 1050 Cabinet complete with 8" No-Koil Reproducer with Universal Transformer to match all output tubes. **\$10.50** List Price

Write for description of other models and general catalog. Buy through Wright-DeCoster distributors. They are always anxious to cooperate.

WRIGHT-DeCOSTER, INC.

2257 University Ave., St. Paul, Minn.

Export Dept.—M. Simons & Son Co., New York.
Cable Address: "Simontree"

Canadian Office, Wright-DeCoster, Inc., Guelph, Ont.

SHORT WAVE NOISES KILLED!

With the New United 3-tube Noise Silencer.



Acclaimed by all leading radio magazines and newspapers throughout the world—Short Wave Fans can now listen to DX stations they could never hear before—Kills all noises—Eliminates ignition noises, static, power line noises and all other disturbances from domestic and industrial equipment—No need of installing special short-wave antennas or line filters—Easily attached to any set—Requires no external filament supply—This unit is completely shielded and measures 7½" x 5½" x 3"—Employs three latest type metal tubes. 6L7, 6J7 and 6116.

Custom built to match your short or all-wave superheterodyne—Money back guarantee—Send stamp for FREE descriptive circular No. 420—Special low prices to Short Wave Craft Readers.

UNITED RADIO & TEL. CO.
155 Washington St. New York, N. Y.

Build YOUR OWN TRANSMITTER—POWER SUPPLY OR RECEIVER WE STOCK ALL

RADIO EQUIPMENT

FOR EVERY PURPOSE

Licensed Radio Amateurs

At Both of Our Stores

Our catalog on request only to those living in Pennsylvania, Ohio, W. Virginia

CAMERADIO

601-3 GRANT ST. PITTSBURGH, PA. 38 TWELFTH ST. WHEELING, W. VA. Established 1919

Please mention SHORT WAVE CRAFT when writing advertisers

... SHORT WAVE ESSENTIALS FOR MEMBERS OF THE SHORT WAVE LEAGUE ...

Application for Membership
SHORT WAVE LEAGUE

99-101 Hudson Street, New York, N. Y. 5-36

I, the undersigned, herewith desire to apply for membership in the **SHORT WAVE LEAGUE**. In joining the **LEAGUE** I understand that I am not assessed for membership and that there are no dues and no fees of any kind. I pledge myself to abide by all the rules and regulations of the **SHORT WAVE LEAGUE**, which rules you are to send to me on receipt of this application. I consider myself belonging to the following class (put an X in correct space): Short Wave Experimenters Short Wave Fan Radio Engineer Student I own the following radio equipment:

Transmitting.....
Call Letters.....
Receiving.....

Name.....
Address.....
City and State.....
Country.....

I enclose 10c for postage and handling for my Membership Certificate.

A FEW WORDS AS TO THE PURPOSE OF THE LEAGUE

The **SHORT WAVE LEAGUE** was founded in 1930. Honorary Directors are as follows: Dr. Lee de Forest, John L. Reinarts, D. E. Replogle, Hollis Baird, E. T. Somerset, Baron Manfred von Ardenne, Hugo Gernsback, Executive Secretary.

The **SHORT WAVE LEAGUE** is a scientific membership organization for the promotion of the short wave art. There are no dues, no fees, no initiations, in connection with the **LEAGUE**. No one makes any money from it; no one derives any salary. The only income which the **LEAGUE** has is from its short wave essentials. A pamphlet setting forth the **LEAGUE'S** numerous aspirations and purposes will be sent to anyone on receipt of a 3c stamp to cover postage.

FREE MEMBERSHIP CERTIFICATE

As soon as you are enrolled as a member, a beautiful certificate with the **LEAGUE'S** seal will be sent to you, providing 10c in stamps or coin is sent for mailing charges.

Members are entitled to preferential discounts when buying radio merchandise from numerous firms who have agreed to allow lower prices to all **SHORT WAVE LEAGUE** members.

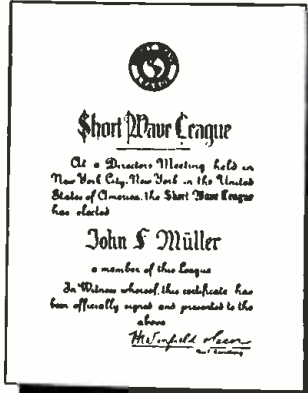


Illustration of engraved free membership certificate

SHORT WAVE ESSENTIALS LISTED HERE SOLD ONLY TO SHORT WAVE LEAGUE MEMBERS

They cannot be bought by anyone unless he has already enrolled as one of the members of the **SHORT WAVE LEAGUE** or signs the blank on this page (which automatically enrolls him as a member, always provided that he is a short wave experimenter, a short wave fan, radio engineer, radio student, etc.).

Inasmuch as the **LEAGUE** is international, it makes no difference whether you are a citizen of the United States or any other country. The **LEAGUE** is open to all.

SHORT WAVE LEAGUE LETTERHEADS

A beautiful letterhead has been designed for members' correspondence. It is the official letterhead for all members. The letterhead is invaluable when it becomes necessary to deal with the radio industry, mail order houses, radio manufacturers, and the like; as many houses have offered to give members who write on the **LEAGUE'S** letterhead a preferential discount. The letterhead is also absolutely essential when writing for verification to radio stations either here or abroad. It automatically gives you a professional standing.

A—SHORT WAVE LEAGUE letterheads, per 100..... **50c**

OFFICIAL SHORT WAVE LISTENER MAGAZINE

The finest magazine of its kind ever published—totally different in get-up and contents from any other. Contains the largest listing of short wave stations in the world, up-to-the-minute, including "Police," "Television" and short-wave stations, as well as a special list of the star short-wave stations with their frequencies and call letters. Also contains photos and descriptions of short-wave broadcasting stations in various parts of the world with photos of short wave studio artists—how to locate "weak" distance stations, and other hints for the "short-wave listener"—Question and Answer Department for the "listener"—Silver Cup Trophy for best photo of readers' listening "Posts," etc.

B—Official Short Wave Listener Magazine..... Prepaid **15c**

RADIO MAP OF THE WORLD AND STATION FINDER

The finest device of its kind published. The world's map on heavy board is divided into 23 sections, while the rotary disc shows you immediately the exact time in any foreign country. Invaluable in logging foreign stations. Also gives call letters assigned to all nations. Size 11" x 22".

C—Radio Map of the World and Station Finder..... Prepaid **25c**

GLOBE OF THE WORLD

This highly important essential is an ornament for every den or study. It is a globe, 6 in. in diameter, printed in fifteen colors, glazed in such a way that it can be washed. This globe helps you to intelligently log your foreign stations. The base is of solid walnut, and the semi-meridian of a nickel-like metal. Entire device substantially made, and will give an attractive appearance to every station, emphasizing the long-distance work of the operator.

D—Globe of the World..... Prepaid **89c**

SHORT WAVE LEAGUE LABEL BUTTON

This beautiful button is made in hard enamel in four colors, red, white, blue and gold. It measures three quarters of an inch in diameter. By wearing this button, other members will recognize you and it will give you a professional air. Made in bronze, gold filled, *not plated*. Must be seen to be appreciated.

E—SHORT WAVE LEAGUE label button..... Prepaid **35c**

EE—SHORT WAVE LEAGUE label button, like the one described above but in solid gold..... Prepaid **\$2.00**

SHORT WAVE LEAGUE SEALS

These seals or stickers are executed in three colors and measure 1 1/4 in. in diameter, and are gummed on one side. They are used by members to affix to stationery, letterheads, envelopes, postal cards and the like. The seal signifies that you are a member of the **SHORT WAVE LEAGUE**. Sold in 25 lots or multiples only.

G—SHORT WAVE LEAGUE seals..... per 25, Prepaid **15c**

SHORT WAVE MAP OF THE WORLD

This beautiful map, measuring 18x26 in. and printed in 18 colors is indispensable when hung in sight or placed "under the glass" on the table or wall of the short wave enthusiast. It contains a wealth of information such as distances to all parts of the world, political nature of the country in which a broadcast station is located, etc., and from the manner in which the map is blocked off gives the time in different parts of the world at a glance.


F—SHORT WAVE Map of the World..... Prepaid **25c**

PLEASE NOTE THAT ABOVE ESSENTIALS ARE SOLD ONLY TO MEMBERS OF THE LEAGUE—NOT TO NON-MEMBERS WITH EXCEPTION OF ITEM B.

Send all orders for short wave essentials to **SHORT WAVE LEAGUE, 99-101 Hudson Street, New York City.**

If you do not wish to mutilate the magazine, you may copy either or both coupons on a sheet of paper.

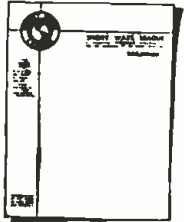SHORT WAVE LEAGUE 99-101 Hudson St., New York, N. Y.



A—50c per 100



B—15c per copy



C—25c each



C—25c each




D—89c each



E—35c each



G—15c for 25

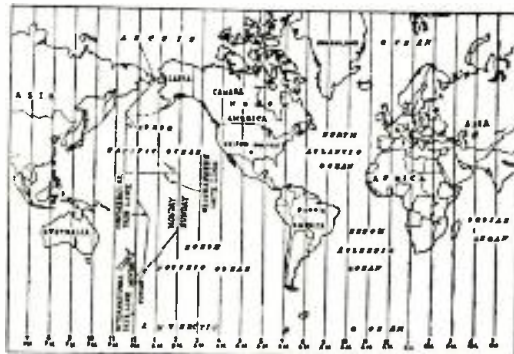

F—25c each

SHORT WAVE LEAGUE, 99-101 Hudson Street, New York, N. Y.

Gentlemen:

I am already an enrolled member in the **SHORT WAVE LEAGUE**

I am a new member and attach my application to this coupon

Please send me the following short wave essentials as listed in this advertisement:

.....

.....

.....

for which I enclose \$..... herewith.

(The **LEAGUE** accepts money order, cash or new U. S. Stamps in any denomination. Register cash and stamps.)

Name.....

Address.....


City and State.....

Country.....

5-36

Please mention **SHORT WAVE CRAFT** when writing advertisers

DATAPRINTS

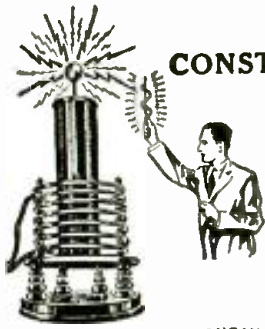

Just the
CONSTRUCTION
Information
You Need
To Build
Electrical
Apparatus

TESLA OR OUDIN COILS

Dataprint containing data for constructing this 3 ft. spark Oudin-Tesla coil. Requires 1 K.W. 20,000 volt transformer as "exciter"; see list below. Includes condenser data. . . **\$0.75**

- 8 inch spark, data for building, including condenser data; requires $\frac{1}{4}$ K. W. 15,000 volt transformer; see list below. **0.50**
- Violetia type, high frequency coil data; 110 volt A.C. or D.C. type; 1" spark; used for "violet ray" treatments and "Experiments" **0.50**
- How to operate Oudin coil from a vacuum tube oscillator **0.50**
- 3 inch spark Tesla coil; operates on Ford ignition coil **0.50**
- 3 inch spark Oudin coil; 110 volt A.C. "Kick-Coll" **0.50**
- 20 Tricks with Tesla and Oudin Coils **0.50**

TRANSFORMER DATA

- 1 k.w. 20,000-volt transformer data, 110-volt, 60-cycle primary. Suitable for operating 3 ft. Oudin coil **0.50**
- $\frac{1}{4}$ k.w. 15,000-volt transformer data, 110-volt, 60-cycle primary. Suitable for operating 3-ft. Oudin coil **0.50**
- Electric Welding Transf. (2 K.W. 110 Vt. Prim. 18 Vt. Sec. Other Sec. Vt. data given.) **0.50**
- Induction Coils—1 to 12 inch spark data. **0.50**
- ARTIFICIAL FEVER APPARATUS** **0.75**

(Low, Medium & High Power Data Given)



SLIDE RULE

MIDGET

Metal 4" Dia.
Price \$2.00.

With case and instructions

This rule solves any problem in multiplication, division, addition, subtraction, and proportion; it also gives roots and powers of numbers, sines, cosines, tangents and cotangents of all angles; also logs of numbers. Adds and subtracts fractions. Approved by colleges.

8" Dia. 25" Scale "Special" Rule, \$5.00

TELEGRAPHONE — Records voice or "Code" signals on steel wire by magnetism. Code can be recorded "fast" and translated "slow." Construction data (special) **\$0.80**

MAGNET COIL DATA

- Powerful battery electro-magnet; lifts 40 lbs. **\$0.50**
- 110 Volt D.C. magnet to lift 25 lbs. **0.50**
- 110 Volt D.C., 300 lb. Lift electromagnet. **0.50**
- 110 Volt D.C. solenoid; lifts 2 lb. through 1 in. **0.50**
- 110 Volt D.C. solenoid, lifts 6 lb. through 1 in. **0.50**
- 12 Volt D.C. solenoid, lifts 2 lb. through 1 in. **0.50**
- A. C. Solenoid, powerful, 110-volt, 60-cycle. **0.50**
- MOTOR**—1/18 H.P., 110 volt A.C., 60 cycle (suitable for driving 12" fan, etc.)—Data. **0.50**
- 60 or 1,200 cycle Synchronous motor Data. **0.50**

MISCELLANEOUS DATAPRINTS

- Electric Furnace Regulator. **\$0.50**
- Treasure Locator. **0.50**
- Water Turbines. **0.50**
- 20 motor circuits—hook-ups. **0.35**
- 20 practical telephone hook-ups **0.35**
- 100 mechanical movements for inventors. **0.50**
- Polarized Relay—Ultra Sensitive **0.50**
- Electro-medical coil (shocking coil). **0.50**
- Water-Wheels—How to Build and Light Your house **0.50**
- 20 Electric Bell circuits. **0.50**
- Public Address System **0.50**
- Electric chime ringet; fits any clock. **0.50**

20 "Electrical Tricks" for LODGES and PARTIES **\$0.50**

How to Fry Eggs on Cake of Ice Electrically. **\$0.50**
"Rewinding" Small Motor Armatures. **0.50**

"ENGINEERING SERVICE BY MAIL"
(20% off on orders for \$3.00 or more. No C.O.D.)

The DATAPRINT COMPANY
RAMSEY, N. J.

A "Loop Aerial" S-W Receiver

(Continued from page 17)

Layout of Parts on Sub-Panel

Now turn your attention to some descriptive details for the arrangement of the parts on the subpanel. On the left are the two clips for connecting the filament-supply batteries. (Only two No. 6 dry cells in series will prove more than sufficient for a long-time operation of this receiver.) Then following across the panel is the detector tube, the 6:1 (5:1 is OK) audio transformer, the amplifier tube and finally on the extreme right are the three "B" voltage clips—one 45-volt tap, the other two serve as phone connections and one of these also as the 90-volt tap. The negative side of the "B" connects to the negative of the "A" battery.

Then back of the audio transformer is placed the grid-leak R2 and grid-condenser C2 and towering up for a distance of four feet is the house-lath and small cross-pieces which support the loop-coils L1 and L2.


When this completed support is fastened in place, a wire (with one end scraped) is slipped through the clip and held taut while passing to and over the top cross-piece and terminating its other scraped end in the second clip. This makes the loop coil L1, and since a small hole is drilled through the subpanel on the inner side of these two clips, a similar method is used to put the loop coil L2 into place. However, the ends of L2 are soldered to the proper wires underneath the subpanel.

The other item of description is the radio frequency choke coil—labelled RFC. This choke coil is made on a 3" length of $\frac{1}{4}$ " diameter wood dowel, with 1000 turns of No. 36 D.C.C. copper wire close-wound. If you want to try a ground wire on this set, connect it to the A—, B— clip, but in my case, such a wire dampened the regeneration quite a lot.

If the constructor is a "fan" for a particular short-wave band, a little experimenting with various sizes of loops L1 and L2 (and condensers C1 and C3) will bring in the desired results.

Parts

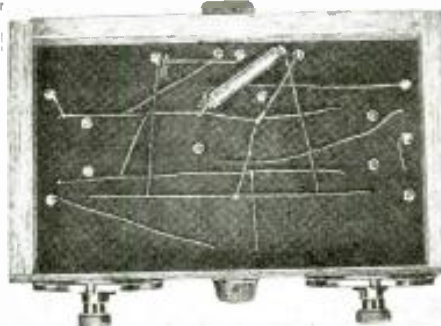- 2 .00035 mf. variable condensers
- 2 vernier dials
- 10-ohm rheostat and knob
- 2 UX sockets
- 5:1 audio transformer
- 5 megohm gridleak
- 1 .00025 mf. fixed grid-condenser.
- 1 top cross piece $4\frac{1}{2}'' \times \frac{1}{2}'' \times \frac{3}{8}''$
- 3 cross pieces $4\frac{1}{4}'' \times \frac{1}{2}'' \times \frac{3}{8}''$
- 1 RFC coil
- 17 feet of No. 18 D.C.C. copper wire for L1 and L2
- 2 type '30 tubes
- 2 No. 6 dry cells
- 1 90-volt "B" battery with 45-volt tap



Bottom View

(The loop as constructed, when tuned by a 250 mmf. condenser, will cover the range approximately from 21 to 100 meters. If a 100 mmf. condenser is used, the range will be from approximately 19 to 35 meters. With the smaller condenser, of course, there will be less crowding of stations and tuning will be easier. Unless the wire on this loop is made very rigid, considerable difficulty will be experienced with frequency instability, the slightest vibration causing the set to be detuned quite severely. The best solution would be to use copper tubing instead of copper wire.—Editor)

UP IN A JIFFY AT ANY ANGLE

RCA RK-40

All-Wave Antenna \$5.50



It's simple to install. Goes up in a few minutes, at any angle, wherever you can put a 60-foot straight wire. Gets more stations on both broadcasting and short wave bands. A really fine antenna that will be especially valuable in difficult locations. Factory assembled, all joints soldered. Get it from your RCA Parts Distributor.

RCA Mfg. Co., Inc., Camden, N.J.

A subsidiary of the

RADIO CORPORATION OF AMERICA



ANTENNA SYSTEMS



NEW
DUAL BAND
7-TUBE AC-DC
AMERICAN
& FOREIGN
SUPER

A \$40 value for only

KADETTE-77-

\$26.95

A real radio thoroughbred that brings an instant consciousness of charming originality. The clean flowing beauty of all things new and modern are superbly reflected in this exquisitely fashioned model.

Cabinet in beautiful sliced straight grain American walnut with Bull hand inlay. Illuminated convex crystal enclosed airplane dial with vernier drive. Large Electro Dynamic speaker and "Modern to the Minute."

See your dealer or write for full information

INTERNATIONAL RADIO CORPORATION
Ann Arbor Michigan, U.S.A.

NATIONALLY KNOWN!

McMurdo Silver No. 5D
Patterson PR-16
Midwest—All Models
Super Skyriders


EASY TERMS WRITE FOR DETAILS.

DAVEGA 63 Cortlandt St.
Dept. S, New York City
Nationally Known Distributors

Here are the Six BEST SHORT-WAVE RADIO BOOKS!

Without doubt you will have to go a long way to buy better books on short waves than you find on this page. Each book is written by a well-known authority on short waves . . . each book has been carefully illustrated with photographs and diagrams to

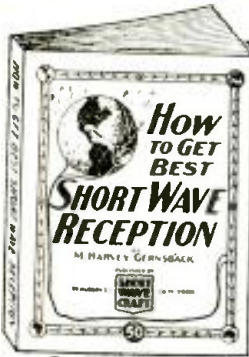make the study of this field of radio much simpler. The volumes on this page are the finest books on short-waves which are published anywhere today. Order one or more copies today . . . find out for yourself how fine they are. Prices are postpaid.



How to Get Best Short-Wave Reception

By M. HARVEY GERNSBACK

This book tells you everything you ever wanted to know about short-wave reception.

The author, a professional radio listener and radio fan for many years, gives you his long experience in radio reception and all that goes with it.

Why is one radio listener enabled to pull in stations from all over the globe, even small 100 watters, 10,000 miles away, and why is it that the next fellow, with a much better and more expensive equipment, can only pull in the powerful stations that any child can get without much ado?

The reason is intimate knowledge of short waves and how they behave. Here are the chapters of this new book:

1. What are Short Waves and what can the listener hear on a short-wave receiver or converter?
2. How to tune and when to listen in on the short waves.
3. How to identify short-wave stations.
4. Seasonal changes in short-wave reception.
5. Types of receivers for short-wave reception.
6. Aerial systems for short-wave receivers.
7. Verifications from short-wave stations.
8. The book makes excellent reading matter. There are many tricks in short-wave reception that even some of the "old-timers" do not know. Be sure to get it.

40 Illustrations, 72 Pages. Stiff, flexible covers

50c

HOW TO BUILD AND OPERATE SHORT-WAVE RECEIVERS


THIS is the best and most up-to-date book on the subject. It is edited and prepared by the editors of SHORT WAVE CRAFT, and contains a wealth of material on the building and operation, not only of typical short-wave receivers, but short-wave converters as well. Dozens of short-wave sets are found in this book, which contains hundreds of illustrations; actual photographs of sets built, hookups and diagrams galore.

This book is sold only at a ridiculously low price because it is our aim to put this valuable work into the hands of every short-wave enthusiast.

We know that if you are at all interested in short waves you will not wish to do without this book. It is a most important and timely radio publication.

150 Illustrations, 72 Pages. Stiff, flexible covers

50c

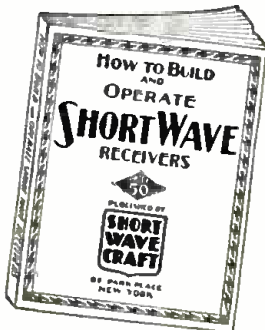


THE SHORT-WAVE BEGINNER'S BOOK

HERE is a book that solves your short wave problems—leading you in easy stages from the simplest fundamentals to the present stage of the art as it is known today. It is the only low priced reference book on short waves for the beginner. The book is profusely illustrated—it is not "technical." It has no mathematical and no technical jargon. It also gives you a tremendous amount of important information, such as time conversion tables, all about aerials, noise elimination, all about radio tubes, data on coil winding and other subjects.

Partial List of Contents

- Getting Started in Short Waves—the fundamentals of electricity, symbols, the Short Hand of Radio—how to read schematic diagrams. Short Wave Coils—various types and kinds in making them.
- Short Wave Aerials—the points that determine a good aerial from an inefficient one.
- The Transposed Lead-in for reducing Static.
- The Beginner's Short-Wave Receiver—a simple one tube set that anyone can build.
- How to Tune the Short-Wave Set—telling the important points to get good results.
- Audin Amplifiers for S-W Receivers.
- Learning the Code—for greater enjoyment with the S-W set.
- Wave length to Kilocycle Chart.
- Wire Chart—to assist in the construction of coils.

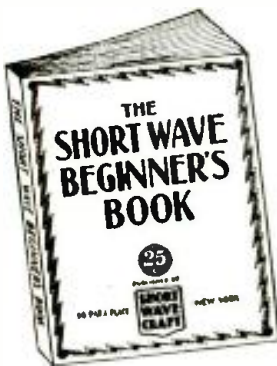25c 75 Illustrations, 40 Pages. Stiff, flexible covers



All the books shown on this page are published exclusively by

SHORT WAVE CRAFT

99-101 Hudson Street, New York, N. Y.

CLIP-MAIL

SHORT WAVE CRAFT, 99-101 Hudson Street, New York, N. Y. SW-5-36

Gentlemen: I enclose herewith my remittance for the amount of \$..... for which you are to send me, postpaid, the books checked below.

- | | |
|----------------------------------------------------------------|------------------------------------------------------------------------------------|
| () How to Get Best Short-Wave Reception..... 50c each | () How to Become an Amateur Radio Operator..... 50c each |
| () 101 Short-Wave Hook-ups..... 50c each | () Ten Most Popular Short-Wave Receivers. How to Make and Work Them..... 25c each |
| () How to Build and Operate Short-Wave Receiver..... 50c each | () The Short Wave Beginner's Book..... 25c each |

Name.....
Address.....
City..... State.....

(Send remittance in form of check or money order. If letter contains cash or unused U. S. Postage Stamps, register it.)


Please mention SHORT WAVE CRAFT when writing advertisers

101 SHORT-WAVE HOOKUPS

Compiled by the Editors of SHORT WAVE CRAFT


EACH and every hook-up and diagram illustrated is also accompanied by a thorough explanation of what this particular hook-up accomplishes, what parts are required, coil-winding information, values of resistors, etc. In fact, everything you want to know in order to build the set or to look up the data required.

To be sure, all of the important sets which have appeared in print during the past five years are in this double book. Sets such as the Doerle, Blumner, the "Big" Tripler, Oscillodyne, Denton "Stand-by," Megalyne Tripler; "Hobo-Fruiter," 2-Tube Superhet, Minklyn, "Lup-tery," "Doerle" 2-tube A.C., "Doerle" 2-tube A.C. Double Signal Tripler, Duo R.F. 4-tube Receiver, The Sergeant 9-33 Tapped Coil Receiver, Globe-Glimmer 7, The 2-Tube "Champ"—2 Tubes Equal 3. Ham Band "2-Tube Peg-Wee" With All-Way 6, Denton Economy 3, 2 Tube "Regenerative-Oscillodyne" will be found here, with full descriptions. In many cases, we have also included a picture of the set for those who do not wish to follow the regular symbolic hook-up, but wish to have a regular wiring diagram. This is a very handy volume, especially for those "fans" who wish to study the best sets in the short-wave art, from one tube up to ten tubes.

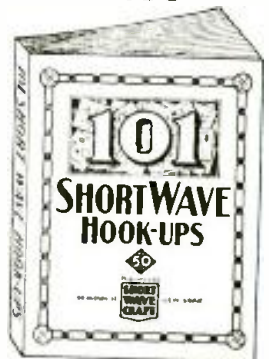

100 Illustrations, 72 Pages. Stiff, flexible covers 50c

HOW TO BECOME AN AMATEUR RADIO OPERATOR

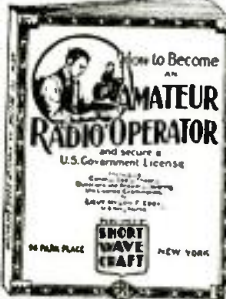

WE chose Lieut. Myron F. Eddy to write this book because his experience in the amateur field has made him pre-eminent in this line. For many years he was instructor of radio telegraphy at the R.C.A. Institute. He is a member of the I.R.E. (Institute of Radio Engineers), also the Veteran Wireless Operators' Association.

If you intend to become a licensed code operator, if you wish to take up phone work eventually—this is the book you must get.

Partial List of Contents

Ways of learning the code. A system of sending and receiving with necessary drill words is supplied so that you may work with approved methods. Concise authoritative definitions of radio terms, units and laws, brief descriptions of common pieces of radio equipment. The chapter gives the working terminology of the radio operator. Graphic symbols are used to indicate the various parts of radio circuits. General radio theory particularly as it applies to the beginner. The electron theory is briefly given, then waves—their creation, propagation and reception. Fundamental laws of electric circuits, particularly those used in radio are explained next and typical basic circuits are analyzed. Descriptions of modern receivers that are being used with success by amateurs. You are told how to build and operate these sets. Amateur transmitters with specifications are furnished so construction is made easy. Power equipment that may be used with transmitters and receivers, rectifiers, filters, batteries, etc. Regulations that apply to amateur operators. Appendix which contains the International "Q" signals, conversion tables for reference purposes, etc.

50c 150 Illustrations, 72 Pages, Stiff, flexible covers

TEN MOST POPULAR SHORT-WAVE RECEIVERS


—HOW TO MAKE AND WORK THEM

THE editors of SHORT WAVE CRAFT have selected ten outstanding short-wave receivers and their sets are described in the new volume. Each receiver is fully illustrated with a complete layout, pictorial representation, photographs of the set complete, hookup and all worth-while specifications. Everything from the simplest one-tube set to a 5-tube T. R. F. receiver is presented. Complete lists of parts are given to make each set complete. You are shown how to operate the receiver to its maximum efficiency.

CONTENTS

- The Doerle 2-Tube Receiver That Reaches the 12,500 Miles Mark, by Walter C. Doerle.
- T.R.F. Pentode S-W Receiver having two stages of Tuned Radio Frequency, by Clifford E. Denton and H. W. Secor.
- My de Lusa S-W Receiver, by Edward G. Ingram.
- The Binswett 2-Tube 12,000 Mile DX Receiver, by A. Binswett, Jr.
- Build a Short-Wave Receiver in Your "Brief-Case," by Hugo Gernsback and Clifford E. Denton.
- The Denton 2-Tube All-Waves Receiver, by Clifford E. Denton.
- The Denton "Stand-By," by Clifford E. Denton.
- The "Stand-By" Electrified.
- A COAT-POCKET Short-Wave Receiver, by Hugo Gernsback and Clifford E. Denton.
- The S-W PENTODE-4, by H. G. Cisin, M. E.
- Louis Martin's Idea of A GOOD S-W RECEIVER, by Louis Martin.

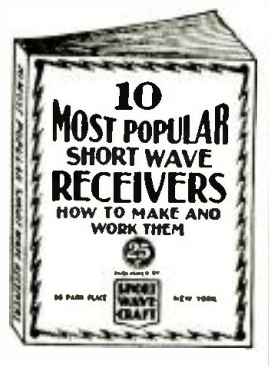75 Illustrations, 40 Pages, Stiff, flexible covers 25c



OVERSEAS READERS!

These books can be obtained from the following houses:

GREAT BRITAIN
Gerringe's
9a, Green Street, Leicester Square
London, England

FRANCE
Editions Radio
42 Rue Jacob
Paris

AUSTRALIA
McGill's
183-195, 218 Elizabeth St.
Melbourne, C. I.

Oh! for a Ham "Shack" Like One of These

(Continued from page 21)

Lt. W. W. Johler

oscillator, a 841 buffer, and a 203A final, and a Collins impedance-matching network. LIEUT. W. W. JOHLER, Kemper Military School, Boonville, Missouri.

W9NTP

(Continued from page 21)

input modulated by a pair of 46's in class "B." I use a Collins 7Y speech amp. which consists of a 53 and a 2A5, and a Turner type G crystal microphone on both of the above rigs. These outfits were built by W9NBZ. The receivers are a RME9D-S.S.S. pictured, and a National ACSW5 Thrill Box not shown. I have a 47 xtal osc. and a 45 final amp. with about 20 watts input on 40 and 80 meter CW on a 3630KC and 7260 KC.

BILLY BRENTLINGER, W9NTP, (The Noisy Talking Politician) 1625 South 11th Street, Terre Haute, Indiana.

Paul Bauerle

(Continued from page 21)

watts input. Rack and panel are made of steel, and all parts well insulated. The station is remote controlled by relays operated by push-buttons on desk.

PAUL BAUERLE, W8AHV, Lansing, Mich.

VU2FY

(Continued from page 21)

so that either receiver may be used by the flick of a switch.

The aerial used is a half-wave Zepp, with 64-foot feeders, and it's non-directional. Efficiency is the keynote of the station which is classed as the finest in all Asia.

LIONEL F. STETSON, 1945 Argyle St., Chicago, Ill.

One Year's Subscription to
SHORT WAVE CRAFT
FREE
for the "Best" Station Photo
Closing date for each contest—75 days preceding date of issue: April 15 for July issue, etc. The editors will act as judges and their opinions will be final. In the event of a tie a subscription will be given to each contestant so tying.

New ACR-175 Amateur Communication Receiver

(Continued from page 23)

single-ended pointer simultaneously traverses a vernier scale of 100 divisions spaced equidistant around the entire circumference of the dial, this pointer making a complete revolution per vernier index division. Thus, any station can be logged accurately by noting in sequence the band letter, vernier index scale number and vernier scale number.

This article has been prepared from data supplied by courtesy of RCA Manufacturing Company.

A Long-Lines Oscillator and Modulator

(Continued from page 28)

erage double-button carbon microphone. As a matter of convenience to the purchaser some antenna specifications are given, which will enable him to construct a fairly efficient radiating system for the Eagle Long Lines Transmitter. This article has been prepared from data supplied by courtesy of Eagle Radio Co.

CLASSIFIED

Advertisements are inserted at 5c per word to strictly amateurs, or 10c a word to manufacturers or dealers. Each word in a name and address is counted. Cash should accompany all orders. Copy for the June issue should reach us not later than April 6.

GENERATORS
TURN SCRAP INTO MONEY. Autopower shows you how easily and economically auto generators can be converted into A.C. or D.C. generators and D.C. motors, 2 to 1000 volts; for sound, radio, power, light, or welding. No previous experience necessary—complete information all in new book, with simple instructions and illustrations. Endorsed by thousands. Only \$1.00 postpaid. Autopower, Inc., 414 S. Hoyne Ave., Chicago.

"HAM" OFFERS AND WANTS
SKYRIDERS CHEAP!—SELL OR trade—Can use cameras, lenses, binoculars, etc. Wells-Smith Radio Corp., 26 N. Wells St., Chicago.

WANTED COPY OF LODGE'S "Signalling Through Space Without Wires." State price and condition. H. W. Secor, % Short Wave Craft, 99 Hudson St., New York City.

SELL OR SWAP CANDLE CODE Course with Key, Phones, Oscillator, 3 Tube battery Short Wave Receiver, Hand Spread Cols. Want 5 Meter Transceiver. W3FYI, Hollywood, Penn.

SALE TRADE KOLSTER 6D Receiver, Bernard AC Test Oscillator, Large Samson Two Fifty Address Amplifier. Want Short Wave Receiver. Glenn Watt, Chanute, Kansas.

I WISH TO TURN SOME OF MY used short wave parts, etc., into cash. Ideal bargains. When writing, state your needs. Albert Freeman, South Hanson, Mass.

NORDEN NAVY MODEL 34, 9 tube superheterodyne, Weston Meters, AVC, 8 to 550 meters, complete \$57.50. Nelson, 3725-64 St., Woodside, N.Y.C.

COMPLETE TWENTY WATT phone transmitter, receiver, and monitor—Twenty dollars. L. N. Wolfe, Monmouth, Illinois.

USED SKYRIDER COMPLETE \$17.50, used Super Skyrider complete \$35.00, used Silver Masterpiece HX complete \$35.00, used Masterpiece 111N complete \$15.00. Write, W9ARA, Butler, Mo.

5 METER AC RECEIVERS \$3.80, Phone Transmitters \$2.75, Postpaid, wired, tested, Edwards, 3512 N. Phillip St., Philadelphia.

INSTRUCTION
AMATEUR LICENSES. Complete training, Resident and correspondence courses. Every graduate a licensed operator. \$1.50 weekly. Booklet, New York Wireless School, 1123 Broadway, New York.

RADIO ENGINEERING. BROADCASTING, aviation and police radio, Servicing, Marine and Morse Telegraphy taught thoroughly. All expenses low. Catalog free. Dodge's Institute, Colt St., Valparaiso, Ind.

MISCELLANEOUS
OHM'S LAW CALCULATOR—Lightning Slide Rule; solves all problems of Voltage, Current and Resistance, Power, Wire Sizes, etc. Range: 1 micro-amp. to 1000 amps.; 1 micro-volt to 10,000 volts; 1 micro-ohm to 10 megohms; 1 micro-watt to 10 megawatts; wire sizes 0 to 36 B. & S. gauge. Introductory Price \$1.00 prepaid. The Dataprint Co., Box 322, Ramsey, N.J.

QSL—CARDS—SWL
SHORT WAVE LISTENER'S, QSL Cards. Attractive. Reasonable. Samples (8 stamps), W-8-E-S-N, 1827 Cune, Toledo, Ohio.
DIRECTORY—100 SWL TRADERS—10c! Glenn Godwin, 5 Mildred, Binghamton, New York.
SWL'S WITH OFFICIAL SHORT Wave League Emblem, W9NIF, Spring Road, Hinsdale, Ill.
QSL CARDS, NEAT, ATTRACTIVE, reasonably priced, samples free. Miller, Printer, Ambler, Pa.

RADIO ENGINEERING
EXACT COPIES OF APPARATUS described in this magazine or any other radio equipment—custom built with parts bought at lowest prices anywhere! Expert workmanship. Results guaranteed. Quotations cheerfully given. Custombuilders, Dept. A, 113 West 57th, New York City.

SHORT WAVE RECEIVERS
INSTRUCTIONS 18 DISTANCE Crystal Sets—record 2100 miles; "Radiobuilder" year; 25c. Laboratories, 151-A Liberty, San Francisco.

SHORT WAVE SETS BUILT Right. Guaranteed. John Keegan, Childs, Pa.

IN STOCK: PR-16s \$95.70 complete prepaid, PR-16c's \$101.70 prepaid, Bretting 12s \$93.00 prepaid, Super-Sevens \$49.50, 89 Super Skyriders \$79.50, 8X9s \$89.50, ACR-175 \$119.50, National, Hammarlund receivers. Trade-in your receiver. Code machines rented. Write, Henry Radio Shop, Butler, Missouri.

RECEIVERS—NEW AND USED, sold and traded in. Hammarlund, Nationals, RME, Skyrider. Schwarz Radio Service, 15 Lawrence Ave., Dumont, N. J.

TRANSMITTING EQUIPMENT
ALL METAL CRYSTAL HOLDER, for Transmitters, guaranteed \$1.45. Schwarz Radio Service, Dumont, N. J.

CRYSTALS 80 AND 160 METER bands 95c. A stock of 1,000 crystals insures you prompt delivery. New type shielded holder 60c. Fits five or seven prong socket. Specify type. White Radio Laboratory, Sandpoint, Idaho.

S. W. COMPONENTS
PLUG-IN COILS. WRITE FOR catalogue. Noel, 728 Birch, Scranton, Pa.

FREE—

NEW 1936 BARGAIN RADIO TREATISE
64 Illustrated Pages—Two Colors
For Radio Servicemen, Dealers, Experimenters and Short-Wave Fans.

Get this FREE Radio Treatise and data book today. Merely send a 2c stamp for postage together with your name and address. No waiting; book by return mail.

Contains valuable radio information, diagrams, useful formulae, short-wave hook-ups and coil-winding data, hints on receiver circuit analysis, calculation of shunts and multipliers, etc.

Aside from this, you will find a large array of interesting radio merchandise such as European, American and Short-Wave receivers; Public Address apparatus from 6 up to 40 watts; new all-metal tube equipment; etc. etc.

WRITE TODAY—Enclose 2c stamp in letter for postage. Radio Treatise sent by return mail. **IT'S ABSOLUTELY FREE.**

RADIO TRADING CO.
101A Hudson St. New York, N. Y.

AMATEUR HANDBOOK **NEW from RESISTOR HEADQUARTERS**

24 pages of ingenious tables and charts tell how to choose voltage dividers, bleeder resistors, filament rheostats, etc., without difficult calculations or formulas. Complete data on hand-switching. Price 10c from your jobber or Ohmite Mfg. Co., 4839 Flournoy St., Chicago.

We Make to Your Specifications

Metal Cabinets, Chassis, Shield Cans to fit Chassis, Panels—Aluminum or steel.


Send us your drawing for estimates.

KORROL MFG. CO. Inc., Dept. S-5
232 Greenwich St., New York City

Please mention SHORT WAVE CRAFT when writing advertisers

W2AMN's All-Band Transmitter

(Continued from page 11)

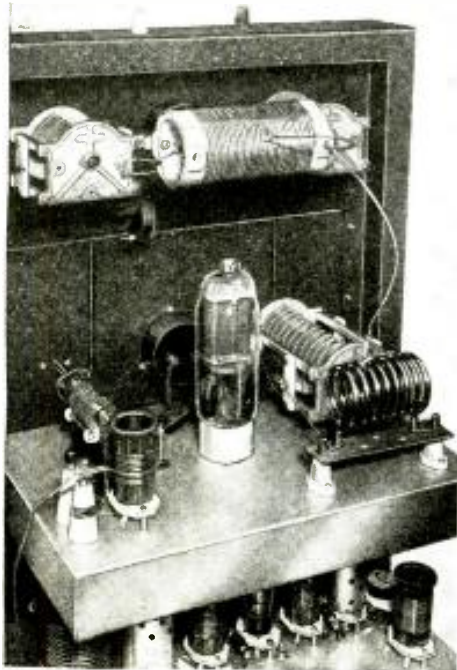

This view clearly shows the antenna tuning "network," together with a complete pentode final amplifier. The plate tank coil and tuning condenser are on the right, and the grid tuning circuit is on the left.

voltage ratings, because a failure of a part due to breakdown can cause serious damage and no doubt, where high-power equipment is used, considerable expense.

The modulator is very simple and adequate for close-talking into a crystal microphone and of course for natural operation of a double-button carbon mike. Any fairly high-gain audio amplifier, delivering an output of from three to five watts, will serve.

Key-down meter readings of the transmitter as described will be as follows. Plate current maximum 160 ma. Screen current max. 50 ma. D.C. grid current max. 18 to 20 mills. Output 240 watts with 2,000 volts on the plate, 45 plus on the suppressor and 45 minus on the control grid. These are for "CW" operation.

For "phone"—plate current 75 ma., grid current 15 ma. 135 volts negative on the suppressor and 45 volts negative on the control grid. Screen-grid current 50 ma. carrier output, approximately 55 watts. The above is for the 803.

If the RK28 is used the readings will be approximately the same except that the suppressor negative voltage will only have to be around 45 to 50 for phone.

This transmitter was used in every band from 80 down to 10 meters. And the ten meter operation was quite surprising; good output was obtained on both phone and C.W. with the plate voltage reduced to around 1,500. The phone carrier appeared to be around 30 watts and over 130 on C.W. We worked Europe, Asia and Africa the first week on the air, with the transmitter in the 10 meter band. On other bands the DX was equally as gratifying.

Amplifier Plate Coil Data

80 m. band. 22 turns of No. 12 tinned copper wire on a Bud 3 in. dia. grooved ceramic form.

40 m. band. 16 turns of ¼ in. copper tubing 2 ¾ in. inside diameter wound to a 5 ½ in. length.

20 m. band. 8 turns ¼ in. copper tubing 2 in. inside diameter, wound to a length of 3 ½ in.

10 m. band. 4 turns of 3/16 in. copper

tubing 1 in. inside diameter, wound to a length of 3 ½ in.

Two sets of jacks are provided for these coils, one set spaced 5 ½ inches and another 3 ½ inches. They are Bud medium size (1 ¼ in.) jacks and plugs.

Amplifier Grid Coils

80 m. band. 38 turns No. 22 D.C.C. close wound.

40 m. band. 8 turns No. 22 D.C.C. close wound.

20 m. band. 8 turns No. 22 D.C.C. spaced to length of 1 ½ in.

10 m. band. 3 ½ turns No. 22 D.C.C. spaced to length of ¾ in.

The grid coils are all wound on 4 prong XP-53 Hammarlund coil forms, 1 ½ in. diameter.

Antenna Loading Coil

34 turns of No. 12 tinned wire on a 3 in. Bud ceramic form with clip to short out unused turns for the higher frequency bands.

Link coupling consists of one turn each end of twisted pair of heavy wire.

Power Amplifier Unit

3—.001 mf. mica condensers (5,000 volt) Aerovox.

3—.001 mf. mica condensers (1,000 volt) Aerovox.

2—.002 mf. mica condensers (5,000 volt) Aerovox.

1—50 mmf. midget variable condenser, Hammarlund.

1—100 mmf. transmitting condenser (6,500 volt), Hammarlund.

2—200 mmf. transmitting condensers (2,000 volt), Hammarlund.

1—50,000 ohm 200-watt resistor with slider, I.R.C.

1—10,000 ohm 10-watt resistor, I.R.C.

1—0—200 ma. meter, Triplett.

1—0—2.5 amp. thermo-couple meter, Triplett.

2—3 in. grooved coil forms (ceramic), Bud.

1—5 prong large socket for 803, Bud.

4—4 prong XP-53 coil forms, Hammarlund.

1—Transmitting R.F. choke, Hammarlund.

1—19x10 ¼ in. panel, Wholesale Radio.

1—2 ¼ x11 in. chassis for above, Wholesale Radio.

2—4 ½ in. dials and flange-type knobs, I.C.A.

2—3 ½ in. dials and flange-type knobs, I.C.A.

1—803 tube, R.C.A.

Jacks, switches, etc.—Bud.

Power Supply Unit

2—2 mf. high-voltage filter condensers (3,000 volt) Sprague.

2—15 henry 250 ma. Filter chokes, Thordarson.

1—100,000 ohm 200-watt resistor, I.R.C.

1—2 ½-volt, 10 ampere, filament transformer, Thordarson.

1—high-voltage transformer, 2,300 volts each side of center-tap, with split primary, Thordarson.

1—10-volt filament transformer, Thordarson.

2—front-panel mounting sockets for 866's, Bud.

2—866 tubes, R.C.A. Radiotron.

1—19x10 ¼ in. panel, Wholesale Radio.

Modulator

1—300-volt power transformer, Thordarson.

2—30 henry "receiving type" chokes, Thordarson.

3—8 mf. electrolytic condensers, Cornell-Dubilier.

1—15,000 ohm 25-watt resistor, I.R.C.

1—suppressor-grid coupling transformer for pentode, Thordarson.

1—3 meg. ½-watt resistor, I.R.C.

1—3,500 ohm ½-watt resistor, I.R.C.

2—100,000 ohm ½-watt resistor, I.R.C.

2—¼ meg. ½-watt resistor, I.R.C.

1—500 ohm, 1-watt resistor, I.R.C.

The above small resistors are I.R.C. insulated type.

2—.1 mf. by-pass condenser, Cornell-Dubilier.

3—4 mf. by-pass condenser, Cornell-Dubilier.

1—20 mf. by-pass condenser, Cornell-Dubilier.

1—.006 mf. by-pass condenser, Cornell-Dubilier.

1—57 tube, R.C.A. Radiotron.

1—2A5 tube, R.C.A. Radiotron.

1—80 tube, R.C.A. Radiotron.

1—panel 19x8 ¾, Wholesale Radio.

General

4—"heavy-duty" layer-built 45-volt batteries, Eveready. (These also serve as bias for low-power stages.)

1—6 foot by 19 inches relay rack, Wholesale Radio.

Rack and panels are finished in black crackle enamel. The various insulators, jacks and switches used were Bud. The relays were constructed from material on hand. However any efficient commercial type relay may be used. The microphone shown in the photo is an Astatic crystal microphone.


5 Meter "Long Lines"

(Continued from page 28)

without turning off the plate supply voltage. In this particular model, larger copper tubing is used than found in the average transmitter, and it can be expected that the efficiency will be somewhat increased because of this fact.

The design is such that the transmitter can be fastened to the wall or mounted on a table; rigidity is one of its outstanding features.

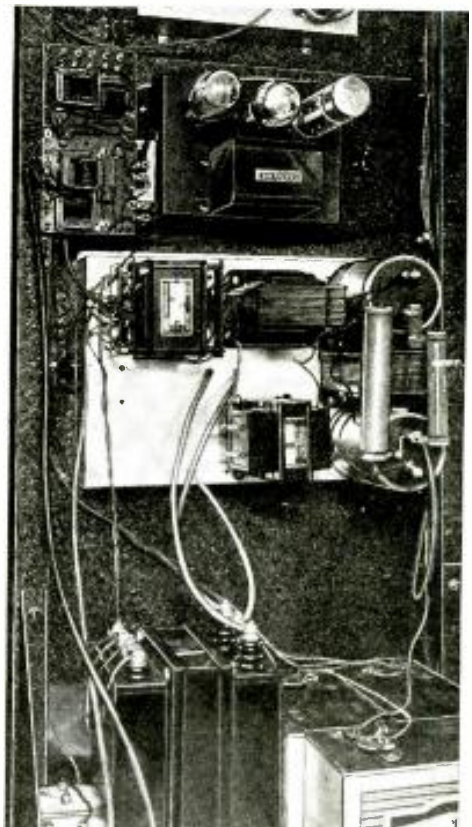This article has been prepared from data supplied by courtesy of American Radio Hardware Co.



This view shows the high-voltage "power-supply" and the modulator, with the relay panel in the upper left-hand corner.

● Index to Advertisers ●

A	
Ace Radio Laboratories.....	42
Aerovox Corporation.....	55
Allied Radio Corp.....	49
American Micophone Co.....	55
American Radio Hardware Co.....	44
Astatic Microphone Laboratory, Inc.....	38
B	
Birnbaach Radio Co., Inc.....	38
Biley Electric Co.....	40
Breakers, The.....	40
Brush Development Co., The.....	51
Bud Radio, Inc.....	51
C	
Cameradio Co.....	57
Candler System Co.....	38
Cannon, C. F., Co.....	48
Centrallion Engineering Co.....	51
Chicago Radio Apparatus Co., Inc.....	48
Classified Advertisements.....	61
Commonwealth Products Company.....	42
Cornell-Dubilier Corporation.....	38
Coyne Radio & Electrical School.....	3
Crowe Name Plate & Mfg. Co.....	39
D	
Dataprint Company.....	59
Davega.....	59
Dodge's Institute.....	46
E	
Eagle Radio Co.....	63
Eilen Radio Laboratories.....	37
Electrad, Inc.....	38
Electric Institute, Inc.....	5
Everyday Science & Mechanics.....	55
F	
First National Television, Inc.....	46
G	
General Engineering Corp.....	63
Goldentone Radio Co.....	63
Gold Shield Products Co.....	42, 53
G-S Radio Company.....	Inside Front Cover
H	
Hallcrafters, The.....	41
Hammarlund Manufacturing Co., Inc.....	40
Harrison Radio Company.....	39, 45
I	
Instructograph Company.....	40, 46
Insulcort Corp. of America.....	53
International Correspondence Schools.....	46
International Radio Corporation.....	59
J	
Jobs & Careers.....	47
K	
Korrol Mfg. Co., Inc.....	61
L	
Lancaster, Allwine & Rommel.....	48
Lejay Manufacturing Co.....	63
Lynch, Arthur H., Inc.....	45
Mc	
McElroy, T. R.....	38
M	
M. & H. Sporting Goods Co.....	40
Marine Radio Company.....	47
Midwest Radio Corp.....	Back Cover
Miller, J. W., Co.....	63
N	
National Carbon Co., Inc.....	43
National Company, Inc.....	Inside Back Cover
National Radio Institute.....	1
O	
Ohmite Mfg. Co.....	61
Oxford-Tartak Radio Corp.....	48
P	
Pilot Radio Corporation.....	44
R	
Radio & Television Institute, Inc.....	46
Radio Constructors Labs.....	43
Radio-Craft.....	46
Radio Handbook, The.....	46
Radio Publications.....	51, 52
Radio Trading Co.....	56, 61
Radio Training Assn. of America.....	46
RCA Institutes, Inc.....	46
RCA Manufacturing Co., Inc.....	47, 59
Rim Radio Mfg. Co.....	63
S	
Sargent, E. M., Co.....	45
Short Wave Coil Book.....	57
Short Wave Guide.....	64
Short Wave League.....	48, 58
Short Wave Listener Magazine.....	53
Short Waves.....	50
Sprague Products Co.....	42
Sundt Engineering Corp.....	53
T	
Teleplex Co.....	46, 63
Thordarson Electric Mfg. Co.....	48
Trimm Radio Mfg. Co.....	42
Triplett Electrical Instrument Co.....	53
Try-Mo Radio Co., Inc.....	55
U	
Uncle Dave's Radio Shack.....	42
United Radio & Tel. Co.....	57
Uno All-Wave Coil Co.....	41
W	
Wellworth Trading Company.....	45, 55
Wholesale Radio Service Co., Inc.....	53
Wright-DeCoster, Inc.....	57
X	
X.L. Radio Laboratories.....	42

(While every precaution is taken to insure accuracy, we cannot guarantee against the possibility of an occasional change or omission in the preparation of this index.)

Two New Tubes

(Continued from page 57)

D.C. Plate Voltage—750—1000 Volts.
D.C. Grid Voltage (Approx.)—290—310 Volts.
Peak R.F. Grid Voltage (Approx.)—415—435 Volts.
D.C. Plate Current—90—90 Milliampers.
D.C. Grid Current (Approx.)—20—17.5 Milliamperes.
Driving Power (Approx.)—7.5—6.5 Watts.
Power Output (Approx.)—42—58 Watts.

As R.F. Power Amplifier and Oscillator—Class C Telegraphy

Key-down conditions per tube without modulation

D.C. Plate Voltage—1250 max. Volts.
D.C. Plate Current—100 max. Milliampers.
D.C. Grid Current—20 max. Milliampers.
Plate Input—125 max. Watts.
Plate Dissipation—50 max. Watts.

Typical Operation:

Filament Voltage (A.C.)—7.5—7.5—7.5 Volts.
D.C. Plate Voltage—750—1000—1250 Volts.
D.C. Grid Voltage (Approx.)—175—200—225 Volts.
Peak R.F. Grid Voltage (Approx.)—300—325—350 Volts.
D.C. Plate Current—90—90—90 Milliampers.
D.C. Grid Voltage (Approx.)—20—17.5—15 Milliampers.
Driving Power (Approx.)—5.5—5—4.5 Watts.
Power Output (Approx.)—42—58—75 Watts.

Cathode Ray Oscillograph

(Continued from page 53)

and a rapid "cut and try" procedure may be used.

A transient is usually a rapid intense change in voltage in a circuit, accompanied by a corresponding change in current, serving to temporarily unbalance all voltages, excite circuits by "impact," modulate voice, D.C. and high frequency components and cause general trouble.

While most other troubles of a periodic or recurrent nature can be identified, measured and controlled by ordinary means although tedious, the Cathode Ray Oscillograph is the only instrument yet developed that can deal directly with transients.

"Keying" Problems

If, for example, we attached the top vertical plate of the Cathode Ray Oscillograph to point 1 of Fig. 6A, and the lower one to point 2 while the horizontal ones were being supplied with the highest possible frequency saw-tooth wave (between 90 and 100 kc.) we might get a pattern somewhat like that in Fig. 6B, which would indicate serious key clicks in the transmitted wave as well as broadness of transmission. A condenser across the key might reduce as in Fig. 7B or even intensify this effect as in Fig. 7C, due to instantaneous charging. A resistor in series with the condenser to reduce its charging rate when the circuit is opened will be very helpful. If made variable, the resistor may be varied for minimum transient effects for both opening and closing of the key circuit. Good key operating characteristics are indicated in Fig. 8B with the circuit of Fig. 8A. The adaptability of chokes in various key circuits may also be given a decisive test in this way. These problems are almost entirely a matter for the Cathode Ray Oscillograph, as the "ham" has nothing else but his ear by which to make circuit corrections of this nature.

Degrees of coupling to prevent transient effects and the formation of sub-harmonics due to "tight coupling" may be discovered. The antenna may be adjusted to the best possible impedance match to the transmitter circuits by variation of factors controlling the impedance of each circuit until the best product of oscillograph amplitude and antenna current exists.

(This article was specially prepared for SHORT WAVE CRAFT by Mr. Sprayberry, President of the Sprayberry Academy of Radio.—Editor)

Please mention SHORT WAVE CRAFT when writing advertisers

Calling All HAMS
ANNOUNCING THE LATEST

EAGLE RECEIVING TRANSMITTING APPARATUS

5 METER 2-TUBE LONG LINE OSCILLATOR \$4.95
Less Tubes, Unwired
COMPLETELY WIRED \$5.95
2 RAYTHEON 45 TUBES 84c

EAGLE TUBE MODULATOR \$8.95
24 Watts, Class B, Complete Kit, Unwired, less Tubes & Meter.
Labor for Wiring \$2.00 extra.
TRIPLETT 0-200 MA. METER \$2.94
THREE 46 and ONE 57 RAYTHEON TUBES 1.80

EAGLE 1-TUBE POWER \$12.95 ONE RAYTHEON 83 TUBE
SUPPLY for Modulator
Using Standard High Grade Parts
500 V. 150 Ma. Complete Kit, less Tube, Unwired. Labor for Wiring \$2.00 Extra 53c

EAGLE MINUTEMAN
DESIGNED BY W2CQI AND W2DHN

2-TUBE RECEIVER
2 1/2 to 10 Meter \$4.75
For Complete Details See April Issue of Short Wave Craft, Pages 729 and 751
Less Tubes, Power Supply and Speaker, Unwired
FREE CIRCUITS AND DETAILS ON REQUEST
ORDER DIRECT FROM THIS AD
EAGLE RADIO CO.
84 CORTLANDT ST., Dept. S, NEW YORK CITY

PURE DC POWER PACK MODEL XPC
An efficient power supply for Short-Wave receivers of small transmitters using 2-45 tubes. Delivers 300 volts pure D.C. at 65 M.A., tapped at 180, 90 and 22 1/2 Volts. Also supplies 2 1/2 Volts C.T. at 5 amperes. Requires type 40 tube. Mounted on sturdy steel chassis. \$4.95 Completely wired and tested. YOUR PRICE, less tube. \$4.95
Write for catalog on complete transmitting equipment.
General Engineering Corp., Dept. S-5, Charlotte, Michigan

THE NEW "Rebroadcaster" EXPLORER

Makes any Radio a Complete All-purpose Amplifying System. Attach phonograph pick-up, microphone, or short wave set to its input—for amplification by the entire radio receiver and loud-speaker reproduction with tremendous volume! Also operates as best oscillator wave-meter, etc. Many amazing features.
Net Price, \$8.95 complete less tube. Send now for FREE Literature.



RIM RADIO MFG. CO., 693 Grand St., Brooklyn, N. Y.

RADIOS..SAVE UP TO 50%

DEAL DIRECT: Factory Price vs. Many models to select from. AC-DC. All-wave. Extra. Car and new metal Tube Models. Your name and address on postcard brings you N.W. 24 page 1936 Bargain Catalog in colors FREE. Get details of 30-DAY TRIAL plan and Agent-User proposition.
Goldentone Radio Co., Dept. 271 8790 Grand River, Detroit, Mich.


ELIMINATE Line Noise with the NEW MILLER LINE FILTER
J. W. MILLER COMPANY
1971 S. Main St., Los Angeles, Calif.

"HAM" SPECIAL Standard Teleplex
A highly efficient code teacher using heavy specially prepared waxed paper tape, having two rows of perforations. Write for Free folder "S.W. DEALER" Correspondence invited with dealers for protected territories.
We are the originators of this type instrument.
TELEPLEX CO.
72 Cortlandt St., New York City

Build YOUR OWN Slow Speed Wind Charger
from old auto generator. We show you how. Make money building for others. Light your buildings and play radio. Dime brings complete plans and catalog, with 20 other generator changes. Satisfaction guaranteed or dime refunded.
LEJAY MANUFACTURING CO.
1417 W. Lake St., Minneapolis, Minn.

AMAZING!—

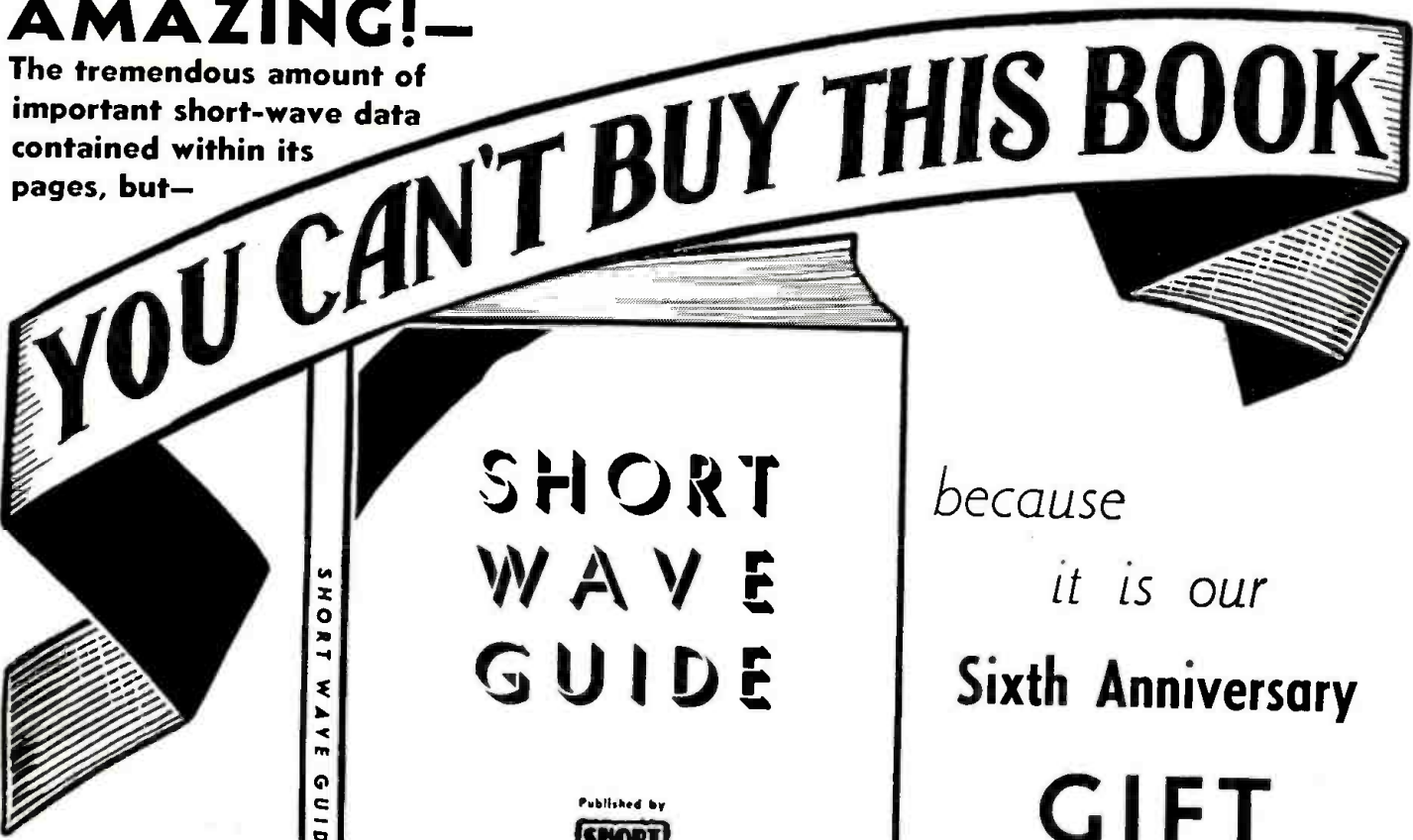The tremendous amount of important short-wave data contained within its pages, but—



because
 it is our
Sixth Anniversary
GIFT
to YOU!

Every short-wave fan should add this new book to his technical library. It is one of the finest books written for those interested in this branch of radio. It's right up-to-the minute in news.

The size of SHORT WAVE GUIDE is 5½x8½ inches—with over a hundred wiring diagrams and photographs.

This year, SHORT WAVE CRAFT celebrates its Sixth Anniversary. Annual increases in circulation, plus authentic, exclusively short-wave editorial material, makes SHORT WAVE CRAFT unquestionably the leading magazine in its field. To commemorate this notable occasion, the Editors have written this outstanding book.

WITH YOUR \$1.00 SUBSCRIPTION TO SHORT WAVE CRAFT MAGAZINE YOU GET THIS BRAND NEW BOOK FREE!

Partial Contents of Short Wave Guide

Short-Wave Questions and Answers

It is impossible to publish each month in SHORT WAVE CRAFT all the questions (and their answers) sent to us from short-wave fans. In view of the importance of these questions (and their answers) we have printed with full illustrations, in SHORT WAVE GUIDE hundreds of those which have been recently received.

Short-Wave Kinks, Illustrated

Every short-wave fan is interested in learning some new kink or short-cut. Dozens of kinks, wrinkles, or "call them what you want" reach us every week—and in SHORT WAVE GUIDE you will find printed and carefully illustrated a variety of them. They will prove valuable to you in more ways than one.

Simple, Efficient Short-Wave Receivers Which Anyone Can Build

Complete constructional plans for building a number of one, two, and three-tube receivers, will also be found in SHORT WAVE GUIDE. Schematic diagrams, lists of parts—everything you need to know to build these sets and make them function properly is included.

If you enter your subscription, during this month only, you will receive, absolutely FREE, a copy of "SHORT WAVE GUIDE." The special subscription rate is 7 months for \$1.00. (Regular newsstand rate is \$1.75.)

Send the coupon today, with your remittance of One Dollar (\$1.00). When your subscription is received, a copy of our SPECIAL ANNIVERSARY GIFT will be sent to you—POSTPAID.

You do not have to be a new subscriber to receive this gift. If you are a subscriber at present, a copy of "SHORT WAVE GUIDE" will be sent you upon receipt of \$1.00, and we will advance your subscription by seven months.

Best Aerials for Short-Wave Reception

The many elaborate antenna systems suitable for short-wave receivers often present problems for set owners. SHORT WAVE GUIDE will give you information which will help you to decide which aerial is best adapted for your receiver. The many types of antenna will be illustrated.

Practical Hints on Short-Wave Tuning

There are thousands of short-wave stations broadcasting daily. Hundreds of these stations are heard by short-wave fans—and hundreds more could be heard distinctly if only you knew more about how to tune them in. Expert advice on proper short-wave tuning is included in SHORT WAVE GUIDE.

"Police Call" Receiver and How to Build It

The most stirring signals on the air today are police calls and every short-wave fan wants to hear these exciting alarms. Complete details for building and operating a "police call" receiver will be found in SHORT WAVE GUIDE.

A Simple "Ham" Transmitter


There are thousands of short-wave fans who want to experiment in building a simple transmitter. Well, here is the ideal transmitter for beginners. It is practical, yet inexpensive to construct. All the details, including list of necessary parts, wiring diagrams, and construction details are included.

SHORT WAVE CRAFT, 99C Hudson Street, New York, N. Y. 5
 Gentlemen: Enclosed you will find my remittance of One Dollar (\$1.00) (Canada and Foreign \$1.30) for which enter my subscription for Seven Months to SHORT WAVE CRAFT. You are also to send me absolutely FREE, and postpaid, a copy of the Special Anniversary Gift Book—SHORT WAVE GUIDE.

Name _____
 Address _____
 City _____ State _____
 New Subscriber Old Subscriber
 Send remittance in form of check, money order or unused U. S. Postage Stamps. (Foreign: Internat'l Postal Money Order.) Register letter if it contains cash or stamps.

Please mention SHORT WAVE CRAFT when writing advertisers

KABLE BROS. CO., PRINTERS

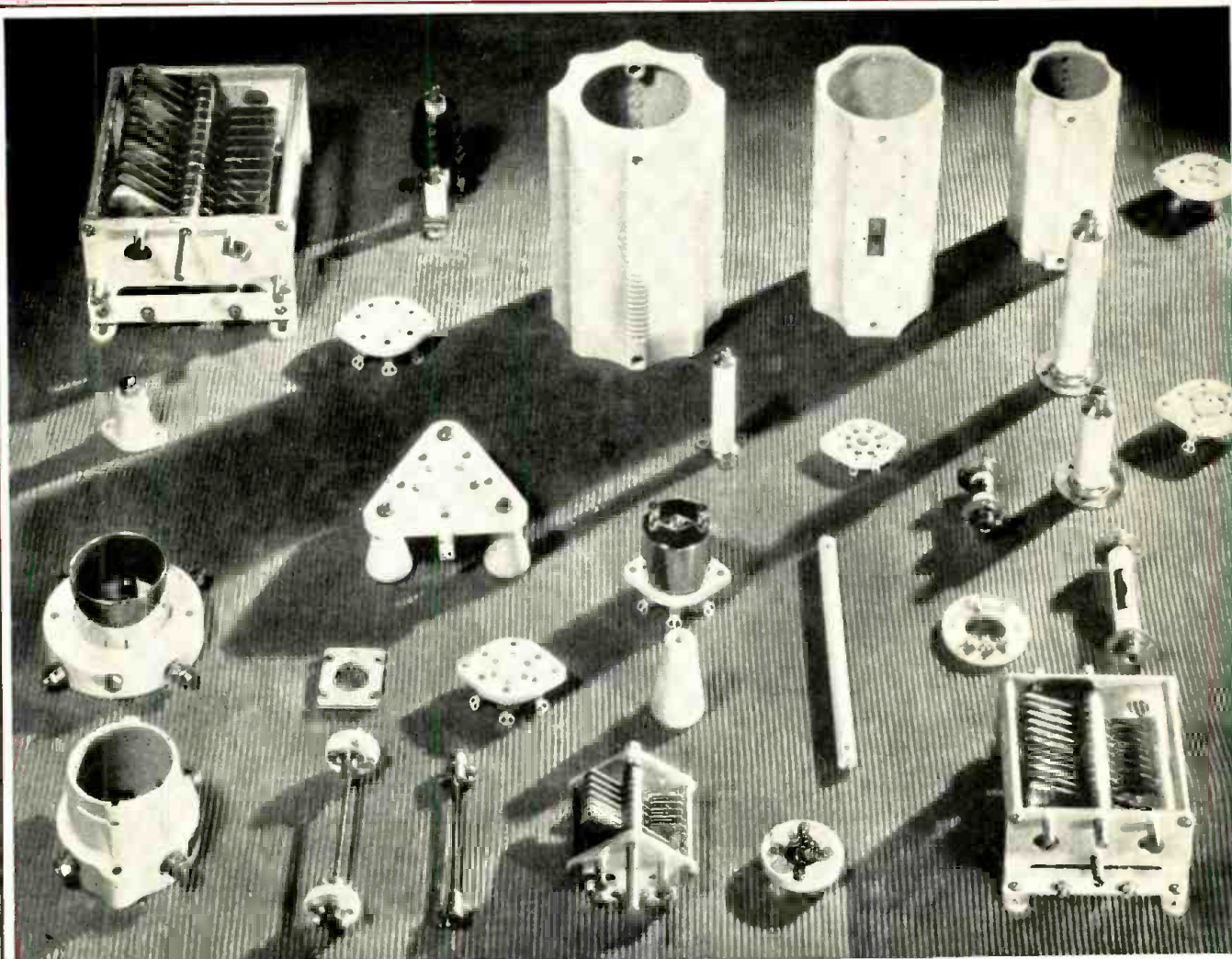

National offers a thoroughly engineered part for nearly every radio purpose. The entire line cannot be compressed into our twenty-page catalogue, much less a single page. But look over the group above. Transmitting condensers from the little 1000 volt TMS in the foreground to the 12,000 volt TMA at the rear. Low loss ceramic coil forms for every amateur band. Low loss sockets for nearly every tube type, from acorns to power pentodes. Flexible couplings from the little TX-12, which will work around a corner, to the big fellows for heavy condensers, high voltages, and low-losses. Strain insulators, spreaders, lead-ins for the antenna: stand-offs, chokes, dials for the rig. National has what it takes.


NATIONAL
61 SHERMAN STREET



COMPANY
MALDEN, MASS.

QUALITY INSIDE AS WELL AS OUTSIDE... *That's the Secret of Midwest's Leadership*

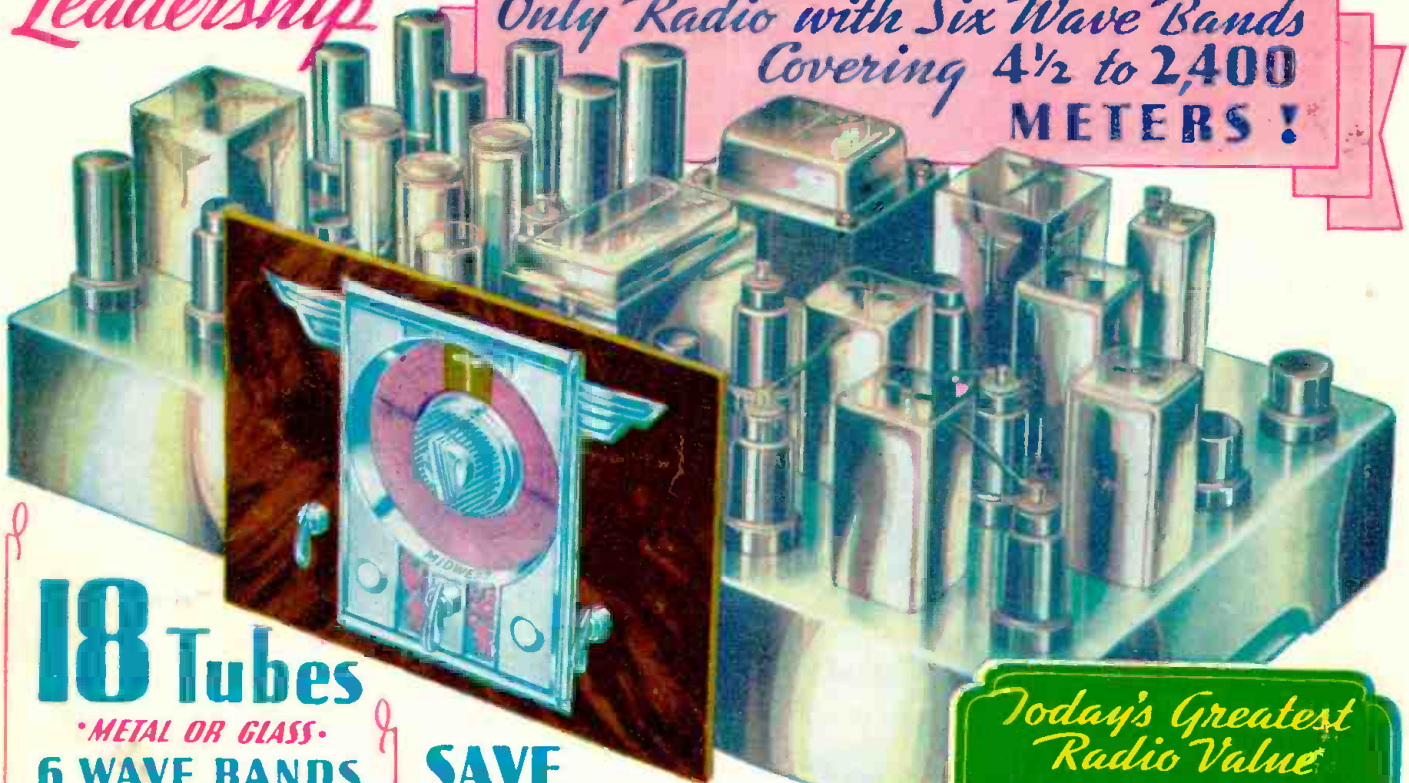Only Radio with Six Wave Bands Covering 4 1/2 to 2,400 METERS!



18 Tubes

METAL OR GLASS

6 WAVE BANDS

80 Advanced Features

18 Tubes and 6 wave bands are but two of the 80 advanced features that include every worthwhile advantage, that even the most critical radio technician and enthusiast could ask for. Some of the other exclusive features are: Station Finder Button, enabling "hams" to secure CW—Silencer Button, which silences the set between stations—38 Tuned Circuits give Maximum Selectivity—4 Gang Condensers—Reinforced Capacitors and Pre-aged Intermediate Frequency Transformers prevent drift, etc. The balance of the 80 features are described in detail on pages 12 to 21 inclusive, of the new FREE 40-page catalog.

Before you buy any radio, write for the free 40-page 1936 catalog, and learn about the successful Midwest Laboratory - To - You policy that saves you 30% to 50%, that gives you 30 days free trial in your own home. No middlemen's profits to pay. You buy at wholesale price, direct from Laboratories... making your radio dollar go twice as far. You can order your 1936 Midwest radio from the new 40-page catalog with as much certainty of satisfaction as if you were to come yourself to our great laboratories.



SAVE

UP TO **50%** Direct from Midwest Laboratories.

ONCE again, Midwest demonstrates its leadership by offering the world's most powerful super deluxe 6-tuning range radio. It is a master achievement...today's most highly perfected, precisely built, laboratory tested unit. It is a radio-musical instrument that will thrill you with its marvelous super performance...glorious new acousti-tone...crystal-clear "concert" realism...and magnificent foreign reception.

Only Midwest Gives 6 Tuning Ranges (4 1/2 to 2400 Meters)

Midwest is the only radio in the world that positively covers every possible and useful wave band. Accurately made, precisely assembled, rigidly tested, this 18-tube Super De Luxe radio assures the brilliant super performance that radio "hams" and enthusiasts demand. The 18 tubes permit of advanced circuits making it possible to use the tremendous reserve power, and to exert the sustained maximum output of the powerful new tubes. These sets are vibration tested, many times, until "creeping screws" and other means of adjustment are locked permanently in position. It is interesting to note that this is the only home receiver that is "aged." All shrinkage and drift are completely eliminated by the use of such features as reinforced capacitors, pre-aged intermediate frequency transformers, as well as elaborate pre-aging tests and processes.



Today's Greatest Radio Value

\$77.45

COMPLETE with 18 Tubes and GIANT THEATRE-SONIC SPEAKER

TERMS AS LOW AS \$5.00 DOWN

The Midwest "A" band chart, illustrated at left, shows how the perfect reception of the Midwest equalizes the widely varying powers assigned to those fortunate stations enjoying cleared channel and semi-cleared channel broadcasting. These stations come in clearly and with equal volume. The short wavering lines indicate that many stations are operating on the same wave length. These stations are useful only when one of them is located close to your set. Charts, illustrating the stations that can be secured on the five additional bands, are pictured on pages 20 and 21 of the Midwest catalog. You save 30% to 50%...you get 30 days FREE trial...as little as \$5.00 down puts a Midwest radio in your home. You are triply protected with a One-Year Guarantee, Foreign Reception Guarantee and Money-Back Guarantee. Write for FREE 1936 catalog. See for yourself that this super radio will out-perform sets costing two and three times as much.

MAIL COUPON TODAY for FREE 30-DAY TRIAL OFFER and 40-PAGE FOUR COLOR CATALOG

MIDWEST RADIO CORPORATION, Dept. 14-M, Cincinnati, Ohio.

Without obligation on my part, send me your new FREE catalog, complete details of your liberal 30-day FREE trial offer, and FREE Miniature Rotating 18-tube Dial. This is NOT an order.

Name _____

Address _____

Town _____ State _____

Check if interested in a Midwest All-Wave Battery Radio

User-Agents Make Easy Extra Money
Check Here for details