

SILICON CHIP



MARCH 2021
ISSN 1030-2662
9 771030 266001
\$995* NZ \$1299
03

The VERY BEST DIY Projects!

High-Current Battery Balancer




Isolated Serial Link



use it with our Battery Balancer

FREE with this issue*

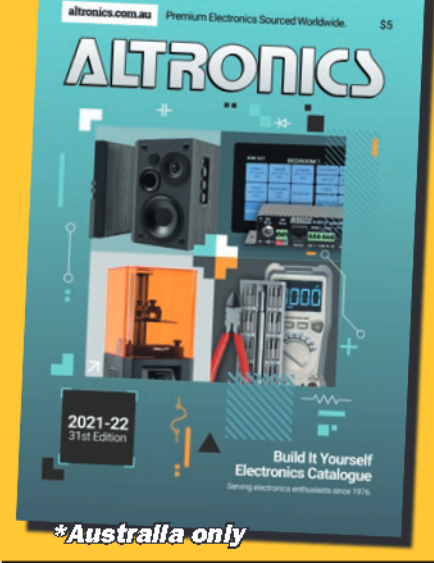

*Australia only

The History of Videotape

quadruplex | helical scan | cassettes | digital

All About Capacitors

how they work and where to use them

Want to build your very own Smart plug?

Here's a great project that lets you use your Smartphone (using Bluetooth®) to turn on/off any appliance such as a TV, computer, table lamp, etc. directly from the power point without getting up off the couch or out of bed.

SKILL LEVEL: Beginner

CLUB OFFER
BUNDLE DEAL
\$69⁹⁵
SAVE 20%
KIT VALUED AT \$89.75




For step-by-step instructions scan the QR code.

www.jaycar.com.au/bluetooth-powerpoint
See other projects at www.jaycar.com.au/arduino

What You Need:

- | | |
|---|----------------|
| 1 x Arduino® Compatible UNO Board | XC4410 \$29.95 |
| 1 x Arduino® Compatible Bluetooth®V4.0 BLE Module | XC4382 \$29.95 |
| 1 x Wireless Transmitter Module 433MHz | ZW3100 \$13.95 |
| 1 x Mains Outlet | MS6149 \$9.95 |
| 1 x 40 Piece 150mm Plug to Socket Jumper Leads | WC6028 \$5.95 |

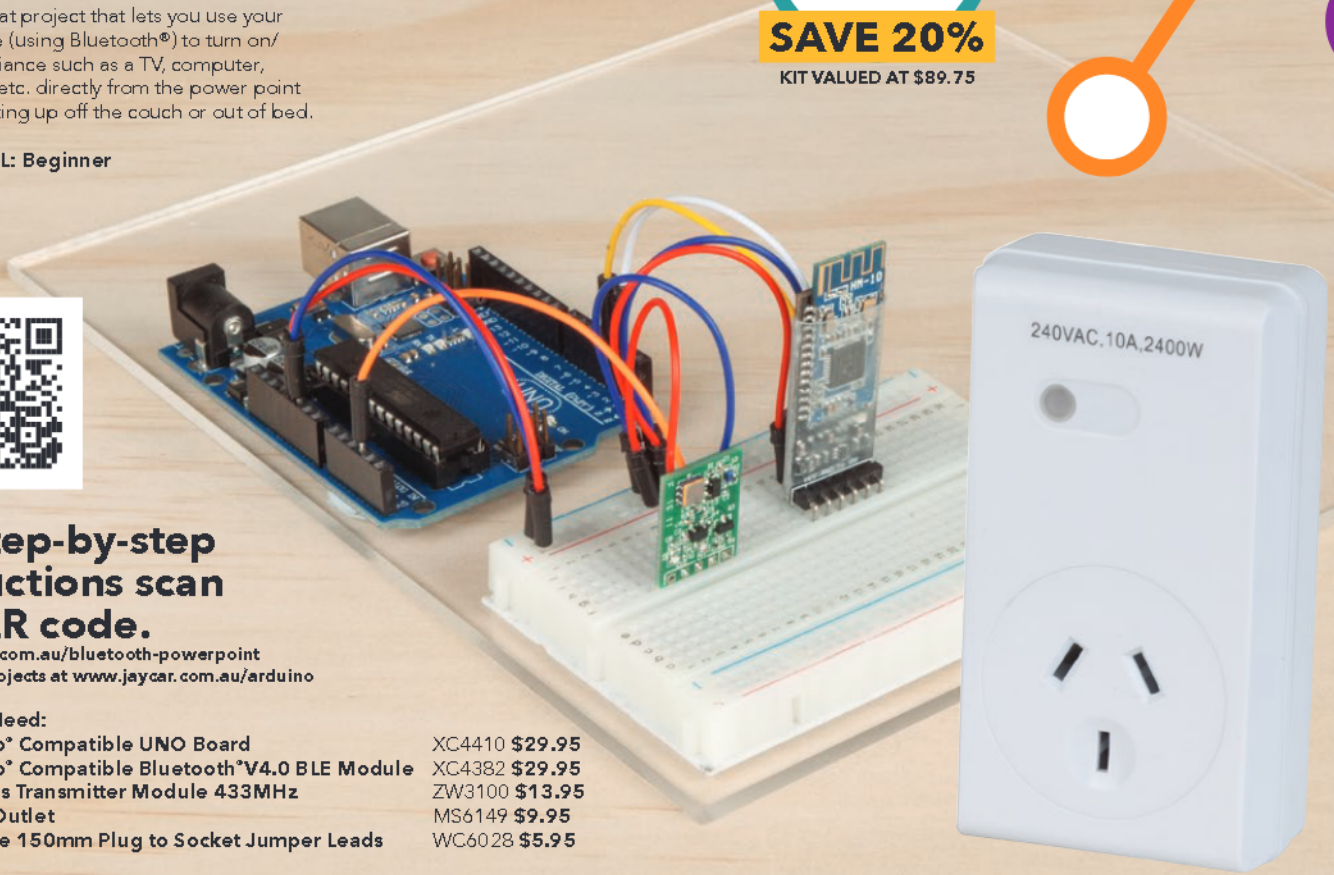

JUST
\$14⁹⁵

Jumper Leads Mixed Pack 100 Pieces
A mixed pack of jumper leads for your Arduino®, breadboarding and prototyping projects. 150mm long. WC6027

JUST
\$39⁹⁵

Light Duty Hook-up Wire Pack 8 Rolls
Quality 13 x 0.12mm tinned hook-up wire on plastic spools. 8 rolls of different colour included. 25m on each roll. WH3009

JUST
\$44⁹⁵

Heatshrink Pack with Gas Powered Heat Blower
An assortment of 160 heatshrink tubes in 7 different colours and sizes, plus 1 gas powered heat gun with Piezo ignition. TH1620

\$100
gift card

Got a great project or kit idea?

If we produce or publish your electronics, Arduino or Pi project, we'll give you a complimentary \$100 gift card.
Upload your idea at projects.jaycar.com

Looking for your next build?

Silicon Chip projects:
jaycar.com.au/silicon-chip-kits
Kit back catalogue:
jaycar.com.au/kitbackcatalogue

Awesome projects by

On Sale 24 February to 23 March, 2021

jaycar
think. possible.



1800 022 888
www.jaycar.com.au

Shop online and enjoy 1 hour click & collect or free delivery on orders over \$99*

*Exclusions apply - see website for full T&Cs.

Contents

Vol.34, No.3

March 2021

SILICON CHIP

www.siliconchip.com.au

Features & Reviews

10 Hoarding: Urban Electronic Archaeology

Sorting through an extensive collection of electronic items is a task not too dissimilar to working on an archaeological dig site. It's why it's important to have items properly recorded to help sort the 'rubbish' from the 'gems' – by Dr David Maddison

30 Fetrons, and the All-Fetron Radio

Fetrons are a solid-state replacement (typically drop-in) for pentode (sometimes triode) valves. I was so fascinated by them I decided to design a radio using only Fetrons – by Dr Hugo Holden

44 The History of Videotape – Quadruplex

The first article in a series of four detailing the history of tape-based recording, starting with Ampex's quadruplex recorder and ending with the move to digital video – by Ian Batty, Andrew Switzer & Rod Humphris

72 All About Capacitors

There's a lot to consider when choosing what capacitors to use for a design, due to the huge variety of them. This article explains how most capacitors are made, how each type differs and what performance you can expect – by Nicholas Vinen

Constructional Projects

21 High-Current Four Battery/Cell Balancer – Part 1

Many battery balancers are inefficient due to dumping excess charge for a given cell. But our new Battery Balancer redirects that extra charge into other cells, charging faster with little heat or waste – by Duraid Madina

68 Mini Isolated Serial Link

This postage-stamp sized module provides isolated, bi-directional, full-duplex serial communications. It can easily be used with our new Battery Balancer to charge even more batteries or cells – by Tim Blythman

84 Battery Multi Logger – Part 2

Following on from last month, we will go over the construction, setup, testing and calibration required to finish your Battery Multi Logger – by Tim Blythman

92 Electronic Wind Chimes – Part 2

In the final part of this series, we cover how to modify the wind chime itself so that it can be driven by a series of solenoids. You can then play your own tunes without relying on the wind – by John Clarke

Your Favourite Columns

39 Circuit Notebook

(1) Low-noise mic preamp (2) Two quartz crystal oscillators using a flip-flop (3) Displaying digits using single RGB LEDs (4) The Omnidetector

61 Serviceman's Log

If it isn't one thing, it's another – by Dave Thompson

100 Vintage Radio

Kriesler Triplex 41-21 portable transistor radio – by Ian Batty

Everything Else


- | | |
|-----------------------------|-----------------------|
| 2 Editorial Viewpoint | 107 Ask SILICON CHIP |
| 4 Mailbag – Your Feedback | 111 Market Centre |
| 98 SILICON CHIP Online Shop | 112 Notes and Errata |
| 106 Product Showcase | 112 Advertising Index |




Our Battery Balancer can handle up to four series-connected batteries per unit, and suits most common battery types. It can handle batteries or cells from 2.5-15V, with a charging current up to 50A – Page 21



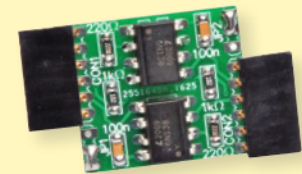A look at the beginnings of videotape recording, starting with systems like the BBC's Vera and Ampex's quadruplex VR-1000A – Page 44



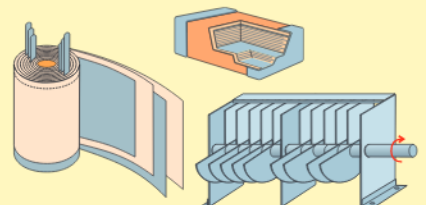This Mini Isolated Serial Link can be used with our Battery Balancer to manage even more batteries or cells. But it's also useful any time you need to send isolated signals between two boards – Page 68



Capacitors come in all shapes and sizes, and because of this it is confusing trying to pick one. So we've detailed some of the important aspects of capacitors, such as dielectrics etc – Page 72

Publisher/Editor
Nicholas Vinen

Technical Editor
John Clarke, B.E.(Elec.)

Technical Staff
Jim Rowe, B.A., B.Sc.
Bao Smith, B.Sc.
Tim Blythman, B.E., B.Sc.
Nicolas Hannekum, Dip. Elec. Tech.

Technical Contributor
Duraid Madina, B.Sc, M.Sc, PhD

Art Director & Production Manager
Ross Tester

Reader Services
Ann Morris

Advertising Enquiries
Glyn Smith
Phone (02) 9939 3295
Mobile 0431 792 293
glyn@siliconchip.com.au

Regular Contributors
Dave Thompson
David Maddison B.App.Sc. (Hons 1),
PhD, Grad.Dip.Entr.Innov.
Geoff Graham
Associate Professor Graham Parslow
Ian Batty

Cartoonist
Brendan Akhurst

Founding Editor (retired)
Leo Simpson, B.Bus., FAICD

SILICON CHIP is published 12 times a year by Silicon Chip Publications Pty Ltd. ACN 626 922 870. ABN 20 880 526 923. All material is copyright ©. No part of this publication may be reproduced without the written consent of the publisher.

Subscription rates (12 issues):
\$105.00 per year, post paid, in Australia.
For overseas rates, see our website or
email silicon@siliconchip.com.au
Recommended & maximum price only.

Editorial office:

Unit 1 (up ramp), 234 Harbord Rd,
Brookvale, NSW 2100.


Postal address: PO Box 139,
Collaroy Beach, NSW 2097.

Phone (02) 9939 3295.

E-mail: silicon@siliconchip.com.au

ISSN 1030-2662

Printing and Distribution:

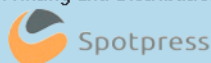

24-26 Lillian Fowler Pl, Marrickville 2204

Editorial Viewpoint



Older devices involved creative engineering

While I am not particularly into 'retro' electronics like vintage radios, vintage computers etc, I find some of the articles on these topics quite interesting. You can tell that the designers of these devices had to be very clever to use the meagre resources available to them to solve some quite tricky problems.

Take the four-part series of articles on Videotape Recording starting in this issue (on page 44). Younger readers (say, those under 30) probably don't remember much about videotape.

I was young when the VHS/Beta 'war' was raging, and by the time I was old enough to use a VCR, VHS had taken over. I remember the machines being quite finicky, and they would sometimes go wrong (in the worst case, 'eating' a tape) for no apparent reason. But for the most part, they worked quite well, albeit with video quality that I now consider awful.

Having read the articles mentioned above, I realise now how complicated the loading systems were. With so many parts having to move in concert, in a device produced at a relatively low cost, it's no wonder they went wrong sometimes! So my hat's off to the engineers that designed those mechanisms; it must have been a lot of effort to get them to work reliably.

Another thing that's apparent in reading these articles is how much 'outside-the-box' thinking went into developing the core technologies enabling video recording, especially helical scan. It seems kind of obvious in retrospect, but it took lots of smart people many years to develop a device which could record an hour or two of video on a reasonably compact, easy-to-use and low-cost cassette.

It was an incremental, evolutionary process too, as is so common with technological advancements. There were several generations of video recording between the first useful machines (Ampex quadruplex) and the final 'sorted' generation of consumer machines, which I guess you could say was hifi VHS.

Each generation made certain improvements, but often retaining shortcomings that would be addressed in future. It helped that the later semiconductor technology allowed more signal processing to be crammed into smaller machines.

I guess my point is that you might enjoy those articles even if you're too young to remember the technology being described, and aren't terribly interested in the topics themselves. You might still learn something and enjoy the journey of discovery.

I can make a similar comment about the article on Fetrons; they are interesting because they give you a glimpse of the transitional period when valves were being phased out in favour of transistors. Again, it took innovative engineering to make transistors operate like valves.

Also, consider some of the techniques described in our Vintage Radio columns like reflexing, combined mixers/oscillators and some of the design choices in early transistor sets. Even if you aren't really into radio, you can appreciate the amount of work that went into getting the most performance out of a few (then costly) active devices.

That's the sort of engineering that I really appreciate, and I think the people who came up with those ideas must have done a lot of brainstorming to reach those 'Eureka!' moments.

Nicholas Vinen

In-Stock@Digi-Key

Reliability You Can Count On



1,200+ INDUSTRY-LEADING SUPPLIERS

1.9 MILLION+ PRODUCTS IN STOCK

NEW TECHNOLOGIES ADDED EVERY DAY

9.6 MILLION+ PRODUCTS ONLINE

**FREE
SHIPPING**
ON QUALIFIED ORDERS*



AUSTRALIA
DIGIKEY.COM.AU
1800 285 719

NEW ZEALAND
DIGIKEY.CO.NZ
800 449 837



*Australia: A shipping charge of \$24.00 AUD will be billed on all orders of less than \$60.00 AUD. A shipping charge of \$20.00 USD will be billed on all orders of less than \$50.00 USD. All orders are shipped via UPS, Federal Express, or DHL for delivery within 3-4 days (dependent on final destination). No handling fees. All prices are in Australian dollar or United States dollar. New Zealand: A shipping charge of \$26.00 (NZD) will be billed on all orders of less than \$66.00 (NZD). A shipping charge of \$20.00 USD will be billed on all orders of less than \$50.00 USD. All orders are shipped via UPS for delivery within 3-4 days (dependent on final destination). All prices are in New Zealand dollar or United States dollar. Digi-Key is an authorized distributor for all supplier partners. New product added daily. Digi-Key and Digi-Key Electronics are registered trademarks of Digi-Key Electronics in the U.S. and other countries. © 2020 Digi-Key Electronics, 701 Brooks Ave. South, Thief River Falls, MN 56701, USA

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

Brushless DC


AC Induction

Stepper

Permanent Magnet Synchronous

Mixed-Signal MCUs Redefined

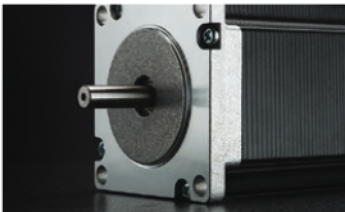Smaller Packages and Upgraded Peripherals for PIC32MK




PIC32MK is a performance-intensive 32-bit Microcontroller (MCU) family with seamlessly integrated analog. Expanding on the lineup of 100- and 64-pin packages, PIC32MK is also now available in a space-saving 48-pin QFN, measuring just 6 x 6 mm for size critical mixed-signal applications.

Optimized for dual motor control systems, these devices are also well-suited for the automotive space, industrial controls, and anywhere else precision analog functions in an MCU are required.

Family Highlights

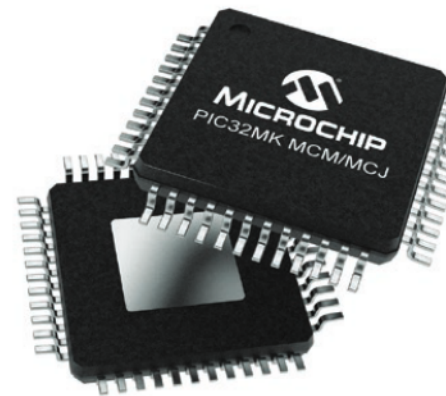- 7x 12-bit 3.75 Msps ADCs, configurable as a single, 12-bit, 25.4 Msps interleaved ADC
- 4x high-bandwidth op amps
- 5x high-speed analog comparators
- Up to 1 MB of ECC enabled Flash and 256 KB of SRAM
- Up to 4x CAN FD and 2x USB controllers
- Package options from 48 to 100 pins in both TQFP and QFN types
- Automotive-qualified (AEC-Q100) - Grade 1



Contact Information

Microchip Technology Australia
Email: aust_nz.inquiry@microchip.com
Phone: +61 (2) 9868-6733

microchip.com/SC-PIC32MK

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

Delivering more

The widest selection of semiconductors and electronic components in stock and ready to ship



au.mouser.com



australia@mouser.com

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

Preview only.

DIY SPEAKER KITS



the **loud**
speaker
kit.com 



Australia's #1 source
for DIY audio kits
& components

**VISIT OUR
ONLINE STORE**

www.theloudspeakerkit.com

Ph: (02) 8120 8010

HOARDING: URBAN ELECTRONIC ARCHAEOLOGY

Don't let this happen to you! If you have a large collection of anything (including electronics), you must have a succession plan. It would also be a good idea for you to periodically 'clean house' and allow collectors – young and old – to pick up items you don't absolutely need.

I recently had the task of sorting through an extensive collection of electronic items which were part of a deceased estate. As I had been a long-time friend of the deceased, I was permitted to 'rescue' any interesting items I found, as they would otherwise end up in a landfill.

There were a vast number of items in the hoard, but before I had a chance to go through it, drug addicts and other thieves were reported to have broken in and taken anything that could be sold on the street.

What remained (see opposite for an example) was of little-to-no monetary value, but still of interest to electronic enthusiasts. In fact, by taking items away, I was probably saving the estate the cost of disposing of them.

The collection was accumulated over a lifetime, mostly being purchased from second-hand markets, one being the well-known Laverton Market in Leakes Rd, Laverton, Vic.

Many of the other items seem to have been discarded by industrial or government laboratories.

Most of the items were filthy, with 50 or so years of accumulated dust and grime, plus damage from being thrown into a heap rather than stacked correctly. To get the items shown here into presentable condition required extensive cleaning

Unlike some hoards, I did not find much actual rubbish, just a lot of 'stuff' in several general categories:

- 1) A staggering number of generic desktop PCs. These were mostly from the 1990s and 2000s, and not collectible computers (such as original IBM, Apple or Commodore PCs

might be). He had told me that he usually paid \$2-5 each for these at the weekend markets.

- 2) Huge numbers of CDs and floppy disks, mostly for computer games, likely never used.
- 3) Many car parts, mostly incomplete or used, mostly Holden-related and including at least two 'grey motors' and one 'red motor'.
- 4) Lots of scrap metal.
- 5) Numerous pieces of electronic or mechanical equipment, usually incomplete or broken, in various states of disassembly with components missing or, in the case of many electrical or electronic items, with the power cords cut off. This is likely because it is illegal in Victoria to sell electrical items without an electrical safety test, and for the low value of many items, that is not worthwhile.
- 6) Many broken items, as items covered the floor nearly everywhere. Apart from a few 'goat tracks' with limited visibility of the floor, mostly one had to walk on these items to move around the house. If they weren't broken when acquired, they soon would be. (Some rooms were unreachable due to items stacked floor to ceiling).

The full extent and composition of the hoard is not known at the time of writing, because what was recovered and presented here is only what was obvious and at the surface level. In many areas, the hoard was a metre or more thick.

A variety of older electronic items I found were handmade for various scientific or technical purposes. Back in the day, it was common for large government, university and com-

By Dr David Maddison

mercial laboratories to make their own equipment as it wasn't always commercially available, or it would take too long to order it from overseas.

The items I recovered represent an interesting cross-section of electronics for virtually the whole of the twentieth century. The collection of articles presented here also includes items he gave me while he was alive.

Where I found multiple similar items, I will show the Australian-made item if there is one.

Postscript

Although my friend was known by work colleagues to be brilliant, when he passed away, there were no funeral arrangements.

So besides showing some interesting items, this article also serves as something of a memorial or tribute to his life.

Appropriately for a collector of electronics, his initials were A. C.



Just a small part of what I was faced with . . . after drug addicts and thieves had already gone through it.

Vintage Gallenkamp switchboard ammeter (1910s)

I found this Gallenkamp ammeter, estimated to be made around 1910, based on a very similar one I found in a catalog (see below). It was found half-immersed in water.




Philips valve radio 'battery eliminator' (1920s)

Valve radio batteries were expensive. These devices replaced two of the three battery types (the "B" and "C" batteries) with a mains supply. The technology at that time made it difficult to eliminate the "A" battery.

The one I found is a Philips 3003, made in Holland and very popular in Australia. It appears that somebody tried to repair it as many wires were disconnected.

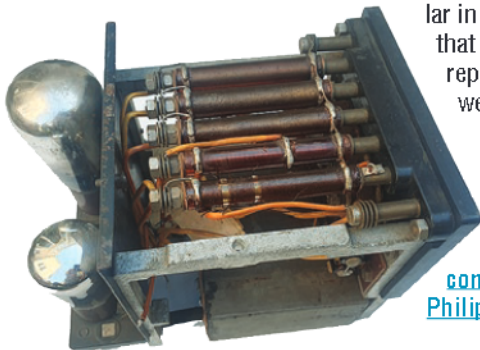For more information on this device, including a circuit diagram, see www.tuberadio.com/robinson/museum/Philips_3003/



Ormond variable condenser (capacitor) (1920s)

This was in a pile of rubbish, but it caught my attention because it had screw terminals. I measured its maximum capacitance as 450pF and determined it to be from the UK brand Ormond, and almost certainly the No. 3 model. It featured "S.L.F." or "straight-line frequency". This meant that through the rotation of the dial, the corresponding frequencies would be linearly proportional to the dial position.

According to Radio Retailing magazine of December 1925, this "improves the tuning of a set and has been developed to meet conditions which were becoming almost intolerable, namely, the crowding of the stations in the lower part of the present broadcast range".

Headphone and headphone parts (1920s to 1940s)

The oldest such item I found was made by Brandes Ltd, London, and marked "superior matched tone". It is one driver from a pair of headphones. According to radiomuseum.org, this item dates from approximately 1924-1932. It is marked "BBC" (probably not the broadcaster) and "Made in England". Its nominal impedance is 1000Ω.

I also found a Brunet & Cie driver from their Casques et Écouteurs Type F model, dated around 1924 (according to radiomuseum.org). It was available with an impedance of either 500Ω or 2000Ω.

Another was a complete set of Australian-made Q-Plus brand headphones. I could not find any information online about them, but Q-Plus was an Australian manufacturer operating from 1947 to at least 1965.



SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

altronics.com.au

Premium Electronics Sourced Worldwide.

\$5

ALTRONICS



2021-22 Catalogue **OUT NOW!**

424 pages filled with the latest in electronics. Over 1200 new lines!

2021-22
31st Edition

Build It Yourself
Electronics Catalogue

Serving electronics enthusiasts since 1976.

Yours FREE with this issue of Silicon Chip. If you didn't receive your copy, contact your newsagent or register at www.altronics.com.au/catalogue to receive one by post for FREE!

1300 797 007

Shop online 24/7 @ altronics.com.au

ALTRONICS

Build It Yourself Electronics Centres®

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

Preview only.



Helping to put you in Control

Universal Input to 4-20mA Transmitter

Universal Thermocouple, RTD and voltage Input to 4-20mA Transmitter mounted in an IP65 weatherproof box.

SKU: KTA-367
Price: \$132.28 ea



ESP32 Controller

Arduino-compatible ESP32 controller with 2 relay outputs, 2 transistor outputs, 2 opto-isolated inputs, 2 0/4-20 mA analog I/Os, 2 0-10 VDC analog I/Os and 4 GPIOs. Interfaces using USB, RS-485 serial, I2C, Wi-Fi or Bluetooth. DIN rail mountable.



SKU: KTA-332
Price: \$251.90 ea

Digirail OEE WiFi

The DigiRail OEE is the ideal tool to monitor and examine the performance of your production lines. It reads the sensors that monitor the operation of machines, devices or processes and determine operation time.

SKU: SIG-111
Price: \$241.95 ea



N1030-RR PID Temperature Controller

N1030-RR Compact sized PID Temperature Controller with auto tuning PID 230VAC powered. Input accepts thermocouples J, K, T, E and Pt100 sensors. Two Relay outputs.



SKU: NOC-322
Price: \$105.55 ea

750W ELDM Brushless AC Servo Motor

Leadshine ELDM8075V48HM-A4 750 W brushless AC servo motor with 1000 line encoder.

SKU: MOT-457
Price: \$306.85 ea



Brushless Servo Motor Drive

The ELD2-RS7030 brushless servo drive, power range from 25W to 1200W, are special DC input, motion control product designed for machines and applications that request a best balance between reasonable cost and outstanding performance with MFC/vibration suppression.



SKU: SMC-411
Price: \$380.83 ea

RTD Temperature probe with magnet fixing

RTD probe with magnet fixing for surface temperature measurement. -50 to 200 °C. Silicon Cable 3 meters.

SKU: CMS-007
Price: \$142.95 ea



**For Wholesale prices
Contact Ocean Controls
Ph: (03) 9708 2390
oceancontrols.com.au**

Prices are subjected to change without notice.

Our capabilities

CNC Machining
UV Colour Printing



Enclosure Customisation



Cable Assembly

Box Build

System Assembly

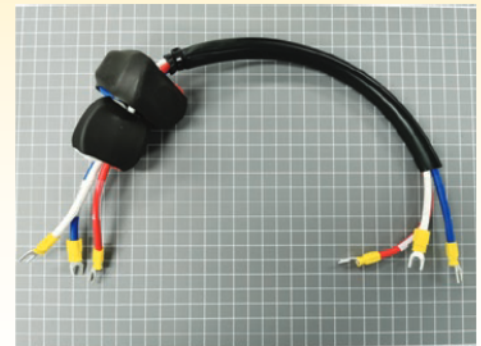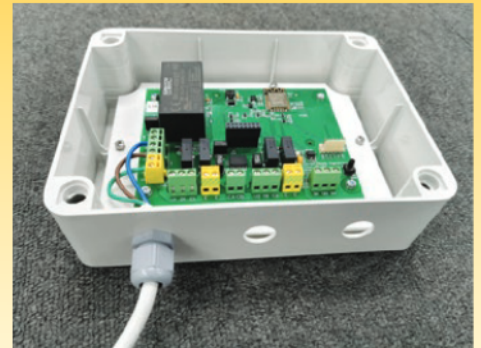

Ampec Technologies Pty Ltd

Tel: (02) 8741 5000

Email: sales@ampec.com.au Web: www.ampec.com.au



Care for your rechargeable batteries. . .

High-current Battery Balancer

Part 1 - by Duraid Madina

Properly balancing batteries is critical for a long life, especially if they are lithium-based rechargeable types. But many balancers are inefficient, as they dump excess charge for a given cell, restricting how fast you can charge the batteries and wasting power. Not this one – it redirects that extra charge into other cells, so you can charge fast with little heat or waste!

Most rechargeable batteries consist of an array of nominally identical cells, connected in series, parallel or series/parallel to meet particular voltage, current, and capacity requirements.

Batteries with many series-connected cells often only expose the connections at the extreme ends.

For example, a typical lead-acid car battery has six cells ($2V \times 6 = 12V$) but only two terminals.

To charge such a battery, we apply a higher voltage than the total of all the cells across those two terminals, and current flows through all six cells, increasing their state of charge.

But there is no guarantee that each cell starts with an identical voltage, and despite their identical construction, cell capacity can vary, especially as the battery ages.

This is not a big problem with car batteries because lead-acid cells toler-

ate slight overcharging well. By overcharging the battery a little, cells with a lower charge get a chance to 'catch up' to the others, while the most highly charged cells dissipate the charging current as heat.

Despite this, large lead-acid battery banks (as might be used in a renewable energy installation) will last longer if they are kept balanced. In this case, you might have several batteries in series, so not only do you need to be concerned about inter-cell balancing within a given battery, you also need to consider balancing the charge between batteries.

The fact that you might be using batteries with different ages and possibly even from different manufacturers makes this even more critical.

Then there is the case of lithium-ion and similar rechargeable cells. There is a great variety of lithium chemistries around, but many of them do not tol-

erate overcharging. They also can be easily damaged by over-discharging.

So keeping lithium rechargeable batteries balanced is even more crucial.

Since this Balancer can handle cell voltages as low as 3V and as high as 15V, it is suitable for a wide range of balancing tasks, including balancing the cells within a lithium-ion battery, or balancing individual lithium-ion or lead-acid batteries.

Each Balancer can handle up to four cells (or groups of cells) or batteries, and you can combine multiple balancers for larger installations.

Avoiding cell damage

One conservative option would be to immediately stop charging as soon as any cell reached its maximum permissible voltage, but that would leave the remainder of the cells not quite fully charged.

Left unchecked, what might start as

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

Preview only.

SWITCHMODE POWER SUPPLIES PTY LTD

ELECTRONICS SPECIALISTS TO
• DEFENCE • AVIATION • MINING
• MEDICAL • RAIL • INDUSTRIAL

Our Core Services:




Electronic
DLM Workshop
Repair



NATA
ISO17025
Calibration



37 Years
Repair
Specialisation

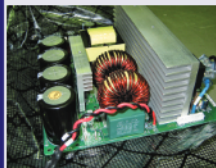

Power Supply
Repair to
50KVA



Convenient
Local
Support

SWITCHMODE



SWITCHMODE POWER SUPPLIES Pty Ltd ABN 54 003 938 050

Unit 1/37 Leighton Place Hornsby NSW 2077

(PO Box 606 Hornsby NSW 1630)

Tel: 02 9476 0300

Email: service@switchmode.com.au Website: www.switchmode.com.au

Not quite vintage radio . . . or is it?

by
Dr Hugo
Holden

The **Fetron** . . .



and the one and only **all-Fetron** radio

You would probably be aware that there are some similarities between valves (aka vacuum tubes) and field-effect transistors, or FETs. You may also know that some people have created valve-equivalent devices based on FETs.

But did you know that there were commercially-made semiconductor-based triode and pentode equivalents known as “Fetrons”?

I am fascinated by these, so I built a superhet using little else.

The Fetron, a unique combination of N-channel Junction Field Effect Transistors (JFETs), using the Cascode configuration, was a product of research and development in the Aerospace and Avionics industry (by the Teledyne Company in the USA) in the early 1970s.

They were built primarily as a plug-in valve or solid-state pentode replacement, although triode equivalents were also made.

The basic idea behind the Fetron was to have the electrical properties of a pentode, but no microphony and no heater power consumption, along with the other advantages of semiconductors: greater efficiency and reliability, with lower noise and higher gain.

Fetrons usually had a much higher amplification factor than the valve they replaced. Teledyne also produced a range of semiconductor devices such as high-voltage Junction FETs and they still produce beyond excellent-quality miniature RF relays.

Every Teledyne product I have inspected and used has always impressed me with its innovative nature, outstanding manufacturing quality, excellent physical appearance and electrical performance.

Because of this, I decided to engineer a multi-band radio composed of entirely Fetrons, powered by a single 90V battery or DC supply, and incorporating some of my other favourite Teledyne devices.

Replacing valves with semiconductors

The idea of replacing a valve with a plug-in transistor substitute has occurred to many people since the invention of the transistor.

Although there are mathematical models for transistors as voltage-to-



Reproduced rather significantly larger than life size, this is the TS6AK5 used in the Fetron Receiver. The type number is designed to show its equivalence to the 6AK5 valve.

current control devices, fundamentally, they are current-to-current control devices.

I know that some people disagree with this (for example, audio guru Douglas Self), but it is generally accepted to be true.

In most instances, the input (base-emitter) current controls the output (collector-emitter) current.

Valves, on the other hand, are voltage-to-current control devices or transconductance amplifiers, where usually the grid-to-cathode voltage controls the anode-to-cathode current.

Transistors in the grounded-emitter configuration have a much lower input resistance than valves in the grounded-cathode configuration.

When high-voltage JFETs arrived on

the scene, they were possible substitutes for the triode valve. They had a similar transfer function of gate voltage versus drain current, compared to grid voltage versus anode current for the triode. Also, JFETs have a similarly high input impedance to a valve.

In the grounded-source or grounded-cathode circuit, both the JFET and the triode are influenced by the effective amplification of the drain-to-gate (or anode-to-grid) capacitance – known as the Miller effect.

This capacitance, which is intrinsic to the device, is multiplied by its amplification factor. This limits the high-frequency response and results in significant input to output feedback as the operating frequency increases.

In triode circuits, if a tuned circuit with a similar resonant frequency is placed in both the grid and the anode circuit, oscillations occur due to the feedback capacitance and the two resonant circuits exchanging energy with each other.

Historically, the Miller capacitance problem was solved with an added neutralisation capacitor feeding back an out-of-phase signal from a coil extension on the anode resonant circuit to the grid (or to the base in a transistor circuit) via a small adjustable capacitor.

In early transistor radios, intermediate frequency (IF) amplifiers using devices such as the OC45, which had a sizeable internal feedback capacitance, required neutralisation.

Later, better transistors such as the OC169, AF117 or AF127 had a much lower feedback capacitance and didn't require neutralising in 455kHz IF stages.

In vintage TRF radios based on triode valves, the added neutralising capacitor was called a Neutrodon and

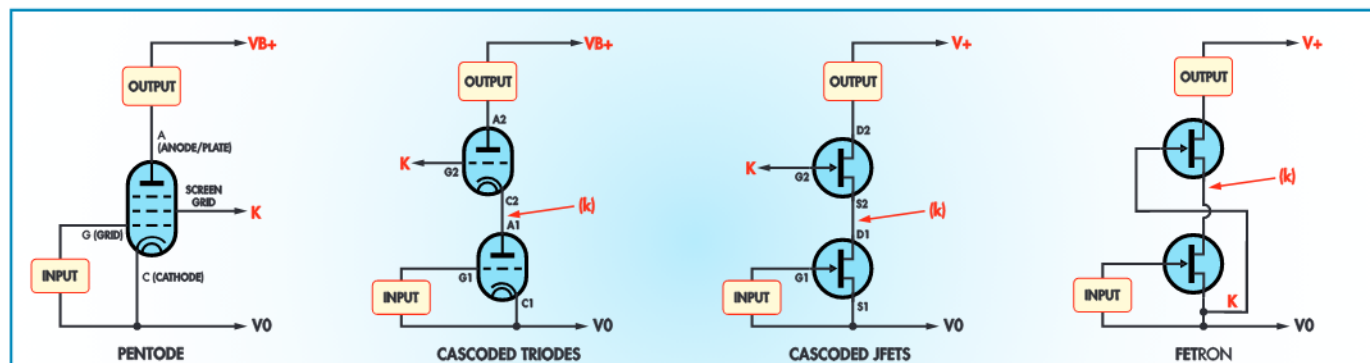


Fig.1: four more-or-less equivalent inverting amplifier circuits. At left is the pentode valve, followed by a pair of triodes in a cascode configuration, two JFETs in the same configuration and the simplified scheme used in the Fetron (which requires specific JFET characteristics).

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

The History of Videotape – part 1

Quadruplex

By Ian Batty, Andre Switzer & Rod Humphris



Analog videotape is now obsolete. But it was state-of-the-art for many decades, and during that time, a video recorder was arguably the most advanced piece of electronic equipment in many homes. The history of video recording is quite fascinating, and this series of articles provides an in-depth explanation of how it came about and changed over the years.

www.historyofrecording.com/ampexvrx1000aniv.html

Audiotape recording and playback predate videotape, with early magnetic recording of audio demonstrated in 1898. Oxide tape was invented in Germany in 1928. By the time serious work on videotape recording started in the 1950s, audiotape was already widely used.

Audiotape use amplitude-based recording; a stronger signal creates proportionally stronger magnetic patterns on the tape. Audio signals are in the frequency range of 20Hz to 20kHz, a range of ten octaves or three decades. This is not especially difficult to achieve with magnetic tape.

Videotape, however, needs to cover

the range of 60Hz to at least 4.2MHz for the US NTSC standard, or 50Hz to 5MHz for CCIR/PAL (see Fig.1). This is a range approaching 17 octaves. That's a much bigger challenge.

On playback, tape head output doubles for every doubling in frequency (ie, output increases at 6dB/octave).

Let's say that we can get away with a video signal that has a signal-to-noise ratio (SNR) of 40dB. From 50Hz to 5MHz, the signal ratio due to the 6dB/octave effect is 100dB! That means that our tape system SNR needs to be at least 140dB (Fig.2). That is simply not possible. So video signals cannot be recorded and played back using

conventional amplitude recording.

Another reason why amplitude recording cannot be used for video is that any tiny variations in tape-to-head contact (dropouts) would severely affect the replayed picture (Fig.3). Variations in the tape's oxide layer would also cause major visual disruptions, especially if the signal level falls and the synchronising signals cannot be detected.

Tape-to-head speeds

Tape systems work well up to a frequency where the wavelength of the recorded magnetic pattern approaches the width of the tape head's magnetic

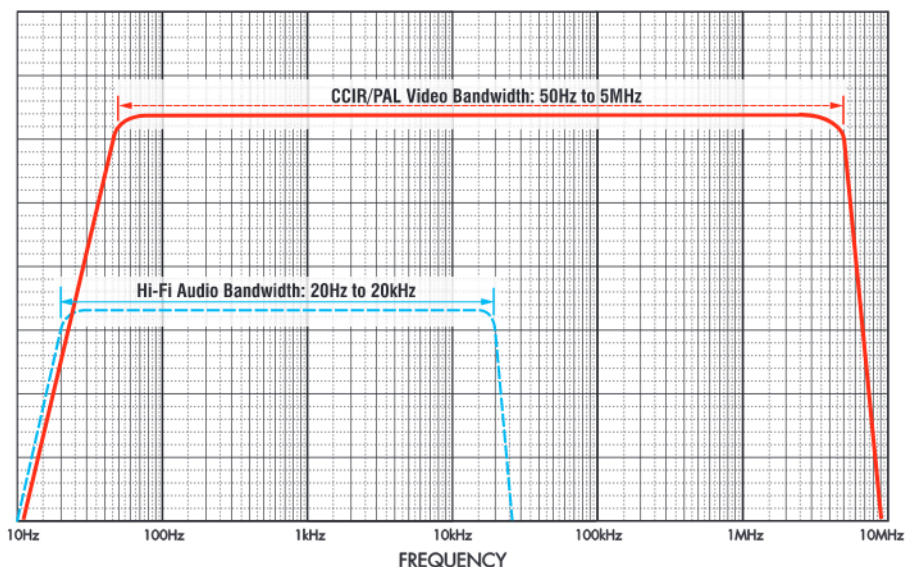


Fig.1: the recording bandwidth needed for a direct (linear) analog transcription of standard audio and video (PAL) signals. The horizontal axis is logarithmic; video covers 16.5 octaves (five decades) while audio covers 10 octaves (three decades).

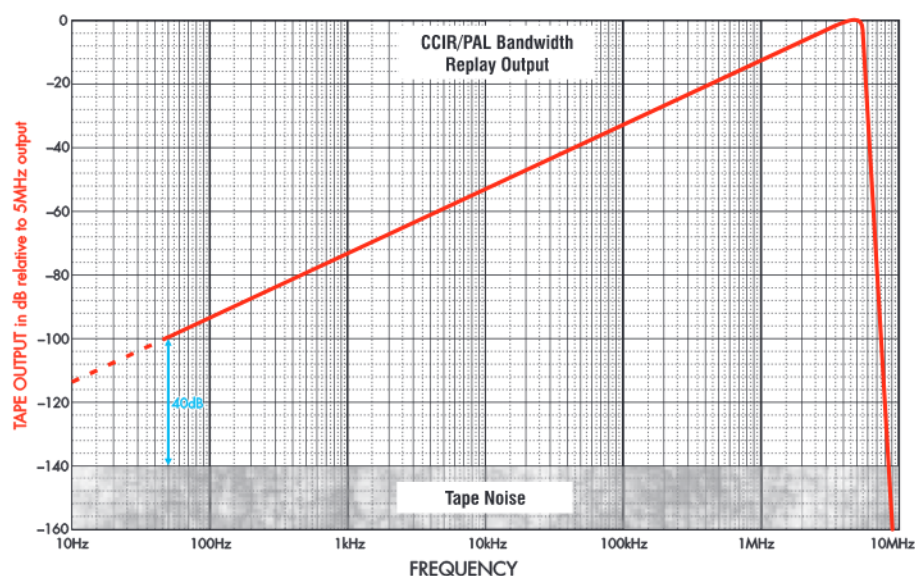


Fig.2: the signal from the tape head increases by 6dB for every doubling in frequency. This shows the impossibility of recording a video signal directly to tape, since to avoid saturation at 5MHz and signals below 50Hz being lost in the noise, the system would need an impossibly high dynamic range of 140dB.

gap. At precisely one wavelength, the signal on one side of the head has the same amplitude and polarity as that on the other side. With no difference in the magnetic field, there is no output from the head.

So the combination of head gap width and tape speed determines the frequency at which head output falls to zero, and thus the maximum recordable frequency.

For the NTSC limit of 4.2MHz and a practical head gap of only 2.5µm, the required tape speed is 21 metres/sec ($2 \times 2.5 \times 10^{-6} \times 4.2 \times 10^6 \times 10^3$). That's the entire length of an old-fashioned 2400 foot/731m reel in about 35 seconds! It's

worse for the CCIR/PAL bandwidth of 5MHz, needing a tape speed of 25m/s, giving a reel playtime under 30 seconds. So it is not practical to use linear tape recording for video recording.

VERA

Despite all these apparent problems, some hardy folks did give amplitude recording a try. The BBC's Video Electronic Recording Apparatus (VERA) from 1952 took on the challenge, using stationary heads and a very high tape speed.

Unable to accommodate the required 405-line standard's bandwidth of 3MHz with amplitude recording, Dr



The BBC's Video Electronic Recording Apparatus (VERA) was an attempt to record video onto tape in a similar manner to audio. It used stationary heads and a very high tape speed, necessitating huge tape reels. Despite their size, each reel only lasted 15 minutes! Source: www.vtoldboys.com



Ampex's Harold Lindsay (left) and Alexander M. Poniatoff (right) with the well-regarded Ampex 200 audiotape recorder. Source: www.historyofrecording.com

Peter Axon's team ingeniously split the entire signal into three bands.

Band A contained signals 50Hz~100 kHz (including synchronising signals), frequency modulated onto a 1MHz carrier. Band B contained signals 100kHz~3MHz using amplitude modulation. Band C frequency-modulated the audio signal onto a 250kHz carrier.

Splitting the video bandwidth did allow the 405-line bandwidth of 3MHz to be accommodated, and demonstrated the principle of recording video on tape.

VERA's development lasted until 1956, by which time US company

...continued on page 48

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

DIY Hobby Hardware

Hardcore electronics by

jaycar

think. possible.

On Sale 24 February to 23 March, 2021

Bonus Gift
FREE
1kg Filament
Buy 1 x TL4256
Get 1 x 1kg Flashforge Filament of your choice free TL4269-TL4276.

Flashforge Adventurer 3 3D Printer

Compact structure with no angular design. Ready to use and no levelling printing. Removable, heatable and bendable plate. Automatic filament feeding. Print up to 150Lx150Wx150Hmm. TL4256

ONLY
\$899

Digital Microscopes

Excellent for educational purposes and suitable for many applications.

600x magnification.

USB CC3191

NOW \$79.95 SAVE \$20

Rechargeable with

4.3" Screen CC3193

NOW \$99 SAVE \$30

NOW FROM
\$79⁹⁵
SAVE UP TO \$30

Arduino® Starter Kit

This official kit from Arduino®. Kit includes UNO board, breadboard and plenty of prototyping accessories. Perfect gift for a young electronics enthusiast or maker in the making. XC9200 See website for details.

JUST
\$169



1 Hour
click & collect

Quad 14 Segment Alphanumeric Display Module

Displays numbers, alphabet & special characters. Amber colour backlight. XC3715

new

JUST
\$14⁹⁵

2 FOR
\$249
SAVE \$49

new

Pair through True Wireless Stereo (TWS)

Bookshelf Style Bluetooth® Speaker

Stylish retro style with built-in subwoofer and 30WRMS sound output. Support True Wireless Stereo (TWS). Hands-free calls. Input via Bluetooth® or 3.5mm Aux. XC5250 **\$149**

ALSO AVAILABLE: Sci-Fi Inspired Bluetooth® Speaker XC5252
INTRO SPECIAL \$129 SAVE \$20

new

JUST
\$239

OBD II 4G/GPS Tracking Device

Locate and track the whereabouts of your vehicle in realtime. Track via the Internet on a PC or Smartphone. 4G SIM card required. Built-in microphone, SMS alerts and more. LA9039

new

JUST
\$399

Uniden Dash View® 30 Dual Band Wi-Fi Car Event Camera

Allows direct footage transfer, preview and even record via Smartphone or Tablet using the free Uniden app. Built-in speed and red light camera warning. 2.5K Recording resolution. 140° wide angle. Voice control / guidance. Sony Starvis sensor. QV6004

new

JUST
\$39⁹⁵

USB Retro Arcade Game Controller

Pairs with any USB compatible gaming system. Suits PC, Nintendo Switch, PS3 & Android TV Arcade Games. USB powered. XC5802

Shop the catalogue online!

Free delivery on online orders over \$99*

*Exclusions apply - see website for full T&Cs.

www.jaycar.com.au 1800 022 888

Workbench wonders

LOTS OF FILAMENT
COLOURS & STYLES
AVAILABLE
FROM \$19.95



3X FILAMENT
COLOUR MIXING
TECHNOLOGY



NOW
\$1299
SAVE \$50

3D Printer/ CNC/Laser Etcher

3D print, engrave and laser cut with a single machine. Easy swap & interchangeable modules. Includes easy to use software. Prints up to 125Lx125Wx25Hmm. TL4400 See website for details.



NOW
\$1299
SAVE \$200

Dobot MOOZ-3Z Triple Filament 3D Printer

Equipped with a three-colour print head for colour mix print. Easy-to-use controller and mobile app. Features 3.5" LCD touch pad, Wi-Fi or USB connectivity, magnetic heat bed and more. Prints up to 100Hx100(Dia).mm. TL4412 See website for details.



NOW
\$1299
SAVE \$200

Desktop 3D Scanner

Watch real life objects become digitised before your eyes. Scans up to 250Hx180Dmm. Folds for easy storage. Supplied with MFStudio software with +Quickscan. TL4420 See website for details.



JUST
\$299

32GB microSD Card
XC4992 Worth \$36.95
bonus
free gift

Inspection Camera with Record

Pocket-size endoscope with camera and LED illumination on a 1m semi-flexible 5.5mm tube to inspect hard to reach areas. 3" display. Records to microSD card (sold separately). HD 720P resolution. Drop resistant. QC8716

**True RMS Autorange
Multimeter**
Non-contact voltage detection. 1000VDC CATIII rating. 4000 display count. AC/DC current 10A. QM1321



JUST
\$39.95

0-30VDC 0-5A Regulated Power Supply

Power your devices with precise voltage level and current limits. Digital control, large LED display. Built-in over-current & short circuit protection. MP3840



JUST
\$189

**Non-Contact
Thermometer
with Laser Pointer**
Measure temperatures from -50°C up to 600°C in hard to reach places. 12:1 Distance to Spot Ratio. Adjustable emissivity. Large colour LCD display. Powered from 2 x AAA batteries included. QM7424



JUST
\$99.95



**400ml 30W
Ultrasonic Cleaner**
Clean your jewellery, fountain pens, dentures, eye glasses, and other small machined parts. Mains powered. YH5414

NOW
\$69.95
SAVE \$20



1kg Digital Bench Scale
Weighs in grams, ounces, pounds etc. Auto power-off after 60 seconds. Mains powered or 4 x AA Batteries (SB2425 \$3.25 sold separately). QM7264

JUST
\$199



ONLY
\$29.95

LED Headband Magnifier
Fits over prescription or safety glasses. Adjustable head strap. 1.5x, 3x, 8.5x or 10x magnification. Requires 2 x AAA batteries (SB2426 \$1.95 sold separately). QM3511



ONLY
\$29.95

Large Rare Earth Magnets
Exceptionally strong (SCARY!). Made from NdFeB (Neodymium Iron Boron). Nickel plated. LM1652

JUST
\$37.95
EA.

Nashua Gaffer Tape
Professional quality. Leaves no residue and sticks to most clean surfaces, including carpet. 48mm wide x 40m long.
Black NM2812 | Silver NM2814



**LED Magnifying
Lamp & Third Hand**
Perfect for PCB assembly & soldering. 3x magnification. Powered by 4 x AA batteries (SB2425 \$3.25 sold separately). TH1989

ONLY
\$49.95

More ways to pay:



Tool time

Soldering Iron Stands
Economy
TS1502
\$9.95
Deluxe
TS1507
\$16.95

FROM
\$9.95



Solder Flux Paste
Non-flammable, non-corrosive.
56g tub. NS3070

ONLY
\$17.95

Soldering Iron Tip Cleaner
Static-safe, suitable for lead-free solders.
Spare insert included.
TS1510

ONLY
\$17.95

3-in-1 Function Heat Blower and Soldering Iron

Flame or flameless function. Adjustable temp control. Piezo ignition. Temp range up to 450°C/500°C hot blow. TH1604

NOW
\$29.95
SAVE \$5



Portasol Pro Piezo Gas Soldering Iron

Adjustable tip temperature up to 580°C. 15-75W equivalent electrical power. Internal piezo crystal ignitor. TS1310

NOW
\$99
SAVE \$20



Portasol Pro Piezo Gas Soldering Tool Kit

Quality pro piezo iron. Includes tips, cleaning sponge/tray and storage case. Temp range up to 480°C. Piezo ignition. 75W equivalent electrical power. TS1318

NOW
\$129
SAVE \$16



JUST
\$18.95

19 Compartment Storage
Made from sturdy ABS with solid clasps. Removable compartment trays. 335Lx420Wx60Dmm. HB6305




JUST
\$14.95

127mm Precision Angled Side Cutters
Easily cut leads, ideal for fine PCB work. Soft padded handles. Carbon steel. TH1897



JUST
\$44.95

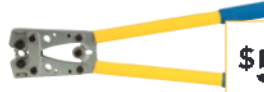150mm Precision Side Cutters
Designed for sharp cutting in precision wiring. Insulated soft-grip handle. Carbon steel. TH1891 **THIS IS A LIFETIME PRODUCT**



JUST
\$54.95

Heavy Duty Terminal Crimper
Used for crimping lug/eye terminals. Built-in rotating die. Hex crimper. 450mm long. TH1849



NOW
\$24.95
SAVE \$3

100 Piece Driver Bit Set
Includes magnetic holder, Phillips bits, slotted bits, torx, tamperproof, pin drive, wing nut driver etc. Suits standard 1/4" driver handle. TD2038 See website for full contents.



NOW
\$39.95
SAVE \$10

73 Piece Multifunctional Screwdriver Set
Open all kinds of electronic devices. S2 Steel precision bits. Storage case. TD2136



JUST
\$39.95

110 Piece 12V Rotary Tool Kit

Drill, saw, sand, polish, carve or grind in your workshop or out on the road. 12V @ 12,000RPM. TD2451



JUST
\$39.95

ABS IP66 Enclosure
Gasket seals, stainless steel hardware and IP66 rated. Opaque cover. 200Lx200Wx130Dmm. HB6404



ONLY
\$22.95

Quick Connect Crimp Connector Pack
Consists of all the standard 1/4" (6.35mm) QC tabs and receptacles and odd QC sizes i.e.: 3.3mm & 4.8mm. 160 pieces. PT4530



ONLY
\$24.95

Heatshrink Assortment Trade Pack
Contains 160 lengths of different sizes in a handy storage case. WH5524



ONLY
\$26.95

Cable Tie Box
Kit consists of 100 pcs x 200mm, 100 pcs x 150mm, 200 pcs x 100mm. See-through flat storage case. 400 pieces. HP1216



ONLY
\$39.95

Assorted Solder Splice Heatshrink Pack
Quickly create sealed soldered joint in one go. Includes assorted colours and sizes to suit various cable size. 42 pieces. WH5668

Looking for more product information?
Visit your local store or our website jaycar.com.au

We reward our industry professionals



Power it up!



FROM
\$279

12V Deep Cycle AGM* Batteries

Designed to store large amounts of energy. Superior deep cycling performance for different recreational and industrial applications.

75Ah SB1680 **\$279**
100Ah SB1682 **\$299**
120Ah SB1683 **\$399**

*AGM = Absorbant Glass Mat

NEED A LARGER CAPACITY?

150Ah & 200Ah available for special order only.

See in-store or online for details.



NOW
\$149
SAVE \$40

12V-7.2A/24V-3.6A Battery Charger

Fully automatic 9 state charger for 12 or 24V lead acid (Wet cell, Gel cell, AGM) and lithium iron phosphate (LiFePO4) batteries. Built-in protection. IP65 rated. MB3613



NOW FROM
\$49.95
SAVE UP TO \$20

Modified Sinewave Inverters

Power small appliances such as laptops, stereos, computers, phone chargers etc. where mains socket isn't available. 12VDC to 240VAC. Includes battery lead and alligator clips.

300W MI5302 **NOW \$49.95 SAVE \$10**
500W MI5304 **NOW \$69.95 SAVE \$10**
800W MI5308 **NOW \$109 SAVE \$20**



JUST
\$99.95

12V 140A Dual Battery Isolator Kit

Power your electrics without flattening your main starter battery. Automatic isolation. Easy to install. MB3880



FROM
\$64.95

Mains Laptop Power Supplies

Replace your lost or broken laptop charger. All models feature short circuit and overload protection. Compatible with most brands.

65W Fixed Slim MP3321 **\$64.95**
90W Manual MP3476 **\$79.95**
120W Fixed Slim MP3329 **\$119**



JUST
\$49.95
EA.

High Power Mains Power Supplies

Slim design perfect for power boards, with low energy consumption. Regulated output voltage. Supplied with 7 changeable DC tips.

12VDC 5A 65W MP3560
24VDC 2.5A 65W MP3562
48VDC 1.25A 65W MP3564



FROM
\$49.95

Desktop Style Power Supplies

Versatile switchmode power supplies in a range of different configurations.

12VDC 5A MP3242 **\$49.95**
12VDC 5A (5 Plugs) MP3243 **\$54.95**
24VDC 2.7A MP3248 **\$49.95**

Ultra High Capacity 1000A 12/24V Lithium Jump Starter

Lightweight and ultra-compact. 12V/24V compatible starting with automatic detection. USB charging outlet and light. Mains & car charger included. MB3759

NOW
\$349
SAVE \$20



FROM
\$36.95

Heavy Duty Jumper Leads with LED

Surge protected. Built-in LED light.

400A 3.0m Long WH6012 **\$36.95**
700A 4.5m Long WH6014 **\$69.95**

3-30VDC Tester With Voltage/Polarity Readout

Works on 6/12/24V systems. Stainless steel testing probe. LED Indicators: Green (-), Red (+). QP2216

JUST
\$19.95

Non-contact AC Voltage Detector

Detects AC voltages from 200 to 1000V. Green and red LED indicators. Flashlight function. QP2268

JUST
\$24.95



600A True RMS AC/DC Clampmeter

Non-contact voltage testing. 6000 display count. CATIII 600V rated. QM1632

JUST
\$89.95



FROM
\$4.95
/m

High Current 2 Core Power Cables

Figure-8 tinned.
25A WH3087 **\$4.95/m** **\$379/roll**
56A WH3063 **\$9.95/m** **\$429/roll**
90A WH3067 **\$14.95/m** **\$639/roll**

FROM
\$14.95

Loom Tubes

Keep wiring in place. 10m long.
7mm dia. HP1223 **\$14.95**
10mm dia. HP1225 **\$18.95**
See website for full range.

Stainless Steel Wire Stripper/Cutter/Pliers

Strips wire up to 2.6mm and cut steel wires up to 3.0mm. TH1841

ONLY
\$19.95



Improve your sound & vision



NOW
\$29⁹⁵
SAVE \$10

Audio Mixer With Bluetooth® Technology
Compact & rechargeable, ideal for street busking, outdoor parties, etc. 3.5mm Auxiliary input & output. 6.5mm microphone input. 1500mAh rechargeable battery. AA4230

Rechargeable Headphones with Bluetooth® Technology
Amazing sound quality. Listen to your music wirelessly via Bluetooth®. USB Rechargeable. Built-in mic. AA2129

JUST
\$39⁹⁵



2 Channel Soundbar Speaker With Bluetooth® 5.0

Enhance the sound of your TV, and can also be used as a standalone speaker. Includes 3.5mm stereo and digital optical inputs. 2x14W Output. Wall Mountable. XC5233

GREAT FOR TV OR MUSIC

JUST
\$79⁹⁵

Bluetooth® 5.0 Transmitter & Receiver with Optical

Multi-directional. Can stream audio to or from your Bluetooth® device to play on your stereo, speaker etc. TOSLINK Optical input & output. AA2112



JUST
\$99⁹⁵

Concord Flexible TV Coax Leads
Super flexible. Easy to run through entertainment cabinets and along skirting boards. RG6 quad shielded.
TV Plug To TV Plug 3m WW7460 **\$14.95**
TV Plug To F-Plug 3m WW7464 **\$14.95**
TV Plug To F-Plug 20m WW7470 **\$34.95**
See website for full range.

FROM
\$14⁹⁵

Replacement Power Supply for Masthead Amplifier
F-socket power injector. 14VDC@150mA. LT3256

JUST
\$29⁹⁵



Kingray VHF/UHF Masthead Amp
High gain with LTE/4G filters to compensate for redistribution of broadcast frequencies. LT3251
See website for details.

JUST
\$119



Digital TV Signal Strength Meter
Easy to read pocket sized DVB-T meter. Correctly adjust the angle of your digital TV antenna. LT3332

NOW
\$29⁹⁵
SAVE \$10



Speaker Polarity Tester With Tone Generator
Sinewave tone generator, speaker polarity and RCA cable tester. Output range: 0V-8V. 9V speaker popper. RCA or alligator clips connection. AA0414

NOW
\$26⁹⁵
SAVE \$8



NOW
\$79⁹⁵
SAVE \$10

Roadies Cable Tester
Test Speaker, RCA, USB, RJ45 cables. LED indicators. Bullet-proof metal construction. AA0405

HDMI Adaptors
Socket to Socket PA3640 **\$9.95**
Plug to DVI-D Socket PA3642 **\$9.95**
Socket to DVI-D Plug PA3644 **\$9.95**
Mini Plug to Socket PA3645 **\$12.95**



DVI-D to HDMI Cable
1.5m Long WQ7407 **\$19.95**
3.0m Long WQ7406 **\$29.95**



Concord 4K HDMI 2.0 Amplified Cables
Amplified transmission. Avoids signal loss.
10m WQ7437 **\$79.95**
15m WQ7438 **\$99.95**
20m WQ7435 **\$119**
30m WQ7439 **\$139**

FROM
\$79⁹⁵

4K UHD



Concord 2-Way 4K HDMI Splitter
Simultaneously split to two HDMI displays from one HDMI source. Up to 4Kx2K video resolution. High-Dynamic-Range (HDR) video support. Mains adaptor included. AC5000

4K UHD

JUST
\$89⁹⁵



Concord 4-Way 4K HDMI Switcher
Switch up to 4 different HDMI displays. Up to 4Kx2K video resolution. High-Dynamic-Range (HDR) video support. 3.5mm stereo audio output socket. AC5010

4K UHD

JUST
\$129




1080p HDMI Cat5e/Cat6 Over IP Extender
Send high definition AV signals to a screen in another room up to 150m away using a Cat5e/6 cable through a common router or Ethernet switch. Infrared remote control extender. AC1752
Additional Receiver AC1753 \$99.95

1080P HD

JUST
\$179

TERMS AND CONDITIONS: REWARDS / CLUB MEMBERS FREE GIFT, % SAVING DEALS, & MEMBERS OFFERS requires ACTIVE Jaycar Rewards / membership at time of purchase. Refer to website for Rewards / membership T&Cs. **IN-STORE ONLY** refers to company owned stores and not available to Resellers. Page 1: FREE 1 x 1kg Flashforge Filament with purchase of Adventurer 3D Printer (TL4256), select from TL4269-TL4276. Page 1: Multibuy: 2 x XC5250 for \$249. Page 2: FREE 32GB microSD card (XC4992) with purchase of Inspection Camera (QC8716). **SUPPLY CHAIN DISRUPTION:** We apologise for factors out of control which may result in some items may not being available on the advertised on-sale date of the catalogue.


Make with microcontrollers

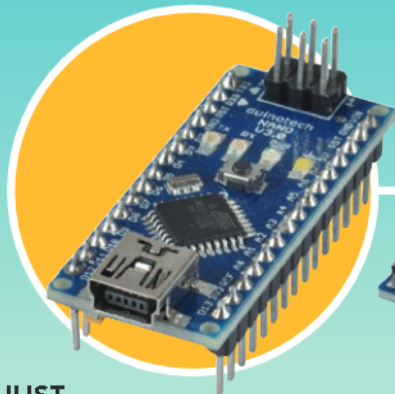

JUST
\$29⁹⁵

Arduino® Compatible NANO Board

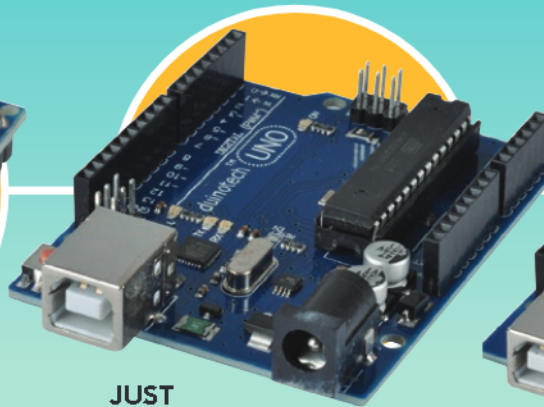
Fully compatible with all the features of the full Duiinotech boards but on a tiny DIP-style form. ATmega328P microcontroller. 46Lx18Wx18Hmm. XC4414



JUST
\$29⁹⁵

Arduino® Compatible UNO R3 Board

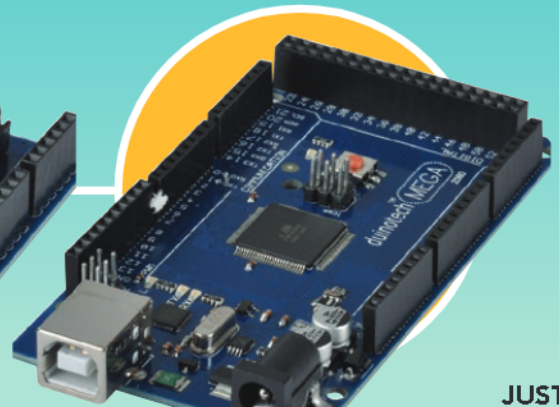Stackable design makes adding expansion shields easy. Powered from 7-12VDC or from your computers USB port. ATmega16u2 USB-Serial chipset. 53Lx75Wx13Hmm. XC4410



JUST
\$49⁹⁵

Arduino® Compatible MEGA 2560 R3 Board

Our most powerful Arduino® compatible board. Boasting more IO pins, more memory, more PWM outputs, more analogue inputs and more serial ports. ATmega2560 microcontroller. 53Lx108Wx15Hmm. XC4420



NOW
\$7⁹⁵
20% OFF



RS-232 to TTL UART Converter Module
Connect a legacy device (or computer) to your existing Arduino® board to directly communicate with a huge variety of serial peripherals. Full RS-232 port. XC3724




NOW
\$3⁹⁵
10% OFF



Infrared Receiver Module
Read the signals sent by most IR remote controls. Pair it with the TX Module (XC4426 \$4.95 sold separately) to make a universal remote control. XC4427




NOW
\$7⁹⁵
20% OFF

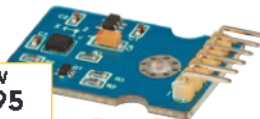

Tri-Axis Digital Tilt Sensor
Use this high performance acceleration sensor in your project to detect direction, as well as free fall, pulse, and shake detection. 12 bit and 8 bit digital outputs. I2C digital output interface. XC3732



NOW
\$3⁹⁵
20% OFF

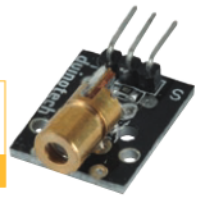

Red Laser Diode Module
Need a red laser light for your latest project? Just connect this diode module to 5VDC and you're good to go! Use it with our light sensor module (XC4446 \$5.95 sold separately) to make a laser tripwire. XC4490




NOW
\$31⁹⁵
20% OFF

Ethernet Expansion Module
A network shield that enables you to set your Arduino® up as web server, control your project over your network or even connect your Arduino® to world wide web. XC4412



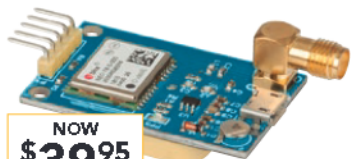RF Transceiver Module
Adds a versatile 433MHz radio to your Arduino® project allowing two-way wireless communication between Arduinos. Includes antenna. 1.9-3.6VDC operating voltage. XC4522




NOW
\$39⁹⁵
10% OFF

GPS Receiver Module With On-board Antenna
Add GPS functions to your next Arduino® project. 2.5m accuracy to pin point your location. Flash memory retains data even when power is disconnected. Onboard & external antenna options. XC3710



NOW
\$4²⁵
10% OFF

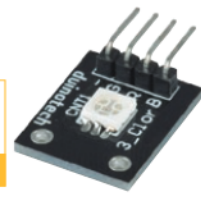

RGB LED Module
Can be interfaced with a variety of microcontrollers. 4 pin header. 3.3-5VDC. XC4428


Jiffy Boxes
Manufactured from ABS plastic. Sizes are compliant with industry standards externally and PCB fitting internally. Various sizes available. Black/grey colour.
UB5 HB6015 \$3.45
UB3 HB6013 \$4.50
UB2 HB6012 \$7.95
UB1 HB6011 \$5.25



FROM
\$3⁴⁵

Breadboard Layout Prototyping Boards

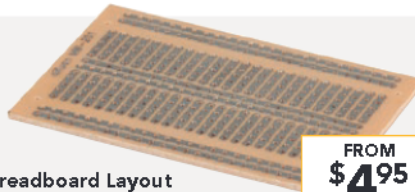Transfer your breadboard design without having to rework it.
Small 25 Rows/400 Holes HP9570 \$4.95
Large 59 Rows/862 Holes HP9572 \$9.95



FROM
\$4⁹⁵

Flexible Light Duty Hook-up Wire
Quality 13 x 0.12 tinned hook up wire on plastic spools. 8 different colours available. 25m roll.
Red WH3000
Black WH3001
See website for full range.




ONLY
\$5⁹⁵
EA.

Expand your project's capabilities



NOW
\$6⁹⁵

10% OFF

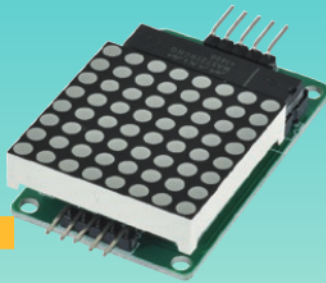

8 x 8 LED Dot Matrix Module

64 red LED matrix. Easily controlled with the LED Control library. Display custom characters, or use multiple modules together to make a scrolling display. XC4499



NOW
\$23⁹⁵

20% OFF

128 x 64 LCD Dot Matrix Module

A larger display with cool white on blue graphics. Similar to the character LCD's with inbuilt character ROM, but the flexibility to show graphics as well. 8 bit, 4bit and serial interfaces available. XC4617




NOW
\$19⁹⁵

20% OFF

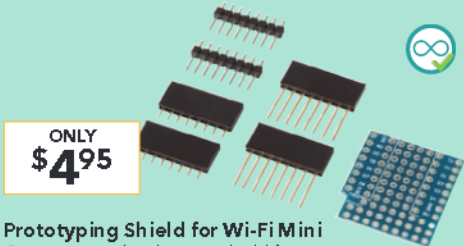1.3" 128 x 64 OLED Monochrome Module


For projects that don't require full colour. Wide viewing angle to eliminate eye strain. XC3728
ALSO AVAILABLE: 15" OLED Colour Module XC3726 NOW \$54.95 20% OFF



ONLY
\$4⁹⁵

Prototyping Shield for Wi-Fi Mini

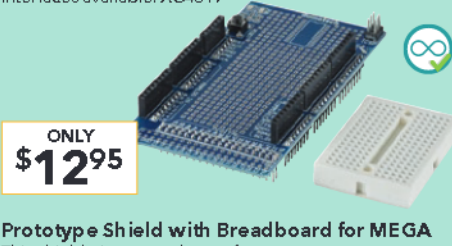
Create custom hardware and add features to your project or build custom sensor nodes or output modules. XC3850



ONLY
\$12⁹⁵

Prototype Shield with Breadboard for MEGA

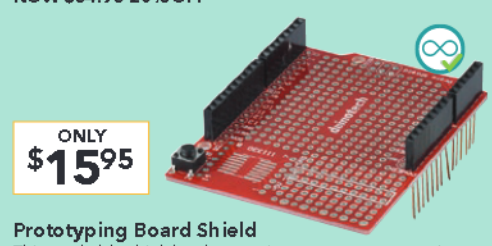This shield gives you plenty of room to prototype your latest MEGA project. Stackable. Provides access to all of the MEGA's pins and plenty of solder pads to prototype on. XC4416



ONLY
\$15⁹⁵


Prototyping Board Shield

This stackable shield makes semi-permanent prototyping simple. Provides solder-pad access to all of the Arduino's pins, and a large area of isolated pads. Includes reset button. XC4482



NOW
\$11⁹⁵

20% OFF

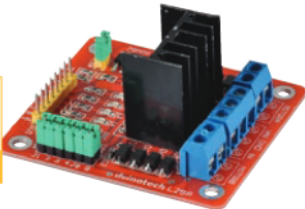

Stepper Motor Controller Module

Allows full control of two DC motors or one stepper motor. Provides 4A at up to 30V. Onboard 5V regulator to power your Arduino* main board. 3-30VDC. XC4492



NOW
\$9⁹⁵

20% OFF



Motor & Servo Controller Module

Has 2x5V servo ports connected to the Arduino's high-resolution dedicated timer to ensure jitterfree operation. Control up to four DC motors or two stepper motors. 5-16VDC. XC4472




NOW
\$5⁹⁵

25% OFF



24V 5A MOSFET Driver Module

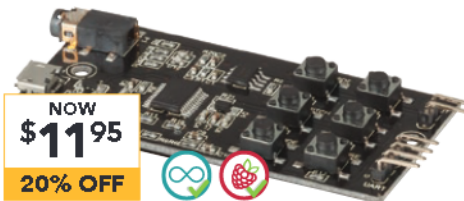Accepts Pulse Width Modulation (PWM) input to drive 24VDC loads from your Arduino*. Operate lighting, DC motors, pumps, solenoids, etc. 3.3V-5VDC. XC4488



NOW
\$11⁹⁵

20% OFF

MP3 Audio Player Module

Play MP3, WAV, or WMA files from an onboard microSD card (16GB XC4989 \$19.95 sold separately) with your next electronics project. 5W power. XC3748



NOW
\$5⁹⁵

25% OFF



Microphone Sound Sensor Module

Great for any project to detect sounds. Includes both analogue (for waveform) and digital output with adjustable threshold for simple sound detection. XC4438



NOW
\$3⁹⁵

20% OFF



Active Buzzer Module


The easy way to add sound to your project. Hook up a digital pin and ground, and use the tone() function to get your Arduino* beeping. XC4424

LED Tester
Checks function, brightness, colour and polarity of light emitting diodes (LED). AA0274



ONLY
\$13⁹⁵

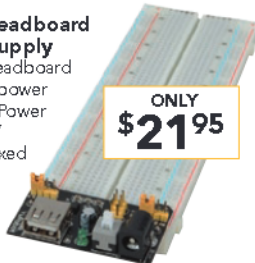Solderless Breadboard with Power Supply
830 tie-point breadboard with removable power supply module. Power from USB or 12V plugpack. 64 mixed length/colour jumper wires. PB8819



ONLY
\$21⁹⁵



ONLY
\$24⁹⁵

Assorted LED Pack

Contains 3mm and 5mm LEDs of mixed colours. 10x5mm mounting hardware. 100 pieces. ZD1694

5 Piece Stainless Steel Tool Set
Set of 5x115mm cutters & pliers. Soft ergonomic grips. TH1812



ONLY
\$34⁹⁵



ARDUINO® COMPATIBLE
This icon indicates that the product will work in your Arduino® based project.



RASPBERRY PI COMPATIBLE
This icon indicates that the product will work in your Raspberry Pi project.

Not sure what to build next?
Here's some inspiration:
jaycar.com.au/projects



NOW
\$169
SAVE \$50

13.8V 40A Switchmode Bench Power Supply

High current general workshop power supply for equipment, component testing, etc. Banana socket style binding post output. Internal cooling fan. MP3089



NOW
\$169
SAVE \$50

9" High Resolution Auto LCD Monitor with HDMI Input

Ideal for car or truck. Equipped with anti-glare shield to improve visibility. RCA & HDMI inputs. QM3874

SAVE
\$50
ON THESE
PRODUCTS

Solder/ Desolder Rework Station

60W Soldering iron and 300W rework blower. Dual digital display. Adjustable temperature up to 480°C. Quick heat-up. TS1648

NOW
\$199
SAVE \$50



NOW
\$319
SAVE \$50

12V 30A Charger for Lithium & Lead Acid Batteries

Charges 12V and 24V lead acid, AGM and lithium (LiFePO4) batteries from 50Ah to 300Ah, with or without load. Automated 5-stage charging for Lead Acid and 2-stage charging for LiFePO4 batteries. 12V 30A or 24V 15A output. MB3621



get
that thing
you need,



win
that thing
you want.

ISUZU
D-MAX

SPEND \$50 OR MORE FOR A CHANCE TO WIN AN ISUZU D-MAX*

For full details on how to enter, drawing & rules head to: jaycar.com.au/dmax-jaycar

*Terms and conditions. Starts 12:01 AM AEST 26/2/21. Ends 11:59 PM AEST 30/4/21. Open to AUST residents who fulfil the entry/eligibility requirements. Prize is a 21MY Isuzu D-MAX 4x4 LS-U Automatic valued at up to \$61,998 (inc GST). Prize draw 10:00 AM AEST 13/5/21 at Level 2, 11 York St Sydney NSW 2000. Winners notified via email by 14/5/21 and published at jaycar.com.au/dmax-jaycar by 17/5/21. Promoter is Jaycar Pty Ltd. ABN 65 000 067 936. 320 Victoria Rd Rydalmere NSW 2116. Authorised under NSW Authority No. TPY00716, and ACT Permit No. TP 21/00078 and SA Permit No. T21/71. Actual prize vehicle not shown, specifications may vary. For full terms and conditions refer to jaycar.com.au/dmax-terms



Your Club,
Your Perks.
KEEP UP TO DATE WITH THE LATEST
OFFERS & WHAT'S ON! JOIN NOW!
1800 022 888
www.jaycar.com.au

jaycar
think. possible.

HEAD OFFICE
320 Victoria Road,
Rydalmere NSW 2116
Ph: (02) 8832 3100
Fax: (02) 8832 3169

ONLINE ORDERS
www.jaycar.com.au
techstore@jaycar.com.au

Over 100 stores & 130 resellers nationwide

Arrival dates of new products in this flyer confirmed at the time of print. Call your local store to check stock. Occasionally discontinued items advertised on a special / lower price in this flyer have limited to nil stock in certain stores, including Jaycar Authorised Resellers, and cannot be ordered or transferred. Savings off Original RRP. Prices and special offers are valid from 24.02.2021 - 23.03.2021.

SERVICEMAN'S LOG



Dave Thompson

If it isn't one thing, it's another

Sometimes, even when there are no customers lining up, work comes along anyway. It isn't always welcome, but when your tools go down, you have to fix them. It doesn't help that I'm afflicted with the Serviceman's Curse, so I'm allergic to paying for replacement tools when it's possible to (uneconomically) fix them!

Over the past year, plenty of local businesses have folded; there simply isn't the customer traffic to keep the doors open any more due to lockdowns and general economic malaise.

While our overall revenue has dropped, as you would expect with a lot less work coming in, the silver lining is that I finally have some free time to get onto those little jobs that I'd been putting off.

Those of you who live the rock and roll life of a serviceman know that sometimes things don't go according to plan. An anticipated five-minute job can easily turn into a two-day mission in the flash of a shorted battery connector or a clumsily-placed screwdriver. That sort of thing doesn't happen to me, of course! But I do hear rumours that it happens to other, less-careful people.

The first small job created itself when I went to use my soldering station, and the pencil was still cold 10 minutes after I switched it on. The astute among you will know soldering irons are meant to be hot, so the fact that I could hold on to the wrong end of it without being burnt told me that something was up!

Items Covered This Month

- It's always the other thing
- Coin counter repair
- Alternative security systems
- LED rose garden repair
- Electric fence energiser repair

*Dave Thompson runs *PC Anytime* in Christchurch, NZ.

Website: www.pcanyttime.co.nz
Email: dave@pcanytime.co.nz

The pencil connects to the soldering station using one of those multi-pin screw-on plugs, sometimes called a GX-16 series connector. I removed and re-connected it, and it seemed sound, so I guessed that the pencil's element had gone open-circuit.


Confirming this theory proved to be more difficult than I imagined, mainly because the pencil itself appears to be a moulded unit. Everything is set into it at manufacture, and it cannot be disassembled to reveal the innards. The cable stress reliever at the bottom can be prised out, but the element appears to have no means of being removed, other than by cutting into the pencil's plastic body.

This makes them inexpensive to manufacture, but not great for repairs. I think they expect people to throw away the dead pencil and buy a new one. The problem is that I've used this pencil for a while now and having just 'broken in' a new tip, it is perfect for the work I do. To bin it without at least trying to repair it would be, well, frankly against my serviceman's code!

So electrical checks would have to be made via the GX connector. I searched for circuit diagrams online for my model. Once located, my multimeter confirmed there was no resistance or continuity through the element from any of the pins, let alone the designated ones, which told me all I needed to know. It was dead!

Borrowing a spare

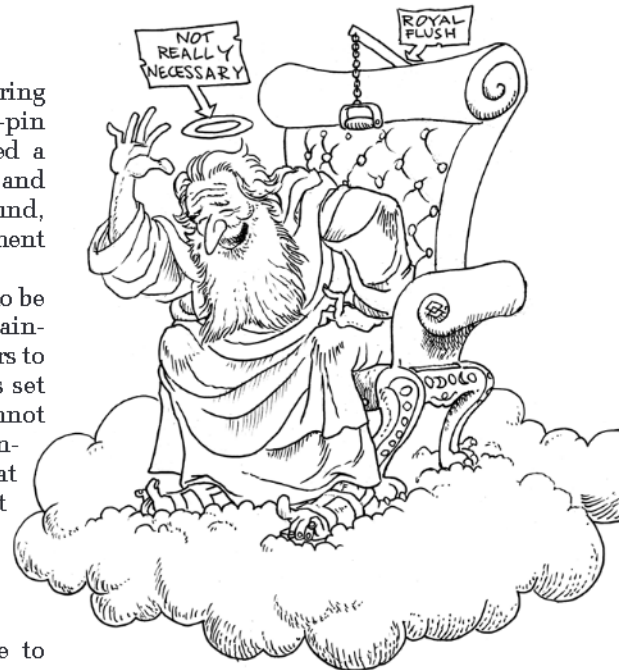Fortunately, I have a spare pencil. But when I say spare pencil, I mean spare soldering station. While it is very much like my usual one, I originally



SOMETIMES THINGS DON'T GO ACCORDING TO PLAN (serviceman plans, God laughs)

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.


For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

Wagner

ELECTRONICS SUPER STORE

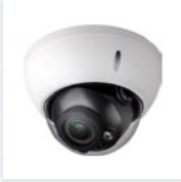**OVER 40 THOUSAND PRODUCTS
ONLINE 1500+ PAGE CATALOGUE
AUSTRALIA WIDE SHIPPING**



**AUDIO/VISUAL ACCESSORIES
SPEAKERS / PRO AUDIO
ELECTRONIC COMPONENTS
DATA & ELECTRICAL
TOOLS & TEST EQUIPMENT
BATTERIES & MORE!**

**BUY ONLINE AT
WAGNERONLINE.COM.AU**

**VISIT OUR SYDNEY STORE
84-90 PARRAMATTA ROAD,
SUMMER HILL, NSW 2130
02 9798 9233**

Preview only.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

Mini Isolated Serial Link

This tiny module (about the size of a postage stamp) provides bidirectional, isolated, full-duplex serial communication. That makes it ideal for when two (or more) boards running from separate supplies need to pass information to each other. It can also carry isolated logic signals. Among its many other uses, it can be used to join two of the Battery Balancers (described in this issue).

By Tim Blythman

The High-current Four Battery Balancer project starting on page 21 can handle more than four batteries (or cells) by stacking multiple units.

But for that to work, they need to communicate with each other, even though their ground potentials will be quite different; possibly as much as 60V DC apart.

To connect their onboard serial links so they can work as a single unit, a serial isolator is needed. This little device uses optoisolators to provide thousands of volts of effective isolation while allowing the serial data to pass through unchanged.

Another important use for a device like this is connecting a computer to a device that you're testing, to prevent any possibility of damage should the device malfunction and feed a high voltage to its serial pins.

If you have a single Battery Balancer and wish to monitor or control its operation on a computer, it would be a good idea to use this isolator between the two, for safety.

We already published the Zero Risk Serial Link in January 2019 (siliconchip.com.au/Article/11360) for this purpose, but that board includes a power supply for the isolated

device, which often isn't necessary. That makes the board much larger and more complicated than necessary. In cases where both communicating devices have individual power supplies, this design is a better choice.

New design

By dispensing with the power circuitry and using six passive SMDs, we've managed to squeeze the required circuitry into a PCB that measures just 26.5 x 23.5mm.

That's small enough to be connected inline with your serial link and encased in a short length of large diameter

heater shrink tubing. Despite this small size, it isn't hard to build.


Fig.1 is the complete circuit diagram. The operation is simple. On the transmitting side, a current loop is formed between the TX pin and the selected supply rail (3.3V or 5V) via one optoisolator LED (OPTO2 for CON1 and OPTO1 for CON2). This is via a 220Ω current-limiting series resistor.

So when the TX pin is high, no current flows through the LED, and when it is low, about 10mA (for a 3.3V supply) or 18mA flows. This pulls the RX pin at the opposite end low by activating the Darlington transistor in the other half of the optoisolator.

When no current is flowing through the LED, the Darlington is off, so that pin is held high by a 1kΩ pull-up resistor.

The configuration is identical for data flowing from CON2's TX pin to CON1's RX pin as it is in the other direction. A 100nF bypass capacitor stabilises the voltage across the Darlington on either side.

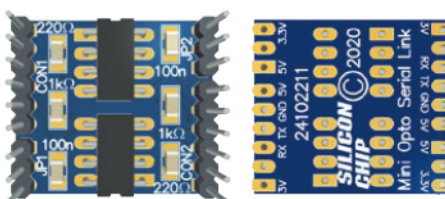Pin headers CON1 and CON2 are identical, and could be soldered directly to one of the communicating boards (eg, a Battery Balancer) using four of the six pins.



These same-size renders of the front (left) and rear (right) of the Isolated Serial Link PCB show just how tiny it is. Whether you use vertical header pins, as shown here, or horizontal, as shown in our photos, is up to you. Incidentally, the renders were taken directly from the new Altium Designer 21, which we reviewed in January (siliconchip.com.au/article/14705).

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

Preview only.

Build the world's most popular D-I-Y computer!

ALL-NEW COLOUR

MAXIMITE 2




See SILICON CHIP July & August 2020

Plastic Case Optional

480MHz,
32-bit processor;
9MB of RAM;
2MB flash memory;
800 x 600 pixel
colour display

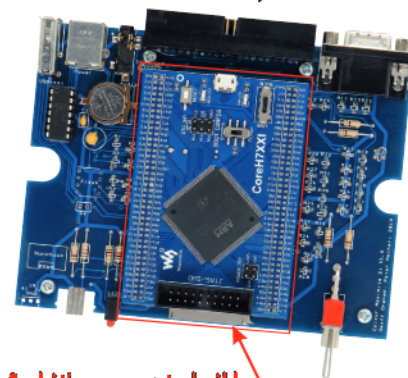Don't miss your opportunity to experience Australia's own world-class, world-famous single board computer that you build and program yourself, using the world's easiest programming language - MMBASIC. Learn as you build!



And it's so easy to build because all the hard work is done for you: the heart of the Colour Maximite II, the Waveshare CPU Module (arranged) is completely pre-assembled and soldered. YOU SIMPLY CAN'T GO WRONG!

SHORT FORM KIT INCLUDES:

- Waveshare CPU module pre-loaded with MMBasic
- the PCB – with solder mask and screen overlay
- front & rear panels to suit plastic case shown above
- and all other components required to build the Colour Maximite 2

Does not include plastic instrument case, CR120x cell or USB power supply/cable

All this for only \$140.00 Plus \$10.00 p&p in Aust

SILICON CHIP SUBSCRIBERS: SAVE 10%!*

Subscriber's price just \$126 plus p&p

Order now (or more information) at www.siliconchip.com.au/shop/20/5508

All About Capacitors

Capacitors are probably the most misunderstood of the passive components, due to the many different types available, their many parameters and greatly varying performance. This article should give you an understanding of the most common types, how they differ, and how to choose the right ones for your design.

By Nicholas Vinen

Capacitors come in all shapes and sizes. Some are much smaller than a grain of rice, while others are huge and used in banks to launch aircraft weighing many tonnes into the air!

Because there are so many different types, it can be very confusing trying to choose one. Even if you know what capacitance and voltage rating you need, there could be hundreds or even thousands of matching parts. Some of those might not work at all in your circuit, while others might work but not very well, and some will be very expensive. You need to narrow the choice down to just a handful and then pick one.

We have tried to break the following descriptions into digestible sections, despite their complexity. If you find yourself overwhelmed, give yourself time to digest what you have read so far, then read the rest later.

Capacitor dielectrics

Fundamentally, a capacitor is just two conductors (originally flat plates) separated by an insulator (the “dielectric”). But because the area of the plates required for any significant capaci-

tance is quite large, modern capacitors are typically arranged as many layers of smaller conductors and insulators connected in parallel, allowing for a more compact package.

In some cases, the ‘plates’ are not even flat but instead are spiral coils, or 3D structures such as the etched surface of a metal foil or granular materials.

Etched or granular materials have a much higher capacitance per volume, as capacitance is proportional to surface area and inversely proportional to the distance between the plates.

This creates a tradeoff; thinner dielectrics give more capacitance, but have a lower breakdown voltage, so the maximum voltage applied to the capacitor must be kept lower. This is the main reason that a capacitor with a higher voltage rating, but the same capacitance, tends to be physically larger; its dielectric layer(s) need to be thicker.

The type of insulating (dielectric) material used has a strong effect on capacitor behaviour, and for this reason, capacitors are mostly categorised by the dielectric type. Different dielec-

tric types have their own trade-offs in terms of capacitance, voltage ratings, linearity, current handling and more.

Some widely used dielectric materials for capacitors are:

- Ceramics (typically metal oxides)
- Metal oxide layers (in electrolytic capacitors)
- Plastic films
- Mica
- Paper
- A Helmholtz plane of solvent molecules (as in ‘double layer’ super/ultracapacitors)

The most common types of capacitors in use today are ceramic and electrolytic, followed by plastic film types. These three types of capacitors have important sub-categories which strongly affect their behaviour.

One property of all dielectric materials is the dielectric constant (“K”). The larger this number, the higher the capacitance for a similarly constructed device. K can vary with temperature, voltage, age and other properties. While high K values make for greater capacitances in a small volume, there are significant penalties in other areas, as we describe below.

Ceramic capacitors

If you look at the PCB of just about any modern electronic device, you will find it covered in ceramic capacitors. They are cheap, reliable, perform very well and are available in a wide range of capacitances and voltage ratings.

Because modern ceramic capacitors are fabricated in bulk, they can have anywhere from one to many thousands of layers. This gives them a wide capacitance range, from fractions of a picofarad up to hundreds of microfarads, in a small package – see Figs.1-3.

Ceramic capacitors are typically robust and long-lasting, and are not polarised (they can handle negative or positive voltages).

Ceramic capacitors are available with voltage ratings from just a few volts up to several kilovolts. Ceramic capacitors with voltage ratings above 500V tend to use different types of ceramic to those below 500V, and have slightly different properties.

The most common ceramics used are based on titanium dioxide (TiO₂) or barium titanate (BaTiO₃) with additives to tweak their properties.

As there are so many different possible combinations, they are arranged in various categories based on their performance. The categories are based on the initial tolerance of the capacitor (ie, the variation of real samples from the rated value), how the capacitance changes with temperature (the temperature coefficient) and how it changes with applied voltage (the voltage coefficient).

The most common type codes are NP0 or C0G (different names for the same category), JB, SL0, X5R, X5S, X6S, X7R, X7S, X8L, Y5V and Z5U.

To take three examples, NP0/C0G types have very close tolerances and no or minimal capacitance variation with temperature or voltage. They also have a low dielectric constant, so they are relatively large for a given capacitance value and voltage rating. As a result, they are also quite expensive.


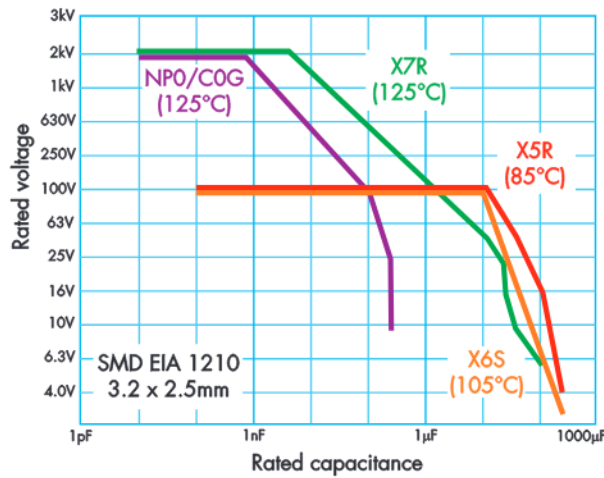


Fig.1: the range of capacitances and voltages available in 3.2 x 2.5mm SMD ceramic capacitors today. Both larger and smaller sizes are available, extending the range of values down to 0.1pF (1.6 x 0.8mm) and up to 470µF (4.5 x 3.2mm). Note how some types of ceramic dielectric are available to higher working voltages, and others to a higher maximum capacitance. (original source: Wikipedia)

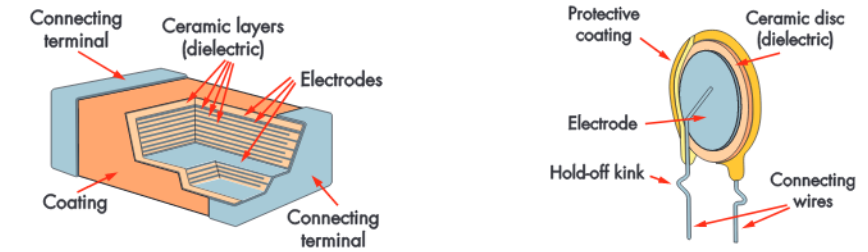

$$\text{Capacitance} = \frac{\# \text{ Layers} \times \text{Dielectric Constant} \times \text{Active Area}}{\text{Dielectric Thickness}}$$

Voltage Rating is determined by the Dielectric thickness

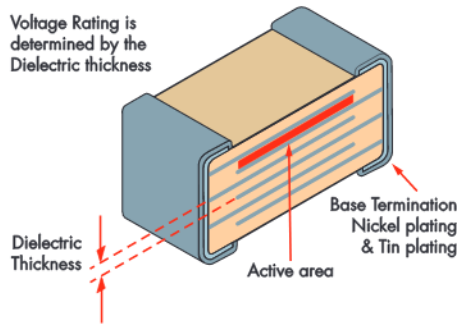


Fig.2: the structure of typical SMD and through-hole ceramic capacitors. SMD 'chip' ceramics are made of many layers; through-hole disc capacitors may have a single layer construction, as shown here, or increasingly these days, a similar internal structure to a multi-layer SMD capacitor. Multi-layer through-hole capacitors are usually encapsulated in epoxy, while the single-layer disc types can be encapsulated in ceramic. (original source: Johanson Dielectrics)

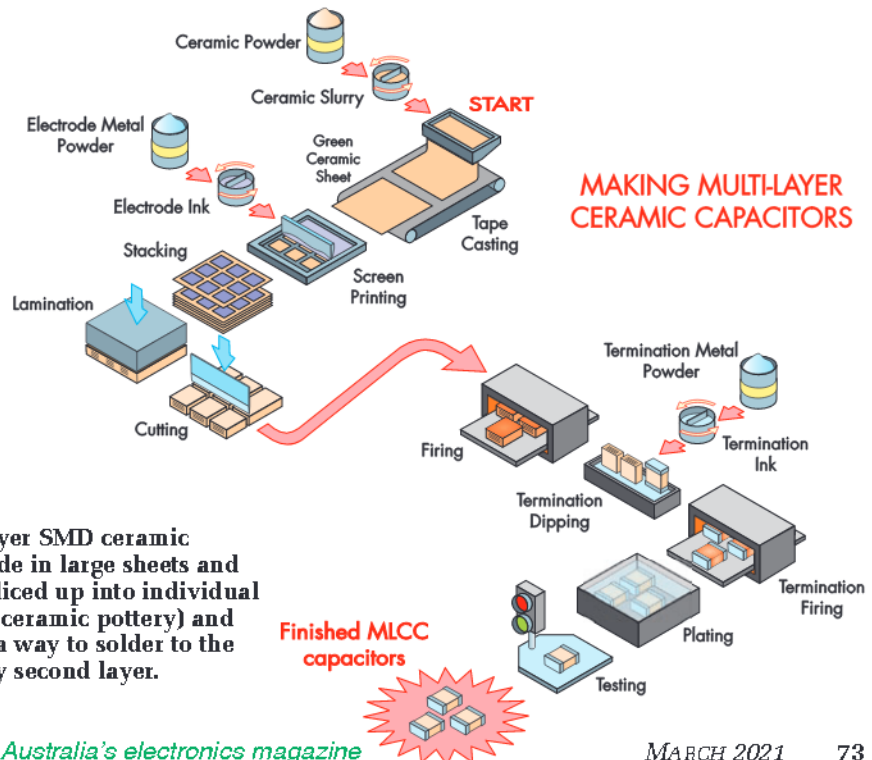


Fig.3: the manufacturing process for multi-layer SMD ceramic capacitors. To keep the cost low, they are made in large sheets and after lamination is complete, the sheets are sliced up into individual capacitors. Those are then fired (similarly to ceramic pottery) and the end terminals are added, which provide a way to solder to the capacitor while also electrically joining every second layer. (original source: Johanson Dielectrics)

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

VERSATILE BATTERY MULTI-LOGGER WITH TOUCHSCREEN LCD

Part 2 –
By TIM BLYTHMAN

In Part 1 of our new Battery Multi-Logger last month, we described how it combines the functions of a Micromite LCD BackPack along with voltage and current sensing hardware, and power-saving techniques, all on a single PCB. Now we'll go over the construction, testing, setup and calibration procedures so you can build and use it.

Before getting to the assembly instructions, let's quickly review the Logger's capabilities.

- It can handle batteries from 6-100V and monitor up to three bidirectional currents of up to 10A using its onboard shunts, or much more (to 100A or beyond) using external shunts.
- Its own power consumption is less than 1mA while actively logging with the screen off.
- It can display the current and historical data on a 2.8-inch backlit LCD touchscreen, and the data can also be downloaded to a computer over USB for further analysis.
- It tracks the current battery state-of-charge in both amp-hours (Ah)

and watt-hours (Wh), and it has a current measurement resolution of around 0.1% of full-scale, which equates to 10mA steps when using the internal shunts.

All of these functions are built onto a small PCB. As all the user interface features are accessed via the touchscreen, it can easily be integrated into other devices through a rectangular cutout in the case.

Construction

The Battery Logger is built on an 86mm x 50mm double-sided PCB coded 11106201. Fig.5 shows where the components go, on both sides of the board.

As usual for assembling a board

with many SMDs, it is useful to have the following on hand: flux paste, solder braid (wick), a magnifier, tweezers and an adjustable temperature iron. The smallest parts have pad spacing under 1mm, so solder bridges are almost inevitable, hence the need for flux paste and solder wick.

Since flux tends to generate smoke, use a fume extraction hood or work in an outdoor area, where the smoke can more easily dissipate.

One of the most fiddly parts is the USB socket, CON5, so start by fitting that. Dispense flux onto the pads and then sit the USB socket in place; it should lock into the holes in the PCB. Add some more flux to the tops of the pins.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

Preview only.

THIS...



OR THIS:



Every article in every issue of *SILICON CHIP* Nov 1987 - Dec 2019 Can now be yours forever in digital (PDF) format!

- High-res printable PDFs* ● Fully searchable files - with index ● Viewable on 99.9% of personal computers & tablets

* Some early articles may be scans

Software capable of reading PDFs required (freely available)

Digital edition PDFs are supplied as five-year+ blocks, covering a minimum of 60 issues. They're copied onto quality metal USB flash drives (at least 32GB). Just order which block(s) you want!

- Nov 1987 - Dec 1994 ● Jan 1995 - Dec 1999 ● Jan 2000 - Dec 2004 ● Jan 2005 - Dec 2009 ● Jan 2010 - Dec 2014 ● Jan 2015 - Dec 2019

Each five-year block is priced at just \$100, and yes, current subscribers receive the normal 10% discount. If you order the entire collection, the 6th block is FREE (ie, pay for five, the sixth is a bonus!). All PDFs are high resolution (some early editions excepted) and the USB Flash Drives are high quality metal USB3.0, so if you save the files to your PC hard disk, the USB Flash Drives can be used over and over!

Want to know more? Full details at siliconchip.com.au/shop/digital-pdfs

ELECTRONIC Wind Chimes

Part 2: finishing it off – by John Clarke

Last month, we described how our new Electronic Wind Chime worked, and how to build the electronics. Now we get to the tricky bit – modifying the wind chime itself so it can be driven by a series of solenoids.

Fear not, because we have detailed instructions on how to accomplish this, and finish the build by putting it all together and setting up the electronics.

We modified a Carson Home Accents “Amazing Grace” 640mm Sonnet Wind Chime to incorporate the solenoid drivers.

It is a 5-chime type with 31.5mm outside diameter tubes.

The longest tube is 590mm and shortest at 450mm.

The solenoids are supported on a circular ring made from 9mm MDF (medium-density fibreboard). This ring is held in place with an inverted U-shaped piece made from MDF and a couple of right-angle brackets. The whole frame is attached to the wind chime’s attachment hook with an M5 screw and nut.

For our prototype, the clapper plate was made using an 80mm diameter piece of 1mm aluminium sheet. The plate (shown in Fig.7) is designed to cater for the 5-chimes arranged 72° apart around the diameter.

The plate includes holes for the strings and a slot to allow the clapper plate to be placed over the clapper while its central support string is still attached.

The frame needs to be sized so the base plate can be positioned at a height where the solenoids and levers are in-

line with the top of the clapper plate.

There are two holes for the string attaching each solenoid to its chime. These need to be far enough apart so that the string does not touch the chime tube when pulled taut. This clapper plate can be glued in place, or held with a small self-tapping screw into the clapper after the string has been threaded.

The 100mm x 10mm rectangular solenoid levers are made from 1mm aluminium sheet; the two end holes are 3mm in diameter. Note that two holes are not centred, but placed close to one side, to give the best rotational movement when attached to the solenoid plunger.

The pivot point is a wood screw into the base plate. This should be long enough and screwed in sufficiently for the lever to sit horizontally, without being too tight to move.

The hole in the solenoid plunger was drilled to 2.5mm and then tapped for an M3 thread. That allows the lever to be secured at the fulcrum with just a 10mm-long M3 screw and no nut, with the screw acting as a bearing. Alternatively, you could drill 3mm diameter holes and secure them with machine screws and nuts.



Our finished Electronic Wind Chime. It's based on a commercial wind chime but ours works when there's no wind.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.



HOW TO ORDER

INTERNET (24/7)

siliconchip.com.au/Shop

PAYPAL (24/7)

silicon@siliconchip.com.au

EMAIL (24/7)

silicon@siliconchip.com.au

MAIL (24/7)

PO Box 139, COLLAROY, NSW 2207

PHONE - (0)5:00 AET, Mon-Fri

(02) 9839 3295, +612 for international

You can also pay by cheque/money order (Orders by mail only) or bank transfer. Make cheques payable to Silicon Chip.

03/21

YES! You can also order or renew your **SILICON CHIP** subscription via any of these methods as well! The best benefit, apart from the magazine? **Subscribers get a 10% discount on all orders for parts.**

PRE-PROGRAMMED MICROS

For a complete list, go to siliconchip.com.au/Shop/9

\$10 MICROS

ATmega328P	RF Signal Generator (Jun19)
ATmega328P-AUR	RGB Stackable LED Christmas Star (Nov20)
ATtiny85V-10PU	Shirt Pocket Audio Oscillator (Sep20)
ATtiny816	ATtiny816 Development/Breakout Board (Jan19)
PIC10F202-E/DT	Ultrabrite LED Driver (with free TC6502P095VCT IC, Sep19)
PIC12F1572-I/SN	LED Christmas Ornaments (Nov20; specify variant)
PIC12F617-I/P	Temperature Switch Mk2 (Jun18), Recurring Event Reminder (Jul18) Door Alarm (Aug18), Steam Whistle (Sep18), White Noise (Sep18) Trailing Edge Dimmer (Feb19), Steering Wheel to IR Adaptor (Jun19) Car Radio Dimmer (Aug19), MiniHeart Heartbeat Simulator (Jan21)
PIC12F675-I/P	Motor Speed Controller (Mar18), Heater Controller (Apr18) Useless Box IC3 (Dec18)
PIC12F675-I/SN	Tiny LED Xmas Tree (Nov19)
PIC16F1455-I/P	Microbridge (May17), USB Flexitimer (June18) Digital Interface Module (Nov18), GPS Finesaver (Jun19) Digital Lighting Controller LED Slave (Dec20)
PIC16F1455-I/SL	01' Timer II (Jul20), Battery Multi Logger (Feb21)
PIC16F1459-I/P	5-Way LCD Panel Meter (Nov19), IR Remote Control Assistant (Jul20) Ultrasonic Cleaner (Sep20), Electronic Wind Chime (Feb21)
PIC16F1507-I/P	Wideband Oxygen Sensor (Jun-Jul12)
PIC16F1705-I/P	Flexible Digital Lighting Controller Slave (Oct20)
PIC16F88-E/P	Auto Headlight Controller (Oct13), Motor Speed Controller (Feb14) Automotive Sensor Modifier (Dec16)
PIC16F88-I/P	Remote-controlled Preamp with Tone Control (Mar19) UHF Repeater (May19), Six Input Audio Selector (Sep19) Universal Battery Charge Controller (Dec19)

\$15 MICROS

PIC16F1459-I/SO	Four-Channel DC Fan & Pump Controller (Dec18)
PIC16F877A-I/P	6-Digit GPS Clock (May09), 16-bit Digital Pot (Jul10), Semtest (Feb12)
PIC32MM0256GPM028-I/SS	Super Digital Sound Effects (Aug18)
PIC32MX170F256D-501P/T	44-pin Micromite Mk2 (Aug14), 4DoF Simulation Seat (Sep19)
PIC32MX170F256B-501/SP	Micromite LCD Backpack V1-V3 (Feb16 / May17 / Aug19) Touchscreen Voltage / Current Ref. (Oct16), Deluxe eFuse (Aug17) Micromite DDS for IF Alignment (Sep17), Tariff Clock (Jul18) GPS-Synched Frequency Reference (Nov18), Air Quality Monitor (Feb20) RCL Box (Jun20), Digital Lighting Controller Micromite Master (Nov20)
PIC32MX170F256B-I/SO	Battery Multi Logger (Feb21)
PIC32MX270F256B-501/SP	ASCII Video Terminal (Jul14), USB M&K Adaptor (Feb19)
PIC32MX795F512H-801/PT	Maximite (Mar11), miniMaximite (Nov11), Colour Maximite (Sep12), Touchscreen Audio Recorder (Jun14)

\$20 MICROS

dsPIC33FJ64MC802-E/SP	1.5kW Induction Motor Speed Controller (Aug13)
dsPIC33FJ128GP306-I/PT	CLASSIC DAC (Feb13)
dsPIC33FJ128GP802-I/SP	Digital Audio Delay (Dec11), Quizzical (Oct11) Ultra-LD Preamp (Nov11), LED Musicalcolour (Oct12)
PIC32MX470F512H-I/PT	Stereo Echo/Reverb (Feb14), Digital Effects Unit (Oct14)
PIC32MX470F512H-120/PT	Micromite Explore 64 (Aug16), Micromite Plus (Nov16)
PIC32MX470F512L-120/PT	Micromite Explore 100 (Sep16)

\$30 MICROS

PIC32MX695F512L-801/PF	Colour MaxiMite (Sep12)
PIC32MZ2048EFH064-I/PT	DSP Crossover/Equaliser (May19), Low-Distortion DDS (Feb20) DIY Reflow Oven Controller (Apr20)

KITS, SPECIALISED COMPONENTS ETC

siliconchip.com.au/Shop/

MINI ISOLATED SERIAL LINK COMPLETE KIT (CAT SC5750) (MAR 21)

All parts required to build the project including the PCB **\$10.00**

MINIHEART HEARTBEAT SIMULATOR (CAT SC5732) (JAN 21)

All SMD parts, including IC2 - **does not include PCB** **\$5.00**

AM/FM/SW RADIO (JAN 21)

- PCB-mount right-angle SMA socket (SC4918) **\$2.50**
- Pulse-type rotary encoder with integral pushbutton (SC5601) **\$3.00**
- 1.6x2 LCD module (does not use I²C module) (SC4198) **\$7.50**

LED CHRISTMAS ORNAMENTS (CAT SC5579) (NOV 20)

Complete kit including micro but no coin cell (specify PCB shape & colour) **\$14.00**

RGB STACKABLE LED CHRISTMAS STAR (CAT SC5525) (NOV 20)

Complete kit including PCB, micro, diffused RGB LEDs and other parts **\$38.50**

FLEXIBLE DIGITAL LIGHTING CONTROLLER PARTS (OCT 20)

4 x Si8751AB ICs, 8 x Si1HB15N60E-GE3 Mosfets, switchmode converter module, 6N137 opto, high-voltage resistors and capacitors plus SMD LEDs. **\$100.00**

D1 MINI LCD WIFI BACKPACK KIT (OCT 20)

Complete kit including 3.5-inch touchscreen, PCB and ESP8266-based module **\$70.00**

SHIRT POCKET AUDIO OSCILLATOR (SEP 20)

Kit including 3D-printed case, and everything else except the battery and wiring **\$40.00**
- 64x32 pixel white OLED (0.49-inch/12.5mm diagonal) **\$10.00**
- Pulse-type rotary encoder with integral pushbutton **\$3.00**

COLOUR MAXIMITE 2 (JUL 20)

Short form kit: includes everything except the case, CPU module, power supply, optional parts and cables (Cat SC5478) **\$80.00**

Short Form kit (with CPU module): includes the programmed Waveshare CPU module and everything included in the short form kit above (Cat SC5508) **\$140.00**

MICROMITE LCD BACKPACK V3 KIT (CAT SC5082) (AUG 19)

Includes PCB, programmed micros, 3.5in touchscreen LCD, UB3 lid, mounting hardware, Mosfets for PWM backlight control and all other **mandatory** on-board parts **\$75.00**

Separate/Optional Components:

- 3.5-inch TFT LCD touchscreen (Cat SC5062) **\$30.00**

- DHT22 temp/humidity sensor (Cat SC4150)	\$7.50
- BMP180 (Cat SC4343) OR BMP280 (Cat SC4595) temp/pressure sensor	\$5.00
- BME280 temperature/pressure/humidity sensor (Cat SC4608)	\$10.00
- DS3231 real-time clock SOIC-16 IC (Cat SC5103)	\$3.00
- 23LC1024 1MB RAM (SOIC-8) (Cat SC5104)	\$5.00
- AT25SF041 512KB flash (SOIC-8) (Cat SC5105)	\$1.50
- 10µF 16V X7R through-hole capacitor (Cat SC5106)	\$2.00

VARIOUS MODULES & PARTS

- CP2102 USB-UART bridge	\$5.00
- 15mΩ 3W SMD resistor (Battery Multi Logger / Arduino PSU, Feb21)	\$2.50
- DS3231(M) real-time clock SMD IC (Battery Multi Logger, Feb21)	\$3.00
- MCP4251-5.02E/P (Arduino Power Supply, Feb21)	\$3.00
- Pair of CSD18534 (Electronic Wind Chimes, Feb21)	\$6.00
- IPP80P03P4L04 (Dual Battery Lifesaver / Vintage Radio Supply, Dec20)	\$5.00
- 16x2 LCD module (Digital RF Power Meter, Aug20)	\$7.50
- WS2812 8x8 RGB LED matrix module (01' Timer II, Jul20)	\$15.00
- MAX038 function generator IC (H-Field Transanalyser, May20)	\$25.00
- MC1496P double-balanced mixer (H-Field Transanalyser, May20)	\$2.50
- AD8495 thermocouple interface (DIY Reflow Oven Controller, Apr20)	\$10.00
- Si8751AB 2.5kV isolated Mosfet driver IC (Charge Controller, Dec19)	\$5.00
- I/O expander modules (Nov19): PCA9685 - \$6.00 ; PCF8574 - \$3.00 ; MCP23017 - \$3.00	
- SMD 1206 LEDs, packets of 10 unless stated otherwise (Xmas Ornaments, Nov20): yellow - \$0.70 ; amber - \$0.70 ; blue - \$0.70 ; cyan - \$1.00 ; pink (1 only) - \$0.20	
- ISD1820-based voice recorder / playback module (Junk Mail, Aug19)	\$4.00
- 23LCV1024-I/P SRAM & MCP73831T (UHF Repeater, May19)	\$11.50
- MCP170D 3.3V LDO regulator (suitable for USB M&K Adaptor, Feb19)	\$1.50
- LM4865MX amplifier & LF50CV regulator (Tinnitus/Insomnia Killer, Nov18)	\$10.00
- 2.8-inch touchscreen LCD module with SD card socket (Tide Clock, Jul18)	\$22.50
- ESP-D1 WiFi Module (EI Cheapo Modules, Apr18)	\$5.00
- WiFi Antennas with U.FL/IPX connectors (Water Tank Level Meter with WiFi, Feb18): 5dBi - \$12.50 ; 2dBi (omnidirectional) - \$10.00	
- NRF24L01+PA+NA transceiver, SMA connector & antenna (EI Cheapo, Jan18) \$5.00	
- WeMos D1 Arduino-compatible boards with WiFi (Sep17, Feb18): ThingSpeak data logger - \$10.00 ; D1 R2 with external antenna socket - \$15.00	
- ERA-25M+ MMIC & ADCH-80A+ choke (6GHz Frequency Counter, Oct17) \$15.00	
- DS3231 real-time clock module with mounting hardware (EI Cheapo, Oct16) \$5.00	

PRINTED CIRCUIT BOARDS & CASE PIECES

For a complete list, go to siliconchip.com.au/Shop/8

PRINTED CIRCUIT BOARD TO SUIT PROJECT	DATE	PCB CODE	Price
THEREMIN	JAN18	23112171	\$12.50
PROPORTIONAL FAN SPEED CONTROLLER	JAN18	05111171	\$2.50
WATER TANK LEVEL METER (INC. HEADERS)	FEB18	21110171	\$7.50
10-LED BAROGRAPH	FEB18	04101181	\$7.50
↳ SIGNAL PROCESSING	FEB18	04101182	\$5.00
FULL-WAVE MOTOR SPEED CONTROLLER	MAR18	10102181	\$10.00
VINTAGE TV A/V MODULATOR	MAR18	02104181	\$7.50
AM RADIO TRANSMITTER	MAR18	06101181	\$7.50
HEATER CONTROLLER	APR18	10104181	\$10.00
DELUXE FREQUENCY SWITCH	MAY18	05104181	\$7.50
USB PORT PROTECTOR	MAY18	07105181	\$2.50
2 x 12V BATTERY BALANCER	MAY18	14106181	\$2.50
USB FLEXITIMER	JUN18	19106181	\$7.50
WIDE-RANGE LC METER (INC. HEADERS)	JUN18	SC4618	\$7.50
↳ WITHOUT HEADERS	JUN18	04106181	\$7.50
↳ CASE PIECES (CLEAR)	JUN18	SC4609	\$7.50
TEMPERATURE SWITCH MK2	JUN18	05105181	\$7.50
LiFePO ₄ UPS CONTROL SHIELD	JUN18	11106181	\$5.00
RASPBERRY PI TOUCHSCREEN ADAPTOR	JUL18	24108181	\$5.00
RECURRING EVENT REMINDER	JUL18	19107181	\$5.00
BRAINWAVE MONITOR (EEG)	AUG18	25107181	\$10.00
SUPER DIGITAL SOUND EFFECTS	AUG18	01107181	\$2.50
DOOR ALARM	AUG18	03107181	\$5.00
STEAM WHISTLE / DIESEL HORN	SEP18	09106181	\$5.00
DCC PROGRAMMER (INC. HEADERS)	OCT18	SC4716	\$7.50
↳ WITHOUT HEADERS	OCT18	09107181	\$5.00
OPTO-ISOLATED RELAY (INC. EXT. BOARDS)	OCT18	10107181/2	\$7.50
GPS-SYNCHED FREQUENCY REFERENCE	NOV18	04107181	\$7.50
LED CHRISTMAS TREE	NOV18	16107181	\$5.00
DIGITAL INTERFACE MODULE	NOV18	16107182	\$2.50
TINNITUS/INSOMNIA KILLER (JAYCAR VERSION)	NOV18	01110181	\$5.00
↳ ALTRONICS VERSION	NOV18	01110182	\$5.00
HIGH-SENSITIVITY MAGNETOMETER	DEC18	04101011	\$12.50
USELESS BOX	DEC18	08111181	\$7.50
FOUR-CHANNEL DC FAN & PUMP CONTROLLER	DEC18	05108181	\$5.00
ATtiny816 DEVELOPMENT/BREAKOUT PCB	JAN19	24110181	\$5.00
ISOLATED SERIAL LINK	JAN19	24107181	\$5.00
DAB+FM/AM RADIO	JAN19	06112181	\$15.00
↳ CASE PIECES (CLEAR)	JAN19	SC4849	\$0.00
REMOTE CONTROL DIMMER MAIN PCB	FEB19	10111191	\$10.00
↳ MOUNTING PLATE	FEB19	10111192	\$10.00
↳ EXTENSION PCB	FEB19	10111193	\$10.00
MOTION SENSING SWITCH (SMD) PCB	FEB19	05102191	\$2.50
USB MOUSE AND KEYBOARD ADAPTOR PCB	FEB19	24311181	\$5.00
LOW-NOISE STEREO PREAMP MAIN PCB	MAR19	01111119	\$25.00
↳ INPUT SELECTOR PCB	MAR19	01111112	\$15.00
↳ PUSHBUTTON PCB	MAR19	01111113	\$5.00
DIODE CURVE PLOTTER	MAR19	04112181	\$7.50
↳ UB3 LID (MATTE BLACK)	MAR19	SC4927	\$5.00
FLIP-DOT (SET OF ALL FOUR PCBs)	APR19	SC4950	\$17.50
↳ COIL PCB	APR19	19111181	\$5.00
↳ PIXEL PCB (16 PIXELS)	APR19	19111182	\$5.00
↳ FRAME PCB (8 FRAMES)	APR19	19111183	\$5.00
↳ DRIVER PCB	APR19	19111184	\$5.00
iCESTICK VGA ADAPTOR	APR19	02103191	\$2.50
UHF DATA REPEATER	MAY19	15004191	\$10.00
AMPLIFIER BRIDGE ADAPTOR	MAY19	01105191	\$5.00
3.5-INCH LCD ADAPTOR FOR ARDUINO	MAY19	24111181	\$5.00
DSP CROSSOVER (ALL PCBs - TWO DACs)	MAY19	SC5023	\$40.00
↳ ADC PCB	MAY19	01106191	\$7.50
↳ DAC PCB	MAY19	01106192	\$7.50
↳ CPU PCB	MAY19	01106193	\$5.00
↳ PSU PCB	MAY19	01106194	\$7.50
↳ CONTROL PCB	MAY19	01106195	\$5.00
↳ LCD ADAPTOR	MAY19	01106196	\$2.50
STEERING WHEEL CONTROL IR ADAPTOR	JUN19	05105191	\$5.00
GPS SPEEDO/CLOCK/VOLUME CONTROL	JUN19	01104191	\$7.50
↳ CASE PIECES (MATTE BLACK)	JUN19	SC4987	\$10.00
RF SIGNAL GENERATOR	JUN19	04106191	\$15.00
RASPBERRY PI SPEECH SYNTHESIS/AUDIO	JUL19	01106191	\$5.00
BATTERY ISOLATOR CONTROL PCB	JUL19	05106191	\$7.50
↳ MOSFET PCB (2oz)	JUL19	05106192	\$10.00
MICROMITE LCD BACKPACK V3	AUG19	07106191	\$7.50

PRINTED CIRCUIT BOARD TO SUIT PROJECT	DATE	PCB CODE	Price
CAR RADIO DIMMER ADAPTOR	AUG19	05107191	\$5.00
PSEUDO-RANDOM NUMBER GENERATOR	AUG19	16106191	\$5.00
40of SIMULATION SEAT CONTROLLER PCB	SEP19	11109191	\$7.50
↳ HIGH-CURRENT H-BRIDGE MOTOR DRIVER	SEP19	11109192	\$2.50
MICROMITE EXPLORE-28 (4-LAYERS)	SEP19	07108191	\$5.00
SIX INPUT AUDIO SELECTOR MAIN PCB	SEP19	01110191	\$7.50
↳ PUSHBUTTON PCB	SEP19	01110192	\$5.00
ULTRABRITE LED DRIVER	SEP19	16109191	\$2.50
HIGH RESOLUTION AUDIO MILLIVOLTMETER	OCT19	04108191	\$10.00
PRECISION AUDIO SIGNAL AMPLIFIER	OCT19	04107191	\$5.00
SUPER-9 FM RADIO PCB SET	NOV19	06109181-5	\$25.00
↳ CASE PIECES & DIAL	NOV19	SC5166	\$25.00
TINY LED XMAS TREE (GREEN/RED/WHITE)	NOV19	16111191	\$2.50
HIGH POWER LINEAR BENCH SUPPLY	NOV19	18111181	\$10.00
↳ HEATSINK SPACER (BLACK)	NOV19	SC5168	\$5.00
DIGITAL PANEL METER / USB DISPLAY	NOV19	18111182	\$2.50
↳ ACRYLIC BEZEL (BLACK)	NOV19	SC5167	\$2.50
UNIVERSAL BATTERY CHARGE CONTROLLER	DEC19	14107191	\$10.00
BOOKSHELF SPEAKER PASSIVE CROSSOVER	JAN20	01101201	\$10.00
↳ SUBWOOFER ACTIVE CROSSOVER	JAN20	01101202	\$7.50
ARDUINO DCC BASE STATION	JAN20	09207181	\$5.00
NUTUBE VALVE PREAMPLIFIER	JAN20	01112191	\$10.00
TUNEABLE HF PREAMPLIFIER	JAN20	06110191	\$2.50
4G REMOTE MONITORING STATION	FEB20	27111191	\$5.00
LOW-DISTORTION DDS (SET OF 5 BOARDS)	FEB20	01106192-6	\$20.00
NUTUBE GUITAR DISTORTION / OVERDRIVE PEDAL	MAR20	01102201	\$7.50
THERMAL REGULATOR INTERFACE SHIELD	MAR20	21109181	\$5.00
↳ PELTIER DRIVER SHIELD	MAR20	21109182	\$5.00
DIY REFLOW OVEN CONTROLLER (SET OF 3 PCBs)	APR20	01106193/5/6	\$12.50
7-BAND MONO EQUALISER	APR20	01104201	\$7.50
↳ STEREO EQUALISER	APR20	01104202	\$7.50
REFERENCE SIGNAL DISTRIBUTOR	APR20	CSE200103	\$7.50
H-FIELD TRANSANALYSER	MAY20	06102201	\$10.00
CAR ALTIMETER	MAY20	05105201	\$5.00
RCL BOX RESISTOR BOARD	JUN20	04104201	\$7.50
↳ CAPACITOR / INDUCTOR BOARD	JUN20	04104202	\$7.50
ROADIES' TEST GENERATOR SMD VERSION	JUN20	01005201	\$2.50
↳ THROUGH-HOLE VERSION	JUN20	01005202	\$5.00
COLOUR MAXIMITE 2 PCB (BLUE)	JUL20	07107201	\$10.00
↳ FRONT & REAR PANELS (BLACK)	JUL20	SC5500	\$10.00
OL' TIMER II PCB (RED, BLUE OR BLACK)	JUL20	19104201	\$5.00
↳ ACRYLIC CASE PIECES / SPACER (BLACK)	JUL20	SC5448	\$7.50
IR REMOTE CONTROL ASSISTANT PCB (JAYCAR)	JUL20	15005201	\$5.00
↳ ALTRONICS VERSION	JUL20	15005202	\$5.00
USB SUPERCODEC	AUG20	01106201	\$12.50
↳ BALANCED ATTENUATOR	NOV20	01106202	\$7.50
SWITCHMODE 78XX REPLACEMENT	AUG20	18105201	\$2.50
WIDEBAND DIGITAL RF POWER METER	AUG20	04106201	\$5.00
ULTRASONIC CLEANER MAIN PCB	SEP20	04105201	\$7.50
↳ FRONT PANEL	SEP20	04105202	\$5.00
NIGHT KEEPER LIGHTHOUSE	SEP20	08110201	\$5.00
SHIRT POCKET AUDIO OSCILLATOR	SEP20	01110201	\$2.50
↳ 8-PIN ATtiny PROGRAMMING ADAPTOR	SEP20	01110202	\$1.50
D1 MINI LCD WIFI BACKPACK	OCT20	24106121	\$5.00
FLEXIBLE DIGITAL LIGHTING CONTROLLER SLAVE	OCT20	16110202	\$20.00
↳ FRONT PANEL (BLACK)	OCT20	16110203	\$20.00
LED XMAS ORNAMENTS	NOV20	16111191-9	\$3.00
3D LED STACKABLE STAR	NOV20	16109201	\$12.50
↳ RGB VERSION (BLACK)	NOV20	16109202	\$12.50
DIGITAL LIGHTING MICROMITE MASTER	NOV20	16110201	\$5.00
↳ CP2102 ADAPTOR	NOV20	16110204	\$2.50
BATTERY VINTAGE RADIO / SPACER SUPPLY	DEC20	11111201	\$7.50
DUAL BATTERY LIFESAVER	DEC20	11111202	\$2.50
DIGITAL LIGHTING CONTROLLER LED SLAVE	DEC20	16110205	\$5.00
AM/FM/SW RADIO	JAN21	CSE200902A	\$10.00
MINIHEART HEARTBEAT SIMULATOR	JAN21	01109201	\$5.00
I'M BUSY GO AWAY (DOOR WARNING)	JAN21	16112201	\$2.50
BATTERY MULTI LOGGER	FEB21	11106201	\$5.00
ELECTRONIC WIND CHIMES	FEB21	23011201	\$10.00
ARDUINO 0-14V POWER SUPPLY SHIELD	FEB21	18106201	\$5.00
NEW-PCBs			
HIGH-CURRENT BATTERY BALANCER (4-LAYERS)	MAR21	14102211	\$12.50
MINI ISOLATED SERIAL LINK	MAR21	24102211	\$2.50

We also sell an A2 Reactance Wallchart, RTV&H DVD, Vintage Radio DVD plus various books at siliconchip.com.au/Shop/3

VINTAGE RADIO

Kriesler's 41-21 mantel/portable set

By Ian Batty



The Kriesler "Triplex" 41-21 is an all-transistor, battery-powered radio which uses reflexing. It was produced in the late 50s/early 60s and was sold with a plastic case that came in one of three colours (pink, brown or red).

Engineers are a chummy lot. During my Air Force days, I encountered a variety of engineering types needed to keep an aircraft flying: mechanical engineers for the engines, airframes and controls, electrical engineers for the electrical systems and controls, electronics engineers for the radio, radar navigation and instrument systems, and commerce types for supplying all the parts needed.

But when I took a look at the Kriesler 41-21 (manufactured from 1959 to 1961), I started wondering whether the

mechanical engineering folks at Kriesler were 'in dispute' with the electronics engineering cohort.

Surely no-one could have come up with the labyrinthine dial drive in this otherwise fine set unless they had some axe to grind. Yes, I get that it's a way of accommodating a 130mm long dial with a 41mm diameter drum on the tuning gang, when an 82mm diameter drum would otherwise be needed. But I would have put in a 2:1 gear set to the drum and simplified the rest of the arrangement.

Electrically, the set is also somewhat interesting. It uses a reflexed second intermediate frequency (IF) amplifier, with that transistor also acting as an audio preamp. The design is similar to the Philips MT4 that I described in September 2017 (siliconchip.com.au/Article/10806).

Like that set, the reflexed stage needs carefully-managed signal levels, so the 41-21 has a two-gang volume control potentiometer. More on that later.

So despite its dial drive, it's an Australian set worth an article.

First appearances

The curved, rippled front with its coloured inset and black case rear is a pleasing alternative to the "square black box" so often resorted to in the late 50s/early 60s.

The "slide rule" dial is some 130mm long; plenty of space to list all the stations of the day. The side-mounted volume control is placed for easy adjustment. The separate on/off switch eases the load on the volume control; ie, it doesn't need to be rotated every time you turn the set on or off, giving a longer trouble-free life.

Circuit details

The set's circuit is shown in Fig.1. The main difference between the 41-21 and the identically-cased 41-21A is the 21A's use of a single-tuned third IF transformer.

All transistors are Philips/Mullard "OC" series germanium PNPs, with a negative power supply (ie, positive ground).

Ferrite rod L2 is tuned by the antenna section of the tuning gang, C3A. A low-impedance secondary matches to the base of the converter via capacitor C2, in parallel with 2.2kΩ resistor R1 (the bottom half of the converter's bias divider). C2 is there to overcome the resistance of R1 at radio frequencies

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

WHAT DO YOU WANT? PRINT? OR DIGITAL?



EITHER . . . OR BOTH The choice is YOURS!

Regardless of what you might hear, most people still prefer a magazine which they can hold in their hands. That's why SILICON CHIP still prints thousands of copies each month – and will continue to do so.

But there are times when you want to read SILICON CHIP online . . . and that's why the online version www.siliconchip.com.au is maintained at the same time.

WANT TO SUBSCRIBE TO THE PRINT EDITION? (as you've always done!) No worries!

WANT TO SUBSCRIBE TO THE DIGITAL (ONLINE) EDITION? No worries!

WANT TO SUBSCRIBE TO BOTH THE PRINT AND THE DIGITAL EDITION? No worries!

SILICON CHIP, Australia's most read, most respected and most valued electronics reference magazine, makes it so easy for you. And even better, we offer short-term subscriptions (as short as six months) so you can effectively "try before you commit".

And, of course, as a subscriber, you'll know you'll never miss an issue AND save money!

Here's the deal:

If you're in Australia, you can subscribe to the print edition (only) of SILICON CHIP for \$105 for a full 12 months (12 issues) – that's almost \$15 less than the over-the-counter price AND we pick up the postage.

If you're overseas, you can subscribe to the print edition – email us for the rates for your particular country.

If you're anywhere in the world, you can subscribe to the online edition of SILICON CHIP for \$AU85.

And, of course, from anywhere in the world, you can subscribe to both print and online editions – in Australia, the price is just \$125 (only \$20 more than the print edition price). Overseas – again email us for the rates in your country.

While your subscription is current, you can download software, PCB patterns, panel artwork etc FREE OF CHARGE!

Want more information? Log onto our website and click on "subscriptions"


www.siliconchip.com.au

PRODUCT SHOWCASE

Raspberry Pi Pico – available from element14

element14 has announced the availability of the first product built on Raspberry Pi-designed silicon: Raspberry Pi Pico. This new product brings high performance, low cost, and ease of use to the microcontroller market, in a \$5 development kit.

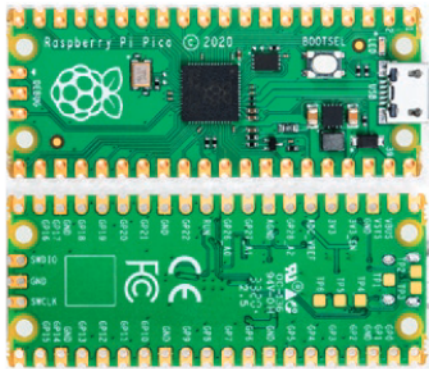The Raspberry Pi Pico is available to purchase from <https://au.element14.com/3643332>



At the heart of the Raspberry Pi Pico is the RP2040, a Raspberry Pi-designed micro. It features two 133MHz ARM Cortex-M0+ cores; 264KB of on-chip SRAM; 26 GPIO pins; dedicated hardware for commonly used peripherals and a programmable I/O subsystem for extended peripheral support; a 4-channel ADC with internal temperature sensor; and built-in USB 1.1 with host and device support.

The RP2040 microcontroller offers high performance for integer workloads, a large on-chip memory, and a wide range of I/O options, making it a flexible solution for a wide range of microcontroller applications.

Key features include:

Memory: 264KB of on-chip SRAM; 2MB of on-board QSPI Flash.

Interfacing and mechanicals: 26 GPIO pins, of which three can be used as analog inputs. 0.1-inch through-

hole pads with castellated edges for SMT assembly.

Power: on-board power supply to generate 3.3V for the RP2040 and external circuitry. Wide input voltage range, from 1.8V to 5.5V, giving designers the flexibility to select their preferred power source.

Developer tools: simple drag and drop programming via micro-USB. 3-pin Serial Wire Debug (SWD) for interactive debugging, C-based SDK, MicroPython port, and extensive examples and documentation.

To find out more about the Raspberry Pi Pico, visit www.element14.com/community/docs/DOC-96021/

element14

72 Ferndell Street
Chester Hill, NSW 2162
Phone: 1300 361 005
Web: <https://au.element14.com/>

Crocus CT220 – the industry's first TMR contactless current sensors

Mouser is now stocking the CT220 XtremeSense contactless current sensors from Crocus Technology.

The CT220 sensors are powered by Crocus' XtremeSense tunnel magneto-resistance (TMR) 1D technology, which enables them to detect slight changes in AC or DC. The sensors offer a 2.7V to 5.5V supply voltage range and 1.2mA supply current rating in a 5-lead SOT23 package. It measures the magnetic field

of the current flowing through a busbar or PCB trace and converts it to an analog output voltage that represents the field and current.

These sensors achieve a typical total output error of $\pm 0.5\%$ while sensing fields as low as 5mA. CT220 current sensors feature an inherently high isolation, making them the ideal solution for applications where product safety compliance is a requirement.

These applications include motor controls, solar inverters, power distribution units and power supplies, and Internet of Things (IoT) devices.

To learn more, visit www.mouser.com/new/crocus-technology/crocus-ct220-xtremesense-sensors/

Mouser Electronics Inc.

Phone: (852) 3756 4700
Web: www.mouser.com/

Postponement of ElectroneX to September 2021

AEE, organisers of ElectroneX, have been closely monitoring the COVID-19 situation and following recent outbreaks and border closures over the Christmas period, and have made the decision to postpone ElectroneX (Electronics Design and Assembly Expo) at Rosehill Gardens in Sydney until 15-16 September 2021 which also brings the Expo back into the normal September timeframe.

This cautious approach will provide sufficient time for the vaccine roll-out to be implemented and for state governments to provide more certainty in relation to their border closure policies

which is currently having a major impact on interstate business.

Due to the lead time that is required for the promotion of the show and the need for companies and visitors to be able to freely travel to NSW, we believe this is the best decision to help ensure the overall success of the Expo.

In accordance with the terms and conditions, all contracts and payments that have been made will be transferred to the rescheduled dates.

If you have any questions in relation to the rescheduling please contact Noel Gray on 0407 943 817 or Vee Johnson on 0422 399 818.



AEE ElectroneX

Noel Gray – Managing Director AEE
PO Box 5269
South Melbourne, VIC 3205
Phone: (03) 9676 2133
Mobile: 0407 943 817
Web: www.electroneX.com.au/
Mail: ngray@auexhibitions.com.au

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

SILICON CHIP

This is a preview of the March 2021 issue of
SILICON CHIP.

For access to the full 112 pages of content in
the magazine, purchase the issue at our
website: www.siliconchip.com.au

Or take out an online subscription for access to
the latest issues.

MARKET CENTRE

Cash in your surplus gear. Advertise it here in SILICON CHIP

PCB PRODUCTION

PCB MANUFACTURE: single to multi-layer. Bare board tested. One-offs to any quantity. 48 hour service. Artwork design. Excellent prices. Check out our specials: www.ledelectronics.com.au

FOR SALE

GREAT VALUE PARTS and more are found in the Tronixlabs eBay store via tronixlabs.com.au – for enquiries or support please email support@tronixlabs.com

LEDs, BRAND NAME and generic LEDs. Heatsinks, fans, LED drivers, power supplies, LED ribbon, kits, components, hardware, EL wire. www.ledsales.com.au

ASSORTED BOOKS FOR \$5 EACH
Selling assorted books on electronics and other related subjects – condition varies. All books can be viewed at: siliconchip.com.au/link/aawx

Email for a postage quote, quote photo numbers when referring to a book: silicon@siliconchip.com.au

KIT ASSEMBLY & REPAIR

VINTAGE RADIO REPAIRS: electrical mechanical fitter with 36 years experience and extensive knowledge of valve and transistor radios. Professional and reliable repairs. All workmanship guaranteed.

\$17 inspection fee plus charges for parts and labour as required. Labour fees \$38 p/h. Pensioner discounts available on application.

Contact Alan, VK2FALW on 0425 122 415 or email blgalradloshack@gmail.com

DAVE THOMPSON (the Serviceman from SILICON CHIP) is available to help you with kit assembly, project troubleshooting, general electronics and custom design work. No job too small. Based in Christchurch, NZ but service available Australia/NZ wide. Email dave@davethompson.co.nz

KEITH RIPPON KIT ASSEMBLY & REPAIR:

* Australia & New Zealand;

* Small production runs.

Phone Keith: 0409 662 794

keth.rippon@gmail.com

Silicon Chip Binders

REAL VALUE AT \$19.50* PLUS P&P



Keep your copies safe, secure and always available with these handy binders

These binders will protect your copies of SILICON CHIP. They feature heavy-board covers, hold 12 issues & will look great on your bookshelf.

Silicon Chip Publications

Order online from www.siliconchip.com.au/Shop/4

ADVERTISING IN MARKET CENTRE

Classified Ad Rates: \$32.00 for up to 20 words (punctuation not charged) plus \$1.20 for each additional word. Display ads in Market Centre (minimum 2cm deep, maximum 10cm deep): \$82.50 per column centimetre per insertion. All prices include GST. Closing date: 5 weeks prior to month of sale. To book, email the text to silicon@siliconchip.com.au and include your name, address & credit card details, or phone Glyn (02) 9939 3295 or 0431 792 293.

WARNING!

SILICON CHIP magazine regularly describes projects which employ a mains power supply or produce high voltage. All such projects should be considered dangerous or even lethal if not used safely. Readers are warned that high voltage wiring should be carried out according to the instructions in the articles.

When working on these projects use extreme care to ensure that you do not accidentally come into contact with mains AC voltages or high voltage DC. If you are not confident about working with projects employing mains voltages or other high voltages, you are advised not to attempt work on them. Silicon Chip Publications Pty Ltd disclaims any liability for damages should anyone be killed or injured while working on a project or circuit described in any issue of SILICON CHIP magazine.


Devices or circuits described in SILICON CHIP may be covered by patents. SILICON CHIP disclaims any liability for the infringement of such patents by the manufacturing or selling of any such equipment. SILICON CHIP also disclaims any liability for projects which are used in such a way as to infringe relevant government regulations and by-laws.

Advertisers are warned that they are responsible for the content of all advertisements and that they must conform to the Competition & Consumer Act 2010 or as subsequently amended and to any governmental regulations which are applicable.

Notes & Errata

USB SuperCodec, August-October 2020: in the Fig.13 circuit diagram on page 88 of the September 2020 issue, pin 12 of IC7 (SDOUT) should not be shown connected to pin 9 of IC6. Instead, it goes to the I2S_ADC1 connection at the right edge of Fig.12 on p86.

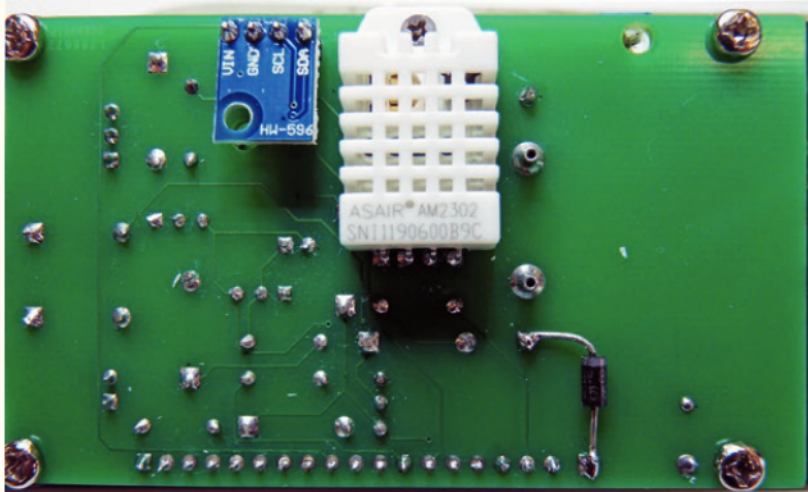Car Altimeter, May 2020: the design is missing one schottky diode (D8) which connects from the cathode of ZD1 (schottky anode) to the positive terminal of the battery (schottky cathode). This is needed to charge the battery. It can be added to the underside of the PCB, as shown in the accompanying photograph.



6GHz Touchscreen Frequency Counter, October-December 2017: in the circuit diagram on pages 30 & 31 of the October 2017 issue, a $1\mu\text{F}$ bypass capacitor is missing between the anode and cathode of REF1. Also, in the overlay diagram (Fig.3) on p86 of the November 2017 issue, the board shown is RevA; the final (RevB) board adds a $100\mu\text{F}$ capacitor just to the left of REG2, with its positive lead towards the regulator.

The April 2021 issue is due on sale in newsagents by Thursday, March 25th. Expect postal delivery of subscription copies in Australia between March 23rd and April 9th.

Advertising Index

Altronics.....	17, CATALOG
Ampec Technologies	20
Analog Devices	OBC
Dave Thompson	111
Digi-Key Electronics	3
Emona Instruments	IBC
Jaycar	IFC,53-60
Keith Rippon Kit Assembly	111
LD Electronics	111
LEDsales	111
Microchip Technology	5
Mouser Electronics	7
Ocean Controls	19
SC Colour Maximite 2	71
SILICON CHIP Binders.....	111
SILICON CHIP Shop.....	98-99
SILICON CHIP PDFs on USB.....	91
Switchmode Power Supplies	29
The Loudspeaker Kit.com	9
Tronixlabs	111
Vintage Radio Repairs	111
Wagner Electronics	64

Preview only.

“Rigol Offer Australia’s Best Value Test Instruments”



Oscilloscopes



RIGOL DS-1000E Series

- ▶ 50MHz & 100MHz, 2 Ch
- ▶ 1GS/s Real Time Sampling
- ▶ USB Device, USB Host & PictBridge

FROM \$**429** ex GST



NEW
200MHz
\$649
ex GST

RIGOL DS-1000Z/E - FREE OPTIONS

- ▶ 50MHz to 100MHz, 4 Ch; 200MHz, 2CH
- ▶ 1GS/s Real Time Sampling
- ▶ 24Mpts Standard Memory Depth

FROM \$**649** ex GST



New
Product!

RIGOL MSO-5000 Series

- ▶ 70MHz to 350MHz, 2 Ch & 4Ch
- ▶ 8GS/s Real Time Sampling
- ▶ Up to 200Mpts Memory Depth

FROM \$**1,569** ex GST

Function/Arbitrary Function Generators



New
Product!

RIGOL DG-800 Series

- ▶ 10MHz to 35MHz
- ▶ 1 & 2 Output Channels
- ▶ 16Bit, 125MS/s, 2M Memory Depth

FROM \$**479** ex GST



RIGOL DG-1000Z Series

- ▶ 25MHz, 30MHz & 60MHz
- ▶ 2 Output Channels
- ▶ 160 In-Built Waveforms

FROM \$**725** ex GST



RIGOL DM-3058E

- ▶ 5 1/2 Digit
- ▶ 9 Functions
- ▶ USB & RS232

ONLY \$**789** ex GST

Power Supplies



RIGOL DP-832

- ▶ Triple Output 30V/3A & 5V/3A
- ▶ Large 3.5 inch TFT Display
- ▶ USB Device, USB Host, LAN & RS232

ONLY \$**749** ex GST

Spectrum Analysers



RIGOL DSA Series

- ▶ 500MHz to 7.5GHz
- ▶ RBW settable down to 10 Hz
- ▶ Optional Tracking Generator

FROM \$**1,321** ex GST

Real-Time Analysers



New
Product!

RIGOL RSA Series

- ▶ 1.5GHz to 6.5GHz
- ▶ Modes: Real Time, Swept, VSA & EMI
- ▶ Optional Tracking Generator

FROM \$**3,210** ex GST

Buy on-line at www.emona.com.au/rigol

Sydney

Tel 02 9519 3933
Fax 02 9550 1378

Melbourne

Tel 03 9889 0427
Fax 03 9889 0715

Brisbane

Tel 07 3392 7170
Fax 07 3848 9046

Adelaide

Tel 08 8363 5733
Fax 08 83635799

Perth

Tel 08 9361 4200
Fax 08 9361 4300

EMONA

email testinst@emona.com.au

web www.emona.com.au

An aerial photograph of a two-lane asphalt road with white dashed lines, stretching horizontally across the center of the frame. The road is flanked on both sides by a dense forest of green trees, with some sunlight filtering through the canopy, creating bright spots on the foliage.

WHAT IF

WHAT IF WE MADE CARS MORE LIKE TREES? A LOT OF TREES.

Electric vehicle batteries, equipped with Analog Devices' battery management technology, can prevent 60 million tons of CO₂ emissions every year. Which is the same as 71 million acres of trees, but maybe not quite as pretty.

Analog Devices. Where what if becomes what is.
See What If: analog.com/WhatIf

