


wireless world

MAY 1975 30p


50MHz oscilloscope


SB Review
EXCLUSIVE DOLBY KIT (Part 1)

10p

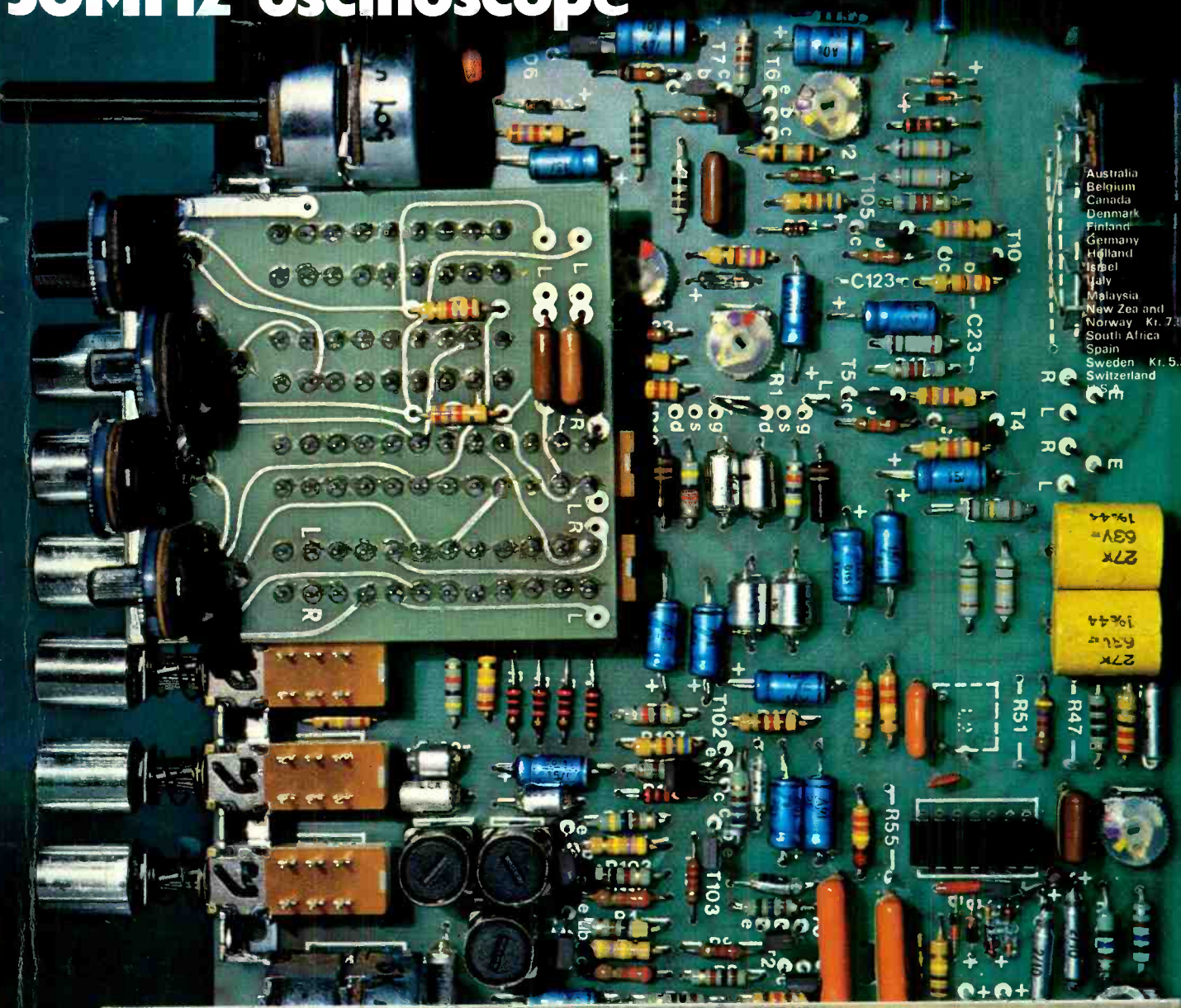

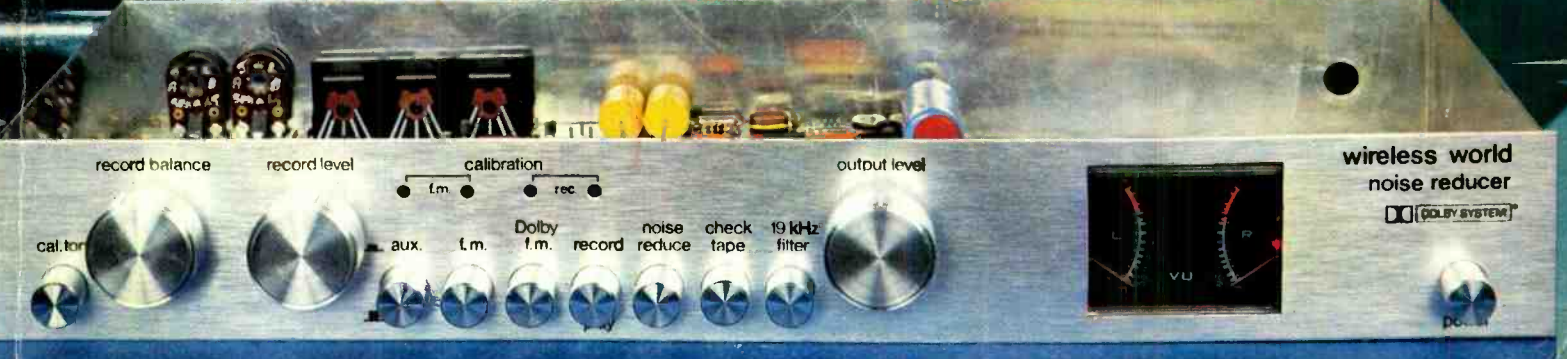- Australia 80 Cents
- Belgium Fr. 52.00
- Canada \$1.10
- Denmark Kr. 9.00
- Finland Fmk 4.50
- Germany Dm 4.00
- Holland Dfl 3.75
- Israel 1£3.95
- Italy L. 700
- Malaysia M \$2.60
- New Zealand 78 Cents
- Norway Kr. 7.30 inkl Moms
- South Africa 77 Cents
- Spain Ptas 65.00
- Sweden Kr. 5.35 inkl Moms
- Switzerland Fr. 4.70
- USA \$1.10



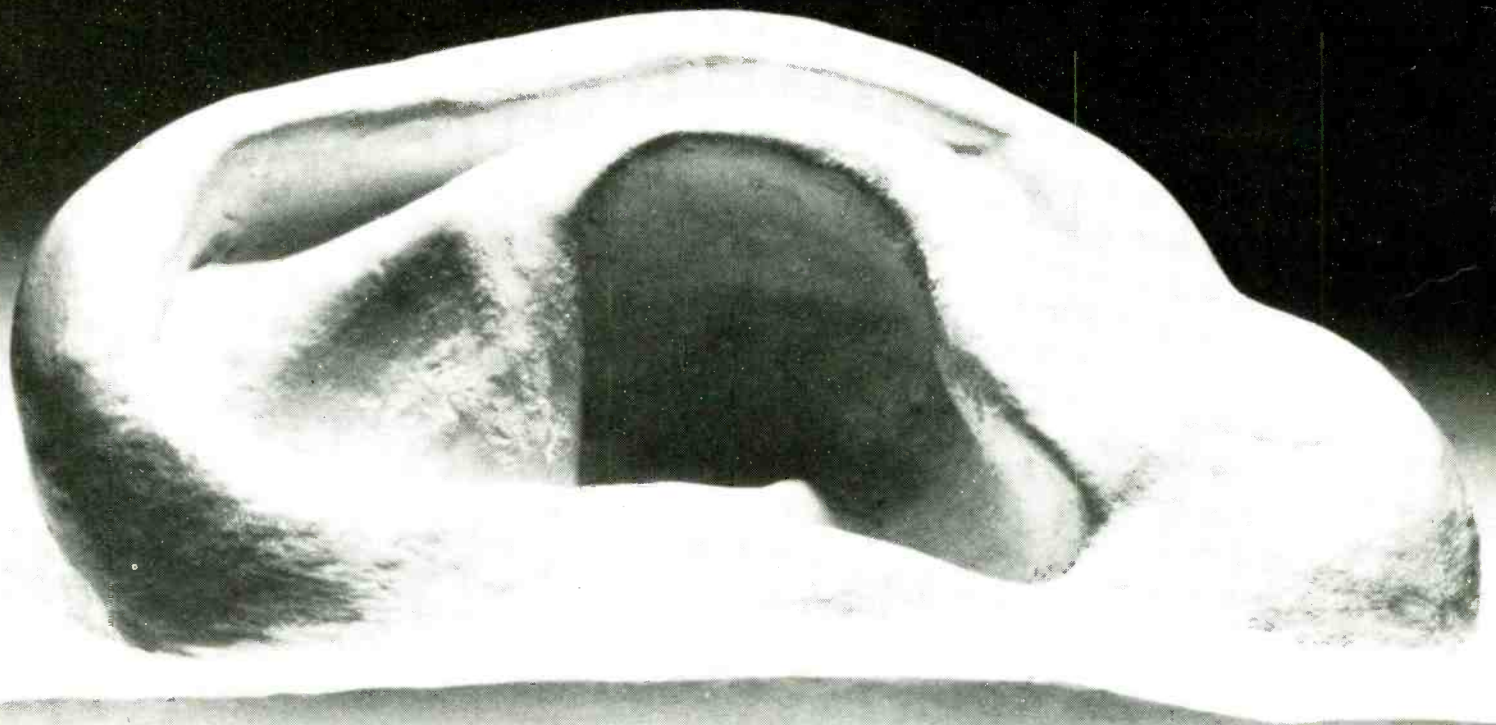

Research Instrument

The human ear must be one of the oldest research instruments in the business. Yet many of the ultra-modern Marconi instruments used in today's most advanced research projects owe a debt to it.

At **mi**, you see, we don't believe in Ivory Towers. So we ponder the constant feedback of information from you through our sales engineers far and wide, and keep our ear to the grounds of component technology and measurement trends throughout the world.

Requests, suggestions, remarks, ideas... they all lead us to what you are going to need - or they reveal possible new approaches to the solutions of those needs.

We have our ears in all the national and international committees of measurement standards and recommendations too.

We even lend sympathetic ears to you who need special equipment - and lend ears to PTT authorities, broadcast authorities and defence departments who often set the trends for new standards.

All **mi** instrument specifications are the result of this constant research - specialized P.C.M. test gear, low cost versatile signal generator TF 2015, new generation HF spectrum analyser, automatic TV transmitter monitor....

Be one of the heard - talk to us!
We're listening.

mi: THE GOOD LISTENERS

MARCONI INSTRUMENTS LIMITED

Longacres • St. Albans • Hertfordshire AL4 0JN • England • Telephone: St. Albans 59292 • Telex: 23350



A GEC - Marconi Electronics company.

LOW COST VOLTMETERS



LEVELL

PORTABLE INSTRUMENTS

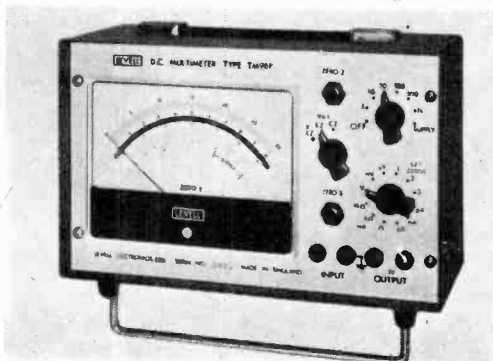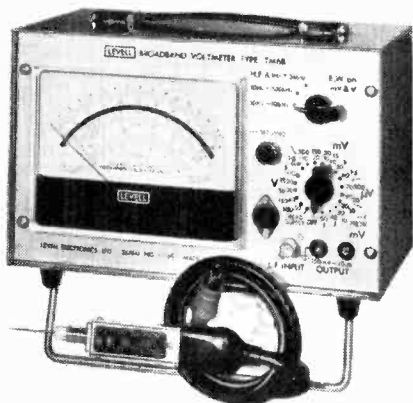

These highly accurate instruments incorporate many useful features, including long battery life. All A type models have $3\frac{1}{2}$ " scale meters, and case sizes 5" x 7" x 5". B types have 5" mirror scale meters and case sizes 7" x 10" x 6".

A.C. MICROVOLTMETERS

VOLTAGE & dB RANGES: 15 μ V, 50 μ V, 150 μ V... 500V f.s.d. Acc. $\pm 1\% \pm 1\%$ f.s.d. $\pm 1\mu$ V at 1 kHz. -100, -90... +50dB, scale -20dB/+6dB rel. to 1mW/600 Ω .
RESPONSE: ± 3 dB from 1 Hz to 3MHz, ± 0.3 dB from 4Hz to 1MHz above 500 μ V. Type TM3B can be set to a restricted B.W. of 10Hz to 10 kHz or 100 kHz.
INPUT IMPEDANCE: Above 50mV: $> 4.3M\Omega < 20$ pf. On 50 μ V to 50mV: $> 5M\Omega < 50$ pf.
AMPLIFIER OUTPUT: 150mV at f.s.d.

type **£65** type **£80**
 TM3A TM3B

BROADBAND VOLTMETERS

H.F. VOLTAGE & dB RANGES: 1mV, 3mV, 10mV... 3V f.s.d. Acc. $\pm 4\% \pm 1\%$ of f.s.d. at 30MHz. -50dB, -40dB, -30dB to +20dB. Scale -10dB/+3dB rel. to 1mW/50 Ω . ± 0.7 dB from 1MHz to 50MHz. ± 3 dB from 300kHz to 400MHz.

L.F. RANGES: As TM3 except for the omission of 15 μ V and 150 μ V.
AMPLIFIER OUTPUT: Square wave at 20Hz on H.F. with amplitude proportional to square of input. As TM3 on L.F.

type **£110** type **£125**
 TM6A TM6B

D.C. MICROVOLTMETERS

VOLTAGE RANGES: 30 μ V, 100 μ V, 300 μ V... 300V. Acc. $\pm 1\%$, $\pm 2\%$ f.s.d., $\pm 1\mu$ V. CZ scale.
CURRENT RANGES: 30pA, 100pA, 300pA, 300mA. Acc. $\pm 2\%$, $\pm 2\%$ f.s.d., ± 2 pA. CZ scale.
LOGARITHMIC RANGE: $\pm 5\mu$ V at $\pm 10\%$ f.s.d., ± 5 mV at $\pm 50\%$ f.s.d., ± 500 mV at f.s.d.
RECORDER OUTPUT: ± 1 V at f.s.d. into $> 1k\Omega$

type **£67**
 TM10

D.C. MULTIMETERS

VOLTAGE RANGES: 3 μ V, 10 μ V, 30 μ V... 1kV. Acc. $\pm 1\% \pm 1\%$ f.s.d. $\pm 0.1\mu$ V. LZ & CZ scales.
CURRENT RANGES: 3pA, 10pA, 30pA... 1mA (1A for TM9BP). Acc. $\pm 2\% \pm 1\%$ f.s.d. ± 0.3 pA. LZ & CZ scales.
RESISTANCE RANGES: 3 Ω , 10 Ω , 30 Ω ... 1kM Ω linear. Acc. $\pm 1\%$, $\pm 1\%$ f.s.d. up to 100M Ω .
RECORDER OUTPUT: 1V at f.s.d. into $> 1k\Omega$ on LZ ranges.


type **£95** type **£114**
 TM9A TM9BP

LEVELL ELECTRONICS LTD.

Moxon Street, High Barnet, Herts. EN5 5SD
 Tel: 01-449 5028/440 8686

Prices include batteries and U.K. delivery. V.A.T. extra. Optional extras are leather cases and mains power units. Send for data covering our range of portable instruments.

WW-039 FOR FURTHER DETAILS

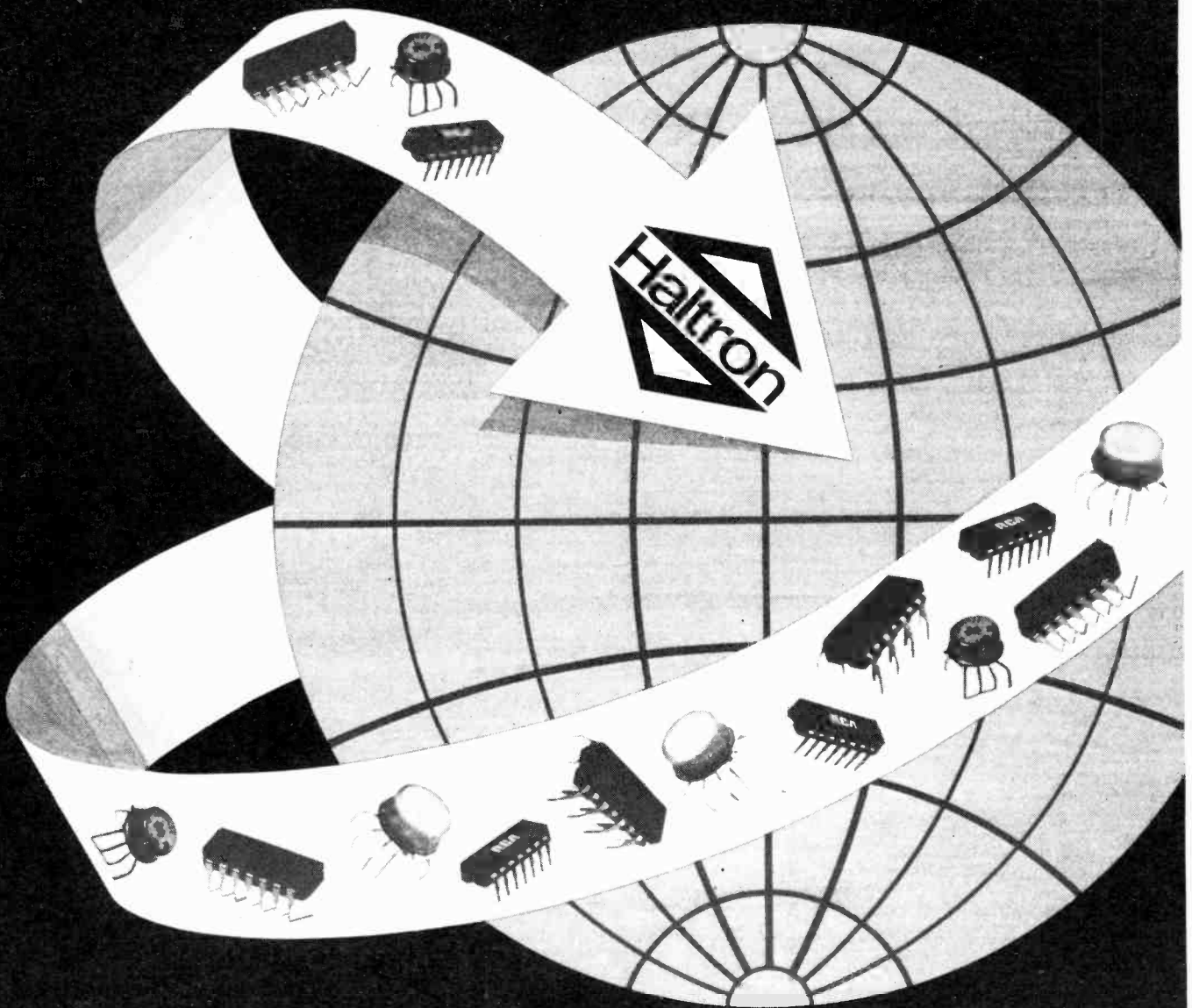

**The world over-
You get the
best service
from Haltron**

For high quality electronic valves, semiconductors and integrated circuits – and the speediest service – specify Haltron. It's the first choice of Governments and many other users throughout the world. Haltron product quality and reliability are clearly confirmed. The product range is very, very wide. And Haltron export expertise will surely meet your requirements. Wherever you are, get the best service. From Haltron.



Hall Electric Limited,
Electron House,
Cray Avenue, St. Mary Cray,
Orpington, Kent BR5 3QJ.
Telephone: Orpington 27099
Telex: 896141

WW—086 FOR FURTHER DETAILS

You could easily make our 12-speed chart recorder faster than you thought possible.

Send away for our 12-speed, 10" chart recorder kit—the IR-18M. And you'll receive a very clear, easy to understand instruction manual with it. Which explains every single step. To make light work of assembly and provide you with a high quality chart recorder a lot quicker than you thought.

And just look what you'll be getting. Multi-speed capability. With fast, pushbutton switch selection of speeds from 5 seconds per inch to 200 minutes per inch. To give you all the versatility you need.

You'll also get two input ranges, giving accurate voltage measurements of 1 millivolt and 10 millivolts full scale. Excellent repeatability. And a full scale pen response time of one second many much higher than many other priced recorders. Take a look at the 1G-18 Solid State kit too. Outputs available using repeatable

—comparing favourably with priced recorders. Take a look at Sine-Square Wave Generator from 1Hz to 100KHz are available using repeatable switch selection.

And its sine and square wave outputs are available simultaneously. With less than 0.1% sine wave distortion. And less than 50 ns square wave rise time.



And, for quick accurate testing of diodes, FETs, transistors, SCRs and triacs, there's the IT-121 Tester kit.



You can see these and other Heathkit electronic kits at the London Heathkit Centre, 233 Tottenham Court Road. Or at our showroom in Bristol Road, Gloucester.

Otherwise just clip the coupon and we'll send you the complete Heathkit catalogue.

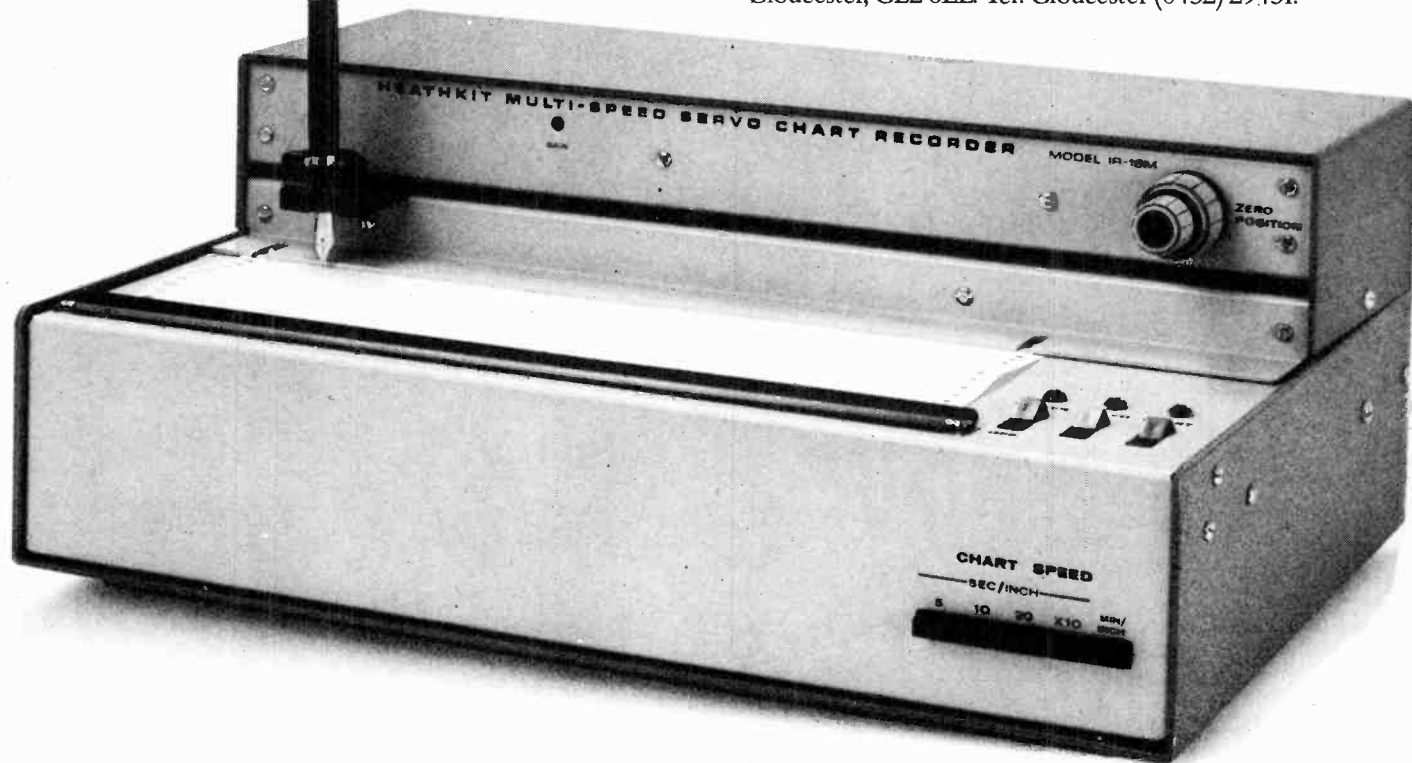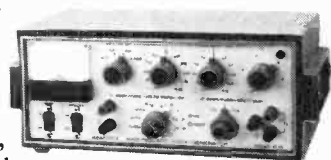Faster than you thought possible. Heath (Gloucester) Limited, Dept WW-55, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.



To: Heath (Gloucester) Limited, Dept WW-55, Gloucester, GL2 6EE.
Please send me my free Heathkit catalogue.

Name _____

Address _____

Postcode _____



SYSTEM 2000

VORTEXION

A new range of sound equipment from **Vortexion, System 2000** has been designed by our engineers to combine the aesthetics of design in the domestic equipment field with the near flexibility of a modular system. Like all our equipment **Vortexion System 2000** is built to last.

No matter what your sound problem, whether hotel or local pop group, ask our Design Consultants how it can be solved with **System 2000**.


CSI VORTEXION

Vortexion Ltd., 257-263 The Broadway, Wimbledon, SW19 1SF
Telephone: 01-542 2814 and 01-542 6242/3/4
Telegrams: "Vortexion London SW19"

WW-204 FOR FURTHER DETAILS

Stable companions

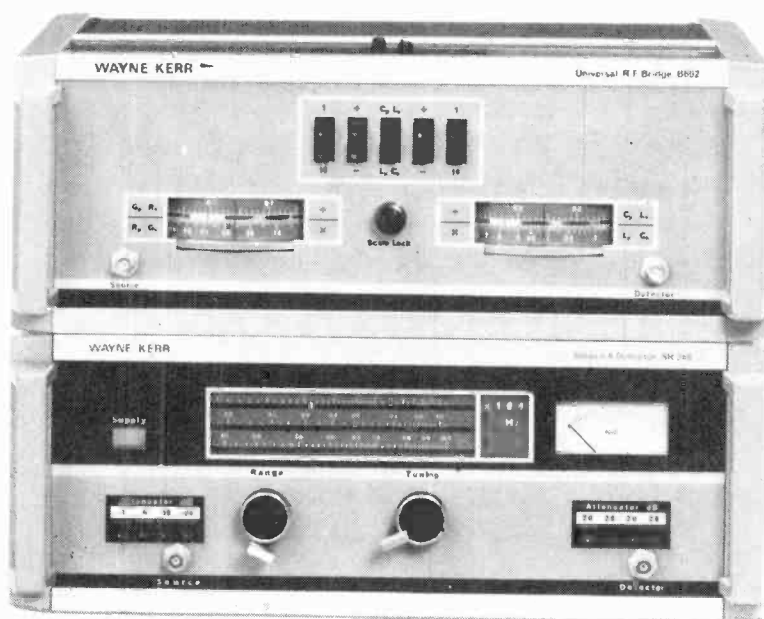Wide-range universal bridge **B602** 0.1-100MHz source/detector **SR268** from Wayne Kerr



SPECIFICATION

B602

Frequency range:	100kHz to 10MHz
Accuracy:	1% up to 3MHz, 1pF to 10nF 10 Ω to 100k Ω 1 μ H to 10mH
Overall impedance range:	1fF to 1mF 100 $\mu\Omega$ to 100M Ω (10n Ω to 10k Ω) 10pH to 10H

SR268

Frequency Range:	100kHz to 100MHz in 9 bands (SR268L 46.5kHz to 46.5MHz) 2-3% according to band used.
Frequency accuracy:	0.01%
Short Term Frequency Stability:	0.01%
Output level:	0.5-2.0V according to band used.
Output attenuator:	3, 6, 10, 20 dB additive steps, 75 Ω
Input sensitivity for 10% meter deflection:	1 to 30 μ V according to frequency setting
Input attenuator:	4 steps of 20 dB, 75 Ω
Detector bandwidth:	2-3% according to band used

For more information, either phone Bognor Regis (02433) 25811 or write to the address below:

WAYNE KERR

Durban Road, Bognor Regis, Sussex
Telex: 86120. Cables: Waynkerr, Bognor

A member of the Wilmot Breeden group

The B602 transformer ratio arm bridge measures impedance in all four quadrants of the complex plane over the frequency range 100kHz to 10MHz. Because of novel features incorporated in the design, values from virtually a short circuit to an open circuit can be measured. This bridge has established a standard of performance and flexibility which is unobtainable from any other radio frequency bridge.

A standard inductor is included in the bridge network in addition to standards of capacitance and resistance enabling a periodic calibration of the scales which are correct at any frequency between 100kHz and 10MHz.

There are only two balance controls. One is direct reading in resistance and conductance, the other in capacitance and inductance and there is no interaction between them.

The stability realised allows a discrimination of 0.1% to be obtained for all types of measurement with a general accuracy of 1% over most of the impedance and frequency range.

The bridge is shown together with the SR268 Source and Detector which can also be used with other bridges in the Wayne Kerr range over the frequency band 100kHz to 100MHz. Nine frequency ranges are provided by this instrument and a single tuning control adjusts both source and detector to the exact frequency required.

Meticulous screening between the two sections provides freedom from bridge measurement errors due to leakage of the source signal into the detector. Common mode rejection transformers are incorporated in the input and output networks to reduce interference from unwanted signals, and push button attenuators are included to assist the logarithmic detector circuit to indicate approach of the bridge balance point.

Strictly professional

Eddystone communication receivers in the range 10 kHz to 1000 MHz are built to exacting professional standards. Special versions are made in large numbers to satisfy the stringent demands of the Ministry of Defence, Ministry of Posts and Telecommunications and broadcasting authorities in the UK and overseas. The range of Eddystone ancillary units includes panoramic display units, SSB adaptors and drive units, FSK adaptors and electronic keying units of advanced design.

Photo by Aerofilms Ltd.


Eddystone Radio Limited

Member of Marconi Communication Systems Limited

Alvechurch Road, Birmingham B31 3PP, England.

Telephone: 021-475 2231 Telex: 337081


A GEC - Marconi Electronics Company

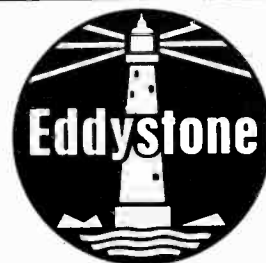

WW-191 FOR FURTHER DETAILS

BARR & STROUD ELECTRONIC FILTERS

The 3 aspects of our service

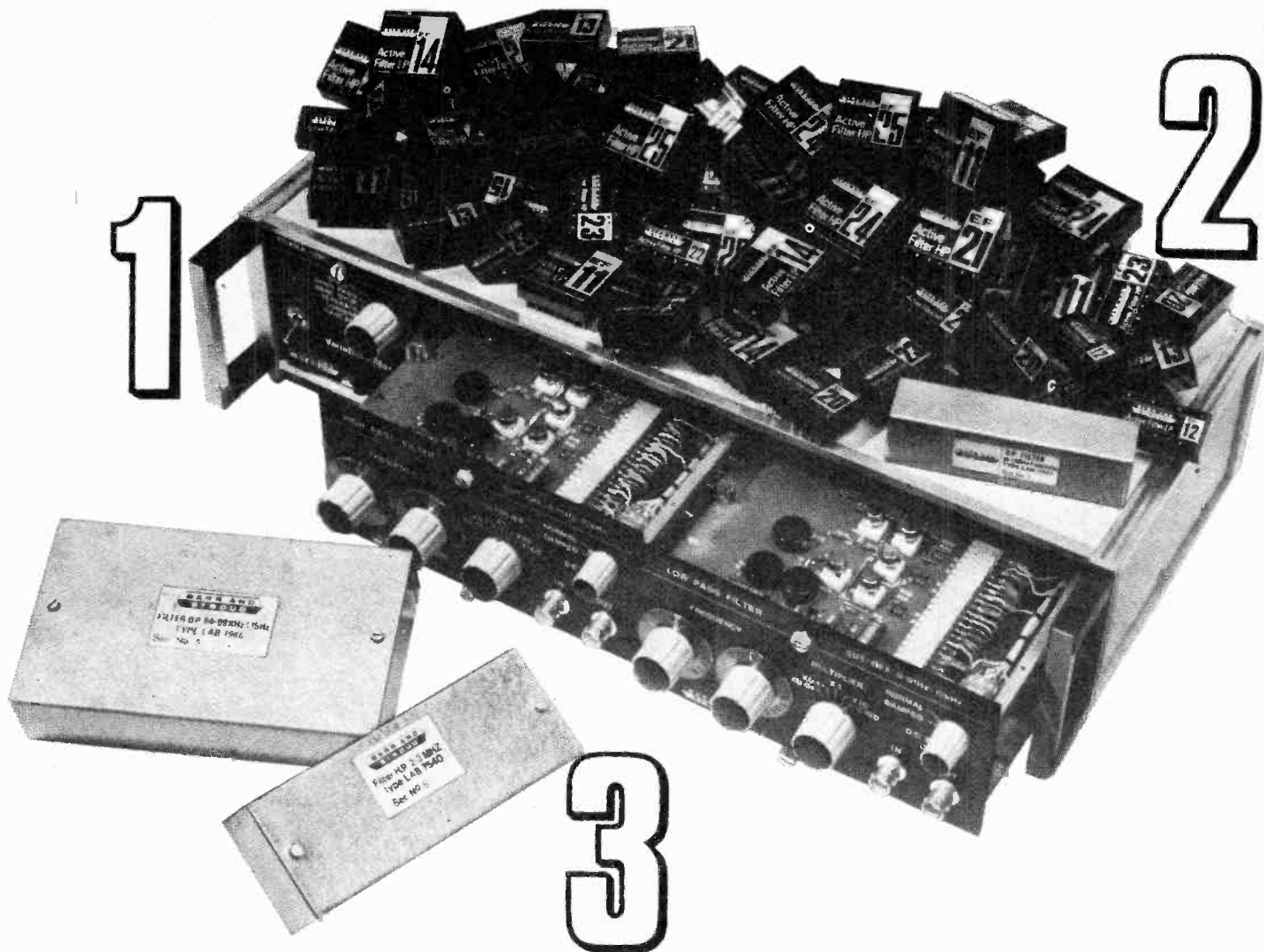

1. System EF3

A flexible system of filter instrumentation using a modular approach to give plug-in interchangeability. The mainframe carries a power unit and accepts up to two filter units of either Low Pass or High Pass function. Integral switching allows individual or cascade operation and can give Band Pass, Band Stop, Band Separate or Band Combine modes.

2. Active Filter Modules

These are compact, solid state, encapsulated units providing basic filter functions to be customer set for cut-off frequency and characteristic. The present range contains Low Pass and High Pass types with cut-off frequency coverage from 1.0Hz to 30kHz in overlapping ranges, with attenuation rates up to 24dB/octave/module. Universal modules specifically for Band Pass and Band Stop operation are part of the range.

3. Custom Build Service

If our standard filter range does not meet your specification we welcome the opportunity to study your requirement. Broadly our capability stretches from d.c. to 25MHz with experience in passive and active designs. We can work to normal commercial standards or strict defence requirements and construction can be as dictated by the environmental conditions of your application.

BARR & STROUD LIMITED
 London Office: 1 Pall Mall East, London SW1Y 5AU
 Telephone: 01-930 1541 Telex: 261877




Glasgow and London

WW-208 FOR FURTHER DETAILS

COUTANT 'L' SERIES


... more variable power than ever before with 13 types available from stock

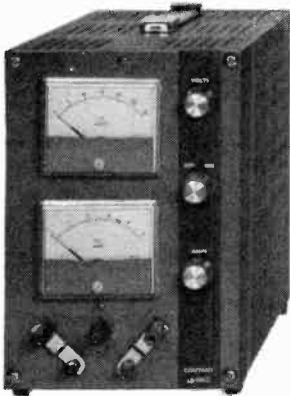With the addition of the new LQT Twin Power Supply, offering double the voltage range, the Coutant 'L' Series is ideally suited for the wide range of laboratory and general applications where continuously variable high performance power is essential.




LB SERIES

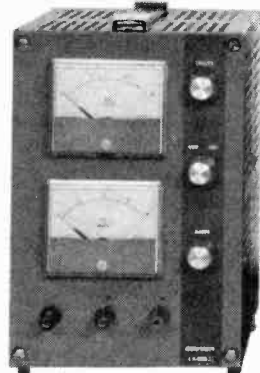LB 200 : 0 to 50V " 0 to 2A
LB 500 : 0 to 30V " 0 to 5A
LB 1,000 : 0 to 15V " 0 to 10A



LA SERIES

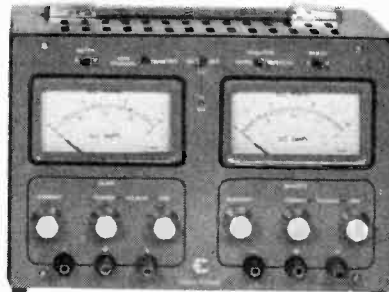LA 100 : 0 to 50V " 0 to 1A
LA 200 : 0 to 30V " 0 to 2A
LA 400 : 0 to 15V " 0 to 4A




LQT SERIES

LQT 100 : 0 to $\pm 30V$ " 0 to 1A x 2
or 0 to 30V " 0 to 2A
or 0 to 60V " 0 to 1A
LQT 200 : 0 to $\pm 15V$ " 0 to 2A x 2
or 0 to 15V " 0 to 4A
or 0 to 30V " 2A



LQ SERIES

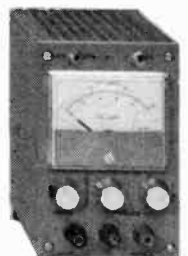LQ 50 : 0 to 50V " 0 to 0.5A
LQ 100 : 0 to 30V " 0 to 1A
LQ 200 : 0 to 15V " 0 to 2A



LM SERIES

LM 50 : 0 to 30V " 0 to 0.5A
LM 100 : 0 to 15V " 0 to 1A

OVERSEAS REPRESENTATION

Austria	Dipl. Ing. Peter Marchetti Elektronische Gerate Wien 6 Sandwirtgasse 14 A 1061 Postfach 455 Austria	France	Commerciale Chauvin Arnoux 188 Rue Championnet Paris 18 France	Norway	Skandinavisk Elektronik A/S Ostre Aker vei 99 P.O. Bix 99—veitvedt Oslo 5 Norway
Belgium	Ets. L. DeGreef S.P.R.L. Electronic Chaussee d'Alseberg 367 1180 Bruxelles Belgium	Germany	Zentro-elektrik 7530 Pforzheim Postfach 2070 Sandweg 20 West Germany	South Africa	Dowson & Dobson 29 Webber Street Selby P.O. Box 7764 Posbus Johannesburg South Africa
Canada	Duncan Instruments 65 Millwick Drive Weston Ontario Canada M9L 1Y4	Holland	Air Parts International N.V. Ryswyk (A.H.) 149 Haagweg P.O. Box 4094 Holland	Sweden	Gunnar Petterson Box 117 12321 Farsta Sweden
Finland	Nores & Co OY Fabianinkatu 32 Helsinki 10 Finland	Israel	Rapac Electronics Ltd. P.O. Box 18053 Tel Aviv Israel	Switzerland	Automation & Elektronik Industriestrasse CH-B604 Voketswil Schweiz Switzerland
		Italy	Celdis Italiana S.P.A. Via Luigi Barzini 20 Milano 20125 Italy		

Coutant Electronics Limited

Trafford Road, Reading RG1 8JR Tel 0734 55391 Telex 84519 **Coutant take the initiative in new technology**



ELECTROTECH 'STANDBY'

provides power when no power exists!

Now you can be totally independent of a mains power supply. The Electrotech 'Standby' provides up to 500 W of power instantly when connected to a 24V source. If linked to two ordinary 12V car batteries the unit will deliver 240V 50Hz power for at least 2½ hours.


- Open circuit on low battery condition
- Electronically protected against short circuits
- Will not wander off frequency if battery supply deviates
- Protected against reverse battery connection

Electrotech 'Standby' supplied by:

LEKTROKIT LIMITED

Trafford Road, Reading, Berkshire.

Tel: Reading (0734) 55394

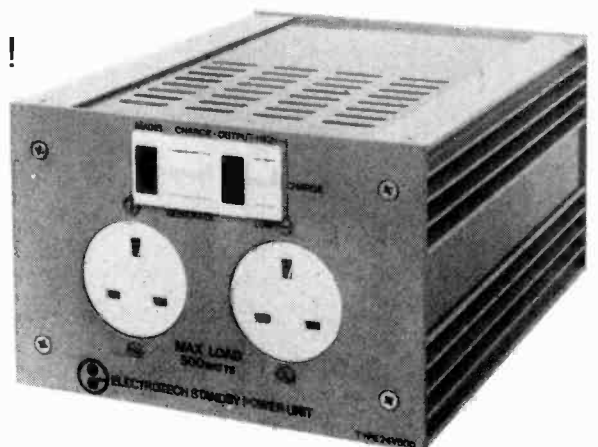

WW-233 FOR FURTHER DETAILS

One colour camera that gives you more than your £6500 worth.

The ITC CTC-3X is a lot of camera for the money. £6500 buys you a high performance colour television camera, that can be used in studio, telecine, mobile or remote colourcasting.

It comes complete with f1.8 10:1 zoom lens, servo and cable controlled.

A view-finder monitor which can be easily removed or tilted both upward and downward.

A camera control unit which gives you remote controls including colour balance, iris, R.B. channel positions and gain, and on-off power and beam.

A separate mains lead that allows camera to be operated without CCU.

Plus features such as turret colour temperature correction filters.

A built-in colour bar generator.

A set of matched vidicon tubes. A waveform colour sampler for easy colour balance adjustment.

That's the ITC CTC-3X. A lot of camera for £6500. If you want it fitted with Plumbicon® Tubes with extended red, it will cost you £8125.

Also available is the SC 701P Genlock colour sync generator at £1265.

Plus the MEA 7100P six channel special effects generator at £2415.

At Dixons Technical, of course.

Prices subject to VAT.

**To: Dixons Technical,
3 Soho Square, London, W.1. Tel: 01-437 8811.**

Please send me full details of the ITC CTC-3X colour camera and ancillary equipment.

NAME _____

ADDRESS _____

**Dixons
Technical Ltd**


OF SOHO SQUARE

WW/39a/5

Also available from our agents. Southern Counties: Action Video. In the north: Holiday Brothers Ltd.

Registered Trade Mark of Mullard Ltd

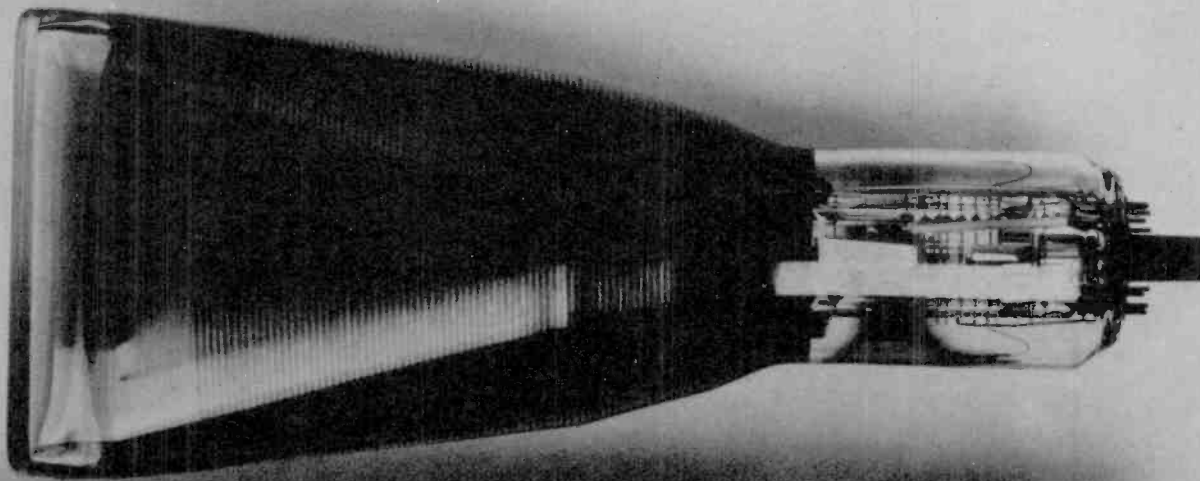There's only one thing the new Brimar D18-130 tube is short on: length.



More space on the screen with less for the tube – that's what the new Brimar **D18-130** offers you for your next portable display instrument design.

With a useful display area of 12.3 cm. x 10 cm. its overall length is only 310 mm. And that's the shortest length for its screen size of any electrostatic focus industrial tube available.

The tube has a high brightness and good focus performance (under typical operating

conditions a line width of 0.25 mm. can be expected.)

The new **D18-130** can be supplied with internal graticule and various phosphors to special order. The standard phosphor is GH, which gives a medium-short persistence green trace. A magnetic shield and twist coil are available.


We'll gladly send you a descriptive leaflet on request.



Thorn Radio Valves and Tubes Limited
Mollison Avenue, Brimsdown, Enfield, Middlesex, EN3 7NS. Telephone: 01-804 1201.



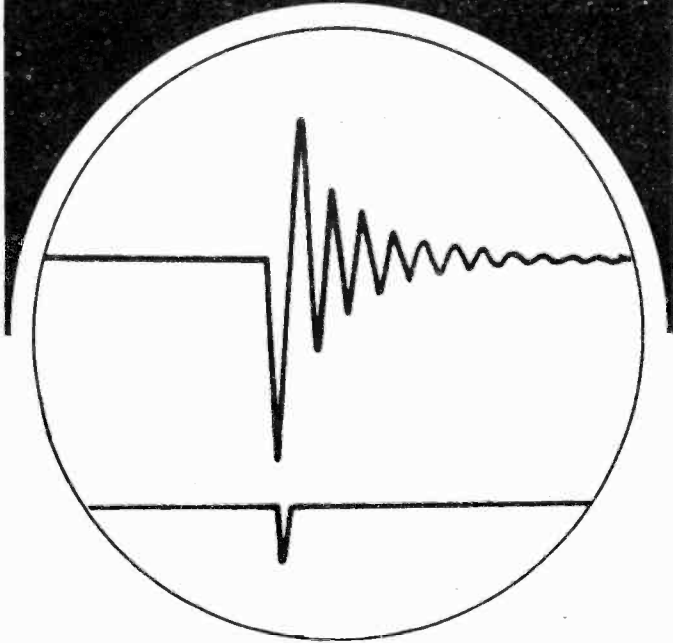SEND FOR THE FACTS ON FIBRE OPTIC RECORDING!



Medelec Limited, with a firmly established reputation earned in the exacting field of medical instrumentation, have developed a range of equipment combining the facilities of conventional oscilloscopes, strip chart and X-Y recorders, to provide unique capability.

Fibre Optic Recording increases the clarity and efficiency of data recording, gives low cost records and extends the field of application to new areas of industrial research and development.

To learn more about Fibre Optic Recording and Medelec equipment send today for a new publication "Medelec Fibre Optic Recording". This gives full information on development, comparisons, economics, case histories and general applications.

Medelec Limited, Woking, Surrey.
Tel: Woking (048 62) 70331 Telegrams: Medelec Woking


medelec



Leaders in
Fibre Optic Recording

WW-202 FOR FURTHER DETAILS

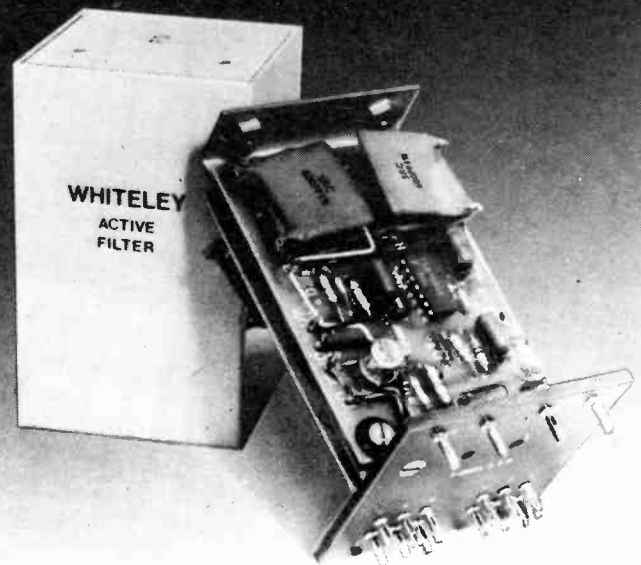New active filter takes over from passive networks



These active filters are designed to take over the functions of passive filter networks in audio telecommunications systems. They offer several advantages, in space-saving, economy and reliability.

As a size comparison, one active filter will take up the same space as two Post Office Type 3000 relays. By using the same fixing and terminal holes as the relays, it offers an extra convenience when baseboards are being prepared. By replacing inductive components with solid state devices, filter characteristics have been obtained at less cost, without insertion loss, and with increased flexibility and economy. These new active filters have B.P.O. approval, and have wide applications, in the audio area and in signalling and control systems.

Whiteley

versatility...

ELECTRONIC & ELECTRICAL DESIGN

PRODUCTION CAPABILITY

CABINET MAKING

SHEET METAL FORMING/FINISHING

PLASTICS MOULDING

ENCAPSULATION


WHITELEY ELECTRICAL RADIO CO. LTD.
Mansfield, Notts, England. Tel. Mansfield 24762
London Office: 109 Kingsway, W.C.2. Tel. 01-405 3074

WW-221 FOR FURTHER DETAILS

ELEKTOR

Elektor 3 comes
out on 30 April

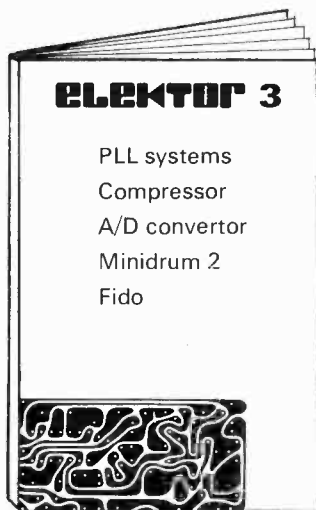Elektor for lab and leisure
—new ideas in electronic
projects using modern
components. Out every
two months till August,
then each month.



Use the Elektor
printed circuit
board service
for immediate
delivery of
high quality
epoxy glass
boards for all
major projects

Also in Elektor 3


Touch control audio preamp.
LED level indicator.
Time lapse cinematography.
High quality disc preamp.

Write to us enclosing 35p P.O. or
cheque for Elektor 3. If you would like
a subscription for the next six issues
(£2.70 to U.K. addresses) send no
money, write or phone for subscription
card

Elektor Publishers Ltd Telex 965504
6 Stour Street, Canterbury CT1 2XZ.
Tel Canterbury (0227) 54439

3

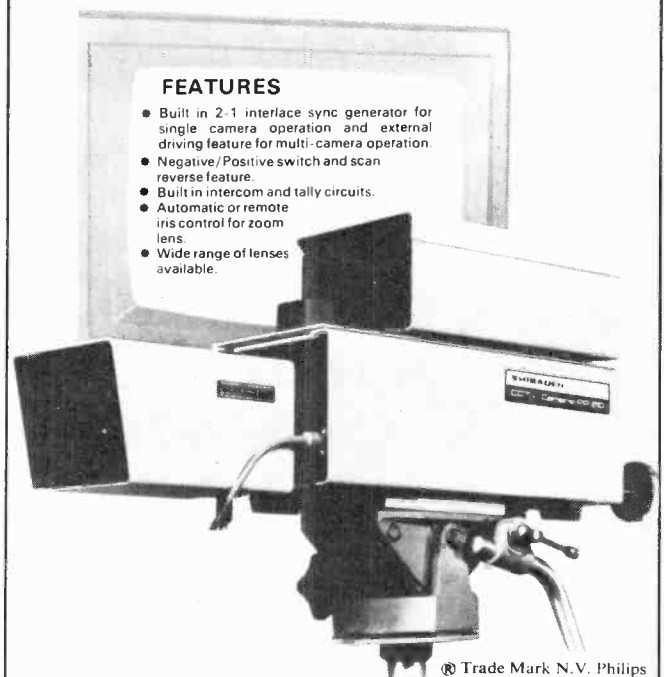The FP 210K, Shibadens popular 1" Plumbicon[®] Camera



FEATURES

- Built in 2-1 interlace sync generator for single camera operation and external driving feature for multi-camera operation.
- Negative/Positive switch and scan reverse feature.
- Built in intercom and tally circuits.
- Automatic or remote iris control for zoom lens.
- Wide range of lenses available.

This is the camera that will operate anywhere – in the studio or on outside location – and guarantee excellent results for a wide range of T.V. requirements in the fields of industry, education and commercial applications.

Equipped with a 5" electronic viewfinder for accurate picture composition and focus, the FP 210K is automated to ensure all major functions are easily handled.


If you prefer, a separate mesh type vidicon tube can be used, which, like the 1" Plumbicon[®] gives high definition picture reproduction.

To see the FP 210K in action, or for complete technical information, contact Shibaden's Technical Service Department at 01-203 4242/6 or write to:

 **Hitachi
Shibaden (UK) Limited**
BROADCAST & CCTV EQUIPMENT MANUFACTURERS
Lodge House · Lodge Road · Hendon · London
NW4 4DQ. Telephone: 01-203 4242/6

A NEW STANDARD FOR SOUND REPRODUCTION

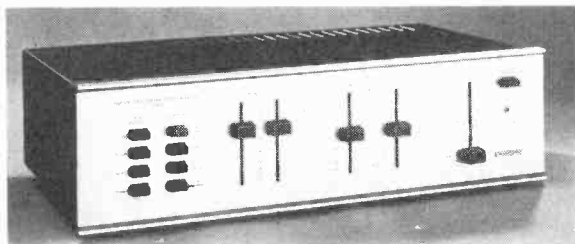HD250 High Definition Stereo Control Amplifier



Designed for disc and tuner input and two tape machines, with complete recording and reproducing facilities.

The HD250 amplifier establishes a new standard in amplifiers for sound reproduction in the home. Improvements have been made in respect of performance, engineering design and quality of construction. We believe that no other amplifier in the world can match the overall specification of the HD250. Look at extracts from the specification below.

Power output.

Rated: 50 watts average continuous power per channel, into any impedance from 4 to 8 ohms, both channels driven.
Maximum: 90 watts average power per channel into 5 ohms load.

Distortion.

Pre-amplifier: Virtually zero. (Cannot be identified or measured as it is below inherent circuit noise.)
Power amplifier, at rated output: Less than 0.02% (typically 0.01% at 1kHz).
at 25w output:

Overload margin.

Disc input 40 dB min.

Hum and noise output

Disc: —83dBV Measured flat with noise bandwidth of 23kHz (ref. 5mV.)
 —88dBV Measured with 'A' weighted characteristic (ref. 5mV.)
Line: —85dBV Measured flat (ref. 100mV.)
 —88dBV 'A' weighted (ref. 100mV.)

Size: 17 inches X 4 $\frac{3}{4}$ inches X 11 inches deep overall.


Weight: 21 lb.

Write or phone for leaflet which describes the design philosophy and conception of the HD250 together with a complete specification.

RADFORD AUDIO LIMITED, BRISTOL, BS3 2HZ Telephone: 0272 662301

WW—060 FOR FURTHER DETAILS

ELECTRONIC INDUSTRIAL THERMOMETER

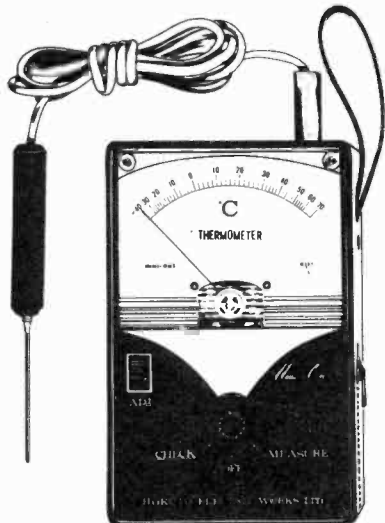

THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied in zippered vinyl case with transparent front and carrying loop, Probe, and internal 1 $\frac{1}{2}$ volt standard size battery.

Model "Mini-On 1" measures from - 40°C to + 70°C, price £17.50
Model "Mini-On Hi" measures from + 100°C to + 500°C, price £20.00 (V.A.T. EXTRA)

Write for further details to

HARRIS ELECTRONICS (LONDON),
138 GRAY'S INN ROAD, LONDON WC1X 8AX
 ('Phone 01-837 7937)

WW—214 FOR FURTHER DETAILS

PRODUCTION TESTING


DEVELOPMENT

SERVICING

EDUCATION

POWER UNITS

NOW AVAILABLE WITH 3 VARIABLE OUTPUTS

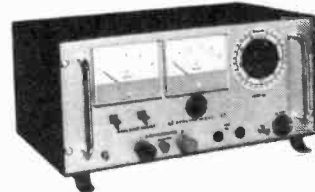

Type VRU/30/25—£175.00 + 8% VAT

Input 200–250V. 50Hz
 or 100–120V. 60Hz to order
 Output 1:0–30V. 25A. D.C.
 Output 2:0–70V. 10A. A.C.
 Output 3:0–250V. 4A. A.C.

Other units are also available with outputs of:
 0–60V 12A.
 0–120V 6A.
 0–240V 3A.

ALL CONTINUOUSLY VARIABLE

SEND FOR FURTHER DETAILS OF THESE VERSATILE UNITS TO

Valradio LIMITED, BROWELLS LANE,
 FELTHAM, TW13 7EN, MIDDLESEX.
 TELEPHONE 01-890 4242

WW—110 FOR FURTHER DETAILS

CONTINUOUS IMPROVEMENT



We are always at work on better production methods and the use of new materials.

These cartridge fixing screws are moulded in glass reinforced nylon which is only half the weight of aluminium. At 73p per set you can probably afford them better than the weight of those you are using.

We can send you as many sets as you want by return if you send us the money.


SME

The best pick-up arm in the world

Write to SME Limited
Steyning · Sussex · England
Telephone: Steyning (0903) 814321

LTD/S31A

WW—206 FOR FURTHER DETAILS

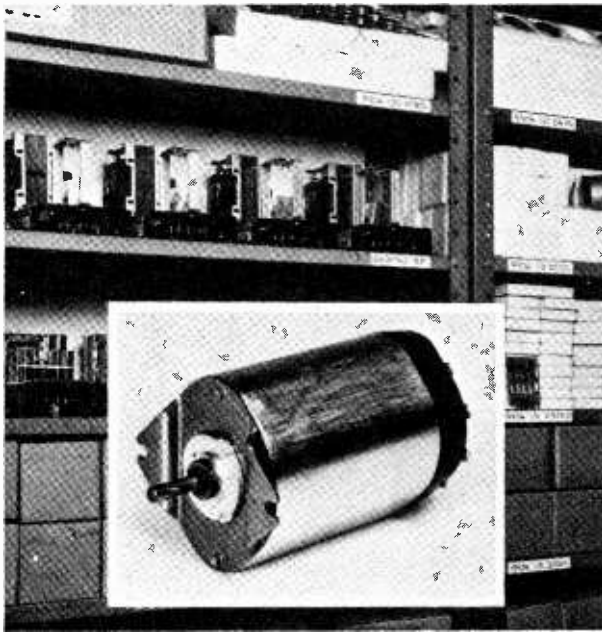

impex motors and drive systems off the shelf

A new division of McLennan Engineering Ltd has been formed to stock the full range of Impex Small Electric Motors and drive systems together with a wide range of standard industrial servo components and electronic control systems.

Motors include DC, Uni-directional and Reversible Synchronous and Stepping types offering a comprehensive spectrum of specifications suitable for a wide variety of applications.

In addition to offering an off-the-shelf supply facility for motors and components, McLennan have considerable experience in the solution of actuator and servo problems using synchronous, stepping and DC motor techniques.

So whether you require one motor or one hundred; or you simply have a problem about which you would like a second opinion, contact

McLennan Engineering Ltd.
Kings Road, Crowthorne, Berkshire.
Telephone: Crowthorne 5757/8

McLennan




Please send me further details of Impex motors and drive systems

Name _____
Position _____
Company _____
Address _____
Tel _____

FYLDE

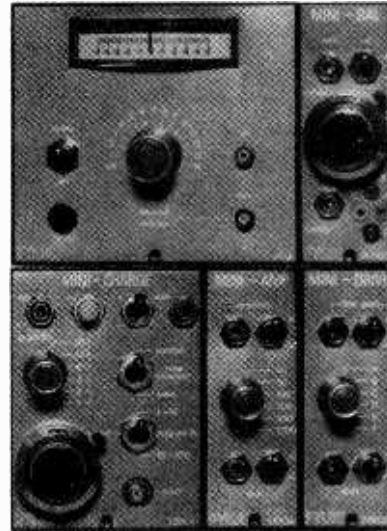TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE

Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston
PR1 2XQ
Telephone 0772 57560

WW—211 FOR FURTHER DETAILS



The
new
Rank**

WOW & FLUTTER Meter Type 1742

Fully transistorised
for high reliability

Versatile

Meets in every respect all current specifications for measurement of Wow, Flutter and Drift on Optical and Magnetic sound recording/reproduction equipment using film, tape or disc

High accuracy
with crystal controlled oscillator

Simple to use
accepts wide range of input signals with no manual tuning or adjustment

Two models available:
Type 1742 'A' BS-4847: 1972 DIN 45507
CCIR 409-2 Specifications
Type 1742 'B' BS 1988: 1953 Rank Kalee Specifications

For further information please address your enquiry to
Mrs B. Nodwell

Rank Film Equipment, PO Box 70
Great West Road, Brentford
Middlesex TW8 9HR

Tel: 01-568 9222 Telex 24406 Cables Rankaudio Brentford



**RANK FILM
EQUIPMENT**

Join the Digital Revolution

Teach yourself the latest techniques of digital electronics

Computers and calculators are only the beginning of the digital revolution in electronics. Telephones, wristwatches, TV, automobile instrumentation — these will be just some of the application areas in the next few years.

Are you prepared to cope with these developments?

This four volume course — each volume measuring 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ " and containing 48 pages — guides you step-by-step with hundreds of diagrams and questions through number systems, Boolean algebra, truth tables, de Morgan's theorem, flipflops, registers, counters and adders. All from first principles. The only initial ability assumed is simple arithmetic.


At the end of the course you will have broadened your horizons, career prospects and your fundamental understanding of the changing world around you.

Digital Computer Logic and Electronics

A Self-instructional Course

C. F. Goss MA (Cantab)
A. W. Lynch BA (Cantab)

Book 1	Basic computer logic
Book 2	Logical circuit elements
Book 3	Designing circuits to carry out logical functions
Book 4	Flipflops and registers

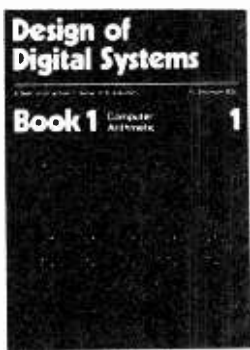

Design of Digital Systems
Book 1 Computer Arithmetic

£5.95 inc p&p

Design of Digital Systems contains over twice as much information in each volume as the simpler course. Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics.

Also available — a more advanced course in 6 volumes:

1. Computer Arithmetic
2. Boolean Logic
3. Arithmetic Circuits
4. Memories & Counters
5. Calculator Design
6. Computer Architecture

Offer: Order this together with Digital Computer Logic & Electronics for the bargain price of £9.25.

**Designer
Manager
Enthusiast
Scientist
Engineer
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

Guarantee — no risk to you

If you are not entirely satisfied with Digital Computer Logic and Electronics or Design of Digital Systems, you may return them to us and your money will be refunded in full, no questions asked.



£3.95

including packing and surface mail anywhere in the world.

Quantity discounts available on request.

Payment may be made in foreign currencies.

VAT zero rated.

To: Cambridge Learning Enterprises,
FREEPOST, St. Ives, Huntingdon, Cambs
PE17 4BR

*Please send me.....set(s) of Digital Computer Logic and Electronics at £3.95 each
*or.....set(s) of Design of Digital Systems at £5.95 each
*or.....combined set(s) at £9.25 each.

Name.....
Address.....
.....
.....

* delete as applicable.
No need to use a stamp — just print FREEPOST on the envelope.

NOW IT'S THE AMCRON M600

M600 POWER AMPLIFIER



1350 watts

DC-Coupled

The M600 amplifier is a new high-power amplifier capable of providing 1,350 watts RMS over a bandwidth of DC to 20 kHz. 70 volts RMS at the output terminals, very low noise, and distortion, AC/DC selector switch, plug-in front panel circuit board, built-in fan for cooling, and the ability to connect two M600s together to double the power, and output voltage, are just some of the features which place the Amcron M600 in the forefront when considering power amplifiers.

Driving shakers, and vibrators, motors, and difficult speaker systems, providing power for material or components testing, or used as a large distribution amplifier, the M600 is equally at home.

Brief specifications:

RMS power out	750 watts into 8 ohms 1,350 watts into 4 ohms
DC output	20 amps (supply fuse limited)
Power bandwidth	DC to 20 kHz + 1 db. - 0 db. 600 W into 8Ω
Phase response	+ 0 db. - 15 db DC—20 kHz
Slew rate	16 V/μsecond
Damping factor (8Ω)	greater than 400 DC—1 kHz
Hum & noise	120 db below 600 Watts
THD	less than 0.05% DC—20 kHz, 600 W into 8Ω
Dimensions	19" std. rack, 8 3/4" H, 16 1/2" deep. Wt. 92 lb.

Coupling two M600s together through a socket provided at the back of each amplifier produces a 140 Volt balanced output. This configuration is called an M2000, and produces 2 kilowatts into an 8 ohm load. A peak catching meter, and threshold lights provide convenient front panel output monitoring.



MACINNES LABORATORIES LTD

MACINNES HOUSE, CARLTON PARK INDUSTRIAL ESTATE,
SAXMUNDHAM, SUFFOLK IP17 2NL
TEL: (0728) 2262 2615

WW—194 FOR FURTHER DETAILS

LOW-COST INSTRUMENTS




NEW!

£82
+ £1.50 p.p. + VAT

745 COUNTER TIMER

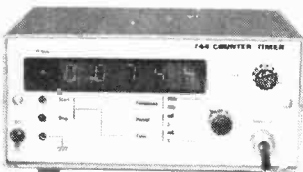Measures frequency, period, time and totalises
32 MHz frequency range (DC coupled)
5-digit .3" LED display
6 Gate times/Time units, 10μs to 1 S in decades
Sensitive, protected FET input



744 COUNTER TIMER

£74 + £1.50 p.p. + VAT

Measures frequency, period and time
30MHz frequency range (DC coupled)
5-digit, long-life incandescent display
Sensitive, protected FET input



643 FUNCTION GENERATOR

£86 + £1.50 p.p. + VAT


Accurate, digital frequency setting
.01Hz—1MHz
Wide range external control of frequency
Triangle, Squarewave and Low Distortion
Sinewave outputs
50Ω + simultaneous outputs
DC offset

Delivery is normally ex-stock—telephone for confirmation
Prices correct at time of going to press, subject to change without notice

OMB ELECTRONICS
Riverside, Eynsford, Kent DA4 0AE
Tel. Farningham (0322) 863567

WW—150 FOR FURTHER DETAILS

INSIST
ON
VERSATOWER

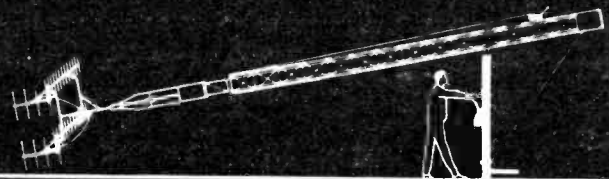

Acclaimed as the World's leading
telescopic tiltover tower in the
field of radio communication
Models from 25' to 120'



Look for the name
STRUMECH

Strumech Engineering Co Ltd
Coppice Side, Brownhills, Walsall, Staffs

WW—219 FOR FURTHER DETAILS



Midas


Studio Sound Mixing Console as supplied to the NORWEGIAN OPERA COMPANY.

Abridged Specification:

Mic I/P noise - 128 dbm; Max mic gain 80 db; Max mic I/P level + 2 dbm, line + 26 dbm; Max O/P level + 20 dbm into 600 ohm at 0.05% THD, typically 0.02% at + 4 dbm; Frequency response ± 0.5 db from 20 Hz to 20 KHz.

A full range of modules are available giving facilities from standard to comprehensive, and a modular chassis system allowing variable format from a 6 I/P - 2 O/P to a 30 I/P - 24 O/P desk. Penny & Giles faders are fitted as standard and PPM metering to BBC or DIN specification if required.

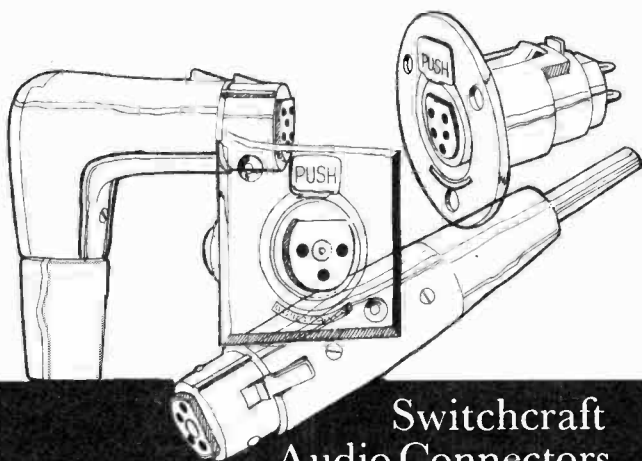MIDAS AMPLIFICATION 54-56 Stanhope Street, London NW1 3EX. 01-387 7679.



**Switchcraft
Audio Connectors**

Complete range of Switchcraft audio connectors for all studio and ancillary equipments.

Versatile— 3, 4, 5 or 6 pole; wide variety of matching plugs receptacles; readily interchangeable with other leading makes.

Streamlined — simple positive snap-in connection; cable clamping and latch lock.

Safe— self polarisation; captive insert screw provides rigid assembly and electrical continuity; firm and constant ground contact between mating connector shells through the use of an exclusive Ground Terminal and Contactors.

Low Cost-Ex-stock-Quantity Discounts

Write now for free descriptive literature.
Sole U.K. Agent for Switchcraft QG Connectors

F.W.O. BAUCH LIMITED

19 Theobald Street, Boreham Wood, Herts. WD6 4RZ Telephone: 01-953 0091

WW—052 FOR FURTHER DETAILS



- ★ BRITISH MADE
- ★ EX-STOCK DELIVERY



- ★ SIX DECADES
- ★ SCALE FACTOR & REF LEVEL (adjustable)
- ★ 1nA to 1mA OPERATING RANGE (std)
- ★ TRUE LOGARITHMIC FUNCTION
- ★ SCALE FACTOR SLOPE 1v per DECADE
- ★ REF. LEVEL 0 Volts OUT for 1 μ A IN
- ★ ACCURACY ± 0.25 db
- ★ BUILT IN AMPLIFIER
- ★ ANTI-LOG MODULE AVAILABLE

ancom Ltd devonshire street
cheltenham, glos.

WW—166 FOR FURTHER DETAILS



analogue instruments

TM2
A.C./D.C. MILLIVOLTMETER
1mV to 300V f.s.d.
10Hz to 5MHz frequency range
10MΩ input impedance
Mains or battery operated

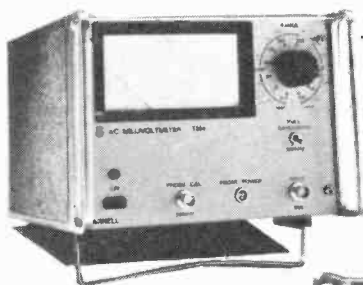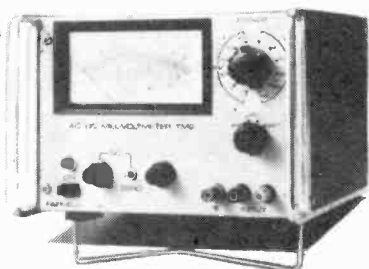


TM4
A.C. MILLIVOLTMETER
300 μV to 100V f.s.d.
20Hz to 18MHz
10MΩ input impedance via probe
H.F. spurious and noise filter

PM1
PHASEMETER
Meter indicates phase difference 0-180°. Lamps indicate leading or lagging phase 10Hz to 100kHz
PM1/B operates from mains or rechargeable batteries

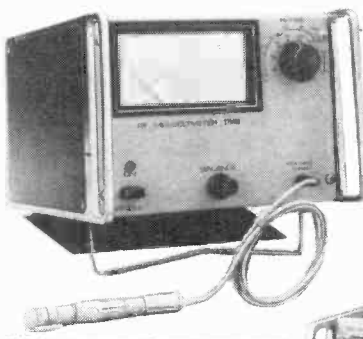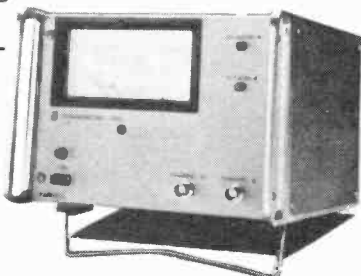

TM6
R.F. MILLIVOLTMETER
1mV to 300V r.m.s. f.s.d.
50kHz to 1,500MHz
Accuracy ± 3% of f.s.d.
Mains or battery operated

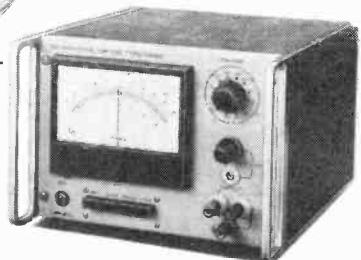TM39
D.C. MICROVOLTMETER
± 100 μV to ± 30V f.s.d.
Log. mode for null detection
Excellent zero stability
Mains or battery operation




Ask for details

from  Farnell

FARNELL INSTRUMENTS LIMITED · INSTRUMENTS DIVISION
SANDBECK WAY · WETHERBY · YORKSHIRE LS22 4DH · TEL. 0937-3541

WW—222 FOR FURTHER DETAILS

TPA SERIES - D integrated circuit power amplifier

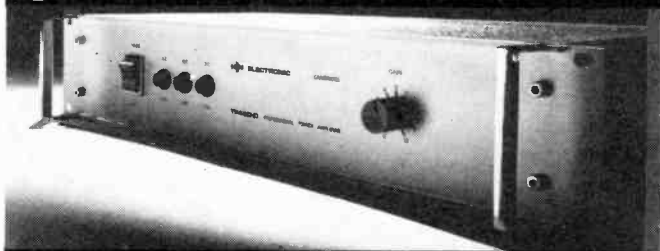

TPA 50 - D Specification

Power Output	100 watts rms into 4 ohms 65 watts rms into 15 ohms
Freq Response	±0.1dB 20Hz to 20KHz into 15 ohms. -1dB at 150KHz
Total harmonic distortion	Less than 0.04% at all levels up to 50 watts rms into 15 ohms
Input sensitivity	0dBm
Noise	-100dB
Rise time	2 μ seconds
Price	£70 plus V.A.T.

100V Line (C.T.) and balanced inputs available.

For full technical information contact:

H|H ELECTRONIC

CAMBRIDGE ROAD, MILTON, CAMBS
TELEPHONE CAMBRIDGE 65945/6/7

WW—217 FOR FURTHER DETAILS

Keep those
Contacts **CLEAN**

BY USING A

**DIACROM
SPATULA**



Manufactured in France
British Patents applied for

No other cleaner has all these advantages:—

1. Only 100% pure, natural diamond grains are utilised.
 2. Blades are treated with hard chrome to reinforce the setting of the diamond grains, to obviate loosening or breakaway during use. This process also prevents clogging of the diamonded surface by residues resulting from use.
 3. All diamonded blades are rectified to ensure an absolutely smooth surface by eliminating diamond grains which may rise above the surface. This eliminates all excessive scratching during use.
 4. All diamond grains are rigidly calibrated to ensure a perfectly uniform grain size of either 200, 300 or 400.
 5. The chrome gives a very weak co-efficient of friction and the rigidity of the nylon handle is calculated to permit proper utilisation and yet pliant enough to avoid undue pressures on highly delicate relays.
- Grain size 200, thickness 55/100 mm., both faces diamonded. For quick cleaning of industrial relays and switching equipment, etc.
 - Grain size 300, thickness 55/100mm., both faces diamonded. For smaller equipments, like telephone relays, computer relays, etc.
 - Grain size 400, thickness 25/100 mm., one face diamonded. For sensitive relays and tiny contacts. Two close contacts facing each other can be individually cleaned, because only one face of the spatula is abrasive.


Sole Distributors for the United Kingdom
SPECIAL PRODUCTS (DISTRIBUTORS) LTD
81 Piccadilly, London W1V 0HL. Phone: 01-629 9556
As supplied to the M.O.D., U.K.A.E.A., C.E.G.B. British Rail and other Public Authorities;
also major industrial and electronic users throughout the United Kingdom.

WW—011 FOR FURTHER DETAILS

This new frequency multiplier produces an output frequency which is either 60X or 100X the input frequency. Thus LF e.g., low audio, can be resolved without counting for ages. 60X range converts Hz to RPM with any 1 sec. gate counter. NO WAITING

NO RECIPROCAL

Shelton

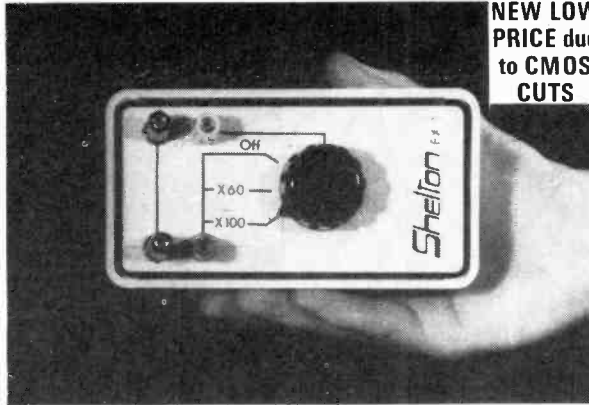

NEW LOW PRICE due to CMOS CUTS

FREQUENCY MULTIPLIER FX-1

RESOLVE 0.01Hz IN ONLY FOUR SECONDS OR READ RPM DIRECTLY.


WORKS WITH ANY FREQUENCY METER.

ONLY £27.50 inc p&p ex vat

INSTRUMENTS LTD., 24 Copenhagen Street, LONDON N1. Tel: 01-278 6273

WW—053 FOR FURTHER DETAILS

brenell PROFESSIONAL TAPE TRANSPORTS and multi-channel electronics for studio and industrial use

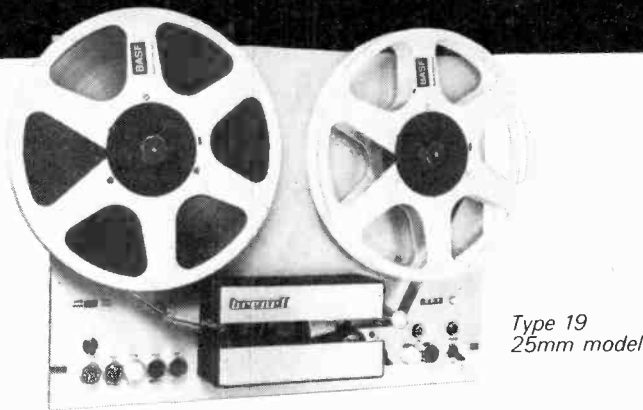

Type 19
25mm model

- * Tapewidths up to 25mm
- * Speeds: 3mm/s minimum up to 152cm/s max 2 and 4 speed models
- * Reel Capacity up to 29cm
- * Remote Control Facility
- * Tape Tension Control
- * Automatic Interlock against misuse
- * Special models to customer requirements

Finance available

BRENELL ENGINEERING CO LTD

231-5 Liverpool Road, London N1 1LY. Tel: 01-607 8271

WW—077 FOR FURTHER DETAILS

ALL SPEEDSERVICE

A new service from one of the largest United Kingdom exporters of tubes and semiconductors

AEL · GATWICK HOUSE · HORLEY · SURREY · RH6 9SU
Telex 87116 · Cables Aerocon Telex Horley · Telephone Horley 5353

WW—107 FOR FURTHER DETAILS

Contractors to H.M. Govt. P.O.

REPAIRS OF ELECTRICAL MEASURING INSTRUMENTS 7-14 DAYS SERVICE

◀ MODEL 8 MK.V



STOCKISTS
ALSO SUPPLIERS OF GEC
RISSO AND OTHER
MULTI-RANGE TEST SETS

WE SPECIALISE IN ASSEMBLIES, AND IN THE REPAIR, CALIBRATION AND CONVERSION OF ALL TYPES OF INSTRUMENTS, INDUSTRIAL AND PRECISION GRADE

LEDON INSTRUMENTS LTD.

GLADSTONE WORKS, GLADSTONE RD,
FOLKESTONE, KENT.
TEL: (STD) 0303 57555

WW—092 FOR FURTHER DETAILS



MODEL U-50DX

sanwa MULTI TESTERS

USED THROUGHOUT THE WORLD, SANWA'S EXPERIENCE OF 30 YEARS ENSURES ACCURACY, RELIABILITY, VERSATILITY, UNSURPASSED TESTER PERFORMANCE COMES WITH EVERY SANWA

MODEL P28	£9.76	MODEL F80TRD	£25.26
MODEL JP50	£11.58	MODEL AT45	£21.52
MODEL BK 505	£29.12	MODEL 380CE	£29.12
MODEL 360YTR	£15.28	MODEL N101	£31.81
MODEL U50DX	£15.60	MODEL 480E	£35.89
MODEL A303TRD	£17.45	MODEL EM800	£81.06
MODEL K30 THD	£24.01	MODEL R1000CB	£75.27

THESE PRICES ARE SUBJECT TO AN ADDITIONAL CHARGE OF 8% FOR V.A.T. Cases extra, available for most meters, but not sold separately.


Excellent Repair Service
Please write for illustrated leaflet of these and other specialised Sanwa meters

SOLE IMPORTERS IN U.K.

QUALITY ELECTRONICS LTD.

47-49 HIGH STREET, KINGSTON-UPON-THAMES, SURREY. KT1 1LP
Tel: 01-546 4585

WW—013 FOR FURTHER DETAILS

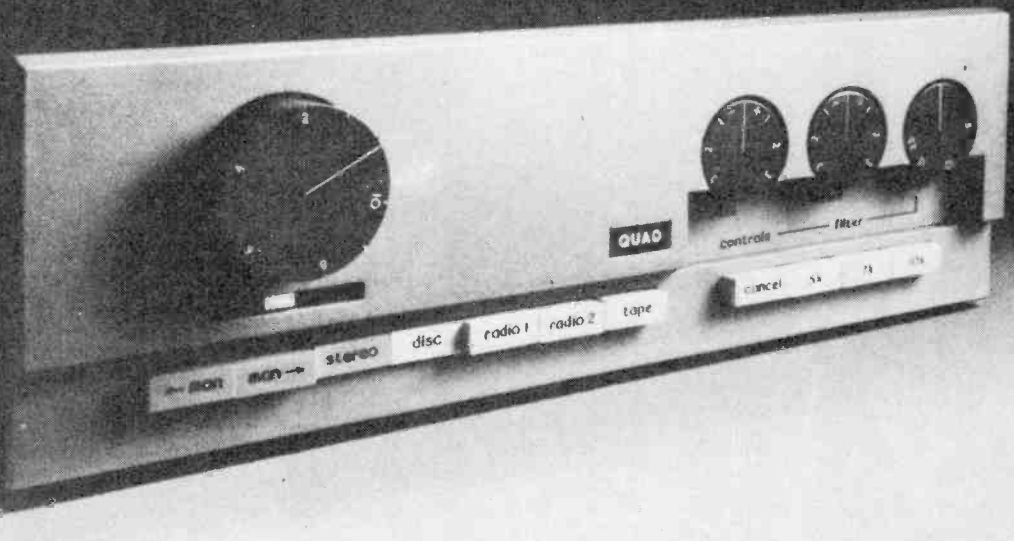

Now and Forever Today

With a Quad 33, any pickup can be properly matched to give the finest performance of which that pickup is capable (1).

Tomorrow

The Quad 33 pickup input is uniquely placed to meet the needs of the future (2).




Send postcard for illustrated leaflet to Dept. WW
Acoustical Manufacturing Co. Ltd., Huntingdon PE18 7DB.
Telephone (0480) 52561.

- 1 (a) Equivalent input noise at the exceedingly low figure of $0.5 \mu\text{V}$.
- (b) An input load which is a pure resistance at all frequencies. $5^\circ 0\text{-}20 \text{ KHZ}$.
- (c) An input dynamic range of close on 100dB, 30dB better than the finest recordings now available.
- (d) Provision to place the pickup dynamic range (60-70dB) in proper relation to the amplifier range so there need be no compromise between overload requirements and low noise.
- 2 Digital mastertapes for disc cutting and further refinement of the pickup cartridge will lead to lower noise and less distortion, and may make a major contribution to better sound in the next decade. The Quad 33 can do full justice to each and all of these possibilities.

QUAD
Products of
The Acoustical Manufacturing Co. Ltd.
for the closest approach to the original sound
QUAD is a Registered Trade Mark

WW—230 FOR FURTHER DETAILS

METER PROBLEMS?

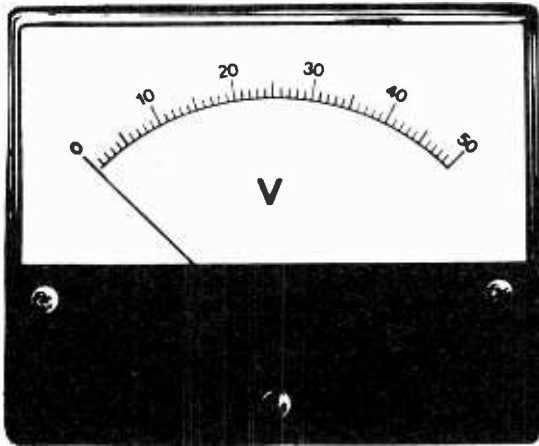

A very wide range of modern design instruments is available for 10/14 days' delivery.

Full Information from:

HARRIS ELECTRONICS (London)

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW—016 FOR FURTHER DETAILS



Make contact with Teonex

for electronic valves (a really comprehensive range), semi-conductors (a wide variety), integrated circuits. Prices on request.

Teonex offers more than 3,000 devices. They are competitively priced and they are superlative in performance, because the company imposes strict quality control. Teonex concentrates entirely on export and now operates in more than sixty countries, on Government or private contract. All popular types in the Teonex range are nearly always available for immediate delivery. Write now for technical specifications and prices to Teonex Limited, 2a Westbourne Grove Mews, London W11 2RY, England. Cables: Tosupply London W11. Telex: 262256 Electronic valves, semi-conductors and integrated circuits available only for export.



sounds international

WW—050 FOR FURTHER DETAILS



Now suitable for U.K., European and American voltages...

Minimod, the versatile British range of encapsulated power supplies first introduced in 1973, has now been extended to cover European and North American mains voltages (and is interchangeable with most American types). Normally available ex-stock, all units are fully stabilised with fold back current limiting – the 5V models have over voltage crowbar too!

STANDARD MODELS

Type Number	Output Voltage	Output Current Amps	Short Circuit Current mA (Typical)	% Regulation Line and Load (Typical)
PU01	5 ± 0.1	0.5	370	0.3
PU02	5 ± 0.1	1.0	770	0.5
PU03	15 - 0 - 15 ± 0.2	0.10	37	0.1
PU04	15 - 0 - 15 ± 0.2	0.20	84	0.1
PU05	12 - 0 - 12 ± 0.2	0.12	45	0.1
PU06	12 - 0 - 12 ± 0.2	0.24	120	0.2
PU11	18 - 0 - 18 ± 0.2	.15	50	0.1
PU10	15 ± 0.2	.10	37	0.1
PU12	12 ± 0.2	.10	45	0.1
PU13	18 ± 0.2	.065	23	0.1

Input voltage ranges 103 - 126V, 200 - 240V, 210 - 250V. Frequency 50 - 400 Hz all types.

Comprehensive specification given in brochure GT 29b which is available on request.

★ SPECIAL DESIGN SERVICE

Custom built units for applications requiring different specifications are produced as part of our standard service. Try us first.



Specialists in Electronic Transformers & Power Supplies.

GARDNERS
TRANSFORMERS LIMITED

Gardners Transformers Limited, Christchurch, Dorset, BH23 3PN.
Tel. Christchurch 2284 (STD 0201 5 2284) Telex. 41276 GARDNERS XCH
WW—056 FOR FURTHER DETAILS

Collect Wireless World Circards. And build a valuable dossier on circuit design.


Circards is a new and comprehensive system, launched by Wireless World, to provide professional engineers and enthusiasts with valuable and up-to-the-minute data on circuit design. Data not available from any other single source.

Each Circard is 8" x 5" and shows a specific circuit, a description of the circuit operation; component values and ranges; circuit limitations; circuit modifications; tested circuits; performance data and graphs.

The double-sided format enables the Circard to be filed in standard boxes for easy reference. And the plastic wallet provided keeps the cards well-protected.

Circard sets come in wallets and cost £1.50 per set. A subscription for 10 consecutive sets costs £13.50.

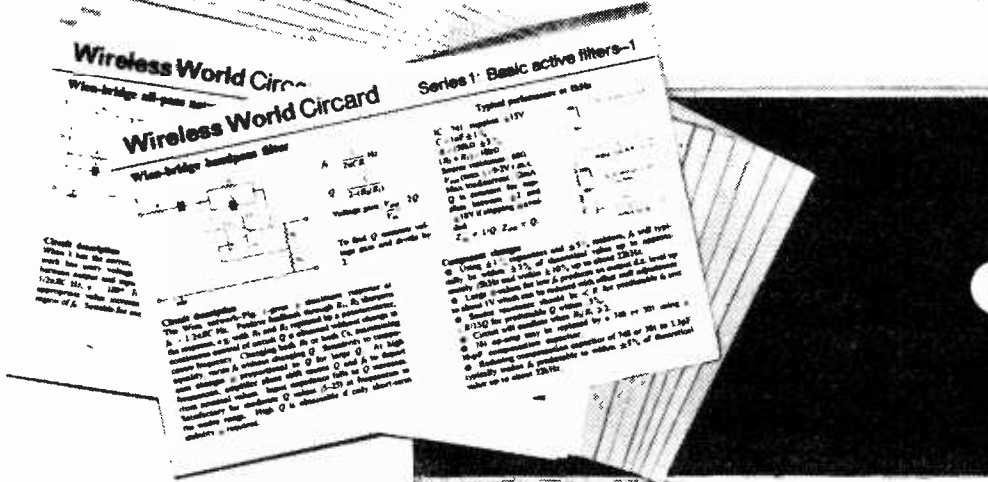Start your personal dossier on circuit design by completing and returning the coupon below.



Subjects already covered by Circards

1. Basic active filters. 2. Switching circuits comparators and schmitts.
3. Waveform generators. 4. AC measurements.
5. Audio circuits: preamplifiers, mixers, filters and tone controls.
6. Constant current circuits. 7. Power amplifiers.
8. Astables. 9. Opto-electronics.
10. Micropower circuits. 11. Basic logic gate circuits.
12. Wideband amplifiers. 13. Alarm circuits.
14. Digital counters. 15. Pulse modulators.
16. Current differencing amplifiers—signal processing.
17. Current differencing amplifiers—signal generation.
18. Current differencing amplifiers—measurement and detection.
19. Monostable circuits. 20. Transistor pairs.
21. Voltage to frequency converters.

Subjects planned for immediate future

Multipliers and dividers, Code converters, DC amplifiers and choppers, Amplitude modulation and detection, Transistor arrays.

To: General Sales Dept., IPC Business Press Ltd., Room 11
Dorset House, Stamford Street, London SE1 9LU

Please send me set no(s) @ £1.50 each *

I wish to subscribe to set no(s) @ £13.50 *

I enclose cheque/money order for £

*Tick as required/Cheques to be made payable to IPC Business Press Ltd.

Name

Address

Company registered in England. Registered address, Dorset House,
Stamford Street, SE1 9LU England. Registered Number 677128

"Worldwide Market is our aim," says Vitavox MD . . .



Reporting that the 1975 export order book of Vitavox Limited was the biggest in their 44-year history, the Company's Managing Director, Mr. Neil Young, said: "The expansion and strength of our export programme has always been a top priority with us. In today's industrial and economic climate this priority is more vital than ever".

Getting his priorities right has always been a first essential with Neil Young. On leaving school, where he studied modern languages, he joined the Royal Electrical and Mechanical Engineers: "To see if I had any technical ability". From here he went to English Electric, carrying out research work on technical literature with their Technical Publications Department. He moved on to the EWS Technivision Publications Division and then to Elliott Aviation, in both cases working on technical

instruction literature for the Services.

In 1962, at the age of 25, Neil Young joined Vitavox, the firm his father founded in 1931. He then became an Associate of the Institution of Works Management. Seven years later, after a period during which, among other projects, he and his brother David helped to develop the costing and production control systems of the Company, he succeeded his father, the late Mr. Len Young, as Managing Director; Mr. Young senior becoming Chairman of the Company, the post he held until his death in 1974.

"My policy has been to streamline production wherever possible, to continue to up-date production and, of course, to develop our export markets—all policies very much in tune with my father's beliefs."

With a turnover 100 times that of the Company's founding year, a home market as healthy as that for overseas and with the export market currently covering 34 countries across the world, Vitavox today is living proof that Neil Young's priorities are spot on.



VITAVOX
Limited
Westmoreland Road
London NW9 9RJ
Telephone: 01-204 4234



"I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn—and pave the way to a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating technatron course, you learn by building!

You build a modern transistor radio . . . a burglar alarm. You learn radio and electronics by doing actual projects you enjoy—making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of radio and electronics are growing faster than they can find people to fill the jobs!

No soldering—yet you learn faster than you ever dreamed possible.

Yes! Faster than you can imagine, you pick up the technical know-how you need. Specially prepared step-by-step lessons show you how to: read circuits—assemble components—build things—experiment. You enjoy every minute of it! You get everything you need, tools, components. Even a versatile multimeter that we teach you how to use. All included in the course AT NO EXTRA CHARGE! And this is a course anyone can afford. You can even pay for it by easy instalments.

So fast, so easy, this personalised course will teach you even if you don't know a thing today!

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-

to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions who don't understand. And you could pave the way to a great new career. To add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own transistor radio. And after the course you can go on to acquire high-powered technical qualifications, because our famous courses go right up to City & Guilds levels.


Send now for FREE 76-page book—see how easy it is—read what others say!

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

Switching problems? Rely on Zettler.

Producing 30 basic types of relay and 15,000 variants with regard to contact stacks, terminals, energizing current and contact material, Zettler is among the largest manufacturers of electro-mechanical components.

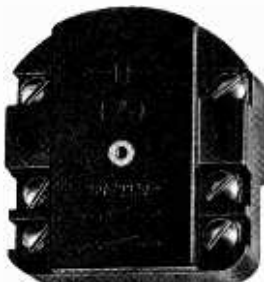Our product range comprises:
Low profile (flatform) · Timing · Miniature · Low contact capacity · Hermetically sealed · Stepping · Mains switching · Latching · Contact stacks · Solenoids



Impulse Latching Relay AZ 340

Make contacts:
Resistive load: 10 A/240 V AC.
Lamp load: 8 A/240 V AC.
Compensated fluorescent tubes: 3.7 A/240 V AC.
Break contacts:
Resistive load: 8 A/240 V AC.
Lamp load: 5 A/240 V AC.
Compensated fluorescent tubes: 3.7 A/240 V AC.

We resolve your switching problems rapidly and expertly. Please contact us for further details.

 **ZETTLER** Zettler UK Division
Equitable House, Lyon Road
Harrow, Middx. HA1 2DU, Tel. (01) 8636329
A member of the worldwide ZETTLER electrical engineering group, est. 1877

WW—205 FOR FURTHER DETAILS

POST TODAY FOR FREE BOOK

To: **BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**
Aldermaston College, Dept CWW02, Reading RG7 4PF

Yes, I'd like to know more about your course. Please send me free details—plus your big, 76-page book that tells about all your courses.

NAME

ADDRESS


POSTCODE

BIET


HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

IP I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

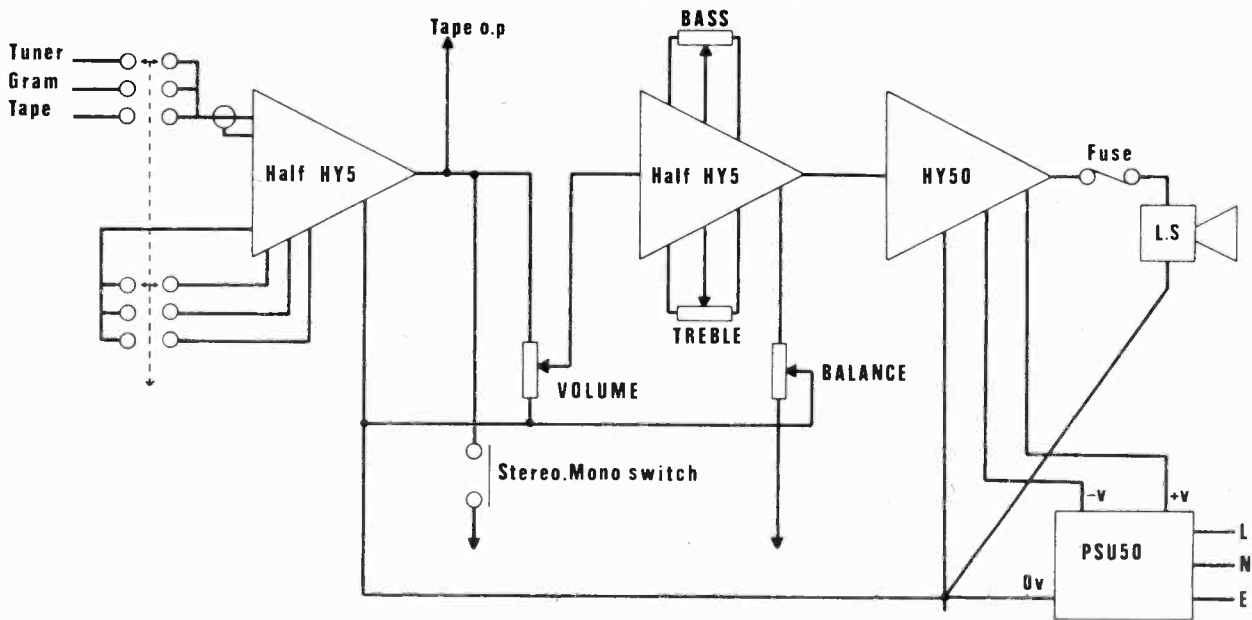

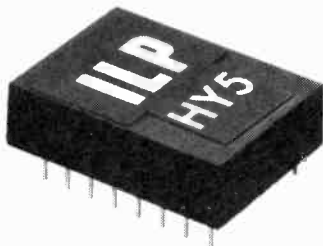Mono electrical circuit diagram with interconnections for stereo shown



The HY5 is a complete mono hybrid preamplifier, ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs
 Magnetic Pick-up 3mV.RIAA
 Ceramic Pick-up 30mV
 Microphone 10mV
 Tuner 100mV
 Auxillary 3-100mV
 Input impedance 47kΩ at 1kHz

Outputs
 Tape 100mV
 Main output Odb (0.775 volts RMS)

Active Tone Controls
 Treble ±12db at 10kHz
 Bass ±12db at 100Hz

Distortion 0.05% at 1kHz
Signal/Noise Ratio 68db
Overload Capability 40db on most sensitive input


Supply Voltage ±16-25 volts.
 PRICE £4.50 + 0.36 V.A.T. P & P free.



The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided: Input, output, power lines and earth.

TECHNICAL SPECIFICATION

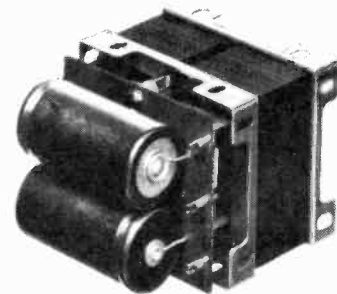Output Power 25 watts RMS into 8Ω
Load Impedance 4-16Ω
Input Sensitivity Odb (0.775 volts RMS)
Input Impedance 47kΩ
Distortion Less than 0.1% at 25 watts typically 0.05%
Signal/Noise Ratio Better than 75db
Frequency Response 10Hz-50kHz ±3db
Supply Voltage ±25 volts
Size 105 x 50 x 25 mm.
 PRICE £5.98 + 0.48 V.A.T. P & P free.



The PSU50 incorporated a specially designed transformer and can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage 50 volts (25-0-25)
Input voltage 210-240 volts
Size L.70. D.90. H.60 mm.
 PRICE £6.00 + 0.48 V.A.T. P & P free.

TWO YEARS GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd,
Crossland House,
Nackington, Canterbury,
Kent CT4 7AD
Tel (0227) 63218

Please Supply _____
 Total Purchase Price _____
 I Enclose Cheque Postal Orders Money Order
 Please debit my Access account Barclay card account
 Account number _____
 Name & Address _____
 Signature _____

Q: HOW CAN YOU MEASURE FREQUENCIES UP TO 180 MHz WITH A STANDARD 20 MHz DFM?

A: BY USING A 'CATRONICS' PRESCALER!

COMPLETELY AUTOMATIC IN OPERATION, this exclusive unit enables you to measure frequencies between 1 MHz and approx. 180 MHz without any range switching, input level control adjustment or other operation. The signal is connected to the input socket on the Prescaler and the ÷10 output is connected to a standard DFM capable of measuring up to 18 MHz.

Uses 'state of the art' ECL integrated circuits for accuracy and reliability. Built-in mains PSU or will operate on battery supply for portable use.

PRICE ONLY £39 + VAT + 40p P.P.
Delivery: generally from stock.

A full range of Digital Frequency Meters is also available from 5 digit 40 MHz models to 7 digit 180 MHz models—write for details.

CATRONICS LTD. Dept. 504, 20 THORNTON CRESCENT, OLD COULSDON, SURREY CR3 1LH (Tel: Downland 51413)

WW—236 FOR FURTHER INFORMATION



Phoenix Electronics (Solent) Ltd

139-141 Havant Road, Drayton, Portsmouth, Hants PO6 2AA

You already know us—get to know us better!
Our catalogue is now only 20p—returnable on your first order.
Our prices on a wide range of semiconductors, i.c.s and passive components include VAT, and, despite rising postal costs, carriage is only 20p, too!

THIS MONTH'S BARGAIN OFFER

The Emihus GEMINI 1 POCKET CALCULATOR with the expensive specification—five function operation—percentage key—automatic constant—full floating or fixed decimal point—8 digit display—carrying case—overflow/error indicator. Our ultra-low price of **£14.95** even includes batteries!

Please send your catalogue—now!


Name

Address

..... WW1

FREQUENCY COUNTERS

HIGH PERFORMANCE REASONABLY PRICED ELECTRONIC INSTRUMENTS

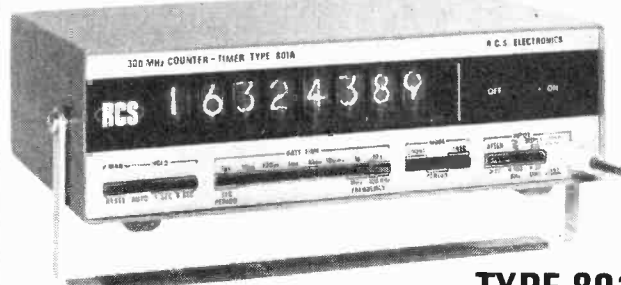

TYPE 801

300MHz 8 Digits 10mV Sensitivity

Stability 3 parts in 10⁸ Crystal Oven.

Two tone blue case 12 1/4" x 8" x 3 3/4" **£285**

301M	32MHz 5 Digit £75	401	32MHz 6 Digit £115
501	32MHz 8 Digit £170	701	50MHz 8 Digit £180
701	80MHz 8 Digit £190	801M	300MHz 8 Digit £285
901M	520MHz 8 Digit £370	Memory versions available if not suffixed M £25 extra	
Start/Stop versions plus £12			
101 1MHz 100KHz 10KHz Crystal Standard £80			
103 Off/Air Standard £78			

Supplied to and acclaimed by professional engineers for a decade




R. C. S. ELECTRONICS
NATIONAL WORKS, BATH ROAD,
HOUNSLOW, MIDDX. TW4 7EE
Telephone: 01-572 0933/4

WW—207 FOR FURTHER DETAILS



SQ10
Sine/Square Oscillator

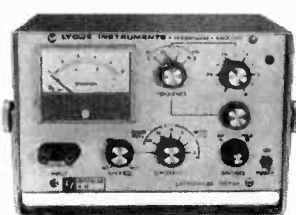

D10
Distortion Meter

Full information on the SQ10 and D10, and on LI's fine range of pulse generators available on request.

AF OSCILLATOR DISTORTION METER

SQ10 Sine/Square Oscillator

- 10Hz-1MHz
- 10V p-p from 50Ω
- sine distortion 0.1%
- square risetime 100ns

D10 Distortion Meter

- 0.1%-10% THD
- 10Hz-100kHz
- 0.05% intrinsic distortion


low cost high performance **INTERLAB** instruments



made in England by
LYONS INSTRUMENTS
Hoddesdon Herts EN11 9DX
Telephone 67161 Telex 22724
A Claude Lyons Company

WW—229 FOR FURTHER DETAILS

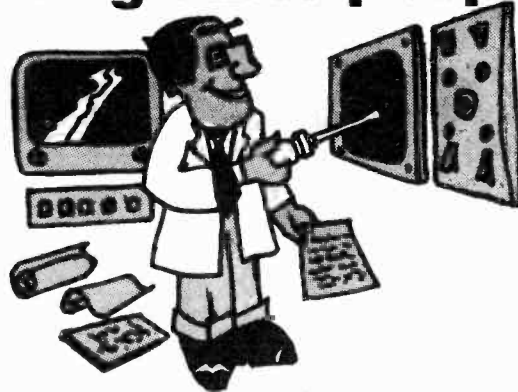We enjoy solving other people's problems!



Jasmin take a slightly different approach to their customers and they are proud of the rapport they attain with them. Research and development staff are always available to offer advice on technical issues. This in turn means that Jasmin are able to offer a unique service if you have problems in the following spheres

- Complex automatic text and evaluation apparatus.
- Digitalized video and Ceefax/Oracle display equipment.
- Mini computer orientated systems.
- Specialist contract engineering.

Jasmin ELECTRONICS LIMITED

BOSTON HOUSE, ABBEY PARK ROAD, LEICESTER LE4 5AN
TELEPHONE: 0533-58128/9 TELEX: 341581

ARISTOCRATS IN CONTROL

WW-144 FOR FURTHER DETAILS

Nagra tape recorders

overseas and home enquiries invited

Nagra III
Series Machines Fully
Overhauled
by Factory Trained
Personnel.
Guaranteed
for six months.

Please apply to the exclusive UK agents :

NAGRA KUDELSKI

HAYDEN

Hayden Laboratories Ltd.
Hayden House, 17 Chesham Road,
Amersham, Bucks. HP 5 AG. Telephone: (02403) 5511

Y&R HAZ

New LOGIC PROBE 340

Generates a single minus pulse
of 02 ± 0.05 millisecond.
Built-in pulse generator

- RED & GREEN-LED APPLIED LOGIC LEVEL INDICATOR
- * Wrong polarity & overload protectors provided
 - * Detection of the peak value of input waveform
 - * Open circuit or faulty IC can be detected
 - * All logic levels are visible at a glance
 - * Unique high/low level probe

For use in
detecting TTL,
DTL flip-flop
and other pulse
circuits.


Each **£14.00**
including pp + VAT
Discounts for quantity

JH

ASSOCIATES LIMITED
52 Silver Street, Stansted, Essex. Tel: (0279) 814929. Telex: 81675 Jaylamps.

WW-020 FOR FURTHER DETAILS

J E S AUDIO INSTRUMENTATION

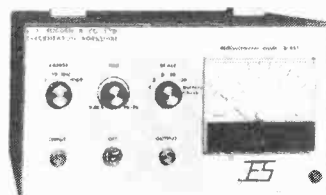

Illustrated the Si 451
Millivoltmeter — pk-pk
or RMS calibration with
variable control for rela-
tive measurements. 40
calibrated ranges **£42.50**

Si 452 **£35.00**
Distortion Measuring Unit.
15 Hz — 20 KHz — .01%


Si 453 **£50.00**
Low distortion Oscillator.
Sine — Square — RIAA

J. E. SUGDEN & CO., LTD. Tel. Cleckheaton (09762) 2501
CARR STREET, CLECKHEATON, W. YORKS BD19 5LA

WW-042 FOR FURTHER DETAILS

1/2 watt ATTENUATORS TERMINATIONS IMPEDANCE TRANSFORMERS

MANUFACTURED BY ELCOM SYSTEMS INC.

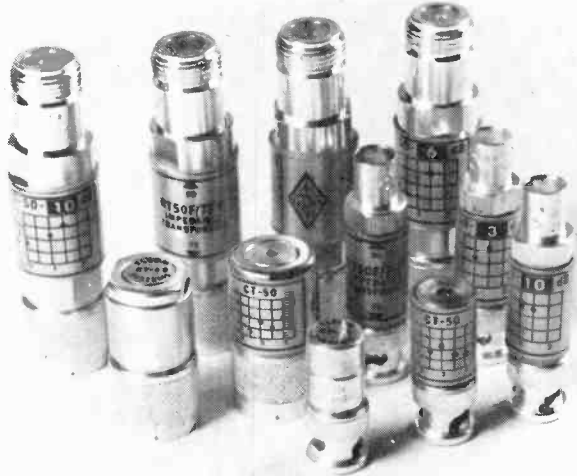

LOW COST **FAST DELIVERIES**
FROM

aspen electronics limited
18a HIGH ST NORTHWOOD MIDDX HA6 1BN
TELEPHONE NORTHWOOD 27688

NEW!...the decon-dalo 33 PC Quick -Dri etch -resist marker



A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB.

A fine-tipped marking pen charged with free-flowing etch-resist ink — new formulation QUICK-DRI ink is ready for etching in just two minutes!

Simply draw the desired circuit onto copper laminated board — etch — clean.

The circuit is ready to use

NO MESS — NO MASKING
A perfect circuit every time!

Still only £1.00 for one-off, £4.00 for six, £8.00 for twelve
VAT and post extra. Available now in every country
in Europe.


Decon Laboratories Ltd., Ellen Street,
Portslade, Brighton BN4 1EQ Phone: 0273 414371

Please send me further details on the 33 PC Quick-Dri

Name

Address

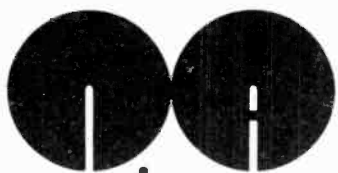Post to: **DECON LABORATORIES LTD.**
FREEPOST
PORTSLADE, BRIGHTON, ENGLAND
(No Stamp Needed) Phone 0273 414371



naim audio the preamplifier

BE FAIR TO YOUR MUSIC

Reproduction of sound and its acceptability is dependent on a combination of physical parameters not yet fully explored. We believe that only a compatible combination of specifications will enable a system to reproduce music.

We have taken care that the NAC 12 and NAP 160 pre and power amplifier will do so faithfully, while accepting the output of any pickup cartridge and driving any loudspeaker.



Naim Audio Ltd. 11 Salt Lane, Salisbury, Wilts. Tel: (0722) 3746

WW—220 FOR FURTHER DETAILS

S-2020TA STEREO TUNER/AMPLIFIER KIT

NEW PRODUCT

A high-quality push-button FM Varicap Stereo Tuner combined with a 20W r.m.s. per channel Stereo Amplifier.

Brief Spec. Amplifier: Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc), THD less than 0.1% at 20W into 8 ohms. All sockets, fuses, etc, are PC mounted for ease of assembly. Tuner section: uses Mullard LP1186 module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88–104MHz. 30dB mono S/N @ 1.8µV. THD typ. 0.4%.

PRICE: £47.95 + 99p p&p + VAT.



SOLID MAHOGANY CABINET



NELSON-JONES STEREO FM TUNER

A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter/dual IC IF amp.

Brief Spec. Tuning range 88–104MHz. 20dB mono quieting @ 0.75µV. Image rejection—70dB. IF rejection—85dB. THD typically 0.4%. IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

**PRICE: Mono £25.46 + 85p p&p + VAT;
With Portus-Haywood Decoder £31.96 + 85p p&p + VAT;
With ICPL Decoder £29.73 + 85p p&p + VAT.**

NEW PRODUCT

S-2020A AMPLIFIER KIT

Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring.

Typ. Spec. 20+20W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Head-phone output. Tape In/Out facility (for noise reduction unit, etc). Toroidal mains transformer.

PRICE: £29.95 + 99p p&p + VAT.



STEREO MODULE TUNER

A low-cost Stereo Tuner based on the Mullard LP1186 RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC. Variable INTERSTATION MUTE. PLL stereo decoder IC.

Typ. Spec. Sens. 30dB S/N mono @ 1.8µV. Tuning range 88–104MHz. LED sig. strength indicator. LED Stereo indicator. THD typically 0.4%.

PRICE: Stereo £26.32 + 85p p&p + VAT. Mono £22.40 + 85p p&p + VAT.

ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS.

SUB ASSEMBLIES

BASIC NELSON-JONES TUNER

Supplied as a printed circuit board with all components and screening box to build a varicap tuner module. Performance spec as above for complete N-J Tuner. For suitable stereo decoders see below. (Illustrated without screening box.)

PRICE: £12.88 + 25p p&p + VAT.



BASIC MODULE TUNER

Supplied as a printed circuit board with all components and screened Mullard LP1186, to build a mono or stereo tuner module. Performance spec as above for Stereo Module Tuner complete kit.

PRICE: Mono £11.11 + 25p p&p + VAT; Stereo £13.89 + 25p p&p + VAT.



PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER

Mk II version of this design (WW Sept. 1970). The lowest distortion phase-locked stereo decoder kit available (Typ. 0.05% @ N-J Tuner O/P level). Separation 40dB up to 15KHz. Complete kit comprises PCB and all components, inc. stereo LED.

PRICE: £7.68 + 25p p&p + VAT.



PHASE-LOCKED IC DECODER

Integrated circuit phase-locked stereo decoder based on the MC1310. THD typically 0.3%. Separation 40dB @ 1KHz.

PRICE: £4.27 + 20p p&p + VAT.



PUSH-BUTTON UNIT

The six-position push-button unit used in our tuners and tuner/amp. Each track has the required diode law for stability of tuning. There are approx. 40 turns on each button and there are six separate moving pointers. An AFC disable switch is incorporated with each button. The unit is finished in black with red pointers.

PRICE: £3.00 + 20p p&p + VAT.



Please send SAE for complete lists and specifications.

INTEGREX LIMITED, Portwood Industrial Estate, Church Gresley, Burton-on-Trent, Staffs, DE11 9PT.
Tel. Swadlincote (0283 87) 5432. Telex 377106.




sound equipment
by **Grampian**

GRAMPIAN REPRODUCERS LTD. HANWORTH TRADING ESTATE FELTHAM MIDDLESEX TELEPHONE 01-894 9141

X209

WW—234 FOR FURTHER DETAILS

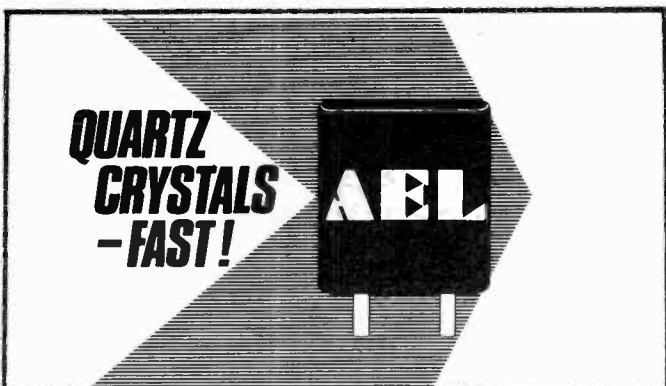

AEL GATWICK HOUSE, HORLEY, SURREY, ENGLAND
Tel: Horley (02934) 5353
Telex: 87116 (Aerocon Horley) · Cables: Aerocon Telex Horley

WW—026 FOR FURTHER DETAILS

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP
(as in 'W.W.' July '72)

MOTOROLA MC1310P EX STOCK DELIVERY
SPECIFICATION

Separation: 40dB 50Hz-15kHz. Distortion: 0-3%
I/P level: 560mV rms. O/P level: 485mV rms per channel.
Input impedance: 50kΩ. Power requirements: 8-16V at 16mA
Will drive up to 75mA stereo 'on' lamp or LED.

KIT COMPRISES FIBREGLASS PCB
(Roller tinned), Resistors, I.C., Capacitors,
Preset Potm. & Comprehensive Instructions

ONLY WHY PAY
£3-98 MORE?
post free.

LIGHT EMITTING DIODE
Suitable as stereo 'on' indicator for above

RED 29p
GREEN 59p

MC1310P only £3-15 plus p.p. 6p

NOTE
As the supplier of the first MC1310P decoder kit, of which we have sold literally thousands,
our customers can benefit from our wide experience.

V.A.T.

Please add V.A.T. at 8% to all prices

FI-COMP ELECTRONICS

PORTWOOD IND. EST., CHURCH GRESLEY, BURTON ON TRENT, STAFFS.
DE11 9PT

PETITE PRECISION!


A 12V DC POWER TOOL FOR THE DESIGN
AND RESEARCH ENGINEER

AVAILABLE IN KIT FORM OR SEPARATES



Diameter 33mm
Weight 160g
Length 125mm
Torque 105cmg
RPM approx 3000
at 12V DC
Power 9/14V DC
Batteries
or AC/DC
transformer

PRECISION EXAMPLE OF FRENCH ENGINEERING

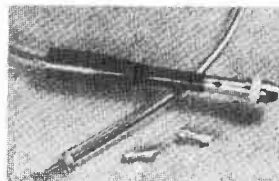

Now in use by the following:
GPO, BBC, Atomic Energy
Authority, British Nuclear Fuels,
Weekend TV, Ministry of Defence,
Hospitals, Opticians, etc.



UK DISTRIBUTOR

PRECISION PETITE LTD
(Les Applications Rationnelles Paris)

119A HIGH STREET, TEDDINGTON,
MIDDX, UK.
TEL. 01-977 0878

SAE for leaflets, price list and order form

Eliminate TV receiver distortion with Celestion *TELEFI*

TELEFI




At last you can enjoy TV entertainment with the added pleasure of true Hi-Fi sound. Telefi is a unique electronic invention which picks up VHF from the TV and relays this through your own Hi-Fi equipment. Telefi ensures crisp, full-range, distortion-free reproduction of music and speech providing an improvement over ordinary TV sound which will amaze you. Telefi is safe and requires no permanent connection to the TV set. Telefi is indispensable to the TV viewer who requires Hi-Fi TV sound.

"As selected for The Design Centre, London".

LOUDSPEAKERS

Celestion Loudspeakers are engineered to the highest standard and provide superlative sound reproduction. The cut-away illustration shows the high, mid and bass speakers used in the Ditton 44 Monitor, one of the most popular loudspeakers available to the discerning listener.

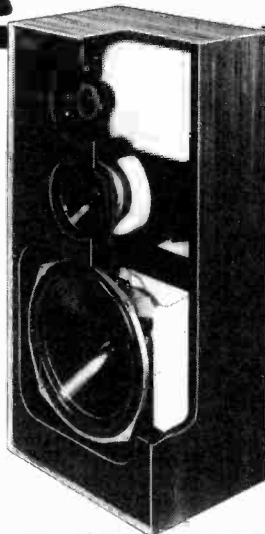A range of models is available to suit your personal requirements, Celestion Hi-Fi Loudspeakers carry a five-year guarantee.



The Hadleigh loudspeaker, was specially created to meet a public demand for a high quality speaker of compact proportions. Not a difficult task for Celestion who produce the most popular bookshelf speaker ever (Ditton 15) – but we set out not only to produce an immaculate loudspeaker with a sparkling performance, but to do so at a budget price. For the enthusiast seeking a really excellent Hi-Fi system at reasonable outlay we recommend without hesitation the Hadleigh.




Celestion



Loudspeakers for the Perfectionist
DITTON WORKS, FOXHALL ROAD, IPSWICH, SUFFOLK IP3 8JP.

WW—059 FOR FURTHER DETAILS

Audio Test Set

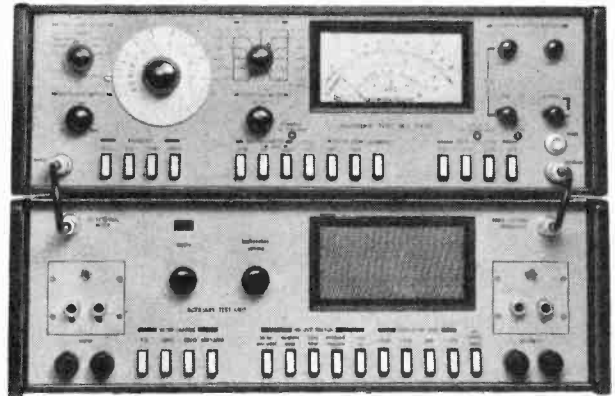

for amplifiers, mixers tape recorders

Checks . . . frequency response
signal/noise ratio
distortion
cross-talk
wow & flutter
drift
erasure
sensitivity
output power
gain
. . . in one compact unit.

Auxiliary Unit provides extra
facilities for Studio testing.

Send for leaflet RTS2

Ferrograph Company Limited Auriema House 442 Bath Road
Cippenham Slough Buckinghamshire SL1 6BB
Telephone: Burnham (062 86) 62511 Telex: 847297

FERROGRAPH

A member of the Wilmot Breeden group

WW—094 FOR FURTHER DETAILS



SHEET METAL PUNCHES FOR QUICK CLEAN HOLES



- ★ Easiest and quickest way of punching holes in sheet metal (up to 1.625mm)
 - ★ Simple operation ★ 100% British
 - ★ Burr-free holes—no jagged edges
 - ★ 57 Metric and Linear sizes.
- Lists obtainable from us.

Used by all Government services—Atomic, Military, Naval, Air, G.P.O. and Ministry of Works; Radio, Motor, and Industrial manufacturers, Plumbing and Sheet Metal Trades, Garages, etc. Available from all leading factors.

"Q-MAX" (ELECTRONICS) LTD
 44 PENTON STREET · LONDON N19QA Tel: 01-278 2500

WW—235 FOR FURTHER DETAILS



INDUSTRIAL PRICES FOR THE HOBBYIST
 ALL 'BIG NAME' BRANDED GOODS
 SAME DAY SERVICE
 MONEY BACK GUARANTEE

LINEAR 1/C'S		DIODES		ZENER DIODES	
709C	0.24	IN4001	4	BZY88	400mW
710C	0.24	IN4002	4	Voltages 3.3v—30v	
741C (8P In Minidip)	0.20	IN4003	5	6p	
CA3046	0.50	IN4004	5	AUDIO 1/C'S	
LM309K	1.25	IN4005	6	TAA661B	1.0
COS/MOS		IN4006	6	CA3089E	1.5
CD4001	0.24	IN4007	2	CA3090Q	3.0
CD4009	0.40	OA47	4	CA3028	1.0
CD4011	0.20	OA200	6	CA3048	2.0
CD4012	0.20	IN4148	1.5		
CD4018	1.50				
CD4029	1.50				
TRANSISTORS					
BC107	0.07	BFY50	14	2N696	0.15
BC108	0.07	BFY51	0.12	2N697	0.20
BC109	0.07	BFY52	0.15	2N706	0.10
BCY70	0.09	BFY90	0.60	2N930	0.18
BCY71	0.09	BSY95A	0.10	2N1302	0.16
BCY72	0.09	C426	0.28	2N1303	0.12
BFX29	0.16	40360	0.40	2N1304	0.20
BFX84	0.16	40361	0.40	2N1305	0.20
BFX85	0.16	40362	0.40	2N2160	0.50
BFX86	0.16	40669	0.80	2N2646	0.40
BFX87	0.16	40673	0.50	2N3053	0.15
BFX88	0.16	40602	0.40	2N3054	0.40
BC237	0.08			2N3055	0.40

TERMS: CWO—10p POST & PACKING—ADD 8% VAT

ROWNSGEM LTD.

Rosebank Parade, Plough Road, Yateley, Camberley, Surrey.
 Phone No. 0252 871388

THE PROFESSIONAL ORGANISATION FOR THE 'HOBBYIST'

TRANSISTORS					DIODES					THYRISTORS, TRIACS AND TRIACS WITH TRIGGER					
Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)	Type	Price (£)
BD115	0.85	BD123	0.80	BD130Y	1.42	BD132	0.50	BD135	0.48	BD137	0.40	BD138	0.50	BD139	0.55
BD139	0.50	BD140	0.82	BD141	2.19	BD142	0.75	BD143	0.75	BD144	0.75	BD145	0.75	BD146	0.75
BD147	0.75	BD148	0.75	BD149	0.75	BD150	0.75	BD151	0.75	BD152	0.75	BD153	0.75	BD154	0.75
BD155	0.75	BD156	0.75	BD157	0.75	BD158	0.75	BD159	0.75	BD160	0.75	BD161	0.75	BD162	0.75
BD163	0.75	BD164	0.75	BD165	0.75	BD166	0.75	BD167	0.75	BD168	0.75	BD169	0.75	BD170	0.75
BD171	0.75	BD172	0.75	BD173	0.75	BD174	0.75	BD175	0.75	BD176	0.75	BD177	0.75	BD178	0.75
BD179	0.75	BD180	0.75	BD181	0.75	BD182	0.75	BD183	0.75	BD184	0.75	BD185	0.75	BD186	0.75
BD187	0.75	BD188	0.75	BD189	0.75	BD190	0.75	BD191	0.75	BD192	0.75	BD193	0.75	BD194	0.75
BD195	0.75	BD196	0.75	BD197	0.75	BD198	0.75	BD199	0.75	BD200	0.75	BD201	0.75	BD202	0.75
BD203	0.75	BD204	0.75	BD205	0.75	BD206	0.75	BD207	0.75	BD208	0.75	BD209	0.75	BD210	0.75
BD211	0.75	BD212	0.75	BD213	0.75	BD214	0.75	BD215	0.75	BD216	0.75	BD217	0.75	BD218	0.75
BD219	0.75	BD220	0.75	BD221	0.75	BD222	0.75	BD223	0.75	BD224	0.75	BD225	0.75	BD226	0.75
BD227	0.75	BD228	0.75	BD229	0.75	BD230	0.75	BD231	0.75	BD232	0.75	BD233	0.75	BD234	0.75
BD235	0.75	BD236	0.75	BD237	0.75	BD238	0.75	BD239	0.75	BD240	0.75	BD241	0.75	BD242	0.75
BD243	0.75	BD244	0.75	BD245	0.75	BD246	0.75	BD247	0.75	BD248	0.75	BD249	0.75	BD250	0.75
BD251	0.75	BD252	0.75	BD253	0.75	BD254	0.75	BD255	0.75	BD256	0.75	BD257	0.75	BD258	0.75
BD259	0.75	BD260	0.75	BD261	0.75	BD262	0.75	BD263	0.75	BD264	0.75	BD265	0.75	BD266	0.75
BD267	0.75	BD268	0.75	BD269	0.75	BD270	0.75	BD271	0.75	BD272	0.75	BD273	0.75	BD274	0.75
BD275	0.75	BD276	0.75	BD277	0.75	BD278	0.75	BD279	0.75	BD280	0.75	BD281	0.75	BD282	0.75
BD283	0.75	BD284	0.75	BD285	0.75	BD286	0.75	BD287	0.75	BD288	0.75	BD289	0.75	BD290	0.75
BD291	0.75	BD292	0.75	BD293	0.75	BD294	0.75	BD295	0.75	BD296	0.75	BD297	0.75	BD298	0.75
BD299	0.75	BD300	0.75	BD301	0.75	BD302	0.75	BD303	0.75	BD304	0.75	BD305	0.75	BD306	0.75
BD307	0.75	BD308	0.75	BD309	0.75	BD310	0.75	BD311	0.75	BD312	0.75	BD313	0.75	BD314	0.75
BD315	0.75	BD316	0.75	BD317	0.75	BD318	0.75	BD319	0.75	BD320	0.75	BD321	0.75	BD322	0.75
BD323	0.75	BD324	0.75	BD325	0.75	BD326	0.75	BD327	0.75	BD328	0.75	BD329	0.75	BD330	0.75
BD331	0.75	BD332	0.75	BD333	0.75	BD334	0.75	BD335	0.75	BD336	0.75	BD337	0.75	BD338	0.75
BD339	0.75	BD340	0.75	BD341	0.75	BD342	0.75	BD343	0.75	BD344	0.75	BD345	0.75	BD346	0.75
BD347	0.75	BD348	0.75	BD349	0.75	BD350	0.75	BD351	0.75	BD352	0.75	BD353	0.75	BD354	0.75
BD355	0.75	BD356	0.75	BD357	0.75	BD358	0.75	BD359	0.75	BD360	0.75	BD361	0.75	BD362	0.75
BD363	0.75	BD364	0.75	BD365	0.75	BD366	0.75	BD367	0.75	BD368	0.75	BD369	0.75	BD370	0.75
BD371	0.75	BD372	0.75	BD373	0.75	BD374	0.75	BD375	0.75	BD376	0.75	BD377	0.75	BD378	0.75
BD379	0.75	BD380	0.75	BD381	0.75	BD382	0.75	BD383	0.75	BD384	0.75	BD385	0.75	BD386	0.75
BD387	0.75	BD388	0.75	BD389	0.75	BD390	0.75	BD391	0.75	BD392	0.75	BD393	0.75	BD394	0.75
BD395	0.75	BD396	0.75	BD397	0.75	BD398	0.75	BD399	0.75	BD400	0.75	BD401	0.75	BD402	0.75
BD403	0.75	BD404	0.75	BD405	0.75	BD406	0.75	BD407	0.75	BD408	0.75	BD409	0.75	BD410	0.75
BD411	0.75	BD412	0.75	BD413	0.75	BD414	0.75	BD415	0.75	BD416	0.75	BD417	0.75	BD418	0.75
BD419	0.75	BD420	0.75	BD421	0.75	BD422	0.75	BD423	0.75	BD424	0.75	BD425	0.75	BD426	0.75
BD427	0.75	BD428	0.75	BD429	0.75	BD430	0.75	BD431	0.75	BD432	0.75	BD433	0.75	BD434	0.75
BD435	0.75	BD436	0.75	BD437	0.75	BD438	0.75	BD439	0.75	BD440	0.75	BD441	0.75	BD442	0.75
BD443	0.75	BD444	0.75	BD445	0.75	BD446	0.75	BD447	0.75	BD448	0.75	BD449	0.75	BD450	0.75
BD451	0.75	BD452	0.75	BD453	0.75	BD454	0.75	BD455	0.75	BD456	0.75	BD457	0.75	BD458	0.75
BD459	0.75	BD460	0.75	BD461	0.75	BD462	0.75	BD463	0.75	BD464	0.75	BD465	0.75	BD466	0.75
BD467	0.75	BD468	0.75	BD469	0.75	BD470	0.75	BD471	0.75	BD472	0.75	BD473	0.75	BD474	0.75
BD475	0.75	BD476	0.75	BD477	0.75	BD478	0.75	BD479	0.75	BD480	0.75	BD481	0.75	BD482	0.75
BD483	0.75	BD484	0.75	BD485	0.75	BD486	0.75	BD487	0.75	BD488	0.75	BD489	0.75	BD490	0.75
BD491	0.75	BD492	0.75	BD493	0.75	BD494	0.75	BD495	0.75	BD496	0.75	BD497	0.75	BD498	0.75
BD499	0.75	BD500	0.75	BD501	0.75	BD502	0.75	BD503	0.75	BD504	0.75	BD505	0.75	BD506	0.75
BD507	0.75	BD508	0.75	BD509	0.75	BD510	0.75	BD511	0.75	BD512	0.75	BD513	0.75	BD514	0.75
BD515	0.75	BD516	0.75	BD517	0.75	BD518	0.75	BD519	0.75	BD520	0.75	BD521	0.75	BD522	0.75
BD523	0.75	BD524	0.75	BD525	0.75	BD526	0.75	BD527	0.75	BD528	0.75	BD529	0.75	BD530	0.75
BD531	0.75	BD532	0.75	BD533	0.75	BD534	0.75	BD535	0.75	BD536	0.75	BD537	0.75	BD538	0.75
BD539	0.75	BD540	0.75	BD541	0.75	BD542	0.75	BD543	0.75	BD544	0.75	BD545	0.75	BD546	0.75
BD547	0.75	BD548	0.75	BD549	0.75	BD550	0.75	BD551	0.75	BD552	0.75	BD553	0.75	BD554	0.75
BD555	0.75	BD556	0.75	BD557	0.75	BD558	0.75	BD559	0.75	BD560	0.75	BD561	0.75	BD562	0.75
BD563	0.75	BD564	0.75	BD565	0.75	BD566	0.75	BD567	0.75	BD568	0.75	BD569	0.75	BD570	0.75
BD571	0.75	BD572	0.75	BD573	0.75	BD574	0.75	BD575	0.75	BD576	0.75	BD577	0.75	BD578	0.75
BD579	0.75	BD580	0.75	BD581	0.75	BD582	0.75	BD583	0.75	BD584	0.75	BD585			



P.B. ELECTRONICS LTD.

SCOTLAND

57 HIGH STREET, SAFFRON WALDEN,
ESSEX TEL: (0799) 22876
TELEX: 817201

62 LARGO ROAD, ST. ANDREWS, FIFE,
SCOTLAND TEL: ST. ANDREWS 2641
TELEX: 76404

HALF PRICE OFFER FIBRE GLASS CIRCUIT BOARD

BOARD SIZE	RESIST COATED FIBRE GLASS RESIST COATED												PAPER	
	5/64" or 3/32" or 1/8"—1 oz				1/32"—1 oz				1/16"—1 oz				1/16"—1 oz	
	Single Sided		Double Sided		Single Sided		Double Sided		Single Sided		Double Sided		Single Sided	
	Positive	Negative	Positive	Negative	Positive	Negative	Positive	Negative	Positive	Negative	Positive	Negative	Positive	Negative
75mm x 100mm	14p	12p	15p	13p	8p	8p	8p	8p	16p	15p	14p	13p	8p	8p
100mm x 150mm	27p	24p	29p	26p	15p	14p	19p	15p	33p	30p	29p	26p	15p	14p
150mm x 200mm	53p	48p	56p	51p	30p	27p	37p	30p	66p	60p	60p	54p	30p	27p
200mm x 250mm	88p	80p	92p	84p	51p	45p	63p	51p	£1.10	£1.00	£1.02	92p	51p	45p
250mm x 250mm	£1.10	£1.00	£1.15	£1.05	65p	55p	80p	65p	£1.38	£1.25	£1.30	£1.15	65p	55p
12" x 6"	80p	70p	85p	75p	55p	45p	65p	55p	£1.00	90p	£1.10	£1.00	55p	45p
12" x 12"	£1.60	£1.40	£1.65	£1.45	£1.05	85p	£1.25	£1.05	£1.95	£1.75	£2.10	£1.90	£1.05	85p

Extra Discounts 5 sheets 5%, 10 sheets 10%, 20 sheets 20%, 50 sheets and above 30%.

All goods add 8% VAT+ post and packing 30p. 10 sheets or more free. Hurry limited stocks delivery subject to availability. Prices may be changed without notice.


P.S. We also specialise in printed circuit board manufacture. Lowest prices, fastest delivery.

WW—195 FOR FURTHER DETAILS

brenell

PROFESSIONAL TAPE TRANSPORTS

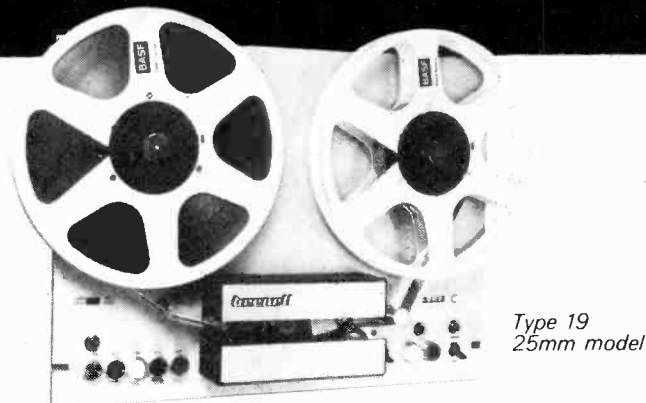and multi-channel electronics
for studio and industrial use



Finance available



- * Tapewidths up to 25mm
- * Speeds: 3mm/s minimum up to 152cm/s max
2 and 4 speed models
- * Reel Capacity up to 29cm
- * Remote Control Facility
- * Tape Tension Control
- * Automatic Interlock against misuse
- * Special models to customer requirements

BRENELL ENGINEERING CO LTD
231-5 Liverpool Road, London N1 1LY. Tel: 01-607 8271

WW—077 FOR FURTHER DETAILS

OSCILLATORS

Why build

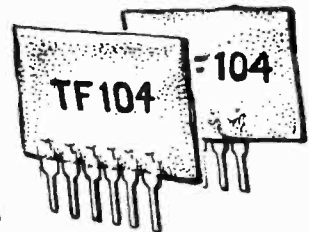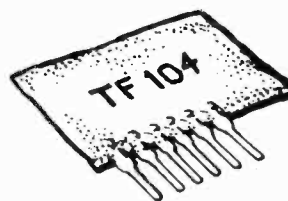

your own?

WE'VE GOT THEM EX STOCK

DO YOU HAVE THE TIME:
To design, develop & perfect.
To source the components.
To manufacture them. — IS IT REALLY WORTH IT ?

1+ 10+ 100+
£4 £3.50 £2.80 each

Our modules are tuneable from 100Hz to 20KHz and need only two external capacitors. The output frequency stability is 0.1% at 20KHz, and up to 2V.r.m.s.

FOR 24 HR. DESPATCH SEND ORDER TO ADDRESS BELOW OR PHONE 01-668 7151.

Redlands, Coulsdon, Surrey, CR3 2HT

Guest Distribution



WW—243 FOR FURTHER DETAILS

TRANSFORMERS

CASED TRANSFORMERS

Housed in smart resin-coated steel cases with 3-core power cable and outlet socket, fused primary winding. Isolation types are fitted with 3 pin outlet sockets, and are available with 110 volt or 240 volt output (Please state). Auto types are fitted with 2 pin flat style sockets up to 500 VA. 3 pin sockets from 750 to 3000 VA. See Auto and Isolation sections for prices. Plug extra.



SAFETY ISOLATING

Prim. 120/240V. Sec. 120/240V. Centre Tap with screen

VA (WATTS)	REF. No.	PRICE Cased £	PRICE Plugs 2 Pin + 1 Earth	PRICE Open £	Post £
60	149	8.35	0.88	4.37	0.56
100	150	9.15	0.88	4.90	0.64
200	151	11.45	0.88	8.14	0.80
250	152	12.90	0.88	9.80	0.88
350	153	15.50	0.88	11.88	0.95
500	154	17.25	0.88	13.62	1.13
750	155	27.10	1.10	20.59	0.88
1000	156	35.40	1.10	29.15	0.88
1500	157	42.00	1.10	33.37	0.88
2000	158	49.75	2.64	37.10	0.88
3000	159	73.15	2.64	58.55	0.88

MINIATURE & EQUIPMENT

Primary 240V with Screen		MILLIAMPS		TYPE	PRICE £	Post £
Sec. 1	Sec. 2	Sec. 1	Sec. 2	No.	£	£
3-0-3	—	200	—	238	1.50	0.25
0-6	0-6	500	500	234	1.38	0.25
0-6	0-6	1000	1000	212	1.90	0.47
0-9	—	100	—	13	1.40	0.25
0-9	0-9	330	330	235	1.50	0.25
0-8-9	0-8-9	500	500	207	1.93	0.34
0-8-9	0-8-9	1000	1000	208	2.75	0.47
15-0-15	—	40	—	240	1.35	0.25
0-15	0-15	200	200	236	1.38	0.25
20-0-20	—	30	—	241	1.35	0.25
0-20	0-20	150	150	237	1.38	0.25
0-15-20	0-15-20	500	500	205	2.73	0.56
0-20	0-20	300	300	214	1.93	0.47
0-20	—	3500	No Screen	1116	3.30	0.64
20-12-0	—	700	—	221	2.20	0.47
12-20	—	(D.C.)	—	—	—	—
0-15-20	0-15-20	1000	1000	206	3.50	0.56
0-15-27	0-15-27	500	500	203	3.00	0.56
0-15-27	0-15-27	1000	1000	204	3.85	0.56

12 and 24 VOLTS PRIMARY 200-240 Volts.

AMPS	TYPE	PRICE £	Post £
12V	24V	—	—
0-3	0-15	242	1.58
0-5	0-25	111	1.38
1	0-5	213	1.74
2	1	71	2.30
4	2	18	2.96
6	3	70	4.18
8	4	108	4.56
10	5	72	5.20
12	6	116	5.51
16	8	17	7.00
20	10	115	10.42
30	15	187	13.25
40	20	232	14.85
60	30	226	16.83

30 VOLTS

AMPS	Ref. No.	PRICE £	Post £
0.5	112	1.90	0.47
1	79	2.40	0.56
2	3	3.50	0.64
3	20	4.50	0.64
4	21	5.15	0.72
5	51	6.40	0.72
6	117	7.16	0.88
8	88	9.55	0.95
10	89	9.67	0.95

50 VOLTS

AMPS	Ref. No.	PRICE £	Post £
0.5	102	2.58	0.47
1	103	3.48	0.56
2	104	5.03	0.64
3	105	5.81	0.72
4	106	7.58	0.88
6	107	12.30	0.95
8	118	13.20	1.13
10	119	17.02	0.88

60 VOLTS

AMPS	Ref. No.	PRICE £	Post £
0.5	124	2.30	0.56
1	126	3.41	0.56
2	127	5.09	0.72
3	125	7.52	0.80
4	123	8.75	0.95
5	40	9.75	0.95
6	120	11.20	1.01
8	121	15.00	1.19
10	122	18.20	0.88
12	189	18.50	0.88

AUTO TRANSFORMERS

VA (Watts)	Ref. No.	PRICE Cased £	PRICE Plugs 2 & 3 pin £	PRICE Open £	Post £
Tapped at 115, 220, 240 Volts					
20	113	3.85	0.20	1.71	0.47
Tapped at 115, 200, 220, 240 Volts					
150	4	6.38	0.20	4.12	0.56
200	65	7.04	0.20	4.95	0.64
300	66	8.00	0.20	5.81	0.72
500	67	10.99	0.20	8.85	0.88
750	83	13.82	0.85	10.80	0.95
1000	84	17.27	0.85	13.68	1.13
1500	93	21.87	0.85	18.31	0.88
2000	95	33.11	1.60	24.25	0.88
3000	73	47.94	2.10	35.10	0.88

BRIDGE RECTIFIERS

ONEAMP	Price	FOURAMP	Price
50P.I.V.	0.25	100P.I.V.	0.55
100P.I.V.	0.25	200P.I.V.	0.59
200P.I.V.	0.28	400P.I.V.	0.65
600P.I.V.	0.30	600P.I.V.	0.75

SPECIAL OFFER!

2 KVA ISOLATORS
Fully impregnated & screened
2 primary windings 110V each
2 secondary windings 115V each
(2 matching transformers)
£29.50 plus carr. & VAT.

TWO AMP	Price	SIX AMP	Price
50P.I.V.	0.35	50P.I.V.	0.65
100P.I.V.	0.40	100P.I.V.	0.70
200P.I.V.	0.45	200P.I.V.	0.80
400P.I.V.	0.50	400P.I.V.	0.90

POWER UNIT TYPE CC12-05



Output switched 3, 4.5, 6, 7.5, 9 and 12 Volts at 500 mA D.C. Operates from 240 V mains, suitable for Radios, Tape Recorders, Record Players etc. Size 75 x 50 x 14.0 cm. Price £3.95. Post 25p.

NEW! 2" AND 4" PANEL METERS

2"		4"	
SIZE: 60mm High	Wide X 40mm	SIZE: 110mm High	Wide X 43mm
0-50 micro A	1250	0-50 micro A	1400
0-100 micro A	580	0-100 micro A	730
0-500 micro A	170	0-500 micro A	200
0-1 mA	170	0-1 mA	200
0-5 mA	170	0-5 mA	200
0-10 mA	6	0-10 mA	6
0-50 mA	0.5	0-50 mA	0.5
0-100 mA	0.5	0-100 mA	0.5
0-500 mA	0.5	0-500 mA	0.5
0-1 AMP	0.5	0-1 AMP	0.5
0-2 AMP	0.5	0-2 AMP	0.5
0-25 Volt	15K	0-25 Volt	15K
0-50 Volt	50K	0-50 Volt	50K
0-300 Volt	300K	0-300 Volt	300K
VU Meter	170	VU Meter	200
VU Meter	5250	VU Meter	5250

VU Meters are complete with detectors. Modern wide view. Price 2" £3.20 Post 10p. Price 4" £4.00 Post 10p. Lamps 60p per set.

C1000 MULTI-METER

Compact General Purpose Mini Multimeter
Input Resistance 1000 ohms per volt.
Ranges: AC Volts 0-15 50 250 1000 Volts
DC Volts 0-10 50 250 1000 Volts
DC Current 0-1 mA 0-100 mA
Resistance 0-150K ohms
Size 60 x 24 x 90 mm
Complete with: Batteries, Test Prods, Instructions
Special price **£3.30** Post 25p.



1/4-WATT CARBON FILM RESISTORS

also available 1/2 watt at 70°C E 12 range 10Ω-1MΩ. 5% tol. above 470KΩ 10% tol. at 95p per 100.

MINIATURE NEONS

6mm dia., 12mm length leads length approx. 20mm. Recommended ballast resistor 150K ohms for 240 Volt operation. Price: Packet of 10 for 60p. Postage 15p.

PLEASE ADD 8% FOR VAT

A.S.P. LTD.
DEPT WW5, SIMMONDS ROAD, WINCHEAP, CANTERBURY, KENT. Tel: (0227) 52436

Problem.


Where to obtain devices for push-pull audio power amplifiers which give good linearity and don't blow up on the slightest overload.

Solution.

M-OV audio beam tetrodes. A pair of KT66s will give up to 50W and a pair of KT88s will give up to 100W.

And M-OV audio triodes, too: a pair of DA42s gives up to 200W and a pair of DA 100s gives up to 300W.

EEV and M-OV know how.

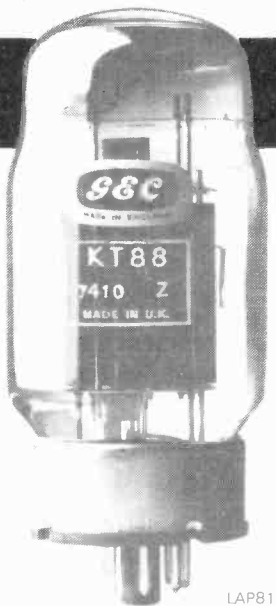


LAP81

THE M-O VALVE CO LTD, Hammersmith, London, England W6 7PE.
Tel: 01-603 3431. Telex: 23435. Grams: Thermionic London **S&C** **E**
WW—134 FOR FURTHER DETAILS

when reliability and quality count
Suppliers of Television Valves, Picture Tubes, Industrial and Transmitting Tubes to the Electronic Industry.

Enquiries from Agents and Importers welcome.

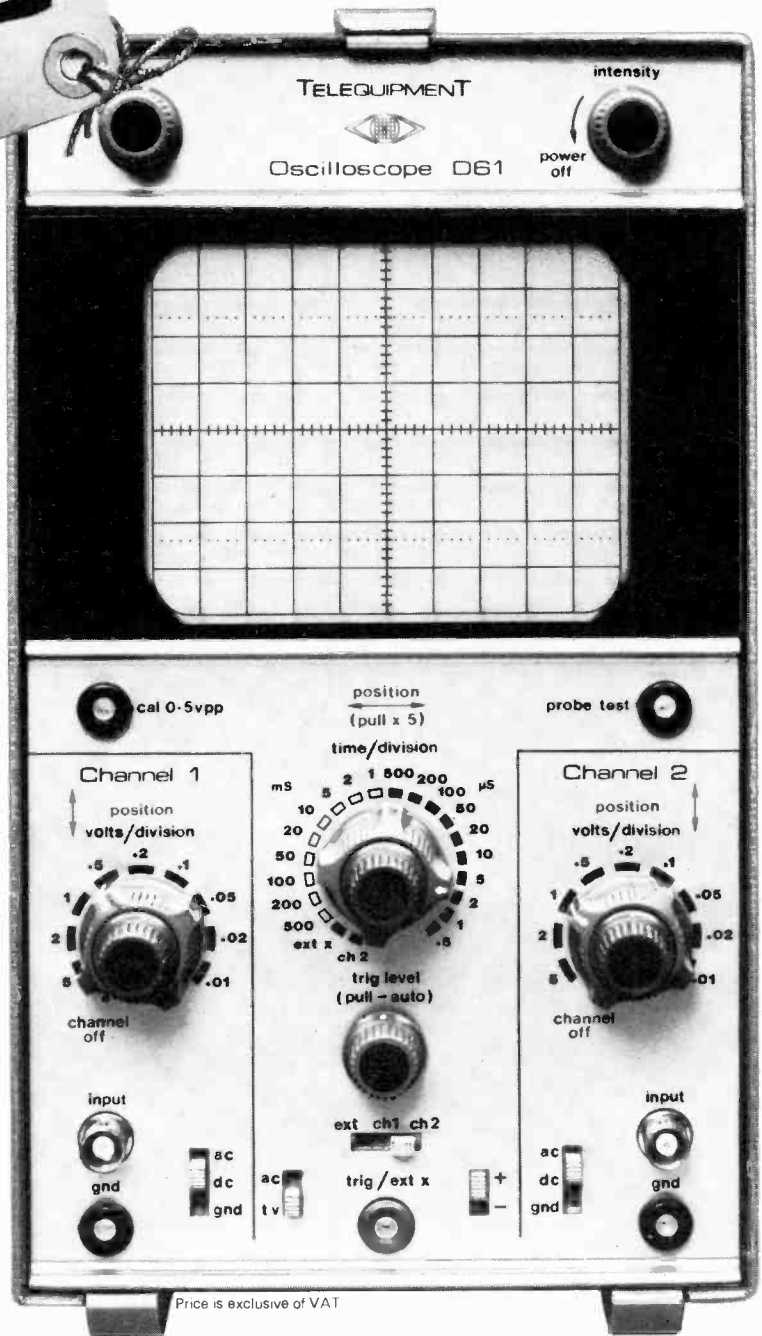EDICRON LIMITED
Redan House, 1 Redan Place, London W2 4SA
Telephone: 01-727 0091/2 Telex: 265531
Cables: Edicron London W2
WW—108 FOR FURTHER DETAILS



...and many more good reasons why Telequipment's D61 offers the greatest scope for your budget

- Like the price, it's small in size 11 x 6¼ x 16½ in. — ideal for the busy workbench.
- Weighs only 14.3lb; not just portable but positively easy to carry.
- Easy to use.
- Can be used as a Single Beam, Dual Trace or an X-Y oscilloscope.
- 10mV Sensitivity at 10MHz.
- Automatically Selects for Chopped or Alternate modes of operation.
- Automatically Selects for TV Line or Frame Displays.
- 8 x 10cm Display Area.
- Nationwide maintenance and user advisory service available.

Already chosen by over 8,000 customers as the best-value-for money dual trace 'scope on the market, the D61 at £138 must be seen to be appreciated.

Write for full details now!



Tektronix U.K. Ltd., Beaverton House, P.O. Box 69, Harpenden, Herts.
Telephone: Harpenden 63141 Telex: 25559

Telequipment gives you more scope for your budget


wireless world

Electronics, Television, Radio, Audio

MAY 1975 Vol 81 No 1473

Contents

- 199 Computers and us
200 Wireless World Dolby noise reducer
205 Books received
206 Tidal-wave warnings from the ionosphere
206 Meetings. Announcements
207 Audio Engineering Society 50th Convention
209 News of the month
Video disc player on the market
Bristol community cable TV experiment closes
Underground rescue radio system
211 A 50MHz oscilloscope by *C. M. J. Little*
215 Literature received
216 Digital synthesis of frequency by *D. C. Ayre and K. G. Woodard*
218 New m.o.s. centre
219 Letters to the editor
Interference from pocket calculators
F.m. tuning indicators
Easier to become a radio amateur?
222 75 years of magnetic recording—3 by *Basil Lane*
226 Circuit ideas
Accurate current generator
Wobbulator
Stabilizing a symmetrical power supply
227 London Electronic Component Show 1975
229 Display devices
235 Noise—confusion in more ways than one—3 by *K. L. Smith*
238 Oscilloscope capacitance meter by *H. v. Z. Smit*
239 HF predictions
240 Coastguard v.h.f. repeaters by *J. B. Tuke*
242 World of amateur radio
243 New products
a79 APPOINTMENTS VACANT
a96 INDEX TO ADVERTISERS

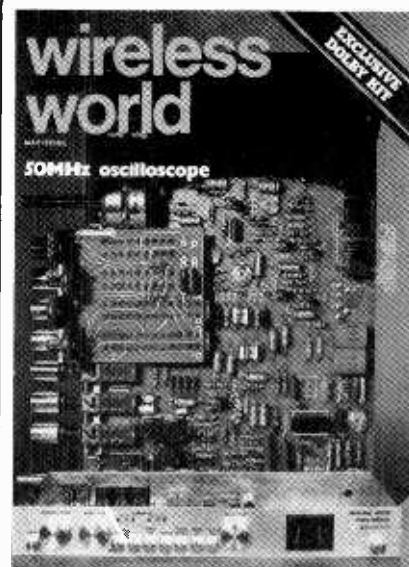

This month's front cover shows the chassis and printed circuit board of the Wireless World Dolby noise reducer. Principle of operation is described in this issue.

IN OUR NEXT ISSUE

Time by radio

A digital clock synchronized to the atomic frequency standard broadcast at 60kHz on MSF Rugby

Wireless World Dolby noise reducer

The second article will deal with the circuitry and construction of this unique audio project

Circuit calculations simplified

Quite sophisticated design can be done with simple arithmetic. Part 1 is on calculating resistance values

Price 30p. (Back numbers 50p, from Room 11, Dorset House, Stamford Street, London SE1 9LU.)

Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.

Telephones: Editorial 01-261 8620; Advertising 01-261 8339.

Telegrams/Telex, Wiworld Bisnespres 25137 London. Cables, "Ethaworld, London SE1."

Subscription rates: 1 year, £6 UK and overseas (\$15.60 USA and Canada); 3 years, £15.30 UK and overseas (\$39.80 USA and Canada). Student rates: 1 year, £3 UK and overseas (\$7.80 USA and Canada); 3 years, £7.70 UK and overseas (\$20.00 USA and Canada).

Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01-837 3636.

Subscriptions: Oakfield House, Perrymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 53281.

Subscribers are requested to notify a change of address four weeks in advance and to return envelope bearing previous address.

© I.P.C. Business Press Ltd, 1975

SIXTY-FIFTH YEAR
OF PUBLICATION



NOW, more than ever,

S

**single
SOURCE
makes
sense**

for **CINCH**

Terminal Blocks
Edge Connectors
Sub-miniature Connectors
Multi-Way Plugs & Sockets

TO MINIMISE INVESTMENTS AND SOLVE STOCK PROBLEMS

You can increase your efficiency, too, by ordering large or small quantities of any one part, or making up an order of any number of assorted small quantities through the United-Carr Supplies service. We can deliver with more than usual promptitude because we carry such large and varied stocks of CINCH, DOT and FT electronic and electrical components. Fastenings and assemblies.

**So, make United-Carr *Supplies* your SINGLE SOURCE
for**

CINCH

DOT

FT

See us on
STAND 401
L.E.C. SHOW

Send now, stating possible requirements, for free and post free catalogue.

United-Carr Supplies Ltd., 112 Station Road, Ilkeston, Derbyshire DE7 5LF.
Tel: Ilkeston 787111 STD 06072 787111. Telex 377117. C.H.F.A.d.

WW-148 FOR FURTHER DETAILS

wireless world

Computers and us

Editor:

TOM IVALL, M.I.E.R.E.

Deputy Editor:

 PHILIP DARRINGTON
 Phone 01-261 8429

Technical Editor:

 GEOFFREY SHORTER, B.Sc.
 Phone 01-261 8443

Assistant Editors:

 BILL ANDERTON, B.Sc.
 Phone 01-261 8620

 BASIL LANE
 Phone 01-261 8043

 MIKE SAGIN
 Phone 01-261 8429

Drawing Office:

LEONARD H. DARRAH

Production:

D. R. BRAY

Advertisements:

 G. BENTON ROWELL (*Manager*)

 A. PETERS (*Classified Advertisements*)
 Phone 01-261 8508 or 01-928 4597

 JOHN GIBBON (*Make-up and copy*)
 Phone 01-261 8353

I.P.C. Electrical-Electronic Press Ltd

Managing Director: George Fowkes

Administration Director: George H. Mansell

Publisher: Gordon Henderson

The "computer on a chip" that we used to talk about ten years ago has now arrived. It is, of course, the integrated-circuit "microprocessor", which, in the space of a cubic centimetre or so and at the cost of a few pounds, provides the central functions of a stored-programme digital computer. Before long this device will be a familiar object in our lives. No doubt we shall see it in cars and washing-machines, in cash registers and petrol pumps, and in a great variety of "distributed processing" applications in industry and commerce. What will its impact be? The average citizen will accept this minor revolution with bland indifference, unaware that once again his mode of life is being subtly changed by technology. The engineer or technically-informed person, though more aware of the potentialities, will display a different form of complacency. Secure in the knowledge that he understands how these things work, how they are designed, manufactured and applied, he will believe that everything is under control. Computers can never exceed the capabilities of those who design and programme them and therefore they can never get out of hand.

These are naive attitudes. Technology has modified the surface pattern of our lives, and hence by introjection our inner selves, since the beginning of man. The Industrial Revolution in Britain changed the mode of life and work drastically and irrevocably. Today the changes tend to creep up and take us unawares. With the computer, for example, while we were worrying that it might usurp human brain power and lead to mass unemployment we did not notice that in one field of use, business and administration, it was subtly changing from a calculating machine into an automated filing system. Suddenly there were "computer banks" that held personal information on us—information we had supplied in tax returns, census answers, and records to do with health, insurance, credit-worthiness, military service and the like. While this information stays distributed in separate computers the threat to privacy and freedom remains a threat. But the danger is that the scattered data could be collated into dossiers. An "identikit" picture of each citizen based purely on data could be used to make decisions about him, without anybody actually speaking to him or telling him that a decision had been made. Remember that this is *technologically* quite possible. To what extent it becomes reality depends on the ability of our ethics to restrain our technology.

Information collated by computers is also being used to make decisions on a national level. Theoretically the administrators' ability to get more data, quicker, should result in better decisions. But there is the hidden danger of the increasing isolation of the decision maker from his sources of data and his decreasing ability to check their validity.

As engineers and technicians we cannot take refuge in the limitations of computers as we see them now. There are certainly inherent limitations to the capabilities of the conventional stored-programme digital computer in its present form, but there are no inherent limitations to computer technology as a whole—consider, for example, the work that is being done on artificial intelligence. At some point we must realize that we are not mere instruments of technological progress. We must stop and ask ourselves what we want to do with these machines and what effect these technological aims will have on the shape and quality of our lives.

Wireless World Dolby noise reducer

1—An introduction to the Dolby noise reduction system

by Geoffrey Shorter

This noise-reducer design is intended mainly for hiss reduction in magnetic-tape recording machines. The unit can be switched to decode commercially available Dolby B-encoded cassette tapes, Dolby B-encoded f.m. radio transmissions (as in the USA), or to encode blank tapes from any source. As an alternative, it can be used in trading some of the noise improvement for reduced distortion at peak recorded levels. The *Wireless World* processor can be aligned without any additional test instruments, the circuit board being arranged to provide the necessary alignment and calibration tones. This article gives background to the B system and to the functioning of the noise reducer and subsequent articles describe construction, alignment and calibration of the unit. A complete kit is available only through *Wireless World* (see panel on page 205)

In audio systems dynamic range can be defined as the ratio of the largest to the smallest programme signal. Dynamic range is typically limited at the high-level end by tape saturation or amplifier signal handling problems: there is usually a fairly well-defined level beyond which compression occurs and distortion rises at a rapid rate. At the other extreme there is a limit on the lowest signal that can be handled, set typically by the noise level of electronic circuits, tape noise, surface noise on discs, or granularity on optical soundtracks.

In concerts, dynamic range can be as high as 90 to 100dB, but once such programme material has been recorded, dynamic range is reduced to 60 or 70dB. (When broadcast the range can be as low as 20 to 40dB.) In this situation there are three options—lose that part of the programme below noise level, distort the peaks, or distort the range by compression either manually or automatically. None of these options is altogether acceptable in itself, all distort the original in some way. What is needed is a way of getting round this limitation of dynamic range without the distortion of overmodulation, without losing programme in noise and without distortion of range. Before discussing various techniques that have been proposed and tried, we will be more specific about what is required.

As well as not introducing any perceptible non-linear or dynamic range distortion of both steady-state and transient signals, any proposed technique for high quality use should not perceptibly alter the signal in respect of frequency response and transient response. Any signal processors must be able to operate to the normal constraints of audio

channels, i.e. operation should not depend on freedom from phase and amplitude versus frequency errors or changes, nor on a linear phase-frequency response; channel overload characteristics should not be worsened. In addition to compatibility with transmission channels, there must be compatibility between processors to the extent that recordings can be interchanged. In reducing perceptibility of noise, there should be no noticeable noise modulation effect and ideally all noises should be reduced by a similar amount, otherwise reducing one kind might unmask another.

Noise-reducing techniques

“Static” methods. The most well-established methods of avoiding the constraints imposed by high noise levels are “static” ones. Examples are the high-frequency pre-emphasis, and subsequent de-emphasis, applied to f.m. broadcasts and gramophone records and the low-frequency pre-emphasis used in tapes. They are static because the amount of emphasis given is fixed and does not take account of the signal in any way. At some frequencies, there is thus an intrusion into the possible range of levels that signals can occupy which may mean that some lower than normal limit must be placed on the programme level.

Single-ended methods. An alternative approach is the dynamic one of altering the level of a signal by an amount that depends on the signal level, at either the sending/recording end or at the listening end. In examining such dynamic techniques it is expedient to look at the possibilities from a steady-state signal level point of view, with the thinking that frequency and time-dependent variations

can be seen as special categories within a level classification. In practice, however, the success of each kind will undoubtedly depend on how well complicated time-varying multi-frequency signal patterns are responded to by the processing circuitry; and to whatever psychoacoustic, or perceptual, effects such as auditory masking, can be discovered and made use of.

The simplest kind of device, within our terms of reference, is the low-level noise gate, depicted graphically in Fig. 1(a), which eliminates signals below a certain threshold level. More useful is a stepped noise gate, where signals and noise below a certain threshold are attenuated by a finite amount rather than an infinite amount—Fig. 1(b). There are a host of variants on this theme, Fig. 1(d) showing another possibility.

A number of commercially-available expanders have used the general approach of Fig. 1(b), including H. H. Scott's “dynamic noise suppressor” and R. Burwen's “dynamic noise filter”, operating only at low and high frequencies and with a passband that varies according to signal level. The Philips “dynamic noise limiter” is another example, though its operation is restricted to high frequencies. With these devices, the bandwidth restriction at low signal levels must inevitably cause some loss of programme. Further, any reduction of noise level that can be achieved is likely to be modulated by intermittent mid-frequency signal components, giving rise to what is called breathing. Because they are “single-ended” these techniques must result in a distortion of dynamic range. Thus you can either have the original dynamic range plus on reduced noise, or a distorted dynamic range and loss of some

low-level information with a reduced noise level—but not both at the same time.

Besides altering the level of low-amplitude signals, a similar expansion can be achieved by expanding high-amplitude signals, Fig. 2(c), but as well as exhibiting the two major disadvantages already mentioned, this would suffer a third. By having a variable-gain element operating at a high level there are obviously greater risks of generating intrusive unwanted signals as a result of overshooting, high non-linear distortion and a high circuit noise level.

Dynamic processing is often carried out prior to recording or transmission. The low-level compression characteristics of Figs. 1(c) and (e) and the high-level characteristic of Figs. 2(a) and (b) both enable average signal level to be increased relative to the noise level. But in themselves they suffer from the same disadvantage as do the expanders. Clearly, single-ended methods are inappropriate to normal high quality reproducing systems.

Complementary methods. The only way of avoiding the difficulty of alteration to dynamic range is by the complementary method—the dynamic equivalent of static “equalization”. In complementary systems, signal processing before transmission and recording, normally compression, is followed by an equal degree of complementary processing, normally expansion, prior to audition so that the original dynamic range is restored. Noise added by the medium after compression is reduced by the degree of expansion used. In the expander of Fig. 1(b) the complementary compressor characteristic would be (c) and the complement of (d) would be (e). Likewise, the transfer characteristics of Figs. 2(b) and (c) form another compander system.

Fig. 1. Low-level noise gate (a) simply loses both noise and signal below a certain threshold level. Finite attenuation of low-level signals is achieved with the expansion transfer characteristics of (b) and (d). Such “single-ended” expanders reduce noise at the expense of distorting dynamic range. Compressors at the signal source end can raise low level signal above noise levels, but similarly distort range (c) and (e).

Fig. 2. High-level limiter and compressors (a) and (b) and expanders (c) suffer an additional disadvantage because of processing at a level where distortions would be more obvious.

Fig. 3. Complementary high-level system (a) is able to reproduce original dynamic range while either reducing maximum level to give more overload margin (b), reducing noise (c), or giving a combination of both.

Fig. 4. Low-level complementary system (a) has the advantage that any distortion products are at a low level where they are less likely to be audible.

Another kind of diagram makes it easier to visualize what happens so far as levels are concerned. Fig. 3(a) is a typified high-level compander characteristic, showing both the compression and expansion curves. Its equivalent level diagram of Fig. 3(b) shows the reduced dynamic range (indicated by arrows) where the maximum level to be handled by the interposing medium is assumed to be the same—the region marked “overload margin” giving an increased margin against overload and thus lower distortion. Fig. 3(a) shows the same reduced dynamic range

produced by the characteristic of Fig. 3(a), but with the intermediate gain shifted so that the low signal levels can be increased in relation to the noise level.

Fig. 4(a) shows low-level compander characteristics, with the level diagram of Fig. 4(b) illustrating the use of the compressed dynamic range to bring up the low-level signals relative to the noise. Fig. 4(c) shows how, by reducing the levels by a constant amount, increased overload margin can be obtained. (Notice the similarity between Figs. 3(b) and 4(c) and between Figs. 3(c) and 4(b), the

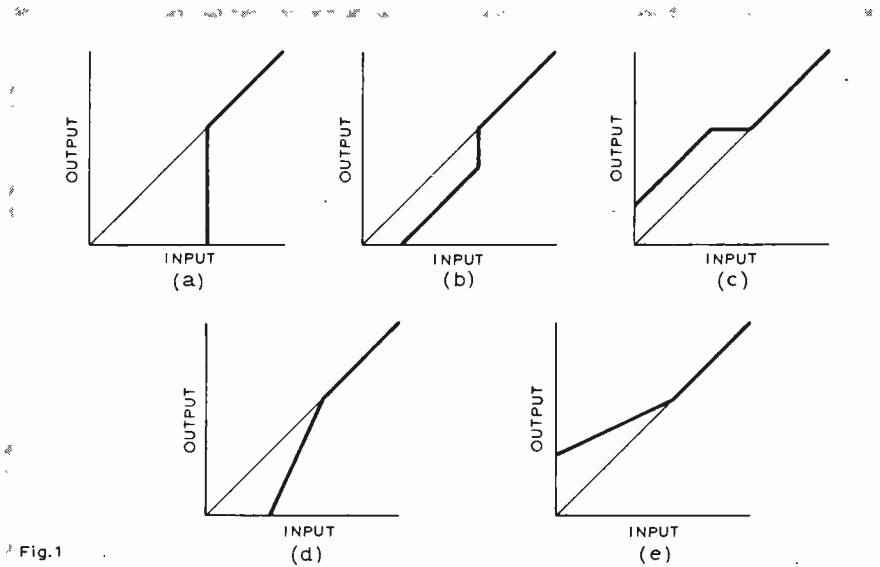


Fig. 1

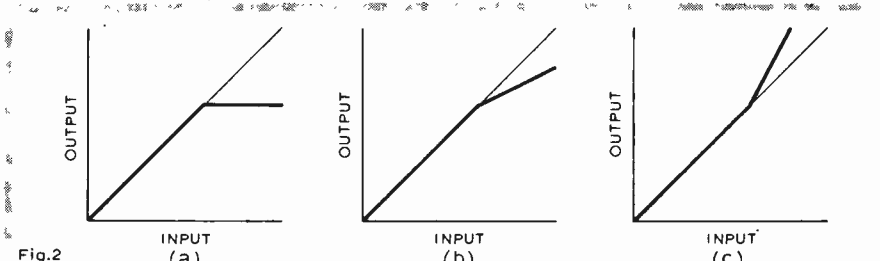


Fig. 2

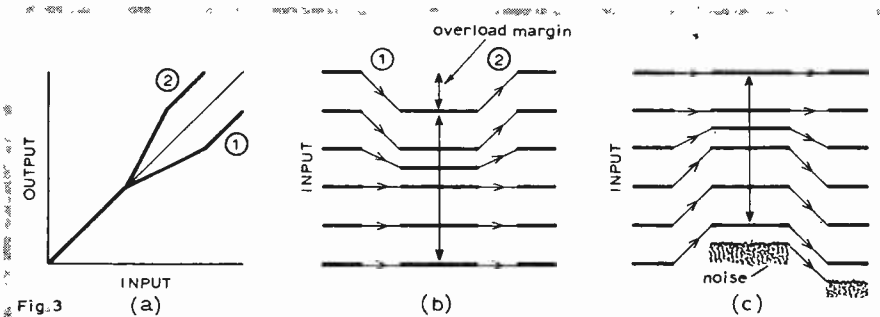


Fig. 3

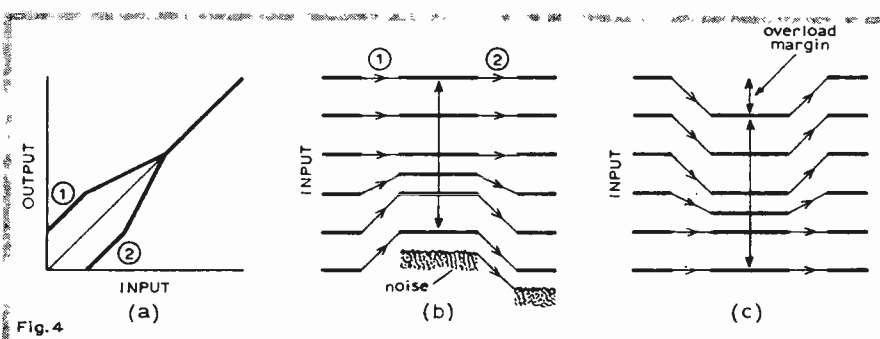



Fig. 4

difference being the siting of the region of "linear" operation at either a high level or a low level. Despite the immediate visual contrast between Figs. 3(a) and 4(a) there is clearly a close resemblance between curves 1.)

In practice the characteristic curves do not have the discontinuities shown, corners being rounded to prevent objectionable noise modulation. The curves should be capable of easy realization, be readily reproducible and the two complementary curves must be matched to within the required tolerance.


Two recently-introduced studio compressors use the general approach of Fig. 2(b) and (c), but with a threshold that is much lower than indicated. The dbx Inc. compressor uses a square-law curve above a certain threshold (-60dBm), which in logarithmic terms is a 2:1 compression ratio. The Burwen "noise eliminator" uses a cubic law (logarithmically, a 3:1 compression ratio) above a certain threshold. (A fixed h.f. pre-emphasis and a level-independent bandwidth are also features of these systems.)

In general, such high level companding techniques suffer from a number of drawbacks: poor tracking between the two processors, high sensitivity to errors in gain in-between processors, overshooting and a risk of overmodulation, both of which could lead to compression in the transmission medium that would go uncorrected on expansion, noise modulation by signals, modulation-product formation as a result of rapid gain changes, all of which are undesirable in a high quality link. High level compressors can be very useful however in telephone circuits for example and the Post Office's Lincom-

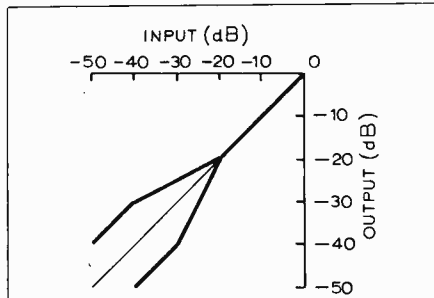

In most electronic signal processing systems there is usually some maximum level beyond which the signal must not be allowed to go and to which levels are frequently referred. Transfer characteristics are therefore usually given in the quadrant shown in which the point of reference is made to be some arbitrary maximum level, rather than the zero signal level of Figs. 1 to 4. (A zero at the axes intersection would represent 0dB and not an origin as in cartesian coordinates.) In practice such curves are not discontinuous but are smoothly connected to prevent unwanted modulation and to permit easy realization and matching.

Fig. 5. Conventional compressors use the equivalent complementary systems of (a) or (b) whereas the Dolby system (A and B) uses an additive to method (c) enabling processing circuitry to be separated from the main signal path.

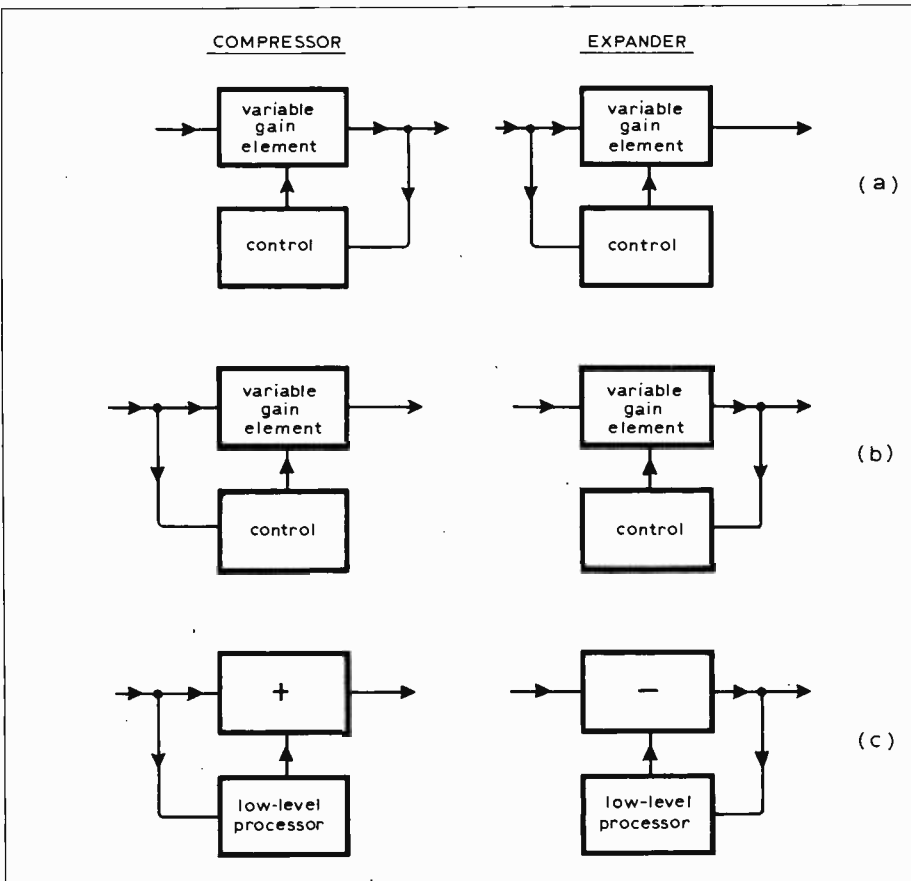

pex scheme is an example of a compressor in which dynamic range is reduced to zero. (Subsequent expansion would not be possible were it not for the fact that information on signal amplitudes is contained in separate pilot or control channel.)

The low-level method (Fig. 4) has a high tolerance of channel gain errors, produces modulation distortion at low signal levels rather than high levels, and there is less risk of overloading the medium. It seems a good idea anyway because one might expect the ear to be less sensitive to low-amplitude effects than to the same effects at high level. This then is the basic companding technique chosen for the Dolby system.

Dolby low-level compressor

In conventional companding systems there are two equivalent ways of achieving compression and expansion. One is to derive a control signal, after subjecting the input signal to a variable-gain element (compressor); expansion or "decoding" would then be achieved by the converse process—the control signal being derived prior to a variable-gain element (expander), Fig. 5(a). The equivalent, alternative, way is to derive the control in the compressor part before the variable-gain element and to subsequently expand by using a control obtained after the variable-gain device, Fig. 5(b). (The first-mentioned method is used in the dbx and Burwen high-level compressors and in the JVC a.n.r.s. low-level compressor.)

The Dolby technique makes use of a different approach—with an important difference; compression is achieved by deriving a special low-level signal that is added to the main signal, and expansion is obtained by subtracting a low-level signal from the main one, Fig. 5(c). (Within the low-level processor block, compression is achieved with method (a).)

Of course, the required compressor characteristics could have been derived in the normal way, i.e. by direct action of a compressing circuit on the main signal path Figs. 5(a) and (b); but in the low-level approach the whole range need not be subjected to processing. It is obviously in the interests of quality that low-level signals be processed separately, leaving the main signal to a linear path whose quality is not restricted by that of the variable-gain path.

Tracking at high levels becomes easier using this low-level approach, and a tracking error due to channel gain variation would occur at an unobtrusively low level. Additionally with this technique, it is found that sufficiently accurate tracking can be maintained using a control derived from peak and average signal values. Thus the elaboration of an r.m.s.-derived control, which would strictly be necessary for channels having a non-linear phase-frequency response, is avoided.

Notice that in the subtractive part of Fig. 5(c), a negative feedback loop is effectively formed in the low-level "contribution" to the main path. Advantage of this is taken in the Dolby system (and in

the JVC a.n.r.s. system) in that an identical network to that used to produce the additive low-level signal at the encoder, can be used in forming the subtractive component at the decoder, merely by inserting the network in the negative feedback loop of a main path amplifier. Among other things this means a single processor can be used for both encode and decode functions by a suitable switching arrangement.

In a wideband compander of this kind having the kind of characteristic at Fig. 4, a low-amplitude signal below the operating threshold would result in the maximum amount of low-level boost being applied, and on decoding the noise level will be appropriately reduced; a high-amplitude signal would result in no noise reduction. Thus an intermittent high-amplitude signal could modulate the noise level, producing breathing (unless high-level signals were present in the same frequency band as the noise. This breathing can occur in any kind of wideband compander, of course).

In the Dolby A system this effect is overcome by splitting the audio band into sections in the additive signal path, each section having its own compression and control circuitry. A high-amplitude signal in one band will not then prevent noise reduction being obtained in bands above and below. Within each band, the presence of a high-amplitude signal is relied on to mask, that is reduce the perceptibility of, noise components close to that signal. Studies of auditory masking show a shift in the hearing threshold in the presence of a (masking) tone, which effect can extend upward in frequency to a considerable extent; downward to a much lesser extent, the amount depending on the level of the masking tone.

When the economics of band splitting are judged against the extent of this masking effect, the amount of noise reduction required, and the value of threshold level in relation to the benefits of the additive technique, it turns out that four bands give a satisfactory compromise of cost versus performance. Splitting the band with 12dB per octave filters in the ranges 80Hz low pass, 80Hz to 3kHz band pass, 3 to 9kHz band pass, and 9kHz high pass would give a uniform 10dB boost (and hence noise reduction) to low-level signals, as determined by setting compression threshold at 40dB below peak operating level. By making the 3 to 9kHz bandpass filter into a high-pass filter, an additional boost is obtained, gradually increasing from about 5kHz to a maximum at 15kHz. The lowest band provides reduction in the hum and rumble range, the second reduces mainly broadband noise, tape print-through and cross-talk, while the upper bands reduce hiss.

Dolby B-type system

The cost and complexity of the A system is not really appropriate to consumer products. Moreover, in slow-speed tape machines in particular the noise spectrum has a different distribution to that occurring in the studio situation, on account of the slower tape speed and thin

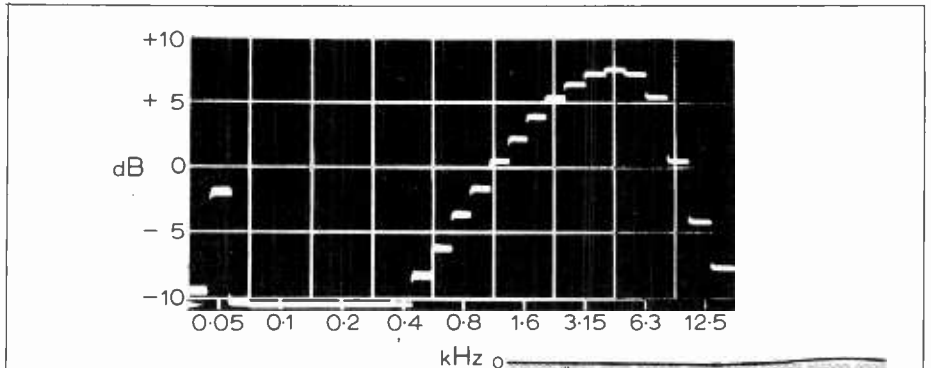


Fig. 6. Noise spectrum of low-noise ferric oxide cassette tape shows problem is a mid- to high-frequency one, rather than a broadband one for which the Dolby A system was developed.


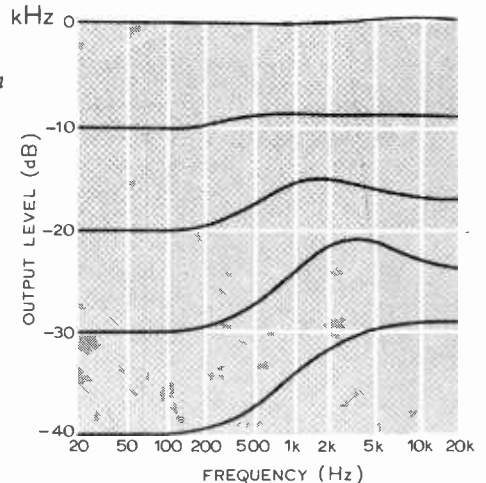


Fig. 7. In the Dolby B and JVC a.n.r.s. systems, low-level high-frequency signals are boosted during encoding by 10dB at low levels, the amount of boost decreasing as input level increases. Characteristics shown are amplitude-frequency response curves, with input level as a parameter, for the encoding process.

Fig. 8. Because the compressor circuit is made frequency sensitive in B-type processors, frequency at which boost, and hence noise reduction, occurs rises with increasing input level. Thus noise reduction is preserved in the presence of mid-frequency signals at high amplitude, which would otherwise reduce or prevent noise reduction. Curves show response below threshold level in presence of 0dB tones.

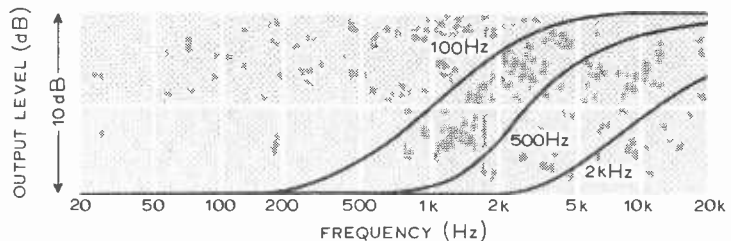


oxide layers used in tape cassettes. Fig. 6 gives a typical DIN-weighted noise spectrum taken from a low-noise ferric oxide tape cassette, showing the noise problem is mainly a mid- to high-frequency one. Noise reduction in the B-type system is therefore limited to this frequency range and Fig. 7 shows the amount of boost (hence noise reduction) applied at various input levels; a fixed high-pass filter placed in the subsidiary signal path, as is done with the JVC a.n.r.s. system, would achieve this end. What, then, about noise modulation which in the A system was reduced to imperceptible amounts by the multiband feature?

In the B system, such a filter prevents high-level low-frequency tones from activating the compression circuit, so there is no noise modulation by l.f. components. But there could still be modulation by high-level signals close in

frequency to the filter cut-off. The trick to avoid this, unique to the Dolby B circuit, is to move the filter passband higher in frequency, so that the high-level signal would then be below the filter passband. The curves of Fig. 8 show the effect of the variable-frequency filter under the influence of a high-level tone at three different frequencies; the lowest-frequency curve representing the lower limit of the combined filter's translation in frequency. As the figure shows, with a high-amplitude tone of 500Hz applied, there is some 8 or 9dB of noise reduction at 10kHz; even with a tone at 2kHz there is still some noise reduction obtained. Had the filter passband remained fixed, these high-level tones would have caused the variable-gain element to operate, resulting in reduced or zero contribution from the subsidiary path, and hence little or no noise reduction.

Fig. 9 shows a simplified block diagram

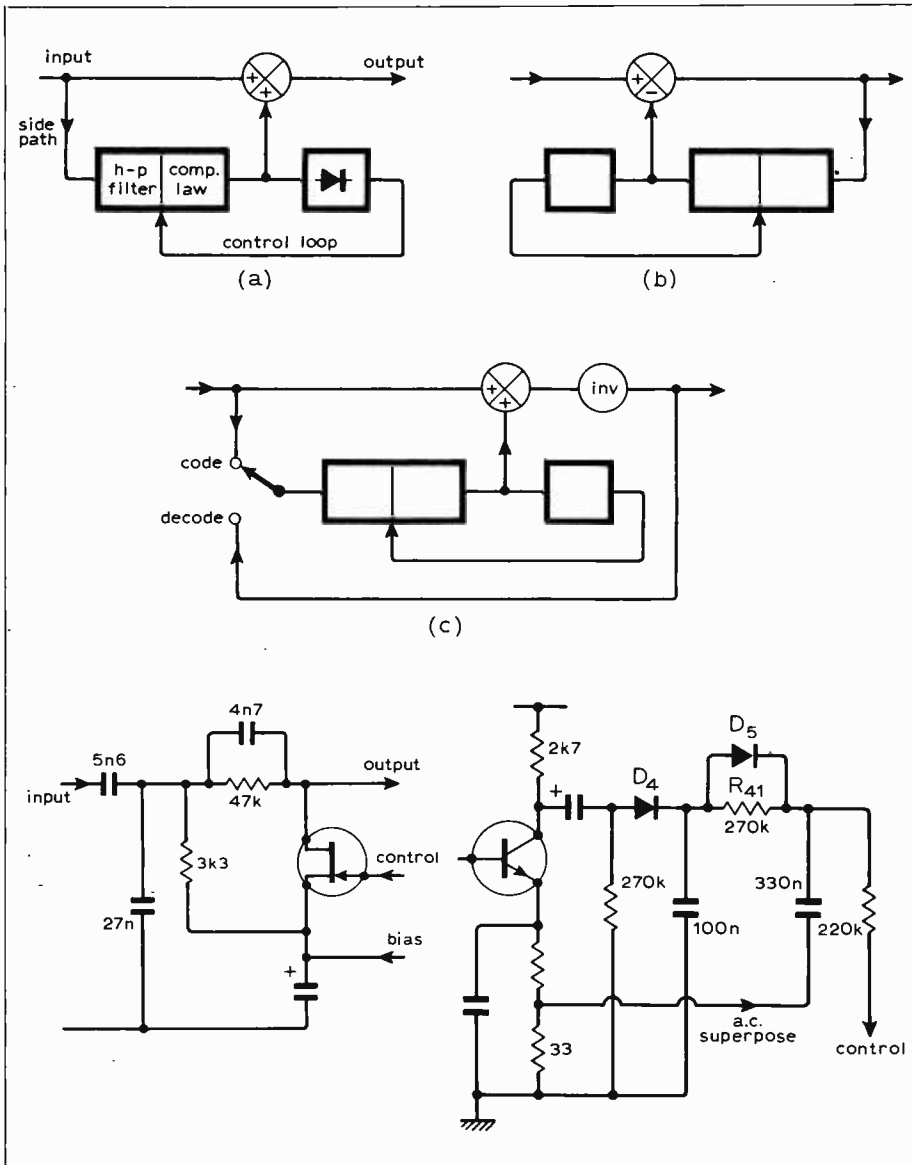

of B-type processors, the encoder at (a), and the decoder at (b) with the same filter and compressor circuitry now in a negative feedback loop. In (b) a phase inversion is clearly required, which in (a) it is not. A simple dodge, that leads to a simplified encode/decode switching arrangement, is to re-site this phase inverter in the main signal path after the summing amplifier. The inverter can now remain in-circuit permanently, forming part of the feedback loop only during decode, Fig. 8(c).

Circuit operation. The way in which the voltage-variable filter and compressor operates is interesting. A fixed high-pass filter, formed by the parallel combination of the 5.6 and 27-nF capacitors (fed from a low impedance source, they are effectively in parallel) and the 3.3kΩ resistor determines a turnover frequency of 1.5kHz (Fig.10). Imagine that a simple compressor then follows, i.e. a variable attenuator formed by a fixed resistor and the f.e.t. voltage-variable resistor (ignoring the 4.7nF capacitor). The f.e.t. is to be controlled by a direct voltage obtained after rectification of the signal passed by the filter/f.e.t. combination. Without any direct voltage applied to the f.e.t. gate, as would be the case for inputs of any level below the filter passband and

for low-level inputs within the passband, the f.e.t. resistance is nominally infinite. The filter circuit would thus give minimum attenuation of h.f. signals and pass them to the main path, allowing h.f. noise reduction to be obtained. When an h.f. input is of sufficiently high level for the control signal to overcome the f.e.t. bias (this determining the compression threshold), the direct voltage to the gate would cause the f.e.t. resistance to fall, attenuating the signal, and reducing the amount passed to the main path. As the h.f. signal increased, a progressively smaller amount would be returned to the main path. Operation of this principle is shown by the curves in Fig. 7(a), which in fact apply to the Dolby B and a.n.r.s. circuits.

By replacing the fixed resistor with a capacitor (4.7nF) in series with the f.e.t. resistance a second, variable, high-pass filter is formed. With increasing f.e.t. gate voltage, actioned by an increasing signal frequency and/or level, the filter characteristic rises in frequency, "overtaking" the fixed filter curve to largely determine a new, higher, passband (after equilibrium between signal level control and filter is reached). Thus the frequency at which a significant signal is returned to the main path is raised, as depicted in

Fig. 9. Characteristics of Fig. 8 are realized by a voltage-controlled filter and compressor which adds up to 10dB of subsidiary signal to the main path during encoding (a). In decoding, a similar network is used to subtract from the main path (b), the network forming part of a negative feedback loop. This loop means that identical networks can be used for encoding and decoding. By placing the phase inversion in the main signal path, as shown (c), it can be left permanently in-circuit, simplifying encode-decode switching.

Fig. 10. Output of high-pass filter decreases after the compression threshold, set by gate bias, has been exceeded by the control signal. Response curve of combined fixed and variable filter sharpens when the two turnover frequencies coincide.

Fig. 11. Control-loop integrator has variable attack and decay times depending on speed and amplitude of signal changes. Large transients cause D₅ to conduct, shortening loop response time. Superposition of a.c. signal on control loop is to allow f.e.t. to operate symmetrically, thus keeping second harmonic distortion to a low level.

Fig. 8, preserving some h.f. noise reduction in the presence of mid-frequency signals. In the region where the two filter curves are close, the combined filter shape is sharpened to around 10dB/octave, so the effect of the filter action is heightened in this region, and the immunity of the circuit to noise modulation therefore improved.

Dynamic operation

To avoid modulation products being generated by rapid changes of gain in the compressor, which may or may not be cancelled in the complementary expansion process, a long attack time is desirable in the rectifier circuit providing the f.e.t. control voltage. On the other hand, a short attack time is needed to minimize the effect of overshoots, which could have an amplitude equal to the amount of compression.

The extremely elegant solution chosen is to use a time constant that depends on the rate of change of signal. Referring to Fig. 11, the 2.7-kΩ collector resistor and the 100-nF capacitor allow rapid following of a slowly changing input signal. But the time constant of the 270kΩ (R₄₁) and 330-nF component gives an attack time for the control signal of 100ms—long enough to prevent audible modulation products being formed. Diode D₅ is not brought into conduction because the voltage drop across it is never large enough (the discharge time of the 100-nF path being shorter than through the 330-nF capacitor). For large transient changes of input signal the potential across the 100-nF rises faster than that at the 330-nF capacitor so D₅ conducts, reducing

Noise reducer kit



Complete kits for the *Wireless World* Dolby B noise reducer are available through the address given below. The two-channel design features:

- a noise reduction of 10dB at 5kHz and above
- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for

alignment

- suitability for both open-reel and cassette tape machines

The kit includes:

- complete set of components for a stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, two meters, front panel, knobs,

mounting screws and nuts

Price is £37.10 inclusive.

Calibration tapes are available, costing £1.94 inclusive for 9.5cm/s open-reel use and for cassette (specify which).

Send cash with order, making cheques payable to IPC Business Press Ltd, to:

Wireless World noise reducer
 General sales department
 Room 11, Dorset House
 Stamford Street
 London SE1 9LU

attack time to around 1ms or less. Between these two extremes charging of the 330-nF capacitor is shared by D_5 and R_{41} , as determined by the p.d. across them.

While the effects of transients are limited by the variable attack time, high amplitude transients require more rigorous treatment. Overshoots, as a result of the control loop not operating quickly enough, are limited to a maximum amplitude of 2dB by two silicon clipper diodes. When added back to the main path the clipped subsidiary signal can result in a momentary distortion of 1%, lasting for around 1 or 2 ms, but this occurs at a time when, because of the casual transients in the main path, the ear is least susceptible to it.

As with attack time, recovery time is as much a problem—it must be so short that noise reduction immediately following a high amplitude signal is restored within the time the ear takes to recover its normal hearing threshold, but not so short that low-frequency or modulation distortion results. The circuitry ensures a 100-ms decay time normally, but for large sharp reductions in signal level this value is reduced.

In Fig. 11 there is a proportion of a.c. signal from the emitter resistors superimposed on to the direct control voltage. This is to maintain symmetry of operation in the f.e.t. and thus keep second harmonic distortion to a low level by ensuring that

$v_{gd} = v_{gs}$. Therefore an a.c. signal is applied to the gate that is half the value of that at the drain. By this means, and by keeping the signal voltage at the f.e.t. low by the capacitance divider prior to the f.e.t., distortion is reduced from a peak of 0.5% to 0.05% (at 1.5kHz and -15dB).

This simplified introduction to noise-reducing systems should help in understanding operation of the B-type circuit, to be given in next month's issue in full.

To be continued.

Acknowledgement. We wish to thank Dolby Laboratories Inc. for their co-operation in developing this *Wireless World* design and particularly Ian Hardcastle for his valuable assistance.

Books Received

The latest editions of the D.A.T.A. book series are now available, covering **transistors, semiconductor diodes, digital integrated circuits, linear integrated circuits and semiconductor applications** notes. Other annual publications in the series include those on semiconductor heat sinks, sockets and associated hardware, discontinued integrated circuits and **discontinued transistors**. Each book lists the majority of devices currently available, throughout the world, together with their relevant parameters. London Information (Rowse Muir) Ltd, Index House, Ascot, Berks SL5 7EU.

Radar Precision and Resolution by G. J. A. Bird is aimed at providing the practising engineer with an understandable treatment of the radar uncertainty function together with a foundation of the underlying transform theory. Chapters include signal processing methods, Laplace and Fourier transforms, Hilbert transforms and complex analytical signals. Much of the book comprises mathematical treatments and worked examples with diagrams and graphs where necessary. The text concludes with a series of appendices which define terminology used in the book. Price £5.80, cloth. Pp.160. Pentech Press Ltd, 8 John Street, London WC1N 2HY.

Tidal-wave warnings from the ionosphere?

Tidal waves have nothing to do with tides. They are generated by undersea earthquakes: a sudden fall in sea-floor level due to an earth slip transfers energy to the water above. This propagates as a long-wavelength high-speed water wave. In a ship on the ocean the wave may pass unnoticed because, even if the amplitude is great, the gently sloping wavefront makes no impact. When the wave strikes the shore, however, there is a devastating inrush of water. Nowadays geophysicists call this type of wave by its Japanese name, tsunami ("harbour wave").

The islands which form the state of Hawaii are at great risk from tsunamis since they lie in the middle of the Pacific Ocean, which is ringed by earthquake zones. A tsunami warning system for such an area is very desirable, provided that it is reliable and does not give a lot of false alarms. For some time seismologists have attempted to give tsunami warnings, making use of the fact that the earth slip which causes the wave also sets up a Rayleigh surface wave through the sea floor. This travels about 20 times as fast as the tsunami and in principle, with the distance involved, could give the people of Hawaii at least a few hours warning.

Unfortunately the Rayleigh wave is small and of very long period. This makes it difficult to pick out from all the seismic noise which seismometers register all the time. For this reason a new, indirect method of detecting the Rayleigh wave is of great interest since it seems to offer a cheap and reliable way of doing the job. It has been developed by workers at the department of electrical engineering at Hawaii University and in principle involves little more than the monitoring of standard frequency transmissions in the area.

The method is possible because the Rayleigh wave on the sea floor disturbs the water above. The change of sea-floor level in effect lifts the sea surface over a wide area. The sea surface then acts as a huge piston or diaphragm and sends a very-low-frequency acoustic wave (period 30-200 seconds!) upwards into the atmosphere. When this wave reaches the ionosphere it causes a change in the refractive index to radio frequencies. The corresponding changes in the path length of reflected radio wave causes phase delays which are detectable, when the reflected radio waves return to earth, as Doppler frequency shifts. The shift may be small (1Hz for a 5 or 10MHz transmission) but detectable if the transmitted frequency and receiver local oscillator are stable enough. In the Hawaii experiments the local standard frequency transmitter WWVH was used, with monitoring receivers on three islands. Observed Doppler shifts were found to correlate well with seismic records of known earthquakes.

The beauty of this indirect method of tsunami detection lies in the fact that the atmosphere both amplifies the acoustic wave and filters out short-period noise. Amplification is the result of decreasing air pressure with altitude, which lengthens the wavelength, and also of the fact that a small change of refractive index of the ionosphere makes a big difference to the path length of a reflected radio wave. Low-pass filtering happens because acoustic waves do not propagate well if the mean path of air particles is comparable with the acoustic wavelength. In the thin air of the ionosphere this discriminates in favour of very-long-wavelength acoustic waves.

Meetings

LONDON

1st. IEE—Discussion on "Engineering management decisions in the current economic climate", at 17.30 at Savoy Pl., WC2.

1st. RTS—"Methods of digital coding for television transmission," by I. F. Macdiarmid, at 19.00 at London Weekend Television South Bank TV Centre, Upper Ground, SE1.

6th. IEE/I.Phys.—Colloquium on "Laser instrumentation", at 10.30 at Savoy Pl., WC2.

6th. IEE—"Motor car performance: acquisition and analysis of road vehicle service data," by Dr M. T. G. Hughes, at 17.30 at Savoy Pl., WC2.

7th. IERE—Colloquium on "Millimetric wave propagation", at 14.00 at 9 Bedford Sq., WC1.

7th. IEE/IERE—"Electromagnetic flowmeter design," by Dr D. Wyatt and Dr J. Hemp at 17.30 at Savoy Pl., WC2.

8th. IEE/IERE—Colloquium on "Patient monitoring", at 10.30 at Savoy Pl., WC2.

9th. IEE—Colloquium on "Breakdown phenomena and influence of electrode surfaces in high pressure gases", at 10.00 at Savoy Pl., WC2.

9th. IEE—Colloquium on "Handling information in the day-to-day running of large service organisations", at 10.30 at Savoy Pl., WC2.

9th. IEE—"Motor car performance: acquisition and analysis of road vehicle service data," by Dr M. T. G. Hughes, at 17.30 at Savoy Pl., WC2.

12th. IEE/IERE—Colloquium on "Computer simulation of communication systems", at 10.30 at Savoy Pl., WC2.

13th. IEE—Discussion on "Transducers for measuring electrical alternating quantities", at 14.00 at Savoy Pl., WC2.

13th. IEE—Colloquium on "Civil applications of underwater acoustics", at 14.30 at Savoy Pl., WC2.

13th. AES—"Measurement of loudspeaker dynamic performance", by Roger C. Driscoll, at 19.15 at the IEE, Savoy Pl., WC2.

14th. R.I.Nav.—"Navigation for fishing craft", by Gregory Haines, at 17.00 at the Royal Institution of Naval Architects, 10 Upper Belgrave St, SW1.

14th. IEE—"Spark ignition in the automobile", by C. Bowden, at 18.30 at Savoy Pl., WC2.

15th. IEE—"The INTELSAT system after 10 years", by D. J. Withers, at 17.30 at Savoy Pl., WC2.

15th. RTS—"Television cameras—how light, how small?" by W. P. Vinten at 19.00 at London Weekend Television South Bank TV Centre, Upper Ground, SE1.

20th. IEE—Colloquium on "Solid state scanning", at 14.30 at Savoy Pl., WC2.

21st. IERE—Colloquium on "The CEI Examination and the Colleges", at 14.30 at 9 Bedford Sq., WC1.

21st. IEE—"Electronic aids for the detection and prevention of crime", by G. Phillips, at 17.30 at Savoy Pl., WC2.

22nd. IERE/IEE—Colloquium on "Distributed information systems", at 14.30 at 9 Bedford Sq., WC1.

28th. IERE—Colloquium on "Recent developments in high quality sound", at 14.00 at the Engineering Lecture Theatre, University College, Gower St, WC1.

28th. IEE—"Electronics in medicine," by Dr D. W. Hill at 17.30 at Savoy Pl., WC2.

BEESTON

6th. IEE—"Feedback—the history of an idea," by Prof A. G. J. Macfarlane, at 19.00 at The Nurseryman, Derby Rd.

LIVERPOOL

9th. IEETE—"Modern trends in sound reproduction," by speaker from the GEC at 19.30 at MANWEB Social Club, Thingwall Road.

BRIGHTON

13th. IEE—Discussion on "I am an engineer", at Sussex University.

GLASGOW

8th. SERT—Section AGM and "The certificate of competence in colour television servicing," by A. J. Kenward at 19.30 at Weir Hall, Institution of Engineers and Shipbuilders in Scotland, Rankine House, 183 Bath St.

BIRMINGHAM

21st. SERT—"Modern technology in the service of the police, including the new Birmingham computerized command and control system," by A. T. Burrows at 19.00 at the Byng Kenrick Suite, University of Aston, Gosta Green.

NEWCASTLE

19th. IEE—"Electronics in the service of music", at 17.45 at the University.

Tickets are required for some meetings: readers are advised, therefore, to communicate with the society concerned.

Announcements

Bib Hi-Fi Accessories Ltd have moved to new premises in Wood Lane End, Hemel Hempstead and the new address is: PO Box 78, Hemel Hempstead, Herts HP2 4RH. Telephone Hemel Hempstead 61291.

"Industrial Instrumentation" is the title of a one-week course which is being organised by the Electronics Division of the Institution of Electrical Engineers (IEE) to take place at the University of Sussex, Brighton, between July 21 to 25, 1975.

A one-day seminar organised by Sira Institute and devoted to "The role of market research in product planning in the instrument industry" will be held at The City University, London EC1 on May 7, 1975. The seminar is designed to interest staff within companies manufacturing instruments and other high-technology products, who are new to market research techniques or who want to brush up their knowledge of them.

The proceedings of the 2nd European Electro-Optics Conference are now available on application to the publishers and organisers, Mack-Brooks Exhibitions Ltd, 62-64 Victoria Street, St. Albans, Herts. The 400-page hard-covered publication contains 50 papers and 18 abstracts of papers first presented at Montreux, Switzerland in April 1974.

Waycom Ltd, Wokingham Road, Bracknell, Berkshire RG12 1ND has successfully concluded negotiations for an exclusive UK marketing agreement with the AVX Corporation of America, manufacturers of monolithic ceramic capacitors.

Tony Chapman Electronics Ltd, 80 High Street, Epping, Essex CM16 4AE, have been appointed exclusive representative, in the UK, of the Vari-L Company, Inc. of Denver, Colorado, USA. Vari-L manufacture wideband signal processing components such as double balanced mixers, transformers, hybrid power dividers/combiners and variable inductors.

Audio Engineering Society 50th Convention

A report on the papers heard and products seen by two of our editorial staff

Part 1: by W. E. Anderton

Not a great deal of equipment on view at the exhibition was new to visitors, but the majority was of exceptionally high quality, reflecting the standard of modern technology in the field of audio engineering. Among the new items, Quad were showing a prototype of their power amplifier—to be launched during the autumn. No specification is available yet, but the continuous output power is rated at 100W per channel. The output stage of this power amplifier was the subject of a paper presented at the convention, “Current Dumping Audio Amplifier”, by P. J. Walker and M. P. Albinson of the Acoustical Manufacturing Co. The paper described the operation of an output stage design in which linearity of the main current-carrying output transistors has no bearing on the overall amplifier performance, hence the need for biasing and allied problems associated with crossover are eliminated. “The solution presented in this paper relies on the fact that a low-powered amplifier of one or two watts does not have the same restrictions as one of higher power. It can be simple class A, for example, and the higher cut-off frequencies enable a wide bandwidth to be obtained. Thus we start by providing a low-powered, high-quality amplifier of well defined mutual conductance capable of the full output voltage swing but with limited current capability. Next we arrange that current drawn by the load turns on heavy-duty current-dumping transistors which then carry the major part of the output current. This dumping current is separately monitored and fed back to the common input. The amount of feedback is such that the mutual conductance is the same whether or not the current dumpers are operating.”

The Dolby cinema units, 364 Cinema Noise Reduction Unit and E2 Cinema Equalizer were on view. Used together, the two permit cinemas to reproduce Dolby-encoded optical sound tracks with high accuracy. The model 364 contains accurate electrical reproducing characteristics for all optical and magnetic sound tracks, selected by push-buttons. The E2 provides four independent types of adjustment: gain adjustment to match projector output to the 364 and to match input requirements of the theatre power amplifier; high-

frequency adjustment to correct sound-head aperture loss; separate high-frequency and low-frequency adjustments for the overall theatre sound system; and 27 independently adjustable level controls for narrow-band filters.


The Bruel & Kjaer phase meter type 2971 was on demonstration. This instrument, released several months ago, gives direct phase indication from a digital display in degrees and radians or an analogue meter display in radians. Triggering can be achieved on positive or negative going waveform slopes. The instrument's frequency range is 2Hz to 200kHz and signal voltage range is 10mV to 15V with “out-of-range indication”. A d.c. output proportional to phase angle is available and there is also a digital output for use with tape punch or computer systems. If the meter is to be used for relative phase measurements as, for example, in measuring the phase response of a loudspeaker, it is necessary to use the meter in conjunction with a delay line. Other uses include checking the phase characteristics of filters, amplifiers and transformers, mechanical impedance measurement, determination of loss factor and hence the complex modulus of material samples, trim-balancing aircraft

jet engines and general phase measurement of electrical signals.

The latest professional Ampex video recorder was on demonstration during the week. This is the AVR-2 which has an extended range, digital timebase corrector to eliminate drift and offer a wider correction window and contribute to a fast lock-up time—one second in NTSC, two seconds in PAL/SECAM. Ampex credit the fast lock-up time to the timebase corrector, a direct-coupled printed-circuit capstan drive, the new Mark XV video head and the digital servo systems. All the electronic sub-systems are constructed on a modular basis for easy maintenance.

Lecture notes

An all-day session on loudspeakers revealed several interesting and controversial papers. “Loudspeaker evaluation using digital techniques”, by J. M. Berman, and “Loudspeaker system simulation using digital techniques”, by L. R. Fincham, presented a method of testing loudspeakers to obtain amplitude and phase responses derived from a unit impulse input. Automatic Fourier analysis is necessary for the system to be practical in terms of the length of time taken for measurements. By

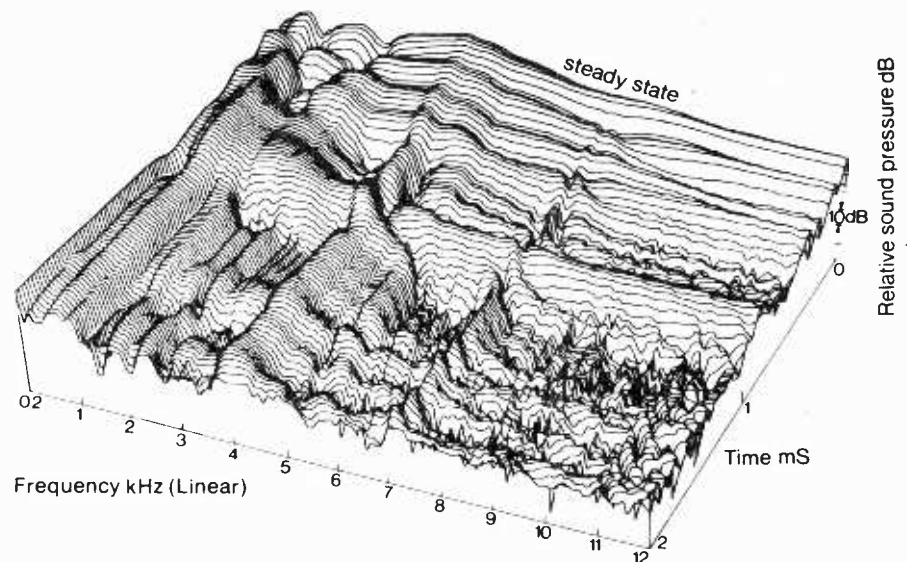

Example of a loudspeaker's cumulative display amplitude spectrum—see text.

using an averaging and correlation technique to eliminate noise, the testing can be done without the need of an anechoic chamber. It is also possible to display cumulative display spectra. Similar analysis to that in obtaining the amplitude frequency response can also be carried out but measured at narrow intervals of time after the initial impulse has been received by the measurement microphone. The result, which can be displayed on a visual display unit, has x- and y-axis of amplitude versus frequency, but also a third z-axis representing time to show the pattern of build-up and decay of resonances in the loudspeaker. We hope to publish more details on this system in the near future.

Still on the subject of loudspeaker testing and performance, R. C. Driscoll in his lecture "Narrow-band transient test function", described the development of a test signal whose frequency spectrum can be defined within definite limits that can be varied to order. The idea is to view a selected, limited frequency spectrum produced by the loudspeaker under test so that effects within a single, or between two or more, bands can be observed. The test signal was derived from the observation that the transform from time to frequency domain of a square pulse produced a spectrum envelope $\sin\omega/\omega$. By using the notion of Fourier pairs and producing a function $\sin\omega/\omega$ in the time domain (not easy!), and then transforming this, a frequency spectrum whose "shape" is that of a square "pulse" is obtained. Refining the system allows the width of this defined spectrum pulse to be varied and also the repetition rate. We look forward to hearing the results of this research work, which overcomes the problems of swept sine-wave testing (individual frequencies tested only) and noise measurements (*fixed* bands of frequencies tested only).

In his lecture "Influence of loudspeaker cabinet walls", H. D. Harwood revealed that doubling the thickness of a cabinet material to reduce colouration could often, surprisingly, make the colouration worse. Several materials used for cabinet construction had been examined during a period of research.

A presentation entitled "Loudspeakers—the Missing Link", by E. Baekgaard, stirred up a discussion on the audibility of phase distortion. The problem has not yet been resolved.

Several papers on digital techniques in audio were presented. "A multiplex stereo decoder with automatic phase error correction", by M. J. Hawksford, described a sub-system which continually monitors and corrects inherent phase errors whether these are generated at source, during reception or within the decoder. "Digital on-line audio processing", by K. Bäder, B. Blessar and R. Zaorski, gave an introduction to the techniques behind the design of digital equipment used in audio processing.

Two interesting papers were presented during the so-called Pop Forum. "Pop Music studios in German Radio; acoustics and recording techniques", by E. J. Volker and F. Moehrke, examined four studios—

Norddeutscher Rundfunk in Hamburg, Südwestfunk in Baden-Baden, Westdeutscher Rundfunk in Köln and Hessischer Rundfunk in Frankfurt. "Multitrack recording techniques", by P. E. Brown, was a retrospective talk on the historical development of this subject up to the present day.

Government sponsors

Strathearn Audio is a new company which has been established on a major scale by the Northern Ireland Finance Corporation (a government body) providing production facilities in Belfast and international marketing headquarters in London. Two papers presented by this company described the theory behind the first product launches planned for later this year. The first paper entitled "A novel planiform loudspeaker system", by R. C. Whelan, described a mid-range and high-frequency transducer operating an electrodynamic motor system as applied to a plane radiator (in this case a thin, flat strip of mylar is used as the plane radiator). A conductive ribbon is attached along the centre of the diaphragm and has a series of permanent magnets assembled along its length. It was shown that the strip dimensions could be made consistent with the required sound pressure levels and efficiency. Further, if the unit were operated with its long axis vertical, acceptable dispersion could be achieved.

The second paper, "A new direct-drive turntable with parallel tracking arm", by K. D. Ridler and J. H. Pope, contained several new developments. We are hoping to publish detailed information on this system in a future issue. The prototype appears to be true "state of the art" but two novel features include a ring of l.e.d.s for observing fine-speed adjustment and a system of Helmholtz coils and magnet coupled to the short pickup arm whereby tracking weight can be adjusted without any clumsy mechanical operation and can be done while a record is actually playing. The motor and suspension of this turntable are both worthy of explanation in detail but space does not permit.

All in all an excellent convention—our congratulations to exhibitors, lecturers and especially the organizers.

Part 2: by B. Lane

As mentioned previously, there was little new equipment on view in the exhibition (except perhaps the Playboy Bunnies on the AKG stand!) but one particular item noticed, directly related to an unannounced paper by P. A. Fryer of Rank Radio International. This was a signal gating system used for delay gating the output of a

measurement microphone. This device is used to examine the output of a loudspeaker for a specific period of time, after a precise interval timed from the cessation of the electrical input to the loudspeaker under test.

The measurement technique is designed to provide an amplitude versus frequency plot of a loudspeaker output, for different intervals of time delay. Dr Fryer's findings indicated that delayed resonances with a Q of between one and five were considerably more noticeable than those of high values of Q .

In a paper entitled "The elimination of scratch noise from 78 r.p.m. recordings", and read by Dr Peter G. Craven of the University of Oxford, an electronic system, using the vertical component of the record groove modulation, is used to identify the presence of scratches. This information is then applied to a sample and hold circuit which will switch the lateral information which contains the wanted information. Records are tracked with a stereo pickup cartridge and the output decoded, using a matrix to provide the required information for the sample and hold circuit. Dr Craven pointed out that the system was most effective on early electrical recordings rather than on the more complex acoustic versions.

Duplicating musicassettes

A particularly intriguing paper was jointly read by G. W. R. Taylor and D. L. Watson, Mr Taylor heads the development laboratory at EMI tape and Mr Watson is associated with the development laboratories of EMI records. The two presentations related to the improvement of high-speed duplicated musicassettes.

The introduction related to improvements in the quality of duplicating tapes produced by EMI, namely Type 152 for C60 and Type 161 (C90). It was demonstrated that with the improvement in performance, a reduction in intermodulation distortion occurred and it was possible to make use of the improved high-frequency short-wavelength performance to offset duplicating losses.

Complementing this performance improvement, Mr Watson pointed out that getting the best out of cassette duplication involved considerable care and expertise. In this he particularly referred to the problem of dynamic range and noise. Dangling a "carrot" before his audience, Mr Watson announced that EMI Records had been able to effect significant improvements in this direction by the development of a new electronic circuit which was the subject of a patent application. The demonstration that followed was a comparison between disc and duplicated cassette using the same original recording. Differences were negligible, indicating that the claims made are of quite a remarkable nature.

As a final note, further information concerning the availability of a bound book containing the papers presented at the convention can be obtained from the society's secretary at 1 Crown Close, Orpington, Kent VR6 6JP.

News of the Month

Video first

The video disc player developed by AEG-Telefunken, Teldec of Hamburg and Decca (London) was launched on the West German market on March 17. The machine, which is now known as TeD (Telefunken Decca), was originated in 1965 and first demonstrated in Berlin on June 24, 1970. It uses a thin, flexible plastic disc with hill-and-dale recording at a pitch of around 280 grooves per mm and revolving at 1500 r.p.m. A diamond stylus and ceramic transducer detect the vision and sound signals, which are then modulated on a u.h.f. carrier and passed to the aerial socket of an ordinary receiver. TeD has been developed to the PAL colour standard for sale in German-speaking areas at first, but NTSC and SECAM versions have also been produced. Fifty programmes are available on discs costing as little as £2 and lasting up to ten minutes. It is claimed that by the end of the year, there will be more than 350 programmes. Handling of the discs will not be a problem, as they are "posted" into the machine still in their sleeves, the record being extracted and inserted again automatically, so that the disc itself is not under attack by dust or greasy finger marks. The discs are 0.1mm thick, 21cm diameter and weigh 5g.

The price of the machine in Germany is around DM.1500 (£266). In compari-

TeD video player (UK version shown by Decca), now on sale in Germany. The centre push switch selects repeated playing of single frames.



son with other disc systems and video tape machine it suffers from the short playing time, but scores heavily on the cost. The programme material at £12 per hour is not much cheaper than unrecorded video tape at £14-£18 per hour (recorded tape will be much more than this) but the machine cost is only half that of the cheapest video tape machine. The chief limitation is that no recording by the user is possible, a snag shared by optical disc systems (Philips VLP, Thomson-CSF, etc.) although the MDR, by Erich Rabe, will overcome this restriction by means of its magnetic recording principle.

A detailed description of TeD was given in *Wireless World*, August 1970, although development has continued since then.

Bristol community TV experiment concluded

The local community cable television experiment in Bristol closed down on March 14 (see leader, April issue). The experiment provided a considerable amount of valuable information on the role of locally originated television programmes in a city community. Although the licence in theory could have run for another four years, Rediffusion, who conducted the experiment, say they did not consider that any further useful information could be obtained by continuing the experiment.

Bristol Channel was launched in May 1973 as part of an experiment in local television authorized by the Government. It has cost over £200,000 and been available to 23,000 subscribers to the Rediffusion cable network in the city, at no extra charge. Under the rules of the licence, practically all the programmes presented had to be made in the locality about the locality and by the people of the locality. Rediffusion could see no reason for continuing Bristol Channel within the restrictions of its present licence for what would be several years before the government of the day decided in which way cable television was to develop.

The Greenwich community TV experi-

ment closed several months ago. This now leaves only Sheffield, Swindon and Wellingborough of the original five stations licensed.

Rescue radio system

An experimental radio communication system which provides two-way speech contact between underground workers and the surface was successfully used in operations at the Moorgate Tube disaster in London. The equipment consists of mobile base station and a number of special waistcoats containing portable transmitter-receivers, all of which may be rushed to the scene of a fire or other disaster. Each waistcoat contains an integral loop antenna and the three-channel transceiver is designed to leave the operator's hands completely free. Total weight of each transceiver is about 5lb while the base station equipment, with a weight of 30lb, is also portable. With this equipment communication can be fully maintained from within steel-framed buildings, cellars, tunnels, caves, mines and similar locations. Each rescue worker is permanently in two-way contact with the base station and a talk-through facility is available which permits person-to-person contact. The transmitter is voice operated. There is no press-to-talk or similar transmit/receive switching. Only two controls are fitted, an on/off switch combined with a volume control and a channel selector. The life of a battery is two hours, the same as that of an oxygen cylinder.

The system, known as Fire Ground radio, is in the early development stages and is not yet generally available. It is being developed by Plessey Avionics and Communications under a contract from the Home Office Directorate of Telecommunications for use by fire fighting services.

Memory store for coloured weather display

A data memory system forms a significant part of an automated weather radar network being developed for the Meteorological Office by the Royal Radar Establishment of Malvern. So far, seven weather radar display stores have been supplied for various stations. The RRE had experimented previously with other forms of storage but all were abandoned through economy or limitations of display or speed.

The memory store is built from Jasmin Electronics' range of digital logic modules. Basically, the system stores digital rainfall data transmitted by radar signals. This data is then converted into a colour code for clear grid type display on a colour television set. Alternatively, it can be logged or further processed by computer. Data is continually updated every 15 minutes and an ordinary tape recorder can be used as a back up store so that recorded data can be displayed at any

time.

The system has sufficient capacity to store up to nine different area pictures or one composite picture covering the entire country. Precipitation data in six degrees from light rain to thunderstorm with large hail is held for a period of two hours. The user can immediately view rainfall distribution in his selected area at any one of nine different times almost instantaneously. Alternatively he could play back the nine pictures in sequence to give a true picture of weather developments both in and outside his own area which in turn would enable him to anticipate conditions hours ahead.

Symposium on broadcasting satellites

The European Space Research Organization held a symposium on broadcasting by satellite at Frascati, Italy from February 12-14. The expressed purpose of the symposium was to bring the technical and operational possibilities and the economic features of this new method of broadcasting sound and television to the notice of potential users. Attendance was by invitation and included demonstrations and presentations by research establishments and industrial companies active in the field.

The first day was devoted to various systems aspects including a presentation by Dr G. J. Phillips (BBC) who expounded on the principles of assigning frequency channels and satellite orbit positions with particular reference to a plan for broadcasting national programmes to European countries. He described trial plans and explained the limitations imposed by technical requirements. The second day was devoted to discussion of receiver design

problems of which Mr E. Alder (S.E.L., Germany) described and demonstrated a method of transmitting two sound signals as digital modulation in an extended back-porch period of the line blanking. The method requires modification of the video signal waveform in reduction and displacement of the line-synchronizing pulse and colour burst periods. The final day was devoted to satellite systems.

Whether the conference achieved its purpose is hard to say. Certainly it brought together many of those in Europe concerned respectively with satellite technology, broadcasting and receiver design and some aspects of the subject were discussed ad nauseam. However, attendance by representatives from developing countries seemed disappointingly low and perhaps insufficient attention was given to their problems.

Satellite navigator helps food search

Positional accuracy to within 20 feet is claimed to be obtainable from the RSN2 Satellite Navigator in use by the captain of a scientific research vessel which recently left Southampton on a seven-month voyage prospecting for new food resources.

This first fitting of an RSN2 aboard an ocean going surface vessel was made in 3½ hours by Redifon Telecommunications engineers. Direct readout of latitude, together with GMT, is given on an illuminated display on the front of the unit which occupies 3½ cubic feet of space.

Operation is automatic—an inbuilt computer does all the work using information transmitted by six orbiting satellites (see "Navigation by satellite" by W. Blanchard, *Wireless World*, February 1975, pp.52-57). The ship—*Profesor*

Siedlecki—is a Polish research vessel working for the International Sea Fisheries Institute and partly financed by the Food and Agriculture Organization of the United Nations.

It will explore the open ocean for new fishing areas, of which maps will be made, and also look for krill, small crustaceans which are the main food of the balin whale and a possible new source of nutritious food.

Communications 76

With enlarged terms of reference, Communications 76 promises to be the largest and most important event in the field of international telecommunications. Subtitled "communications equipment and systems," it now takes in radio, civil, public and private and defence communications interests. The four-day "exposition" is being sponsored by six authorities (Ministry of Defence, Home Office, British Overseas Trade Board, Electronic Engineering Association, Telecommunications Engineering and Manufacturing Association, and the Institution of Electrical Engineers) and will feature an enlarged exhibition, three-tier conference with parallel sessions devoted to the theme subject, user topics and technical matters, and a number of "inward missions". There will be at least four of these, in which the British Overseas Trade Board subsidize parties of senior buyers having specific interests in the four themes.

Each of the four days of the conference, under the chairmanship of Dr D. M. Leakey, will be devoted to a single theme—radio communications, sponsored by the EEA (first day); civil communications, sponsored by the Home Office (second day); public and private telecommunications, sponsored by TEMA (third day); and defence communications, sponsored by the Ministry of Defence (fourth day). Communications 76 will be held June 8-11, 1976 at the Hotel Metropole, Brighton.

The first quadrasonic Nowell

The BBC's second experimental quadrasonic broadcast, with a seasonal message this time, will start at midnight on December 23 and will last for about an hour. It will be a nativity play "The First Nowell", based on medieval pageantry to music by Vaughan Williams. As with the first quadrasonic broadcast last July, two groups of v.h.f. stereophonic transmitters will be used. Radio 3 transmitters will carry the front left and right signals and Radio 4 the rear left and right. In the absence of a second stereo receiver, some interesting, though not completely representative effects could be obtained by using a mono receiver, preferably v.h.f., tuned to Radio 4, to provide the rear information from a central position.

All three of London Fire Brigade's new control room v.d.u. installations are now operational. At Croydon, pictured here and controlling the entire Greater London area south of the Thames where there are about 965,000 dwellings, 100 emergency calls are handled each day and passed to the 45 stations in that 420 square mile area.



A 50MHz oscilloscope

An advanced design using semiconductor techniques 1—Y amplifier and X amplifier

by C. M. J. Little, B.A.

Department of Electronics, Southampton University

The oscilloscope design presented in this article is the final result of five years' development and construction work carried out in my spare time. The project started with the purchase of a new Brimar cathode ray tube, the large cash outlay ensuring that an oscilloscope of some sort would eventually be built. From the first rather crude instrument, I became afflicted with a desire for perfection, and the present design is the result of continual improvement. To give an example of the amount of development work that I have done: three versions of the Y amplifier have been built, two of the e.h.t. inverter, two of the Y attenuator, two of the ramp generator, and no less than five of the X amplifier.

The oscilloscope offers all the usual facilities to be found in high quality commercial instruments, such as directly-coupled amplifiers, stabilized e.h.t., calibrated triggered timebase, and wide bandwidth. It lacks dual-trace operation, Y signal delay, and delayed timebase. The performance can be judged from the specification and some waveform photographs which will show the limits of the performance in some respect or other. Although I cannot guarantee these performance figures for all examples built, I am confident that the circuits are repeatable and will work well without further development.


I should point out that this design is complicated and that its construction should only be attempted by those readers with considerable practical experience. It is also expensive, costing at least £80, which is probably sufficient deterrent to those who are not wholly confident of their ability. However, the finished result is as useful and as easy to use as commercial instruments costing much more. It also seems to be reliable, having survived six months in the hands of the Southampton University Radio Club! It is recommended that the full series of articles is read and digested before starting work on the oscilloscope, as they will be published in the order considered best for description, not for construction. The list of components will, for this reason, be printed with the final article.

Y amplifier

The Y amplifier is a general purpose wide band amplifier, directly-coupled throughout, and with a bandwidth of 50MHz, although the attenuator degrades this. The basic sensitivity of 100mV/cm, and all other lesser sensitivities are obtained by switching a 1M Ω compensated attenuator in front of the fixed gain amplifier. A switch increases the basic amplifier sensitivity to 10mV/cm, maintaining the direct coupling but decreasing the bandwidth to 17MHz. A capacitor-coupled pre-amplifier with a gain

of 100 may be switched in front of the attenuator to increase the maximum gain to 100 μ V/cm, but use of this degrades the bandwidth to 10Hz–600kHz. The input impedance is constant at 1M Ω , 25pF on all ranges to allow the use of a "divide-by-ten" probe.

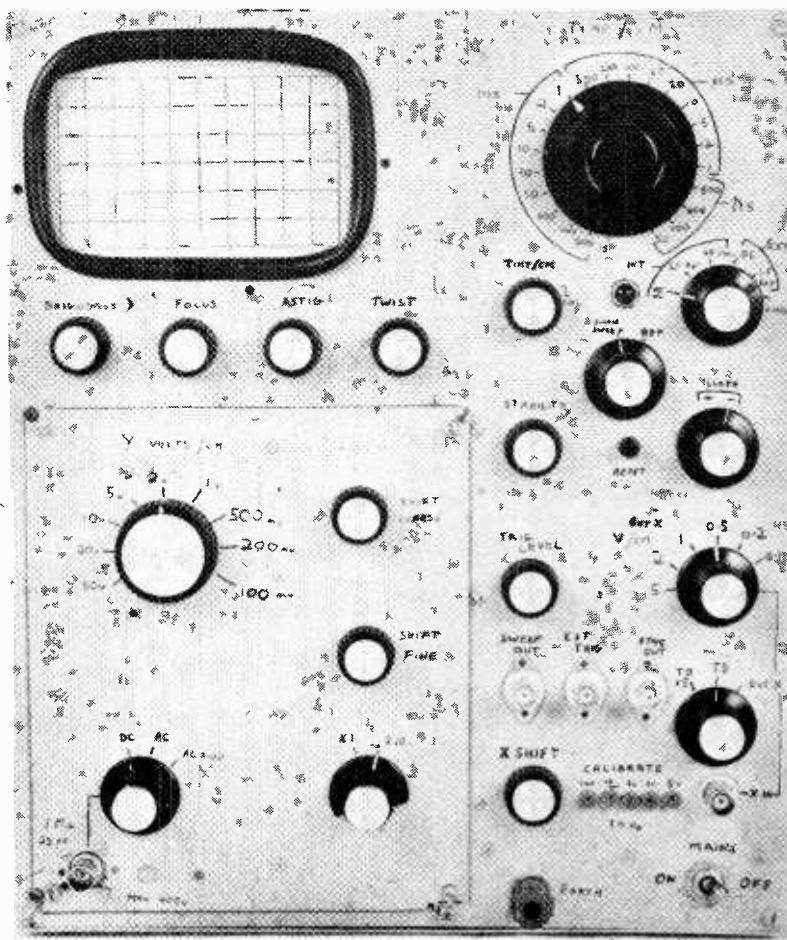The Y amplifier is divided into two parts, one of which, the pre-amplifier, is mounted in a removable plug-in unit, while the output amplifier is in the main unit next to the tube base. The removable Y plug-in unit facilitates the construction of alternative Y pre-amplifiers. More will



be said about this in the section on modifications.

The Y output amplifier circuit is shown in Fig. 1. The basic configuration is a differential cascode amplifier with Tr_3 and Tr_4 as the common-base pair, and Tr_5 and Tr_6 the common-emitter amplifiers. The base voltage of Tr_3 and Tr_4 is held at a constant d.c. potential of +14V, adjustable with R_2 . The common-mode input voltage is 11V, this voltage and the emitter resistors R_{13} and R_{14} defining the current through each half of the cascode to be 26.5mA. The mean Y plate potential is therefore about 30V. The gain of the stage is defined by R_{15} to be 13 times. L_3, L_4, C_7 and R_{16} compensate for a fall in gain due to capacitive loading at the collectors of Tr_3 and Tr_4 . These components are adjusted to give a good pulse response. L_1, L_2, R_8, R_9 and R_4 reduce the effect of mismatch and reflections in the wires connecting the output amplifier with the plug in. They were adjusted experimentally to give a reasonable pulse shape. Tr_2 provides a low impedance feed to the trigger generator.

The Y pre-amplifier circuit is shown in Fig. 2. The main active component is a

$\mu A733$ integrated circuit, which is a differential wideband amplifier, and could almost have been designed especially for the present application. Fixed gains of 10, 100 and 400 can be selected by shorting various pins on the TO5 package, with a bandwidth of 100MHz, or the gain may be varied between 10 and 400 with a preset between pins 4 and 9. The maximum supply voltage is $\pm 8V$ so R_{17} is used to drop the 18V rail to 15V. The output common mode voltage is 10.4V and the input common mode voltage 7.5V.

The minimum gain of the 733 is 10, so the total gain of the output amplifier and the 733 is 130. With a deflexion sensitivity of 8V/cm, this gives a final sensitivity of 60mV/cm. The input stage, therefore, has a gain of about 0.5.

The input stage is a differential amplifier using two junction f.e.t.s in common-drain, and two n-p-n transistors in common-emitter. The input stage provides

firstly a high input impedance and secondly, a voltage shift from the 0V input to the 7.5V input to the 733. The collector loads of Tr_{11} and Tr_{13} are 500 Ω in order to ensure a wide bandwidth. At one stage in the design I thought that the Y amplifier might be made fully differential, with two input terminals. This was not done, but explains R_{28} to adjust the common mode rejection to a maximum, and also the current sources Tr_{12} and Tr_{14} . R_{30} adjusts the gain of the whole amplifier, and R_{23} adjusts the common mode input voltage of the 733 to exactly 7.5V.

The Y shift voltage is applied to the gate of Tr_{15} from a network which provides fine and coarse shift controls. The coarse control acts as a balance adjustment in the $\times 10$ gain position. The shift network is fed from the $\pm 11V$ rails. Input protection is provided by D_1, D_2 and R_{20} .

The $\times 10$ gain switch operates RL_1 , which switches R_{46} across the gain control pins of the 733, increasing its gain to 100 \times . A reed relay is used here to avoid long leads to the pins of the 733. The capacitance from pins 4 and 9 to earth must be as small as possible.

The final parts of the Y amplifier are shown in Fig. 3 and Fig. 4. The Y attenuator switches a separate section for each gain position. Each section is compensated and has a capacitor to standardize the input impedance. A further discussion of the Y attenuator will be given in the construction section.

The a.c. pre-amplifier has a gain of 100, and is placed between the attenuator and the input socket. This means that noise generated in the pre-amplifier will be attenuated as the sensitivity of the main amplifier is reduced. The circuit has zero phase shift between input and output, maintaining the convention that up is positive on the screen. The prototype showed instability due to capacitive coupling between the input and output. C_{21} was added to eliminate this, and could be removed if the screening was made more efficient. In particular, S_{2b} and S_{2c} could be on separate wafers, with a screen in between. It was not anticipated that the " $\div 10$ " probe would be used with the " $\times 100$ " gain position.


This concludes the circuit description of the Y amplifier.

X amplifier

This part of the oscilloscope gave easily the most trouble, and about four completely separate versions of the X amplifier have been built and rejected. At this point I have to admit that I looked at the circuits of various commercial oscilloscopes to see how to overcome the problems I had experienced. The present circuit, shown in Fig. 5, is based on one used by Solartron.

The problem is that the circuit has to provide very fast slew rates with very fast recovery from overload. Consider the X amplifier operating from the 50ns/cm sweep. The total deflexion voltage required is about 170 volts peak to peak, which corresponds to a slew rate

Fig. 1. The Y output amplifier. L_1, L_2 are ferrite beads.

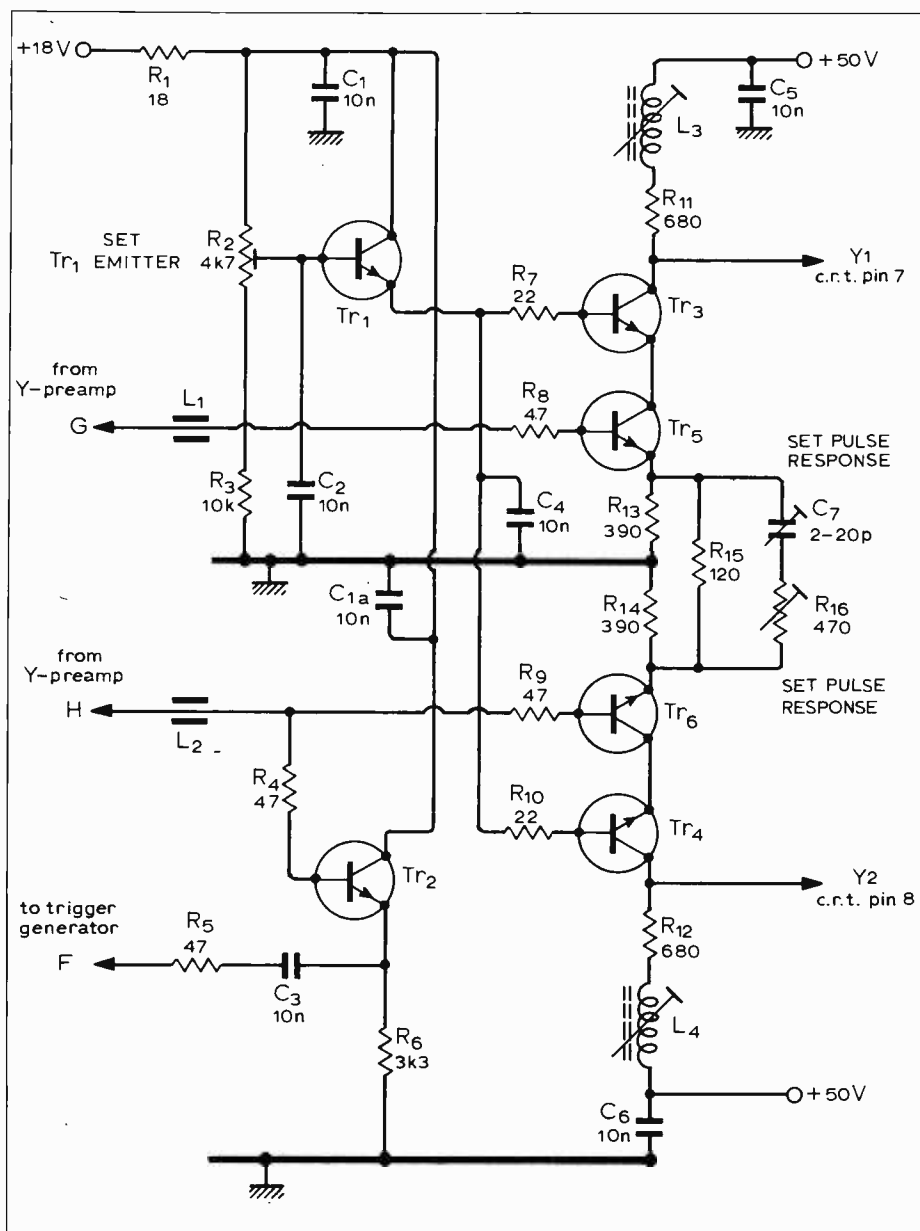

of 340V/ μ s. Now the problems really begin when the $\times 5$ expansion switch is operated. The slew rate is now 1700V/ μ s! Worse than this, the amplifier will be overloaded for about three-quarters of the sweep, as it is trying to produce a sweep voltage of 850 volts, when it has a maximum voltage swing of about 200 volts. The result of all this is to produce an impossibly non-linear sweep, sometimes even doubling back on itself! The secret is to ensure that all collector-base

junctions remain reversed biased during overload, as a saturated transistor takes too long to recover. It is also equally important to avoid base-emitter junction reverse breakdown for the same reasons. The degree to which the circuit avoids these troubles may be judged from a photograph of a 100MHz sine wave displayed at 50ns/cm with $\times 5$ expansion.

The basic configuration of the output stage is again a differential cascode amplifier. This is operated between the

-50V rail and the +130V rail in order to obtain sufficient voltage swing. The mean output voltage with no spot deflexion is 50V, which gives a current of 24mA in each half of the differential amplifier. The bases of Tr_{36} and Tr_{37} are held at -24V by D_{14} and D_{15} . D_{16} to D_{19} prevent the collector voltages from falling below -11V, thereby avoiding saturation of Tr_{36} and Tr_{37} .

The emitter voltages of Tr_{34} and Tr_{35} are at -39V, requiring collector voltages


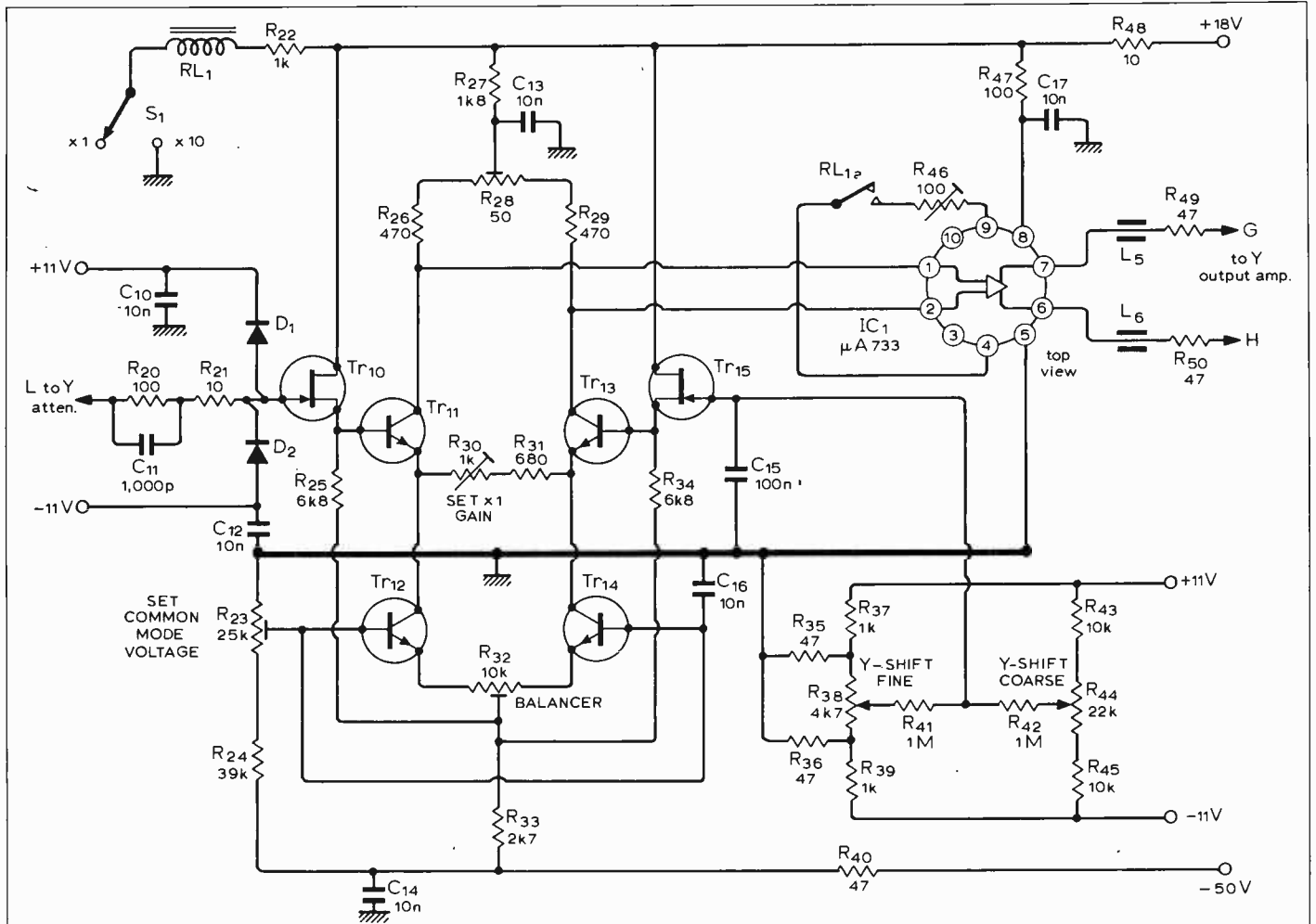


Fig. 2. Circuit diagram of the Y pre-amplifier.

Fig. 3. The Y input circuit and a.c. pre-amplifier. The attenuator is shown in Fig. 4.

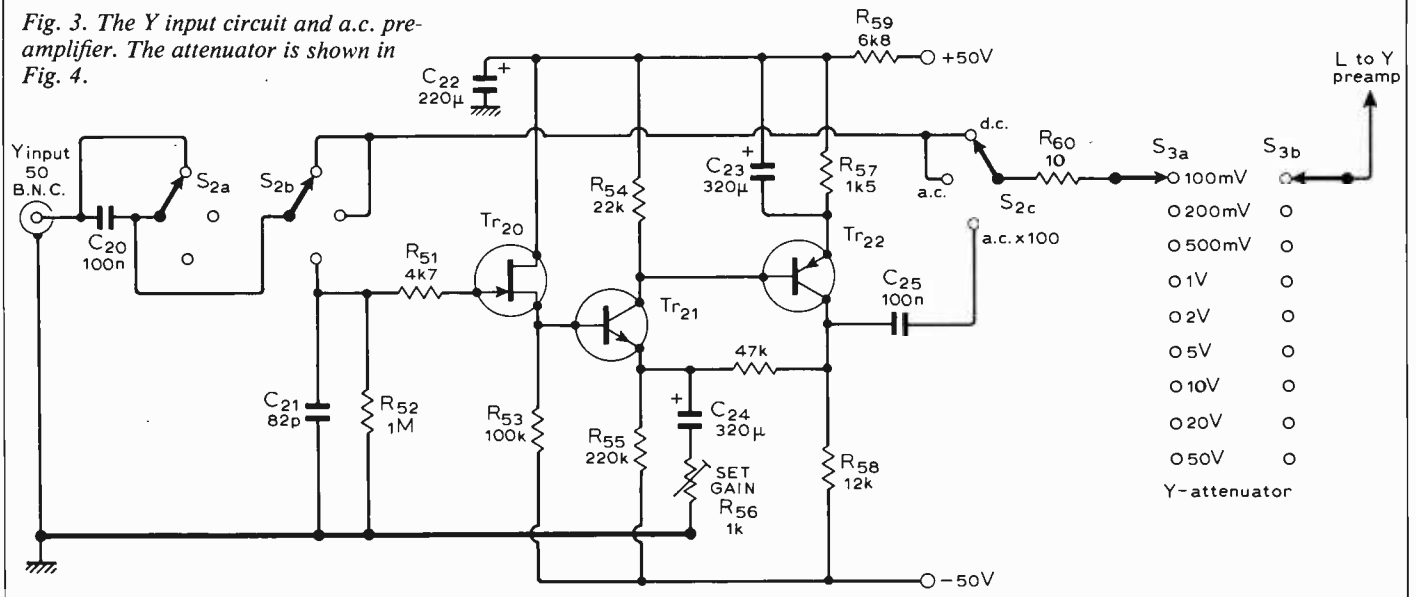

of about $-27V$ on Tr_{32} and Tr_{33} . This p-n-p input stage will accept the full 20V peak-to-peak sweep voltage without overloading. The constant-current source Tr_{31} prevents saturation of Tr_{32} or Tr_{33} , and sets the overall working point of the amplifier. D_{10} and D_{11} prevent breakdown of the base-emitter junctions of Tr_{32} and Tr_{33} . The gain of the amplifier is adjusted to give a sensitivity of 2V/cm with R_{93} . When the $\times 5$ expansion switch is operated, R_{90} is switched into circuit

via-relay RL_2 and the sensitivity increases to 400mV/cm.

To summarize the horizontal deflexion system, Fig. 6 shows the interconnexion of the various horizontal sub units, and also shows the circuit of the external X preamplifier. This has a fixed gain of 4, and is protected in the same way as the Y amplifier. A switched attenuator provides sensitivities from 100mV/cm to 5V/cm. The $\times 5$ gain relay RL_2 is operated in the external X position of S_5 . Although the

external X preamplifier is a negative feedback amplifier no compensation seems to be necessary. (To be continued)

Fig. 4. Y attenuator sections, selected by S_3 in Fig. 3.

Fig. 5. The X amplifier for both timebase and external signals. Letter symbols refer to Fig. 6.


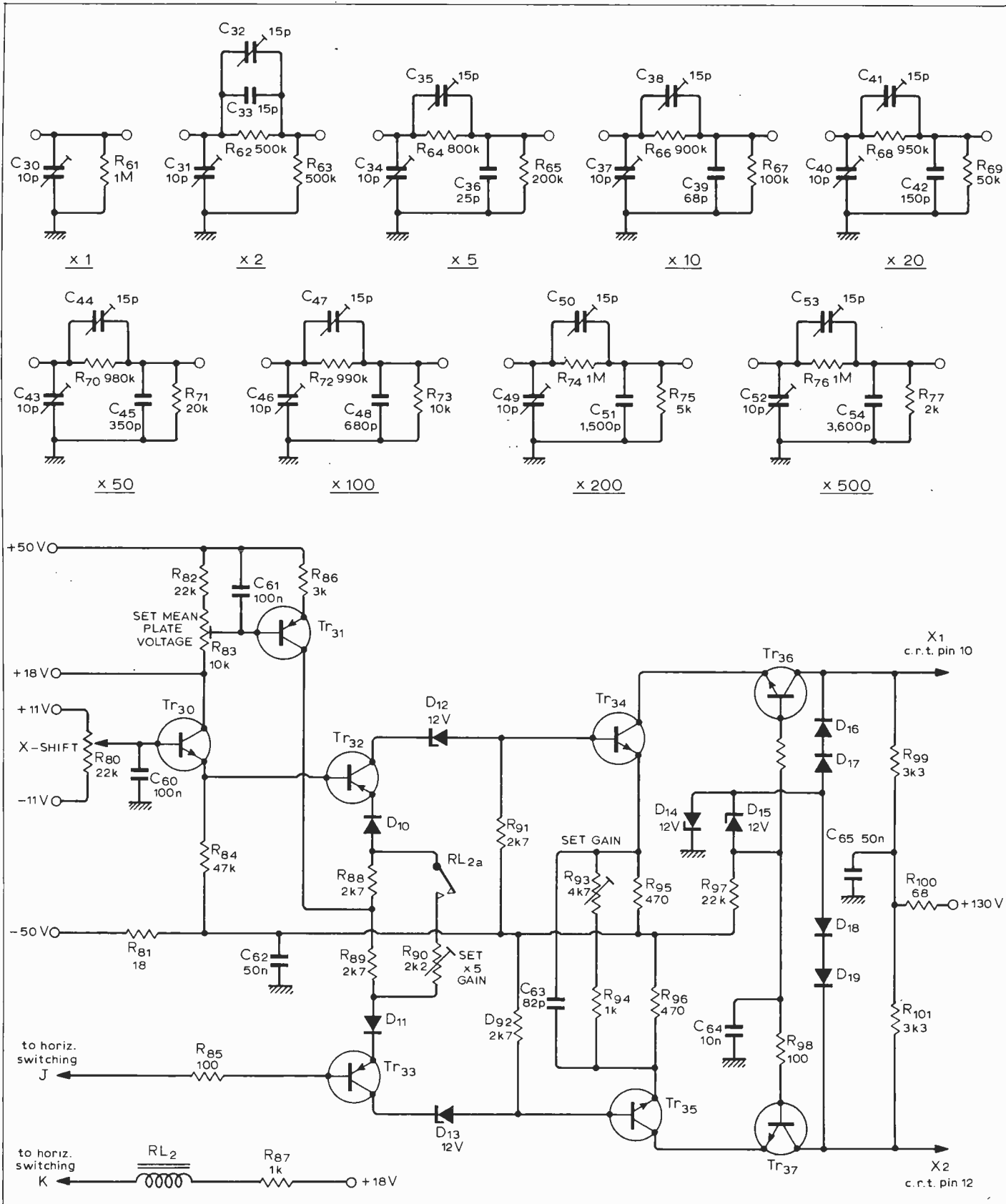


Fig. 6. The horizontal axis switching and X input amplifier.

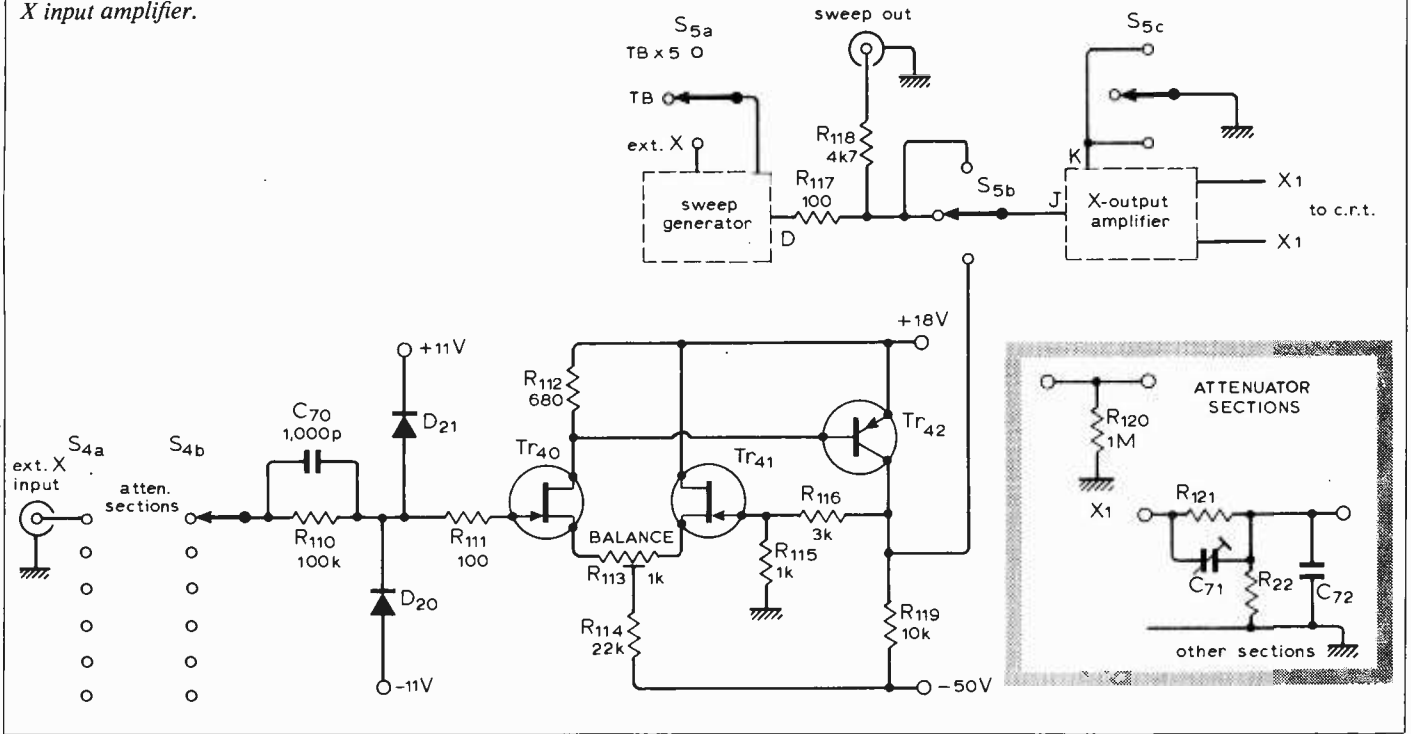

Specification of the oscilloscope

C.r.t.

Spiral p.d.a. tube operated at 4kV. E.h.t. derived from feedback-stabilized inverter. Built-in graticule inside tube face. Screen area 10cm X 6cm. Directly-coupled retrace blanking.

Calibrator

1kHz square wave calibrator giving voltage outputs of 5 volts, 1 volt, 0.1 volt, 10mV, 1mV to sockets on front panel. Voltage accuracy ±1%. Time accuracy ±0.5%.

Y amplifier

1MΩ, 25pF input impedance. Nine-position switch giving vertical sensitivities of 100mV/cm to 50V/cm in 5, 2, 1 sequence. Switch giving gain increase of 10X on all ranges. A.c. preamplifier giving gain increase of 100X for a maximum sensitivity of 100μV/cm.

Bandwidths (at -3dB points)

- gain x 1 d.c.—50MHz, rise time 7ns
- gain x 10 d.c.—17MHz, rise time 20ns
- gain x 1000 10Hz—600kHz, rise time 0.5μs

Hum and noise

0.5cm peak to peak at 100μV/cm

X amplifier

External input with input impedance of 1MΩ. Six sensitivities of 100mV/cm to 5V/cm in 5, 2, 1 steps. Bandwidth d.c.—5MHz.

Sweep generator

23 switch-selected ranges from 1s/cm to 50ns/cm in 5, 2, 1 sequence. Uncalibrated fine adjustment with 3:1 range. Linearity of sweep better than 0.1% except on 50ns range, when 0.5%. Accuracy of all ranges ±2%. Expansion switch giving X expansion of

5X. Usable on all sweep ranges giving a maximum rate of 10ns/cm.

Single sweep facility

Triggering

Trigger level control with +/— slope switch. Trigger selector switch giving the following positions:
 "Int." A.c.-coupled signal taken from Y amplifier.
 "L.f. rej." As int. but via high-pass filter.

These two positions provide stable triggering up to 10MHz. The minimum signal level is 0.3cm.
 "H.f. sync." Stable synchronization up to 100MHz with 0.2cm signal.
 "Ext. d.c." External triggering. Minimum signal 50mV at 1kHz.
 "Ext. l.f. rej." Input impedance 1MΩ.
 "Line." Triggering from 50Hz mains.

Cost to build using mainly new components £80.



ACTIVE DEVICES

Burr-Brown have sent us a leaflet on the Model 3660 i.c. instrumentation amplifier, which features a voltage drift of less than 2.5μV/°C and a bias current drift of less than 2nA/°C. Common-mode rejection ratio is at least 110dB and the input impedance is 20GΩ. Burr-Brown International, 25A King Street, Watford, WD1 8BT WW401

A booklet from Micro Electronics gives design and applications information on the MEU21/22 programmable unijunction transistors. Applications include oscillators, a TV deflection circuit, delays and s.c.r. control. Micro Electronics Ltd, York House, Empire Way, Wembley, Middlesex . WW402

An eight-page leaflet giving connexions and application notes for several manufacturers' audio integrated circuits is available from Chromasonic Electronics, 56 Fortis Green Road, London N103HN. The cost is 10p, or free with more than £1 of components.

PASSIVE DEVICES

We are informed by Plessey that they have published a brochure setting out full information on a range of c.r.t. deflection components for professional use. The publication, which is in English, French and German, is obtainable from Plessey Windings, Abbey Works, Titchfield, Fareham, Hants PO14 4QA WW403

MATERIALS

A brochure entitled *Adhesive on both sides* describes the uses of double-sided adhesive tapes in various industries. There is a page of characteristics of 14 types of tape made by Tesa Tapes Ltd, Ascot Road, Bedfont, Feltham, Middlesex TW14 8QP. WW404

EQUIPMENT

Appliance Components Ltd tell us that they have available a leaflet on the ETA series of electronic

delay timers for the range 3s to 20m. Appliance Components Ltd, Cordwallis Street, Maidenhead, Berks SL6 7BQ WW405

Crystal oscillators, compatible with c.m.o.s. circuitry, are available from Lyons Instruments and the Vectron CO-236 range, which covers frequencies from 0.01Hz to 10MHz, is described in a leaflet available from Lyons at Ware Road, Hoddesdon, Herts WW406

Cambion say that they have issued a brochure of Euro-Card component mounting boards and Euro-Rack assemblies. Cambion Electronic Products Ltd, Castleton S30 2WR WW407

Transducers using strain gauge, piezo or differential transformer techniques for the measurement of pressure, force, acceleration and displacement are described in a new short-form catalogue from Bryans Southern Instruments Ltd, Willow Lane, Mitcham, Surrey CR4 4UL WW408

A 64-character, 16-column alphanumeric printer from Gay of Milan, named the Printina, is briefly described in a leaflet from Claude Lyons Ltd, Hoddesdon, Herts WW409

Digital frequency-synthesis— a new approach

by D. C. Ayre, Dip. Tech. (Eng.); and K. G. Woodard, B.Sc.

Farnell Instruments Ltd

Although the idea of the phase-locked loop synthesizer has been in existence for some time, it has never been possible to use the type of phase comparator having infinite pull-in range with a resolution of six digits and still produce a signal with very low residual f.m. This article shows how the residual f.m. can be greatly reduced while retaining a fast response time and high resolution.

In the last few years there has been a vast expansion in semiconductor technology, and in particular in integrated circuits, which has done much for digital circuit design by providing many new building blocks of great internal complexity and overall versatility. It is the introduction of this type of device, and notably high speed dividers up to 1GHz, that permits a new look at old techniques. One area that has benefited is digital frequency synthesis, using a phase-locked loop, a technique which has been in existence for over forty years.

Fundamentally, the phase-locked loop

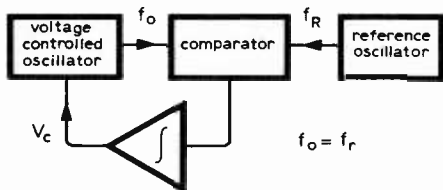


Fig. 1. Elementary phase-locked loop.

is a means of controlling the frequency of a voltage-controlled oscillator so that its frequency is equal to a reference frequency or some multiple or sub-multiple of it. For this purpose a phase comparator is required. An elementary phase-locked loop is shown in Fig. 1. This is a first-order system, the error being in phase only. It is this phase error that is used to control the v.c.o. to the correct frequency. As the output of the phase comparator contains oscillator frequency components of high relative level, a low-pass filter is used—Fig. 2. Components of this filter are carefully selected to produce a good

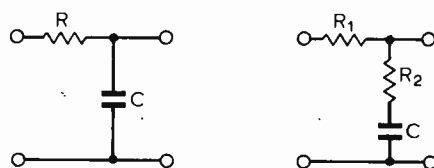


Fig. 2. Typical low-pass filters.

phase margin in the loop characteristic. As the bandwidth of the loop is usually very much smaller than the oscillator frequency, there is virtually no r.f. fed back to the frequency control of the oscillator.

To make this loop into a basic synthesizer a programmable divider is added—Fig. 3. If the divide-down ratio is very large, then the comparison frequency becomes very low. This frequency may now be getting into the region of the control bandwidth, in which case it will be fed directly on to the frequency control line causing frequency modulation. This has been a limiting area ever since the devices made this type of synthesizer possible. The resolution must therefore be kept relatively low if the residual f.m. and the settling time of the loop are also to be kept low.

Originally, the phase comparator was an analogue circuit using diodes and transformers, similar to a mixer, but with the advent of complex integrated circuits the comparator has become digital, at frequencies that can be reached by digital integrated circuits. The output from these comparators tends to be of a digital nature which is easily filtered if the comparison frequency is high.

The comparator waveforms of Fig. 4, with their inherent problems, are easily produced using modern integrated circuits. The advantages gained by these circuits, such as logic level outputs that indicate the lock condition or the ability to search over a very wide frequency range to allow lock to be obtained, make it worthwhile finding a way to overcome the major disadvantages. A phase comparator of this type but with a ripple-free output would make it possible to build a synthesizer with up to six decades of frequency control and to restrict the unwanted f.m. to negligible proportions.

The area for greatest improvement is in the waveshape of the correction pulses. The present comparators tend to produce a wide energy spectrum with the maximum power in the lower frequency components.

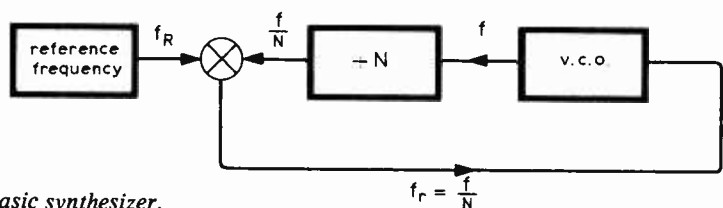


Fig. 3. Basic synthesizer.

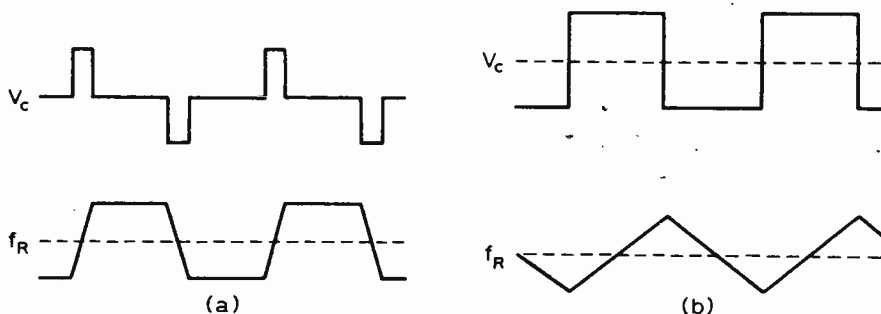


Fig. 4. Comparator waveforms and their effect.

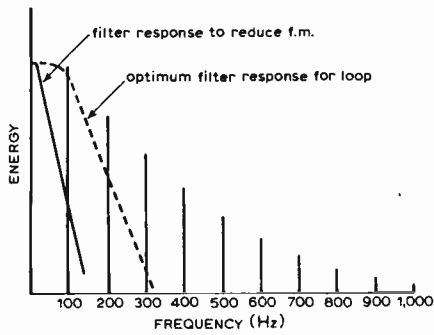


Fig. 5. Comparator energy spectrum.

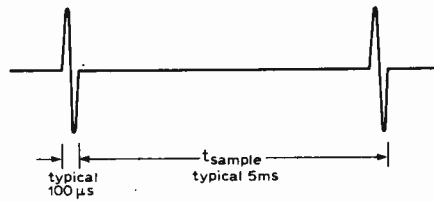


Fig. 6. Ideal waveform.

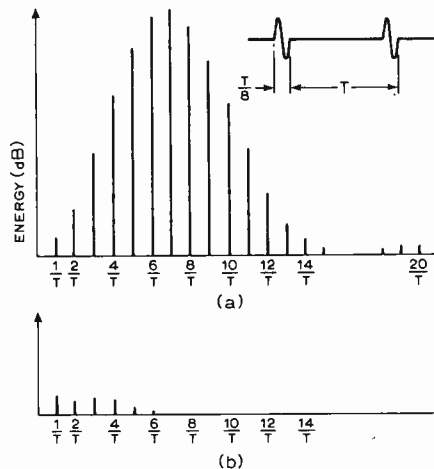


Fig. 7. Energy spectrum of (a) ideal waveform, (b) practical system with two stage filter.

Filters that attenuate these components would badly affect the phase response and settling time of the control loop. This means that to be able to effectively remove the unwanted components without altering the loop parameters, it will be necessary to concentrate the more powerful components to higher frequencies as in Fig. 5. Such a waveform would tend to concentrate all of its correction power into a very short time, compared with the time between such pulses.

An ideal waveform is basically a single cycle of a sine wave at a frequency far in excess of the repetition rate—Fig. 6. The energy of this waveform is concentrated in the spectral lines corresponding to the frequency of this sine wave and its harmonics, see Fig. 7(a). In practice, the energy of the low frequency components will increase if the loop is compensating for oscillator drift, see Fig. 7(b). To obtain the best results, it will be necessary to use a very low drift oscillator for the v.c.o.

Frequency-locked signal generator

The prescaler, in Fig. 8, is needed to reduce the maximum input frequency to the presettable dividers to the maximum

clocking speed of the logic used which is approximately 20MHz in the case of t.t.l. Thus if a resolution of 1kHz is required of a 100MHz signal, the comparison frequency will be 1kHz divided by the prescaler—200Hz in this example. The programmable divider is shown with six digits, representing a division ratio of up to 10^6 , and is typical of modern telecommunications equipment. The comparator output of the system will suffer from the faults previously mentioned; in particular any jitter from the comparator will be magnified by a factor of up to 10^6 , the value of the programmable divider. To overcome this fault some extra circuitry needs to be added. Fig. 9 shows the system in more detail with the extra blocks.

The output of the v.c.o. and reference lines both drive monostables whose outputs alternatively set and reset the flip-flop to produce a square wave when the frequencies are equal. Once the v.c.o. pulse has set the flip-flop, the output is NAND-ed with the v.c.o. line to see if another pulse appears before the reference pulse resets the flip-flop. If a pulse appears, then the v.c.o. is too high in frequency and the NAND gate produces a “go-down” pulse.

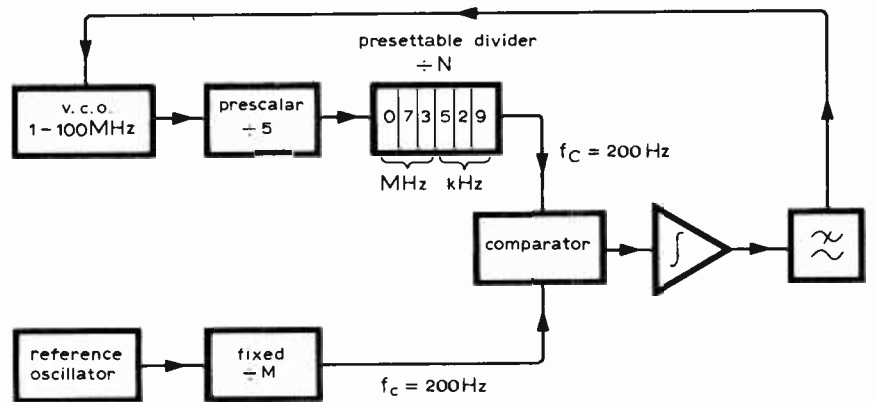


Fig. 8. Frequency-locked signal generator.

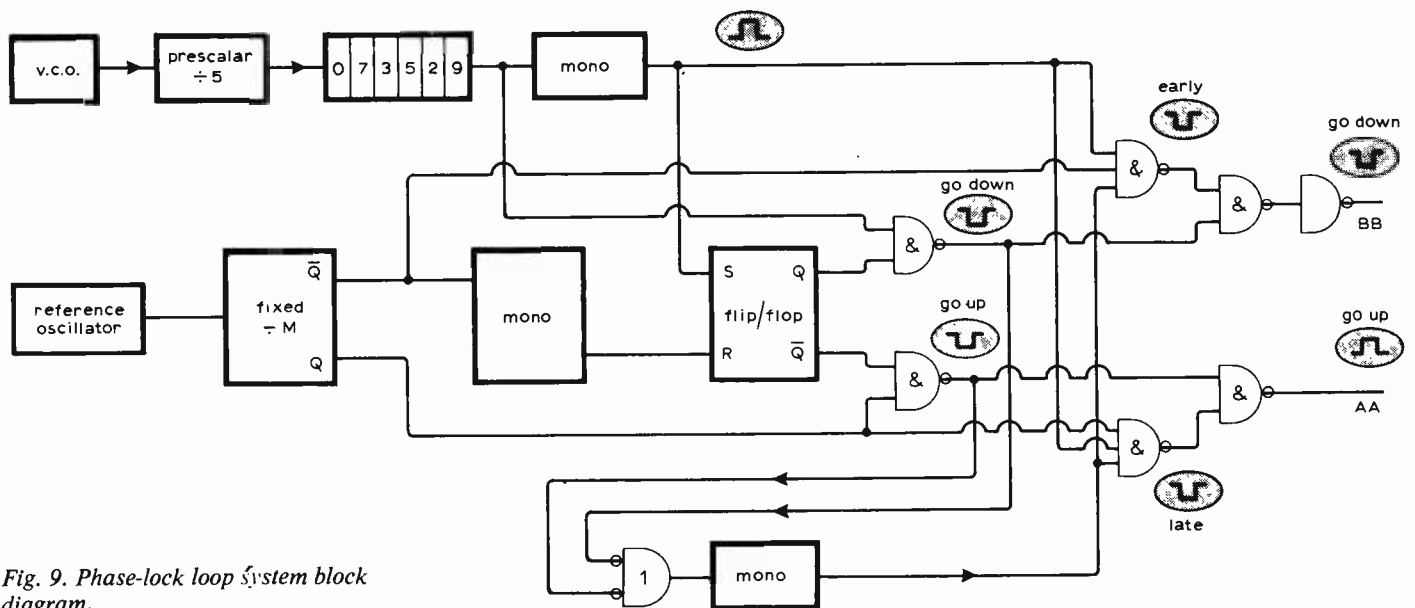


Fig. 9. Phase-lock loop system block diagram.

The same function is performed with the flip-flop's other output and the reference oscillator pulse to produce a "go-up" pulse when the v.c.o. is too low in frequency. The monostables on the v.c.o. and reference lines provide a delay so that the flip-flop output cannot be combined with its own set or reset trigger which would give false up and down pulses. This method is preferred to relying on propagation delays.

There is now a series of go-up and go-down command pulses. When the two frequencies are equal the flip-flop output has an equal mark/space ratio square wave and there are no up or down pulses. In this condition the v.c.o. is free to drift in either direction until a correction pulse returns it to equality. Ultimately, the drift would be balanced against up or down pulses at the sampling rate of 200Hz. These pulses constitute the residual frequency modulation.

Phase lock

The method of reducing this 200Hz f.m. is to carry out a phase-lock operation which produces "late" and "early" pulses as soon as the flip-flop output departs from an equal mark/space square wave.

The set pulse and the divider Q output, NAND-ed, produce a "late" pulse, the Q output and the set pulse giving an "early" pulse. These are referenced to earth and summed to produce a composite signal. An effect of the summation is to round off the composite signal to form a complete cycle of sine-wave, with a period of typically 100µs. If the v.c.o. drifts low with respect to the reference oscillator the width of the late pulse increases by a small amount, and vice-versa if the v.c.o. drifts high. Thus the balance between the areas contained in the late and early pulses gives an extremely sensitive fine-tuning control of the v.c.o. Moreover, this control is instantaneous in its action since it is an "on-line" control.

This complete cycle of sine-wave is an extremely important point and is the basis of the reduced f.m. system. When the two frequencies are locked, the two areas of the halves of the sine-wave are equal except for a small amount to balance the v.c.o. drift. As can be seen from Fig. 7(a), the cycle is very narrow, typically 100µs or less, corresponding to a frequency of 10kHz. This means that the only f.m. produced by this phase-lock technique is at a frequency of 10kHz or more, and not at the comparison frequency of 200Hz, because there are no up or down pulses when locked. This absence of up or down pulses when near phase lock is used to inhibit the phase-lock section during "search" to prevent locking onto harmonics.

Performance of a synthesized signal generator

When this system of synthesis is applied to a signal generator it is possible to produce accuracy and stability figures comparable with those produced by a full synthesizer. However, the noise performance of the system cannot be better than

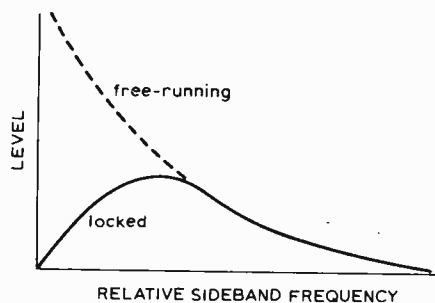


Fig. 10. Typical sideband noise spectrum of a synthesized signal generator.

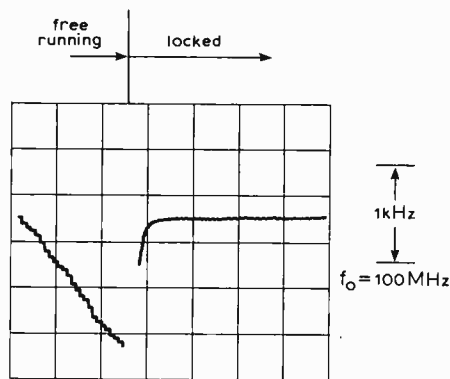


Fig. 11. Typical X-Y plot of frequency stability.

that of the unstabilized oscillator for the spectrum outside the bandwidth of the phase-locked loop.

The lower components of noise are very much attenuated compared with those of the unstabilized oscillator, while the outer components are hardly affected—Fig. 10. Another factor which will compare unfavourably with the full synthesizer is resolution, which in the case of this synthesized generator is only 1kHz. This figure is arrived at by a compromise concerning cost, complexity and speed of operation, speed being another factor that compares unfavourably with the more expensive system.

To consider some of the advantages, one has first to consider what is required of the synthesized signal generator. The disadvantages of a standard signal generator are drift and inaccuracy of frequency setting. To overcome these factors several manufacturers have produced add-on synchronizers which solve the problem of inaccuracy and drift but are very inconvenient to use, requiring the frequency to be set manually to a high degree of accuracy before locking can take place. Also if this is done only a short time after the unit is switched on, it is likely to lose lock again.

This add-on synthesizer, however, has none of these disadvantages, being capable of finding and locking on to any frequency dialled up on the thumbwheel switches, even if this means changing range. No external frequency counter is required and no digital display for confirmation of frequency as it is not possible for the system to settle on the wrong

frequency and also indicate that it has locked.

This ability to move to a frequency that has been set-up digitally means also that external digital programming is possible, including a digital sweep.

The frequency stability of a system using an "unovened" crystal in and out of lock is shown in Fig. 11.

The time taken in practice for the frequency to be altered from 10MHz to 100MHz (four range changes required) is around 5 seconds. The time taken to move 1kHz is in the order of milliseconds.


Resolution is considered to be of no problem in general as there is little real requirement for the frequency to be set any more accurately than 1kHz, this being about the practical limit with standard signal generators.

New m.o.s. centre

At a cost of DM 20 million, a plant for the production of m.o.s. components has been set up in Munich. The new facilities comprise six diffusion ovens for doping the semiconductor crystals with impurities and three ion implantation systems for i.c.s with particularly low operating voltages. The new plant has been set up by Siemens.

Integrated metal oxide semiconductor circuits require fewer fabrication steps than bipolar circuits, have smaller structures and consume less power. It is therefore possible to accommodate a particularly large number of transistors on a limited area. Engineers were discussing possible methods of manufacturing such circuits as early as 1961; five years later the first samples were on the market. Over the next few years m.o.s. sales are expected to increase at a rate of 30%, a figure well above the average for the components sector.

The new production centre takes the place of a number of widely scattered production locations. Its overall isolation from the environment allows a previously unattainable, but now obligatory freedom from dust during the production processes. The dust content of the rooms does not exceed 150 particles/cubic metre. Water with a purity of 10⁻⁹ ions/litre is available for the photographic masking processes that precede each individual diffusion step. The high degree of purity of the air in the centre with its area of over 1000 square metres is achieved despite the fact that 80 persons are directly involved in the manufacturing processes.

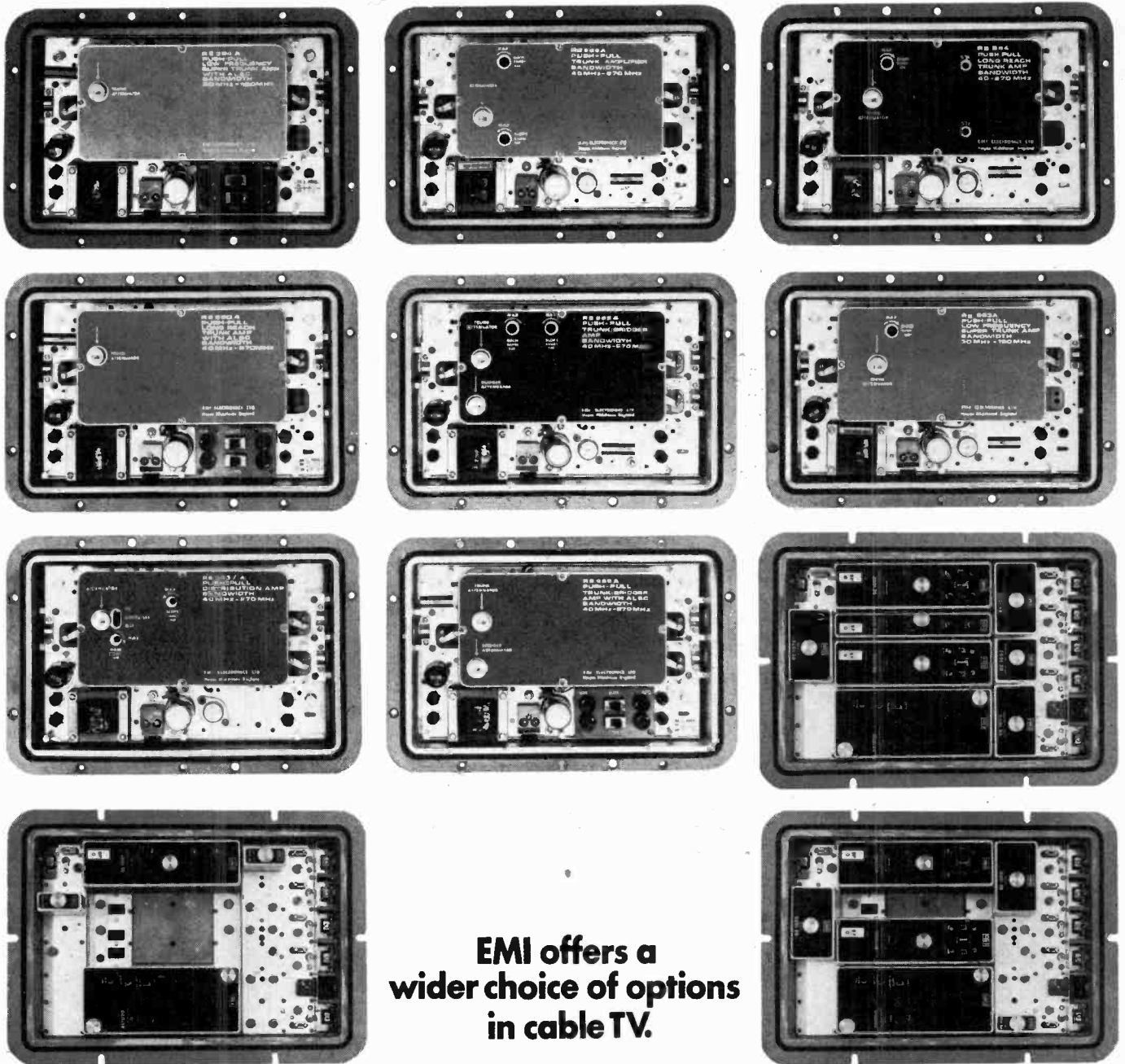

EMI offers a wider choice of options in cable TV.

The quality of EMI Colorline cable television equipment is proved daily in systems bringing high quality television to hundreds of thousands of people—particularly in Europe.

Now EMI introduces a new range of modular VHF network amplifiers offering full two-way facilities.

The new range—the Colorline RE1000 series—has a basic forward bandwidth of 40-300 MHz with optional reverse band-widths of 5-30 MHz or 5-100 MHz. At the same time EMI also introduces a unique multi-channel VHF/UHF Distribution Converter. It enables up to seven channels to be converted from a VHF trunk network into the UHF bands for local distribution.

This new equipment, complemented by our Colorline RE900 series of VHF push-pull equipment and by the ME 690 modular series of VHF/UHF

MATV equipment provides the systems designer with an even greater variety of options to meet virtually every requirement of VHF and UHF cable distribution.


As pioneers in the development of high definition television, EMI has accumulated nearly forty years experience in every aspect of television broadcasting—embracing hardware, software and practical operating 'know-how'. This unique breadth of experience makes us highly competent to help you. Contact us at the planning stage.

That's what we're in business for.



EMI Telecommunications

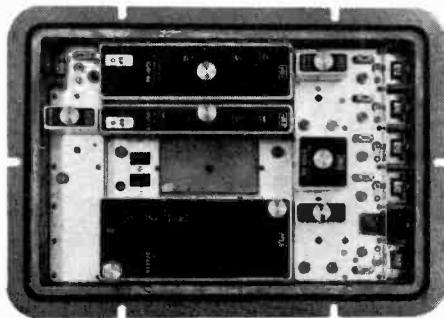
A member of the EMI Group of Companies, International leaders in music, electronics and leisure. EMI Telecommunications Division, EMI Limited, 252, Blyth Road, Hayes, Middx., England. Tel. 01-573 3888, Telex: 25145. Cables: EMISOUND London.



WW—181 FOR FURTHER DETAILS

Go quad for around £50

(including the speakers!)

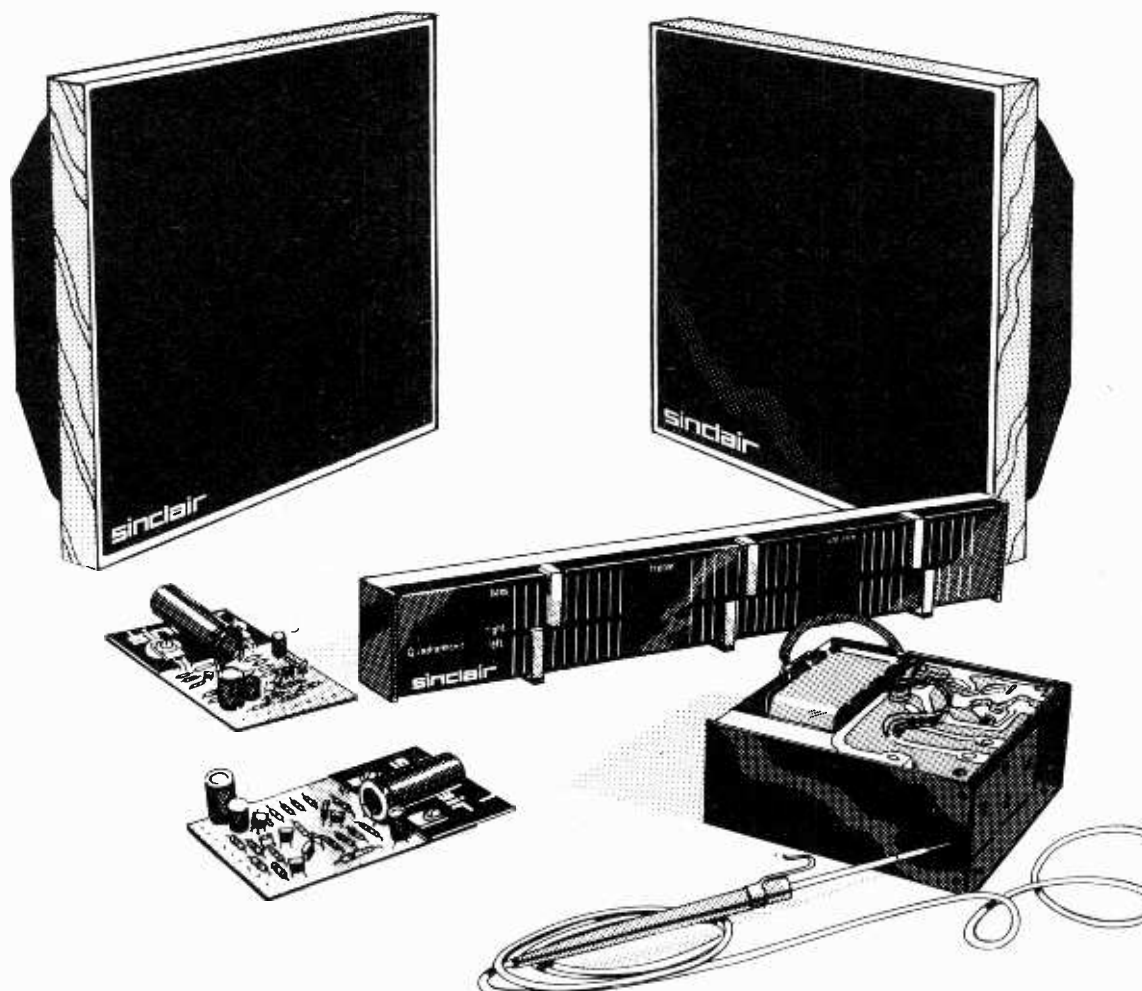

Sinclair Project 80 hi-fi modules

If you've thought of switching to quad, you've probably found it an expensive process. Do you part with your existing stereo amp – which probably cost you a lot in the first place – and replace it with an even more costly quad amp? Or do you buy an expensive add-on kit – often costing as much as £90 even *without* the extra speakers?

With Sinclair Project 80 hi-fi modules, you can keep your existing amplifier ... add a quad decoder, two power amps and a power supply unit ... a couple of Sinclair Q16 speakers and you've got a high-quality, true quad system which will have cost you only £50 or so to convert!

How does Sinclair Project 80 work?

Project 80 is a comprehensive set of hi-fi modules or sub-assemblies. Amps ... pre-amps ... FM tuner ... quad decoder ... control units ... everything you need to assemble hi-fi units. They're all designed to look alike and are all completely compatible with each other. Simply decide on the specification of the unit (stereo or quad) you want to build ... buy the necessary modules ... connect them up and house them.

You can even build a quad amp entirely from Project 80 modules. Two power amplifiers, a control unit and a power

supply give you a stereo amp for as little as £31.80 plus VAT. The necessary add-on quad modules cost only £36.80 + VAT. Together, they make up a true hi-fi quad amp for only £68.60 + VAT!

And whenever you choose, you can add extra Project 80 refinements. An FM tuner ... a scratch/rumble filter ... higher-output power amps – Project 80 is an enjoyable way to develop your own hi-fi system!

Is it difficult to build?

Not at all. All Project 80 module circuitry is complete in itself – all you have to do is connect the external wiring to numbered solder points.

And if you're not so hot with a soldering iron? Use Project 805 kits. Project 805 uses Project 80 modules, but provides special clip-on tagged-wire connections – positively no soldering! There are two Project 805 kits – the basic 805 stereo amplifier kit, and the 805Q quad conversion kit.

805Q can be used to convert a Project 80 or 805 stereo system, or your existing stereo system.

You'll find more details and some system suggestions opposite.

Project 80 hi-fi modules – the easy way to true quadraphonics.

Quad system suggestions from Sinclair



Project 80 SQ quadraphonic decoder

Combines with and exactly matches Project 80 control unit for true quadraphonics. This unit is based on the CBS SQ system and is a complete quadraphonic decoder, rear channel pre-amp and control unit.

Specification
(9½ in x 2 in x ¾ in.) Connects with tape socket on Project 80

control unit or similar facility on any stereo amplifier. Separate slider controls on each channel for treble, bass and volume. **Frequency response:** 15 Hz to 25 kHz ± 3 dB. **Distortion:** 0.1%. **S/N ratio:** 58 dB. **Rated output:** 100 mV. **Phase shift network:** 90 ± 10, 100 Hz to 10 kHz. **Operating voltage:** 22 V – 35 V.

Price: £18.95 + VAT

Project 80 power amplifiers

Two different amplifiers, designed to be used separately or combined, with Project 80 modules or as add-ons to existing equipment. Protected against short circuits and damage from mis-use.

Z40 Specification
(2¼ in x 3 in x ¾ in.) 8 transistors. **Input sensitivity:** 100 mV. **Output:** 12 W RMS continuous into 8 Ω (35 V). **Frequency response:** 30 Hz – 100 kHz ± 3 dB. **S/N ratio:** 64 dB. **Distortion:** 0.1% at 10 W into 8 Ω at 1 kHz. **Voltage requirements:** 12 V – 35 V. **Load imp:** 4 Ω – 15 Ω; safe on open circuit. Protected against short circuit.

Price: £5.95 + VAT

Z60 Specification
(2¼ in x 3¼ in x ¾ in.) 12 transistors. **Input sensitivity:** 100 mV – 250 mV. **Output:** 25 W RMS continuous into 8 Ω (50 V). **Frequency response:** 10 Hz to more than 200 kHz ± 3 dB. **S/N ratio:** better than 70 dB. **Distortion:** less than 0.1% at 12 W into 4 Ω at 1 kHz. **Voltage requirements:** 12 V – 50 V. **Load imp:** 4 Ω min; max safe on open circuit. Protected against short circuit.

Price: £7.45 + VAT

Project 80 power supply units

Range of power supply units to match desired specification of final system.

P25 Specification
Unstabilised. 30 V output. Including mains transformer.

Price: £5.95 + VAT

P26 Specification
Stabilised. 35 V output. Including mains transformer.

Price: £8.95 + VAT

P28 Specification
Stabilised. Output adjustable from 20 V to 60 V approx. Re-entrant current limiting makes damage from overload or even shorting virtually impossible. Without mains transformer.

Price: £8.45 + VAT

Project 80SQ quadraphonic add-on kit

Converts your existing stereo hi-fi system to quad using solderless connections

Contains following Project 80 units:

Project 80 SQ quad decoder/rear channel pre-amp and controls unit

2 x Z40 power amps
P25 power supply unit
Masterlink unit
On/off switch
plus pre-cut wiring loom with clip-on tagged wire connections, nuts and bolts, instruction manual.

Price: £44.95 + VAT

Sinclair Q16 speaker

Original and uniquely designed speaker of outstanding quality.

Specification
(10¾ in square x 4¾ in deep.) Pedestal base. All-over black front. Teak surround. Balanced

sealed sound chamber. Special driver assembly. **Frequency response:** 60 Hz to 16 kHz. **Power handling:** up to 14 W RMS. **Impedance:** 8 Ω.

Price: £8.95 + VAT

1. Add-on quad to existing system:

12 W per rear channel RMS

Quadraphonic decoder + 2 x Z40 amps + 1 x PZ6 power supply + (existing stereo amplifier) + 2 x Q16 speakers + (2 existing speakers) + (turntable). Total Project 80 cost: £57.70 + VAT.

2. Add-on quad to existing system:

25 W per rear channel RMS

Quadraphonic decoder + 2 x Z60 amps + 1 x PZ8 power supply + (mains transformer) + (existing stereo amplifier) + (2 x equivalent speakers) + (2 x existing speakers) + (turntable). Total Project 80 cost: £42.30 + VAT.

3. Quadraphonic system built from scratch:

12 W per channel RMS

Pre-amp/control unit + quadraphonic decoder + 4 x Z40 amps + 2 x PZ6 power supply + 4 x Q16 speakers + (turntable). Total Project 80 cost: £110.40 + VAT.

What more can we tell you?

All Project 80 modules are backed by the remarkable no-quibble Sinclair guarantee. Should any defect arise from normal use within a year, we'll service the modules free of charge. And our Consumer Advisory Service is always available if you run into any problems. You'll find Project 80 at stores like Laskys and Henry's – but before you look, why not get really detailed information? Clip the FREEPOST coupon for the fully-illustrated Project 80 folder – today!

Sinclair Radionics Ltd,
London Road, St Ives, Huntingdon, Cambs., PE17 4HJ.
Telephone: St Ives (0480) 64646.

sinclair



To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me, by return post, a copy of the fully-illustrated Project 80 folder.

Name _____


Address _____

Please print FREEPOST – no stamp needed

WW/5/75

Switch to complete protection. Switch to EEV.

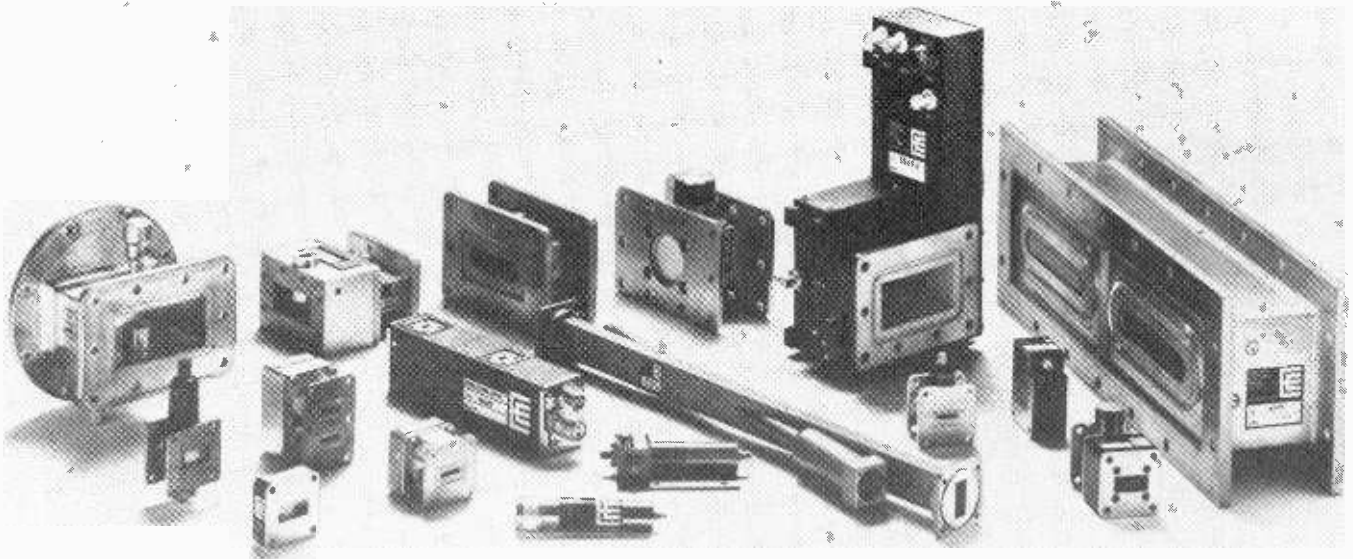A selection from the EEV range. We have more than 300 types of duplexer devices currently in production.



The receiver is one of the most important components in radar equipment. And one of the most delicate.

Unless the receiver is completely protected, sensitivity will be degraded and performance adversely affected.

You can give your receiver the protection it needs — by using EEV duplexer devices.

We can supply high-quality devices for all power levels and radar functions. The EEV range includes:

- TR tubes. ● TR limiters (primed and primerless). ● Pre-TR tubes. ● Protector tubes.

- PIN switches. ● Solid state limiters.
- Balanced duplexers. ● Mixer receivers.
- RF heads. ● Monitor diodes. ● Noise sources.

EEV appreciates the importance of duplexer devices. They are a major part of our total microwave capability.

Backed by Europe's best research, production and test facilities, we can provide devices which exactly meet your needs.

Whatever you want to protect, try EEV's range for size. Write or 'phone for duplexer device data. Or, even better, tell us your precise requirements.

EEV and M-OV know how.

Letters to the Editor

INTERFERENCE FROM POCKET CALCULATORS

Widespread use of the pocket calculator is creating interest in the levels of its radiated interference especially in certain electromagnetically critical environments such as aircraft. Instances have been recorded of interference with radio navigation equipment as a result of the operation of pocket calculators within several metres of aircraft radio direction-finding equipment. I hasten to add that for commercial aircraft, however, tests have indicated that passenger use of pocket calculators has not affected flight deck instrumentation.

As a related example I observed severe interference in the measurements obtained from an electro-encephalograph (e.e.g.) as the result of the operation of a hand-held calculator in the vicinity of the e.e.g. pick-up unit. Needless to say, the results of measurements performed under such circumstances would be useless.

It must be pointed out that the signal levels emanating from pocket calculators are not their "exclusive property". Any operating digital processing system suffers from the same malady, and at most computer installations great pains are taken to provide adequate shielding of electromagnetically sensitive components (magnetic tapes, memory unit, etc.).

As a final item of possible interest I would like to quote from an issue of *Approach*, the naval aviation safety review of the US Navy, December 1974:

"A Word To The Wise

Recent tests by the Canadian Department of Communications have established that hand-held electronic calculators cause a degree of interference in ADF signals when the calculator is operated in close proximity to the ADF antennas. It is not necessary that operations be performed on the calculator, only that the calculator be turned on. Pilots should be aware of this and use ADF indications cautiously when hand-held calculators are being used in the cockpit."

Charles Thomas Ristorcelli,
US Navy Postgraduate School,
Monterey,
California, USA.

Later this year we shall be publishing an article by Lt Ristorcelli on radio interference from pocket calculators.—Editor.

CAPACITORS AS TRANSMISSION LINES

I found Mr R. A. Fair's article on capacitors in the December 1974 issue of your magazine interesting and useful. However, this article, as well as many others I had read, omits an equivalent circuit of greatest importance to designers of v.h.f. and u.h.f. circuits.

Tubular and flat ceramic capacitors, especially with high-K dielectric, often exhibit a behaviour of open-ended, lossy transmission line stubs, with periodic impedance peaks and valleys of decaying amplitude *v.* frequency.

This transmission line effect can be easily demonstrated by using a grid-dip meter in the oscillating mode. For example, if a 5nF bare disc capacitor is inserted in the cut inductance for the 100 to 250MHz band (thus completing the interrupted loop of the inductor), one will observe at least two oscillator drop-out frequencies when tuning through the band, with strong fluctuations of the meter reading between these points. The frequencies of high impedance where oscillator activity ceases depend on many factors: physical dimensions of the capacitor (length of stub) including the location of coil connections to the capacitor's plates, dielectric constant of the ceramic material (propagation constant), etc.

I have seen occasional references in technical periodicals to some "mysterious" and erratic behaviour of bypass capacitors at very high frequencies. I am certain that there is no mystery if one considers such capacitor as a transmission line, and the erratic behaviour of some capacitors of same value can be explained by differences in physical dimensions, in the value of K, location of lead connection to the plates, and losses of the dielectric material, even if capacitance is the same.

Alex Azelickis,
Morton Grove,
Illinois, USA.

SINGLE LAMP F.M. TUNING INDICATORS

Having let several letters on the above subject go unchallenged, I now feel that it is time to speak.

The challengers have in general all fallen into the same trap, which stems from the fact that they have all been intelligent, technical people! The emphasis here is on the "technical", in the electronic meaning, which is not a virtue when trying to understand the requirements of the non-technical, who, almost by definition, do not read *Wireless World*.

I was recently visiting a friend who had just purchased a new tuner-amplifier. The friend in question is not unintelligent, being well up the ladder in civil engineering, but qualifies as non-technical in the electronic meaning. During conversation I was asked to explain the legend "contour"

against one of the push-buttons of his amplifier. I leave to your readers' imagination the trouble I had.

My friend can cope with his two-lamp system, after it has been explained to him. A person with less intelligence (unfortunately the vast majority) will have trouble even when it has been explained. For instance, both lamps are lit when there is no station tuned at all! Confusion right away.

I agree that the two-lamp system displays more information, if we know how to read it, but is it really useful? It is human nature, I submit, to converge onto the correct point with a less than critically damped oscillation. Once tuned, the a.f.c., which can make use of the extra information, should eliminate the need to readjust, or it is not worth having. Let the inter-station mute circuit mute the indicator lamp also, as in our design (June 1974 issue, p.173), and the lamp becomes a "station" indicator rather than a "tuning" indicator proper.

It is hard for people who have been brought up with a soldering-iron in their hand to understand that others have not been blessed likewise, and it is a pity that so much of what is made for the general public has to be designed by these informed ones. Perhaps all design labs should have a "standard idiot" on the payroll to test our efforts. I think we would all get a shock.

J. A. Skingley,
Icon Design,
Purton,
Wilts.

EASIER TO BECOME A RADIO AMATEUR?

Cyril Parsons, 1975 President of the RSGB, will get a great deal of advice on how to run things in Doughty Street but I hope he doesn't take too much notice of the hints dished up by Pat Hawker in your January issue.

There are very good reasons why we should have expansion of amateur radio by making it easier to become an operator. If we don't fill up some of those wide open spaces on the 21 and 28 MHz bands with "operators" the consequences could well be worse than a possible devaluation of the amateur licence. A listen around 21 and 28 on Sundays at local midday will show just how active the real c.w. operators are: the hush is deafening, but not because of "conditions".

Pat Hawker is concerned about mode and band rivalries. Surely they are the same thing and stem from the one cause, that is, the technically competent operator limited to short distance communications due to a lack of a c.w. capability who would give his ears to work s.s.b. dx.

There is a simple and perfectly logical answer to the problem, and that is to remove the requirement for a Morse test from the amateur radio exam conditions. By all means let those of us who would rather use c.w., and I am one of these,

do so. The exam is an anachronism; a bad operator need not be listened to or communicated with.

Having freed our amateur operator from the rigours of the Morse code let us now take the next bold step and emulate the American FCC by getting rid of the requirement to keep a log of communications. Basically there is no logical reason why an amateur operator should keep a log; who he contacts and at what times are of absolutely no interest to anyone but himself. The only constraint placed on amateur operating is on message content and this is not logged anyway, so away with the log book; contest operators and certificate claimants will have to make their own arrangements.

Maybe the reason Japan outsells Britain in electronic products by almost ten to one is because the amateur radio operators in the respective countries are in the same proportion.

J. F. Dunglinson, G4CGW, ex 5Z4JX,
Blantyre,
Malawi.

F.M. TUNING INDICATOR

In Circuit Ideas in the July 1974 issue, J. S. Wilson contributed a d.c. op-amp circuit for general a.f.c. applications in f.m. tuners. I have built a Nelson-Jones tuner and found that the author's "winking l.e.d." tuning indicator extinguished asymmetrically under off-tune conditions.

I have used the contributor's op-amp circuit to provide extra gain in the a.f.c. feedback loop and I have added two l.e.ds, driven by the output (which is limited to 25mA on short circuit), as a tuning indicator, as shown in the diagram.

The gain of 100 (1M Ω feedback) was too strong for use during tuning but lowering the gain too far reduced the sensitivity of the indicator. The compromise adopted is a gain of 10 (100k Ω feedback) but a higher gain could be employed for l.e.d. sensitivity with a larger series resistor to buffer the local

oscillator, although its effect on the audio filter (1M Ω decoupled by 100nF) should be taken into account.

R. D. Post,
London, W10.

DOPPLER EFFECT

I note the comments made by Mr J. Moir (October 1974) and "Cathode Ray" (December 1974) concerning Doppler effect and respect their views, but I still require convincing that this effect is responsible for the distortion measured, despite the correlation of actual and predicted results. There is no question concerning the existence of phase modulation in loudspeakers, due to the imperfect piston action of the cone.

Although it would seem to be a "red herring" the controversy concerning the simultaneous existence of carrier and sidebands in an electromagnetic propagating medium is elegantly resolved by considering the practical working and results obtained from such devices as the threshold extension demodulator, where we suppress our tendency to think of the signal transformed by the use of Bessel's functions and consider the physical actuality of instantaneous frequency. However, we are handicapped by the elusive nature of the propagating medium and final judgement on this issue must wait for future developments.

There is no such handicap when considering sound propagation in air. The physical properties of the medium are well known. The nature of sound propagation is accepted as the devolution in wave fashion of the adiabatic expansion and contraction of adjacent volumes of air in a periodic manner. The periodic motion is only sinusoidal when the medium is propagating a single frequency. "Cathode Ray" is therefore incorrect when he writes concerning one "small amplitude high frequency wave being carried by that sinusoidally moving air" (my italics). We may resolve the wave into its sinusoidal

components, but, as I tried to explain in my letter published in the August 1974 issue, the conception of the propagating medium, whether it is a loudspeaker cone or air vibrating at two sinusoidal frequencies simultaneously, requires parts of the medium to be in two places at the same time. The physics of the medium preclude this conception which, I stress, is a mathematical transform of the reality.

Finally, can Mr Moir explain how he eliminates the supposedly present Doppler effect from his measuring device? If it exists in loudspeakers then it must be present in microphones and all similar transducers. The problems in deciding whether it is additive or cancelling should take some fairly strenuous analysis to resolve! Of course, the ear, as the final arbiter of good sound, would prove an even more difficult topic for consideration.

David H. Edgar,
Suva,
Fiji.

LIQUID-COOLED POWER AMPLIFIER

I have studied with great interest Messrs Stefani and Perryman's liquid-cooled power amplifier design (December 1974 issue) and have come up with a few questions.

Have they experienced problems with the power output short-circuiting through the water coolant? (I would assume the "Prestone" inhibitor is to increase corrosion resistance, not decrease conductivity.)

Why have they used MJ4030 and MJ4033 transistors, which can dissipate up to 150 watts each at 25°C? When using water cooling they could probably have used lower power and therefore probably cheaper Darlington pairs (e.g. MJ900 and MJ1000s which, incidentally, have an h_{FE} of about 6000 at $I_C=3A$ d.c. as opposed to 3500 at 10A d.c.).


What is the input sensitivity to the pre-amplifier for the rated output?

Apart from possibly changing one or two transistors (such as the BSY95A) for higher voltage equivalents (for example BSY54), would any other components need to be changed to run at (say) 50 volts supply?

Paul Lenartowicz,
Hounslow,
Middlesex.

Dr Perryman and Mr Stefani reply:

No problems have been experienced with leakage currents through the water. The resistance of the water will be of the order of 1k Ω and this provides only a slight additional load. However, if any water escapes near the input pins of the transistors the whole stage becomes inoperative and damage may result. Mr Lenartowicz is correct in assuming the purpose of the "Prestone" is to act as an inhibitor of corrosion and organic growth.

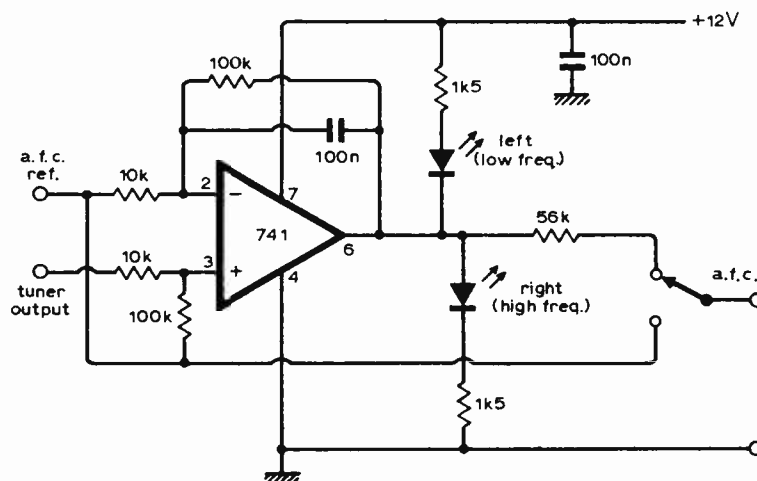

The MJ4030 and MJ4033 transistors were selected for their very high peak collector currents, because the amplifier was required to supply large current pulses to saturated iron specimens. If lower currents are needed there may well be more suitable types of output transistor.

The input to the preamplifier for full output of 230W is approximately 150mV.

Finally, if the voltage is to be raised substantially it will be necessary to use transistors of higher rating and also to raise the load resistors of the driving stages (marked R_1 in Fig. 5). For a 50V supply it is suggested that 10k Ω resistors should replace the 5.6k Ω ones used in the original circuit. It will also be necessary to increase the signal handling capacity of the pre-amplifier, and if this is done by raising the voltage to 50 then the 4.7k Ω load resistors at the output of the preamplifier should be increased to 10k Ω .

SOLID STATE DIGITAL CLOCK

Several readers have asked whether it is possible to use a larger display in my digital clock (Feb. and Mar. 1975). I used a Texas TIL360 in the original design to reduce to a minimum the printed board area taken up by the display. A larger display can easily be used if required. The procedure is as follows:

1. In place of the TIL360 on the p.c. board mount a 16 pin dual-in-line i.c. socket.
2. Mount the selected displays on a small piece of Veroboard or p.c. board fitted with 16 wire pins and plug it into the i.c. socket on the main p.c. board.
3. The displays used must be common cathode GaAsP displays. Suitable types are Litronix Data-Lit 4 or Data-Lit 44, or Monsanto Man-4.

These displays give a useful increase in display size without any circuit changes. The peak segment current is about 15mA; this represents a peak digit current of 120mA. The segment current may be increased by reducing the value of R_{24} to R_{30} and R_{16} from 680 ohms. I would not advise an increase in segment current above about 20mA (R_{24} , R_{30} and R_{16} > 470 ohms).

Some of the large seven-segment displays require quite large peak currents, particularly the green GaP displays; also, due to saturation effects in gallium phosphide these displays are often unsuitable for high-brightness multiplexed displays of more than four digits.

David D. Clegg,
London SW10.

SDS Components Ltd have told us that they do not handle the MOSTEK clock chip used in the digital clock.

Having read Mr Clegg's articles in the February and March issues with interest I would like to offer some constructive criticism based on my own experiences.

Basically, I cannot accept his argument

for the rejection of mains as the frequency standard. If, as the article suggests, one assumes that the clock will be used mainly for recording off-air programmes then it will most likely be built into or near to any existing radio and recording equipment and thus portability will be of little consequence.

The frequency stability of the mains is sufficiently accurate for the recording of off-air programmes since the BBC uses electro-mechanical time-switches to switch on Open University programmes and the accuracy of these is only a couple of minutes.

If the mains fails you are unlikely to be able to make a recording either!

The use of a crystal controlled frequency standard may be technically more aesthetically pleasing but I feel that in this instance it is unnecessary.

Having accepted the premise that the clock will be closely associated with any existing recording hardware, a better clock chip to use is the Emihus EDC 6051. This is cheaper and as a bonus has full stop-watch facilities which are invaluable when timing programmes or elapsed recording time, etc. Another possibility with this chip would be to combine it with the Emihus ETT 6016 touch tuner and so provide "touch control" of the logic functions.

R. M. Sinden,
East Sheen,
London, SW14.

Mr Clegg replies:

I can only agree with Mr Sinden's statement that the mains frequency stability is sufficient for the recording of the Open University Programmes in the early morning, since, as he points out, the BBC uses electro-mechanical time switches. The use of the mains as a frequency standard is also ideal for a four digit domestic clock displaying only hours and minutes; it is not suitable, however, for a six digit clock which also displays seconds, there being little point in a seconds display which is incorrect by more than a few seconds!

The problem of off-air recording *in absentia* provided the initial incentive to design this clock and I felt that a small, self-contained clock would have many additional uses.

I designed this clock between July and September 1973; were I to start the design today I would probably use the same chip.

ELECTRODYNAMICALLY INDUCED E.M.F.

Only the tip of an electromagnetic iceberg is indicated by C. P. J. Meade's letter in your February issue. Argument as to the true source of electro-dynamically induced e.m.f. has continued since Faraday's time. A relativistic hypothesis which seems to have attracted little notice until recent times advances the idea of relative motion between a conductor system and an observer as being a fundamental requirement for such induction¹. This would

appear to be substantiated by simple experiment², albeit for non-uniformity of magnetic field and motoring behaviour.

Further disputation on this subject may appear futile to your readers; but there is strong personal opinion that each bout of controversy advances our knowledge a little further; and with an intuition akin to that displayed by "Cathode Ray's" reply to Mr Meade, I feel that the hidden portion of our iceberg contains profound secrets relating to the true nature of electricity, magnetism and gravity.

John Gray,
College of Technology,
Belfast.

References

1. "Unipiece Electrodynamically Rotating Machines". J. Gray, *Marine Engineers Journal*, September 1968, pp.4-6.
2. Various letters throughout 1970 in *I. E. E. News*, J. Gray, with particular reference to issues dated February 23, 1970 (p.4) and October 12, 1970 (p.4).

TRANSISTOR CIRCUIT DIAGRAMS

We have had the transistor since 1948 but have not yet reached a satisfactory standard method of drawing transistor circuits. The matter is brought to mind by the article "The monostable . . ." in the January issue.

The authors' Fig. 9 contains a complementary pair of transistors and a negative supply line at the top of the diagrams. What then is the meaning of the sketch which indicates the triggering pulse? Does it mean that the base potential of Tr_1 is to be driven in the direction of the emitter, as indicated by a glance at the diagram? Or does it mean that this is the appearance of the waveform as viewed on the screen of an oscilloscope as normally operated? Had I not known the answer before examining this diagram I would not know it now.

In a circuit where all transistors are of the p-n-p type there does exist an argument (in my opinion a very poor one) for having the negative line at the top of the diagram, but what is the argument for so doing when the circuit contains an equal number of p-n-p and n-p-n transistors, and even, as I have seen in some examination questions, only n-p-n transistors?

It is a pity that Mr Amos did not mention this subject in his November 1974 article on diagrams. (Incidentally, I do not like the technique employed elsewhere by Mr Amos of mixing the two conventions in one diagram.)

Bearing in mind the facts that the "positive-upwards" convention has been standardized for so long, and that we must all work with conventionally connected oscilloscopes, should we not retain the positive-up convention as our standard?

Roy C. Whitehead,
Cape Town,
South Africa.

75 years of magnetic recording

3—From steel to plastic

by Basil Lane, Assistant Editor, Wireless World

From 1939 the Magnetophone entirely supplanted other methods of master recording in German broadcast studios. It was this unique state of affairs, discovered by the Allied forces after World War II, that was to revolutionize design in Europe and America from 1945 and sound the death knell for steel tape and wire.

The national political situation in Germany was explosive and international relations were deteriorating fast, the dark years of World War II were drawing in on the Western World. For those outside Germany it was as if the Magnetophone had never been; very few reports on the machine had been written and fewer engineers had heard it. The war was to reduce information on the Magnetophone to nothing and it was not until 1945 that the world (that is the recording world) was to be rocked by the progress made during the war.

In America, progress was slow, probably due to the early embargo on published information about the Telegraphone set by Rood, the President of the American Telegraphone Company some years earlier. Bell Laboratories developed experimental steel tape machines,³⁸ and in 1939 made the first ever stereo recording on a magnetic recorder. In this instance the machine used steel tape on two reels locked in synchronism on the same machine. In 1937 the Brush Development Company produced its Soundmirror, a steel tape-loop machine designed for laboratory investigation of transient phenomena. By 1939 they had also introduced a black oxide paper tape, presumably for the Soundmirror.

In 1941 Brush, General Electric and the Armour Research Institute went into production with wire recorders for the armed services.¹³ A young man with a brilliant career ahead, Marvin Camras, developed the long-forgotten a.c. bias method and Armour Research applied for a patent on it. In 1942 Camras designed the Model 50 wire recorder, bought for use by the BBC³⁹ and used extensively in airborne service, followed by the Webcor wire recorder used by the US Navy.

Just before the end of World War II, Brush asked Minnesota Mining (3M) to develop better tapes and under Dr Ralph Oace, work commenced in 1944.

The revelation—1945

With the war over and the Allied Forces occupying Germany it became possible to see just how much tape recording had progressed. There are many quite amazing and fascinating accounts of those who studied the German recording techniques, some quite official, forming part of Government committees such as the British Intelligence Objectives Sub-Committee (BIOS) and FIAT the American equivalent, others being quick private investigations by those who had a fascination for these things. Many post-war companies specializing in the production of tape recorders or tape were started by these men, including the Mincom division of 3M, initially Crosby Enterprises, and Rangertone run by Col. Ranger, one of the American Army engineers in Germany at the end of the war.

The first surprise for those who investigated broadcasting in Germany was the extent to which magnetic recording had been adopted. All broadcast stations had Magnetophones and in addition they were in use in the signals sections of the German Army, the Intelligence and in some cases in use in the telephone system. Almost none of the radio station output was live, since tape was used as a method of censoring the programmes. This idea was developed way back in 1939 as an expediency for political broadcasts, all of which were carefully vetted.

The really surprising feature of those machines at the radio stations was the quality of the output. This had been due to the development by Dr Braummühl and his colleague Weber of the a.c. bias system, first applied experimentally to the K4 Magnetophone. In fact the variety of machines had proliferated and just to give an idea of what had become available the following is a list of those for which the author has documentary record. The K4, also designated R.24 by the RRG was made with d.c. bias but con-

verted in some instances to a.c. bias by RRG and called the R22. It was originally introduced in late 1938. There was a dictating machine, the FT-3 few details of which are available. The Tonschreiber b: portable field unit used by the Wehrmacht for signals, fitted with a rotating pitch restoring lead. Tonschreiber c: spring-driven lightweight signals recorder. Tonschreiber d: conversion of the Tonschreiber b for use by war correspondents. Tonschreiber f: dictating machine used as a successor to the FT-3. The A1000—L40 naval communications recorder also known as the RE-3. The R-26: spring driven portable for war correspondents. The model HTS: a high quality studio recorder with a.c. bias, also designated the R122a by RRG.⁴⁰ The K7: studio machine developed in 1945, produced in immediate post-war period.

A stereo Magnetophone had been developed by RRG starting about 1942 using the R22 version of the K4. Approximately four machines were made with stacked stereo record and replay heads.⁴¹

The Magnetophone

One of the most remarkable features of the Magnetophone machine produced by AEG was how little it differed, in mechanical detail, from those studio and high-quality domestic machines we see today.

Fig. 1 is an early K4 Magnetophone showing how the tape is spooled on open platters with a large hub of similar dimensions to the now commonly known NAB reel. In this, and all other machines up to about 1948, the tape is reeled with the oxide out, thus siting the head block, which is interchangeable, on the near side of the machine facing to the back.

On the left of the head block, which contains erase, record and playback heads, is a heavy guide roller designed to reduce longitudinal flutter in the tape to a minimum. To the right of the heads under the cover is the drive capstan and pinch-wheel assembly from which the tape feeds directly to the

take-up spool.

The transport arrangements also included a lifting device which allowed the tape to be moved away from the heads during fast rewind. Three, or in some cases four, motors were used to transport the tape, two being used as reel motors. These motors had an inverse torque versus speed characteristic and were originally commutator-type, series wound. Later versions used a.c. motors without commutators.

Constant-speed tape drive was achieved with a two-phase capacitor-type of synchronous motor. Solenoid-operated brakes were fitted to each reel motor and an interlock was provided on the record and play button, reducing the chance of accidental erasure of the tape. The K4 mechanism and subsequent machines to the end of World War II, all followed this arrangement but differed in detail from model to model.

After the general adoption of the K4 by the Reichs Rundfunk-Gesellschaft (RRG) in 1939, there was considerable co-operation between them and AEG in the development of further models. In fact in late 1939, Dr Hans Joachim Braummühl and Dr Walter Weber of the Research Department of RRG developed the a.c. bias system for use in the K4 types in broadcast service²¹. The broadcast version of the K4 was designated R22 or R22a and the subsequent modified versions with a.c. bias were redesignated R122 or R122a.

One of the novel features of all of the Magnetophone models was the use of ring-core heads and longitudinal recording instead of the previous arrangements used on steel-tape machines. A parallel development seems to have been made by British Thompson-Houston in December, 1933, since they made an application for a patent⁴², granted in 1935, which describes various configurations of ring-core heads, including the notion of cross-field biasing* and the use of compressed iron powder cores for erase heads.[†]

Several non-broadcast tape recorders were also produced by AEG during the war years, one of the most remarkable being the version known as the Tonschreiber b. This machine was used principally by the Wehrmacht to record high-speed telegraph signals from a radio⁴³. A secondary playback head could then be brought into use to "slow down" the replayed signals without loss of pitch. The head was a rotating drum assembly, shown on the left of the main head block in Fig. 2 and marked with the number 11.

It consisted of four reproducing heads equally spaced around the periphery and a commutator which connected each head to the replay amplifier for 90 degrees of the revolution. This complete assembly could be driven by a separate variable-speed motor which would revolve the drum in the same direction as the tape. This effectively reduced the head-to-tape speed

* See concluding part of this series.

† In practice, BTH may have had some sort of co-operative agreement with AEG since a later patent was taken out by BTH on behalf of AEG.

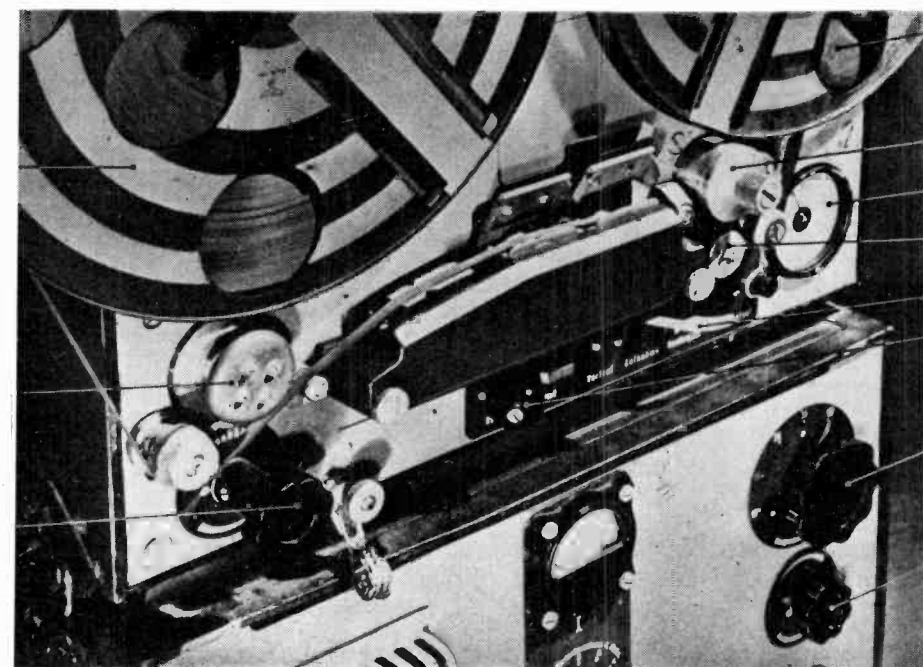


Fig. 1. An early K4 Magnetophone. The amplifier and speaker were contained in two other separate boxes. (Courtesy AEG Telefunken.)

Fig. 2. A close-up of the transport arrangements of a Tonschreiber b. The picture is taken from a BBC Research Department Report and carries their legends. (Courtesy BBC.)

and thus the pitch of the tone without reducing the rate at which the total signal could be transcribed.

The Tonschreiber b had the facility of being operated at any one of nine tape speeds from 9cm/s up to 120cm/s, this being achieved by altering the frequency of the master oscillator supplying the speed-regulating synchronous control motor.

This low-powered motor was directly coupled to a more powerful non-synchronous motor which provided most of the torque required to transport the tape. Using this double-motor arrangement thus reduced the power requirement from the oscillator.

The BBC carried out some voice tests using this recorder, and which the author has heard. The effect on playback is quite peculiar, being somewhat akin to the sound of someone talking down a long length of metal pipe. Obviously not intended for high-quality recording, the Tonschreiber b was, however, a very clever device designed for pure signals use.

Stereophonic recording

Although P. O. Pederson had described a method of multiplexing two audio signals on to a telegraph wire in 1903 and Bell had succeeded in making binaural trans-

missions⁴⁴ by telephone in 1892, there had been few attempts to record a genuine binaural or stereophonic signal by the time of World War II starting.

There had been one classic example of a stereo magnetic recording made at the American World's Fair in 1939 by Bell Laboratories⁴, but this used a steel-tape machine with two reels of tape of a new alloy called Vicalloy, clamped in parallel on the same transport and driven by a common shaft. The tape speed for this new type of tape had dropped to 16 inches per second, a cut of more than half the speed of the Blattnerphone machines.

However, as far as magnetic recording is concerned, this is where the matter seems to have rested—except for Germany. The broadcast organization RRG had, in 1942, commenced experiments with some prototype models of stereo tape recorders. These were adapted from the model K4 (R122 type) by RRG Laboratories and fitted with the first known examples of a multiple ring-core head with the tracks in the same vertical alignment⁴¹.

No record pre-emphasis appears to have been applied, the entire equalization being achieved in the replay chain. This was not an entirely satisfactory state of affairs and in the immediate post-war period suggestions made by the BBC to divide equalization between the record and replay amplifiers was adopted.

By the end of the war the Magnetophone had become quite highly developed. The broadcast versions then in use, type HTS, were capable of a very good performance at a tape speed of 77cm/s—relative, that is, to the steel-tape and wire machines in use elsewhere. Frequency response was ± 4 dB from 60Hz to 10kHz with a signal-to-noise ratio of 35dB, which improved to 50dB when the excessive hum in the replay chain was filtered out. The replay amplifier was not particularly well designed since it had a signal-to-noise ratio of only 55dB⁴⁵.

At the end of the war a new type of Magnetophone was being developed, called the K7. Parts for the first 16 production models were found in the French sector of occupied Germany and an arrangement

was made for these to be assembled and divided between the French, British and Americans⁴⁶. This machine had several improvements made in the transport, and the bias frequency had been raised to 150–200kHz, but the erase frequency remained at 60kHz.

Before passing on to note the tape developments in Germany in the period 1939–45, mention should perhaps be made of other interesting machines⁴⁹. The first, called the Kassetengerät, was a playback-only machine using a continuous loop cartridge of $9 \times 5 \times 0.25$ in. Inside the cartridge was 300 metres of tape, a free loop of which was brought across a rectangular hole cut in the cartridge case. The loop of tape would be slipped over the replay head and capstan and the tape driven at 28cm/s. The high-frequency cut-off point was said to be about 4kHz.

The second idea was a proposal for recording signals on a sheet of magnetic material in the shape of a quarto sheet of paper. No models of this seem to have been made.

Tape manufacture

Mention has been made of the experimental tapes first produced by Fritz Pfelemer and his subsequent co-operation with AEG and IG Farben. By 1936 steel-tape recording had become quite popular in broadcast applications, even to the extent that AEG felt it had to maintain a foothold by patenting a novel thin layer steel foil mounted on a paper backing tape⁴⁷. However, the two companies had by then formulated several satisfactory forms of tape⁴⁶. The earliest of these consisted of spherical particles of iron of 10–15 micrometres diameter, glued to a paper or cellulose tape with an organic compound⁴⁸. Shortly after, in 1934, it was realized that an improvement in the structure of the coating could be obtained by using a film-casting technique⁴⁹. Here the magnetic powder was mixed with cellulose or p.v.c.

and a solvent, and was then cast on to a continuous travelling metal band having a highly polished surface. When set, this layer would be affixed to a paper of cellulose base and slit into tape form.

Although this was a big improvement there were still problems in obtaining a good high-frequency performance, due to the large size of the magnetic particles used. The search for suitable alternatives led the chemists of IG Farben to the magnetic oxides of iron Fe₃O₄ and gamma Fe₂O₃. Thus, by 1935 the company registered an application describing suitable preparations of these two oxides, for use as magnetic powders on tapes⁵⁰. It would appear that little further development on oxides was to occur from this date until after the war, since it had not yet been realized that there was an advantage to be gained from adopting an acicular (needle-like) form of magnetic particle.

Had this happened the tapes found by the Allies might have been much better as in one patent published, IG Farben had clearly discovered the advantages of using magnets to improve particle packing in the still-liquid casting film, and they would have also therefore discovered the advantages of particle orientation.

Historically, therefore, by the end of the war, three types of tape had been developed by IG Farben. The first of these, based on the old film-casting techniques described above, was type C manufactured at Wolfen using a cellulose acetate base. A later, rather odd type was then developed called type L. This was a homogeneous p.v.c. tape in which the oxide and base material were mixed together, plasticized and then rolled into a single-layer film. The finished product was finally stretched to reduce the possibility of deformation on the tape machine. This tape was not too successful for a variety of reasons and its manufacture appears to have ceased in 1945 or 1946. The original plant, manufacturing type L tape, was at Gendorf which was taken as part of the Russian reparations.

The last development right at the end of the war, was type LG manufactured at Wald-Michebach and Ludwigshaven. This was a coated tape using pre-stretched p.v.c. (Luvithermed) as the base material and a coating of the same sort as type C, which used γ Fe₂O₃ spherical particles as the oxide.


A comment by an investigating official on the quality of these tapes, was that batch uniformity of type C was poor and that, owing to the low elasticity of the base foil, breakage was common⁴⁶. Type L appeared to be quite uniform but suffered from print-through and finally type LG proved a considerable improvement over both types.

During the period 1939 to September 30, 1944, a total of 174,890km of tape had been sold from the Wolfen and Ludwigshaven factories together with 3,332 tape machines. This against a nil return from the rest of the world for this type of tape machine!

Reparations and recovery

After the war the Allies developed a policy

Fig. 3. The pitch-restoring head from a Tonschreiber b shown dismantled. (Courtesy BBC.)

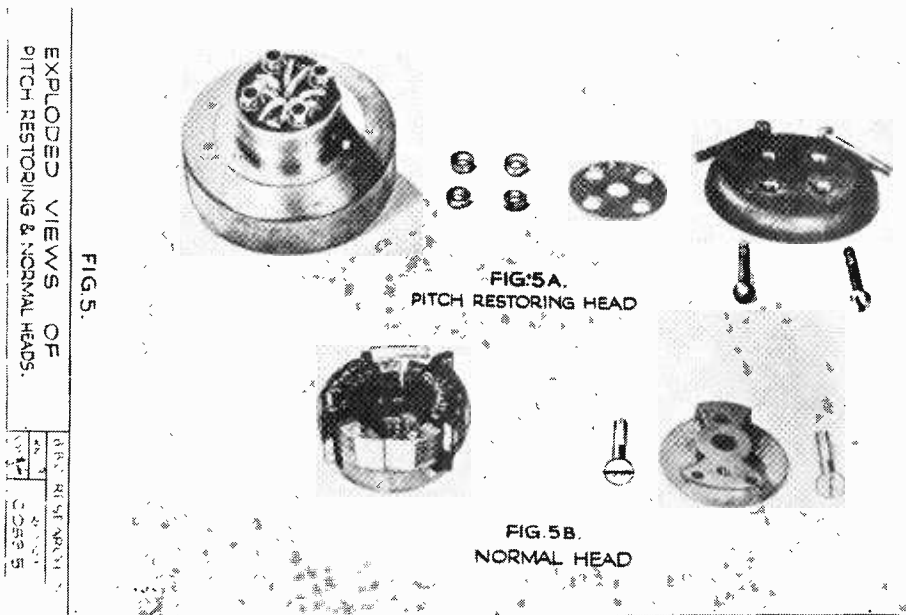

of breaking some of the very large monopolistic companies into smaller units and this was to happen to IG Farben. The factory at Wolfen, which specialized in type C magnetic tape and photographic film, became the now well-known Agfa company and the main Ludwigshafen plant became part of Badische Anilin & Soda-Fabrik (BASF). As for the Magnetophone, it was regarded as quite a novel idea—so much so that many still believe that AEG and IG Farben had deliberately kept its early development secret as part of the initial war and propaganda effort of politicians in Germany before 1939.

Certainly the Allies were not slow to make use of the Magnetophone, a large number of examples being officially and unofficially “exported” to Britain and America. They were also kept in service in the broadcast stations of occupied territories where some were quick to see the same advantages that Hitler had seen—that the tape recording could be used to pre-record political propaganda for simultaneous repeat broadcasts.

This gave rise to one rather amusing incident illustrating a vagary of Magnetophones. It would seem that one of the Allied war chiefs, probably Eisenhower, had to make a broadcast from Radio Luxembourg shortly after its capture and chose to make a tape recording prior to the occasion which would then be transmitted. This was done, and the transmission was well under way, when to everyone's horror Hitler's voice suddenly broke in on the recording. The tape was an old one which had been inadequately erased! The close of this apocryphal tale is that a prompt order came from a furious Eisenhower that fresh tapes were to be used on all future similar occasions.

From here on, the threads representing the development of magnetic recording become much more intertwined, since the rest of the world still had to be convinced that plastic-based tape was better than wire or steel tape.

There had been no development in magnetic recording to speak of in the UK during the period 1939–45; the BBC were sticking to their complement of Marconi-Stille machines and a few dozen model GE 50 American wire recorders imported some time late in the war years. In fact eight of these were installed in a mobile unit called the “Octopus” and used during the 1947 Olympic Games. However, there was a strong preference for disc recording and their use was extremely limited.

In America the story was somewhat different with two main areas of development almost competing with each other in the search for more versatile means of magnetic recording. Some time in 1940, Marvin Camras, subsequently responsible for a flood of inventions associated with magnetic recording, joined the Armour Foundation and developed a wire recorder using a.c. bias which was then produced by General Electric as the GE 50 and also by the Brush Development Company. A version found its way into USAF service and as a result of a US Navy contract, Brush went on to develop a steel-tape version.

In 1941 Marvin Camras applied, through Armour Research, for a patent on his a.c. bias method, and in 1942 completed the design for the USAF recorder. During 1943 another American company, Webcor, produced wire recorders for the US Navy and in 1944 Minnesota Mining (later 3M) started its first hesitant steps towards developing powder-coated tapes¹³.

This occurred as a result of Brush Development asking Dr Oace of Minnesota Mining to develop a thin tape, coated with magnetic powder. Results were slow in coming, partly because Minnesota had no test gear and had to return samples to Brush for testing. It seems that Minnesota did not even know what they were supposed to be producing until it became obvious, with other developments appearing elsewhere.

In 1946 Brush brought out a new Sound-mirror machine quite different from its predecessor, but seemingly entirely developed without reference to the Magnetophone, which by then was well known. The first broadcast use of this machine and its paper tape, coated with spherical particles of Fe₃O₄, was during the 1946 New York State political conventions when CBS recorded continuously for 24 hours and then used the material to edit into a “highlights” programme broadcast at the end of the day⁵¹.

This and later machines and their paper tapes were marketed in the UK from 1949 by Thermionic Products—now Racal Thermionics—who are still firmly in the business of producing magnetic tape recorders.

The birth of an industry

Although tape machines using paper-based tapes were beginning to appear in America during 1946 and 1947, it was the “liberated” Magnetophone arriving in Britain and America that was to lend a tremendous impetus to a totally new industry. Here in Britain, EMI went to work and by November, 1947 announced its first-ever tape recorder for studio use, the BTR1 console machine. Although much was owed to the Magnetophone, there were many modifications which produced a very creditable performance.

By 1948 the Abbey Road studios of EMI were using the BTR1, and some machines had entered service in the BBC. In America two men, Colonel Richard H. Ranger and John T. Mullin, had returned from Europe with samples of Magnetophones and were busily lecturing on their finds. In May, 1946, Mullin demonstrated his machines to a meeting of 250 members of the IRE, and the following day received a visit from Alex Poniatoff and others from Ampex, who showed much interest in the German machines. This meeting led to a fascinating chain of events that started the production of the first Ampex 200 in 1948. John Mullin joined forces with Crosby Enterprises to produce a taped version of the Philco-sponsored Bing Crosby Show for NBC in 1947, an event which was to do much to promote the use of tape in broadcasting. Much later Crosby Enterprises were to become what is now known as the Mincom Division of 3M.

Ranger had also been busy, since he had formed a company called Rangertone, marketing first machines and later tape. Most importantly, tape was a big problem because the German product was far from being completely satisfactory.

By a curious coincidence parallel work by Dr W. W. Wetzel, H. K. Smith and R. Herr of 3M versus Marvin Camras at Armour resulted in the production of an acicular form of γ Fe₂O₃ which Camras was first to patent.

The first practical tape from 3M was called type 100 and was a paper-based black-oxide type produced in 1947. It was followed in the same year by type 110, coated on a plastic base and using the new red oxide.

The world had at last woken up to the tape recorder and if at times the allegiance to the Magnetophone was obvious as in our own RGD domestic console type, much research and development was to ensue, resulting in a vast variety of professional and domestic products by the year 1949.

(To be continued)


References

38. Hickman, C. N. Sound Recording on Magnetic Tape. *Bell Laboratories Record* Vol 16, April 1937, pp 165–177.
39. “BBC Mobile Recording equipment” *Wireless World* Vol 50, No 5. May 1944 pp 133–135.
40. Pulling, M. J. L. B.I.O.S. Final Report No 951.
41. Menard, James Z. FIAT Final Report No 705.
42. British Pat. 429,987, (1935).
43. BBC Research Department Report, German Magnetic Recorders, First Report: Tonschreiber b. Report No. C.053, Ser. No. 1945/28, March, 1946.
44. Tinkham, Russell J. Anecdotal History of Stereophonic Recording. *Audio* May, 1952, pp. 25–31, 91 and 93.
45. BBC Research Department Report, German Magnetic Recorders, Second Report: The Magnetophone type HTS. Report No. C.053/2, Ser. No. 1946/10, August, 1946.
46. Ranger, Richard H. Further Studies in Magnetophones and Tapes, FIAT Final Report No. 923.
47. British Pat. 489,261 (1938).
48. British Pat. 333,154 (1930).
49. British Pat. 459,884 (1937).
50. British Pat. 466,023 (1937).
51. Chinn Howard, A. Magnetic Tape Recorders in Broadcasting. *Electronic Engineering*, Dec., 1947, pp. 393–395.

Circuit Ideas

Accurate current generator

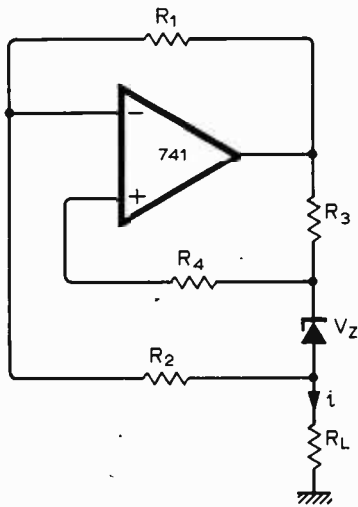Most operational amplifier constant-current circuits suffer from the disadvantage that they require a load isolated from ground. The circuit shown uses a grounded load and, using the 741 op-amp, can achieve a Norton equivalent of an ideal current source in parallel with a resistor of greater than 100MΩ when delivering one milliamp of current.



The output impedance of the current source is primarily decided by the common-mode rejection of the amplifier used. As current through R_2 is also approximately constant it does not affect the output impedance.

In the diagram

$$i = \frac{R_1 V_z}{R_2 R_3} + \frac{V_z}{R_2}$$

(the second term may be neglected if R_2 is large) and

$$R_4 = \frac{R_1 R_2}{R_1 + R_2}$$

Normally $R_L < R_1 = R_2$ and $i = V_z / R_3$.

R. Morcom,
Glenrothes,
Fife.

Voltage stabilizing a symmetrical power supply


The following description of a stabilized symmetrical power supply with overload protection may be useful to readers interested in L. D. Thomas's circuit* idea in the October 1973 issue. Voltage stabilization is by adding two transistors.

Considering the positive rail, stabilization is performed by D_1 cutting off Tr_1 and Tr_2 when the output voltage exceeds the zener voltage minus V_{be} of Tr_1 . Current through R_1 is kept constant due to the constant negative rail voltage.

In the case of heavy overload of the positive rail, the protection acts as follows. Maximum rail current is determined by R_1 and the current gain of Tr_2 . When D_1 ceases to conduct, the positive rail voltage will drop rapidly, which in turn will decrease the current through R_2 to the negative rail so that D_2 will cease conduction too. Then the negative rail voltage rises, switching Tr_1 and Tr_2 off, followed by Tr_3 and Tr_4 .

The power supply is not necessarily

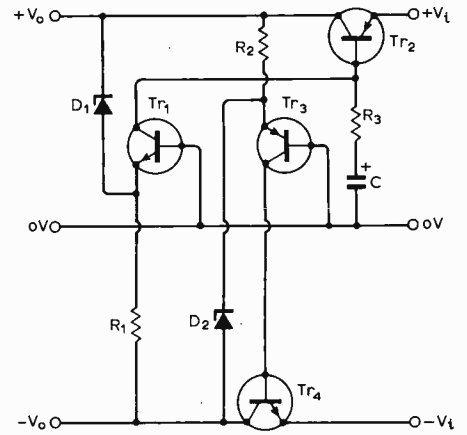*In L. D. Thomas's circuit, a 2.2kΩ resistor should be inserted between the junction of the upper zener diode and R and the reset push button and series RC components.



self-starting when connected to the proper load. A suitable C-R combination should then be used to switch Tr_2 on. If unconnected, the leak currents of Tr_2 and Tr_4 will normally activate the circuit.

The circuit has been an adequate protection of my transformer-coupled 20-watt Bailey amplifiers since 1967. It has not been possible to blow the output fuses or destroy the output transistors.

Ole Holmskov,
Hørning,
Denmark.

Wobbulator

The circuit to be described is derived from a voltage-controlled oscillator mentioned by F. Butler in a *WW* article of December 1965, page 602. In this the effective inductance of the coil is controlled by the amount of feedback.


The circuit shows how this has been modified to produce a wobbulator circuit which is cheap, and simple to set up. Feedback is now taken, without phase change, via Tr_3 . This transistor can vary the feedback in accordance with a control voltage at its base. If this is derived from the ramp output of the oscilloscope timebase the frequency of the oscillator will follow the variations in the timebase sweep voltage.


The centre frequency of the sweep may

be varied readily by adjustment of C_1 and C_2 . The circuit as described is used at 450 to 500kHz, but there seems no reason why, with a change of coil, it should not operate at 1.6 or 10.7MHz. Versions using BC107s, BF115s and BF194s have been made. Resistor R_x may need to be varied to give the best waveform with different transistors and probably for use on different frequency bands.


When the ramp voltage, which can be derived from the timebase, cannot be used directly at low impedance it is suggested that an emitter follower should be used and a suitable proportion of the output tapped off the emitter resistor.

E. C. Lay,
Eastbourne.

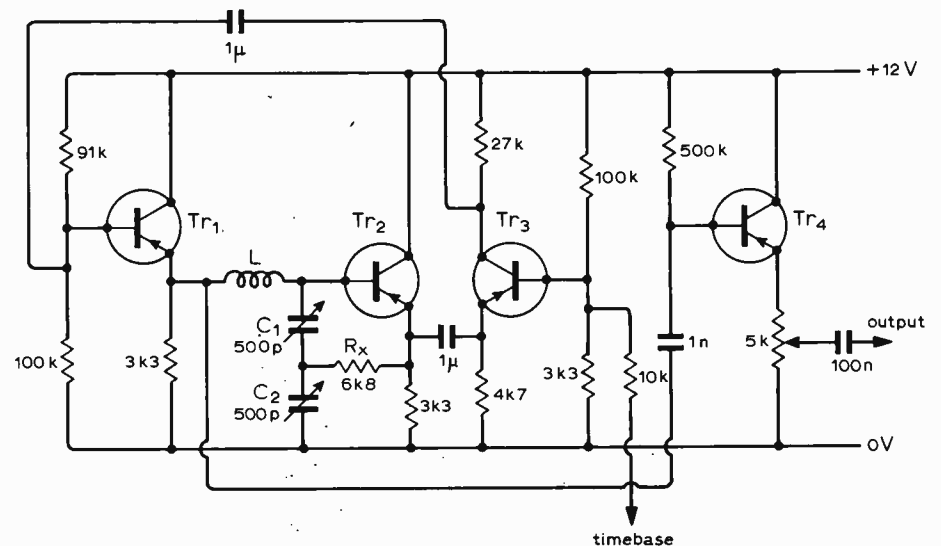


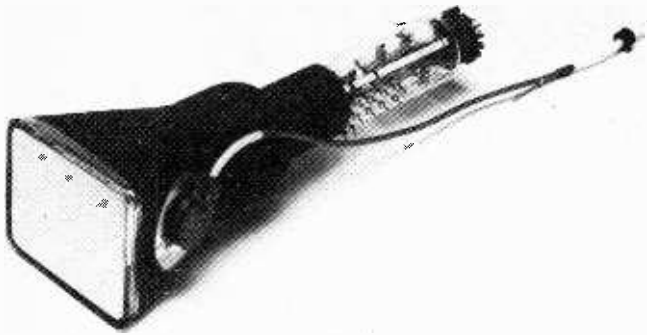

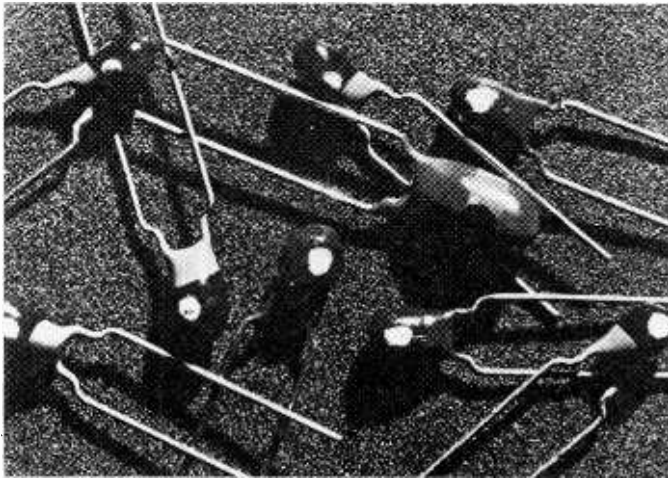
This rectangular-faced instrument cathode-ray tube, type D14-240GH/37, is one of a new range of 14cm-diagonal tubes being shown by Mullard. For use at bandwidths from 100 to 250MHz, it has a minimum writing speed of 1.5ns. Overall length is 385mm.



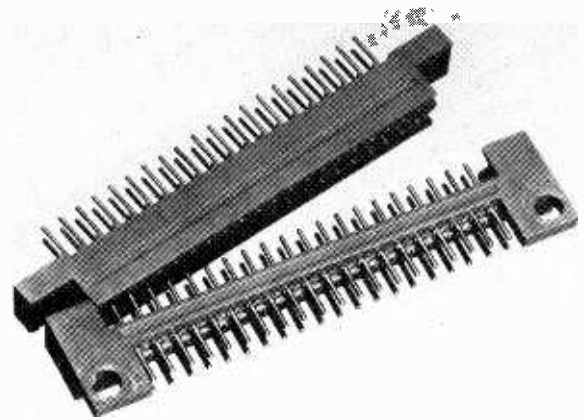A selection of "E" series capacitors produced by Union Carbide UK at its Aycliffe factory. Twelve case sizes are included in the range, covering 0.1 to 680 microfarads in voltages from 3 to 63 volts.



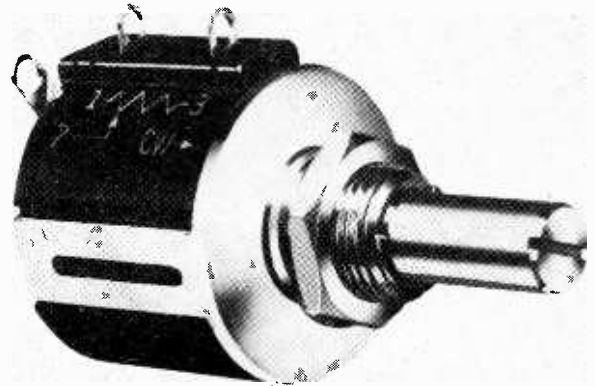This new Smiths Industries Hypertac 40-way two-part p.c.b. connector, type HPE, has parallel 0.63mm diameter contacts set in a 2.54mm grid. The free connector, containing the pin contacts, is designed for double-sided daughter board mounting while the fixed connector, containing the socket contacts, is designed for mother board mounting.



Model 3540, one of Bourns precision potentiometers to be shown at LECS.

Permanoid
Pickering Electronics
Plasmoulds
Plastic Capacitors
Plastic Screws
Plastic Seals
Plessey Interconnect
Portescap UK
Preh Werke
Pressac
Pudenz, Germany
Pye of Cambridge

Quality Audio Supplies (Q.A.S.)
Quebec Dept. of Ind. & Commerce

Racal Group Services
Radiall Microwave Components
Radiatron Components
Rafi, Faimund Finsterhoelzl.
Raytheon-Tag Components
RCA
RCL Electronics
Redpoint
Rendar Instruments
Research Instruments
Resista GmbH
Resistances
Rilton Electronics
RKB Precision Products
Roederstein & Tuerk GmbH
Ropel, France
Rosenthal China (London)
Roxburgh Electronics
Ryetric Suppressors

Saarlaendische Kondensatoren-fabrik
Saft (UK)
Sakae Tsushin Kogyo
Salford Electrical Instruments
Scanbe Manufacturing Corp
Schoeller & Co
Scopex Instruments
Sealectro
Seddon & Bramhall
S.E.E.M.
Sellotape Products UK
Semiconductor Specialist
Semikron (UK)
Siemens
Sifam
Silco, France
Silicon Transistor Corporation
Siliconix
Smith Industries (Rugby)
Smiths Industries (Cricklewood)
Sogie
Sonnenschein Accumulatoren-fabrik GmbH
Souriau (UK)
South London Electrical Equipment Co
SP Electronica SpA
Special Products Distributors
Spectrol Reliance
Spectrum Controls
Sprague Electric UK
Standard Pneumatic Motor Co
Stanley Palmer, G.A.
Steatite Insulations
Stettner & Co

Stocko Metallwarenfabriken
Stolec
Suhner Electronics
Surrey Steel Components
Suvicon
Switchcraft Inc.

Tape Recorder Spares
TDK Electronics Co
Techna International
Techni Measure
Tekdata
Telcon Metals Group
Teledyne Philbrick
Temco
Thomson-Brandt
Thorn Electrical Components
Tinsley Telcon
Tinsley, H., & Co
Toko UK
Tokyo Cosmas Co
Tokyo Sokki Kenkyujo Co
Transistor A.G.
Transradio
Transtector Systems

Ultra Electronics (Components)
Union Carbide UK
United Carr Supplies
United Systems Corp. (Monsanto)
United Trade Press
Unitrode

Varta (Great Britain)


Verity Fans (Holdings)
Vero Electronics
Vitrohm Elektroteknisk Fabrik A/S
V.T.M. (UK)

Wallis Electronics
Waycom
Wego Condenser Co
Weller Electric
Welwyn Electric
West Hyde Developments
Weyrad (Electronics)
Whiteley Electrical Radio Co
Wickmann
Widmaier, Germany
Wilson Automation
Wolsey Electronics

Zettler UK Division



Microphones matter most.

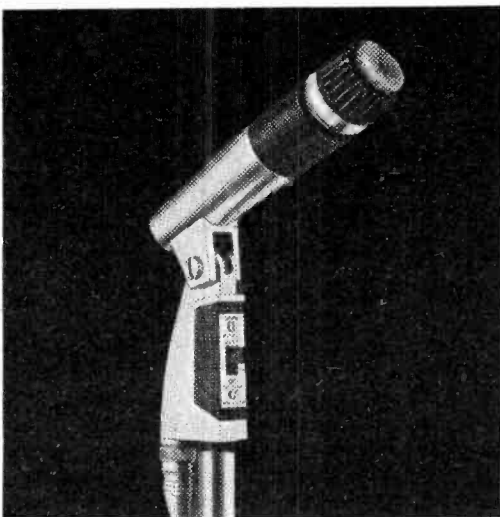

Never have so few words said so much about sound system installations. The truth is that a carefully chosen, top-quality microphone makes a measurable difference in sound system quality—regardless of the other components in the system. It is false economy at its worst to be a microphone miser. Install *Shure Unidyne* or *Unisphere* microphones—for installations with a marked superiority in voice intelligibility (and fewer service calls due to microphone problems). For the name of your local sound specialist, write:

Shure Electronics Limited
Eccleston Road, Maidstone ME15 6AU
Telephone: Maidstone (0622) 59881



WW—180 FOR FURTHER DETAILS

NEW LOW PRICES!

Sinclair Scientific kit

(Was £19.95 - save £5!)

£14.95
(INC. VAT)

Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range - features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £21.55 (including VAT).

And as a kit it costs under £15!

Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle *directly*

sin and arccsin,

cos and arccos,

tan and arctan,

automatic squaring and doubling,

log₁₀ antilog₁₀, giving quick access to x^y (including square and other roots),

plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied - all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer - they're still exceptional value. Use the order form.

Components for Scientific kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc.)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

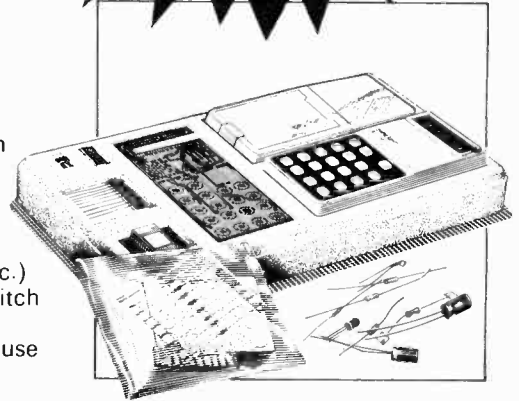

Features of the Sinclair Scientific

- **12 functions on simple keyboard**
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.
- **Scientific notation**
Display shows 5-digit mantissa, 2-digit exponent, both signable.
- **200-decade range**
- **Reverse Polish logic**
Post-fixed operators allow chain calculations of unlimited length - eliminate need for an '=' button.
- **25-hour battery life**
4 AAA manganese alkaline batteries (e.g. MN 2400) give 25 hours continuous use. Complete independence from external power.
- **Genuinely pocketable**
4 1/3" x 2" x 11/16". Weight 4 oz. Attractively styled in grey, blue and white.



DIGITAL DISPLAYS

DL707	Common-Anode 0.3" LED display	£ 1.70
DL704	Common Cathode DL707	£ 1.70
DL701	Common-Anode 0.3" ±1	£ 1.70
DL747	Common-Anode 0.6" LED display	£ 2.45
DL750	Common-Cathode DL747	£ 2.45
DL746	Common-Anode 0.6" ±1	£ 2.45
3015F	Minitron filament 12.5mm	£ 1.25
3017F	Minitron filament 17.5mm	£ 2.00
RDS1	Itoka filament 2.5"	£ 8.00
RDM2	Itoka filament 5.0"	£24.80
DG12	Phos-diode 12.5mm	£ 1.20
5LT01	Phos-diode 4 digit clock display	£ 5.80

DIGITAL CLOCKS

Digitronic I16	six digit clock	£31.00
Digitronic I1K	kit version	£29.00
Quartz and Stopwatch versions also available please ring for details and prices.		
Digitronic III	Time/date/alarm clock	£37.50
Chanticleer	4 digit alarm clock	£19.60
Industrial and laboratory clocks — ring for details or give us your specification.		
		!New Price on Chanticleer £16.60!!

DIGITAL CLOCK CHIPS

CLOCK CHIPS:

MM5314	Basic 12/24Hr, 6 digit, 50/60Hz chip. 7 seg outputs. Very popular, simple chip.	£ 7.20*
MM5311	As MM5314 but with additional BCD outputs.	£ 9.00
MK50250	6 digit alarm chip with alarm tone output, Standard basic alarm facilities.	£ 7.60*
CT7001	Time, Date & Alarm on one 6 digit chip. The Alarm can be used in 3 modes including a time switch. Clock-Radio & Snooze features. 7 seg outputs, 50/60Hz or 100.8KHz input frequency.	£ 9.80*
CT7002	As CT7001 but with BCD outputs not 7 seg.	£ 9.80
TMS3952	Stopwatch chip, most reqd. stopwatch functions 6 digits (hhmmss or mmssss), 300kHz input. 7 seg output. Special price.	£10.50
HEEC2	8 digit (HhMmSsss), stop/start/reset, 50Hz/60Hz/100kHz input, BCD output hard-wired alarm with repeat (snooze). Can also be used as 8 digit decade counter.	£ 8.50
CT6002	CMOS chip for Liquid-crystal displays, 12Hr, 1Hz colon, input 32768Hz or 65536Hz. Runs on 1.5V hearing aid battery for a year.	£15.00
MM5316	4 digit non-mplx'd alarm chip, will direct drive l-c or phosphor-diode displays.	£15.00

* Available in a MHI kit.

We advise the use of sockets for all ICs, 24/28/40 pin £1.00.

All prices on this advert exclude VAT.

BYWOOD ELECTRONICS,
181 Ebbens Road,
Hemel Hempstead,
Herts. HP3 9RD.
Tel: 0442 - 62757



WW—232 FOR FURTHER DETAILS

Your copy?



CT Series
2A 250V AC
5A 29V DC

Single and double pole, 2 and 3 position lever switches with solder lugs



T Series
5A 115V AC
2A 29V DC

Special Duty. Single and double pole, 2 and 3 position lever switches with solder lug or printed circuit terminals



PM Series

1A 115V AC
2A 29V DC
Single, double and triple pole push button switches with momentary action. Solder lug or PC terminals

It's the new easy guide to the **ARROW** subminiature superstars

Send today for your copy of this new Arrow subminiature switch brochure



Arrow-Hart (Europe) Limited,
Plymbridge Road, Estover,
Plymouth, PL6 7PN
Tel: Plymouth (0752) 701155

WW—226 FOR FURTHER DETAILS

Display devices

Survey of techniques and types on the market

The increasing use of digital techniques in measurement and information processing has, of course, demanded digital methods of displaying the information produced. As a result we have seen the emergence of a variety of electrical devices for displaying numerals, letters of the alphabet, arithmetical signs and other symbols—the general term for these being alphanumeric display devices. A typical device takes the form of a small panel on which any of the numerals 0 to 9 may be shown—particular numerals being selected by switching voltages to appropriate terminals. Several of these panels may be assembled in a row to permit a display of numbers consisting of multiple digits with a decimal point and perhaps plus and minus signs—as, for example, in a digital voltmeter.

There are various ways of generating the characters, and the methods dealt with in the separate sections of this survey are: incandescent filaments, gas-discharge devices, light-emitting semiconductor diodes, electroluminescent panels and liquid crystals. These methods also involve different techniques for constructing the shape of the characters—either forming them in continuous lines, for example with bent wires in gas-discharge tubes, or by patterns of dots or bars. A very popular “bar” technique is that seen in the so-called “seven-segment” display; this has seven bars, arranged like a “square” figure eight, from which any of the ten numerals may be built up by activating individual bars or “segments”.

L.e.d. displays

Light-emitting diodes were the first of a new breed of devices to break the hold of displays using gas discharge tubes and filament light sources. Early l.e.d. devices used gallium arsenide phosphide (GaAsP) material and normally emitted red light. To construct a single-digit seven-segment display, a large rectangular slice or several smaller slices of GaAsP would form each segment. The segments were bonded on to a ceramic substrate by epoxy and then the complete assembly was encapsulated in clear epoxy. The problems with the early devices were—large quantities of GaAsP used, misalignment of segments, optical mismatching between the l.e.d. and clear epoxy, and bubbles forming in the epoxy.


More modern displays use much less l.e.d. material for the same size characters. For small displays, around 0.040in, fabrication is normally carried out by

diffusing seven junction regions, forming the segments, into a monolithic chip of l.e.d. material. A plastic lens with good optical matching can be bonded to the chip to increase the effective digit size with little light loss. The normal magnification of the lens is $\times 2$ with $\times 2.8$ being a maximum, beyond which point lens aberrations become too great and viewing angle too small. For medium size displays, such as calculator types, segments of l.e.d. material are mounted on a glassfibre or plastic board and protected by a plastic cover which can also be a lens and/or a filter.

For larger displays, magnification is provided by light-pipes or, in the case of transparent gallium phosphide displays, reflector cavities can be used. In the light-pipe method of fabrication the top of a metal pin is used as a support/base as well as the electrical contact. A small piece of l.e.d. material is bonded to the pin and the narrow end of a cone-shaped “pipe” is placed over the l.e.d.—the wide end, which has the shape of a complete segment, goes to the top of the display. This surface can have 20 times the surface of the l.e.d. Glass-impregnated epoxy fills the light pipe and holds the complete assembly in place. When the l.e.d. is illuminated light is reflected off the side walls of the pipe and off the glass particles, giving uniformly diffused light at the surface of the pipe and a bigger and better-shaped segment. The reflective cavity method of construction is used in displays manufactured from gallium phosphide, GaP, because unlike GaAsP, GaP is transparent to red light which is emitted from the sides and bottom of the chip as well as the top. This extra light is reflected to the visible segment area.

L.e.d. materials

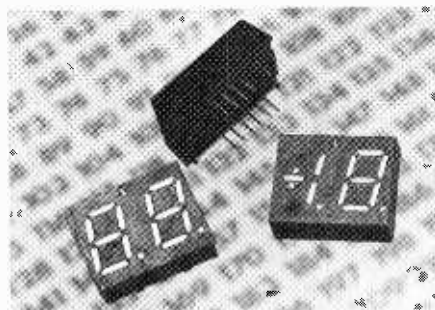The first l.e.d.s were produced by epitaxially growing a mixture of 60% gallium arsenide, 40% gallium phosphide on a



Seven-segment numeric l.e.d.s.

gallium arsenide substrate. The mixture is in the form of a vapour under pressure and high temperature in a reactor. Diodes made with the 60/40 mixture emit red light at a wavelength of 650nm. If the mixture is altered to 80% GaP, 20% GaAs the emission is yellow and at reduced efficiency. GaAsP absorbs its own radiation and light is emitted from only the top of the material. This produces well-defined displays which are inefficient by comparison with other materials, maximum efficiency, for red types, being 2%. One important advantage of GaAsP as a l.e.d. material is its non-linear current/light-output curve—the light output increases faster than the current until a thermal limit is reached. This effect is useful in multiplexed systems where short, high-current pulses are used, because it allows a reduction in total current without sacrificing brightness. Single digits can also be pulsed to achieve the same effect. Non-linearity is also apparent in GaAsP l.e.d.s of different colours from red through yellow to green.

A more recent material used in the construction of l.e.d.s is gallium phosphide, GaP. Devices using this material are manufactured by epitaxially growing 100% GaP on a GaAs substrate. Yields are not yet as high as for GaAsP devices and costs are higher. The main advantage of this material is greater efficiency, due to light emission from all sides of the junction. This type of material needs a dopant to provide emissions in the visible portion of the spectrum. If the GaP is doped with nitrogen green emission occurs at 565nm; zinc oxide gives a wavelength of 700nm (red); to obtain yellow the green can be filtered. Doping with both nitrogen and ZnO will also give yellow if the device is operated at medium current levels. As with GaAsP the efficiency drops for colours other than red but not to the same extent. One disadvantage of GaP is the lack of non-linearity, and saturation of light emission at a certain current. This makes GaP unsuitable for multiplex systems or pulsed applications.

Types of display

The most popular l.e.d. display is the seven-segment type which produces ten numerals. These are available in many sizes and four colours with the segments being single/double bars or dots. Another format called a hexadecimal display has the appearance of a seven-segment display with each segment composed of at least

MANUFACTURERS

Bowmar:	Single 7-segment; 3½- and 4½-digit displays; 9- and 14-digit miniature calculator displays, all red.
Contraves:	7-segment panel meter, red. Decode and drive logic.
IEE:	7-segment, with or without decode and drive logic, red. Dot-matrix, red.
Opcoa:	7-segment, red, green, and yellow.
Fairchild:	7-segment, red; 6- and 9-digit calculator displays, red.
Eldema/Genisco:	7-segment, red.
Hewlett-Packard:	7-segment, red; dot-matrix 3-, 4- or 5-digit, red; 3- or 5-digit miniature calculator display, red. Limited alphanumeric, red (hexadecimal).
Sanyo:	7-segment, red; 6- and 11-digit dot-matrix panels.
Litronix:	7-segment, red; dot-matrix, red; 2-, 3-, 4- and 9-digit miniature calculator displays, red.
Monsanto:	7-segment, red, yellow, green, orange; dot-matrix, red; hexadecimal, red.
National Semiconductor:	7-segment, red; 6-, 8- and 9-digit miniature calculator displays, red.
Norbain:	7-segment, red.
Diode-Lite:	7-segment, red. Decode and constant-current drive; dot-matrix, red; hexadecimal with decode and c.c. drive, red.
FM:	7-segment, red; panel meter.
Marconi:	l.e.d. arrays to customer's specification.
EEP:	7-segment, red and green.
Siemens:	7-segment, red, yellow, green or orange.
Spectra-Tek:	7-segment, red; panel meter, decode and drive logic.
Texas:	7-segment, with and without decode and drive; 3- and 4-digit dot-matrix, red; hexadecimal, with decode and drive, red.
Toshiba:	7-segment, red.
Xciton:	7-segment, red, green, yellow, with and without decode and drive.
Oki:	7-segment, red; dot-matrix, red.
TEC:	7-segment, red, green, yellow, with decode and drive; dot-matrix, red, with ROM, drive and clock; hexadecimal, red, with drive.
Plessey:	l.e.d. arrays to customer's specification.
Oshino:	7-segment, red.

four dots, producing ten numerals and six letters, A to F. For alphanumeric displays providing ten numerals and 26 letters, 14/16 segment displays or 7 × 5 dot-matrix types are used: the latter is generally preferred.

New devices

Much development is still taking place. Blue emission is one aim, and one method which has been tried is the coating of infra-red devices with a suitable phosphor. This has not been very popular because of low efficiencies. Other materials have been investigated such as silicon carbide, gallium nitride and zinc sulphide—all with little success, the main problem being that semiconductors with the large band gap necessary are very difficult to grow. Recent compounds to be studied for blue emission are indium-gallium phosphide, indium aluminium phosphide and aluminium gallium arsenide, but at the time of writing no commercial device has been announced.

A new material recently developed for general l.e.d.s is manufactured by epitaxially growing a GaAsP layer on a GaP substrate. This produces a material with the advantages of both current types—a transparent substrate which improves efficiency, generally an order better, and a non-linear characteristic making it suitable for multiplexing. Doping of the material with oxygen/nitrogen produces colours also of better efficiency.

Although there have been new devices such as the "thyropter"—a latching GaP device which, by optical feedback, stays illuminated until switched off—most development seems to be in reducing consumption for increased efficiency, and reducing the amount of l.e.d. material used for lower costs. Another area of development is in displays with integral current limiting and built-in decoder/driving chips. Several dot-matrix and seven-segment types are already available and the next two years should see a significant reduction in the cost of these devices.

Liquid crystal displays

The liquid-crystal effect is a "maverick" in the display field because light is not generated but modulated. A display operates by either reflecting light from its surface or controlling light that is passing through it; in the latter mode the device has been referred to as a light valve. As shown in Fig. 1 a display is basically a glass cell with electrodes across two surfaces of a liquid-crystal material. The electrodes are etched, in mirror images, to form characters, such as seven separate segments, and a voltage is applied across the cell. This alters the optical characteristics of the l.c. material between opposite electrodes and results in a character being displayed against unaltered l.c. material.

Liquid crystal is the name given to an organic compound which is a physically mobile fluid having a molecular order similar to that of a crystalline solid. If the temperature is raised to a certain point

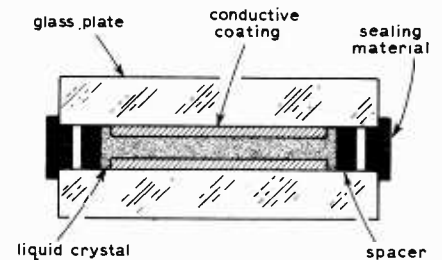


Fig. 1. Basic liquid crystal cell.

the compound will transform into a normal liquid; conversely if the l.c. is cooled it reverts to a crystalline solid. Three classes of liquid crystal have been identified and are named smectic, nematic, and cholestric. The smectic structure has parallel orientation of molecules in discrete layers, the nematic structure also has parallel orientation but no layers, and the cholestric structure has parallel orientation within the plane of a layer but the axial direction of each layer is twisted slightly, thus forming a helix through the layers. One characteristic which is common to all l.c.s is the long rod-shaped molecules.

Up to date more than half a dozen electro-optical effects in l.c.s have been observed but only two of these are used in displays.

Dynamic scattering

The first l.c. display, produced in 1967, used the dynamic scattering effect—Fig. 2(a), (b). In this mode the l.c. is doped with an electrolyte producing a resistivity in the order of $10^{10}\Omega$ cm. As a result of the doping the l.c. solution conducts current. Under non-energized conditions the molecules align themselves perpendicular to the treated electrodes, and in this condition light can pass through the liquid. When the electrodes are energized the light is scattered due to microscopic variations in the refractive index and disruptions of the molecular alignment. These disruptions are caused by turbulence in the liquid which is a phenomenon that is not well understood, but occurs at a threshold voltage of around 5–10kV/cm.

Dynamic scattering displays can be used in either the reflective or transmissive mode. Fig. 2 shows a transmissive cell with both electrodes transparent but the rear electrode may be made to reflect light to produce a reflective display. In this mode a contrast ratio of 20:1 is possible and the ratio is almost independent of the ambient light level. The appearance is whitish digits on a specular background but the display is not visible in darkness.

In the transmissive mode the appearance is whitish digits on a transparent background and the characters may be viewed in darkness using an auxiliary light source behind the display.

Field effect

The field effect display, often referred to as a twisted-nematic type, was first suggested in 1970. A twisted nematic l.c. structure occurs when the molecules on the two surfaces of a l.c. film are con-

strained to lie mutually at 90° so that as light traverses the film the optical axis of the liquid rotates by 90°. This alignment of molecules is achieved in a display cell by treating the electrode surfaces which then produce forces at 90°. To complete the display linear polarizing plates are bonded to the cell with their planes of polarization at 90°. When light passes through the cell it is polarized. The plane of polarization is then twisted through 90° and the light passes out of the cell which appears transparent—Fig. 3(a). When an electric field is applied across the cell the molecules tend to orientate themselves with their long-axis normal to the field. If a threshold voltage necessary to overcome the intermolecular forces, typically 1.5–10V, is applied the net effect is an untwisting of the helix. In this energized state polarized light traversing the cell will not be twisted and hence is absorbed by the back polarizer plate—Fig. 3(b). When the field is removed the molecules twist back through 90°. Some molecules twist to the right, others to the left, causing a mottled appearance on the display. This problem was overcome at the Royal Radar Establishment by adding optically active materials to produce a “memory”.

The appearance of the display is dark characters on a bright background. This can be reversed by positioning the polarizer plates parallel to one another. Coloured displays can be created by adding dyes to the l.c. material or selecting special polarizers. Field effect displays can also be used in the reflective mode by adding a diffuse reflector behind the back polarizer. In this mode a contrast ratio of 40:1 is possible but, as with the dynamic scattering types, the display cannot be seen in darkness.


The general trend in l.c. technology is towards field-effect types because of several advantages, as follows:

	field effect	dynamic scatter
Lower drive voltage	1–10V	15–20V
Lower current/cm ²	10–500na	1µA
Longer life	10,000+	10,000 h

The main problems of field effect displays are, first, alignment of the glass plates, which is critical otherwise the light rotates through the wrong angle, and second, a 50% light loss in the polarizer plates.

Liquid crystal displays have several advantages over other types in current use but they also have their own problems. These are dealt with briefly below.

Liquid crystals have relatively small temperature ranges, which makes them unsuitable for use in certain environments. The normal range is from –10 to +60°C; this can be raised or lowered by selecting the nematic compound. If the l.c.s should be subjected to temperatures outside of their normal range they will transform to a solid or liquid, in which case no display will appear. The electronics will still operate, e.g. in the case of a watch, and when the l.c.s return to their normal temperature the display will also return.

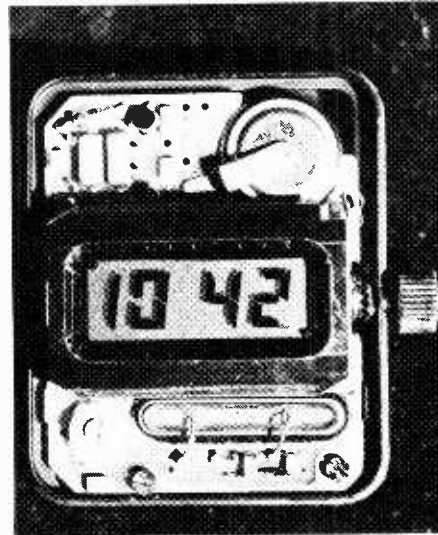

Liquid-crystal watch display.

Switching speeds of l.c.s are comparatively slow; the turn on and off times are given by:

$$t_{on} \propto \frac{\eta}{\Delta\epsilon V^2}$$

$$t_{off} \propto \eta d^2$$

where η =viscosity, $\Delta\epsilon$ dielectric anisotropy of l.c., V =applied voltage. The switching speed is dependent on temperature cell thickness, frequency of drive voltage and l.c. material. Typical switching times for both types of display are t_{on} =2–10ms, t_{off} =30–300ms.

Liquid crystal displays should be driven by an alternating voltage to prevent electrochemical reaction in the cell, such as electrolysis. Any d.c. component in the

drive voltage will shorten the life of the display.

Most a.c. drives are a square wave in the frequency range 25Hz to 1kHz. This type of drive is very difficult to multiplex so each segment of the display requires a separate drive circuit—this extra cost is normally offset by the lower current required.

Developments of liquid crystals

Liquid crystal displays, if you will excuse the pun, have a bright future. Much R & D work is being carried out in order to solve some of the shortcomings of the l.c., such as the susceptibility to hydrolysis by absorbed water vapour and decomposition by exposure to u.v. light. One major breakthrough was in 1973 when a team of chemists led by Dr George Gray of Hull University produced a family of l.c.s which are exceptionally stable and almost immune to water vapour contamination and exposure to u.v. light.

Several types of multiplexing have been proposed to overcome the switching limitations of l.c. materials. One of the most promising is a 3:1 a.c. coincident addressing scheme that is continually updated at a rate faster than the natural decay of the electro-optic effect.

Other developments include a small flat-panel TV screen based on a 128 × 128 matrix of twisted nematic displays. The TV operates at 25 frames per second with eight shades of grey. Another project is Xerox’s “electronic note paper”. This system uses a l.c. that changes from transparent to opaque and persists until it is erased by a high frequency field.

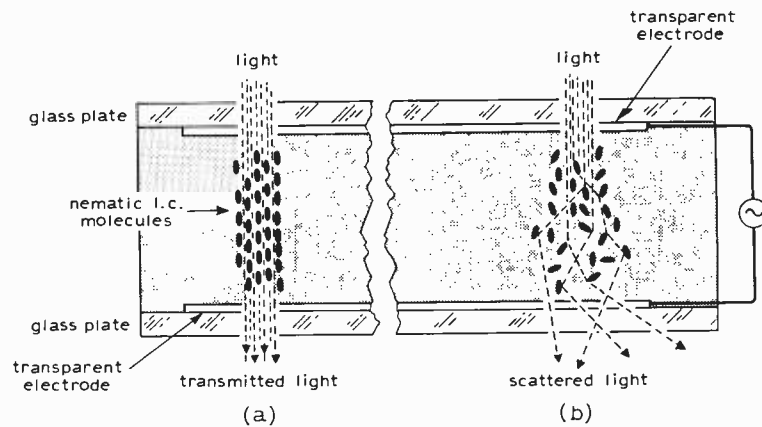


Fig. 2

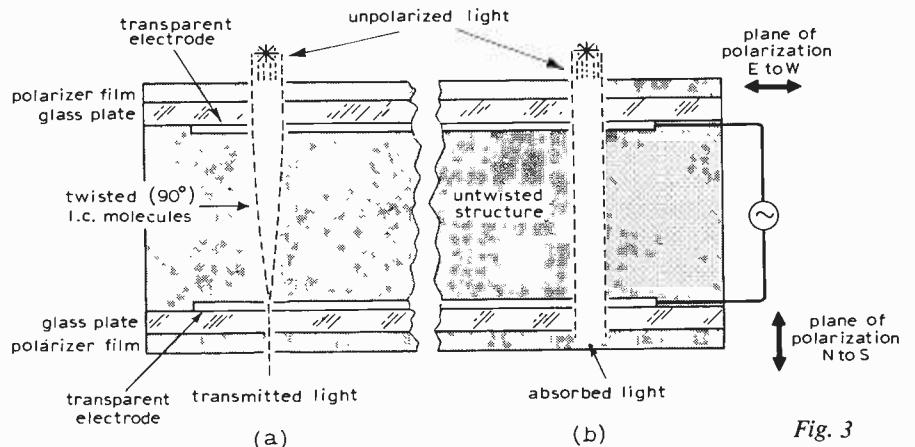


Fig. 3

RCA scientists have developed a simple technique for observing electron pulses flowing through i.c.s by placing some nematic i.c. on the surface of the device. The minute electric fields produced by the i.c. cause the l.c. to react thus indicating where a pulse is.

The Royal Radar Establishment have developed an electro-optically controlled colour-switch by placing a thin birefringent layer, such as cellophane, between linear polarizers. A l.c. cell then rotates the light and switches a colour or colours on or off.

MANUFACTURERS

AEG Telefunken	FE/R:W,I,C; FE/T:I,C.
American Microsystems:	FE/R:C.
British Brown Boveri:	FE/R:I,W.
Hamlin:	FE/R:W; DS/R:W,C,I & 8-digit CA; DS/T:C,I & 8-digit CA.
IEE:	FE/R:I; FE/T:I.
LXD:	FE/R:W,C.
Marconi:	DS/R; DS/T (for special applications).
Norstron:	DS/R:C,I; DS/T:C,I.
Princeton:	FE/R:W; (FE/T:W to special order)
Rank:	FE/R:C,I; FE/T:C,I.
RCA:	FE/R; FE/T.
Walter Scott:	FE/R:W,C,I; FE/T:W,C,I.
Siemens:	FE:8-digit CA; DS/R:C,I; DS/T:C,I.
Swarovski:	FE/R:W,C,I; FE/T:C,I; DS/T:C,I; DS/R:C,I.
Tekelec:	FE/R:panel meter.
Thomson CSF:	FE/R:C,I; FE/T:C,I; DS/R:C,I; DS/T:C,I.
Toshiba:	FE/R:W,C; DS/R:8-digit CA; DS/R:I.

Code
FE—field effect; DS—dynamic scattering;
R—reflective; T—transmissive; W—watch;
C—clock; I—instrument; CA—calculator.

Gas discharge displays

Perhaps the most familiar gas-discharge display is the Nixie tube, made by Burroughs and by many others under different names. As an indicator for counters and many earlier types of digital instrument, it was almost unchallenged for many years. It is easy to use, reliable, and gives a very bright display, but suffers from the drawbacks of an anode voltage which is high in relation to voltage levels used in modern equipment and of a stacked array of cathodes, some of the rear ones being partially obscured by those nearer the front. It is still widely used, however, and looks likely to continue for some time.

It takes the form of a common anode with ten cathodes, each cathode being a wire shaped to form one of the characters, the whole contained in a neon-filled envelope. The application of a voltage of 160V or over between a selected cathode and the anode causes a discharge to be established between the two electrodes. The selected cathode glows red and is viewed through the glass, either from the side or the end. Numerical characters and a few signs are available.

Neon gas discharges are used to great advantage in the more recently developed "plasma panel". In essence, the panel consists of a large number of neon "cells" arranged in a matrix in a flat panel. The rows and columns are bussed and each cell is thereby addressable. For instance, the cell at the intersection of row *x* and column *y* will, when the row bus and column bus are connected to *V* volts, have impressed across it *2V* volts, which will fire it. All other cells in row *x* and column *y* will have *V* volts across them and will not fire, assuming that the cell firing requirement is between *V* and *2V*. The electrodes and cover are transparent and the glow is seen as a point of light. In many cases the applied voltage is at high frequency and ignition takes place at each reversal of voltage, giving two illuminations per cycle.

These displays are extremely flexible and not restricted in size. For instance, a device named Plasmar and made by National Electronics, is a clock and calendar display exhibiting a six-digit time readout, a six-digit calendar and three letters (WED, etc.) to show the day of the week. Additionally, there are 21 "message blocks" which illuminate a stencil to indicate any fixed indicator such as am, pm, hours, seconds, etc. The displays can be multiplexed.

The use of a.c. discharge possesses several advantages over the d.c. type also in use. The construction of the panel is such that the applied voltage effectively "sees" a capacitance, as the electrodes are separated from the gas by a dielectric casting. The effect of this is to ensure that all areas of the panel are displayed equally brightly, the current being shared by capacitors in parallel on the basis of area. In a d.c. panel, current would not be equally shared; the emissivity of each area of electrode being different with area leads to an effect known as "hogging". D.c. panels also allow the gas to be in contact with the electrode, with consequent limitations in cathode life. There is one advantage of d.c. or unipolar-pulsed panels in that there is an inherent memory, rendering external memory devices redundant. In a.c. types the discharge is continually "refreshed" at a frequency high enough to avoid flicker.

Single-character neon displays are also fabricated in a flat format by, for example, Telefunken. An array of stainless-steel strips in a 14-segment formation is connected to input pins and faces a common transparent anode. Application of 130V to any segment causes a discharge between that segment and the common anode in the normal way. The advantage, of course, is that the display is planar, with no obstruction of cathodes.

The phenomenon of fluorescence is used in alphanumeric displays by several firms, mainly in multi-digit tubes, although Tung-sol make single-digit devices. In these, a filament produces an electron cloud, which is attracted to a selected, fluorescent anode by an arrangement of grids and anode voltage selection. The multi-digit tubes are multiplexed and the discharge is a blue-green colour.

MANUFACTURERS

Mullard:	Neon indicator tubes for numeric, limited alpha and sign information. Side or end viewing. Pins or wire ended. Orange.
ITT:	Neon indicator tubes for numeric, limited alpha and sign information. Side or end viewing. Pins or wire ended. Orange.
Burroughs:	Neon indicator tubes for numerals 0 to 9 ("Nixie" tubes). "Self-Scan" alphanumeric dot-matrix panel displays including drive electronics and memory. Up to eight rows of information. "Panaplex II" single row, numeric panel display, 9 or 16 digits.
Nippon Electric:	Dot-matrix plasma panels for the display of characters, numerals, graphics and permanent message blocks. Refresh driven. Multiplexed.
National Electronics:	"Plasmac" plasma panel for use as digital calendar and clock display. Six 7-segment, 1.25in digits for time; six 0.5in digits for date; three 14-segment 1in alpha characters for day of week; 21 message blocks. A.c.-driven.
Ferranti:	D.c.-driven plasma panel. Dot-matrix characters in 7 × 5 format. 32 rows of 40 characters. Memory.
Cherry:	Single row numeric panels. 7-segment, 0.4in characters, with decimal points, commas and operational signs.
Elesta:	Indicator modules with neon tubes, decode and drive electronics. Modules match Contraves edge switch housings.
Contraves:	Indicator modules with neon tubes, count, decode and drive electronics. Modules match edge switch housings.
AEG-Telefunken:	"Varisymbol" flat, 14-segment, neon indicator modules, with decimal point.
Beckman:	Seven-segment neon modules with t.t.l.-compatible decode and drive electronics.
TEC:	Neon indicator tube module with counter, latch, decoder and drive electronics.
Spectra-Tek:	Panel meter with neon tubes, decode and drive electronics.

Fluorescent indicators

Toshiba:	Multiple, single row, fluorescent tubes for up to 12 digits. Filament voltage 3 to 5.5V a.c. Seven-segment characters.
Futaba:	Multiple, single-row fluorescent tubes for up to 17 digits. Filament voltage 2.6 to 4.7V a.c. Seven-segment characters.
Tung-Sol:	Single-digit, seven-segment, side-viewing fluorescent indicators. Filament voltage 1.6V a.c.

Electroluminescent displays

An electroluminescent panel is basically a layer of phosphor, similar to that used in television tubes, sandwiched between two electrodes which may be shaped to produce a seven-segment format. When energized, phosphor between the electrodes emits light and a shape/character is illuminated against passive phosphor.

Electroluminescence will occur when electrons in a semiconductor solid are excited—in the case of phosphor, luminescence is from the excitation of impurity centres to a high energy state which, when returning to the normal energy state, emit photons. The impurity centres are created by doping the phosphor material.

At present there are two categories of electroluminescent displays—a.c. and d.c. energized.

A.c. panels

There are two methods of constructing a.c. panels depending on the application. The first type is called a ceramic panel which is normally the easiest and cheapest to produce. A metal plate is shaped to the required format then a white-enamel reflective-coating is fused to the plate. Powdered phosphor, normally zinc sulphide doped with manganese, is mixed with a binding material and fused on to the enamel surface. While the coating is still hot stannic oxide is sprayed onto the phosphor which forms a transparent conductive electrode. The complete assembly is then glazed with a protective insulating coating apart from a small area where the leads are bonded. An alternating current is applied between the electrode and metal plate and causes electroluminescence. This type of construction is suitable for mass production displays such as exit signs.

The second type of a.c. display is called an organic panel. A glass plate has a transparent conductive film of tin-oxide bonded to it, this film is then coated with a phosphor layer followed by a reflective layer. A back electrode is applied to the panel which is then sealed with a moisture-proof layer. Characters can be formed by etching either the front or back electrodes across which is applied the alternating current. This type of display is suitable for special panels with characters such as a seven-segment display or a dot matrix.

A new type of panel which is constructed similarly to the organic type uses a transparent flexible plastic encapsulation for the front window; this produces a semi-flexible panel about 1mm thick.


These displays all operate at voltages between 50 and 300V and at frequencies between 50Hz and 5kHz to produce green, blue and yellow light dependent upon the type of phosphor used. By using a fluorescent paint other colours can be produced. The phosphor powder is in a binding material and particles do not touch each other so most of the current flow is capacitive.

The luminance, and to a certain extent colour, is dependent on the frequency of the applied voltage because excitation occurs once every half cycle; above 10kHz the light output decreases due to electrical loss in the panel. Luminance also increases with voltage; a typical display will emit 8cd/m² at 240V 50Hz. The life of a panel is inversely proportional to the frequency and also dependent on the voltage but generally an exponential decay occurs over several thousand hours of continuous use. The panels can be driven from transistor inverters and can be dimmed to extinction by varying the applied voltage.

D.c. panels

These panels are newer and have a higher luminance/voltage ratio with outputs up to 500cd/m² possible. The efficiency is, however, comparable with the a.c. types being around 0.1%. Construction of a d.c. panel is more difficult because a barrier layer has to be formed in the phosphor coating. Zinc sulphide doped with manganese is again used which emits yellow light at 580nm; colours from red to green can be obtained by filtering. The construction of a d.c. panel is similar to that of an organic a.c. type. A glass plate has a transparent conductive coating bonded to it and this is etched to produce the required characters. An insulating layer then covers the leads adjacent to the display; next the phosphor layer is applied. In the case of phosphor powder types a mixture of powder and bonding material is applied by spraying or silk-screen. With thin-film types a layer is deposited by evaporation. Finally, a metal back-electrode is applied also in the shape of required characters. The complete panel is then encapsulated.

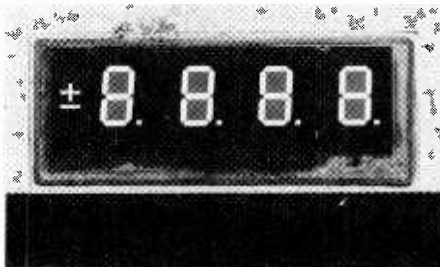Before the display will work an irreversible treatment called "forming" has to be carried out to produce the correct characteristics. The untreated panel has a low resistance and does not emit light. A



Seven segment d.c. electroluminescent display.

suitable voltage is applied which causes a decrease in current slowly at first then rapidly as a barrier layer is formed leaving the panel in a high impedance light-emitting condition. The process is completed by raising the voltage to the normal level.

The powder construction produces panels that operate at around 100V d.c. with a life-time of up to several thousand hours dependent on the way it is operated. Thin-film panels, however, operate at 10 to 20V d.c. but with reduced efficiency and life-time. Both types of d.c. panel operate in a resistive mode and suffer from a gradual ageing due to an increase in resistance. The phosphor is specially prepared for each application, the main parameters being brightness, voltage and current. Normal current densities are between 0.5 and 2mA/cm² dependent on brightness, but the mean brightness can be increased by driving the panel with overvoltage pulses although the efficiency remains the same. Pulsed operation can extend the life of d.c. panels and makes multiplexing possible.

Developments of displays

Because electroluminescent panels can be made in almost any format and size, with single areas of up to 500cm² and over being prepared, they have an advantage in mimic displays.

Most of the development will be in extending the life of panels, reducing power consumption and drive voltages, and making larger display areas. Westinghouse Electric Co have built a prototype a.c. panel consisting of 12,000 elements suitable for alphanumeric displays or, because the brightness of each element is independently variable, a flat television display is possible.

MANUFACTURERS

GEC:	D.c. 4- and 9-digit, 7-segment, yellow; and user specified.
Phosphor Products:	D.c. displays to user's specification.
Saunders-Roe:	A.c. displays to user's specification.
Thorn:	A.c. panels to user's specification.

Incandescent filament displays

Although these displays are considered old-fashioned, incandescent filament (i.f.) devices still have advantages over other devices. Bulbs emit a bright white-yellow light which may be filtered to produce colours. The bulbs are individually replaceable, have a life of around 10,000 hours and can be driven from t.t.l. logic devices. The main disadvantages of i.f. displays are: if there is a failure it is complete; and when a bulb is switched on there is a current surge due to the low cold resistance of the filament. In addition to conventional bulbs there are filament indicator tubes and seven-segment filament displays.

With i.f. lamp displays there are two modes of operation. The most common is to distribute the emitted light over a

character/segment area; the other mode of display uses direct viewing of the lamps. For seven-/sixteen-segment displays an equal number of bulbs is used, the light from each bulb being directed, by means of a light pipe or lens, to the surface of the display. Projection types of display have a number of bulbs corresponding to the number of complete characters required; the light shines through a stencil of the character and is focused onto the surface of the display. A variation of this system is a single bulb with a rotating stencil.

Directly viewed displays are normally in the form of a matrix of 5×7 individual lamps, the required characters being formed by lighting particular groups of the lamps. These types are very bright and can be used in outdoor displays such as score-boards. To make the display more visible in daylight lenses can be placed over the lamps, but this also restricts the viewing angle.

Stencil displays are the simplest method of conveying information. When a bulb is illuminated behind a transparent film a message or character is displayed. Fibre optic and optical plastic (edge-lit) displays are easily read because the characters can be formed precisely in the required shape. Each bulb in the package directs light along a number of optical fibres or plastic plates which go to the surface of the display. The fibres can either form complete characters or segments of a character, by dots of light. The plastic plates have dots on the surface, in the shape of the characters, which are illuminated; a separate plate is used for each character and the plates stand vertically behind one another.

Indicator tubes use filament wires either shaped to form individual characters or seven segments from which characters can be assembled. The tube is evacuated and when a low voltage, typically 5V, is applied to a filament/s the character glows. The seven-segment principle is also used in a flat-package display which resembles the seven-segment I.e.d. type.

Even though many solid-state/gas-discharge displays are on the market, i.f. types continue to find applications. Very little development is taking place but, because of the advantages mentioned, these types of display will not be replaced until some significant improvements are made in other types.

MANUFACTURERS

Bulgin:	Illuminated stencil. Any message can be displayed.
Conrac:	Matrix of bulbs to form characters.
IEE:	7- and 16-segment fibre optics. Projection types. 7-segment lamp.
Davy:	Matrix of bulbs to form characters.
Apollo:	Filament tubes.
FR:	7- and 16-segment filament.
Shelly/Datatron:	7- and 16-segment fibre optics. Projection types.

Hird-Brown:	Matrix of bulbs to form characters.
Neill:	7-segment lamp.
NEC:	7-segment lamp and illuminated stencil.
Fuji:	7-segment filament.
Diode-Lite:	7-segment lamp.
Setpoint:	Matrix of bulbs to form characters.
Tung-Sol:	7- and 16-segment lamp. Illuminated stencil.
Master	7- and 16-segment.

Specialities:	fibre optic.
TEC:	7-segment lamp with logic. Projection. Filament tube.
RCA:	Filament tube.
Siemens:	Filament tube.
KGM:	Edge lit. Matrix of bulbs to form characters.
Okaya:	7-segment filament. Filament tube.
Itoka:	7-segment lamp.
Spectra-Tek:	Filament-tube panel meter with drive/decoder logic.

Manufacturers' addresses with UK agents where applicable.

AEG Telefunken UK Ltd, Bath Road, Slough, Berks.

American Microsystems Inc. Adrian Electronics Ltd, 28 High Street, Winslow, MK18 3HF.

Beckman Instruments Ltd, Queensway, Glenrothes, Fife.

Bowmar Instruments Ltd, 1 Ormond Avenue, Hampton, Middx.

British Brown Boveri Ltd, Albany House, 41 High Road, Brentford, Middx.

Bulgin, A. F. & Co Ltd, Bye Pass Road, Barking, Essex IG11 0AG.

Burroughs Electronic Brokers, 49 Pancras Road, London NW1 (neon indicators); Walmore Electronics Ltd, 11 Betterton Street, Drury Lane, London WC2 (self-scan types).

Cherry Electrical Products, Lattimore Road, St. Albans, Herts.

Conrac Ltd, 346 Kensington High Street, London W14.

Contraves Industrial Products Ltd, Times House, Station Approach, Ruislip, Middx.

Davy & United Instruments Ltd, Darnall Works, Sheffield S9 4FA.

Diode-Lite Pye TMC Components Ltd, Controls Division, Roper Road, Canterbury, Kent.

EPP Rastra Electronics Ltd, 275 King Street, Hammersmith, London W6 9NF.

Eldema/Genisco } Fieldtech Ltd, No. 2
Maintenance Area,
Shelly/Datatron } Heathrow Airport,
Hounslow, Middx.

Elesta Britec Ltd, 17 Devonshire Road, London SE26.

FM Kynmore Engineering Co, 19 Buckingham Street, London WC2.

Fairchild Semiconductor Ltd, Kingmaker House, Station Road, New Barnet, Herts.

Ferranti Ltd, Special Components Department, Gem Mill, Chadderton, Oldham, OL9 8NP.

Fuji Perdix Components Ltd, Perdix House, 31 Green Lane, Chislehurst, Kent.

GEC Ltd, Hirst Research Centre, East Lane, Wembley, Middx.

Hamlin Electronics, 14 New Road, Southampton, Hants.

Hewlett Packard Ltd, 224 Bath Road, Slough, Berks.

Hird-Brown Electronics Ltd, Lever Street, Bolton, Lancs.

IEE Counting Instruments Ltd, 5 Elstree Way, Borehamwood, Herts.

ITT } ITT Ltd, Brixham Road, Paignton,
Sanyo } Devon.

Itoka } Walter Scott Industries,
Futaba } Imp House, 35 Malden
WalterScott } Way, New Malden,
Surrey.

KGM } KGM Electronics Ltd, Clocktower
Okaya } Road, Isleworth, Middx.

LXD Inc, Transworld Scientific Ltd, Short Street, High Wycombe, Bucks.

Litronix, Bevan House, Bancroft Court, Hitchin, Herts.

Marconi Communication Systems Ltd, Radford Crescent, Billericay, Essex.

Marconi Company Ltd, Research Laboratories, West Hanningfield Road, Gt. Baddow, Essex.

Master Specialities Co, Waycom Ltd, Wokingham Road, Bracknell, Berks.

Monsanto Ltd, 10 Victoria Street, London SW1H 0NQ.

Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD.

NEC } Nimrod Electronics Ltd, Vann
Norstron } Lane, Chiddingfold, Surrey.

National Electronics Inc, Magnus Electronics Ltd, 23 King Street, London W3.

National Semiconductor, The Precinct, Broxbourne, Herts.

Neill Controls Ltd, Neills Road, St. Helens, Merseyside.

Nippon Electric Co, Impectron Ltd, Impectron House, 23 Kings Street, London W3.

Norbain Electronics Ltd, Norbain House, 44 London Street, Reading RG1 4SQ.

Oki Twentieth Century Electronics Ltd, King Henry's Drive, New Addington, Croydon CR9 0BG.

Opcoa } F. R. Electronics Ltd, Wimborne,
Apollo } Dorset.
FR }

Oshino Seatronics Ltd, 22 Finsbury Square, London EC2A 1DT.

Phosphor Products, 100 Drawkins Road, Hamworthy, Poole, Dorset.

Plessey Co Ltd, Optoelectronics & Microwave Unit, Wood Burcote Way, Towcester, Northants.

Princetown Material Science, Sprague Ltd, 159 High Street, Yiewsley, West Drayton, Middx.

RCA Ltd, Electronic Components Division, Lincoln Way, Sunbury-on-Thames, Middx.

Rank Research Laboratories, PO Box 33, Phoenix Works, Great West Road, Brentford, TW8 9AG.

Saunders Roe Developments Ltd, North Hyde Road, Hayes, Middx.

Setpoint Ltd, Ingate Place, London SW8.

Siemens Ltd, Great West House, Great West Road, Brentford, Middx.

Spectra-Tek, Kirbymoorside, York.

Swarovski Bywood Electronics, 181 Ebbens Road, Hemel Hempstead, Herts.

TEC West Hyde Developments Ltd, Ryfield Crescent, Northwood, Middx.

Tekelec Euro Electronic Instruments Ltd, 27 Camden Road, London NW1 1YE.

Texas Instruments Ltd, Manton Lane, Bedford.

Thomson CSF UK Ltd, Ringway House, Bell Road, Deneshill, Basingstoke, Hants.

Thorn Electrical, Bond Road, Mitcham, Surrey.

Toshiba UK Ltd, Toshiba House, Great South West Road, Feltham, Middx.

Tung-Sol Walmore Electronics Ltd, 11 Betterton Street, Drury Lane, London WC2.

Xciton Tranchant Electronics Ltd, Tranchant House, 100A High Street, Hampton, Middx.

“Ampex and WHAT?...”

The JAMES SCOTT Alignment Units for D.R. and F.M. Multi-Channel Tape Recorders.



The F.M. Alignment Unit Type FMU/1 illustrated was designed at the Royal Radar Establishment, Malvern, to suit Ampex Recorders working on the IRIG intermediate band specification (using ES 100 Electronics) e.g. Model Numbers FR 1200, FR 1260, FR 1300, FR 1800L, FB 400, PR 500.

If you have a sophisticated Ampex Recorder—Align it to the Manufacturers specification using our Alignment Units for D.R. & F.M. Systems.

Speedy and inexpensive

For Further information and Technical Literature Write or telephone.




JAMES SCOTT
(Electronic Engineering) Ltd

CARNTYNE INDUSTRIAL ESTATE
GLASGOW G32 6AB
Tel: 041-778 4206

WW—212 FOR FURTHER DETAILS

Liquid Crystal Display Connector

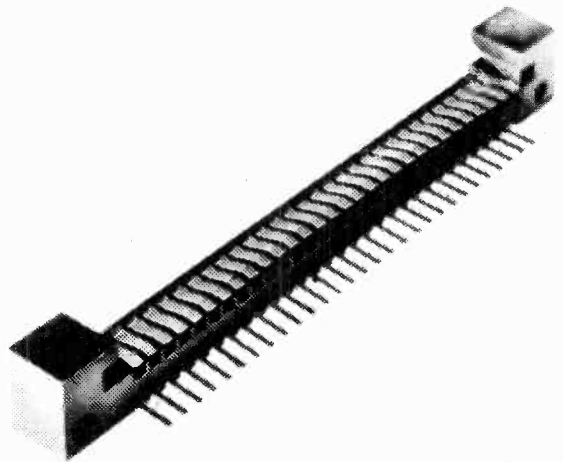

These electrical connectors are self-indexing for fast, precise display plug-in, give rigid mechanical support for liquid crystal and other types of digital display panels. They are available in two styles for parallel and 90 mounting.

Manufactured with a rugged glass-filled phenolic body, corrosion and film resistant contact alloy (variety of optional platings available) of high strength, the cone-pointed spring contacts permit high integrity connections for both static and mobile use.

HELLERMANN ELECTRONIC COMPONENTS

For full details and literature:
Imberhorne Way
East Grinstead
Sussex RH19 1RW
Tel. East Grinstead 27411



The TIME SAVERS


WW—225 FOR FURTHER DETAILS

The Sinclair DM2 Multimeter.

Comprehensive. Accurate. Portable.

And really rugged.

Yet only £59. (PLUS VAT)

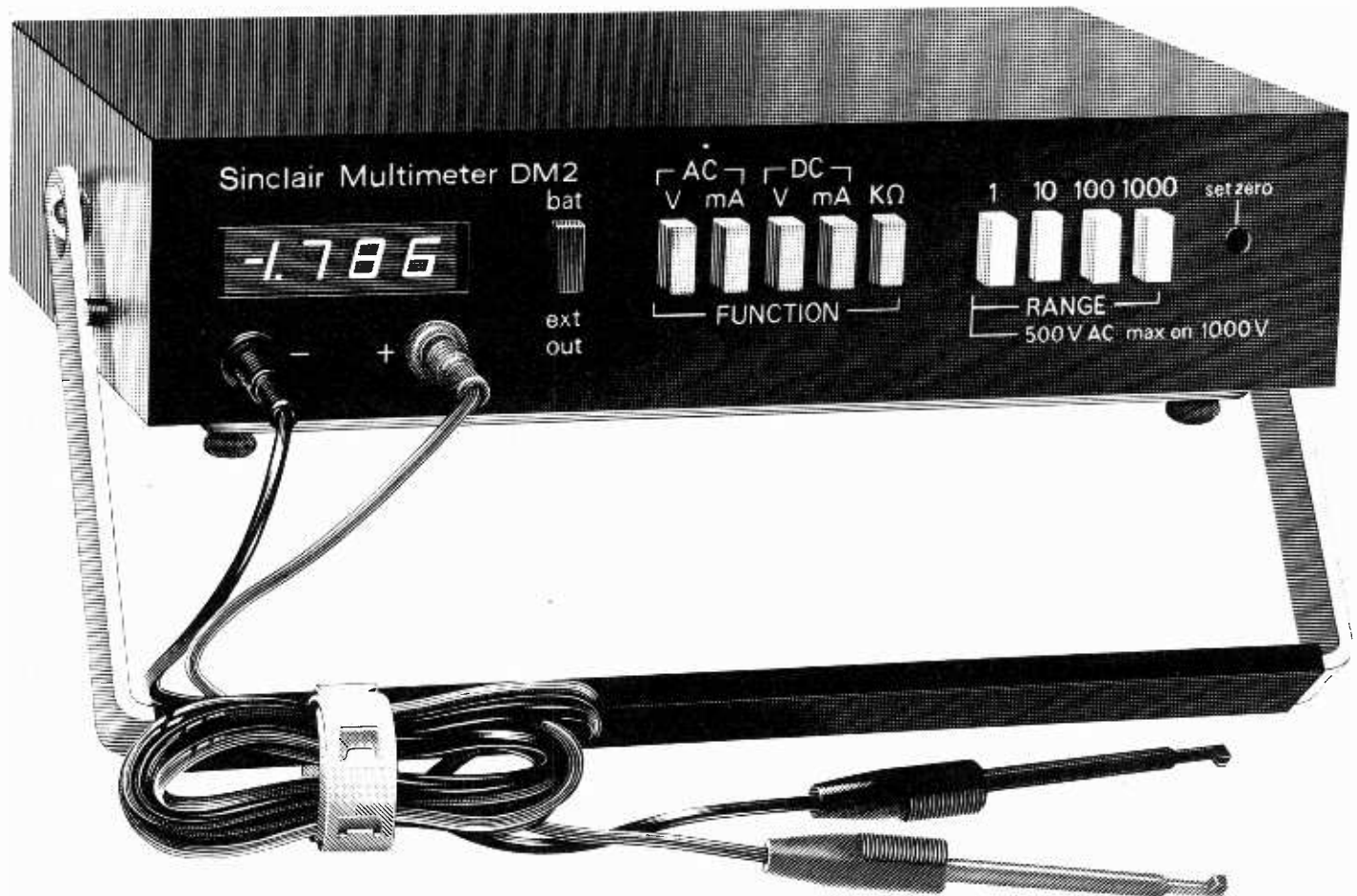

State-of-the-art circuit design, incorporating high-quality components, has resulted in a professional, $3\frac{1}{2}$ digit instrument of outstanding performance and reliability at a realistic price.

A custom-designed MOS LSI digital processing IC controls the auto-polarity dual-slope-integration A to D converter. The circuit built around this IC uses a MOSFET op-amp input buffer with 0.1% metal-film resistors. The result is excellent accuracy and stability with a very high basic input impedance.

The instrument reads to ± 1999 and has a basic accuracy on the 1 V DC range of $0.3\% \pm 1$ digit. Four 8 mm LED displays provide excellent legibility and angle of view. Battery operation allows complete independence of mains supply.

The Sinclair DM2 has all the capability you need. Just take a look at its features and compare them with higher-priced multimeters. You'll find the DM2 is their equal in virtually everything – except price!

Features of the Sinclair DM2

5 functions giving 22 ranges

DC volts – 1 mV to 1000 V
AC volts – 1 mV to 500 V
DC current – 0.1 μ A to 1 A
AC current – 1 μ A to 1 A
Resistance – 1 Ω to 20 M Ω

Easy to use

Automatic polarity, bush-button selection for all ranges and modes from a single input terminal pair.

Easy to read

Big, bright 8 mm LED display gives a quick, clear reading.

$3\frac{1}{2}$ digit display

Display reads from 000 to 1999. Overload indicator.

Protected

Separate fuses for current and resistance circuits.

Accurate

Dual slope integration. High stability.

Rugged construction

Tough metal casing takes the roughest treatment – try standing on it!

Two power sources

Supplied with a 9 V battery, giving 60-hour typical life. Mains adaptor also available.


Portable

Weighs only 2 $\frac{1}{2}$ lb approx, including battery. Measures only 2 in x 9 in x 6 in approx.


Optional extras

Mains adaptor – £3.19 inc VAT.
Carrying case – £5.40 inc VAT.
12-month no-quibble guarantee

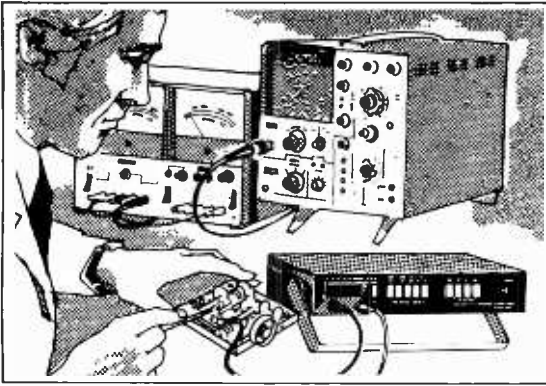
The Sinclair DM2 Multimeter: full technical story



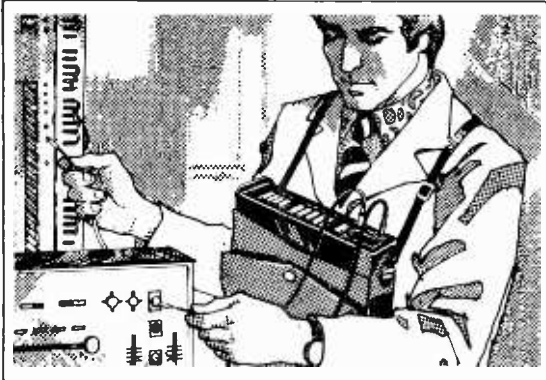Use it in your laboratory. The DM2 sits rigidly on its combined carrying handle/stand.



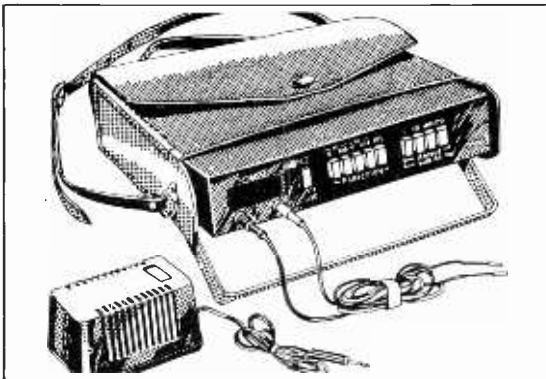Use it on the move. Keep the DM2 in its carrying case – it's always ready for use.



All you need to use the DM2... anywhere. Mains adaptor... carrying case... multimeter... you're ready for quick, efficient metering – whatever the situation.

Take advantage of this money-back, no-risk offer today

Test the Sinclair DM2 for yourself. Simply send us a cheque, your Access/Barclaycard number, or an official company order, with the coupon below. And in the unlikely event you find it's not what you need, return it to us within 10 days and we'll refund your money in full.

Interested in a quantity discount?

Use the coupon to arrange a demonstration and get details of prices on 5 or more instruments.

Sinclair Radionics Ltd,
London Road, St Ives, Huntingdon,
Cambs., PE17 4HJ.

Tel: St Ives (0480) 64646.

VAT Registration No: 213 8170 88.

sinclair

DC Volts Range	Accuracy	Input Impedance	Resolution
1 V	0.3% ± 1 Digit	> 100 MΩ	1 mV
10 V	0.5% ± 1 "	10 MΩ	10 mV
100 V	0.5% ± 1 "	10 MΩ	100 mV
1000 V	0.5% ± 1 "	10 MΩ	1 V

Maximum overload – 350 V on 1 V range
1000 V on all other ranges.

AC Volts Range	Accuracy	Input Impedance	Frequency Range
1 V	1.0% ± 2 Digits	10 MΩ/40 pF	20 Hz–3 KHz
10 V	1.0% ± 2 "	10 MΩ/40 pF	20 Hz–3 KHz
100 V	2.0% ± 2 "	10 MΩ/40 pF	20 Hz–3 KHz
1000 V	2.0% ± 2 "	10 MΩ/40 pF	20 Hz–1 KHz

Maximum overload – 300 V on 1 V range
500 V on all other ranges.

DC Current Range	Accuracy	Input Impedance	Resolution
100 μA	2.0% ± 1 Digit	10 KΩ	100 nA
1 mA	0.8% ± 1 "	1 KΩ	1 μA
10 mA	0.8% ± 1 "	100 Ω	10 μA
100 mA	0.8% ± 1 "	10 Ω	100 μA
1000 mA	2.0% ± 1 "	1 Ω	1 mA

Maximum overload – 1 A (fused).

AC Current Range	Accuracy	Frequency Range
1 mA	1.5% ± 2 Digits	20 Hz–1 KHz
10 mA	1.5% ± 2 "	20 Hz–1 KHz
100 mA	1.5% ± 2 "	20 Hz–1 KHz
1000 mA	2.0% ± 2 "	20 Hz–1 KHz

Maximum overload – 1 A (fused).

Resistance Range	Accuracy	Measuring Current
1 KΩ	1.0% ± 1 Digit	1 mA
10 KΩ	1.0% ± 1 "	100 μA
100 KΩ	1.0% ± 1 "	10 μA
1000 KΩ	1.0% ± 1 "	1 μA
10 MΩ	2.0% ± 1 "	100 nA

Overload protection – 50 mA (fused).

To: Sinclair Radionics Ltd, FREEPOST, St Ives, Huntingdon, Cambs., PE17 4BR.

Please send me: *I enclose a cheque for £

..... Multimeters @ £63.72
inc VAT. _____

..... Mains adaptors @ £3.19
inc VAT. *My Access/Barclaycard number: _____

..... Carrying cases @ £5.40
inc VAT. _____

I am interested in 5 or more multimeters *I enclose an official company order – signed and dated.

..... Please arrange a demonstration. _____

..... Please send details of quantity discounts. *Please complete or delete as applicable.

Name _____

Address _____

Please print

FREEPOST – no stamp needed with address above. ww/5/75

THE STORY OF RADIO

W M Dalton

WHO KNOWS how many good ideas, abandoned as impracticable in their time, are waiting to be tried again by some man of vision — and perhaps by YOU!
Endlessly fascinating and inspiring, unassuming in style, Mr Dalton's volumes are bursting with all the ideas that led radio engineering from its humble origins to the mighty miracle of colour television from the planets.
Compulsive reading for every radio engineer and every radio ham.

PUBLICATION IN MAY

the first three volumes of **The Story of Radio** by W. M. Dalton M.I.E.R.E. Price to be announced

Vol. 1 HOW RADIO BEGAN

Magnetism and Electricity; Electrical Engineering; Wireless Telegraphy; The Thermionic Valve.
160 pp, 28 line drawings, 13 b/w illustrations

Vol. 2 EVERYONE AN AMATEUR

After World War I; Amateur Wireless; The British Broadcasting Company; Home Constructors; The Rediscovery of Short Waves. 168 pp, 40 line drawings, 33 b/w illustrations

Vol. 3 THE WORLD STARTS TO LISTEN

Receiver Measurements; The British Broadcasting Corporation; Compromise in Design; Telephones, Talkies and Television. 184 pp, 52 line drawings, 35 b/w illustrations

IN PREPARATION

Vol. 4 RADIO BECOMES A PROFESSION

All Mains Receivers; Broadcasting Techniques; The Superhet Wins Out; The Service Engineer.

Vol. 5 THE BIRTH OF T.V.

Public Address; All-Wave Receivers; Shorter Waves; High-definition Television.

Vol. 6 THE PRESS-BUTTON AGE

Automatic Radio; Communications Receivers; Television Settles Down; The End of an Era.

Vol. 7 DURING THE WAR AND AFTER: RADIO BECOMES ELECTRONICS

Wartime Activities; Post-war Radio and Television; Analog Computers; Digital Computers.



If you would like further information or would like to purchase any of the above books please complete the form and send to:
ADAM HILGER LTD
Publishers
29 KING STREET LONDON WC2E 8JH

Without committing me to any obligation whatsoever, please send me full information on W. M. Dalton's THE STORY OF RADIO
Name.....
Address.....
.....

Noise—confusion in more ways than one

3—Microwave noise generators and aerial temperature

by K. L. Smith
University of Kent at Canterbury

Techniques for measuring noise temperature in the microwave region are discussed in this article, together with interesting and in some ways unexpected effects on the performance when attenuation is present at the front end of receivers. Noise from external and sometimes distant sources is considered and its effect on the idea of aerial temperature.

I find that the upper end of the frequency spectrum offers many interesting techniques, as we have seen from the recent series of articles by M. W. Hosking in *Wireless World*. The main point to bear in mind about microwaves is that distributed techniques are used and lumped circuit components as well as definite voltages and currents, are no longer in evidence. For example, a matched load on the end of a transmission line (waveguide) is not a small resistor, but is often a wedge of lossy material tapered for a number of wavelengths. Certainly the thermionic diode noise sources are out and the distributed circuit ideas have to be exploited for noise generation. The easiest microwave noise source is one of the matched loads heated to a known temperature in an oven (T_{hot}). For measurements on low-noise receivers, instead of being heated, the load is often cooled by solid carbon dioxide or liquid nitrogen, for instance. This yields a known T_{cold} value. (" T_{hot} " is then usually room temperature.)

I will now describe the gas discharge tube as a most useful noise source for the microwave region. The tubes are usually similar to a small fluorescent lamp, with heater, the positive column of which is coupled into a microwave system by passing the tube diagonally across a waveguide, as shown in Fig. 9. The noise temperature seen by a receiver connected to the gas discharge source is constant and related to

the electron temperature in the plasma, in a way that can be calculated. It is virtually independent of the current through the tube, but it does depend to some extent on the type of gas and the pressure in the tube, and on the diameter of the discharge. Tubes containing argon have temperatures 9900K to 11000K. As an example, tube type N1067 has a temperature of 11000K.

The custom in specifying noise tube sources usually involves the excess noise ratio in decibels, so that an argon tube whose noise temperature is 10000K has an excess noise ratio of

$$10 \log_{10} \left(\frac{10000 - 290}{290} \right) = 15.25 \text{ dB}$$

The gas tube source has a limitation and that is once the tube has been made and put into operation, the noise temperature is fixed (as we have seen, it is always at about 10000K). This temperature is rather high and you might think that it would produce a very large A in the ratio method for measuring T_e . So it would, but with a bit of manoeuvring based on the discussion in the next section, we can get over this.


Fig. 9. Electron noise temperature inside an ionized gas tube is surprisingly constant. Tube is placed diagonally across the waveguide to couple or match into the system efficiently.

Effect of attenuation on noise temperatures

At first sight, it might appear that an attenuator with a loss L placed between the output of a source of noise power and the input terminals of an amplifier, could be handled as a stage having a gain of less than one. If this was true the first two terms of the cascading formula could be used directly. The situation is not quite so simple as this in practice, because the attenuator is a lossy passive circuit which contributes thermal noise according to its physical temperature, T_L . The use of the excess temperature simplifies the arguments somewhat, at the expense of always having to remember that 290K has to be added to get the true temperature.

I will now go on to consider how one deals with a lossy network in a system. The problem can be looked at from two points of view. The first considers the output terminals of the attenuator. The attenuator is bracketed in with the source, as it were. The discussion then deals with the question of the source temperature seen by the receiver (whose effective input temperature is, say, T_{eR}) considering the original source and attenuator together forming the new source. The other way is to bracket the attenuator in with the receiver to give a new receiver (with new T_e) with which to face the original source. Of course, both points of view amount to the same thing, it is just the position in the cascade at which we refer to the noise temperature which differs.

The first requirement is for us to consider the effective input temperature of the attenuator alone. Think of an attenuator of loss L , with a matched source resistance, all in a box at a physical temperature T_L . After a little thought, you should see that the available noise power from the output terminals of the whole thing is $kT_L B$. The available noise power at the input of the attenuator is $k(T_L + T_{eL})B$, where T_{eL} is the effective input temperature of the attenuator. This power multiplied by the gain, i.e. $1/L$, must be equal to the output power

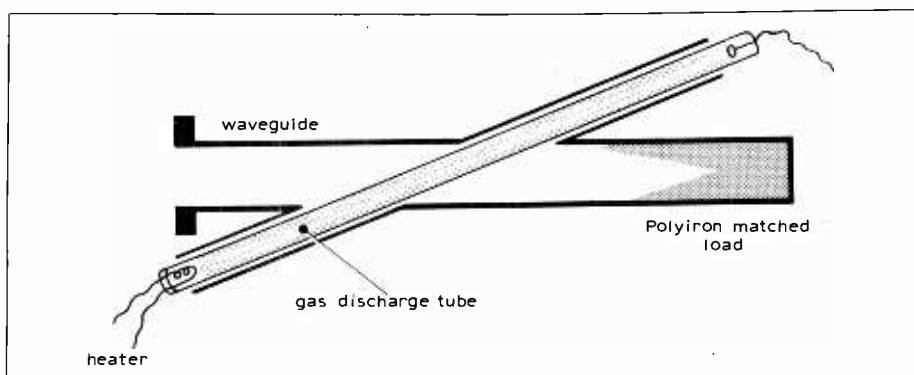

$$\frac{k(T_L + T_{eL})B}{L} = kT_L B \text{ or } T_{eL} = (L-1)T_L \quad (8)$$

Now we can go ahead and use the equation for T_e on page 172 (April issue) to get the overall effective input noise temperature of a receiver with an attenuation of L between its input terminals and the source terminals

$$T_e = T_{eL} + \frac{T_{eR}}{\left(\frac{1}{L}\right)} \quad (9)$$

Fig. 11 shows diagrammatically a few steps to assist in arriving at this last equation. You will see that attenuation not only increases the receiver's effective input temperature by L , but adds noise of its own, amounting to $(L-1)T_L$. A typical example of where you will get this kind of thing is an aerial connected to a receiver via a lossy feeder.

We are now in a position to look at the problem in the other way I mentioned. Suppose the aerial temperature is T_a and is connected to the attenuator input terminals, as shown in Fig. 12. The available power coming out of the attenuator is $k(T_a + T_L)/L$, so the temperature seen by the receiver is

$$T_{a(eff)} = \frac{T_a}{L} + \left(1 - \frac{1}{L}\right)T_L \quad (10)$$

by using equation (8).

This means that the effective aerial

temperature is not only reduced to $1/L$ of the actual value, but a spurious or masking noise $(1 - 1/L)T_L$ is added by the attenuator. Whichever way one looks at it, attenuation between aerial and receiver has a nasty effect on the noise performance of a low noise system.

Just to check that equations (9) and (10) are ways of saying the same thing, you might like to calculate the output noise power, P_{NO} , in both cases. From (9) and Fig. 11


$$P_{NO} = k(T_a + T_e) \frac{BG}{L} \\ = k(T_a + [L-1]T_L + LT_{eR}) \frac{BG}{L}$$

and from (10) and Fig. 12

$$P_{NO} = k(T_{a(eff)} + T_{eR})BG \\ = k\left(\frac{T_a}{L} + \left[1 - \frac{1}{L}\right]T_L + T_{eR}\right)BG$$

Fig. 11. Including the attenuator in with the receiver gives a new receiver complete with new overall T_e with which to face source.

Fig. 12. Same system as Fig. 11 but now considered from the point of view of attenuator bracketed in with source to form a new source... feeding the original receiver.

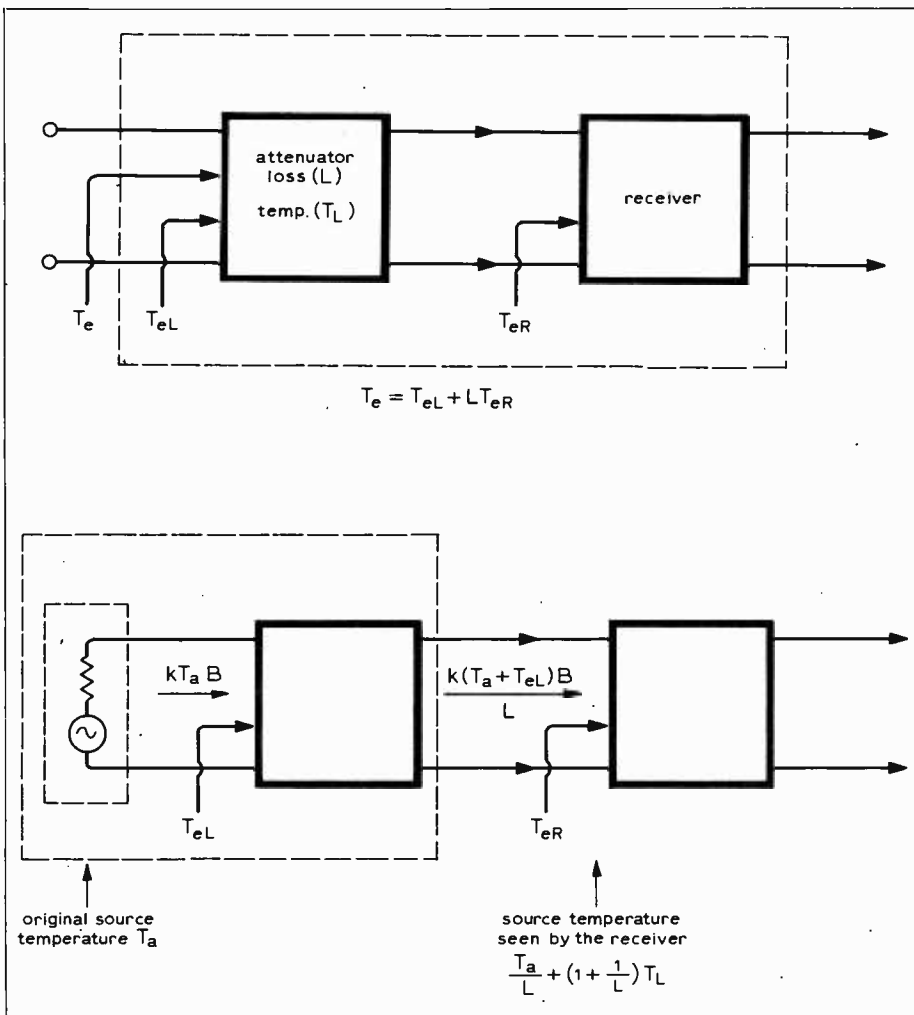

Factorizing out $1/L$ in the second equation shows it to be exactly the same as the first.

There is one situation in which an attenuator is useful when dealing with noise. If you have a noise source which has a known fixed, but high noise temperature, you can obtain a lower noise temperature by exploiting equation (10). Of course the attenuator must be a highly accurate calibrated one to give a known value of L . From equation (10) you can see that with no attenuation, ($L = 1$), the temperature seen is that of the source. If L is very large, the first term in the equation becomes negligibly small, so does $1/L$ in the bracket and the noise temperature seen by the receiver is simply T_L , no matter how high T_a is—if L is large enough. In most situations, $T_L = T_o$ or nearly so and if we deal in terms of excess temperatures then equation (10) can be rewritten

$$T_{a(eff)} - T_o = \frac{T_a}{L} + \left(1 - \frac{1}{L}\right)T_o - T_o$$

which is

$$T_{a(eff)} - T_o = \frac{T_a - T_o}{L}$$

This argument shows that the effective excess noise temperature of a source is just the actual excess temperature divided by L . L must be a numerical ratio and as virtually all attenuators are calibrated in decibels, you must do a conversion back first. This is easy to do and I will finish this section with a simple example.

Suppose you have a gas tube noise source whose excess noise temperature is 10000K. If a 10dB attenuator at room temperature is placed between it and a receiver, then L is 10 and the result recorded by the receiver is an effective excess noise temperature of 1000K. If 20-dB attenuation is inserted, you would observe 100K. 30dB would give 10K excess temperature and so on. This technique is useful when using gas tube noise sources for measuring performances of low noise receivers and sensitivity of radiometers.

Aerial temperatures

My earlier discussion attempted to highlight the distinction between T_a and T_e . It underlined the fact that T_a measures the noise coming in with the signal. You might be tempted to think that we cannot do anything about a naturally occurring T_a and have to put up with it. That is not the whole picture and a much closer look is required.

One of the first questions you might ask is where does the noise external to the receiving equipment originate? We already have partial answers. The sun radiates at noise equivalent temperatures of about 6000K near the infra-red end of the spectrum, up to hundreds of thousands of degrees at longer wavelengths. Occasionally the sun produces bursts of noise which are orders of magnitude greater than the "quiet" sun value. The earth radiates at about 300K over much of its surface away from the poles. The moon and planets radiate at their characteristic temperatures and there

is a general background hubbub (especially at long wavelengths) from the galaxy. At millimetre wavelengths the atmosphere radiates and absorbs, together with acute and rapidly changing effects by rain and clouds—all very much under scrutiny by many observers.

A summary of these effects is illustrated in Fig. 13, where the main curve shows the variation of aerial temperature over the radio spectrum. It is not surprising that S band (10cm wavelength) and X band (3cm) figure prominently in space mission communications and radar, because the value of T_a in this region is very low, around 10K. The rise to millions of degrees at long and medium waves is clearly seen. Time spent on careful low noise design of communications receivers at this end of the spectrum would be time wasted. Other considerations, such as good cross modulation and low spurious response performance, become prominent.

From the beginning of the v.h.f. region upwards in frequency, low-noise design for minimum T_e becomes important as can be inferred from the parts of Fig. 13 where aerial temperatures lower than room temperature occur. Moving to higher frequencies still, we see a rising T_a as water molecules in the atmosphere produce a peak in atmospheric absorption at about 23GHz. This overlaps another rise at 60GHz which is explained by the existence of a cluster of molecular oxygen spectral lines around this frequency. The small dip between the peaks near 35GHz is a window at Q band (8mm wavelength).

At higher frequencies the atmospheric gases have more and more resonances and propagation becomes impossible, except for very short distances. The atmosphere is virtually opaque until the visible light window at 600000GHz, except for a few rather foggy windows in the near infra-red region. The effective temperature of the atmosphere varies with its physical temperature as well as its opacity. In turn, the opacity varies with the fogginess at any frequency and the physical thickness. The distance to the outer edge is obviously much less looking upwards than along towards the horizon. One would expect the noise from the atmosphere to be greater looking horizontally than vertically, as borne out by the curve on Fig. 13.

The natural production of noise giving high aerial temperatures is not always looked upon as an annoying and expensive interference. Radio astronomers and experimenters who carry out work on atmospheric absorption mechanisms look for and measure changes in T_a for their bread and butter. Radio link, radar and space communication engineers on the other hand look on high aerial temperatures as a bug-bear. This is a very good example of the saying, "One man's meat is another man's poison."

Radio aerials have quite wide beam widths, although extremely large microwave dishes are built to reduce the pattern width and give a directivity more like a searchlight beam. There are always the side lobes to consider. The aerial temperature recorded by a receiver is the average value


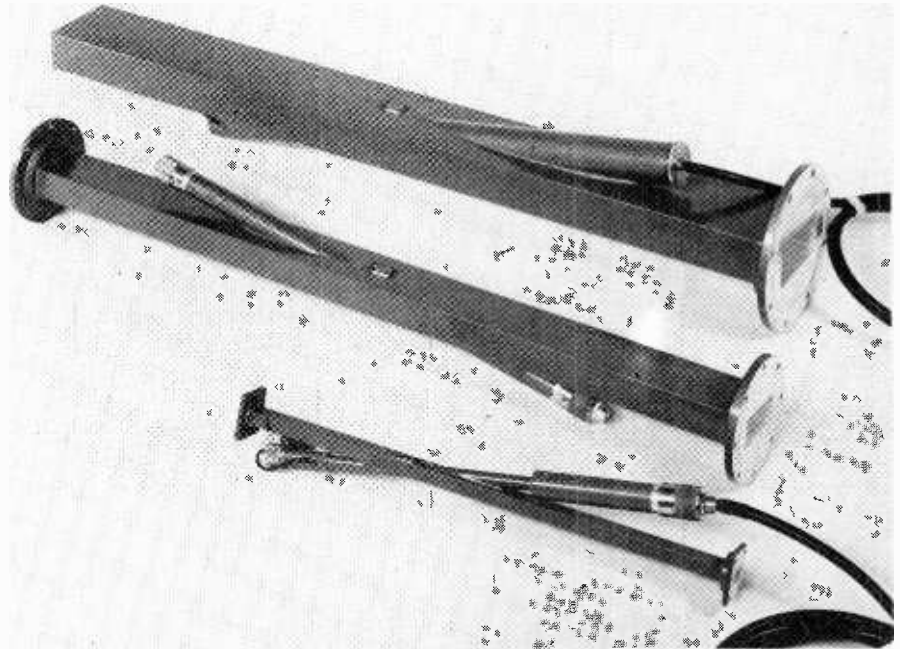


Fig. 10. Typical waveguide gas tube noise sources. Tube is struck by impulse from power supply and operates at 150mA until switched off. (Mid-century Microwave-eng Ltd.)

Fig. 13. Atmosphere does not transmit equally well across the whole radio spectrum. Molecular absorption begins to set in above 10GHz. High transparency region between 0.8 to 10GHz is already becoming crowded with traffic. Rapid increase of noise at low frequencies is radiation from the galaxy and varies with aerial direction relative to it. Noise contributions of moon and planets will only be observed if they are fully resolved by the aerial, which is most unlikely because of their small angular size.

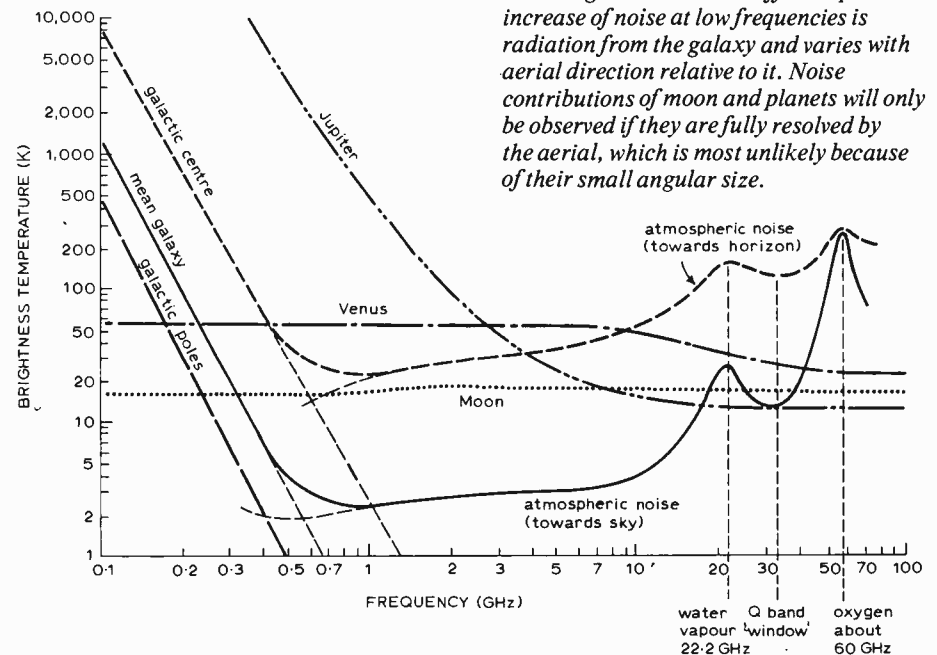

seen by the aerial beam. Any peaks in the temperature distribution in space (a "point" source like a planet, for instance) will be missed with a broad beam. It is a matter of resolving power as in any other telescope problem.

I briefly discussed this kind of idea in reference 12 under the heading convolution. What this means is that the averaging over the large aerial beam area dilutes the effect of a small hot source and it fades into insignificance. If the aerial beam is small and covers the source, the hot source will be seen at its full or "brightness" temperature.

A very important effect is the possibility

of the aerial beam, and certainly the side lobes looking at the earth, especially in radar or horizontal point to point communication systems. A large contribution to the T_a of a low noise receiver can arise from this source. The sun and moon have already been mentioned, but they are small in size and can be avoided with care. The operating frequency, chosen for the lowest T_a and available signal power at the receiver, finally gives us the information, which enables the value of T_{op} to be worked out, thus yielding the signals to noise ratio expected at the output of the system.

(To be continued)

Oscilloscope capacitance meter

Simple measurement technique utilizes the timebase sawtooth waveform to obtain an accuracy better than 5%

by H. v. Z. Smit, B.Sc., B.Eng.(Elec.)

From time to time various methods of measuring the value of a capacitance by means of an oscilloscope have been published^{1, 2}. Many of these methods depend on the determination of the shape of a phase ellipse and therefore a sine-wave source is essential. Also, the value of the capacitance has usually to be calculated from the readings taken. Thus such methods tend to be of academic interest rather than useful in practice.

In the method described here, which can also be used to determine the capacitance/voltage characteristic of tuning diodes, use is made of only one selected resistor to convert the oscilloscope into a direct-reading capacitance meter covering a range between about 1pF and several μ F. The accuracy of measurement is sufficient for most practical purposes. It is necessary for the timebase sawtooth of the oscilloscope to be available externally.

The vertical shift control is first set to fix the zero line on the lowest line of the graticule. The unknown capacitance C and the resistor R are then connected as shown in Fig. 1. Next the vertical deflection control is set for maximum d.c. sensitivity and the horizontal (time scale) is adjusted to give a display such as that shown in Fig. 2. The capacitance value is directly proportional to the vertical deflection after steady state conditions have been reached. This value can be easily read off the vertical centre line of the graticule.

In accordance with the expression given (derived in the Appendix), the value of R should be chosen to give the desired vertical scale factor (pF per cm or μ F per cm).

$$R = TV/vF$$

where V is V /sensitivity of y -input in volts/cm; T is the timebase setting in μ s/cm; v is the sawtooth slope in volts (vertical) per cm (horizontal); and F is the required vertical scale factor in μ F/cm.

For example if: $V=20\text{mV/cm}$, $v=0.92$ volts per horizontal cm and $F=1000\text{pF/cm}$ (required). Choose $T=1\text{ms/cm}$ and the equation gives $R=21.7\text{k}\Omega$. The display shown in Fig. 2 was obtained with this value of R and for the above con-

ditions. The value of the unknown can be read off as 6700pF.

Accuracy of measurement depends on the accuracy of the vertical and time scales, the accuracy with which R is known, the accuracy with which the slope of the sawtooth can be determined, the linearity of the sawtooth and finally the reading accuracy which in turn depends on line thickness, graticule quality and

parallax. Errors attributable to these factors are negligible in practice.

The method has the advantage that the limits of valid measurement are immediately apparent in the display. The minimum capacitance which can be measured is limited by stray capacitances to earth and at the input of the oscilloscope. These capacitances do not introduce errors of measurement but make


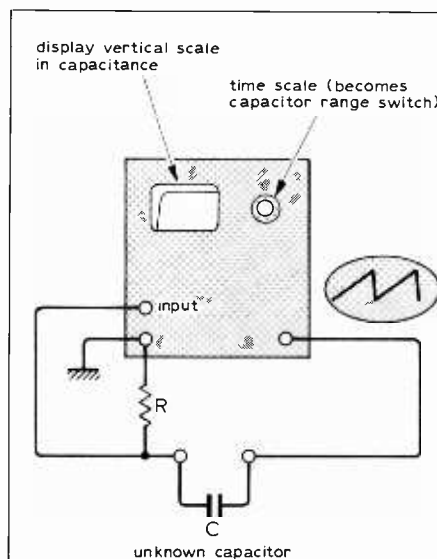


Fig. 1. Circuit used for measuring the value of capacitor C .

Fig. 2. Measurement of a 6700pF capacitor. Time scale is 1ms/cm (corresponding to 1nF/cm). Voltage setting is 20mV/cm.

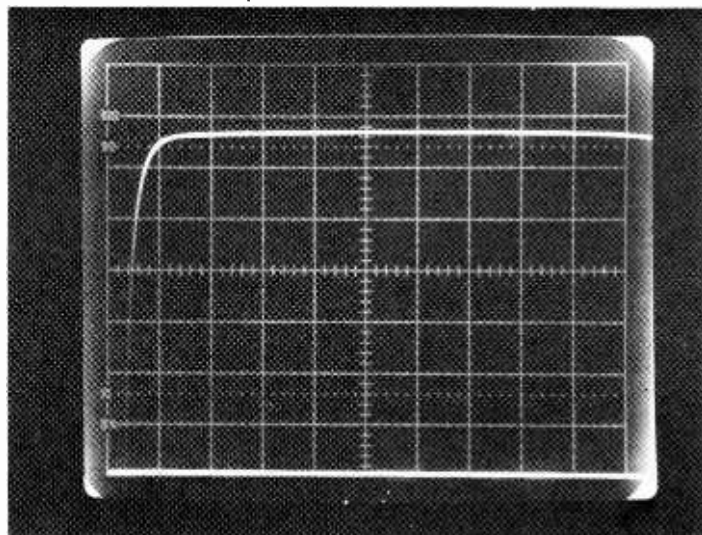

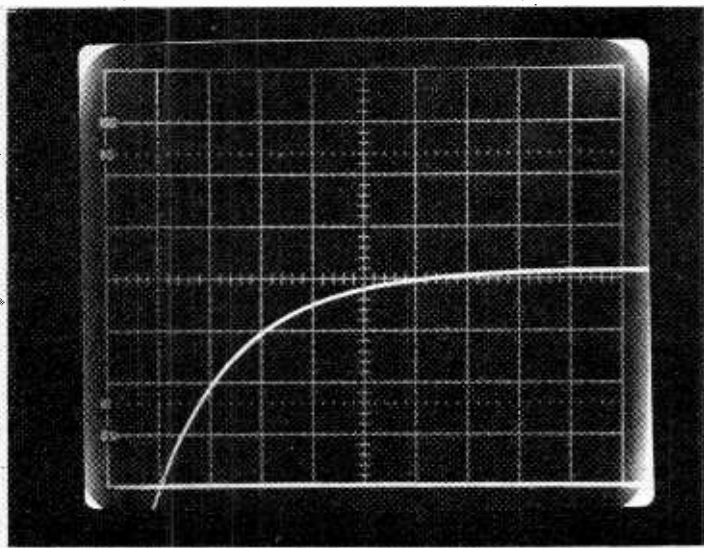


Fig. 3. Measurement of a 2.1pF capacitor. Time scale is 0.5µs/cm (corresponding to 0.5pF/cm). Voltage setting is at 20mV/cm and the oscilloscope input capacitance is 30pF.

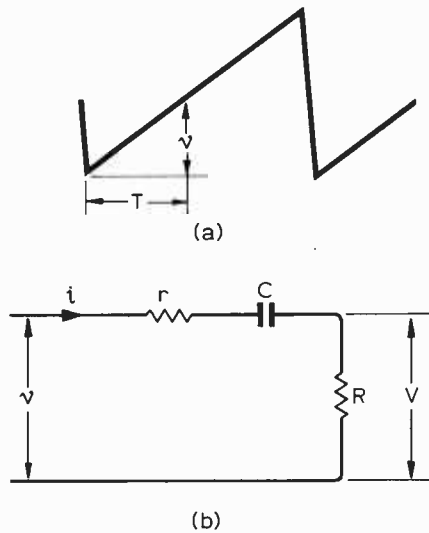


Fig. 4 (a). Timebase sawtooth waveform and (b) the circuit to which it is applied — see appendix.

accurate reading of the display difficult, as shown in Fig. 3.

It is possible to measure capacitances an order smaller than the stray capacitance. Fig. 3 shows a 2.1pF capacitor being measured although the input stray capacitance is 30pF. Theoretically there is no upper limit to the value of the capacitance which can be measured. In practice, however, the time consumed in taking a reading eventually becomes unrealistic, 100s/cm corresponding to 100µF/cm, for instance. On the other hand the practical range can be extended by a factor of 20 to 100 by decreasing the value of *R*. A lower limit to *R* is reached when the time constant *rC* (where *r* is the sawtooth generator output resistance) becomes so great that it “distorts” the waveform on the oscilloscope and a trace similar to that shown in Fig. 3 results.

If reasonable care is taken during the measurement procedure, results can be accurate to well within 5%. Accuracy can be optimized by a suitable choice of *R* and use of a standard capacitor *C* whose value is accurately known.

Appendix

Refer to Fig. 4 (a) which shows the timebase sawtooth waveform. Quantity *T*,

represented by 1cm horizontal deflection, is by definition the time in µs at which the vertical deflection voltage is *v*. At any time *t* voltage is *v_t*, and therefore

$$v_t = vt/T$$

This voltage is applied to the series circuit of Fig. 4 (b) where *r* is the output impedance of the sawtooth generator, *R* is the resistance of the calibrating resistor and *C* is the unknown capacitance. By summing voltages,

$$v_t = vt/T = iR + ir + (1/C) \int i dt$$

Differentiating with respect to *t*

$$v/T = (R + r) di/dt + i/C$$

As *t* → ∞, *di/dt* → 0 and thus *i* → *vC/T*.

The voltage *V* across *R*, as applied to the vertical input of the oscilloscope, is equal to *iR*, therefore

$$V = vCR/T$$

$$\text{or } C = VT/vR$$

By a suitable choice of *R* and *T*, any given value of *V* can be made to correspond with a convenient value of *C*. Thus if *C* is replaced by *F* (µF per cm) then *F* = *VT/vR*, where *V* is now in volts per cm.

References





1. Rider & Usion, “Encyclopaedia on cathode-ray oscilloscopes and their uses”, 1959 edition, pp.14-4 to 14-7.
2. Millay, J., “Progress in semiconductor testing”, *Tekscope*, Nov. 1972, p.3.

HF predictions

Frequency predictions are the expected monthly mean values of HPF, FOT and LUF for a given state of the ionosphere. Since the charts below refer to a specific future period the given state must also be predicted in terms of ionospheric index. A commonly-used index is the 12-month running-mean sunspot number given by

$$R_{12} = \frac{1}{12} \left[\sum_{n=-5}^{n=5} R_{k+n} + \frac{1}{2}(R_{k+6} + R_{k-6}) \right]$$

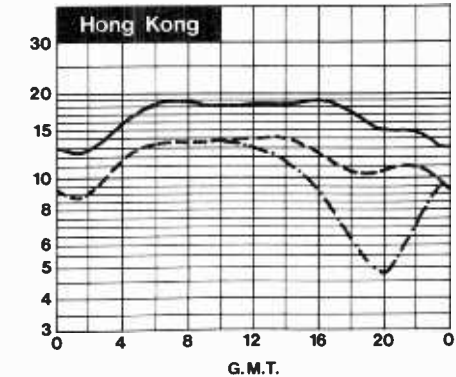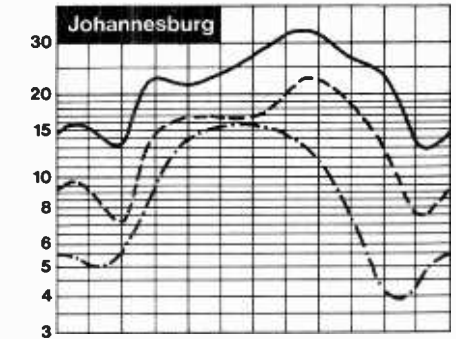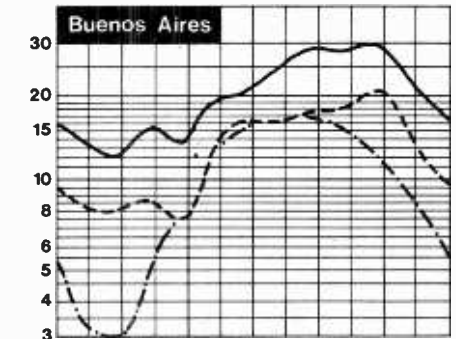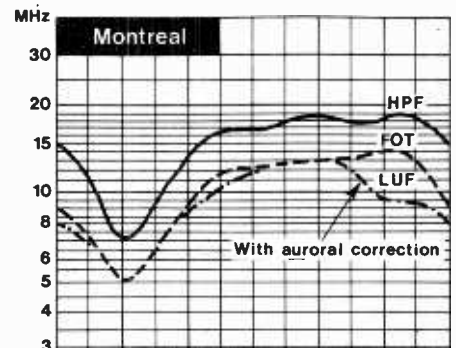where *R* is the mean of daily sunspot numbers for a month represented by its subscript and *R₁₂* is the smoothed index for the month represented by *k*=0. Hence a prediction of *R₁₂* requires an extrapolation of the series at least six months ahead of the last available value.



Coastguard v.h.f. repeaters

System in Scotland using solar power

by J. B. Tuke

National Air Traffic Services

When the Civil Aviation Authority assumed responsibility for aspects of HM Coastguard radio communication services one of the difficulties which had to be studied was the problem of communication between coastguard teams, carrying out routine patrol or rescue work, and their base station. The base may be situated some miles from the scene of action, and the rugged terrain of the Scottish coast makes v.h.f. "walkie-talkie" communication more difficult than usual. By its very nature, a coastguard station is unlikely to be situated on very high ground so that practical v.h.f. range is often restricted to no more than a few miles. In the event of an incident it is essential that any coastguard mobile parties are kept in communication with their base, no matter where in their area they are operating. This can only be arranged by the use of "talk-through" repeaters. The indented coastline with high hills between posed the initial problem, but it also provided the solution since a repeater could be set up on a strategic hilltop having line of sight along the coast.

Unfortunately the most suitable sites are often the most remote and it was soon evident that if the best site was to be used in most cases there could not possibly be an access road or any form of external power supply for the kind of money HM Coastguard could afford.

After consideration, a design formula was evolved which solved both engineering and economic aspects of the problem, reasoning along the following lines. The capital cost of an outside power supply and a road to a remote high site is heavy, likewise the maintenance costs. A self-contained power supply together with highly reliable equipment, on the other hand, could eliminate the need for a road and outside electricity provided that the installation could operate for, say, a year without attention. Further substantial capital and revenue savings could be achieved if the whole station were no more than a weatherproof container capable of being delivered by tracked vehicle or helicopter. In theory the total capital and running costs of such a device would be very small when compared with the cost of a conventional installation, provided that a solution could be found to the engineering problems. The essential parameters are:


- Total reliability.
- Attention, say, only once a year.
- 24-hour capability.
- Ability to withstand extreme climatic conditions.

Attention was given to obtaining a repeater which had minimal current drain in the receive mode, and looking for a suitable power supply. There was something of a "chicken and egg" situation here as the choice of one was dependent on the other.

After study of a number of repeater specifications it appeared that the CQF series manufactured by Storno might well fill the bill. These sets are in themselves weatherproof, having been made in the form of a hinged box where the receiver is in the lid and the transmitter in the box, the two folding together with a weathertight joint. The company were enthusiastic to assist and modify a CQF 612 to reduce the standing receiver current to under 50mA at 24V. The transmitter remained unmodified and delivered 10W output for 24V, 1 amp input. An attractive property of the set is its ability to work well with reduced input—the receiver performance remaining virtually unchanged down to 21V and the transmitter still delivering a good 5W at this figure. In fact the equipment was found to operate—though with some degradation of performance, of course—down to as little as 16V input. This meant that if some form of battery power supply were decided upon a fair amount of latitude existed with regard to input voltage.

Discovery of a suitable battery came about to some extent by chance. A magazine article described extremely long-life cells which at one time were used to operate point motors on railway tracks, and some amateur sleuthing, together with the assistance of the advertising department of the magazine *Electron*, eventually provided the name of Le Carbone—a company in Sussex manufacturing very-long-life, high-capacity alkaline primary cells. The total life capacity of these cells (type AD 608) is over 2,000 ampere-hours, and it was calculated that this would be sufficient to run the repeater for some 400 days for a capital outlay of some £130 assuming the receiver to be on continuously and the transmitter to be operating for not more than one hour daily. Thirty of these cells would be used to power the repeater (nominal voltage 1.2V per cell) with a simple series regulator reducing the initially high battery voltage to 24. As the end-of-life voltage is around 0.8V, a figure approaching 24V total could be expected even a year after installation.

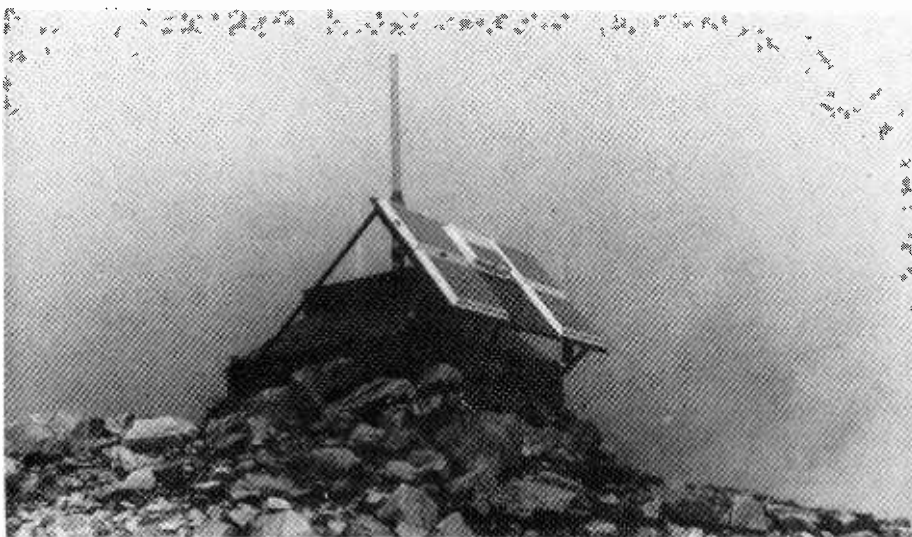The next question was the physical form of the container. There were severe environmental problems if any sort of portable building were to be considered.



Repeater station on Beinn Bheigar in Islay, showing solar panels.

A "hut" on a Scottish hilltop should either be a substantial brick building which simply cannot blow away, or should be something minimal in size and wind resistant—and this latter was decided upon. A metal box 4ft 6in square, 2ft 6in high with a slightly domed roof was constructed. Internally, a two-storey partition was fitted, the batteries to be housed in the lower portion of the box and the radio equipment in the upper. The weight of the batteries (nearly 900lb) would surely keep the box immovable even in the worst of gales, as wind resistance is very low compared with its weight. The container would be completely weatherproof, but with adequate ventilation for the battery compartment (essential for the particular cells used as they are air-depolarized), aided in the unlikely event of calm weather by the natural "breathing" of the device due to daily warming and nightly cooling of the environment.

Consideration had been given to using a short end-fed vertical dipole on the roof of the box for an aerial (in fact this has been used as will be described later) but the first installation was to use a conventional mast with end-fed dipole at the top. A small 25-ft mast was decided upon—this is in fact one section of CAA's standard non-directional beacon mast and has four wire guys to hold it in place.

For purposes of field trials, the North Minch was selected as being most in need of improved communication and typical of the other problem areas in Scotland. The area included the coasts of the Outer Hebrides, the islands of Harris and Lewis, the north-west coast of the Scottish mainland and the northern half of the Isle of Skye. There is a centrally disposed coast-guard station in this area situated in the north of Skye at Duntulm, but v.h.f. communication from here was quite impossible to the south and only a limited range could be expected round an arc between approximately 200 and 080 degrees true. Surveys showed that a repeater on top of Meall Nan Suireamach, just south of Duntulm near the Quirang, would "see" almost all of the area to be covered.

Next came the question of transportation. Since reconnaissance showed the site access to be rock-free and with slopes not exceeding 30 degrees, it was decided to use a tracked vehicle (Sno-Trac), which is used elsewhere by the Authority to gain access to some of the more remote Scottish hill-top radio stations in winter. It is a light tracked vehicle, capable of being transported on a three-ton lorry, and makes its way happily over any soft, boggy or heather-covered ground. Because of its very low gear ratio it can carry quite a considerable weight over quite difficult countryside.

The repeater was duly installed in Skye in the summer of 1972. The ascent of the hill proved relatively simple and the station was established without any real problem. Results were excellent from the start, coverage being from Barra right round through Stornoway and down almost to Kyle of Lochalsh. As expected, the power supply lasted just over the year, and

an "expedition" last year and again this year to replace the battery has found the equipment in good order, both electrically and physically.

A further station was installed in 1973—this time on top of Beinn Bheigar in Islay. As part of an "exercise" the Royal Naval Air Service at Prestwick agreed to position the repeater by helicopter, the entire station being installed and commissioned on the hilltop in about an hour. In this case the end-fed dipole was built on to the top of the equipment container, as the site chosen falls away rapidly on all sides; thus an aerial only some 3ft high at the base provides adequate cover over the southern area of the Inner Hebrides and right across to Northern Ireland.

Having successfully operated the Skye repeater for over two years, and the Islay one for over a year, we turned our attention to further economies, the battery power supply being the most obvious subject for attack. There were three alternative sources of power for study, wind power, atomic power and solar power. The first was ruled out on mechanical grounds—while there is no shortage of wind on the Scottish west coast, no proven windmill system exists capable of withstanding the wind speeds and icing conditions which would be experienced. Atomic power cells suitable for this application do exist, but require prohibitively expensive installation works due to safety restrictions. This left solar power as the only line of enquiry worth following.

The firm of J. Lucas are actively engaged in this field and a comprehensive study was made by them of our requirements. A hilltop site in the west of Scotland may not appear to be the ideal spot for sunshine, but in fact the study showed that the small requirements of our repeater system could be met without undue difficulty, and for a total cost of about £900. With battery and transport costs escalating rapidly, we could expect to "break even" financially in about three years, even at present levels of expenditure.

A solar panel array delivering something over 1 amp at 24V in bright daylight is used to charge a bank of secondary cells, and after relating weather conditions which determine charging, battery efficiency and power consumption, it was decided to use 14 Lucas heart pacemaker batteries of 50 ampere hour capacity in a series-parallel arrangement. This number was based on the worst-case premise that there would be no charging at all during the six weeks either side of the winter solstice. In fact there will, of course, be some small amount of charging, so that all calculations have been made with a good margin for error.

Theoretically the system should go on for ever, the only attention required being the topping up of the batteries. It was for this reason that pacemaker models were chosen, as their topping up requirements are minimal. To reduce this still further special oil has been added to the electrolyte, as floating this on top will reduce losses by evaporation.

The solar panel measures 3½ft square and is mounted on the side of the equipment

box facing due south and angled at 55 degrees. As with the primary cells, the batteries are placed in the lower compartment and the system is at present on a year's trial at the Islay site. Indications so far are most encouraging.

There will still be a yearly visit to the site, but as there is no need to transport a large stock of heavy batteries, it will be a simple hill walk to top up the batteries and generally look over the installation, and under these conditions the costs will be only a small fraction of that entailed when the Sno-Trac has to be used.

If all continues to go well two further sites, in Arran and Mull, are to be fitted with solar power systems as they are installed, and the remaining station in Skye will be converted this year when the routine primary battery change becomes due. It is hoped that with reliable radio equipment and solar power, major visits at only three-to five-year intervals will be necessary when the secondary cells themselves have completed their useful life. Visits of this frequency should ensure a reliable and very cost-effective system for many years to come.

Sixty Years Ago

The editorial leader of the May, 1915, issue of *The Wireless World* in its philosophical attitude towards the essence of wireless telegraphy has not grown outdated in the passing of 60 years. "At such a time as this when the thoughts of the whole world are directed to war, the fact that looms largest in the attention of the general public is that wireless telegraphy is daily proving its utility as a means of establishing communication with ships at sea, both naval and mercantile, with aeroplanes and aircraft, with submarines and on the battlefield. The public imagination has been fired by the revelation of what it can do in regions hitherto untouched, somewhat to the exclusion of recognition of its utility in familiar fields. . . . In fact, it is immaterial whether we look at the manifold activities of the civilized world or let our vision range geographically over the various parts of the globe: whether we confine our attention to the earth or extend it to the air or to the sea—we still feel that a stage has been reached in the development of wireless telegraphy which justifies our contention that ubiquity forms its most striking characteristic."

World of Amateur Radio

End of "BERU"

The 38th BERU contest, held on March 8-9, was the last under the traditional scheme of the old "British Empire Radio Union" although the RSGB has stated that a new form of British Commonwealth contest will be introduced in 1976. Fittingly, BERU bowed out in a burst of good h.f. conditions with even 28MHz opening to Africa, with Australian and New Zealand stations heard at good strength on 7MHz and with stations towards the west of Canada providing good signals on 14MHz. This, perhaps more than any other h.f. contest, has always provided something rather better than a point-slogging frenzy, requiring considerable knowledge of the times at which various paths are likely to be open on the different bands to obtain high scores. Many British amateurs would have been prouder to claim they had finished ahead of the field in a BERU contest than, for example, to have won one of the trendy contests such as those providing free holidays to the winner!

Low-cost s.s.b. generation

In the first enthusiasm for single-sideband operation, many amateurs in the fifties and sixties used phasing-type s.s.b. generation, mostly with wideband networks such as the Dome and "s.s.b. Jr" or commercial units based on similar configurations. The problem was the need for precise values of components that were not too readily affected by temperature or changes in operating frequency. A few amateurs eliminated the need for accurate wideband quadrature networks by adoption of the "third method" though this requires good balance in one pair of mixers to prevent the radiation of a continuous audio tone. Because of these problems and the difficulties of pre-set adjustment amateurs turned increasingly to filter systems based on h.f. or m.f. bandpass crystal filters or m.f. mechanical filters. For the past decade these have been almost universally used both in factory-built and home-built s.s.b. transmitters and transceivers, even though good s.s.b. filters are significantly more expensive than phasing or third method techniques. Filters have proved reliable

in operation and maintain good sideband suppression over long periods without adjustment.

Recently, however, there have been signs that the introduction of digital methods of obtaining 90° phase shifts on r.f. signals (see *Wireless World*, September 1973) has opened the way to low-cost s.s.b. generators that are much easier to set up and require little adjustment over long periods. A number of amateurs have in the past few months successfully implemented both phasing and "third method" systems based on standard integrated circuits as balanced modulators and digital phase-shifters.

But possibly still unique is the work of Peter Martinez, G3PLX of Gosport who is now using on 144MHz a 10.7MHz s.s.b. generator based on the polyphase technique described and patented by M. J. Gingell of STL (*Electrical Communication*, vol. 48, No 1-2, 1973) for use in connection with line telecommunications. Some time ago Peter Martinez designed a six-stage polyphase network based entirely on preferred value components (*Amateur Radio Techniques*, 5th edition, page 181). He has now completed an exciter based on this network in association with a Schottky-clamped 74S74 digital phase shifter, two MC1596 double-balanced modulators, with the "clock" input on 42.8MHz and s.s.b. output on 10.7MHz. Sideband suppression has been adjusted to better than 50dB and he believes that using 1% tolerance resistors it would be quite possible to achieve 40dB.

It seems likely that this is the first time that the polyphase approach has been successfully used in a v.h.f. transmitter—and it is the first reported use of this system in an amateur station. The polyphase network is, in effect, a new way of making a wideband audio phase-shift network and is more tolerant of component values.

Licence trends

The Home Office statistics for licences issued at December 31, 1974 show the continuing trend towards Class B (v.h.f. phone-only) licences which now account for virtually one quarter of British amateur licences, having increased by 638 during 1974 compared with an additional 374 Class A licences. All classes of licence continue to show increases during the year with the total now exceeding 25,000. Fastest rising class of licence is the Class B mobile permit, reflecting the large number of 144MHz n.b.f.m. equipment now in use and the growing number of "repeaters" to extend their range of operation. Since "mobile" licences are usually held by amateurs having also a Class A or Class B permit the total number of British amateurs is now in the region of 20,500.

Amateur licences

	end-1971	end-1972	end-1973	end-1974
Class A	14,065	14,462	14,930	15,304
Class B	3,012	3,718	4,328	4,966
Class A/M	2,666	2,854	3,081	3,424
Class B/M	545	826	1,176	1,549
Television	214	227	254	277
Totals	20,502	22,087	23,769	25,520

Mixed grill

An interesting 20-page account of the development of the original "radio microphone" (at first called a "telesonic" microphone to disguise the fact that a miniature transmitter was involved before the time when the Post Office introduced licences for this application) has been published by Reg Moores of 117 Horton Road, Brighton, who made the first unit in 1947. He is a former professional ice-skater and amateur radio enthusiast (one-time G3GZT I believe) and conceived the idea in the thirties. The first model worked on about 28MHz and later units about 70MHz using three valves. First operational use was for the 1949 Christmas season ice show "Aladdin" at the Brighton Sports Stadium, with the microphone hidden in the clothes of the skater-performers, transmitting signals via a closed loop aerial to an R1481 surplus receiver with the output amplified by a 120-watt Vortexion amplifier. Less happily Reg Moores also believes that this was, in effect, the first "radio bug".

An amateur who has held amateur licences for nearly 50 years is H. E. F. Taylor, G6HT of Torquay who was first licensed as 6FZ in January 1926 (although he had previously operated on 400 to 1000 metres using ex-trench sets of the Felsted OTC) but who, from 1928 to 1956, operated in India under the call-signs VU2FS and VU2AT and during the war in the wireless sections of an Indian Auxiliary Force unit and the Royal Signals.

The RSGB 21st National VHF Convention is being held at the Winning Post Hotel, Whitton, Twickenham, Middlesex on May 10-11 with lecture sessions on the Saturday afternoon and Sunday morning, a dinner-dance on the Saturday evening, trade show and exhibition of home-constructed equipment and with an anticipated attendance of over 700 (details from "VHF Convention", RSGB, 35 Doughty Street, London WC1).

The h.f. beacons ZL2MHF (28.170MHz) at Mount Climie, New Zealand and PY1CK (28.160MHz) at Rio de Janeiro, Brazil, are now in operation but a recent hurricane has put 3B8MS, Mauritius, temporarily out of action. Incidentally, does any reader know the location of the single-letter "beacons" that operate around 20,995kHz and in the 3.5MHz band? I believe they are part of the American Military Affiliate Radio System. Their considerable value as a guide to 21MHz conditions would be enhanced by knowing even roughly where they are located!

R. W. Addie, G8LT recently had a 20-minute r.t.t.y. contact with W2LFL over the Oscar 7 satellite. Battery conditions on the Oscar 6 satellite could mean another year of operational life—it was launched in October 1972 and still going strong.

The Amateur Radio Mobile Society's rally, due to be held on May 18 at Northwick Park Hospital, has had to be cancelled.

PAT HAWKER, G3VA


New Products

100MHz counter-timer

A new 100MHz multifunction counter-timer, known as the model 9838, has been added to the range of counter-timers manufactured by Racal Instruments Ltd. The instrument has a basic sensitivity of 10mV throughout its range, and will directly measure frequency, single and multiple periods or ratios, single and double line time intervals including positive or negative pulses or contact closures and also multiple events. A six-digit filament tube display is provided with gate and overflow i.e.ds to ensure unambiguous measurement in all modes of operation. The counter-timer, which is fully portable, measures 96.5 × 240 × 268mm and conforms to BS4743 safety recommendations. Racal Instruments Ltd, Duke Street, Windsor, Berks SL4 1SB.
WW315 for further details

Heat Pipe

A forced-cooled heat pipe system uses four 18in pipes with a fan-cooled condenser section 6in cubed. The thermal resistance from the pipes to ambient air is 0.05°C/W which allows, say the makers, a dissipation of up to 1.2kW. The system,

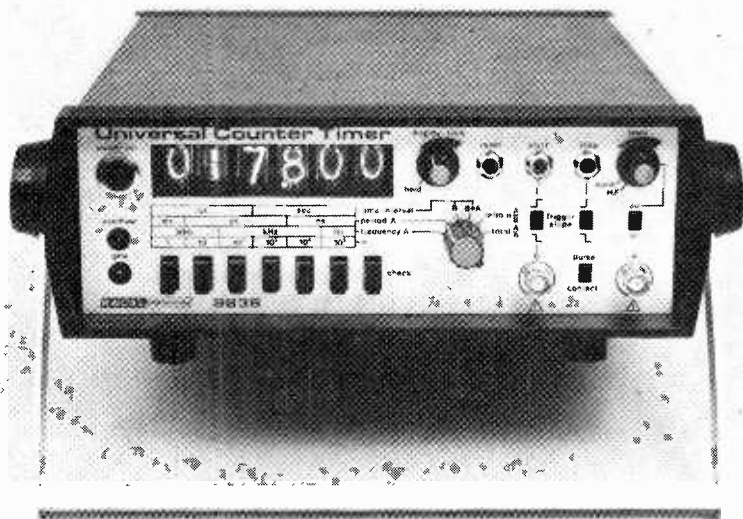

WW315

which may be used to cool fluids or banks of power semiconductors, will operate at temperatures up to 150°C. Solek Ltd, 16 Hollybush Lane, Sevenoaks, Kent.
WW314 for further details

Wire stripper

A pneumatic gun that will cut and strip up to five p.v.c. wires in one operation is now available from ITT. The tool has been designed for fast precision work on cable forms in telecommunication-wiring type operations. Wires from 0.3 to 0.8mm can be cut and stripped at a speed of around 6,000 per hour. ITT Components Group Europe, Equipment Products Division, Thornton Industrial Estate, Milford Haven, Dyfed.

WW316 for further details

Electroplated p.t.f.e. microstrip

Polyplate microstrip substrates in electroplated p.t.f.e. offer low interface losses due to the absence of discontinuity and chemical adhesives between metal electrode deposit and substrate, as well as good machinability, mechanical strength and adhesion. The makers, Polyflon Resine, of Milan, claim a high pulse propagation speed, high dielectric strength and a dielectric constant essentially unchanging with frequency, making them suitable for L-, S-, C- and X-band wavelengths. Polyflon Resine, Via Mezzago, 20050 Sulbiate, Milan, Italy.

WW322 for further details

Camera tubes

The XQ1410 series of Plumbicon television camera tubes features a resolution of better than 700 TV lines and a typical sensitivity of 400µA/lumen. The tubes have a 30mm diameter lead-oxide photoconductive target and use magnetic focusing and deflection. The tubes, which

are directly interchangeable with the less sophisticated XQ1020 series, have a range of matched deflection coil assemblies available to ensure optimum performance. Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD.
WW318 for further details

Temperature alarm

The Digilimit 205 is a temperature indicator which operates from thermocouples or resistance thermometers, and has two independent alarm points. The alarms are digitally set to any point in the temperature range and digital circuitry compares the actual and selected temperatures. The output from each alarm is via a solid-state switch which is isolated from the signal input. Control and Readout Ltd, Burrell Buildings, Churchill Industrial Estate, Lancing, Sussex BN15 8TZ.

WW310 for further details

Coil set


A set of coils for the Motorola MVAM1 varicap diode tuner is announced by Toko. They are medium-wave coils, and the set comprises aerial, r.f. oscillator, detector coils and ceramic filters for use with the µA720/CA3123E integrated circuit series. The set is designated the 6a/3123 and is obtainable from Ambit International, 37 High Street, Brentwood, Essex.

WW320 for further details


Thermostats

The 28030 series of bi-metal thermostats by Electrovac will switch 4A at 25V, 50Hz. It is said to be capable of 10⁵ switching operations and is obtainable with several lead arrangements. Body dimensions are 11mm diameter × 7.5mm and there is a mounting lug. Joseph Electronics Ltd, Westminster House, 188-190 Stratford Road, Shirley, Solihull, West Midlands.

WW321 for further details

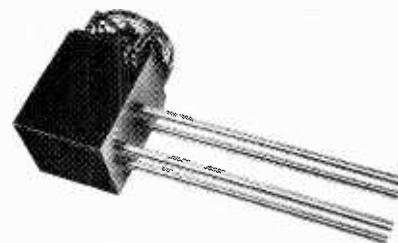

WW314

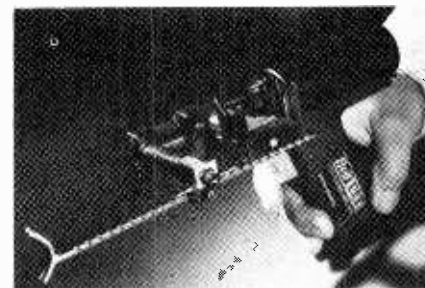

WW316

Oscillator

Type TG200DMP is a sine/square-wave RC oscillator with a frequency range from 1Hz to 1MHz in 12 semi-decade ranges. The instrument incorporates a fine control calibrated from 0 to +1%, and an output voltage variable from 200 μ V to 7V r.m.s. Sine-wave distortion is less than 0.1% below 5V output and between 10Hz and 100kHz. Square-wave rise time is less than 150ns at all frequencies. Levell Electronics Ltd, Moxon Street, Barnet, Herts.

WW308 for further details

Ribbon cable

A new range of ribbon cables includes bonded and extruded types with solid or stranded copper conductors providing a choice of current ratings. The cables have a p.v.c. colour-coded insulation with an operating temperature range from -10 to +70°C. Belling & Lee Ltd, Great Cambridge Road, Enfield, Middlesex.

WW317 for further details

Resistors

A range of resistors from 1 Ω to 100M Ω is available in a $\frac{1}{4}$ W package measuring only 0.25 \times 0.09in diameter. These miniature components have resistance variations of less than 2% in the temperature range -15 to +85°C with a failure rate of less than 0.001%/1000hrs. Jermyn Distribution, Sevenoaks, Kent.

WW319 for further details

Power supplies

Marconi Instruments has introduced a new range of general-purpose d.c. power supplies comprising the TF2153/154/155. These supplies provide a choice of voltages

up to 60V and currents up to 4A, with a maximum power of 30W. Push-buttons alongside the panel-meter select monitoring of output voltage or current, with two sensitivities for each mode. Marconi Instruments Ltd, Longacres, St Albans, Herts.

WW311 for further details

200-way switch

A new switch from Sakae can be supplied for switching 30, 50, 100 or 200 ways; the switches can also be ganged. The contacts are arranged on a helical mounting strip, the wiping contact traversing the switch contacts in 3, 5, 10 or 20 complete rotations respectively. The indexing mechanism for the switch is contained in a multi-turn dial, giving an accuracy of switching to within $\pm 2^\circ$. Techni Measure Dell House, Eastern Dene, Hazlemere, High Wycombe, Bucks HP15 7BT.

WW313 for further details

Coaxial attenuators

The Elcom Systems AT-50 series of calibrated 50 Ω fixed attenuators can be used from 0 to 1500MHz. The devices are rated at 0.5W c.w. or 1000W peak power in the temperature range -25 to +85°C and are available as separate components or in sets with values of 1 to 10dB in 1dB steps and 10 to 20dB in 2dB steps. Aspen Electronics Ltd, 18a High Street, Northwood, Middlesex HA6 1BN.

WW312 for further details

Decade resistance box

The DB5R decade resistance box uses thumbwheel switching to select resistances from 10 Ω to 1M Ω in five decades. The unit is housed in a plastic box with two

sockets for the output. A chart for selecting resistor values is also available from the manufacturers. H & W Logitek Electronics Ltd, 13 Carron Place, Kelvin Industrial Estate, East Kilbride.

WW307 for further details

Capacitance meter

A direct-reading capacitance meter with dimensions of 150 \times 85 \times 40mm will measure capacitances up to 0.5 μ F in five switched ranges. The meter is powered from two 9V batteries and incorporates a battery-check facility. Chinaglia (UK) Ltd, 19 Mulberry Walk, London SW3.

WW304 for further details

Multimeter


The model 2000 Danameter is one of the few instruments to use a liquid crystal display which, because of the very low power consumption, gives a claimed battery life of one year. The meter will measure direct and alternating voltages up to 1000V with a resolution of 1mV, direct current up to 2A with a resolution of 0.01 μ A, and ohms up to 200M Ω with a resolution of 0.1 Ω . Dana Electronics Ltd, Collingdon Street, Luton, Beds.

WW303 for further details


Digital to d.c. converter

The model 1501 converts a 14-bit digital input into two d.c. output voltages which are proportional to the sine and cosine of the input phase angle from 0° to 360°. Specifications of the instrument are an accuracy to within $\pm 5\%$ at 25°C, and individual outputs accurate to within $\pm 0.1\%$ f.s.d. at 25°C.

The input is buffered and includes a storage register that holds each data bit. A positive pulse, t.t.l. level, 2 μ s in width

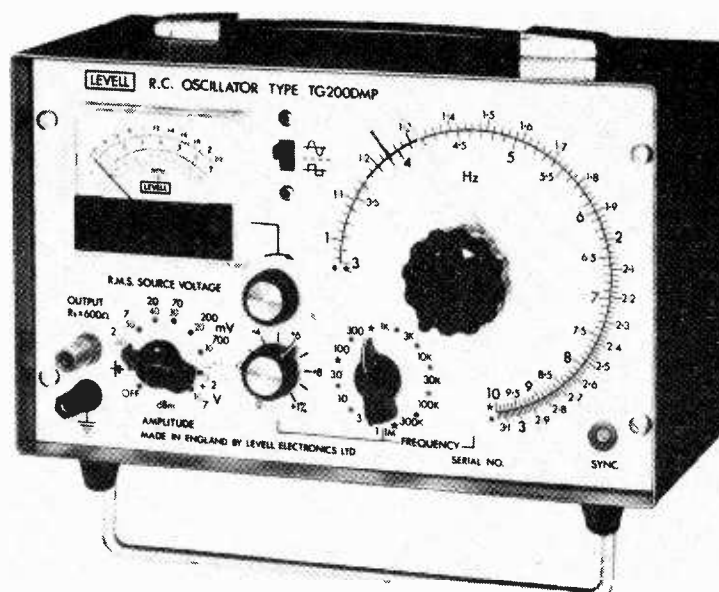

WW308

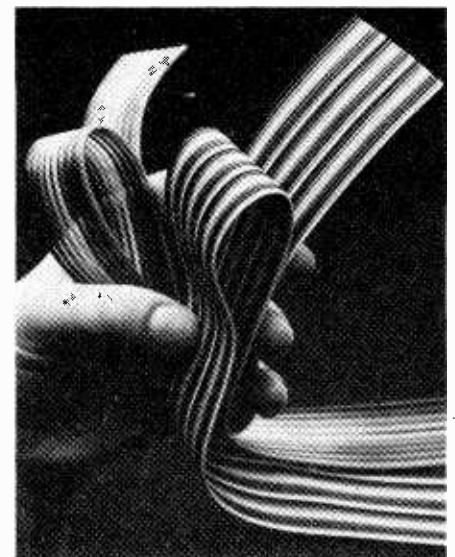


WW317

controls the transfer of data into the input register. The output voltages vary from 0 to $\pm 10V$ d.c. with an output impedance of 1Ω for each source. REL Equipment and Components Ltd, Croft House, Bancroft, Hitchin, Herts SG5 1BU.
WW302 for further details

Level recorder

B & K Laboratories has announced a portable graphic level-recorder weighing only $7\frac{3}{4}lb$. The instrument, type 2306, provides three recording modes—logarithmic a.c. and d.c. in two dynamic ranges, and linear d.c. with variable zero calibration. In the a.c. mode, r.m.s. values of waveforms in the frequency range 1Hz to 20kHz are recorded with an accuracy to within $\pm 0.5dB$. In the d.c. modes, sinusoidal signals up to 1.6Hz may be recorded. B & K Laboratories, Cross Lances Road, Hounslow, Middx.
WW309 for further details

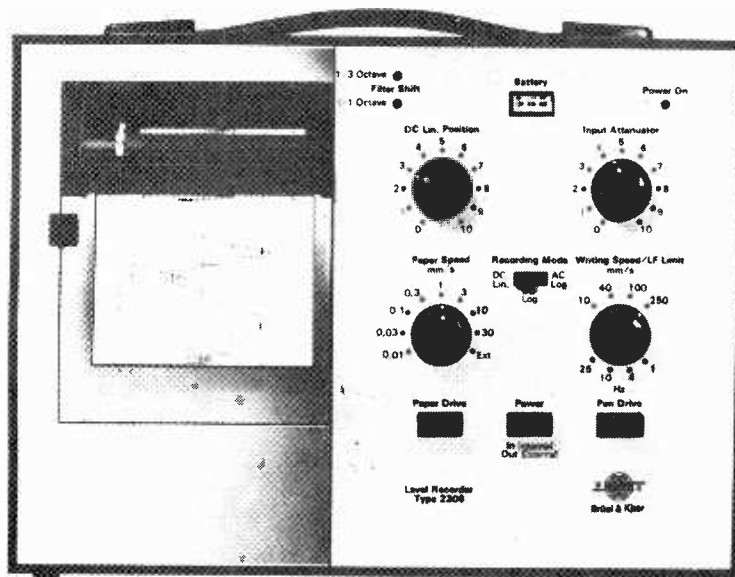


WW309

Mixing desks

Cambridge Electronic Workshop has developed a new range of portable, stereophonic sound-mixing desks for theatre use. Features of the equipment are continuously variable presence-frequency and gain, separate mic. and line inputs and two auxiliary sends with pre/post switching on all ten channels. Other useful items on the desk are cue lights, intercom system, monitoring facilities and loudspeaker switching. The desks, which have 0.1% distortion and input noise better than $-126.5dBm$, measure 24in square \times 11in high for the standard version with special requirements on request. Cambridge Electronic Workshop, 8 Perowne Street, Cambridge.

WW306 for further details

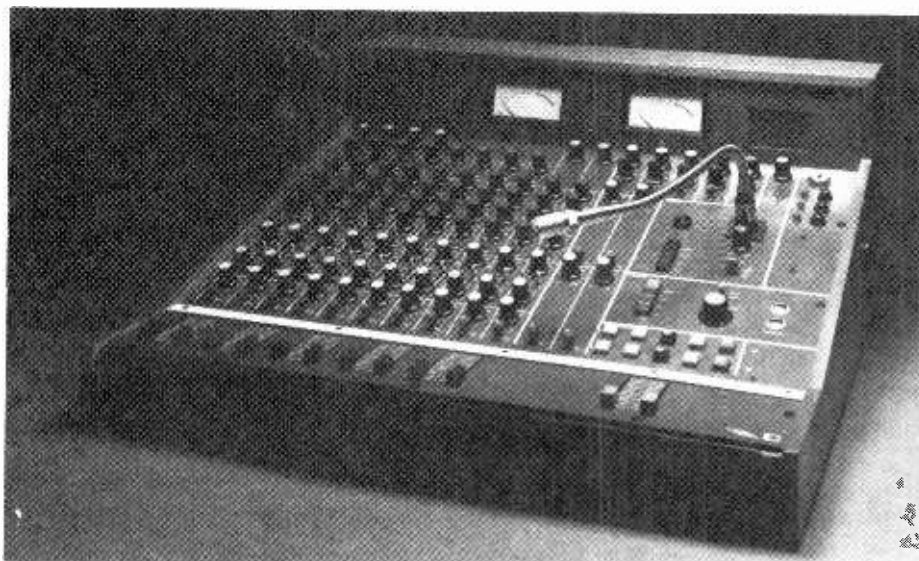


WW306

p.c.b. assembly frame

The DURO-04 p.c.b. assembly frame will accept boards from $1.5 \times 1.5cm$ up to $30 \times 42cm$. The boards can be located in any position on the frame where they are held in position by special clips. After the components have been inserted they are held in place by closing the lid, which is lined with a foam material. The frame is then turned over to expose the underside of the p.c.bs for soldering. Circuitape Ltd, New Street, Aylesbury, Bucks.

WW305 for further details

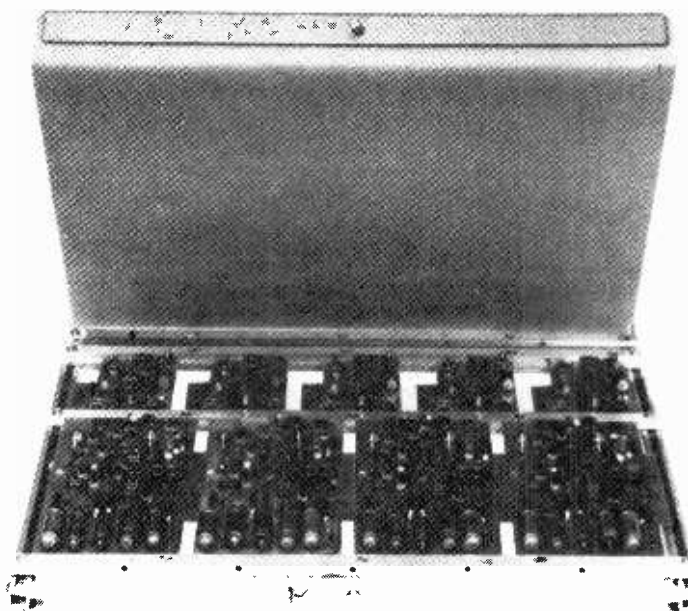

WW305

Digital i.c. tester

Electro Scientific Industries has introduced an i.c. tester suitable for evaluating t.t.l., d.t.l. and c.m.o.s. logic in d.i.l. packages. The tester, model 1248, does not require a reference i.c. because each device is separately switch-programmed. Tranchant Electronics UK Ltd, Tranchant House, 100a High Street, Hampton, Middlesex TW12 2ST.

WW301 for further details

Microwave detector

A hand-held r.f. monitor has been designed to measure leakage fields emanating from microwave ovens. Operating frequency is 2450MHz \pm 25MHz and the indicated power range is from 0 to 10mW/cm². R. E. L. Equipment Ltd, Croft House, Bancroft, Hitchin, Herts.

WW327 for further details

Modular benching

Modular benching from Modulux is based on standard bench modules with a variety of ancillary equipment including drawers, databoards and trunking. Metal parts of the systems are stove-enamelled and the bench tops are covered in either a laminate or a non-slip material. Modulux, St. Michael's Road, Aldershot, Hants GU12 4JW.

WW326 for further details

Boxes

Boplast polycarbonate boxes are built to VDE standards, will withstand temperatures up to 140°C, and are water/oil/petrol resistant. The range contains 28 sizes from 35×52×5mm rising to 36×20×15cm with two sizes available with clear covers. Prices vary from 75p to £9 depending on size and quantity. West Hyde Developments Ltd, Ryefield Crescent, Northwood, Middx HA6 1NN.

WW325 for further details

Miniature coaxial cables

Miniature coaxial cables, suitable for applications up to 3GHz, feature a silver-plated copper conductor, p.t.f.e. dielectric, silver-plated copper screen and an outer sleeve, allowing operation in the -90 to +200°C temperature range. Type 50VMTX is a 50Ω cable with a diameter of 1.17mm and type 75VMTX is a 75Ω cable of 1.22mm in diameter, Waycom Ltd, Wokingham Road, Bracknell, Berks RG12 1ND.

WW328 for further details

Solid State Devices

The names of suppliers of devices in this section are given in abbreviation after each entry and in full at the end of the section.

Stripline mixer diodes

Models 5082-2207/10 are passivated silicon Schottky diodes in the beam-lead configuration, intended as mixers for microwave i.c.s, microstrip or stripline

application. Lowest noise figure (5082-2207) is 6dB at .9GHz, with a v.s.w.r. of 1.5:1. Matched pairs are available.

WW350 for further details

Hewlett-Packard

Bipolar RAMS

256-bit bipolar random-access memories in low-power Schottky format. Access time is 45ns over the temperature range 0°C to 75°C and device dissipation is 275mW. Both models—Am27LS00/1—are organised as 256 words by 1 bit with either tri-state ('00) or open outputs.

WW351 for further details

Advanced Micro Devices

Calculator chip

A m.o.s. calculator i.c., C596 intended for eight-digit "slide-rule" calculators, offers the four arithmetic functions, trigonometric (in degrees or radians) and log functions. There is also provision for \sqrt{x} and $1/x$ and a key for π . The chip can be used either in dual-function key calculators or in 35-key single-function units. Floating point or scientific operation can be used, overflow causing the automatic change to scientific notation of mantissa and exponent. The new i.c. has the same pin connexions and voltage levels as the C594 and C595, which means that four-function calculators can be updated very easily.

WW352 for further details

GIM

Peripheral interface

MC6820 is a peripheral interface adaptor for use between input/output equipment and the Motorola microprocessor and contains six registers with a control and selection logic section. Control lines between the microprocessor and p.i.a. give the former control of the latter, although the p.i.a. can interrupt to allow a peripheral unit access.

WW353 for further details

Motorola

Power transistors

A range of TO-3 metal power transistors from Thomson-CSF, using the n-p-n triple-diffusion technique. Types are BUX10 to BUX15, rated at 150W at between 125V V_{ce0} at 25A and 500V V_{ce0} at 8A. BUX20 to BUX25 are 250W devices for up to 500V V_{ce0} at 15A.

WW354 for further details

Lock

Si rectifiers

Three families of power diodes. The BYX98 family possess a non-rep. surge rating of 60A and rep. p.r.v. from 300V to 1200V. BYX99 are rated similarly at 160A and up to 1200V, and BYX96 are 20A types at up to 1600V. All types are in DO-4 encapsulations and reverse polarity versions are available.

WW356 for further details

Mullard

A/d converter

MN 5210 is a family of 12-bit analogue-to-digital converters with a maximum conversion time of 12μs. Power dissipation is 700mW from 15–0–15V and 5V rails, and input ranges are 0 to -10V, \pm 5V or \pm 10V with internal or higher-precision external references. Accuracy of $\pm \frac{1}{2}$ least significant bit is offered over commercial or military temperature ranges.

WW355 for further details

Tranchant

Thyristor

The CS651 thyristor possess a built-in, auxiliary thyristor which is switched on by a small pulse. When the forward current of this device reaches a high value it is applied to the main thyristor gate. This feature is claimed to provide a 75A/μs di/dt rating. The unit is in disc form and withstands repetitive p.r.v. of 2.4kV, continuous limiting current of 650A and a surge current of 14000A.

WW357 for further details

Brown Boveri

Timer

A product of the Ferranti collector diffusion isolation technique for the provision of digital and linear elements on one chip. A variable-frequency RC oscillator drives a divided-by-4096 counter, the frequency being externally adjustable, and the timed period is 4096 CR, where C and R are external components.

WW358 for further details

Ferranti

Yellow l.e.ds

Siemens have added yellow-light devices to their range of light-emitting diodes. Types LD35 (3mm) and LD55 (5mm) are gallium phosphide units, and LD48 contains up to 10 characters per row.

WW359 for further details

Siemens

Hewlett-Packard Ltd, King Street Lane, Winnersh, Wokingham, Berks RG11 5AR.
Advanced Micro Devices Inc., 901 Thompson Place, Sunnyvale, California 94086, USA.

General Instrument Microelectronics Ltd, 57-61 Mortimer Street, London W1N 7TD.
Motorola Ltd, York House, Empire Way, Wembley, Middlesex.

Lock Distribution, Neville Street, Middleton Road, Oldham, Lancs OL9 6LF.

Tranchant Electronics (UK) Ltd, Tranchant House, 100a High Street, Hampton, Middx.
Mullard Ltd, Mullard House, Torrington Place, London WC1E 7HD.


British Brown-Boveri Ltd, Albany House, 41 High Street, Brentford, Middx TW8 0BH.

Ferranti Ltd, Electronic Components Division, Gem Mill, Chadderton, Oldham OL9 8NP.

Siemens Ltd, Great West House, Great West Road, Brentford, Middx.

SIEMENS

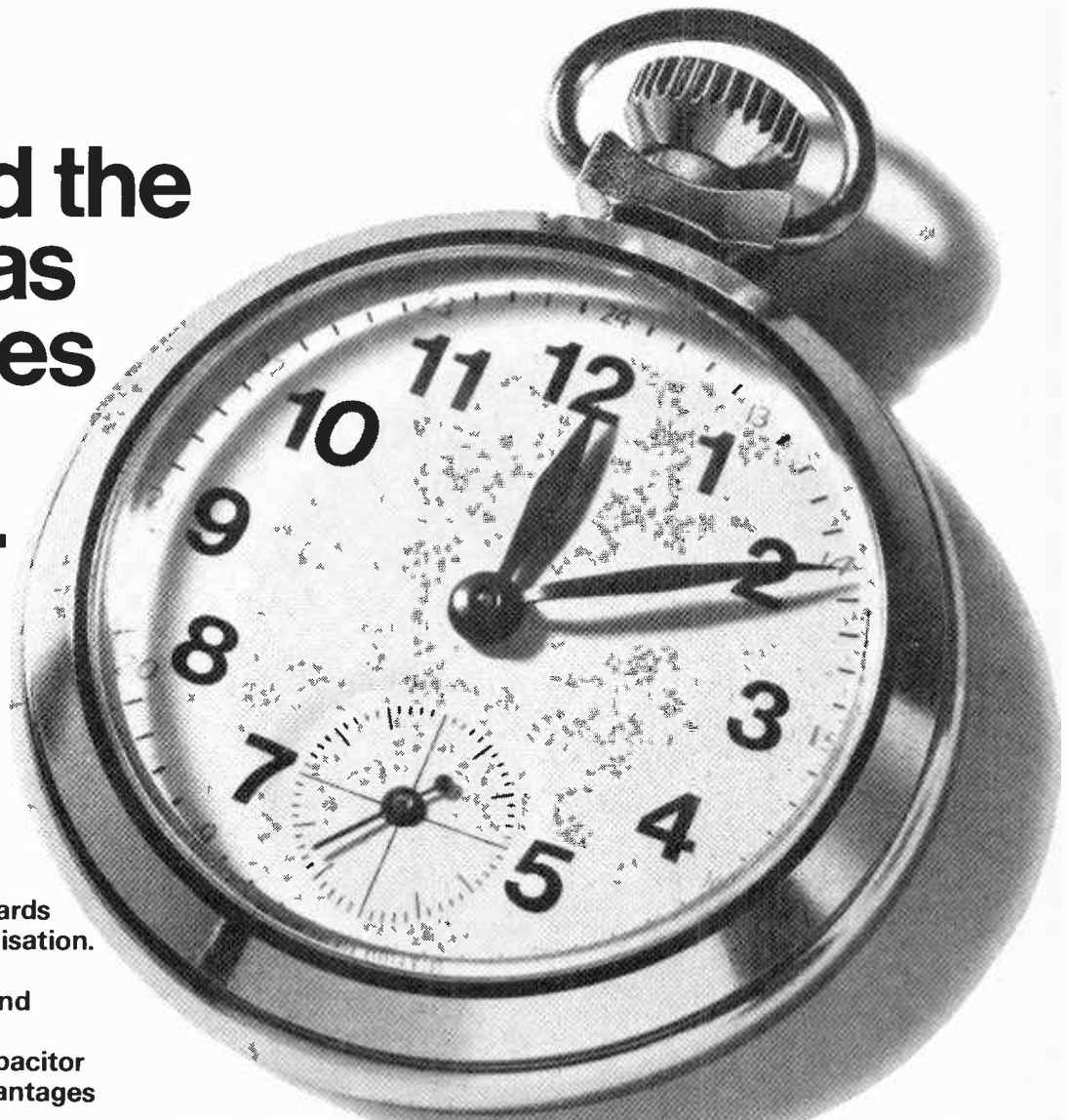You'll find the best ideas 10 minutes from Olympia.



- The Siemens approach to Professional Electronic Components.
- Quality Assurance, Standards and Specification harmonisation.
- Memory I.C.'s. Review of Research, Development and current production.
- Modern techniques in Capacitor manufacture and the advantages to the user.
- Analogue I.C.'s for the Industrial user.
- Why Surge Voltage Protectors? A review of the technology and their application.
- Electro-mechanical components for the Electronics Industry.
- Low Speed High Noise Immunity Logic (LSL) : A logic system for industrial applications.

Being a company vitally involved with the future of electronic components, Siemens personnel include leading experts in many areas of our profession. So we've arranged a daily symposium on these 8 subjects.

The Siemens Symposia 1975 will be held at the Kensington Close Hotel, off Kensington High Street, W.8. from Tuesday, May 13th to Friday, May 16th, between 1.30 pm and 5.30 pm daily.

As space is restricted, please complete the coupon below and return it to us as quickly as possible. We will be delighted to send you a special invitation.

Do join us for an interesting and valuable experience.

At the Siemens Symposia 1975 (RECMF Week)

To Siemens Limited, Marketing Services Division, Great West House, Great West Road, Brentford, Middx. TW8 9DG.

Please send me a special invitation to the Siemens Symposia 1975.

Name _____ Position _____

Address _____ Company _____

I would like to join you on
 MAY 13th 14th 15th
 16th (Please tick date
 box preferred for 1st
 alternative date.)
 wwz

MAPLIN ELECTRONIC SUPPLIES

Get your 1975
CATALOGUE!

Includes dozens of useful and interesting circuits you can build; data; hundreds of pictures, transistor equivalents list and hundreds of new lines. Packed with information. Only 40p



SUPERSONIC SAME-DAY-SERVICE - MEANS QUALITY COMPONENTS - FAST!

RESISTORS

CARBON FILM
1/4W 10 to 1M : 5%, IM2 to 10M : 10% E12
1/4W 10 to 100 : 5%, IM2 to 10M : 10% E12
1/10 to 910k : 5% E12 & E24 1p each.

METAL OXIDE
1/4W 100 to 1M : 2% E12 & E24 4p each

WIREWOUND
3W 0.22Ω, 0.27Ω, 0.33Ω, 0.47Ω : 10%
1.2Ω to 270Ω : 5% E12 17p each
1.2Ω to 270Ω : 5% E12 13p each

Other ranges stocked. See our catalogue for details.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades.
E24: 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades.

POTENTIOMETERS

Rotary miniature carbon track 1" spindle. Values available:
5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M.

Log single-gang 16p, Lin single-gang (+1k) 16p
Log or Lin, single-gang with switch 33p
Log, or Lin, dual-gang without switch 49p
Slider 60mm track. Metal-cased overall length 86.15mm less knob (7p extra).
Log, or Lin, 1k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M. Single-gang 36p, Dual-gang 45p

Presets: 0.1W Vertical or Horizontal.
100Ω, 220Ω, 470Ω, 1k, 2k2, 4k7, 10k, 22k, 47k, 100k, 220k, 470k, 1M 7p each.

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1.83 6p	68 6.3 6p		
1.5 63 6p	68 16 6p		
2.2 63 6p	68 63 14p		
3.3 63 6p	100 4 6p	Mfd V Price	
4.7 63 6p	100 10 6p	470 6.3 6p	
6.8 40 6p	100 25 6p	470 10 14p	
6.8 63 6p	100 40 6p	470 25 16p	
10 25 6p	100 63 16p	470 40 25p	
10 63 6p	150 6.3 6p	680 6.3 14p	
15 16 6p	150 16 6p	680 16 16p	
15 40 6p	150 25 6p	680 25 25p	
15 63 6p	150 40 14p	680 40 28p	
22 10 6p	150 63 16p	1000 4 14p	
22 25 6p	220 4 6p	1000 10 16p	
22 63 6p	220 10 6p	1000 16 25p	
33 6.3 6p	220 16 6p	1000 25 28p	
33 16 6p	220 25 14p	1500 6.3 16p	
33 40 6p	220 40 16p	1500 10 25p	
47 4 6p	220 63 25p	1500 16 28p	
47 10 6p	330 4 6p	2200 6.3 25p	
47 25 6p	330 10 6p	2200 10 28p	
47 40 6p	330 16 14p	3300 6.3 28p	
47 63 6p	330 63 28p	4700 4 28p	

SWITCHES

Rotary adjustable stop, 1 pole, 2 to 12 way; 2 pole, 2 to 6 way; 3 pole, 2 to 4 way; 4 pole, 2 or 3 way 36p each.

Slide Sub-min. DPDT 9p
Slide min. DPDT 13p
Push to make non-locking SPST 14p
Push-on, push-off locking DPDT 250V 4A 36p
Rocker white DPST 250V 10A 40p
Rotary mains DPST 250V 2A 24p
Toggle with ON/OFF plate DPDT 250V 1.5A 25p

BCD OUTPUT SLIDE SWITCH
Marks the end of the old-fashioned thumb-wheel switch. With 7-segment type read-out. Full details in our catalogue 11.38

TRANSISTORS & DIODES

AC127	18p	BFY52	20p
AC128	18p	8Y126	13p
AC176	17p	BY127	13p
AD161/		BY164	45p
162MP	93p	BZ988	65p
BA100	9p series		
BA145	22p	MPF102	36p
BC107	11p	OA91	6p
BC108	10p	QA200	7p
BC109	13p	OC71	20p
BC109C	15p	SC146D	88p
BC142	23p	T1543	28p
BC143	26p	W005	30p
BC147	10p	W04	33p
BC148	10p	1N914	4p
BC149	12p	1N4001	6p
BC168C	12p	1N4002	6p
BC169C	12p	1N4003	7p
BC187	17p	1N40K	73p
BC182L	10p	1N4005	8p
BC183L	12p	1N4006	8p
BC184L	12p	1N4007	9p
BC212L	14p	1N4148	4p
BC213L	15p	2N1302	20p
BC214L	18p	2N1303	20p
BCV71	22p	2N1304	30p
BD131	45p	2N1711	24p
BD132	54p	2N2219	25p
BD131/		2N2646	45p
BD132MP		2N2905	33p
	£1.20	2N2926 Ye12p	
BD135	36p	Gn	13p
BD139	49p	2N3053	18p
BD140	69p	2N3055	49p
BF258	35p	2N3819	22p
BF259	25p	2N5459	51p
BFX29	30p	7400	16p
BFX30	33p	7413	39p
BFX84	30p	7447	£1.10
BFX85	36p	7473	54p
BFX87	30p	7474	45p
BFX88	25p	7490	82p
BFY50	20p	7493	82p
BFY51	22p	74121	39p

L.E.D. RED.
2mcd 1" 15p
Panel mtg. clip 5p
(Other colours and 7-seg displays in our catalogue.)

INTEGRATED CIRCUITS

CA3046 (14-pin DIL)	69p
LH0042CH (TO99)	£4.25
MC1310P (14-pin DIL)	£2.50
MC1496 (UA796) (14-pin DIL)	78p
MFC4000B MFC6040	59p
NE555V (8-pin DIL)	83p
SG1495 (14-pin DIL)	65p
SG3402 (14-pin DIL)	£2.70
µA741C (8-pin DIL)	£1.69
µA741C (14-pin DIL)	36p
µA747C (14-pin DIL)	45p
µA747C (14-pin DIL)	£1.05
µA748C (8-pin DIL)	39p
ZN414 (TO18)	£1.20

VOLTAGE REGULATORS
µA7805 5V 1.5A (TO3) £1.75
µA7815 15V 1.5A (TO3) £1.75
MVR 5V, 12V, 15V 500mA (TO3) £1.60
µA78M05 5V 500mA (Plastic power) £1.05
µA78M15 15V 500mA (Plastic power) £1.05
µA78L05 5V 100mA (TO92) 60p
µA78L15 15V 100mA (TO92) 40p
µA723C variable 2 to 37V (TO99) or 14-pin DIL 75p
Our catalogue contains application circuits and data for all the above I.C.s and many more.

DISCOUNTS

Details in our catalogue. Start collecting MES Discount Vouchers NOW!

PLUGS AND SOCKETS

DIN	PLUG	CHASSIS SOCKET
2-pin	8p	6p
3-pin	9p	7p
4-pin	10p	7p
5-pin A(180°)	10p	7p
5-pin B(240°)	10p	7p
6-pin	10p	9p
7-pin	10p	8p

JACK PLUGS

2.5mm plastic barrel	9p
2.5mm metal barrel	15p
3.5mm plastic barrel	9p
3.5mm metal barrel	15p
1/2 in. std. mono plastic barrel	13p
1/2 in. std. mono metal barrel	24p
1/2 in. std. stereo plastic barrel	18p
1/2 in. std. stereo metal barrel	30p

JACK CHASSIS SOCKETS

2.5mm open-type metal	9p
3.5mm open-type metal	9p
1/2 in. std. mono open-type metal	13p
1/2 in. std. mono moulded with 2 break contacts	14p
1/2 in. std. stereo open-type metal	15p
1/2 in. std. stereo moulded with 3 break contacts	21p

In-line sockets also stocked: see catalogue

PHONO

Plastic-topped plug	5p
Screened plug	12p
Chassis socket single	5p
Chassis socket twin	7p

MAINS CONNECTORS

P360 3-pin 1.5A chassis plug with line socket	33p
SA21903 3-pin 5A chassis plug	25p
SA1862 Line socket for SA2190	28p
PA37 3-pin 5A chassis socket with line plug	66p

TRANSFORMERS

LT700 min. output. Pri. 1k2; Sec. 5Ω 200mW	50p
Sub-min mains 6-0-6V 100mA	95p
12-0-12V 50mA (Size both approx. 30x27x25mm)	95p
Min. mains 0-6V 500mA, 0-6V 500mA	£1.55
0-12V 250mA, 0-12V 250mA	£1.55
0-20V 150mA, 0-20V 150mA	£1.55
0-24V 125mA, 0-24V 125mA	£1.55
Mains MT3AT: Sec: 12-15-20-24-30V 2A	£3.98
Mains MT206AT: Sec: 0-15-20V 1A, 0-15-20V 1A	£3.98

ORGAN CONSTRUCTION

A Full-Scale Electronic Organ that you can build to your own specification.

FULL CONSTRUCTIONAL DETAILS IN OUR LEAFLETS

Leaflet MES 51: price 15p, describes a fully polyphonic basic organ which can later be used as the basis of a large sophisticated instrument. Leaflet MES 52: price 15p, continues the description of the MES 50 series organs and shows you how to add a second keyboard with lots more stops. Further leaflets to follow at approx. two-monthly intervals.



THE AMAZING DMO2


A ready-built, tested and guaranteed digital master oscillator. Accurately generates the top 13 notes for your organ system and reduces the complete tuning of your organ to ONE SIMPLE adjustment. New design gives selectable C to C output ranges of (approx.) 4k to 8k (highest) or 2k to 4k or 1k to 2k, etc., right down to 16Hz to 32Hz! And this new compatible design is even smaller: only 3.5in. x 3.7in., including gold-plated edge connexion. DMO2T includes built-in variable depth and rate frequency shift tremulant. DMO2 £12.25 DMO2T £14.25
SAJ 110: 7-stage frequency divider in 14-pin DIL package. Sine or square wave input. Square wave output may be converted to saw tooth. £1.80 each or 6 for £9.94 or 12 for £18.16.

ORGAN COMPONENTS

Keyboards high quality, fully sprung.
Flat-front 48-note F to E £15.95
Sloping-front 49-note C to C £15.95
Sloping-front 61-note C to C £20.35
Swell pedal with 10k log. pot £6.33
*Spring line unit (short) £3.05
*Spring line unit (long) £8.29
*Reverberation driver module £5.34
*S.a.e. please, for full details: leaflet MES 24.
Gold-clad phosphor-bronze wire 30p per yd.
Palladium earth bar 15p per octave length.
Contact blocks 2-make (GB2) 22p
Stop tabs, rocker type, not engraved (white, red, grey or black) with DPDT switch 59p

"ELECTRONICS TODAY INTERNATIONAL" 4600 SYNTHESIZER

We stock all parts for this brilliantly designed synthesiser. This includes all the PCBs, metalwork and drilled and printed front panel giving a truly professional finish. Authoritative opinions agree the ETI International Synthesiser is technically superior to most of today's models. Complete constructional details in our booklet, available shortly. S.a.e. please, for price lists and specification.
We also stock all parts for the P.E. Synthesiser and Minisonic.

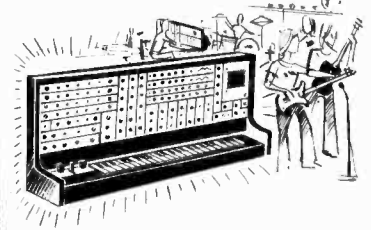

P.O. Box 3, Rayleigh, Essex. Tel: Southend-on-Sea (0702) 44101.

VAT. Please add 8% to the final total. Post and packing FREE in U.K. (15p handling charge on orders under £1) First-class post pre-paid envelope supplied free with every order.

CHROMASONIC electronics

Dept 5
56, Fortis Green Road, London, N10 3HN
telephone 01 883 3705

OPTOELECTRONICS

Monsanto

Xelton

litronix



Color	Common Anode	Common Cathode	Overflow (+1)	DL 707 0.3" high character 14 pin DIL	DL 747 0.6" high character L.H. Dec Pt.
Red	MAN 72	MAN 74	MAN 73		
Green	MAN 52	MAN 54	MAN 53	DL 701 (±1)	DL 746 (±1)
Yellow	MAN 82	MAN 84	MAN 83	Common Anode Red Only	Common Anode Red Only
	L/H Dec. Pt.	R/H Dec. Pt.			
	OUR PRICE £1.83	£1.83		£2.65	

LIGHT EMITTING DIODES

Free snap-on plastic retainer

0.125" dia

0.2" dia

TIL209 size

MLED650 size



	Our Usual price	Special Pack Price	Our Usual price	Special Pack Price
10 RED	£2.40	£1.99	£2.80	£2.39
10 GREEN	£1.10	£3.40	£4.50	£3.99
10 YELLOW	£3.80	£7.99	£9.90	£5.99
10 WHITE	£3.50	£3.39		
10 ORANGE	£3.10	£2.59	£4.90	£4.39
10 RED			0.175" dia T092 size	£1.70 £1.39

LINEAR I.C.'s

709 (8 pin dip)	33p				
709 (TO-99)	39p	LM377	£2.91	SL414	£1.72
709 (14 pin dip)	34p	LM380	£1.08	SL415	£2.24
710 (8 pin dip)	34p	LM381	£2.26	SL440	£2.84
710 (TO-99)	39p	LM382	£2.19	SN75491	£1.43
710 (14 pin dip)	38p	LM3900	73p	SN75492	£1.62
711 (TO-99)	44p			TAA263	80p
711 (14 pin dip)	38p	MC1303L	£1.85	TAA300	£1.76
723 (TO-99)	94p	MC1306P	54p	TAA310	£1.34
723 (14 pin dip)	64p	MC1310P	£2.45	TAA320	97p
741 (8 pin dip)	31p			TAA350	£2.51
741 (TO-99)	44p	MC 1312	£2.42	TAA370	£5.05
741 (14 pin dip)	42p	MC 1314	£4.05	TAA550	80p
747 (14 pin dip)	90p	MC 1315	£5.37	TAA570	£1.62
748 (8 pin dip)	41p			TAA700	£3.56
748 (TO-99)	44p	MC1330P	86p	TAD100	£1.53
748 (14 pin dip)	42p	MC1339P	£1.26	TBA231	88p
		MC1350	81p	TBA500	£2.85
AY-1-0212	£5.99	MC1351	£1.08	TBA520	£2.66
AY-5-1224	£4.59	MC1352	£1.08	TBA530	£1.94
AY-5-3507	£7.45	MC1357	£1.56	TBA540	£1.96
AY-5-3510	£6.92	MC1358	£1.65	TBA560C	£2.92
		MC1375	£1.38	TBA625A	£1.03
		MC1456CG	£1.71	TBA625B	£1.03
		MC1458CP	£2.37	TBA625C	£1.03
		MC1468G	£2.47	TBA651	£1.62
8HA0002	£3.87	MC1495	£5.54	TBA800	90p
		MC1496G	£1.46	TBA810S	£1.07
CA3046	93p	MC3302	£1.30	TBA810AS	£1.07
CA3065	£1.53	MC3401	75p	TBA820	74p
CA3075	£1.62			TCA940	£1.94
CA3081	£1.61	MFC4000B	40p	TDA1200	£2.10
CA3082	£1.62	MFC4060A	76p	TDA1405	97p
		MFC6030A	81p	TDA1412	97p
		MFC6040	£1.08	TDA1415	97p
LO05T1	£1.45			ULN 2111A	1.56
LO36T1	£1.45	MMS314	£7.76	ZN402E	1.94
LO37T1	£1.45	MMS316	£16.17	ZN414	1.29
L129	£1.39				
L130	£1.39				
L131	£1.39				

Back in stock again!

HC244R

The Stabilized Power supply
for which demand always exceeds supply
switched 3, 6, 7 & 9 volts up to 400 mA

Polarity reversal switch, Neon Mains Indicator, on/off switch, 4ft Lead
Multi-Way output plug adaptor, Metal Case, Rubber Feet

£4.89 + p & p 16p

74 SERIES TTL

1st. GRADE BRANDED PRODUCTS

7400	17p	7442	90p	7490	68p
7401	17p	7445	1.20	7491	1.10
7402	17p	7447	1.15	7492	80p
7403	17p	7447A	1.76	7493	70p
7404	17p	7448	1.47	74100	2.32
7408	25p	7470	32p	74121	50p
7409	29p	7473	33p	74122	85p
7410	17p	7474	40p	74141	1.07
7413	29p	7475	62p	74154	1.76
7420	17p	7476	42p	74192	2.11
7430	17p	7486	35p	74193	2.45
7441	90p	7489	4.65	74196	1.70

F.M. STEREO TUNERS

Transistor F.M. Tuner

Chassis, 9 volt
Operation
A1005 S
£8.04



Stereo Decoder
to match A1005 M5 £6.08

New Mini F.M. Tuner
+ 12 volt supply
£6.76
Matching Stereo Decoder
£4.86

SIEMENS LCD's




LIQUID CRYSTAL DISPLAY complete with
socket and removable reflective backing.
Ref AN4132R 13mm character height. Can
be directly driven by National Semiconductors
Alam Clac1 chip MMS316.

OUR PRICE £13.99

24 HOUR DESPATCH NOW IN OPERATION

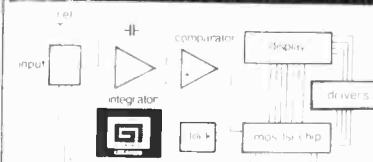3 1/2 DECADE DIGITAL VOLTMETER INTEGRATED CIRCUIT



This state-of-the-art MOS LSI chip contains
all the logic necessary for a 3.5 decade, dual
slope integrating, automatic polarity detecting
DVM. Supplied with free data and circuit
booklet. AY-5-3507

OUR PRICE ONLY £7.46

(booklets alone 20p)

PHOTO-DARLINGTON



2N5777

Vceo, Vcbo 25v, Vcbo 8v
Vceo, Vcbo 25v, Vcbo 8v
hfe 2500, Ic 250 mA


46p

MINITRON

Filament Indicators, 16 Pin DIL 10mm
Character Height
0-9 Digit Ref 3015F
-1 Overflow/Polarity Ref 3015G

NEW PRICE £1.26

Mullard

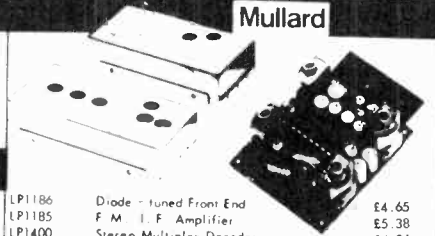

LP1186 Diode - tuned Front End £4.65
LP1185 F.M. I.F. Amplifier £5.38
LP1400 Stereo Multiplex Decoder £4.86

This trio make one of the most fabulous F.M. tuners
of all time. Typical channel separation 50 db

SPECIAL OFFERS

Left Hand Decimal Point

All Common Anode
Character Height 0.3"

4 for £5.99
5 for £7.45
6 for £8.93

RED (Led 7)
GREEN (Led 18)
YELLOW (Led 21)



VAT INCLUDED AT 8%

OVERSEAS CUSTOMERS DEDUCT 2/27
VAT INVOICES ON REQUEST
P&P On U.K. Orders min. 15p.

CALLERS WELCOME

PATRICK & KINNIE

191 LONDON ROAD · ROMFORD · ESSEX
ROMFORD 44473 RM7 9DD

E.H.T. POWERUNIT. 110/240v. 50Hz giving 5Kv. at 50 m/a. METERED OUTPUT. £18.50. P.P. £1.50.

COPPER LAMINATE P.C. BOARD
8 1/2 x 6 x 1/8 inch, 3 for 75p. P.P. 25p.
10 x 4 x 1/8 inch, 5 for 75p. P.P. 25p.
10 1/2 x 5 1/2 x 1/8 inch, 3 for 75p. P.P. 25p.
Offcut pack (smallest 4 x 2 inch), 75p. P.P. 25p.
(300 sq. inches).

PRECISION A.C. MILLIVOLTMETER (SOLARTRON). 1.5mv. to 15v., 60dB to 20dB. 9 ranges. Excellent condition. £24. P.P. £2.

TELEPHONE DIALS (new) £1. P.P. 15p.
EXTENSION TELEPHONES (Type 706). Various colours. £3.95. P.P. 75p.
RATCHET RELAYS (310 ohm). Various types. £1.20. P.P. 20p.
UNISELECTORS (New) 25 way, 12 Bank (Non bridging), 68 ohms. £6.50 P.P. 50p.
1,000 TYPE KEY SWITCHES.
Single 2 x 4 c/o Locking. 50p. P.P. 10p. Bank of 4—2 x 4 c/o each switch (one biased), £1.20. P.P. 15p.



OVERLOAD CUT-OUTS. Panel mounting (1 1/2 x 1 1/2 x 1/2 in.). 800 M/A/1.8 amp.-10 amp. 45p. P.P. 5p.

ALL PRICES INCLUSIVE OF V.A.T.

QUADROPHONIC DECODER MODULE. C.B.S./S.Q. Type, using I.C. MC 1312P. With slight modification direct substitute for P.E. "RONDO" Board. Complete with Data. £4 each.

S.T.C. CRYSTAL FILTERS (10.7 Mhz).
445-LQU-901A (50 KHz spacing). £3. P.P. 20p.
445-LQU-901B (25 KHz spacing). £4. P.P. 20p.
V.H.F./U.H.F. POWER TRANSISTORS (Type BLY38). 3 watt output at 100-500 Mhz. £2.25. P.P. 10p.

HIGH CAPACITY ELECTROLYTICS
2,200µf. at 50v. 55p. P.P. 15p. 2,200µf. at 100v. (1 1/2 x 4 in.) 90p. P.P. 30p. 3,150µf. at 40v. (1 1/2 x 4 in.) 80p. P.P. 20p.
10,000µf. at 25v. (1 1/2 x 4 1/2 in.) 80p. P.P. 20p. 2,240 µf at 40v. (3 1/2 x 1 1/2 in.) 75p. P.P. 25p.

H.D. ALARM BELLS. 6in. Dome, 6/8v. D.C. £2.75. P.P. 97p.

MULTICORE CABLE. 6-core (6 colours) 14/0076 Screened P.V.C. 22p per yard; 100 yards at £16.50. P.P. 2p. a yard. 7-core (7 colours) 7/22mm. Screened P.V.C. 22p per yard; 100 yards £16.50. P.P. 2p per yard. 30-core (15 colours) 25p per yard; 100 yards £20. P.P. 2p per yard.

RIBBON CABLE (8 colours). 10m. £1.65. P.P. 20p. 100m. 8-core 7/.mm Bonded side by side £11.50. P.P. £1.

WE REGRET THAT ALL ORDERS VALUE UNDER £5 MUST BE ACCOMPANIED BY THE REMITTANCE.

HIGH - SPEED MAGNETIC COUNTERS. 4 digit (non reset) 24v. or 48v. (state which), 4 x 1 x 1 in. 65p. P.P. 15p.
5 digit (non reset) 24v. £1.15. P.P. 15p.
3 digit 12v. (Rotary Reset) 2 1/2 x 1 1/2 x 1 1/2 in. £1.30. P.P. 15p.
6 digit (Reset) 240v. A.C. £3.50. P.P. 25p.



RELAYS. SIEMANS/VARLEY. PLUG-IN. Complete with transparent dust cover and base. 2 pole c/o. 45p; 6-make contact 50p; 4-pole c/o contact 60p each. P.P. 10p each. 6-12-24-48v. types in stock.

12v. 2 c/o 5 amp. H.D. RELAY, 65p. P.P. 15p.

240v. A.C. RELAY (PLUG-IN TYPE). 3 c/o 10 amp. contact with base. 85p. P.P. 25p.

Alter. 3.10 TURN POTENTIOMETERS (M.P.C.) 10 K ohm. 0.5% Lin. 38mm x 22mm. 14mm Standard Spindle. £2. P.P. 15p. (Dials 50p each.)

24v. A.C. RELAY (PLUG-IN). 3 pole c/o. 75p. P.P. 15p. 2-pole change over. 85p. P.P. 15p.

BULK COMPONENTS OFFER. Resistors/Capacitors, 600 new components. £2.50. P.P. 35p. Trial order 100pcs. 60p. P.P. 20p.

REGULATED POWER SUPPLY. Input 110/240v., output 9v. D.C. 1 1/2 amp., 12v. D.C. 500 m/a. £4.75. P.P. 75p.

MINIATURE "ELAPSED TIME" INDICATORS. (0-5000 hours), 45 x 8mm. 75p.

TRANSFORMERS

ADVANCE TRANSFORMERS "VOLSTAT". Input 242v. A.C.
CV.50. 38v. at 1 amp.; 25v. at 100 m/a; 75v. at 200 m/a. £2.60. P.P. 65p.
CV.75. 25v. at 2 1/2 amp. £3. P.P. 75p.
CV.100. 50v. at 2 amp.; 50v. at 100 m/a. £3.75. P.P. 75p.
C.V.250. 25v. at 8 amp.; 75v. at 1 1/2 amp. £6.50. P.P. £1.50.
C.V.500. 45v. at 3 amp.; 35v. at 2 amp. £10. P.P. £1.75.
H.T. TRANSFORMER. Prim. 110/240v. Sec. 400v. 100 m/a. £2.50. P.P. 65p.
L.T. TRANSFORMER "TOROIDAL". Prim. 240v. Sec. 30v. at 1/2 amp. Size 3 in. dia. thick. £1.65. P.P. 20p.
L.T. TRANSFORMER. Prim. 240v. Sec. 27-0-27 at 800 m/a. 7.5 amp. £2.25. P.P. 50p.

L.T. TRANSFORMER. Prim. 110/240v. Sec. 0/24/40v. 1 1/2 amp. (Shrouded) £1.95. P.P. 50p.
L.T. TRANSFORMER. Prim. 200/250v. Sec. 20/40/60v. at 2 amp. (Shrouded) £3. P.P. 50p.
L.T. TRANSFORMER (H.D.). Prim. 200/250v. Sec. 18v. at 27 amp.; 40v. at 9.8 amp.; 40v. at 3.6 amp.; 52v. at 1 amp.; 25v. at 3.7 amp. £17.50. P.P. £2.50.
L.T. TRANSFORMER. Prim. 240v. Sec. 16-0-16v. at 2 amp. £2. P.P. 50p.
L.T. TRANSFORMER. Prim. 110/240v. Sec. 23-0-23v. at 1.8 amp.; 50v. at 300 m/a.; 3.15-0-3.15v. at 300 m/a. £2. P.P. 50p.

POWER UNIT (TRANSFORMER/RECTIFIER). Prim 240v., output 177v. (unsmoothed) at 1 amp. £1.85. P.P. 45p.
L.T. TRANSFORMER ("C" CORE). Prim. 110/240v. Sec. 1/3/9/27v. at 10 amps. £7.50. P.P. £1.50.
L.T. TRANSFORMER ("C" CORE). Prim. 200/240v. Sec. 1-3-8-9v. All at 1.5 amp.; 50v. at 1 amp. £2.50. P.P. 50p.
L.T. TRANSFORMER. Prim. 110/240v. ("C" CORE). Sec. 13.5v. at 4 amp.; 39v. at 2 amp. £3. P.P. 50p.
L.T. TRANSFORMER ("C" CORE). 110/240v. 1/3/9/20. 20v. at 4 amp. £5.50. P.P. 75p.
L.T. TRANSFORMER ("C" CORE). 110/240v. Sec. 1-3-9v. All at 10 amps: 35v. at 1 amp.; 50v. at 750 m/a. £6.50. P.P. 75p.

TOUCH AND GO

SELF-CUE BROADCAST CARTRIDGE MACHINE

ACCEPTS CARTRIDGE SIZE A, B, C

30Hz-16KHz ± 1dB
S/N-70dB

RESONANCE

123 WINDMILL ROAD
BRENTFORD
MIDDX

HART ELECTRONICS

Audio Kit Specialists since 1961

BAILEY/BURROWS/QUILTER PRE AMP This is the tone control section of the best pre-amp kit currently available. Consider the advantages:—*First quality fibreglass printed circuits with roller tinned finish and all component locations printed on reverse. *Low noise carbon film and metal film resistors throughout. *Finest quality low-noise ganged controls with matched tracks and shafts cut to length. *Well engineered layout for total stability. *Special decoupling and earthing arrangements to eliminate hum loops. *Controls, switches and input sockets mount directly on the boards to TOTALLY ELIMINATE wiring to these components. (We know of one pre-amp kit which claims its controls mount directly on the board—and so they do, by their shaft bushes! You still have to wire them up!)

*We incorporate the Quilter modification which is most important as it reduces distortion and increases the bass and treble control range.

As can be seen from the photograph the tone control unit is very slim (only 1 1/2" from front to back) and may therefore be used in many other applications than our Bailey metalwork which it is designed to fit.

METALWORK AND WOODEN CASES These have been under review for some time: please send for latest information.

F.M. TUNER This latest addition to our range is designed to offer the best possible performance allied to the ease of operation given by push button varicap tuning. We have taken great care to look after the constructors' point of view and there are no coils to wind, no RF circuits to wire and no alignment is required, in fact the whole unit can be easily completed and working in an evening as there are only 3 transistors, one IC and two ready built and aligned modules comprising the active components. We have abandoned the concept of having a tuner as large as the amplifier and this new unit has a frontal size of only 1 1/2 in. x 4 in. It can be mounted on the side of our Bailey amplifier metalwork thus turning it into a tuner/amplifier whilst only increasing its width by 1 1/2 in. Cost of tuner chassis (no case) is £22 for mono. £25.45 for stereo. Metal case £35.50. An extended wooden case to fit tuner and amplifier will be offered shortly.

STUART TAPE CIRCUITS Our printed circuits and components offer the easy way to convert any suitable quality deck into a very high quality Stereo Tape unit. Input and output levels suit Bailey pre amp. Total cost varies but around £35 is all you need. We can offer tape heads as well if you want new ones.

All above kits have fibreglass PCB's. Prices exclude VAT but P&P is included.


FURTHER INFORMATION ON ALL KITS FREE if you send us a 9 in. x 4 in. S.A.E.

REPRINTS Post free, no VAT.
Bailey 30W 18p.
STUART TAPE RECORDER All 3 articles under one cover 30p.
BAILEY/BURROWS/QUILTER Preamp circuits, layouts and assembly notes 15p.
All prices exclude VAT.

Penylan Mill, Oswestry, Salop

Personal callers are always welcome, but please note we are closed all day Saturday

Pack	Price	Pack	Price
1 Fibreglass printed circuit board for front end, 1 F strip, demodulator, AFC and mute circuits	£2.15	9 Function switch, 10 turn tuning potentiometer, knobs	£5.30
2 Set of metal oxide resistors, thermistor, capacitors, cermet preset for mounting on pack 1	£4.80	10 Frequency meter, meter drive components, fibreglass printed circuit board	£8.60
3 Set of transistors, diodes, LED, integrated circuits for mounting on pack 1	£6.25	11 Toroidal transformer with electrostatic screen. Primary: 0-117V-234V	£4.45
4 Pre-aligned front end module, coil assembly, three-section ceramic filter	£8.80	12 Set of capacitors, rectifiers, voltage regulator for power supply	£2.95
5 Fibreglass printed circuit board for stereo decoder	£1.10	13 Set of miscellaneous parts, including sockets, fuse holder, fuses, inter-connecting wire, etc.	£1.50
6 Set of metal oxide resistors, capacitors, cermet preset for decoder	£2.60	14 Set of metal work parts including silk screen printed fascia panel, acrylic silk screen printed tuning indicator panel insert, internal screen, fixing parts, etc.	£6.50
7 Set of transistors LED, integrated circuit for decoder	£3.45	16 Teak cabinet	£7.35
8 Set of components for channel selector switch module including fibreglass printed circuit board, push-button switches, knobs, LEDs preset adjusters, etc.	£8.30	One each of packs 1-16 inclusive are required for complete stereo FM tuner.	£74.10
		Total cost of individually purchased packs	

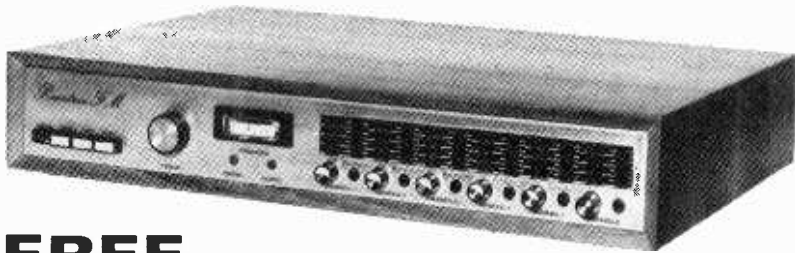

FREE TEAK CASE WITH FULL KITS
£66.75 post free (U.K.)
 KIT PRICE only

NOVEL STEREO FM TUNER

In the April and May 1974 issues of *Wireless World* there was published by J. Skingley and N. C. Thompson a novel design for an f.m. tuner which combines consistent high performance with the elimination of the critical setting-up procedure required by too many earlier tuners. The front end is a ready built pre-aligned module which then feeds an amplifier driven screened three section ceramic filter leading to an integrated circuit five-stage limiting amplifier providing excellent a.m. rejection. This is followed by a single coil integrated balanced demodulator from which the audio output may be taken. Temperature compensated varicap tuning allows stations to be selected either by a ten-turn tuning potentiometer or by a choice of six preset push-button controls. Each of the preset controls can be adjusted on the front panel with the settings being indicated by six LED lamps behind an acrylic silk screen printed fascia panel insert. Additional circuitry includes temperature compensated AFC restricted to less than station spacing, inter-station muting, a single-lamp LED tuning indicator and a linear scale frequency meter. The stereo decoder, built on a separate board, is based on a well-proven integrated circuit phase-locked-loop to which has been added active filters to remove sub-carrier harmonics and 'birdies'. The power supply, to ensure station holding stability, uses an integrated circuit voltage regulator which is powered via a low-hum field specially designed TOROIDAL TRANSFORMER.

STYLED TO COMPLEMENT THE WORLD-WIDE ACCLAIMED LINSLEY-HOOD 75W AMPLIFIER

THE FM TUNER KIT YOU HAVE WAITED FOR!
 for further information please write for **FREE LIST**

NEW!

FROM


POWERTRAN ELECTRONICS

MORE ON NEXT PAGE!

DESIGNER APPROVED KIT

In *Hi-Fi News* there was published by Mr Linsley-Hood a series of four articles (November 1972-February 1973) and a subsequent follow-up article (April 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power levels. The power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Liniac which is employed in the two most critical points of the system, namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimline unit pictured has been made practical by highly compact PCBs and a specially designed Toroidal transformer.

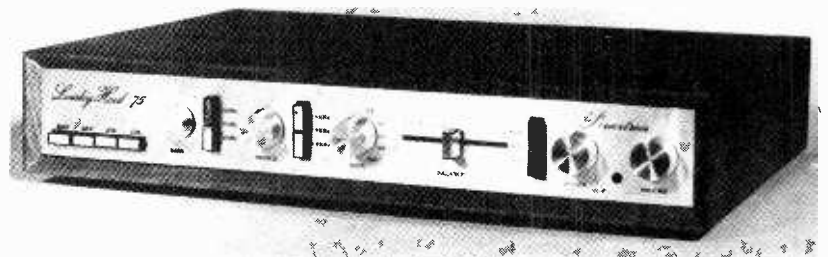Hi-Fi News Linsley-Hood 75W/Channel Amplifier Mk III Version (modifications as per *Hi-Fi News* April 1974)



Full circuit description in handbook (pack 15—price 30p)

FREE TEAK CASE WITH FULL KITS
£62.40 post free (U.K.)
 KIT PRICE only

V A T Please add 8%* to all U.K. orders

(*or at current rate if changed)
 U K ORDERS—Post free (mail order only)
 SECURICOR DELIVERY: For Securicor delivery to mainland—add £2 + VAT per kit.
 OVERSEAS—Postage at cost + 50p special packing

Dept. WW05
POWERTRAN ELECTRONICS
 PORTWAY INDUSTRIAL ESTATE
 ANDOVER, HANTS SP10 3NN

Pack	Price	Pack	Price
1 Fibreglass printed-circuit board for power amp.	£0.85	11 Fibreglass printed-circuit board for power supply	£0.65
2 Set of resistors, capacitors, pre-sets for power amp.	£1.70	12 Set of resistors, capacitors, secondary fuses, semiconductor for power supply	£3.50
3 Set of semiconductors for power amp. (now using BDY56, BD529, BD530)	£6.50	13 Set of miscellaneous parts including DIN skts, mains input skt, fuse holder, inter-connecting cable, control knobs	£4.25
4 Pair of 2 drilled, finned heat sinks	£0.80	14 Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc.	£6.30
5 Fibreglass printed-circuit board for pre-amp.	£1.30	15 Handbook	£0.30
6 Set of low noise resistors, capacitors, pre-sets for pre-amp.	£2.70	16 Teak cabinet	£7.35
7 Set of low noise, high gain semiconductors for pre-amp.	£2.40	2 each of packs 1-7 inclusive are required for complete stereo system	
8 Set of potentiometers (including mains switch)	£2.05	Total cost of individually purchased packs	£69.75
9 Set of 4 push-button switches, rotary mode switch	£3.70		
10 Toroidal transformer complete with magnetic screen/housing primary: 0-117-234 V, secondaries: 33-0-33 V, 25-0-25 V.	£9.15		

QUALITY AMPLIFIER KITS by POWERTRAN ELECTRONICS

WIRELESS WORLD AMPLIFIER DESIGNS

Component packs for a choice of three outstanding amplifiers are stocked together with packs for a regulated power supply suitable for use with a pair of any of them. Also stocked are packs for a very well-established pre-amplifier—the Bailey-Burrows design which features six inputs, a scratch and rumble filter and wide range tone controls which may be either rotary or slider operating.

30W BAILEY

- Pk. 1 F/Glass PCB £0.80
- Pk. 2 Resistors, capacitors, pots £1.75
- Pk. 3 Semiconductor set £4.70

20W LINSLEY-HOOD

- Pk. 1 F/Glass PCB £0.85
- Pk. 2 Resistors, capacitors, pots £2.40
- Pk. 3 Semiconductor set £3.35

60V REGULATED POWER SUPPLY

- Pk. 1 F/Glass PCB £0.75
- Pk. 2 Resistors, capacitors, pots £1.40
- Pk. 3 Semiconductor set £3.10

BAILEY-BURROWS PRE-AMP

- Pk. 1 F/Glass PCB £2.05
- Pk. 2 Resistors, capacitors, pre-sets, transistors £4.95

- Pk. 3R Rotary potentiometer set £1.60
- Pk. 35 Slider potentiometer set (with knobs) £2.70

STUART TAPE RECORDER

A set of three printed-circuit boards has been prepared for the stereo integrated circuit version of this high-performance *Wireless World* published design.

- TRRP Pk. 1 Reply amplifier F/Glass PCB £0.90
- TRRC Pk. 1 Record amp./meter drive cct. F/Glass PCB £1.40
- TROS Pk. 1 Bias/erase/stabilizer cct. F/Glass PCB £1.00

For details of component packs for this design please write for free list.

20 WATTS/CHANNEL



FREE TEAK CASE and HANDBOOK with full kits

KIT PRICE STILL ONLY **£28.25** post free (U.K.)

- | Pack | Price |
|------|--|
| 1 | Set of all low noise resistors £0.95 |
| 2 | Set of all small capacitors £1.50 |
| 3 | Set of 4 power supply capacitors £1.40 |
| 4 | Set of miscellaneous parts including DIN sockets, fuses, fuse holders, control knobs, etc. £1.90 |
| 5 | Set of slide and push-button switches £1.20 |
| 6 | Set of potentiometers and selector switch £2.00 |
| 7 | Set of all semiconductors £7.25 |
| 8 | Special Toroidal Transformer £4.95 |
| 9 | Fibreglass PC Panel £2.50 |
| 10 | Complete chassis work, hardware and brackets £4.20 |
| 11 | Preformed cable/leads £0.40 |
| 12 | Handbook £0.25 |
| 13 | Teak Cabinet £2.75 |

SEMICONDUCTORS AS USED IN OUR RANGE OF QUALITY AMPLIFIERS

2N699 £0.25	2N5459 £0.45	BC184L £0.11	MC1351 £1.05	SN72741P £0.40
2N1613 £0.20	2N5461 £0.50	BC212L £0.12	MFC4010 £0.95	SN72748P £0.40
2N1711 £0.25	2N5830 £0.30	BC214L £0.14	MJ481 £1.20	TIL209 £0.30
2N2926G £0.10	40361 £0.40	BCY72 £0.13	MJ491 £1.30	TIP29A £0.50
2N3055 £0.45	40362 £0.45	BD529 £0.85	MJE521 £0.60	TIP30A £0.60
2N3442 £1.20	BC107 £0.10	BD530 £0.85	MPSA05 £0.25	TIP29C £0.71
2N3704 £0.10	BC108 £0.10	BDY56 £1.60	MPSA12 £0.55	TIP30C £0.78
2N3707 £0.10	BC109 £0.10	BF257 £0.40	MPSA14 £0.35	TIP41A £0.74
2N3711 £0.09	BC109C £0.12	BF259 £0.47	MPSA55 £0.25	TIP42A £0.90
2N3904 £0.17	BC125 £0.15	BFR39 £0.25	MPSA65 £0.35	1N914 £0.07
2N3906 £0.20	BC126 £0.15	BFR79 £0.25	MPSA66 £0.40	1N916 £0.07
2N4062 £0.11	BC182 £0.10	BFY51 £0.20	MPSU05 £0.60	1S920 £0.10
2N4302 £0.60	BC212 £0.12	BFY52 £0.20	MPSU55 £0.70	5805 £1.20
2N5087 £0.42	BC182K £0.10	CA3046 £0.70	SBA750A £2.50	FILTERS
2N5210 £0.54	BC212K £0.12	LP1186 £5.50	SL301 £1.30	FM4 £0.80
2N5457 £0.45	BC182L £0.10	MC1310 £2.90	SL3045 £1.60	SFG10.7MA £2.80

ACTIVE FILTER CROSSOVER

An essential and critical component in a high-quality speaker system is the crossover unit conventionally comprising of a series of passive networks which unfortunately, though introducing reactive impedances between the amplifier and the speakers, result in the loss of the advantage of high amplifier damping factor and renders the speakers prone to overshoots and resonances. An elegant solution to this problem, described by D. C. Read in *Wireless World*, involves the use of a series of active filters splitting the output of the pre-amplifier into three channels, of closely defined bandwidth, each of which is fed to the appropriate speaker by its own power amplifier. A design for a suitable 20-watt amplifier, based on a proven Texas circuit, was also described by Mr Read. The printed-circuit board for this has been designed such that three amplifiers may be stacked and mounted together on a common heat sink to achieve a conveniently compact module.

ACTIVE FILTER

- Pack 1 Fibreglass PCB (accommodates all filters for one channel) £1.05
- 2 Set of pre-sets, solid tantalum capacitors, 2% metal oxide resistors, 2% polystyrene capacitors £4.20
- 3 Set of semiconductors £2.65
- 2 off each pack required for stereo system

SUITABLE ALSO FOR FEEDING ANY OF OUR HIGH-POWER DESIGNS

READ/TEXAS 20w amp.

- Pack 1 Fibreglass PCB £0.70
- 2 Set of resistors, capacitors pre-sets (not including O/P coupling capacitors) £1.10
- 3 Sets of semiconductors £2.40
- 6 off each pack required for stereo system
- 4 Special heat sink assembly for set of 3 amplifiers £0.85
- 5 Set of 3 O/P coupling capacitors £1.00
- 2 off packs 4, 5 required for stereo system


POWER SUPPLY

- FOR 20W/CHANNEL STEREO SYSTEM
- Pack 1 Fibreglass PCB £0.50
- 2 Set of rectifiers, zener diode, capacitors, fuses, fuse holders £2.60
- 3 Toroidal transformer £4.95

MORE KITS ON PAGE 55

for further information please write for **FREE LIST NOW!**

★ SPECIAL OFFER ★

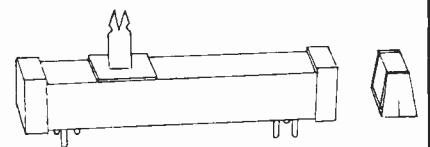

SLIDER POTENTIOMETER SALE!

Most values 1K-1M lin/log available

	Normal price	Sale Price
Single	35p	25p
Dual	55p	35p
Knob	15p	10p

V.A.T. Please add 8%* to all U.K. orders

(*or at current rate if changed)

U.K. ORDERS—Post free (mail order only)

SECURICOR DELIVERY—for this optional service (Mainland only) add £2.00 + VAT per kit
OVERSEAS—Postage at cost + 50p special packing, handling

Dept. WW05

POWERTRAN ELECTRONICS

PORTWAY INDUSTRIAL ESTATE ANDOVER, HANTS SP10 3NN

BI-PRE-PAK

Bargains in Semi-Conductors, components, modules & equipment.

Today's big value in transistors!
offers **ALL AT 50p EACH**
★ **Tested and Guaranteed**

B79	4	IN4007 Sil. Rec. diodes. 1.000 PIV 1 amp plastic
B81	10	Reed Switches. 1" long. 1/8" dia. High Speed P.O. type
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked.
H38	30	Short lead Transistors, NPN Silicon Planar types
H39	6	Integrated Circuits. 4 Gates BMC 962, 2 Flip Flops BMC 945
H41	2	Sil Power transistors comp pair BD131/132
H63	4	2N3055 type NPN Sil. power transistors. Below spec. devices
H64	4	3819 N Channel FETs 2N3819 in plastic case



★ **Unmarked untested**
PACKS ALL AT 50p EACH

B1	50	Germanium Transistors PNP, AF and RF
B66	150	Germanium Diodes Min. glass type
B83	200	Transistors, manufacturers rejects. AF, RF, Sil. and Germs.
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202
B86	100	Sil. Diodes sub. min. IN914 and IN916 types
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can.
H67	10	3819N Channel FETs plastic case type

Bi-Pre-Pak X-Hatch Generator Mk. 2 (P. & P. add 30p)



Four-pattern selector switch
3" x 5 1/4" x 3"
Ready-built
and tested

In kit form

£9.93

£7.93

Is invaluable to industrial and home user alike. Improved circuitry assures reliability and still better accuracy. Very compact; self-contained. Robustly built. Widely used by TV rental and other engineers. With reinforced fibreglass case, instructions, but less batteries. (Three U2 type required.)

SUNDRY (P. & P. add 35p)
MAINS TRANSFORMERS

A. 18V 1 amp (suitable for SS. 103)	£1.50
B. 25V 2 amp (suitable for SS. 110)	£2.00
C. 30V 2 amp (suitable for SS. 140)	£3.25

BRIDGE RECTIFIERS	
Type A 45V/1A 27p. B & C 100V/2A	38p

MAINS RELAYS	
230/240V AC. 3-pole change-over. Heavy duty contacts	60p
Ex-GPO Telephone Handsets, each	55p

BI-PRE-PAK LTD

Co Reg No B20919

222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 9DF.
TELEPHONE: SOUTHEND (0702) 46344.



Made and sold direct by Bi-Pre-Pak

Stirling Sound

Today's most challenging values!

AMPLIFIER MODULES

SS100	Active tone control unit to provide Bass and Treble facilities (stereo).	£1.60
SS101	Pre-amp for stereo ceramic cartridges, radio and tape.	£1.60
SS102	Pre-amp for low-output stereo magnetic cartridges, radio and tape.	£2.25
SS103	Compact I.C. amp. 3 watts R.M.S. Single channel (mono). On P.C.B. size 3" x 2". Needs 6-22V supply.	£1.75
SS103-3	Stereo version of above. (Two I.Cs.)	£3.25
SS105	A compact all-purpose power amp. Can be run from 12V car battery. Size 2 1/2" x 1 3/4". Useful 5w output (mono). Excellent value.	£1.95
SS110	Similar in size to SS105 but will give 10w output (mono). Two in stereo give first-class results, suitable for many domestic applications.	£2.40
SS140	Beautifully designed. Will give up to 40w R.M.S. into 4Ω. Excellent S.N.R. and transient response. Fine for P.A., disco use, etc. Operates from 45V DC. Two in bridge formation will give 80w R.M.S. into 8Ω.	£3.60


FM Tuners

SS201	Front End Assembly. Ganged tuning with well engineered slow-motion geared drive in robust housing. A.F.C. facility. Requires 6-16V. Excellent sensitivity. 88-108MHz.	£6.25
SS202	I.F. Stage (with I.C.). Designed to use with SS201 uses I.C. Carefully checked before despatch.	£5.25
SS203	Stereo Decoder. Designed essentially for use with SS201 and SS202, this excellent decoder can also make a stereo tuner of almost any single channel FM tuner. Supplied ready aligned. A L.E.M. can easily be fitted.	£5.62
SS300	POWER SUPPLY STABILISER. Add this to your unbalanced supply to obtain a steady working voltage from 16 to 60V for your audio system. Money saving and very reliable.	£5.62

- **ALL MODULES TESTED & GUARANTEED**
- **FULLY DETAILED & WELL PRINTED INSTRUCTIONS**
- **Postage—Add 20p for packing & postage (UK) + 8% VAT to total value.**

Plastic Power Transistors

40 WATT SILICON				90 WATT SILICON			
Type No.	Gain	VCE	Polarity Price	Type No.	Gain	VCE	Polarity Price
40N1	15	15	NPN 20p	90N1	15	15	NPN 25p
40N2	40	40	NPN 30p	90N2	40	40	NPN 35p
40P1	15	15	PNP 20p	90P1	15	15	PNP 25p
40P2	40	40	PNP 30p	90P2	40	40	PNP 35p

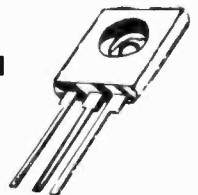

There's more in our latest catalogue: *More bargains—better price-values. Send large S.A.E. (6p stamp please) for your free copy. COMPONENTS, EQUIPMENT, AND OF COURSE SEMI-CONDUCTORS.*

TERMS OF BUSINESS VAT Add 8% to total value of order including postage and packing charges. No VAT on overseas orders. **POST & PACKING** Add 20p for UK orders. Minimum mail order acceptable—50p. Overseas orders, add £1. Any difference will be credited or charged **PRICES** Subject to alteration without notice. **AVAILABILITY** All items available at time of going to press when every effort is made to ensure correctness of information.

**To BI-PRE-PAK, 222-224 WEST RD,
WESTCLIFF-ON-SEA, ESSEX**

Please send
for which I enclose inc. VAT
NAME
ADDRESS


www5

RTVC

EMI SPEAKERS AT FANTASTIC REDUCTIONS

LE-4 SPEAKERS

Superb performance and beautifully finished in selected teak veneers. A professional standard four-way speaker system giving 25 watts RMS power handling. Bass unit is 14" x 9" with 8" x 5" unit for mid-range and twin 3" high frequency units to give monitor type quality and performance. **Specification** - Size 33" x 14" x 16" approx. Impedance 8 ohms. Power handling 25W RMS. (Peak 50 watts.) Frequency range 35 Hz-20 KHz. **Our Price £29.00** (normally £56.97) +£5 p & p.

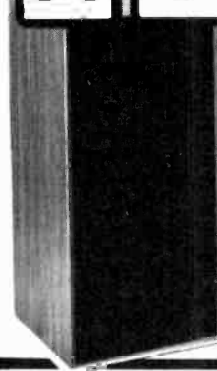

EMI 350 KIT

System consists of a 13" x 8" approx. woofer with a 3" tweeter, crossover components and circuit diagram. Frequency response: 20 Hz to 20 KHz. Power handling 15 watts RMS into 8 ohms. (Peak 30 watts.) **Complete with crossover components and circuit diagram** **£5.50** +£1 p & p.



*20 WATT SPEAKER SYSTEM

System consists of a 13" x 8" (approx.) elliptical woofer unit with a 8" x 5" (approx.) mid-range unit incorporating parasitic tweeter and crossover components. **Technical Specification:** Bass Unit: Flux density - 100 K, speech coil - 1 1/2". Cone Triple laminated paper with P.V.C. surround. Mid-Range Unit: Flux density - 33 K, speech coil - 1" with parasitic tweeter. Power handling: 20 watts RMS. Impedance - 8 ohms. Frequency response - 20 Hz to 18,000 Hz. **Our Price £7.50** Complete +£1.35 p & p.



EASY TO BUILD SPEAKER KITS

These superb simulated teak-finished speaker kits have been specially designed by RT-VC for the cost-conscious hi-fi enthusiast who wants top quality speakers but doesn't want to spend the earth. Built to EMI's exacting specification, these new RT-VC speaker kits (350 type kit) incorporate 13" x 8" woofer, 3 1/2" tweeter and matching crossover. Easily put together with just a few basic tools. **Specification (each speaker):** Impedance 8 ohms. Power handling 15 watts RMS (30 watts peak). Response 20-20,000 Hz. Size 20" x 11" x 9 1/2" approx. Comparable built units (EMI LE3) sold elsewhere for over £45 pair. **£18.95 pair complete** +£4.50 p & p. Complete with crossover components and circuit diagram.



*DISCO AMPLIFIER



Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts RMS into 8 ohms (suitable for 15 ohms). Inputs * 4 electrically mixed inputs. * 3 individual mixing controls. * Separate bass and treble controls common to all 4 inputs. * Mixer employing F.E.T. (Field Effect Transistors). * Solid State circuitry. * Attractive styling. **INPUT SENSITIVITIES** - Input - 1). Crystal mic. guitar or moving coil mic. 2 and 10mV. (Selector switch for desired sensitivity.) - Inputs - 2). 3). 4). Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains. 240V operation. Size approx: 12 1/2" x 6" x 3 1/2". **£17.00** +£1.15 p & p.

*PORTABLE DISCO CONSOLE



TECHNICAL SPECIFICATION: Pre-amp - Output - 200mV. Auxiliary inputs - 200mV and 750mV into 1 meg. Mic input - 6mV into 100K. 240 volt operation. Turntables capacity - 7", 10" or 12" records. Rumble, wow and flutter. Rumble Better than -35dB. Wow Better than 0.2%. Flutter Better than 0.06% (Gaumont kaize meter). Finish - Satin black mangleplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables. Two B.S.R. MP60 type single play professional series decks, fitted with crystal cartridges.

Console size - Unit Closed - 17 1/2" x 13 1/2" x 8 1/2" (approx.) Unit Open - 35 1/2" x 13 1/2" x 4 1/2" (approx.) This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier. The unit is finished in black PVC with contrasting simulated teak edging, diamond spun control knobs with matching control panel. **Yours for only £49.00** +£5.60 p & p.

*PUSH BUTTON CAR RADIO KIT - THE TOURIST TT

NO SOLDERING REQUIRED!



NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO
Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board. **TECHNICAL SPECIFICATION:** (1) Output 4 watts RMS output. For 12 volt operation on negative or positive earth. (2) Integrated circuit output stage, pre-built three stage IF Module. Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands. Size chassis 7" wide, 2" high and 4 1/2" deep approx. **£8.00** +90p p & p. Speaker including baffle and fixing strip £1.65 +37p. p & p. Car Aerial Recommended - fully retractable £1.37 + 32p. p & p. The Tourist I Kit For the experienced constructor. If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist TT. **Price £7.00** +90p p & p.



*COMPLETE STEREO SYSTEM

System 1a. £62.00 40 Watt Amplifier, Viscount III - R102 now 20 watts per channel. (40 watts peak). All systems include: Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket. **Specification:** 20 watts per channel into 8 ohms (40W peak). Total distortion @ 10W @ 1kHz 0.1% P.U.I. (for ceramic cartridges) 150mV into 3 Meg. P.U.I. (for magnetic cartridges) 4mV @ 1kHz into 47k, equalised within ±1dB R.I.A.A. Basis 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mV per channel. Tone controls and filter characteristics: Bass +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal to noise ratio (all controls at max.) - 58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 1/2" x 9" x 3 1/2". Garrard SP 25 deck with magnetic cartridge, de luxe plinth and hinged cover. Two Duo Type IIa matched speakers - Enclosure size approx. 19 1/2" x 9 1/2" x 7 1/2" in simulated teak. Drive unit 13" x 8" with 3" tweeter. 15 watts handling. 30 watts peak. Complete System with these speakers £62.00 +£5.50 p & p. **System 2. £82.00** Viscount III amplifier (As System 1a) Garrard SP 25 deck (As System 1a) Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 1/2" in teak simulate. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters. 20 watts R.M.S., 8 ohms frequency range - 20 Hz to 18,000 Hz. Complete System with these speakers £82.00 +£6.50 p & p. **PRICES: SYSTEM 1a** Viscount III R102 amplifier £27.00 +£1.60 p & p. 2 Duo Type IIa speakers £26.00 +£5.50 p & p. Garrard SP 25 with Mag. cartridge de luxe plinth and cover £21.00 +£2.80 p & p. **Total if purchased separately: total: £74.00** **Available complete for only: £62.00** +£5.50 p & p. **PRICES: SYSTEM 2** Viscount III R102 amplifier £27.00 +£1.60 p & p. 2 Duo Type III speakers £39.00 +£6.40 p & p. Garrard SP 25 with Mag. cartridge de luxe plinth and cover £21.00 +£2.80 p & p. **Total if purchased separately: total: £87.00** **Available complete for only: £82.00** +£6.50 p & p.

Scotland P & P Surcharge System 1a £1.75 System 2 £3.50

*8 TRACK HOME CARTRIDGE PLAYER

Elegant self selector push button player for use with your stereo system. Compatible with Viscount III system. Unsound module and the Stereo 21. Technical specification Mains input, 240V. Output sensitivity 125mV. Comparable unit sold elsewhere at £24.00 approx. Yours for only **£12.95** +£1.45 p & p.



Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K. Leaflets available for all items listed thus * Send stamped addressed envelope. All items subject to availability. Prices correct at 1st April 1975 and subject to change without notice. All prices include V.A.T. at 8% rate.



DO NOT SEND CARD Just write your order giving your credit card number

DECCA STEREO AMPLIFIER CHASSIS

Specification: 4+4 watts into 8 ohms. Input Sensitivity 4mV into 47k (for magnetic cartridges). AC Mains only 240V. Controls - volume, bass, treble, on/off, mono/stereo switch. Chassis size 11" x 5 1/2" x 3 1/2" approx. **£5.95** +£1 p & p.



RTVC


21A HIGH STREET, ACTON, LONDON W3 6NG
323 EDGWARE ROAD, LONDON W2
Personal Shoppers EDGWARE ROAD: 9 a.m. - 5.30 p.m. Half day Thurs.
ACTON: 9.30 a.m. - 5 p.m. Closed all day Wed.

G. F. MILWARD

ELECTRONIC COMPONENTS

Wholesale/Retail:

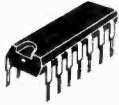369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339



CALLING ALL INDUSTRIAL BUYERS!!



We are glad to say that it is now possible to supply from stock the following integrated circuits. **ALL ARE BRANDED, FULL SPECIFICATION** devices offered at unbeatable prices! This is **YOUR** chance to cut manufacturing costs and greatly increase profit margins!

7400	1/99	100/499	500/1000	7442	1/99	100/499	500/1000	7494	1/99	100/499	500/1000
7401	£0-15	£0-125	£0-10	7443	£0-645	£0-537	£0-43	7495	£0-495	£0-412	£0-33
7402	£0-15	£0-125	£0-10	7444	£1-275	£1-062	£0-85	7496	£0-63	£0-525	£0-42
7403	£0-15	£0-125	£0-10	7445	£0-855	£0-712	£0-57	7497	£0-72	£0-60	£0-48
7404	£0-18	£0-15	£0-12	7446	£1-05	£0-875	£0-70	74104	£0-315	£0-262	£0-21
7405	£0-18	£0-15	£0-12	7446A	£1-05	£0-875	£0-70	74105	£0-315	£0-262	£0-21
7406	£0-375	£0-312	£0-25	7447	£1-05	£0-875	£0-70	74107	£0-315	£0-262	£0-21
7407	£0-375	£0-312	£0-25	7447A	£1-05	£0-875	£0-70	74121	£0-315	£0-262	£0-21
7408	£0-15	£0-125	£0-10	7448	£0-855	£0-712	£0-57	74122	£0-45	£0-375	£0-30
7409	£0-15	£0-125	£0-10	7450	£0-15	£0-125	£0-10	74123	£0-63	£0-525	£0-42
7410	£0-15	£0-125	£0-10	7451	£0-15	£0-125	£0-10	74141	£0-75	£0-625	£0-50
7412	£0-195	£0-162	£0-13	7453	£0-15	£0-125	£0-10	74151	£0-69	£0-575	£0-46
7413	£0-345	£0-287	£0-23	7454	£0-15	£0-125	£0-10	74153	£0-69	£0-575	£0-46
7416	£0-345	£0-287	£0-23	7460	£0-15	£0-125	£0-10	74155	£0-69	£0-575	£0-46
7417	£0-345	£0-287	£0-23	7472	£0-255	£0-212	£0-17	74156	£0-69	£0-575	£0-46
7420	£0-15	£0-125	£0-10	7473	£0-315	£0-262	£0-21	74160	£1-005	£0-837	£0-67
7423	£0-27	£0-225	£0-18	7474	£0-315	£0-262	£0-21	74161	£1-005	£0-837	£0-67
7425	£0-27	£0-225	£0-18	7475	£0-465	£0-387	£0-31	74162	£1-005	£0-837	£0-67
7426	£0-27	£0-225	£0-18	7476	£0-315	£0-262	£0-21	74163	£1-005	£0-837	£0-67
7427	£0-27	£0-225	£0-18	7480	£0-435	£0-362	£0-29	74166	£1-425	£1-187	£0-95
7430	£0-15	£0-125	£0-10	7482	£0-75	£0-625	£0-50	74174	£1-20	£1-00	£0-80
7432	£0-25	£0-225	£0-18	7483	£0-825	£0-687	£0-55	74175	£0-975	£0-812	£0-65
7437	£0-27	£0-225	£0-18	7485	£1-275	£1-062	£0-85	74192	£1-275	£1-062	£0-85
7438	£0-27	£0-225	£0-18	7486	£0-315	£0-262	£0-21	74193	£1-275	£1-062	£0-85
7440	£0-15	£0-125	£0-10	7490	£0-465	£0-387	£0-31	74198	£2-10	£1-75	£1-40
7441A	£0-825	£0-687	£0-55	7492	£0-465	£0-387	£0-31	74199	£2-10	£1-75	£1-40
				7493	£0-465	£0-387	£0-31				

To secure the above prices, all orders for these devices must exceed £10 in total value. Price rating is established by TOTAL NUMBER OF DEVICES ORDERED. Any mix may be made. For special quotations for large orders ring 021-327 2339 NOW!!!

MICROWAVE DEVICES

CL8300	Gunn effect oscillator	9-4GHz	£40
CL8370	ditto	9-5GHz	£10
CL8380	ditto	10-5GHz	£10
CL8390	ditto	11-5GHz	£10
CL8430	ditto	9-35GHz	£40
CL8450	ditto	9-35GHz	£40
CL8470	ditto	9-35GHz	£40
BXY27	Varacter Diode. "S" Band. Cut-off	70GHz	£1
BXY28	Varacter Diode. Cut-off	100GHz	£1
BXY32	Frequency Multiplier. "X" Band	150GHz	£1
BXY35A/C	ditto	25GHz	£1
BXY36C/D	ditto	75GHz	£1
BXY37C/D	ditto	100GHz	£1
BXY38C/E	ditto	120GHz	£1
BXY39C/D	ditto	150GHz	£1
BXY40D/E	ditto	180GHz	£1
BXY41C/D/E	ditto	200GHz	£1

12 VOLT FLUORESCENT LIGHTING



Inverter transformers 13/15W (circuit included) **70p**
 "Current economy" transistor (600 ma.) **50p**
 "Maximum light" transistor (1-3A) **50p**
 Resistors/capacitors to suit **15p**
 Lampholders (long lead) (needed with cases) Pair **30p**
 (short lead) Pair **20p**
 White enamel case 21in (postage 30p) **70p**
 Tube. 21in-13W **45p**
 (Note: tube only supplied if case ordered, to prevent postal damage).
 13W fitting ready built and tested—including tube (postage 30p) **£3-75**
 Post/packing. 25p per order except where shown.

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.
 Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.
 Light sensitive aerosol spray **£1-00 plus postage**
 Developer and Etchant **50p plus postage**

Single-sided Copper-clad Fibreglass Board **75p sq. ft.**
 Double-sided Copper-clad Fibreglass Board **£1-00 sq. ft.**
 Boards cut to any multiple of 6". Max. size 3' x 4'.

1,000,000

POTENTIOMETERS

We have bought a huge assortment of volume controls.

Pre-sets, sliders, etc. All are in manufacturer's original packing.

Manufacturing quantities of some types available.

Write or phone for details.

Sample bag
100 mixed £2-50

ELECTROLYTIC CAPACITORS

Several thousand of each of the following types. Silly price to clear!

ALL NEW STOCK

5µf 10V	35p dozen
10µf 10V	35p dozen
50µf 10V	35p dozen
100µf 10V	35p dozen
330µf 16V	45p dozen
330µf 25V	60p dozen
330µf 35V	80p dozen
2200µf 16V	£1 dozen
15000µf 25V	50p each

HOBBY CORNER!

BRAN TUB !!!

- ★ Resistors, Wire-wound and Carbon
- ★ Capacitors, Silver-mica, Paper, Ceramic, Polyester and Electrolytic
- ★ Controls, Volume, Pre-set, Carbon, Wire
- ★ Diodes, Silicon, Germanium, Zener
- ★ Transistors, Silicon, Germanium

All the above are new and unused stock.

We have made up packs of 2lb gross weight, all are different in content, and contain a mixture of components from the above list. This is a fantastic, unrepeatable offer that will enable you to get a good stock of spares at a tiny fraction of normal price!

To make things even more interesting — TWENTY OF THESE BAGS ALSO CONTAIN A POUND NOTE! TWENTY CUSTOMERS WILL BE VERY PLEASED INDEED!

And the price that we are asking? Only **£1-50** including both postage and VAT!

Rush your order now! This offer is only made to reduce our surplus stock! It is unlikely that in these days of rising prices we shall ever be able to repeat!

£1 100 1/2 WATT RESISTORS
 100 CERAMIC CAPACITORS
 100 DIODES

POSTAGE 25p PACK No. 1

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 100 POLYSTYRENE CAPACITORS

POSTAGE 25p PACK No. 2

£1 100 RESISTORS
 100 CERAMIC CAPACITORS
 50 MULLARD POLYESTER CAPACITORS

POSTAGE 25p PACK No. 4

£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108 ETC.

POSTAGE 25p PACK No. 5

£1 1 TRANSISTORISED SIGNAL TRACER KIT
 1 TRANSISTORISED SIGNAL INJECTOR KIT

POSTAGE 25p PACK No. 6

£1 100 RESISTORS
 100 CAPACITORS (ASSORTED TYPES)

POSTAGE 25p PACK No. 8

REMEMBER!

ALL GOODS PLUS 8% V.A.T.

G. F. MILWARD, 369 Alum Rock Rd., Birmingham B8 3DR. Postage (minimum) per order 25p.

Marshall's

A. Marshall & Son (London) Limited Dept. W W
42 Cricklewood Broadway London NW2 3HD Tel: 01-452 0161
& 85 West Regent Street Glasgow G2 2QD Tel: 041-332 4133

Everything you need is in our new 1975 catalogue. Available now price 25p

Trade and export enquiries welcome

OUR RANGE COVERS OVER 7,000 ITEMS THE LARGEST SELECTION IN BRITAIN

TOP 200 IC'S TTL, CMOS & LINEARS

CA3018A	0.85	CD4043	1.80	NE565	4.48	SN7448	0.90	SN74157	0.95
CA3020A	1.80	CD4044	1.80	SL414	1.80	SN7450	0.16	SN74160	1.10
CA3028A	0.79	CD4045	2.65	SL610C	1.70	SN7451	0.16	SN74161	1.10
CA3035	1.37	CD4046	2.84	SL611C	1.70	SN7453	0.16	SN74162	1.10
CA3046	0.70	CD4047	1.65	SL012C	1.70	SN7454	0.16	SN74163	1.10
CA3048	2.11	CD4049	0.81	SL60C	2.60	SN7460	0.16	SN74164	2.01
CA3052	1.62	CD4050	0.66	SL621C	2.60	SN7470	0.33	SN74167	4.10
CA3088E	1.96	LM301A	0.48	SL623C	4.59	SN7472	0.26	SN74174	1.25
CA3090U	4.23	LM308	2.50	SL640C	3.10	SN7473	0.36	SN74174	1.25
CD4000	0.36	LM05TL	1.50	SN7400	0.16	SN7474	0.36	SN74175	0.90
CD4001	0.36	LM380	1.10	SN7401	0.16	SN7475	0.50	SN74176	1.44
CD4002	0.36	LM381	2.20	SN7401AN	0.38	SN7476	0.35	SN74180	1.40
CD4006	1.58	LM702C	0.75	SN7402	0.16	SN7480	0.50	SN74181	1.95
CD4007	0.36	LM709	0.38	SN7403	0.16	SN7481	1.25	SN74190	2.30
CD4008	1.63	8DIL	0.45	SN7404	0.19	SN7482	0.75	SN74191	2.30
CD4009	1.18	14DIL	0.40	SN7405	0.19	SN7483	0.95	SN74192	1.15
CD4010	1.18	LM710	0.47	SN7406	0.45	SN7484	0.95	SN74193	1.15
CD4011	0.36	LM723C	0.90	SN7407	0.45	SN7485	1.25	SN74196	1.60
CD4012	0.36	LM741C	0.40	SN7408	0.19	SN7486	0.32	SN74197	1.58
CD4013	0.66	8DIL	0.40	SN7409	0.22	SN7490	0.45	SN74198	2.25
CD4014	1.72	14DIL	0.38	SN7410	0.16	SN7491	0.85	SN74199	2.25
CD4015	1.72	LM747	1.05	SN7411	0.25	SN7492	0.45	SN76003N	2.92
CD4016	0.66	LM748	0.60	SN7412	0.28	SN7493	0.45	SN76013N	1.95
CD4017	1.72	LM14DIL	0.73	SN7413	0.35	SN7494	0.82	SN76023N	1.62
CD4018	2.55	LM3900	0.70	SN7416	0.35	SN7495	0.72	SN76033N	2.90
CD4019	0.86	LM7805	2.00	SN7417	0.35	SN7496	0.75	TAA263	1.10
CD4020	1.91	LM7812	2.50	SN7420	0.16	SN74100	1.25	TAA300	1.80
CD4021	1.72	LM7815	2.50	SN7423	0.29	SN74107	0.36	TAA350A	2.10
CD4022	1.66	LM7824	2.50	SN7425	0.29	SN74118	1.00	TAA550	0.60
CD4023	0.36	MC1303L	1.50	SN7427	0.29	SN74119	1.92	TAA611C	2.18
CD4024	1.24	MC1310P	2.59	SN7430	0.16	SN74121	0.27	TAA621	2.03
CD4025	0.32	MC1330P	0.90	SN7432	0.28	SN74122	0.50	TAA661B	1.32
CD4027	0.43	MC1351P	0.80	SN7437	0.35	SN74123	0.60	TBA641B	1.32
CD4028	1.50	MC1352P	0.80	SN7438	0.35	SN74141	0.85	TBA651	1.69
CD4029	3.50	MC1466L	3.50	SN7440	0.16	SN74145	0.90	TBA800	1.40
CD4030	0.87	MC1469R	2.75	SN7441AN	0.85	SN74150	1.50	TBA810	1.40
CD4031	5.19	NE555V	0.70	SN7442	0.65	SN74151	0.85	TBA820	1.15
CD4037	1.93	NE556	1.30	SN7445	0.90	SN74153	0.85	TBA920	4.00
CD4041	1.86	NE560	4.48	SN7446	0.95	SN74154	1.50	DIL sockets	0.17
CD4042	1.38	NE561	4.48	SN7447	0.95	SN74155	1.50		

PW TELETENNIS KIT—£42.50 + VAT Reprint 75p
TRY OUR GLASGOW SHOP

POPULAR SEMICONDUCTORS


2N696	0.22	2N3906	0.27	AF139	0.65	BD139	0.71	MPSA56	0.31
2N697	0.16	2N4037	0.42	AF239	0.65	BD140	0.87	OC25	0.765
2N698	0.82	2N4036	0.67	AF240	0.90	BF115	0.36	OC35	0.60
2N699	0.59	2N4058	0.18	AF279	0.70	BF117	0.55	OC42	0.50
2N706	0.14	2N4062	0.15	AF280	0.79	BF154	0.20	OC45	0.32
2N708	0.17	2N4289	0.34	AL102	1.00	BF159	0.27	TP29A	0.49
2N916	0.28	2N4920	1.10	BC107	0.14	BF180	0.35	TP29C	0.58
2N918	0.32	2N4921	0.83	BC108	0.14	BF181	0.36	TP31A	0.62
2N1302	0.185	2N4923	1.00	BC109	0.14	BF184	0.30	TP32A	0.74
2N1304	0.26	2N5245	0.47	BC147B	0.14	BF194	0.12	TP33A	1.01
2N1306	0.31	2N5246	0.48	BC148B	0.15	BF196	0.12	TP34A	1.51
2N1308	0.47	2N5296	0.48	BC149B	0.15	BF196	0.13	TP35A	2.00
2N1711	0.45	2N5457	0.49	BC157A	0.16	BF197	0.15	TP36A	3.70
2N2102	0.60	2N5458	0.46	BC158A	0.16	BF198	0.18	TP42A	3.90
2N2147	0.78	2N5459	0.49	BC167B	0.15	BF244	0.21	TP2955	0.98
2N2148	0.94	2N6027	0.45	BC168B	0.15	BF257	0.47	TP3055	0.50
2N2218A	0.22	3N128	0.73	BC169B	0.15	BF258	0.53	TS43	0.28
2N2219A	0.26	3N140	1.00	BC182	0.12	BF259	0.55	ZTX300	0.13
2N2220	0.25	3N414	0.81	BC182L	0.12	BF561	0.27	ZTX301	0.13
2N2221	0.18	3N200	2.49	BC183	0.12	BF598	0.25	ZTX500	0.15
2N2222	0.20	40361	0.40	BC183L	0.12	BFR39	0.24	ZTX501	0.13
2N2369	0.20	40362	0.45	BC184	0.13	BFR79	0.24	ZTX502	0.18
2N2646	0.55	40406	0.44	BC184L	0.13	BFX29	0.30	1N914	0.97
2N2904	0.22	40407	0.35	BC212A	0.16	BFX30	0.27	1N375A	0.15
2N2905	0.25	40408	0.50	BC212LA	0.16	BFX84	0.24	1N4007	0.10
2N2906	0.19	40409	0.52	BC213LA	0.15	BFX85	0.30	1N4148	0.07
2N2907	0.22	40410	0.52	BC214LB	0.18	BFX88	0.25	1N5404	0.22
2N2924	0.20	40411	2.00	BC237B	0.16	BFY50	0.225	1N5408	0.30
2N2926G	0.12	40594	0.74	BC238C	0.15	BFY51	0.23	AA119	0.08
2N3053	0.25	40595	0.84	BC239C	0.15	BFY52	0.205	BA102	0.25
2N3054	0.60	40636	1.10	BC257A	0.16	BRY39	0.48	BA145	0.18
2N3055	0.75	40673	0.73	BC258B	0.16	ME0402	0.20	BA154	0.12
2N3391	0.28	AC126	0.20	BC259B	0.17	ME0412	0.18	BA155	0.12
2N3392	0.15	AC127	0.20	BC301	0.34	ME1102	0.11	BB103B	0.23
2N3393	0.15	AC128	0.20	BC307B	0.17	MJ480	0.95	BB104B	0.45
2N3440	0.59	AC151	0.27	BC308A	0.15	MJ481	1.20	BY126	0.12
2N3442	1.40	AC152	0.49	BC309C	0.20	MJ490	1.05	BY127	0.15
2N3638	0.15	AC153	0.35	BC327	0.23	MJ491	1.45	BY211	0.51
2N3702	0.12	AC176	0.30	BC328	0.22	MJ2955	1.00	8Y212	0.51
2N3703	0.13	AC187K	0.35	BCY70	0.17	MJE340	0.48	OA47	0.06
2N3704	0.15	AC188K	0.40	BCY71	0.22	MJE370	0.65	OA81	0.18
2N3706	0.15	AD143	0.68	BCY72	0.15	MJE371	0.75	OA90	0.06
2N3708	0.14	AD161	0.50	BD121	1.00	MJE520	0.60	OA91	0.06
2N3714	1.38	AD162	0.50	BD122	0.82	MJE512	0.70	W021A200	0.32
2N3716	1.80	AF106	0.40	BD124	0.67	MJE595	1.20	BY126	0.57
2N3771	2.20	AF109	0.40	BD131	0.40	MJE3055	0.75	ST2 diac	0.20
2N3773	2.65	AF115	0.35	BD132	0.50	MP8113	0.47	40669	1.00
2N3789	2.06	AF116	0.35	BD135	0.43	MPF102	0.39	TC144	0.29
2N3819	0.37	AF117	0.35	BD136	0.47	MPSA05	0.25	C106D	0.65
2N3820	0.64	AF118	0.35	BD137	0.55	MPSA06	0.31	ORP12	0.60
2N3904	0.27	AF124	0.30	BD138	0.63	MPSA55	0.31		

Prices correct at March 1975, but all exclusive of V.A.T. Post & Package 25p

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Price £	P & P p
07	20	1 8	7.0x 7.0x 6.0	2.80	38
149	60	3 12	9.9x 7.7x 8.6	4.37	45
150	100	5 8	9.9x 8.9x 8.6	4.89	45
151	200	8 0	12.1x 9.3x 10.2	8.13	53
152	250	13 12	12.1x 11.8x 10.2	9.83	73
153	350	15 0	14.0x 10.8x 11.8	11.88	73
154	500	19 8	14.0x 13.4x 11.8	13.65	91
155	750	29 0	17.2x 14.0x 14.0	20.51	•
156	1000	38 0	17.2x 16.6x 14.0	29.15	•
157	1500	46 0	21.6x 13.4x 18.1	33.23	•
158	2000	60 0	21.6x 13.4x 18.1	37.57	•
159	3000	85 0	23.5x 17.8x 19.7	58.55	•

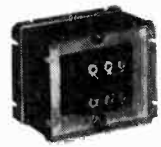

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	Price £	P & P p
113	20	1 0	5.8x 5.1x 4.5	0-115-210-240	1.67	30
64	75	2 4	7.0x 6.7x 6.1	0-115-210-240	2.90	38
4	150	3 4	8.9x 7.7x 7.7	0-115-210-240	4.12	45
87	500	12 8	12.1x 11.2x 10.2	"	5.82	53
84	1000	19 8	14.0x 13.4x 14.3	"	8.82	67
93	1500	30 4	14.0x 15.9x 14.3	"	13.68	91
95	2000	32 0	17.2x 16.6x 14.0	"	18.31	•
73	3000	40 0	21.6x 13.4x 18.1	"	24.20	•
					35.09	•

CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2 pin outlets. 20VA £3.13. P. & P. 38p. 500VA £10.45. P. & P. 80p. 1000VA £17.51. Via B.R.S.

LOW VOLTAGE TRANSFORMERS

Ref. No.	Amperes	Weight lb oz	Size cm.	Secondary Windings	Price £	P & P p
213	0.5	0.25	4.8x 2.9x 3.5	0-12V at 0.25A x 2	1.47	23
71	2	1 12	6.1x 5.8x 4.8	0-12V at 0.5A x 2	1.74	



TRAMPUS

Electronics Ltd.
WINDSOR BERKS.
58/60 GROVE RD.
SEND C.M.O. ADD VAT TO ALL PRICES IN U.K. P&P 15p. EXPORTS 60p.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS, LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC. DEVICES. CALLERS WELCOME.
CATALOGUE/LIST FREE SEND SAE.
BARCLAYCARD & ACCESS. POST.

Digital Displays

SLA7 RED LED 0.3" DIGIT 0-9DP 89p ea
GREEN&YELLOW £1.40
JUMBO LED 0.6" 747 DISPLAY £2.25 ea.
3015F 0-9DP £1 ea.
ZENON FLASH TUBE £4. Data 15p.

LEDS red 13P

LEDS 209 STYLE ONLY 13p ea
TIL 209 WITH CLIP RED 15p ea
TIL 211 & CLIP GREEN 29p ea
LARGE 0.2" & CLIP RED 17p ea
LARGE 0.2" CLIP GREEN 30p ea
209 STYLE OR .2"ORANGE 29p ea
INFRA RED LED £1.2N5777 33p.

PHOTO IC 81P

TEC12 PHOTO AMP/SCMITT/RELAY DRIVER or LED TTL INTERFACE 81p



FLUORESCENT LIGHTS 12V MADE IN UK
8 WATT 13" £3. 13W 22" £3.50

DIGITAL CLOCK

IC AY51224 4 DIGIT CLOCK £3.75
MM5311/4 6 DIGIT CLOCK £7

CASSETTE MECHANICS £13.75

NEW 8tk CARTRIDGE MECHANISM £8
STEREO CASSETTE MECHANISM £13.75
Suitable for 'PW ASCOT' recorder with heads etc. SEND 15p for DATA

INTEGRATED CIRCUITS

709 DIL14 29p	LM377 2x2Wf2.87
555 TIMER 54p	LM380 2W AF 49p
703 RF/IF 26p	LM381 2xPre £2
709 T099 23p	LM3900 4xOPA69p
709 DIL 14 26p	MC1303 £1.20
710 DIL 14 34p	MC1306 40p
723 Reg 54p	MC1310&LEDf2.65
741 DIL 8 27p	MC1312 SQ £2.10
741 DIL 14 28p	MC1330 40p
741 T099 28p	MC1339 2xPre £1
747 2x741 70p	MC1350 55p
748 DIL 8 33p	NE536 fetOPA £2
7805 5V £1.40	NR540 Driver £1
7812 & 15 £1.40	NR550 2vRef 79p
76013 6W AF £1	NR555 Timer 55p
8038 SIG GEN £3	NE556 2x" £1.20
CA3078 £1	NE560 PLL £3.15
CA3046 35p	NE561 PLL £3.15
CA3048 £2	NE562 PLL £3.19
CA3052 £1.50	NE565 PLL £2.69
CA3054 £1	SN72709 709 28p
LM390 2-20V £2	SN72741 741 26p
LM301 OPA 45p	SN72748 748 33p
LM304 0-40V £3	SN76660 IF £1
LM307 OPA 49p	SN76611 IF £1.25
LM308 H180 95p	TAD110 & IF £2
LM309K 5V £1.48	TBA810 7WAF 99p
LM372 IF £1.80	ZN414 RX £1.09

SPECIAL OFFERS

2N3055 FULL HIGH SPEC C115W 37p
741C 8PIN DIL 27p. MFC4000B 33p
NE555 TIMER 55p. ZN414 RX £1.09
BC109 9p. 2N3819e 16p. BFY51 15p

7400 TTL

7400 GATES 13p	7473/74/76 29p
7404 INVERT 17p	7475 45p
7401/2/10etc14p	7490 32p
7413 SCMITT 31p	7491/2/3/4 39p
7440 BUFFER 14p	74100 74175 £1
7447 DRIVER 89p	74121 32p
7470 & 7472 29p	74123 59p
	74141(&7441)73p

TRANSISTORS & DIODES

Price each	MATCHING	10p
AC127 & 128 16p	INS, BUSH SET	10p
AC187 & 188 18p	TIP 41	70p
AD149 43p	TIP 42	88p
AD161 & 162 33p	TIP 2955	90p
BC107 & 108 90p	TIP 3055	55p
HM109 10p	TIS43 see 2N2646	
BC147/8/9 10p	ZTX109&301 13p	
BC157/8/9 12p	1N4001	4p
BC167/8/9 12p	1N4004 & 7 7p	
BC177/8/9 18p	1N4148 & 914 4p	
BC182/3/4&4L10p	2N697	14p
BC212/3/4&4L11p	2N706&8	11p
BCY70/1/2 17p	2N2646 UJT	32p
BD131 & 132 39p	2N2904 & 5 20p	
BFY51 23p	2N2926royg	9p
BFR50/51 23p	2N3053	17p
BPR88 250V 29p	2N3055 115W	17p
BFY50/1/2 15p	2N3563 & 64 16p	
BSX19/20/21 16p	2N3614	49p
MJE2955 90p	2N3702 & 3 8p	
MJE3055 65p	2N3704 & 5 10p	
MPI131 PUT 49p	2N3706 & 7 9p	
OA91 OA81 6p	2N3708 & 9 8p	
OA81 & OA91 6p	2N3710 & 11 10p	
TIP 29 & 30 52p	2N3819E FET 16p	
TIP 31 & 32 69p	2N3823E FET 17p	
	2N3904/5/6 15p	

FULL SELECTION IN OUR FREE LISTS.

NEW TRAMPUS FULL SPEC PAKS

PAK A 10 RED LEDS our choice	£1
PAK R 4 741 OP AMP	£1
PAK C 4 2N3055 £1.D 12 BC109	£1
PAK E 10 BC182 £1.F 11 2N3704	£1
PAK G 8 BFY51 £1.H 9 2N3819e	£1
PAK J 9 2N3053 £1.K 40 1N914	£1

BZY88 400mw	1A/50V SCR	36p
ZENER DIODES 9p	TAG1/400	53p
BRIDGE RECT	C106 & 7 SCR	01
1A 50V	4A/400V	53p
BR100 DIAC	SC146D TRIAC	75p
	10A 400V	75p

VERO

VERO PINSx36 28p
COPPER CLAD VEROBOARD 0.1
2 1/2"x5" 29p 2 1/2"x3 1/2" 26p. 3 1/2"x3 1/2" 31p.
3 1/2"x5" 31p 3 1/2"x 17" £1.50
DIL IC's BOARDS 6x4 1/2" £1.50
24 way edge connector 60p.
36 way 90p. PLAIN 3 1/2"x17" £1.
FACE CUTTER 45p. FEC ETCH PAK 50p

DAOpen69p

PRINTED CIRCUIT BOARD KIT £1.69
DECON NO MESS ETCH PAK NEW 69p
DECON DESOLDER BRAID REEL 59p

HEATSINKS

5F/T05 & 18F/T018 5p ea. TV4 15p
TV3/T03 16p. EXTRUDED 4" 4Y1 29p

CAPACITORS

CERAMIC 22pf to 0.1uf 50v 5p.
ELECTROLYTIC: 10/50/100 uf in
10v 5p, 25v 6p, 50v 8p, 2uf/10v 5p.
1000 uf/25v 18p, 200/500 25v 9p.

POTENTIOMETERS (POTS) AB or EGIN

LIN or LOG ROTARY 13p. SWITCH 14p
DUAL 45p. SLIDERS 29p. STEREO 57p
KNOBS 7p. PRESETS 6p. RESISTORS 14p
SWITCHES: SPST 18p. DPDT 25p.

DIN PLUGS ALL 12p. SOCKETS 10p.
ALL CASES AB5/AB7 50p. AB13 65p.
TRANSFORMERS 1A 6v/6v or 12v/12v
Only £1.34. 100mA type CT 75p.

OIL sockets

TEXAS GOLD
LOW PROFILE ea
8, 14, & 16 PIN 13p
SOLDERCON STRIPS
100 PINS 50p. 1K £3.

WW-213 FOR FURTHER DETAILS

REDIFON TELEPRINTER RELAY UNIT NO. 12: ZA-41196 and power supply 200-250V a.c. Polarised relay type 3SE1TR. 80-0-80V 25mA. Two stabilised valves CV 286. Centre Zero Meter 10-0-10. Size 8in. x 8in. x 8in. New condition. £8.50. Carr. 75p.

SOLARTRON PULSE GENERATOR TYPE G1101-2: £75.00 each. Carr. £2.00.

TELEPRINTER TYPE 7B; Pageprinter 24V d.c. power supply, speed 50 bauds per min. second hand cond. (excellent order) no parts broken. £15 each. Carriage £3.

INSULATION TEST SET: 0-10 kV negative, earth with amplifier provision for checking ionisation. 110/230V a.c. input. S/hand good cond. £30 + £1 carr.

BRIDGE MEGGER: 250V. (Evershed Vignoles) series 2. £30 each. Carr. £1.

BRIDGE MEGGER: 2,500V., series 1. £30 each. Carr. £1.

CRYSTAL TEST SET TYPE 193: used for checking crystals in freq. range 3000-10,000KHz. Mains 230V 50Hz. Measures crystal current under oscillatory conditions and the equivalent resistance. Crystal freq. can be tested in conjunction with a freq. meter. £17.50. Carr. £1.50.

TYPE 174/1 FREQUENCY SHIFT ADAPTOR (Northern Radio Co.): Convert mark and space frequencies from the output of one or two Receivers into d.c. pulses. Suitable to operate Teleprinters or similar devices. 110/220V. Further details on request, s.a.c. £55 each. Carr. £1.50.

TELEGRAPH TERMINAL UNIT (A.T.E.) TYPE TFSS3: Converts signals from Receivers into d.c. pulses. Complete with monitor. £75 each. Carr. £2.

FURZHILL SENSITIVE VALVE VOLTMETER V.200: Freq. 10Hz-6MHz (can be used beyond 6MHz). Probe in circuit—voltage range 1mV-1kV in 6 decade ranges; full scale deflection 10mV, 100mV-1kV. Without probe 100µV-100V in 6 decade ranges; full scale deflection 1mV, 10mV-100V. Accuracy ±5%. £30 each. Carr. £1.

NOISE FIGURE METER TYPE 113A (Magnetic AB, Sweden): £125 each. Carr. £1.

PRECISION PHASE DETECTOR TYPE 205: Freq. 0.1-15MHz in 5 ranges. Variable time delay microsecond 0-0.1c, 115V input. £55 each. Carr. £1.

ROHDE & SCHWARZ HF MILLIVOLTMETER: 30Hz-30MHz Type UVH, 1mV-1V in 7 ranges, 220V. £75 each. Carr. £2.

ROHDE & SCHWARZ VHF WATTMETER TYPE NAK: with matching indicator, 30 watts, 300-470MHz. £25 each. Post 70p.

CT-38 ELECTRONIC MULTIMETER: A.C./D.C. volts 1-10,000 A.C./D.C. current 1µA-25 amps. £30 each. Carr. £1.00

PHILLIPS VALVE VOLTMETER TYPE GM6014: 1-300mV in 6 ranges, 70-20dB, probe 1000Hz-30MHz, 300mV maximum. £35 each. Carr. £1.

TF-1345/2 DIGITAL FREQUENCY COUNTER: Range 10KHz-100MHz with extension units. Details on request, s.a.c. £100. Carr. £2.

UHF MICROWAVE MILLIWATTMETER TYPE 14: Direct reading, can be used to measure power from 100MHz upwards. F.S.D. on 4in. scale meter 2.5mW. £40 each. Carr. £1.

MARCONI HF SPECTRUM ANALYSER OA. 1084/3. Further details on request. £250 each. Carr. £5.

Q METER: 30MHz-200MHz. £55. Carr. £1.

SIGNAL GENERATOR AIRMEC TYPE 701: 30KHz-30MHz, 7 ranges. £85. Carr. £1.50.

TF-1278/1 TRAVELLING TUBE WAVE AMPLIFIER: £125. Carr. £2.

BPL A.C. MILLIVOLTMETER TYPE VM.348-D Mk. 3: 2 millivolts-2 volts, 6 ranges. £30. Carr. £1.

WAYNE KERR WAVEFORM ANALYSER A.321: Low scale 0-1200 c/s. High scale 1-20 Kc/s, 600 ohms. Harmonic level is 0-55 dB in 12 steps. £75. Carr. £1.50.

SPECTRUM ANALYSER TYPE MW.68S (Decca): Further details on request. £200.

MARCONI DUAL TRACE UNIT TM-6456: £30. Post 60p.

SIGNAL GENERATOR TS-403B/U (or URM-61A): (Hewlett Packard). A portable, self-contained, general-purpose test equipment designed for use with radio and radar receivers and for other applications requiring small amounts of RF power such as measuring standing-wave ratios, antenna and transmission line characteristics, conversion gain, etc. Both the output freq. and power are indicated on direct-reading dials. 115V, AC, 50 c/s. Freq.—1800-4000 Mc/s. CW, FM, Modulated Pulse—40-4000 pulses per sec. Pulse Width—0.5-10 microseconds. Timing—Undelayed or delayed from 3-300 microseconds from external or internal pulse. Output—1 milliwatt max., 0 to -127 dB variable. Output Impedance—50 ohms. Price: £120 each + £2 carr.

H.V. TRANSFORMER: 8000/8000. Output 300mA. rms. Size: 12in. x 12in. x 3in. 230V input. £40. Carr. £4.

TELEPHONE CABLE: (Twin) 1,300ft. on metal reel. £7.50 per reel. Carr. £1

FIRE-PROOF TELEPHONES: £25-00 each, carr. £1-10.

TF.2000 A.F. SIGNAL SOURCE: £175-00, carr. £1-00.

POWER UNIT: 110/230 volts a.c. input. 28 volts d.c. at 40 amps output. £30-00 each, carr. £3-00.

SMOOTHING UNIT (for the above): £10-00 each, carr. £2-00.

X-BAND MODULATOR CALIBRATOR TYPE MC-4420-X: Mnfr. James Scott. £125 ea., Carr. £1.

HP-766D DUAL DIRECTIONAL COUPLER: 940-1975MHz. £35 ea., 75p post.

BACKWARD WAVE OSCILLATOR TYPE SE-215: 6.3 heater, 105V Anode, 7.9mA. Mnfr. Watkins & Johnson. £85 ea., Carr. £1.

TEKTRONIX TIME MARK GENERATOR TYPE 180-S1: 5, 10, 50 MHz. £85. Carr. £2.

TRANSISTOR ANALYSER TA 1001 (K. & N. Electronics Ltd.): £95. Carr. £3.

ABSORPTION FREQUENCY METER (Measurements Corporation): Consisting of 3 units 1-45, 2.2-400, 420-1000 Megacycles. £55. Carr. £1.

CHRONOTON MODEL 25E: 0.4-10 seconds in seven ranges. £50. Carr. £1.

AIRMEC MODULATION METER TYPE 409: AM or FM, 3-600 MHz. £85. Carr. £2.

LISTS OF EQUIPMENT AVAILABLE: MOTORS; TELEPRINTERS; AR88 SPARES; TEST EQUIPMENT ETC. Send 10p for above lists.
ALL CARRIAGE QUOTES GIVEN ARE FOR 50 MILE RADIUS OF LONDON ONLY.

ALL U.K. ORDERS SUBJECT TO 8% VALUE ADDED TAX. THIS MUST BE ADDED TO THE TOTAL PRICE (including post or carriage).

If wishing to call at stores, please telephone for appointment.

W. MILLS

3-B TRULOCK ROAD, LONDON, N17 0PG
Phone: 01-808 9213 and Bedford 740605 (STD 0234).

**TAUT SUSPENSION MULTIMETERS
TYPE U4315**



DC current:
50-100-500µA-1.5-25-100-500mA-2.5A
AC current:
0.5-1.5-25-100mA-0.5-2.5A
DC Voltage:
75mV-1.25-5-10-25-100-250-500-1,000V
AC Voltage:
1-2.5-5-10-25-100V-150-500-1,000V
Resistance:
300Ω-6-50-500kΩ
Capacity:
30,000pF-0.5µF

Transmission level:
-15 to +2db

Sensitivity
DC: 20,000kΩ/V; AC: 2,000kΩ/V

Accuracy
DC: 2.5%; AC: 4%
86mm plain scale.

PRICE, incl. pressed-steel carrying case, set of leads and manual £10.00.

1-AMP SILICON RECTIFIERS

20 pieces	1N4001	50 p.i.v.	£1.12
"	1N4002	100 p.i.v.	£1.25
"	1N4003	200 p.i.v.	£1.35
"	1N4004	400 p.i.v.	£1.45
"	1N4005	600 p.i.v.	£1.55
"	1N4006	800 p.i.v.	£1.85
"	1N4007	1000 p.i.v.	£2.10

This is a special offer and minimum quantity of 20 pcs must be ordered. These prices are inclusive of P.P. and VAT.

TRANSISTORS

AC113	0.15	ASZ16	0.80	BD136	0.32	OC45	0.12
AC125	0.30	ASZ17	0.80	BD232	0.75	OC70	0.10
AC126	0.20	ASZ18	0.80	BF115	0.28	OC71	0.12
AC127	0.17	ASZ20	0.25	BF154	0.20	OC72	0.12
AC128	0.15	ASZ21	0.70	BF161	0.35	OC73	0.30
AC132	0.25	BC107	0.12	BF167	0.25	OC75	0.15
AC154	0.15	BC107A	0.12	BF173	0.28	OC76	0.15
AC157	0.17	BC108	0.12	BF177	0.18	OC77	0.45
AC176	0.25	BC109	0.12	BF178	0.32	OC78	0.25
AC187	0.20	BC113	0.15	BF179	0.35	OC81	0.15
AC188	0.20	BC113	0.15	BF180	0.35	OC83	0.20
ACY17	0.35	BC117	0.20	BF181	0.35	OC84	0.30
ACY18	0.20	BC118	0.20	BF184	0.30	OC122	0.60
ACY19	0.25	BC134	0.20	BF185	0.30	OC139	0.30
ACY20	0.20	BC135	0.20	BF194	0.12	OC140	0.55
ACY22	0.14	BC147	0.10	BF195	0.12	OC141	0.60
AD139	0.40	BC148	0.09	BF196	0.14	OC170	0.25
AD149	0.45	BC149	0.11	BF197	0.15	OC171	0.30
AD161	0.38	BC151	0.22	BF200	0.30	2N404	0.17
AD162	0.38	BC158	0.11	BFX88	0.20	2N456	1.10
ADZ11	1.25	BC159	0.13	BFY10	0.50	2N457	1.10
ADZ12	1.25	BC171	0.20	BFY11	0.50	2N696	0.15
AF106	0.25	BC175	0.20	BFY17	0.40	2N697	0.15
AF114	0.17	BC179	0.18	BFY18	0.25	2N698	0.30
AF115	0.17	BC182A	0.10	BFY19	0.25	2N705	0.70
AF116	0.17	BC184	0.20	BFY50	0.23	2N706A	0.10
AF117	0.17	BC186	0.25	BFY51	0.20	2N708	0.15
AF118	0.25	BC187	0.25	BFY52	0.21	2N916	0.20
AF124	0.25	BC212A	0.12	BFY90	0.60	2N929	0.20
AF125	0.25	BCY30	0.75	BSX19	0.15	2N930	0.20
AF126	0.25	BCY31	0.75	BSY26	0.17	2N987	0.40
AF127	0.25	BCY32	1.20	BSY27	0.20	2N1131	0.25
AF139	0.30	BCY33	0.75	BSY28	0.17	2N1132	0.25
AF178	0.50	BCY34	0.75	BSY29	0.35	2N1302	0.17
AF180	0.50	BCY39	1.40	BSV65	0.20	2N1303	0.15
AF186	0.40	BCY56	0.30	BSV95A	0.12	2N1304	0.20
AFZ39	0.36	BCY70	0.15	OC16	1.00	2N1305	0.20
AFZ11	0.75	BCY71	0.20	OC22	0.60	2N1306	0.27
AFZ12	1.00	BCY72	0.15	OC23	0.60	2N1307	0.25
ASZ26	0.25	BCZ10	0.50	OC24	0.60	2N1308	0.25
ASZ27	0.30	BD115	0.80	OC25	0.50	2N1309	0.25
ASZ28	0.25	BD116	0.65	OC26	0.40	2N1613	0.17
ASZ29	0.30	BD121	0.65	OC28	0.70	2N1711	0.18
ASZ54	0.25	BD123	0.80	OC29	0.60	2N2160	1.00
ASZ74	0.60	BD124	0.60	OC35	0.20	2N2369A	0.15
ASZ77	0.35	BD131	0.40	OC36	0.65	2N2646	0.25
ASZ82	0.20	BD132	0.50	OC42	0.30	2N2926	0.10
ASZ86	0.20	BD133	0.55	OC43	0.40	2N3053	0.20
ASZ15	0.80	BD135	0.30	OC44	0.15	2N3055	0.60

LINEAR INTEGRATED CIRCUITS

—Please note reductions in prices—


Mullard TAA263. Direct coupled three stage low level amplifier for use from DC to 600 kc/s. Supply voltage 6-8v. Typical power gain 77 db. into 150Ω load. Output power 10mW. T072 four-lead encapsulation £0.65*

Mullard TAA293. Medium frequency amplifier with frequency response of 600 kc/s. Nominal supply voltage 6v. Typical power gain 89 db. Maximum power dissipation 160 mW. Power output 10 mW into 150Ω load. T074 ten-lead encapsulation £0.65*

Mullard TAA320. Metal oxide silicon low frequency pre-amplifier consisting of a MOST stage followed by a bi-polar transistor. Gate to source voltage 9-14v. Total power dissipation 200 mW. Drain current 1 µA. Output conductance 0.65 mmho. T018 3-lead encapsulation £0.60*
741 operational Amplifiers 8 DIL £0.30

L.E.D. TYPE HP5082/4850

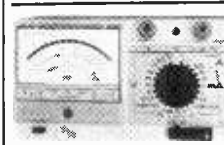Red Light GASP Light Emitting Diodes giving bright diffused light of 0.8 mcd at forward voltage of 1.6V and DC current of 20 mA. Plastic wide angle lens 0.200" diameter. Ideal for panel lights, etc.
Price for 12 pieces £1.75 incl. VAT and p.&tp.



U4317-20kΩV DC -2kΩV AC high accuracy AC/DC multimeter. 42 ranges covering AC/DC volts up to 1,000V and AC/DC current up to 5 amps.

Mirror scale. Accuracy 1.5% DC, 2.5% DC. Meter incorporates transistorized cut-out protective relay.
Price £17.00

Prices do not include VAT and carriage except where indicated. When remitting cash with order please add £0.50 per multi-meter and £0.15 per £ for other items, subject to a minimum charge of £0.25. VAT at prevailing rate should then be added to the total.

MINIMUM ACCOUNT ORDER CHARGE £10.00 PLUS VAT. OTHERWISE CASH WITH ORDER PLEASE

Our new Catalogue is ready. Please send £0.20 for your copy.

Retail Branch:
85 TOTTENHAM
COURT ROAD
LONDON W2

Z & I AERO SERVICES LTD

Tel. 727 5641 44A WESTBOURNE GROVE, LONDON W2 5JF Telex 261306

WW-156 FOR FURTHER DETAILS

**ALL MAIL ORDER BY
RETURN.C.O.D. SERVICE
WELCOME**

C. T. ELECTRONICS


We are open from 9.30 a.m.—6.00 p.m. Monday-Saturday

All mail order and enquiries to 270 Acton Lane, Chiswick, London, W4 5DG. Tel: 01-994 6275

SEMICONDUCTORS

AC107	35p	BCY32	95p	MM1712	60p
AC125	25p	BCY34	60p	MFP102	45p
AC126	25p	BCY38	65p	MFP103	45p
AC127	27p	BCY39	£1.00	(2N5457)	35p
AC128	25p	BCY55	£1.50	MFP104	35p
AC176	25p	BCY70	22p	(2N5458)	35p
AC188	30p	BCY71	22p	MFP105	35p
ACY17	25p	BCY72	22p	(2N5459)	40p
ACY18	30p	BD121	75p	OA47	10p
ACY19	30p	BD123	75p	OA70	10p
ACY20	25p	BD124	65p	OA71	10p
ACY21	30p	BD131	40p	OA79	10p
AD140	60p	BD132	50p	OA81	10p
AD142	50p	BDY53	75p	OA90	10p
AD149	60p	BDY56	75p	OA91	10p
AD161	44p	BDY11	£1.40	OA200	10p
AD162	44p	BDY17	£1.80	OA202	10p
AF114	25p	BDY19	£1.90	OA210	35p
AF115	25p	BDY20	£1.40	OA211	35p
AF116	25p	BF182	20p	OC16	90p
AF117	25p	BF184	14p	OC19	85p
AF118	60p	BF185	15p	OC22	55p
ASZ21	60p	BF186	15p	OC26	65p
ASZ23	30p	BF197	20p	OC28	90p
BA102	35p	BF200	30p	OC35	60p
BA112	50p	BF244J	30p	OC36	65p
BA114	16p	BFX29	30p	OC42	40p
BA156	15p	BFX34	30p	OC44	20p
BC107	12p	BFX35	30p	OC45	25p
BC108	12p	BFX36	30p	OC70	15p
BC109	14p	BFX38	30p	OC71	12p
BC115	15p	BFY10	35p	OC72	20p
BC116	16p	BFY50	25p	OC75	25p
BC117	20p	BFY51	25p	OC76	25p
BC118	12p	BFY52	25p	OC77	40p
BC147	11p	BFY53	25p	OC81	25p
BC148	11p	BFY90	15p	OC83	25p
BC149	12p	BSW63	65p	OC84	25p
BC153	15p	BSW68	80p	OC130	30p
BC157	14p	BY127	20p	OC170	25p
BC158	15p	BY184	65p	OC171	30p
BC169	15p	IS102	15p	OC200	60p
BC182	15p	IS103	15p	OC201	60p
BC183	12p	MJ340	50p	OC202	60p
BC184	14p	MJ481	35p	OC203	60p
BC186	25p	MJ2801	£1.25	OC204	60p
BC212L	16p	MJ2801	£1.85	OC205	60p
BC213	14p	MJ370	75p	OC206	60p
BC214	14p	MJ371	60p	OC207	60p
BC301	25p	MJ4520	65p	OC208	60p
BC302	25p	MJ2955	£1.20	OC209	60p
BC303	40p	MJ3055	75p	OC210	60p
BCY30	55p	MM1613	45p	OC211	60p
BCY31	55p	MM1613	45p	OC212	60p

TIP31B	85p	2N2218	25p
TIP32B	77p	2N2219	25p
TIP33B	£1.40	2N2222	25p
TIP34B	£1.62	2N2224	25p
TIP35B	£2.71	2N2224A	25p
TIP36B	£3.50	2N2477	70p
TIP41B	78p	2N2640	50p
TIP42B	95p	2N2846	£1.50
TIP29C	68p	2N2904	25p
TIP30C	72p	2N2906	25p
TIP31C	80p	2N2907	25p
TIP32C	£1.00	2N2925	12p
TIP33C	£1.20	2N3053	12p
TIP34C	£1.80	2N3054	65p
TIP35C	£3.90	2N3055	50p
TIP38C	£3.74	2N3232	70p
TIP41C	90p	2N3252	95p
TIP42C	90p	2N3643	30p
TIS50	40p	2N3702	14p
ZTX107	15p	2N3703	12p
ZTX300	15p	2N3704	12p
ZTX500	16p	2N3706	12p
ZTX501	20p	2N3706	12p
ZTX504	50p	2N3707	12p
ZTX531	30p	2N3708	12p
ZTX550	25p	2N3709	12p
IN659	8p	2N3771	£1.70
IN914	8p	2N3772	£2.00
IN916	8p	2N3773	£2.50
IN4001	35p	2N3319	35p
IN4002	9p	2N3220	55p
IN4003	9p	2N3386	85p
IN4004	10p	2N3904	22p
IN4005	12p	2N3905	25p
IN4006	14p	2N4058	12p
IN4007	1		

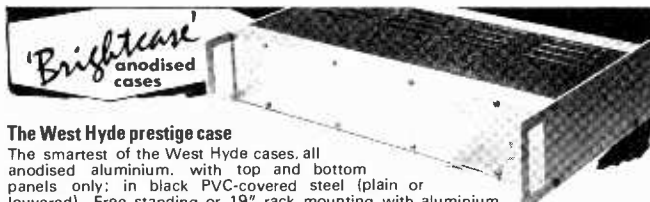

The West Hyde prestige case

The smartest of the West Hyde cases, all anodised aluminium, with top and bottom panels only; in black PVC-covered steel (plain or louvered). Free standing or 19" rack mounting with aluminium brackets. Supplied ex-stock, fully assembled, with SS Pozidriv screws.

Brightcase	1 off	Pr. Brackets	Extra for Louvres
BC21 (3 1/2" whole rack)	£14.96	86p	79p
BC22 (3 1/2" half rack)	£12.16	86p	79p
BC31 (5 1/2" whole rack)	£17.20	£1.22	79p
BC32 (5 1/2" half rack)	£14.02	£1.22	79p

Prices include panels, feet, P. & P. and VAT. State whether 1/2, 1/3 or full panels required. Prices correct April 1975.

Available in a range of six sizes in 21-gauge Zintec with blue Acrylic texture. Front panels white Zintec steel or PVC/Aluminium.

CONTIL TEXTURED CASES

Width	Depth	Height	No.	Case cost	Extra for ali panel
7"	5"	5"	755	£6.41	12p
8	6	7	867	£7.54	23p
9	7	5	975	£7.54	23p
12	7	7	1277	£8.61	15p
12	7	7	1277	£6.56	unpainted
16	12	7	16127	£12.06	35p
19	10	10	191010	£16.35	—

Prices correct April 1975.

Less for quantities. Prices include steel panel with feet and screws, P. & P. and 8% VAT.

A smart miniature case in tough, rigid, high-gloss black ABS. Front panels in either aluminium or white PVC/Steel. Built-in slots for PC cards, dividers, or screens. Chassis or PC boards can be supported on "P" clips for internal pillars. Excellent as encapsulation boxes.

MINOS PLASTIC CASES

	1 off	10 off
M2 65mm x 100mm x 50mm 2 1/2" x 3 3/4" x 2"	56p	48p
M3 100mm x 130mm x 50mm 3 3/4" x 5 1/8" x 2"	72p	62p

Less for quantities. Prices include P. & P. and VAT. Also available without panel and screws. Prices correct April 1975.

BRADRAD DRILLING AND DEBURRING TOOL

BRADRAD DRILLING & DEBURRING TOOL equals eleven drills. One cut drills and deburrs the normal run of steels, aluminium, brass copper and all types of plastics perspex, fibreglass, etc., and hardboard. Should the need arise it is designed to overcome all the problems associated with drilling thin materials—it drills interlocking holes for instance.

1/2"-2 1/2" in 1/8" steps or 6-36mm in 3mm steps. Both with 1/8" shanks: £11.66. Also 1 1/2"-2 1/2" and 36-60mm £30.78. All prices include P. & P. and 8% VAT.

Q-MAX METAL PUNCH


Q. MAX PUNCHES

3/8"	£1.39
1/2" & 5/8"	£1.60
3/4" & 7/8"	£1.70
1", 1 1/8", 1 1/4"	£2.12
1 1/2"	£2.47

Prices correct April 1975.

ADEL NIBBLING TOOL

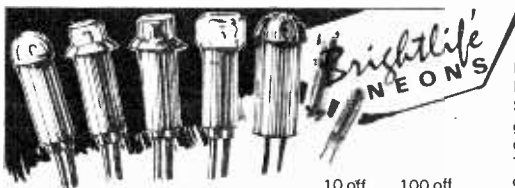ADEL The Adel cuts holes of virtually any shape and size starting from a 1/16" hole, cutting clean like a punch and die. Ideal for notching clearances on flanges of cabinets or chassis. £6.75.



Brightlife neons (illustrated as PC/A or C, PC/F, PC/E, PC/G or I, PP/A or B, Q and S) are brighter and give an average of 25,000 hrs. life. The 0.5" dia. are red or white, the 0.375" are red, amber or white; these have three cap shapes and all may be supplied for 1.15, 240V or the PP neons in 110, 240, and 440V with 6" or 30" leads.

dia.	leads	volts	10 off	100 off
6"	PC/A to I	110 or 160-260	17 1/2p	16 1/2p
30"	PC/A to I	110 or 160-260	19 1/2p	18 1/2p
6"	PP/A	110 or 160-260	17 1/2p	16 1/2p
30"	PP/A	110 or 160-260	19 1/2p	18 1/2p
Q type	none	110 or 160-260	29p	27p
S type	none	—	23p	21p

Add 8% VAT. Min. quantity each type 10 off. Prices correct April 1975.


WEST HYDE

WEST HYDE DEVELOPMENTS Ltd, Ryefield Cres., Northwood Hills, Northwood, Middx HA6 1NN
Tel: Northwood 24941/26732 WRITE OR PHONE FOR NEW FREE CATALOGUE Telex: 923231

WW—224 FOR FURTHER DETAILS



SQ IS A TRADEMARK OF CBS INC.

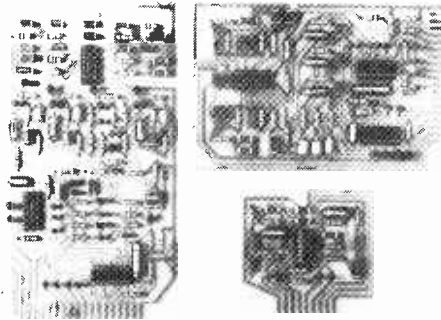

SQ QUADRAPHONIC DECODERS

SQ the leading quadraphonic system, designed by CBS engineers, offers not only 4 channel ambiphony from the fast expanding range of SQ encoded discs but also immensely increased depth and fullness of sound from standard stereo recordings too.

Feed 2 channels (200-1000mV as obtainable from most pre-amplifiers) into your choice of any of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume, Front-Back, LF-RF, LB-RB and Dimension controls can all be implemented by simple single gang potentiometers—no need for exotic 4-gang units!

These state-of-the-art circuits, used under licence from CBS, are offered in kit form comprising first grade components only—fibre glass circuit boards of professional quality designed for edge connector insertion, all resistors 2% metal oxide, all polystyrene and polycarbonate capacitors 5% or better and in decoder L2 ultra low noise (MPS A18-0.5dB typ.) transistors used in each amplifying stage.

M1 Basic matrix decoder with fixed '10-40' blend. 10 Resistors, 14 Capacitors, 1 Integrated Circuit, Printed Circuit Board. £6.64.

L1 Full logic controlled decoder with 'wave matching' and 'front-back logic' for enhanced channel separation using three specially designed Integrated Circuits, 24 Resistors, 42 Capacitors, 3 Integrated Circuits, Printed Circuit Board. £19.90.

L2 More advanced full logic decoder with 'variable blend', extended frequency response, increased front-back separation, 43 Resistors, 44 Capacitors, 3 Integrated Circuits, 9 Transistors, 6 Diodes, Printed Circuit Board. £28.20.

All kits include IC sockets and construction notes. Prices include CBS licence fee. Please write for further details in FREE LISTS.


United Kingdom: Post Free. Please add 8% VAT. Overseas: No VAT. Please add (per kit) £2.00 p & p AIR MAIL or £1.00 p & p SURFACE MAIL.



PO BOX 3000
ANDOVER, HANTS SP10 3EQ

WW—215 FOR FURTHER DETAILS

ELECTROVALUE

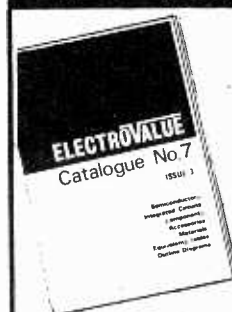

Catalogue 7 issue no 3 now ready

- UP-DATED PRODUCT & PRICE INFORMATION
- REFUND VOUCHER

We have made it just about as comprehensive and up-to-the-minute as possible. Thousands of items from vast ranges of semi-conductors including I.C.s to components, tools, accessories, technical information and diagrams are included as well as a refund voucher worth 25p for spending on orders list value £5 or more. SEND NOW FOR YOUR COPY BY RETURN 30p post paid

+ **E.V. PRICE STABILIZATION POLICY**
PRICES shown in Catalogue No 7 issue 3 will be maintained—(except in severe cases of market fluctuation) and reviewed only at 3-month intervals, commencing April 1st, instead of making day-to-day price changes.

+ **E.V. DISCOUNT PLAN**
Applies to all items except the few where prices are shown NETT. 5% on orders from £5 to £14.99; 10% on orders value £15 or more

+ **FREE POST & PACKING**
In UK for pre-paid mail orders over £2 (except Baxandall cabinets) If under there is an additional handling charge of 10p.


+ **QUALITY GUARANTEE**
All goods are sold on the understanding that they conform to makers' specifications. No rejects, seconds or sub-standard merchandise.

ELECTROVALUE LTD

All communications to Dept WW.4
28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB.
Telephone Egham 3603. Telex 264475. Shop hours: 9-5.30 daily, 9-1 p.m. Sats.
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA.
Telephone (061) 432 4945. Shop hours: Daily 9-5.30 p.m., 9-1 p.m. Sats.
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore PA 19081.

Henry's Radio

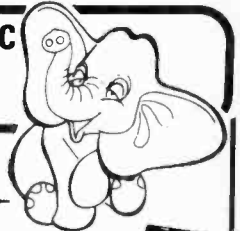LARGEST SELECTION OF ELECTRONIC COMPONENTS AND EQUIPMENT. LOW PRICES— MEAN LESS VAT.



You can build the Texan and Stereo FM Tuner

TEXAN 20 + 20 WATT IC STEREO AMPLIFIER

Features fibre glass PC board. Gardeners low field transformer, 6-ICs. 10 transistors plug diodes etc. Designed by Texas Instruments engineers for Henry's and P.W. 1972. Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply, overall size 15½ in. X 2½ in. X 6½ in. mains operated. Free teak sleeve with every kit. **£31.00** (Carr. 50p). Built and tested **£37.50**



HENELEC STEREO FM TUNER

Features capacity diode tuning, led and tuning meter indicators, stabilized power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8 in. X 2½ in. X 6½ in. Complete kit with teak sleeve **£21.00** (Carriage 50p). Built and tested **£24.95**



JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

NEW SPECIAL PURCHASE

AM/FM TUNER MODULES

Mullard type LP1179 and LP1171

These two modules together form a high quality AM/FM tuner covering the long, medium and VHF broadcast bands. Requires only 16 resistors and capacitors and a switch to complete. Supplied with circuits and spec. data.

LP1179

FM Coverage 87-108MHz
Bandwidth 300KHz
Selectivity 35dB
Signal to noise at limiting threshold 40dB
Audio output 75mV



LP1171

AM Bandwidth 6.5KHz
Sensitivity 1mV
Built-in AGC
Supply 6V negative earth
LP1179 and LP1171 **£4** each or **£7.50** pair
suitable Ferrite aerial **£0.75**



AMPLIFIERS WITH CONTROLS

E1210	12 volt 2½+2½ watts 8 ohms	£8.25
SAC14	Mains 7+7 watts 8 ohms	£11.75
SAC30	Mains 15+15 watts 8 ohms	£14.95
CA038	9 volt 1½+1½ watts 8 ohms	£6.95
CA068	12 volt 3+3 watts 8 ohms	£10.50

MULLARD MODULES

LP1157 AM/Type	£2.50
LP1185 10.7I.F. Unit	£4.50
LP1186 10.7F/M Tuner	£4.85
Gorlier Perm. F/M Tuner	£4.20

FM AND AM TUNERS AND DECODERS

FMS231 (tu 2) 6-volt FM tuner	£7.95
FMS231 (tu 3) 12-volt version	£7.95
SD4912 decoder for tu 3	£7.95
SP621 6-volt stereo FM tuner	£14.80
Sinclair FM tuner	£11.95
Sinclair decoder for above	£7.95
A1007 9-volt MW-AM tuner	£4.80
AJ018 cased FM tuner	£13.95
A1005M (s) decoder for above	£7.50

PREAMPLIFIERS

Sinclair Stereo 60 Preamplifier	£6.75
E1300 CART/TAPE/MIC INPUTS 9 volt	£2.85
E1310 Stereo 3-30mV mal cart 9 volt	£4.75
FF3 Stereo 3mV tape head 9 volt	£4.95
3402 Stereo 5-20mV Mag. cart. mains	£5.95
EQ25 Mono 3-250mV Tape/cart/flat. 9 volt	£1.95

POWER SUPPLIES—Mains input (†chassis-rest cased)

470C 6.7/9V 300mA with adaptors	£2.25	*P1081 45 volt 0.9A	£7.80
P500 9 volt 500mA	£3.20	P12 4½-12 volt	£13.95
HC244R 3/6/7½/9 volt 400mA stabilised	£5.50	SE101A 3/6/8/12 volt 1 amp stabilised	£12.75
*P11 24 volt ½ amp	£3.30	P1076 3/4½/6/7½/9/12 volt ½ amp	£4.20
*P15 28 volt ½ amp	£3.30	SE800A 1-15 volt 0-½A stabilised	£17.50
*P1080 12 volt 1A	£4.70		

SINCLAIR MODULES AND KITS



ST80 stereo preamplifier	£11.95	Sinclair Project 80	
Audio filter unit	£6.95		
240 15 watt amplifier	£5.45	PACKAGE DEALS (Carriage/Packing 35p)	
260 25 watt amplifier	£6.95		
P25 power supplies for 1 or 2 240	£4.98	2 X 240, S780, P25	£25.00
P26 power supplies (STA3) for 1 or 2 240	£7.98	2 X 260, S780, P26	£27.75
P26 power supplies (STA3) for 1 or 2 260	£7.98	2 X 260, S780, P28	£34.40
Transformer for P28	£4.90	+ Trans	£35.95
FM tuner	£11.95	805 kit	
Stereo decoder	£7.95		
IC20 power amp kit	£7.95	SINCLAIR SPECIAL PURCHASES	
P22Q power supply for 1 or 2 IC20	£5.45	* Project 60 stereo preamplifier	£6.75 post 20p
All above post paid (IGB only)		* Project 605 kit	£19.95 post 25p

EMI SPEAKERS Special Purchase

13 X 8 chassis speakers (carr/packing 30p ea or 50p pr)
*150 TC 10 watt 8 ohm twin cone **£2.20**
150A built in tweeter 8 ohms **£3.85**
EW 15 watt 8 ohm with tweeter **£5.25**
350 20 watt 8. 15 ohm with tweeter **£7.80** each
*Polished wood cabinet **£4.80** carr., etc. 35p each or 50p pair



EXCLUSIVE 5 WATT IC AMPLIFIERS

Special purchase 5 watt output 8-16 ohm load. 30 volt max DC operation complete with data.
Price **£1.50** ea. or 2 for **£2.85**.
Printed Circuit Panels **50p**.



UHF TV TUNERS

625-line receiver UHF transistorised tuners. UK operation. Brand new. (Post/packing 25p each)
TYPE A variable tuning. Slow motion drive **£3.00**
TYPE B 4-button push-button (adjustable) **£4.00**
TYPE C variable tuning **£2.50**
TYPE D 6 push-button **£4.50**

PA-DISCO-LIGHTING EQUIPMENT



Without doubt UK's best range of modular and complete equipment. Lighting, mixing, microphones accessories, speakers, amplifiers, lenses, etc., etc. FREE stock lists (Ref. No. 18) on request CALL IN AND SEE FOR YOURSELF at HENRY'S DISCO CENTRE, 309 EDGWARE ROAD, 01-723 6963.

8 DIGIT POCKET ELECTRONICS CALCULATORS

Sinclair Cambridge Built	£11.00
Sinclair Cambridge Kit	£9.00
Sinclair Cambridge Memory Built	£17.50
Sinclair Scientific Built	£16.00
Sinclair Scientific Kit	£13.50

L450 RECHARGEABLE BATTERY

2v 400mA/HR 50p p.p. 15p.

PHILIPS 12V FLUORESCENT INVERTOR

for 8w fluorescent tube. Supplied with instr. and tube **£3.50** p.p. 30p.

TEST EQUIPMENT MULTIMETERS

(carr/packing 35p)



U4324 20KΩV with case	£9.85
U4311 Laboratory meter	£52.00
U4312 20KΩV with case	£10.75
U4315 20KΩV with case	£10.00
U4317 20KΩV with case	£17.00
U4313 20KΩV with steel case	£13.80
U4317 20KΩV with case	£17.00
U4341 33KΩV plus transistor tester steel case	£11.00
U4323 20KΩV plus 1KHz 465KHz OSC with case	£8.00
IT1-2 20KΩV slim type	£5.95
THL33D (L33DX) 2KΩV robust	£7.50
TP55N 20KΩV (Case £2.00)	£10.75
TPS10S 2KΩV	£8.50
TW20S 20KΩV	£13.00
TW50K 50KΩV	£14.50
S100TR 100KΩV plus transistor tester	£22.50
New Revolutionary Supermeter 880R Multimeter	£18.50
† TE40 AC multivoltmeter	£19.75
† TE15 Grid dip meter 400Hz-28MHz	£19.95
† TE85 28 range valve voltmeter	£22.50
† TE200 RF generator 120KHz-500MHz	£18.95
† TX22D AF generator 20Hz-200KHz	£19.95
* THM350 In circuit transistor tester	£19.50
* TT145 Compact transistor tester 400Hz-28MHz	£14.75
* C3042 SWR Meter	£18.75
* SE350A De-luxe signal tracer	£12.95
* SE400 Mini-lab all in one tester	£15.50
CT-5 Scope 500.000KHz (carr. £1.00)	£44.00
Radio activity counter 0-10r (carr. £11)	£9.97
Mains unit for above (carr. 50p)	£3.75

TAPE HEADS

Marriot XRPS/17 ½ track high	£2.50
Marriot XRPS/18 ½ track med	£3.50
Marriot XRPS/36 ½ track med	£5.00
Marriot XRPS/63 ½ track high	£1.75
Marriot ½ tr. Erase 13 X 12E 343	£0.75
Marriot erase heads for XRPS 17/18/36 (XESII)	£0.75
R/RPI record/play ½ track	£0.45
H/RP Single-track rec/play	£0.35
Bogen type UL290 erase	£1.50
Miniature stereo-cassette rec/play	£2.25

STC & ITT MINIATURE RELAYS

150R 6v	2 p.c.o.	BRAND NEW 60p p.p. 15p
180R 6/12v	2 p.c.o.	
185R 12v	2 p.c.o.	
1250R 12/55	2 p.c.o.	
1700R 18/24v	2 p.c.o.	
1800R 24v	4 p.c.o.	
2500R 18/24v	2 p.c.o.	
4000R 24v	2 p.c.o.	

10.7 MHZ MINIATURE CERAMIC

IF FILTER 40p per pair p.p. 15p
EP27 LOW COST SEVEN SEGMENT I.e.d. Digit Height ½ inch **£1.35** p.p. 15p.

SL414

Plessey Sw Power Amp IC **£1.65** p.p. 15p

40KHZ ULTRA SONIC TRANSDUCERS

£5.90 p.p. 25p
TAA 960 40KHZ AMP IC **£1.75** p.p. 15p

VAT 8% EXTRA ON ALL ITEMS

FREE— SEND NOW FOR OUR NEW FREE LIST No. 36 FOR OUR COMPLETE RANGE OF OVER 10,000 SEMICONDUCTOR DEVICES AT NEW LOW PRICES.



TRANSISTORS AND INTEGRATED IC'S

TTL "7400 series" ICs from **16p** each
Cosmos "4000 series" ICs from **25p** each
Linear Op-Amps from **40p** each
Signotronics Phase Lock ICs
RCA Linear ICs
TO3 Power Devices in PNP and NPN BC107 and "BC range" from **12p**
Range of "OC" types
Plastic Power Devices, Rectifiers, Zener Diodes up to 10 watts
Power Regulator ICs and many others.
DIL SOCKETS 8 PIN **14p** 14 PIN **15p** 16 PIN **17p** 24 PIN **£1.15** 28 PIN **£1.25**

NOMBREX TEST EQUIPMENT

MODEL 35 STABILISED POWER SUPPLY
A Short-circuit proof power supply delivery up to 30v at 1A. Built-in volts and ammeters. **£34.00**

MODEL 40 WIDE RANGE AUDIO SIGNAL GENERATOR

A high stability signal generator using the low distortion Wien bridge principle. **£34.00**

MODEL 41 RF SIGNAL GENERATOR

Covering 150KHz to 220MHz in eight ranges. Built-in AF mod. Output up to 50mV. **£38.00**

MODEL 42 WIDE RANGE RF SIGNAL GENERATOR

Covering 150KHz to 300MHz in eight ranges. Highest range in harmonic. **£24.50**

MODEL 43 RC BRIDGE

Null indicating bridge for resistors and capacitors. Resistance range 10R to 10M ± 2% at Centre Scale. Capacity range 10pF to 10pF. **£26.00**

MODEL 44 INDUCTANCE BRIDGE

Measures 1µH to 100H in four ranges ± 5% accuracy. Q measurement from 0.1-1,000+10%. **£34.00**

MODEL 45 DIRECT READING FREQUENCY METER

10Hz to 100KHz in four ranges. Input from 10mV to 5v **£36.00**

All models except Model 35 are internally powered from 9v battery (extra). Carriage and packing all models 37p.

THE NEW VIDEO SPORT ELECTRONIC BALL GAME (FOOTBALL, TENNIS, HOLE IN THE WALL) £37.50 inc. VAT & £1.50 CARRIAGE/PACKING & INSURANCE.

NOW OPEN SUPERMARKET:— COME AND BROWSE ROUND THE NEW COMPONENTS SUPERMARKET AT 404 EDGWARE ROAD. BARGAINS GALORE. GOODIE BAGS. COMPONENTS, ETC. WATCH FOR FURTHER DEVELOPMENTS!

EXTRA DISCOUNTS Semi-conductors. Any one type or mixed SN 74 Series 'IC' 12 + EXTRA 10% 25 + EXTRA 15% 100 + EXTRA 20%.

Henry's Radio

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW
Prices correct at time of preparation. Subject to change without notice. E.&O.E

Hi Fi and Electronics Centres Open 9 am - 6 pm

TRANSISTORS AND DIODES

Type	Pc	VCBO	FT MHz	
BSY29 (SNPN)	30mw	15	20	17p
BD107 (SNPN)	11.5w	64	100	65p
2N711B/2G106 (SNPN)	150mw	18	120/150 Tot. Sw. Time 275 nS	45p
2N985 (GNPN)	300mw	15	Tot. Sw. Time 115 nS	£1.00
2N1304 (GNPN)	150mw	30	6	17p
2N1309 (GNPN)	150mw	30	15	32p
2N1046 (GNPN)	50w	100	20	£2.60
2N1146A (GNPN)	90w	70	15	50p
2N1557 (G)	106w	40	0-35	55p
2N2080 (G)	170w	70	0-2	£1-20
2N2082 (G)	170w	40	0-2	£1-20
2N2405 (SNPN)	1w	120	120	57p
2N3054 (SNPN)	29w	90	1-2	45p
2N3055 (SNPN)	11.5w	100		47p
2N3375 (SNPN)	11-6w	65	500	£3-60
2N4427 (SNPN)	3-5w	40	700	55p
2N5322 (SNPN)	10w	65	325	55p

AS216/OC26 25p OC35
 45p - OC42 45p, OC71
 12p. CV7006/OC72 20p.
 OC75 25p, OC83 28p.
 GET110/NK303 25p.
 OC702 10p, OA10 25p.
 RAS508AF 25p, RAS310AF 25p.
 STC Wire End 400PIV1A 4 for 50p.
 IN3193 13p, IN3194 14p.
 IN3255 20p.

RECTIFIER STACKS
 GEX541B1P2 £6-88
 GEX541D2P1 £3-50
 GEX541NB1P1F £6-00
 GEX541HP3F £6-00
 SX751N1B1P1F £6-00

INTEGRATED CIRCUITS
 MC353G Half Adder £2-20
 MC356G 3 Inp OR/NOR GATE £1-60
 MC358AG AC coupled JK Flipflop £5-50
 MC365G Line Driver £5-50
 CA3020 Wideband Pow. Amp. £1-00
 CA3021 Low power video £1-30
 CA3026A RF 1F Amp. £1-00
 CA3038A Operational Amp. £2-30
 CA3055 Pos. Volt. Regulator £1-35
 CA3085 Pos. Volt. Regulator 90p
 CD4035AE 4-stage Serial Register £2-00
 CD4017AE Decade Counter Divider £4-00
 CD4047AD Monostable Astable Multivibrator £4-00

THYRISTORS
 GE2N1774 200v, 5a. £1-20
 CR1-021C 20v, 1a. .25p
 CR10-101B 100v, 10a. £1-00
 CR10-021 10a. £1-00
 CR10-40B 10a. £1-00
 CR10-051 10a. £1-00
 CR10-017 10a. £1-00
 BTX 92 1200R 16a 1200v. £2-85

CAPACITORS
 Daily Electrolytic 9000µF 25v 60p p/p 15p; 500µF 50v 35p p/p 10p; TCC 16µF + 16µF + 8µF 450v 75p p/p 15p; CCL 50µF + 50µF 275v 45p p/p 10p; CCL Suppressor Unit Type SU103/1 comprising capacitor Diode and Resistor 45p p/p 10p; Dubilier Metallised Paper type 426 100µF 15v 60p p/p 25p; RIC 1-8½F 440v a.c. 40p p/p 10p.


FANS, CENTRIFUGAL BLOWERS & MOTOR
Airmax Type M1/Y3954 (3 blades) Cast Aluminium alloy impeller & casing (corresponds to current type 3965 7½") 230v, 1ph 50c 2900rpm Class "A" insulation 425cfm free air weight 9½lbs. inc. p.p £23-00.
Woods Aerofoil short casing type S. Ref HSB95/4/66 Cap. 2.5µF. Non-reverse 220/240v 1ph 50c 0-13a 2700rpm, 6" cast alum. impeller 4 blades width casing 2½" total 5½" weight 5½lbs incl. p.p. £13-00. Aerofoil Code 7.5 280K 200/250v, 1-0a 1ph 50c 2700rpm 550cfm free air, 7½" impeller 14 blades incl. p.p. £14-50.
Service Electric Hi-Velocity Fans, suitable for Gas combustion Systems, Steam exhausting, Pneumatic conveying, Cooling Electronic equipment, Air blast for Oil burners. **Secomak** Model 365 (corresponds to 575) Airblast Fan, 440v 3ph 50c 0-75hp 2850rpm, continuous 160cfm 12 in. w.g., nett weight 44lb, price incl. carr. £45-00. **Secomak** model 350 250v 1ph 50c 0-166hp, 2800rpm continuous 50cfm 2 in. w.g. net weight 34lbs, price incl. carr. £30-00.
Air Controls type VBL4 200/250v 1ph 50c 110cfm free air weight 7½lbs price incl. p.p. £15-50.
Type VBL5 200/250v 1ph 50c 172cfm free air. Weight 10½lbs, price incl. p.p. £19-50.
William Allday Alcose rotary vane oil free Single Stage Vacuum Pump Model HSP0B 8 HG. Rpm 1420, E.E. 3 phase induction motor 1/3hp cont 220/250v, 380/440v, Class E ins. incl. carr. £28-00.
Alcose Blower FAD 3-8cm at 5psi, Rpm 1420, Motor EE 3ph 50c ½hp 1400rpm, incl. carr. £28-00.
Gast MFG. Vacuum pump 0522-P702-R26X, Motor 110/120v a.c., 1ph 60c 1725rpm, Class E, 10cuff to 10in Mercury in 2 mins maintains vacuum, 635mm Mercury. Or as compressor 10psi int. or 15psi cont. incl. carr. £28-00.
 3 phase 2HP motor 60/50c., 1800/1500 RPM, 208/220/440v £23-50 incl. Carriage
 Cat. 2026391 Potter Instruments flange mounting capstan motor, 0.2HP cont, 110v DC 4 amp £27-50 incl. carr.

Where p.p. not advised add 10p per £ handling and post (in UK). Cash with order. Personal callers welcome. Open Mon.-Wed. 9.30-5.00 Fri.-Sat. 9.30-5.00. Free Car Park adj. PRICES SHOWN ARE EXCLUSIVE OF V.A.T.

W. & B. MACFARLANE

126 UXBRIDGE ROAD, HANWELL, LONDON W7 3SL

WW-043 FOR FURTHER DETAILS

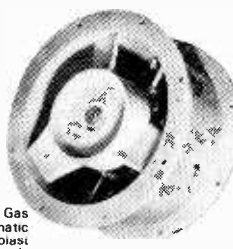

P. F. RALFE 10 CHAPEL ST. LONDON NW1. Phone 01-723 8753

SIGNAL GENERATORS

MARCONI TF801D/IS. 10-480 mHz P.O.A.
MARCONI TF801B/2S. 10-480 mHz £225.
MARCONI TF144H 10kHz-72 mHz P.O.A.
ADVANCE SG63D. AM/FM 7.5-230mHz £125.
HGN MS4U AM/FM 9.6-240mHz. N.Dev.Fac.
ROHDE & SCHWARZ SMLR 15-30mHz power generator. P.O.A.
RACAL/AIRMEC 201A. 30kHz-30mHz. As new. P.O.A.
ADVANCE SG21 VHF Square-wave generator 9kHz-100mHz. £25.



OSCILLOSCOPES

TEKTRONIX 661 Sampling scope with 4S1 & 5T1A plug-in units. 3GHz. £200.
TEKTRONIX 545A with CA unit. DC-30mHz. Price only £295-00.
TEKTRONIX 531 DC-15mHz with L type plug-in
TEKTRONIX 535 DC-15mHz with L type plug-in
TEKTRONIX 545B DC-30mHz with 'CA' plug-in.
 NB: Due to the fragile nature of CRTs we regret that these oscilloscopes cannot be despatched by post. Collection only or delivery could be arranged.



MISCELLANEOUS TEST EQUIPMENT

MARCONI TF1400S double pulse generator with TM6600/S secondary pulse unit. £105.
MARCONI TF791D deviation meter. 4-1024mHz. 0-100kHz deviation.
MARCONI 455E Wave Analyser £120.
MARCONI TF2600 Valve Voltmeter 1mV-300V. Excellent. £75.
ROHDE & SCHWARZ USVD calibrated receiver 280-4, 600mHz.
ROHDE & SCHWARZ A.F. Wave Analyser type FTA 0-20kHz plus log/lin AF meter incorporated. Excellent condition.
ROHDE & SCHWARZ URV milli-voltmeter BN10913 (late type) 1mV-10V. With 'T' type insertion unit, free probe and attenuator heads. 1kHz-1,600mHz. £175.
COSSOR 1453 True RMS milli-voltmeter. Excellent. £75.
ADVANCE PG54 Pulse generator. AS NEW.
SOLARTRON EM1006 production-line resistance tolerance check-set. 0-15Mohm digital read-out.
AIRMEC TYPE 210 modulation meter. Excellent condition.
WAYNE KERR B521 LCR Bridge. Excellent condition. £55.
RACAL SA520 Digital Frequency counter/timer. 300kHz. £47.50.
CAMBRIDGE A.C. Test Set. £75.00.
GAMBRELL Precision 4 Decade Resistance Box. 1-11, 110 ohms. £24.50.

BOXER INSTRUMENT FANS

Dimensions 4-5 x 4-5 x 1-5 ins. Very quiet running, precision fan specially designed for cooling electronic equipment, amplifiers etc. For 110v. AC operation—(practise is to run from split primary of mains transformer or use suitable mains dropper). CC only 11 Watts. List price over £10 each. Our price, in brand new condition, is £4.50.

AVO VALVE TESTERS

Brief-case type 160. Full working condition throughout. £65.

AERIAL CHANGE/OVER RELAYS

of current manufacture designed especially for mobile equipments, coil voltage 12v., frequency up to 250 MHz at 50 watts. Small size only, 2 in. x ½ in. Offered brand new, boxed. Price £1-50, inc. P.&P.

RACAL/AIRMEC VHF/UHF Milli-voltmeter type 301A.

Frequency range 50Hz-900MHz. Voltage range 300µV-3V in eight ranges. Co-axial input 50 and 75 ohms BNC connectors. DC Ranges 100µV-10V in ten ranges. Light-weight mains operated instrument in as new condition with handbooks. Other makes of voltmeter also available from stock.

POLARAD Model SA84WA SPECTRUM ANALYSER

10MHz-63GHz. I.F. Markers. Spectrum calibrator. Log/Lin scale. NB. This is not the instrument with the expensive TWT to replace. Supplied in full working, excellent condition. Guarantee.

EDDYSTONE U.H.F. RECEIVER type 770S.

Continuous coverage from 500-1000mHz. AM/FM. Sensitivity approx. 10µV absolute. Completely self-contained with speaker. Excellent condition.

MANY TYPES OF RF plugs and sockets in stock:—

BNC plugs 50Ω. 30p. BNC sockets 50Ω. 25p. N. Type plugs 50Ω. 50p. Burndept plugs. 40p. Burndept sockets. 40p. Miniature PYE. 20p. Miniature sockets. 20p.
 All connectors are brand new. Immediate delivery. Please add appropriate postage.

HEWLETT PACKARD/BOONTON TYPE 8900B

Peak-power calibrator. Measures true peak power ±.6 db absolute. Frequency range 50-2000Mhz. RF power range 200mW peak, full-scale. RF Impedance 50 ohms. P.O.A.

MINI HELIPOTS

500Ω Beckman Linearity Tolerance 0.075% (10 Turn). 1KΩ Beckman Linearity Tolerance 0.25% (10 Turn). 20Ω Colvern CLR 26/6310/9S (3 Turn). 5KΩ Colvern (10 Turn).

MARCONI TF995A2/M AM/FM R.F. SIGNAL GENERATORS.

1.5-220mHz. 0-100kHz Deviation. 1µV-100mV output. Sold in excellent condition. P.O.A.

PLEASE ADD 8% V.A.T. TO THE TOTAL AMOUNT WHEN ORDERING. INCORRECT AMOUNTS WILL CAUSE DELAY IN DESPATCH. THANK YOU.

Ex-BEA CONTROL UNITS by UNIVAC

A free-standing, modern style diecast case consisting of:

2-50way gold-plated plug and sockets; sub-assembly with 3-multiway switch assemblies; 4-decade push button assembly with electrical reset; 2-decade push button assembly with electrical reset; single-bank 8-push button assembly; 1-decade lamp assembly; 1-2-decade lamp assembly; 1-12 X 3-lamp assembly; 4-decade thumb wheel assembly; 16-bit inline card code assembly; 6-15way plug and sockets.

Limited stocks at **£12.50** ea plus £2 carriage

ALSO MODERN STYLE TYPEWRITER KEYBOARD

with 21 separate function keys. Housed in simline diecast case. Transistorised.

No information but a "buy" at **£15** ea plus £2 carriage

MARCONI TF801A/1 Signal Generator 10 to 310 MHz **£55** ea.
MARCONI TF801B Signal Generator **£120** ea.
MARCONI TF801C Signal Generator **£180**.
MARCONI TF791B Carrier Deviation Meter **£30** ea.
MARCONI TF934/2 FM Deviation Meter **£35**.
MARCONI TF1020A RF Power Meter 150 and 300 Watts. As New **£75** ea.
MARCONI TF1020A RF Power Meter 50 and 100 Watts. As New **£50** ea.
MARCONI TF1094A/S HF Spectrum Analyser. Late model. Must go. **£160**.
MARCONI TF1434/2 Counter Range extension unit 10-100MHz **£25** ea.
KELVIN & HUGHES Single Channel Recorders with spare paper **£18** ea.
HEWLETT PACKARD Power Meter 1mV to 300V dB scale **£20**.
DAWE Digital Printer type 3094A. As new

£27.50 ea.
WESTON THERMOPROBE -60 to +100 degrees Centigrade **£70**.
WANDEL & GOLTERMAN TFEK41 Level Meter **£60**.
PROSSER SCIENTIFIC INSTRUMENTS Model A100 Waveform Generator. Multi wave forms **£160**.
RHODE & SCHWARZ Admittance Meter VLUK-BN3511. As new **£140**.
TEKTRONIX Oscilloscope type 545B. Main frame only. As new condition **£370**.
HEWLETT PACKARD DB Oscilloscope type 175A. 3dB-50MHZ twice. Large 6 X 10cm screen **£185**.
AIRMEC 4 trace Oscilloscope. DC to 3MHz. Good condition **£50**.
PYE SCALAMP GALVANOMETER. Hammer grey. Tested **£5** ea.
SOLARTRON Multipurpose stab PU type 1094.

Standard mains input. Outputs: +250V DC 200MA; +18V DC 2A; +6V DC 8A; -3.5V DC 100MA; -6V DC 8A; -18V DC 4A; 25V AC 150MA. All DC lines will withstand short-circuits to earth. With copy of manual **£20** ea.
DUAL TRACE PLUG-IN units for CD1212 Scopes DC-24MHz **£35** ea.
TEKTRONIX Colour Monitor type 654 **£550**.
MARCONI TF2950 Mobile Radio Test Set **£650**.
TEKTRONIX RM527 Waveform Monitor **£250**.
TELONIC Sweep Generator SM2000/1. Main frame with 0-20kHz plug-in **£300**.
COLLINS RECEIVER IP-10ULR. 90MHz to 10GHz in 8 bands. Panoramic. Analyser or DF modes. With power unit **£350** ea.

HUNDREDS OF SQ. FT. packed with CLEARANCE ITEMS, TEST GEAR ETC. All individually priced. CALL or SEND for LISTS.

EX-MINISTRY CT436 Double Beam Oscilloscope DC-6 megs. Max Sensitivity 10mV/cm. Small compact. Size 10 X 10 X 16 in. Suitable for Colour TV servicing. Price **£85** each including copy of manual.

HARTLEY 13A Double Beam Oscilloscope TB 2c/s-750 kc/s. Bandwidth 5.5Mc/s. Sensitivity 33Mv/cm. Calibration markers 100kc/s and 1Mc/s. **£30** each.

TELEPHONES

MODERN STYLE 706 BLACK OR TWO-TONE GREY **£3.75** ea. P. & P. 45p. **STYLE 7006** TWO-TONE GREEN OR GREY **£3.75** ea. P. & P. 45p.
HANDSETS—complete with 2 insets and lead **75p** ea. P. & P. 37p.
DIALS ONLY **75p** ea. P. & P. 30p.
STILL AVAILABLE MODERN STANDARD TELEPHONES IN GREY OR GREEN WITH A PLACE TO PUT YOUR FINGERS LIKE THE 746. **£3.00** ea. P. & P. 45p.

CAPACITOR PACK 50 Brand new components only **50p**. P. & P. 27p.

P.C. MOUNT SKELETON PRE-SETS. Screwdriver adjust 10, 5 and 2.5M @ **2p** ea. 1M, 500, 250 and 25K @ **4p** ea. Finger adjust 10, 5 and 2.5M @ **3p** ea. 1M, 500, 250 and 25K @ **5p** ea. Min. P. & P. 15p.

Beehive Trimmer 3/30 pf. Brand new. Qty 1-9 **13p** ea. P. & P. 15p; 10-99 **10p** ea. P. & P. 25p; 100-999 **7p** ea. P. & P. free.

DELIVERED TO YOUR DOOR 1 cwt. of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY **£4**. N. Ireland **£2** extra.
P.C.B. PACK S & D. Quantity 2 sq. ft.—no tiny pieces. **50p** plus P. & P. 25p.
TRIMMER PACK, 2 Twin 50/200 pf ceramic;

2 Twin 10/60 pf ceramic; 2 min strips with 4 preset 5/20 pf on each; 3 air spaced preset 30/100 pf on ceramic base. ALL BRAND NEW **25p** the LOT. P. & P. 15p.
PHOTOCELL equivalent OCP71. **13p** ea.
MULLARD OCP70 10p ea.
GRATICULES. 12 cm. by 14 cm. in High Quality plastic. **15p** each. P. & P. 8p.

Vast quantity of good quality components —NO PASSING TRADE—so we offer **3 LB. of ELECTRONIC GOODIES for £1.50 post paid.**

HF Crystal Drive Unit. 19 in. rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) **£5** ea. Carr. **£2**.

ROTARY SWITCH PACK—6 Brand New switches (1 ceramic; 1-4 pole 2 way etc.). **50p**. P. & P. 25p.
BOURNS TRIMPOT POTENTIOMETERS.

20: 50: 100: 200: 500 ohms: 1: 2: 2.5: 5: 10: 25k at **35p** ea. ALL BRAND NEW.

RELIANCE P.C.B. mounting. 270: 470: 500 ohms: 10K at **35p** ea. ALL BRAND NEW.

VENNER Hour Meters—5 digit. wall mount —sealed case. Standard mains. **£3.75** ea. P. & P. 55p.

TRANSFORMERS. All standard inputs. Gard/Parm/Part. 450-400-0-400-450. 180 MA. 2 X 6.3v. **£3** ea.

FANTASTIC VALUE Miniature Transformer. Standard 240V input. +3V 1 amp output. Brand New. **65p** ea. P. & P. 20p. Discount for quantity.

FIBREGLASS PRINTED CIRCUIT BOARD. Brand New. Single or Double sided. Any size **13p** per sq. in. Postage 20p per order.

HIGH VALUE PRINTED BOARD PACK. no two boards the same—no short leaded computer boards. **£1.75** post paid.

METER PACKS—3 different meters for **£2**. P. & P. 55p.

RESETTABLE COUNTERS—4 digit by Stonebridge/Sodeco. 1.000 ohm coil. **£2** ea. P. & P. 35p.

E.H.T. CAPACITORS 1 mfd 7.5 KV working. 2 mfd 5 KV working. 8 mfd 2.5 KV working. 0.5 mfd 10 KV working **£2** each.

RAPID DISCHARGE 1 mfd 5.6 KV **£2.50** ea. 0.9 mfd 15 KV **£3.50** ea. 0.15 mfd 120 KV **£7** ea. Carriage extra.

DON'T FORGET YOUR MANUALS S.A.E. WITH REQUIREMENTS

LOW FREQUENCY WOBBLATOR
 For alignment of Receivers, Filters, etc. 250KHz to 5MHz, effective to 30MHz on harmonics. Three controls—RF level, sweep width and frequency. Order LX63. Price **£8.50** P. & P. 35p.
 As above but can have extended cover range down to 20KHz by addition of external capacitors. Order LX63E. Price **£11.50** P. & P. 35p.
 Both models can be used with any general-purpose oscilloscope. Requires 6.3V AC input. Supplied connected for automatic 50Hz sweeping. An external sweep voltage can be used instead. These units are encapsulated for additional reliability, with the exception of the controls (not cased, not calibrated).

20HZ to 200KHZ

SINE AND SQUARE WAVE GENERATOR

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent sine and square wave amplitude controls. 3V max sine 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. **£8.85** each. P. & P. 25p. Sine Wave only **£6.85** each. P. & P. 25p.

WIDE RANGE WOBBLATOR

5 MHz to 150 MHz (Useful harmonics up to 1.5 GHz) up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V AC and use within minutes of receiving. All this for only **£6.75**. P. & P. 25p. (Not cased, not calibrated.)

TRANSISTOR INVERTORS

TYPE A Input: 12V DC Output: 1.3kV AC 1.5MA Price £3.45	TYPE B Input: 12V DC Output: 1.3kV DC 1.5MA Price £4.70	TYPE C Input: 12V to 24V DC Output: 1.5kV to 4kV AC 0.5MA Price £6.35	TYPE D Input: 12V to 24V DC Output: 14kV DC 100 micro amps at 24V. Progressively reducing for lower input voltages Price £11
--	--	--	---

Postage & Packing **36p**


MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2 HZ to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY **£6.25**. P. & P. 25p.
STILL AVAILABLE our 20 MHz version at **£9.75**. P. & P. 25p.

Unless stated - please add **£2.00** carriage to all units.

VALUE ADDED TAX not included in prices—please add **8%**

Official Orders Welcomed, Gov./Educational Depts., Authorities, etc., otherwise Cash with Order

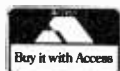Open 9 am to 6.30 pm any day (later by arrangement.)



CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, Kings Road) Tel.: Reading 582605/65916

RS VALVE MAIL ORDER CO.

16a Wellfield Rd., London, SW16 2BS
Tel: 01-677 2424 Telex: 946 708.

VALVES				INDUSTRIAL VALVES						
ECH35 1.50	EZ80 0.30	PEN45DD	UCL83 0.70	6CD6G 1.60	12BH7 0.60	6060	CV131	CV3986	EF54	OD3
AZ31 0.60	ECH42 0.85	EZ81 0.31	UF41 0.75	6CH16 1.50	30C15 1.00	6061	CV132	CV3988	EF55	OG3
AZ41 0.70	ECH81 0.35	EZ90 0.45	UF89 0.50	6E5GT 0.75	30C17 1.00	6062	CV133	CV3991	EF804	OZ4
CB131 1.40	ECH84 0.50	GZ50 0.90	UL41 0.85	6F23 0.90	30C18 0.90	6063	CV135	CV3998	EF960	OZ4A
CL33 1.50	ECL80 0.50	GZ30 0.65	UL84 0.50	6J5G 0.45	30F5 1.00	6064	CV137	CV4002	EL91	PT15
CV31 0.60	ECL82 0.42	GZ34 0.75	UY41 0.55	6J5GT 0.55	30FL1 1.00	6065	CV138	CV4003	EN30	QA2400
DAF91 0.40	ECL86 0.55	H63 0.90	VP4B 1.25	6K6GT 0.80	30FL14 1.00	6067	CV140	CV4004	EN31	QA2403
DAF96 0.60	ECLL800	HL41DD	VR75/30	6K7GT 0.35	30L15 0.95	6072	CV142	CV4005	EN32	QA2404
DCC90 1.35	3.50	0.70	VR150/30	6K8GT 0.50	30L17 0.95	6074	CV144	CV4006	EN91	QA2406
DF91 0.40	EF37A 1.20	HN309 1.50	VR150/30	6P25 2.50	30P19 0.95	6080	CV146	CV4007	ESU74	QA2407
DF96 0.60	EF39 1.25	KT61 2.00	VR150/30	6P25 2.50	30P19 0.95	6080	CV148	CV4008	ESU76	QA2408
DK91 0.50	EF41 0.75	KT66 2.50	VR150/30	6P25 2.50	30P19 0.95	6080	CV150	CV4009	ESU77	QA2409
DK92 1.00	EF55 1.50	KT81 (7C5)	VR150/30	6P25 2.50	30P19 0.95	6080	CV152	CV4010	F6057	QA2410
DK96 0.75	EF80 0.35	17C30	VR150/30	6P25 2.50	30P19 0.95	6080	CV154	CV4011	F6060	QA2411
DL92 0.50	EF85 0.45	KT88 3.25	VR150/30	6P25 2.50	30P19 0.95	6080	CV156	CV4012	F6063	QA2412
DL94 0.48	EF86 0.50	KTW61 1.50	VR150/30	6P25 2.50	30P19 0.95	6080	CV158	CV4013	F6066	QA2413
DL96 0.55	EF89 0.35	KTW62 1.50	VR150/30	6P25 2.50	30P19 0.95	6080	CV160	CV4014	F6069	QA2414
DM70 0.70	EF91 0.40	N78 3.50	VR150/30	6P25 2.50	30P19 0.95	6080	CV162	CV4015	F6072	QA2415
DY86/7 0.45	EF92 0.50	OA2 0.45	VR150/30	6P25 2.50	30P19 0.95	6080	CV164	CV4016	F6075	QA2416
DY802 4.07	EF98 0.80	OB2 0.45	VR150/30	6P25 2.50	30P19 0.95	6080	CV166	CV4017	F6078	QA2417
EAB3C 0.80	EF183 0.40	OZ4 0.55	VR150/30	6P25 2.50	30P19 0.95	6080	CV168	CV4018	F6081	QA2418
EA42 0.38	EF184 0.40	PC86 0.65	VR150/30	6P25 2.50	30P19 0.95	6080	CV170	CV4019	F6084	QA2419
EAF801 0.70	EH90 0.60	PC88 0.65	VR150/30	6P25 2.50	30P19 0.95	6080	CV172	CV4020	F6087	QA2420
EB33 1.00	EL13 2.50	PC90 0.55	VR150/30	6P25 2.50	30P19 0.95	6080	CV174	CV4021	F6090	QA2421
EB34 0.75	EL34 2.70	PCC84 0.45	VR150/30	6P25 2.50	30P19 0.95	6080	CV176	CV4022	F6093	QA2422
EB38 0.40	EL37 2.50	PCC89 0.55	VR150/30	6P25 2.50	30P19 0.95	6080	CV178	CV4023	F6096	QA2423
EBF80 0.40	EL41 0.95	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV180	CV4024	F6099	QA2424
EBF83 0.40	EL42 1.85	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV182	CV4025	F6102	QA2425
EBF89 0.32	EL44 0.35	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV184	CV4026	F6105	QA2426
EBL31 2.00	EL46 1.00	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV186	CV4027	F6108	QA2427
ECC40 1.00	EL48 0.50	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV188	CV4028	F6111	QA2428
ECC42 0.38	EM81 0.60	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV190	CV4029	F6114	QA2429
ECC43 0.38	EM84 0.40	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV192	CV4030	F6117	QA2430
ECC85 0.50	EY81 0.45	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV194	CV4031	F6120	QA2431
ECC88 0.50	EY86 0.45	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV196	CV4032	F6123	QA2432
ECCF80 0.45	EZ40 0.60	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV198	CV4033	F6126	QA2433
ECCF82 0.45	EZ41 0.60	PCF80 0.40	VR150/30	6P25 2.50	30P19 0.95	6080	CV200	CV4034	F6129	QA2434

TRANSISTORS & ICs				DIL SOCKETS						
AA119 0.7	BF179 0.33	OC44 0.20	2N697 0.16	3N141 0.81	SN7476 0.45	6066	CV131	CV3986	EF54	OD3
AAZ13 0.12	BF180 0.36	OC45 0.20	2N706A 0.12	40360 0.40	SN7480 0.60	6061	CV132	CV3988	EF55	OG3
AAZ15 0.10	BF181 0.36	OC71 0.18	2N706A 0.12	40361 0.40	SN7482 0.87	6062	CV133	CV3991	EF804	OZ4
AC107 0.15	BF194 0.10	OC72 0.28	2N1302 0.24	40430 0.85	SN7484 1.00	6063	CV135	CV3998	EF960	OZ4A
AC126 0.25	BF195 0.13	OC76 0.30	2N1303 0.18	SN7400 0.16	SN7486 0.47	6064	CV137	CV4002	EL91	PT15
AC127 0.25	BF197 0.15	OC77 0.54	2N1304 0.28	SN7401 0.16	SN7490 0.55	6065	CV138	CV4003	EN30	QA2400
AC128 0.15	BF200 0.32	OC81 0.29	2N1305 0.28	SN7402 0.16	SN7491 0.55	6067	CV140	CV4004	EN31	QA2403
AC176 0.26	BF211 0.25	OC81D 0.28	2N1306 0.28	SN7403 0.16	SN7492 0.70	6072	CV142	CV4005	EN32	QA2404
AC187 0.21	BF598 0.25	OC81Z 0.45	2N1307 0.28	SN7404 0.26	SN7493 0.70	6074	CV144	CV4006	EN91	QA2406
AC188 0.20	BFW10 0.61	OC83 0.27	2N1308 0.28	SN7405 0.22	SN7494 0.80	6080	CV146	CV4007	ESU74	QA2407
AC191 0.22	BFX29 0.28	OC140 1.14	2N1309 0.30	SN7406 0.42	SN7495 0.80	6080	CV148	CV4008	ESU76	QA2408
AC193 0.78	BFX88 0.24	OC170 0.30	2N1613 0.21	SN7407 0.28	SN7496 0.95	6080	CV150	CV4009	ESU77	QA2409
AD140 0.50	BFY50 0.21	OC171 0.30	2N1614 0.45	SN7408 0.28	SN7497 0.95	6080	CV152	CV4010	F6057	QA2410
AD149 0.50	BFY51 0.20	OC200 0.54	2N1615 0.78	SN7409 0.16	SN7498 0.95	6080	CV154	CV4011	F6060	QA2411
AD161 0.44	BFY52 0.20	OC201 1.00	2N1616 0.78	SN7410 0.16	SN7410 1.89	6080	CV156	CV4012	F6063	QA2412
AD162 0.44	BY100 0.27	OC202 0.90	2N2369A 0.16	SN7411 0.25	SN7410 1.89	6080	CV158	CV4013	F6066	QA2413
AF115 0.25	BY126 0.14	OC203 0.55	2N2646 0.50	SN7412 0.30	SN7411 0.86	6080	CV160	CV4014	F6069	QA2414
AF116 0.25	BY127 0.12	OC203 0.55	2N2646 0.50	SN7413 0.36	SN7411 0.86	6080	CV162	CV4015	F6072	QA2415
AF117 0.24	BZK61 series	ORP12 0.60	2N2904A 0.25	SN7414 0.36	SN7411 0.86	6080	CV164	CV4016	F6075	QA2416
AF196 0.48	0.20	ORP60 0.20	2N2905 0.32	SN7415 0.36	SN7411 0.86	6080	CV166	CV4017	F6078	QA2417
AF239 0.44	BZ878 series	TC44 0.29	2N2905A 0.25	SN7416 0.36	SN7411 0.86	6080	CV168	CV4018	F6081	QA2418
AS27 0.33	0.10	TC226D 1.50	2N2906 0.20	SN7417 0.36	SN7411 0.86	6080	CV170	CV4019	F6084	QA2419
AS28 0.25	CRS1 0.05 0.35	TIL209 0.20	2N2926 0.12	SN7418 0.36	SN7411 0.86	6080	CV172	CV4020	F6087	QA2420
BA102 0.25	CRS1 0.40 0.50	ZTX107 0.12	2N3053 0.18	SN7419 0.36	SN7411 0.86	6080	CV174	CV4021	F6090	QA2421
BA115 0.10	CRS3 0.05 0.40	ZTX108 0.08	2N3056 0.45	SN7420 0.36	SN7411 0.86	6080	CV176	CV4022	F6093	QA2422
BC107 0.14	CRS3 0.65 0.10	ZTX109 0.13	2N3125 0.91	SN7421 0.36	SN7411 0.86	6080	CV178	CV4023	F6096	QA2423
BC108 0.13	MJE340 0.47	ZTX301 0.14	2N3614 0.65	SN7422 0.25	SN7411 0.86	6080	CV180	CV4024	F6099	QA2424
BC109 0.14	MJE370 0.68	ZTX302 0.18	2N3615 0.65	SN7423 0.37	SN7411 0.86	6080	CV182	CV4025	F6102	QA2425
BC113 0.15	MJE520 0.63	ZTX304 0.24	2N3702 0.11	SN7424 0.37	SN7411 0.86	6080	CV184	CV4026	F6105	QA2426
BC117 0.21	MJE2955 1.27	ZTX500 0.13	2N3703 0.12	SN7425 0.37	SN7411 0.86	6080	CV186	CV4027	F6108	QA2427
BC143 0.30	MJE305 0.75	ZTX501 0.16	2N3704 0.13	SN7426 0.37	SN7411 0.86	6080	CV188	CV4028	F6111	QA2428
BC147 0.10	MPF102 0.40	ZTX531 0.25	2N3705 0.15	SN7427 0.37	SN7411 0.86	6080	CV190	CV4029	F6114	QA2429
BC148 0.8	MPF103 0.36	ZTX531 0.25	2N3706 0.11	SN7428 0.40	SN7411 0.86	6080	CV192	CV4030	F6117	QA2430
BC169C 0.15	MPF104 0.35	ZTX550 0.18	2N3707 0.13	SN7429 0.40	SN7411 0.86	6080	CV194	CV4031	F6120	QA2431
BC182 0.12	MPF105 0.36	IN914 0.06	2N3708 0.07	SN7430 0.37	SN7411 0.86	6080	CV196	CV4032	F6123	QA2432
BC184 0.13	NKT404 0.66	IN4001 0.05	2N3709 0.10	SN7431 0.37	SN7411 0.86	6080	CV198	CV4033	F6126	QA2433
BCY32 0.85	OA70 0.10	IN4003 0.18	2N3710 0.11	SN7432 0.37	SN7411 0.86	6080	CV200	CV4034	F6129	QA2434
BCY33 0.38	OA79 0.10	IN4004 0.18	2N3711 0.11	SN7433 0.37	SN7411 0.86	6080	CV202	CV4035	F6132	QA2435
BCY34 0.45	OA81 0.18	IN4005 0.10	2N3820 0.50	SN7434 0.37	SN7411 0.86	6080	CV204	CV4036	F6135	QA2436
BCY70 0.18	OA91 0.7	IN4006 0.12	2N3823 0.20	SN7435 0.37	SN7411 0.86	6080	CV206	CV4037	F6138	QA2437
BCY71 0.22	OA200 0.06	IN4007 0.12	2N3903 0.15	SN7436 0.37	SN7411 0.86	6080	CV208	CV4038	F6141	QA2438
BCY72 0.15	OA202 0.06	IN4009 0.06	2N3904 0.20	SN7437 0.37	SN7411 0.86	6080	CV210	CV4039	F6144	QA2439
BCZ11 0.65	OC16 1.00	IN4148 0.06	2N3905 0.25	SN7438 0.37	SN7411 0.86	6080	CV212	CV4040	F6147	QA2440
BD121 1.00	OC20 2.00	IS131 0.13	2N3906 0.25	SN7439 0.37	SN7411 0.86	6080	CV214	CV4041	F6150	

SERVICE TRADING CO

Available in black, red, white, yellow, blue and green. New 15p each. Post Paid



RELAYS

SIEMENS PLESSEY, etc. MINIATURE RELAYS

1	2	3	4	1	2	3	4
52	4-8	c/o	70p*	700	16-24	4 M2B	60p*
58	5-9	c/o	80p*	700	16-24	4 c/o	80p*
185	8-12	M	80p*	1250	18-36	2 c/o	60p*
230	9-18	2 c/o	70p*	2500	36-45	6 M	60p*
430	15-24	4 c/o	80p*	2500	31-43	2 c/OH0	60p*
700	12-24	2 c/o	60p*	9000	40-70	2 c/o	60p*
				15k	85-110	6 M	60p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price HD=Heavy Duty. All Post Paid. (*including Base)

OPEN TYPE RELAYS

6 VOLT D.C. 1 make con. 35p. Post 15p.

9 VOLT D.C. RELAY

3 c/o 5 amp contacts. 70 ohm coil 75p. Post 15p.

12 VOLT D.C. RELAY

3 c/o 5 amp contacts. 120 ohm coil 75p. Post 15p.

24 VOLT D.C. 3 c/o 600 ohm coil 75p. Post 15p.

2 HD c/o 700 ohm coil 75p. Post 15p.

4 c/o 300 ohm coil 85p. Post 15p.

ENCLOSED TYPE RELAYS

24 VOLT D.C. M.f.g. IIT 3 h.d. c/o contacts 55p.

Post 15p. Base 15p extra.

55 VOLT A.C.

3 heavy duty c/o contacts. Price 55p. Post 15p. Base 15p.

100 VOLT A.C.

2 c/o sealed type, octal base 75p. Post 15p. Base 15p.

240 VOLT A.C. RELAY

240V. A.C. heavy duty 3 c/o contacts. Price 75p. Post 15p. Octal base 15p extra.

220/240 VOLT AC RELAY

3 c/o 5 amp cont. Sealed M.f.g. ISKRA. £1.25. Post 15p. Base 15p extra.

ARROW 230/240V AC 2 c/o 15 amp contacts.

Amp connectors. £1.00. Post 15p.

110 VOLT A.C. 2 c/o. 20 amp. £1.25. Post 15p.

CLARE-ELLIOT Type RP 7641 G8

Miniature relay. 675 ohm coil. 24V D.C. 2 c/o. 70p. P.P.

MANY OTHERS FROM STOCK, PHONE FOR DETAILS



BLOWER UNIT
200-240 Volt A.C. BLOWER UNIT
Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120mm. dia. x 60mm. deep. Price £3.00. Post 30p.

PRECISION CENTRIFUGAL BLOWER

Mfg. Airflow Developments Ltd., continuously rated, smooth running, 230/240v A.C. motor. 80 c.f.m. £6.50. Post 50p.

SUB-MINIATURE REED RELAY 3-9 VOLT D.C.

1 make, size 1 1/2" x 3/4". STANDING VALUE ONLY £1.00 for six. £1.50 for ten. Post 15p. (Min. order six).

VERY SPECIAL OFFER

Micro Switch, 5 amp. c/o contacts. NEW. 20 for £2.00. Post 10p. (Min. order 20.) Ditto. Press to break. 20 for £1.50. Post 10p.

'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH

Each bank comprises of a change-over rated at 10 amps 240 volt A.C. Black knob 1 in. dia. Fixing hole 3/8 in. Prices: 1-bank 30p, 3-bank 50p. (Illustrated) inc. P. & P. Special quotes for quantities.

COIN MECHANISM (Ex-London Transport)

Unit containing selector mechanism for 1p, 2p & 5p coins. Micro switches, relays, solenoid-operated hopper. 24 volt D.C. Precision built to high standard. Incredible VALUE at only £2.50. Post 70p.

230-250 VOLT A.C. SOLENOID

Similar in appearance to illustration. Approximately 1 1/2 lb. pull. Size of feet 1 1/4" X 1 1/4". Price £1.00 Post 15p.

24 VOLT DC SOLENOIDS

UNIT containing: 1 heavy duty solenoid approx. 25 lb. pull at 1 in. travel. 2 solenoids of approx. 1 lb. pull at 1/2 in. travel. 6 solenoids of approx. 4 oz. pull at 1 in. travel. Plus 1 24V D.C. Precision built to high standard. Incredible VALUE at only £2.50. Post 70p.

600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600 watts of all lighting except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.

2000 WATT POWER CONTROL

For Power tools. Heating. Lighting etc. incorporating 13 amp. outlet and mains lead. £8.00 Post 27p.

METERS NEW! 2 1/2 in. FLUSH ROUND

available as D.C. Amps 1, 5, 10, 15 or A.C. Amps 1, 5, 10, 15, 20. Both types £2.50. Post 20p. VOLTMETER 0-300V A.C. £2.50. Post 20p.

VARIABLE VOLTAGE TRANSFORMERS

Carriage extra
INPUT 230 v. A.C. 50/60
OUTPUT VARIABLE 0/260 v. A.C.
BRAND NEW. All types.
200W (1 Amp) £10.00
0.5 KVA (Max. 2 1/2 Amp) £11.50
1 KVA (Max. 5 Amp) £16.50
2 KVA (Max. 10 Amp) £30.00
3 KVA (Max. 15 Amp) £33.00
4 KVA (Max. 20 Amp) £72.50
(Max. 37.5 Amp) £102.50
1 Amp OPEN TYPE
(Panel Mounting) £10.00

300 VA ISOLATING TRANSFORMER

115/230-230/230 volts. Screened. Primary two separate 0-115 volts for 115 or 230 volts. Secondary two 115 volts at 150 VA each for 115 or 230 volts output. Can be used in series or parallel connections. Fully tropicalised. Length 13.5 cm. Width 11 cm. Height 13.5 cm. Weight 15 lb. SPECIAL OFFER PRICE Only £5.00. Carr. 80p.

LT TRANSFORMERS

0, 6, 12 volt @ 10 amp. £5.60 Post 70p.
0, 10, 17, 18 volt @ 10 amp. £7.90 Post 70p.
0, 6, 12 volt @ 20 amp. £9.00 Post 70p.
0, 12, 24 volt @ 10 amp. £9.20 Post 70p.
0, 4, 6, 24, 32 volt @ 12 amp. £9.90 Post 70p.
0, 6, 12, 17, 18, 20 volt @ 20 amp. £10.40 Post 70p.
Other types to order at short notice—Phone your enquiries.

AUTO TRANSFORMERS

Step up step down 0-115/200/220/240 volts.
At 75 watt £2.64 Post 40p. 150 watt £3.50 Post 50p. 300 watt £6.20 Post 60p. 500 watt £9.20 Post 75p. 1000 watt £12.00 Post 90p.

20 r.p.m. GEARED MOTOR

230/240 volt 20 r.p.m. motor. £1.00 Post 15p.

9/12 VOLT DC GOVERNED REVERSIBLE MOTOR

Machine-cut gear train, giving final speed of 2 r.p.m., with cam driving 3 sub-miniature micro-switches (removable). Spindle 12mm long. 6mm dia. Built to PO spec, in heavy metal hinged case. £3.75 Post 40p.

BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle 38 amp.
(Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50 cycle 28 amp. The above two precision made U.S.A. motors are offered in as new condition. Input voltage of motor 115v A.C. Supplied complete with transformer for 230/240v A.C. input. Price, either type £6.25 Post 65p, or less transformer £3.75 Post 50p.
These motors are ideal for rotating aeriels, drawing curtains, display stands, vending machines, etc. etc.

BENDIX MAGNETIC CLUTCH

A superb example of Electro-mechanics! The main body is in two sections. The coil section is fixed and has a 3/8 in. sleeve. The drive section rotating on the outer perimeters. The uniting plate has 3/8 in. ID bearing concentric with main section and 18-tooth cog wheel. When energized transmission is extremely powerful. 24V d.c. at 240 MA. OUR PRICE JUST £2.50. Post 30p.

POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.
25 WATT 10, 25, 100, 150, 250, 500, 1k, 1.5k, 2.5k ohm. £1.70 Post 15p. 50 WATT 1, 5, 10, 25, 50, 100, 500, 1k ohm. £2.10 Post 20p. 100 WATT 1/10, 25/50/100/250/500/1k/1.5k/2.5k/5k ohm £3.30. Post 25p.
Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia brass bush. Ideal for above Rheostats, 22p ea.

TRIAC

Raychem Tag symmetrical Triac Type TAG 250/500V. 10 amp. 500 p.i.v. Glass passivated plastic triac. Swiss precision product for long-term reliability. £1.00 Post 10p. Incl. data and application sheet. Suitable Diac. 18p.

INSULATION TESTERS (NEW)

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L. 8 in., W. 4 in., H. 6 in., weight 6 lb.
500 VOLTS. 500 megohms £30.00. Post 80p.

VAT

All prices are subject to 8% VAT. (8p in the £)
To all orders add 8% VAT to total value of goods including carriage/packaging.

STROBE! STROBE! STROBE!

* FOUR EASY TO BUILD KITS USING XENON WHITE LIGHT FLASH TUBES, SOLID STATE TIMING + TRIGGERING CIRCUITS, PROVISION FOR EXTERNAL TRIGGERING. 230-250v. A.C. OPERATION.
* RANGE OF 4 STROBE KITS FROM STOCK.
* PRICES FROM £6.30-£22.00. SAE FOR DETAILS.

COLOUR WHEEL PROJECTOR

* Complete with oil filled colour wheel. 100 watt lamp.
* 200/240V A.C. Features extremely efficient optical system. £20.50. Post 80p.
* I R.P.M. MOTOR and COLOUR WHEEL
* 200/240 volt A.C. 1 r.p.m. motor, and wheel £5.60. Post 40p. (Motor not available separately.)
* Extra colour effect wheels from stock. SAE for details.



BIG BLACK LIGHT

* 400 Watt. Mercury vapour ultra violet lamp. Extremely compact and powerful source of U.V. Invulnerable industrial applications also ideal for stage display, discos etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £18.00. Post £1. Spare bulb £8.00. Post 40p.
* BLACK LIGHT FLUORESCENT U.V. TUBES
* 2ft. 20 watt £4.25. Post 40p. (For use in stan bi-pin fittings.) 1Mft. 12in. 8 watt £1.60. Post 25p. 9in. 6 watt £1.30. Post 25p. Complete ballast unit and holders for either 9" or 12" tube. £1.70. Post 25p. (9in. X 12in. measures approx.)

U.D.1. SINGLE CHANNEL. 750 watt MANUAL/AUTO DIMMER

* 750W Solid State Fader, with three functions. Manual fade; Auto fade-up; Auto fade-down. Automatic cycling up and down. Functions selected with 'three position' rocker switch. Two ranges of cycling for 'Flashing' or 'Slow blending'. Ready built module 6" X 3" glass fibre board incorporating 10 amp TRIAC. Two or more modules for top quality colour blending and flashing effects. PRICE £15.00. Post 45p.

50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering. No special tools required. The Kit includes Speaker, meter, Relay, transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound level Meter, 2 Transistor Radio, Amplifier etc. Price £7.75 Post 50p. (price including VAT & Post £8.91.)

'GENTS' 6" ALARM BELL

200/250 volt AC/DC. Brand New. Price: £5.00 Post 60p. (Illustrated)

'STC' 6" RED ALARM BELL

Brand New. Price: £4.00 Post 50p. 24/48V DC.

'FRACMO' 240VOLT A.C. 50 cycle SINGLE PHASE GEARED MOTOR

33 r.p.m. 30 lb. ins. Reversible, fitted with mounting feet. Brand New. £14.00. Post £1.00. (Total price incl. VAT £16.20.)

REVERSIBLE MOTOR

A.E.I. 1/10th h.p. reversible motor, 100/120V A.C., 50/60 cycle, 1400/1680 r.p.m. Flange fixing. Dia. 4" length 6 1/2" shaft 1" X 3/8". Price £2.50 Post 50p. Brand new. Suitable 110/240V 150 watt Auto Transformer, £3.50 Post 50p. (Post for both items together 75p.)

ROTARY VACUUM AIR COMPRESSOR AND PUMP

Carbon vane oil-less, 100/15V A.C., 1/12 h.p. motor. 50/60 cycle, 2875/3450 r.p.m. 20" vacuum. 1.25 c.f.m., 10 p.s.i. (approx figures). New unused surplus stock, with elect. connection data. Fraction of maker's price. £12.00 Post 50p. Suitable transformer as above.

240 V.A.C. SOLENOID OPERATED FLUID VALVE

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body, stainless steel core and spring. 1/2 in. b.s.p. inlet/outlet. Precision made. British mfg. PRICE: £2.00. Post 25p. NEW original packing.

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp single-pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time, from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm X 130 mm X 60 mm. Price £2.00. Post 40p. (Total incl. VAT & Post £2.59.)

PROGRAMME TIMERS

230/240 Volt A.C. 15 RPM Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays etc. Ex equipment tested, similar to illustration.
2 cam model £2.00 post 35p
4 cam model £2.50 post 35p
8 cam model £4.75 post 40p
8 cam model, each cam fully adjustable. 6 r.p.m. M.f.g. by Magnetic Devices. £7.50. Post 35p.

ALL MAIL ORDERS, ALSO CALLERS AT:

57 BRIDGMAN ROAD, CHISWICK, LONDON, W4 5BB. Phone: 01-995 1560. Closed Saturdays.

SHOWROOMS NOW OPEN AMPLE PARKING

PERSONAL CALLERS ONLY

9 LITTLE NEWPORT STREET, LONDON, WC2H 7J.J. Tel.: 01-437 0576

MAINS TRANSFORMERS

All standard to 230-250 volt primaries

1v	1 amp (special)	1.75
2.4v	5 amp	65
6.3v	2 amp	1.00
6.3v	3 amp	1.50
9v	1 amp	95
9v	3.5 amp	1.95
12v	2 amp	1.50
12v	1 amp	1.00
6.5-0-6.5v	3 amp	1.35
18v	1 amp	1.25
20v	1 amp	1.00
24v	1 amp	1.50
24v	3 amp	3.50
12-0-12v	50mA	1.20
8-0-8v	50mA	1.20
8-0-8v	1 amp	1.25
18-0-18v	2 amp	3.50
25v	1 1/2 amp	1.95
50v 2 amp & 6.3v	1 amp	5.50
60v 5 amp & 5v		
27v	8 amp	7.50
30v	37 amp	22.00
80v tapped 75v & 70v	4 amp	5.50
230v-60mA & 6.3v	1.5 amp	1.75
275-0-275v at 90mA & 6.4v	3 amp	2.25

Charger Transformers

6v and 12v	2 amp	1.25
6v and 12v	3 amp	2.25
6v and 12v	5 amp	3.50

HT Transformer 5kVA at 23mA (intermittent) 5.50

NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac XN.3. Price 99p each, 10 for £9.

OIL PUMP

Driven by Redmond Motor of approx. 1/20th horse power. Pump originally intended for oil-fired boilers etc. with normal inlet and outlet pipes and unions. £2.15 plus 30p post and insurance.

LIGHT DIMMER KIT

For dimming up to 150W without heat sink or 750W with heat sink. This comprises quadric variable control potentiometer, condenser, resistors, tag strip for mounting and data. Price £1.50.

RELAY BARGAIN

Type 600 relay, 2 changeover one open and one closed contact. Twin 500 ohm coils make this suitable for closing off DC 6v, DC 12v, DC 24v or AC mains using resistor and inductor. 33p each.

AM/FM TUNER


Unit made by the American GEC company, 8 transistor, all-wired ready to work. Complete with tuner condenser, needs only scale and pointer. Tunes AM range 540 to 1620 KHz. FM range 88 to 108 MHz. Switches for on-off and AFC. Output for MXP or direct. Special snip price £5 plus 30p post. Three or more post free.

7 WATT STEREO AMPLIFIER

Again by the American GEC company. This has exceptionally good tone quality. Is complete with pre-amp and treble base, volume and balance controls. Also has mains smoothing circuit and rectifiers so requires only mains transformer. Output for 15 ohm speakers. Inputs for tuner, pick-up, mike, etc. Special snip price £6 plus 30p post. Three or more post free.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips. Thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs. per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers probably over £20 each. Special snip price £8.50 plus 25p post and insurance. Don't miss this terrific bargain.

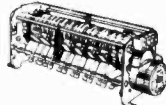

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in X 18in £1.90. 13in X 10in £1.50.

MULLARD UNILEX STEREO SYSTEM

There is no doubt that it is a good system, we believe that for the money it is without comparison. We demonstrate gladly at our Tamworth Road depot. Prices of the individual items for this:

- 1 Unilex Amplifier Ref. EP.9000 £1.75
- 1 Unilex Amplifier Ref. EP.9000 £1.75
- 1 Unilex Pre-Amp Ref. EP.9001 £2.00
- 1 Unilex Power Unit Ref. EP.9002 £2.50
- 1 Control panel kit with spun aluminium-faced knobs £3.80

Or the complete outfit—£11.50 post paid. Pair of 15 ohm speakers made by Goodmans are also available if required, price £3.30 the pair. No extra postage if ordered with the above, otherwise add 25p.



STEREO RADIO CABINET

Long, Low and Modern. Teak veneered with sliding front and tapered legs. Speaker spaces each end. Size approx. 4ft 2in X 13in X 15in. Probably cost over £20.00 to make. Our Price £8.10 each. Plus £1 per 100 miles carriage.

HORSTMANN 24-HOUR TIME SWITCH

With 6 position programmer. When fitted to hot water systems this could programme as follows:

Programme	Hot Water	Central Heating
0	Off	Off
1	Twice Daily	Off
2	All Day	Off
3	Twice Daily	Twice Daily
4	All Day	All Day
5	Continuously	Continuously

Suitable, of course, to programme other than central heating and hot water, for instance, programme upstairs and downstairs electric heating or heating and cooling or taped music and radio. In fact, there is no limit to the versatility of this Programmer. Mains operated. Size 3in X 3in X 2in deep. Price £4.35 as illustrated but less case.

TAPE DECK

In metal case with carrying handle, heavy fly wheel and capstan drive. Tape speed 3 1/2. Mains operated on metal platform with tape head and guide. Not new but in good order. Price £1.95 plus £1 post and insurance.

TERMS. ADD 8% V.A.T. Send postage where quoted—other items, post free if order for these items is £6, otherwise add 30p.

J. BULL (ELECTRICAL) LTD.
(Dept. W.W.)

102/3, TAMWORTH ROAD, CROYDON CR0 1XX

NEW ITEMS THIS MONTH

AC mains operated relay with single changeover 10 amp contacts. Open type single screw fixing through the base 50p each.

Battery condition testers. This is another item which has been out of stock temporarily but we are pleased to say, in stock again. Price now £3.50.

AM/FM tuning condenser as fitted to many Japanese and Hong Kong portables, this has two main tuning sections and four trimmers, approx size 1 1/4" X 1 1/4" X 1 1/4" 60p each.

Battery charger kit comprising a lead acid charger, 2 amp full wave rectifier and 2 amp meter suitable for charging 6v or 12v. Special bargain price £1.50 the kit + 30p post.

MacDonald record auto-changer with cueing arm and ceramic stereo cartridge. This is a very superior auto-changer and one we can thoroughly recommend. Limited quantity, special price £7.35 + £1 post and insurance. Plinth and cover the plinth has to be modified (very slightly) available, price £4.95 + £1 post, or if you buy both together you can get a discount of £1.

Instrument case measures 18" X 12" X 12". This is a very well-made case built on an angled framework, has rounded corners and edges. Into this framework fit the 8 panels. All panels are lacquered for ventilation, side panels are also fitted with handles, the bottom panel has 4 rubber feet. These instrument cases would probably cost around £15 each. We have approx. 100, not new but in very good condition and offer them at £3 each.

Laboratory volt meter, BS1. This is the conventional square case, size 7" X 7" X 3 1/2". This is a leather carrying handle and rubber feet for horizontal and vertical standing. The meter is intended for horizontal use on the bench and has a mirrored scale. Hefty terminals along the top select the 3 ranges 0-150v, 0-300v and 0-600v DC. Price £6 + £1 post and insurance.

Laboratory amp meter, companion instrument to the above but to read 0-20 amps 50 cycles. £5 + £1 post and insurance.

Soil heating transformer, 4v, 5v or 6v output, very heavy duty secondary rated at 250 amps, price £20 + carriage £2 first 100 miles then £1 per 100 miles extra.

7 watt stereo/mono amplifier with usual switching and controls, in attractive teak style case. £3.

3 core lead, 7' 8" long, ribbed, virtually non-kinkable 23/36 conductors, so OK for 8 amps. Price 10p each.

0-1 mA meter 2 1/2" square. Flush mounting. English make ex equipment but perfect. £1.75.

0-100 microamp meter, as the above, but £2.25.

Solenoid 4-6v, size approx. 1 1/2" X 1" X 0.4" thick twin coils give excellent pull. Mounted in frame but easily removable from this frame, fitted with lever giving approx. 0.4" push or pull. Price 30p each.

Cold cathode tube Swiss made "Elasta" type No. ER 12A. We have no technical information on this tube and if any reader has this we will be obliged for any information. Price of the tubes 30p each.

Push switch, double pole changeover contacts rated at 10 amps 250 volts with plenty of applications. Offered plastic body, snap fitting into a hole size 1 1/2" X 1/2". Dipped at only a fraction of its proper price, namely 20p each.

Dimmer but single pole changeover, fits into a hole size 1" X 1/2". Price 15p each.

(Note: the two switches above do not require a knob as they have a finished and tapered plunger.)

Dimmer, but dished knob. 10p extra with knob.

Samson's
(ELECTRONICS) LTD.
9 & 10 CHAPEL ST., LONDON, N.W.1
01-723 7851 01-262 5125
ADJACENT TO EDGWARE ROAD MET. LINE STATION

CURRENT RANGE OF NEW L.T. TRANSFORMERS FULLY SHROUDED TERMINAL BLOCK CONNECTIONS ALL PRIMARIES 220/240v

Type	Sec. Taps	Amps	Price	Postage
1A	25-33-40-50v	15	£14.00	75p
1B	25-33-40-50v	10	£12.00	75p
1C	25-33-40-50v	6	£8.50	60p
1D	25-33-40-50v	3	£7.50	60p
2A	4-16-24-32v	12	£10.00	75p
2B	4-16-24-32v	8	£8.00	60p
2C	4-16-24-32v	4	£4.95	45p
2D	4-16-24-32v	2	£3.50	40p
3A	24-30-36v	10	£9.00	60p
3B	24-30-36v	5	£7.50	50p
3C	24-30-36v	2	£4.50	40p
4A	12-20-24v	20	£12.00	75p
4B	12-20-24v	10	£7.50	60p
4C	12-20-24v	5	£4.95	40p
5A	3-12-18v	20	£10.00	60p
5B	3-12-18v	10	£6.95	60p
5C	3-12-18v	5	£4.50	40p
6A	48-56-60v	2	£4.50	40p
6B	48-56-60v	1	£3.50	40p
7A	6-12v	20	£7.90	60p
7B	6-12v	10	£4.50	40p
7C	6-12v	5	£3.50	40p
8A	17-32v	8	£8.00	60p
9A	12-24v	1	£2.50	30p
10A	9-15v	2	£2.50	30p
11A	8-0-8v	2	£2.50	30p

PLEASE ADD 8% V.A.T.

HEAVY DUTY UNSHROUDED TYPES 9 INCH FLYING LEADS ALL PRIMARIES 240v.

Type No.	Sec. Volt Tap.	Amps.	Price	Carr.
1	24-30-36	20	£15.75	£1.25
2	12-20-24	30	£15.75	£1.25
3	3-12-18	30	£15.75	£1.25
4	6-12	50	£15.75	£1.25

TRANSFORMERS FOR LINSLEY HOOD AMPLIFIERS

Fully shrouded, terminal block connections. Pri. 220-240v. Screen tap. Sec. 30-25-0-25-30v., 2 amps. £4.75, carr. 40p. Heavy duty type 36-25-0-25-36v. 5 amps. £9.75, carr. 50p.

STEP DOWN 240/110v AUTO TRANSFORMERS

3000 watts. Built into steel case with two American 2 pin grounded socket outlets. Carry handle, 6 ft. mains lead. £29.50, carr. £2. Without case and fittings £22.00, carr. £1.50.

Other Types Available. 80-1500 watts, fully shrouded, with American socket outlet and 6 ft. mains lead. Let us know your requirements. Lists available.

PARMEKO OIL FILLED POTTED H.T. TRANSFORMERS

No. 1, Pri. 115-220-230v. Sec. 400-0-400v. 400 M/A. £5.75, Carr. £1. No. 2, Pri. 115-220-230v. Sec. 350-0-350v. 200 M/A. 6.3v. 6A., 5v. 3A. £4.50, Carr. 75p. No. 3, Pri. 115-220-230v. Sec. 330-0-330v. 200 M/A. 6.3v. 6A., 5v. 3A. £4.90, Carr. 75p. No. 4, Pri. 200-220-240v. Sec. 250-0-250v. 320 M/A. 6.3v. 10A. £4.50, Carr. £1.00. No. 5, Pri. 115-220-240v. Sec. 187.5v. 60 M/A. and 500v. 31 M/A. £4.95, Carr. £1.00.

HT TRANSFORMERS BY FAMOUS MAKERS

No. 1, Pri. 110-210-230-250v. Sec. 230v. 200 M/A. and 6.3v. 7A. Potted type, £3.90, Carr. 50p. No. 2, Pri. 110-220-240v. Sec. 250v. 80 M/A. 15v. 12A., 6.3v. 4.5A. Open type table top connections. £2.25, Carr. 35p. No. 3, Pri. 220-240v. Sec. 250-0-250v. 75 M/A., 6.3v. 3A. £1.75, Carr. 35p. No. 4, Pri. 110-220-240v. Sec. 70v. 1A. and 30v. 1A. Separate windings, potted type. £3.75, Carr. 50p. No. 5, Pri. 220-240v. Sec. 140v. 195v. 6.3v. CT 1.25A. and 50v. 1A. £3.50 Carr. 50p. No. 7, Pri. 220-230-240v. Sec. 175v. 5 M/A. 400-100-0-100-400v. 120 M/A. 6.3v. 8A., 4v. 1A., 4v. 2A. Fully shrouded terminal block connections. £6.50, Carr. £1. No. 8, Pri. 230v. Sec. 125-0-125v. 100 M/A. "C" Core type. £20.0. P.P. 35p. No. 9, Pri. 220-240v. Sec. 250-0-250v. 50 M/A. 6.3v. 1A, 6/3v, 0.6A, 6.3v. 0/7A. "C" core type. £2/25 P.P. 35p.

PARMEKO L.T. TRANSFORMERS

Open types, Pri. 110-220-240v. Sec. 30v 5-5 amps and 12v. 2.2 amps. Table top connections. £4.95, P.P. 75p. Pri. 240v. Sec. 26v. 10 amps and 12v. 0.1 amps. Table top connections. £5.50, P.P. 75p. Potted types, Pri. 115-230v. Sec. 24-30-36v. 2 amps. £2.75, P.P. 35p. Pri. 220-240v. Sec. 50v. 0.4 amps. £1.50, P.P. 35p. Pri. 115-220-230v. Sec. 6-6v. 6A. twice, and 5v. 6A. The following outputs can be obtained from this transformer: 6-6v. 6A., 6-6v. 6A., 5v. 1A., 13-6v. 6A., 5v. 2A., 6-6v. 12A., 6v. 11-6v. 6A., 18-2v. 6A. Potted type: £4.95, Carr. 75p. Pri. 220-240v. Sec. 24-0-24v. 470 M/A., 150v. 15 M/A., 4-5v. 1A. Potted type £2.00, P.P. 35p.

GARDNERS C CORE L.T. TRANSFORMERS

Table top connections. Primaries 200-220-240v. No. 1. Size 2.5-0-2.5v. 42 amp. £4.50, P.P. 70p. No. 2. 25v 10 amps and 2.5v 5amps twice. £3.50, P.P. 60p. No. 3. 24v 3 amps. £3.00, P.P. 40p. No. 4. 25-0-25v. 15A/M/A and 7v. 1.35 amps. £1.75, P.P. 25p. No. 5. 36v 350 M/A. £1.00 P.P. 25p. No. 6. 75v. tapped at 36v. 0.6 amp. £2.50, P.P. 35p. No. 7. 35p. No. 8. 4.2v. 1 amp. 75p. P.P. 25p.

GRESHAM MULTI TAPPED L.T. TRANSFORMERS

Pri. 110-220-240v. Sec. 21-22-23-27-28-30v 10a and 23-24-26v. 2.5a. Twice and 15-16-18v 15a Twice and 25-0-25v. m/a three times. C. core type. Table top connections £10.00, carr. £1.00.

GEC L.T. TRANSFORMERS

Pri. 220-240v. Sec. tapped. 51-61-65-67-69v. 10A. Unshrouded terminal block connections. £8/75, Carr. £1/25. Pri. 220-240v. Sec. tapped 58-63-69-74v. 3A. £3/75, Carr. 75p.

GARDNERS HEAVY DUTY TRANSFORMER

Pri. 240v. Sec. 50v. 20A. Very conservatively rated, unshrouded terminal block connections size 9x8x8 inches. £17.50, Carr. £2.00. Hoden, Pri. 110-220-230-240v. Sec. tapped 27-30-33v. 10A. £7.50, Carr. £1.

HOWELLS 'C' CORE TRANSFORMERS

Pri. 200-220-240v. Sec. 18-0-18v. 12-5A. Very conservatively rated, table top connections. £10.00, Carr. £2. Pri. 230v. Sec. 1.25-0-1.25v. 10A. £2.00, P.P. 35p. Siemens, Pri. 115-220-240v. Sec. 18v. 2A. twice. Unshrouded terminal block connections. £3.00, P.P. 35p.

GRESHAM E.M.T. TRANSFORMERS

Pri. 240v. Sec. 2300 M/A. 6.3v. 1.5A. Table top connections. Size. 5 3/4" X 3 1/2" ins. £3.00, Carr. 50p.

L.T. SMOOTHING CHOKES

By famous makers. 'C' Core types. 10 M/H. 25A. £8.75, Carr. £1.00. 140 M/H. 5A. £3.00, P.P. 75p. Potted types, 100 M/H. 2A. £3.00, Carr. 60p. 130 M/H. 1.5A. £1.25, P.P. 35p. Unshrouded types, terminal block connections. 150 M/H. 3A. £3.00, P.P. 60p. 4/8 M/H. 10A. £3.00, P.P. 60p. Swinging types. C core. 7.5 M/H 6A-75 M/H 0.5A £3.75, P.P. 50p. 10 M/H 4A-100 M/H 0.5A open type £2.50, P.P. 25p. 50 M/H 5A-100 M/H 0.5A C core £2.25, P.P. 35p.

LEMAR L.T. TRANSFORMERS

Pri. 240v. 16-0-16v. 2.5A. 24v. 630 m/a twice. 24v. 65 m/a and 115v. 2a. auto tap on primary. Open frame table top connections £3.50, carr. 50p. Pri. 240v. Sec. 20-0-20 1/2 v. 5-0-5 1/2 v. £1.75, carr. 35p. All above transformers have a screen winding. Pri. 220-240v. Sec. 56v. CT. 10a. Shrouded terminal block connections. £8.50, carr. 75p.

AIR CONTROL LTD AIR BLOWERS

50-50v D.C. HP. 1400 RPM. 6000 cont. rating. Size of motor 4x2 1/2 ins. Cowling 5 ins. dia. Outlet 1 1/2 x 1 1/2 ins. £2.50 carr. 45p.

PLEASE ADD 8% VAT TO ALL ORDERS INCL. CARR.

H.T. SMOOTHING CHOKES

GARDNER 'C' core types. 10H 250 M/A £2.00, post. 40p. 20H 180 M/A £2.00, post. 40p. 12H 100 M/A 85p, post. 25p. 50H 25 M/A £2.00, post. 40p. PARMEKO Potted type: 10H 180 M/A £2.00, post. 40p. 5-2H 350 M/A £2.50, post. 50p. 10H 300 M/A £2.50, post. 50p. 100 M/A 75p, post. 25p. 50H 25 M/A 75p, post. 25p. 50H 25 M/A 75p, 25p.

GENTS ALARM BELLS

6 volt DC 8 inch dia. Gong. Overall size 4 1/2 x 6 inches. £3.90, P.P. 50p.

MOTOR START CAPACITORS TUBULAR TYPES

4 MFD 250v AC. 2.6 MFD 500v DC. 2.5 MFD 360v AC. 2.2 MFD 250v AC. All at 50p, P.P. 10p. Eire Miniature 2.2 MFD 400v Size 1 1/2 x 1 1/2 inches. 50p post paid. TCC 8 MFD 800v DC WKG electrolytics 75p, P.P. 15p.

ITT LEVER SWITCHES

Type 801 AAO 72-42 A CO switches, overall size 1 1/2 x 2 1/2 ins. White lever gold flash contacts, 60p. Three for £1.50, post paid.

PLESSEY MINIATURE MICRO SWITCHES

Type LIC 7134. One CO one break. Gold flash contacts. Size 1 1/4 x

TEST EQUIPMENT

Fantastic DUAL BEAM DC-6MHz GENERAL PURPOSE PORTABLE OSCILLOSCOPE As used by H.M. Forces OSCILLOSCOPE CT436

Commercial Designation Solartron CD1014 General Purpose Dual Beam DC6MHz flat faced double gun cathode ray tube operating at 1.6kV. The time base velocity is continuously variable between 1cm/usec. and 1cm/sec. TIME BASE Free running or triggered from positive or negative pulses. Sweep speed 1cm/usec to 1cm/sec.

Synchronisation: positive or negative going internal from either channel or external continuous waves. Internal 3mm P/P.

External 100mV/P. Sensitivity 100mV/cm; maximum on Y2 amplifier 1mV/cm. Size: 9 1/2" x 11 1/2" x 15". Wt. 25lb. PRICE: £79.50. Solartron 1014 £85.

ADD 8% VAT TO ALL PRICES

MISCELLANEOUS TEST EQUIPMENT SAMPLE OF OUR EXTENSIVE RANGES

UHF ATTENUATOR MARCONI INSTRUMENTS TF21635 0-142dB in 1dB steps. 50Ω Impedance DC-16GHz. £125

ELECTROLYTIC CAPACITOR BRIDGE BY B.P.L. Type CB 154-D. 0.2µF-22,000µF at 50Hz P.O.A. £235

DIGITAL VOLTMETER SOLARTRON LM1420.2 2.5µV-1KV in 6 ranges. 0.05% DC accuracy. £235


VHF ALIGNMENT SCOPE MARCONI TF1104 RF41-68MHz, 80-110MHz, 150-216MHz. IF10-40MHz, VF5KHz-10MHz. Output (Nom) 100µV-100mV. Sweep Width 500KHz-10MHz Variable. £150

DOUBLE PULSE GENERATOR MARCONI TF1400/S Ministry type CT434. CW Secondary Pulse Generator plug in TM6600. 10Hz-100KHz. 100nsec-100µsec. Negative pulses up to 200V EMF. +VE pulses up to 60V EMF and simultaneous +VE and -VE pulses up to 20V EMF. £100

TRANSFER OSCILLATOR BECKMAN 7580H DC-15GHz with counter. 7.5MHz-15GHz without counter. Sensitivity 100mV (RMS). £295

DISTORTION FACTOR METER MARCONI TF142F Fundamental frequency range 10Hz-8KHz. Distortion measurement ranges 0-5% and 0-50% £80

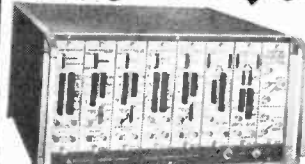SPECIAL PURCHASE OF ADVANCE EX-DEMONSTRATION TEST EQUIPMENT



MODULAR PULSE GENERATOR PG56

P1 Clock Gen. P2 Width or Delay, PL P2, P3 P3 Outputs, P5 Variable Slope. Complete switched decade steps. Delay 25nS to 1S in switched decade steps. Output up to 20V in 500 Ohms. Variable slope-rise and fall rates 1nS/V to 100mV independently adjustable over 10:1 range. Double pulse output. Short circuit protection. PRICE £275

ADVANCE PG 56 DOUBLE PULSE GENERATOR


Independently variable 2Hz-3MHz pulse width. Delay 70nS-0.2 secs in 19 steps. Rise time better than 10nS. External trigger and internal rate generator. PRICE £120

Advance T.V. Dot and Cross Hatch Generator SG73

Output in form of modulated signal at VHF and UHF at level suitable for aerial sockets of (MOD). Band IV & V On Harmonics (-MOD). Modulation 405 Lines or 625 Lines. Ex-Demonstration, Brand New. SPECIAL OFFER THIS MONTH ONLY £29.50

ALPHANUMERIC NIXIE TUBES B7971

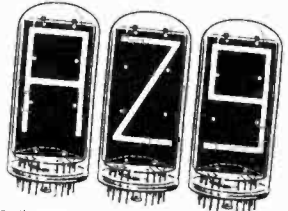The Alphanumeric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube.



From the standpoint of both readability and electrical characteristics, the Alphanumeric NIXIE tube provides many unique benefits including:
 * 170V-21mA * All DC operation
 * Uniform, continuous line characters of equal height
 * Memory with simple solid state drive circuits
 * Readability in high ambient light... 200 footcandle brightness * Long life with no loss of brightness
 * Character height 2 1/4 ins.

Price only 99p each plus 16p Bases for above 60p each DISCOUNT GIVEN FOR QUANTITY ORDER

JUST ARRIVED IN NUMERIC INDICATOR TUBES ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V D.C. Current 14mA. Pulse duration 100µs. Character height 0.51. Overall size manufacturers requirements. Type B5853st. Price 1-25 £1.00. 25+ 90p. 100+ 80p. 1000+ price on application.

THE REVOLUTIONARY SUPERTESTER 680R

FOUR INTERNATIONAL PATENTS - SENSITIVITY 20,000 Ohms per Volt 10 FIELDS OF MEASUREMENT AND 80 RANGES. ACCURACY 1% in D.C. 2% in A.C.

OUTSTANDING FEATURES:
 • Fully screened against external magnetic fields
 • 20,000 Ohms per Volt sensitivity (128 x 95 x 32mm)
 • Accuracy and stability
 • Scale width and small case dimensions
 • Simplicity and ease of use and readability (1% in D.C., 2% in A.C.) of indicated readings
 • Printed circuit board, is removable
 • Full range of accessories • 1,000 times overload
 • VOLTS A.C. = 11 ranges: without de-soldering • More ranges than any other meter. VOLTS D.C. = 4-20-100-500 and 2000 Volts
 • 4-20-100-500 and 2000 Volts
 • 200 mV-4V-20-100-400 and 100µA-1 2-10-50-250-1000-2500. Volts and 50µA-500µA-5 mA-50 mA-500 mA-50 mA-25 mA-250 mA-10 mA-100 mA-1 Amp and 10 Amp. AMP. A.C. = 10 ranges: 250µA-2.5 mA-5 mA-25 mA-50 mA-2.5 Amp and 500µA-5 mA-50 mA-500 mA-5 Amp. OHMS REACTANCE = 6 ranges: x1-x10-x100-x1000-x0.000 and Low Ohms. DETECTOR = 1 range: from 0 to 10 Megohms. FREQUENCY = 2 ranges: from 0 to 500 and from 0 to 5000Hz. V. OUTPUT VOLTAGE = 9 ranges: 10-50-250-1000-2500 from 0 to 50,000 and from 0 to 500,000 pF using the mains and from 0 to 20, from 0 to 200, from 0 to 2,000 and from 0 to 20,000 Micro farad using the incorporated 3 Volts battery. Bold figures indicate depress button.

THESE ACCESSORIES CAN BE USED IN CONJUNCTION WITH THE SUPERTESTER 680R AND MICROTTESTER 80

Signal Injector
 Producing 1KHz and 500 KHz signals for circuit testing. £5.95

Gauss Meter
 For measuring magnetic field strengths. £11.95

Transistor Tester
 For transistors and diodes. £11.95

Electronic Voltmeter
 Input resistance of 11Mohms for d.c. and 1.6Mohms shunted by 10pF for a.c. £24.00

Amperclamp
 For measuring a.c. currents from 250mA to 500 amps. £11.95

Temperature Probe
 Covering the range -50 to +200°C £11.95

Phase Sequence Indicator
 To indicate the phase sequence of a 3 phase supply. £5.95

OTHER ACCESSORIES AVAILABLE: LIGHT METER £11.95. RESISTOR MULTIPLIER £9.95. SHUNTS D.C. 25, 50 and 100 amps. £4.50 each. CURRENT TRANSFORMERS A.C. 25 and 100 amps. £7.00 each. E.H.T. PROBE Extends D.C. voltage to 25,000V. £5.95.



£18.50 with shockproof case

SPECIAL OFFER OF COLOUR T.V. AND F.M. MEASURING EQUIPMENT BY WANDEL AND GOLTERMANN

VZM1 Measuring set for measuring phase and amplitude modulation distortion for Colour T.V. Sub carrier (PAL Systems) £495.00

VZM2 Measuring set for measuring phase and amplitude modulation distortion for Multichannel FM radio systems with base bands up to 12 Mc/s. £295.00

VZM83 Generator and Receiver used to measure transmission distortion on FM radio link systems. Superimposed signal 52/304/55KHz. £275.00

PROGRAMME BOARDS BY SEAELECTRO
 These boards are basically a multi-pole multi-throw switch device consisting of a X-Y Matrix with two contact decks in the Z Plane running at 90 degrees to each other. Contact is made by either, shorting or plugging in pins. Ideal for prototype work, etc. Boards available in 2 planes. 24 x 50 £29. 20 x 11 £15. Pins now available at 15p each.

Stop Press

AMPEX SP-300 FM/DIRECT RECORDER/REPRODUCER 4 Channels. Speed 1 1/2, 3 1/2, 7 1/2 ips. Flutter 0.15% at 151 ips. Frequency Response: Instrumentation 50Hz to 40KHz at 15 ips. Audio 50Hz to 18KHz at 15 ips. £1950



SPECIAL OFFER OF TELEPHONE CARRIER TEST EQUIPMENT

An unusual offer of a system up to 15 Mc/s for the measurement of level attenuation on telephone carrier equipment and wide band radio relay systems.

SIEMENS sweep frequency system consisting of: 3W518 Level Oscillator 10 Kc/s-17 Mc/s; 3D335 Level Selective Meter 10 Kc/s-17 Mc/s; 3W933Sweep Attachment; 3D346 Large Screen Level Tracing Receiver. Offered as a complete system as a 32M701. Special Offer less than Half-Price. £1950.00

Enquire for individual items P.O.A. Also available manual point to point system consisting of: 3W518 Selective Level Oscillator 10 Kc/s-17 Mc/s; 3D335 Selective Level Meter 10 Kc/s-17 Mc/s

Price Per Pair £950.00

Cossor CDU 150 (CT531) DC 35MHz 5mV/cm Sensitivity fully transistorised P.O.A.

FANTASTIC NEW MICROTTEST 80

MEASURES ONLY 90x70x18mm AMAZING VALUE

at £11.95

8 fields of measurement and 40 ranges
 • 20,000 ohm per volt sensitivity • 1000 times overload (on the ohmic ranges only) • Scale board is removable without soldering • Fully screened against external magnetic fields • Fully indicated reading <2% in A.C.-D.C.> • Full and ease of use and readability
Volts D.C. 6 ranges: 100mV-2V-10V-50V-200V-1000V. (20kΩ/V). **Volts A.C. 5 ranges:** 1.5V-10V-50V-250V-1000V. (4kΩ/V). **Ohms 4 ranges:** 250Ω-2.5kΩ-25kΩ-250kΩ. **Amp. A.C. 5 ranges:** 500µA-5mA-50mA-500µA-5mA-50mA. **Ohms 4 ranges:** Low-Ω-X1-1000Ω. **Output 5 ranges:** 1.5V-10V-50V-250V-250µF-2500µF-25,000µF. **Capacity 4 ranges:** 25µF-



BURMAN

LIMITED QUANTITY
 Made to meet the most stringent Government Service Standards

DC-40MHz DUAL TRACE



Solatron C.T.484 oscilloscope. 3% accuracy. Dual Trace Displays.

DUAL TRACE Y AMPLIFIER. Bandwidth: D.C.-24 Mc/s. Rise Time: 14 nanosecs. Input Impedance: 50 mV/cm. Measuring Accuracy: ±5% 1 M.ohm 26pF. Measuring Accuracy: ±5% direct. ±3% with calibrator.

TIME BASE. 100 nanosecs/cm-5 secs/cm or continuously variable up to 12 secs/cm. Sweep expansion X 5. Accuracy: ±3%.

X AMPLIFIER. Bandwidth: D.C.-150 Kc/s. Sensitivity: 200 mV/cm and 1 V/cm. Input Impedance: 1 M.ohm 40 pF.

INTERNAL CALIBRATOR. Accuracy: ±3%.

WIDE BAND Y AMPLIFIER PLUG ALSO AVAILABLE: Bandwidth: D.C.-40 Mc/s. Rise Time: 8 nanosecs. Sensitivity: 50 mV/cm. Input Impedance: 1M.ohm 22pF Measuring Accuracy: ±5% direct. ±3% with calibrator. P.O.A.

£149.50

HERE! NOW! FOR IMMEDIATE DELIVERY!



AVO'S
 Fully tested and checked, guaranteed 12 months with one free calibration. Inc.batts. Test Set No.1 panamic Avometer similar to specification as model 9. **£42**

7X £28 8X £38
 Leads extra

Ever-ready case enables the meter to be used while in its case £5
 *Please note: X stands for fully tropicalised, splash-proof and mu-metal shield.

FABULOUS RANGE OF SIGNAL GENERATORS

H.P. VHF Signal Gen. 608B
 10MHz to 400MHz **£175**

H.P. UHF Signal Gen. 612A
 450MHz to 1250MHz **£495**

H.P. UHF Signal Gen. 614A
 800MHz to 2100MHz **£225**

H.P. Sweep Oscillator 693D
 4GHz to 8GHz **£450**

801B.3 **£155**

TF801D Series **£275**

General Radio UHF Unit Oscillator + PSU 250MHz to 960MHz p.o.a.
 Marconi PHM/AM Signal Generator TF2003 400KHz to 12.5MHz p.o.a.


Marconi 801A as is **£25.00**
CALLERS ONLY. NO GUARANTEE

NEW TOUCHLESS RETRO-REFLECTIVE TACHOMETER

FEATURES

- Reads RPM from as far as 24" away!
- Four ranges: 0-1,000, 3,000, 10,000, 30,000 RPM*
- Instant field calibration
- Reads low or high speed on any type of machinery
- Battery powered—built-in voltage checker
- "Touchless" (no torque loss) measurements
- Direct reading, mirror type scale
- Hand portable (only 32 oz.) (0.9 kg)
- Accuracy: 1 1/2% if full scale
- Aluminium case—baked enamel finish
- Reads on marked shafts as small as 1/16 dia.
- Marking tape provided
- Complete solid-state circuitry
- Push-button reading
- Hidden probe cable, extends to 24" (60cm)

ONLY £89.50

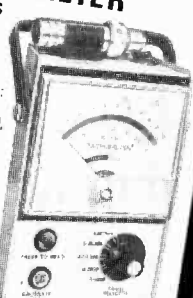


6V 25A Power Supplies

10% VARIABLE VOLTAGE HIGH CURRENT HIGH STABILITY HIGH RELIABILITY

These power supplies were designed for continuous operation in computer equipment. Manufactured to highest engineering standard for long-term reliability and stability. Independent voltage and current meters. Core Transformer. Manufacturer's price probably in excess of £200.

£25



MULTI OUTPUT POWER SUPPLIES
 Ex-Computer offered at mere fraction of original manufacturer's cost.

APT 13334 Mk III
 Input 200/240V. +10V -5Amp. -10V -2Amp. +24V -2Amp. +20V -5Amp. -20V -2Amp. **PRICE £19.50**



Advances DC197
 6V 7.5Amp. 6V 11Amp. 28V 9Amp. **PRICE £35**

BRAND NEW MINIATURISED STRIP CHART RECORDER BY RUSTRAK Model 88

This recorder indicates the magnitude of applied currents of voltages by a continuous distortion free line on pressure sensitive paper. Moving coil movement scale calibrated 1 milliamper D.C. internal resistance 100 ohms. Chart Drive motor 240V 50Hz. Chart speeds 90" per hour **£39** 1" per hour **£45** or 6" or 12".

SINGLE PEN RECORDER by Record Electrical
 3" chart sensitivity 1 millamp chart speed 1 and 6" per hr. Size 8" X 11" X 6". Offered complete with pen assembly. Listed at over £120—this month's special price due to bulk purchase.

1mA version £50
500µA version £60

Potentiometers

TEN TURN 360° ROTATION

Res Ohms	Linearity	Manufacturers	Model	Price
50	0.5	Beckman	AR/S	£2.25
100	0.5	Beckman	A.S.	£2.00
200	0.5	Beckman	A	£2.00
500	0.1	Beckman	S	£2.50
500	1.0	Relcon	HEL107-10	£2.25
2K	0.5	Beckman	SA1101	£3.00
2K	0.25	Beckman	7218	£3.00
2K		Reliance	GPM15	£2.00
2K		Central Controls	GPA15/4	£2.00
5K		Relcon	07-10	£2.50
5K		Colvern	CLR2503	£3.00
10K	0-1	Beckman X	A	£3.50
15K		Colvern	CLR2402	£3.00
25K	0.5	Beckman	SA1337	£3.00
30K	0.1	Beckman	A.88	£3.50
30K	0.5	Beckman	SA1892	£3.00
50K		Reliance	07-10	£2.25
50K		Beckman	07-5	£2.25
50K	0.5	Beckman	A	£3.00
100K	0.1	Beckman	A	£3.50
100K		Colvern	2501	£2.25

THREE TURN 780° ROTATION
 100/100 Beckman Type C £3.00

FIFTEEN TURN 5400° ROTATION
 25K/25K Beckman B 10 watts £6.50
 46K/46K Beckman B 10 watts £6.50

FANTASTIC BUYS IN PEN RECORDERS

10 CHANNEL EVENT RECORDER
 Response time 100 milliseconds. Chart width 110mm. Chart length 50ft. Inv. capacity 72 hours. Chart speeds 20-60-180-600-1800-5400 mm/hour. Size 160 X 160 X 255mm. Weight 9 lbs. Price complete with accessories. **£52.00**

HIGH SPEED PEN RECORDER
 Chart length 175 ft. Footage indicator. Width of recording channel 60mm. Chart speeds (selected by push buttons) 1.2-6-12-30-60-120-300-600-3000mm per minute. Full deflection current 8mA. Internal impedance 210 ohms. External impedance 800 ohms. Dimensions 320 X 340 X 175mm. Weight 35 lbs. Price complete with accessories.

PORTABLE AC/DC RECORDING VOLTMMETER
 Fitted with separate zero-marking pen. Accuracy 1.5% DC, 2.5% AC. Measurements ranges—AC and DC: 5-15-50-150-250-500mA 1.5-5 Amps 5-15-50-150-250-500V. DC only 150mV. Frequency range 45 to 1000 c/s. Chart width 100mm. Chart speeds 20-60-180-600-1800-5400 mm/hour. Price complete with accessories. **£78.00**

MINIATURE PEN RECORDER
 Chart width 80mm. Chart length 40ft. Chart speeds: Slow 20-60-180 mm/hour. Fast 600-1800-5400 mm/hour. Dimensions 120 X 120 X 285mm. Weight 7.7 lbs. (3.5 kg). Price complete with accessories. **£39.00**








AC CLAMP VOLTAMMETER
 Clamp-on Voltammeter is used for measurements of AC voltages and currents without breaking circuits.

Specification
 Measurement ranges:—Current 10-25-100-250-500 Amps. Voltage 300, 600 V. Accuracy 4%. Scale length 60mm. Overall dimensions 283 X 94 X 36mm. Weight 1.5 lbs.

£12.50

Combined Stroboscope-Tachometer. 200 to 6000 flashes per minute. 200 to 6000 r.p.m. Accuracy 3% or better. Beam angle 80°. Flash Duration: 10 to 25 microseconds. Light colour Xenon white 500°. Compact lightweight (27 oz.) easy to use one/off and on switch.

Carriage and packing charge extra on all items unless otherwise stated. Please note: all instruments offered are second-hand and tested and guaranteed 12 months unless otherwise stated. NEW CATALOGUE AVAILABLE EARLY IN THE NEW YEAR. WRITE IF YOU WISH TO RECEIVE A COPY. ADD 8% VAT TO ALL PRICES

ELECTRONIC BROKERS LIMITED

49-53 Pancras Road, London NW1 2QB. Telephone 01-837 7781

PROMPT DESPATCH MAIL ORDER. CALLERS WELCOME MON-FRI 9 A.M. to 5.30 P.M.

The largest selection

BIB HI-FI ACCESSORIES



De Luxe Groov-Kleen
Model 42 £1-95
Chrome Finish
Model 60 £1-50

Ref. B. Stylus and Turntable Cleaning Kit 34p
 Ref. 36A. Record/Stylus Cleaning Kit 23p
 Ref. 43. Record Care Kit £2-42
 Ref. 31. Cassette Head Cleaner 58p
 Ref. 32. Tape editing Kit £1-68
 Model 9. Wire Stripper/Cutter 93p

Ref. P. Hi-Fi Cleaner 31p
 Ref. 32A. Stylus Balance £1-37
 Ref. J. Tape Head Cleaning Kit 62p
 Ref. 56. Hi-Fi Stereo Hints & Tips 42p

EX-COMPUTER STABILISED POWER MODULES
 complete with circuit diagrams, etc., 99p each 22p p & p.

LOW COST CAPACITORS
 .01 µF 40V 3p each 3p each
 500 µF 50V Elect. 10p each

DECON-DALO 33pC Marker
 Etch resistant printed circuit marker pen 99p each

VEROBOARDS
 Packs containing approx., 50sq. ins. various sizes, all 0-1 matric 55p

REPANCO CHOKES & COILS
 RF Chokes
 CH1. 2.5mH 29p CH2. 5.0mH 30p
 CH3. 7.5mH 31p CH4. 10mH 33p
 CH5. 1.5mH 28p

COILS
 DRX1 Crystal set 31p DR2 Dual range 45p

COIL FORMERS & CORES
 NORMAN 1" Cores & Formers 5p
 1/2" Cores & Formers 10p

SWITCHES
 DP/DT Toggle 36p SP/ST Toggle 30p

FUSES
 1" and 20mm, 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A QUICK-BLOW 5p ea.

EARPHONES
 Crystal 2.5mm plug 42p
 Crystal 3.5mm plug 45p
 8 ohms 2.5mm plug 25p
 8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES
 B123. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1-85

3-WAY STEREO HEADPHONE JUNCTION BOX
 H1012 £1-87

2-WAY CROSSOVER NETWORK
 K4007. 80 ohms Imp. Insertion loss 3dB £1-21

TRANSISTOR EQUIVALENT BOOK 9th EDITION
 256 pages of cross references and equivalents for European, American and Japanese transistors. Approximately 9,000 types with more than 56,000 substitutes have been included. The tables were compiled with the utmost care from manufacturers own specifications. The most comprehensive Equivalents Book on the market today!
ONLY £2-30

INSTRUMENT CASES



(Black Vinyl covered)
 No. Length Width Height Price
 BV1 5" x 6 1/2" x 2" £1-35
 BV2 11" x 6" x 3" £1-75

ALUMINIUM BOXES

BA1	5 1/2"	x	2 1/2"	x	1 1/2"	49p
BA2	4"	x	4"	x	1 1/2"	49p
BA3	4"	x	2 1/2"	x	1 1/2"	49p
BA4	5 1/2"	x	4"	x	1 1/2"	58p
BA5	4"	x	2 1/2"	x	2"	49p
BA6	3"	x	2"	x	1"	42p
BA7	7"	x	6"	x	2 1/2"	85p
BA8	8"	x	6"	x	3"	£1-10
BA9	6"	x	4"	x	2"	70p

p & p 15p on each box

PLEASE NOTE: ALL OUR PRICES INCLUDE V.A.T. AMTRON KITS

Model No.	Description	Price
UK65	Simple transistor tester	£1-79
UK145	Amplifier 1.5W	£5-14
UK290	Signal Injector	£3-53
UK230	AM/FM Antenna Amplifier	£3-35
UK275	Mike Pre-amplifier	£7-38
UK300	4-channel Radio Control Transmitter	£7-80
UK310	Radio Control Receiver	£3-60
UK325	'GXX2' Channel splitting unit 1,000 & 2,000 Hz	£9-75
UK330	'GXX2' Channel splitting unit 1,500 & 2,500 Hz	£9-75
UK345	Superhetrodyne Radio Control Receiver	£7-25
UK325	VHF Tuner 120 to 180 MHz	£12-48
UK555	Radio Control Field Strength Meter	£7-25
UK705	Windscreen Wiper timer	£7-33
UK710	4-Channel AF mixer	£11-65
UK780	Electronics Unit for Metal Detector	£12-89
UK835	Guitar pre-amplifier	£5-37
UK876	Capacitive Discharge Electronic Ignition for Internal Combustion Engines	£14-47

VISIT OUR COMPONENT SHOP
 18 BALDOCK ST., WARE, HERTS. (A10)
 Open Mon.-Sat. 9-5.30 p.m. Tel. 61593

ANTEX SOLDERING IRONS

X25. 25 watt £2-05
 CCN 240. 15 watt £2-48
 Model G. 18 watt £2-26
 SK2. Soldering Kit £3-25
 STANDS: ST1 £1
 SOLDER: 189SWG Multicore 7oz £1-61
 22SWG £1-16. 18SWG 22ft 51p
 228SWG Tube 33p

ANTEX BITS AND ELEMENTS

Bits No.
 102 For model CN240 42p
 104 For model CN240 42p
 1100 For model CCN240 42p
 1101 For model CCN240 42p
 1102 For model CCN240 42p
 1020 For model G240 42p
 1021 For model G240 42p
 1022 For model G240 42p
 50 For model X25 48p
 51 For model X25 48p
 52 For model X25 48p

ELEMENTS
 ECN 240 £1-30 EOCN 240 £1-32
 EG 240 £1-07 EX 25 £1-16

ANTEX HEAT SINKS 10p

V A T Included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No. Qty.	Description	Price
C1	200 Resistors mixed values approx. count by weight	0-54
C2	150 Capacitors mixed values approx. count by weight	0-54
C3	50 Precision Resistors mixed values 1-2%	0-54
C4	75 1/2W Resistors mixed preferred values	0-54
C5	5 Pieces assorted Ferrite Rods 0-54	
C6	2 Tuning Gangs, MW/LW VHF0-54	
C7	1 Pack Wire 50 metres assorted colours	0-54
C8	10 Reed Switches	0-54
C9	3 Micro switches	0-54
C10	15 Assorted Pots & Pre-Sets	0-54
C11	5 Jack Sockets 3 x 3.5m 2 x Standard Switch Type	0-54
C12	30 Paper Condensers preferred types mixed valued	0-54
C13	20 Electrolytics Trans. types	0-54
C14	1 Pack assorted Hardware—Nuts/Bolts, Grommets etc.	0-54
C15	5 Mains Slide Switches, 2 Amp 0-54	
C16	20 Assorted Tag Strips & Panels 0-54	
C17	10 Assorted Control Knobs 0-54	
C18	4 Rotary Wave Change Switches 0-54	
C19	2 Relays 6-24V Operating 0-54	
C20	1 Sheets Copper Laminate approx. 10" x 7" 0-54	

Please add 20p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19 & C20.

PLUGS

PS 1 D.I.N. 2 Pin (Speaker) 0-11
 PS 2 D.I.N. 3 Pin 0-12
 PS 3 D.I.N. 4 Pin 0-15
 PS 4 D.I.N. 5 Pin 180° 0-16
 PS 5 D.I.N. 5 Pin 240° 0-16
 PS 6 D.I.N. 6 Pin 0-17
 PS 7 D.I.N. 7 Pin 0-18
 PS 8 Jack 2.5mm Screened 0-18
 PS 9 Jack 3.5mm Plastic 0-12
 PS 10 Jack 3.5mm Screened 0-18
 PS 11 Jack 1/2" Plastic 0-15
 PS 12 Jack 1/2" Screened 0-22
 PS 13 Jack Stereo Screened 0-36
 PS 14 Phono 0-10
 PS 15 Car Aerial 0-22
 PS 16 Co-Axial 0-15

INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0-14
 PS 22 D.I.N. 3 Pin 0-20
 PS 23 D.I.N. 5 Pin 180° 0-20
 PS 24 D.I.N. 5 Pin 240° 0-20
 PS 25 Jack 2.5mm Plastic 0-18
 PS 26 Jack 3.5mm Plastic 0-16
 PS 27 Jack 1/2" Plastic 0-30
 PS 28 Jack 1/2" Screened 0-35
 PS 29 Jack Stereo Plastic 0-30
 PS 30 Jack Stereo Screened 0-38
 PS 31 Phono Screened 0-18
 PS 32 Car Aerial 0-22
 PS 33 Co-Axial 0-22

SOCKETS

PS 35 D.I.N. 2 Pin (Speaker) 0-08
 PS 36 D.I.N. 3 Pin 0-11
 PS 37 D.I.N. 5 Pin 180° 0-11
 PS 38 D.I.N. 5 Pin 240° 0-11
 PS 39 Jack 2.5mm Switched 0-12
 PS 40 Jack 3.5mm Switched 0-20
 PS 41 Jack 1/2" Switched 0-20
 PS 42 Jack Stereo Switched 0-30
 PS 43 Phono Single 0-18
 PS 44 Phono Double 0-10
 PS 46 Co-Axial Surface 0-10
 PS 47 Co-Axial Flush 0-20

LEADS

LS 1 Speaker lead 2 pin D.I.N. plug to open ends approx. 3 metres long (coded) 0-20

CABLES

CP 1 Single Lapped Screen 0-07
 CP 2 Twin Common Screen 0-11
 CP 3 Stereo Screened 0-12
 CP 4 Four Core Common Screen 0-23
 CP 5 Four Core Individually Screened 0-30
 CP 6 Microphone Fully Braided Cable 0-10
 CP 7 Three Core Mains Cable 0-09
 CP 8 Twin Oval Mains Cable 0-07
 CP 9 Speaker Cable 0-05
 CP 10 Low Loss Co-Axial 0-15

CARBON POTENTIOMETERS

Log and Lin
 4-7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M
 VC 1 Single Less Switch 0-15
 VC 2 Twin D.P. Switch 0-28
 VC 3 Tandem Less Switch 0-46
 VC 4 1K Lin Less Switch 0-15
 VC 5 100K Log anti-Log 0-46

HORIZONTAL CARBON PRESETS

0-1 watt 0-06 each
 100, 220, 470, 1K, 2-2K, 4-7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4-7M

SELENIUM BRIDGE RECTIFIERS

18V. 2A. Ideal for those building battery, chargers. 15p each. 10 for 50p

REPANCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tappings 4V, 7V, 8V, 10V, 14V, 16V, 17V, 19V, 21V, 25V, 31V, 33V, 40V, 50V, and 25V-0-25V.

Type	Amps	Price	P & P
MT50/4	1	£1-93	45p
MT50/1	1	£2-42	48p
MT60/2	2	£3-30	60p

WORLD SCOOP! JUMBO SEMICONDUCTOR PACK

Transistors-Germ and Silicon
 Rectifiers-Diodes-Triacs-Thyristors
 I.C's and Zeners ALL NEW AND CODED
APPROX 100 PIECES!

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak
ONLY £2 p & p 30p

MAMMOTH I.C. PAK APPROX. 200 PIECES


Assorted fall-out integrated circuits including: Logic, 74 Series, Linear, Audio and D.T.L. Many coded devices but some unmarked—you to identify.
OUR SPECIAL PRICE
 £1.25 including V.A.T. & p. & p.

SPECIAL PURCHASE by BI-PAK 2N3055. Silicon Power Transistors NPN

Famous manufacturers out-of-spec devices free from open and short defects—every one able 115 watts TO3. Metal Case.
OUR SPECIAL PRICE 8 for £1.

8-TRACK CART-CASES
 Holds 14. 13" x 5" x 6" £1-95.
 Holds 24. 13 1/2" x 8" x 5 1/2" £2-70.
 Both with lock and handle.

CASSETTE CASES £1-30
 Holds 12. 10" x 3 1/2" x 5". Lock & Handle

SOLVE THOSE STICKY PROBLEMS!
 with 

CYANOACRYLATE C2 ADHESIVE
 The wonder bond which works in seconds—bond plastic, rubber, transistors, components permanently, immediately!

OUR PRICE ONLY 54p for 2gm phial

BATTERY HOLDERS
 Takes 6 h.p. 7s complete with terminal clip and lead. 34p each.

CARTRIDGES

AC08 GP92-1SC 200mV at 1-2cms/sec £1-35
 AC08 GP93-1 280mV at 1cm/sec £1-85
 AC08GP96-1 100mV at 1cm/sec £2-80
 TTC J-2005 Crystal/Hi Output £1-05
 TTC J-2010C Crystal/Hi Output Compatible £1-20
 TTC J-2006S Stereo/Hi Output £1-75
 TTC J-2105 Ceramic/Med Output £1-95
 TTC J-2203 Magnetic 5mV/5cm/sec, including stylus £4-95
 TTC J-2203S Replacement stylus for above £3-00
 TTC AT-55 Audio-technica magnetic cartridge 4mV/5cm/sec £3-30

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors. 1 watt available in PAKS of 50 pieces, assorted into the following groups:—
 R1 50 Mixed 100 ohms-820 ohms 50p
 R2 50 Mixed 1K ohms-8-2K ohms 50p
 R3 50 Mixed 10K ohms-82K ohms 50p
 R4 50 Mixed 100K ohms-1 Meg. ohms 50p
THESE ARE UNBEATABLE PRICES—JUST 1p EACH INCL. V.A.T.

BI-PAK SUPERIOR QUALITY LOW-NOISE CASSETTES

C60, 32p C90, 41p C120, 52p

SEE OUR COMPLETE RANGE IN

PRACTICAL ELECTRONICS, PRACTICAL WIRELESS, RADIO CONSTRUCTOR, EVERYDAY ELECTRONICS, ELECTRONICS TODAY INTERNATIONAL
OR SEND 5p. FOR THE FULL LIST OF ALL BI-PAK PRODUCTS

BOOK BARGAIN BUNDLE

- 8 Books comprising:
 - 2 Transistor Equivalent books 35p
 - 1 Radio & Electronic colour code and data chart 40p
 - 1 Radio valve guide PLUS 40p
 - 3 Other constructional books on Receivers, EM Tubers, etc. 40p
 - ALSO 1 General construction book VALUE £3. OUR PRICE £2 p & p 10p.
- BP1 Handbook of Transistor Equivalents & Substitutes 40p
- BP2 Handbook of Radio, T.V. & Industrial Tube & Valve Equip. 40p
- BP3 Handbook of Tested Transistor Circuits 40p
- BP4 International Handbook of the World's Short Wave Radio Stations and FM/T.V. Listings 35p
- BP5 Handbook of Simple Transistor Circuits 35p
- BP7 Radio and Electronics colour codes and Data Charts 15p
- BP8 Sound and Loudspeaker Manual 50p
- BP9 38 Practical Tested Diode Circuits for the Home constructor 35p
- BP10 Modern Crystal and Transistor Set Circuits for beginners 35p
- BP11 Practical Transistor Novelty Circuits 40p
- BP13 Electronic Novelties for the Motorist 50p
- BP14 Second book of Transistor Equivalents 95p
- BP15 Constructors Manual of Electronic Circuits for the home 50p
- 129 Universal Gram Motor Speed Indicator 8p
- 138 How to make FM and T.V. aerials Bands 1/2/3 15p
- 141 Radio Servicing for Amateurs 20p
- 146 High Fidelity Loudspeaker enclosures 37p
- 156 Transistor Circuits Manual No. 1 15p
- 160 Coil design and Construction Manual 30p
- 161 Radio T.V. and Electronic Data book 25p
- 174 Transistor sub-miniature receivers 33p
- 175 Transistor Test Equipment & Servicing Manual 25p
- 176 Manual of Transistor Audio Amplifiers 40p
- 178 A comprehensive Radio Valve Guide—Book 5 30p
- 183 How to receive foreign T.V. programmes on your set by simple modifications 35p
- 196 AF-RF Reactance-Frequency chart for Constructors 15p
- 200 Handbook of Practical Electronic Musical Novelties 50p
- 201 Practical Transistors & Novelties for Hi-Fi Enthusiasts 35p
- 202 Handbook of Integrated Circuits Equivalents and Substitutes 75p
- RCC Resistor Colour Code Disc Calculator 10

-the lowest prices!

74 Series T.T.L. I.C.'S

BI-PAK STILL LOWEST IN PRICE FULL SPECIFICATION
GUARANTEED. ALL FAMOUS MANUFACTURERS

1			25			100+					
SN7400	0.15	0.14	0.13	SN7453	0.15	0.14	0.13	SN74153	£1.00	0.95	0.90
SN7401	0.15	0.14	0.13	SN7454	0.15	0.14	0.13	SN74154	£1.70	£1.65	£1.60
SN7402	0.15	0.14	0.13	SN7460	0.15	0.14	0.13	SN74155	£1.20	£1.15	£1.10
SN7403	0.15	0.14	0.13	SN7470	0.32	0.29	0.27	SN74156	£1.20	£1.15	£1.10
SN7404	0.15	0.14	0.13	SN7472	0.32	0.29	0.27	SN74157	£1.00	0.95	0.90
SN7405	0.15	0.14	0.13	SN7473	0.41	0.39	0.35	SN74160	£1.40	£1.35	£1.30
SN7406	0.39	0.34	0.31	SN7474	0.41	0.39	0.35	SN74161	£1.40	£1.35	£1.30
SN7407	0.39	0.34	0.31	SN7475	0.60	0.58	0.56	SN74162	£1.40	£1.35	£1.30
SN7408	0.25	0.24	0.23	SN7476	0.44	0.43	0.42	SN74163	£1.40	£1.35	£1.30
SN7409	0.25	0.24	0.23	SN7480	0.60	0.58	0.55	SN74164	£1.80	£1.75	£1.70
SN7410	0.15	0.14	0.13	SN7481	£1.10	£1.05	£1.00	SN74165	£1.80	£1.75	£1.70
SN7411	0.25	0.24	0.23	SN7482	0.90	0.85	0.80	SN74166	£1.60	£1.55	£1.50
SN7412	0.28	0.27	0.26	SN7483	£1.20	£1.15	£1.05	SN74174	£1.60	£1.55	£1.50
SN7413	0.33	0.31	0.30	SN7484	£1.00	0.97	0.95	SN74175	£1.10	£1.05	£1.00
SN7416	0.30	0.29	0.28	SN7485	£1.60	£1.55	£1.50	SN74176	£1.25	£1.20	£1.15
SN7417	0.30	0.29	0.28	SN7486	0.35	0.34	0.33	SN74177	£1.25	£1.20	£1.15
SN7420	0.15	0.14	0.13	SN7489	£4.00	£3.75	£3.50	SN74180	£1.25	£1.20	£1.15
SN7422	0.30	0.29	0.28	SN7489	0.65	0.63	0.60	SN74181	£3.95	£3.85	£3.75
SN7423	0.40	0.39	0.38	SN7491	£1.10	£1.05	£1.00	SN74182	£1.25	£1.20	£1.15
SN7425	0.40	0.39	0.38	SN7492	0.74	0.71	0.64	SN74184	£1.25	£1.20	£1.15
SN7426	0.40	0.38	0.36	SN7493	0.74	0.71	0.64	SN74184	£1.80	£1.75	£1.70
SN7427	0.40	0.38	0.36	SN7494	0.86	0.82	0.75	SN74190	£1.95	£1.90	£1.85
SN7428	0.45	0.42	0.40	SN7495	0.86	0.82	0.75	SN74191	£1.95	£1.90	£1.85
SN7430	0.15	0.14	0.13	SN7496	0.96	0.93	0.88	SN74192	£1.95	£1.90	£1.85
SN7432	0.40	0.38	0.36	SN74100	£1.50	£1.45	£1.40	SN74193	£1.95	£1.90	£1.85
SN7433	0.42	0.40	0.38	SN74104	0.60	0.58	0.55	SN74194	£1.30	£1.25	£1.20
SN7437	0.35	0.32	0.30	SN74105	0.60	0.58	0.55	SN74195	£1.10	£1.05	£1.00
SN7438	0.35	0.32	0.30	SN74107	0.44	0.42	0.40	SN74196	£1.20	£1.15	£1.10
SN7440	0.15	0.14	0.13	SN74110	0.60	0.58	0.55	SN74197	£1.20	£1.15	£1.10
SN7441	0.74	0.71	0.64	SN74111	0.60	0.58	0.55	SN74198	£2.75	£2.70	£2.65
SN7442	0.74	0.71	0.64	SN74112	£1.00	0.95	0.90	SN74199	£2.60	£2.40	£2.30
SN7443	£1.20	£1.15	£1.10	SN74119	£1.50	£1.40	£1.30				
SN7444	£1.20	£1.15	£1.10	SN74121	0.50	0.48	0.45				
SN7445	£1.60	£1.55	£1.50	SN74122	0.70	0.68	0.65				
SN7446	£1.20	£1.15	£1.10	SN74123	0.75	0.73	0.70				
SN7447	£1.10	£1.07	£1.05	SN74141	0.85	0.82	0.79				
SN7448	£1.10	£1.07	£1.05	SN74145	£1.30	£1.25	£1.20				
SN7450	0.15	0.14	0.13	SN74150	£1.50	£1.40	£1.30				
SN7451	0.15	0.14	0.13	SN74151	£1.10	£1.05	£1.00				

NOW WE GIVE YOU 50w PEAK (25w R.M.S.) PLUS THERMAL PROTECTION!
The NEW AL60 Hi-Fi Audio Amplifier
FOR ONLY £4.25

- Max Heat Sink temp. 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 1KHz
- Supply voltage 15-50 volts
- Thermal Feedback
- Latest Design Improvements to 100KHz
- Load—3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm x 105mm x 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

FULLY BUILT—TESTED and GUARANTEED



STABILISED POWER MODULE SPM80 £3.25

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63 mm x 105 mm x 20 mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disc Systems, Public Address, Intercom Units, etc. Handbook available, 10p.

TRANSFORMER BMT80 £2.75 p. & p. 40p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

Specifications: Frequency response 20Hz—20kHz ±1dB, Harmonic distortion better than 0.1%, Inputs: 1. Tape head 3-25mV into 60KΩ, 2. Radio, Tuner 75mV into 50KΩ, 3. Magnetic P.U. 3mV into 50KΩ. All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ±1dB from 20Hz to 20KHz.

MK 60 AUDIO KIT

Comprising: 2x AL60, 1x SPM80, 1x BTM80, 1x PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. Complete Price: £29.75 plus 45p postage.

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16 1/2" x 11 1/2" x 3 1/2", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets etc. Kit price: £9.95 plus 45p postage.

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power device has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po=3 WATTS f=1KHz	0-25%
LOAD IMPEDANCE	—	8-16Ω
INPUT IMPEDANCE	f=1KHz	100 KΩ
FREQUENCY RESPONSE ± 3dB	Po=2 WATTS	50 Hz-25KHz
SENSITIVITY FOR RATED O/P	Vs=25V, R1=8Ω f=1KHz	75mV. RMS
DIMENSIONS	—	3" x 2 1/2" x 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	80
Power output for 2% T.H.D. (RL=8Ω f=1 KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.
PRICE	£2.50	£2.85	£3.20

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications. But are ideal for learning about I.C.'s and experimental work.

PAK No.	Contents	Price
UI000—12x7400	0.54	
UI001—12x7401	0.54	
UI002—12x7402	0.54	
UI003—12x7403	0.54	
UI004—12x7404	0.54	
UI005—12x7405	0.54	
UI006—8x7406	0.54	
UI007—8x7407	0.54	
UI010—12x7410	0.54	
UI020—12x7420	0.54	
UI030—12x7430	0.54	
UI040—12x7440	0.54	
UI041—5x7441	0.54	
UI042—5x7442	0.54	
UI043—5x7443	0.54	
UI044—5x7444	0.54	
UI045—5x7445	0.54	

PAK No.	Contents	Price
UI046—5x7446	0.54	
UI048—5x7448	0.54	
UI050—12x7450	0.54	
UI301—12x7481	0.54	
UI053—12x7463	0.54	
UI054—12x7464	0.54	
UI056—12x7466	0.54	
UI070—8x7470	0.54	
UI072—8x7472	0.54	
UI073—8x7473	0.54	
UI074—8x7474	0.54	
UI075—8x7475	0.54	
UI076—8x7476	0.54	
UI080—5x7480	0.54	
UI081—5x7481	0.54	
UI082—5x7482	0.54	
UI083—5x7483	0.54	
UI086—5x7486	0.54	

PAK No.	Contents	Price
UI090—5x7490	0.54	
UI091—5x7491	0.54	
UI092—5x7492	0.54	
UI093—5x7493	0.54	
UI094—5x7494	0.54	
UI095—5x7495	0.54	
UI096—5x7496	0.54	
UI100—5x74100	0.54	
UI121—5x74121	0.54	
UI141—5x74141	0.54	
UI151—5x74151	0.54	
UI155—5x74155	0.54	
UI193—5x74193	0.54	
UI199—5x74199	0.54	
UICX1—25 Assorted 74's	1.65	

LINEAR I.C.'S—FULL SPEC.

Type No.	1	25	100+
72702	0.50	0.48	0.45
72709P	0.25	0.23	0.20
72710	0.35	0.33	0.30
72711	0.30	0.29	0.28
72714C	0.28	0.27	0.26
72714P	0.30	0.29	0.28
72747	0.85	0.80	0.75
72748P	0.38	0.38	0.34
SL201C	0.59	0.45	0.40
SL701C	0.50	0.45	0.40
SL702C	0.50	0.45	0.40
TAA263	0.80	0.70	0.60
TAA293	£1.00	0.95	0.90
TAA350A	£1.85	£1.80	£1.70
PA703C	0.28	0.26	0.24
PA709C	0.20	0.19	0.18
PA711	0.35	0.33	0.30
PA712	0.35	0.33	0.30
TBA800	£1.50	£1.45	£1.40
75028	£1.50	£1.45	£1.40
76023	£1.50	£1.45	£1.40
76660	0.95	0.93	0.90
LM380	£1.00	0.97	0.95
NE555	0.65	0.63	0.60
NE556	0.95	0.93	0.90

DTL 930 SERIES LOGIC I.C.'S

Type	1	25	100+
BP930	0.15	0.14	0.13
BP932	0.16	0.15	0.14
BP933	0.16	0.15	0.14
BP935	0.16	0.15	0.14
BP936	0.16	0.15	0.14
BP944	0.16	0.15	0.14
BP945	0.30	0.28	0.25
BP946	0.15	0.14	0.13
BP948	0.30	0.28	0.25
BP951	0.70	0.65	0.60
BP952	0.15	0.14	0.13
BP953	0.45	0.43	0.40
BP954	0.45	0.43	0.40
BP957	0.45	0.43	0.40
BP959	0.45	0.43	0.40

DUAL-IN-LINE SOCKETS

14 & 16 Lead Sockets for use with DUAL-IN-LINE I.C.'S. TWO RANGES PROFESSIONAL & NEW LOW COST. PROF. TYPE NO. 1-24 25-99 100up TSO 16 pin type 33p 30p 27p TSO 18 " " 38p 35p 32p TSO 24 " " 75p 70p 65p LOW COST NO. BPS 14 " " 16p 14p 13p BPS 16 " " 17p 15p 15p BPS 8 pin type 15p 13p 11p


NUMERICAL INDICATOR TUBES

Type Description Price
3015F Minutorn £1.20
MAN 3M L.E.D. 7-segment 0-127 " £1.90
All indicators 0.9 + Decimal point. All side viewing. Full data for all types available on request.
SHP80 STEREO HEADPHONES, 4-16 ohms impedance. Frequency response 20 to 20,000Hz. Stereo/mono switch and volume controls. £4.95

BI-PAK 1975 CATALOGUE & LISTS Send S.A.E. and 10p

THE STEREO 20

The 'Stereo 20' amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm. x 14 cm. x 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractive printed front panel and matching control knobs. The 'Stereo 20' has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. 4mV control ±12dB at 60Hz typically 0-25% at 1 watt. Treble con. ±14dB at 14kHz. £14.45 p&p 45p

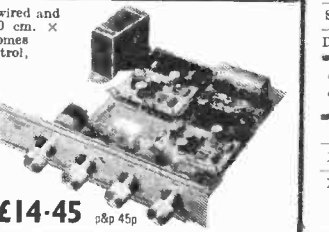

TEAK VENEERED CABINET for:

STEREO 20
TC 20. £3.95 p&p 45p
E.M.I. LEK 350 Loudspeaker System Enclosure kit in teak veneer, including speakers. Rec. retail price £45.50 per pr. OUR SPECIAL PRICE £30 per pair P. & P. £3. ONLY WHILE STOCKS LAST!


3 TERMINAL POSITIVE VOLTAGE REGULATORS

A revolution in the recording industry



**The Itam 805 8-track
master recorder. £1790**

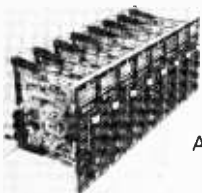Comprehensive facilities include sync on all channels, servo controlled capstan, modular electronics, variable speed (optional), relay solenoid operation.



Fully modular electronics using plug-in PCBs throughout. Separate sync and replay amps give identical levels. Switchable VUs with slow decay. Individual oscillator for each channel, Dolby A switching facility.

Compact console presentation for easy portability. £1,790 + VAT. Full console optional extra.



itam

Industrial Tape Applications, 5 Pratt Street, London NW1 OAE.
Tel: 01-485 6162/7833. Telex: 21879.

WW—190 FOR FURTHER DETAILS



Audio Connectors

Broadcast pattern jackfields, jackcords, plugs and jacks

Quick disconnect microphone connectors
Amphenol (Tuchel) miniature connectors with coupling nut

Hirschmann Banana plugs and test probes
XLR compatible in-line attenuators and reversers

Low cost slider faders by Ruf



Future Film Developments Ltd.
90 Wardour Street,
London W1V 3LE
01-437 1892/3

WW—109 FOR FURTHER DETAILS

Robotics

John F. Young

The object of this book is to present a comprehensive and orderly account of the principles and practice of robotics. It will provide a valuable source of reference for research workers and those in related fields.

1973 304 pp., illustrated 0408 705222 £6.00

Obtainable through any bookseller or from
NEWNES-BUTTERWORTH

Borough Green, Sevenoaks,
Kent TN15 8PH. Tel. Borough Green 2247.



QUADROPHONIC TAPE PLAYERS

Tape Transports

Brenell Mark V Series III Tape Decks mounted on Imhof Case IMP503/1915 size 21 in. wide x 19 in. front to back and 10 in. high overall including deck. This rugged unit can be purchased separately or fitted with the amplifiers described below. Others are available giving up to eight tracks. Price from £118

Playback Pre-amplifiers

A self-powered unit size 19 in. x 5½ in. x 4½ in. deep with four plug-in low noise preamplifiers giving 1V output into 100 ohm line. Price £32

Quad Power Amplifiers

A complete amplifier size 7 in. x 10½ in. x 4 in. high with four plug-in power amplifiers each giving 8W RMS into 8 ohms from TIP31/32 output stage. 30V supply. Price £37

Tax and carriage extra

Ask about tape controlled teaching equipment, with illuminated panel display, for typewriting and playing the piano or organ.

DEIMOS LIMITED

Simmonds Road, Wincheap Industrial Estate,
Canterbury, Kent.
Tel: 0227 68597

Wilkinsons RELAYS P.O. TYPE 3000 AND 600



**BUILT TO YOUR SPECIFICATION.
HIGHEST QUALITY AT COMPETITIVE PRICES WITH A QUICK DELIVERY SERVICE. QUOTATIONS BY RETURN HOME AND OVERSEAS.**

P.O. type 2201a **MINIATURE UNISELECTORS** including Jack 12 outlet 2 bridging 1 non-bridging wipers. This compact ratchet-driven 3-level selector is of unique design and occupies no more space than a standard 3000 type Relay. £8.50 each. P.O. Type 2 Uniselectors 25 outlet 8-level non-bridging wipers 25 outlet 4 level including single homing arc 1 bridging 3 non-bridging wipers 100 ohms. £10.50 each.

We can supply from stock a complete range of G.E.C. miniature sealed and Ericsson cylindrical type Relays, also P.O. type High Speed open Relays 88 and 89 series. latest type 100 AM 2 x 53 ohms £3.50 each.

BRIDGE MEGGERS 1,000 volts range 0/100 meg—ohms/infinity with resistance box £85.

MINIATURE DIGITAL INDICATOR size of digits ½ inch illuminated by 28 volt midge flanged lamps, weight 3¼ ozs., reading 0 to 9 with decimal points, quick disconnect rear of unit for easy lamp replacement £4.50 ea.

HIGH SPEED COUNTERS £1.75 each 3½ in. x 1 in. 10 counts per second with 4 figures. The following D.C. voltages are available 6 v., 12 v., 24 v., 50 v., or 110 v. Auxiliary contacts, normally open. 40p extra.

All prices shown are carriage paid UK only but subject to VAT at the standard rate.
**L. WILKINSON (CROYDON) LTD., LONGLEY HOUSE,
LONGLEY RD., CROYDON, CR0 3LH. Phone 01-684 0236. Grams: WILCO CROYDON**

WW—066 FOR FURTHER DETAILS

SEMICONDUCTORS

TRANSISTORS & DIODES

AC126	0.15	BC267A	0.12	BSX60	0.60	2N2926R	0.10
AC127	0.16	BC300	0.30	CRS3/05	0.31	2N3053	0.15
AC128	0.15	BC301	0.28	CRS3/10	0.38	2N3054	0.38
AC141	0.16	BC303	0.30	CRS3/20	0.42	2N3055	0.42
AC142	0.18	BC307B	0.10	CRS3/40	0.65	2N3415	0.12
AC176	0.16	BC328	0.15	OA5	0.60	2N3442	0.80
AC187	0.20	BC338	0.15	OA9	0.20	2N3714	1.16
AC188	0.20	BC377	0.20	OA10	0.37	2N3715	1.21
AC128K	0.25	BCY32	1.07	OC44	0.08	2N3716	1.28
AC141K	0.28	BCY39	1.25	OC45	0.08	2N3771	1.25
AC142K	0.26	BCY70	0.13	OC70	0.08	2N3773	2.18
AC176K	0.28	BCY71	0.18	OC71	0.08	2N3904	0.12
AC187K	0.30	BCY72	0.12	OC75	0.08	2N3906	0.12
AC188K	0.28	BDY60	0.61	OC139	0.45	2N4036	0.38
AD142	0.46	BDY61	0.53	OC140	0.65	2N4123	0.12
AD143	0.40	BDY62	0.45	OC205	1.25	2N4124	0.12
AD149	0.48	BDY90	2.28	OC206	1.25	2N5064	0.25
AL102	0.65	BDY91	2.16	OC207	1.40	ICS	
AL103	0.65	BDY92	1.75	TIC47	0.35	TAA435	0.55
BA102	0.15	BD131	0.32	2N697	0.11	TAA611	0.68
BC107	0.14	BD132	0.44	2N930	0.14	TAA861	0.68
BC108	0.13	BD135	0.32	2N1302	0.15	TBA560	2.90
BC109	0.14	BD136	0.34	2N1303	0.15	TBA570	1.20
BC147	0.10	BD137	0.36	2N1304	0.18	TBA641	0.88
BC148	0.10	BD138	0.38	2N1305	0.18	LM309K	1.80
BC149	0.10	BD139	0.41	2N1306	0.22	7 seg LEDs	
BC153	0.15	BD140	0.45	2N1307	0.22	DL704	1.19
BC157	0.11	BDY10	0.85	2N1308	0.23	DL707	0.90
BC158	0.11	BDY11	0.90	2N1309	0.23	DL747	1.75
BC159	0.11	BDY20	0.80	2N2102	0.32	All prices inclusive	
BC160	0.28	BDY38	0.60	2N2904	0.17	VAT. Post & packing	
BC161	0.30	BFY50	0.20	2N2905	0.18	0.20 extra. Matching	
BC171A	0.10	BFY51	0.18	2N2905A	0.20	charge (Gain only)	
BC171B	0.10	BFY52	0.19	2N2926G	0.10	0.20 extra/pair.	
BC168B	0.10	BSX19	0.14	2N2926O	0.10	SEND S.A.E. FOR	
BC261A	0.10	BSX20	0.15	2N2926Y	0.10	COMPLETE LIST.	

LYNX ELECTRONICS (LONDON) LTD,
8 CULLEN WAY, LONDON NW10
Tel. 01-965 2243

Low cost circuit assembly



5 assembly boards plus 500 solder pins
 (Approx.)


ONLY £4-32 inc. VAT and post and packing.

'Lektrokit' offers you a re-usable Circuit Assembly kit at a price you can afford. Designed for double sided circuitry, these unique assembly boards and pins are continuously re-usable—cutting your development time and material costs. With the 'Lektrokit' system, circuitry is so simple to modify time and time again.

Send cash with order to:

LEKTROKIT LTD.

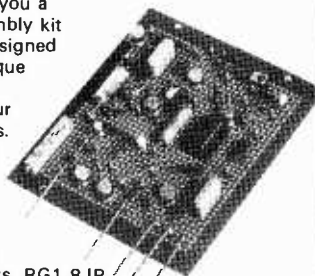
Trafford Road, Reading, Berks. RG1 8JR
 Trade enquiries invited.



WW—244 FOR FURTHER DETAILS

OLSON

MINICASES

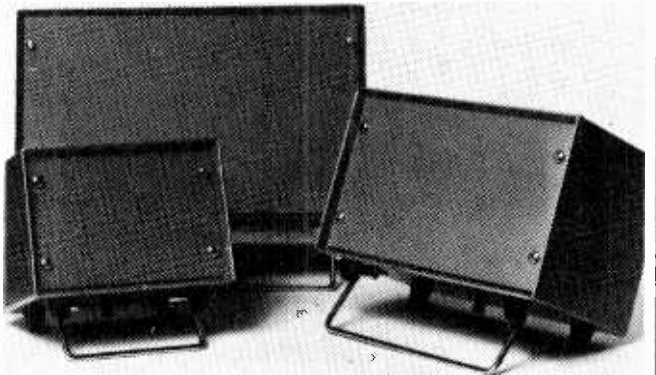


Standard minicases are made from 20g. mild steel sheets zinc-coated and finished in silver grey hammer-tone stove enamel. Front panels made from 18g. steel, finished in light grey high gloss enamel.

Type	Overall Dimension			Case no vents	Case with vents	Chrome leg
	Width	Height	Depth			
21	6½"	4½"	4½"	—	3.57	0.82
22	8½"	5½"	5½"	—	4.01	0.82
23	10½"	6½"	6½"	—	4.78	0.88
24	12½"	7½"	7½"	—	5.22	0.88
25A	6½"	4½"	4½"	3.46	3.90	0.82
25B	6½"	4½"	6¼"	3.63	4.07	0.82
26A	8¾"	5¾"	6¼"	4.89	5.33	0.88
26B	8¾"	5¾"	8¼"	5.11	5.55	0.88
27A	12¼"	7½"	5½"	5.33	5.88	0.88
27B	12¼"	7½"	8"	5.77	6.32	0.88
28A	14"	10½"	6½"	6.32	6.87	—
28B	14"	10½"	8½"	6.87	7.42	—
29A	10"	4"	6"	4.40	4.84	0.88
29B	10"	4"	8"	4.67	5.11	0.88
30A	12"	5"	6"	4.78	5.33	0.88
30B	12"	5"	8"	5.06	5.61	0.88
31A	14"	6"	6"	5.22	5.77	0.88
31B	14"	6"	8"	5.50	6.05	0.88
61	15½"	7½"	9½"	—	7.97	—
62	17½"	8½"	9½"	—	9.24	—
63	16½"	9½"	9½"	—	9.24	—
64	15½"	7½"	12½"	—	9.24	—
65	17½"	8½"	12½"	—	10.56	—
66	16½"	9½"	12½"	—	10.56	—

Types 21, 22, 23 and 24 are finished in olive green hammertone with front panels in light straw gloss enamel. Fitted with ventilated rear panels only. No louvres in the base.

PORTABLE POWER DISTRIBUTION

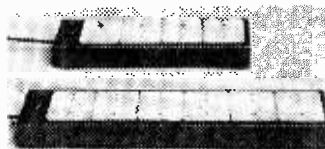

COMPLETE WITH 6FT CABLE AND 13AMP PLUG

4 SOCKETS 13A.	£8.00
6 SOCKETS 13A.	£9.50
4 SOCKETS 13A. + SW.	£9.15
6 SOCKETS 13A. + SW.	£10.10

PLEASE ADD 8% FOR V.A.T. including P. & P.

Trade Counter is open for personal callers from 9 a.m. to 5.00 p.m. Monday-Friday

OLSON ELECTRONICS LTD., TEL: 01-739 2343
 5-7 LONG ST., LONDON, E.2.

WW—231 FOR FURTHER DETAILS

BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX. Tel. 6743

ALL PRICES SHOWN INCLUDE V.A.T.

OB2	0-40	6AX4	0-75	6K80	0-45	12AV6	0-50	30P4MR	1-00	AC/TH11-00	EBF89	0-32	EL35	2-50	N339	1-10	PY80	0-40	UY85	0-35	Transistors	AF121	0-38	BYZ13	0-28	OA211	0-75	
024	0-47	6BBG	0-30	6L1	2-00	12AX7	0-33	30P12	0-86	AL60	1-00	EB21	2-00	EL37	2-30	PA6C80	0-50	PY82	0-30	U12/14	1-00	and Diodes	AF124	0-28	BYZ15	1-98	OC19	1-38
1ASG	0-45	6BA6	0-30	6LGGT	0-58	12AY7	0-80	30P19	1-00	AF4	0-50	EB22	1-00	EL81	0-60	PC86	0-60	PY83	0-38	U16	1-00	1N1124A	5F8	AF125	0-19	OC22	0-42	
1A7GT	0-85	6BE6	0-35	6L18	0-55	12BA6	0-45	30P4	0-75	AZ1	0-25	EC4	1-00	EL83	0-55	PC88	0-60	PY88	0-40	U17	0-75	1N4932	0-55	AF128	0-20	CG12E	0-42	
1B3GT	0-50	6BG6G	1-05	6L19	2-00	12BE6	0-50	30P4	0-75	AZ31	0-60	EC86	2-00	EL84	0-31	PC95	0-60	PY301	0-50	U18/20	1-00	1N4934	0-55	AF129	0-72	CG64H	0-22	
IC2	0-70	6BH6	0-60	6LD12	0-38	12BH7	0-50	30PL1	0-88	AZ41	0-25	EC88	0-70	EL85	0-44	PC97	0-35	PY500	0-95	U19	2-50	1N4935	0-55	AF130	0-75	CG74	0-42	
1G6	1-00	6BJ6	0-55	6LD12	0-38	12BH7	0-50	30PL13	0-95	BZ3	2-00	EC92	0-45	EL86	0-38	PC98	0-35	PY500A	0-95	U22	0-75	1N4936	0-55	AF131	0-75	CG81E	0-42	
1HG0T	0-80	6BK7A	0-60	6N7GT	0-80	12J6GT	0-33	30PL14	1-10	CL33	1-60	KC32	1-50	EL88	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4937	0-55	AF132	0-75	CG82E	0-42	
1L4	0-28	6BQ5	0-31	6PL12	0-34	12J7GT	0-30	30PL15	0-80	CV6	0-53	KC33	1-50	EL89	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4938	0-55	AF133	0-75	CG83E	0-42	
1LD5	0-60	6BQ7A	0-55	6Q7G	0-50	12K5	1-00	35A3	0-85	CV83	0-75	KC35	0-95	EL90	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4939	0-55	AF134	0-75	CG84E	0-42	
1LN5	0-60	6BR7	1-00	6Q7GT	0-50	12K5	1-00	35A3	0-85	CV88	0-25	KC40	1-00	EL91	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4940	0-55	AF135	0-75	CG85E	0-42	
1NSGT	0-85	6BR8	1-50	6Q7GT	0-50	12K7GT	0-45	35C5	0-75	CY1C	1-00	KC81	0-34	EL92	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4941	0-55	AF136	0-75	CG86E	0-42	
1R5	0-45	6BS7	1-40	6R7G	0-70	12Q7GT	0-45	35LGT	0-75	CY31	0-50	KC82	0-33	EL93	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4942	0-55	AF137	0-75	CG87E	0-42	
1R4	0-33	6BW6	0-80	6R7M	0-70	12SCT	0-50	35W4	0-50	D63	0-25	KC83	0-33	EL94	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4943	0-55	AF138	0-75	CG88E	0-42	
1R5	0-30	6BW7	0-70	6S4T	0-44	12SGT	0-40	35Z3	0-75	DAC32	0-60	KC84	0-35	EL95	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4944	0-55	AF139	0-75	CG89E	0-42	
1U4	0-60	6BY7	0-30	6S6GT	0-44	12SHT	0-35	35Z4GT	0-70	DAPF96	0-60	KC85	0-40	EL96	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4945	0-55	AF140	0-75	CG90E	0-42	
1U5	0-75	6BY7	0-30	6S6GT	0-44	12SHT	0-35	35Z4GT	0-70	DD4	1-00	KC88	0-44	EL97	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4946	0-55	AF141	0-75	CG91E	0-42	
2D21	0-45	6C24	0-48	6SH7	0-44	12SHT	0-35	35Z4GT	0-70	DF91	0-30	KC89	0-45	EL98	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4947	0-55	AF142	0-75	CG92E	0-42	
2GK5	0-55	6C6	0-40	6S7	0-55	12SHT	0-35	35Z4GT	0-70	DF96	0-50	KC80A	0-60	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4948	0-55	AF143	0-75	CG93E	0-42	
2X2	0-60	6C5G	0-50	6SK7GT	0-44	12SHT	0-35	35Z4GT	0-70	DH63	0-50	KC80B	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4949	0-55	AF144	0-75	CG94E	0-42	
3A4	0-80	6C6	0-40	6SK7GT	0-44	12SHT	0-35	35Z4GT	0-70	DH76	0-45	KC80C	0-60	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4950	0-55	AF145	0-75	CG95E	0-42	
3B7	0-45	6C9	1-00	6U4GT	0-70	12SHT	0-35	35Z4GT	0-70	DH81	0-75	KC80D	0-45	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4951	0-55	AF146	0-75	CG96E	0-42	
3D6	0-60	6CB6A	0-40	6V6GT	0-40	12SHT	0-35	35Z4GT	0-70	DK32	0-65	KC80E	0-75	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4952	0-55	AF147	0-75	CG97E	0-42	
3Q4	0-60	6CD6G	1-25	6X4	0-40	14H7	0-55	72	0-80	DK40	0-70	KC80F	0-75	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4953	0-55	AF148	0-75	CG98E	0-42	
3QG5T	0-55	6C17	2-00	6V6GT	0-40	14H7	0-55	72	0-80	DK92	0-70	KC80G	0-75	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4954	0-55	AF149	0-75	CG99E	0-42	
3S4	0-40	6CD6G	1-25	6X4	0-40	14H7	0-55	72	0-80	DK96	0-60	KC80H	0-75	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4955	0-55	AF150	0-75	CG100E	0-42	
3V4	0-70	6CG8A	0-75	6X6GT	0-40	14H7	0-55	72	0-80	DL92	0-40	KC80I	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4956	0-55	AF151	0-75	CG101E	0-42	
4CB8	0-55	6CL6	0-65	6Y6G	0-60	18	1-00	85A	0-85	DL96	0-55	KC80J	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4957	0-55	AF152	0-75	CG102E	0-42	
5C9B	0-85	6CLA	0-80	6Y7G	1-00	19G6	0-60	90CV	2-40	DM70	0-60	KC80K	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4958	0-55	AF153	0-75	CG103E	0-42	
5R4G	0-80	6CM7	0-75	7A7	1-00	19H1	2-00	90C1	0-75	DM71	1-50	KC80L	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4959	0-55	AF154	0-75	CG104E	0-42	
5T4	0-40	6C9	0-75	7A7	1-00	20D1	0-50	150B2	0-75	DW47/350	1-00	KC80M	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4960	0-55	AF155	0-75	CG105E	0-42	
5U4G	0-40	6CW4	1-00	7B7	0-70	20D1	0-50	150B2	0-75	DW47/350	1-00	KC80N	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4961	0-55	AF156	0-75	CG106E	0-42	
5V4G	0-50	6D3	0-60	7F8	1-50	20D4	2-00	2156G	0-50	DW47/350	1-00	KC80O	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4962	0-55	AF157	0-75	CG107E	0-42	
5Y3GT	0-45	6E7G	0-75	7H7	0-75	20P2	0-75	301	1-00	DW47/350	1-00	KC80P	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4963	0-55	AF158	0-75	CG108E	0-42	
5Z5	0-75	6D7EA	0-75	7R7	0-60	20L1	1-10	302	1-00	DW47/350	1-00	KC80Q	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4964	0-55	AF159	0-75	CG109E	0-42	
5Z4G	0-45	6E6W	0-75	7V7	1-50	20P1	0-55	303	1-00	DW47/350	1-00	KC80R	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4965	0-55	AF160	0-75	CG110E	0-42	
630L2	0-40	6E5	1-00	7Y4	0-75	20P3	0-60	305	1-00	DW47/350	1-00	KC80S	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4966	0-55	AF161	0-75	CG111E	0-42	
6A8G	1-25	6F6G	0-60	9BW6	0-75	20P4	1-00	807	1-00	DW47/350	1-00	KC80T	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4967	0-55	AF162	0-75	CG112E	0-42	
6A7	0-49	6F12	0-87	8D7	0-65	25A6G	0-60	1821	1-00	DW47/350	1-00	KC80U	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4968	0-55	AF163	0-75	CG113E	0-42	
6A05	0-57	6F13	0-70	10C2	0-65	25L6G	0-60	4033X	0-50	DW47/350	1-00	KC80V	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4969	0-55	AF164	0-75	CG114E	0-42	
6A16	0-60	6F14	0-75	10D1	0-70	25Y5	0-80	5702	1-00	DW47/350	1-00	KC80W	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4970	0-55	AF165	0-75	CG115E	0-42	
6A18	0-65	6F15	0-85	10E7	0-75	25Y5G	0-70	5763	1-50	DW47/350	1-00	KC80X	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4971	0-55	AF166	0-75	CG116E	0-42	
6A18	0-33	6F18	0-55	10F1	0-75	25Z4G	0-40	6057	1-00	DW47/350	1-00	KC80Y	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4972	0-55	AF167	0-75	CG117E	0-42	
6A15	0-40	6F19	0-55	10F4	0-60	25Z5	0-50	6050	1-00	DW47/350	1-00	KC80Z	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4973	0-55	AF168	0-75	CG118E	0-42	
6A16	0-60	6F24	0-65	10F18	0-55	25Z6G	0-70	6067	1-00	DW47/350	1-00	KC80A	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4974	0-55	AF169	0-75	CG119E	0-42	
6A18	0-38	6F25	0-60	10L14	0-45	28D7	1-00	7193	0-53	DW47/350	1-00	KC80B	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4975	0-55	AF170	0-75	CG120E	0-42	
6A15	0-20	6F26	0-30	10L11	0-70	30A5	0-65	7475	1-00	DW47/350	1-00	KC80C	0-70	EL99	0-38	PC99	0-35	PY500A	0-95	U22	0-75	1N4976	0-55	AF171	0-75	CG121E	0-42	
6A18A	0-55	6F28	0-87	10L12	0-40	30C1	0-40																					

APPOINTMENTS VACANT

DISPLAYED APPOINTMENTS VACANT: £6.08 per single col. centimetre (min. 3cm).
LINE advertisements (run on): 86p per line (approx. 7 words), minimum three lines.
BOX NUMBERS: 35p extra. (Replies should be addressed to the Box number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU).
PHONE: Allan Petters on 01-261 8508 or 01-261 8423.
Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

Advertisements accepted up to 12 noon Wednesday, May 7th, for the June issue subject to space being available.

Electronics Engineers -multiple potential

Potential relating to Pye Telecom's future in a situation where worldwide demand for radio communication products is increasing considerably and constantly. Potential in an organisation where the only limiting factor is your own ability. Potential for pleasant living in one of the most attractive parts of Britain. And finally, potential in any of these three major areas of the Company's activities:

Development

Lab work on portable, mobile, fixed station and digital equipment. BSc is preferred, but lower qualifications with sufficient RF experience and interest may be acceptable. Age range is 21-28 and you will probably have either a recent qualification or a relevant background of 3 years in radio communication equipment. It's a pleasant working atmosphere, with small team operation, using the very latest RF technology. If you merit advancement, it's there for the taking.

Systems

You'll be involved as a member of an engineering team in planning systems including VHF/UHF links, fixed stations, extensive control functions

and a range of mobile, portable radios and ancillaries. Close marketing involvement includes customer contact. Experience of VHF/UHF equipment and telecommunications practice are preferred, but if you're young and qualified you may well be eligible.

Commissioning

Testing, installing, commissioning and surveying for systems in both the UK and overseas after a 6-month training programme. HNC or C & G Final are ideal qualifications, but ONC or C & G Inter plus experience of either installing, testing, servicing or maintaining radio equipment may be an acceptable alternative. A current driving licence is essential.

If your background is appropriate find out more. All the information you need will be yours as soon as you phone or write to Richard Turner at:

 **Pye Telecommunications Ltd**
Newmarket Road, Cambridge CB5 8PD
Telephone: Cambridge 61222

A member of the Pye of Cambridge Group

4592

**NATIONAL AUDIO
VISUAL AIDS CENTRE**
254 Belsize Road, London, N.W.6.
**CCTV and Sound Technician
for Training Department**

in direct support of courses for lectures and trainers from education and industrial establishments. Additional interest in photography and reprographic processes desirable. Salary negotiable according to qualifications and experience.
Further details from Col. Parker. Tel: 01-624 8812. [4612]

**VISUAL AND
AURAL AIDS TECHNICIAN**

Applications are invited from suitably qualified persons to maintain and repair a range of Audio and Video equipment including T.V. Receivers in schools and other Education Establishments.

Average weekly earnings including bonus up to £50 per 40 hour week.

CROYDON

Applications to (or further particulars may be obtained from) The Superintendent, Croydon Education Committee, Service Centre, Princess Road, Croydon, CR0 2QZ.
Tel: 01-684 9393. [4506]

Radio Operators. How to see more of your wife without losing sight of the sea.



Join the Post Office Maritime Service. We have openings for Radio Operators at several of our coastal stations.

The work is just as interesting, just as rewarding as aboard ship, but you get home to see your wife and family more often. You need a United Kingdom General or First Class Certificate in Radiocommunications, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting pay for a man of 25 or over is £2,270, plus cost of living allowance with further

annual increases after that. Though we're happy to take people from 19 up.

In addition to your basic salary, you'll get an average allowance of £450 a year for shift duties and there are opportunities for overtime.

Other benefits include a good pension scheme, sick pay and prospects of promotion to Senior Management.

For more information, write to: ETE Maritime Radio Services Division (L534), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London, EC1A 1AS.

**Post Office
Telecommunications**

Production Engineer (TV Systems)

As leading, worldwide designers and makers of TV broadcast equipment and services, Pye TVT have excellent opportunities for a Production Engineer. Preferably in his early 30s he should be experienced in short-run batch production in the electronics industry, with a minimum of ONC in Electronic Engineering through an apprenticeship. He should enjoy working in a challenging environment, where job responsibility is properly delegated and a commonsense approach is vital. The work involves:

- ★ Methods Engineering/Aspects of work study
- ★ Evaluating new assembly processes
- ★ Influencing new design
- ★ Designing cableforms, producing assembly/wiring diagrams, instructions and planning layouts
- ★ Control throughout the production cycle on an instructing/troubleshooting capacity

We offer a competitive starting salary and full employee benefits, including assistance with relocation expenses in approved circumstances.

Please write, with details of qualifications and career, to: Mrs J. A. Macnab, Personnel Manager

4607



Pye of Cambridge Ltd

St Andrews Road Cambridge
CB41 DP Tel: Cambridge (0223) 58985

Storno LIMITED,

Manufacturers of modern FM radio communication systems for all branches of industry, transport and Public Authorities require additional

TEST TECHNICIANS

based in Camberley to assist in the final testing of personal and mobile radio equipment and sophisticated control systems.

Knowledge of RF, digital and thick film techniques desirable with academic levels to ONC or C. & G. Final, but for an applicant with exceptional experience and knowledge these qualifications may be waived.

Pleasant working conditions, good salary and overtime. Opportunities for further study and training.

Hours: Monday–Thursday:

8.15 am–1.00 pm. 1.30 pm–4.45 pm.

Friday:

8.15 am–1.00 pm. 1.30 pm–3.30 pm.

Apply: The Personnel Officer,

**Storno
LIMITED,**

Frimley Road,

Camberley. Telephone: 0276 29131

Storno SERVES THE NATION...

TEES 257

The Independent Local Radio Station based on Teesside is seeking technical staff. The staff will be responsible to the Chief Engineer for the full range of operational and maintenance requirements, including outside broadcasts.

The studios, based in Stockton, will be equipped with the most up-to-date stereo equipment, and transmissions are expected to start early this summer.

Salaries offered will reflect the experience of the candidate and there will be a contributory pension scheme.

Please write, giving brief career and personal details, to:

The Chief Engineer
"Tees 257"
74 Dovecot Street
Stockton-on-Tees
Cleveland

4590

Communications Engineer

NORTH SEA GAS AND OIL

Conoco North Sea Inc., a Company actively engaged in the development of gas and oil discoveries in the North Sea, are seeking a Communications Engineer for their London (West End) office.

His main responsibilities will be to co-ordinate and plan communications services to support the Company's drilling and production activities, which will of course involve frequent travel to the drilling operations bases at Dundee and Great Yarmouth, and to the gas production facilities at Mablethorpe in Lincolnshire.

Candidates aged 30-35 should possess a Degree in Electrical/Electronic Engineering, and have several years practical experience in radio systems engineering. A working knowledge of current Post Office radio and transmission regulations is very desirable, particularly with relation to North Sea Exploration and Production activities.

The post carries a highly competitive salary, there is a non-contributory Pension Scheme and there are good promotional prospects.

Write, giving full details of career history to:-

R. E. Horley,
Conoco North Sea Inc.,
Park House, 116 Park Street,
London W1Y 4NN.




4610

*Looking
for
a
new
job?*

Perhaps we can help!

We have regular contact with hundreds of Electronics and Electrical companies needing qualified technicians and engineers and can therefore help you find an interesting and well paid job. All you need do is to return the coupon below or give us a ring. Our service is confidential and costs you nothing.

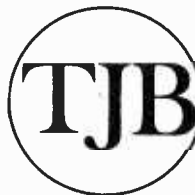**TJB Technical Services Bureau,
3A South Bar,
Banbury, Oxfordshire.
Banbury (0295) 53529**



Technical Services Bureau is a division of Technical & Executive Personnel Ltd and is solely concerned with job placement in the Electronics and Electrical Industries

Please send me an "Application for Employment" form
NAME
ADDRESS
.....4603

Electronics Engineer

Telemotive UK Limited is a company in association with a major USA manufacturer with world leaderships in the radio control of industrial machines, systems, and processes, in collision prevention, in remote positioning, and in other industrial electronics activities.

Our principal products are founded on the near field induction effect and on other inductive techniques in the 300kHz band. No other UK company has a comparable product line, and our business therefore offers engineering opportunities of unusual interest. Training in our techniques is provided.

Our current requirement is for a young engineer with versatile abilities because at different times his work will involve application engineering, production testing, commissioning of systems on customers' sites, field and base service, the anglicisation of designs originating in other countries, and a measure of production control. In each of these fields there is scope for personal engineering contributions.

The position involves some travelling within the UK and will take the engineer into a wide variety of industries. The base from which he will work is in Byfleet, Surrey.

Telemotive is a good employer. It only employs people who are exceptional in their particular job, and it treats them accordingly. The salary will depend upon the capability of the chosen applicant.

Please forward personal details to:

telemotive u.k. ltd

TELEMOTIVE HOUSE, 100 HIGH ROAD, BYFLEET, WEYBRIDGE, SURREY
BYFLEET 47117

4620

Senior Maintenance Engineer

Tape Duplicating

The Tape Duplicating Co., the leading independent production company in this field, require an experienced electronics engineer to take charge of the calibration and maintenance of the extensive, modern electronic and electro-mechanical equipment at their plant in Waltham Abbey.

Applicants, aged 22-25, with at least ONC, should preferably have experience of tape recording techniques and be capable of working with the minimum of supervision.

A good salary, commensurate with age and experience, will be paid and there are opportunities for well-paid overtime.

Apply, Personnel Manager, (ref. RMW)
The Tape Duplicating Co. (Gt. Britain) Ltd.
Audio Works, Cartersfield Road,
Waltham Abbey, Essex, EN9 1JF
Tel: Lea Valley 712712.

4595

CATV — MATV ENGINEERS AND TECHNICIANS

Canada's Leader in cable Television requires personnel for research and production Departments.

Openings for research in amplifier, Passives, Converter Designing.

Opening for Director of Electronics Engineering—should have CATV or related experience.

Electronics person strong in leadership, Methods and Mechanical Acumen required for capacity of Production Manager.

Good Salaries, generous benefits.

Please Airmail complete Personnel History and references to:

Mr. J. E. Thomas,
Lindsay Speciality Products Ltd.,
50, Mary St.,
W. Lindsey, Ontario,
Canada.

[4600

SIEMENS MEDICAL ENGINEERING Service and Sales Engineering

Service and Sales Engineers required for Electro-Medical Department, to work in the London area. Previous experience in this field an advantage, but knowledge of electronics essential.

Applications to:

SIEREX LTD.,
Heron House, 109 Wembley Hill Road,
Wembley, Middlesex, HA9 8BZ.

[4570

Royal Postgraduate Medical School and Institute of Child Health

Department of Medical Physics and Paediatrics

Research Fellow

required for development of instrumentation and research in a clinical team concerned with the investigation and intensive care of sick newborn infants and children. There is particular interest in cardiopulmonary physiology and the analysis of arterial blood gases in the servo control of the treatment.

Applicants should hold appropriate degree qualification in Physics or Electronic Engineering, and have practical ability and experience relevant to this field.

Initial salary in range up to £3,108 per annum plus £399 London Allowance plus threshold.

The post is available for one year in the first instance with the possibility of an extension for a further 2 years.

Applications, with full c.v., naming 2 referees to the Personnel Officer, RPMS, Hammersmith Hospital, DuCane Road, London W12 0HS, quoting ref. No. 8/220. [4601

**WEST SUSSEX
COUNTY COUNCIL
INSTRUCTOR
ELECTRONICS**

Industrial Training Centre,
College Road, Crawley.

The person appointed will be required to give industrial training in electronics to First Year "Off the job" trainees at both Craft and Technical level. Candidates for this post should possess qualifications of at least an appropriate Ordinary National Certificate level. The present salary scale is £1,900 x £54 (3) x £57 (9) to a maximum of £2,575 (under review) plus London Allowance and current Threshold Payments. The commencing point on the scale is determined by qualifications and previous experience. Application forms and further particulars may be obtained from the Manager (Electrical) at the above Centre. Requests for application forms should be made within 14 days of this advertisement.

[4606



*Opportunities in the
**ELECTRONICS
FIELD***

Men with analogue or digital qualifications/
experience seeking higher paid posts in:
TEST - SERVICE - DESIGN - SALES.
Phone Mike Gernat. Ref. WW.

NEWMAN APPOINTMENTS
360 Oxford St. W1
01-629 7306

[194

**COVENTRY AREA
HEALTH AUTHORITY
ELECTRONIC TECHNICIAN
GRADE II**

Electronic Technician is required to take charge of the Medical Engineering Maintenance Department dealing with the maintenance of a wide variety of electronic and electro medical apparatus. Applicants must possess HNC or HND in Electronics or equivalent qualifications.

Several years experience in the field of Electronic Engineering in particular diagnostic maintenance is necessary. The ability to manage and supervise staff will play an important part of the job and training in the maintenance of specialised hospital equipment will be given.

Salary from £2,601-£3,390 p.a. plus Threshold. Additional payments are made if overtime is required.

There are many advantages of living and working in Coventry so find out more by writing, stating age, qualifications and experience together with the names of two referees to the Area Works Officer, Coventry Area Health Authority, The Birches, Tamworth Road, Keresley End, Coventry CV7 8NN.

[4615

**Electronics Test
Engineers:
career openings
that affect all
sorts of people...**



... you most of all, naturally. Mainly because, by joining the world's largest exporter of radio-telephone equipment you will inevitably open up for yourself career advantages that very few companies can provide. Pye Telecom is growing at an ever-increasing rate - and the potential for its products has as yet been only fractionally utilised.

But the work you do will also be vital to an incredible number of others. Very frequently, life itself depends on the efficiency of the UHF and VHF equipment you'll be working on. Police, firemen and ambulance staff are a small sample of the extensive range of users. Which explains the exacting specifications of the test procedures in operation - and why previous fault-finding and testing experience is an essential requirement. If it relates to communications equipment, so much the better, but this is not absolutely essential. More important is practical proficiency, which may well have been gained in the armed forces.

Find out more right now by phoning or writing to Mrs Audrey Darkin at:



Pye Telecommunications Ltd

Cambridge Works, Elizabeth Way,
Cambridge CB4 1DW. Tel: Cambridge 58985

A member of the Pye of Cartridge Group

4496

**A Career with Marconi
is a Qualification in
itself**



If you are a skilled Electronic Technician and want to hear more about career prospects salaries etc contact:- J. Prodger

mi MARCONI INSTRUMENTS LTD

Longacres, Hatfield Road,
St Albans, Herts.
Tel: St Albans 59292

A GEC Marconi Electronics Co.

THE UNIVERSITY OF HULL

Applications are invited for
the post of

**VIDEOTAPE/
TELECINE ENGINEER**

in the Audio Visual Centre (a University Service unit). Duties include operating and maintaining the helical scan videotape system—including editing and telecine. The post is one of responsibility, working in an extensive and well equipped television unit. Candidates should have experience of broadcasting or educational television operations.

Preferred qualifications: H.N.C. or City & Guilds. Salary on scale £2,844-£3,450 (Grade 6). Applications quoting the names of two referees and ref. no. AV/1 to the Technical Staff Officer, University of Hull, by 13 May, 1975.

[4627

UNIVERSITY OF LIVERPOOL

Department of Physics

OPERATOR

Required to assist with running a 12 MeV Tandem Van de Graaff Accelerator. Candidates must possess an HNC or equivalent qualification, and practical experience of installation and maintenance of one of the following: electrical machinery, electric equipment, vacuum systems. Salary on the scale £2,439-£2,895 p.a. plus bonus for shift work (at present 30%).

Application forms may be obtained from the Registrar, The University, P.O. Box 147, Liverpool L69 3BX. Quote ref. RV/427/WW.

[4618

VISION ENGINEER

required to join small team
operating a

TV Unit for Horseracing

If you have an HNC or equivalent qualification and have experience in operating and maintaining mobile TV equipment and VTRs together with a willingness to travel and to work in a demanding field, then this Company offers you:

- 1 the opportunity to join an organisation that is forward looking and is planning to develop and expand in the field of television and electronics;
- 2 a job that is located in varied surroundings on British race courses;
- 3 a basic salary between £2,700-£3,375 plus expenses when on location.

Telephone: The Secretary, Racecourse Technical Services, 88 Bushey Road, London SW20. 01-947 3333. [4594

Radiomobile

BRITAIN'S CAR RADIO SPECIALISTS

**SENIOR
ELECTRONICS
ENGINEER**

Reporting to the Production Engineering Manager, he will be responsible for providing a day-to-day service to manufacturing, ensuring maximum continuity of production.

He will liaise with design engineers to provide information concerning preferred production practice on the electronic aspect of radio assembly. Experience in FM radio is highly desirable plus the ability to control a small section of electronic engineers.

A degree in electronic engineering is preferred, but candidates with HND or HNC will be considered.

It is considered that this position will be of interest to those in their late twenties or thereabouts. The starting salary will depend on the degree to which you can meet our requirements, and the conditions of service are those associated with a progressive organization.

Please write or telephone for an Application Form to:

**Miss I. S. Thom, Personnel Manager,
RADIOMOBILE LIMITED,
North Circular Road, London, NW2, 452 3333, Ext. 4340 or 4518.**

4587

RADIO OFFICERS

Do you have PMG I, PMG II, MPT 2 years operating experience?

Possession of one of these qualifies you for consideration for a Radio Officer post with composite signals organisation.

On satisfactory completion of a 7-month specialist training course, successful applicants are paid on a scale rising to £3,242 pa; commencing salary according to age—25 years and over £2,383 pa. During training salary also by age, 25 and over £1,724 pa with free accommodation.

The future holds good opportunities for established status, service overseas and promotion.

Training courses commence at intervals throughout the year. Earliest possible application advised.

Applications only from British-born UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered.

Full details from:

**Recruitment Officer,
Government Communications Headquarters,
Room A/1105, Priors Road, Oakley,
Cheltenham, Glos GL52 5AJ
Telephone Cheltenham 21491 Ext 2270**

[192]

Southern Television Limited

requires an

ENGINEER

A vacancy has occurred for an Engineer at DOVER to undertake the operation and maintenance of broadcasting equipment.

Candidates should be aged 23-30 and qualified to minimum H.N.C. in Electronics, or preferably a Degree. Previous experience in the Broadcasting Industry would be an advantage.

Working conditions are excellent and include Pension, Life and Accident Insurance Schemes and four weeks annual holiday.

Please apply in writing to:-

**The Personnel Administrator,
Southern Television Limited,
Northam,
Southampton SO9 4YQ**

[4604]

Electrical and Electronic Engineering Instructor

Effective training is vital to keep Pye of Cambridge as one of Britain's leading electronic groups.

With this in mind, we seek an electrical and electronic engineering instructor to join the well-equipped Pye Technical Training Centre.

The work involves instruction, both theoretical and practical, of first-year craft and technician trainees in the electrical and electronic part of their course. This means lecturing, demonstrating and supervision, to develop basic skills and knowledge.

The man appointed will need as a minimum qualification ONC or C & G final or equivalent; HNC or equivalent and previous training experience would be desirable, but we are prepared to give necessary training in instructional techniques. He should also have factory experience of current assembly and wiring techniques, including printed circuits.

This vacancy could suit an electronic technician interested in training, as well as a more experienced person.

We offer a good starting salary and the benefits and job security of a major international group. Please send details of qualifications and experience to:

T. D. Humphreys, Personnel Manager

4591



Pye of Cambridge Ltd

St Andrews Road Cambridge
CB41DP Tel: Cambridge (0223)58985

FOREIGN AND COMMONWEALTH OFFICE

We have a continuing commitment for

BROADCAST RELAY ENGINEERS

To serve a one year (unaccompanied) tour of duty on the Island of Masirah (off the coast of Oman).

Applications are invited from engineers with experience of the operation and maintenance of high powered transmitters, and who hold a third year City and Guilds Certificate in Telecommunications or its equivalent.

SALARY :

£6,563 per annum plus a cost of living supplement of £229.68 per annum. In addition a tax free allowance of £480 per annum is payable for a single officer, or £985 per annum for a married unaccompanied officer.

Free furnished accommodation and passages are available.

For an application form and further details, please write to:

**Recruitment Section
Foreign and Commonwealth Office
Hanslope Park
Hanslope
Milton Keynes MK19 7BH**

[4585]

Join the EMI Service Team at Hayes

We urgently require

Electronic Repair & Calibration Engineers

for the repair and calibration of a wide range of electronic instrumentation, including oscilloscopes, DVMs, pulse generators, power supplies etc.

Applicants should be aged 18 years and should have had at least two years background in electronics. Further training will be given in appropriate cases.

Close Circuit Television Engineers

for the servicing and commissioning of CCTV, VTRs etc.

Applicants should be aged at least 19 years, and must have had some experience in television receiver servicing.

For both of these positions, there will be attractive starting salaries according to age, experience and ability.

37½ hour week, plus paid overtime.

Don't delay, for further details telephone or write to M. Ford, 01-573 3888 Ext. 2268, EMI Service, 254 Blyth Road, Hayes, Middlesex.



The international music, electronics and leisure Group.

4621

RADIO TECHNICIAN FOR CENTRAL AMERICA

Needed to work in Guatemala with the Radio Schools Movement, training a team of Guatemalans in the maintenance and repair of station equipment. A British Volunteer Programme post.

Information:

Paddy Coulter, Overseas Volunteers/CIIR, 41 Holland Park, London W.11. [4577]

SITUATIONS VACANT

ELECTRO-MECHANICAL wire man/assembler required for work on professional recording equipment. Experience preferred but not essential. Good prospects for conscientious person capable of working to a high standard. Bias Electronics Limited, 572 Kingston Road, London SW20 8DR. 01-540 8808. [4608]

HI-FI AUDIO ENGINEERS. We require experienced Junior and Seniors and will pay top rates to get them. Tell us about your abilities. 01-437 4607. [19]

TELEVISION ENGINEER required, for independent Company in West London. Must be fully experienced with Monochrome and Colour TV's. Able to drive. Top salary paid for the right applicant. Please contact Mrs Gostelow on 01-603 8488 for interview. [4619]

UNIVERSITY OF LEEDS. A vacancy exists in the Department of Electrical and Electronic Engineering for an Electronic Technician in the Electronics Workshop. The duties will involve the development and construction of prototype electronic equipment together with the modification, testing and maintenance of a wide range of electronic equipment used in teaching and research. Minimum qualifications ONC, OND, or City & Guilds certificates in Electronic Engineering, together with at least 7 years relevant experience. Initial salary corresponding to the Grade 5 scale of £2,439 to £2,895 per annum. Applications in writing to Mr. C. S. Petch, Department of Electrical and Electronic Engineering, The University, Leeds LS2 9JT. [4605]

ARTICLES FOR SALE

ARVAK, SOUNDLIGHT Converters, from £9; Strobes, from £21; loads more, free catalogue, 98A (W), West Green Road, London, N15 5NS; 01-800 8656. [23]

CLEARING distributor stocks, transistors, diodes, components, etc. Sample pack 65p incl., postage or send stamp for list. Redhawk Sales Ltd, 10 Maple Lodge Close, Rickmansworth, Herts. Mail Order Only. [4499]

CONSTRUCTION AIDS—Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and board, one-off or small numbers. Send 9p for list. Ramar Constructor Services, 29 Shelbourne Road, Stratford on Avon, Warwks. Tel. Stratford on Avon (std 0789) 4879. [28]

DIGITAL CLOCK CHIP, AY-5-1224, with data and circuit diagram, £3.66 plus VAT. 'Jumbo' LED digits (16mm high) type DL-747, only £2.04 each plus VAT, post free. Greenbank Electronics, 94 New Chester Road, Wirral, Merseyside L62 5AG. [183]

EX GPO Miscellaneous parts and equipment for sale. Phone: 01-856 7923. [4599]

HEATH 10-102 DC—5MHz Scope. Solid-State. Like new. Less than 25 operating hours. £60. 26 Oberon Close, Hartford, Huntingdon, Cambs. [4515]

LADDERS unvarnished 14ft. 1in. closed, 25ft. 4in. extd. £21.40 delivered. Tel: Telford 586644. [13]

COLOUR. UHF and TV SPARES. Colour and UHF lists available on request. 625 TV. If unit, suitable for Hi-Fi amp or tape recording, £6.75, P/P 35p. Television construction cross hatch kit, £3.85, P/P 15p. Bush CTV 25. New convergence panels plus yoke and blue lat., £3.85, P/P 40p. New Philips single standard convergence panels complete, incl. 16 controls, coils, P.B. switches, leads and yoke £5.00, P/P 40p. New Colour Scan Coils, Mullard or Plessey plus convergence yoke and blue lateral. £10.00, P/P 40p. Mullard AT1025/05 Convergence Yoke, £2.50, P/P 35p. Mullard or Plessey Blue Laterals, 75p P/P

ELECTRONIC CRAFTSMEN

Is your present job routine and uninteresting?

We are a research establishment and our craftsmen are engaged on a wide variety of work in the fields of prototype and small batch wiring and assembly, test and inspection, maintenance fault finding and repair. Why not join us and enjoy working in first class conditions in the country.

You can expect gross earnings including overtime of £45 per week, and we can offer good housing at low rental (for applicants who reside outside the radius of our Assisted Travel Area) together with 3 weeks paid holiday with holiday bonus, free pension and excellent sick benefit scheme.

Applicants who should have served a recognised apprenticeship or have had equivalent training together with experience in one of the fields detailed should phone Tadley 4111 (STD 073 56 4111) Ext. 5230, or write to:

**INDUSTRIAL RECRUITMENT OFFICER
(PA/79/WW) PROCUREMENT EXECUTIVE
MINISTRY OF DEFENCE
AWRE ALDERMASTON
READING, BERKS.
RG7 4PR.**

[4316]

20p. BRC 3000 type Scan Coils, £2.00 P/P 40p. Delay Lines DL20, £3.50, DL1E, DL1, £1.50, P/P 25p. Lum Delay Lines, 50p, P/P 15p. EHT Colour Quadrupler for Bush Murphy CTV 25 111/174 series, £8.25, P/P 35p. EHT Colour Tripler ITT TH25/1TH suitable most sets. £2.00 P/P 25p. KB CVCI Dual Stand, convergence panels complete incl. 22 controls £2.75, P/P 35p. CR1 Base panel, 75p. P/P 15p. Makers Colour surplus/salvaged Philips G8 panels part complete; Decoder, £2.50, IF incl. 5 modules, £2.25. T. Base, £1.00, P/P 25p. CRT base, 75p, P/P 15p. GEC 2040 panels, Decoder, £3.50. T. Base £1.00, P/P 35p. CRT Base 75p, P/P 20p. B9D valve bases 10p, P/P 6p. VARICAP TUNERS. UHF ELC 1043 NEW, £4.50. Philips VHF for Band 1 and 3, £2.85 incl. data. Salvaged VHF and UHF Varicap tuners, £1.50, P/P 25p. UHF TUNERS NEW, Transistorised. £2.85 or incl. slow motion drive, £3.85. 4 position and 6 pos. push-button transistorised, £4.95. All tuners P/P 35p. MURPHY 600/700 series complete UHF Conversion Kits incl. tuner, drive assy., 625 IF amplifier. 7 valves, accessories housed in cabinet plinth assembly, £7.50 P/P 50p. GEC 405/625 Dual standard switchable IF amplifier and output chassis incl. cct., £1.50 P/P 35p THORN 850 Dual standard time base panel, 75p P/P 35p. PHILIPS 625 IF amplifier panel incl. cct., 75p. P/P 30p. VHF turret tuners AT7650 incl. valves for K.B. Featherlight, Philips 19TG170, GEC 2010, etc., £2.50. PYE miniature incremental for 110 to 830, Pam and Invicta, £1.00. A.B. miniature with UHF injection suitable K.B. Baird, Ferguson, 75p. New fireball tuners Ferguson, HMV, Marconi, £1.80 P/P all tuners 30p. Mullard 110° mono scan coils, new suitable all standard Philips, Stella, Pye, Ekco, Ferranti, Invicta, £2.00, P/P 35p. Large selection LOPTS. FOPTS available for most popular makes. 200+200+100 Microfarad 350v Electrolytic, £1.00 P/P 20p. MANOR SUPPLIES, 172 WEST END LANE, LONDON, N.W.6. Shop premises, callers welcome. (No. 28, 59, 159 Buses or W. Hampstead Bakerloo and Brit. Rail). MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON. N.W.11. Tel. 01-794 8751.

HIGH intensity electronic sirens for Police—ambulances—emergency cars. Representatives wanted World Wide. Polar Electronics. Box 710-3191 Horten, Norway. [4597]

LOW COST IC MOUNTING. Use Soldercon IC socket pins for 8 to 40 pin DIL's. 70p (plus 5p VAT) for strip of 100 pins, £1.50 (plus 12p VAT) for 3 strips of 100, £4 (plus 32p VAT) for 1,000. Instructions supplied. Send for sample. SINTEL, 53c Aston Street, Oxford. Tel: 0865 43203. [167]

VACUUM is our speciality, new and second-hand. rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish outgassing equipment from £40. V. N. Barrett (Sales) Ltd., 1 Mayo Road, Croydon. 01-684 9917. [24]

VALVE TESTER AVO 160. Portable suitcase model with handbooks, £50 o.n.o. St Albans 69236. [4622]

VALVES 1930 to 1975 types in stock, many obsolete. List 15p. Transistors. List 15p. We buy new and boxed valves, also transistors. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex, West Wittering 2023. [4598]

VIDEO TAPE RECORDER. Ikegami TVR 301-3E. Records/plays T.V. programmes. 1 hour tape and handbook, £100 o.n.o. St Albans 69236. [4623]

60 KHz MSF Rugby and 75 KHz Neuchatel Radio Receivers. Signal and Audio outputs. Small, compact units. Two available versions. Toolex, Bristol Road, Sherborne (3211), Dorset. [21]

51MM B. & H. 631 Sound Projector C/W Speaker & Transformer, £135. Hilton, 9 West Hill, Dartford 20009. [4574]

16MM B & H 631 Sound Projector, C/W Speaker and Transformer £135. Hilton, 9 West Hill, Dartford 20009. [4596]

ARTICLES WANTED

SURPLUS Components, Equipment and Computer panels wanted for cash. Ring: Southampton 772501. [4616]

TELEPHONES WANTED. Candle stick type or older (Foreign & English). 01-722 4151. [4624]

WANTED, all types of communications receivers and test equipment.—Details to R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [63]

WE BUY modern 16mm sound projectors. Burgess Lane & Co. Ltd., Thornton Works, Thornton Avenue, Chiswick W.4. 994 5752/5953. [4387]

ELECTRONICS VACANCIES

Ministry of Defence Experimental Establishment in the Lake District requires experienced electronics mechanics to build, develop and diagnose a wide range of instrumentation.

Rate of pay for 40-hour, 5-day week £33.41 plus Productivity Bonus of £4 and Cost of Living Allowance of £4.40 per week.

The posts are pensionable, there is a sick pay scheme, three weeks' annual paid holiday and an assisted travel scheme. There is a prospect of housing accommodation within a reasonable period for a married man, hostel accommodation is immediately available for single men.

If you have served a recognised apprenticeship or have had equivalent service training and would like to work in a beautiful part of the country, send for an application form to:

**Personnel Officer,
Ministry of Defence (Procurement Executive),
Eskmeals,
Bootle Station,
CUMBRIA LA19 5YR**

Telephone: Ravenglass 214/5/6

4593

Department of Anaesthetics Technician

required to be responsible for the deployment, servicing and maintenance of electro-mechanical equipment in the Intensive Care Units of Guy's Hospital. The post carries responsibility for the cleaning and sterilization of ventilators and humidifiers to the highest bacteriological control standards, the proper functioning of oxygen delivery equipment and the supervision of equipment for resuscitation. In addition there will be a need to monitor the accurate performance of such equipment using suitable measurement techniques and there will be an opportunity to become involved in other technical and research procedures. There is a well-equipped workshop available in which the successful applicant's electrical and mechanical skills can be fully utilized. The ability to liaise with all levels of hospital personnel is an important feature of the post.

The appointment will be on the Medical Physics Technician IV scale (salary £2.315-£3.005) depending on qualification and experience.

Applications should be made to the Personnel Department, Guy's Hospital, London SE1 9RT as soon as possible, quoting ref. no. L255417. Tel. 01-407 3662, ext. 35.

4586

Guy's
HEALTH DISTRICT

THIS COULD BE YOUR OPPORTUNITY
TO WORK AS AN
ELECTRONIC ENGINEER
IN
TELEVISION

With the continued increase in our sales we are looking for more engineers to work on the testing and commissioning of the studio broadcast equipment we make, which ranges from amplifiers and monochrome cameras to outside broadcast vans and our latest colour camera, all employing the latest semiconductor circuit techniques.

As an independent and well established company we have kept a young and flexible outlook and attach great importance to people fitting in. Apart from an above average salary we also offer free life and health insurance, a pension scheme of course, and a subsidised canteen as well as a congenial environment which we think is very important. We will help with relocation expenses where necessary. Andover is a growing town in an attractive part of rural Hampshire, close to Salisbury and Winchester and within easy reach of London and the South Coast.

You should be about 23-30 and have experience of working in a professional electronic atmosphere, not necessarily in television. Ability to fault find down to component level is essential and you should have a good knowledge of digital and linear circuit techniques.

Either telephone Mic Comber at Andover 61345 (reverse charge if you wish) or write with brief details so that we can send you an application form for you to use to tell us all about yourself. [4609]

Electronics Engineers a change of appointment?

Due to increasing demand for diagnostic medical X-ray equipment, and because of the introduction of new and more sophisticated apparatus, we are now looking for engineers with good electronics experience to take up a variety of challenging positions.

These include test, design, development and evaluation (environmental test) engineering, and attractive salaries will be offered to suitable applicants.

For application form, please write to or telephone :-

The Personnel Manager, GEC Medical Equipment Ltd., East Lane, North Wembley, Middx. Tel : 01-904 1288. [4589]

BRITISH NUCLEAR FUELS LIMITED

Windscale and Calder Works
Sellafield, Nr. Seascale, Cumbria

IF YOU ARE A TIME SERVED

INSTRUMENT MECHANIC

we can offer you varied and interesting work in a modern, expanding industry, covering the maintenance of flow, level and pressure measuring instruments, electronic and nucleonic instruments and complex pneumatic and electronic control systems and computers.

- *Rate of Pay: £47.60 a week, including bonus earnings
- *Good Holidays
- *Assisted Travel Scheme
- *Contributory Pension Scheme
- *Excellent Sports and Social Facilities
- *External educational concessions
- *Housing at economic rents within easy reach of Wasdale, Eskdale and Ennerdale
- *Hostel accomodation for single men and married men awaiting housing

Men of skilled status with relevant experience are invited to write for an application form (quoting reference SE202) to the Work Labour Manager at the above address or telephone Seascale 333 Extension 291 between 8.30 am and 4.00 pm on any weekday. [4611]

CAPACITY AVAILABLE

AIRTRONICS LTD., for Coil Winding—large or small production runs. Also PC Boards Assemblies. Suppliers to P.O., M.O.D., etc. Export enquiries welcomed. 3a Walerand Road, London, SE13 7PE. Tel. 01-852 1706. [61]

BATCH Production Wiring and Assembly to sample or drawings. Deane Electricals, 19B Station Parade, Ealing Common, London, W.5. Tel: 01-992 8976. [20]

CAPACITY available to the Electronic Industry. Precision turned parts, engraving, milling and grinding both in metals and plastics. Limited capacity available on Mathey SP33 JIG BORER. Write for lists of full plant capacity to C.B. Industrial Engineering Ltd., 1 Mackintosh Lane, E9 6AB. Tel. 01-985 7057. [14]

CAPACITY available for the Assembly of Electronic or Electrical Components P.C.B.'s, etc. Small or large batch production. Remploy Ltd., Jupiter Road, Norwich NR6 6SU. [31]

DESIGN, development, repair, test and small production of electronic equipment. Specialist in production of printed circuit assemblies. YOUNG Electronics Ltd., 184 Royal College Street, London, NW1 9NN. Tel: 01-267 0201. [29]

ENGINEER makes anything unusual. Inventors models, displays. Special tools and equipment. Seymour, 30 Devonshire Drive, Stapleford, Nottingham. [4229]

LABELS, NAMEPLATES, FASCIAs on anodised aluminium or perspex. Any quantity, superb quality, fast delivery. G.S.M. GRAPHICS LTD., 1-5 RECTORY LANE, GUISBOROUGH (Tel: 02873-4443), YORKS. [26]

SMALL Batch Production, wiring assembly, to sample or drawings. Specialist in printed circuit assemblies. D. & D. Electronics, 42 Bishopsfield, Harlow, Essex. Tel: Harlow 33018. [17]

COURSES

RADIO and Radar M.P.T. and C.G.L.I. Courses. Write: Principal, Nautical College, Fleetwood, FY7 8JZ. [25]

NEW GRAM AND SOUND EQUIPMENT

GLASGOW HI FI, Recorders, Video, Communications Receiver always available we buy sell and exchange for photographic equipment. Victor Morris Audio Visual Ltd., 340 Argyle Street, Glasgow, G.2. 31 Sauchiehall Street, Glasgow, G.1; 8/10 Glassford Street, Glasgow, G.2. Tel: 041-221 8958. [11]

RECEIVERS AND AMPLIFIERS—SURPLUS AND SECONDHAND

HRO Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [65]

SIGNAL generators, oscilloscopes, output meters, wave voltmeters, frequency meters, multi-range meters, etc., etc., in stock.—R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley. 4986. [64]

SERVICE AND REPAIRS

SCRATCHED TUBES. Our experienced polishing service can make your colour or monochrome tubes as new again for only £2.75, plus carriage £1. With absolute confidence send to Retube Ltd., North Somercote Louth, Lincs, or 'phone 0507-85 300. [27]

VALVES WANTED

WE buy new valves, transistors and clean new components, large or small quantities, all details, quotation by return.—Wolton's, 55 Worcester St., Wolverhampton. [62]

APPOINTMENTS CONT.

TV Broadcasting Project Engineers

Fully experienced broadcasting engineers are needed to help the growth of Pye TVT as a leading international designer and manufacturer of TV broadcasting systems and equipment.

The applicants appointed as Project Engineers (Commercial) will closely liaise with all relevant departments in defining and design of Studio, Outside Broadcast and sometimes radio schemes or transmitters to meet customers' specific requirements. They will be responsible for the preparation of tenders and will assist in their negotiation, which will involve some travel overseas. They should be qualified to at least H.N.C. level and fully experienced in either design, installation or operation of TV Studio and/or Outside Broadcast vehicles, or Transmitters.

The appointments are based in Cambridge, and relocation expenses will be paid where applicable. There is a good starting salary, with a pension and other company benefits.

Please apply, with brief details of experience, to:
Mrs. J. A. Macnab, Personnel Manager.



Pye of Cambridge Ltd
St Andrews Road Cambridge
CB4 1DP Tel: Cambridge (0223) 58985

ARTICLES FOR SALE

Economise on Semiconductors

All prices include VAT

- ★ Lower 741C prices 100 + 24p
- ★ Plastic 3 terminal Regulators
- ★ Low Price CMOS
- ★ Low price DIL sockets

	1+	10+	25+		1+	10+	25+
709C Op Amp + data 8 pin DIL	34	32	30	TTL Mixed prices			
723C Reg. + data 14 pin DIL	65	63	59	7400	17	18	15
741C Op Amp + data 8 pin DIL	30	28	26	7402	17	18	15
748C Op Amp + data 8 pin DIL	39	37	35	7403	17	18	15
NE555 Timer + data 8 pin DIL	65	62	59	7404	18	17	16
CA3048 Array 14 pin DIL	76	73	69	7405	18	17	16
TDA1405 Reg. 5V 850mA	100	92	85	7410	17	18	15
TDA1412 Reg. 12V 500mA	100	92	85	7413	38	34	32
TDA1415 Reg. 15V 450mA	100	92	85	7420	17	18	15
BC107, 108, 109	10	9.5	9	7442	70	66	63
BC182, 184	11	10.5	10	7447	90	85	80
BC212, 214	12	11.5	11	7473	38	36	34
HP Red LED 1/2"	18	18	15	7474	35	33	31
HP Red LED 0.2"	19	17	16	7476	38	36	34
DIL Sockets.				7486	30	28	26
low profile	8 pin	11	10	7490	55	52	49
	14 pin	12	11	7492	55	52	49
	16 pin	13	11	7493	55	52	49
				74121	44	42	40
				CMOS Mixed Prices			
BC109C	11	BZX88C-	1N914	4000	27	25	
BC177	18	3V3-15V	1N4001	4001	27	25	
BC178	18	2N3702	1N4002	4002	27	25	
BF244	24	2N3704	1N4004	4007	27	25	
BF244B	27	2N3708	1N4148	4011	27	25	
BFY51	17	2N3055		4012	27	25	
				4013	60	54	
				4015	150	140	
				4023	27	25	
				4025	27	25	
				4027	80	82	
				4030	63	57	

AY-5-1224 Digital Clock IC, 12 or 24hr. 7 segment or BCD outputs, drives LED Minitron. LED displays. Simple interfacing. 16 pin DIL. IC + data + circuits £4.65. HP 5082-7740 0.3" digits £2.00. IC + 4 0.3" digits £12. IC + 4 0.3" digits + transistors + transformer £14.00
TBA810AS 7W Audio Amp. Thermal protection + data + circuit £1.20
TCA940 10W Audio Amp. Thermal protection, current limit + data + circuit £2.60
TAD100 Radio IC + filter + data £1.60
Carbon film High Stability 1/2W 5% resistors 10 ohm-2m2 1p ea., 10 9p, 100 80p same value.
By return service. Prices include VAT. P & P 10p (UK) overseas at cost. All items new TI, Motorola, Mullard, SGS etc. SAE lists, enquiries. Data sheets 4p. Colleges etc. supplied.

SILICON SEMICONDUCTOR SERVICES

41 Dunstable Road, Caddington, Luton LU1 4AL

40

ARTICLES WANTED

Are you obtaining the full benefit from the disposal of your electronic and computer scrap?

As refiners of base and precious metals we purchase manufacturers' and distributors' scrap arisings and redundant components including...

PRINTED CIRCUITS · RELAYS · TRANSISTORS · PLUGS · CONNECTORS · ETC.

Contact us for prompt and personal attention

The COMMERCIAL SMELTING & REFINING Co. Ltd.
171, Farringdon Rd., London EC1R 3AL. 01-837 1475

4614

TOP PRICES PAID

for semiconductor and component redundant or excess inventories

P.R.S. ELECTRONICS

126 Headstone Road
Harrow, Middlesex
Tel: 01-965 2243

[34]

Scholarship Awarded by

The Institution of Electrical Engineers

The Council of the Institution of Electrical Engineers will consider for award this year Undergraduate and Postgraduate Scholarships with a maximum value of £600 per annum.

The closing date for the receipt of applications is 1st May, 1975 and late applications cannot be considered.

Full particulars of the conditions governing the award of these Scholarships may be obtained from:

The Director, Qualifications Department, The Institution of Electrical Engineers, Savoy Place, London WC2R 0BL.

[4625]

C AND G EXAMS

Make sure you succeed with an ICS home study course for C and G Electrical Installation Work & Technicians Radio/TV/Electronics Technicians. Telecomms Technicians and Radio Amateurs.

COLOUR TV SERVICING

Make the most of the current boom! Learn the techniques of servicing Colour and Mono TV sets through new home study courses, approved by leading manufacturers.

TECHNICAL TRAINING

Home study courses in Electronics and Electrical Engineering, Maintenance, Radio, TV, Audio, Computer Engineering and Programming. Also self-build radio kits. Get the qualifications you need to succeed.

Free details from:

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept 734, Intertext House, London SW8 4UJ.
Or Phone 01-622 9911 (all hours).

[4391]

SERVICE & REPAIRS

ABRASIVE CLEANING

OF Buildings, Factories, Transport Chassis, Containers, Industrial Plant, Stone, Steel and Concrete Structures.

For professional opinion:

PALMTREE SANDBLASTING LTD.
67 HAWORTH ROAD, BRADFORD, YORKS.
TEL. BRADFORD 492318.

[4631]

BUSINESS OPPORTUNITIES

Hair Transplant

For free brochure, clip this ad. and send to:

Room 6
HAIR TRANSPLANT INTERNATIONAL
502 Ecclehall Road, Sheffield
[4224]

TAPE RECORDING ETC.

RECORDS MADE TO ORDER

DEMO DISCS
MASTERS FOR
RECORD COMPANIES

VINYLLITE
PRESSINGS

Single discs, 1-20, Mono or Stereo, delivery 4 days from your tapes. Quantity runs 25 to 1,000 records
PRESSED IN VINYLLITE IN OUR OWN PLANT.
Delivery 3-4 weeks. Sleeves/Labels. Finest quality NEUMANN STEREO/Mono Lathes. We cut for many Studios UK/OVERSEAS. SAE list.

DEROY RECORDS
PO Box 3, Hawk Street, Carnforth, Lancs.
Tel. 2273

[82]

★ PHONE YOUR CLASSIFIED ADVERT ★

TO
ALLAN PETTERS

01-261 8508

01-261 8423

★

The Shop Window for the Very Best...



**COMBINED
PRECISION
COMPONENTS
(PRESTON)LTD**

194-200 North Rd,
Preston PR1 1YP
Tel: 55034
Telex: 677122.

TOSHIBA VALVES

Type	Price (p)	Type	Price Each (p)
DY87	30.0	AD149	40
DY802	30.0	AD161	38
ECC82	28.0	AD162	38
EF80	29.5	AF114	24
EF183	34.5	AF115	21
EF184	34.5	AF116	22
EH90	35.5	AF117	19
PC900	24.5	AF118	50
PCC89	40.0	AF139	35
PCC189	41.0	AF178	46
PCF80	31.5	AF180	45
PCF86	39.0	AF181	45
PCF801	42.0	AF239	40
PCF802	40.0	AF240	60
PCL82	39.0	BC107	11
PCL84	39.0	BC108	10
PCL85	44.5	BC109	14
PCL86	41.0	BC109C	14
PFL200	69.5	BC113	13
PL36	55.5	BC116A	19
PL84	25.0	BC117	14
PL504	64.5	BC125B	15
PL508	67.0	BC132	25
PL519	£1.50	BC135	15
PY88	35.5	BC137	19
PY800	33.0	BC138	26
PY500A	85.0	BC142	23

SEMI CONDUCTORS

Type	Price Each (p)	Type	Price Each (p)
AC127	17	BC148	10
AC128	13	BC149	10
AC141K	25	BC153	15
AC142K	25	BC154	15
AC151	20	BC157	14
AC154	18	BC158	10
AC155	18	BC159	11
AC156	20	BC173	18
AC176	22	BC176B	11
AC187	19	BC182L	12
AC187K	24	BC183L	12
AC188	17	BC187	25
AC188K	24	BC214L	15
AD142	45	BC328	28
		BC337	19

DIODES

Type	Price Each (p)	Type	Price Each (p)
BD124	75	BF115	20
BD131	45	BF160	15
BD132	38	BF167	20
BD160	£1.39	BF173	20
BD235	48	BF178	35
BD237	52	BF179	40
BDX32	£2.40	BF180	31
		BF181	32
		BF184	25
		BF185	25
		BF194	9
		BF195	8
		BF196	10
		BF197	12
		BF198	23
		BF200	25
		BF218	30
		BF224	23
		BF258	34
		BF336	28
		BF337	35
		BF355	54
		BFX86	28
		BFY50	19
		BFY52	20
		BSY52	38
		BT106	£1.20
		BU105/02	£1.95
		BU108	£2.10
		BU208	£2.95
		BU222	30
		BU2340	45
		CC71	15
		CC72	16
		R2008B	£2.00
		R2108B	£2.00
		RCA16334	80
		RCA16335	80

INTEGRATED CIRCUITS

Type	Price Each	Type	Price Each
BA115	7	TAA550	49p
BA145	14	TAA700	£2.95
BA148	19	TBA120AS	£1.00
BA154/201	11	TBA120SQ	£1.00
BY126	11	TBA480Q	£1.40
BY127	12	TBA520Q	£2.35
BY199	27	TBA530Q	£1.75
BY206	21	TBA540Q	£1.75
BV238	25	TBA560Q	£2.40
OA90	5	TBA800	£1.50
OA202	7.5	TBA920Q	£2.90
IN60/OA91	5	TBA990Q	£2.90

NEW TOSHIBA TUBES

19" A49/191X	£48.95	TC270Q	£2.90
20" 510DJB22	£50.75	ETTR6016	£2.00
22" A56/120X	£54.25	SN76013ND	£1.50

EHT MULTIPLIERS MONOCHROME (BRC)

Type	Price Each
2HD 950MK1, 960	£1.70
2TQ 950MK2, 1400	£1.85
2DAK 1500 (17" & 19")	£1.85
2TAK 1500 (23" & 24")	£2.00

EHT MULTIPLIERS - COLOUR

11TAQ IIT CVCI, 2 & 3	£4.50
ITN GEC/Sobell	£4.50
11TAZ GEC 2110	£4.85
11TAM Philips G8	£4.50
11TBD Philips 550	£4.50
3TCW Pye 691/693	£3.50
11TH Decca 30 Series	£4.50
11TAQ Decca 'Bradford'	£4.50
3TCU Thorn 3000/3500	£5.00
11HAA Thorn 8000	£1.90
11HAB Thorn 8500	£4.25

PRICES SUBJECT TO 8% V.A.T.
All goods subject to settlement discount of 5% 7 days and 2% monthly
No postage charges or minimum order values.
Write or phone for full details now.

...In Prices, Quality and Service.

B. BAMBER ELECTRONICS

5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE
TEL: ELY (0353) 860185 (TUESDAY-SATURDAY)

ELECTROLYTIC CAPACITORS

AXIAL LEAD AND SINGLE ENDED

MFD 6.3V 10V 16V 25V 35V 50V	
22 30p	40p
33 - 30p 35p 40p 45p	
47 - 40p 45p	
100 35p 40p - 45p 60p	
220 40p 40p - 50p 75p	
330 40p 45p 60p 75p 95p	
470 45p 60p - 95p	
1000 - 95p 95p	
3300 95p 95p	

PRICES PER PACK OF 5
Trade enquiries welcome for quantity

MAINS TRANSFORMERS

240V in, voltages quoted approx. RMS.
TYPE 10/2 10-0-10V at 2A, £1.50
TYPE 125BS Approx. 125V at 30mA, 65p
TYPE 72703 400V at 10mA, 200V at 5mA, 6.3V at 400mA, £1.25
TYPE 18/8 18V at 8A, £4.50 each
TYPE 16/6 16V at 6A, 45V at 100mA, £4.00
TYPE 28/4 28V at 4A, 125V at 500mA, £4.00
TYPE 129 400V at 20mA, 200V at 10mA, 6.3V at 500mA, £1.25
TYPE 70462 250-0-250V, 50-0-50V, 6.3V, £1.75

RADIO SPARES 500-WATT AUTO TRANSFORMER. 100/110/150/200/220/240/250V tapped input and output, step up or step down facility, ex new equip. £6.00

MAINS ISOLATING TRANSFORMER. 375VA, tapped primary, 240V output, new, £6.00.

MAINS ISOLATING TRANSFORMER. (ex equip), in metal cases, totally enclosed, tapped mains input, 110-240V etc., output 240V at 3A + 12V at 0.5A, £11.00.

AS ABOVE, output 240V at 12A + 12V at 3A + 22V at 2.5A, £27.50, carriage £2.

MISCELLANEOUS

MAGNETIC DEVICES PROGRAMMERS. contain 9 microswitches with 9 adjustable drums for period switching (needs slow-motion motor to drive drum) many switching applications £1.00 each.

ITT HIGH-GRADE ELECTROLYTICS, 6800 mfd at 25V, screw terminals, complete with capacitor clip for vertical mounting, 50p each (quantity discount available).

PLESSEY ELECTROLYTICS, 10,000 mfd at 63V, size 115 x 51mm, 75p each.

MULTICORE CABLE, 1/2" dia. PVC covered, in 22ft. lengths with plug and socket fitted, 24 core stranded + 1 screened + 1 twin screened (ideal mobile control lead) £2.10 each.

TWIN HEAVY DUTY CABLE, PVC-covered, 50/0.25mm, 15p per metre, or £10.20 per 100 metre reel.

CURLY LEADS, 4-core telephone-type 18in. closed, approx. 5ft. extended, 2 for 20p.

MANUFACTURERS AND COMPONENT RETAILERS

PLEASE NOTE:
We have large stocks of electrolytic capacitors by well-known manufacturers, all at very competitive prices for quantities.
Send S.A.E. for latest list by return.

VALVES

QQV03/10 (ex equipment) 75p each
2C39A (ex equipment) £1.00 each
QQV02/6 (ex equipment) £1.00 each
4X250B (ex equipment) £2.10 each
4X250B (ex equipment) £1.50 each
DET-22 (ex equipment) 2 for £1.00
EF80 (new) 25p, EZ81 (new) 25p

PYE RADIO-TELEPHONE EQUIPMENT

Cambridge. Westminster. Motofone. Europa series. Send s.a.e. for full details, stating requirements, frequency, channel spacing, etc.

TERMS OF BUSINESS: CASH WITH ORDER.

ALL PRICES INCLUDE POST & PACKING (UK ONLY)
EXPORT ENQUIRIES WELCOME. PLEASE ADD 8% VAT.
CALLERS WELCOME BY APPOINTMENT MINIMUM ORDER £1
PLEASE ENCLOSE STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES £613

PYE MF TRANSMITTERS

2 x 5B254Ms in final, VFO 340 to 540kHz (can be modded upward), 2 x 5B254Ms in Modulator, cw/mcw (can be modded for AM), units complete, but no PSUs, (supplied with circuits of TX and PSU) brand new, boxed, £20.00.

PLUGS AND SOCKETS

TV PLUGS (metal type) 6 for 50p
TV SOCKETS (metal type) 50p
TV LINE CONNECTORS 5 for 50p
PL255 (PTFE) PLUGS 50p each or 5 for £2.25
S0239 (PTFE) SOCKETS 50p each or 5 for £2.25
25-WAY ISEP PLUGS and SOCKETS 40p set (1 plug + 1 skt). Plugs and sockets sold separately at 25p each
DIN SPEAKER SKTS. 2-pin, 4 for 30p
ANDREWS 44AN FREE SKTS (N-TYPE) for FH4/50B or FHJ4/50B cable £1.00 each
S0239 BACK-TO-BACK SOCKETS £1.25 each
BNC INSULATED SOCKETS (single-hole type) 65p each

HIGH-QUALITY SPEAKERS

3 1/2in. x 6in. elliptical, 2in. deep, 4 ohms, inverse magnet, rated up to 10Watts, £1.50 each, or 2 for £2.75 (quantity discount available).

ELECTRONIC IGNITION FOR YOUR CAR!

Cut petrol costs by up to 15%. Install Electronic Ignition in your car in minutes. Reduces petrol consumption, increases overall performance. Prolongs contact-breaker and spark-plug life. Makes starting so much easier. Each unit (British manufacture) tested and guaranteed for 2 years/50,000 miles. IMPORTANT: STATE POSITIVE EARTH or NEGATIVE EARTH when ordering. £11.80 + VAT (84p). Post paid.

TEST EQUIPMENT

FENLAND 3 + 3 AUDIO MIXER. 6-channel, separate bass, treble, and slider fade on each channel. Mint condition, solid state £50.

RACAL 125MHZ DIGITAL FREQUENCY METER. Type 801R/2, 0.01V to 1V sensitivity, 8-digit readout, new condition, £275.00

ROHDE AND SCHWARZ SIGNAL GENERATOR. SMAF, 4-300MHz, AM/FM, attenuation to 0.05 microvolt, deviation and modulation metered, complete, but needs attention, £300.00

ROHDE AND SCHWARZ FREQUENCY DEVIATION METER. FMV, AM/FM, 20-300MHz £300.00

MARCONI UHF SIGNAL GENERATOR. TF762B, 300-600MHz, £50.00

MARCONI STANDARD SIGNAL GENERATOR. TF867/2, 15kHz-30MHz, £100.00

MARCONI AMPLITUDE MODULATOR. TF1102, £35.00

MARCONI VALVE MILLIVOLT-METER. TF899A, £30.00

MARCONI STANDARD SIGNAL GENERATOR. TF144H, 10kHz-72MHz, £195.00

WAYNE KERR VHF FREQUENCY STANDARD. 12-channel, £20.00

ARMEC BRIDGE HETERODYNE DETECTOR. Type 775, £65.00

ARMEC SIGNAL GENERATOR. Type 201, 30kHz-30MHz, £75.00

HEWLETT PACKARD UHF SIGNAL GENERATOR. Type 614A, 800-2300MHz, £175.00

SOLARTRON DIGITALVOLT-METER. Type LM1420/2, with "TRUE RMS AC UNIT", 10mV-1000V, 5-digit display, new condition, £400.00

ROHDE AND SCHWARZ POWER SIGNAL GENERATOR. SMLM, 30-300MHz, up to 5V output, £300.00

GRESHAM LION 625-LINE PULSE/BAR/STAIRCASE GENERATOR. £25.00
TEKTRONIX 924P SCOPE. DC-10MHz, £70.00



ARTICLES FOR SALE CONT.

SURPLUS BARGAINS

EASTER LINE ANGUS
 chart recorders, model A601R
 500-0-500u.a. f.s.d. 110v AC,
 as new, with manual. **£35.00**
 (carr. £1).
 Kent Chart recorders single point **£20**,
 multipoint **£30** (£1.50).
 A.E.I. 4-stage sequential transistorised
 electronic timer, many applications, inc
 3 channel auto-light flasher (750 watts
 240v). Circuits provided for fully inter-
 rupted and dim/bright flashing. Modification
 instructions and mains transformer. **£4.50**
 only (50p).
 Printed circuit Kits. **£1.25** (30p).
 Instant Heat Soldering Irons. 240v 100 watt
£2.65 (30p).
 Veedor root 4 digit resettable counters 115v
 AC **£1.25** (10p).
 AMPEX VIDIO Tape 2" x 1670'. New **£9**
 (50p).
 Ferric Chloride **25p** lb (20p). 10 lbs for
£2.50 (45p).
 TELEPRINTER PAPERS and TAPES. 8½"
 wide, 3-ply carbon, buff manilla **60p** (35p),
 ditto 7-ply NCR, no carbon required **£1**
 (35p). TAPES, ¼", white **£2** per 8 rolls (65p),
 ½" buff **£2** per 10 rolls (65p). 1" tape suit
 Friden, etc. **£2** per 7 rolls (65p).
 B & R VHF change over coaxial relays 50v
 DC operating coil 2½" x 2½" x 2½" **£1.25**
 (15p).
 35 watt Mains transformer outputs 2, 3, 6,
 20, 24, 27, 30, **£1.25** (25p).
 All prices plus (p&p) total plus VAT 8%.
 Large S.A.E. for list.
CASEY BROS, 235 Boundary Rd, St Helens,
Lancs.



ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	½lb Reel
10-14	£2.05	£1.15
15-19	£2.15	£1.20
20-24	£2.20	£1.25
25-29	£2.25	£1.30
30-34	£2.35	£1.38
35-40	£2.50	£1.45

All the above prices are inclusive in U.K.
COPPER SUPPLIES
 102 Parrwood Rd., Withington, Manchester 20
 Telephone 061-224 3553

PARTRIDGE ELECTRONICS


MANUFACTURERS OF AUDIO MIXER SYSTEMS
 NEW PEAK READING
 * **VU METER SYSTEMS**
 Which gives the advantages normally only associated with
 PPM systems at much lower cost.
 REF. W.W.
 21/25, Hart Road, Benfleet, Essex.
 (Established 23 years) [43]

MINI ACCUMULATORS

2 volt MULTI-USE Sealed
 Lead Acid Rechargeable
 Cells.
 Size L450—1.4" x 1.1" x
 0.44"
 3 for **£1.85** inc. P. & P.
 Size GA2—1.7" x 1.3" x
 0.5".
 3 for **£2.35** inc. P. & P.
GARFIELDS, 269 Rye Lane, London, SE15 [4017]



MINIATURE FM/VHF TRANSMITTER

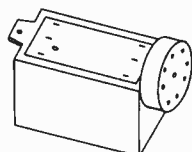

KIT REQUIRING FIVE SIMPLE SOLDERED CONNECTIONS. SIZE 2" x 1" x 1". RANGE UP TO 500 YARDS.

COMPLETE WITH MICROPHONE AND BATTERY.

EXPORT ENQUIRIES WELCOME. OUR PRICE COMPLETE £6.75

Return post delivery. Not licensable in U.K.
 S.A.E. for further details:
EES, THE AIRPORT, EXETER.

PM ELECTRONIC SERVICES

CRYSTALS FOR PROFESSIONAL AND AMATEUR USE

We can supply crystals to most commercial specifications, with an express service for that urgent order. For the amateur we carry a large stock of the more popular frequencies, backed by a quick service for those "Specials". Please send SAE for details or telephone between 4.30-7 p.m. and ask for Mr. Norcliffe.

7A, ARROWE PARK ROAD, WIRRAL, MERSEYSIDE L49 0UB.
Tel: 051-677 8918 (until 7 p.m.)

[58]

Going DIGITAL?

PLANS AND DATA

Module 1: Crystal Counter-Timer, Frequency Meter, event Counter and stopclock, 4 Gelger Circuit. 4 Digits. 85p.

Module 2: FET Multimeter—volts, current, capacitance, resistance, & crystal-calibrated audio oscillator. (6 ICs.) 90p. Interface with M1.

Also TV Doppler Detection, 88p. Multi-mode IC Detectors/Alarms (Intruder, Baby, Optical). 75p.

10p P.&P. orders under £2.

R & E Publications, Highlands, Needham Market, Suffolk IP6 8DR.

Designers of advanced circuits since 1969. 4602

WE SELL

CONSTRUCTION PLANS

Phonevision, Television Camera, Police Radar Detector, Voice typewriter, Scrambler, Answering machine, Wireless quarter mike. Plans: **£7.50** each.

COURSES

Detective-Electr. **\$36.50.** Security-Electr. **\$43.50.** Telephone Eng. **\$59.**

OVER 750 ITEMS

Ask for Catalogue—Airmailed **\$0.75**

T. STRIK,

Postbox 618, Rotterdam, Holland. [44]

SALES AND SERVICE ADVERTISEMENTS

£6.08 per single column centimetre.
01-261 8508

SUB-MINIATURE MAINS TRANSFORMERS

SCN-0-240V/12V-0-12V, 50 m/a max. 28mm W, 20mm H, 26mm D 90p each.

PHONO LEADS

Phono Plug to Phono Plug, Single Screened Grey Cable, Length 2 Yards Min. 5 for 90p (Single Sockets available with above 5p each)

CERMET TRIMMERS

Morganite Type 81E, 5K ohms ... Min. 5 for **£1.00**
 All prices include V.A.T., Postage free. C.W.O.
OR Call at our retail shop (Mon-Sat. 9.30-6.00).

LINWAY ELECTRONICS

843 Uxbridge Road, Hayes End, Middx. UB4 8HZ.
Tel. 01-573 3677 [4626]

S.I.G.A. TRANSFORMERS

- * We offer a comprehensive coil winding service including Laminated, C-Cored and Toroidal Transformers for many applications.
- * Large or small quantities at competitive price and delivery.
- * S.I.G.A. Toroidal A.W. range for Audio Power Supply Units includes:

REF SECONDARY WINDINGS

	O.D. (cms.) HT.	
284 0-45v 1A rms	9.5 x 4.4	£6.69
285 25-0-25v 2A rms	10.8 x 5.1	£8.63
291 33-0-33v 4A; 25-0-25v 0.2A rms	14.0 x 5.7	£14.57
301 0-33v 2A; 0-33v 2A rms	12.1 x 4.4	£10.47

Primaries: 0-235v 50Hz, screened.
 Dimensions are approximate.
 Prices include P&P and VAT.
 Quantity discounts available.

S.I.G.A. (ELECTRONICS) LIMITED,
Sunderland Road, Sandy, Beds SG19 1QY. Tel: Sandy (0676) 81266.

4630

ELECTRONIC KITS

requires reliable firms well connected in own markets for handling exclusive sales in countries where no organisation yet exists.

Send enquiries to:

AMTRON
Casella Postale 4160,
Milano,
Italy

zero88

Build a mixer to your own spec. using our easy to wire **AUDIO MODULES**
 For full details contact Richard Brown at Zero 88, 115 Hatfield Road, St. Albans, Herts, AL1 4JS Tel. 63727

59

CRYSTALS

Fast delivery of prototypes and production runs.

INCLUDING:

- Statek LF crystals in TO5 package
- Buckman LF, clock, and mobile radio crystals
- Astro Filter crystals
- Jan General purpose crystals

Interface Quartz Devices Limited,
 29 Market Street, Crewkerne, Somerset.
Tel: (046031) 2578 Telex: 46283 [57]

CARBON FILM RESISTORS—E12 SERIES

High Stab. ¼W OR ½W 5%. 1p, 75p/100, £5-50/1000 (22Ω-1MΩ).

RESISTOR KITS 22Ω-1MΩ E12 SERIES
 10E12 KIT 10 of each value (Total of 570) ¼W, **£3-85;**
 ¼W **£3-85;** 25E12 KIT 25 of each value (Total of 1425) ¼W, **£8-35;** ½W, **£8-45.**

EQUIPMENT SALE

Regulated power supply modules. New in original packing. ATC 24V/2A, £19. Fenlow ±15V/1A, with F/Panel, £12.50. NGN Vacuum Meters PRU3 (Used) £15. Marconi D-A Converters TF2402, £20. Code Converter TF2403, £20. Limits Indicator TF2404, £20. HAAKE Const Temp. Water Circulators type F-Junior (± 0.10) Used, £50. Transformers 50V/30A £20. 7.5KV/0.015A, £7. Honeywell Chart Recorders £50. Solartron VF252 Precision Millivoltmeter £35. Solartron CA512 V.S.W.R. Indicators £25. 400V, 250mA Bench Power Supplies £15. Hatfield Ins. PUM1/16 400 cycle Generators £30. Multihead 2PH. Dec. Osc., £30. Many other items available. Please add £1 carriage and 8% VAT.

METAL FILM KITS ALSO AVAILABLE.


CATALOGUE No. 3 (Approx. 2000 Parts) 20p.

C.W.O. P. & P. 10p on orders under £5. Overseas at cost.

B.H. COMPONENT FACTORS LTD
 Dept. WW, 61 Cheddington Road, PITSTONE,
 Nr. Leighton Buzzard, Beds. LU7 9AQ,
 Cheddington (0296) 688446 [32]

You've asked for it!

Time and again we are asked for reprints of Wireless World constructional projects: tape, disc, radio, amplifiers, speakers, headphones. Demand continues long after copies are out of print. To meet the situation we have collected fifteen of the most sought after designs and put them in one inexpensive book. And we've updated specifications where necessary to include new components which have become available. A complete range of instruments is presented, from the Stuart tape recorder and Nelson-Jones f.m. tuner, through the Bailey, Blomley and Linsley Hood amplifiers, to the Bailey and Baxandall loudspeakers – some of which have been accepted as standard in the industry.

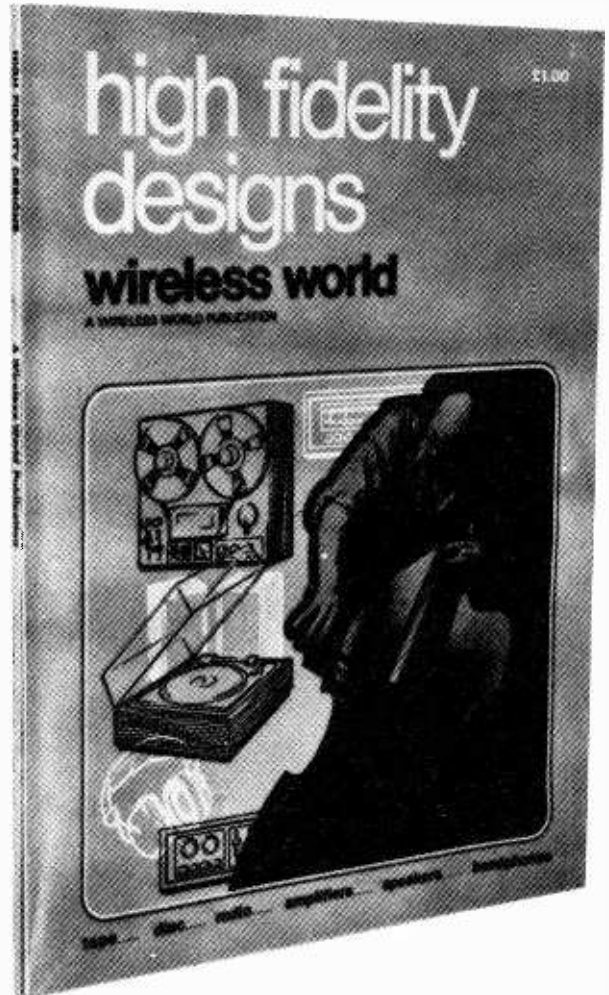

high fidelity designs

£1 from newsagents and bookshops
or £1.35 (inclusive) by post from the publishers.

A book from

Wireless World

To: General Sales Department, Room 11, Dorset House,
Stamford Street, London, SE1 9LU

Please send me copy/copies of High Fidelity Designs
at £1.35 inclusive. I enclose remittance value £.....
(cheques payable to IPC Business Press Ltd.).

NAME
(please print)
ADDRESS

Company registered in England No. 677128
Regd. office; Dorset House, Stamford Street, London SE1 9LU

SINTEL

Data and circuits supplied with orders, or available separately (send s.a.e.)

Economy DL704 Red 0.3" LED 7 seg display C.Cath. **Only 95p**
DL707 Red 0.3" LED 7 seg display C. Anode **£1.35**
FN5005 Fairchild Superdigit 2.5" 7 seg LED Red C.C. **£1.15**
NSN33 Type 12" 3 digit LED C.C. Red **£1.85** **4 for £5.00**
MK50250N Alarm Clock IC **£5.80** **CT7001** **£5.95**
MK2050N plus 4 x DL704 **£9.20**; plus 8 x **DL704** **£10.95**
CT7001 plus 4 x DL704 **£9.75**; plus 6 x **DL704** **£11.65**
Clock and Driver PCBs for MK50250N inc. IC skt etc. **£2.45**
Clock Display PCB for 4 or 6 DL704s **£1.35**
75492 LED dig driver **£1.02**; **75491 quad seg driver** **81p**
 Other displays, clock and calculator ICs etc. are available—phone (9.30am to 5pm) or send s.a.e. for list.
32.768 kHz (2 1/2") High precision crystal from ITT—can be used with CMOS to provide 60cps for clocks (circuit provided) **£3.60**
195K Calculator Keyboard: 18 keys plus On/Off switch. **£3.90**
SOLDERCON IC Socket Pins **100 pins for 50p** (supplied in strips of 100 pins)
3000 pins for £1.50
1000 pins for £4.00
 Instructions included
 —send s.a.e. for sample
 Nylon supports available—samples encl. with any pin order.
RCA CMOS at new low prices—send s.a.e. for stock/price list.
RCA 1975 CMOS Data Book (645 pages) **£2.30** (No VAT) +44p p.& p.
ADD VAT at 8%—Add 10p p.& p. for orders under £2
SINTEL, 53c ASTON STREET, OXFORD Tel: 0865 43203

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N12 8JG.

Telephone: 01-445 0749 01-445 2713 01-958 7624

MAY WE ASSIST YOU TO DISPOSE OF YOUR SURPLUS AND REDUNDANT STOCKS.

We will call anywhere in the British Isles, and pay SPOT CASH for Electronic Components and Equipment.

SANDOWN

Practical Wireless, October, November, December 1974
 State of the Art STEREO FM TUNER
 Typical Performance—Limiting voltage 0.5µV
 Sensitivity—30dB quieting mono 15µV, 50dB stereo 12µV
 Basic Stereo Module Kit £26.85. INTERESTED?
 S.A.E. for further details to:-
FW ELECTRONICS, 40 TUDDEHAM ROAD, IPSWICH, SUFFOLK IP4 2SL. Mail Order Only

PRECISION POLYCARBONATE CAPACITORS

All High Stability—Extremely Low Leakage

440V AC (±10%) **GSV Range**

0.1µF (1" x 1")	50p	0.47µF	±1%	±2%	±5%
0.22µF (1" x 1")	50p	0.47µF	56p	46p	36p
0.25µF (1" x 1")	62p	1.0µF	68p	56p	46p
0.47µF (1" x 1")	71p	2.2µF	80p	68p	56p
0.5µF (1" x 1")	75p	4.7µF	£1.30	£1.05	86p
0.68µF (2" x 1")	80p	6.8µF	£1.64	£1.29	£1.09
1.0µF (2" x 1")	81p	10.0µF	£2.00	£1.60	£1.40
2.0µF (2" x 1")	£1.22	15.0µF	£2.75	£2.15	£1.90

TANTALUM BEAD CAPACITORS—Values available:
 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 15V/25V or 35V;
 10.0µF at 16V/20V or 25V; 22.0µF at 6V/10V or 16V;
 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V.
 ALL at 10p each, 10 for 96p, 50 for 44.

TRANSISTORS

BC107/8/9	9p	BC183/183L	11p	BFY50	20p
BC114	12p	BC184/184L	12p	BFY51	20p
BC147/8/9	10p	BC212/212L	14p	BFY52	20p
BC163/7/8	12p	BC247/658A	12p	AF178	30p
BC182/182L	11p	BF194	12p	OC71	12p
		BF196/197	13p	2N3055	50p

POPULAR DIODES—1N914 8p, 8 for 45p, 18 for 90p
 1N916 8p, 6 for 45p, 14 for 90p; 1N44 5p, 11 for 50p,
 24 for £1.00; 1N4148 5p, 6 for 27p, 12 for 48p; 1N4001
 5p; 002 6p; 003 6p; 004 7p; 005 7p; 006 8p; 007 8p.
LOW PRICE ZENER DIODES—400mw, Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V,
 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 13V, 13.6V,
 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V. All at 7p
 each, 6 for 39p, 14 for 84p. SPECIAL OFFER: 100 Zeners
 for 45-50.

RESISTORS—High stability, low noise carbon film 5%.
 1/4W at 40°C, 1/2W at 70°C. E12 series only—from 2.2Ω to
 2.2MΩ. ALL at 1p each, 8p for 10 of any one value, 70p
 for 100 of any one value. SPECIAL PACK; 10 of each
 value 2.2Ω to 2.2MΩ (730 resistors) 45.

SILICON PLASTIC RECTIFIERS—1.5 amp. brand new
 wire ended DO27; 100 P.I.V. 7p (4 for 26p) 400 P.I.V. 8p
 (4 for 30p).

BRIDGE RECTIFIERS—2 1/2 amp, 200V 40p; 350V 45p;
 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only.
 ALL at 5p each; 50Ω, 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ,
 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 22kΩ, 47kΩ, 68kΩ,
 100kΩ, 250kΩ, 680kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 10p POST AND PACKING ON ALL
 ORDERS BELOW £5. ALL EXPORT ORDERS ADD
 COST OF SEA/AIRMAIL.

PLEASE ADD 8% V.A.T. TO ORDERS.
 Send S.A.E. for lists of additional ex-stock items.
 Wholesale price lists available to bona fide companies.

MARCO TRADING (Dept. D11)

The Old School, Edstaston, Nr. Wem, Shropshire
 Tel. Whixall (Shropshire) (STD 094872) 464/5
 (Proprs.: Minicoast Trading Ltd.)

Illustrations in Applied Network Theory

F.E. Rogers

A hundred numerical and algebraic illustrations designed to exemplify practical circuit problems and introduce, in analysis, principles consistent with studies of synthesis that may be pursued later.

1973 240 pp., illustrated
 0 408 70425 X cased £5.00
 0 408 70426 8 limp £2.50

Obtainable through any bookseller

Newnes-Butterworths

TRANSFORMER LAMINATIONS

enormous range in Radiometal, Mumetal and H.C.R., also "C" & "E" cores. Case and Frame assemblies.

MULTICORE CABLE IN STOCK CONNECTING WIRES

Large quantities of miniature potentiometers (trim pots) 20 ohm to 25K. Various makes. Wholesale and Export only.

J. Black

OFFICE: 44 GREEN LANE, HENDON, NW4 2AH
 Tel: 01-203 1855. 01-203 3033
STORE: LESWIN ROAD, N.16
 Tel: 01-249 2260

QUARTZ CRYSTAL UNITS from

- 1.0-60.0 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 5271-A

WRITE FOR LEAFLET AT 1
MCKNIGHT CRYSTAL Co.
 HARDLEY INDUSTRIAL ESTATE, MYTHE, SOUTHAMPTON SO4 6ZY.

TEL. HYTHE 848961
 STD CODE 0703

EXPRESS

PRINTED CIRCUITS - ROLLER TINNING - GOLDPLATING - FLEXIBLE FILMS. ETC.

Electronic & Mechanical
 Sub-Assembly Co. Ltd
 Highfield House, West Kingsdown
 Nr. Sevenoaks, Kent
 Tel: West Kingsdown 2344

EXCLUSIVE OFFERS

WORLD-WIDE RANGE NEVER BEFORE OFFERED

COMPLETE TRANSPORTABLE H.F. COMMUNICATIONS CENTRE housed in Air Conditioned TRAILER fitted two COLLINS KWT-6 600W B.S.B. Transmitter-Receiver and one COLLINS Receiver all fully tuneable 2 to 30 m/cps digital readout synthesised frequency control, with line amplifiers and inputs, operating position and remote control facilities and ancillary equipment. Power input 115V or 230V A.O. Full details on application.

PHILCO RC-150 POINT-TO-POINT STRIP RADIO HF RECEIVERS 2/30 m/cps. Ten fully tuneable channels to 0.5 kecs with synthesiser. Single and diversity reception on 1SB, DSB, SSB with 4 sub-bands to each channel. Full details and prices on application.

HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS

Our Ref.	Height in inches	Width in inches	Depth in inches	Rack Panel Spacing in inches	Price
CD	69	21	13	68	£10.00
CL	30	20	36	42	£12.50
OR	69	30	20	—	£24.00
DM	70	20	26	188	£21.00
PA	85	22	36	160	£22.00
FC	52	25	22	47	£17.00
FD	40	22	24	72	£14.00
FG	11	19	18	10	£11.00
FH	15	21	17	11	£12.00
FJ	15	21	15	12	£12.00
FN	70	24	20	68	£17.00
FL	84	22	17	80	£21.00
LL6	11	21	17	9	£15.00
LL7	16	20	12	14	£15.00
LL8	10	20	10	9	£15.00
LL9	17	21	17	14	£15.00

Also Consoles, twin and multi-way Cabinets.

OPEN RACKS

Our Ref.	Height in inches	Channel Depth	Rack Panel Spacing	Base	Price
RF	85	3	79	15	£11.00
BG	57	2	51	14	£9.00

Full details of all above on request.

We have a large quantity of "bits and pieces" we cannot list—please send us your requirements we can probably help—all enquiries answered.

- ★ Hewlett Packard 524 Digital Counter P.U.R.
- ★ Tektronix 519 Oscilloscopes 1 GMC P.U.R.
- ★ Ferrograph Model 808 Recorders **£45.00**
- ★ Alrmec 701 Sig. Generators 30 k/cps/30 m/cps **£30.00**
- ★ Alrmec 702 Sig. Generators 30 c/cps/30 k/cps **£23.00**
- ★ CT. 381 Test Sets Freq. Response **£140.00**
- ★ Rustrak Chart Recorders 1-0-1 m/s (New) **£30.00**
- ★ URA 8 Teleprinter Converters **£85.00**
- ★ Portable Mains Battery Floodlights **£24.00**
- ★ 400 channel Pulse Height Spectrum Analysers P.U.R.
- ★ Hewlett Packard Audio Oscillators **£24.00**
- ★ Solartron 5/25000 c/c. Oscillators **£24.00**
- ★ Southern Inst. 1800 F.M. Meters **£24.00**
- ★ Belling Lee T.V. Relay Equipment P.U.R.
- ★ Addo 6/8 track Tape Punches **£45.00**
- ★ Tally 6/8 track Tape Readers **£48.00**
- ★ 80 column Card Hand Punches **£40.00**
- ★ Auto Electric Carillon Chimes **£250.00**
- ★ 10 foot Triangular Lattice Mast Sections 6 inch sides **£12.00**
- ★ Ditto 15 foot with 15 inch sides **£20.00**
- ★ Casella Assmann Electric Hygrometers **£24.00**
- ★ Rasal RA63 SSB Adapters (New) **£70.00**
- ★ Amper Audio Stereo Tape Machines **£250.00**
- ★ Astrodats 5190 Time Code Generators **£80.00**
- ★ Geotech 4983 Hello Amplifiers **£16.00**
- ★ 19" Chrome trims 1 1/2" to 1 5/8" from **£0.25**
- ★ DG7/5 CRT's 2 1/2" **£3.00**
- ★ 3AZP/51 CRT's 3 1/2" **£3.00**
- ★ GOC-3 Lightweight Teleprinters **£35.00**
- ★ FX-1 Facsimile Transmitter Receivers **£85.00**
- ★ Teletype 28, 3-speed tape printers **£35.00**
- ★ 5 1/2" dia. Meteorological Balloons **£2.50**
- ★ Laboratory Radio Interference Filters **£2.50**

FREE

40-page list of over 1,000 different items in stock available—keep one by you.

INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

AMPEX

FR-600 and FR-100
 1" and 1/2" 14 and 7
 tracks 4 speeds Trans-
 istorised
 Also 1/2" 2 track 6 speeds

MINCOM

CMP-100
 1/2" 1" 1" 7 tracks 6 speeds

E.M.I.

BTR-1 R-301
 Several other smaller
 decks.
 Full details on request.

Prices of above are from £100 to £400.

COMPUTER HARDWARE

- ★ CARD READER 80 col. 600 c.p.m.
- ★ PRINTER, High speed 1000 lines p.m.
- ★ TAPE READER, High speed 5/8 track 800 c.p.m.

Prices on Application
 PLEASE ADD V.A.T. TO ABOVE

P. HARRIS

ORGANFORD-DORSET

BH16 6ER
 BOURNEMOUTH-766051

Wilmslow Audio

**THE firm
for
speakers!**



Baker Group 25, 3, 8 or 15 ohm	£7.75
Baker Group 35, 3, 8 or 15 ohm	£8.50
Baker Deluxe, 8 or 15 ohm	£10.75
Baker Major, 3, 8 or 15 ohm	£8.00
Baker Regent, 8 or 15 ohm	£7.75
Baker Superb, 8 or 15 ohm	£14.50
Celestion HF 1300 Mk II	£6.95
Celestion MH 1000 horn, 8 or 15 ohm	£10.95
EMI 13 x 8, 3, 8 or 15 ohm	£2.25
EMI 13 x 8, 150 d/c, 8 ohm	£2.50
EMI 13 x 8, 350, 8 or 15 ohm	£8.25
EMI 13 x 8, 20 watt bass 8 ohm	£8.60
EMI B x 5, 10 watt d/c, roll/s 4 or 8 ohm	£2.50
ELAC 59RM109 15 ohm, 59RM114 8 ohm	£2.80
ELAC 6 1/2" d/c, roll/s 8 ohm	£3.50
Fane pop 70	£16.95
Fane Crescendo 12A or B, 8 or 15 ohm	£29.00
Fane Crescendo 15, 8 or 15 ohm	£38.00
Fane Crescendo 18, 8 or 15 ohm	£51.95
Fane 701 Horn	£35.00
Fane 801T 8" d/c, roll/s 8 ohm	£7.00
Goodmans 8P 8 or 15 ohm	£5.00
Goodmans 10P 8 or 15 ohm	£5.30
Goodmans 12P 8 or 15 ohm	£12.95
Goodmans 12P-D 8 or 15 ohm	£16.75
Goodmans 12P-G 8 or 15 ohm	£15.75
Goodmans Audiom 100 8 or 15 ohm	£12.00
Goodmans Axent 200 8 ohm	£7.25
Goodmans Axiom 402 8 or 15 ohm	£17.25
Goodmans Twin Axiom 8" 8 or 15 ohm	£8.25
Goodmans Twin Axiom 10" 8 or 15 ohm	£9.00
Kef T27	£5.25
Kef B110	£7.25
Kef B139	£14.25
Kef T15	£8.00
Kef DN8	£2.00
Kef DN12	£4.95
Kef DN13	£3.30
Richard Allan CG8T 8 ohm	£6.35
STC4001G Super Tweeter	£6.19
Wharfedale Super 10 RS/DD	£12.95
Castle Super 8 RS/DD	£8.95
Tannoy 10" HPD	£55.50
Tannoy 12" HPD	£56.50
Tannoy 15" HPD	£72.00
Radford BD25	£14.75
Radford MD9	£8.95
Radford HD3	£6.75
Radford FN12	£8.95
Baker Major Module	each £10.75
Goodmans DIN 20 (4 ohm)	each £9.75
Goodmans Mezzo Twinkit	pair £45.00
Helme XLK25	pair £22.00
Helme XLK30	pair £14.95
Helme XLK50	pair £39.95
Kef kit I	each £20.95
Kef kit III	each £36.75
Peerless 20/2	each £14.95
Peerless 30/2	each £20.95
Peerless 20/3	each £22.95
Peerless 50/4	each £34.95
Peerless 3/15	each £15.00
Richard Allan Twinkit	each £8.95
Richard Allan Triple 8	each £13.75
Richard Allan Triple 12	each £19.95
Richard Allan Super 12	each £23.75
Wharfedale Linton 2 kit	pair £19.25
Wharfedale Glendale 3 kit	pair £34.50
Wharfedale Doveedale 3 kit	pair £52.50

PRICES INCLUDE VAT

Cabinets for PA and HiFi, wadding, Vynair etc.
Send stamp for free booklet "Choosing a Speaker"
FREE with orders over £7—HiFi Loudspeaker Enclosures Book

All units are guaranteed new and perfect
Prompt despatch

Carriage: Speakers 38p each, 12" and up, 50p each, tweeters and cross-overs 25p each, kits 75p each (£1.50 pair)

WILMSLOW AUDIO

Dept. WW

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Discount HiFi, PA etc: 10 Swan Street, Wilmslow, Radio, HiFi, TV: Swift of Wilmslow, 5 Swan Street, Wilmslow. Tel: (Loudspeakers) Wilmslow 29599, (HiFi etc.) Wilmslow 26213

WW—063 FOR FURTHER DETAILS

VIDEO HIRE

EQUIPMENT, EDITING, OPERATORS' STUDIO FACILITIES ETC.
THE MOST EXPERIENCED VIDEO COMPANY IN THE BUSINESS

R.E.W.

R.E.W. HOUSE,
10, 12 HIGH STREET,
COLLIERS WOOD,
LONDON, SW19 2BE PHONE: 01-540 9684

Quartz Crystal Units
ACCURATE RELIABLE

Private enquiries, send 10p in stamps for brochure

THE QUARTZ CRYSTAL CO. LTD.
Q.C.C. WORKS, WELLINGTON CRESCENT,
NEW MALDEN, SURREY. 01-942-0334 & 2988

SOWTER TRANSFORMERS

FOR SOUND RECORDING AND REPRODUCING EQUIPMENT.
We are suppliers to many well-known companies, studios and broadcasting authorities and were established in 1941. Early deliveries. Competitive prices. Large or small quantities. Let us quote.
E. A. SOWTER LTD.
Transformer Manufacturers and Designers
7 Dedham Place, Fore Street, Ipswich IP4 1UP
Telephone 0473 52794

WORLD RADIO TV HANDBOOK 1975

A Complete Directory of International Radio & TV

Price £3.70

THE AUDIO HANDBOOK by G. J. King. Price £5.15

COLOUR TELEVISION SERVICING by G. J. King. Price £4.65

THE RADIO AMATEUR'S HANDBOOK by A.R.R.L. Price £3.50

110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston. Price £1.95

DIGITAL COMPUTER STRUCTURE & DESIGN by R. Townsend. Price £2.85

TOWERS' INTERNATIONAL TRANSISTOR SELECTOR by T. D. Towers. Price £3.15

VIDEOTAPE RECORDING by J. F. Robinson. Price £5.00

SLIDE-TAPE & DUAL PROJECTION by R. Beaumont-Craggs. Price £3.20

REFERENCE DATA FOR RADIO ENGINEERS by ITT. Price £11.00

TRANSISTOR MANUAL by G.E. Price £1.30

★ PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

SPECIALISTS IN SCIENTIFIC & TECHNICAL BOOKS

19-21 PRAED STREET,
LONDON, W2 1NP

Phone 723 4185
Closed Sat. 1 p.m.

J. LINSLEY-HOOD New Phase Locked Loop F.M. TUNER

(As per Wireless World Annual).

Basic kit of parts
*£29.95 (tax £2.40)

Available in pack form as follows:

Pack 1. Res. and capacitors £3.00 2. Semi conductors and I.C's £6.25 3. Tuner head £5.50 4. P.C. boards and drawings £1.50 5. Chassis and tuning mechanism £5.00 6. Ceramic filters £1.50 7. Teak finish sleeve £3.00 8. Meter and muting module £2.50 9. Regulated power supply £5.00 10. Stereo decoder. Ready made £7.50 11. Push button and trimmer pack £2.50 (*Excludes packs No. 8, 10 and 11.) Tax extra.

TELERADIO ELECTRONICS

325 Fore Street, Edmington, London N9 0PE. 01-807 3719.
Closed Thursdays.

S.A.E. for further details of above and other Linsley-Hood superior low distortion designs.

WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC. SPOT CASH

CHILTMead LTD.
7, 9, 11 Arthur Road, Reading, Berks. Tel: 582 605

LONDON CENTRAL RADIO STORES

TELEPHONE CABLE. Plastic covered grey 4-core coloured coded. 9p per yard.

ELECTRICITY SLOT METERS (5p in slot) for A.C. mains. Fixed tariff to your requirements. Suitable for hotels, etc. 200/250v. 15A. £8.38. 20A. £9.30. P.P. 75p. Other amperages available. Reconditioned as new. 2 years guarantee.

MODERN TYPE DESK PHONES, red, green, blue or topaz, 2-tone grey or black, with internal bell and handset with 0-1 dial £6.50.

5-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box handset. Thoroughly overhauled, guaranteed. Price £5.25. Send s.a.e.

10-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box handset. Thoroughly overhauled. Guaranteed. £6.75 per unit. Send s.a.e.

20-WAY PRESS-BUTTON INTER-COM TELEPHONES in Bakelite case with junction box. Thoroughly overhauled. Guaranteed. £7.75 per unit. Send s.a.e.

The "88" Set. This transceiver, weighs approx. 5 1/2 lbs. and measures 3 1/2 in. x 5 1/2 in. x 9 1/2 in. It is a 4-frequency channel set 41-44 mc/s. Crystal Controlled and operates from a dry battery H.T./L.T. 94/1. v. I.E. Ruben Mallory Type No. 1 and employs the following 14 valves: 3A4 1 off; 11A 6 off; 1T4 4 off; 1S5 1 off; 1A3 2 off. £6.50 plus 75p P. & P.

QUARTERLY CHECK METERS 15A £3.90. 20A £4.22. P. & P. 50p.

All prices subject to fluctuation

Multi Relay Units, Group selectors, Final end selectors and Relays in stock, 20-way jack strips and tip ring and sleeve plugs. For callers only.

23 LISLE ST. (437) LONDON W.C.2
(2969)

Open all day Saturday

STEREO DISC AMP

FOR BROADCASTING AND DISC MONITORING
Mainly in. Balanced lines out. Excellent distortion and LF performance. MEETS IBA SPECIFICATION £95.00.

10-OUTLET DISTRIBUTION AMP

One balanced input - 10 isolated balanced outputs
GENERAL STUDIO WORK * FEEDING MULTIPLE SLAVE PA AMPLIFIERS * DRIVING FOLDBACK HEADPHONES
Meets IBA signal path specification. Complete boxed unit £94.00.
Set of parts less case and all XLR connectors £55.00.

PEAK PROGRAM METERS TO BS4297

also 200KHz version for high speed copying.

Drive circuit. 35 x 80mm. for 1mA L.H.z. zero meter to BBC ED1477. Gold 8-way edge con supplied.

Complete kit £12.00 Built and aligned £17.00

ERNEST TURNER PPM meters. scalings 1/7 DR-22/+4. Type 642. 71 x 56mm £12.60; 643. 102 x 79mm £15.00.
Twin movement. scale 86 x 54mm £37.00.



FREQUENCY SHIFTER

FOR HOWL REDUCTION

PUBLIC ADDRESS: SOUND REINFORCEMENT

In any public-address system where the microphones and loudspeakers are in the same vicinity acoustic feedback (howl-round) occurs if the amplification exceeds a critical value. By shifting the audio spectrum fed to the speakers by a few Hertz the tendency to howling at room resonance frequencies is destroyed and an increase in gain of 6-8dB is possible before the onset of feedback.

SHIFTERS IN BOXES with overload LED, shift/bypass switch. BS4491 mains connector and housed in strong diecast boxes finished in attractive durable blue acrylic. Jack or XLR audio connectors.

Type	A	B	C
Input impedance	20Kohm	200Kohm	10kohm
Output impedance	2kohm	20 or 600 ohm	20 or 600 ohm
PRICE	£58.00	£88.00	£94.00

SHIFTER CIRCUIT BOARDS FOR WW July 1973 article

Complete kit and board £24.00 Including p.s.u. and DESIGNER Board built and aligned £31.00 mains transformer APPROVED

SPECTRUM SHIFTER: variable shifts, 0.1-1000Hz.

for weird special effects and phasing. Ring for leaflets.

SURREY ELECTRONICS

The Forge, Luicks Green, Cranleigh,
Surrey GU6 7BG. (STD 04866) 5997
CASH WITH DROER, less 5% UK post free. add VAT

EX-COMPUTER STABILISED POWER SUPPLIES

RECONDITIONED, TESTED AND GUARANTEED

Ripple <10mV. Over-voltage protection, 120-130v. 50 c/s. Stepdown transformer to suit about £3. P & P £1.80.
5/6v. 8A. £12. 5/6v. 12A. £14
50/60 c/s. £3.50 (35p).

PAPST FANS 4 1/2 x 4 1/2 x 2in. 100 cfm. 240v. 50/60 c/s. £3.50 (35p).

PAPST FANS 6; dia x 2 1/2 deep, type 7576 £5.00 (35p). 250w light dimmers £2.70 (15p)

TRANSISTORS p & p 10p
BC107/8/9 BC147/8/9 BC157/8/9 all 9p
BF180 25p. BF182/3 40p. BF184 17p. BFW10 55p.
2N3819 20p. BF336 35p. 741 8 diil 28p. 2N3771 £1.10. BD131 40p. NE555 67p.

ELECTROLYTICS
30,000µ 25v., 68,000µ 16v., 15,000µ 30v., 65p (35p).
5,000µ 35v. 40p (15p), 4,700µ 63v. 60p (13p),
2,000µ 50v. with clip 35p (11p), 2,200µ 63v. 35p (11p).

EX COMPUTER PC PANELS 2 x 4 in. 25 boards £1 (35p).

OPCOA 7 seg led display SLA-7 7mm characters with dec. point. ea £1.50 (10p)
QH bulbs 12v. 55w. 55p (8p)
150 mixed HI STABS. 60p (11p)
250 mixed resistors. 60p (15p)
250 mixed capacitors. 60p (15p)
20A. 100 piv Si RECS. 4 for £1 (12p)
2N3055 Equiv. 4 for £1 (12p)
200 Si Planar Diodes. 50p (9p)

SMALL ELECTROLYTICS
2.2µ 10/16v., 10µ 35v., 50µ 40v., 100µ 40v., 100µ 6v., 150µ 10v., 64µ 10v. 12 for 45p (7p)

PIHER PRESETS 100mW
220, 470, 4k7, 10k, 100k 12 for 50p (6p)

Postage and packing shown in brackets

Please add 8% VAT to TOTAL

KEYTRONICS

Mail Order only.
44 EARLS COURT ROAD, LONDON, W.8
01-478 8499

DIRECT ELECTRONICS LTD.

EX-MINISTRY INSTRUMENTS & EQUIPMENT

ELECTRONIC VOLTMETER CT343.

Steel-case (20in. X 10in. X 13 1/2in.D). 110-250v/50-400Hz mains. 3in. meter 12 scales. 1.2 millivolts to 400 volts. External metering and A.C. output fac's. £55.00 (£2.00). W/o case 19in. unit only £45.00 (callers).

AF SIG. GEN. CT420 case as above. Batt op 90/1.5v (check metered) 200 to 8,000Hz continuous switched range. Output 4v/5k ohm direct or 1v/75ohm and 10mv/0.1ohm attenuated. 100 and 500Hz callibrator £85.00 (£2.00).

BC221T FREQUENCY METER in canvas carrying case P.O.A.

MINE DETECTOR No.4A KIT No.1 Ref: ZA27931/1. New in transit case. P.O.A.

RECT. SUPPLY UNIT No.25. All-weather type. 110-250vac 45/65Hz in. Conservative rating: 600vdc/80ma Super-smoothed + 12vdc 0.9A Super-smoothed + 20vac/2A screened + bias. £32.50 (£2.00). plugs extra.

DITTO No.19 Bench type 12v + 12v (or 24v)dc 3/amps £25.00 (£1.50).

CREED REPERFORATORS 7TR/3. P.O.A.

TELEPRINTER TERM UNIT MARK 4 c/w 299 AN Relay. New Cond. £40.00. Used £30.00 (£1.00).

TYPEWRITER TELEGRAPH (used but good) 9A/9B Imperial. Rollfeed. Cased £16.00 (£3.00). uncased £12.00 (callers).

GEC REGENERATOR UNIT (No. HE31105) £3.50 (50p).

A.E.E. BITUMEN POTTED TRANSFORMERS. 110-250v Pri. Scr. 45/1amp sec £3.00 (50p).

GRESHAM DITTO 240v Pri. Scr. 270-0-270/80ma + 45-0-45/40ma + 6.3-0-6.3/2.7amp sec £4.50 (50p).

PYE WESTMINSTER R/T CONTROL UNITS, MICS and SPEAKERS as seen (callers). Racks-Cabinets-Panels, etc. P.O.A.

SPECIAL ITEM

SOUND RECORDING AND REPRODUCING UNIT

Type 2. Equip A8A Rack-Mounted. Ref: 10U/16873. Also substantial qty spares (Units-Gearboxes-Sapphires, etc.). Details and prices on application.

MANY OTHER ITEMS of Test equipment/Teleprinter - peripherals/Components/Meters/Connectors, etc., in stock.


CALL ON US OR WRITE YOUR REQUIREMENTS. WHOLESALE ENQUIRIES WELCOMED. (U.K. CARRIAGE, ETC.) SHOWN. ADD 8% VAT to TOTAL. CASH WITH ORDER EXCEPT BY PRIOR ARRANGEMENT: 34 LISLE ST., LONDON WC2H 7BD
TEL: 01-437 2524

AC125 11p	BC142 35p	BF115 22p	MJ491 130p	ZTX109 13p	2N2369 14p	2N4059 10p	SIGNAL DIODES	RECTIFIER DIODES	ZENER DIODES	BRIDGE RECTIFIERS
AC126 11p	BC143 35p	BF167 23p	MJE340 45p	ZTX300 14p	2N2484 30p	2N4060 13p	BAX13 5p	BY100 15p	3.3V to 33V	250mA 16p - - -
AC127 11p	BC147 7p	BF170 23p	MJE370 72p	ZTX301 14p	2N2904 20p	40360 35p	BAX16 6p	BY126 12p	400mV 9p	1 Amp 22p 24p 27p 30p
AC128 11p	BC148 7p	BF173 23p	MJE371 84p	ZTX302 18p	2N2905 18p	40361 36p	BA16 6p	BY127 12p	1.3V 18p	2 Amp 30p 35p 45p 48p
AC141 18p	BC149C 8p	BF177 26p	MJE520 68p	ZTX303 15p	2N2906 20p	40362 38p	OA47 7p	BY133 15p	1.5W 30p	6 Amp 55p 60p 78p
AC142 18p	BC157 10p	BF178 26p	MJE521 80p	ZTX304 24p	2N2926RB	40409 50p	OA70 9p	BY130 15p	10W 55p	
AC176 11p	BC158 8p	BF179 33p	MJE2955 99p	ZTX500 15p		40410 50p	OA79 10p	BYZ10 55p	20W 70p	
AC187 12p	BC159 9p	BF180 33p	MJE3055 65p	ZTX501 15p	2N2926 8p	40411 200p	OA81 8p	BYZ10 55p		SCR-THYRISTORS
AC188 11p	BC169C 12p	BF181 33p	MPSA12 50p	ZTX502 19p	2N2926YG	40594 65p	OA85 10p	BYZ12 55p		50V 100V 400V 600V
AD140 46p	BC171 12p	BF182 33p	MPSA06 30p	ZTX503 45p		40595 75p	OA90 7p	BYZ12 55p		1 Amp 40p 42p 52p 70p
AD142 55p	BC177 18p	BF184 22p	MPSA56 32p	2N404 26p	2N3053 18p	40600 69p	OA91 7p	BYZ13 55p		3 Amp 43p 49p 75p
AD143 50p	BC178 17p	BF185 22p	MPSU06 62p	2N696 15p	2N3054 45p		OA95 7p	IN4001 5p		7 Amp - 80p 84p -
AD149 43p	BC179 18p	BF194 10p	MPSU56 78p	2N697 13p	2N3055 49p		OA97 7p	IN4004 6p		16 Amp - 82p 98p -
AD161 36p	BC182 10p	BF195 10p	OC26 40p	2N698 30p	2N3444 80p		OA98 7p	IN4006 5p		Other
AD162 36p	BC183 10p	BF196 10p	OC28 55p	2N706 12p	2N3442 140p	FETs	OA99 7p	IN4007 7p		C106D 45p. 2N3525 91p.
AF114 13p	BC184 11p	BF197 15p	OC35 48p	2N708 18p		BF244 36p	OA200 8p	IN4008 7p		2N4444 185p.
AF115 13p	BC212 11p	BF200 32p	OC36 52p	2N918 18p	2N3702/3	MPF102 30p	OA202 10p	IN4009 7p		TRIACS
AF116 13p	BC213 10p	BF257 32p	OC41 15p	2N919 40p	2N3704/5	MPF103 30p	IN914 4p	IN4010 5p		100V 400V 500V
AF117 13p	BC214 10p	BF259 32p	OC42 15p	2N929 20p	2N3705/6	MPF104 30p	IN916 6p	IN4011 5p		3 Amp 85p 99p 120p
AF118 50p	BC237 12p	BF240 30p	OC44 11p	2N930 18p	2N3705/6	MPF105 20p	IN4148 4p	IN4012 5p		6 Amp 88p 120p 150p
AF121 30p	BC238 11p	BF241 30p	OC45 11p	2N931 18p	2N3705/6	2N3819 20p		IN4013 5p		10 Amp 109p 154p 165p
AF124 30p	BC239 12p	BF279 30p	OC70 11p	2N1132 18p	2N3707 11p	2N3820 57p		IN4014 5p		16 Amp 145p 180p 200p
AF125 30p	BC307 11p	BF280 30p	OC71 11p	2N1302/3	2N3708/9	2N3821 57p		IN4015 5p		Other
AF126 30p	BC308 11p	BF281 30p	OC72 11p	2N1303/4	2N3771 17p	2N3822 57p		IN4016 5p		40430 90p. 40486 99p.
AF127 30p	BC309 12p	BF282 30p	OC73 50p	2N1304/5	2N3772 180p	2N3823 57p		IN4017 5p		40669 95p.
AF139 33p	BCY70 18p	BF283 30p	OC74 30p	2N1306/7	2N3773 220p	2N3824 57p		IN4018 5p		D.I.A.C. For use with above
AF181 45p	BCY71 22p	BF284 30p	OC81 12p	2N1308/9	2N3774 180p	2N3825 57p		IN4019 5p		triacs 21p.
AF186 48p	BD115 55p	BF285 20p	OC82 12p	2N1309/9	2N3775 180p	2N3826 57p		IN4020 5p		
AF239 38p	BD121 100p	BF286 24p	OC83 20p	2N1308/9	2N3776 180p	2N3827 57p		IN4021 5p		
BC107 9p	BD123 100p	BF287 15p	OC84 18p	2N1613 20p	2N3777 220p	2N3828 57p		IN4022 5p		
BC108 9p	BD124 65p	BF288 15p	OC200 50p	2N1711 20p	2N3778 220p	2N3829 57p		IN4023 5p		
BC109 10p	BD131 40p	BF289 15p	OC201 50p	2N2218 21p	2N3779 220p	2N3830 57p		IN4024 5p		
BC115 20p	BD132 45p	BF290 15p	OC202 50p	2N2219 20p	2N3780 220p	2N3831 57p		IN4025 5p		
BC135 17p	BD153 65p	BF291 16p	OC203 50p	2N2220 19p	2N3781 220p	2N3832 57p		IN4026 5p		
BC136 17p	BD156 60p	BF292 16p	OC204 50p	2N2221 20p	2N3782 220p	2N3833 57p		IN4027 5p		
BC137 17p	BDY60 75p	BF293 16p	OC205 50p	2N2222 20p	2N4058 15p	2N3834 57p		IN4028 5p		
BC138 17p	BDY61 65p	MJ490 220p	OC206 50p	ZTX107 12p		2N3835 57p		IN4029 5p		
			OC207 50p	ZTX108 12p		2N3836 57p		IN4030 5p		
			OC208 50p	ZTX109 13p		2N3837 57p		IN4031 5p		
			OC209 50p	ZTX110 13p		2N3838 57p		IN4032 5p		
			OC210 50p	ZTX111 13p		2N3839 57p		IN4033 5p		
			OC211 50p	ZTX112 13p		2N3840 57p		IN4034 5p		
			OC212 50p	ZTX113 13p		2N3841 57p		IN4035 5p		
			OC213 50p	ZTX114 13p		2N3842 57p		IN4036 5p		
			OC214 50p	ZTX115 13p		2N3843 57p		IN4037 5p		
			OC215 50p	ZTX116 13p		2N3844 57p		IN4038 5p		
			OC216 50p	ZTX117 13p		2N3845 57p		IN4039 5p		
			OC217 50p	ZTX118 13p		2N3846 57p		IN4040 5p		
			OC218 50p	ZTX119 13p		2N3847 57p		IN4041 5p		
			OC219 50p	ZTX120 13p		2N3848 57p		IN4042 5p		
			OC220 50p	ZTX121 13p		2N3849 57p		IN4043 5p		
			OC221 50p	ZTX122 13p		2N3850 57p		IN4044 5p		
			OC222 50p	ZTX123 13p		2N3851 57p		IN4045 5p		
			OC223 50p	ZTX124 13p		2N3852 57p		IN4046 5p		
			OC224 50p	ZTX125 13p		2N3853 57p		IN4047 5p		
			OC225 50p	ZTX126 13p		2N3854 57p		IN4048 5p		
			OC226 50p	ZTX127 13p		2N3855 57p		IN4049 5p		
			OC227 50p	ZTX128 13p		2N3856 57p		IN4050 5p		
			OC228 50p	ZTX129 13p		2N3857 57p		IN4051 5p		
			OC229 50p	ZTX130 13p		2N3858 57p		IN4052 5p		
			OC230 50p	ZTX131 13p		2N3859 57p		IN4053 5p		
			OC231 50p	ZTX132 13p		2N3860 57p		IN4054 5p		
			OC232 50p	ZTX133 13p		2N3861 57p		IN4055 5p		
			OC233 50p	ZTX134 13p		2N3862 57p		IN4056 5p		
			OC234 50p	ZTX135 13p		2N3863 57p		IN4057 5p		
			OC235 50p	ZTX136 13p		2N3864 57p		IN4058 5p		
			OC236 50p	ZTX137 13p		2N3865 57p		IN4059 5p		
			OC237 50p	ZTX138 13p		2N3866 57p		IN4060 5p		
			OC238 50p	ZTX139 13p		2N3867 57p		IN4061 5p		
			OC239 50p	ZTX140 13p		2N3868 57p		IN4062 5p		
			OC240 50p	ZTX141 13p		2N3869 57p		IN4063 5p		
			OC241 50p	ZTX142 13p		2N3870 57p		IN4064 5p		

The Greenwood guide to professional soldering.


The Ersa Multitip. A top-quality iron that's ultra-light, offering reliability so necessary to achieve constant production flow. A range of different shaped tips simply

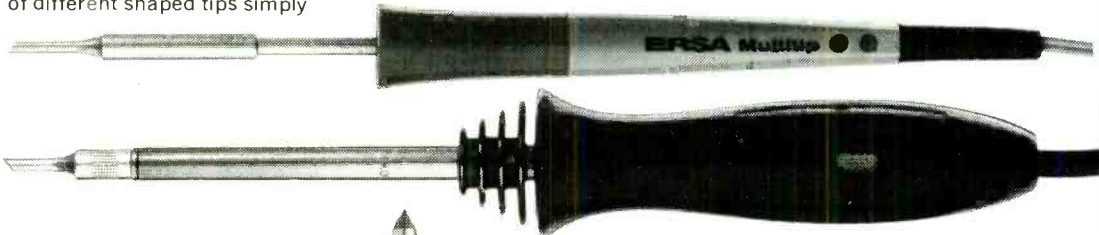push onto the stem of the iron. It has the unique advantage that you can change the element in seconds.



The Iso-Tip. A safe, high-powered iron which works anywhere without a mains lead. The breakthrough? Nickel Cadmium cells that are re-chargeable. (A charging stand is included for 240v or 115v A.C.) Each charge gives at least 60 soldering joints. Weight? Only 6oz.

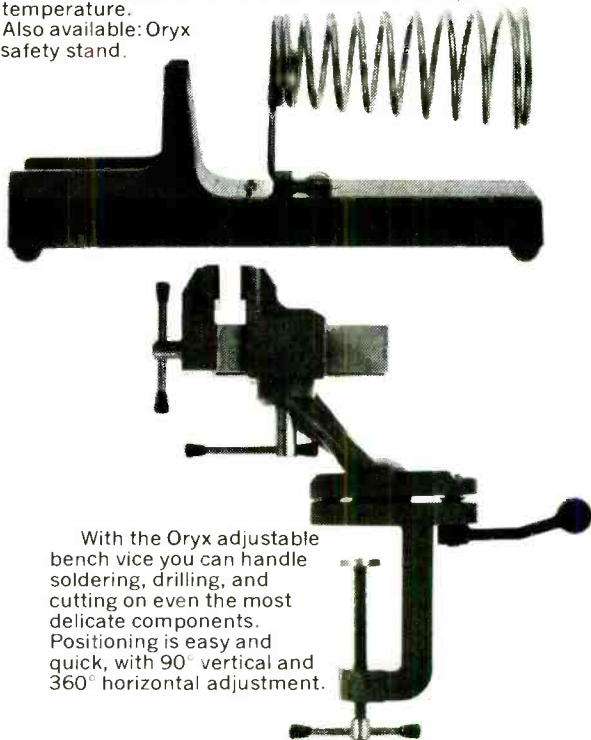The Oryx 50. A temperature controlled mains soldering iron. (Temperature control within $\pm 2\%$.) Adjustment (200°-400°C) can be made whilst iron is operating using the same tip. Light, compact and easy to handle. A large 50W element loading gives rapid heating and high performance with constant tip temperature. Also available: Oryx safety stand.



The Ersa Sprint. Unique - it heats up to maximum temperature in only 10 seconds, and is the lightest gun on the UK market. Ideal for the service-man. With its lightweight (only 7oz.) and compact construction, it can be manoeuvred in even the most awkward areas.

With the Oryx adjustable bench vice you can handle soldering, drilling, and cutting on even the most delicate components. Positioning is easy and quick, with 90° vertical and 360° horizontal adjustment.

Oryx SR3A desoldering tool. Ideal where components are tightly grouped. Instantly removes unwanted solder from printed circuits etc. Accurate, reliable, speedy, and safe.



Greenwood Electronics offer a range of highly advanced products specifically for professional soldering applications. For more detailed information about the comprehensive Greenwood range, write to address below.

Greenwood Electronics

Portman Road, Reading RG3 1NE.
Tel: Reading (0734) 595844. Telex: 848659.

Due to expansion we are seeking additional distributor/stockists.

What's new in Soldering Chemicals?

Multicore's R & D Laboratories are still making news—three important new chemicals for electronics manufacturers.

MULTICORE PC 26 ROSIN FOAM FLUX

A completely new general purpose liquid soldering flux particularly suitable for the automated soldering of all types of printed circuits. PC 26 provides a unique combination of desirable properties.

- Complies with U.K. Ministry Flux Specification D.T.D. 599A.
- Eliminates "icicles" and "bridging".
- 0.5% max. halide content and yet gives better soldering than non-approved fluxes with high halide contents.
- Leaves negligible flux residues so p.c. boards are dry after soldering, can be handled and inspected easily and have better sales appeal.

MULTICORE PC 81 SOLVENT CLEANER & FLUX REMOVER

A unique blend of polar and non-polar solvents formulated for degreasing electronic hardware prior to soldering as well as for removing rosin flux residues including ionizable activators after soldering. Its intermediate boiling range of 71 to 80°C and selective solvency make it ideal for vapour degreasing.

The boiling range of PC. 81 is higher than fluorinated solvents (approx 46°C) and lower than either trichloroethylene (87°C) or perchloroethylene (121°C). Also its solvency properties for rosin flux removal are superior to fluorinated solvents without in any way affecting most electronic hardware. As a result, PC. 81 solvent will perform its vapour cleaning function longer and more effectively than fluorinated solvents whose vapour condensation ceases at 46°C with a consequent end to flux removal.

Solvent evaporation rate is substantially lower than that of the fluorinated solvents, making it more economical to use in open tanks and vapour degreasers.



Multicore PC. 81 is a highly stabilized solvent blend, extremely resistant to thermal or chemical breakdown during prolonged heating or as a result of the introduction of activators from the solution of rosin during its working life. Its relatively narrow boiling range and high stability make it readily useable again without property changes after distillation.

PC. 81 can also be used for cold cleaning and to reinforce ultrasonic cleaning. Even though its toxicity is relatively low, well ventilated areas are required.

PC. 81 is expected to be particularly welcome as it is non-flammable and non-combustible under the new British "Highly Inflammable Liquid" Regulations.

Supplied in one gallon metal cans and 45 gallon steel drums.

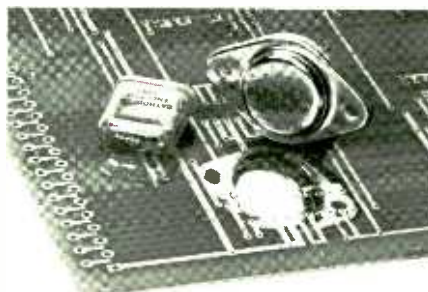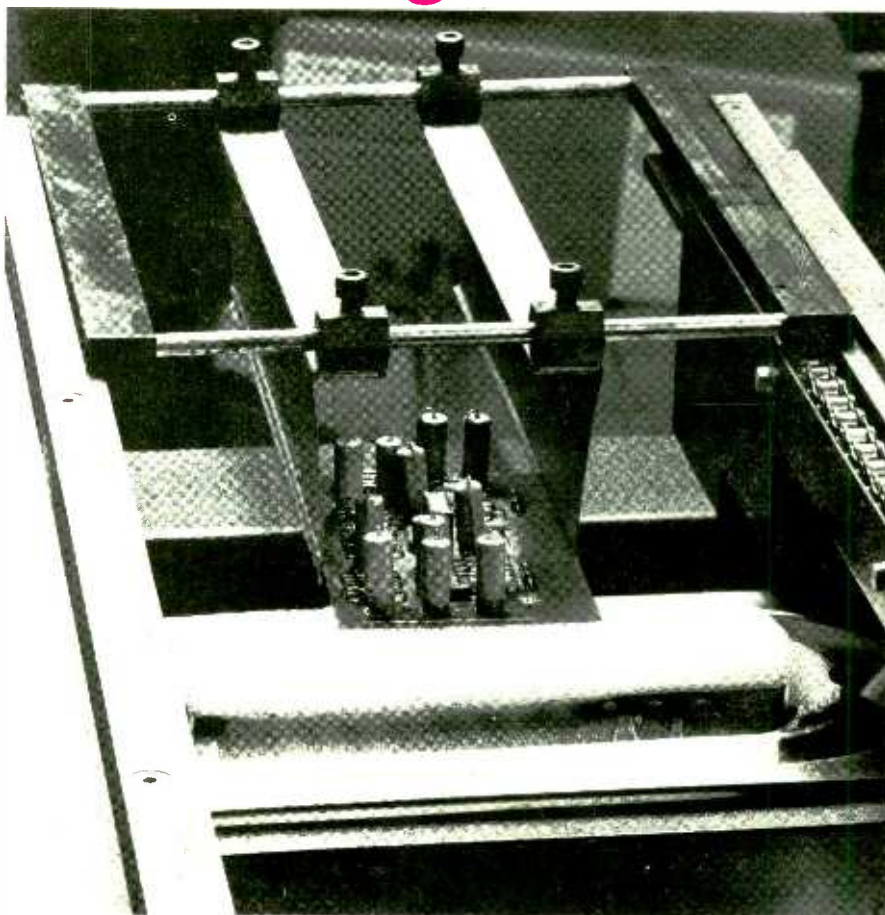Specific Gravity (20°C) — 1.256
Boiling Range ————— 71–80°C
Toxicity (TLV) ————— 340 ppm
Residue on Evaporation— less than 10 ppm



MULTICORE PC 54 CONFORMAL COATING

Fully meets the requirements of the new U.K. Defence Standard 59-47/issue 2 and U.S. Spec. MIL-I-46058C, which are becoming mandatory for the protection of many electronics assemblies against adverse environment, contamination and attack by chemicals.

PC. 54 is a two-part epoxy resin system which is conveniently mixed in equal parts by volume. It may be applied by dip, spray or brush to either one or both sides of p.c. boards and components where it forms a thin tough coating after curing. PC. 54 will dry in 1 hour under normal ambient conditions and develop its full properties after several days at room temperature or it may be cured in 2 to 4 hours at 65°C. A glass fibre brush can be used to remove the coating locally to enable rework and repair.

Other Multicore Soldering Chemicals include a complete range of liquid fluxes and the following special chemicals.

PC 2 Multicore Tarnish Remover

Cleans tarnish from metal surfaces prior to soldering.

PC10A Activated Surface Preservative

Applied after pre-cleaning, preserves solderability and need not be removed.

PC 10D

A special version of PC 10A for application by roller coating machines.

PC 90 Peeloff Solder Resist and PC 91 Thinners

A temporary solder resist for edge-connector contact areas etc. Replaces masking tape.

PC 41 and PC 43

Solder Bath dross inhibitors.

PC 52 Protective Coating

One-part conformal coating. Can be soldered through.

PC 70 Thinners

Compatible Solvent blend for use with all rosin fluxes, PC 10A and PC 52.

Please write for Technical Bulletins on your Company's letterhead for products which interest you to:



MULTICORE SOLDERS LIMITED

Hemel Hempstead, Herts. HP2 7EP

Tel: Hemel Hempstead 3636 Telex 82363