Wireless World

Australia A\$ 2.40 Canada C\$ 4.25 Denmark DKr. 20.25 Germany Dm. 6.00 Greece Dr. 125 00 Holland Df. 5 Haly L 2300 Norway NKr. 2 Sigapore M\$ 5.50 Stain Pts. 180.00

APRIL 1981 60g

70 years of publication Active cross-over networks Low-noise amplification



Opto-electronic contact breaker



Soldering blind just burns up profit.

Given that some metallic substances are more easily soldered than others, and that there are significant differences both in the speed with which they can be soldered and in the strength of adhesion of the solder to their surfaces, it is clearly necessary to make absolutely sure that the procedure used to solder components is correct. Testing for solderability greatly reduces the risk of failed joints and that can mean appreciable savings on rejects.

Multicore, the world's leading authority on soldering, has developed a simple-to-use piece of equipment designed to assess solderability. It is called a MUST – Multicore Universal Solderability Tester – and it really is a must if you want to avoid the costly problems of inefficient soldering.

The built-in microprocessor takes the complex force/time curve and reduces it to just two values, making the application of the sophisticated test method to quality control particularly simple.

The MUST

can be used

to evaluate the

solderability of any

plain or plated metal

in sheet, strip or wire

form. It is, however, ideal

for use with electronic component

terminations, metal clad laminate,



printed circuit boards and platedthrough holes.

It can be used for the Edge Dip Test that appears in IPC-S-801, EIA RS-178 and EIA RS-319 Method 2 for evaluating quality of wetting, and

evaluating quality of wetting, and for the Globule Test as described in many national and international standards including IEC 68-2-20, BS 2011: 2T and DIN

40046 to measure wetting speed.
This speed, together with the wetting force, may also be measured by the quick and easy addition of ting balance.

easy addition of a wetting balance. The Multicore Universal Solderability Tester could make a big difference to your soldering operations and to your profits. For the eye-opening facts use the reader reply service, cut the coupon or contact Multicore direct.



WIRELESS

VOL 87

NO 1543

The biggest name in solder worldwide

Please send me full details on the MUST☐ Please telephone me☐
Name Position Company Address
Telephone

Sales Department, Multicore Solders Limited, Maylands Avenue, Hemel Hempstead, Hertfordshire HP2 7EP. Telephone (0442) 3636. Telex 82363.

Wifeless World

PRII 1981 60m

70 years of publication

Active cross-over networks

Low-noise amplification



Opto-electronic contact breaker



TESTING MOBILE RADIOS?

. . . catch this bus with Farnell

and arrive economically at an efficient ATE workstation.

Comprehensive testing under low cost desk computer control.

Manual systems too.






INTERFACE WITH US NOW!

Ask for details from:

WIRELESS WORLD APRIL 1981

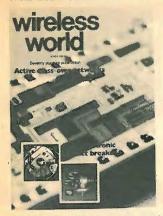

Front cover shows (inset) de-tails of the opto-electronic contact breaker described in this issue on the background of a Marconi Space and Defence Systems hybrid microelectronic circuit.

IN OUR NEXT ISSUE

Digital capacitance meter uses the timed charge-injection method of measurement, with an input pro-tection circuit, optimized to reduce errors.

Wien oscillator is a new design by Linsley Hood, using a different connexion of the standard Wien bridge to give a total harmonic distortion of 0.001%.

Active television deflector receives tv signal, amplifies viewers in no-signal reception areas.

Current issue price 60p, back issues (if available) £1.00, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hop-ton Street, London SE1. Available on microfilm; please contact editor.

contact editor.
By post, current issue 96p, back issues (if available) £1.50, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.
Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton Surrey SM2 5AS.
Telephones: Editorial 01-661

Telephones: Editorial 01-661 3500. Advertising 01-661 3129. Telegrams/Telex: 892084

Telegrams/Telex: BISPRS G. Subscription rates: 1 year £10.00 UK and \$33.80 outside UK.

Student rates: 1 year £5.00 UK and \$16.00 outside UK. Distribution: 40 Bowling Green Lane, London EC1R ONE. Tele-

phone 01-837 3636.
Subscriptions: Oakfield House,
Perrymount Road, Haywards
Heath, Sussex RH16 3DH. Telephone 0444 59188. Please notify

usa change of address.
USA mailing agents: Expediters of the Printed World Ltd, 527 Madison Avenue, Suits 1217, New York, NY 10022. 2nd-class postage paid at New York.

© IPC Business Press Ltd, 1981 ISSN 0043 6062

wireless

ELECTRONICS/TELEVISION/RADIO/AUDIO

APRIL 1981 Vol 87 No 1543

37 The next seventy years

38 Opto-electronic contact breaker by J. R. Watkinson

41 More on active cross-over networks by David Read

44 News of the month

Flat c.r.t. from Sinclair. Custom-built I.s.i. Microcomputers in space

48 Circuit ideas Pre-amp and multi-section control. Divide by (2n - 1)

> 51 Radio observation of the 'active' sun by R. A. Ham

55 Letters to the editor Artificial intelligence. Commercial broadcasting.
Designing with microprocessors.

59 Dividing by fractions by Gilbert Pearson

62 Phase measurements with an oscilloscope by I. D. MacArthur

65 Wireless World, 1911-1981

66 Designing with microprocessors - 7 by D. Zissos

70 World of amateur radio

71 Introduction to low-noise amplifier design by A. Foord

> 74 Magnetic recording review - 2 by J. Moir

79 Surface acoustic wave devices - 2 by R. J. Murray and P. D. White

> 83 Multipath distortion by Pat Hawker

86 Novatexts: amplitude sensing and control by P. Williams

88 New products

90 Sidebands by Mixer

Electronic Brokers-Europe's Premier Test Equipment Company offer SUPERLATIVE USED EQUIPMENT CALIBRATED TO ORIGINAL SPEC

Electronic

Unless otherwise stated all test equipment sold by us carries a 12 month warranty; For VDUs and Teletypes we offer a 90 days warranty, and computers are offered with on site acceptance and diagnostic tests (which may qualify them for independent ongoing maintenance). When you buy from Electronic Brokers you know the equipment is in 'top notch' condition. It is refurbished in our Own service laboratories and checked to meet the original manufacturer's sales specifications. And it's serviced by our own highly qualified technicians.

A copy of our Trading Conditions is available on request.

Electronic Brokers |

..... April 1981..... Latest Test Equipment.....

AND MULTIMETERS



Fluke. 883AB AC/DC Differential Voltmeter. 20Hz-100KHz. 1mV-

Philips.
PM2454B AC Millivoltmeter. 10Hz-12MHz.
Im/-300V £195.00

ANALYSERS

Biomation. 1650D 16 Channel Logic Analyser. Displays Timing, Map, Nex, octal. Clock rate upto

Dymar. 1771 LF Wave Analyser. 20Hz-50KHz. 30µV-300V General Radio: 1911A Sound and Vibration Analyser. C/W Graphic leve recorder. 4.5Hz-25KHz. 1/3 or

£950.00 _ 8600A/8601A sweeper. 0.1-110MHz

1L5 Spectrum Analyser. 10Hz-1MHz ..**£750.00** 491 Spectrum Analyser. 10MHz-2GHz direct. Up to 40GHz with optional mixers...**£4150.00**

BRIDGES & COMPONENT

Boonton. 63H Inductance Bridge. 0-110mH. Bridge £1250.00 frequency 5-500kHz £1250.00 280AP VHF Q Meter. Q 20 to 25,000. 210-610MHz £650.00

General Radio

1607 A Transfer Function and Immitance Bridge, 25-1500MHz. Direct reading...**£750.00**

ANALOGUE VOLTMETERS

TF1313/2M10.25% LCR Bridge. 0.1μH-110H, 0.1pF-100μF. 3mΩ-110MΩ. 1 and 10KHz

Rohde & Schwarz. KRT (BN5100) Capacitance Meter. 1pF-100µF. 2.2-285KHz. <u>\$395.00</u> LRT (BN6100) Inductance Meter. 1pH-100µH. 2.2-285KHz. <u>\$395.00</u>

Wayne Kerr.
B221 0.1% LCR Bridge. 0.0002pF-11.1μF,
9Ω-500GΩ, 0.9mH = 5MH, 2pp-111mv

E225.00
B641 0.1% LCR Bridge. 0.002pF. 50,000μF,
200nH-5MH, 2mΩ-50,000MΩ, 20pu-500v

E445.00

CALIBRATION EQUIPMENT

Advance.
OFS2B Off Air Frequency Standard. O/P 1 and Bradley. 125B AC Calibrator. 0-511V in 0.1V steps @

50-60-400Hz.....

Hewlett Packard.

741B DC Voltage Source and AC/DC Differential Voltmeter..... £695.00 1 Constant Amplitude Generator. 350KHz-

DVM's AND DMM's

resistance, 1µV resolution. 30 day warranty

volts and current, resistance £115.00 PM2527 4½ Digit DMM. AC/DC volts, current and resistance. 10µV resolution. True RMS

Solartron.
A243 5½ Digit DMM. AC/DC volts, resistance.

1µV resolution. 30 day warranty........£375.00
7055 Microprocessor
DMM. Scale length
200,000. AC/DC volts,

Weston. 4440 3½ Digit DMM. AC/DC volts, DC

FREQUENCY COUNTERS

7 digits. Mains / battery operation £3; 1912A Frequency Counter. 5Hz-520MHz

digits....PM6614 Frequency Counter. 10Hz-520MHz £450.00



MULTIMETERS

8 MK 5 Multimeter 20KΩ/volt... Super 50 Selectest, 20KΩ/volt...

OSCILLOSCOPES

Hewlett Packard

Hewlett Packard. 1707A Dual Trace Portable Oscilloscope. DC — 75MHz Full delayed sweep. 30 day £450.00



1707B Dual Trace Portable Oscilloscope. DC — 75MHz. 10mV-5V/div. Full delayed and intensified sweep. Trigger hold off

Philips.
PM3212 Dual Trade Portable Oscilloscope. DC 25MHz. 2mV-10V/div



432 Dual Trace Portable Oscilloscope. DC — 25MHz. 1 mV sensitivity. 20nS-55. Auto setting mains input 100-250V

464 Dual Trace Portable Storage Oscilloscope, DC — 100MHz. 5mV-5V/div. Full delayed sweep. Max writing speed 110 div/µS£2250.00

465 Dual Trace Portable Oscilloscope. DC — 100MHz, 5mV-5V/div. Full delayed sweep £1195.00

VU-Data.

..... April 1981.... Latest Test Equipment.....

OSCILLOSCOPE PROBES EB90 X1 Probe. 1.2 mtr length DC - 20MHz EB91 X10 Probe 1-2 mtr length DC —

£11.00 100MHz..... EB95 X1, X10 Probe. 1.2 mtr length DC 10MHz or DC — 100MHz..... £15.00 **POWER SUPPLIES**

Advance.
PMA47 0-15V preset @ 3A.....
PMA50 0-15V preset @ 5A.....
MG5-60 5V @ 60A switching...
MG5-20 5V @ 20A switching...
MG5-10 5V @ 10A switching... MG24-12 24V @ 12A switching... .£130.00

RECORDERS

Hewlett Packard. 2FA XYY A3 Plotter. 2 Pens on Y axis. Internal X sweep. Electric paper grip£725.00 S.E. Labs. 3006/12 12 Channel UV Recorder. Grid and 5006/12 12 Channel UV Recorder. Grid and

drive upto 5 metrs/sec. 12" paper£1100.00

MC641 6 Channel Chart Recorder, 1mV-

Yokagawa. 3047 2 Channel Chart Recorder. 0.5mV-100V.

SIGNAL SOURCES

Avo.

HF135 AM Signal Generator. 100KHz240MHz. 1μV-100mV into 75Ω. AM 0-30% @
1KHz. £190.00

HF136 AM/FM Signal Generator. 4.0-120MHz.
0-100mV in 20dB steps plus fine control. O/P
Z = 75Ω. £410.00

Hewlett Packard. 203A Variable Phase Oscillator, 0.005Hz-60KHz, 0-360°. 60KHz. 0-360°. £450.00
4204A Decade LF Oscillator. 10Hz-1MHz.
1mV-10V into 6000. £695.00
606B AM Signal Generator. 50KHz-65MHz.
AM 0-95%. £850.00
612A AM/PM UHF Generator. 450-1230MHz.
0.1µV-0.5V. £775.00
616B UHF Signal Generator. 1.8 to 4.2GHz. Int £450.00

Marconi.
TF144H/4 AM Signal Generator. 10KHzE750.00



£550.00

TF995B/5 AM/FM Signal Generator. 200KHz-220MHz. 1µV-200mV. Narrow deriation for mobiles. £695.00 TF1370A Wide Range RC Oscillator. 107 100Hz. Sine wave, square wave upto 100KHz £275.00

TF2002B AM/FM Signal Generator. 10KHz-88MHz. 0.1µV-1V. 20Hz-20KHz Mod

frequency £1200.00

Philips.
PM5108 Function Generator. 1 Hz-1MHz.
Sine, square and triangle. Triangle O/P
.£250.00
PM5127 Function Generator. 0.1HZ-1MHz. PM5127 Function Generator. 0.112 £395.00
Sine, square and triangle £395.00
PM5167 Function Generator. 1MHz-10MHz.
Sine, square, ± pulse, ramp and triangle £500.00

PM6456 Stereo Generator, Separate L and R Radiometer.

Schulmberger. 4000C Frequency Synthesizer. 300Hz-520MHz. Max O/P IV into 50Ω. 0-139.9dB

Tektronix. 2101 Pulse Generator. 2.5Hz-25MHz. + and £375.(

- O/P

SOUND LEVEL METERS

Bruel and Kjaer.
2203 Sound Level Meter. C/W 4145 1"
Microphone. A, B, C, weighting.......£395.00

General Radio. 1933 Sound Level Meter C/W 1935 Cassette Data Recorder, 10-130dB, ABC weighting

£195.00

TRANSMISSION **MEASURING EQUIPMENT**

Marconi.

OA2805A PCM Regenerator Test Set.
Comprised of TF2801/2, TF2802/2 and
TF2823. For use on systems at 1.536 and
2.048Mbits. £2700.00
TF2807A PCM Multiplex Tester. Comprises TF2807 A PCM Multiplex 1636... Noise / Sinewave source and level meter £1500.00

TF2332 AF Transmission Test Set. 20Hz-20KH:



D2040 Selective Level Analyser and Voltmeter, 10Hz-60KHz. —110dB to + 50dB. 3µV-300V Lin and log indication. 5 digit frequency readout

D2072 + W2072 Level Meter and Oscillator. 50KHz-100MHz. -- 110dB-0dB. Receive bandwidth 3.1 and IOKHź

Scale expander:
SPM-6 and PS-6 Level Measuring Set.
6KHz-18.6MHz. — 110dB to + 20dB. Mains L
battery operation.£2150.00
Andmat (PSM-4 2MHz Automatic PCM Testing System) composed of the following
PCM-1 PCM Test Set, PDA-64 PCM Signalling PCM-1 PCM Test Set, PDA-64 PCM signalling Analyser, PMD-1 Digital Level and Noise Measuring System, PDG-1 Digital Signal Generator, PDA-1 PCM Digital Signal Analyser, PSM-4 Level Measuring Set, MU-4 Scanner, R1-1 computer interface......£6500.00

MISCELLANEOUS

Avantek. UA101 RF Modular Amplifier. 5-500MHz,

Avo. VCM163 Valve Tester.....

Dymar. 1581 RF Power Meter. DC — 500MHz. £350.00

Ferrograph.
RTS2 Recorder Test Set Measures Wow &

C/W Auxiliary Test unit. Superb condition......

Hewlett Packard.
335E Programmable Attenuator. 0-12dB. DC
-10GHz, 50Ω £75.00
432A Power Meter with 478A Thermistor Head. 10MHz-10GHz. 100µW-10mW £450.00

Marconi. TF791D Deviation Meter. 4-1024MHz

£195.00
TF893A AF Power Meter. 1mW-10W£185.00
TF2300 AW/FM Modulation Meter.
0.5-1200MHz £375.00
TF2337 Automatic Distortion Meter. Frequncy range 400Hz and 1KHz 0-30% in 4 ranges £245.

Rohde and Schwarz. Radiometer. BKF10 Automatic Distortion Analyser. 20Hz-20KHz. 0.02%-10% £1100.00 20KHz. 0.02%-10%

EVV 300 Microprocessor Development Kit.

Based on Motorola 6800 TTY interface

£235.00

M515 Main Frame C/W FG504. 0.001Hz-

WW-200 for further details

Electronic Brokers Limited 61/65 Kings Cross Road London WC1X 9LN England Telephone: 01-278 3461 Telex: 298694 Elebro G

peripherals. Established 14 years ago we have pioneered the second user



Electronic Brokers-Europe's Prem ier Used Computer Company offer

SUPERLATIVE U SED COMPU QUIPMENT-AS NEW CONDI

PDP11 SYSTEMS



PEC PDP11/34A System complete with 256kB MOS memory DL 11 W Asynchronous Interface / Line Clock, KY11-LB Programmers Panel, VT100 Terminal, 2 x RL01 5-meg Disk Drives, D211A 8-Line multiplexer, FP11A Floating Point, 1804 H960 Cabinet. . . . £17,500.00

PDP11/34A System complete with 256KB MOS memory, 2 x RK07 28-meg Disk Drives, TMB11 magnetic tape station, DZ11 16-line multiplexer, Data system cabinet and expander box, LA36 console terminal.... £27,750.00

PDP11/60 System with 2 RK07 PDP11/60 System with 2 holds
Disk Drives, choice of console
P.O.A.

PDP11/03 System (desk-mounted) 20KW MOS, RX11 dual floppy disk drive and control, 3 serial interfaces, LA180 Printer, VT100 Console terminal. .

PDP11 C.P.U.s

DEC.	
PDP11/03-SD Processor in 3½" chassis complete with 16KW MOS	
memory and E1S option.	
BRAND NEW - ONLY £1495.0	0
PDP11/04 Processor in 101/2" chassis complete with 16KW MOS	
memory and DL11W Interface.	
BRAND NEW (can be enhanced to 28KW) £4500.0	0
PDP11/34 in 10½" chassis complete with 64KB MOS memory	
£5500.00	
PDP11/34 Processor (non-A) in 101/2" chassis complete with 128KB	

MOS memory, DELLAW interface and programmers from	
	£5900.00
PDP11 MEMORY	
FDF IT IVIEIVIOR I	
DEC.	
MFIIL 8KW core memory c/w 9-slot system unit	E075 00
MM11L 8KW core memory	. £/95.00
MM11LP 8KW parity core memory	. £750.00
MM11DP 16KW core (ex DEC-maintained 11/34 systems	1
BARGAIN OFFER — ONLY	E30E 00
DANGAN OFFER - ONE I	2375.00
MM11UP 16KW Parity core memory complete with 9-slo	
runit	£1500.00
MM11UP 16KW parity core memory (pre-requisite MF111	
4401 to 1/107/1406	
MS11JP 16KW MOS memory	£6/5.00
MSV11C 16KW MOS memory (LSI11)	£495.00
MJ11-BE 64KW 11/70 memory	F4500 00
MK11-BE 64K/Y/ MOS memony for 11/70	E30E0 00
MK11-BE 64KW MOS memory for 11/70	23730.00
MS11-MB 256KB ECC MOS memory for 11/44 (NEW)	£3942.00

DISKS



DEC.	
RK05 J add-on disk drive 21/2 med	a
Exchangeable cartridge type.	
From£1850.	.(

0
0
٩.
0
0
0
0
0

MAGNETIC TAPE

DEC.Available from time to time — TU10, TU45, TE16 TS03 etc.

PDP11 OPTIONS

	I DI II OI IIOIAS	
	DEC.	
	AA11D VT01 Controller with 4-slot System Unit	£125.00
	DD11A 4-slot System Unit	£125.00
	DD11B 4-slot System Unit	£150.00
	DD11-DK 9-slot backplane	£465.00
	DL11 Serial Interface	
	DL1 I WA/B Serial Interface/Line Clock	
,	DR11C General Purpose Interface	
	DRV11B 16-bit Parallel Interface	£225.00
	DZ11A 8-line E1A MUX	
	FP11A Floating Point	
	KL11 TTY Interface	£150.00
	KW11L Real Time Clock	
	KW11P Programmable Clock	
1	M105 Device Selector	£30.00
	M792 ROM Diode Matrix	
	M920 Unibus Connector	
	M9301-YB Bootstrap	

POWER SUPPLIES

DEC.
H720 Power supply for BA11 Expander Box, BRAND NEW SURPLUS.
£175.00

PDP8A C.P.U.

DEC. PDP8A Processors, systems and add-on memory usually available.

PDP8A MEMORY
DEC.
MM8AA 8KW Core
MM8AB 16KW Core

PDP8E CPU, MEMORY, OPTIONS

DEC.	
DP8EB Communications Adaptor	£395.00
KA8E Positive 1/0 Bus	£95.00
KD8E Databreak	£145.00
KL8E Asynchronous Interface	£250.00
KP8E Power fail/auto restart	. £95.00
MM8E 4KW Core memory stack	£350.00
VT8E Set graphics Control Modules	£250.00
	DPSEB Communications Adaptor KASE Positive 1/0 Bus. KDSE Databreak KLSE Asynchronous Interface KPSE Power fail/auto restart

TERMINALS



LA36 DECwriter 11 Keyboard Printer Terminal. The Terminal that has become an industry standard, with 132 column upper/lower case printing and switch-selectable speeds of 10, 15 & 30cps. Available with either 20mA or RS232 Ferminal featuring full upper/lower case ASCII character set, 24 × 80 case ASCII Character Set, 24 x 8d display, auxiliary keypad, direct cursor addressing and tabulation, scroll or hold screen mode with X-off facility, 9 switch-selectable baud rates (75-9600 baud) choice of 20mA or RS232 interface.

BRAND NEW SURPLUS.

VT100 — Also available from time to time, DEC's latest 132 column display terminal. Please enquire for latest price and delivery £750.00



Heavy Duty Matrix printer with 64 ASCII upper case character set. 165 cps operation. 132 print positions with adjustable tractor feed Parallel input. ONLY.£495.00

BRAND NEW - LOW COST MATRIX PRINTER IDEAL FOR MICROPROCESSOR USERS SUCH AS HOBBYISTS & EDUCATIONALISTS OR ANY LOW-BUDGET APPLICATION



characters (12 cpi and 6 cpi) 30 cps print speed with 1-line

Standard parallel (Centronics-type) interface Optional interfaces available for RS232, IEEE488, Tandy, PET,

(Mail order total..... GE Terminet 1200.

RO printer, 80 columns, tractor feed, upper/lower case, ASCII, 20mA

£325.00

Thermal printer, 80 columns, 30 cps silent RO with parallel TTL input

Tally 1602.

Matrix printer, parallel input, upper/lower case, tractor feed, as new £995.00

ICL-type keyboard. £50.00 £20.00 £25.00 £30.00 Remote reader control



Low Cost Printer Offer.
Teletype 33 printer mechanism including case but no keyboard or electronics, 64 upper case ASCII,

electronic hobbyist ONLY . £85.00 Termiprinter 7075. Impact printer, upper/lower case, pin feed, RS232£325.00

Texas.733 ASR terminal utilising high performance twin cassette drive for /33 ASK terminal utilising high performance twin cassette diffast time-saving transmission and off-line storage.

* Silent operation

* Switch-selectable transmission speeds 10, 15, & 30 cps

* Full tape editing capability

* High-speed duplication and rewind

* Standard RS232 interface



745 Portable Data Terminal carrying case. Total weight only

April 1981 Latest Computer Equipment

PAPER TAPE PUNCHES





The top quality punch that has become an industry standard. Asynchronous 75cps operation. Adjustable for punching 5, 6, 7 or. 8 level tape. Self-contained desktop unit incorporating supply and take-up spools, chad box, and TTL-compatible control logic ... £650.00

KEYBOARDS NEW



KB771 Superb 71-station ASCII keyboard incorporating separate numeric/Cursor control pad and numenc/Cursor control pad and installed in custom-built steel enclosure with textured blue enamel finish. Ideal for the VDU builder. Case dimensions: 1714" x 7½" x 3\{\}^2\]. Total weight 4kg. PRICE.....£85.00 Mail Order Total.....£103.50

KB756 56-station ASCII keyboard mounted on P.C.B..... Mail Order Total. KB756MF as above, fitted with metal mounting frame for extra Mail Order Total KB710 10-key numeric pad, supplied with connecting cable... Mail Order Total KB701 Plastic enclosure for KB756 or KB756MF. Mail Order Total £18.00

KB702 Steel enclosure for KB756 or KB756MF KB15P Edge connector for KB756 or KB756MF Mail Order Total. DC-512 DC convertor to allow operation at 5V only (plugs in to P.C.B.) £7.50

Discounts available for quantities

PROGRAMMABLE CALCULATORS

MODEMS

Racal Milgo. Modem 26 Isi 1200/2400 baud, 2 or 4 wire, full/half duplex

GENERATORS




H1000 The low, low priced H100 The low, low prices teletypewriter-compatible video display terminal, offering your choice of transmission speeds up to 9600 baud as well as parity generation and checking. 12 x 80 display upper case ASCII, RS232 intention, processor for the prices of the prices interface, choice of baud rate: SUPER VALUE£199.00

H2000 Superb spec. including full XY cursor addressing and edit facility, 27 x 74 display, upper case ASCII, RS232 interface, switch-selectable baud rates£299.00

H2000C NOW ALSO AVAILABLE

Modular One Now with upper/lower case, XY cursor addressing, 24 x 80 line display, dual intensity detachable keyboard, choice of 8 transmi rates up to 9600 baud £399.00

MONITORS

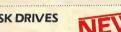

★ Capacity (unformatted): 110Kb (single density) 220Kb (double

density)
 Transfer rate: 125/250 kilobits/sec.
 Average access time: 463ms.
 Read/Write and Write Protect electronics
 Power requirements + 5VDC + 12VDC Dimensions 53* X3* X8* weight 3lbs
 Supplied complete with technical manual.

Supplied complete with technical manual.

Application notes are available on interfacing the SA400 to Intel

£195.00



Shugart SA450.
Double-sided, double density minifloppy providing 440KB unformatted storage capacity, yet the same compact size and weight as the SA400......£299.00

Shugart SA801. 8" FLOPPY (NEW)

★ Capacity (unformatted):
400Kb (single density)
800Kb (double density)
★ Transfer rate: 250/500 kilobits/

Average access time: 211ms


 Read/Write and Write Protect
electronics

Power requirements
+ 24VDC + 5VDC — 5VDC
Dimensions 48" × 9½" × 14½" Supplied complete with technical

Hours of Business: 9 a.m.-5 p.m. Mon-Fri. Closed lunch 1-2p.m. ADD 15% VAT TO ALL PRICES Carriage and Packing charge extra on all items unless

W/W-201 for further details

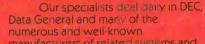Electronic Brokers Limited 61/65 Kings Cross Road London WC1X9LN England Telephone: 01-278 3461 Telex: 298694 Elebro G



specialist buyer and seller of used

manufacturers of related systems and peripherals such as Teletype, Hazeltine, Texas, Hewlett Packard, Textronix All computer equipment offered by Electronic Brokers is. maintenance eligible by the original manufacturer.

Our customers come from the fields of industry, education, research, government and general commerce. We have met their needs time and time

quick replacement, low cost development systems, additional capacity for existing equipment, or a cost effective used configuration - we are only a phone call or telex away

Call us on 01-278 3461 and speak to one of our skilled sales specialists familiar with your equipment needs





!service

ance

hi!com

Low cost excellence

with a 2 YEAR guarantee



AG 203 LOW DISTORTION **OSCILLATOR** £110

AG 202A SINE-SQUARE OSCILLATOR £60



AG203 Low Distortion Oscillator — 10Hz to 1MHz in 5 ranges — < 0.1% distortion — very flat O/P to 7V r.m.s. sinewaye from 600 ohms, squarewave 10V pp - Ext. Sync. - > 60dB's of variable

AG202A 200KHz R.C. Oscillator — 20Hz to 200KHz in 4 ranges — Sine and Squarewave — Flat O/P to 10V r.m.s. from 600 ohms — < 0.5% distortion — > 60dB of variable O/P atten — Ext. Sync. — Large easy to read single dial with smooth precise tuning control — Instant stable signals - Solid State.



30 MHz A.M. SIG. GEN. £59

CO 1303D 5 MHz OSCILLOSCOPE £100




SG402 A.M. Signal Generator — 100KHz to 30MHz in 6 bands — 100mV of O/P with variable attenuator — Int. and Ex. A.M. — Solid State — Lightweight and portable — Large clear easy to read frequency dial.

CO1303D, DC to 5MHz Oscilloscope — 10mV/div sensitivity with variable atten. — Int. variable sweep frequency in 4 ranges from 10Hz to 100KHz — Int. and Ext. sync. — Direct deflection terminals can monitor R.F. up to 450MHz. CO1303G as above, plus 1:8 to 54MHz. monitor freq. range from 1 to 500W direct coupling — Two Tone gen. 1KHz and 1.575KHz — ideal for SSB, A.M. C.W. etc.



FG 270 **FUNCTION GEN.**

CS 1562A 10 MHz **DUAL TRACE** £224

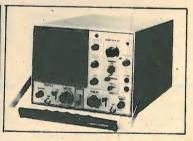

FG270, Function Generator — 0.1Hz to 1MHz in 6 ranges sine, square and triangle — 20V p-p open circuit output — < 1% distortion — D.C. offset — TTL O/P — Ext. VCO for sweep tests. FG271 as above plus 0.02Hz to 2MHz in 7 ranges — Int. sweep — Pulse, Tone Burst and A.M.

CS1562A Dual Trace 10MHz Oscilloscope — 10mV to 20V/div sensitivity in 1-2-5 sequence with fine control — 1 µs to 0.5 s/div sweep time plus X5 Mag. — Auto, Manual and T.V. triggering — Z mod and X-Y operation. A single trace version CS1559A is available

Plus many other Trio Products such as high sensitivity electronic voltmeters, Wow and Flutter meters, DIP meters and of course the main range of Trio scopes up to 100MHz — JUST ASK FOR THE CATALOGUE



House of Instruments Ltd., Clifton Chambers, 62, High Street. Saffron Walden. Essex CB10 1EE. Telephone: (0799) 24922

House of Instruments Ltd.


WW - 022 FOR FURTHER DETAILS

DAL 9622

WIRELESS WORLD APRIL 1981





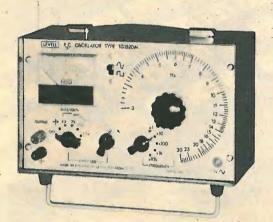



DON'T GAMBLE WITH PERFORMANCE BUY LEVELL OSCILLATORS

FREQUENCY

ACCURACY

SINE OUTPUT

DISTORTION

SQUARE OUTPUT

SYNC OUTPUT METER SCALES

SIZE & WEIGHT

1Hz to 1MHz in 12 ranges. 0 to 1% fine control on TG200DMP $\pm 1.5\% \pm 0.01$ Hz up to 100kHz.

± 2% up to 1 MHz. 7V r.m.s. down to < 200 µV with Rs = 6000

<0.05% from 50Hz to 15kHz, < 0.1% from 10Hz to 50kHz, < 0.2% from 5Hz to 150kHz, < 1% at 1Hz and

TG200D, DM & DMP only, 7V peak down to <200 µV. Rise time <150nS.

< IV r.m.s. sine in phase with output ± 1% freq. lock range per volt r.m.s. TG200M, DM & DMP only. 0/2V' 0/7V& -14/+6dBm.

260 × 130 × 180mm. 4.3kg with

TG200M TG200D TG200DM TG200DMP

FREQUENCY ACCURACY

SINE OUTPUT DISTORTION

SQUARE OUTPUT SYNC OUTPUT METER SCALES

SIZE & WEIGHT

3Hz to 300kHz in 5 decade ranges ± 2% ± 0.1Hz to 100kHz. Increasing to ± 3% at 300kHz. 2.5V r.m.s. down to < 200 µV

< 0.2% from 50Hz to 50kHz. < 1% from 10Hz to 200kHz. 2.5V peak down to < 200 µV. 2.5V r.m.s. sine. 0/2.5V & -10/+10dB on

TG 152DM $260 \times 130 \times 180$ mm. 3.4kg with

TG152D

Without

TG152DM

FREQUENCY ACCURACY.

SINE OUTPUT

DISTORTION

METER SCALES

SIZE & WEIGHT

0.2Hz to 1.22MHz on four decade controls

+ 0.02Hz below 6Hz.

+ 0.3% from 6Hz to 100kHz. + 1% from 100kHz to 300kHz.

+ 3% above, 300kHz. 5V r.m.s. down to 30 µV with Rs =

< 0.15% from 15Hz to 15kHz.

< 0.5% at 1.5Hz and 150kHz. 2 Expanded voltage and -2/+4dBm 260 × 180 × 180mm. 5,4kg.

TG66B

TG66A

Prices are ex works with batteries. Carriage, packing and VAT

Optional extras are leather cases and mains power units. Send for data covering our range of portable instruments

ELECTRONICS LTD.

MOXON STREET, BARNET, HERTS., EN5 5SD. TEL: 01-449 5028/440 8686

New! Sinclair ZX81
Personal Computer.
Kit: £49. 25 complete

Reach advanced computer comprehension in a few absorbing hours Built:

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. At £99.95, the ZX80 offered a specification unchallenged at the price.

Over 50,000 were sold, and the ZX80 won virtually universal praise from computer professionals.

Now the Sinclair lead is increased: for just £69.95, the new Sinclair ZX81 offers even more advanced computer facilities at an even lower price. And the ZX81 kit means an even bigger saving. At £49.95 it costs almost 40% less than the ZX80 kit!

Lower price: higher capability
With the ZX81, it's just as simple to
teach yourself computing, but the
ZX81 packs even greater working
capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8KBASICROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, or to select a program off a cassette through the keyboard.

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!


Proven micro-processor, new 8K BASIC ROM, RAM – and unique new master chip.

Built: £69.95 complete

Kit or built – it's up to you!

The picture shows dramatically how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

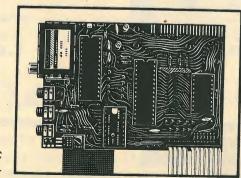Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



New Sinclair teach-yourself BASIC manual

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC program-

ming, from first principles to complex programs. You need no prior knowledge – children from 12 upwards soon become familiar with computer operation.

New, improved specification

(X) LIR I=N THEN GO TO 5 X=1 TO N B(X)=1(X)

LE B(X)=||(X) NET X LE J=0 LE J=U+1 IF J=U+1 LE T=J+1 NOT A(J) >A(T) THEN GO TO

> Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.

> > Unique 'one-touch'
> > key word entry:
> > the ZX81
> > eliminates a great
> > deal of tiresome
> > typing. Key words
> > (RUN, LIST, PRINT,
> > etc.) have their own
> > single-key entry.

- Check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animateddisplay facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer (not available yet but coming soon!)
- Advanced 4-chip design: microprocessor, ROM, RAM, plus master chip unique, custom-built chip replacing 18 ZX80 chips.

Sinclair ZX8I

Sinclair Research Ltd,

6 Kings Parade, Cambridge, Cambs., CB2 1SN. Tel: 0276 66104. Reg. no: 214 4630 00

If you own a Sinclair ZX80...

The new 8K BASIC ROM used in the Sinclair ZX81 is available to ZX80 owners as a drop-in replacement chip. (Complete with new keyboard template and operating manual.)

With the exception of animated graphics, all the advanced features of the ZX81 are now available on your ZX80 – including the ability to drive the Sinclair ZX Printer.

Coming soonthe ZX Printer.

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumerics across 32 columns, and highly sophisticated graphics. Special features include COPY, which prints out exactly what is on the whole TV screen without the need for further instructions. The ZX Printer will be available in Summer 1981, at around £50—watch this space!



16K-BYTE RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.



How to order your ZX81

BY PHONE – Access or Barclaycard holders can call 01-200 0200 for personal attention 24 hours a day, every day. BY FREEPOST – use the no-stampneeded coupon below. You can pay by cheque, postal order, Access or Barclaycard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST 7, Cambridge, CB21YY. Order				
Qty	Item	Code	Item price	Order Total
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	a.
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack(s).	18	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95
*I enc	e tick if you require a VAT receipt □ lose a cheque/postal order payable to Sinclair Resea se charge to my Access/Barclaycard account no.	rch Ltd,	TOTAL £	
*Pleas	e delete/complete as applicable.		Plas	ase print.
	Mr/Mrs/Miss			J
Addre	ss Liliania			11
		1 1		
FREEF	OST - no stamp needed.	1		WRW 04

WW - 047 FOR FURTHER DETAILS

For World-wide Telecommunications in the 1980's


Clark Masts Ltd. are specialists in the design and manufacture of telescopic and sectional mast systems. With over 25 years' experience in supplying masts to meet exacting military and civil specifications we have the expertise you can

Extended heights 4m-30 metres capable of lifting headload 1Kg-200Kgs, sectional or telescopic air-operated for field or vehicle mounting. Write or telephone us for details today.

SCAM Telescopic air-operated 12-metre mast kit shown in radio relay role for field or vehicle mounting 9-, 12- 15- and 21-metre ver-

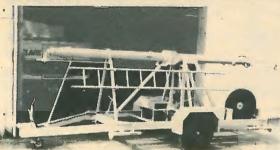Mobile air-operated 21 metre telescopic trailer mast. Horizontally stowed for transit, raised to vertical





CLARK MASTS LTD Binstead, Isle of Wight, PO 33 3PA England.

Telephone Ryde (0983) 63691,

Telex 86686



Make it for a Song!



The New Maplin Matinée

Amazing Value £299.95 + £99.50 for cabinet if required.

Easy to build. Latest technology - means less cost, less components and 80% less wiring. Comparable with organs selling for up to £1,000.00. Two 49-note manuals. 13-note pedalboard. All organ voices drawbars. Preset voices: Banjo, Accordion, Harpsichord, Piano, Percussion. Piano sustain Sustain on both manuals, and pedalboard. Electronic rotor, fast and slow. Vibrato and Delayed vibrato. Reverb. Manual and Auto-Wah. Glide (Hawaiian Guitar Sound). Single finger chording plus memory. 30 Rhythms! 8-instrument voicing. Major, Minor and Seventh chords. Unique walking bass lines with each rhythm. Unique countermelody line with each rhythm. Truly amazing value for money. Full construction details in Electronics & Music Maker magazine.



The complete buyers' guide to electronic components. With over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. Get a copy now — it's the one catalogue you can't

Post this coupon now for your copy of	of our 1981
catalogue price £1.	1
Please send me a copy of your 320 p	age catalogue. I
enclose £1 (Plus 25p p&p). If I am no	ot completely
satisfied I may return the catalogue	to you and have my
money refunded. If you live outside t	he UK send £1.68
or 12 International Reply Coupons.	**
I enclose £1.25.	
	The second second
Name	
	,
Address	
The state of the s	i v

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR Telephone: Southend (0702) 554155. Sales (0702) 552911.

159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926. 284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000. Both shops closed Mondays.

Catalogue now on sale in all branches of WHSMITH Price £1.00 WW - 023 FOR FURTHER DETAILS

WW481

WIRELESS WORLD APRIL 1981

OSCILLOSCOPES

Top Performance In Every Range



FIRM 312

V Sandwitth DC-2088Hz (-3d8) • Sensitivity 5mV-26V/cm (±3%)
X: Timebase 0.2e-40ne/cm incl. x5 Mago. • Trig. 3Hz-30MHz (4mm)
Dual trace • X-Y Operation • Calibrator • Screen 8x10cm • 2kV

Y: Bendwidth DC-20MHz (-3dB) • Sensitivity 2mV-20V/cm it 3%)
X: Timebase 2s-40ns/cm incl. x5 Magn. • Trig. DC-40MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Sweep delay • Overscan, Trigger, Delay indications • Trigger filter
Z-Modulation • Calibrator • Graticule Illumination • 2kV

Y: Bandwidth DC-50MHz (-3dB) • Sensitivity 5mV-50V/cm (±3%)
X: Timebase 5s-20ns/cm incl. x5 Magn. • Trig. DC-70MHz (5mm)
Dual trace • Algebr. addition • X-Y Operation • Screen 8x10cm
Delay Rine • Sweep delay • After delay triggering • Trigger filter
Single shot + Reset • Overscan, Trigger, Ready, Delay indications
var. Hold-off • Z-Modulation • Graticule illumination • 12kV

Y: Bandwidth DC-50MHz (-3dB) * Sensitivity 5mV-50V/div. (±3%)
X: Timebase 5s-20ns/div. incl. x5 Magn. * Trig. DC-70MHz (0.5div.)
Dual trace analog storage with var. Persistence and Auto-Storage
Aigebr. addition * X-Y Operation * Screen 8x10div. (7.2 x 9cm)
Delay line .* Sweep delay * After delay triggering * Trigger filter
Single shot * Overscan, Trigger, Ready, Delay, AS indications
var. Hold-off * Z-Modulation * X-Guard circuit * Calibrator * 8.5kV

HM 812 Storage



For more information contact:

HAMEG LTD. 74-78 Collingdon Street LUTON Bedfordshire LU11RX Telephone (0582) 413174 Telex 825484

Linear I/Cs

Analog Systems, the fast growing linear I/C company of Arizona whose products are available from Pascall, offer a wide range of high performance linear integrated circuits.

Hi-Speed Amplifiers

MA 207 - 1.5 GHz gainbandwidth product. ± 800 V/µS slew rate.

MA 401 \pm 225 V/ μ S slew rate ± 20V swing.

MA 324 \pm 130 V/ μ S slew rate, 450 MHz gain-bandwidth product.

MA 326-350 MHz gainbandwidth product. 400nS settling time

ANALOG

Send for full product listings of Analog Systems exciting product range

Pascall Flectronics Limited Hawke House, Green Street, Sunbury-on-Thames, Middlesex TW16 6RA

Telephone: (09327) 87418 Telex: 8814536 ■ Def Stan 05-31/BS9000/CECC approved

• WW - 012 FOR FURTHER DETAILS

New KONTAKT Sprays

NTAK

for the Electronics & **Electrical Industries**

KALTRON 601

A new cleaner for Magnetic Recording Units. Kaltron 601 has an extremely low surface tension thereby enabling the cleaning of magnetic sound heads leaving no deposit or other traces.

It is chemically pure (99.8%) - non conductive non-flammable

It can be used on energised electrical installations and electronic equipment, e.g. video units, tape recorders, data processing systems etc.

Also NEW

601

Spray cleaner for type wheel printers, matrix printers and chain printers. Can also be used for cleaning normal typewriters.

Specially for the cleaning of all types of screens, including data terminals and T.V. Screens.

VASELINE SPRAY 701

For use in communications engineering and construction of antennae. Proved successful as corrosion inhibitor for cable clamps, connecting screw joints etc. Application from spray can with capillary tube is clean and simple.

Special Products Distributors Ltd.

81 Piccadilly, London, W1V 0HL

Tel: 01-629 9556 : Cables: Speciprod, London, W.1 Telex: 265200 (answerback RACEN)

WW - 025 FOR FURTHER DETAILS



IMO can now offer you the high quality and reliability that you have come to expect in Omron relays, in their new series of low profile, printed circuit mounting subminiatures.

There's a tremendous range for every Interface, communication and output application, suitable for mounting with sockets or directly onto printed circuit boards. There are low cost types like the LC1-NE, where price is a major consideration, and high reliability types like the LZN's with gold-clad, bifurcated crossbar contacts and card lift-off operation.

With contact ratings up to 10A and 240VAC and down to 10μ A, all in a variety of housing styles and sizes, and up to four changeover contacts per relay, this range from IMO offers

you real design flexibility. All usual AC and DC coil voltages are available from stock.



With the increased requirement for complete reliability in electronic circuitry, you'll need relays at the right price and the highest quality.

In a word, Omron-from IMO.

Much more than you may know

IMO Precision Controls Ltd., 349 Edgware Road, London W2 1BS. Tel: 01-723 2231/4 or 01-402 7333/6.

HERE IT IS! THE BRAND NEW 8022A HAND-HELD DMM

Consider the following features: 6 resistance ranges from 200 ohm-20 ohms 8 current ranges from 2mA-2A AC/DC 10 voltage ranges from 200 mv-1000v DC-200 mc-750V AC

Pocket size - weighing only 70 gms.
Full overload protection — will withstand 6kv spikes
Rugged construction — virtually indestructable
Meets tough military specs —

drop proof
In line, pushbutton operation for single-handed useage Incorporates low power cmos chip for low power consumption All this plus a 2-year full guaran-

Carriage and Insurance £3

For only £75 + VAT SOFT CARRYING CASE £7 extra

Even more sophisticated the Fluke 8020A Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

Price £125

Carriage and insurance £3.00 A handsome soft carrying case is included (this model only)

ms 127 x 90 x 32 mm £10.95 P &P 75p

DC volts: 0 to 0.25, 1, 2.5, 10, 25, 100, 250, 1000.DC current: 0 to 50 ua, 5 ma, 50 ma, 12 amp. Resistance: 0 to 6K, 60K, 6 meg, 60 meg. Decibels: -20 to +56 db.

£20.50, PAP 750

OFF THE SHELF
DELIVERY ON THESE

DIGITAL MULTIMETERS
BRAND NEW FROM FLUKEIII
NOW AVAILABLE
THE 8024A HAND HELD DMM

This model incorporates all the features of the 8020A but in addition has:

A peak hold switch which can be used in AC or DC for volts and current functions.

Audible continuity testing and level detection for sensing logic levels.

A temperature (°C) range for use with a thermocouple. £149

Carriage and Insurance £3

The following accessories are in stoc	k now
Y8008 Touch and Hold Probe	£18.0
80K-40 High Voltage Probe	£45.0
	£324
80T-150C Temperature Probe (C)	€55.0
	£55:0
	1

8010A AND 8012A BENCH MODEL D.M.M.s

resources than ever offered for such a low price. Its co-identical characteristics except that it has two additional low 2001 to replace the 8010A's 10 ampere current range. The 8010A and 8012A feature:

10 voltage ranges from 20mv - 1000v dc, 200mv - 75v ac.

2 conductance ranges from 20mS - 200 nS.

ranges from 200Ω - 200 nS. ε ranges from 200Ω - 20mΩ - the 8012A has two additional resistance ranges nd ZUNI.

Jirent ranges from 200µA - 2A AC/DC — the 80T0A has two additional currents

s 10A AC and 10A DC.

8010A £159 8012A £199
Carriage and Insurance £3
The 80 10A is also available with two rechargeable Niced size C batteries installed in option 01 or £179.00.

LOW COST, AUTORANGING MULTI-FUNCTION COUNTER MODEL 1900A

Event counting to 10⁵ events with overflow indicator
 Signal input conditioning with switchable 1 MHz low pass filter and attenuator
 Rugged moulded case with convenient tilting / carrying handle
 Optional parallel date output with decimal point and annunciation
 I raditional high Fluke quality
 Self cheek.

£235 Carriage and Insurance £3

A sturdy and reliable in-strument. Has internal buzzer. AC volts: 0 to 2.5, 10, 25, 100, 250, 500, 1000.

PLEASE ADD 15% VAT TO ALL ORDERS EXCEPT WHERE 'VAT INCLUDED.'

CALLERS WELCOME

We are open 9 a.m. 6 p.m.

Monday-Saturday

We carry a very large, selection of electronic

components and electro-mechanical items

ROTARY STUD SWITCH

£3.25 P&P 50p

BENDIX MAGNETIC C. HCH


BENDIX MAGNETIC
Superlo example of electro-mechanics. Main body in two sections, coit section fixed with %" sleeve, drive section rotating on outer perimeter. Uniting plate has %" ID bearing concentric with main section and 18-tooth cog wheel. Extremely powerful transmission. 24V D.C. 240 m/a.





COM PONEN 364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667

INSTRUMENT CASES AND BOXES

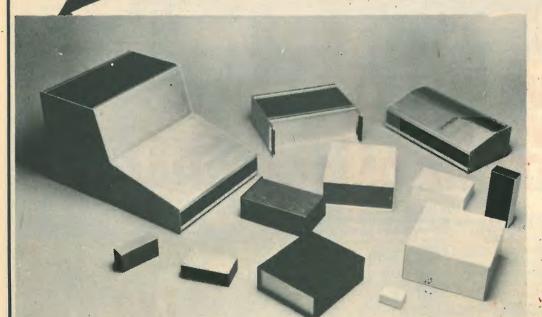



Zaerix **Electronics** Limited

46 Westbourne Grove London, W2 5SF

PROFESSIONAL OUALITY

Desk consoles, instrument cases and boxes which feature anodised aluminium extrusions and panels, with integral facilities to mount sub chassis and PCBs.

Telex: 261306 Tel. 01-221 3642

WW - 041 FOR FURTHER DETAILS



WW - 026 FOR FURTHER DETAILS

Since it's introduction, the CS1830 has been our top seller, and no wonder, when you glance at the comprehensive specification and the extremely attractive price which includes two matching X1/X10 probes.

Add to that the fact that we can normally supply from stock and you have a winner. Some of the details are listed here but if you need further information, just contact us and we'll be happy to assist.

120 x 96 mm rectangular PDA with internal graticule

Y Bandwidth: DC - 30MHz

Sensitivity: 5mV/div (30MHz) 2mV/div (20MHz)

Input RC: 1M/23pF

Risetime: 11.7nS **Beam Switch:**

Chop/alternate Modes:

CH1, CH2, Dual, Add, Subtract Time Base:

Triggered, auto, or single shot

Sweep Time: 0,55/div-200nS/div (40nS using X5 mag) 20 ranges in 1-2-5 sequence

Sweep Delay:

100mS-1uS adjustable with trace bright up for delay location

Z Modulation:

TTL compatible 10K impedance 5MHz bandwidth **Trace Rotation:**

Electrical And the Price?

£455 + VAT (includes 2 probes)



CS1577A Dual 30Mhz/2mV Signal Delay etc

£410 + VAT



receiving for the discerning few.



NRD 515 SYNTHESISED HF MONITORING RECEIVER NHD 515 MULTICHANNEL MEMORY UNIT £161.00 inc. VAT NVA 515 LOUDSPEAKER UNIT £27.60 inc. VAT CFL 260 600Hz CW FILTER £34.50 inc. VAT

The NRD 515 is a PLL-synthesised communications receiver of the highest class featuring advanced radio technology combined with the latest digital techniques. The new NRD 515 is full of performance advantages including general coverage, all modes of operation, PLL digital VFO for digital tuning, 24-channel frequency memory (option), direct mixing pass-band tuning, etc. JRC's 65 years of radio communications. experience will give you "the world at your fingertips". The NRD 515 is but a single item from the JRC product range which extends all the way to full marine radio installations for supertankers.

LOWE ELECTRONICS Ltd CHESTERFIELD ROAD, MATLOCK, DERBYSHIRE DE4 5LE

TEL, 0629 2430/2817

WW - 046 FOR FURTHER DETAILS

ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS

WIRELESS WORLD APRIL 1981

• ELECTRONIC TEST EQUIPMENT SPECIALISTS

ALL PRICES INCLUDE VAT

£68.00

£63 25

£92 50

£253.00

£437 00

£90.85

£73 60

£126.50

£146.00

A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dualtrace.

• ALL MODELS ON DISPLAY

● RETAIL - MAIL ORDER -EXPORT - INDUSTRIAL

OPEN SIX DAYS A WEEK • CALL IN AND SEE FOR YOURSELF

ALL PRICES INCLUDE VAT

SINGLE TRACE (UK c/p etc £2.50)

GENERATORS

(UK c/p etc £2.50)
Hm 307-3 10mHZ. 5mV, 6 x 7 cm display plus component test
C01303D 5mHZ, 10mHZ, 7 x 7cm display plus component test
£158.78
£109.25
\$C110 10mHZ Battery portable, 10mV 3.2 x 2.6cm display (Optional case 98.86. Nicads £8.63 Mains unit £4)
+LB012A 10mHZ 10mV. 5" display
£195.00
+C31559A 10mHZ 10mV. 5" display

- C.... C..... ()

#V151 15mH7 1mV 5" display Price includes free Probe(s)

PULSE

XI £6.50, X10 £8.50, X100 £12.95, X1-X10 £10.95
HAMEG • TRIO • SINCLAIR • LEADER • HITACHI

Mains and Battery/Mains portables.

Many on demonstration.

OPTIONAL PROBES (ALL MODELS)

RF SG402 100 KHZ 30mHZ with AM

2001 1HZ 100KHZ (function) TG105 5HZ 5mHZ 4001 0.5HZ 5mHZ

200P 0.00 2H2 5.5mHZ

AG202A 20HZ— 200KHZ LAG26 20HZ— 200KHZ

AG203 10HZ— 1mHZ sine/sq

LSG16 100KHZ (300mHZ on Harmonics)

LSG231 100m HZ 1mHZ (adjustable) FM

stereo generator, pilot and mod £195.00

LAG120A 10HZ— 1mHZ £146.0
Also in stock range of Protoboard kits and

'PRO' MULTIMETERS

(UK c/p £1.20) M1200 100K/Volt 30 ranges plus AC/ DC 15 amp £67.00 K1400 20K/Volt 23 range large scale

£79.95 M1500 20K/Volt 42 range plus AC/DC 10 amp £53.50 K200 38 range FET 10m OHM input £95.00

20Hz to 30MHz multimeter LOGIC PROBES/ MONITORS

Logic probes indicating high/low, etc., states that scopes can miss. All circuit powered for all ICs. LP3 50 MHz logic probe

£55.95 LP1 10 MHz logic probe £35.50 LP2 11/2 MHz logic probe £19.95 LM1 Logic monitor £33.

LDP076 50 MHz logic probe with case £33.00

CS1566A 20mHZ, 5mV, 5" display

*LB03085 70mHZ, 2mV, 5 x 6.3cm display. Battery/mains. Po Nicads
HM412-4 20mHZ, 5mV, 8 x 10cm display plus Sweep Delay
C51577A 35mHZ, 2mV, 5" display
C51830 30mHZ, 2mV, 5" display plus sweep delay and delay £482.00 £569.00

£267.00 £284.00 £253.00

£339.00

 model
 £559.00

 Hm 512-8 50mHZ, 5mV, 10 x 8cm display. Delay Sweep
 £667.00

 xLBQ514 10mHZ, 1mV, (5mV) 5" display
 £294.00

 xV132 15mHZ, 1mV, 5" display
 £326.00

 xV302 30mHZ, 1mV, 5" display
 £447.35

 xV550 50mHZ, 1mV, 10 x 8cm Delay sweep + 3 channel display
 £799.25

SWR/FS AND

POWER METERS Ü

Range in stock covering up to 150mHZ and up to 1K watt power PL259 sockets. Also 250 UHZ Grid Dipmeter.

SWR9 SWR/S 3-150mH7£9.50

SWR50 SWR/Power meter 3½-150mHZ 0-1000 watts

3½-150mHZ 0-1000 watts
£13.95
110 SWR / Power 1½-144mHZ
0/10/100 watts
£11.50
171 As 110 Twin meter plus E/S
£14.50
Plus large range of BNC / PL259
etc leads plus adaptors / connectors
always in stock.

etc leads plus auaprono.
always in stock.
176 SWR/Power/FS 1½144mHZ 5-50 watt Plus 2540mHZ ac match
£16.60
KDM6 Gnd Dip 1½-250mHZ

MULTIMETERS A range of LED and LCD Bench and Hand DMM s bettsry operated with optional Mains Adaptors — some with optional Micros. All supplied with batteries and leads. DEFINIOUS TO SEE THE SECONDARY SECONDARY SEE THE SECONDARY SECONDA HAND HELD (UK post etc 85p) GL35C 3½ Digit LCD in AC / DC with case



FREQUENCY

COUNTERS

283158 49







LEADER • TRIO • NEWTRONICS • LEVELL

0.1% 6200 3½ Digit LCD 0.2A AC/DC. Auto £45.95 **6220** As 6200 plus 10A AC/DC **£55.95**

Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.

HAND HELD (UK post etc 85p)

PFM200 20HZ to 200mHZ 8 Digit LED

MAX50 100HZ to 50mHZ 6 Digit LED

MAX550 30KHZ to 550mHZ 6 Digit LED

610.00

(UK c/p £1)
MAX100 8 Digit LED 5HZ to 100mHZ £89.00

BENCH PORTABLES

BENCH PORTABLES (UK C/P ET DM235 3½ Digit LED 21 ranges, 0.5% AC/DC 2A £60.38 £37.50 AC/DC 2A £60.38 DC and DM350 3½ Digit LED 34 ranges AC/DC TM352 31/2 Digit LCD plus 10A DC and Hfe checker £54.95 ME502 3½ Digit LED plus 10A DC and

DC and 10A £54.95 TM353 3½ Digit LCD AC/DC 2 amp £96.60

TM351 31/2 Digit LCD AC/DC 10 amp LM100 3½ Digit LCD AC/DC 2 amp £86.50

DM450 41/2 Digit LED 34 ranges AC/DC

6220 As 6200 plus 10A AC/DC £85.95
6100 As 6200 plus Cont. test/range hold
£69.95
Micads £8.63 Mains adaptor £4)
10 amp
(DM series options. Carry case £8.86
Micads £8.63 Mains adaptor £4)
1503 434 Digit LCD 28 range AC/DC 10 TM354 3½ Digit LCD 2A DC with case amp includes mains adaptor £159.95

CLAMP METERS/ INSULATION TESTERS



X2303 30 AMPS 500 VAC 2Z1.95 3101 300 AMPS 600 VAC 1K 0HM £32.95 K2803 300 AMPS 600 VAC 2K 0HM £53.95 K2903.900 AMPS 750 VAC 2K K3103 Transistorised incu K3103 Transistorised insulation/continuity tester. 100 MEG. 600 VAC 0/2½K £95.00 M500 Insulation tester 100 MEG. 500 VOLT. 0/200 OHMS continuity £67.50

Also digital and DC types in stock

£106.00

Stockists of electronic equipment, speakers/kits, PA equipment plus huge range of accessories ● UK carriage/packing as indicated ● Export — prices on request
● All prices correct at 1.2.81 E & OE ● All prices include VAT

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564

CSC SINCLAIR OPTOELECTRONICS NEWTRONICS

OPEN SIX DAYS A WEEK

MULTIMETERS (UK c/p 75p)



AT1020 20K/Volt 19 range de luxe plus hfe test

7081 50K/Volt 36 range plus 10 amp DC £16.95
TR303TR 20K/volt plus 12A DC plus hfe test £15.95
AT20 20K/Volt 21 range de luxe plus 10A DC and 5 KV £21.95

AT205 50K/Volt 21 range de luxe plus 10A DC 7080 20K/Volt 26 range large scale, 10A DC plus 5KV £26.95

AC/DC
AT2050 50K/Volt 18 range de luxe plus hfe test
£28.50 AT210 100K/Volt 21 range de luxe 12A AC/DC

£29.95 360TR 100K/Volt 23 range plus hee checker and AC/DC 10 amps £34.95

CHOOSE FROM UK'S LARGEST SELECTION TV GENERATORS

LCG-393V PAL 8VHF 6 patts £137.00 SCG-392U £217.00

PAL B UHF 15 patts





WW - 009 FOR FURTHER DETAILS

-	
B	ARCLAYCARD
	VISA
	المسد

ı	SEMIC	CON	DUCTO			0.09	BD116 BD124	0.52	BF178 BF179	0.26	BF459 BFT42	0.36	BU500 MJE340	0.40	I.C.s		SN76660N	0.60	TBA920	1.65	וטטוט	52
I	AC126	0.22	BC108A	0.10	BC184LA BC208	0.09	BD131	0.32	BF180	0.29	BFT43	0.27	MJE520	0.44	MC1307	1.00	SN76666N TAA550	0.70	TBA920Q TBA950	1.65	AA119	0.07
1	AC127		BC108C	0.10	BC212	0.09	BD132	0.35	BF181 BF182	0.29	BFX29 BFX84	0.30	R2008B R2010B	1.70	MC1327 MC1349	1.00	TAA661B	1.20	TBA990	1.49	BA102	0.17
	AC128 AC141K	0.28	BC109B BC114	0.11	BC212L BC213	0.09	BD133 BD135	0.40	BF183	0.29	BFX85	0.28	R2540	2.48	MC1350	1.00	TAA700	1.70	TBA990Q	1.49	BA115	0.13
	AC141K	0.30			BC213L	0.09	BD136	0.30	BF184	0.28	BFX86	0.30	TIP29C	0.42	MC1351	1.00	TB641-B11 TBA120B	1.90	TCA270Q	1.10	BA156 BAX13	0.15
1	AC176	0.22	BC140	0.31	BC214	0.09	BD137	0.28	BF185	0.28	BFX88 BFY50	0.25	TIP30C TIP31C	0.43	MC1352 ML231B	1.00	TBA120S	0.70	TCA800 TCA940	1.65	BAX16	0.05
	AC176K AC187	0.31	BC141 BC142		BC214L BC237	0.09	BD138 BD139	0.30	BF194 BF195		BFY51	0.21	TIP32C	0.42	ML232B	2.10	TBA120SA	0.70	TDA440	2.95	BB105B	0.30
	AC187K	0.28	BC143	0.24	BC238	0.09	BD140	0.30	BF196		BFY52	0.25	TIP33B	0.55	SAS5605	1.60	TBA120SB TBA120SQ	0.70	TDA1004A TDA1170	1.85 1.95	BY126 BY127	0.10
	AC188	0.22	BC147	0.09	BC251A	0.12	BD144 BD182	1.20	BF197 BF198	0.11	BFY90 BR100	0.77	TIP41C TIP42C	0.45	SAS5705 SL901B	1.60 4.45	TBA120U	1.00	TDA1190	2.15	BY164	0.45
	AD149 AD161	0.70	BC148 BC149	0.09	BC252A BC258A	0.15	BD201	0.83	BF199		BR101	0.30	TIP47	0.65	SL917B	6.25	TBA395	1.50	TDA1327	1.70	OA90 IN914	0.05
	AC161/2	1.04	BC157	0.10	BC303	0.26	BD203	0.78	BF200		BRC4443	0.85	TIP2955	0.84	SL1310	1.80	TBA396 TBA480Ω	0.75 1.25	TDA1470 TDA2030	1.95	IN4001	0.04
	AD162	0.39	BC158	0.09	BC307	0.09	BD204 BD222	0.70	BF241 BF257		BT106 BT108	1.00	TIP3055 TIS91	0.66	SL1327Q SN76003N	1.10	TBA510	1.65	TDA2522	2.40	IN4002	0.04
	AF124 AF125	0.34	BC160	0.28	BC327 BC337	0.10	BD225	0.46	BF258	0.25	BT116	1.20	2N3054	0.59	SN76013N	1.65	TBA520Q	1.10	TDA2530	1.95	IN4003 IN4004	0.04
ı	AF126	0.32	BC161	0.28	BC338	0.09	BD237	0.30	BF259	0.26	BU105	1.22	2N3055	0.59	SN76013ND	1.65	TBA530 TBA530Q	1.10	TDA2532 TDA2540	2.40	IN4005	0.05
	AF127	0.32	BC170B	0.10	BC461 BC478	0.30	BD238 BD410	0.33	BF273 BF336	0.13	BU108 BU124	1.69	2N3702 2N3703	0.12	SN76023N SN76033N	1.35	TBA540	1.25	TDA2541	2.15	IN4006	0.05
	AF139 AF150	0.42	BC171A	0.10	BC4/8 BC547	0.20	BDX32	1.50	BF337	0.29	BU126	1.22	2N3704	0.12	SN7611N	0.89	TBA540Q	1.35	TDA2560	2.15	IN4007 IN4148	0.06
1	AF239	0.42	BC172	0.09	BC548	0.10	BF115	0.35	BF338		BU205	1.30	2N3705		SN76131N SN76226N	1.30	TBA550Q TBA560CQ	1.55	TDA2581 TDA2590	1.25	IN5401	0.12
	AU110	1.48	BC1/2C	0.10	BC549A BC550	0.08	BF127 BF158	0.24	BF355 BF363	0.37	BU208 BU208A	1.52	2N3706 2N3708		SN76225N	1.05	TBA570	1.10	TDA2600	2.95	IN5402	0.14
	AU113 BC107	0.10	BC174A	0.09	BC557	0.07	BF160	0.27	BF371	0.20	BU208-02	1.89	2N5294	0.38	SN76532N	1.40	TBA720AQ TBA750Q	2.45	TDA2640	2.50 1.35	IN5403 IN5406	0.12
1	BC107B	0.10	BC182	0.09	BC558	0.07	BF167	0.24	BF457	0.23	BU326A	1.42	2N5296	0.48	SN76533N SN76544N	1.30	TBA800	0.89	TDA2690 TDA3950	2.50		0.16
-	BC108	0.10	BC182LB	0.10	BD115	0.30	BF173	0.22	BF458	0.23	BU407	1.24	10000000		NIPPCOVEIC	1.35						

	BC107B BC108	0.10	BC182 BC182LB	0.09	BC558 BD115	0.07 0.30	BF167 BF173	0.24	BF457 BF458		BU326A BU407	1.42	2N5296	0.48	SN76533N SN76544N	1.30	TBA800	0.89	TD
April 1	NE	W E	BRANC	DED V	ALV	ES	EY86/87 EY500A	0.56 1.50	PCC85 PCC88	0.80	PY88 PY500A	0.79 1.35	VLS631 VR105/30	13.00	6F28 6F33	1.50 8.50	92AG 92AV	9.00	V
	A2087 A2293 BT5B DM160 DM86/87 DY802 E80CC	11.50 7.20 33.00 1.50 0.55 0.60 4.75	ECC88 ECC91 ECC189 ECC804	0.60 0.65 0.65 0.78 0.46	EF183 EF184 EH90 EK90 EL33 EL34 EL36	0.56 0.56 0.65 0.65 2.50 1.54 1.60	EZ80 EZ81 EZ90 GN4 GN10 GT1C GU50 GXU1	0.48 0.56 0.96 5.00 15.00 13.50 11.75 13.50	PCC89 PCC189 PCF80 PCF82 PCF86 PCF200 PCF201 PCF801	0.80 0.80 0.72 0.70 1.10 1.35 1.35 0.92	QQV06-40A QQZ06-40A	13.95 45.25	X65 X66 YL1060 Z759 Z803U ZC1040 ZM1001	0.85 0.85 15.00 9.00 15.00 8.00 5.00	6GH8A 6JS6C 6J5GT 6KD6 6L7 6LD20 6L6GC 6L6GT	0.80 4.00 0.75 3.95 0.75 0.60 1.75 1.10	150B2 150B3 155UG 807 811A 813 833A 866A	1.50 3.90 25.00 1.09 9.00 11.30 47.85 2.50	VH E1 E1 BE L5
	E80F E81CC E82CC E83CC E83F	6.25 3.90 1.50 1.50 2.00	ECF80 ECF82 ECH81 ECH83	0.65 0.60 0.58 0.78 0.96	EL37 EL38 EL41	4.00 4.50 1.50 1.09 0.60	GXU50 GY501 GZ30 GZ32 GZ33	12.50 1.25 0.76 0.76 1.85	PCF801 PCF802 PCF805 PCF806 PCF808 PCH200	0.72 1.95 0.60 1.48	QS150/45 QS1200 QS1209 QS1212 QV03-12 QV05-25	7.50 3.15 1.50 3.25 3.50 1.75	2D21W 2K25 3AW2 3A/147J 4CX250B	2.00 10.50 3.35 7.50 26.60	6SL7GT 6SN7GT 6V6GT 6X5GT 6X8A	0.90 0.90 0.90 0.65 1.25	2050A 5636 5642 5687 5696		L7 W

9.00	VIDEO TA	PES
1.50 3.90 5.00 1.09	VHS E120 TDK E180 TDK	6.90 8.15
1.30 7.85 2.50 3.90	BETAMAX L500 Ampex L750 Sony	6.50 8.35
6.00 5.15	WIRE.	BASES

3.90	L/50 50	пу	•	0.33
6.00 5.15 2.55	WIR	E-	BASES	3
3.00 3.20 2.75	WOU		B7G B7G Skirted B8G	0.15 0.30 0.70
8.25 3.90 3.00	TOP		B9A B13B Int. Octal	0.16 0.70 0.35
2.75 1.20	4 WATT 4R7-1K8	£ 0.13	Cans	0.30
3.00 4.20 4.45	2K2-6K8 10K	0.16	DUR	Α -
4.85 11.50 1.50	7 WATT R47-4K7 5K6-12K	0.14 0.15	CELL B A	۲ -
7.50 11.50	15K-22K	0.18	TERIES	


MN1300 MN1400 MN1500 MN1604

Many other types available.
Please phone or send list for quotation P&P 50p ON ALL ORDERS PLEASE ADD VAT @ 15% Export & Trade Enquiries Welcome


Chokes, block filters, ceramic filters, resonators, IFTs, oscillator coils, audio filter blocks etc.


LOW PASS FILTERS

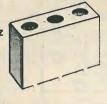Now from 10kHz to 20MHz TOKO's recently expanded LPF series covers from the audio spectrum through to 20MHz in a series of LPFs for mpx, video, radio etc.



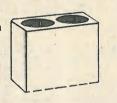The LPFs are based on 7&10mm formats with up to 4 LC tuned elements per block. Many stock types available.



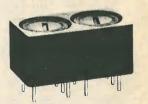

for VHF and UHF:





-80dB at the +/- 21.4MHz points. Ask for details.



Audio buzzers now down to 1kHz - low cost 400-600kHz crystal replacements for MPUs, RCs etc. Low cost - wide range.

Video frame stores are a new add-

ition to TOKO's memory product

processing of picture information

(including the VFM10D with 8"

resolution than available from VTR

disk drive) with much better

range. They permit easy analysis of low dose X-Ray pictures, digital



525/625 operation

Local or remote control

Top/bottom & L/R reverse Models available with digitized I/O

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG 200 North Service Road, Brentwood, Essex

WW - 049 FOR FURTHER DETAILS

WIRELESS WORLD APRIL 1981

a special 24~page supplement in Elektor

The new generation of 16-bit microprocessor systems can equal or even better the performance of present day minicomputers. This means that a 'real' computer is now within the reach of any enthusiast. The only question is: "Which system do you choose?"

The April issue of Elektor contains a special 24 page supplement giving a brief survey of the field, concentrating in particular on the following types:

Manufacturer Type Second sources Intel 8086 Mitsubishi, Mostek, Siemens Motorola 68000 Hitachi, Rockwell, Thomson


National Semiconductor 16000 family Texas Instruments 9900 AMI, ITT

Zilog 8001 AMD, SGS-ATES

Comparisons are given of the basic capabilities, register sets, addressing modes, instruction sets, memory maps and support chips. The article has been checked for technical accuracy by specialists from the respective manufacturers.

April issue on sale now, price 60p Or direct from address below, price 80p (inc. 20p P&P) Elektor Publishers Ltd., 10 Longport, Canterbury, Kent CT1 1PE. Tel. (0227) 54439/0

WW - 029 FOR FURTHER DETAILS

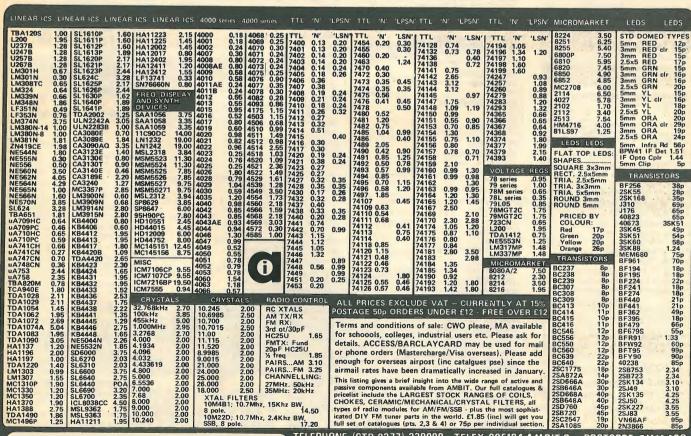

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G. POSTCODE CM14 4SG 200 North Service Road, Brentwood, Essex

5303B DC-520 MHz. (Plug-on)

5308A 0-75 MHz. Universal Module

5267A Time Interval Plug-in 10ns

5345 DC-500 MHz Time Int. Ave. Burst Total Ratio

9024 10 Hz-600 MHz 7 + 1 digits 9835 6 Digit DC-20 MHz 10mV

9837 DC-80 MHz 6 digits

SYSTRON DONNER

10590A Adaptor converts 5245

125mV sens. 50Ω

50mV sens. 1MΩ

Plug-ins to 5345

RACAL

120

120

1225

225

115



8 . 4	Prices		Prices		Prices from £
Bridges	from £		from £	Oscilloscopes	from E
GENRAD				ADVANCE	
GR1657 Digibridge LCR,		6054A/04 11 Digit 20 kHz-18 GHz	2800	OS1000A DC-20 MHz. dual trace	200
auto, LED display	850	BCD O/P	2800	3300B Dual Trace DC-50 MHz	200
CINTEL		Function Generators		5mV/div. Dual Timebase	600
277 Measures iron core inductances		INTER-STATE		GOULD ADVANCE	
0,01H-1000H (with a Q value not		ELECTRONICS		OS1000B DC-20 MHz Dual Trace	
ess than 2)	130	F51A Multi-Mode. + and - offset:		X-Y TV Sync	250
HEWLETT PACKARD		0.0005 Hz to 10 MHz. 10/15V/50Ω	250	HEWLETT PACKARD	
4342A 'Q' Meter QLC complete	1250	F55A Multi-Model 0.0025 Hz-10		1703A Storage 1000Div/ms.	
MARCONI		MHz. 10V/50Ω. Ext. VGC. Burst		DC-35 MHz. Dual trace Mains/Ext	
	250	O/P up to 100k bursts/sec	350	DC	1200
TF868A Universal Bridge	250	PHILIPS		181A Storage 1000Div/ms	
TF1313A Universal LCR Bridge 0.1%	375	PM5127, O.1 Hz-1 MHz. Sine/		DC-100 MHz Main frame only	650
WAYNE KERR		Square/Triangular/Pulse outputs.		182C DC-100 MHz Mainframe, large	
B224 Wide range LCR Bridge	475	External sweep facility 30Vp. p max		screen	525
B500 Log LCR Bridge	225 125	output	325	MEDELEC	
B601 RF LCR Bridge (Detector and Oscillator not incl).	125	Logic Analysers		M-scope 4 channel DC-100 kHz U/V	
B641. Measures L/C/R/G Accuracy		HEWLETT PACKARD		Chart .	1650
of 0.1%	450	1601L Logic state analyser		PHILIPS	
Q801. Y parameter test set. Plus		12 channel display	250	PM 3211 DC-15 MHz Dual Trace 2mV	425
transistor adaptor unit	230	1600A 16 channel 20 MHz clock		PM3233 Dual Beam DC-10 MHz	
Cable Test Equipment		MAP A & B store	1850	2mV/div.	400
		1607 16 channel 20 MHz clock		TEKTRONIX	
MARCONI	575	(Display scope required)	1500	475 Dual Trace DC-200 MHz 2mV	1125
TF2333 Transmission Test set	3/3	TEKTRONIX		485 Dual Trace DC-350 MHz 50Ω	****
HEWLETT PACKARD		7D01F 16 channel up to 50 MHz		1 MΩ 250 MHz	2100
3556A For psophometric		clock MAP	2650	545B/1A1. DC-30 MHz. dual trace.	325
measurements from 20 Hz-20kHz.	475	Mains Monitors		Delayed timebase	325
0.1mV-30V input level	4/5	***************************************		585A/82. DC-80 MHz. dual trace 10 mV sensitivity	525
NEC		COLE		547/1A1, DC-50 MHz, dual trace	020
TTS-37B. Noise, level and VU		T1007 200-260V. 35-65 Hz	75	DTB	525
measurement. Sensitivity -80dBm	275	Thresholds 10V, 50V, 100V, 200V	/5	547/1A4, DC-50 MHz, four trace	
up to + 20dBm	2/3	DATALAB		DTB	625
STC		DL019 Power line interface for	250	7403N DC-60 MHz 3 Plug-in	
74216A Noise Generator CCITT	240 475	transient recording	350	Mainframe	450
74261A Psophometer CCITT	4/5	DL905 Digital Storage Unit DC-3 MHz 10mV	1055	7704A DC-200 MHz. CRT Readout.	
TEKTRONIX	10.00		1033	Mainframe for 4 Plug-in	1200
1502 Portable TDR Cable Tester	2,725	DRANETZ		TELEQUIPMENT	
WANDEL u. GOLTERMANN	1	606-3 Disturbance Analyser Avg,	2625	D34 Dual Trace DC-15 MHz 2mV	
DLM-1. Send/receive system	1500	Sag/Surge	2023	Mains/Batt	525
LDS-2, 200Hz-600kHz sender for		GAY		D75 Dual Trace DC-50 MHz Dual	500
measuring group delay and		LDM Records + ve/ - ve transients	1250	Timebase	600
attenuation variations	3250	of 50ns on AC or DC Lines	1200	D83 DC-50 MHz. Dual trace. Large	650
LDEF-2. Filters for DLM unit	250	Modulation Meters		6½" CRT. Dual Time Base	600
Counter Timers		AIRMEC		Oscilloscope Plug-ins	
HEWLETT PACKARD		409 3-1500 MHz. AM/FM	295	HEWLETT PACKARD	
5300A/5303B DC-520 MHz 6 digits	210	MARCONI		1804A DC-50 MHz Four channel	
5300A Display Module. 6 Digits.		TF2300A 1-1000 MHz. AM/FM	450	20 mV-10V/div.	575
3 × 10 ⁷	90				
5302A DC-50 MHz. 100mV sens.					

As New Ex Stock delivery TEKTRONIX 465 DC-100 MHz Dual Trace TEKTRONIX 475A DC-250 MHz Dual Trace 5mV-5V Div 0.01µs-0.5s Div Delayed T B XY DC 3 MHz These instruments sold with ONE YEAR FULL GUARANTEE

sale is fully refurbished

to manufacturers' original specifications

WIRELESS WORLD APRIL	1981
	Prices
	from £
1825A Dual Timebase 50ns-1s/div.	525
1805A Dual Trace DC-100 MHz 5mV. 1MΩ/50Ω	550
TEKTRONIX	
Type R. Transistor R.T. tester, Pulse rate 120 pulses/sec. R.T. Less than	
5 mµs Type G. Differential amplifier, 100:1	100
CMR DC-20 MHz. 50 mV sensitivity Plug-ins for 500 series	50
1A1 dual trace Plug-in DC-50 MHz	225
1A2 dual trace Plug-in DC-50 MHz 1A4 four trace Plug-in DC-50 MHz	180 375
1A5 Differential Plug-in Z Differential Plug-in	175
81 Adaptor Plug-in 1A Series to 580	75
Series 7A12 Dual Trace DC-105 MHz	410
5mV/div. 7A22 High gain diff. amp.	450
0.1 Hz-1 MHz 10µV 7A26 Dual Trace DC-150 MHz	525
5mV-5V/div. 7B53A Dual Timebase 5ns-5s/div.	550
Oscilloscopes (storage)	
TEKTRONIX 549/1A1. DC-30 MHz. 5mV	
sensitivity. Dual trace. Storage	
scope, Writing speed: 5cm/µs with enhancement. Includes trolley	675
564B/3A6/2B67. DC-10 MHz. Dual trace 10mV sensitivity, split screen	
storage oscilloscope	750
466 Storage 1350 cm/μs Variable Persist DC-100 MHz	2225
7313 Split screen 4.9 cm/µs. DC- 25 MHz (M/F for 3 Plug-ins)	1650
Phase Meter	
DRANETZ 301A 5 Hz-500 kHz. Z in 100kΩ.	
Accuracy ±1° to ±2°. Analogue	400
O/P Power Meters	
DYMAR	
2081/100 True RMS, DC-500 MHz. 30mW-100W	425
HEWLETT PACKARD	90
478A Thermistor Mount for 432A 435A 0.3µW to 100mW 5 MHz-	
18GHz 8481A Power Sensor for 435A	475 200
MARCONI SANDERS	
. 6460 10 MHz-40 GHz (Depending on Head)	300
6420 10 MHz-12.4 GHz 10mw	110
MARCONI TF2512 DC-500 MHz 0.5-30w 50Ω	130
TF 893A 10 Hz-20 kHz. 20μW-10W.	120
Power Supplies	100
BRANDENBURG 475R 10-2100V 5mA DC Stab.	150
FARNELL L30B 0-30V 1A DC Stab.	55
FLUKE	
415B 0±3100V 30mA 0.005% reg. Protected	350
ITT	
Power Lab. up to 30V Dual Supply	90
MARCONI TF2154/1 0-30V 1A. 0±15V 2A	60
0±7.5V 4A SMITHS	60
4701 5-7V o/p Power Pack	32
SORENSEN DCR 300-2.5 0-300V 2.5A DC Stab.	375
Pulse Generators	
DB ELECTRONICS 150. I.C. pulse generator	50
EH RESEARCH	
122. 1 KHz-200 MHz 5V/50Ω RT 12ns	220
139(L). 10Hz-50 MHz 10V/50Ω RT 5ns	175
1221. Timing Unit 6 Channel 0-10 MHz 5V/50Ω RT 8ns	50
HEWLETT PACKARD	117
214A 100V/50Ω. Double pulse O/P.	350
W50ns-10ms, 10 Hz-1 MHz, 15ns R1 MARCONI	
TF2025 0.2 Hz-25 MHz ±10V/50V RT 7ns	350
Recorders and Signal	
Conditioning Equipment	
PR2200 Instrumentation Recorder	
up to 16 channels. FM/DR. Record	
I.R.I.G. DC-40 kHz FM. 100 Hz-	
200 kHz DP	6500
300 kHz DR BRUNO WOELKE ME102B. Wow and flutter meter	6500 75

Bigger stock investment greater equipment range means wider choice

Temperature Measuring Frices from E Equipment (NB Thermocouples not incl.) COMARK

				-	
DEVIANCE CONTRACTOR	Prices	•	Prices		Price
BRYANS SOUTHERN	from £	DYMAR	from £	Spectrum Analysers	from
BS314 4 channel 1mV-10V		1525 100 kHz-184 MHz Int/Ext	- box	HEWLETT PACKARD	
16 speeds BS316 6 channel 1mV-10V	1650	AM/FM Batt/Mains	525	8443A Tracking Gene/counter	
16 speeds	2350	GENERAL RADIO		100 kHz-110 MHz	
	2300	1362 UHF, 220-920 MHz	450	8445A Automatic pre-selector	
HEWLETT PACKARD		GOULD ADVANCE		10 MHz-18 GHz	13
680M. 5 inch. Stripchart Single Pen	-	SG70 5 Hz-125 kHz 600Ω 4w	85	8555A RF Plug-in 10 MHz-18 GHz	- 15.
5mV-120V I/P 20cm/min 2.5 cm/Hr	275	HEWLETT PACKARD		1 kHz Res	30
7046A Two pen A3 0.25mV-5V/cm	995	204D 5 Hz-1.2 MHz. 600Ω. 80dB att.		851B/8551B Display & RF Section	
KUDELSKI		0/P 5V RMS	150		1,3
Nagra 4.2 LSP Professional Audio				NELSON ROSS	
Recorder (Batt optd)	1215	620B 7-11 GHz 50Ω FM/PM 1mw 8614A 800 MHz-2,4 GHz + 10dBm	1100	011. DC-20 kHz. 80dB dynamic	
PHILIPS		to - 127 dBm 50Ω AM/FM	1950	range. Dispersion: 100 Hz-6 kHz	3
PM 8251 Single pen 10in chart		8616A 1.8-4.5 GHz Ext AM/FM/PM	1330	022. DC-100 kHz. Dynamic range 60dB fits into various 500 series	
10mV-50V FS	450	10 mw	925	CRO's	
RACAL		MARCONI		TEKTRONIX	3
Store 4. Uses D/4 inch magnetic		TF144 H/4S HF Generator			
tape. Will record 4 F.M. channels.		10 kHz-72 MHz AM	550	3L5. Plug-in unit fits into various 500B series CRO's, 50 Hz-1 MHz.	
Operates at 7 different speeds.	1675	TF791. FM Deviation Meter		Greater than 60dB dynamic range	
S E LABORATORIES		4-1024 MHz	95		4
6150/6151 12 channel UV		TF801/D1. 10-470 MHz AM. FM.	255	Sweep Generators	
1250 mm/s-25 mm/min 6 in chart	1400	TF995A/2. 1.5-220 MHz AM. FM.	350	HEWLETT PACKARD	
994 6 Channel Pre-Amp ± 1% ± 1V		TF2171 Digital Synchroniser for		8690B Mainframe. Int/Ext AM. Ext	
o/p	450	TF2015	525	FM ~~	6
6008 25 Channel µV 8 in 4m/sec to		TF2002/AS 10 kHz-72 MHz FM/AM 0.1-1V o/p	205	8693B / 100 3.7-8.3 GHz.5mW. PIN	
25mm/min	895	TF2012 UHF, FM 400-520 MHz,	625	levelled 'N' connectors	6
SMITHS INDUSTRIES		0.03uV. Counter o/p	650	8699B/100 0.1-4 GHz.6mW. (20mW	
RE541.20 Single Pen. 0.5mV-100V				to 2 GHz). PIN levelled. 'N'	40
FSD. 3-60cm/min and hour	350	TF 2012 UHF, 400-520 MHz. FM	550	connectors	12
YOKOGAWA		RACAL		TEXSCAN	
3046. 10 inch Chart Single Pen. 0.5		9081 5-520 MHz LED Display O/P -		9900 Sweep Generator 10-30 MHz	
mV-100 VI/P2.60cm/min and/hr	350	130dBm AM/FM	1875	CRT Display	5.
3047. 2 Pen Version of 3046	425	SCHAFFNER		VS60 Sweep Generator 5-100 MHz	_
Signal Sources and		NSG330 Ignition Interference		Rate 60 Hz	9
Generators		Attachment	150	TV Markers set of 5: 31.5, 32.5, 35, 39.5 & 41.5 MHz	
		NSG200B Mains Interference		LN40A Log Amplifier	1
BOONTON		Simulator (Mainframe)	250	LINHUA LOG Amplifier	1
102B 4.3-520 MHz Int/Ext FM/AM	4705	STC			
0.1μV-1V 50Ω	1725	74216 Noise Generator 20 Hz-4 kHz			
		Flat/CCITT Wtg	315		

COMARK 1601BLS 87°C to 1000°C Type K Thermocouples
1604BLS — 60°C to + 170°C
Type K Thermocouples
1625BLS — 100°C to + 300°C Type T Thermocouples 1642BLS — 120°C to +800°C Voltmeters-Analogue AVO 8 Mk IV AC/DC V.AC/DC Ampś. Ω BOONTON 92AD/01/09 10 kHz-1.2 GHz 1999 FSD 10μV Res 92C 10 kHz-1.2 GHz 500μV-3V. 1% HEWLETT PACKARD 400E Millivoltmeter 10 Hz-10 MHz B/W 1mV FSS 427A. AC/DC/Ω multimeter 3406A. 10 kHz-1.2 GHz 3400A 10 Hz-10 MHz 1mV-300V True RMS KEITHLEY 610C Electrometer DC 1mV-100V, Amps 10⁻¹ Recorder o/p LEVELL TM3B 5µV-500VAC 1 Hz-3 MHz + MARCONI TF2603. AC voltmeter to 1.5 GHz PHILIPS PM2454B-1mV-300V. 10 Hz 12 MHz Z in 19MΩ. DC O/P RACAL 9301 RMS Millivoltmeter 10 kHz-1.5 GHz with carry case Voltmeters-Digital ADVANCE DMM 7A/01 1999 FSD AC/DC/Ω/Current FLUKE

Prime Equipment £1975 9081 5-520 MHz Generator 130 dBm AM/FM HEWLETT PACKARD HEWLETT PACKARU

8640B Precision AM-FM Signal Generator
1417 Spectrum Analyzer — Mainframe
1552B Spectrum Analyzer — IF Section
8553B Spectrum Analyzer — RF Section
8555A Spectrum Analyzer — RF Section
8556A Spectrum Analyzer — LF Section
8556A Spectrum Analyzer — LF Section
8556A Spectrum Analyzer — LF Section £3550 £2995 TEKTRONIX 485 Dual Trace 350 MHz Oscilloscope T912 Dual Trace Storage Oscilloscope DC-10 MHz 250 cm/ms writing speed £2200 €699 7313 Storage Oscilloscope Mainframe 4.9 cm/µs writing speed DC-25 MHz 7A22 Differential Plug-in. As new DC-1 MHz 8558B Spectrum Analyser (for 180 Mainframe) £670 10μV-10V/Div (12 month guarantee) 1600A 16 Channel Display Logic Analyzer 7A26 Dual Trace Plug-in. DC-150 MHz 5mV-5V/Div. 7853A Dual Timebase 5ns-5s/Div CRT Readout PM 3212 Dual Trace 25 MHz 2mV/Div

Carston Prime Equipment brings you recent "State-of-the-Art" instruments

at competitive prices, with fast delivery (2-4 weeks). Every "Prime" instrument carries the Carston 90 Day Full Guarantee covering parts and labour.



ALL PRICES LISTED ARE EXCLUSIVE OF VAT (Standard Rate

CARSTON ELECTRONICS LTD. SHIRLEY HOUSE, 27 CAMDEN ROAD LONDON NW1 9NR. Telex 23920

PLEASE NOTE:

8000A 1999 FSD. AC/DC/OHMS/Current

SOLARTRON

True RMS/DC A200 19999 FSD DC only

DRANETZ

HEWLETT PACKARD 34740A/34702A 9999 FSD.AC/DC/OHMS

A203.19999 FSD AC/DC/ Ω . Sensitivity: (1 μ V DC, 10 μ V AC, 100mΩ resistance) A205.19999 FSD AC/DC/Ω

A243, 119999 FSD AC/DC/Ω

7050.99999 Auto AC/DC/Ω Voltmeters Vector/Phase

Sensitivity: (1μV DC, 10μV AC, 10mΩ resistance)

305B 9999 FSD Mainframe for PA

HEWLETT PACKARD

10.V-1000V AC & Q


LM1420.2. 2300 FSD DC only 0.05% LM1420.2BA. 2300 FSD AC

LISTED HERE IS ONLY A SELECTION OF OUR WIDE STOCK OF EQUIPMENT -FOR SPECIALIST NEEDS OR FOR DETAILS OF OUR FULL STANDARD RANGE OF EQUIPMENTS -

RING US TODAY!

Redundant **Test Equipment**

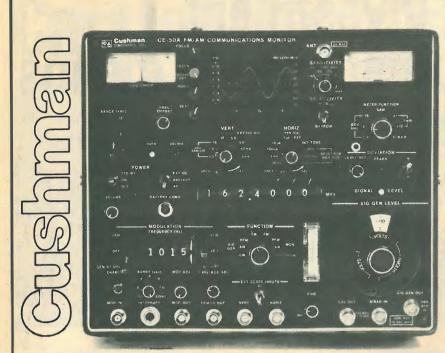Why not turn your under-utilized test equipment into cash? Ring us and we'll make you an offer



Compact, versatile field service monitors for two-way radio maintenance

CE-50A: FM/AM Field Service Monitor CE-50A-1: FM/AM Field Service-**Spectrum Monitor**

Exclusive representative.

Aspen Electronics Limited

Communications Equipment and Components

2 Kildare Close, Eastcote, Ruislip, Middlesex HA4 9UR Telephone: 01-868 1188 Telex: 8812727

WW - 034 FOR FURTHER DETAILS

AS TRANSFORMERS FROM TITAN

NEW FRANCHISE AT FANTASTIC PRICES - EX STOCK WE GUARANTEE THESE PRICES TO BE UNBEATABLE ANY WHERE!!

		and the same of th						
12/24V RANGE PRI 220/240V SEC: \$\overline{1}{00000000} \overline{1}{00000000} \overline{1}{00000000} \overline{1}{00000000} \overline{1}{000000000} \overline{1}{000000000} \overline{1}{000000000} \overline{1}{0000000000} \overline{1}{000000000000000} \overline{1}{12} \overline{1}{00000000000000000000000000000000000	15/30V RANGE PRI 220/240V SEC: #70000000 #70000000 #70000000 #70000000 #70000000 #70000000 #70000000 #70000000 #70000000 #7000000 #7000000 #7000000 #7000000 #7000000 #7000000 #7000000 #70000000 #7000000 #7000000 #7000000 #7000000 #7000000 #7000000 #70000000 #70000000 #70000000 #70000000 #70000000 #70000000 #700000000	25/50VRANGE PRI120/220/240V SEC: #700700000 V 250 25V V 8V 18V 18V 25V VOLTS OUT 5 == 25 0 25 TYPE AMPS PRICE P/P 102 1.0.50 2.88 1.43 103 2 1.0 3.60 1.43 104 4 2 7.04 1.73 105 6 3 8.33 1.90 106 8 4 11.19 2.20 107 16 6 14.79 2.20 118 16 8 20.49 2.55 119 20 10 24.52 2.55 119 20 10 24.52 2.55	30/60 V RANGE PRI 120/220/240V SEC: \$600000000 VOLTS 6 == 30					
187 30.15 17.72 2.45 232 40 20 25.16 3.50 226 60 30 35.35 4.00 25.16 3.50 226 60 30 35.35 4.00 25.16 3.50 2.00 25.16 3.50 2.00 25.16 3.50 2.00 25.16 3.50 2.00 25.16 2.00 25.16 2.00 25.16 2.00 25.16 2.00 25.16	AUTOTRANSFORMERS 240/220—115V (00000000000000000000000000000000000	CASED AUTOTRANSFORMERS 240V LEAD IN:115V 2PIN SOCKET OUT TYPE VA PRICE P/P 56W 20 5.52 0.58 64W 80 7.63 1.43 4W 150 9.63 1.73 69W 250 11.98 1.90 67W 500 18.67 2.20 84W 1000 26.90 2.65 95W 2000 48.45 7.00 73W 3000 69.18 8.00	LINE ADJUSTMENT AUTOTRANSFORMERS (00000000000000000000000000000000000					
MAINS ISOLATORS (SAFETY SCREEN) CONTROL	TYPE VA PRICE P/P 243F 60 7.35 1.43 244F 100 8.61 1.73 245F 200 12.15 2.05	TYPE VA P/P 277PI 750 £ £ 279PI 1500 50.60 7.00 280PI 2250 68.26 7.00	MAINS ADAPTORS 13 amp plus in type, reverible spider jack lead TYPE VA MA PRICE P/P 100 6-7.5-9v 250 3.85 0.58 REGULATED 101 6-7.5-9v 300 4.70 0.58					
152F 250 14.75 2.20 153F 350 18.22 2.55 154F 500 22.70 2.65 135F 750 32.08 7.00 156F 1000 41.26 7.00	350 18.22 2.55 500 22.70 2.65 249F 500 27.70 2.65 750 32.08 7.00 250F 1000 41.26 8.00 CENTRAL HALL CHAMBE							

WW-018 FOR FURTHER DETAILS

Introducing the first 41/2 digit handheld DMM in a market that's been the exclusive domain of 31/2 digit models. Until now . .

The new Keithley 135.

Combining outstanding specification with impeccable performance. And confirming Keithley's position as a major innovator in D.M.M. technology:

- 0.05% DCV accuracy
- Five functions
- Low battery indicator
- Full overload protection:

1000V max DCV


1000V peak ACV

300V max Ohms

- 10 amp range
- ACV pandwidth to 20 kHz

The price – only £139 + VAT Need a bench unit? Then take a look at the new Keithley 176. Five functions, $4\frac{1}{2}$ digits, $\pm 0.05\%$. DCV accuracy, and full function annunciators. Built up to a standard – not down to a price. Yet at only £179 + VAT, the 176 gives quality, 41/2 digit performance at a cost some 31/2 digit manufacturers would dearly love to match. To find out more, fill in the coupon. And see what keeps Keithley one step ahead.



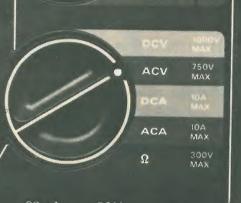

KEITHLEY

Keithley Instruments Ltd 1 Boulton Road Reading Berkshire RG2 0NL Telephone (0734) 861287

Telex 847047

WW - 43 FOR FURTHER DETAILS



320 pages worth of the latest & best in signal processing components.

Write to Pascall for this new M80 catalogue which covers the complete Merrimac range of signal processing components and integrated networks from DC to 4GHz. It also provides reliability data in the form of MTBF calculations for each product area.

Merrimac is one of the World's most technically advanced companies specialising in low frequency lumped element components and integrated networks; microwave stripline components, subsystems, high power ferrite isolators and circulators.

So write to Pascall today for your copy of the M80 on your company's notepaper (or phone

your area of interest - we

if you prefer) indicating


guarantee you'll find it one of the best.

in signal processing

Def Stan 05-31/BS9000/CECC approved

Pascall Flectronics Limited Hawke House, Green Street, Sunbury-on-Thames, Middlesex TW16 6RA Telephone: (09327) 87418 Telex: 8814536 the best in electronics

WW - 042 FOR FURTHER DETAILS

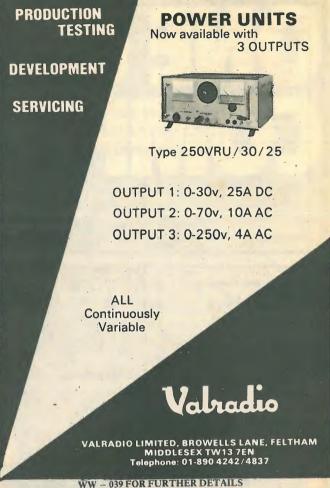






WIRELESS WORLD APRIL 1981



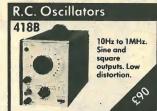
















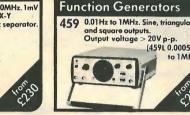





















Just some of the extensive range of

KIKUSUI HIGH QUALITY ELECTRONIC TEST INSTRUMENTS


Post the coupon for your full, informative catalogue now



Name	e the full, informative Kikusui cated are correct at time of supplying copy to publication	credit cards accepted Use Acce	ess here
11/0/2	Telephone		
	O C II LUIT AA :	I I I D I I' CI/ 4	ID

2, Castle Hill Terrace, Maidenhead, Berkshire SL6 4JR TELONIC/BERKELEY U.K Telephone: Maidenhead (0628) 73933 Telex: 849131 Telber G

100,000,000,000,000 Ohms

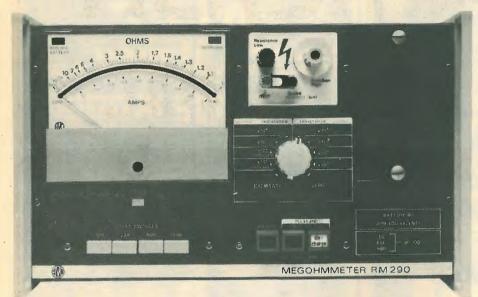

The AVO RM290 is a bench type megohmmeter with a resistance range that goes up to $10^{14} \Omega$: making it ideal for those applications where there is a need to measure the electrical resistance of

You can use the RM290 for tests on insulating components in electronic test voltages of 100, 250, 500 or 1000 V. Readout from the single resistance scale on the meter is direct, irrespective of the test voltage selected.

You'll find the AVO RM290 a great asset. Get in touch with us today and we'll let you have


You'll never meet a better meter

WW - 060 FOR FURTHER DETAILS



AVOLimited, Archcliffe Road Dover, Kent, CT17 9EN Tel: 0304 202620 Telex: 96283

Thorn Measurement & Components Division

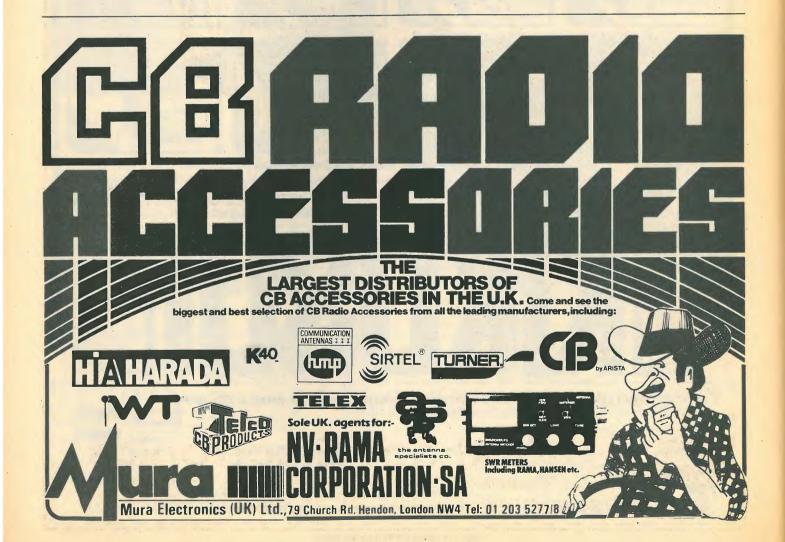



amcron INDUSTRIAL MUSCLE



Model - M600

- POWER RESPONSE DC 20KHz ± 1dB.
 ★ OUTPUT POWER IN EXCESS OF 1.5kW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.).
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KVa.
- * HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- * OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- * FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- * TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- **★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.** * 3-YEAR PARTS AND LABOUR WARRANTY

For full details on all Amcron Products write or phone Chris Flack



Kirkham Electronics

MILL HALL, MILL LANE, PULHAM MARKET, DISS, NORFOLK IP21 4XL DIVISION OF K.R.S. LIMITED TELEPHONE (037 976) 639/594

WW - 059 FOR FURTHER DETAILS



We use advanced winding technology to make our toroidal transformers. They have only half the weight and height of their laminated equivalents and are appreciably more efficient. Our toroidals cost virtually the same as the older types which they are rapidly replacing. Induced hum is reduced by a factor of ten. Supplied with rigid mounting kit with centre bolt, steel and neoprene washers.

(+£1.80 p.p. +£1.60 VAT) SECONDARY SECONDARY RMS VOLTS RMS CURRENT 80mm dia. x 35mm £5.19 50va 110mm dia. × 45mm **£10.59** (+£1.30 p.p. + 0.97 VAT 110 220 240 90mm dia. × 30mm £5.76 110mm dia. × 50mm **£12.27** Weight I Kg 300va Weight 2.6 Kg (+£1.50 p.p.+£1.09 VAT (+£2.00 p.p. +£2.14 VAT) 7X026 7X025 7X028 7X029 7X030 140mm dia. × 60mm **£16.35** 120vx 90mm aid. 1.2 Kg Weight 1.2 Kg (+£1.60 p.p. +£1.25 VAT) 500vk Weight 4 Kg (£2.10 p.p. + £2.77 VAT) 8X028 8X029 8X030 110 220 240 • I.L.P. TOROIDAL TRANSFORMERS ARE GUARANTEED FOR 5 YEARS

CHOICE OF 3 PRIMARY INPUTS

I.L.P. Toroidal Transformers are available in choice of 110V, 220V, 240V, coded as follows: (Secondaries can be connected in series or parallel)

For 110V Primary insert 0 in place of "X" in type number.
For 220V Primary (Europe) insert 1 in place of "X" in type number
For 240V Primary (U.K.) insert 2 in place of "X" in type number.

Example - 120VA 240V 15+15V. 4A = 42013.

* CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.


FREEPOST facility.(U.K. only).

Simply address envelope to FREEPOST to address below. NO STAMP REQUIRED.

TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P.
Electronics Ltd or quote your ACCESS or BARCLAYCARD
account No. To pay C.O.D. add £1 extra to TOTAL value of order.
Also available from ELECTROVALUE and MARSHALLS.



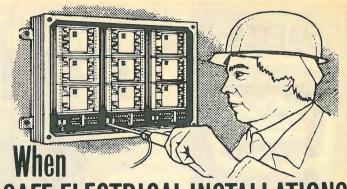FREEPOST T5, GRAHAM BELL HOUSE, ROPER CLOSE CANTERBURY CT2 7EP Phone (0227) 54778 Technical (0227) 64723 Telex 965 780



SAFE ELECTRICAL INSTALLATIONS are your concern

Measures earth resistance from equipment to distribution board earth up to 100m apart Measures contact resistance of circuit breakers.

WIRELESS WORLD APRIL 1981

Also a boon to manufacturers of transformers, chokes and coils, wire and cables etc

Test current up to 5A ensures contact 'wetting'

Resolution 1 miliiohm

Smaller and lighter than alternative instruments

Costs a lot less too ... only £210 UK ex VAT

Good range of optional accessories

Wholesaler enquiries welcomed

Just what do consultants do all day?
 (See Chapter 11.)
 How to market your ideas. (See

Why you'll never have to worry about

competition. (See Chapter 13.)

Perhaps no one is better qualified to

Perhaps no one is better qualified to have written this book than Hubert Bermont. He has served as consultant to more than 70 major companies and trade associations, including the U.S. Chamber of Commerce, McGraw-Hill.

the Electronic Industries Association and the Smithsonian Institution. Yet he made the decision to become a consultant only after being fired from

an executive position at the age of 43.

ou'll learn first-hand how he did it

And much more!

Detailed brochure and price list from

FARNELL INDUSTRIAL CONTROL · WETHERBY · WEST YORKSHIRE LS22 40H · TEL. (0937) 61961 · TELEX 557294 FARIST G WW - 062 FOR FURTHER DETAILS

How to become a SUCCESSFUL CONSULTANT

in your own field.

Have you ever wished you could

you need the new

low resistance test set

Are you ever wished you could quit your job and start working for yourself?

Well, maybe you can! Many people are amazed when they discover the tremendous amount of professional experience and specialized knowledge they've accumulated; experience and knowledge that others will gladly pay for. Literally thousands of people who made that discovery are now pros-pering as independent consultants. full and part time.

full and part time.
The way to begin is by reading How to Become a Successful Consultant in Your Own Field, by Hubert Bermont.
Clear, straightforward, packed with solid information and advice, this authoritative manual tells you everything you need to know to establish your own independent consulting practice. Here's a sampling of the contents:

of the contents: What does it take to be a successful consultant? (See Chapter 1)

How to get started. (See Chapter 3.)
How to operate your business – a collection of "tricks of the trade."

(See Chapter 5.) (See Chapter 5.) What to charge your clients - plus

five helpful rules on fees. (See Chapter 6.)

Why you should never work on a contingency (speculative) basis. (See Chapter 7.)

Ingenious ways to promote yourself, and make people want your services.

 Contracts: why you should avoid them at all cost. (See Chapter 10.) © CHARTSEARCH LTD., REG. NO. 953026. 11 Blomfield Street, London EC2M 7AY.

and how you can do it too! How to Become a Successful Consultant in Your Own Field is just £12.50 (tax deductible if used for business purposes), and you're fully protected by this unconditional money-back quarantee: Keep the book for three weeks. If you're dissatisfied with it for any reason whatever, simply return it and every penny of

your £12.50 will be promptly refunded.


How many times have you told yourself that you're not getting anywhere; that it's time to think eriously about a major change in you

To: CHARTSEARCH LTD, 11-12 Blomfield Street, London EC2M 7AY. Please send me, postpaid, my copy of "How to Become a Successful Consultant in Your Own Field", for which I enclose my payment of £12.50. Nam

Own Field , for which I enclose my payment of £12.50.
Name
Address
and the first containing any in the containing and

Overseas orders, add £3 per order for airmail shipment.

METER PROBLEMS?

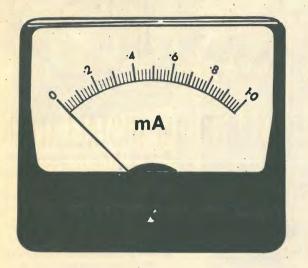

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937 Telex: 892301 HARTRO G

WW-061 FOR FURTHER DETAILS



SEQUENTIAL TONE GENERATOR - A PARAGON WITH MANY **VIRTUES**

This single instrument provides all the signals necessary for testing Pocket Pagers, Selective calling systems, C.T.C.S., Tone Burst Systems as well as R.C.C. systems using PTMF, MTS, IMTS, Interrupt and F.S.K.

The memory also has additional capacity for tomorrows communications needs.

For further information contact Mike Taylor

FieldTech Ltd.

London

Heathrow Airport

Hounslow TW6 3AF

Tel: 01-759 2811

Telex: 23734

FLDTEC G



PARAGON ELECTRONICS

WW - 015 FOR FURTHER DETAILS

Incredible Quality
Incredible Performance
Incredible Price!!!
Incredible Price!!!



HM312 Dual Trace

Oscilloscope DC-20MHz. Sensitivity 5mV 20V/cm. Time base range 0.5uS-0.2S/cm with x5 horiz mag to 100nS/cm, with variable control uncalibrated to 40nS/cm. CRT screen 8 × 10cm. Full XY using chil as X input. 2.3MHz, TV trigger.

NOW BETTER VALUE THAN EVER AT

Trace

with delayed



Sensitivity 5mV-20V/cm Time base range 0.1uS-2.0S/cm with x5 horiz mag to 20nS/cm. Delay ranges 7 decade steps 100ns-1S with fine control CR1

Full XY using ch I as x input, handwidth 4 MHz. Z input. Delay line allows viewing of leading edge Vertical overscar indicated by 2

Other models available.
HM307 10MHz plus component tester.
HM412 20 MHz with sweep delay. £35
HM812 50 MHz storage. £1458.00

World-beating Oscilloscope Offers

Electronic Brokers



London WC1X 9LN. Tel:01-278 3461. Telex 298694

WW - 036 FOR FURTHER DETAILS



FASTER THAN A SCOPE— SAFER THAN A VOLTMETER



Total £37.37 including box and instruction manual

GLOBAL SPECIALTIES CORPORATION

Europe, Africa, Mid-East: GSC UK LTD., Dept. 75 Unit 1, Shire Hill Industrial Estate
Saffron Walden, Essex, CB11 3AQ
Telephone: SAFFRON WALDEN 21682
Telex: 817477

Instant - simultaneous monitoring of the logic state of all IC nodes

Just clip it over your IC.

LM-1 Instantly and accurately shows both static and dynamic logic states on a bright 16 LED display.

LM-1 finds its own power.

LM-1 cuts out guesswork, saves time, and eliminates the risk of short circuits.

LM-1 is suitable for all dual-in-line logic ICs. LED on = logic state 1 (high), LED off = logic state

0 (low), and each LED is clearly numbered 1 to 16 in the conventional IC pattern.

> GLOBAL SPECIALTIES CORPORATION, DEPT. 75 Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex.

		_	٠.	-	4	-			1							1			L	en	cl	0	Sρ	c	h	200		/ء	P	n
										₹E									T	ic	k	bo	ОX			Ī				
										1									F	RI	FI	= ,	ca	ıta	alc	οa	116	,		
ddress																											*			
ime	•	٠	•	•	•	•	٠	•	•	•	•	•	•	•	•	•	*	•	٠	•	•	•	•	•	٠	٠	•	٠	•	•

LM1. £37.37 inc. p & p and VAT

Phone your order with Access, Barclaycard or American Express Card No. Expiry date.

WIRELESS WORLD APRIL 1981

SOUND INVESTMENT



Replacement tape heads from Monolith could mean a big improvement in sound quality from your tape recorder. A full catalogue is available, price 50p, which features a wide range of heads for cassette and reel to reel machines, as well as replacement motors, tape transports, etc.

Universal cassette heads to EIAJ standard, hole centres 17mm apart, 12mm from head face:

B12-02	Mono record/playback	£ 4.62							
B24-01	Stereo playback	€ 4.62							
B24-02	Stereo r/p	£ 7.66							
B24-07	Stereo r/p for Dolby systems	£ 9.05							
C42RPH20	Stereo r/p sendust head, suitable for chrome &								
	metal tapes	£10.67							
C42RPH04	Stereo r/p glass ferrite, the ultimate long life,								
	high performance head	£13.34							
C42RPS18	Stereo twin gap r/p long life head for record								
	monitoring	£28.99							
C21ES18	Mono/Stereo erase head	£ 2.13							
C44RPH03	Four channel/track r/p	£15.15							
C22ES04	Twin half track erase	€ 5.43							
Ex stock deliveries, all prices include VAT. Post and packing 40p.									

electronic products

The Monolith Electronics Co. Ltd., 5/7 Church Street, Crewkerne, Somerset TA18 7HR: Tel: 0460 74321, Telex;

COMMUNICATION TUBES — EX STOCK

4-65A	5763	QQV06-40A
4-125A	6080	QQV07-50
4-250A	6146/A/B	QV08-100
4-400A	6155	QY4-125
4-1000A	6156	QY4-250
4CX250B	7527	QY4-400
4CX350A	8042	QY5-3000A
4CX1500A	QQV03-10	& MORE
4CX1500B	QQV03-20A	

R/F POWER TRANSISTORS — EX STOCK

	9 .		
2N3375	2N5102	BLY33	BLY88
2N3553	2N5590	BLY34	BLY89
2N3632	2N5591	BLY36	BLY91
2N3733	2N5641	BLY53A	BLY92
2N4040	2N5642	BLY55	BLY93
2N4127	2N5643	BLY83	BLX13
2N4128	2N6080	BLY84	BLX14
2N5070	2N6081	BLY85	BLX67
2N5071	2N6082	BLY87	BLX68
2N5090	2N6083		& MORE
	2N3553 2N3632 2N3733 2N4040 2N4127 2N4128 2N5070 2N5071	2N3553 2N5590 2N3632 2N5591 2N3733 2N5641 2N4040 2N5642 2N4127 2N5643 2N4128 2N6080 2N5070 2N6081 2N5071 2N6082	2N3553 2N5590 BLY34 2N3632 2N5591 BLY36 2N3733 2N5641 BLY53A 2N4040 2N5642 BLY55 2N4127 2N5643 BLY83 2N4128 2N6080 BLY84 2N5070 2N6081 BLY85 2N5071 2N6082 BLY87

WW - 064 FOR FURTHER DETAILS



SEND FOR DETAILS TO: AERO ELECTRONICS (AEL) LTD GATWICK HOUSE HORLEY, SURREY, ENGLAND TEL: (02934) 5353 TELEX 87116 (AERO G) CABLES AERO G TELEX HORLEY DMM with true RMS on

AC volts and current DC volts 200mV-1KV. 10µV resolution AC volts. 200mV-750V, 10µV resolution. DC/AC current 200μΑ-2Α, 0.01μΑ resolution resistance 200Ω-20MΩ. 0.01Ω resolution. Also reads dB direct referenced to 16 stored impedances. Conductance ranges 2mS and 200nS. £245 mains model £285 mains battery

8012A 31/2 Digit LCD DMM with true RMS on AC volts and current. DC volts 200mV-1KV, 100µV resolution. AC volts 200 mV-750V, 100μV resolution. DC/AC current 200μA-2A, 0.1μA resolution. Resistance 200 Ω -20M Ω , 0.1 Ω resolution Low resistance 2 Ω and 20 Ω 1mΩ resolution Conductance ranges 2mS-20μS-200nS



£199.00 mains model £219.00 mains battery. 8010A 31/2 Digit LCD DMM Same spec as 8012A plus a 10Amp AC/DC current range. but no low resistance £159.00 mains model

£179.00 mains battery. 8024A 3½ Digit hand held LCD DMM with peak hold Level Detector and continuity tester DC volts 200mV-1KV, 100uV resolution

AC volts 200mV-750V, 100µV resolution.DC/AC current 2mA-2A; 1μA resolution. Resistance 200 Ω -20M Ω , 0.1 Ω resolution. Conductance 200nS. Peakhold of AC or DC volts and current. Level detector operates around +0.8V reference. Audio tone on level and continuity, £149.00, carrying case £7.00 extra.

8020A 31/2 Digit hand held LCD DMM. spec as per 8024A with extra conductance range of 2mS but no peak hold, level or continuity ranges. Complete with carrying case. £125.00.

8022A 31/2 Digit hand held LCD DMM. Spec as per 8020A but no conductance ranges and slight reduction in accuracy. £75.00 carrying case £7.00 extra.

> Also available a range of accessories including current shunts, EHT probe, rf probe, Temperature probe and touch and hold probe. Full details on request. The warranty period on all items shown is 1 year other than the 8020A

Electronic Brokers

London, WC1X 9LN Tel: 01-278 3461 - Telex 298694

WW 037 FOR FURTHER DETAILS

WW - 007 FOR FURTHER DETAILS



SIGNAL SUCCESS * Versions available for non-

British TV systems

Reader inquiry number 220

Test & Measuring

Instruments

PM 5326 RF signal generator

* 100 kHz — 125 MHz in nine

overlapping ranges with 5 digit display (
* Built-in 5 digit counter displays external frequencies.

Two versions available: 100 MHz (I kHz resolution) - PM 5326X or I MHz (10 Hz resolution) — PM 5326 \star 50 mV RF output at 75 Ω can be attenuated to over 100 dB

* Electronically stabilized output level * Wobbulator facility for IF amplifiers, AM/FM radio and TV receivers

Reader inquiry number 221

PM 2517 digital multimeter

- Full four digitsChoice of LED or LCD display
- * True RMS AC readings (AC coupled)
- * Autoranging with manual override
- * Current up to 10 A

* Options include temperature and data hold probes

Reader inquiry number 223

- * Reciprocal technique giving fast high resolution measurements down to 10 Hz
- * Auto triggering on all waveforms and duty cycles
- * 15 mV RMS sensitivity
- * High stability X-tal oscillators: 10⁻⁷/month
- * Microprocessor control Reader inquiry number 225

SOME OTHER STARS FROM THE RANGE

PM 5501 colour bar pattern generator

* Ideal for mobile maintenance

* 5 test patterns for colour and b/w

* RF signal switchable between VHF, Band III, and UHF Band IV

* | kHz tone for sound checks Reader inquiry number 226

PM 5107 low distortion LF generator

- * Frequency range 10 Hz 100 kHz
- * Distortion 0.02%
- * Sine and square wave signals
- * Separate TTL output

Reader inquiry number 227

PM 6307 wow and flutter meter

- * X-tal controlled oscillator
- * High accuracy and frequency stability * 3150 Hz or 3000 Hz switchable
- * Separate 'drift' and 'flutter' indication Reader inquiry number 228

PM 6456 stereo generator

- * Complete stereo signal with low crosstalk
- * Separate L and R signals
- * External modulation facility
- * X-tal controlled pilot
- * Adjustable multiplex signal and tunable 100 MHz RF signal

Reader inquiry number 229

WHERE TO BUY YOUR PHILIPS AUDIO AND VIDEO SERVICE EQUIPMENT

The entire range is available from the Philips lectronic Instruments Department (see address below) or from Philips Service Centres ('phone 01-686 0505 for the address of your nearest branch). In addition, the PM 2517 and PM 3207 can be obtained from Wessex Electronics Ltd, 114-116

North Street, Downend, Tel (0272) 571404.



Use the inquiry service to obtain information about the products which interest you. Alternatively, 'phone Cambridge (0223) 358866 and speak to our Commercial Office on extension 145 or 148. Inquiry No.

PM 5519 CTV pattern generator	220
PM 5326 RF signal generator	221
PM 3207 oscilloscope	222
PM 2517, 2505, 2502 multimeters	223
PM 6661 80 MHz frequency	
counter	224
PM 6667/6668 high resolution	-
counters	225
PM 5501 colour bar pattern	
generator	226
	227
PM 5107 LF generator	
PM 6307 wow and flutter meter	228
PM 6456 stereo generator	229

Pye Unicam Ltd

Philips Electronic Instruments Dept York Street, Cambridge CB1 2PX, England Tel. Cambridge (0223) 358866. Telex 817331

BULK EPROM MICROSYSTEAR PROGRAMMING SYSTEMS 81

This unit provides simple, reliable programming of up to 8 EPROMS simultaneously. It has been designed for ease of operator use - a single 'program' key starts the self check - blank check program - verify sequence.

ndependent blank check & verify controls are provided along with mode, pass/fail indicators for each copy socket and a sounder to signal a correct key command & the end of a programming run. Any of the 2704/2708/2716 (3 rail) & 2508/2758/2516/2716/2532/2732 (single rail) EPROMS may be selected without hardware or personality card changes. PRICE £545 + VAT. Postage paid

BULK EPROM ERASING



EX-STOCK

MODEL UV141 EPROM ERASER

- 14 EPROM capacity
- Fast erase time
- Built-in 5-50 minute timer
- Convenient slide-tray loading of devices
- Safety interlocked to prevent eye and skin damage
- Rugged construction MINS & ERASE indicators
- Price £78 + VAT postage paid

MODEL UV140 EPROM ERASER Similar to Model UV141 but without timer. Price £61.50 + VAT



EX-STOCK 1-9 10-24 25-49 50-99 **£6.00 £5.50 £5.00 £4.50** £3.90 £3.50 £3.10 £2.90

Postage and Packing is included in all prices. ADD VAT at 15%. All our EPROMS are manufactured by leading companies and are fully guaranteed, branded and to full specification.

WRITE OR TELEPHONE FOR FURTHER DETAILS OR SEND OFFICIAL COMPANY ORDERS/CHEQUES TO:

PLEASE NOTE NEW ADDRESS & TELEPHONE NUMBER

GPINDUSTRIAL ELECTRONICS LTD.

Unit 6, Burke Road, Totnes Industrial Estate, Totnes, Devon Telephone: Totnes (0803) 863360 sales, 863380 technical

Telex: 42596
DISTRIBUTORS REQUIRED - EXPORT ENQUIRIES WELCOME

WW-064 FOR FURTHER DETAILS

Get a great deal from

available. A veritable treasure house of components, test gear, tools, etc.

Specially interesting to the radio amateur are the following Leader instruments available from stock:

Antenna Coupler LAC895 3.5 to 28 MHz Price: £88.00 Antenna Coupler LAC896 50MHz

Price: £44.00 Antenna Coupler LAC897 Price: £44.00 144--148 MHz TRDIP Meter LDM 815 Price: £45.00

1.5 MHz to 250 MHz Antenna Impedance Meter LDM 870A 1.8 MHz to Price: £44.00 150 MHz RE Power

Meter LPM 880 0.5 to 120W Price: £73.00 SHR/Watt-meter LPM 885 1.0W to Price: £47.00

Send SAE for details or phone Richard Kaise 02407 3568 for specialist advice.

Send for our latest catalogue. Free to industrial private individuals.

A. Marshall (London) Ltd. Kingsgate House, Kingsgate Place, London NW6 4TA Industrial Sales: 01-328 1009 Mail Order: 01-624 8582 24hr service Retail branches: London; Glasgow; Bristol.

MORE SPEC, FOR YOUR MONEY

TYPE 747 UNIVERSAL COUNTER TIMER

DC to 150MHz MEASURES

FREQUENCY

AVERAGES 1 to 1000 events

Ch A

+ Ch A to + Ch B PULSE WIDTH Ch A + or -

Ch A (may be gated



& 3.50 carriage, ins. etc.

TYPE 745 COUNTER TIMER



DC to 32MHz 5 DIGITS MEASURES -FREQUENCY PERIOD

COUNT

6 GATE TIMES / TIME UNITS & £3 carriage, ins. etc.

TYPE 746 AUTORANGING FREQUENCY METER £84,88 1Hz to 99 9KH:

> TYPE 615 OFF-AIR STANDARD £97,13 10MHz, 1MHz and 100KHz

OMB ELECTRONICS RIVERSIDE EYNSFORD KENT DAY OAF Tel. Farningham (0322) 863567


Prices, which are CWO and ex-VAT, are correct at the time of going to press and are subject to change without notice

> FROM OMB ELECTRONICS WW - 011 FOR FURTHER DETAILS

oin the Professionals...

of transient and steadystate distortions ★Envelope distor-tion (below 500 Hz) less than 0.05% ★on-board electronic protection \$P.C.B. pin and edge connector termination.

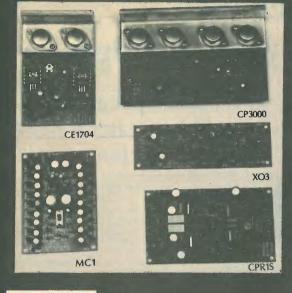\$\pm\$Full range of complimentary components, i.e. P.S.U.'s, heatsinks etc. available from Crimson.



MAX

星马走

uaranteed for two years) and can be used to advantage where high quality signal amplification is required. e power amplifier modules range from 60WRMS to 310WRMS with up to twice this amount in bridge doe. All feature substantial heatsink brackets which can be bolted to any available heatsink or the node. All feature substantial heatsink brackets which can be bolted to any available heatsink or the Crimson purpose designed types. Input sensitivity is set at 775mV and power supply requirements are latered for by one of the three Crimson toroidal power supplies. The Pre-amplifier module (CPR1) is pasically a phono amplifier with sophisticated circuitry incorporating R.I.A.A. equalisation. Also on-loard is auxiliary amplification for tape and tuner inputs. A separate module (MC1) is also available and gives the required boost for low output moving coil type cartridges. External components required are lotted to routing and balance, switches for signal routing and a regulated ± 15V D.C. power lotted (REG1). Complimenting this range, are the electronic crossover modules XO2/XO3 which, with a special muting board (MU1) can be incorporated in all types of active speaker systems.

rous applications are possible with Crimson modules. For example, a complete Hi-Fi Pre & Pov pliffier of 40-125WRMS/channel can be built using our Hardware kits (see Hobby Electronics review gust 1980). Alternatively, Mono or Stereo slave amps of up to 500WRMS can be built into proprietor plnt cases, while other uses include active loudspeaker systems such as designed by R.I. Harcourt in rireless World October/November 1980. Further details of how to use the modules are contained in the Users / Application Manual available at £0.50

Туре	O/P8ohms*	O/P4ohms*	PSU	H/Sinks	Slew	S/N	Sensitivity	T.H.D. (typ)	F.R.	Size
E 608 E1004 E1008 E1704 E1708 CP3000 CPR1(S) AC1(S)	38 44 65 85 125 Output: Output:	70 121 250 775mV 2mV	CPS6 CPS6 REG1 REG1	50mm 100mm 100mm 150mm/FM1 150mm/FM1 FM2	30V/uS 30V/uS 30V/uS 30V/uS 30V/uS 30V/uS 3V/uS	110dB 110dB 110dB 110dB 110dB 110dB 70dB 65dB 90dB	775mV 775mV 775mV 775mV 775mV 775mV 2.8mV/RMS 70uV/150 775mV	0.0035% 0.0035% 0.0035% 0.0035% 0.0035% 0.0035% 0.008% 0.008%	1 5Hz 50Khz (3dB) 1.5Hz 50Khz (3dB) 20Hz 20Khz 20Hz 20Khz X over points	80 - 120 - 25 80 - 120 - 25 80 - 120 - 25 80 - 120 - 25 80 - 120 - 25 161 - 102 - 35 138 - 80 - 35 80 - 120 - 35 130 - 50 - 20
102 XO3	Output:	775-2500mV	WRM!	S and is a	iven for	two m	odules run	off the sa	me power supp	

PRICES-	HELD	FROM N	IAY-1	O APRIL	′81	BARCLAYCARD
Power Amplifier	Modules	Power Supply	Modules	Heatsinks		
CE 608	£21.00	CPS1(80VA)	£19.50	50mm	£1 70	
CE1004	£24 50	CPS3 (150VA)	€23.50	100mm	£2 70	VISA
CE1008	£27.50	CPS6 (250VA)	£30 00	150mm	£3 50	12000
CE1704	£35.00	BEG1	£9.30	FM1	£36 00	
CE1708	€35.00	TR6	£2 50	FM2	£42 00	
021100					and the same	Access
Pre-Amplifier	Modules	Active Cross	sovers	Hardware		A
CPR1	F34 00	XO2	£19.00	Pre Amp	£39 80	
CPR1S	£44.50	XO3	€28.35	Power Amp	€38.00	We welcome loces
MC1	£26.00	MU1	£7 50	Thermal Cutouts	£1 90	IN. MCHURIN, MCG-22
MC1S	£37.00				_	



Now, the hand-held 50MHz For £49.00 counter Various accessories are also available.

> It's true. Our new, diminutive frequency counter, the *Max 50 costs a mere £49.00. Which, when you consider its totally automatic performance, is quite outstanding.

Well, what would you normally expect to pay for a guaranteed frequency range of 100Hz to 50MHz; 6-digit LED display; auto-ranging, polarity, slope trigger and input level; and builtin overvoltage protection?

And there's even more. The high reliability of LSI circuitry; sensitivity of 30MV trigger threshold; 3ppm accuracy; choice of battery or a.c. mains operation, and optional antenna.

True value, and yours for the asking.

Just call us on Saffron Walden (0799) 21682 right away. Your own *Max 50 could be hand-held tomorrow!

Dealer enquiries also welcomed. *For a while, supplies will be labelled 'Mini-max'.



GLOBAL SPECIALTIES CORPORATION G.S.C. (UK) Ltd., Dept 7F Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ. Telephone: Saffron Walden (0799) 21682 Telex: 817477

WW - 006 FOR FURTHER DETAILS



fact: we've put a NEW plus into the Super-Track Plus family of V15 Type III Cartridges



Hyperelliptical tip for audibly greater freedom from distortion

One of the critically acclaimed developments introduced in Shure's incomparable V15 Type IV pickup cartridge is its revolutionary distortion-reducing Hyperelliptical nude diamond tip. It established a new standard of sound purity. through a dramatic reduction of both harmonic and intermodulation distortion. Now, the Hyperelliptica tip is also available in the world-famous V15 Type III Super-Track Plus Cartridge, bringing together the sound purity and flat response of the IV at an eminently affordable price. It is truly second only to one other cartridge in the world—the V15 Type IV.

V15 TYPE III-HE

Stereo Dynetic® Pickup Cartridge

If you already own a V15 Type III you can upgrade it!

If you are one of the thousands of audiophiles who already own a V15 Type III, you too can benefit from the new freedom from distortion offered by the Hyperelliptical stylus. Simply replace your present stylus with the new VN35HE improvement stylus. It will give your Type Ill cartridge the same specifications as the new V15 Type III-HE. Takes only seconds to install (see illustration). requires no tools whatsoever.







V15 TYPE III-HE IMPROVEMENT STYLUS



Shure Electronics Limited, Eccleston Road, Maidstone ME15 6AU-Telephone: Maidstone (0622) 59881 WW - 028 FOR FURTHER DETAILS

wireless world

The next seventy years

TOM IVALL, M.I.E.R.E.

Deputy Editor: PHILIP DARRINGTON 01-661 3500 X3586

Technical Editor: GEOFF SHORTER, B.Sc. 01-661 3500 X3590

Projects Editor: MIKE SAGIN 01-661 3500 X3588

News Editor: MARTIN ECCLES 01-661 3500 X3589

Drawing Office Manager: ROGER GOODMAN

Technical Illustrator: BETTY PAI MER

Production & Design: ALAN KERR

Advertisement Manager: BOB NIBBS, A.C.I.I. 01-661 3130

DAVID DISLEY 01-661 3500 X3593

BARBARA MILLER 01-661 3500 X3592

Classified Manager: **BRIAN DURRANT** 01-661 3106

JAYNE PALMER 01-661 3033

JOHN GIBBON (Make-up and copy) 01-661 3500 X3561

Publishing Director: GORDON HENDERSON

The artist Pablo Picasso once said: "Age only matters when one is ageing. Now that I have arrived at a great age, I might just as well be twenty." Wireless World feels much the same. Being the oldest radio journal in the world and having reached this month the Biblical age of three score years and ten, we can justly consider ourselves - in terms of electronics journalism - to have arrived at a great age. And we might just as well be twenty because it is in the nature of a periodical publication to renew itself with each issue. It doesn't matter whether one has produced 1,500 or only 15 previous issues, the next edition is always a completely new book - a new product belonging uniquely to its own moment in history and reflecting its own world at that moment. We did our reminiscing about the past on our 50th and 60th birthdays. Now, already 15 years into the era of the integrated circuit, we are as curious about the future and what it holds for us as any young person just starting to look at electronics as a possible career.

If we survive the next 70 years, what could we be looking back on in 2051 AD? Here a little humility is called for. If the periodical survives (and not necessarily on paper) it may well be a very different animal from what it is now. Electronics may no longer exist as a definable area of technology and industry. Just as radio spawned electronics, which then proceeded to absorb its parent, the same thing may happen again - several times over. On this principle one might look at other branches of science and technology with which electronics is already conjoined and speculate if they are capable of such absorption. Optics, perhaps, chemistry, biology . . . ? Or one might even consider the complete fragmentation of electronics into a variety of other technologies and interdisciplinary activities, some of which don't yet exist.

Extrapolation from present trends does take us a little way - greater complexity and higher performance in electronic products, more devices on a silicon chip, changes in microprocessor architecture and so on. This is the gadgeteering approach which envisages a world increasingly full of clever robots, wristwatch radios, flat ty screens and information centres in the home. But it doesn't allow for the possibility that a completely new, seminal device will be invented that will transform the technology - just as the valve transformed radio communication and the transistor opened the way to integrated circuits. Several laboratories are now exploring the possible use of biological structures as transducers and energy converters. Could this lead perhaps to a stochastic, rather than deterministic, principle of information processing and transmission, analogous to that in the animal central nervous system?

But it is unrealistic to consider a technology in isolation from the society which produces it. You can say with truth that scientists and engineers discover and invent things which change our lives. These individuals, however, are part of society and subject to its pressures. You can say with equal truth that the technology we have is a symptom of the kind of society we are: it develops in particular directions in response to our material, emotional and spiritual needs. Broadcasting, hi-fi and other electronic diversions are technological responses to the needs of the "nuclear family" for entertainment and even "company" in homes that are becoming socially isolated from communities. As in the past, technology will continue to be both cause

1911, in which we were founded, was the fateful year when Rutherford did the historic experiments that led him to postulate the atomic nucleus and the picture of the atom we have now. Since then our physicists have been discovering ever more fundamental particles and our view of matter and energy has been greatly elaborated. During the next 70 years there could be a discovery or insight that would unify our observations and even depart from the traditional line of thinking started by Democritus. Such an event would not immediately alter the practice of electronic engineering but would certainly affect profoundly the work of the applied scientists who research into physical processes to create new devices.

WIRELESS WORLD APRIL 1981

Opto-electronic contact breaker

Compact and maintenance free switching for electronic ignition systems

by J. R. Watkinson, B.Sc., M.Sc.

The conventional automotive contact breaker is still widely used in modern petrol engines despite its shortcomings. Superior alternatives have been available for several years, but car manufacturers have been slow to remove the weak link in the ignition system. This design is simple, cheap, reasonably easy to install, and provides a maintenance free unit which will drive almost all electronic ignition systems which operate with mechanical contacts.

Although many electronic ignition units are available, and several well designed constructional circuits have appeared, most of them are triggered by the existing contacts and use either inductive or capacitive discharge to improve the spark and extend contact life. Some designs claim to eliminate the effect of contact bounce, but the effects of contact heel wear and timing scatter still remain.

The circuit in Fig. 1 provides an output which, for low currents, simulates the contact breaker and can trigger an electronic ignition unit without modification. The existing centrifugal and vacuum advance mechanisms are retained, and the only mechanical part which must be constructed with any precision is a chopper disc.

The light source is an infra-red l.e.d. with a lens to give a well defined beam, which is received by a spectrally and physically matched phototransistor. Light passing between the two devices is interrupted by a chopper disc which produces a rough square wave. This waveform is cleaned up before it is used for timing because electronic ignition circuits generally require a sharp edge to trigger an s.c.r. A conventional two transistor Schmitt-trigger was not used because the regenerative


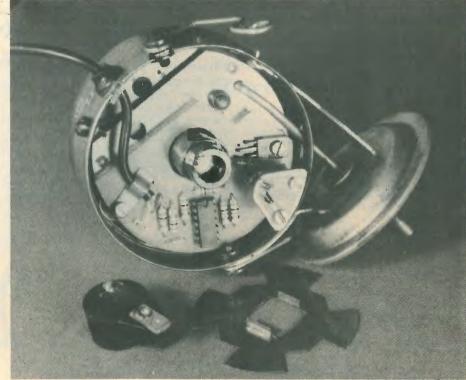


Fig. 2. Printed circuit board mounted on the action plate of a distributor. In the prototype Tr₁ was mounted underneath the board.

action only occurs if the input has a low source impedance and, in this design, the phototransistor is a current source. Instead, an open collector t.t.l. i.c. with two gates connected as a set — reset bistable is used. The inputs are driven in a complementary mode by using a third gate as an inverter, and the remaining gate is used as a buffer. The regenerative action of this circuit gives fast switching, and a conservatively rated series regulator provides reliable operation.

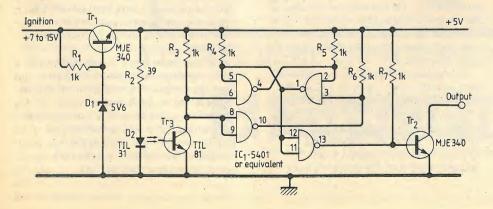
The complete circuit can be built on a glassfibre p.c.b. and mounted inside the



distributor as shown in Fig. 2. The prototype fits a Delco distributor as fitted to many G.M. vehicles, but the layout can be modified to fit most other types. Some foreign vehicles use very small distributors, and for these it is best to house the circuit in a small metal box beside the distributor. Installation is much easier if a replacement distributor is used. Also, the second unit is useful to carry as a spare.

The phototransistor is mounted directly on the p.c.b. and the l.e.d. is mounted about 2.5mm away on a small board supported by 3mm tapped pillars which also carry the l.e.d. current. The main p.c.b. is mounted with spacers on the action plate in the distributor with 3mm screws which must have holes drilled and tapped. As the action plate is rotated by the vacuum advance mechanism, it must not be ob-

Fig. 1. Switching circuit and regulator. Tr_1 and Tr_2 do not require heatsinks, but should be secured with the screws that hold the p.c.b. in place. Note that IC_1 must be a ceramic type to ensure reliable operation during large temperature changes

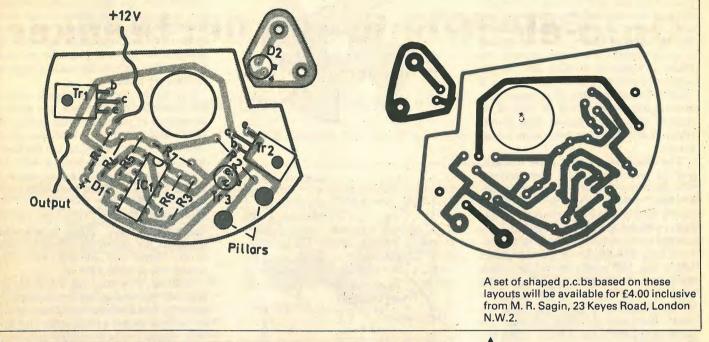

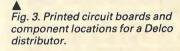




Fig. 4. Phototransistor and I.e.d. mounting. The two pillars must be metal types to carry the I.e.d. current.

Why replace the contact breaker?

A conventional contact breaker consists of a cam, rotated by the engine, which opens and closes a moving contact held in place by a stiff spring. As the contacts are forced open by the cam and closed by the spring, the cam has an alternating torque acting upon it. The cam is turned about the mainshaft by centrifugally operated weights which reach equilibrium with restoring springs to give different spark advance angles for different speeds. Therefore, there are two mass compliance systems which cause a wide distribution of timing. This problem is made worse by manufacturing tolerances in the cam and general wear in the contact breakers. Although a new distributor with correctly adjusted contacts operates fairly well, this peak performance rarely lasts for more than 2000 miles, and most petrol engines spend a significant proportion of their working life with a sub-standard ignition system.

The two most common replacements for the contact breaker are a magnetic pickup, where a lobed rotor varies the flux through a coil, and an optical system, where a light beam is interrupted by a chopper disc. The magnetic system is attractive to a mass producer because magnetic components and coils are familiar, but the optical system is more attractive for conversion of an existing unit because fewer mechanical parts are required.

Both types use the existing centrifugal and vacuum advance systems and, as the amount of energe extracted from the shaft is small in either case, the torsional excitation of the advance mechanism is negligible. Both systems do, however, exhibit a slight hysteresis between acceleration and deceleration as the rotor advances to take up any backlash when the engine slows. This is a small penalty and is normally of little consequence.

structed by the board or swarf, and the manufacturer's recommended lubricant should be restored. If the existing contact pivots on a pillar rivetted to the action plate, the pillar must be removed before the p.c.b. can be installed. Care must be taken to ensure that the small board does not foul the rotor arm or the inside of the distributor cap. When installed, the p.c.b. is connected to the ignition unit by a length of good quality miniature three core stranded cable. The cable should be supported by a small P clip fixed by one of the mounting screws, and by the existing grommet in the distributor body. Remember to leave enough cable loose so that the action plate can revolve.

The circuit can be tested by connecting +12V to the supply lead, and a low power bulb from +12V to the output lead. The lamp should remain on until the light beam is interrupted. Note that the specified device does not emit visible light. If the circuit switches the lamp correctly, connect it to the electronic ignition unit and take the h.t. lead from the coil directly to one spark plug. This will avoid coil breakdown if the rotor arm is not pointing at a segment of the distributor cap. Check that a spark is generated every time the light beam is interrupted and not when it is re-established.

When the circuit has been tested, a chopper disc should be constructed to suit the distributor. The accuracy of this disc affects the overall performance of the system, and the most important parameter is the angle between the leading edge of the blade and the line joining the mainshaft axis with the centre of the rotor arm sector. It is imperative that this angle causes the leading edge of a blade to just obscure the l.e.d., i.e. the point of firing, when the end

of the rotor arm is directly opposite a segment inside the distributor cap, with the vacuum advance at mid-travel. If this condition is not achieved the engine may not run. Another important requirement is that the chopper blades are evenly spaced to avoid scatter. The angle between the blades is found by dividing 360° by the number of cylinders. Although this unit is suitable for any number of cylinders, the greatest improvement will be noticed on engines with six cylinders and above. where multi-lobed cams cause more timing

The disc does not need great strength. and the prototype was cut from tinplate. The centre hole has tabs which are alternately bent up and down to grip the cam as shown in Fig. 5. To construct the disc make a centre punch mark and scribe a straight line through the centre mark. Using a large transparent circular protractor with 0 and 180° marks on the line, mark the position of the blade edges and scribe lines to the centre. If an inductive discharge system is used, the angle between the chopper blades becomes the dwell angle, the angle through which the points remain closed, and must be the same for all cylinders. With a conventional contact breaker the dwell angle has to be short so that the points can open a reasonable distance. Unfortunately, a short dwell angle limits the time available for primary

elsewhere are analysed.

IN OUR NEXT ISSUE

This is a charge-injection capacitance meter, which is

circuit to guard any initial charge on the capacitor to be

measured. Sources of error in the protection circuit and

provided with a well thought out input-protection

John Linsley Hood describes an alternative way of

oscillators. The typical total harmonic distortion of a

simple oscillator of this type is about 0.001%, instead of

0.01% in the conventional configuration. There is also

Constructing a device to help people who live in deep

it and re-transmits it to the viewer's house on the same

broadcasts can't be received normally. Placed on a vantage point nearby, it picks up the tv signal, amplifies

using the Wien network to design low-frequency


Digital capacitance meter

New Wien-bridge oscillator

an optoelectronic amplitude stabilizer.

Active television deflector

valleys or other places where u.h.f. television

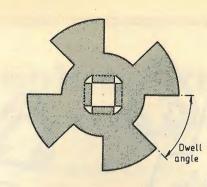

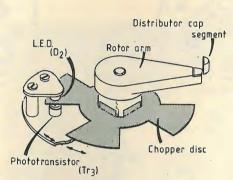


Fig. 5. Typical shape and mounting for the chopper disc. It is imperative that, when the disc just interrupts the light beam, the rotor arm is directly opposite a distributor segment with the vacuum pushrod at mid

current build-up at high revolutions. With this design, the dwell angle can be increased from the manufacturers specification to increase spark energy at high revolutions. If the unit is used with a c.d. ignition system, the angle between the blades is not important because the spark is controlled only by the leading edges of the chopper blades.

Cutting the disc shape is made easier if the tinplate is clamped to a thin sheet of aluminium or plywood. After drilling the centre hole and filing it to shape, cut the disc to the correct diameter, cut the blades to shape and finish with a fine file. Finally, bend the tabs for a good central fit on the cam. The disc is then fixed to the cam with epoxy resin after checking that all the parameters are correct and that the disc revolves freely. When installation is complete, the distributor can be mounted in the engine and adjusted for correct timing with a strobe light.

Although this unit will not produce a dramatic increase in performance from a correctly tuned engine, the firing at high revolutions should be smoother and tickover should be very steady even when cold, which permits sparing use of the choke. However, the main benefit is a maintenance free ignition system. The prototype has now been in use for five years and the distributor cap is only removed to show disbelievers.

BOOKS

Beginner's Guide to Digital Electronics, by Ian R. Sinclair 146pp., paperback.

Only a limited knowledge of electronics is asmuch practical value.

A complete beginner may find the lack of information on application a little worrying: elements are well described, but with little explanation of what their role in a system might be. A microprocessor, for example, is presented as a device whose program is capable of carrying out the action of a truth table as an alternative to a set of gates and registers, with no explanation

The Prestel Business,

104pp., hardback.

This is not a technical approach to Prestel, but an explanation, primarily for business people, of what a viewdata system is, how information is provided and used, some costings and some of the background. This would be a good introduction to the service for those who know little more than the name and who suspect that it could be of assistance in their work. There is no technical description whatever.

Newnes Technical Books, £3.25.

sumed here. The author's intention is to explain the basics of digital technique to those who have no training in electronics, but who may have accumulated information on the active and passive components used in and around integrated circuits. He deals briefly with digital elements from switching devices, through small-scale systems such as counters, to microprocessors, though the chapter on micros, which occupies only fifteen pages, is rather too cursory to be of

of the advantages gained thereby.

by Roger Nicholson and Guy Consterdine. Northwood Books, £4.95.

More on active crossover networks

Using electrostatic loudspeakers with a common bass unit

by D. C. Read, B.Sc. Hons (Elec. Eng.)

Modifications to David Read's 1974 active filter crossover design provide for Quad electrostatic loudspeakers or Isophon tweeters, with appropriate alterations in crossover frequencies.

WIRELESS WORLD APRIL 1981

An article in the November 1974 issue of Wireless World showed how some economies could be achieved in a stereo system using active cross-over networks. One such economy was to have a mixed mono/stereo arrangement using a single bass unit working in that part of the audio band where sounds are non-directional. Sounds in the mid and upper ranges were, in the system suggested, produced by smaller speakers fed via the amplifier/active-filter crossover units as described earlier (Wireless World, December 1973). This economy arrangement worked well, with the added flexibility of the active filters enabling best use to be made of the five conventional cone units - one bass, two

mid-range, two upper-frequency speakers - variously selected for best operation in the chosen ranges.

Given greater financial freedom in the choice of the output units, it seemed an attractive idea to apply such a mixed mono/stereo arrangement to a threespeaker system, using a single cone bass

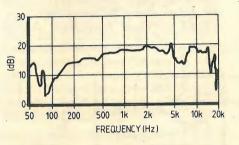


Fig. 1. Basis of modified design is this onaxis speaker response curve.

unit working between a pair of Quad electrostatic radiators. An obvious benefit of band-sharing in this way was that the use of the single bass speaker relieved the electrostatic units of having to produce possibly loud sounds in that part of the audio spectrum where they are at their lowest efficiency and where, especially at


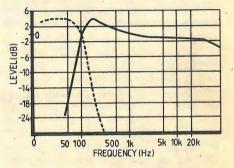


Fig. 2. New crossover frequency of 100Hz is chosen for dual electrostatic + common bass combination.

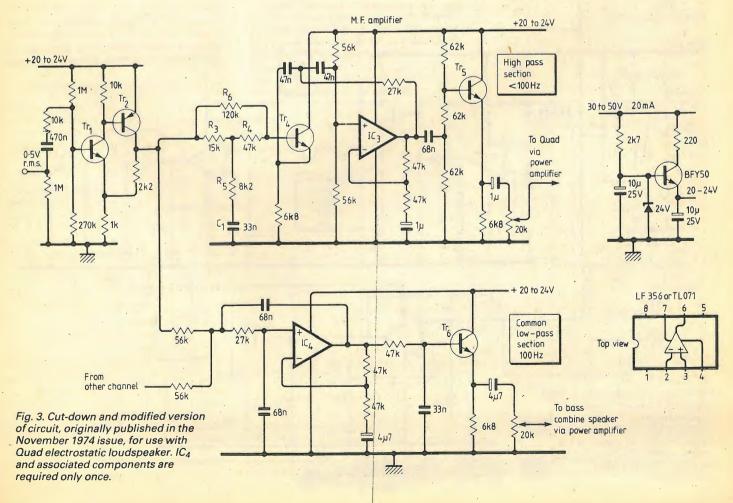

On sale 18 March

frequency.

the very lowest end of the range, they can generate considerable distortion.

I therefore set about making the necessary modifications to the active filter circuit, given as Fig. 2 in the November 1974 article, page 444 or, December 1977, page 575. The basis for the modified arrangement is the on-axis response (sine-wave input) published on page 157 of the 1979 Hi-Fi Choice, repeated here for reference as Fig. 1.

The part of the audio band of particular interest is that between 80 Hz and about 850 Hz. This range of frequencies can be divided into two regions: 80-170 Hz and 170-850 Hz. Considering the lower region first, the Quad electrostatic speaker response curve here shows a fall in output which has an average slope of about 7dB per octave. It has been suggested that the optimum rate of change of loudspeaker response in a crossover region is 18 to 20 dB/octave. I therefore decided that a designed filter slope of about 15 dB/octave would be required so that, over this part of the band, the combined effect of filter and speaker responses would be a fall-off rate

on the high side of optimum, because l.f. energy below 150Hz produces high second and third harmonic distortion in a Quad electrostatic speaker.

The upper part of the response curve section being considered, from 170 Hz up to 850 Hz in Fig. 1, shows a slope in the same sense as before but at a more gentle rate of about 2 dB/octave. This slope does not contribute usefully to the desired effect as in the previous instance and has to be compensated by an opposing active filter characteristic to maintain the loudspeaker output reasonably constant down to the cut-off point of 170 Hz.

These two considerations suggest the general form of the required filter response curve. In addition, I decided to move the stereo/mono change-over point further down the band, to 100 Hz instead of 160 Hz in the original system, which used twin KEF B110 cone units for the mid-range with a single B139 bass speaker. The reason for the change is that in larger living rooms having floor dimensions in excess of six metres square the stereo effect is extended to lower frequencies. As the

electrostatic speakers not only gave good output to this lower point in the band but have a response shape which helps in the crossover arrangement, it seemed reasonable to make the change.

The filter response achieved to satisfy the three requirements detailed above is the full-line curve in Fig. 2. This shows the variation of voltage with frequency of the output labelled m.f. amp in the filter circuit diagram of Fig. 3. This output provides the feed for one Quad electrostatic speaker: an identical circuit serves the other channel. The mono bass speaker - a KEF B139 is suggested but any comparable unit with suitable power-handling capacity would do - is fed via a power amplifier from the channel combining and filter circuit drawn at the bottom of Fig. 3. The response of the output from this circuit is shown as the broken curve in Fig. 2 which intersects with the high-pass filter curve at the new mono/stereo change-over point of 100 Hz.

The active filter itself is a cut-down and modified version of the circuit as originally published in the 1974 article and needs

\$ 22k 30 to 50 V 25 mA LF356 or TL071 High pass 2k7 >2kHz 6n2 BFY50 20-24 100n To KK10/8 47k 10 µ Isophon unit 20k 6k8 via power amplifier +20 to 24V Low pass +20 to _24V 120k i.e. no bas combine To B110 36 k 33k power Low pass+ amplifier high pass i.e. bass combine in use $R_2 \gtrsim 33k$ - 20 to 24V NPN BC 109 2N3704 Common PNP low - pass section BCY72 2N3926 <100 Hz other channels -Fig. 4. Further modification of 1974 design for 0.33 cu.ft boxes and Isophon tweeters. For the 1 cu.ft boxes To B139 housing B110 and Isophon units, short via power amplifier R₃ and omit R₅, R₆ and C₁. A 1µF capacitor should be inserted between Tr_4 emitter and the $20k\Omega$ potentiometer

little further description. Op-amp IC3 provides the high-pass output with the bridged-T section between Tr₂ and Tr₄ giving the 2dB/octave compensating tip-up between 1kHz and 100Hz (with slope controlled by the choice of value for R₆. Op-amp IC₄ provides a mixing point and a suitable low-pass response for feeding the common bass unit.

For people with the room space and the pocket money to suit, an improvement in their arrangement could be obtained by having four such units stacked in pairs. Frames specially designed for this purpose are now available* The resulting increased radiation "frontage" and power-handling capability should gladden the ears of any enthusiast. But you might need to make peace with the neighbours first!

At the other end of the scale, with cost an important factor, the Quad units could be replaced, using the original 0.33 or cu. ft boxes plus the original B110s with a pair of Isophon KK10/8 tweeters, instead of T27s. For those interested in such a variation in the arrangement, the circuit of Fig. 4 gives the alternative component values (bracketed) which would produce a slightly different filter response curve, as shown in Fig. 5, suitable for feeding the Isophon units. The applied volts curve for the KK10/8 and cross-over point to the B110 was adjusted to obtain the flat overall response similar to the curve the 1974 arti-

Listening to the various systems with pink noise (i.e. constant energy per octave) and sweeping through the audio spectrum I have become aware that room acoustics significantly colour the results. Having used an anechoic chamber during the speaker development I realised that a wedge shape filled with sound absorbent material would be available to me by un-

* From Audio-T, West End Lane, London NW6

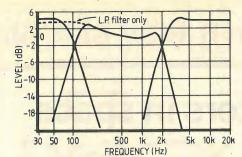


Fig. 5. Applies voltage curve for 0.33 cu.ft box and Isophon tweeters. Broken line shows response with low-pass filter only.

dertaking an attic conversion. The sloping roof to the now-boarded floor provided the wedge behind my electrostatic speakers. This wedge is now filled with sacks of old clothes from a once-too-full wardrobe (all the family have been equally deprived). I have now achieved an excellent listening room where I can pull the ladder up after

The power amplifiers, Fig. 6, use the Hitachi complementary pair 2SK133, 2SJ48 and I obtained a kit from Ambit International the details of which are in their second catalogue. The kit for each power amp, is £16.10 supplied with drilled board, data sheet and component location (heat sink £6.32). After many tests on this amplifier, and accepting the no secondary

Fig. 6. In recommending this power amplifier circuit, David Read points out that power m.o.s.f.e.ts can suffer from h.f. instability between 100 and 1000MHz, which won't be visible on a scope but which will heat the resistor in the RC network across the load (10nF, 10 Ω). He suggests keeping to the Ambit-proven layout, with f.e.ts mounted on the board. (Further details in Ambit catalogue, no. 3 page 61/2, no. 4 page 87/6, available from 200 North Service Road, Brentwood, Essex.) Inductor is 12 turns at 12 gauge wire wound on a 10Ω resistor. Reverse the


breakdown and self-limiting with negative thermal coefficient properties, the only criticism was that the quiescent current fell markedly after a long period at maximum power out and distortion measured a few per cent. I considered adding positive temperature coefficient thermistors at the variable resistor position but as these appear to be highly non-linear devices I felt the best solution was to use large heat sinks on the m.o.s.f.e.ts to minimize the temperature rise. A word of warning - lath and plaster ceiling and loose tiles don't get along with large bass speakers driven by 100W m.o.s.f.e.t amplifiers.

A final point on overload margins. The power amps approaching clipping at 80V pk-pk out, approximately 4V pk-pk in. The worst-case active filter networks is 13V pk-pk clipping in the bandpass or high pass, mid-frequency section, so to obtain similar headroom in each the active filter output pots are at about a third up from the earth end, this being correct for the m.o.s.f.e.t. power amplifiers.

Having listened to Quad pairs and stacked pairs it does seem that the slope between 200Hz and 1kHz should be lessened, so I suggest halving the $120k\Omega$ resistor at Tr4 base. It would seem that as you go down the audio spectrum phase coherence increased and this gives an apparent lift in low end of the m.f. band. This is undoubtedly related to the large radiating area from stacked Quads and the large sound absorbing area of an artic conversion.

If you are aware of sound level peaks in your listening room then some pre-fab-

Continued on page 54

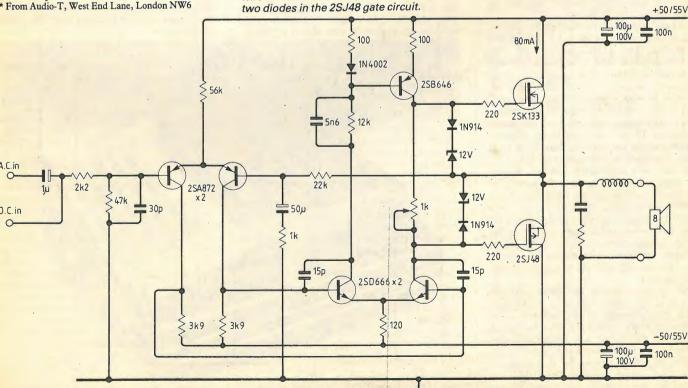

NEWS OF THE MONT

Microcomputers in space

British Aerospace. Space and Communications Division is developing a spacecraft microcomputer module (SMM) as a standard unit suitable for general application in satellite systems. In addition to the hardware, the Division is also developing the necessary computer programs which includes all the basic executive routines needed to control an SMM system.

Eash SMM is a totally self-contained microcomputer. One of the design aspects of particular note is that of flexibility in choice of microprocessor used. The SMM development system at the Space and Communications Division currently comprises a Ferranti F100-L, three Texas Instrument 9900's and a DEC PDP11/34 mini computer, all running with compatible software and common hardware in-

The F100-L which has been selected for use with SMM in the immediate future, is a bipolar microprocessor with low-power dissipation, manufactured by Ferranti as an LSI circuit on a single chip encapsulated in a 40-pin dual-in-line package. Military standard F100-L microprocessors are subjected to additional special testing and screening before being nominated for service in space.

A method of interconnecting up to 64 SMMs has been developed such that not only can their processing capabilities be shared for complex computations, but tasks may be transferred to other units should faults arise in individual devices. Input/output functions are performed by non-intelligent modules which are linked in an SMM system by a two-wire serial data bus designed by the Space and Communications Divi-

An addressable serial bus interface circuit (ASBIC) is used as the standard interface for connecting a module to the bus.

Data and control instructions are transferred as 32-bit long words via the bus at 500 kilobits per second. The ASBIC performs all data synchronisation, module address detection and the serial-to-parallel and parallel-to-serial conversions necessary when transferring information between a module and the bus.

An ASBIC comprises a single 40-pin ceramic dual-in-line package. It is an LSI circuit manufactured by Ferranti using collector diffusion isolation and the uncommitted logic array technology developed by that company. It is TTL compatible, and importantly, operates at very low power levels from a single 5v source, an advance over similar circuits using hybrid and discrete technologies. It contains a 16-bit parallel data highway ideally suited to microprocessor applications and is manufactured to full military specifications. Utilising ASBIC, nonintelligent terminals can be adapted for connection to the data bus with the minimum of additional circuitry.

The configuration of the SMM and the selection of the military version of the Ferranti F100L microprocessor is the outcome of an engineering study carried out over the last 18 months by the Space and Communications Division to assess the operational characteristics required of microprocessors for prolonged service in space, aboard satellites. The F100-L was

it inherently more resistant to radiation damage. with the added merit that it is the only 16-bit

microprocessor wholly designed, developed and manufactured within Europe. Throughout the study, liaison was maintained with the European Space Agency (ESA) to ensure the technical solutions proposed were compatible with data handling requirements for satellites

Before the study began, British Aerospace Dynamics Group had already acquired considerable knowledge of the factors likely to influence computer operations in space as a result of previous privately-funded technical evaluations. The Group is continuing to invest money in the current research and development work, the cost of which is being shared by the Department of Industry as part of the UK Space Technology Programme.

specified by ESA.

The Space and Communications Division will be incorporating SMMs in the next generation of satellite systems they build and have begun evaluating the device with its supporting components to qualify it for use in the space environment. In addition to space, it is envisaged that SMMs will be eminently suited for a wide variety of data handling applications.

China standardizes in Industry

From a previous policy of self-reliance, China has embarked on a comprehensive programme of modernisation including a number of product standards and a building and civil engineering code. Details are included in a report, Exporting to China, prepared by the Standards Association of New Zealand and available from the British Standards Institute's Technical Help to Exporters service.

Chinese standards are divided into three grades - national, ministerial and enterprise and the policy for each grade is explained. Details are given of the types of products covered by the mandatory National Standards. There are two Chinese standards covering labelling requirements for shipped goods and the labels are clearly illustrated. The report includes full addresses of all relevant organisations, corporations and embassies.

As if to underline that such trade is not necessarily one-way, Hitachi have announced the signing of a contract for the establishment of a joint venture company in Fujian Province, China for the production of television sets. Intended for domestic sales and for export, the company expects to be producing 200,000 colour and 180,000 black-and-white tv sets per

Computer in case

Intended for the 'globe trotting' reporter, salesman, engineer, programmer, auditor etc, model 8400 computer is fitted into a briefcase.

Produced by Microdata Computers Ltd. in Hayes, Middlesex, the computer incorporates many features to make it not only portable but also of practical use: it may be connected to a wide range of power supplies' voltages and frequencies and so may be used almost anywhere

in the world; it incorporates a real time clock which can display GMT and local time; it includes acoustic couplers for transmission and reception of programmes or data through the telephone network. There is a full ASCII keyboard, a fold-away dot matrix gas plasma screen with a capacity of 480 characters; there is full text processing capability and the magnetic bubble memory does not lose data when the power



selected because its bipolar technology renders An early prototype of the Microdata model 8400 briefcase computer, now going into production.

Integrated circuits to your own design

Isolated oxide CMOS, or ISO-CMOS, can be used to produce integrated circuit devices of higher speed, lower power consumption, lower propagation delays, higher densities and lower cost per function, according to the new GEC company, Marconi Electronic Devices Ltd which has been set up to combine ISO-CMOS with the established Cellmos computer-aided integrated circuit design service, the combined service to be known as ISO-Cellmos. By the addition of bigger and better computers and improvements in software, the service can now take a logic design, feed it into the computer which can analyse the circuit and can demonstrate the output response to any given input waveform. It can then select the appropriate gates from its own library and place them automatically in relation to each other to produce an optimal layout. The interconnect tracking is also laid out automatically. The layout is then analysed with capacitance measurements and checking for the effects of possible transients. It is also checked against the design rule book.

All this has taken place within seconds of entering the original design into the computer. Two plots are produced; one of the proposed layout with pad positions etc. The other is a diagram of the chip in logic diagram form, allowing the customer to check it against his original circuit. At this stage, changes to the circuit may be made to correct any errors or to

Keyboard research


It has long been known that the 'qwerty' keyboard is not the most efficient way of arranging the letters. In fact it was originally designed to slow down the typist so that the primitive mechanics of early typwriters could cope with the task and not suffer from entanglements. The European Commission is inviting tenders for a unified keyboard layout suitable for the many languages based on the Latin alphabet. The keyboard layout will be used within the Commission and other European or international organisations who need to deal with many languages. Whether the reseach will lead to a major re-design of keyboard layout or just a tidy-up exercise of the comparatively minor differences in the various nationality keyboards remains to

Authors recognise technical writers

The Society of Authors (a professional society representing over 3000 writers) has under consideration a plan to form a Technical Writers' Group within the Society, to cater for the needs of technical and scientific authors. Those who write about technology are themselves much affected by the introduction of new technology in publishing and printing, and by rapid changes occurring in this field of writing.

The formation of a special Group would provide technical writers, in addition to the normal services of the Society, with the benefit of a core of expertise in this expanding area of writing and the opportunity to discuss problems common to technical and scientific writers.

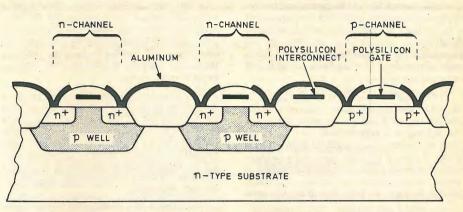These matters were discussed by Stanley Lyons in a special article in The Author recently. Copies of this - and further details about the Society - may be obtained gratis from the Society.



This cross section illustrates the basic principle of ISO-CMOS

add modifications.

Once the layouts are accepted by the customer, they can be simply translated into magnetic tape format for the automatic preparation of production masks. At the same time test tapes are generated for the automatic testing of the finished integrated circuits.

A simpler and even more rapid approach is suitable for those circuits which can be adapted to the ISO-CMOS uncommitted logic array. The Cellmos system can generate a layout for the interconnection pattern which can be added

to ULAs available from stock. As these have fixed connection pad positions a testing faciliy is instantly available

Thus the Cellmos system can design and layout a circuit in seconds - a job that would take a competent design engineer at least three

The new company, Marconi Electronic Devices Ltd, as well as providing the Iso-Cellmos service, has also taken under its wing the microwave, power and hybrid component divisions of the GEC/Marconi group.

Centre to study effects of technology on society

The interaction of electronic systems such as computers and data processing equipment with society at large may well be one of the subjects to be studied by a new research centre now being set up in the UK. Called the Technical Change Centre, it is mainly concerned with the relationship of technology to economic well-being in the UK: it will develop "a major programme of research on the choice, management and acceptability of technical change relevant to the advancement of the national economy" in the words of its official statement. But it will also study changes in society and the economy which act as pressures influencing the course of technical innovation. A related area of research will be "trade-offs" between economic advance and social loss (in such matters as pollution and conservation) and the way technical change could be planned so as to reduce the inevitable disruption it causes in people's social and occupational lives.

The economics bias of the TUC is reflected in the choice of its director, who is an economist, Professor Sir Bruce Williams. Among many other appointments he was economic adviser to the Minister of Technology in 1967. Electronics interests are represented by the organizing committee having as one of its members Philip Hughes, who is managing director of Logica, the well-known software and electronics company. Funding comes from the Leverhulme Trust, which will contribute £1.5m over the first five years, and from the Science Research Council and the Social Science Research Council, each of which will provide £525,000 over the same period. Eventually the Centre is expected to have an annual budget of £750,000, with some of its revenue coming from commissioned

To some extent the TCC resembles the Office of Technology Assessment (OTA) which was established in the USA in 1972 - but by law. It is intended to be of practical help to those technocrats in government, industry and elsewhere who have the task of shaping public policies to respond to technological development and the changing position of the UK in the

Gallium arsenide invades Silicon Valley

The Harris Corporation is moving ahead on its first semiconductor operation in San Franciso's famed 'Silicon Valley' area by approving construction of a \$4 million facility in Milpitas, near San Tosé.

The company is making the investment on behalf of an 80-per-cent-owned new company, Harris Microwave Semiconductor, Inc. The firm was established last June by Harris and a group of local semiconductor executive, specialising in the new field of gallium arsenide technology.

Gallium arsenide is a compound of two elements, gallium and arsenic. As a base material for integrated circuits, it offers significant advantages over silicon in applications requiring very good speed, high frequencies and extreme miniaturisation. Harris will use this technology to produce gallium arsenide transistors. microwave components and integrated circuits to support their communications and information processing equipment now under development.

Flat c.r.t from Sinclair

Clive Sinclair of Sinclair Research Ltd has recently announced the successful development of a flat cathode ray tube which will be incorporated into a miniature t.v. set. The set will include v.h.f./f.m. radio and may be switched to most international t.v. standards, making it of universal use.

The Sinclair tube measures about $4 \times 2 \times \frac{3}{4}$ in. and is three times brighter, requires between one quarter and a tenth of the power and is half the volume of a conventional c.r.t. with the same size screen. It is assembled from just two sheets of glass, a flat front plate and a vacuum-formed backing plate. The phosphor screen is coated on the inside of the backing plate and is viewed through the front face from the same




side that the electrons strike. This gives a brightness of more than double that of a conventional c.r.t. with the same beam energy. In addition to the horizontal and vertical deflection plates there is a third set between the phosphor screen and the front face to bend the electron beam on to the screen.

To correct for distortion the screen height is reduced by as much as half while the width is kept constant. This narrows the angle subtended by the electron beam and the picture height is restored optically by using a horizontal Fresnel lens to give an effective picture size with a 3 in. diagonal. Other distortion is eliminated by careful attention to the modulation applied to the deflection plates.

The tube has been produced in Sinclair's pilot production plant at St Ives, Cambridge but it has just been announced that a full production plant is to be commissioned in Dundee by the Timex Corporation. Timex were awarded the contract by Sinclair because of their expertise in automatic production. It is expected that at the end of the first phase the capacity will exist to produce the tubes at the rate of a million a year.

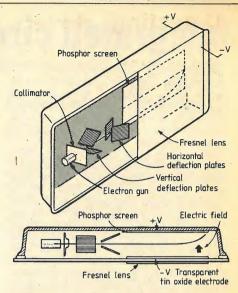The Microvision t.v. set which will incorporate the tube is also to be produced by Timex and should be on the market by mid-1982. Although the exterior design of the set has not been completed, some design models have been produced to show that the set will be about 6×10^{-2}



 4×1 in. or about the size of a paperback book. It will retail for about £50.

Further developments for the tube depend upon the extremely high brightness which may be achieved. This leads to its suitability for use in projection systems. A monitor for the Sinclair personal computer is high on the applications list, as is a colour projection t.v. which would incorporate three of the tubes and the associated electronics in a projector about the size of a shoe box to produce a picture on a wall screen with a 50 in. diagonal.

Electronics bosses disagree on industry's priorities

Opposing views on the future of the British electronics industry were expressed recently by two of its prominent figures, Mr Ernest Harrison, chairman and chief executive of Racal, and Mr Frank Chorley, deputy chairman and managing director of Plessey Electronic Systems. Mr Harrison believes that rationalisation will be necessary in the UK industry to meet foreign competition effectively. In a speech to stockbrokers, industrialists and financial journalists he said: "If we are to survive as a nation in professional electronics, or indeed in any of the electronics industries, we have got to do something about our resources and getting together. We are going to face in the 'eighties the might of Japan and America and these two countries are determined to dominate the world. They spend huge sums on research and development the like of which we cannot imagine. . . . The competition is going to be intense and it cannot be avoided". Referring to the rationalisation that had already taken place - Racal taking over Decca and Thorn taking over EMI - Mr Harrison claimed that "many more people now agree with what I have been saving for a long time".

One exception, however, is Frank Chorley. "I certainly don't agree with Ernie on that," he said, in reply to a question at a press lunch. "It's a good idea to scrap it out, because it makes us all more efficient." Companies in the UK industry were well able to look after themselves. Racal, Marconi and Plessey were all highly successful, though they were perhaps not good in all areas. There was no benefit to be gained by bringing them together.

A further difference of attitude emerged on the two companies' involvement in military electronics. Despite the fact that a large proportion of Racal's business has always been in this field (about 38% recently), and is likely to continue so with the acquisition of Decca, Mr Harrison declared: "We are too much in Defence.

This is much too large a proportion of our total business. What about the many applications for electronics in the old manufacturing industries in the UK? Who's going to do them?" He gave one example of a civil application which was fairly new to Racal — electronic funds transfer. A new company was doing a lot of development in this area and it had a good product but things were moving slowly because "the banks cannot make their minds un".

Mr Chorley's attitude about his own company, however, was that "The Defence industry is very successful in the UK. From time to time Socialist MPs have complained to me that we

ought to make calculators and other such products, but we have got to do what we are good at. We have got to exploit the market that already exists for us. The UK has a significant lead in this field — so why not exploit it?"

One matter on which both men were agreed was that the UK electronics industry should be supported by the government. Referring to the billions of pounds that the present administration is now pouring into steel and motor cars, Mr Harrison commented enviously "Just imagine what you could do in this business if you were given a billion pounds to invest in electronic projects".

Fourth TV channel signal monitoring

The quality of the transmitted signal of the new fourth television network due to go into service in the autumn of 1982 (News, January issue) will be monitored by automatic equipment. Instruments will be provided for the complete network of main stations. Each of these is under the supervision of a station controller which in turn is linked back to a computer at a regional operations centre. The automatic monitoring equipment, based on a Marconi Instruments

insertion signal analyser, operates under software control. All parameters important in the maintenance of picture quality can be monitored and the results compared with limits stored in the equipment. Warnings can then be given and executive action taken if any parame-

ter falls outside its defined limits.

The monitoring equipment is being provided for the IBA by Marconi Instruments under a contract worth over £500,000.

Alternatives for society

Appropriate technology, community communications, alternatives to nuclear energy and self-regulating education are among the alternatives to existing centralized institutions to be discussed in 30 small forums at the First Assembly of the Fourth World, London, July 29-31. According to its convener, John Papworth, "Human survival now depends on the swiftness with which our political, social and economic institutions can be made small enough for them to be manageable and more adequately responsive to human control." The education forum

I be guided by Dr K. L. Smith of the

Electronics Laboratories, University of Kent at Canterbury. Details from Fourth World, 24 Abercorn Place, London NW8 (tel: 01-286 4366).

More news from Sinclair


To be launched at the Microsystems '81 exhibition is a new Sinclair personal computer. It will incorporate a new, British, custom-built master chip, have a 'significantly higher specification' than the successful ZX80 and yet will be marketed at a 'substantially reduced price'. Details are also to be announced of a low cost printer and supporting software libraries.

An electronic indicator which can be laid simply and quickly on a road surface to spot faulty line ends at the arrow'

and quickly on a road surface to spot faulty driving has been developed by engineers and psychologists working in the School of Automotive Studies at the Cranfield Institute of Technology.

Although its most obvious use is to alert police to drivers who are drink-impaired, the Speed and Alignment Indicator can also be used to monitor speed alone. It could play a part in studies of driver behaviour too — a field in which there are many opinions, much speculation, but few certain ways of finding out precisely how drivers drive their cars.

When laid on the road the indicator looks like the rubber tubing used to count passing vehicles. Two tubes are laid parallel to one another across the carriageway and six feet apart. Beyond them is another set of tubes arranged like an arrowhead pointing in the same direction as the traffic flow. Each tube has a transducer which converts the pressure of vehicle wheels passing over them into an electronic signal to a micro-computer by the roadside. The micro converts the signals into the speed of the vehicle and its alignment on the road.

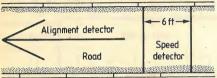

Vehicle speed is computed from the interval in time between the wheels passing over each of the two parallel tubes. Alignment is computed by the driver first of all driving along a straight line laid up the centre of the carriageway. This line ends at the arrow's tip, from which two rubber arms slope away — the shape of an arrowhead. If the driver has aligned the two arms of the arrowhead simultaneously. If one wheel strikes its arm ahead of the other, the

vehicle must be off the centre line.

The micro-computer is both 'Intelligent' and versatile, making a decision in milliseconds on whether a driver has passed or failed each of the two tests set by the operator. He/she can preprogramme the device with the speed limit of the road and can also decide on the margin of error allowed to a driver on the alignment test. British or metric units can be chosen and the indicator will give separate decisions on speed and alignment. The micro's decisions are flashed on a screen in front of the operator as 'pass' or 'fail' together with the figures for speed and the number of inches or centimetres by which the car is veering from the centre line. The decisions are also printed out, and a warning buzzer sounds when the error limits are exceeded. The indicator can be set to record every vehicle passing, or it can print out for failures only - whichever mode the operator chooses.

The equipment is compact and easy to use. It can be carried round in the smallest of cars. The Speed and Alignment Indicator is a prototype only at the moment, but it can be made and marketed easily if there is a demand for it. If police forces were interested in using it, the indicator could be set up on a road with a warning sign telling motorists that they were about to be tested. Drivers would then align with the guide line to the arrowhead and drive along it: if the indicator showed a driver to be

out of alignment he could be stopped further down the road and asked to take a breath test.

At the moment police can stop a motorist and test him if they have 'reason to believe' he might have drunk too much alcohol, but there is no objective test of this and motorists have always opposed random testing.

The indicator could also be used to study driver behaviour by being set up to show, for example, how people take corners, road position, etc. There is no objective, accurate and easy, way of obtaining this information at the moment.

C.b. to become legal with f.m.

Mr William Whitelaw, the Home Secretary, has announced that Citizen's Band, officially still known as Open Channel, radio is likely to become legal in the autumn of 1981. Two wavebands are to be allocated, 27MHz and 930MHz both to be frequency modulated. Amplitude modulation is to remain illegal and f.m. ooperators will require a licence. No details are available as to the maximum permissible signal strength or the number of channels but a draft specification will be issued to potential manufacturers.

The European Communities Commission is attempting to produce a harmonised set of technical regulations covering c.b. sets and are studying French proposals for a 27MHz service with a maximum strength of two watts and fewer than 22 channels.

Wireless World will be publishing a series of constructional articles for those wishing to build a c.b. set.

Approval and dis-approval for telephones

Although, under the policies of the present Government, British Telecom is to lose its monopoly of providing telephones and other attachments for use on telephone lines, it is very much concerned that there will not be a free-for-all. At present the only equipment permitted is that certified by British Telecom as suitable for use as an attachment. This ensures that the equipment is technically compatible with the British

network; it presents a minimal risk of injuring people or damaging the system; it does not interfere with other customers' use of the network; and it is correctly connected, to help in diagnosing faults. Even when British Telecom lose the monopoly, they will still be the sole supplier of the first telephone connected to the exchange line entering a person's home or office, under new arrangements proposed by the

Government. Certification of the suitability of attachments will continue but will be no longer carried out by British Telecom but by an independent Government approved body which will establish and publish standards for privately supplied attachments and then test and certify that the attachments conform to the standards.

British Telecom warns that most telephone equipment now on sale in shops and department stores is not specially designed or modified for use on the British network, despite various claims that it 'meets British Post Office standards'. It is nearly all made and designed for use abroad. If connected to the British network, it may not work properly. Phones designed for overseas use are frequently insufficiently sensitive for satisfactory operation on all lines in the U.K. Mains-powered equipment can be electrically unsafe. Not only do the owners of such equipment suffer, but also the callers whose calls are made inneffective if the apparatus does not respond correctly, or gives poor quality reception. British Telecom are threatening, regretfully, to disconnect the telephone lines of customers who persist in using uncertified equipment.

To counter the sales of such lillicit phones, British Telecom are continuing their programme of offering a wider range of telephones to be supplied direct to the customer. Two additions to the range are illustrated. On the left is Dawn. Intended for the boudoir, it has a low, sculptured profile on a circular base and is available in pale yellow, avocado green and white. The one-piece Eiger telephone, with a pressbutton keypad, includes a memory to store the last number called. It can call again automatically, if required to. The colours are more business-like; red, stone or two-tone brown.



CIRCUIT IDEAS

Divide by (2n-1)

Fig. 1(a) shows a divide-by-(2n-1) circuit which generates an equal mark-to-space ratio output if a divide-by-2 circuit is used in the final stage as shown in Fig. 1(b). With this arrangement, a divide-by- $(n-\frac{1}{2})$ output is available from the divide-by-n counter, but not with an equal mark-to-space ratio. Fig. 2 shows a divideby-3 circuit, based on Fig. 1, where the divide-by-4 counter is clocked by a positive edge of the input waveform and then by a negative edge. During one complete output cycle the divide-by-4 counter receives four clocking pulses for three cycles of the input waveform. A divide-by- $(n-\frac{1}{2})$, i.e. divide-by- $1\frac{1}{2}$, output is avail-

able from Q_A.

With the basic circuit of Fig. 1(a) it is easy to build other odd value counters by inserting the desired divide-by-2n circuit. Also, by combining divide-by-(2n-1) and divide-by-2n circuits, a counter can be designed to divide by any value of (2n-1). Some examples are shown in Fig. 3. Note that inputs and outputs between the various exclusive-OR gates must be separated by a counter.

A. J. Ewins Harrow Middx


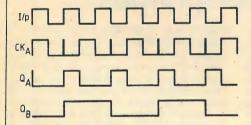


Fig 2 (b) Waveforms of divide-by-3 circuit

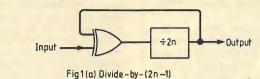

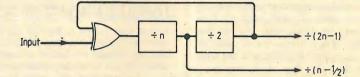


Fig1(b) Divide - by -(2n-1) with ÷ (n-1/2) output



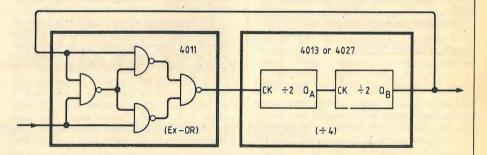


Fig 2 (a) divide-by-3 circuit

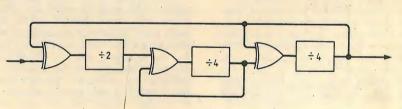


Divide-by-17

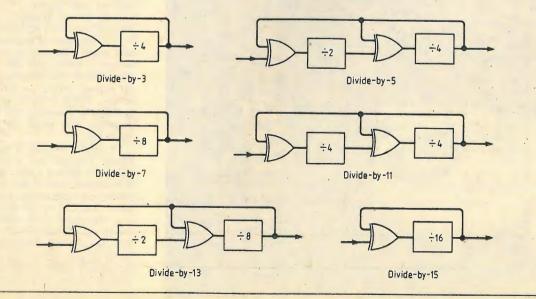

Pre-amp with multisection tone control

The input stage of this preamp, which originates from a studio mixer, will handle signal levels from 500µV to 5V r.m.s. For optimum performance the preset control should feed 5mV to Tr2 which, with A1, amplifies the signal to 3V r.m.s. The filters around gyrators A₃ to A₇ provide low-impedance paths to ground for five frequency bands, and attenuation or gain for these bands is achieved by controlling the lowimpedance paths towards the voltage dividers around A2. Balancing the filter potentiometers gives unity gain at A2 because the input and feedback voltage-dividing networks cancel each other. The open-loop gain of the op-amps determines the maximum number of gyrators that can be used. At 15kHz the paralleled gyrator series resistors, 180Ω and 330Ω , which are boot strapped by the open-loop gain, should still be greater than the divider source impedances, 2k7, and prevent unexpected dips or peaks at high frequencies.
H. Riegstra

H. Riegstra Amsterdam Holland

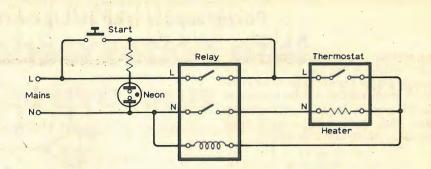


One-shot control of immersion heaters

A conventional immersion heater requires two operations, switching on and later switching off. Although simple, the second step is inconvenient and costly if forgotten. This simple circuit is easy to install and obviates the need to manually switch off the heater. A relay forms a one-shot monostable which is thermally rather than electrically controlled. A trigger is provided by the start button which energizes the relay coil, and the heater is powered until the thermostat cuts out and de-ener-

gizes the coil. Water temperature, and therefore the duration of the on period, can be adjusted via the thermostat setting. Apart from the relay connections, only one extra low-current wire is required between the start button and the thermostat.

This circuit can also be used to isolate equipment from the mains after a power failure.

S. Ho and D. Wibberley Manchester

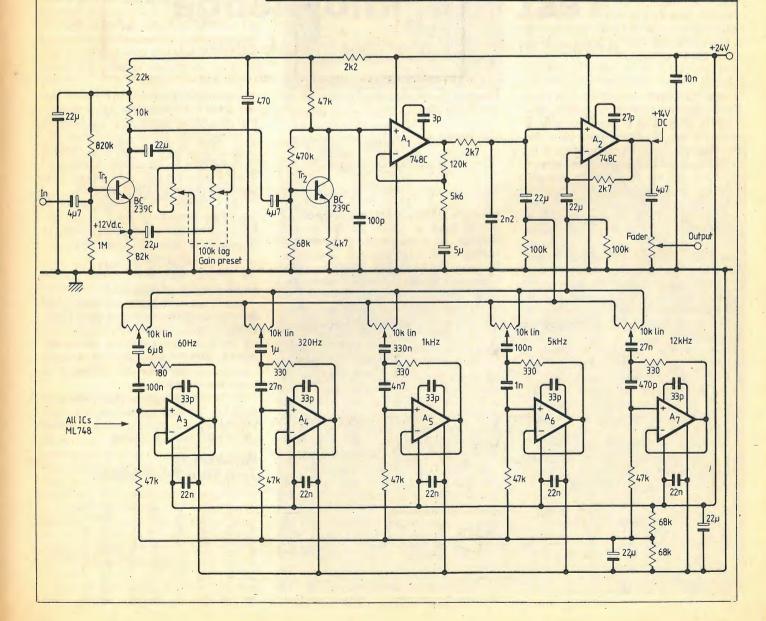


Power supply with stable current limit

One problem with power supply current limits, which use the $V_{\rm BE}$ drop of a transistor, is their drift with temperature variation. A simple solution is to use a programmable Zener diode for current sensing, which offers less than 50 p.p.m./°C variation in $V_{\rm ref}$. In the circuit shown

$$I_{\text{limit}} = \frac{V_{\text{ref}} - aV_{\text{ref}}}{R_{\text{Sc}}}$$

When the voltage at the R terminal of TL431 switches it on, base drive for the output transistors is removed and the output current is limited. However, if the output terminals are shorted, the TL431 is turned on but the voltage across it is 2.5V. Therefore, to take the output voltage to zero, V_z is required which can be any low voltage Zener diode above 2V.

M. S. Suresh Bangalore India

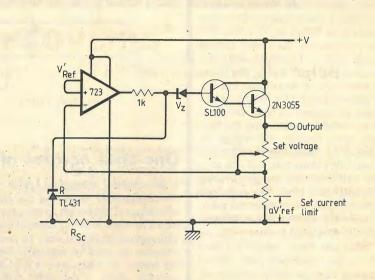

"Test your knowledge"


Answers to the December issue multiple-choice quiz

None of the entries received for Test Your Knowledge was completely correct, and the best entries had at least three of the answers wrong. That was one result of the quiz compiled by R. W. Ellingham and B. L. Hart and published in last December's issue. The stiff test was based on 40 questions, each with multiple answers, given to electronics students at the North East London Polytechnic. We offered prizes of Circuit Designs 3 or a subscription to Wireless World for ten correct entries opened after 5 January for UK readers and 2 March for overseas.

The answers provided by the authors are given in the panel. As almost all entrants gave the incorrect answers to questions 3, 24 and 34 (no-one got this last right), here are their solutions.

Question 3. The assertion is not true. A bipolar junction transistor comprises two p-n junctions both of which are forward biased when the device is saturated. By suitable biasing it is possible to arrange for the two junction drops to be equal in magnitude.

The reason is a true statement. Operation of the b.j.t. depends on the existence of both electrons and holes. Therefore (d) is the correct answer. Most thought (b):

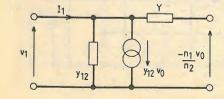

Question 24. See diagram. For neutralization $I_1 = 0$ when $v_1 = 0$.

$$y_{12}v_0 = -\frac{n_1}{n_2}v_0Y$$

$$Y = -\frac{n_2}{n_1} \cdot y_{12}$$

$$= -2(-j0.2) = j0.4\text{mS} \quad (d)$$

Question 34. Upper trip level corresponds to the level at which the comparator switches for a positive-going input. Assuming $V_0 = -12V$, the p.d. across the $8k\Omega$ resistor keeps the + input of the comparator below +4V, hence the output stays at -12V, until i_g increases to $i_g = (+4-(-8))V/8k\Omega$ which is 1.5mA, so (b) is correct, but everyone gave (c).

About half the entrants gave incorrect choices for questions 8, 9, 18, 36 and 37. In Q8, I_e is $((I_c/I_h)+1)I_h = 110$ mA and in Q9 zener current varies between 1mA $(I_b = 9\text{mA})$ and 10mA so the mean dissipation is 5V×5.5mA. In Q18, the solution is found by equating the increase and decrease in charge first across the input C, to give v = -E/3 then across the output C to give $E_0 = Mv/3$. Those who got Q36 wrong gave (e) as the answer but the correct frequency is 50kHz. The period is obtained from $2\times (C\Delta V/I)$, due to current mirror action, giving 50kHz. Most entrants realised that the 150kHz printed for (d) was intended to read 50kHz. The minimum frequency, Q37, is one tenth of

Other answers were less frequently wrong, but more consistently so. In the answers to question 11, emitter current

was invariably given where collector current wasn't. For question 23, it appears that the transformation ratio was taken to be the square of Xc_1/Xc_2 rather than $(Xc_1 + Xc_2)/Xc_2$. As the amplifier of question 27 is matched to the source, actual noise power is twice the ideal noise power. That makes the noise figure 3dB, not 0dB.

The Thévenin equivalent circuit is needed for question 33. For V_0 to be high, the + input at the comparator must be more positive than -1V. This means

$$\frac{R_2((10/3)+2)}{R_2+(R_1/3)} > 1,$$

from which the answer follows.

Only a few got question 22 wrong, but one that did, Jeffrey Borish of Santa Clara, California, wrote to correct his answer saying the question could be a "deliciously wicked trick," depending on whether c.m.r.r. was taken for the differential or single-ended output.

At the time of going to press the cut-off date for overseas readers hadn't been reached but prizes for the best UK entries have already been despatched.

Answers to Test Your Knowledge

1	С	11	D	21	В	31	В -
2	В	12	.E	22 .	В	32	D
3	D	13	Α.	23	В	33	В
4	В	14	В	24	D	34	В
5	В	15	D	25	C	35	В
6	C	16	E	26	В	36	D(50kHz
7 .	C	17	D	27	D	37	A
8	C	18	В	28	A	38	C
9	C	19	E	29	В	39	C
10	E	20	Δ	30	C	40	D

Radio observation of the 'active' sun

Solar effects on propagation recorded on home-made apparatus

by R. A. Ham

Since 1968 the author has used a simple radio telescope constantly to monitor the effects of solar activity on radio frequencies. This article is a brief history of sunspotters followed by a chronicle of solar events and outlines of the equipment used to make the recordings.

Until the advent of radio it was not realized that the sun, and indeed other stars, emitted radio waves. However, suspicions were aroused very early in radio's history as Sir Oliver Lodge tried to detect radio waves from the sun using a receiver with a coherer detector, and the editor of the Scientific American called upon radio enthusiasts to listen carefully during the total eclipse of the sun on 24 January 1925 and report any strange happenings to radio signals.

Short-wave bands

Throughout the pioneering days of the short-wave bands for broadcasting both amateurs and professionals were trying to explain why the propagation of radio signals varied between day and night and was often subject to echoing, fading and sudden blackouts.

Scientists such as Oliver Heaviside, Arthur Kennelly and Professor (later Sir) Edward Appleton had shown how the existence and structure of the ionosphere reflected short-wave signals around the world. But as more evidence was gathered by astronomers, physicists and radio engineers it was soon realized that streams of particles from a solar event, Fig. 1, could disrupt the prevailing state of the ionosphere and consequently upset the normal paths of terrestrial radio signals.

Solar radio astronomy

Signs of radio being used as an astronomer's tool date back at least to 1935 when Karl Jansky first detected radio waves coming from the suns in the Milky Way. Later in the same year Denis Heightman heard a hissing noise in the 10m band which was later confirmed as being caused by radio waves coming from a solar event. Between 1936 and 1939 this same noise was reported by no less than 24 amateurs using the same frequency, and by Miss Barbara Dunn while using a frequency of 56MHz.

Early in 1942 British wartime operators using similar frequencies recorded an



Fig. 1. Solar prominence photographed from the 'spectroheliograph' by Cmdr Hatfield on 10 February 1976.

extraordinarily high level of noise which was also found to be the result of a large sunspot group and soon after the war research into solar radio waves and their effects on radio was stepped up.

Simple radio telescope

Having heard the effects of solar noise, the author decided to build a simple radio telescope*, to find out more about the 'active' sun and its effects on terrestrial radio communications. The radio waves from the sun at 143MHz are collected by four 4-element yagis mounted on a wire mesh reflector, Fig. 2, which has a head amplifier mounted on its frame. The amplified signal passes along a coaxial cable to a 2m converter, where the observational frequency, having being changed to 27MHz, is tuned on an FRG-7 communications receiver which in turn drives a

* The author's radio telescope was featured in 'Tomorrow's World' by the BBC and in a scientific film made by Yorkshire Television and networked by the IBA.

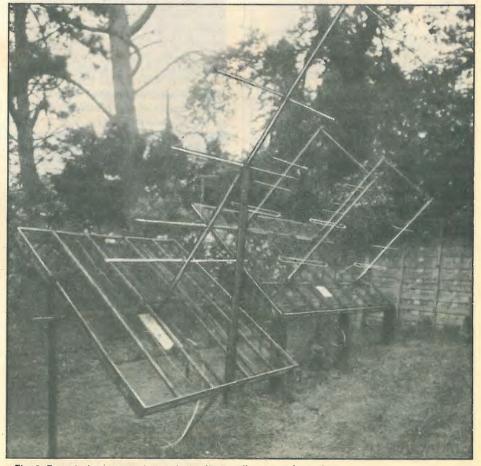


Fig. 2. Four 4-element yagis used to collect radio waves from the sun.

Fig. 3. Chart recording of a typical short duration solar flare.

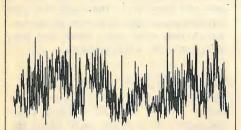


Fig. 4. A ten minute recording of a solar noise storm which occurred on 30 October 1973 at 136MHz.

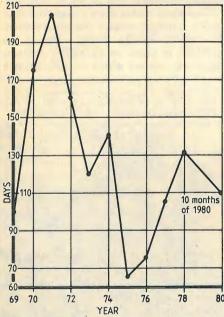


Fig. 5. Solar activity as recorded by the author originally at 136MHz and later at 143MH (see text). Note that the peak in '71, the low in '75/'76 and the rise thereafter correspond with the recognized cycles.

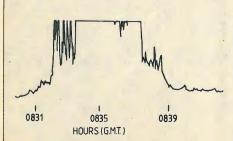


Fig. 6. One of the more memorable solar bursts from 3 July 1974 in which the recorder pen was sent off the scale.

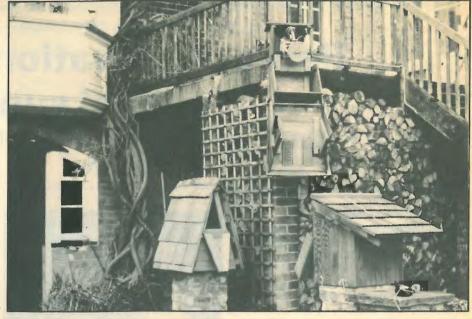


Fig. 7. The spectrohelioscope. A mirror (top centre) follows the sun and reflects light towards the second unit (bottom right) which in turn passes through the garden room door off to the left via the lens housing (bottom left).

d.c. amplifier and pen recorder.

This instrument, although originally using a slightly different frequency and receiver, was brought into operation in 1968 and has operated for three hours daily ever since. Using a chart recording speed of 7cm/h, short-lived solar bursts are easily identifiable.

Sunspots - briefly

When a long-life sunspot, or group of sunspots, appears on the east-limb of the sun it can be visible for about 13 days before leaving on the western limb. The sunspots themselves are stationary but, because the sun revolves once every 27 days, they appear to move across the surface.

Constant observations have shown that when sunspots are present there are two main features of the associated solar r.f. noise, the individual burst, Fig. 3, which may last for several minutes, and the continuous noise storm which may last for days, Fig. 4. These radio waves are often generated by solar flares or prominences, Fig. 1, but the nuclear waste ejected by the event can take up to 50 hours before it reaches the earth and causes some form of atmospheric disturbance.

Sunspot cycle No. 20

The author's observations began on the rising side of sunspot cycle No. 20 (1965 to 1976 approx.) in June 1968. After a quiet start, a large burst of activity from a group of sunspots on 13 August and a noise storm from the 18th to 21st were recorded. Another period of quiet ended on 17 October with a 5-minute burst from a period of solar activity which lasted until 4 November. The main feature of this event was a noise storm which began on the 29th and ended on 1 November: shortly after its termination an aurora borealis manifested and deflected v.h.f. signals from amateur radio stations in northern England, Northern Ireland and Scotland towards the south of England, proving to the author the connection between the 'active' sun and terrestrial radio disturbance.

The number of days on which solar noise was recorded increased towards a peak in 1971 and then decreased until the new cycle began, Fig. 5. One of the largest noise storms recorded began on 11 November 1970 and raged until the 22nd, during which time the solar-noise level was apparently constant as the output from the fixed azimuth aerial increased daily as a large sunspot group approached central meridian and gradually decreased thereafter.

This was an example of following the rotation of the sun using radio. The telescope's recording pen was at full scale throughout the observations on the 15th and 16th, which was not surprising because the Daily Telegraph newspaper reported on 17 November that there were four separate sunspot groups at the time and the biggest passed through the central meridian on the 16th. This solar event upset h.f. communications and one unusual feature was the high atmospheric noise level that was heard on the h.f. bands after sunset. Another major storm, associated with a large sunspot group between 3 and 13 March 1972 was the subject of a special report to the British Astronomical Association (BAAJ June '72) with a special emphasis on the flares which were recorded by radio on the 5th.

Of the many individual bursts recorded during the past decade, a large solar burst at around 08.35hr on 3 July 1974 was the most memorable. The telescope had been recording the radio waves from a severe noise storm on the two previous days so the author decided to check the rising sun by using a 2m beam and some auxiliary equipment. Suddenly the noise increased at 136MHz and other receivers in use at the time emitted noise at 70.5 and 30MHz.

WIRELESS WORLD APRIL 1981

At this point a communications receiver and a long-wire aerial were used to follow the noise and for six minutes it overpowered all terrestrial signals down to 8MHz before it slowly faded away back to 136MHz, Fig.6. Solar noise was also heard at 28.5 and 70MHz on 3, 6 and 28 July.

At 07.45hr on 22 August 1976 strong bursts of solar noise were heard at 28MHz and later at 11.58hr while the author was using a low-band mobile radiotelephone another big burst occurred and blotted out the channel for 16 minutes. This burst was also recorded by the author's radio-telescope at 136MHz.

The sun often produces the unexpected and having been quiet, apart from two tiny bursts, for 18 days it suddenly emitted a 28 minute burst which covered 50MHz of the v.h.f. spectrum at 13.16hr on 29 July 1973. Another notable burst began on 1 August at 11.46hr and for eight minutes the solar noise was strong enough to

overpower static from a local thunder-

Auroral observations

Briefly, an aurora manifests when a stream of particles from the sun collides with the gases of the earth's polar atmosphere causing a temporary ionisation which affects terrestrial radio signals. An auroral reflected signal can be identified by the following characteristics: an s.s.b. transmission sounds like a ghostly whisper, a c.w. signal becomes a low-pitched rasp and the main image on a television screen is accompanied by many distorted images, all frequently changing as the aurora ebbs and flows. Throughout the past decade Mr C. Newton, Auroral Co-ordinator for the RSGB, has organized a large network of radio amateurs who monitor the effects of signals bouncing off aurora.

Following a period of large solar bursts an aurora manifested in two phases on 8

March 1970. During the first phase, 16.00 to 16.47hr, auroral signals were heard in southern England from amateur stations located in parts of Ireland, Scotland, Wales and Holland in the 2m band. The second phase, 18.15hr to 23.30hr, was more intense and auroral signals from many east-European broadcast stations operating between 65 and 73 MHz were received in addition to the amateur stations heard during the first phase.

A large sunspot group was responsible for the noise storm which began on 2 August 1972 and became very intense on the 3rd. At sunrise on the 4th the solar noise was heard at several radio frequencies and by mid-day it had reached large proportions. It was not surprising that from midnight on the 4th until about 03.00hr on the 5th a spectacular aurora manifested which not only had an umbrella effect on v.h.f. radio signals, but its full glory was visible from southern-Eng-



Fig. 8. The yagi used in conjunction with the spectrohelioscope.



Fig. 9. Sunspots photographed at 14.50hr on 11 February 1978.



Fig 10. Clouds of gas from an active region of the sun.



Fig. 11. Solar activity near sunspots recorded on 3 May 1978.



Fig. 12. Sunspots and solar activity from 25 May 1978.

Recorded noise storms of 1971

7 to 14 and 19 to 23 Jan. 28 Jan. to 3 Feb. 10 to 17 Apr. 9 to 12 May. 14 to 19 and 24 to 28 Jul. 18 to 26 Aug. 16 to 19 Nov. 4 to 9 Dec.

land. Although less intense, the prevailing solar storm continued through the 5th, 6th and 7th. At 15.00hr on the 5th another aurora manifested but this time it could only be 'seen' by radio. Without radio both these events may have gone by unrecorded, the first could have been screened by cloudy skies and the second was obscured by daylight.

A special watch was kept on the 4m band during the solar activity from 28 March to 2 April 1973. At 16.00hr on the 1st observers in southern England were rewarded with auroral reflected signals from the Polish broadcast station at Gdansk, 70.31 MHz, and during the following hour auroral signals from 14 European broadcast stations were heard between 49 and 71 MHz.

The auroral events on 15 September and 13 October 1974 were expected because of the prevailing solar activity around these two dates. The September event lasted most of the afternoon and evening and although the October aurora was much shorter, 14.00hr to 17.15hr, the first warning came earlier as signals from the OSCAR-6 satellite crossing the north-pole were affected by the aurora.

At 08.41hr on 23 March 1976 a large solar burst was also recorded by the radiotelescope which Cmdr Henry Hatfield uses at his home in Kent in conjunction with a spectrohelioscope. At noon, Cmdr Hatfield noted that one of the legs of an arched prominence on the east-limb of the sun was very bright, indicating the presence of a new sunspot. This spot later proved to be very active because from 24 March to 1 April a solar noise storm was recorded and auroral propagation was reported during the afternoons of 26 March, 1 and 3 April.

The spectrohelioscope

By the beginning of sunspot cycle 21 Cmdr Hatfield, with his spectrohelioscope†, had introduced another tool for the study of solar activity. This instrument consists of two wave collectors, one a mirror, Fig. 7, and the other a 4-element yagi aerial, Fig. 8, which both follow the path of the sun. The sunlight is passed through a series of mirrors and lenses to an observatory in the garden room below the house. At the same time radio waves collected by the yagi are fed to a radio telescope in the same room.

The output stage of the radio telescope amplifier is used to drive an alarm bell when solar bursts are detected.

Sunspot cycle No. 21

It is understood that cycle 21 began in 1976 when sunspots of the new cycle were seen along the tail enders of cycle 20. From the author's observation cycle 21 got off to a slow start because solar radio noise was only recorded on 47 days out of 304 between 1 November 1976 and 31 August 1977. A marked increase in the daily rate of noise began in September 1977 and was still high at the end of July 1978. Out of

the 212 days from 1 January to 31 July solar noise was recorded on 108 days compared with 34 for the same period in 1977, 35 days in 1976, 34 days in 1975 and around 124 days for the same period in the peak year, 1971. From present records 1978 appears to be the peak year, Fig. 5, of cycle 21 therefore it is worth taking a more detailed look at some of the special events which took place.

On 11 February 1978 the first clear sky for several days enabled Cmdr Hatfield to use his spectrohelioscope and in view of the high level of radio noise which had been coming from the sun on previous days he was not surprised to see some large sunspots. At 14.25hr he watched an explosion take place near the upper sunspot in Fig. 9 and soon after recorded a massive six minute long burst of radio noise at 136MHz. On 6 March at 12.31hr Cmdr Hatfield managed to photograph the solar activity, Fig. 10, responsible for the noise storm which was in progress using the spectrohelioscope.

Around 12.00hr on 9 April a burst of radio noise lasting six minutes was heard sweeping across the spectrum from 1.8 on 144MHz and during the severe noise storm from the 14th to the 17th, solar bursts were frequently heard at 28.5 and 136MHz. The sun was relatively quiet from the 19th to 27th when suddenly at 13.29hr on the 28th an enormous burst of noise lasting 32 minutes occurred which almost instantaneously blacked out the h.f. bands for a couple of hours. Some 50 hours later during the afternoon of the 30th an aurora took place which, with the help of another noise storm on 1 May, rolled around until the early hours of the 4th, Fig. 11. On 25 May Cmdr Hatfield again photographed solar activity around a group of sunspots, Fig. 12, which was causing a radio noise storm and it is possible that these spots were responsible for the solar flare at 10.45hr on 31 May and the sudden ionospheric disturbance that went with it.

Records show that aurora and/or inonospheric disturbance occurred during solar noise storms which manifested on six days in September, 10 in October, eight in December 1977, seven in January, 19 in February, six in March, five in April, six in May, five in June, six in July 1978, two in April, five in August 1979 and nine in April 1980. After 12 years of consistent observation the author has come to the conclusion that the 'active' sun is very unpredictable.

Transient intermodulation distortion

We are sorry that the tutorial article on transient intermodulation distortion intended for this issue (see note in March issue p. 1) has had to be postponed. We hope to be able to go ahead with it later this year.

Literature received

Mallory alkaline and mercury batteries, and Multiplex NiCad rechargeable types are described in a leaflet from Intel Electronic Components Ltd, Henlow Trading Estate, Henlow, Beds. WW401

Brochure on Controlox, a multi-plane, plugboard programming system can be obtained from Oxley Developments Company Ltd, Priory Park, Ulverston, Cumbria LA12 9QG. Controlox is individually designed to undertake multi-programme circuit switching or sequencing.

WW402

Data recorders SR-30 and SR-50 by TEAC are sold and serviced in the UK by International Recorders Ltd, 92 High Street, Berkhamsted, Herts. HP4 2BL, who can provide a brochure on these 7- and 14-channel instruments.

WW403

Toroidal transformers in the OT series are based on stock core sizes to reduce manufacturing time and reduce costs. These custom-built units are described in a leaflet by Avel-Lindberg Ltd, South Ockenden, Essex RM15 5TD.

WW404

The use of the input l.e.ds of an optical isolator to protect the inputs of an operational amplifier is described in a design note from Norbain Electro-Optics Ltd, Norbain House, Arkwright Road, Reading, Berks. RG2 0LT. WW405

Ancom's range of temperature measuring sensors and assemblies are illustrated and characterized in a leaflet, which can be obtained from Ancom Ltd, Devonshire Street, Cheltenham GL50 3LT.

WW406

Unilab, makers of science teaching equipment, produce a set of booklets on the use of their equipment which can also be used in their own right as experimenter's guides. A variety of subjects in physics is covered; microwaves, microelectronics, geophysics, for example, the booklets costing, on the average, around £1.50. A list of 'Notes for Use' can be had from Unilab Ltd, Clarendon Road, Blackburn BB1 9TA.

WW407

More on active cross-over networks

continued from page 43

ricated absorber boxes may provide an improvement. These involve membranes of bituminous roofing felt with mineral wool in hardboard panels 15 cm deep, the sound entering through perforated fronts with 4 mm holes on a 4 cm grid, and approximately 1 m square for the overall panel. The panels, of which several could be needed, are normally mounted on battens attached to the wall and ceiling. This is however a specialized subject involving reverberation time measurements and is a separate topic, discussed for example in BBC engineering division report RD1958/28, available in most university libraries or from the BBC for £1.50.

LETTERS TO THE EDITOR

ARTIFICIAL INTELLIGENCE

In your January issue Malcolm Peltu presents a spirited and cogent defence of artificial intelligence as an important area of study. His already-strong case can be strengthened even further by the observation that a great deal of what is now presented as computer science has its origins in work carried out under the banner of artificial intelligence.

The contribution of AI to computer science is perhaps most readily illustrated by reference to early work. The programming language LISP was devised by McCarthy and his group to aid their work in AI, and this has had a profound influence on computer science. The value of recursion in programming was clearly shown by McCarthy's work as well as by that of Newell, Shaw and Simon on their General Problem Solver. The LISP language is also a paradigm for all the other languages (including PASCAL and ALGOL 68) which allow the construction of trees and other special data structures. Chomsky's pioneering work on the formal representation of syntax was undoubtedly stimulated by the attempts to make computer programs which would manipulate natural language, whether for mechanical translation or

question-answering systems.

In more recent times, interest in distributed array processors has stemmed, at least in part, from the development of pattern recognition techniques and their potential application to specific tasks such as the automatic analysis of bubble-chamber photographs. The special programming languages developed at MIT and referred to as "LISP extensions" certainly embody features which will find their way into future data-base schemes with applications in science and commerce.

I am surprised that there now seems to be a tendency for computer scientists to dissociate themselves from AI. This is surely short-sighted in view of the fact that part of today's AI becomes tomorrow's computer science.

A. M. Andrew
Department of Cybernetics
University of Reading

MULTIPLEX KEYING FOR ORGANS

With reference to the article "Multiplex keying system for organs" by A. W. Critchley in the January and February issues, may I draw your attention to the fact that this company has marketed a multiplexing system for pipe organs for nearly four years.

The system is applicable to organs of any size, transmitting all the organ facilities over a single coaxial pair between console and organ. The system includes the necessary correlation between stops, keyboards and pipes of all ranks at any pitch and between keyboards and couplers at any pitch, thus avoiding the need for multicontact relays and playing keys or the equivalent multiple gates. The customers' requirements are programmed into r.o.m., which controls the standardised modules. A solid-state piston capture system is also available.

We also have a solid-state recording system

which records some ten minutes or more of unrestricted organ playing in 32Kbytes of r.a.m. — a full performance of the well-known Widor Toccata uses just over the capacity. Tape back-up allows permanent retention of an unlimited library, with a C60 cassette holding several hours' playing time.

The transmission system has been installed on many organs, large and small, throughout this country and has been exported to the USA and South Africa.

L. W. Ellen
Christie Music Transmission Systems Ltd
Colchester
Essex

THE DEATH OF ELECTRIC CURRENT

My thanks to Ivor Catt for giving me a good laugh at myself for nearly being duped. I read his article "The death of electric current" (December 1980 issue) carefully, and then came to the analogies. Memorable things analogies (witness that damned mutual impedance somewhere in the hot water system), but so dangerous.

The theory C analogy succeeded in giving me a vivid picture of Catt's travelling wave packets going out into the world along what I used to think were insulators, but which I now see are the very opposite. But just a minute, isn't that the philosophical point from which I started: something travelling along the easiest path? It's just back to the wave-particle duality. They're in different places, that's all. I honestly don't know which to call correct and I should like to hear if Catt will swear that nothing that exists is a particle. The trouble with theoreticians is that they can begin to speak as if their self-consistent mathematics were the fact. OK Catt, your maths may be right, and I don't doubt that it is more helpful in your field of practical endeavour, but for me the AVO meter theory of electrical current has more deductive and predictive power. My money goes on Sprague, but when I need you, Catt, I'll gladly acknowledge it. In the meantime please don't put me down as a fool because I tend to live my life close to one side of the duality only. (I never got a shock from an insulator yet.)

The reference to the phlogiston theory was a red herring; *that* was proved by experiment to be untenable.

J. H. J. Dawson Amsterdam Netherlands

The author replies:

The duality (Theories N and H) inherent in classical electromagnetism is not the same thing as wave-particle duality. (See for instance D. A. Bell, Wireless World Sept. 1980, page 50, first para.) As to "They're in different places, that's all," my reply is that the location of a thing is one of its most important characteristics. As to "... nothing that exists is a particle," it depends what you mean by 'particle'. I have no sympathy for the billiard ball idea, and no sympathy for the notion of wave-particle duality. The idea of wave-particle duality could probably only have been concocted by people who did not know Heaviside's concept of a slab of energy current, now called the Heaviside signal

(see Wireless World, July 1979). In these particular matters my view coincides with Einstein's;

".... We all of us have some idea of what the basic axioms in physics will turn out to be. The quantum or the particle will surely not be amongst them; the field, in Faraday's and Maxwell's sense, could possibly be, but it is not certain."

"Quantum Mechanics and Reality. In what follows I shall explain briefly and in an elementary way why I consider the methods of quantum mechanics fundamentally unsatisfactory." (Max Born, "The Born-Einstein letters", pub. Macmillan 1971, pp. 164, 168.)

The most prominent feature of the maths of "OK Catt" is its virtual non-existence. E-m theory was buried in nonsensical, complex maths a long time ago, and I am extricating it. (See "Maxwell's equations revisited", Wireless World, March 1980, pp 77-78.)

(I would get a real shock if I got a shock from a conductor.) Ivor Catt St Albans

COMMERCIAL BROADCASTING

It is silly to speak of freedom of choice where the main criterion of choice is advertising revenue. It is equally silly to pretend that the best of anything is that which is desired by the majority, who clearly desire pools, dirt as represented by the *News of the World* etc, and poptune after pop-tune regardless of quality; good, bad or indifferent. This morning's paper says that peak viewing is soap-opera. And presumably the finest wartime musical work was "Roll out the Barrel" if popularity is the criterion.

It was as long ago as Hume or J. S. Mill that it was first pointed out that rigid democracy led as surely as any other system to suppression of minority interests. Certainly if longer hours mean more dreary episodes of Coronation Street and the like, more samey westerns and American cop-and-robber sagas and long-since-dated films, then they can have my licence back.

And what is it all for? To try to dupe more people into buying, at ridiculously inflated prices, cosmetics, cancer-sticks, and beer which tastes, as Lawrence Durrell so admirably put it, like a urine sample from a mule. To make matters worse you would think from their attitudes that the advertisers were transmitting the word of God. In fact we would all be much better off if they were all strangled.

F. V. Bale Maidenhead, Berks

With reference to your leader of the December 1980 issue I feel that I must pass comment on a number of salient points.

First, you state that the BBC has already started a course of competing for large audiences on terms set by the commercial broadcasting networks. It is not — it is competing on the same terms as always, but using material which is supposedly more suited to the changing tastes and opinions of the present day. That some find this material displeasing is a consequence of the more depressed financial state of the country as a whole, not just of the BBC itself. There may not exist a desirable level

[†] Cmdr. Hatfield's spectrohelioscope was the subject of the BBC television programme 'The Sky at Night'.

of funds in the Corporation for new developments and the expansion of the network, but on a national level in a period of depressed outlook the discontent with most public services tends to increase anyway.

Secondly, you voice the opinion that, "British life will be impoverished without a good, strong-voiced public service broadcaster, independent of the state, creative and risk-taking...

...". Certainly I agree with most of your underlying sentiments, but I would venture to propound that, with respect to the BBC, the commercial networks have been just as strong-voiced on some important national issues and have demonstrated equal amounts of creativity and willingness to take risks. I would also say it is tenable fact that today they are generally as praiseworthy as the BBC, and state categorically that by definition (and in their modus operandi) they are much more independent of the state.

This brings me to my third point, being your statement that commercial broadcasting "is not independent at all . . ." and does not "sell programmes directly to the public, in the manner of theatres or book publishers . . .". Frankly, I do not follow this line of argument at all, especially as you carry on to say that "It is in the game for profit, and the service which it provides is incidental . . .". Theatres and book publishers produce plays and sell books that in some cases make a significant contribution to our culture, but they are still mainly in the game' for the primary purpose of taking money from our pockets.

Perhaps your leader writer might not have noticed that plays which are box-office disasters (=financial loss) do not tend to stay too long on the stage. Maybe, as a writer, he only has the slightest suspicion that authors receive a warmer welcome at the publisher's office if it is thought that their books may become best-sellers (=financial gain).

The commercial broadcast networks do indeed produce programmes that they calculate will receive the highest audience figures, and they appear to do so quite successfully so that their calculations cannot be too far awry. Therefore the public is paying, albeit indirectly through advertising revenue, mostly for what it wants to receive from these networks: if it were not, advertising revenue would plummet, the networks would go out of business, and the BBC would achieve higher audience ratings. (Somehow, though, I think that previously-advertised products would not be reduced in price; and maybe then the BBC would start to complain about competition from theatres and cinemas?).

The service that the commercial networks provide is anything but incidental; it is their very bread and butter, for if it did not meet the majority of the viewing and listening public's demands it would not receive the revenue income it needs to survive.

Finally, lest I be branded a 'public-sector-basher' or a 'capital extremist", let me wish for the BBC, and our country, better times: let me also ask that we remember that in our time of depression the horns must be drawn in, and that no solution exists in discrediting a service simply because it is *not* public-sector.

F.C.T. Gale, G8FH Hengelo Netherlands

Congratulations on your editorial "Save our public service broadcasting". One has only to view the American broadcasting situation to realise what would happen here if commercial broadcasting got the upper hand. The only reason why it produces good programmes now is because it must compete with the BBC. Had ITV-ILR arrived first, there would have been

no BBC and our programmes would have been at the American level.

The BBC operates two television services and an extensive sound broadcasting service at a lower cost than ITV-ILR operates one television service and a skeleton sound broadcasting service. But the greatest danger facing the public in the event of the demise of the BBC lies in the field of news broadcasts. It is generally believed that most people obtain their news via tv. Those of us who are old enough to remember the so-called "news-reels" of pre-war and just post-war days shudder to think of the type of "news" that would be presented to us by a commercial newshandling monopoly.

Roy C. Whitehead Sutton Surrey

MAIL ORDER BUSINESS

For many years people have bought magazines like Wireless World as a source of up to date information on component prices and availability. In any technical magazine the advertising is as much a service to the reader as is the editorial content. Increasingly, however, the material advertised for mail order is not available. Mail order firms are increasingly banking cheques and delaying months before sending goods either because they are grossly undermanned or because they get interest on the banked money. Alone of your advertisers, Sinclair are honest in admitting that goods will not be supplied from stock. It has been a long tradition in the electronics industry that small orders of components came by return of post. Unless this tradition is restored, I, for one, will no longer order by post. Those firms operating from the West Country are particularly remiss.

I am beginning to wonder if the people Roger Cook pursues have decided to move into the fraudulent component supply racket. Thus far I have not heard of any fraud in the area of electronic supply but the field is wide open. Advertise cheap memory and you could expect at least a thousand cheques for between twenty and thirty pounds. That is a lot of money. Electronics has traditionally been a field where people trusted each other, firms rarely bothering to wait for cheques to clear before sending goods. If criminals are going to move into this area, either by selling kits and data that won't make up into working devices, by sending for goods with bouncing cheques or advertising non-existent goods, a multi-million pound industry could just vanish.

Fred Allen Cambridge

ELECTRONICS AND UNEMPLOYMENT

Though your magazine is not the place for an essay in economics, some comment on the January editorial may be in order.

First consider the overall effect of 'automation', a term which I use as short-hand for any procedure which uses sophisticated capital equipment — whether electronic or mechanical — to reduce the labour content of manufacture. One of the objectives of automation is to reduce manufacturing cost. A large part of the cost of robots, computers etc. is the cost of highly skilled labour employed in their design and manufacture (and marketing). Since there is an overall reduction in cost there must be an overall reduction in labour employed. This is on the basis of constant volume of output; and

there are arguments on grounds of limitation of material resources and 'quality of life' against the older idea of continual expansion of volume of output. Equally important as the reduction in total employment is the upgrading and change in type of skills required.

A reduction in working hours is often demanded. Over the course of history, working hours have been reduced from all the hours of daylight in six days to 60, 50, 40 per week and some further reduction would not be out of line. At constant hourly productivity and constant total output this would require more employees and so reduce umeployment; but in these terms it would be a form of work-sharing and require a reduction in weekly wage — probably not acceptable.

There are many detailed ifs and buts to be added. For example, if morale is improved by shortening the working week, production per man will not be reduced pro rata with hours. Volume of production may be limited by natural resources, but what about the sophistication factor? Automation may reduce cost of manufacture, but this is not the only motive for its introduction. One cannot just say whether or not "chips" will cause unemployment of millions: one must examine each sector of industry in detail and then the interactions between sectors. The one thing which does seem clear, however, is that training in appropriate skills is going to be of supreme importance.

D. A. Bell Beverley North Humberside

MICROCHIPS AND MEGADEATHS

Your editorial of last November, 'Microchips and megadeaths', and some of the letters in reply, remind me almost irresistibly of the words of 'Shooty' in the 'Hitch-hikers' guide to the galaxy': "I don't go round gratuitously shooting people and then bragging about it in seedy space-ranchers' bars. I go around gratuitously shooting people and then agonising about it afterwards to my girlfriend."

May I suggest that any electronics engineer who really agrees with your editorial should resign his job and live on the dole. Thus not only would he avoid the risk of inventing anything that might have a military application, but he would use up funds which could otherwise be spent on arms.

J. S. Linfoot
Oxford

By profession I am an artist; my hobby, since the early 1950s has been electronics. Wireless World has always been of great interest to me, keeping me up to date. Your articles and projects have always been on the highest level. I have built many projects — from Dinsdale, Linsley-Hood, Nelson-Jones, Baxandall etc. — and have received much pleasure from them, although I think the designers would be shocked with the look of some of my efforts. I bend wires instead of using p.b.cs, though, believe it or not, most work extremely well.

The other side of the electronics profession disturbs me very much and, like you, I wonder how highly intelligent, highly skilled electronics engineers can be so blind as to continue to invent and to use their ingenuity with modern circuitry, not to give pleasure and ease the burdens of life alone, but to destroy everything they and every creative person has ever worked for on this planet — including themselves and us!

Your excellent leading article and some letters from engineers in the industry in the No-

vember 1980 issue prompts me to write and congratulate you on your courage and foresight in printing these. Having travelled broadly, I know your magazine is read in many countries, so I hope engineers in the industry will take inspiration from you and stop supporting the industrial and political maniacs around the globe in their blind drive to destroy so much of the work of the Creator.

Please carry on the good work.

Ken Evans
Shaftesbury
Dorset

ELECTRONIC COMBINATION LOCK

I have read with interest the article describing an electronic combination lock (January issue), but what I feel Jan Hruska ought to have developed is a lock that opens to a pre-determined rhythmic operation of a conventional door bell press button. This would save any need for a keypad, and would be of use in situations already equipped with an electric striker, such as buildings with controlled access by "entryphone" type systems, for example blocks of flats.

H.T. Wynne Glasgow

The author replies:

I would like to make the following points in favour of my original design:

1. The hexadecimal code used in my design is equivalent to a combination of 16 dots and dashes, which would be a considerably greater burden of information for a non-user of Morse to learn.

2. Input of code in this form would take longer. However, I had already considered constructing such an alternative device and have built a battery operated prototype using an Intel standalone microcomputer.

Jan Hruska University of Oxford

PICKABACK SPARKS

John T. Lloyd, writing in November 1980 letters, mentions the phenomenon where a third electrode at high voltage initiates a discharge in air between two electrodes connected to a charged capacitor. I can confirm his observation and would add that a high frequency Tesla coil source may not be necessary.

I first observed the effect as a child, when I built an electronic flash gun. Having no xenon tube at the time, I decided to attempt an air discharge. The capacitor was about 200µF charged to 350 volts, and a miniature ignition coil was used (from a model aircraft). At first I was only able to obtain the weak high voltage spark, but by moving the electrodes progressively closer, I was rewarded by the bang and blue flash which discharged the capacitor. I found that a bare copper wire, freshly cut on a diagonal gave the best result.

Much later in life, I suggested the idea of a third electrode to Unilever Research in connection with an explosibility test apparatus. Originally two pointed electrodes were connected to a bank of capacitors which were gradually charged. The gap was sized to fire at a predetermined voltage. Unfortunately, the voltage at which breakdown occurred was not accurately reproducible. Some of the reasons will be apparent from "Sparks gaps" by J Dearden in your November 1980 issue.

Using a third electrode allowed "ignition" of the discharge which then almost completely emptied the main capacitor bank. The significance of this method is that although a high voltage spark is used to ignite the discharge, the energy in the high voltage spark can be minute by comparison with that in the capacitor bank. This discharge starts at a very predictable voltage (that of the capacitor bank itself) and a negligible disturbance is caused by the third electrode.

This idea worked very well in practice. I do not know whether Unilever has used this work or published it since I left. However, I would certainly like to lay claim to the invention; although I would be very surprised if no-one realised that this effect could happen before I discovered it for myself as a child.

A. R. Churchley Sara Ltd Warrington Lancs

OPPORTUNITY LOST?

While in course of conducting research in the technological history of disc sound recording I browsed through a volume of the defunct German scientific journal Akustische Zeitschrift. On the last page of the July 1941 issue there is a review of a demonstration that took place in Berlin on June 10, 1941. The object in question was the "new Magnetophon" which boasted noiseless playback. The paragraph which is of the greatest interest, historically, is the following (translated by me into English):

"In recent research H. J. von Braunmuhl and W. Weber (RRG) succeeded in improving the quality considerably, particularly the dynamic range, because they used high frequency magnetization in the recording head instead of d.c. magnetization. Thereby practically all noises originating from the tape disappear."

Now what does this prove? It proves to me that a fact which was not discovered by the Allied powers until 1945 and which explained certain feats of radio transmission during the 1939-45 war, was in fact publicly disclosed in Germany as early as 1941. The technical description was adequate, i.e. a person skilled in the art would have been able to fathom the advantages, had he read that particular review. The war was a great obstacle, but surely there was at least a trickling distribution of scientific journals in the Allied countries (possibly through the neutral states Sweden or Switzerland). It seems rather a case of too few readers with sufficient fluency in reading German, because none of the standard accounts of the history of magnetic recording mentions this very early publication (e.g. Basil Lane's extremely thorough "75 years of magnetic recording" in Wireless World in 1975). It also proves that research into the history of technology (as any other historical discipline) cannot do without access to every page of an original publication and cannot be done by means of abstracting services or the like.

I hope to be corrected by any of your readers who may know about previous publication of the above reference.

George Brock-Nannestad Gentofte Denmark

DESIGNING WITH MICROPROCESSORS

R. M. O'Connor, writing in October 1980 letters, raises a number of important matters which deserve further discussion.

Firstly, there is no one "best" way of learning about microprocessors and their application. A

method aimed at recent graduates with a formal training in logic design may be completely inappropriate for a practising designer with many years of experience, and now faced with using this new device. Similarly, a programmer with a background in mini-computers is likely to need a quite different approach. I hope that Wireless World will cover these aspects too in due course.

O'Connor makes the point that what the designer needs to know is what micros can do. It is equally important that he also knows those things that micros can't do economically. There has been far too much talk about the wonders of the mighty micro, and far too little about the cold, hard facts of the hidden costs of using them.

On the question of machine independence, neither O'Connor nor Zissos and Valan have said whether they are talking about a single chip controller, a small industrial controller, or a system such as a TRS-80 or an Apple with a large capacity hard disc, line printer, etc. Perhaps it is best summed up by J. L. Alty in his introduction to Professor Zissos's "System Design with Microprocessors" in which he says:

"It is important to realize that the new technology will permeate society in two ways – the high volume/low cost and low volume/high cost categories. The former type will be produced in millions and will be very cheap indeed. They will often be single chips dedicated to one application and, as such, will not even be recognisable as computers.

Computer systems do not however consist of hardware alone. The software required to operate the new technology will also be provided in the same two categories — high volume/low cost and low volume/high cost, and each category will tend to run on the equivalent category of hardware. The software in the single purpose chips for example will also be single purpose, relatively fault free, and very cheap if only because of the large volume of sales. It will be unalterable by the user, and will not be maintained. It will simply have to work."

In the high volume applications, the cost of the hardware is likely to be the deciding factor. A \$1.00 microprocessor is going to face stiff competition from another costing 99c, no matter which language each uses. For these applications it won't make much difference which language is used — so long as the final code will fit in the memory space available, will do what has to be done in the time available, and is highly reliable.

The major part of the cost of software for microprocessor applications is in preparing the detailed specifications, then deciding the program logic and verifying the flow charts. The cost of coding these flow charts is then fairly small, so that if it is necessary to use a different microprocessor at some stage, the conversion cost could well be fairly small — particularly if the original programs have been kept free of sneaky tricks designed to save the odd byte of code by using a special feature of the original microprocessor.

At the other end of the scale, in the one-off and specials, the lowest total system cost will usually be obtained by using "off-the-shelf" standard hardware and software, with the absolute minimum of additions. In these cases, it often pays to modify the requirements to suit what is available to keep the costs down. Although the system may well turn out to be much more powerful than really necessary, does this matter if the costs are reduced?

For small production runs, it is probably better to design the system around a range of "off-the-shelf" modules. In this case, the particular microprocessor used is not as important as the range of modules available, and whether the hardware modules each have any necessary driver software supplied with them. Each module should be supplied with its own service

manual, so that the system documentation can be prepared by assembling the manual for each module, and adding a section on the complete system.

O'Connor raises the question of the disappearing micro. Now although it is true that many microprocessors have appeared, then disappeared just as rapidly, there are three families that have been with us for many years, and look like being around for a long time to come. These are the 6502, the 6800/6809 and the 8080/8085. Not only have the manufacturers taken care to see that it is a simple matter to change the software for new members of each family, but there is considerable support in the form of hardware and software, both from the semiconductor manufacturer and also from a large number of independent suppliers. I have deliberately left out the Z80 for two reasons there is little software available specifically for the Z80 and in most applications they run 8080 code and so do not make use of all the extra facilities, and their future is likely to depend very much on how fast the Z8000 is accepted. The Z80 might simply be phased out and replaced by the 40-pin version of the Z8000.

The moral from this would seem to be - if you are going to make your product in millions then do what you would do for any other product, i.e. specify an interface that is independent of the type of microprocessor used, place an order for the cheapest components from one or two reliable suppliers, and make sure you buy enough for future spares. If the product sells so well that you have to make another 10 million, then it won't matter if new software is needed. After all, a black box is a black box is a black box is a black box to misquote Stein, and if you can't get inside it to repair or change it. does it matter whether it is a microprocessor, a state machine or random logic? What is important is the original unit cost, the reliability, and the replacement unit cost.

On the other hand, if you are only going to produce small quantities you had better stick to one of the above three families, and design around the one which has the best overall hardware and software support available to you locally, and which has a range of readily available modules which meet your needs. Although these modules look expensive at first they turn out to be far cheaper than rolling your own. You have to make a large quantity to recover the development and proving costs, even if you follow the recommended practices and get it right the first time. Designing a unit which works correctly is straightforward - designing a unit which works correctly and can be produced economically requires considerable extra skill and experience.

This leads me to comment on the design steps used by Zissos and Valan in part 5 (October, 1980). They advocate designing the hardware first then the software, then repeating these steps until a satisfactory design is obtained. In each of the failed designs that I have investigated the designers have followed this approach. I cannot stress too strongly that these two steps must be carried out concurrently, and in fact that there are four separate but strongly interwoven areas that must be considered in parallel. These are: 1. Hardware design. 2. Software design. 3. Design for testing. 4. Design for production.

The last two areas are often left till the prototype is completed, and then it's back to the drawing board for some very expensive changes. We should follow the Smallpiece philosophy of "Get it right the first time." Test points, both for production testing and field servicing must be built into the hardware and software during the original design. There is a lot to be said for making a commitment to including signature analysis in every product. Similarly, what is the point of designing a system that can't be produced economically without redesign and the consequent delays in getting your product into the market place? After all, one of the big incentives to using microprocessors is that their use can substantially reduce the development time for the product.

As O'Connor said "Microprocessors are only cheap if they are cheap to use; if the way in which they are used brings crippling costs, they are extraordinarily expensive."

Alan M. Fowler North Balwyn Victoria, Australia

DESIGNING WITH MICROPROCESSORS

I would like to thank D. M. Vaidya for his letter in the March issue (p.62) pointing out the error in our Table 3 (p.73) of Part 6 of our series "Designing with microprocessors" in the December 1980 issue. We understand that the editor hopes to publish a corrected version in the next available issue.

Regarding the second point, we must disagree on this. We have written numerous programs using different microprocessors which show the generality of the approach that can be achieved with these different devices. This will be demonstrated in detail in an article which will follow later in our current series. Meanwhile, any readers who would like to have this information in advance are welcome to write to us at the address below.

D. Zissos and L. Valan
Department of Computer Science
University of Calgary
Calgary, Alberta T2N 1N4
Canada

THE TWINS PARADOX OF RELATIVITY

Alex Jones's letter (January) contains a fundamental flaw which I feel should be corrected.

The relative ageing in the Twins Paradox is not dependent on the accelerations at the start and finish of the journey, because the theory has it that, with the same accelerations, doubling the spatial distance of the trip doubles the age difference at the end (with short acceleration durations compared to total journey duration).

This is certainly the impression Einstein, wished to impose on the world, and it is backed up by the whole series of text-books since. The effect is quite clearly one of Special Relativity, not of General Relativity.

If, as he suggests, the results of SRT are only "apparent", but the Twins Paradox experimentally resolves in Einstein's favour, as numerous text-book writers would have us believe, then Jones's "coincidence" is not only remarkable, but miraculous.

L. J. Higgins Swindon Wilts

WIRELESS WORLD'S 70th ANNIVERSARY

If I give a brief record of my association with Wireless World it will explain how much pleasure it has given me to be invited by the present editor to say a few words on the 70th anniversary.

Looking for a career in journalism I answered an advertisement by the Marconi Company for an editorial assistant which stated "some knowledge of wireless would be an advantage". As I already had a Post Office Experimental Licence and had read all I could on the subject I had no difficulty in securing the job. I found myself on the editorial staff of the Wireless World with the launching of the first number. With a commission in the Royal Engineers, the 1914-18 war took me to Mesopotamia and Persia engaged on interception and direction finding. The Marconi Company kindly kept open the editorship of Wireless World for me on my return after demobilisation and I continued with the journal as editor and then as director and managing editor until my retirement in 1962.

With a career which has been so intimately wrapped up with the story of the Wireless World I welcome with enthusiasm its achievement of 70 years and, under the control of our present editor, we can look forward with every confidence to the future. I am proud to have been associated with a staff which has created Wireless World over the years.

Congratulations and every good wish for the future.

Hugh Pocock



Hugh Pocock, writer of the above letter (centre), with two later editors of Wireless World, H. F. Smith (right) and F. L. Devereux (left), on the occasion of the journal's 50th anniversary.

Dividing by fractions

Digital frequency synthesis using non-integral frequency division

by Gilbert Pearson, Australian Broadcasting Commission

This circuit allows a direct division from PAL/625 sub-carrier frequency to twice-line frequency, or a direct multiplication from twice-line to subcarrier frequency. This is achieved in both cases using only digital counters and a single, phase-locked loop.

Present methods require additions or subtractions in the frequency domain, which in turn require linear stages.

The unit to generate sub-carrier frequency from line frequency has been built and found to work satisfactorily. The greatest use for the circuit may well be found in synchronizing pulse generators, where its low cost and reliability should prove an advantage. But the principles described are applicable to any frequency synthesis problems where fractional divisions or multiplications are required.

The colour sub-carrier frequency as used in the 625/PAL colour television system is 4,433,618.75Hz. It is derived from the relationship –

283³/₄×line frequency+25Hz i.e. 283³/₄×15,625+25Hz

The addition of the 25Hz makes synthesis of one frequency from the other difficult. While straight divisions or multiplications can be done simply, with integrated-circuit dividers and phase-locked loops, the addition or subtraction of frequencies, such as 25Hz, requires precision phase shifters and tuned stages.

A common technique used in the generation of twice line frequency (2LF) from sub-carrier (SC) in a sync. pulse generator is shown in Fig. 1.

New method

The two frequencies can be broken into lower multiples, as shown below.

Thus,
$$\frac{SC}{11 \times 25 \times 25 \times 644.89}$$

$$= \frac{2LF}{2 \times 25 \times 25 \times 25} = 1Hz$$
i.e.
$$2LF = SC \frac{25 \times 2}{11 \times 644.89}$$

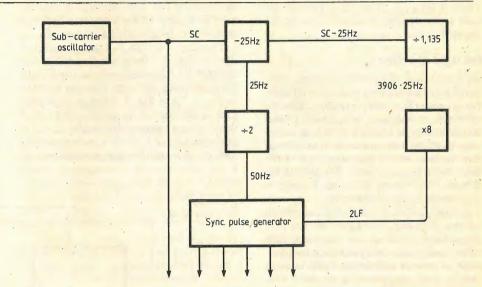


Fig. 1. Typical synthesizing technique.

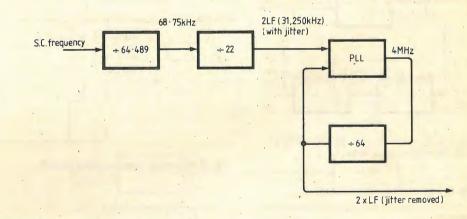


Fig. 2. Twice-line frequency (2LF) derived from sub-carrier frequency.

$$=SC \frac{5}{11} \times \frac{1000}{64,489}$$

It must be pointed out at this stage that 64,489 is prime number and thus cannot be broken up further. From the above, it would seem that we could divide by 64,489, multiply by 1,000, divide by 11, multiply by 5 to generate twice line frequency. The problem with this, however, is that SC divided 64,489 gives 68.75 Hz and it is extremely difficult to stabilize a phase-locked loop (p.1.1. hereafter) with an input frequency which is so low. An ideal solution would be a divider which somehow achieved a fractional division.

i.e.
$$2LF = \frac{SC}{2.2 \times 64.489}$$

A reasonable first reaction is that this is impossible, and strictly this is correct. However it is possible, using programmable counters, to achieve on average a fractional division by dividing by two or more numbers in an appropriate ratio. For example a division of 4.5 could be performed by dividing alternately by 4 and 5. A division of 4.333 could be performed by dividing by 4 and 5 in the ratio of 2:1 respectively. Of course, the problem with such an arrangement is that the output exhibits a large amount of jitter. This can, for our requirements, be eliminated by a phase-locked loop and will be dealt with

If we assume for the moment that both 64.489 and 2.2 dividers are possible, arrangements as shown in Fig. 2 and 3 can

WIRELESS WORLD APRIL 1981

be used to generate 2LF from SC and viceversa. In the schematic in Fig. 2, 2LF is derived directly from the two dividers in cascade. However, this output has large amounts of iitter, so the p.l.l. and divideby-64 is included to remove this. This circuit would seem particularly useful in a sync. pulse generator where a suitable p.l.l. is often included anyway for the purpose of genlocking.

In Fig. 3, the p.l.l. serves two functions. Firstly, in conjunction with digital circuitry, it provides the means of multiplication. Secondly, by selecting the time constants of the p.l.l., it serves to prevent the jitter of the dividers being reflected on the SC output.

64.489 divider

As described in the previous section, fractional divisions are obtained by dividing by two numbers in a suitable ratio. In the case of 64.489, a solution is to divide by 64 and 65 in the ratio of 511:489. There are many ways in which such a ratio can be achieved. but the best one is that which gives the least low frequency jitter. To do this the divisions by 64 and 65 must as near as possible be evenly distributed.

Before moving to a detailed description of the divider, background on the programmable counters is necessary. The 9310 is such a counter, in which it is possible to arrange a division of any number from 1-10 by programming on pins 3 to 6. It is further possible to cascade the coun-

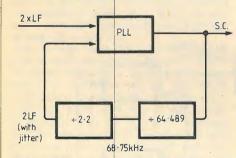


Fig. 3. Sub-carrier frequency (SC) derived from twice line frequency.

ters and so arrange a division of any number. For our particular purpose a division of 64 and 65 can be achieved as shown on Fig. 4. The programming for each division is shown at the bottom as well as the logic required to switch between the two divisions. When point A is high a division of 64 is performed and a division of 65 when low.

If, as in Fig. 4, the output of the divider is divided by 2 and fed to A, the result will be that the principal divider will alternately divide by 64 and 65, giving, on average, a division by 64.5. The output is also shown to be fed back, through a gate, to the PE terminal of the counters, This is a requirement for this particular counter.

The circuit of Fig. 5 is an extension of that in Fig. 4. There are five 9310s designated XI-X5, integrated circuits X1 and X2 performing the same function as those in Fig. 4. As in Fig. 4, when point A goes high a division of 64 occurs. Instead of there being a separate division by 2, this is performed by X3, itself a programmable divider. X3 and X4 are programmed to

divide by 90 and 92 and, since both are even numbers, the Q₀ output of X3 will, regardless of which division is performed, always alternate between 0 and 1.

As stated previously a division of 64.5 is performed by the circuit shown in Fig. 4. This is close to the required division of 64.489. If 11 of the divide-by-65s ("÷65s") in 1,000 are changed into "÷64s" the correct ratio of 511:489 is obtained. This occurs in the circuit of Fig. 5. X3 and X4 divide by 90 and 92 in the ratio of 6:5. This means that they divide by 90.9090 . . . or 1,000/11, and point C will thus have eleven pulses for 1,000 occurring at the clock of X3. Furthermore, these pulses derive from the terminal count of X4, and thus at a time when O₀ of X3 is high and when B would be low, normally giving a ÷ 65 instruction. The 'high' on C thus overrides this through the OR gate and forces a "÷64" instead. The correct ÷90, ÷92 ratio is obtained from X5. A 9310 is not usually used to divide by 11, but it was used in this case to make all the types standard. When X5 is programmed


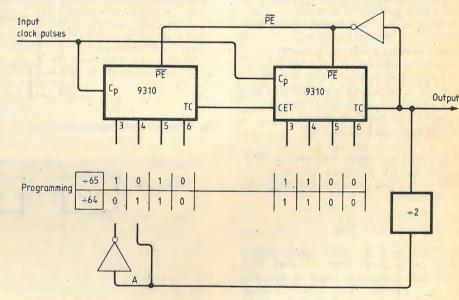


Fig. 4. Alternate divisions of 64 and 65.

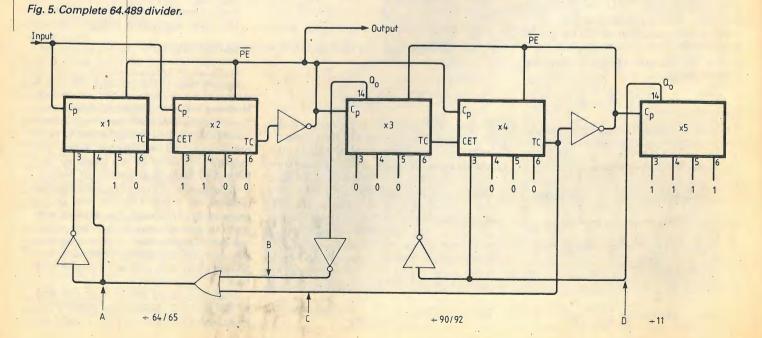

WIRELESS WORLD APRIL 1981

as shown, it will divide by 11 and its Q₀ output will oscillate between 0 and 1, except at the maximum count, when it will give two consecutive 1s. Q₀ will thus be high and low in the ratio of 6:5. It is this point, point D, that is used to command the ÷90/92 counter.

To summarize, X1 and X2 divide by 64 or 65, depending upon the command appearing at point A. This point will go high ("÷64") when either B or C are high. B alternates between low and high and thus, taken in isolation, would alternately command division by 64, 65. Point C goes high for just 11 of 1,000 pulses appearing at the output and it does this when B is low, instructing a "÷65". On these 11 occasions in 1,000 then, a "÷65" is converted to a "÷64" making the ratio of the two divisions 489:511 instead of 500:500 or 1:1.

litter. If the divider is given an input of sub-carrier frequency it has the following jitter components:

Frequency	Jitter (ns-pp)
34.375kHz	226
756.25 Hz	111
378 Hz	1.24
68.75 Hz	1.13
378 Hz	1.24

The first can be easily understood, since the divider for most of the time divides alternately by 64 and 65, meaning that the output phase oscillates about a true mean with a period of two output cycles. Since with a SC input the output will be 68.75kHz, this first jitter frequency must be half this, 34.375kHz. Its peak to peak excursions are 226ns, one period of the input frequency (T hereafter).

The remaining components are best des-

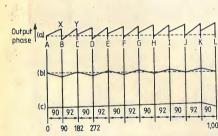


Fig. 6, 756,25 Hz, 378 Hz, and 68,75 Hz jitter components.

cribed with reference to Fig. 6(a). The horizontal axis is calibrated in periods of the output of the divider (1-1,000) and the vertical in its output phase, such that a mean line would be horizontal. The 34.375kHz component has been ignored. Beginning at point A, the divider divides alternately by 64 and 65 and since this is not quite the required division the output phase steadily deviates from the mean as seen by the slope of line A X. Referring to the previous section, instead of the 89 and 90th divisions being 64 and 65 as before, they are both "÷64s" resulting in an abrupt correction in the output phase (X-B). The count sequence from B-C is similar, except that the 91st and 92nd divisions are altered to both be "÷64s". Thus A-B and B-C give slightly different average divisions. The counts from C-D, E-F, G-H, I-J, and K-L are identical with A-B, while the alternate ones, D-E, F-G, H-I and J-K are identical to B-C. It must be noted that there are six of the former sequences and five of the latter, as described in the previous section. After point L, the entire sequence A-L repeats itself. By a quantitive examination of the plot of Fig. 6(a) it is possible to calculate the various jitter components, their waveforms and peak to peak values.

Alternate divisions of 64 and 65 clearly give an average of 64.5. This differs from the final required average by 64.5-64.489. That is 0.011 of an input period (T). This

error repeats itself for every pair of divisions and is accumulative. After 88 divisions, or 44 pairs of divisions, from point A, the accumulated error will be $44 \times .011 = 484T$ at point X. When the correction is made, (X-B) with a double-division-by-64 a step of 64.0-64.489 = -0.489T is made.

It is clear that the sawtooth plot AXBYC ... represents the next most significant jitter frequency. Eleven cycles of this jitter appear within 1,000 divider output periods; thus, its frequency is

$$\frac{68,750\times11}{1,000} = 756.25$$
Hz

Its peak to peak excursions will be 0.489T, i.e., with a SC input - $0.489 \times 226 \text{ns} = 111 \text{ns}$

An error of +0.484T accumulates to point X and a correction is made (X-B) of -0.484T when a double division by 64 takes place. The correction therefore "overshoots" by an amount of 0.005T. As the counter proceeds from B to Y, an error of $45 \times 0.011 = 0.495T$ accumulates. A double division of 64 occurs from Y to C bringing a correction of -0.489T. In this case, the correction is insufficient and "undershoots" by an amount of 0.006T. Since C-D is identical to A-B and D-E is identical with B-C, the process of "overshoot", "undershoot" continues, the jitter waveform of Fig. 6(b) being the result. It is

continued on page 76

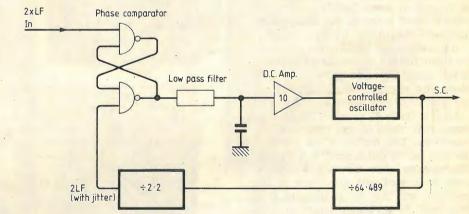


Fig. 7. Phase-locked loop used for synthesis of sub-carrier from twice line frequency.


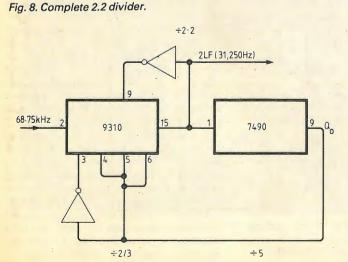


Fig. 9. Complete 4.4 divider.

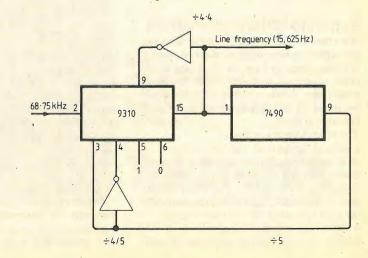

Phase measurement with an oscilloscope

Avoiding the difficulties of Lissaiou figures and time estimation

by I. D. MacArthur

A method of measuring phase angle between two sine waves of the same frequency is described, using a double-beam oscilloscope, which is easy to use up to the full vertical bandwidth of the oscilloscope.

The classical method of measuring phase is by Lissajou figures, as in the example of Fig. 1, a method which suffers from a number of drawbacks. The centre of the ellipse must be accurately aligned with the cross wires of the graticule and then measurements made against the graduations, which are usually on the centre lines themselves. This is tricky and prone to error. Accuracy is poor when the phase angle is near 90° or 270°, and the gain of the horizontal amplifier is usually limited, making it impossible to "open out" the ellipse with small signals. The maximum frequency at which measurements can be made is also restricted by the horizontal amplifier even a very good modern oscilloscope may be limited to about 200kHz before the relative phase shifts in the vertical and horizontal channels become unacceptable.

It must be stated though, that the Lissajou figure has one big advantage in that it is very useful for checking zero (or 180°) phase shift when the ellipse is closed and any small departures are easily visible.

Another method, shown in Fig. 2, is to measure the times of zero crossing of the waveforms. This method is still probably the best for "a quick look" but has the disadvantages that the two waveforms must be aligned with the centre of the graticule, and that the oscilloscope time base must be accurately triggered. One must also choose between the chopped and alternate modes, which both have disadvantages. On some oscilloscopes it is necessary to provide an external trigger.

Sum-and-difference method

Here the two signals are displayed as in the zero-crossing time-interval method, but it is unnecessary to have the timebase accurately triggered, or even synchronized in some cases. Measurements can sometimes be made in the presence of significant amounts of noise.

The procedure is as follows:

- Adjust the gain of the two channels to give equal-amplitude signals approximately half the screen height (to allow for displaying a 2× signal). The exact amplitude and gain settings are unimportant and the time base need not be synchronized.
- Switch the channel selector to A+B (algebraic add) and record the peak to peak

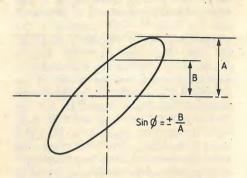


Fig. 1. Phase measurement by the Lissajou figure method. This is difficult, since the graduations on the cursor are usually on

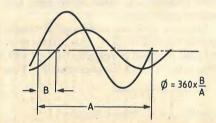


Fig. 2. The zero-crossing method, which can be tricky to set up symmetrically on the

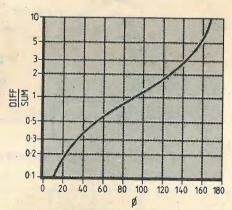


Fig. 3. Graph of diff./sum plotted against

amplitude of the resulting sine wave (the

• Switch the channel selector to A-B (or invert one channel) and record the peak to peak amplitude of the resulting sine wave (the difference voltage).


• Calculate the phase angle from

$$\Phi = 2 \tan^{-1} \frac{\text{difference}}{\text{sum}}$$

or use the graph in Fig. 3.

When using this method one must understand its limitations. When making high-frequency measurements it is vital that probes are equally compensated -

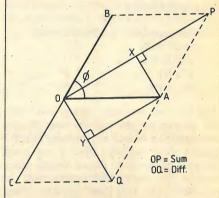In the phasor diagram, OA and OB represent the two signals being compared, with a phase difference of Φ between them, shown for convenience in the first quadrant, OC represents the OB signal shifted in phase by 180°, OP is the vector sum of OA and OB, and OQ is their vector difference. OB, OA and OC have been made equal.



AX and AY are perpendiculars from A to OP and OQ and AOP and AOQ are isosceles triangles.

1	1	angle.	AOP = a	ngle	$APO = \Phi$,
	and	0	X = XP			
	Hence	0	X=AO	cos 4	2/2	
	and	0	P=2A0	cos	Φ/2	
1	Similarly,	. 0	Q = 2AC	sin ($\Phi/2$.	
	Now,	2A0 2A0	sin Φ	/2 =	differer	1
			= tan	Φ/2	Juni	
	Hence		= 2 t		sum	
İ	Fig. 3 plots	this re	sult gra	phic	ally.	

best done by connecting both probes to one signal and adjusting for equal amplitudes. The accuracy of the method deteriorates as Φ approaches 0° or 180°. If the voltage measurement accuracy is ±5% then accuracy will be about 6.3% at Φ =90°, reducing to about 10.5% at $\Phi=12^{\circ}$ or 168°. Accuracy will also be impaired if significant distortion of either sine wave exists: it is useful to synchronize the time base and check the waveforms.

While the sum-and-difference method of phase measurement will never replace an accurate phase meter or vector voltmeter in the eyes of those who can afford them, it does offer a useful technique which can sometimes out-perform these instruments, particularly when the signals are noisy. I have used the technique on a switching regulator to measure 10mV signals in the presence of 100mV of noise.

"Tektronix Walue for money."

We sell the finest low cost oscilloscopes in the world.

The complete range of low-cost oscilloscopes available from Tektronix offers more choice and more value for money.

Because everyone needs a slightly different performance in either band-width/ sensitivity or extra control functions, we offer a range with different specifications. There are 4 dual-trace oscillos- thoroughly pre-tested to meet


copes to choose from in the Telequipment D1000 Series family, with 10 or 15 MHz bandwidths.


And there are 5 different Tektronix T900 Series oscilloscopes ranging from a 15 MHz single trace oscilloscope to a 35 MHz dual-trace oscilloscope with Delayed Sweep.

All our oscilloscopes are

the high standards that go with our name. The result is solidly built oscilloscopes which are not only easy to or rate and maintain but also represent the most reliable buys on the market.

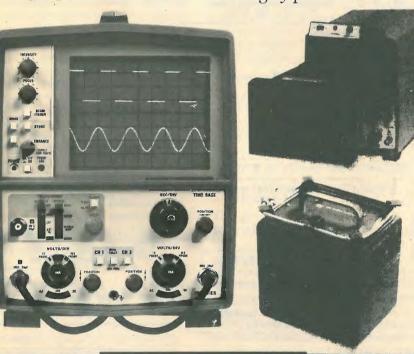The T900 Series is supported by a full range of accessories including battery power packs, cameras & scope stands.



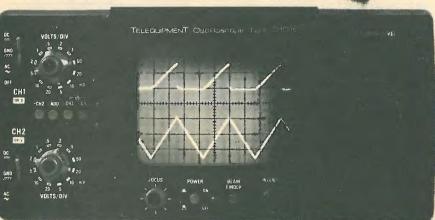



* oscilloscopes are sold & orldwide by Tektronix.

Please send me more information on Teleguisment Oscilloscopes T-900 Series Oscilloscopes

i	Name
ŧ	Position

Company

Address

Telephone

Tektronix International Inc.

European Marketing Centre Postbus 827, 1180 AV Amstelveen The Netherlands




WW-005 FOR FURTHER DETAILS

TOP QUALITY REBUILT TV TUBES

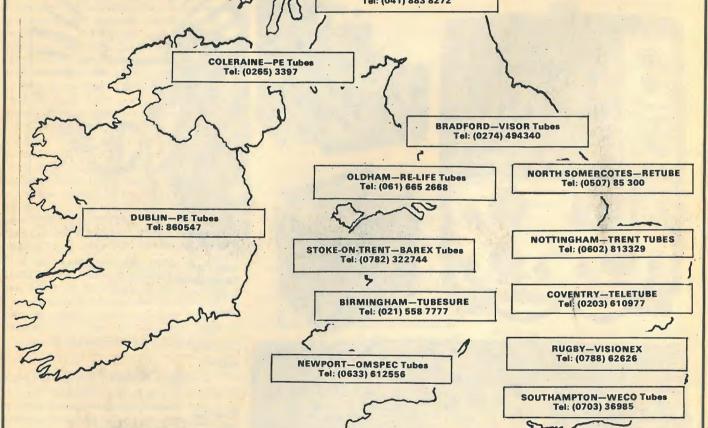Rebuilt on the most modern equipment to original manufacturers' specifications





All these top-class rebuilders use plant and equipment manufactured by Western-Whybrow Engineering acknowledged as the best available, and the product of more than twenty years' experience of rebuilding colour tubes in U.K. and U.S.A. There is a constant interchange of information to ensure the highest standard of rebuilt tube.

PENZANCE—WECO Tubes Tel: (073 676) 2265



No. 1.

WIRELESS WORLD APRIL 1981

April, 1911.

Subscription, 3 = per annum.

Price 2d. Post Free 3d.

In 1911, the name of Marconi was almost synonymous with 'wireless': marine wireless operators were, as often as not, referred to as 'Marconi operators'. The growing profession of operating Marconi stations on board ship demanded a magazine, and the Marconi company responded in April 1911 with The Marconigraph, which carried news of the company, of operators scattered worldwide and of developments in wireless technique. Two years later, for reasons which have been aired before by writers more directly concerned with the event, The Marconigraph became The Wireless World and embarked on its declared life's work of being "of use and interest" to a rather wider fraternity than had been the case in its previous existence. Sticklers for detail may, with some justification, point out that WW is not 70 this month, but 68. We feel, however, that the two larval years should count towards the total for, while laying no claim to be roseate, we think WW quite as sweet as The Marconigraph.

While the new science and technology was at first naturally associated with ships' communications, there is a remarkably close parallel to be drawn between the development of radio (and later electronics) and aviation. Both technologies were emergent in 1911 (Bleriot had landed at Dover only two years earlier and Fleming's two-electrode valve was only seven years old), both were to advance rapidly in the two wars and have each, over the years, called for specific development in the other. In the beginning, communication was all, but even in the early days, direction finding and even radio landing aids were seen. The emergence of radar techniques and navigation systems changed the ways in which both civil and military aircraft were operated and even the design of some of them. Looking at it the other way round, the demands imposed on radio and electronics by military aviation in two wars and by an enormous expansion in civil air travel have hastened the development of avionics to a degree where only marginallystable aircraft become docile, but agile, and where landing aids are capable, in theory at least, of not only landing an aircraft in zero visibility, but getting it to the terminal building as well. Electronics and aviation are now so inextricably interwoven that airliners could hardly be operated without electronic assistance, and military aircraft would be unrecognizably different.

Wireless World, 1911-1981

From crystal detectors to microcomputers in 70 years

Wireless World has always reflected this use of electronics, beginning with the wireless sets used for gunnery spotting in 1916, reporting Lorenz instrument landing systems in 1935, gathering a whole mass of newly released radar information immediately post-war and continuing to report on air communication and navigation when the information is "of use and interest" to readers.

Our two enduring interests over the years have been radio and television broadcasting and reception, and the high-quality reproduction of sound. A great many of the leading figures in high fidelity have written in WW, and continue to do so, on theory and practice - an aspect perhaps best demonstrated by the publication of designs for D. T. N. Williamson's valve amplifier just after World War II, which set a standard to judge the rest by. People still write in to ask for reprints of these

The Williamson standard was and is upheld by writers such as Jack Dinsdale, Arthur Bailey, Laurie Nelson-Jones, John Linsley Hood and many others on the practical side of our content, and contributors of the calibre of Peter Baxandall, Professor David Bell, Thomas Roddam and the immortal Marcus Scroggie (Cathode Ray) have educated thousands of readers in the art of electronics.

Coverage of television began with Baird's first crude experiments, although the tone of some of our reports was a little bemused. It reached peaks in 1947 and 1968 with the publication of one of the first designs for a home-constructed monochrome television receiver (deflection voke and line-output transformer both being home made) and the colour receiver by Walter Cocking, who made an enormous contribution to the standard of our practical articles over many years. The two receiver designs illustrated some of the reasoning behind WW projects, in that they were not necessarily the cheapest way of acquiring the receiver, or whatever was being built. One of the reasons for publishing them was that such a series of articles is undeniably the best way of explaining the operation of equipment. Even if one does not undertake the construction, the text is valuable in its own right.

In those days, of course, there were no integrated circuits. Circuit design was not the cost-effective deployment of the vast range of modules one can now select from, but the basic design that still goes on behind closed doors, its outcome being encapsulated in plastic. Integrated circuits have brought with them enormous opportunities for technical progress, but an unfortunate effect from a journal's point of view is that an article describing a piece of digital equipment often reads a little like a knitting pattern. It is not as easy as it used to be to read such articles in isolation.

Nevertheless, we have no intention of abandoning the ground rules laid down 70 years ago, that Wireless World should entertain, educate and be of use to the new generation, as well as their elders. It is doubtful that G. Marconi would recognize his grown-up brainchild, but we do hope he would approve.

7 - Wait/go systems

by D. Zissos, Department of Computer Science, University of Calgary, Canada

Previous articles have described the synchronization problem and the most widely used solution involving software wait loops. In this article the wait/go concept is explained and step-by-step procedures for the design and implementation of wait/go systems are described. The design steps are illustrated by means of a fully worked out example.

The synchronization problem of microprocessors and the most widely used solution involving software wait loops have been described in previous articles. In this article we shall describe a hardware solution which involves keeping the microprocessor in animated suspension while the peripheral is responding. Systems using this solution are easy to design, program, implement and maintain.

The wait/go concept


Let us assume that we have a microprocessor which automatically enters the wait state when an i/o instruction is being executed. Let us further assume that when in the wait state it generates a logic 1 on wait terminal w, and that it exits the wait state when the signal on go terminal is pulled high (g:=1). The block diagram and state diagram of such a microprocessor are shown in Figs. 1 and 2. If we were to activate the peripheral with the 0 to 1 transition of the wait signal w and keep the microprocessor in the wait state until the peripheral had fully responded, we would clearly have no synchronization problems. Furthermore, if the peripheral is an action-/status device¹, the interface reduces to two wires, as we show next.

The two-wire interface


Our starting point is the block diagram of a wait/go system shown in Fig. 3. The signals w, g, a and r have the following meaning:

Signal w: A '1' on this terminal (the wait line) indicates that the microprocessor has entered the wait state.

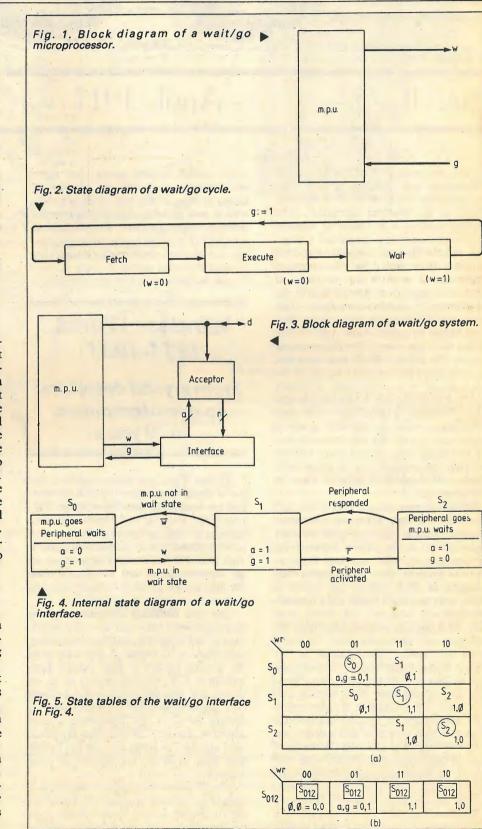Signal g: A signal transition from 0 to 1 on this terminal (the go line) puts the microprocessor out of the wait state. Signal a: A signal transition from 0 to 1 on this line triggers the peripheral into action. Signal r: While the peripheral is responding r=0. When the peripheral has fully responded r changes to 1. No activation is possible when r=0.




WIRELESS WORLD APRIL 1981

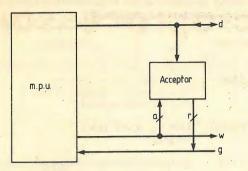

m.p.u.
signals
Wait/go
logic

▲ Fig. 6. The two-wire wait/go interface.

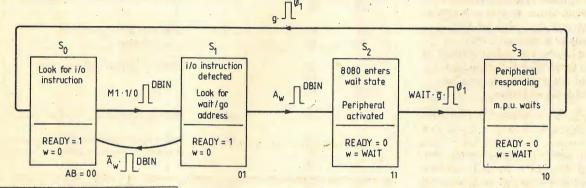▲ Fig. 7. Block diagram of the wait/go logic.



A suitable internal-state diagram of a circuit to implement the above interface is shown in Fig. 4. Applying the reduction steps to its equivalent state table in Fig. 5 (a) allows its three rows to merge into one, as shown in Fig. 5 (b).

By direct reference to the reduced state table, we obtain the following equations $a=wr+w\bar{r}+(\bar{w}\bar{r})=w$ $g=\bar{w}r+wr+(\bar{w}\bar{r})=r$

The corresponding circuit implementation consisting of two wires is shown in Fig. 6.

Advantages

Wait/go systems are:

Easy to understand. The 'wait' and 'go' are everyday concepts, not requiring specialist knowledge.

Easy to design. The hardware is straightforward and presents no difficulty. Specifically, in the case of action/status devices it consists of two wires.


Easy to implement – because of uncomplicated hardware.

Easy to program. Software overheads are minimal.

Easy to maintain — because of their reliability.

Wait/go logic

Although present-day microprocessors are not designed to operate in the wait/go mode, they can be made to do so by means of a relatively simple logic circuit, the wait/go logic, the block diagram of which is shown in Fig. 7. Its function is to look for i/o instructions with wait/go addresses, denoted by A_w , and to put the microprocessor automatically into a wait state when such an instruction is detected. At this point it passes exit control to the go terminal, that is to the outside world.

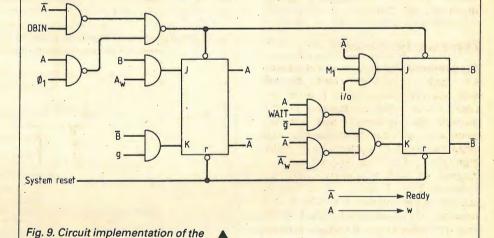

▲ Fig. 8. State diagram of the wait/go logic

The design and implementation of wait/go logic is straightforward, as we demonstrate by means of the following example.

Wait/go logic for the Intel 8080

wait/go logic for the Intel 8080.

The m.p.u. signals of the Intel 8080 were described in the first article (May 1980 issue). Reference to these signals shows that the op code and i/o address are loaded into the m.p.u. registers in timeslots M1·DBIN and the following DBIN respectively. It follows that we can identify an i/o instruction by simply determining whether the signals on the data bus in time slot M1·DBIN are 11010011 or not – 11011011 and 1101011 are the op codes for IN and OUT². Similarly, the wait/go addresses are identified by looking at the data bus with the following DBIN signal. A suitable state diagram is shown in Fig. 8.

By direct reference to it, we obtain $S_A = S1 \cdot A_w$ $= A \cdot B \cdot A_w$ therefore, $\mathcal{J}_A = B \cdot A_u$ $R_A = S3 \cdot g$ $= A \cdot \bar{B} \cdot g$ therefore, $K_A = \bar{B} \cdot g$ $S_B = S0 \cdot M1 \cdot I/0$ $= \bar{A} \cdot \bar{B} \cdot M1 \cdot I/0$ therefore, $\mathcal{J}_B = \overline{A} \cdot M1 \cdot I/0$ $R_B = S1 \cdot \overline{A}_w + S2 \cdot \text{WAIT} \cdot g$ = $A \cdot B \cdot \overline{A}_w + A \cdot B \cdot \text{WAIT} \cdot g$ therefore, $K_B = \overline{A} \cdot \overline{A}_w + A \cdot WAIT \cdot g$ $Clock = (S0+S1) \cdot DBIN + (S2+S3) \cdot \phi 1$ $=(\overline{A}\cdot\overline{B}+\overline{A}\cdot B)\cdot DBIN+(A\cdot$ $B+A\cdot \bar{B})\phi 1=\bar{A}\cdot DBIN$ $+A \cdot \phi 1$ Ready = S0+S1 $= \bar{A}\bar{B} + \bar{A}B = \bar{A}$ w = S2 + S3=AB+AB= A

The corresponding circuit implementation is shown in Fig. 9.

A design problem: PRINT

The problem is to design and implement a wait/go system that would allow the programmer to produce a hard copy of data, which is stored in consecutive memory locations.

Solution

As explained in the previous article the first three design steps are independent of the microprocessor and therefore common to both solutions.

Step 1: aim of the design. The aim of the design is to expose the reader to wait/go systems.

device characteristics. As Step 2: specified.

Step 3: system design. The block diagram of our solution is shown in Fig. 10. Its step-by-step operation is flowcharted in Fig. 11. As in the case of the test-and-skip solution described in the previous article, August issue.

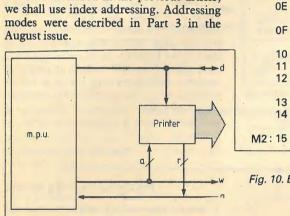


Table 1: Hex listing of the PRINT problem when implemented using the wait/go mode and the Motorola 6800.

Hex address	Hex listing	Mnemonics	Comments
0300 01 02	CE 20 40	LDX	Load index register with line 40 on page 20 — location of the first byte to be printed.
03 04	86 n	LDAA	Load acc. A with block length (n)
05 06 07	97 20 10	STAA	Copy acc. A (n) into memory location (line 10 on page 20) to be used as a counter
M1: 08 09	27 0B	BEQ	Branch to M2, if n=0 – forward 11
OA OB	A6 00	LDAA	Copy into acc. B next byte to be printed
OC OD OE	B7 10 0D	STAA	PRINT – printer address 1000
0F	08	INX	Point to next byte
10 11 12	7A 20 10	DEC	Decrement byte count (held) in memory location 2010)
13 14	20 F3	BRA	Branch to M1 - back 13
M2:15	3E	WA1	Stop

Fig. 10. Block diagram of the PRINT problem.


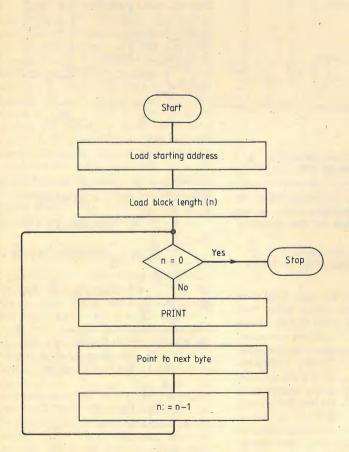



Fig. 11. Step-by-step operation of a wait/go system used to PRINT.

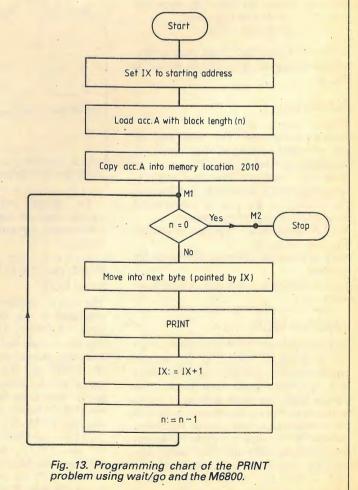

n := n - 12010 2039 20 40 LXI First byte (B7) (A6) Second byte Offset Last byte (=0)

Fig. 12. Programming model for the PRINT problem using the M6800.

WIRELESS WORLD APRIL 1981

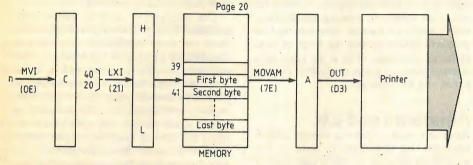

MEMORY

Fig. 14. Programming model for the PRINT problem using the Intel 8080.

Table 2: Hex listing of the PRINT problem when implemented using the wait/go mode and the Intel 8080.

He	ex Idress	Hex listing	Mnemonics	Comments
	1000 01 02	21 40 20	LX1 HL	Set memory pointer to line 40 on page 20 — location of the first byte to be printed
	03 04	0E n	MV1 C	Load register C with block length (n)
	05	0C	INRC	Increment C-sets flags
	L2: 06	0D	DCRC	Decrement C
	07 08 09	CA 11 10	JZ	Jump to L1, if $n = 0$ — that is if the zero flag is set
	0A	7E .	MOV A,M	Move into A next byte to be printed
	0B 0C	D3 06	OUT	PRINT
	0D	23	INXH	Point to next byte in the block
	0E 0F 10	C3 06 10	JMP	Go to L2
	L1:11	76	HLT	Stop

Demetrius Zissos is Professor of Computer Science and Adjunct Professor of Electrical Engineering at the University of Calgary, Canada. Educated in Britain, he has been associated with industry on both sides of the Atlantic for the past twenty years. He has written five books and numerous articles, including a series (with Brian Holdsworth) on logic design in Wireless World. He is currently writing two further books, one on logic design and the other on distributed systems.



6800 Solution

Step 4: hardware design. No interface hardware is required.

Step 5: software design. Our programming model and programming flowchart are shown in Figs. 12 and 13. Memory location 10 on page 20 is used as a counter and the first byte is stored in line 40 of the same page. Note that the programming model is the same as the one used for testand-skip systems.

By direct reference to our programming model and to the M6800 instruction set³. reproduced in Part 4 (September issue), we obtain the hex listing of our wait/go software - see Table 1.

8080 Solution

Step 4: hardware design. As in the case of the 6800, no hardware is required.

Step 5: software design. Our programming model in the case of the Intel 8080 and programming flowchart are shown in Figs. 14 and 15. An m.p.u. register is assumed to be available for use as a counter. The first byte is stored in line 40 of page 20 in memory.

By direct reference to our programming model in Fig. 10 and to the Intel 8080's instruction set reproduced in the prévious article, we derive the hex listing of our wait/go software. It is shown in Table 2.

References

1. Zissos, D., "System Design with Microprocessors", Academic Press, 1980.

2. Intel 8080 Microprocessor User's Manual, September 1975.

3. M6800 Microprocessor User's Manual, Motorola, 1976.

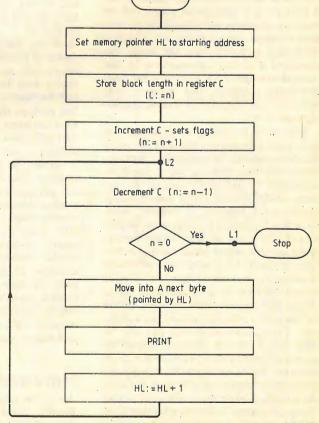


Fig. 15. Programming chart of the PRINT problem using wait/go and the Intel 8080.

WORLD OF AMATEUR RADIO

The earth-less vertical

In one of his series of classic papers on transmitting aerials, Dr George Brown of RCA (Proc IRE, June 1937) analysed the efficiency of monopole radiators in terms of their use with 0.4\(\lambda\) buried radials, showing that typically an efficiency of up to 88 per cent can be achieved with 113 radials, reducing to only 12.4 per cent with just two radials. It is on this work that amateur use of the popular "ground plane" and "vertical" aerials has largely been based for over 40 years, while the standard medium-wave broadcast aerial still tends to use 72, 120 or even 144 radials buried a couple of feet below the surface of the earth by means of mole ploughs, resulting in radiation efficiencies of the order of 75 to 90 per cent. More and more, in recent years, amateurs using verticals on 7MHz and below have been persuaded that an extensive earthing system or "mat" is a vital essential. Since such an earthing system cannot be fitted into the average garden, the h.f. monopole is generally accepted as not providing the sort of performance at long-distances of which it should be theoretically capable.

Recently, Leslie Moxon, G6XN, who has built up a considerable reputation for tilting at the many myths that are part of the "aerial lore" of many amateurs (and professionals), has been investigating what one could call the "cult of the radial" to see if effective h.f. directional arrays can be based on quarter-wave radiators at ground level without the use of any physical connection to earth. In doing so he has paralleled a similar investigation by the Australian amateur VK3AM who has been developing compact but efficient h.f. aerials for use in confined spaces, including small boats.

This work is tending to show that, in fact, good efficiency is possible by using the once-popular "counterpoise" arrangement, but that this can be successfully shortened by inductive loading. In one form, G6XN is using with a base-insulated quarter-wave radiator, a 14MHz counterpoise a few inches above ground, consisting of a 7ft length of dural tubing parallel to the ground, with a linear loading inductance of about 11ft of wire. Such monopole (or dipole?) elements can be readily used as driven elements or as reflectors or directors (a two-element array however should be based on a reflector rather than a director). The counterpoise rods can also be used effectively to increase capacitive coupling between the array elements. Such elements can be easily moved to prepared positions to change the direction of fire of the array and taken down when not in use. The performance of an array formed from such elements would appear to be equivalent to those of a similar array using an extensive earth mat, although, as might be expected, a little inferior to an equivalent horizontal array at moderate height. The vertical array, however, has many advantages of cost and convenience since it requires no tower, no rotating mechanisms and is not a permanent structure and so presumably falls outside the scope of local authority planning, while at the same time offering plenty of scope for further investigation and development.

More and more it looks as though British

amateurs will soon have to learn to live

with, even if some of them may find it

difficult to love, c.b. or Open Channel on

frequencies additional to the proposed

Amateurs and c.b.

928MHz. Indeed by the time these notes appear the die may well have been cast, although the package is likely to be so wrapped as to absolve the Home Office from any suggestion that they have been forced into making a "U-turn". But it is much to be hoped that amateurs will not allow themselves to be provoked into open hostility. Some of the common complaints made by some amateurs against c.b. could easily be represented as "sour grapes". For example, that amateurs always have to pay for licences, pass examinations, adhere to tight regulations, keep accurate logs etc, etc, so why should so many people have been allowed to "get away" with 27MHz operation? . . . and that sort of thing. But there are other, more seriously abrasive, causes of friction. Amateurs fear they will have to take the blame for interference and abuses since the media often fail to distinguish between c.b. operators and "hams". But perhaps the most serious problem of all is that many of the thousands of 27MHz c.b. units now being used in the UK will operate - and indeed often are operated - within the internationally "exclusive" amateur band 28 to 29.7MHz. Since most c.b. units are channelised it is possible that some of this intrusion is accidental, though in other cases it appears to be quite deliberate. Since the c.b. operators make no attempt to abide by "band-planning" or similar conventions, amateurs in many countries are seeing a virtual take-over of parts of their band. Unlike the radio control modellers they are not being offered alternative frequencies! C.b. enthusiasts would be well advised to play it cool and not stray above 28MHz.

Here and there

Australian amateurs are now permitted to handle "third party traffic" subject to three main exceptions. International traffic

must be only with countries that themselves permit such message handling; there must be no question of payment or material compensation, either tangible or intangible, direct or indirect; and no business traffic must be involved.

The problems of electromagnetic compatibility become ever more complex as more and more interference-producing or interference-susceptible electronics comes into use: interference from and to home computers and microprocessor-based appliances; automobile electronics; switchedmode power units (even the common or garden diode rectifier can emit hash); virmally all forms of electronics for entertainment or business. American amateurs are reporting yet another growing problem: transmitters causing false triggering of "smoke detector" alarms The r.f. can be mains-borne and gets into the detector units unless protected by suitable r.f. bypassing. This requires care if the capacitors are not to interfere with the operation of the units.

An increasing problem for mobile operators, particularly since the public interest in c.b., has been the widespread theft of radio equipment from unattended vehicles. Most weeks, amateurs report the loss of several expensive transceivers (presumably when 27MHz units are stolen the illegal operators are reluctant to report the loss to the police). Recently, the West London 144 MHz repeater equipment of the UK FM Group was stolen and the Group has since taken out insurance on its other repeaters.

In brief

The G-QRP club, founded in 1975 to encourage interest in low-power operation, now has more than 1000 members in 24 countries, including over 200 in the USA the traditional home of the "Californian Kilowatt".... The Radio Amateurs Invalid and Blind Club now has a membership of over 600, including more than 300 licensed amateurs PY2AA is the callsign of a new 50.055MHz beacon transmitter, with 25 watts power, located at Sao Paulo, Brazil. A South African multi-band beacon, ZS5VHF transmits on 28.2025, 50.005 and 144.925 MHz, the 28 MHz signals have been received well in the U.K.... The British Amateur Television Club has just published an all-new "Amateur Television Handbook" with over 100 pages devoted to practical and up-to-date designs of amateur television equipment (Non-members £1.50 plus 35p postage from BATC Publications, 14 Lilac Avenue, Leicester LE5 1FN.).

PAT HAWKER, G3VA

Introduction to low-noise amplifier design

How to optimize collector current and calculate noise figure

by A. Foord

Many constructors still settle for more noise in their amplifiers than necessary because of the complexity of a full mathematical treatment and because manufacturers often fail to specify their transistor parameters in a convenient form. This article shows how to calculate the optimum collector current for a given source resistance and the minimum noise figure at that current, and gives practical circuits for instrumentation use and sound reproduction.

WIRELESS WORLD APRIL 1981

Once the basic design requirement of optimum collector current has been satisfied, the remaining amplifier parameters can be determined from the normal design relationships. For example, as the noise figure is independent of the transistor configuration and overall feedback, the usual feedback pair arrangements are practicable. Therefore the transistor and its operating point can be selected to meet the circuit noise requirements and the configuration or feedback can be determined to meet gain, bandwidth and impedance requirements. This approach allows the noise and other circuit constraints to be optimized independently.

The selection of a suitable input device depends mainly on the source resistance and bandwidth requirements. At the lowest values of source resistance it is necessary to use transformer coupling at the input to match the source resistance to the optimum for the amplifier, Fig. 1. Unfortunately transformers introduce extra losses and degrade the basic noise figure of the amplifier. For example, an amplifier designed for a 5kohm source might have a noise figure of less than 1dB. When matched with a transformer to a 30 ohms dynamic microphone this noise figure could be degraded to 2.7dB.

If integrated circuits are used their parameters are well specified by the manufacturer, but their noise levels are in general about two to five times that of a discrete transistor circuit. This makes them more suitable as second and succeeding stages. Fortunately bipolar transistors can be used for most audio front-end applications and this article is restricted to their

There is a slight difference between p-np and n-p-n transistors. A p-n-p transistor can have a lower base spreading resistance due to a higher carrier mobility in its base

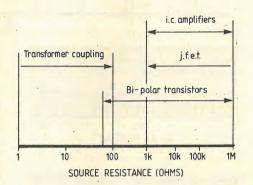


Fig. 1. Choice of input amplifying device depends on source resistance.

region, while an n-p-n transistor often has a slightly larger current gain and bandwidth. This makes the p-n-p type more useful with low source resistances, with the n-p-n transistor useful at the higher end of the resistance range. For this reason, and also for direct coupled circuits, it is desirable to have information on a range of p-n-p and n-p-n devices.

A table of suitable low-noise transistors and their parameters is shown in Table 1. These are measured values and may not agree with those obtained from the manufacturers' specification sheets. Details of

some low-noise i.cs are included for comparison.

Some noise mechanisms are process-dependent and result from faults such as surface defects, surface contamination, defective contacts, impurities, dislocations, and irregularities at the base-emitter junction. For this reason transistors with the same type number may vary from maker to maker. This is particularly true for low frequency noise below 1kHz where poor processing techniques become more apparent.

Any source unavoidably generates an amount of thermal noise power which depends on its temperature, Boltzmann's constant, and the system's noise bandwidth. Noise factor, as a ratio, is defined as

total available output noise power portion of output power caused by source only

Noise figure is simply this noise factor expressed in decibels. NF =

total available output noise power

or $NF = 10 \log F$. The noise figure is a measure of the signal-to-noise degradation attributed to the amplifier. For a perfect

Table 1. Measured values of low-noise device parameters may not agree with manufacturers data

				at I _c o 100μΑ		(Ω)	Application
2N930	n-p-n	-1	300	200	130	700	High source resistance
2N4124	n-p-n		300	200	110	100	Low source resistance
BC109	n-p-n		350	300	200	400	General purpose
2N3707	n-p-n		350	250	200	200	General purpose
2N4403	p-n-p		200	140	80	40	Low source resistance
2N4125	p-n-p		150	120	90	50	Low source resistance
2N3964	p-n-p		350	310	260	150	Low broadband noise
2N4250	p-n-p		350	310	260	150	Low broadband noise

IC type	V _n (nV/Hz ^{1/2})	I _n (pA/Hz ^{1/2})	R _s (kΩ)	f (Hz)	NF at R _s (dB)
TDA1034N	9.0	3.0	3.00	10	6.41
	3.5	0.4	8.75	1k	0.70
RM4739	20.0	4.0	5.00	10	10.41
	10.0	0.5	20.00	1k	2.11
_M201A	22.0	0.74	29.73	10	4.82
and the second second	16.0	0.20	80.00	1k	1.46
OP10EY	10.3	0.32	32.19	10	1.50
	9.6	0.12	80.00	1k	0.58
AD517	35.0	0.05	700	10	0.86
	20.0	0.03	667	1k	0.31
ZN460	0.8	1.0	0.800	5k	0.41

amplifier, one which adds no extra noise to the thermal noise of the source, the noise factor is unity, and the noise figure zero. Usually there is not a great deal of value in reducing the noise figure much below 3dB. A noise figure of 3dB is equivalent to saying that the amplifier and source are contributing an equal amount of noise to the wanted signal. Even if the amplifier noise could be reduced to 0.1 of the source noise, the total system noise is now about 0.7 of the 3dB condition. However it must be remembered that an amplifier with a noise figure of 0.5dB at 1kHz with a source resistance of $5k\Omega$ will have a higher figure at low frequencies and at source resistances away from the optimum.

The normal procedure is to design the amplifier for a minimum noise figure at the desired source resistance. The optimum collector current for the transistor depends on the driving source resistance R_s and the direct current gain β .

Optimum collector current

$$I_{\rm c} = \frac{(\beta)^{1/2}}{40R_{\rm s}}$$

For example, determine the optimum current for a 2N4403 transistor with a source resistance of 400 ohms. Initially β can be taken as 200.

$$I_{\rm c} = \frac{(200)^{1/2}}{40 \times 400} = 0.88 \,\mathrm{mA}.$$

As shown in Table 1 a β of 200 at 0.88mA is possible. If the formula had given a much lower optimum collector current, say 50 μ A, then the β would have to be reduced to about 100 and the optimum collector current recalculated. This procedure is repeated if necessary until the β is believable for the calculated collector current.

The procedure is not too critical because of the wide variations in β between one transistor and the next and because the optimum collector current is proportional to the square root of β .

The minimum noise factor F at the optimum collector current can be calculated from the source resistance R_s , the current gain β , and the intrinsic base spreading resistance $r_{bb'}$

$$F=1+\frac{r_{bb}}{R_s}+\left(\frac{1}{\beta}\right)^{\frac{1}{2}}$$


For the conditions previously discussed for the 2N4403 transistor

$$F = 1 + \frac{40}{400} + \left(\frac{1}{200}\right)^{1/2} = 1.17 \text{ times}$$

Then the minimum noise figure is $NF=10 \log F=10 \log 1.17=0.68 dB$.

Microphone preamplifier example

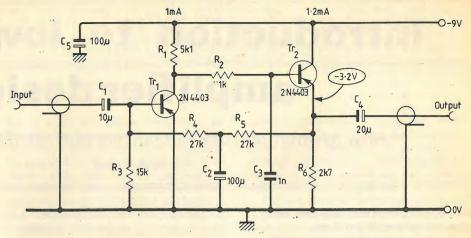Many dynamic microphones have impedances of 200 or 600 ohms. The previous examples suggest that a 2N4403 transistor run at a collector current of about 1mA could be used for this application, and a suitable circuit is shown in Fig. 2.



2-10 H SION 100 1k SOURCE RESISTANCE

Fig. 3. Noise figure plotted against source resistance for the microphone preamplifier (top), and against frequency (bottom).

Fig. 2. Instrumentation preamplifier is

suitable for microphone use.

SOURCE RESISTANCE

SOURCE RESIST

A common-emitter amplifier is followed by an emitter follower. The dc conditions are determined by the bias chain from Tr₂ emitter to Tr₁ base, but this does not provide negative feedback at signal frequencies because of C₂. The low frequency response is determined mainly by the input and output coupling capacitors at 10Hz, while the high frequency response is determined by C₃ at 26kHz. If C₃ is not included the high frequency response would extend to 1MHz, which is undesirable.

The first transistor is essentially an unloaded common-emitter stage, and its gain at room temperature is

$$\frac{V_o}{V_i} \approx 40R_1I_c = 204$$
 times or 46dB.

Measured results on two amplifiers gave gains within 1dB of the calculated value. The input resistance was 2.7k ohms. As

Table 2. Comparison of several transistors for a 6kohm source.

β	Ι _c (μΑ)	r _{bb} ' (Ω)	F	NF
150	51	700	1.198	0.79
150	51	100	1.098	0.41
250	65.9	400	1.130	0.53
220	61.8	200	1.101	0.42
100	41.7	40	1.107	0.44
100	41.7	50	1.108	0.45
280	69.7	150	1.085	0.35
280	69.7	150	1.085	0.35
	150 150 250 220 100 100 280	(μA) 150 51 150 51 250 65.9 220 61.8 100 41.7 100 41.7 280 69.7	(μA) (Ω) 150 51 700 150 51 100 250 65.9 400 220 61.8 200 100 41.7 40 100 41.7 50 280 69.7 150	(μA) (Ω) 150 51 700 1.198 150 51 100 1.098 250 65.9 400 1.130 220 61.8 200 1.101 100 41.7 40 1.107 100 41.7 50 1.108 280 69.7 150 1.085

Tr₁ has a high gain the noise contribution by Tr₂ is negligible. Fig. 3 shows the noise figure plotted against the source resistance, while Fig. 4 shows the noise figure plotted against frequency for a fixed source resistance; in this case the non-optimum value of 50 ohms.


These results confirm the theory, and show that the 2N4403 transistor is particularly suitable for both low source resistances and low frequency applications where noise is important.

Measurements on several 2N4403 transistors suggested that about one quarter of them had excess noise at low frequencies, but mid-frequency results were consistently low. For critical applications the amplifier input should be terminated with a 390-ohm wirewound resistor and Tr₁ selected for a minimum amount of noise. This noise can be measured at the output of the amplifier chain with an oscilloscope or a.c. voltmeter. An oscilloscope is particularly valuable because any low frequency or burst noise can be observed. If the preamp does not dominate the noise generated from succeeding stages (with the gain control at a maximum) then these stages need to be examined!

The full design of a general-purpose audio preamplifier can be quite a problem, and a magnetic pickup may be the most difficult source to match. Its impedance rises with frequency, the amplifier has an equalization curve which gives 20dB boost below 50Hz and 20dB cut at 20kHz, and the basic amplifier noise may be increasing at low frequencies.

The theoretically correct approach is to allow for all these factors and design for the lowest total noise over the complete audio bandwidth. This really demands an exact model for the circuit and a good computer program. In practice a reasonable answer can be obtained by designing for a source impedance of about 6k ohm.

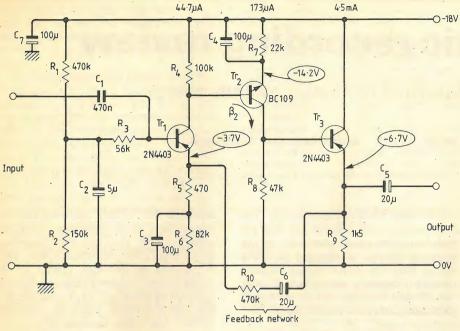In Table 2 several transistors are compared for this source impedance. All of these transistors appear to be suitable,



apart from the 2N930. The 2N4403 transistor has been chosen for the practical circuit, and the examples.

WIRELESS WORLD APRIL 1981

$$I_c = \frac{(\beta)^{1/2}}{40R_s} = \frac{(100)^{1/2}}{40 \times 6 \times 10^3} = 41.7 \mu A$$

$$F = 1 + \frac{40}{6000} + \left(\frac{1}{100}\right)^{\frac{1}{2}} = 1.107$$

$$NF = 10 \log 1.107 = 0.44 dB$$

One practical circuit might be similar to that shown in Fig. 5, where two commonemitter stages are followed by a common collector stage to drive the feedback network and the next stage. When Tr₁ is biased from a potential divider as shown, the only bias component which contributes noise is R₃. The actual voltage drop across R₃ is small and therefore any excess noise generated by the resistor, due to the current flowing through it, is also small. The amount of thermal noise it generates is attenuated by the source. The value shown will provide the load resistance required for most magnetic cartridges, and can be shunted if necessary for other inputs.


The approximate open-loop gain for this type of circuit is


$$\frac{\beta_2 R_8}{R_5 + \frac{1}{40I_{c1}}} = \frac{320 \times 47 \times 10^3}{470 + \frac{1}{40 \times 44.7 \times 10^{-6}}}$$
$$= 14,600 \text{ times} = 83 \text{dB}.$$

A practical measurement of this circuit gave an open-loop gain of 80dB, which is perhaps more realistic.

Unlike the first circuit, where the gain was well defined by the collector current, the gain of this circuit depends on the β of the second transistor. Overall negative feedback is therefore essential to accurately define the closed-loop gain. In Fig. 5 the closed-loop gain is 60dB and the frequency response is 3dB down at 8Hz and 45kHz.

Fig. 4. Preamplifier as shown has flat frequency response; for use with magnetic pick-up replace feedback network with appropriate equalization network. Author recommends metal film or metal oxide resistors, as wirewound ones are bulky and expensive. Tantalum electrolytics are preferred over aluminium because of their lower leakage.

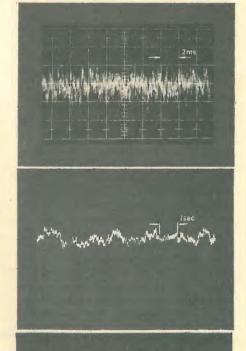

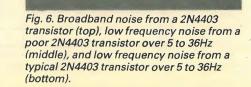

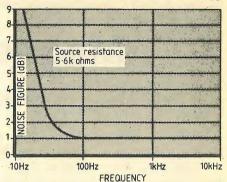


Fig. 5. Noise figure plotted against frequency for the general-purpose preamplifier of Fig. 4.

The closed-loop gain is defined at

$$G=1+\frac{R_{10}}{R_5}$$
times.

Resistor 5 is required so that the closedloop gain can be defined by overall negative feedback. It also provides series local feedback for Tr₁ and reduces the openloop gain by about 7dB. However the open-loop gain of 80dB which was measured is adequate to provide a reasonable amount of feedback at low frequencies even though the equalization curve demands a 20dB gain boost (below 50Hz) above the mid-band gain. The value of R5 cannot be made too low as this will force a reduction in the feedback impedance, reducing the available output voltage swing at high frequencies where the equalization curve falls at 6dB per octave.

Although negative feedback does not alter the amplifier's noise figure, R₅ is effectively in series with the source and can contribute an amount of thermal noise, the effect of which depends on the source resistance. It should be made much smaller than the source resistance. Noise factor with R₅ is

$$F_r = F + \frac{R_5}{R}$$
.

In the example

$$F_{\rm r}=1.107+\frac{470}{6000}=1.185$$
 times

thus
$$NF_r = 10 \log 1.185 = 0.74 \text{dB}$$
.

Although this appears to be a significant degradation the resultant noise figure is still less than the 3dB level considered to be a reasonable value. It does indicate why an approach like Fig. 2 is valuable for critical applications, because the gain can be closely determined by the circuit parameters without using emitter degradation.

Further reading

Low-noise Electronic Design, by C. D. Motchenbacher and F. C. Fitchen (Wiley, 1973) gives many practical examples which are fully specified in terms of gain, bandwidth, and noise for up to four different values of passive compo-

Magnetic recording review

2 - Performance of modern cassette tapes

by J. Moir, F.I.E.E., James Moir and Associates

Mr Moir continues his survey of magnetic recording technology and materials with an examination of modern cassette tapes. A brief look at possible future developments concludes the article.

Equalization

The limited frequency response of the early ferric coated tapes led to the extensive use of electronic equalization, a shaping of the frequency response of the record and replay amplifiers to improve both the frequency response and the s/n ratio. The correction required to achieve a flat overall record/replay response was divided between the record and replay system in a way that eliminated the need for variable equalization in the user's equipment. Standard replay calibration tapes were produced, having a closely specified response curve, and the recording engineer, having equalized his replay equipment to ensure that these standard tapes played with a flat frequency response, was required to vary the equalization of his recording system until the overall record/replay system response gave the same flat overall response.

However, the performance of tape coatings and our knowledge of record and replay head design has so far improved that the equalization originally specified is not only unnecessary but actually degrades the achieved performance of many of the recent types of tape.

The equalization to be applied to the system was specified indirectly as the relation between the signal voltage at the input of the recording chain and the resultant surface induction (now the short-circuit flux) on the tape. It was defined as the combination of two curves, one being the response of an RC circuit with a time constant of 1590 microseconds, defining the low-frequency performance, and a second RC circuit with a time constant of 120 microseconds defining the performance at frequencies above about 800Hz. The combined frequency response can be read from

Table 1: Standard time constants

Tape Speeds	Time Constant			
7	t ₁	t ₂		
76.2 cm/s (30in/sec) and 38.1 cm/s (15in/sec)	35	Infinity		
19.05 cm/s (7½in/sec)	70	Infinity		
9.53 cm/s (33/4in/sec)	90	3 180		
4.76 cm/s (17/sin/sec)	120	1 590		


Fig. 9, using the appropriate curves. The low-frequency signal is boosted and the high-frequency signal attenuated in the recording process to minimize distortion arising from the limited signal handling capacity of magnetic tape at high frequencies. Table 1 provides data on the agreed correction curves for all the current standard tape speeds.

To obtain a flat overall record/replay response, the replay chain must have the inverse response, but to achieve this some additional high-frequency equalization must be included to compensate for the high-frequency losses in the replay head.

The standard replay calibration tapes are recorded with a carefully calibrated, surface short-circuit flux/frequency relation that follows the specified recording curve. When these tapes are used to obtain a flat replay system frequency response the losses in the replay system are automatically corrected and the desired flat response is obtained for the whole record/replay chain.

During the few years following the standardizing of the 120µs equalization, the high-frequency signal-handling capacity of

Fig. 9. Recording characteristics (BS1568)

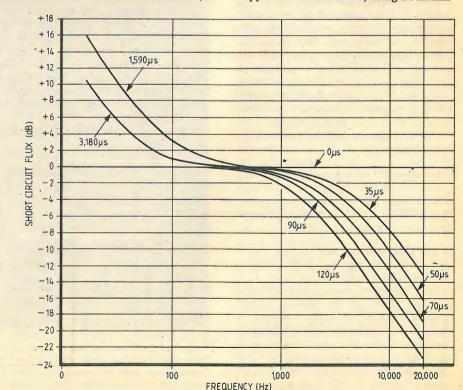

tapes has been greatly improved and designers have taken advantage of this by changing the recommended recording equalization time from 120µs to 70µs. This necessitates an equivalent change in the replay system frequency response, usually achieved by providing two or three alternative switch-selected frequency response curves. The 120µs equalization curve is used for all the ferric tapes and some of the early chromium and cobalt modified tapes, the 70µs equalization curve being employed with the later chromium and pure

Current semi-professional machines and the better domestic units now provide both bias and equalization adjustment, generally using separate controls. Used with understanding, this ensures near-optimum performance with most tapes. Professional and semi-professional machines usually provide a step-less control of bias.

Current tapes

At this point it appears appropriate to change from outlining simple theory to looking at some examples of current practice in tape production. About 100 samples of current cassette tapes from 25 suppliers were examined, using a Nakami**WIRELESS WORLD APRIL 1981**

chi 582 discrete-head machine, which is a good modern machine, with facilities for bias and equalization adjustment, and which is capable of handling metal tapes without saturating the recording head

The bias settings were chosen using the Nakamichi facilities for equalizing the signal outputs at frequencies of 400Hz and 15kHz and with the equalization set to 120µs for the ferric tapes and 70µs for the ferrichrome, chromium dioxide and metal tapes. The bias settings are quoted in dB with respect to the appropriate DIN reference tape, but since there are as yet no metal reference tapes, the bias setting employed for these tests are quoted with reference to the Nakamichi metal tape.

The data for all the examples of each type of tape coating are averaged and these are the values in Table 2. The limits given in the 'Frequency Response' column should only be taken as being generally indicative of the results, the complete curves being used for any more detailed comparison.

The advantage possessed by the metalparticle tape of high saturation values at high frequencies is not immediately obvious from the data in the Table, being masked by the reduction of the high-frequency replay pre-emphasis from 120µs to 70µs. The higher levels of high-frequency signals that the metal tapes accept allows a reduction in the high-frequency attenuation of the standard recording amplifier and this in turn necessitates a reduction in the replay-amplifier high-frequency boost, with a corresponding improvement in the overall signal/noise ratio.

Typical response curves are provided for each type of tape in Fig. 10. Five separate bias levels are needed to enable optimum performance from every type of tape. However, the person who buys budget and 'special offer' tapes is unlikely to be interested in paying for a wide range of bias adjustment on his machine, so three levels of bias are probably adequate for the majority. Few of the cheap machines provide bias adjustments so the best performance is likely to be secured from the simple

The penalty for buying 'special offer' and 'advertisement-by-postal circular' types of tape is illustrated by the frequency. response of Fig. 11. This is measured fre-

Table 2: Typical performance characteristics of cassette tapes

	Bias level	333Hz MOL	Sensit.	10kHz sat.	Noise (CCIR/ARM)	Print through	Freq. Resp. 10kHz-10dB (n.b. see also Fig. 10)
Budget quality Ferric tape	+0.39	+1.98	-1.38	-5.86	-50.65	-55.1	-1.65dB
Good quality Ferric tape	+1.26	+5.14	+0.03	-4.14	-50.76	-53	-1.34dB
FeCr tapes @ ** Cr0 ₂ *	+3.13	+7.3	-0.7	-6.38	-54.75	-49.5	-3.53dB
pseudo-chromes Metal tapes*	+6.33 +11.3	+5.09 +6.82	+0.67 +0.6	-6.12 -3.56	-54.32 -54.48	-47.85 -56.56	-0.83dB -0.2dB

FeCr, Cr02 and metal tapes all tested with 70us equalization. Ferric tapes tested with

- Cr02 sensitivity quoted with respect to DIN Cr02 sensitivity on optimum bias setting
- FeCr sensitivity quoted with respect to DIN Fe sensitivity.
- Metal sensitivity quoted with respect to Nakamichi ZX metal tape. 4. @ Equalization problem on Nakamichi with FeCr tapes.
- All figures guoted with respect to Dolby level unless otherwise stated.
- From an initial inspection of the Table it would appear that the high-frequency saturation level of metal tapes is little better than that of good-quality ferric tapes. However, the tests carried out on the metal tapes were with 70µs equalization whilst those in the ferric tapes were done using 120µs equalization. In absolute terms, the performance of the metal tape in this respect is at least 4dB better than the ferric tapes but, because the manufacturers have chosen to use a different equalization arrangement, the benefits of improved high-frequency saturation are not realized by the user. As far as the average user is concerned, the main advantage of using a metal

tape would be an improvement of 4dB in background noise level.

quency response of a tape widely advertised under the name of, but having no connexion with, a very well known company. Not all such budget tapes are equally, bad, however, and some of the very cheap ferric tapes may well be perfectly satisfactory in a machine bought for a youngster. At an intermediate price level. many own-name tapes from Boots and other well known multiple stores are excellent value for money.

The ferrichrome, two-layer tapes produced an unexpected response curve with a 'step' of about 4dB at frequencies in the region of 2kHz, presumably due to the magnetic discontinuity at the boundary between the chromium dioxide and ferric layers. This step would appear to require a special equalization curve to achieve the optimum performance.

With the bias optimized as described for

each type of tape, the metal tapes are seen to have the highest m.o.l. at 330Hz, the highest saturation level at 10kHz, the lowest noise level and currently the highest price, but note the qualification about optimizing the bias. A less well appreciated limitation to the use of metal tapes and even some of the Cr02 tapes is the inability of many machines to fully modulate the tape at high frequencies, head design and circuit limitations being the apparent

The performance of metal tapes used in machines incapable of providing the optimum bias is generally much worse than that of an intrinsically inferior ferric or ferric-chrome tape.

Some comment about the material employed for the tape base is probably interesting. The original tapes were all pvcbased, but in recent years tensilized poly-

Fig. 10. Typical frequency response curves


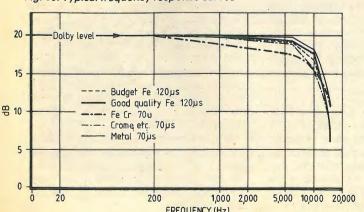


Fig. 11. Cheap tape performance

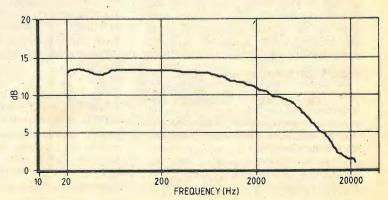

ester has captured the market because of its superior mechanical properties and its relative freedom from the effects of humidity. Polyester has only a slightly greater tensile strength than pvc tapes, but is some eight times less susceptible to the effects of moisture, a great advantage in ensuring good spooling with a freedom from 'cupping' and variation in the tightness of wind. The pvc base is rather smoother than the polyester base but not significantly so. A smooth base is advantageous in reducing noise modulation effects' due to the variation in coating thickness that results from changes in the thickness of the backing tape.

The nominal thickness of the tapes varies somewhat between suppliers but bases about 18µm, 12µm and 6µm thick are usually used for the three common lengths of tape, the C60, C90 and C120 types, the coating thickness being around 6, 4 and 3µm respectively. The C90 size tape is probably the best compromise between playing time and tape strength, the C120 type requiring more care in handling and gentler treatment in machines than is usual.

The use of a thick tape base has the obvious disadvantage of reducing the amount of tape that can be stored in a cassette or on an open spool, but it has advantages in reducing 'print through', the transfer of signals from one layer of tape to adjacent layers. These result in pre and post echoes that are obvious when they occur in the middle of quiet passages. The transfer is accelerated by storage of the tape in a warm environment and by longterm storage without replaying. Some tape coatings are more susceptible to the trouble than others, probably because of their increased temperature dependence.

The future

It is interesting to consider possible further improvements. The cassette format is here to stay, for its convenience clearly outweighs the residual deficiencies in performance. Its mechanical performance is not perfect, but is probably commercially adequate. Tape jamming is rare but still occurs, so the mechanics will be improved in this respect.

Tape saturation at high frequencies produces amplitude compression and harmonic-type distortions that do not occur in reel-to-reel recorders running at higher speeds. There is, therefore, some opportunity for improvement, but in most other respects the performance of the existing coatings is more than adequate for the commercial market. This suggests that achieving the present performance or at least a commercially acceptable performance at half the present tape speed is likely to be the next step.

Development in tape coatings that have contributed so greatly to improvements in performance of the cassette format do not appear to be applicable to 1/4 in tape, or at least do not have the same advantages. Most of the limitations in coating performance are wavelength-dependent and not frequency-dependent effects. An adequate frequency response for all professional requirements can be secured from 1/4 in tape running at the present standard speeds and, in consequence, there appears to be no application for the new coatings in this

This situation does not hold for tapes used for tv and data recording, so the halfinch and wider tapes used for these applications are likely to benefit from coating developments that permit lower tape speeds.

Further reading
Daniel and Axon, The Reproduction Of Signals Recorded on Magnetic Tape, Part 3, May 1953. Axon, Overall Frequency Characteristic in Magnetic Recording, B.B.C. Quarterly, No. 5, Westmijze, W. K., Studies on Magnetic

Recording, Philips Research Laboratories Reprint R213-R214-R217-R222. (Originally in Philips Research Reports, Vol. 8, pp. 148-157, 161-183, 245-269, 343-366, 1953). Daniel, E., A Preliminary Analysis of Surface-Induced Tape Noise, IEEE Trans. on Comm, and Electr., V. 83, No. 72, May 1964. Daniel, Eric D., and P. E. Axon, Accidental Printing in Magnetic Recording, B.B.C. Quarterly, Vol. 5, pp. 241-253, 1950. Wallace, R. L., Reproduction of Magnetically Recorded Signals, Bell System Technical Journal, Vol. 30, Pt. 2, Oct 1951. Review of Progress in Recording Materials, IEEE Trans. on Magnetics. September 1978. Bate, G., Survey of Recent Advances in Magnetic Recording Materials, IEE Trans. on Magnetics, July 1978. British Standard 1568 Magnetic Tape Recording Equipment.

Dividing by fractions

continued from page 61

triangular in form, has a frequency of half the last component, that is 378Hz, and a peak-to-peak amplitude of 0.0055 of an input period or, for a s.c. input,

 $226 \text{ns} \times 0.0055 = 1.24 \text{ns}$

The final component is sketched in Fig. 6(c). The sequence A-B results in a phase error of -0.005T and B-C in an error of +0.006T. B-C has thus over-corrected for A-B by an amount of 0.006-0.005=0.001T. The sequence A-C is repeated by C-E, . . . etc and each time an additional error of 0.001T accumulates. This is repeated five times to point K, when the accumulated error reaches 0.005T. Since the sequence K-L is identical to that of A-B, a correction of -0.005T occurs, exactly eliminating the error. The steady accumulation of this error and its final elimination gives the jitter component seen in Fig. 6(c). It is nearly sawtooth in form, has a frequency of 68.75 Hz and a peak to peak amplitude of

$226 \times 0.005 = 1.13$ ns

It has already been mentioned that removal of these jitter components is done with a phase-locked loop. The count of the divider has been so arranged that the lowfrequency components of jitter are smallest in amplitude, as these are the most difficult to remove. If we set a specification of Ins on the jitter, then both the final two components require little attenuation. The 756.25Hz component is the most difficult as its frequency is relatively low and amplitude high. At this frequency, we require 41dB attenuation, and this can be readily achieved in the phase-locked loop shown in

The 111ns of jitter in a period of 65µs would give a p-p voltage perturbation of 7mV at the output of the phase comparator. For the moment ignoring any attenuation in the low pass filter, after the d.c. amplifier, 70mV jitter will appear at the input of the v.c.o. It can be shown that for a sawtooth variation at the input of a v.c.o. the output phase variation will be

delta $0 = \frac{1}{2} V K/f$

delta Ø=p-p phase deviation at the output V=p-p voltage deviation at the input f=frequency of sawtooth waveform K=sensitivity of the v.c.o. in Hz/volt.

If the sensitivity of the v.c.o. is 100Hz/volt, the output phase jitter will be delta $Q = \frac{1}{2} \times 0.07 \times 100/756$ =0.0046 of an output period

If the input frequency is SC, then the jitter will be 1.05ns. Thus, only a small amount of attenuation need be provided by the low-pass filter to meet specification.

The circuit of Fig. 7 was the one used in the laboratory. If, as in an s.p.g., twiceline or line frequency were being generated from SC (Fig. 2) a phase-locked loop with similar time constants could be used.

2.2 divider

Performing this division is far simpler than that of the previous section. The division is performed by dividing by 2 and 3 in the ratio of 4:1. By taking the output of the last flip-flop within the 7490 as in Fig. 8, we obtain a waveform which is low and high in the ratio of 4:1. This waveform is fed to the programming of the 9310, where it instructs a division of 2 and 3. The output then, as appearing on pin 15, has an average frequency of 2LF, if the input is 68.75kHz. The jitter components present at the output will be 68.75kHz/5, i.e. 13.75kHz. Recalling the jitter analysis done in section 3, it will be clear that this is above that which would cause jitter with the filter and v.c.o. chosen; even though its amplitude is high.

If a division from SC to LF is required, the circuit shown in Fig. 9 would be suitable. This may be preferred, as it avoids the need for an extra flip-flop. The jitter frequencies would be similar to those for the 2.2 divider.





WW - 035 FOR FURTHER DETAILS

SAW devices from Mullard.

Backed by many years of research and development at Philips Research Laboratories, surface acoustic wave devices are now available as production components. * RF front end and IF filters

*Oscillators * Delay lines * TV IF filters

Choose from a range of standard devices or let us make a customised design to your requirements.

For further details contact: Brian Buckingham ext 2679 or Jack McIlravey ext 2767.

MULLARD LIMITED, MULLARD HOUSE, TORRINGTON PLACE, LONDON WC1E 7HD. TELEPHONE: 01-580 6633. TELEX: 264341. Mullard manufacture and market electronic components under the Mullard, Philips and Signetics brands.

WW-065 FOR FURTHER DETAILS

Surface acoustic wave devices

2 - More on bandpass filters, delay lines and oscillators

by R. J. Murray and P. D. White Philips Research Laboratories

This second part gives fuller information on the specification, operation and performance trade-offs of bandpass filters, delay lines and oscillators.

Bandpass filters

There are two types of s.a.w. bandpass filters. The first is the transversal filter, which consists of two or more interdigital transducers (see "principles") and is a travelling wave structure. These filters are wideband, with bandwidths of 0.2% to 100% of centre frequency. Centre frequencies in the range 10MHz-500MHz are readily achievable with a projected upper limit in excess of 1.5GHz. Design procedures are similar to those used for digital filters. The second type of bandpass filter is the resonator kind, which consists of one or more i.d.t.s in a cavity formed by two surface wave reflectors. This structure supports a standing wave. Bandwidths of 0.01% to 1% of centre frequency are feasible, with centre frequencies currently in the range 50-500MHz and ultimately greater than 1.5GHz. Design procedures are similar to those of conventional LC filters.

Transversal filters. Fig. 7 (a) shows a s.a.w. transversal bandpass filter, which consists of two i.d.ts on a piezoelectric substrate. An electrical signal is fed into one transducer, converted to a surface acoustic wave, reconverted to electrical energy at the other i.d.t. and emerges as a filtered signal. An alternative structure is shown in Fig. 7 (b) which incorporates in the s.a.w. propagation path a multistrip coupler consisting of a series of parallel unconnected metal strips. This acts to transfer the surface wave from one track to another, providing discrimination against unwanted bulk waves which are also launched by i.d.ts.

If two i.d.ts have individual frequency responses $H_1(f)$ and $H_2(f)$, where f is the frequency, then the overall filter transfer function H(f) is given by:

$$H(f) = H_1(f) \cdot H_2^{\star}(f) e^{-j2\pi t}$$
 (1)

where $\tau = L/v_0$, L is the geometric centreto-centre separation of the i.d.ts, v is the s.a.w. velocity and * denotes complex conjugate.

The filter amplitude response A(f) is given

$$A(f) = |H_1(f)| \cdot |H_2(f)|$$
 (2)

and the phase $\theta(f)$ by:

$$\theta(f) = -2\pi f \tau + \tan^{-1} \left\{ \frac{\operatorname{Im}\{H_1(f) \cdot H_2^*(f)\}}{\operatorname{Re}\{H_1(f) \cdot H_2^*(f)\}} \right\} (3)$$

If $(H_1(f).H_2*(f))$ is wholly real or wholly imaginary, the phase variation $\theta(f)$ in equation (3) becomes a linear function of frequency. This generally desirable property may be achieved by making each of the i.d.ts symmetrical or antisymmetrical about its geometric centre. S.a.w. transversal filters are usually nonminimum phase filters. This means that the amplitude and phase responses may be designed virtually independently of each other. In particular a very precisely defined amplitude response (e.g. with steep sides, a flat or even equi-ripple passband and good stopband level) can be achieved whilst maintaining a linear phase response i.e. constant group delay, T. Typical delays are in the range 1 to 5µs.

In general, spurious signals will arrive at the output transducer with a different time delay from that of the main signal. These cause ripples in the amplitude, phase and

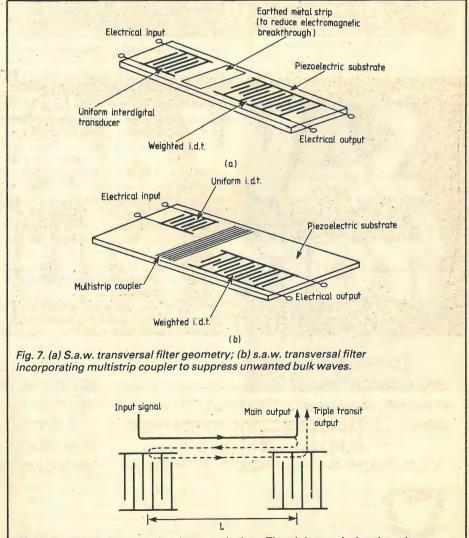


Fig. 8. Triple transit mechanism in s.a.w. devices. The triple transit signal results from successive electrical reflections from the output and input transducers before detection.

The most serious unwanted response is usually the triple transit signal which is illustrated in Fig. 8. This is caused by successive reflections from the output and input transducers before detection. If the main signal delay is τ , then the triple transit signal is delayed by 3τ i.e. 2τ more than the main signal. The period of ripples in the frequency response is thus $1/2\tau$.

The major contribution to the reflections which cause the triple transit signal is electrical and is a consequence of the three port structure of the i.d.t. The i.d.t. has two acoustic ports and one electrical port as shown in Fig. 9. When used for launching surface waves an electrical input

Acoustic O Acoustic

Fig. 9. Three-port nature of the interdigital transducer.

Electrical por

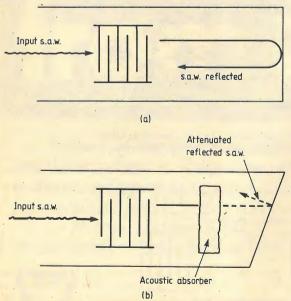


Fig. 10. (a) Spurious s.a.w. reflections from substrate end; (b) suppression of reflections from substrate end. These reflections cause distortion of the filter amplitude and phase responses.

signal causes acoustic signals to be launched at both of the acoustic ports. If the electrical port is perfectly matched then half of the available power is delivered to each acoustic port. Conversely, if surface waves are incident on one acoustic port with the electrical port perfectly matched then half of the energy is delivered at the electrical port and one quarter is delivered at each acoustic port. This, for a filter consisting of two perfectly matched (electrically) conventional i.d.ts, the minimum theoretical insertion loss is 6dB (never quite achievable in practice) and the triple transit signal is only 12dB below this level, which would result in an amplitude ripple of approximately 4dB peak-to-peak and a phase deviation from linear of approximately 25° peak-to-peak.

For most applications ripples of this magnitude are totally unacceptable. The simplest technique for reducing the triple transit signal, and the most widely used in practice, is to operate the filter with a mismatched source and/or load impedance. This increases the insertion loss but drastically reduces the level of the reflected signals. Using this technique a typical insertion loss is 20dB with peak-topeak ripples of less than 0.3dB in amplitude and less than 2° from linear in phase. Therefore, when a filter has been designed to operate with mismatched terminations it is important to remember that any attempt to improve the match and thereby reduce the filter insertion loss will cause increased amplitude and phase ripple. Other, more complicated, methods of suppressing triple transit responses are available for use in filters with particularly difficult specifica-

There are several other spurious signals in s.a.w. devices which can be substantially reduced by suitable design of the i.d.ts and substrate. Reflections from substrate ends are reduced by bevelling and applying acoustic absorber behind the i.d.ts as shown in Fig. 10. Reflections within i.d.ts are reduced by replacing each single electrode (a quarter of a wavelength wide) by a pair of like polarity 'double' electrodes (each an eighth of a wavelength wide) as in Fig. 11. Spurious bulk wave responses can be attenuated by the use of a track changing multistrip coupler on high coupling materials and/or by treatment of the lower surface of the substrate.

Resonator filters. A surface wave resonator consists of one or more i.d.ts suitably positioned in a cavity between two efficient reflectors of surface waves as shown in Fig. 12. Unlike the more familiar bulk acoustic waves employed in bulk wave resonators, surface waves cannot be efficiently reflected by an abrupt discontinuity (e.g. a substrate edge) because this would cause a significant proportion of the energy to be mode converted into bulk waves. S.a.w. reflectors consist of a large number of small impedance discontinuities in the form of metal strips or grooves spaced by half a wavelength. This results in bandpass reflectors with peak amplitude reflection coefficients of typically 99% or higher. The resonant cavity will generally be capable of supporting several standing waves, and the required mode is selected by careful design of the reflectors and the i.d.t.

The electrical equivalent circuit of a

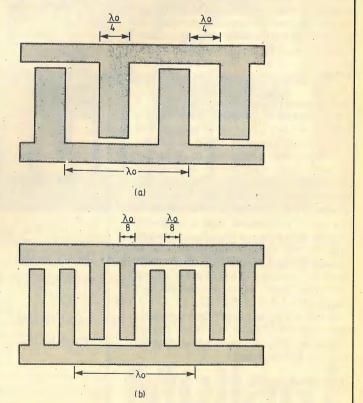


Fig. 11. (a) Conventional 'single electrode' interdigital transducer; (b) equivalent 'double finger' interdigital transducer used to suppress mechanical reflections.

one-port s.a.w. resonator is shown in Fig. 13(a). This is similar to that of the familiar 'quartz crystal' bulk wave resonator, consisting of an LCR resonant section (the cavity) and a shunt capacitance due to the l.d.t. Two or more of these elements may be connected together to produce a coupled resonator. The equivalent circuit of a two port resonator is shown in Fig. 13(b). The capacitor C_c is defined by the coupling transducer and is given by:

$$C_c = 2C_o \frac{N_T}{N_c} \tag{4}$$

where N_T is the length of the input/output i.d.ts and N_C is the length of the coupling i.d.ts.

Normal coupled resonator behaviour is observed as N_C is changed, as illustrated in Fig. 14. By appropriate choice of structure, including in some cases inductive tuning, various standard filter types may be realised (Butterworth, Chebyshev, etc). In general, any number of resonators may be coupled together to form a multipole filter. A third-order filter is shown in Fig. 15.

S.a.w. resonator filters are low loss narrowband filters and are temperature stable if a quartz substrate is used. In the frequency range of application (50-1500MHz) there are very few suitable alternative filtering techniques and so the s.a.w. resonator allows narrowband filtering to be implemented at frequencies at which it has previously not been feasible. This has many implications in the design of modern systems where the filters may be included at the front end of communication systems and in the high frequency section.

Design procedures for s.a.w. resonator filters are similar to those for LC filters and the filters are minimum phase. Unlike transversal filters, the phase response achieved for a given amplitude response is uniquely defined.

Further details of delay lines

S.a.w. delay lines consist of two i.d.ts suitably placed on a piezo-electric substrate. If each i.d.t. is geometrically symmetric or antisymmetric (about its geometric centre) then the delay line frequency response is band-pass with a linear phase characteristic. Identical uniform transducers are usually used and the amplitude response is, therefore, $(\sin x/x)^2$ (see section on "Principles"). Alternatively, with a suitable asymmetric design of the i.d.ts the delay line can be made to be dispersive (i.e. the delay varying as a controlled function of frequency).

Linear phase delay lines can be made with bandwidths of up to 100% of centre frequency over the frequency range of 10MHz -1.5 GHz. Delays ranging from 400 nanoseconds to 30 microseconds or more can be achieved. Relative delays of less than 400 ns can be achieved directly if electromagnetic breakthrough is not a problem, or as the differential delay between two delay lines. The most attractive feature of s.a.w. delay lines is that rela-

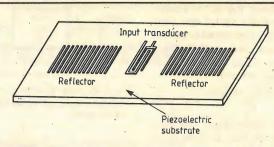


Fig. 12. One-port s.a.w. resonator geometry showing the transducer located between two reflectors.



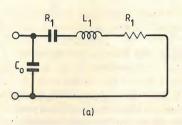


Fig. 13(a) Equivalent circuit of one-port s.a.w. resonator; (b) equivalent circuit of two-port s.a.w. resonator.

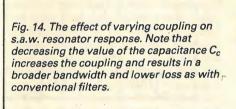

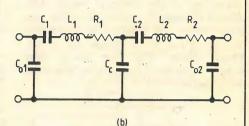

0 20 20 40 60 156-8 157 FREQUENCY (MHz)

tively large delays can be achieved in a small volume. For an ST-X (temperature compensated) quartz substrate, a delay of 1µs can be obtained with an acoustic path length of 3.2mm.

Applications include radar systems, electronic countermeasure systems and target simulators. S.a.w. delay lines can also be used in discriminator circuits such as that shown in Fig. 16 where a signal is fed to a double balanced mixer via two paths, one direct and the other through a s.a.w. delay line. Provided the delay line has a linear phase response the d.c. voltage output from the mixer is a cosine function of the input frequency and is approximately linear over a reasonable bandwidth. Linearity can be achieved over a wider bandwidth by limiting the signals at the mixer inputs to square waves.

Further details of s.a.w. oscillators

There are two distinct types of low noise, stable s.a.w. oscillators. The delay line oscillator employs a conventional s.a.w. delay line in the feedback loop of an amplifier; the frequency may be linearly modulated by typically 0.1%. The one-port s.a.w. resonator can be used in essentially the same oscillator circuits as conventional bulk wave resonators, or two port resonators can be used in an amplifier feedback loop. Resonator oscillators can only provide very narrowband linear frequency



Fig. 15. A third order s.a.w. resonator filter (package size 28mm x 20mm). The central transducers and end absorber are clearly visible.

modulation but can provide better noise performance. Both types of oscillator can work at fundamental frequencies in the range 10MHz-1.5GHz without additional multiplying circuitry. The devices are considerably smaller, cheaper and lighter than conventional oscillator techniques.

Delay line oscillators. Fig. 17 is a schematic representation of a s.a.w. delay line oscillator. The delay line consists of two i.d.ts separated by a distance L, with a delay of L/v corresponding to a phase shift at a frequency of ϕ_{DL} , where:

$$\phi_{DL} = 2\pi \underline{Lf}_{v} \text{ radians}$$

Oscillation will occur when the total phase shift around the loop is equal to an integer (n) multiple of 2π , i.e.

$$\phi_E + \phi_S + 2\pi \frac{Lf}{v} = n2\pi$$

where ϕ_E is the electrical phase shift around the loop (excluding delay line and phase shifter but including the amplifier) and ϕ_S is the phase change due to the phase shifter. The loop would thus support a comb of frequencies separated by Δf , where:

$$\Delta f = \frac{v}{L}$$

The required mode (at f_o) is selected by suitable design of the i.d.ts so that frequency f_o is passed but frequencies $f_o \pm nv/L$, where n is a non-zero integer, are located at nulls of the response of the delay line. One simple way to achieve this is for one i.d.t. to be a uniform transducer with N periods where $N = (L/v)f_o$; this makes the centre frequency f_o with traps of the $\sin x/x$ response at frequencies $f_o \pm nv/L$. This technique is illustrated in Fig. 18. Transducers with a proportion of electrodes removed (thinned i.d.ts) are often used to increase frequency reproducibility and to reduce internal reflections.

The frequency of the oscillator loop may be modulated by variation of the phase in the phase shift circuit which usually incorporates one or more varicap diodes. The output signal can be taken at any point around the loop (but not usually immedi-

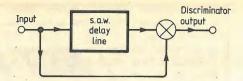


Fig. 16. Delay line discriminator using the good linear phase characteristics of the delay line.

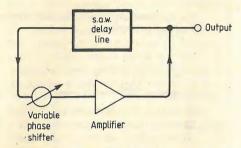


Fig. 17. Delay line oscillator. The circuit will oscillate at a frequency where the total phase shift around the loop is an integral multiple of 2π .

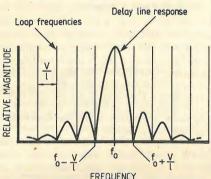


Fig. 18. Loop frequencies and transducer response of s.a.w. delay line oscillator, showing the comb of loop modes, one of which (f_0) is selected by the transducer response.

ately after the modulator). For maximum power this would normally be immediately after the amplifier; for minimum noise, immediately after the delay line is best.

The gain of the amplifier used must be greater than the loss around the loop and it is common to operate the loop with the amplifier saturated. The delay line loss will typically be 10-20dB, depending on the electrical matching.

Resonator oscillators. S.a.w. resonators (see earlier) are high Q components operating at frequencies of 50MHz and above. Unloaded Qs in excess of 20,000 can be achieved at 250MHz. This makes it possible to use these devices as oscillator control elements to provide stable sources at fundamental frequencies in the range 50MHz to 1.5GHz.

A s.a.w. resonator may be used in an oscillator as either a one-port or two-port device. If a two-port configuration is used then the circuit becomes similar to that used for delay line oscillators, i.e. an amplifier and a s.a.w. device in a feedback loop. The advantage of a resonator over a delay line in this case is that the amplifier need only provide 4 to 5dB of gain since the resonator has a lower insertion loss than the delay line. However, because the frequency response of a resonator is not linear phase, except over a very narrow range (approximately 0.02%), there is less potential for linear frequency modulation.

If the resonator is used as a one-port device then the circuit would be similar to that used for bulk wave crystal oscillators (e.g. Colpitts, Pierce), and because of the higher frequency (at u.h.f.) the construction could be based on a cavity or resonator stabilized microwave oscillator. A single transistor can be used in some cases, giving a very compact oscillator.

BOORS

Frequency Synthesizers,
Theory and Design, by Vadim Mannasewitsch.
582pp. hardback.
John Wiley, £19.25.

This is the second edition of a book, first published in 1976, which thoroughly describes a vast number of techniques, both practical and theoretical, for the generation of highly stable multiple frequencies using one reference — a subject which has only been seriously studied for around twenty years. It is written at a level suitable for graduate engineers.

Chapter 1 prepares the ground for the succeeding sections, covering in outline a large number of techniques and circuit blocks used in frequency generation, and being followed immediately by a chapter on the problems of spurious modulation and frequencies, and phase noise in practical synthesizers. Two 'practical' sections provide advice on screening against electric and magnetic fields and on fault-finding, and the three core chapters are concerned with analogue and digital phase-locked

loops and the basic circuits (mixers, amplifiers, dividers, etc.) needed for synthesizer operation. A further two chapters illustrate the techniques described earlier by reference to commercial synthesizers and frequency-reference sources. Important additions for the second edition are descriptions of direct digital synthesis and fractional-N, phase-locked loops.

Mannasewitsch has produced a clearly written treatise on this complex subject, which should be well suited to the needs of a working engineer who needs to acquaint himself quickly with the large number of techniques now in use. It is suggested by the author that the book would serve as a text for a course on the subject.

Handbook for Radio Engineering Managers by J. F. Ross. 947pp., hardback.

Butterworth, £35.00

The role of a manager in technical and economic planning, safety engineering, environmental consideration and the operation and maintenance of large and small radio stations is well covered, in all its aspects, in this enormous book. It is organized in six sections, on management and organization, engineering economy, safety practice, fires in radio installations, environmental aspects and specifications and contracts.

While management theory takes up a good deal of the book it is, in the main, a practical text, clearly the fruit of much experience. It is extremely comprehensive, treating not only the larger considerations of economics and planning, but minutiae such as precautions against the depredations of termites. Many photographs and drawings illustrate the text and it is pleasing to see a chapter on the engineer's obligation to the environment. Of particular interest to the British reader (the author is Australian) is an account of the collapse of the Emley Moor television mast in 1969, complete with photographs.

A very valuable work for anyone involved with planning, installing or running a radio station or network, whatever its size.

Multipath distortion

– does polarization matter?

by Pat Hawker, Independent Broadcasting Authority

Many broadcasting authorities have introduced, or are planning to introduce, vertical or circular polarisation in the transmitted signal to help reception on vertical aerials in cars or on domestic receivers. However, there is some correlation between polarisation and an increase in distortion caused by receiving the signal from more than one source. Research in Japan and Germany has helped to analyse the problem.

A recent survey article — "How serious is multipath distortion?" (Ref 1) — drew attention to the lack of recognition in the UK that multipath propagation is probably the most serious cause of the degradation of quality when v.h.f/f.m stereo broadcasts are reproduced in the home through good quality equipment, even when reasonably careful regard has been paid to aerial installation.

The article stressed that over 25 years after the start of regular v.h.f/f.m mono broadcasting in the UK (May 2, 1955) and about 15 years after the gradual introduction of pilot-tone stereo, there was still widespread lack of knowledge about the extent, and methods of mitigating multipath effects, induced to some degree by the reluctance of broadcasters, long concerned with the problem of encouraging more listeners to use v.h.f/f.m rather than m.f/a.m, to draw attention, except in the most simplistic terms, to this problem.

Since that article was written, several developments have taken place that deserve serious consideration by those interested in high-quality reproduction of broadcasting

broadcasting. (1) While the original article drew attention to the work carried out by NHK in Japan, the information then available was limited to a short English-text summary. Full details of this valuable investigation have since been published by Mitsuo Ohara in IEEE Transactions on Broadcasting (Ref 2). This paper makes it clear that multipath distortion is "far greater" on stereo than on mono transmissions and also reduces stereo separation (although the early investigations in the US and UK between 1940-1960 were of course confined to mono). Additionally it shows that multipath can be the cause of serious crosstalk into the broadcast programme of information carried on additional sub-carriers, including the SCA (subsidiary authorization channel) system widely used in the USA and, by implication, the ultrasonic tone signalling systems used in the UK, and the experimental 'programme labelling' systems, etc.

(2) Investigations carried out in the Cologne area of West Germany, including 212 site tests carried out from five specially equipped vehicles, and reported in EBU Review-Technical Part (Ref 3) indicate that the addition of a vertical component to horizontally polarized transmissions, that is any form of mixed polarization, significantly increases rather than decreases the extent of multipath distortion, even for listeners with good, outdoor horizontally polarized aerials. This report emphasises that from both the economic and purely technical points of view, the adoption of circular polarization in West Germany would be undesirable. This report has been published shortly after the BBC announced its intention (Ref 4) of adding a vertical component to the main BBC. national v.h.f/f.m networks of Radio 1-4 (with Wrotham to be modified in 1981), on the grounds of providing a better service for listeners using car radios, although the German investigators question even this

(3) The vulnerability of digital systems

(including teletext) to short as well as long term echoes was noted in the earlier article. Since then it has become clear that British Telecom are experiencing more problems than they anticipated in the planning of high-speed digital networks (140 Mbit/s etc) even on strictly line-ofsight microwave links. The Post Office Research Review 1979 (Ref 5) notes that: "Analogue f.m (link) systems are relatively tolerant of the signal distortions produced by multipath propagation which will cause an increase in intermodulation noise . . . in digital systems, the signal components arriving by alternative paths cause intersymbol interference . . . errors in the phase of the recovered carrier and timing signal which result in a more severe degradation in system performance". To overcome multipath propagation and deteriorations in cross-polar discrimination, both phenomena which in this context vary rapidly with time, British Telecom are considering such remedies as aerial height diversity, adaptive spectrum shape equalization, adaptive decision feedback, etc -all systems of some complexity, particularly when, as appears likely, it was initially expected that the 'ruggedness' of digital transmission would not require these added costs.

It is now clear that even well-planned

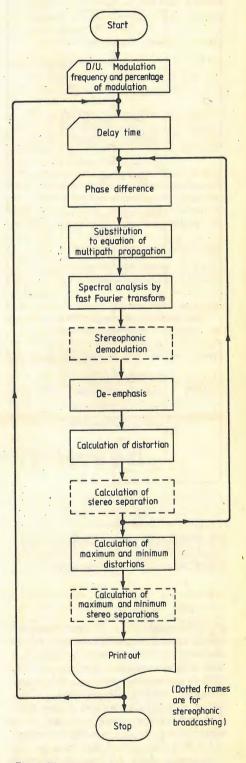


Fig. 1. The procedure used by Mitsuo Ohara (NHK) for computing multipath distortion of monophonic or stereophonic broadcasting.

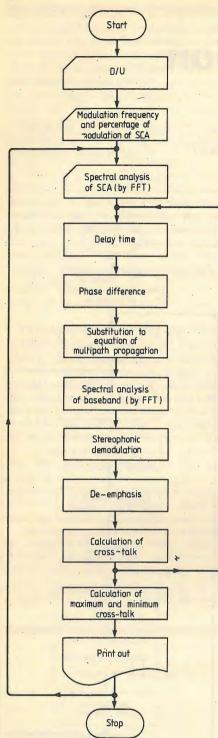


Fig. 2. Procedure for computing crosstalk into a stereo programme channel from 67kHz (SCA) sub-carrier transmission.

microwave links can suffer from multipath effects causing increased error rate, intense short-duration error bursts or unacceptable adjacent channel interference. The IEE E8 professional group (Radio communications Systems) are planning a Colloquium on Multipath Problems in May 1981. Although current thinking tends, for a variety of reasons, to favour digital systems it has to be recognised that there are circumstances where the gradual fall-off in performance of analogue systems is preferable to the 'go/no-go' characteristics of digital.

NHK multipath study

The NHK work on distortion and crosstalk caused by multipath propagation in v.h.f/f.m sound broadcasting constituted the first computer-assisted theoretical analysis of the relationship between multipath distortion and the relevant parameters. It provided a clearer picture of the characteristics of multipath distortion for both mono and stereo transmissions. It also included laboratory tests using a multipath simulator. Subjective listening tests were carried out using the simulator to investigate the relationship between the distortion and the reproduced sound quality under the influence of multipath distortion. It should be appreciated that the Japanese and American pre-emphasis timeconstant is 75 microseconds, whereas the European figure is 50 microseconds: this means that multipath distortion effects may be rather different in Europe than elsewhere. Nevertheless too much should not be made of this difference, since with both time-constants the effects of multipath tend to show up intermittently and selectively rather than as continuous distortion. Mitsuo Ohara shows that distortion increases with low percentages of modulation, particularly where there are long delay times on the reflected signals. A few examples of the results of this work are shown in Figs 3-4 and also in (Ref 1).

Crosstalk - 'monkey chatter' from a 67 kHz-subcarrier SCA system is shown to reach peak values for delay times of about 10 microseconds and about 20 microseconds. There is little doubt that a multiplexed SCA channel can result in severe crosstalk to those listening on the main stereo programme channel; this was the experience noted by the BBC when experiments were carried out several years ago. The significance of the NHK work is that this can now be ascribed partly to multipath effects. Similarly it would not be unreasonable to suppose that the type of interference from the experimental programme labelling signals reported by R. Camp in Wireless World (Ref 6) could arise either from receiver design or from multipath effects, though no indication of this could be gathered from the BBC com-

Polarization and multipath

The work carried out jointly by the Institut für Rundfunktechnik and Westdeutscher Rundfunk is particularly important in view of the increasing use being made in the UK of mixed polarization. In the form of "slant" polarization this was initially adopted by the BBC for their v.h.f/f.m local radio stations, and virtually all the ILR stations have used circularly polarized serials (although it is recognized that true circularity is not necessarily maintained throughout the service area). The main motivation for this was the 7 dB or so increase of signal strength when the signals are received on vertically polarized car radio aerials (or on portable receivers with telescopic rod aerials used out of doors in circumstances where there is little depolarization of the

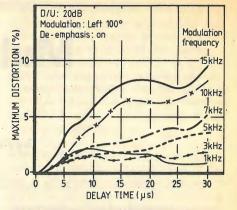


Fig. 3. An example of the relationship between the delay time of an echo and maximum distortion with an aerial direct/unwanted (D/U) ratio of 20 dB for different audio frequencies.

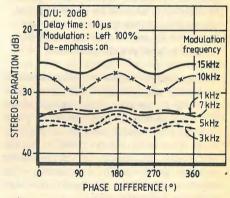


Fig. 4. An example of the relationship between phase difference of an unwanted signal and stereo separation for a D/U ratio

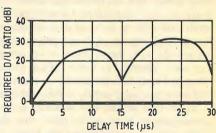


Fig. 5. Relationship between the delay time of an echo and the required D/U ratio if "monkey chatter" crosstalk from an SCA transmission into the main programme is to remain below -55dB (just perceptible). Note that crosstalk into the SCAprogramme from the main programme, due to multipath effects, is greater than crosstalk into the main channel.

signals). There have also been some suggestions that cp may provide more homogeneous coverage and possibly some reduction of multipath distortion.

The German work confirms that close to the transmitter cp transmissions result in 4-6 dB more received car-radio aerial voltage, even where the total power of the cp transmissions is unchanged from that of the normally horizontally polarized transmissions. However, it emphasises that vertically polarized v.h.f signals are not

WIRELESS WORLD APRIL 1981

propagated as well as horizontally polarized signals: but in addition it strongly indicates that in normal terrain, there are many more (typically three times as many) long-term 'echoes' with vertically polarized signals than with purely horizontally polarized signals. Unlike most previous studies, the German work was not confined to the sole criterion of received field-strength, but also the quality of reception. The results are a surprisingly vehement rejection of the value of mixed polarization applied to broadcasting.

The tests appear to have been conducted with typical German thoroughness. If one assumes that the methodology contains no hidden flaws, then the results of these trials would seem sufficiently convincing as to suggest that the BBC should reconsider its decision to adopt mixed polarization for its main networks. It is not my purpose, as a member of the 'other' broadcasting organization, to make a partisan point. Indeed if the German work cannot be 'shot down' then there would appear to be every reason why both IBA and the BBC should at least reconsider future policy on local radio, though (as noted later) on lower-power transmissions a more convincing case for cp can be made on behalf of the v.h.f./f.m car radio listeners. For the qualityconscious domestic listener, the key finding in the German experiment is that "it has been seen that the vertical component excites long-range reflections which are so intense as to affect even reception with a horizontally-polarized aerial. It should be noted that this effect is apparent even with a very directional transmitting aerial. If the transmission is omnidirectional the long-range reflections may be even more severe".

The German study also points out that when a vertical component is introduced, there will be problems of compatibility with existing domestic reception. A certain number of new listeners may be gained "at the expense of others who will lose their service". Existing gaps will not be filled to any great extent.

While the German study indicates that a slightly inclined plane of polarization would help listeners with verticallypolarized receiving aerials, it does not even wholeheartedly support such a compromise. But did the German trials 'prove' only what those concerned wished to

IBA engineers commenting in 1975 on the performance of the early ILR circularly polarized transmissions (Ref 7) noted that "the effects of multipath propagation on stereo broadcasts are well-known but often under-estimated. These effects occur far more often than is generally realised. During the off-air loop tests we have found on occasions that the system performance measured at the studio was severely affected by these phenomena. It has been the case that two aerials, on the same building, often very close together, have had very different multipath performance". It was also noted that although multipath distortion is caused by the fundamental mechanisms brought about by the reflected signals, the actual amount of distortion above this figure is likely to vary greatly between different receivers, depending mainly on the amount of limiting applied to the sub-carrier.

Several years ago EBU Working Party K

undertook a study of the work done by individual broadcasters on choice of optimum polarization for v.h.f./f.m sound broadcasting. Their report (Ref 8) summarised by F. Wise (formerly IBA) differentiated between: (a) "services intended primarily for high-quality receiving installations, probably with stereo, with no improvement to reception conditions for portable or car sets envisaged"; and (b) "primarily to reach the largest audience, especially those using portable or car sets. Account to be taken of those installations equipped to receive any existing transmissions". For (a) the report came out firmly in favour of retaining horizontal polarization for existing and new services in all types of terrain where existing services use horizontal polarization. For (b) the corresponding choice was 'mixed' polarization for 'flat or rolling terrain', but 'horizontal' for 'rugged' terrain. The report noted that reflections from the side of the direct signal path where the reflecting object may be a man-made structure, trees, hills or mountains will generally be of significantly greater magnitude for vertically-polarized transmissions, and that such transmissions are more likely to be affected by multipath. The evidence for increased reflections from behind the receiving point was then considered less convincing and the EBU Panel considered polarization unimportant, though noting that in Germany some evidence existed that buildings tend to reflect vertically-polarized Band II signals more than those which are horizontally polarized". The decision to convert BBC network transmissions to mixed polarization would appear to run contrary to the 1976 EBU report.

To conclude, it is necessary to stress that these comments are not intended as criticism of the BBC for playing down the multipath issue or even for their decision to add a vertical component to their network transmissions. Rather it is a plea that, as listeners or as broadcasters, we should be more aware of the effects multipath radio propagation and polarization have on the transmission of high-quality analogue or high-speed digital signals. Only if we recognise the problem are we likely to overcome the worst effects, or at least minimise them. We are still all in the learning stage, but it is important for quality-conscious listeners to discover whether the results of the German tests can be accepted as correct.

References

. Pat Hawker, "How serious is multipath distortion?" Wireless World, April 1980, pp 46-

2. Mitsuo Ohara, "Distortion and crosstalk caused by multipath propagation in frequencymodulation sound broadcasting", IEEE Transactions on Broadcasting, Vol BC-26, No 3, September 1980, pp 70-81.

3. T. Bossert and A. Lau, W. Blobel and D. Hoff, "Comparison between horizontal and circular polarization for v.h.f./f.m reception in the home and in motor vehicles" EBU Review -Technical Part, No 182, August 1980, pp 175-

4. P. E. Lonsdale, Letter to Electronics & Power, October 1980, p 795.

5. P. James (Ed), "Microwave Radio Digital Links", The Post Office Research Review 1979, pp 42-60.

6. R. Camp, Letter to Wireless World, with comments by D. P. Leggatt, October 1980, p49.

7. D. S. Chambers and J. R. Edwards, "The specification and performance of ILR v.h.f. transmitting systems". IBA internal report: SD&C No R3/75, pp8-10.

8. F. Wise, "Choice of polarization for new Band II services" EBU Review - Technical Part, No 155, February 1976, pp 21-24.

Literature received

A leaflet on the Japanese Izumi range of motordriven timers, which can switch up to 7A, is available from Appliance Components Ltd, Cordwallis Street, Maidenhead, Berks. SL6

Analog Devices has produced a brochure to explain specifications and applications of a-to-d and d-to-a convertors, sample-and-hold amplifiers and v-to-f converters. It can be obtained from AD at Central Avenue, East Molesey, Surrey KT8 0SN.

The FCC 180 series of D-subminiature connectors is made by Alpha for use with flat cables. A copy of their leaflet can be had from Alpha Wire, Ltd, Alpha House, Central Way, North Feltham Trading Estate, Feltham, Middx. WW409

Engineering Recommendation G22/1, published by the Electricity Council, is concerned with the use of devices which use the mains wiring to conduct signals. A copy can be obtained from the Distribution Engineering Branch, the Electricity Council, 30 Millbank, London SW1P 4RD at a cost of £1.


Prolog is a portable, multi-channel data acquisition and replay system, with dual microprocessor control over all operational functions. It is described by Microdata, the manufacturers, in a colour brochure, which can be obtained from the company at Monitor House, Station Road, Radlett, Herts. WD7 8 JX.

Verospeed's new catalogue is now available, containing 2500 items of hardware, components and instruments. The company will supply one off orders. Copies of the catalogue are available from Verospeed Ltd, Stansted Road, Boyatt Wood, Eastleigh, Hants. SO5 4ZY. WW411

The IEC have issued an international standard to achieve compatibility in the sub-systems and combination of sub-systems used in satellite earth receiving stations. The publication sets conditions for the measurement of return loss, input and output levels, amplitude and frequency characteristics, static a.g.c. characteristics, dynamic a.g.c. characteristics, and the group-delay/frequency characteristic. International Electrotechnical Commission, 1 Rue de Varembe, 1211 Geneva 20 Switzerland.

Amplitude sensing and control

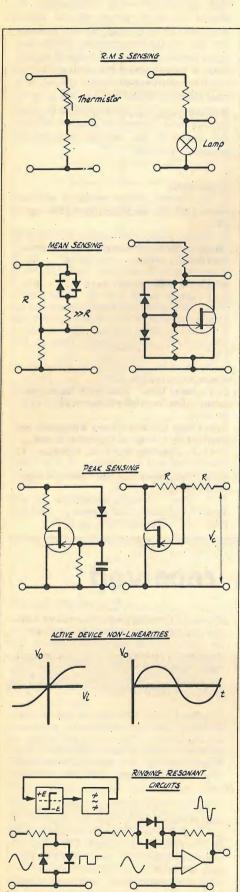by Peter Williams, Ph.D. Paisley College of Technology



There are two reasons for controlling the amplitude of a sinusoidal generator. The obvious one is where that amplitude affects the behaviour of some associated circuit or where its value is involved in consequent calculations. Less obviously any increase in amplitude changes the waveform because the output traverses more of the nonlinear range of the active devices. The harmonics resulting are returned to the input where intermodulation due to the non-linearities produces new components at the fundamental frequency. These are equivalent to a phase-shift in the fundamental and have the same effect in shifting the frequency of oscillation as would any other phase shift. The amplitude control mechanism is essentially a negative feedback system in which some property of the output amplitude is sensed, used to modify the feedback and hence to set the amplitude to a desired level. The first two networks contain elements whose resistance is temperature- and hence dissipation-sensitive. Their time constant is made long compared with the oscillation frequency. Amplitude then settles to a value at which the heating effect (r.m.s. dependent) brings the element resistance to a level at which the oscillation is self-sustaining.

The r.m.s. methods involve elements that consume power and have of necessity a slow response. When to these factors the relatively high cost and possible temperature dependence are added, alternative solutions become increasingly attractive. The condition for sustained oscillation at constant amplitude is that the loop gain be identically unity. When a non-linear network is included in the feedback loop then the loop gain can exceed the critical value at low amplitude ensuring that oscillation build up. As amplitude increases the signal forces the non-linear elements into regions of their characteristics where the loop gain falls to less than unity. The amplitude stabilizes such that the mean value of the loop gain is at the critical level. Stabilizing action is instantaneous in that there are no time-constants involved other than strays. Disadvantage of the method is that it achieves its affect by deliberately distorting the feedback signal, though the remainder of the circuit may attenuate the harmonics as they pass through the frequency dependent network. The most common technique places a symmetrical pair of diodes (or series connected back-to-back zener diodes) so as to increase the feedback at higher amplitudes. A field-effect transistor having a low dynamic impedance at low voltages and then going into current limit would have the same effect placed in the other limb.


A third method combines some of the advantages of the previous two. It uses only electronic devices, consumes negligible power and can introduce negligible distortion. It has the disadvantage that a deliberate time constant has to be introduced into the sensing action, though this time constant can be varied to suit the oscillation frequency (a property not shared by thermistors of lamps whose thermal time constants must be long compared with the period of the lowest desired oscillation frequency). The output is peak-rectified and the direct voltage is applied to the gate of a field-effect transistor. The on-resistance of the drain-source path is varied and can form part of a potentialdivider feedback loop. As shown the positive peaks generate a positive voltage that reverse biases the p-channel f.e.t. The value of rep increases and with it the feedback. Because the f.e.t. characteristic is non-linear it can only be used directly with very small voltage swings - preferably <V_P/10 where V_P is the pinch-off voltage. With additional direct feedback across the f.e.t. as shown it is found that the linearity is markedly improved. The resistance across the capacitor is a compromise between speed of response and distortion; increased ripple worsens the second and is caused by attempting to improve the first.


The methods above have the amplitude sensing mechanism in the passive network, the assumption being that the amplifier is perfectly linear. It is equally feasible to incorporate the non-linearities in the forward path i.e. in the amplifier. The disadvantage is that the harmonics are then fully present at the output, the filtering due to the RC network only being effective in reducing the distortion present at the input. In both cases the distortion is minimized by arranging the loop-gain for small signals to be only slightly greater than that required to sustain oscillation. This reduces the nonlinear excusions needed to bring the overall gain back to unity and hence reduces the distortion. If the non-linearities are symmetrical about the quiescent point then even harmonics are suppressed.

None of the above examples demand high-Q passive networks as the distortion introduced via the non-linearities or the sensing mechanisms need not be large. These methods are thus acceptable for simple RC oscillators even though the attenuation of harmonics offered by these networks is relatively small. With LC oscillators or certain RC oscillators based on high-Q active filters the constraint is removed. If a high-Q band-pass circuit is driven by a square wave whose fundamental frequency is the filter centre frequency, then the harmonics are so reduced at the output that an almost pure sine-wave results. It is difficult to maintain the drive frequency at the filter centre frequency since each is subject to the usual tolerances. If instead the filter output is passed through a squaring circuit then its input is a square-wave of the appropriate frequency and constant amplitude. Provided the filter gain at the centre-frequency is constant then the constant amplitude square wave ensures an equally stable sinusoidal output. The square wave can be obtained either by a simple diode limiter or with greater accuracy using a comparator with precision clipping. Antiphase feedback with diodes in the forward path of an amplifier are also found.

Amplitude sensing and control

THEORY

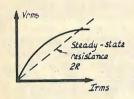

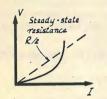

- Networks are used as amplitude-controlled negative feedback. At low amplitudes the steadystate resistance is >2R for the thermistor or <R/2 for the lamp. Hence feedback <1/3 and for standard Wien type oscillators the amplitude increases. Conversely at high amplitudes the feedback >1/3 and amplitude decays, stabilizing at the steady state level where the negative feedback just balances the positive feedback.
- These methods are mostly used where only approximate amplitude limiting is required, though they are instantaneous in their action while using little power. The non-linearity makes analysis difficult.
- The f.e.t. drain current $I_B=k[(V_{GS}-V_p)V_{DS}-V_{DS}^2/2]$ For $V_{DS}\rightarrow 0$, $I_D\rightarrow k$ ($V_{GS}-V_p)V_{DS}$ i.e. conductance

$$\frac{I_D}{V_{DS}} \rightarrow k(V_{GS} - V_p)$$

and is a linear function of the gate-source voltage. Hence varying the gate-source bias varies the conductance and hence the feedback.

For the second circuit

$$V_{GS} = \frac{V_{DS} + V_C}{2}$$

Substituting for V_{GS} in the expression for I_D above

$$I_{D}=k\left[\left(\frac{V_{DS}+V_{C}}{2}-V_{p}\right)V_{DS}-\frac{V_{DS}^{2}}{2}\right]$$

$$=k\left(\frac{V_{C}}{2}-V_{p}\right)V_{DS}$$

Hence the conductance

$$\frac{I_{D}}{V_{DS}} = k \left| \frac{V_{C}}{2} - V_{p} \right|$$

and is linear for all values of VDS while being a linear function of the new control voltage V_C. This modification allows control of the feedback without introducing any additional distortion into

• For a second-order transfer function $v_0 = k_0 + k_1 v_1 + k_2 v_1^2$ and a sinusoidal input vsinωt the output becomes

$$v_0 = k_0 + k_1 v \sin \omega t + k_2 v^2 \sin^2 \omega t$$

= $k_0 + k_1 v \sin \omega t + \frac{k_2 v^2}{2} (1 - \cos 2\omega t)$

Hence there is a second harmonic term in the output which expressed as a percentage of the fundamental term is proportional to the amplitude of the latter. Similarly higher-order terms result in higher harmonics, the absence of the nth harmonic in the output indicating the absence of the nth order term in the transfer function. Symmetrical transfer functions are preferred in that the even-order harmonic terms are thereby cancelled so that the lowest harmonic is the third harmonic.

EXAMPLES

1. A thermistor has a maximum permitted dissipation of 3mW and sets the output of a Wien bridge oscillator to 1V r.m.s. Choose a suitable value of resistor to complete the bridge.

With 1V r.m.s. total voltage, thermistor has p.d. of ≈2/3V r.m.s. assuming a high gain amplifier.

$$\therefore I = \frac{3.10^{-3}}{2/3} = \frac{9.10^{-3}}{2} = 4.5 \text{mA r.m.}$$

$$\therefore I = \frac{3.10^{-3}}{2/3} = \frac{9.10^{-3}}{2} = 4.5 \text{mA r.m.s.}$$

$$\therefore \text{ Series resistor R} = \frac{1/3}{4.5 \cdot 10} = \frac{10^3}{13.5} = 74\Omega$$

A suitable resistor might be 100Ω , to keep the thermistor well below its maximum dissipation.

2. At what output voltage does diode conduction commence in the simple diode amplitude control circuit?

Diode voltage at which current flow commences ~0.5V. But diode voltage is 2/3 of peak output

∴ Output voltage
$$\sim \frac{3}{2} \times 0.5 \text{V}$$

$$\therefore$$
 R.m.s. output voltage= $\sqrt{2} \cdot \frac{3}{4} = 1.08$ V r.m.s.

In practice higher values are required since this level corresponds to only slight conduction, barely modifying the amplitude response and requiring critical resistor adjustments.

3. The peak sensing circuit has $R=1M\Omega$. If the frequency of oscillation is 1kHz, and the ripple across the capacitor is not to exceed 2% peak-peak, choose the corresponding capacitance.

For small ripple, then as in simple recifier theory linear discharge is a reasonable assumption

$$\therefore \frac{\Delta V}{\Delta t} = \frac{I}{C} \quad \text{and } I \approx \frac{V}{R}$$

$$\therefore \frac{\Delta V}{V} = 0.02 = \frac{t}{CR} = \frac{10^3}{G.10^6}$$

$$C = \frac{10^{-9}}{0.02} = 50 \text{nF}.$$

4. The ringing resonant circuit uses a filter with Q=10 a centre-frequency gain of 20 and an approximate square-wave of 1.2V peak-peak. Determine the % 3rd harmonic at the filter output.

For square-wave of amplitude 1.2V peak-peak, the fundamental and 3rd harmonic amplitudes are

$$\frac{4}{\pi} \times 0.6$$
 and $\frac{4}{3\pi} \times 0.6$

 \therefore Fundamental output $20 \times \frac{4}{\pi} \times 0.6$

$$T_{v} = \frac{Hs}{s^{2} + \frac{\omega_{n}}{s} s + \omega_{n}}$$

with Q=10 and $\frac{HQ}{\omega_n}$ =20, i.e. H=20 ω_n

At
$$\omega = 3\omega_n$$

$$\begin{split} T &= \frac{2\omega_{n} \cdot j \cdot 3\omega_{n}}{-9\omega_{n}^{2} + \frac{3j\omega_{n}^{2}}{10} + \omega_{n}^{2}} \\ &= \frac{6j}{-8 + 0.3j} \approx 0.75j \\ &\left| \frac{T_{\omega} = \omega_{n}}{T_{\omega} = 3\omega_{n}} \right| = \frac{20}{0.75} \approx 27 \end{split}$$

Cassette deck

Parts subject to wear have been kept to a minimum by eliminating belt drives, pulleys, friction clutches and mechanical brakes in a cassette recorder, designed by Revox, called the B710. These parts are avoided by using four direct-drive motors, two Hall commutated magnetic-disc drive motors with inductive tacho generators for the capstans and two optical tacho-controlled tape-hub motors. Separate p.l.l. circuits with a common, crystal-based reference are used to control the capstan motor speeds. Damped solenoids engage the Sendust/ferrite heads and lock the cassette in position, and the whole drive mechanism is co-ordinated by a microprocessor to afford maximum protection to the tape. A four-digit display doubles as time-clock/timer readout and tape-position indicator, and has provisions for electronic set, cancel and recall of values for both functions. Bar-type l.e.d. indicators display the peak recording level. This recorder is designed for professional use and switching for equalization, changeover, bias, muting and Dolby is electronic to avoid noise. F.W.O. Bauch Ltd, 49 Theobold St, Borehamwood, Herts.

WW301

Data conversion kit

A data conversion evaluation kit for engineers wishing to assess analogue-to-digital and digital-to-analogue converters for a certain application is offered by Celdis. This kit, designed by Ferranti, costs £28 and comprises two 10-bit a-to-ds, six 8bit d-to-as, two 8-bit a-to-ds and two 8-bit d-to-a/a-to-ds with all the relevant data in folder form. The latter devices require only a comparator and a gate and clock signal to change their operation from d-toa to a-to-d. Celdis, 37 Loverock Rd, Reading, Berks RG3 1ED.

WW302

Colour printer

Printouts in seven colours can be produced using the CX80 matrix printer from Integrex. Each of these colours, four of which are produced by mixing the three primary colours of the ribbon, is selected by one of seven control codes. In addition to 96 ASCII and 64 graphics characters in r.o.m. there are 15 characters which can be programmed by the user and facilities for producing elongated and reversed characters. Line and form feed are also programmable. Nee-

dle addressing allows graphs, logos, teletext and other graphics to be printed in colour. The CX80 uses tractor feed paper up to 10in wide and can produce 80 columns, 60 dots/in and print rates of 150ch/s max. Normal characters have a 5×7 dot matrix and graphics characters a 6×7 matrix. A Centronics interface is standard, but other interfaces are available for the TRS-80, Apple II and for RS-232C, 20mA and IEEE 488. The price is £895 + v.a.t. Integrex Ltd, Church Gresley, Burton on Trent, Staffs DE11 9PT.

WW303

Fibre-optic interfaces

A pair of small fibre-optic interfaces called SEC10-1 can be used to transmit digital data optically over distances in excess of 1km and at data rates of up to 15Mbit/sec. These modules, one a transmitter and one a receiver, are manufactured by Lightdata and measure 30×20×15mm without the fibreoptic connector. The transmitter module operates on a 5V supply, but the receiver can be operated on 4.5 to 12V, to give a t.t.l., d.t.l. or c.m.o.s.-compatible output. Connection is by four wire-wrap pins in d.i.l. formation on the base of each module. Fibre-optic cable can also be supplied by this company to provide a complete data transmission system with a bit error rate of better than 1 in 10^9 . Lightdata Fibre Optic Communications, 129 Lindsey St, Epping, Essex CM16 6RE.


WW304

Computer interfacing a-to-d Analogue input data from sensors is

processed to provide digital I/O data, for use with any computer or terminal which has a 20mA or RS-232C port, by the µMAC-4000 measurement and control system from Analog Devices. This system consists of a single 241×330mm board which provides sensor-signal conditioning, analogue multiplexing, analogue-to-digital conversion, digital I/O, serial communications and a p.s.u. Up to four of these boards, each of which accepts 4, 8 or 12 analogue inputs, can be used together to provide 48 channels: expansion boards can be used to allow up to 384 channels. A variety of isolating and non-isolating signal-conditioning modules which plug directly into the p.c.b. are available for voltage and current sensing and for direct connection to thermocouples, r.t.ds (resistance




WW301

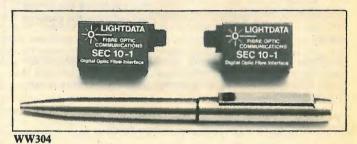



WW302

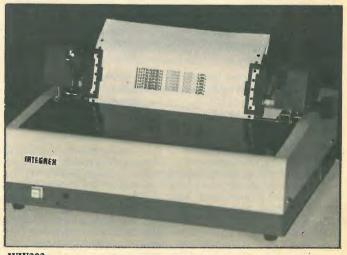

WIRELESS WORLD APRIL 1981

temperature detectors), strain gauges, etc. For control functions, eight t.t.l.-compatible outputs and eight t.t.l. or optically isolated inputs are provided on each board. Conditioned signals are processed by a low-drift, programmable-gain amplifier and 13-bit, integrating ato-d converter. An 8085 processor with 6K r.o.m. and 1K r.a.m. are used to scale, linearize, convert into engineering units and store the converted input data. The data updating rate can be either 15 or 30 channels per second. A full duplex u.a.r.t. receives and transmits data at the serial i/o port over distances of up to 10,000ft from the host computer, using 20mA loops (for baud rates under 600). Baud rates of up to 9600 and odd or even parity are switch selectable and the 20mA interface is isolated to 300V d.c. The two ASCII-based prorocols are compatible with assembly and high-level languages. Analog Devices Ltd, Central Avenue, East Molesey, Surrey KT8 0SN.

WW305

15in oscilloscope

Various face-plates and phosphors are available for the 15in c.r.t. of the 1530 data oscilloscope from Robel Electronics Ltd. This oscilloscope, with its small spot size and high writing speed, can be used in a number of applications, including the monitoring of waveforms from computer-based analysers, radars, sonars and most processing systems, including a.t.e. Slew rates of 0.5µs/cm and one degree phase shift up to 25kHz are quoted for the identical X and Y amplifiers. An internal three-step attenuator, an external continuously variable attenuator, and input impedance selectors are provided for these amplifiers. The Z amplifier, with a rise-time of 30ns, has differential inputs, with voltage ranges from 1 to 10V. A gain/contrast control is also provided. The photo shows the oscilloscope displaying data from an f.f.t. spectrum analyser. Robel Electronics Ltd. Rose Industrial Estate, Cores End Rd, Bourne End, Bucks SL8 5AS.

WW306

Tunable bandpass filters

This series of filters from March Microwave Ltd has octave tuning ranges with direct frequency read-out, accurate to ±0.5%. A total frequency range from 30 to 3000MHz is covered by 14 models and a choice of either 2 or 5% relative bandwidth between 3dB points is offered. Insertion loss at any tuned centre frequency is 2.5dB maximum for a 2% unit at 30MHz, and 1dB maximum for a 5% unit at 3000MHz. Attenuation is a minimum of 45dB at two bandwidths away from the centre frequency, and the power-handling



capability ranges from 35 to 60W. A single knob with slow-motion gearing is used for tuning and the readout dial is connected directly to the main shaft to avoid backlash. Special models can be constructed with different tuning ranges or steeper attenuation curves if required. March Microwave Ltd, 112 South St, Braintree, Essex.


Ceramic resonators


In applications where a timing element is required, cost can often be reduced by using a ceramic resonator instead of a quartz-crystal. Ambit CRM and CFE ceramic resonators are available in the range 200 to 600kHz and drift approximately 0.3% in frequency from -20 to +80°C, with 0.5% drift over 10 years. The CRM type is intended for use as a parallel resonator and the CFE type as a series element for use in bypass and trap applications. Both types are analogous to a quartz-crystal. Prices are 32p each or 19p for 100-up quantities. Ambit International, 200 North Service Rd, Brentwood, Essex CM14 4SG.

L.e.d. arrays


L.e.d. arrays with five or six elements and rectangular faces are manufactured by Impectron Ltd for use as level meter readouts, front panel indicators or simple graphic displays. Each element, measuring 4.5×2mm, is rated at 50mA peak forward current and 2V maximum forward operating voltage, so the GL series arrays can be driven by t.t.l. outputs without buffering. Three one-colour versions, red, yellow or green, and one version with four green and two red elements are available. Luminous intensity varies between 0.2 and 1.7mcd, depending on the colour selected. These l.e.ds are also available in single form. IBR Electronics Group Ltd, Foundry Lane, Horsham, W. Sussex RH13 5PX.

WW309

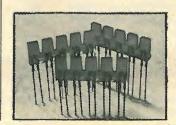

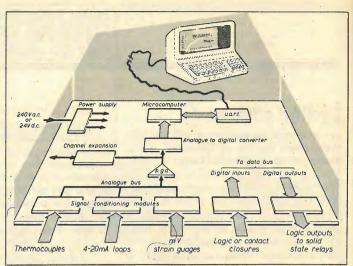

WW305

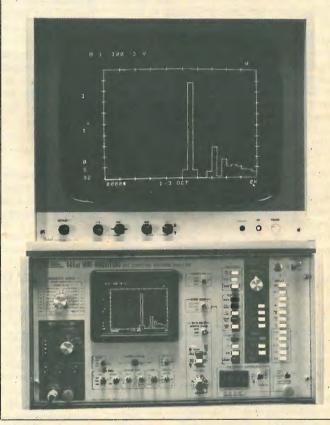

WW306

Zero insertion force sockets

Under conditions where occasional field replacement of i.cs is unavoidable the Econo Zip from BFI Electronics can be used. These zero-insertion-force i.c. sockets are designed for production rather than test applications and the usual locking lever is replaced by a screw head. Otherwise, the socket is similar to other such devices on the market but the cost per unit has been kept low. Six versions are available to take 16, 24, 28, 40, 48 or 64 pin i.c.s, and the contacts are gold-plated to 100µm thickness. BFI Electronics Ltd, 516 Walton Rd, West Molesey, Surrey. WW310

Magnet machining

Permanent magnets from stock or supplied by the customer can be machined by Magnet Developments Ltd. Their factory, they say, is equipped with slitting, slicing and spark-erosion machines, geared to machine and cut permanent magnets accurately for prototypes or short production runs. The range of magnets stocked by the company include sintered and bonded rare-earth types, sintered and flexible ferrites and cast-alnico types. A design advisory service is also available to customers. Magnet Developments Ltd, Unit 7, Headlands Trading Estate, Swindon, Wilts SN2 6JQ. WW311

Cycling stille hertz

My heart-rending experience with the bike (Feb. issue) did not go unnoticed. Keith Matthews, of the Wessex District Cyclists' Touring Association, writes to tell me not to be so lily-livered and to have another go (although he is much too polite to put in those words). It's all my fault, it seems something to do with my not being "bike fit" and not having anything better to ride than a Moulton. Well, I'm quite ready to agree with him about my not being in shape for this sort of thing, but I always thought Moultons were nice little bikes. Maybe that's the trouble: I ought to have one of those spidery contraptions with a saddle like an emaciated razor blade and handlebars bent down to somewhere near the front hub.

I am considerably encouraged, however, by Mr Matthews' assertion that most car drivers will give way to a bikie (I am informed that I cannot be a cyclist until I graduate - maybe by riding the three miles without my feet touching the ground or being provoked to personal abuse) because they realise that if they hit you, you will probably bleed all over the paintwork, which will mean a visit to the car wash, a matter of some inconvenience and ex-

The real point of his letter was not, however, all the above, but was contained in the last sentence. He assumes that I shall take up my cycling career again after its disastrous start, and will want to try the bike computer this all started with in the February issue. When I do, he says, I shall discover that it is unreliable above 30m.p.h. (my italics). That, I think, adequately demonstrates the gulf that separates us bikies from real cyclists. Thirty miles an hour! Come now, Mr Matthews, I had in mind a rather more sedate progress than that. They used to say that people would suffocate and die at speeds over 20m.p.h., and for all I know, they could be right. No, as long as I go fast enough to avoid the danger of falling off sideways, I reckon that's enough for anyone. I have no ambition to achieve the vellow jersey to go with the plaster and bandages that would be the certain result of my travelling at 30m.p.h.

Thing-um-a-jig

O frabjous day! Calloo! Callay! The dual snubberless Schottky is with us!

I do beg your pardon - I was so overcome by the arrival of a bit of paper announcing the availability of the d.s.S. that I felt a little outgrabing of the old momerath was permissible. But it's all right - I'll stop now, or Ed. will vorpal the page right here.

Isn't it lovely, though? Anyone whose imagination is untouched by a chance to use a dual snubberless Schottky must be a cold fish indeed, I should think. Not just one, mark you, but a dual package of the frumious little beasts. Now that they're here, and not before time, if you ask me. we've got to find something really beamish to do with them, before some dreadful old square writes in to say they're intended as rectifiers, or some such earthbound fate.

It doesn't need much thought to see that a dual snubberless Schottky is not a device you can tie down to anything too specific. It needs a free rein - to be allowed to breathe and develop in an atmosphere of (Oh, look, is there going to be a lot more of this? Ed.)

You have no idea how frustrating this iob can be sometimes. I was only going to say that a d.s.S. could be the very thing for one of those electronic games, maybe Hunting the Snark, each player being armed with a paddle-controlled vorpal blade. Every time a v.b. went 'snickersnack' the d.s.S. would light up, or something.

Well, it's only a thought. You can't give a device a name like dual snubberless Schottky and expect people to use it for anything too serious.

Spoilt by choice

I've been watching the domestic television recording scene for some time now (video, it appears to be called, for some reason) with the kind of feelings I would expect Neanderthal Man to have experienced when confronted by an array of arrow heads down at the stonemonger's. All he wanted was a couple of dozen plain, ordinary arrowheads for the start of the bronto-shooting season and here was this character offering him umpteen models to fit different shaft sizes: all equally well chipped, mind you, but totally incompatible. Manners were fairly elementary then, of course, and for such an act of thoughtlessness, Neanderthal was quite likely to split the stonemonger down the middle and use his skin for trousers, appeals to his better nature notwithstanding. Headstrong, they were, in those times, and direct to the point of rudeness.

Time has had its effect on Homo sapiens and I'm not sure that a bit more directness wouldn't be a bad thing, particularly when dealing with all these clever people who keep on inventing video tape recorders and video disc players that do more or less the same job but are just different enough to prevent you using the software from one machine on another. I don't for a moment think that they are deliberately contemptu-

ous of the public's needs and wishes: in fact, I don't even think they give much thought to the public's needs and wishes. apart from the need to 'create' a market and persuade people to buy their wares. If they happen to think that their electronic equivalent to the arrow shaft should be 1/4in in diameter, they'll go ahead and make millions of arrows to fit, regardless of the fact that someone else is making them 5/8 in in diameter, and has been for

It's no good at all saying that it's up to the buyer to make his mind up: how many people who simply want to record the television Shakespeare canon or transfer Nationwide to a more convenient time are in a position to make a difficult technical choice between the different v.c.rs? And how many will be able to decide between the three methods of reading a video disc, or realise that you can't play Philips discs on a JVC player, while all the time considering the claims of several firms to have the best disc library?

Quiet, please! It's breakfast time

When I was a bit younger, I used to have a finely tuned timetable in the morning. Everything was worked out to the nearest couple of microseconds, and a few seconds spent in putting a new blade in the razor, or a serious lapse in concentration resulting in the soap getting itself lost in the bathwater could cause havoc. Many's the time I've been ejected from the house without a second cup of coffee.

I've relaxed a bit, now. For one thing, I don't have to drive my wife to school since she gave up teaching and, for another, I've learned more sense. The move to Sutton has helped, too. I now take my mornings very gently, luxuriating over a leisurely bath, savouring a proper breakfast and invariably having a second cup of coffee.

Even so, taking all this gracious living into account and making due allowance for the need to keep abreast of world affairs, I can see no possibility of television getting a look in at that time in the morning. There are many things I want from life, but television with my crispy bacon and scrambled eggs is not one of them. As far as I am concerned, thanks, but no thanks, particularly if there are to be any of those indecently vivacious commercials for orange juice, or Snappaflakes, or whatever. And what of the news itself? Most of it is quite bad enough when printed in a newspaper, but spoken right out loud, just like that, by a television person - well, it's enough to curdle the milk.

he firm for Speakers



AUDAX HD12.9D25 AUDAX HD11P25EBC

ALIDAY HD20825H4

AUDAX HD20825H4 AUDAX HD13D34H AUDAX HD24S45C AUDAX WFR15S CHARTWELL CEA205

COLES 4001
COLES 3000
COLES 3100
COLES CE2000 6½"
CELESTION HF1300 II
CELESTION HF2000
DALESFORD D10 tweeter

DALESEORD D10 ferrofluir

DALESFORD D10 ferroflui DALESFORD D30/110 DALESFORD D50/153 DALESFORD D50/200 DALESFORD D100/250 DALESFORD D300

SOPHON KKR/R

JORDAN 50mm unit

KEF DN12 KEF DN13 LOWTHER PM6 LOWTHER PM6 Mk I LOWTHER PM7 PEERLESS KO 10DT

PEERLESS DT10HEC

RICHARD ALLAN LP8B

RICHARD ALLAN DT20 RICHARD ALLAN DT30 SEAS H107 SEAS H211 ferrofluid

SHACKMAN ES units

PEERLESS DITORFC
PEERLESS KO40MRF
RICHARD ALLAN CG8T
RICHARD ALLAN CG12T Super

RICHARD ALLAN HP12B

SHACKMAN ES units with cabs £170 pai

JORDAN crossove

KEF B200

KEF B139

DALESFORD D300
DECCA London Horn
ELAC 6NC204 61/2"
ELAC 8NC298 8"
EMI type 350, 13" x 8", 4 ohm
EMI 14A/770, 14" x 9", 8 ohm

ISOPHON KK10/8 JORDAN WATTS Module JORDAN WATTS Module Mk III JORDAN WATTS HF kit

COLES 4001



CELESTION G12/50TC CELESTION G12/80CE CELESTION G12/80TC CELESTION G12/125CE

CELESTION G15/100CF

FANE CLASSIC 80 12" FANE CLASSIC 85 15" FANE CLASSIC 150 15"

FANE CLASSIC 125 18" FANE CLASSIC 175 18"

FANE GUITAR 80B/2 12" FANE DISCO 100 12" FANE PA85 12" FANE BASS 100 15"

FANE CRESCENDO 12E 12"
FANE CRESCENDO 15E 15"

FANE CRESCENDO 15E 15"
FANE CRESCENDO 18E 18"
FANE COLOSSUS 15E 15"
FANE COLOSSUS 18E 18"
FANE J44
FANE J73
FANE J104

FANE J104 FANE J105 GAUSS 3181A 10" 150 watts GAUSS 4281 12" 300 watts GAUSS 4581 15" 300 watts GAUSS 4583A 15" 400 watts

GAUSS 4882 18" 400 watts GOODMANS 8PA

GOODMANS HIFAX 50HX

McKENZIE C12125TC

RICHARD ALLAN HD8T

RICHARD ALLAN HD101 RICHARD ALLAN HD10T RICHARD ALLAN HD12T RICHARD ALLAN HD15 RICHARD ALLAN HD15P RICHARD ALLAN 15" RICHARD ALLAN 18"

McKENZIE TC15
McKENZIE TC15 bass
MOTOROLA PIEZO HORN 3½
MOTOROLA PIEZO HORN 2"

McKENZIE GP15

GOODMANS HIFAX 100HX McKENZIE C12100GP McKENZIE C12100TC McKENZIE C12100 bass McKENZIE C12125GP

GOODMANS PP12 GOODMANS DI12 GOODMANS GR12 GOODMANS 18P

FANE GUITAR 801 12

CELESTION G15/100CE
CELESTION G15/100TC
CELESTION G18/200
CELESTION Powercel 12/150
CELESTION Powercel 15/250
FANE CLASSIC 45 12"
FANE CLASSIC 55 12"

£8.75 £7.50 £14.95

£24.95 £28.50 £10.50 £33.50

£12.25 £13.50 £27.75

£9.95 £10.75 £9.95 £10.95



£19.50 £24.50 £23.75 £42.00 £37.95

£37.95 £38.50 £64.75 £66.00 £88.00 £13.95

£220.00 £5.05

£35.10 £35.10 £59.60 £8.50 £12.25

£20.25

£21.75

£29.75 £52.75 £52.75 £77.00





EVERYTHING IN STOCK FOR THE SPEAKER BAF, LONG FIBRE WOOL, FOAM, CROSSOVERS, FELT PANELS, COM-PONENTS, SPEAKER STANDS, BRACKETS, ETC. LARGE SELECTION OF GRILLE

(Send 22p in stamps for grille fabric

KITS FOR MAGAZINE DESIGNS

Practical Hi Fi & Audio PRO9-TL including felt panels and level controls £152.75

£146.00 Hi Fi Answers Monitor Hi Fi News State of the Art Hi Fi News Midiline Hi Fi News Miniline £189.00 £99.75 £49.00

Hi Fi News Tabor with J4 bass units £66.00 Hi Fi News Tabor with H4 bass units

Hi Fi for Pleasure Compact Monitor

Hi Fi for Pleasure E.C.M. (including felt £125.00 Popular Hi Fi Jordan System 1 Popular Hi Fi Mini Monitor Popular Hi Fi Round Sound

including complete cabinet kit
Practical Hi Fi and Audio BSC3

£65.00 Practical Hi Fi and Audio Monito

Practical Hi Fi and Audio Triangle Practical Hi Fi & Audio DBS4 £85.00 carriage £5

Everyday Electronics EE20 £29.50 Everyday ELectronics EE70 Carriage £5
Wireless World T.L. KEF £125.00
Wireless World T.L. RADFORD £190.00

Smart badges FREE with all the above kits (to give that professional touch to your DIY speakers). Reprints / construction details of the

WILMSLOW AUDIO BA1

above designs 10p each.

£37.95 plus £1 carriage

PRICES PER PAIR CARRIAGE £3.95

COLES NIMBUS KIT £54.00 £57.00 £104.00

UNLESS OTHERWISE STATED

(mounted on baffle)
DALESFORD SYSTEM 1
DALESFORD SYSTEM 2
DALESFORD SYSTEM 3
DALESFORD SYSTEM 4 £110.00 DALESFORD SYSTEM 4
DALESFORD SYSTEM 5
DALESFORD 'D' KIT (includit £142.00

£102.50

KEF Reference 104aB kit £199.00 £181.00 LOWTHER PM/ kit
RADFORD Studio 90
RADFORD Monitor 180
RADFORD Studio 270
RADFORD Studio 270
RADFORD Studio 360
RICHARD ALLAN Tango Twin
RICHARD ALLAN Maramba £243.00 £243.00 £309.00 £450.00 £55.50 £77.50 £111.00 RICHARD ALLAN Charisma

RICHARD ALLAN Super Trip RICHARD ALLAN Super Sara £159.95 £62.75 £98.75 RICHARD ALLAN RAS kit RICHARD ALLAN RA82 kit RICHARD ALLAN RA82L kit £108.00 SEAS 223 SEAS 253 SEAS 403 £42 50 £42.50 £67.00 £79.95 £134.95 £31.45 £40.40 **SEAS 603** WHARFEDALE DENTON XP2 kir WHARFEDALE SHELTON XP2 kit WHARFEDALE LINTON XP2 IN WHARFEDALE LINTON XP2 kit WHARFEDALE L60 kit WHARFEDALE L100 kit WHARFEDALE E50 kit £56.20 £56.20 £52.50 £72.00 £87.00 £129.00 £160.00

CARRIAGE & INSURANCE 4" to 61/2

WHARFEDALE E90 kit

90p each Speaker Kits Mag. Design Kits unless otherwise £3.95 pair £3.95 pair

ALL PRICES INCLUDE VAT @ 15% and are correct at 1/2/81

SEND 50p FOR 56-PAGE CATALOGUE 'CHOOSING A SPEAKER'

(or price list only free of charge) Export Catalogue £1 or \$3 U.S.



Wilmslow, Cheshire

Tel. 0625 529599 for speaker drive units, kits, PA equipment, mail order enquiries, and all export enquiries.

Tel: 0625 526213 for Hi-Fi equipment and complete speaker enquiries.



Lightning service on telephoned credit card orders!



35/39 Church Street Wilmslow, Cheshire

WW - 021 FOR FURTHER DETAILS

Look in our magazine maybe we have the quick answer.

Every month we present designs that are useful both around the home and for leisure - including motoring, music, photography and games.

THIS MONTH:



ELECTRONIC SWITCH FOR MOTORS

A modern triac design to eliminate the troublesome centrifugal starting switch. Suitable for single phase induction motors, reversible or nonreversible.

tween awkward points.


DON'T LET YOUR GOODS GO BAD...

A simple design to alert you to a mains power failure and avert the possibility of ruined food.

Mains powered two-station system. Can be used as a doorbell with speech communication to identify unknown visitors.



APRIL ISSUE OUT NOW 60p

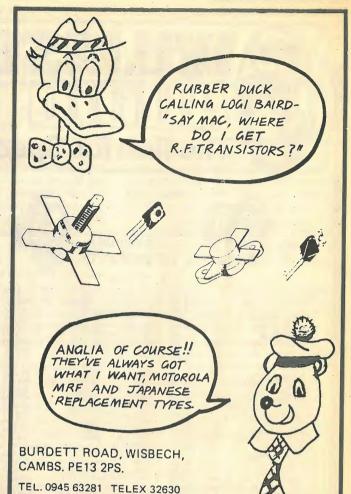

WW - 058 FOR FURTHER DETAILS

PURE GOLD!

Top-quality, low-profile, gold-plated contacts,

IC SOCK	ETS
8 pin	8p
14 pin	14p
16 pin	16p
18 pin	18p
20 pin	20p
22 pin	22p
24 pin	24p
28 pin	28p

Unbeatable value!

Minimum Order £10, Add £1 P.&P. 500 + and one type less 5%. 1,000 + any mix less 10%. Special offer 10 x 8 pin, 20 x 14 pin, 20 x 16 pin. 5 x all others £11.50

ORION

Orion Scientific Products Ltd., 10 Wardour St., London, W.1

10. 20 WORLDRANGER TRIBANDER TRIBANDER

AERIAL £135 Plus VAT

BALUN £12.50 Plus VAT

BARNET METAL & CAR CO. LTD., Tewin Road, Welwyn Garden City Herts. AL7 1AG Telephone: Welwyn Garden 24327
Telex: 28125 Cable: BARMECO WIRELESS WORLD APRIL 1981

TRANSCENDENT 2000 SINGLE BOARD SYNTHESIZER

besigned by consultant him Orr (formerly synthesizer designer or EMS Ltd.) and featured as a constructional article in ETI, this live performance synthesizer is a 3 octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep

The kit includes fully finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or ½% metal film), and it really is complete — right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit — you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price.

Comprehensive handbook supplied with all complete kits! This fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!

COMPLETE KIT ONLY £168.50 + VAT!



Cabinet size 24.6" × 15.7" × 4.8" (rear) 3.4" (front)

NEW! TRANSCENDENT POLYSYNTH



Cabinet size 31.1" x 19.6" x 7.6" (rear) 3.4" (front)

AS FEATURED IN ELECTRONICS TODAY INTERNATIONAL

and published in Electronics Today International, this latest addition to the famous Transcendent family is a 4 octave (transposable over 7½ octaves) polyphonic synthesizer with internally up to 4 voices making it possible to play simultaneously up to 4 notes, whereas conventional synthesizers handle only one at a time. The basic instrument is supplied with 1 voice and up to 3 more may be plugged in. A further 4 voices may be added by connecting to an expander unit, the metallwork and woodwork of which is designed for side-by-side matching with the main instrument. Each voice is a complete synthesizer in itself, with 2 VCOS. 2 ADSRS a VCA and a VCF (requiring only control voltages and power supply, the voice boards are also very suitable for modular systems). One of these voices is automatically allocated to a key as it is operated. There are separate tuning controls for each VCO of each voice. All other controls are common to all the voices for ease of control and to

Although using very advanced electronics the kit is mechanically very simple with minimal wiring, most of which is with ribbon cable connectors. All controls are PCB mounted and the voice boards fit with PCB mounted plug and sockets. The kit includes fully finished metalwork, solid teak cabinet, professional quelity components (resistors 2% metal oxide or metal film of 0.5% and 0.1%), nuts, bolts, etc.

COMPLETE KIT ONLY £320 + VAT (Single Voice)
Extra voices, £52 + VAT or £48 + VAT if ordered with kit.

EXPANDER, COMPLETE KIT £295

TRANSCENDENT DPX

MULTI-VOICE SYNTHESIZER

Another superb design by synthesizer expert Tim Orr published in **Electronics Today International**

COMPLETE KIT ONLY £299 + VAT!



Cabinet size 36.3" × 15.0" × 5.0" (rear) 3.3" (front)

The Transcendent DPX is a really versatile 5 octave keyboard instrument. These are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound—fully polyphonic. i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano as a honky tonk piano or even a mixture of the two Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer — strings on the top of the keyboard and brass as the lower end (the keyboard is electronically split after the first two octaves) or vice-versa or even a combination of strings and brass sounds simultaneously. And on all voices you car witch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds — just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control-for the brass sounds and also a vibrato circuit with variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even migre realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

As the system is based on digital circuitry digital data can be easily taken to and from a compliciter (for storing and playing back accompaniments with or without pitch or key change. computer The Transcendent DPX is a really versatile 5 octave keyboard instrument. These are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed

As the system is based on digital circuitry digital data can be easily taken to and from a computer (for storing and playing back accompaniments with or without pitch or key change, computer

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, etc., even a 13A plug!

MANY MORE KITS AND ORDERING INFORMATION ON PAGE 93

All projects on this page can be purchased as separate packs, e.g. PCBs, components sets. hardware sets, etc. See our free catalogue for full details and prices.



Soldering equipment designed by specialists for professionals.

ADCOLA IOI Soldering Unit

- no moving parts
- no magnetic effect
- no tip voltage
- no mains interference
- no real maintenance costs (bit/tip changes only)
- variable lockable temperature 120°C 420°C
- total 50 watt electronic control (±2%)
- simple plug-in bits/tips
- electrical safety approved 240V 24V
- easy tool interchangeability from one Unit

~or complete 2001 Soldering Station

Soldering tool and control unit as Unit 101 but with the additional features

- filtered two speed fume extraction
- built in bench lighting
- solder reel dispenser
- clear bench area
- Adiron[®] long life bits/tips the same range as that for Unit 101

ADCOLA ADIRON® long life bits/tips simple plug-in type suitable for both Unit 101 and Unit 2001

Forfull

details

contact





Telephone Sales (01) 622 0291 Telex 21851 Adcola G



ADCOLA PRODUCTS LIMITED Gauden Road London SW4 6LH

WW - 051 FOR FURTHER DETAILS



DE LUXE EASY TO BUILD LINSLEY HOOD 75W STEREO AMPLIFIER £85.00 + VAT

This easy to build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Reiew and features include rumble filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%.



T20 + 20 20W STEREO AMPLIFIER £33.10 + VAT

This kit, based upon a design published in Practical Wireless, uses a single printed circuit board and offers at very low cost, ease of construction and all the normal facilities found on quality amplifiers. A 30 watt version of this kit (T30 + 30) is also available for £38.40 + VAT.

MATCHING TUNERS — See our FREE CATALOGUE!

Above 2 kits are supplied with fully finished metalwork, ready assembled high quality teak veneer cabinet, cable, nuts, bolts, etc. and full instructions — in fact everything!



1024 COMPOSER

COMPLETE KIT ONLY £89.50 + VAT!

IN ELECTRONICS TODAY INTERNATIONAL

Programmed from a synthesizer, our latest design to be featured in ELECTRONICS TODAY INTERNATIONAL the 1024 COMPOSER controls the synth, with a sequence of up to 1024 notes or a large number of shorter sequences e.g. 64 of 16 notes all with programmable note length. In addition a rest or series of rests can be entered. It is mains powered but an extensive the state of Nickel Control of the con

BLACK HOLE CHORALIZER

The BLACK HOLE designed by Tim Orr, is a powerful new musical effects device for processing both natural and electronic instruments, offering genuine VIBRATO (pitch modulation) and a CHORUS mode which gives a "spacey" feel to the sound achieved by delaying the input signal and mixing it back with the original. Notches (HOLES), introduced in the frequency response, move up and down as the time delay is modulated by the chorus sweep generator. An optional double chorus mode allows exciting antiphase effect to be added. The device is floor standing with foot switch controls. TED "effect selection indicators, has variable sensitivity, has high signal/noise ratio obtained by an audio compander and is mains powered — no betteries to changel Like all our kits everything is provided including a highly superior, rugged steel, beautifully finished enclosure.



COMPLETE KIT ONLY £49.80 + VAT! (single delay line-system) De Luxe version (dual delay line system) also available for £59.80 + VAT

Cabinet size 10.0" x 8.5" x 2.5" (rear) 1.8" (front)

5 CHANNEL LIGHTING EFFECTS SYSTEM This versatile system featured as a constructional article in ELECTRONICS TODAY INTERNATIONAL has 5 frequency channels with individual level controls on each channel. Control of the

lights is comprehensive to say the least. You can run the unit as a straightforward sound-to-light or have it strobe all the lights at a speed dependent upon music level or front panel control or use the internal digital circuitry which produces some superb random and sequencing effects. Each channel handles up to 500W and as the kit is a single board design wiring is minimal and construction very straightforward. Kit includes fully finished metalwork, fibreglass PCB controls, wire, etc. — Complete right down to the last nut and bolt!



MPA 200 100 WATT (rms into 8Ω) MIXER/AMPLIFIER

Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced — but professionally finished — general purpose high power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward.

The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc — complete down to the last nut and bolt.



CHROMATHEQUE 5000 PERFECTLY!

COMPLETE KIT ONLY £49.50 + VAT!

Panel size 19.0"×3.5". Depth 7.3"

2-CHANNEL 100W AMPLIFIER - NE

The power amplifier section of the MPA 200 has proved not only very economical but very rugged and reliable too. This new de power supplies fed from a common toroidal transformer. Input sensitivity is 775mV.

Power output is 100 rms into 8 ohm from both channels simultaneously. The kit includes

fully finished metalwork, fibreglass PCBs, controls, wire, etc-complete down to the last nut COMPLETE KIT ONLY £64.90 + VAT!

Panel size 19.0" × 3.5". Depth 7.3"

MANY MORE KITS ON NEXT PAGE! OUR CATALOGUE IS FREE! WRITE OR PHONE NOW!

PORTWAY INDUSTRIAL ESTATE ANDOVER HANTS SP10 3NN

ANDOVER (0264)64455



Value Added Tax not included in prices

PRICE STABILITY: Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement until May 31st, 1981, if this month's advertisement is mentioned with vour order. Errors

and VAT rate change excluded.

EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1

Handling and documentation.

U.K. ORDERS: Subject to 15% surcharge for VAT. NO charge is made for carriage. Or current rate if changed.

SECURICOR DELIVERY: For this optional service (U.K. mainland only)

add £2.50 (VAT inclusive) per kit. **SALES COUNTER:** If you prefer to collect your computer from the factory.
Call at Sales Counter. Open 9 a.m.-12 noon. 1-4.30 p.m. Monday-Thursday.

The range grows bigger...better...

0.29018

LOTER LIFE

New Profile Amplifiers - Two New Series

MARINE WAS A STREET THE STREET



CHOOSE AN I.L.P MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P's specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency fromour new MOSFETS, and are easier to mount. Connection is via five pinson the underside. I.L.P MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE COSTLESS TAMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY AFRACTION OF PRICES CHARGED ELSEWHERE.


Model	Output Power RMS	Distor- tion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3µs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	Зµѕ	100dB	£33.46 +£5.02

(Standard O-P Transistors)


CHOOSE AN I.L.P BIPOLAR POWER AMP

where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distor- tion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
НУ30	15W into 4-8Ω	0.015%	15V /μs	5μs	100dB	£7.29 +£1/09
HY60	30W into 4-8Ω	0.015%	15V/µs	5μs	100dB	£8.33 +£1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 +£2.62
HY200	120W into 4-8Ω	0.01%	15V /μs	5μs	100dB	£21.21 +£3.18
HY400	240W into 4Ω	0.01%	15V /μs	5µs	100dB	£31.83 +£4.77

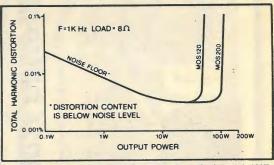

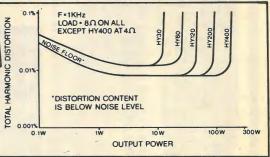Load impedance both models $\begin{array}{ll} \text{Load impedance both models 100K} \Omega \\ \text{4}\Omega - \infty \text{ Input sensitivity both} \\ \text{models 500mV} \end{array}$ Input impedance both models Frequency response both models 15Hz-100KHz - 3dB



Load impedance all models 4Ω - ∞ Input impedance all models 100K Ω Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz - 3dB



THE NEW PROFILE EXTRUSIONS

The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages:—
Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.



HY120

HY60

NO QUIBBLE 5 YEAR GUARANTEE 7-DAY DESPATCH ON ALL ORDERS BRITISH DESIGN AND MANUFACTURE FREEPOST SERVICE

NEW PRE-AMPS


HY6 (mono) and HY66 (stereo) are new to I.L.P's range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.

Sizes — HY6 — 45 × 20 × 40 mm. HY66 — 90 × 20 × 40 mm. Active Tone Control circuits provide ±12dB cut and boost. Inputs Sensitivity — Mag. PU. —3mV: Mic — selectable 1-12mV: All others 100mV. Tape O/P — 100mV: Main O/P — 500mV: Frequency response — D.C. to 100KHz — 3dB.

500mV: Frequency response - D.C. to 100KHz - 3dB.

HY6 mono £6.44+97p VAT Connectors included HY66 stereo £12.19+£1.83 VAT Connectors included B6 Mounting Board for one HY6 78p+12p VAT

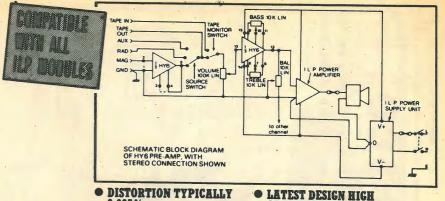B66 Mounting Board for one HY66 99p + 15p VAT



Mag. P.U.

DISTORTION TYPICALLY

 S/N RATIO — 90dB (Mag. P.U. — 68 dB) 38 dB overload margin on **QUALITY CONNECTORS**

ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING

NEEDS ONLY UNREGULATED POWER SUPPLY ±15 to ±60v

NEW POWER SUPPLY UNITS

£10.94 + £1.64 VAT

£13.04+£1.96 VAT

£13.32 + £2.00 VAT

£15.92 + £2.39 VAT

£16.20 + £2.43 VAT £16.20 + £2.43 VAT

£16.32 + £2.45 VAT

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P amps and pre-amps with types to match whatever I.L.P power amps you choose.

PSU30 ± 15V at 100mA to drive up to 12 x HY6 or 6 x HY66

■ THE FOLLOWING WILL ALSO DRIVE I.L.P PRE-AMPS £4.50 + 0.68p VAT £8.10+£1.22 VAT

PSU36 for use with 1 or 2 HY30's ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS PSU50 for use with 1 or 2 HY60's

PSU60 for use with 1 HY120 PSU65 for use with 1 MOS120 PSU70 for use with 1 or 2 HY 120's PSU75 for use with 1 or 2 MOS120 PSU90 for use with 1 HY200 PSU95 for use with 1 MOS200

PSU180 for use with 1 HY400 or 2 HY200 PSU185 for use with 1 or 2 MOS200

£21.46 + £3.22 VAT ★ Freepost facility When ordering or writing about I.L.P products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

TO ORDER Send cheque or money order payable to I.L.P Electronics Ltd and crossed. Or pay by ACCESS or BARCLAY CARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.



TEN YEARS OF PLANNED **PROGRESS**

When, in 1971, lan L. Potts founded his now world-famous company, he saw the need for a different and more rational approach to exploiting to the full, the potential that lay in modular construction. New thinking was badly needed. The result was a range of modules revolutionary in concept. The rightness of this new thinking is shown by the size of the company today, its new factory, its vast exports, its acceptance by constructors as the modules to build with. The range grows bigger and better. Exciting new lines (in no way conflicting with existing ones) are well past drawing board stage. This is why I.L.P are simply ahead and staying there.

ALDESOS

BRITAIN'S FOREMOST QUALITY MODULE SUPPLIERS

1	
	To: I.L.P ELECTRONICS LTD. CANTERBURY CT2 7EP
	Please supply
	Total purchase price £
	I enclose Cheque Postal Orders International Money Order
	Please debit my Access/Barclaycard Account No.
	NAME
	ADDRESS
-	AD E
	Signature
	Signature



Telephone (0227) 54778 [Technical (0227) 64723] Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

WW - 068 FOR FURTHER DETAILS

Freepost F B19 1BR

■ FREEPOST ON ORDERS • ACCESS Birmingham VAT INCLUSIVE PRICES VISA · CASH

■ ADD 30p P&P 021-233-2400 ■ 24 HR PHONE ANSWERING SERVICE

ALL PRICES IN PENCE EACH UNLESS OTHERWISE STATED

C-MO	S 'BUE	ERED)			LINEAR	SEMICON	DUCTO	DRS	
HEE4000	22	HEF4044	105 (HFF4512 138 I	CA3046 84 I	IN914	5 1	BC182L	12
HEF4000	22	HEF4046	133	HEF4516 127	CA3080E 77	IN4001	5	BC184	11
HEF4002	22	HFF4047	109	HEF4517 478	CA3130E 99	IN4002	5	BC184L	12
HEF4002	119	HEF4049	57	HEF4518 118	CA3140E 48	IN4004	7	BC212	11
HFF4007	22	HEF4050	57	HEF4519 69	CA3189E 293	IN4007	9	BC212L	12
HFF4008	100	HEF4051	87	HEF4520 118	LM301AN 34	IN4148	4	BC214	11
HEF4011	22	HEF4052	90	HEF4521 235	LM339N 78	IN5402	15	BC214L	12
HEF4012	22	HEF4053	90	HEF4528 124	LM380N 104	2N2369	21	BC547	13
HEF4013	57	HEF4066	62	HEF4532 150	LM381AN 198	2N2646	46	BC548	11
HEF4014	105	HEF4067	475	HEF4534 638	LM3900N 75	2N2926G	13	BC549	12
HEF4015	100	HEF4068	22	HEF4539 138	MC3403P 156	2N3053	19	BC557	15
HEF4016	57	HEF4069	22	HEF4585 122	NE531 131	2N3054	55	BC558	15
HEF4017	100	HEF4070	22	HEF4724 214	NE536T 259	2N3055	55	BCY70	15
HEF4018	100	HEF4071	23	HEF40097 113	NE555N 28	2N3702	9	BCY71	15
HEF4019	58	HEF4072	23	HEF40098 92	NE556N 66	2N3704	9	BD131	39
HEF4020	112	HEF4073	23	HEF40106 78	NE566N 171	2N3705	10	BD132	39
HEF4023	107	HEF4075	23	HEF40160 149	NE570N 485	2N3773	297	-BD139	39
HEF4022	103	HEF4076	130	HEF40192 149	NE571N 505	2N3819	22	BD140	39
HEF4023	22	HEF4077	22		RC4136 146	2N3B20	39	BFR90	333
HEF4024	. 78	HEF4078	23	Voltage	TBA120S 88	2N3904	9	BFX85	29
HEF4025	22	HEF4081	23		TDA1022 713	2N5457	39	BFY50	17
HEF4026	244	HEF4082	23	Regulators	TDA1034B 239	2N5459	35	BFY51	17
HEF4027	57	HEF4085	80	LM309DA(K) 119	TL081CP 84	40673	88	BRY39	50
HEF4028	89	HEF4086	80	UA723CN 42	TL084CN 156	BC107	14	BSX20	21
HEF4029	113	HEF4093	63	UA7805CU 78	UA741CN 20	BC108	14	CL8960	2850
HEF4030	58	HEF4094	219	UA7812CU 78	UA741CT 47	BC108C	18	TIP31	48
HEF4031	250	HEF4104	208	UA7815CU 78	Zener	BC109	14	TIP32	54
HEF4035	138	HEF4502	114	UA7912CU 97		BC109B	19	TIP41C	76
HEF4040	107	HEF4505	714	UA7915CU 97	Diodes	BC109C	20	TIP42C	76
HEF4041	94	HEF4508	230	UA78L05CS 3B	400mW C4V7-C33	BC148	10	TIP2955	75
nEF4041	83	HEF4510	135	UA7BL12CS 38	BZY88/BZX79	BC158	10	TIP3055	60
		HEF4511	157	UA7BL15CS 38	+ Voltage 9	BC177	17	TIS43	36
HEF4043	100			UA78L15CS 38	+ Voltage 9	BC177	17	TIS43	36

CAPAC Electroly	tic A	cial (Order (Polyeste Dipped 1				Orde	r Code	Electroly1	tic R	adial			Cap		+ μF
μF ∨ 1.0	16	26	40	63	Moulded	Type, 1	0.2mm F	itch		Cap 360 Value	μF V	10	18	25	35	40	50	63
1.5 2.2 3.3 4.7 6.8 10 15 22 33 47 68 100 150 220 330	8 8 9 9	8 8 8 9	9 9 11 13 26 30	9 9 9 9 10 10 11 13 13 31 36 40	μF .001 .0015 .0022 .0033 .0047 .0068 .01 .015 .022 .033 .047 .068	352 6 6 6 6 6 6 6 6 7	360 7 7 7 7 7 7 7 8 8 8 8 8	μF .1 .15 .22 .33 .47 .68 1.0 1.5 2.2	362 7 8 9 11 14 17 21 30 35	360 9 10 11	.68 1.0 1.5 2.2 3.3 4.7 6.8 10 15 22 33 47 68 100 150	7 6 9	7 7 8 8 9 9	7 B 9	11	7 8 9	B 9 11	7 7 7 7 7 8 9 9 11
470 880 1000 1500 2200	21 25 35 42	23 30 30 39	32 39 59	54	B Pin L 14 Pin L 16 Pin L	ow Prof		t Tin	14 DI	L SKT 8 L SKT 14 L SKT 16	P.C.B. C Dato Pen.				Dry	ing		69

RESISTORS	Order Code	Skeleton Presets, Miniature		Order Code
Carbon Film, Fixed		0.1W, E3 Values, 100R-IM, Lin. Vertical Mountaing	8	Min. Preset V
0.25W, E24 Values IRO-10M, 5% Tol.	2 each Res BD%	0.1W, E3 Values, 100R-IM, Lin. Horizontal Mount	8	Min. Preset h
100/100 (Mult 10	/Value)	Skeleton Presets, Standard		+ Value
0.5W, E12 Values IRO-4M7, 10% Tol.		0.3W, E3 Values, 100R-4M7, Lin. Vertical Mounting	11	Std. Preset V
0.011, 2.12 10.121	+ Value	0.3W, E3 Values, 100R-4M7, Lin. Horizontal Mount		Std. Preset H
Metal Film, Fixed		Potentiometer, Rotary		+ Value
0.5W, E24 Values, SRI-IM, 2% Tol.	8 each Res MR30		39	Ro Pot Lin
2.5W, E12 Values, 10R-27K, 5% Tol.	16 each Res PR52		39	Ro Pot Log
	+ Value		-	+ Value
to de la constantina		Potentiometer, Slider		
Metal Glaze, Fixed			45	SI Pot Lin
0.5W, E24 Values, IM-33M, 5% Tol.	16 each Res VR37	0.25W, E3 Values, 1K0 - 1M0 Log.	45	Si Pot Log
0.011, 02. 10.011,	+ Value			+ Value


MAINS TRANSFORMERS Order Co	ode Plastic Boxes - Bos	Industrial Mo	ouldings
Secondaries may be connected in series or	Moulded 8ox and Clos		
parallel to give wide voltage range	A8S Box, C/W Brass B	ushes, and Lid Ir	Orange
Primaries 0-220, 240V			Order Code
	L112 W62 D31	99	Case BIM2003 OF
6VA Clamp Type Construction 235 each	L150 W80 D50	131	Case BIM2005 OF
Approx 18% Regulation F.C. 54, H36, W35	L190 W110 D80	223	Casa BIM2006 OF
0-4.5V, 0-4.5V Secondaries Trans 6VA	Plastic Boxes with M	fetal Lids	
0-3V, 0-6V	Recessed Top Box		
0-12V, 0-12V	ABS Base, C/W Bress E	lushes. In Orange	
0-15V, 0-15V	1mm Aluminium Top		rav
0-20V, 0-20V			Order Code
	L85 W56 D29	112	Case B1M4003 OF
20VA - Clamp Type Construction 360 each	L111 W71 D42	150	Case BIM4004 OF
Approx. 16% Regulation F.C. 70, H4B, W45	L161 W96 D53	208	Case BIM4005 OF
0-4.5V, 0-4.5V Secondaries . Trans 20VA	Discast Boxes		
0.6V, 0.6V	Diecest Box and Flance	ed Lid	
0-12V, 0-12V	Aluminium Box and L		istr
0-15V, 0-15V			Order Code
0-17.5V, 0-17 5V	L113 W63 D31	124	Case BIM5003 NA
0-20V, 0-20V	L152 W82 D50	215	Case BIM5005 NA
	1 400 HILLS DOL	. 224	Core DIMEGOR NA

			L192 W	V113 D61	334	Case	BIM5006 NA
VERO ELECTRONICS PROD 2.5" x 5" .1" pitch Veroboard 3.75" x 5" .1" pitch Veroboard 2.5" x 1" .1" pitch Veroboard 2.5" x 1" .1" pitch Veroboard (5)	71 79 85/Pack	200-21069J 200-21072D 200-21076C	SWITO	CHES ure Toggle H	oneywell		Order Code
3.75" x 5" .1" pitch Plain Board 5.82" x 2.9" .1" pitch V-Q DIP Board	88 135	200-21078H 200-21084E	SPDT	C/Off		67 81	SW BA1011 SW BA1021
Spot Face Cutter Pin Insertion Tool for .040 type pin	107 147	203-21013A 203-21015F	DPDT DPDT	C/Off	o Centre	90 99	SW 8A2011 SW 8A2021
DS Pins .040 (100) SS Pins .040 (100) Verowire Kit (1-pen, 2-wire, 25-comb)	44/Pack 44/Pack 4 454/Kit	200-21087G 200-21017B 200-21341D		ure Push — C &	K		
Verowire Combs (25) Verowire Wire (2)	109/Peck 109/Pack	200-21339F 200-21340G	SP SP	Push To Make Push To Bresk		62 62	SW 8531 SW 8533

۰				
	GMT ELECTRONICS PROJECTS	KIT	BUILT UP	
	FREE-STANDING COMPLETE TELETEXT UNIT - FULL SPEC	£199-90	£275-00	
	TELETEXT DECODER BOARD + REMOTE HAND CONTROL	£135-90	£160-00	
	TELETEXT COMPATIBLE TUNER AND P.S.U.	£ 46-90	£ .57-00	
	TELETEXT COMPATIBLE PAL ENCODER + MODULATOR	£ 22-90	£ 35-00	
	F.E.T.OUTPUT 100W MONO POWER AMPLIFIER MODULE	£ 27-50	£ 35-00	
	X-BAND DOPPLER RADAR ALARM MODULE - MARK II	£ 35-90	£ 44-00	
	ONE AMP P.S.U. MODULE (SPECIFY 5 OR 12 VOLTS)	£ 7-50	£ 10-00	
	SIMULATED INERTIA MODEL TRAIN CONTROLLER	£ 22-50	£ 35-00	
	SIMULATED INERTIA SLOT RACER CONTROLLER	£ 27-50	£ 40-00	
	MODEL TRAIN STEAM SOUND SIMULATOR MODULE	£ N/A	£ 5-00	

WW - 069 FOR FURTHER DETAILS

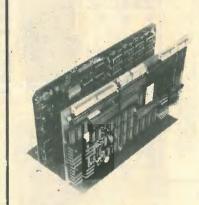Do You Have All These Facilities On Your S 100 System, With Just Two **Boards?**



1. Z80A CPU-2 or 4 MHz

Operation. Z80A CTC — 4 Channels Z80A S10 — 2 RS-232. Z80A P10.

Disk controller; Takes up to 4 disk drives, single or double density operation. 64k Bytes of memory.

EPROM Programmer

Real time clock. Software; Standard 2k Monitor. CP/M Cold Start Loader. CP/M B10S (1.4).

£495.50 FDC-1 Board £327.56 Expandoram Mother Board All prices exclude VAT.

£42.00

SEMEL

MICROCOMPUTER - HARDWARE - SOFTWARE

3c Barley Market Street, Tavistock, Devon PL19 0JF Tel. Tavistock (0822) 5247. Telex: 45263

CLEF ELECTRONIC MUSIC



SIX OCTAVES 6207

2

The most advanced form of Touch Sensitive

y patented

technique.
Four mixable
voices for

serious tone variation plus

electronic chorus and flanger
effects. See lists
for Cabinets, P.A.
and Manufac-



Built sequence opera-Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carr. & Ins. and we operate Telephone BARCLAY-CARD. Visit our Showroom.

CLEF PRODUCTS (ELECTRONICS) LIMITED

Dept. W. 44a Bramhall Lane South Bramhall, Stockport, Cheshire SK7 1AH 061-439 3297

WW - 044 FOR FURTHER DETAILS

HIGH PERFORMANCE BUT LOW COST— **AUDIO SIGNAL GENERATORS** SINE/SQUARE WAVE

Model 146-9. Distortion .0015% (at 1 Khz). Range 10hz-100Khz. Output 1v RMS (600 ohms).

Component ture.

UK P/P £2. Overseas from £5.50.



Model A0113 Distortion .02% (1 Khz) otherwise as 146.9.

TELERADIO ELECTRONICS

325 Fore Street, Edmonton, London, N9 0PE Tel: 807 3719
Also available: R.F. Sig. Gen. P.S.U. T.H.D. Analyser, Frequency Meter, MVMT

PORTABLE CABINETS

RADIO CASE Size: 11 x 8 x 3¾ ins approx. Made from plyapprox. Made from ply-wood, pleasingly covered. Suitable for any normal radio circuit. Has studs for mounting 5" speaker and the front is drilled to take a tuning conden-sor in the centre and pormal controls either. normal controls either side. £2.30 + £1.50 post.

LAST MONTH'S SNIP -- STILL AVAILABLE

LAST MONTH'S SNIP -- STILL AVAILABLE
And it still carries a free gift of a desoldering pump, which we are
currently selling at £6.35p. The snip is perhaps the most useful breakdown parcel we have ever offered. It is a parcel of 50 nearly all
different computer panels containing parts which must have cost at
least £500. On these boards you will find over 300 IC's. Over 300
diodes, over 200 transistors and several thousand other parts, resistors, condensors, multi-turn pots, recifiers, SCR, etc. etc. If you act
promptly, you can have this parcel for only £8.50, which when you
deduct the value of the desoldering pump, works out to just a little
over 4p per panel. Surely this is a bargain you should not miss!
When ordering please add £2.50 post and £1.27 VAT.



MAINS MOTORS Precision made as MAINS MOTORS Precision made as used in record players, blow heaters, etc.

Speed usually 1,400. All have ample spindle length for coupling fan blade, pulley, etc. Power depends on stack size. 5/8" stack £2.00; %" stack £2.50; 7/8" stack £3.00,1" stack £3.50; 1½" stack £4.50. Add 25% to motor cost to cover postage, and then add 15% VAT.

YOUR LAST CHANCE FOR THIS BARGAIN 100 twist drills, regular tool shop price over £50, yours for only £11.50. With these you will be able to drill metal, wood, plastic, etc. from the tiniest holes in P.C.B. right up to about ¼". Don't miss this snip — send your order today.

MAGNETIC LATCH Low voltage (4 - 8 volt AC/DC operation).
Only £1.50 each.

PUNCHED TAPE EQUIPMENT

or controlling machine tools, etc, motorised 8 bit punch with atching tape reader. Ex-computers, believed ingood working der, any not so would be exchanded. £17.50/pair. Post £3.00.

STEREO HEADPHONES Japanese made so very good quality 8 ohm impedance, padded, termplug. £2.99 Post 60n

BRIDGE RECIFIER 1 amp 400v 30p each. 10 for £2.50, 100 for £20.00



SOLENOID WITH Mains operated £1.99 10 - 12 volts DC operated £1.50.

MOTORISED DISCO SWITCH With 10 amp changeover switches. Multiadjustable switches all rated at 10 amps,
this would provide a magnificent display.
For mains operated 8 switch model
£6.25, 10 switch model £6.75, 12 switch
model £7.25.



PANEL METERS

PANEL ME I EMS
Japanese made, full vision front, size 2½"
x 2½". 0 - 100 uA £2.85. Similar but size
2" x 1½" 100 uA, scaled Vu. Ditto, but
scaled 0 - 100. (note: front covers easily
removable if you want to rescale these
£2.30 each) Ditto but size 1½"x 1¾", scalx 150. ed Vu, sensitivity 100 uA, £1.50.

MINI-MULTI TESTER Deluxe pocket size precision moving pilcoil instrument, jewelled bearings — 2000 o.p.v. mirrored scale.

I instant range measures: DC volts 10, 50, 250, 1000.

AC volts 10, 50, 250, 1000.

DC amps 0 — 100 mA.

Continuity and resistance 0 - 1 meg ohms in two ranges. Complete with test prods and insruction book showing how to measure capacity and inductance as welf. Unbelievable value at only £6.75 + 50p post and insurance. FREE Amps range kit to enble you to read

DC current from 0 - 10 amps, directly on the 0 - 10 scale. It's free if you purchase quickly, but of you already own a Mini-Tester and would like one, send £2.50.

SUPER HI-FI SPEAKER

he completed unit is most pleas our black, Supplied in pairs price £6.90 per pair (this is prob ably less than the original cost of one cabinet) carriage £3,50 the pair

Made for an expensive Hi-Fi outfit
— will suit any decor. Resonance
free cut-outs for 8" woofer and
4" tweeter. The front material is
carved Dacron, which is thick and
does not need to be stuck in and

LOUDSPEAKERS 8" woofer and 4" tweeter, 4 ohms 35 watts power rating £6.90 per pair Ditto but 8 ohms, £11.50

per pair. Post £2.00.

T.

ELECTRONIC VOLT-METER/ SENSITIVE RELAY

Consists of a 4½" square drop through panel volt meter, 0 - 10 fed. Built into the front of the meter are two screw adjusters which move two pointers, up and c wn the scale, to set a minimum a 3 maximum. A unique "under" at 3 "over" circuit inside the meter of states one of two reed relays to bring an 'under' or 'over' circuit into action. The scale plate is detachable via two screws to be calibrated to your own individual requirements. The 10 transistor 'under' and 'over' circuit is completely separate from the meter movement and 'over' circuit is completely separate from the meter movement. nd 'over' circuit is completely separate from the meter mo so does not have to be connected to use this as a standard 0 - 1 meter. Many uses including level controls, light controls, auto bat tery chargers, alarm units, etc. Manufacturers list price of over £120 each. An unbelievable snip at £9.95 (less than the value of

THIS MONTH'S SNIP

Vu METER Approximately 1 5/8" square, sensitivity 0 - 500 uA suitable for use also as a recording level meter, power output indicator or many similar applications. Full scale. Special snip price £1, or 10 for £9, post & VAT paid



stereo amplifier. Made for incorporation in a high-class radiogram, this has a quality of our put which can only be described as superb. It size is approx, 14". Push but

tons select long, medium, short and gram. Controls are balance, volume, treble and bass. Mains power supply. The output is 6 + 6 watts. Brand new and in perfections and the selection of the sel

alone, namely £6.90. Post £2.50.

MULLARD UNILEX A Par

MULLARD UNILEX
A mains operated 4 + 4 stereo
system. Rated one of the
finest performers in the
stereo field this would
make a wonderful gift for
almost anyone. In easy to assemble
modular form this should sell at about £30
— but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16.75 including VAT and post.
FREE GIFT — buy this month and you will receive a pair of
Goodman's eliptical 3"x5" speakers to match this amplifier.

VENNER TIME SWITCH Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthe

automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are new but without case, but we can supply plastic cases (base and cover) £1.75 or metal case with window £2.95. Also available is adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/offs per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30. DELAY SWITCH

Mains operated – delay can be accurately set with pointers knob for periods of up to 2½hrs. 2 contacts suitable to switch 10 amps – second contact opens a few minutes after 1st contact. £1.95.

LEVEL METER Size approximately ¾" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200 uA. 75p.

ADVANCE ADVERTISING BARGAINS LIST! Our FREE monthly list gives details of bargains arriving or just arrived — often bargains which sell out before our advertisemen appear — it's an interesting list and it's free — just send S.A.E. Below are a few of the Bargains still available.

TRANSMITTER SURVEILLANCE
Tiny, easily hidden but which will enable conversation to be picked
up with FM radio. Can be made in a matchbox — all electronic
parts and circuit. £2.30.

RADIO MIKE

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90 comp. kit.

Mains quick connector will save you valuable time. Features include quick spring connectors, heavy plastic case and auto on and off switch. Complete kit. £1.95.

LIGHT CHASER

Gives a brilliant display — a psychedelic light show for discos, parties and pop groups. These have three modes of flashing, two chase patterns and a strobe effect. Total output power 750 watts per channel. Comlete kit. Price £16. Ready made up £4 extra.

FISH BITE INDICATOR

Enables anglers to set up several lines then sit down and read a book. As soon as one has a bite the loudspeaker emits a shrill note. Kit.

Frice 24.90.

6 WAVEBAND SHORTWAVE RADIO KIT

Bandspread covering 13.5 to 32 metres. Based on circuit which appeared in a recent issue of Radio Constructor. Complete kit includes case materials, six transistors, and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy if you have an applification. amplifier to connect it to or a pair of high resistance headphones.

Price £11.95.

SHORT WAVE CRYSTAL RADIO
All the parts to make up the beginner's model. Price £2.30. Crystal
earpiece 55p, High resistance headphones (gives best results) £3.75.
Kit includes chassis and front but not case.

RADIO STETHOSCOPE Easy to fault find — start at the arial and work towards the speaker — when signal stops you have found the fault. Complete kit £4.95.

INTERRUPTED BEAM This kit enables you to make a switch that will trigger when a steady beam of infra-red or ordinary light is broken. Main compon-

ents — relay, photo transistor, resistors and caps etc. Circuit diagram but no case. Price £2.30 OUR CAR STARTER AND CHARGER KIT has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £11.50 + £2.50 post.

garage, whichever suits you best. Price £11.50 + £2.50 post. GPO HIGH GAIN AMP/SIGNAL TRACER. In case measuring only 5½ in x 3½ in x 1½ in s an extremely high gain (70dB) solid state amplifier designed for use as a signal tracer on GPO cables, etc. With a radio it functions very well as a signal tracer. By connecting a simple coil to the input socket a useful mains cable tracer can be made. Runs on standard 4½ battery and has input, output sockets and on-off volume control, mounted flush on the top. Many other uses include general purpose amp, cueing amp, etc. An absolute bargain at only £1.85. Suitable 80ohm earpiece 69p.

3 CHANNEL SOUND TO LIGHT KIT

Complete kit of parts for a three-channel sound to light unit con-trolling over 2,000 watts of lighting. Use this at home if you wish, but it is more than rugged enough for Disco work. The unit is hous ed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by %" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Price £14.95, complete kit and case.

8 POWERFUL BATTERY MOTORS r models, Meccanos, drills, remote control planes, boats etc. £2.50.

WATERPROOF HEATING WIRE 60 ohms per yard, this is a heating element wound on a fibre glass coil and then covered with p.v.c. Dozens of uses — around water pipes, under grow boxes in gloves and socks. 23p per metre.

COMPONENT BOARD Ref. W0998

This is a modern fibreglass board which contains a multitude of Ihis is a modern fibreglass board which contains a multitude of very useful parts, most important of which are: \$5 assorted diodes and rectifiers including 4 3amp 400v types (made up in a bridge) 8 transistors type BC 107 and 2 type BFY 51 electrolytic condensers. SCR ref 2N 5062, 25 Ouf 100v DC and 100uf 25v DC and over 100 other parts including variable, fixed and wire wound resistors, electrolytic and other condensers. A real snip at £1.15.

FRUIT MACHINE HEART. 4 wheels with all fruits, motorised and with solenoits for storping the wheels with all fittin incontinuous.

with solenoids for stopping the wheels with a little ingenuity you can defy your friends getting the "jackpot". £9.95. + £4 carriage. DESCUERING PUMP

4-CORE FLEX CABLE White pvc for telephone extensions, disco lights, etc. 10 metres £2, 100 metres £15. Other multicore cable in stock.

MUGGER DETERRENT
A high-note bleeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

HUMIDITY SWITCH

American made by Honeywell. The action of this device depends upon the dampness causing a membrane to stretch and trigger a sensitive microswitch. Very sensitive breathing on it for instance wi switch it on. Micro 3 amp at 250V a.c. Only £1.15.

EXTRACTOR FANS — Mains Voltage

Ex-Computer, made by Woods of Colchester, ideal also as blower; central heating systems, fume extraction etc. Easy fixing through panel, very powerful 2,500 rpm but quiet running. Choice of 2 sizes, 5" £5.50. 6" £6.50. post £1 per fan.



TIME SWITCH BARGAIN Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs. £2,50.

J. BULL (Electrical) Ltd.

(Dept. WW), 34 - 36 AMERICA LANE HAYWARDS HEATH, SUSSEX RH16 3QU. J. BULL (Electrical) Ltd — Established 25 years. MAIL ORDER TERMS: Cash with order -- please add 60p to all orders under £10, to offset packing, etc. ACCESS & BARCLAYCARD WELCOMED. Our shop is open to callers. BULK ENQUIRIES INVITED. Telephone: Haywards Heath (0444) 54563.

NEW HIGH PERFORMANCE TUNER

A high-quality push-button FM Varicap Stereo Tuner with pilot cancel decoder combined with a 24W r.m.s. per channel Stereo Amplifier, using Bifet op. amps.



Brief Spec. Amplifier Low field Toroidal transformer, Mag. input. Tape In / Out facility (for noise reduction unit, etc.) THD less than 0-1% at 20W into 8 ohms. High Slew Rate. Low noise op. amps used throughout. Power on / off FET transient protection. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section uses UM 1181 FET module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC pilot cancel, stereo decoder, LED tuning and stereo indicators. Tuning range 88-108MHz 30dB mono S/N @ 0.7 µV. THD 0.3%. PRICE: £69.95 + VAT

NELSON-JONES Mk. 2 STEREO FM

A very high performance tuner with dual gate MOSFET RF and Mixer ready built front end, triple gang varicap tuning, linear phase I.F. and 3 state MPX de-

PRICE: £74.95 + VAT



NRDC-AMBISONIC UHJ SURROUND SOUND DECODER



The **first ever** kit specially produced by Integrex for this British NRDC backed surround sound system which is the result of 7 years' research by the Ambisonic team. W.W. July, Aug., '77. The unit is designed to decode not only UHJ but virtually all other 'quadrophonic' systems (Not CD4), including the new BBC HJ. 10 input selections. The decoder is linear throughout and does not rely on listener fatiguing logic enhancement techniques. Both 2 or 2 input signals and 4 or 6 output signals are provided in this most versatile unit Complete with mains power supply, wooden cabinet, panel, knobs, etc.

Complete kit, including licence fee £57.70 + VAT or ready built and tested £76.95 + VAT

S5050A STEREO AMP

50 watts rms-channel. 0.015% THD. S/N 90 dB, Mags/n 80 dB. Output device

rating 360w per channel.

Tone cancel switch, 2 tape monitor switches. Metal case — comprehensive

Complete kit only £69.95 + VAT



(Also available our 20w/ch BIFET S2020 Amp)

INTRUDER 1 Mk. 2 RADAR ALARM With Home Office Type approval

The original "Wireless World" published Intruder 1 has been re-designed by Integrex to incorporate several new features, along with improved performance. The kit is even easier to build. The internal audible alarm turns off after approximately 40 seconds and the unit re-arms. 240V ac mains or 12V battery operated. Disguised as a hard-backed book. Detection range up to 45 feet. Internal mains rated voltage free contacts for external bells

Complete kit £52.50 plus VAT, or ready built and tested £68.50 plus VAT.

Wireless World Dolby noise reducer Typical performance Noise reduction better than 9dB weighted. Clipping level 16.5dB above Dolby level (measured at 1% third



Complete Kit PRICE: £49.95 + VAT (3 head model available)

Calibration tapes are available for open-reel use and for cassette (specify which) Single channel plug-in Dolby (TM) PROCESSOR BOARDS (92 x 87mm) with gold plated contacts and all components

We guarantee full after-sales technical and servicing facilities on all our kits, have you checked that these services are available from other suppliers?



BARCLAYCARD VISA

Price £2.75 + VAT

Price £10.50 + VAT

Please send SAE for complete lists and specifications

Portwood Industrial Estate, Church Gresley, **Burton-on-Trent, Staffs DE11 9PT** Burton-on-Trent (0283) 215432 Telex 377106

Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12% Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level at Monitor output WIRELESS WORLD APRIL 1981

ANGREX SUPPLIES LT Climax House, Fallsbrook Rd., Streatham, London SW16 6ED

Tel: 01-677 2424 Telex: 946708

1131	1 e	1: 01-6/	1 2424	elex:	946/0	8		K5 I
AA119	BC172 0.13 BC173 0.13 BC173 0.13 BC173 0.13 BC173 0.16 BC178 0.16 BC178 0.16 BC178 0.16 BC178 0.18 BC178 0.18 BC182 0.13 BC182 0.13 BC182 0.13 BC212 0.13 BC213 0.13 BC213 0.13 BC213 0.13 BC213 0.13 BC214 0.13 BC213 0.13 BC214 0.13 BC213 0.13 BC214 0.13 BC214 0.13 BC215 0.14 BC215 0.15 BC215	BD131	2.30 OAS 1.38 1.50 OA7 0.80 1.73 OA10 0.83 2.30 OA70 0.29 0.46 OA79 0.41 0.15 OA81 0.20 0.20 OA85 0.20 0.12 OA91 0.80 0.12 OA91 0.80 0.12 OA91 0.80 0.12 OA91 0.80 0.80 OA90 0.77 0.89 OA200 0.17	OAZ201 1.72 OAZ205 1.73 OAZ207 1.73 OAZ207 1.73 OCC20 2.88 OCC22 2.88 OCC22 4.80 OCC24 4.80 OCC25 1.15 OCC26 1.73 OCC36 1.73 OCC36 1.73 OCC36 1.73 OCC37 0.73 OCC41 1.04 OCC41 1.04 OCC41 1.04 OCC41 1.04 OCC57 0.73 OCC77 1.15 OCC77 1.15 OCC77 1.15 OCC77 1.15 OCC77 1.15 OCC77 1.15 OCC81 1.38 OCC82 0.92 OCC83 0.92 OCC83 0.92 OCC83 0.92 OCC83 0.92 OCC83 0.92 OCC83 0.92 OCC84 0.93 OCC85 0.93 OCC85 0.93 OCC81 1.98 OCC81 1	OC298 3.45 OC294 3.43 OC295 3.16 OC296 3.16 OC296 3.16 OC296 3.16 OC297 2.88 OCP71 2.39 ORP12 1.15 R2098 2.59 R2009 2.59. R20108 2.30 R2010 0.30 R20108 2.30 R2010	ZTX502	2N1309 1.38 2N1613 0.37 2N1617 1.73 2N1683 0.37 2N2147 4.60 2N2148 4.31 2N2219 0.37 2N2219 0.32 2N221 0.23 2N221 0.23 2N221 0.23 2N222 0.23 2N222 0.24 2N2288 0.20 2N2289 0.37 2N229 0.37 2N290 0.37 2	2N3771 1.61 2N3772 1.84 2N3773 2.67 2N3819 0.35 2N3820 0.45 2N3823 0.69 2N3866 1.15 2N3804 0.20 2N3866 0.20 2N4658 0.21 2N4659 0.23 2N4669 0.18 2N4661 0.18 2N4124 0.18 2N4125 0.18 2N4565 0.17 2N4586 0.17 2N5456
VALVES	EF86 1.74 CEP86 1.84 EF91 2.87 CEP87 1.84 EF91 2.87 CEP87 1.84 EF91 2.87 CEP87 1.84 EF91 2.87 CEP88 1.84 EF91 1.24 CEP88 1.25 CEP\$8	16.10	1.38 QY5-3000A 1.38 QY5-3000A 1.38 QZ06-20 38.48 1.38 R10 5.78 1.39 R17 1.89 1.30 R18 4.89 1.31 1.51 R20 1.68 1.81 1.51 R20 1.68 1.81 1.51 R20 1.68 1.82 1.84 1.84 1.84 1.84 1.85 1.80 8.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.84 1.85 1.84 1.84 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.84 1.85 1.85 1.85 1.84 1.85 1.85 1.85 1.85 1.8	UY41 1.44 UY45 1.49 VISS3 1.52 VISS3 1.62 VISS3 1.63 VI	58254M 23.12 58255M 23.12 58255M 23.12 58255M 23.12 58255M 23.12 58262 74.75 58146P 2.30 5846P 2.30	EBBS 2.44 6EW6 1.73 6F6 2.02 6F23 1.84 6EW6 1.73 6F6 2.02 6F23 1.84 6EW6 1.73 6F33 29.99 6H1 1.33 6F33 29.99 6H1 1.33 6H2N 1.21 6H3N 1.21 6H3N 1.21 6H3N 1.21 6H3N 1.21 6H3N 1.21 6H6 1.73 6K4N 1.44 6K6GT 1.59 6K7 2.67 6K7 1.73 6K6G 2.88 6LGG 7.81 6KGG 2.88 6LGG 7.81 6KGG 2.88 6LGG 7.81 6KGG 1.73 6F7	12E11TT	5718 7.87 5725 5.82 5726 5.82 5727 5.42 5727 5.42 5727 5.42 5727 5.42 5727 5.42 5727 5.42 5727 5.42 5727 5.42 5727 5.42 5727 5.42 5739 5.14 5751 1.30 5876A 1.25 5876 1.55 5879 5.38 5886 1.20 5963 3.38 5963 3.38 5963 3.38 5963 3.38 5963 3.38 5963 3.38 5963 3.38 5963 3.38 5963 3.38 5963 3.38 5963 3.38 5963 4.00 6005 5.62 6005 5.62 6005 1.20 6005 1.20 6005 1.20 6005 1.20 6005 1.20 6005 1.20 6005 1.20 6005 1.20 6005 1.20 6006 1.20 6006 1.20 6006 1.20 6007 4.02 6007 4.02 6007 4.02 6008 1.27 6008 1.27 608 1.27 608 1.27 618 10.03 6146 10.03 6146 10.03 6146 10.03 6146 10.03
BASES B7G unskirted 0.35 B9A unskirted 0.40 B9A skirted 0.40 B9A skirted 0.40 Loctal 0.40 Loctal 0.40 Loctal 0.40 Loctal 0.53 Nuvistor base 0.86 B pin DIL 0.17 14 pin DIL 0.17 16 pin DIL 0.17 16 pin DIL 0.17 20 Valve screening cans all sizes 0.35 BP1 0.30 SRP1 0.30	5 5BPI 11.50 V 5 5CPI 11.50 V 5 5CPIA 44.00 V 5 5FPI5A 17.25 T 5 UP7 16.10 P D DG7-5 28.75 a D DG7-32 41.40 DH3-91 35.65 DH7-11 78.20 VCR97 13.90	7400 7401 7402 7402 7402 7402 7403 7404 7408 7408 7408 7408 7408 7408 7408	EGRATED CIF 0.18 7423 0.38 0.20 7425 0.35 0.20 7425 0.35 0.20 7426 0.35 0.20 7427 0.35 0.20 7428 0.30 0.21 7432 0.30 0.22 7432 0.35 0.46 7432 0.45 0.46 7432 0.45 0.47 7437 0.37 0.23 7440 0.37 0.24 0.37 0.37 7440 0.38 0.37 7440 0.38 0.37 7450 0.21 0.37 7450 0.21 0.37 7451 0.21 0.21 7453 0.21 0.21 7453 0.21 0.21 7454 0.21	7460 0.21 7470 0.44 7472 0.36 7473 0.44 7474 0.44 7474 0.42 7475 0.62 7475 0.62 7475 0.68 7482 0.86 7483 0.45 7484 0.21 7489 0.45 7489 0.45 7499 0.45 7499 0.45 7499 0.89 7499 0.94 7499 0.94	7496 0.94 7497 3.62 74100 1.77 74107 0.52 74109 0.84 74110 0.59 74111 0.82 74116 0.85 74118 1.15 74118 1.15 74119 0.95 74121 0.95 74121 0.95 74122 0.71 74123 0.67 74123 0.67 74128 0.67 74128 0.72 74132 0.85	74141 1.02 74142 2.86 74143 2.89 74144 2.89 74145 1.15 74147 2.20 74148 2.02 74150 2.07 74151 1.88 74155 1.04 74157 0.86 74157 0.86 74157 0.86 74157 0.86 74157 1.63 74158 1.64 74157 1.64 74157 1.64 74157 1.64 74157 1.64	74175 1.17 74176 1.33 74178 1.56 74180 1.38 74180 1.38 74190 2.19 74191 2.19 74192 2.19 74193 2.19 74194 1.44 74195 1.38 74196 1.55 74197 2.65 74198 3.11 76013N 2.02 7AAS700 2.65 TAA630S 4.50	TBA480Q 2.12 TBA520Q 2.65 TBA53Q 2.65 TBA53Q 3.70 TBA56Q 3.70 TBA56Q 3.70 TBA56Q 2.70 TBA70Q 1.75 TBA70Q 1.85 TBA70Q 1.38 TBA50Q 3.34 TBA50Q 3.34 TBA50Q 3.34 TCA76QA 1.59

ess: CWO. Postage a

Price ruling at time of despatch.

In some cases prices of Mullard and USA valves will higher than those advertised. Prices correct when going in some cases prices of Mullard and USA valves will higher than those advertised. Prices correct when going in the prices of the the pr Account facilities available to approved companies with minimum order charge £10. Carriage and packing £1 on credit orders.

Over 10,000 types of valves, tubes and semiconductors in stock. Quotations for any types not listed. S.A.E.

Open to callers Monday-Friday 9 a.m.-5 p.m.

Telephone 01-677 2424/7 Telex 946708 E. & O.E.

Cotswold Electronics Toroidal Power Transformers

			ondary Current		ensions	Weight	
Туре	VA	RMS	RMS	Dia.	Height	Kg	Price
C1000	30	6+6	2.50	70mm	30mm	0.45	
C1001	30	9+9	1.67	70mm	30mm	0.45	£4.55
C1002	30	12+12	1.25	70mm	30mm	0.45	
C1003	30	15+15	1.00	70mm	30mm	0.45	(+£1.10 p.p.
C1004	30	18+18	0.83	70mm	30mm	0.45	+ 0.84 VAT)
C1005	30	22+22	0.68	70mm	30mm	0.45	
C1006	30	25+25	0.60	70mm 70mm	30mm 30mm	0.45	
C1007	1 30	30+30	1 0.30	70111111	f aguin	0.40	
C1010	60	9+9	3.33	87mm	33mm	0.75	
C1011	60	12+12	2.50	87mm	33mm	0.75	£4;86
C1012	60	15+15	2.00	87mm	33mm	0.75	
C1013	60	18+18	1.67	87mm	33mm	0.75	(+£1.43 p.p.
C1014	60	22+22	1.36	87mm	33mm	0.75	+ 0.94 VAT)
C1015	60	25+25	1.20	87mm	33mm	0.75	
C1016	60	30+30	1.00	87mm	33mm	0.75 0.75	
C1017	60	110	0.55	87mm 87mm	33mm 33mm	0.75	
C1018	60	220	0.27	97mm		0.75	

				_		-	23	
ı				ndary				
		1	Volts	Current	Dimer		Weight	
	Туре	VA	RMS	RMS	Dia.	Height	Kg	Price
	C1030	160	18+18	4.44		42mm	1.5	
D.	C1031	160	22+22	3.64	108mm	42mm	1.5	£8.40
ı	C1032	160	25+25	3.20	108mm	42mm	1.5	
L	C1033	160	30+30	2.67	108mm	42mm	1.5	(+ £1.73 p.p.
	C1034	160	35+35	2.29	108mm	42mm	1.5	+ £1.52 VAT)
1	C1035	160	110	1.46	108mm	42mm	1.5	
ľ	C1036	160	220	0.73	108mm	42mm	1.5	- 1
	C1037	160	240	0.67	108mm	42mm	1.5	
	C1040	230	25+25	4.60	115mm	50mm	2.2	
	C1041	230	30+30	3.83	115mm	50mm	2.2	£10.20
ļ	C1042	230	35+35	3.29	115mm	50mm	2.2	
	C1043	230	40+40	2.88	115mm	50mm	2.2	(+ £1.73 p.p.
ı	C1044	230	110	2.09	115mm	50mm	2.2	+ £1.79 VAT)
ı	C1045	230	220	1.05	115mm	50mm	2.2	
	C1046	230	240	0.96	115mm	50mm	2.2	
-	C1050	330	25+25	6.60	130mm	52mm	2.8	3
	C1051	330	30+30	5.50	130mm	52mm	2.8	£11.90
	C1052	330	35+35	4.71	130mm	52mm	2.8	
	C1053	330	40+40	4.13	130mm	52mm	2.8	(+ £1.90 p.p.
	C1054	330	45+45	3.67	130mm	52mm	2.8	+ £2.07 VAT)
	C1055	330	110	3.00	130mm	52mm	2.8	
	C1056	330	220	1.50	130mm	52mm	2.8	
	C1057	330	240	1.38	130mm	52mm	2.8	
	C1060	530	30+30	8.83	145mm	1 60mm	3.8	
	C1061	530	35+35	7.57	145mm	60mm	3.8	£15.80
	C1062	530	40+40	6.63	145mm	60mm	3.8	
ı	C1063	530	45+45	5.89	145mm	60mm	3.8	(+ £2.05 p.p.
	C1064	530	50+50	5.30	145mm	60mm	3.8	+ £2.68 VAT)
i	C1065	530	110	4.82	145mm	60mm	3.8	-
	C1066	530	220	2.41	145mm	60mm	3.8	
	C1067	530	240	2.21	145mm		3.8	

WW - 030 FOR FURTHER DETAILS

MODERN LABORATORY TOOL HOUSED IN ATTRACTIVE STEEL CASE

88mm 40mm 88mm 40mm

100 30+30 1.67 88mm 40mm 1.00 100 110 0.91 88mm 40mm 1.00 100 220 0.45 88mm 40mm 1.00

88mm 40mm 1.00

1.00 £5.70

1.00 (+ £1.43 p.p.

100 15+15 3.33 100 18+18 2.78

100 25+25 2.00

- ★ HOLD SIX EPROMS
- ★ SAFETY INTERLOCKED **EPROM TRAY**
- * SEPARATE ERASE INDICATOR
- **★** MONEY BACK **GUARANTEE**

LOW COST **EPROM ERASURE**

£38.50 FOST

Send cash with order to: NORTHERN FLECTRONICS 51 ARUNDEL STREET MOSSLEY, LANCS. OL5 OLS Tel: 04575 4119

WW - 031 FOR FURTHER DETAILS



Electronic Measurement Services

REPAIR & CALIBRATION SPECIALISTS OF **TEST & MEASURING INSTRUMENTS**

- Fast turn around time High quality backed by warranty
- Competitive rates
- Certification if required
- Nationwide collection and delivery service

Stockport Road, Longsight, Manchester M13 0LF

061-273 4653

WW - 032 FOR FURTHER DETAILS

SAFGAN presents DT-400 series from £169 + VAT

HIGH-QUALITY DUAL TRACE OSCILLOSCOPES A BRITISH PRODUCT EVERYONE CAN AFFORD

Model DT-410 DUAL TRACE 5mv/div 10MHZ @ £169 + VAT Model DT-412 DUAL TRACE 5mv/div 12MHz @ £175 + VAT Model DT-415 DUAL TRACE 5mv/div 15MHz @ £188 + VAT

SPECIFICATION FOR ALL MODELS

- ★ CH1, CH2; 5mv/div 20v/div in 12 col 1-2-5 steps. Input impedance 1MΩ + 22pF
- ★ BANDWIDTH: 10MHz (DT-410), 12MHz (DT-412) 15MHz (DT-415) * TIME BASE: 0.5 ps/div - 200ms/div in 18 cal steps
- X5 Expansion to 100 ns/div X5 Multiplier to 15/div ★ XY FACILITY: Matched Inputs X = CHI, Y = CH2
- * TRIGGER: Level Control, * Slope, Bright Line AUTO, NORMAL, TV Triggering CHI, CH2 0.5 div, EXT Trig 100mv ★ 7 Modulation
- * Cal output / probe compensation
- ★ Graticule blue ruled 8 × 10 div (6.4 × 8cm²)
- * SIZE: H215mm W165mm D280mm Weight 4.5 kg. PROBE (XI-REF-X10) £11.50 + V.A.T.

Orders to: SAFGAN ELECTRONICS LTD. (Goods + 15% + £3.50 P&P). Or £6.50 parcel service 56 Bishop's Wood, St. John's, Woking, Surrey, GU21 3QB Tel: Woking 69560 or Woking 66836 London Stockist: Audio Electronics, Edgware Road, London. Tel. 01-724 3564





WW - 038 FOR FURTHER DETAILS

World Leader in Duplicating & Tape-loading Equipment



C2 In-cassette Copier High quality at low cost. Stereo. Expandable to 11 copies. Ferrite heads. DC servo motors.

Reel to cassette copier. 6 slaves, DC Servo motors and ferrite heads. 2 speed master.

DP2700 Audio Tape-loader A precision loader at a budget price. Compressor not required. Easy to operate and



Video tape loaders also available

Sole UK Distributor:

WIRELESS WORLD APRIL 1981

ITA, 1-7 Harewood Avenue, Marylebone Road, London NW1. Tel: 01-724 2497. Telex: 21879.

DP4050 OCF

WW - 077 FOR FURTHER DETAILS

Happy Memories

4116	200ns	£2.25
2114	200ns	£2.95
2708	450ns	£3.95
2114	450ns	£2.20
2716	5 volt	£5.25

Memorex Soft-sectored mini-discs for PET, TRS-80 etc. Supplied in FREE LIBRARY CASE, £19.95 per 10

Low Profile I.C. Sockets by "Texas" 8 14 16 18 20 22 24 28 40 Pence 10 11 12 16 17 20 21 28 37

Memory Upgrade Kits for Apple, 2020, TRS-80, etc.: from £18, please phone. Quantity prices available on request. Government and Educational Orders welcome. Trade accounts opened.

All prices include VAT. Postage FREE on orders over £15, otherwise add 30p **Access and Barclaycard welcome**

HAPPY MEMORIES, DEPT. W.W. **GLADESTRY, KINGTON** HEREFORDSHIRE HR5 3NY Tel. (054422) 618

Memories	Price
2114L-300ns	£2 10
4116-200ns	f1 89
2708-450ns	f3 15
2716-450ns	£4.99
74LS series	
74LS240	£1.54
74LS243	£1.54
74LS244	£1.54
74LS245	£1.70
Dridge Destifica	
Bridge Rectifiers	
25 Amp 50 volt	£0.74
25 Amp 100 voit	£0.94
25 Amp 200 volt	£1.26
25 Amp 400 volt	£1.68
25 Amp 800 volt	£2.10
20 Amp 000 voit	£2.63

Please add 50 pence for carriage. All prices EXCLUDE VAT Please send s.a.e. for price list.

3c BARLEY MARKET STREET, TAVISTOCK **DEVON, ENGLAND PL19 0JF**

Tel. Tavistock (0822) 5439/5548. Telex: 45263

... the only magazine in Britain that gives the amateur enthusiast and professional engineer alike a comprehensive up-to-date coverage of TV technology. Coverage includes the latest developments in circuitry, video and long distance television . . . with a special emphasis on servicing and fault finding.

Regular construction articles have included test equipment, monochrome/colour receivers, monitors and video cameras.

THIS MONTH

Construction

An 'Arrow' Generator

A special joystick control unit for inclusion between camera and monitor ... drawing attention to points on a TV display by use of a moveable arrow.

Servicing

Greatly increased reliability of modern TV sets means intermittent faults are accounting for a much larger proportion of the servicing workload. We offer guidance on tracking down these, often difficult to locate, faults.

Review

THORN TX 10 Chassis

We review the latest Thorn chassis probably the equal of any in the world.



Sowter **Transformers**

With 40 years' experience in the design and manufacture of several hundred thousand transformers we can supply:

AUDIO FREQUENCY TRANSFORMERS OF EVERY TYPE YOU NAME IT! WE MAKE IT! **OUR RANGE INCLUDES**

Microphone transformers (all types), Microphone Splitter/Combiner transformers. Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Candon Mixing Desk transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra lum frequency transformers, Ultra linear and other transformers for Valve Amplifiers up to 500 watts, Inductive Loop Transformers, Smoothing Chokes, Filter, Inductors, Amplifer to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching transformers (all powers), Column Loudspeaker transformers up to 300 watts or more.

We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible.

OR SMALL QUANTITIES AND EVEN SINGLE THANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible.

OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS, AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas clients in the COMMONWEALTH, E.E.C., USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post quotations between

A. Sowter Ltd

E. A. SOWTER LTD. (Established 1941), Reg. No. England 303990 The Boat Yard, Cullingham Road, Ipswich IP1 2EG, Suffolk Phone: 0473 52794 & 0473 219390

WW - 050 FOR FURTHER DETAILS



WW-066 FOR FURTHER DETAILS



Cable Sleeves and Markers from £1.38 per 1,000.
Crimp Terminals from £9.60 per 1,000.

Audible Warning Devices. Buzztone, Bleeptone, Banshee, Bedlam, etc, from £1.14 each.
Self-adhesive Pcb guides from £5.04 per 100.

PBRA LTD. Golden Green, Tonbridge Kent TN11 OLH Hopfield (073274) 345 mber Crystalate Group

and values on special offer

QUICK ACTING & ANTI SURGE

from £3.15 per 100.

Carbon Film Resistors ¼w 5% £2.50 per 1,000, per value, car-riage and VAT extra. 6R8 33R 100R 120R 360R 470R 560R 2K4 2K7 4K7 5K6 7K5 8K2 100K 120K 150K 220K 300K 390K

Lists available of other wattages

WW-074 FOR FURTHER DETAILS

WIRELESS WORLD APRIL 1981

L. J. ELECTRONICS LIMITED

MICROELECTRONIC AND MICROPROCESSOR SYSTEMS FOR EDUCATION



WW - 051 FOR MORE DETAILS

Send for details of our:-

- Microprocessor Systems
- * Peripheral Hardware
- * Test Equipment
- Digital Patching Systems
- Analogue Patching Systems
- Laboratory Power Supplies

L. J. ELECTRONICS LTD., 9, Francis Way, Bowthorpe Ind. Est., Norwich NR5 91A. Tel: Norwich 746340

Telex: 975504

★ VIDEO MONITOR BARGAIN *

Due to a large purchase of surplus equipment, we are able to offer these superb professional 12in, green phosphor monitors at a fraction of their usual cost —

- ★ Manufactured by US Incoterm Corporation, imported by large mainframe r Manufactured by US incoterni Corporation, hardfacturer.

 ↑ Standard composite video in — just plug into your micro.

 ★ 230v mains. Additional PSU to supply keyboard included.

 ★ Extremely attractive anodised aluminium case.

 ★ 600 line resolution — P39 Phosphor — anti-reflective screen.

 ★ Ideal for graphics or alphanumeric display.

 ★ Complete with mains lead, long video cable and manual.

 ★ Guaranteed brand new in original boxes.

We believe these are the finest monitors available at any price. Trade enquiries invited.
Only £75 each + VAT, Carriage £7.50.

KEYBOARDS

84 Key ASCII with numeric cluster and control keys. LED Status indicators. In very smart case, with all encoding circuitry and on-board regulators, brand new and unused. No circuit available, so only £27 each. We also have some keyboards, as above, but without indicators and case for only £15. Add VAT and £2.50 postage.

OTHER BARGAINS

Diablo series 30 disk drives, 2.5 MByte	£500
FIXED 5 Medabyte disk and controller for 8080	EADO
IDIVI Standard floody drive and controller for 8080	6200
TEAAS SHERT 700 ASCH 30 cps Terminals (KSR)	£175
Nonoo Teletypes, Zuma loop ASCII	£100
Terminet 300 ASCII CDS letter quality term	5300
Fertec industry standard 9-track Magtane drives	CAEO
DASE 12-Sector DISK Cartridges, RK05 type, NEW	£30 00
DECTARES, for 1 USS/SB drives	r hov 12 reals
TALLY high speed tape readers	£75
· · · · · · · · · · · · · · · · · · ·	

Many other items plus full range of PDP8/11 modules in stock — please telephone for latest list. VAT and carriage extra.

CHILTERN ELECTRONICS B.C.M., Box 8085, London WC1N 3XX. Tel. 0494 714483

WW - 72 FOR FURTHER DETAILS

COME TO SPILTH **ELECTRONICS FOR ALL** YOUR **CB NEEDS**

ANTENNAS. COAX CONNECTORS MIKES **SWR METERS** BOOKS 40 & 80 CH RECEIVERS

SPILTH **ELECTRONICS**

3D Barley Market Street Tavistock, Devon Phone 0822 5865 Telex 45236

Registered Office: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

WIRELESS WORLD APRIL 1981

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

BSR DE LUXE AUTOCHANGER

Plays 12", 10" or 7" records, Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 13½-11¼in. 3 speeds. Above motor board 3¼in. Below motor board 2½in. with Ceramic Storeo sertidae. with Ceramic Stereo cartridge





£10.50

£17 Post £2

HEAVY METAL PLINTHS

Cut out for most BSR or Garrard decks. Silver grey finish with tinted plastic cover. Size 16 x 14 x 6in.

PIONEER and J.V.C. TEAK VENEERED PLINTH

19 × 14½ in. with Plastic Cover

TINTED PLASTIC COVERS Sizes: 14½ × 12½ × 3in. £4. 18 × 13¼ × 4in. £6.

18 × 13½ × 4in. £6. 17½ × 9½ × 3½in. £3. 18 × 12½ × 3in. £6. Post £1.50

BSR SINGLE PLAYER DECKS

BSR P200 2 speeds flared aluminium turntable "S" shape arm, cueing device, Less cartridge £30
Belt drive Post Post £2

Ready cut mounting board. Only £1 extra.

BSR P172 RIM DRIVE QUALITY DECK

Manual or automatic play. Th Precision ultra slim arm. Cueing device. Bargain price With steréo ceramic cartridge £20 Post £2 BSR P207 BUDGET SINGLE PLAYER ideal for disco of small two-speed Hi-Fi system with stereo cartridge and

GARRARD 6-200 SINGLE PLAYER DECK

Brushed Aluminium Arm with stereo ceramic cartridge and Diamond Stylus, 3-speeds. Manual and Auto Stop/Start. Large Metal Turntable. Cueing Device and Pause Control. Ready cut mounting board £1 extra.

ELAC HI-FI SPEAKER 10in. TWIN CONE

Large ceramic magnet. 50-16,000 c/s. bass resonance 40 c/s.

8 ohm impedance. 10 watts. RMS. **£7.95** Post 99p

POTENTIOMETERS Carbon Track

5kΩ to 2MΩ. LOG or LIN. L/S **50p.** DP **90p.** Stereo L/S **£1.10.** DP **£1.30.** Edge Pot 5K. SP **45p.** Sliders Mono **65p.** Stereo **85p.**

EMI 131/2 x 8in. LOUDSPEAKERS

With tweeter and crossover 8 ohm. 15 watts, £9.95

£10.95

Bass woofer, EMI 15 ohm. 20 watt. £10.95 Post 99p SUITABLE BOOKSHELF CABINET £10.50. Post £2.50

THE "INSTANT" BULK TAPE ERASER Suitable for cassettes, and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead.

Will also demagnetise small tools
Head Demagnetiser only £5
Post 95p

Head Demagnetiser only £5 Post 95p

RELAYS. 12V DC £1.25p. 6V DC 85p.
BLANK ALUMINIUM CHASSIS. 6 x 4—£1.20; 8 x
6—£1.50; 10 x 7—£1.90; 12 x 8—£2.20; 14 x 9—£2.50;
16 x 6—£2.40; 16 x 10—£2.70.

ANGLE ALI. 6 x ¾ x ¾in—25p.

ALUMINIUM PANELS. 6 x 4—24p; 8 x 6—38p;
14 x 3—40p; 10 x 7—54p; 12 x 8—70p; 12 x 5—44p;
16 x 6—70p; 14 x 9—84p; 12 x 12—£1; 16 x 10—£1.16.

PLASTIC AND ALI BOXES IN STOCK. MANY SIZES
ALUMINIUM BOXES. 4 x 4 x 1½ £1. 4 x 2 x 2 £1. 3 x 2 x 1
80p. 6 x 4 x 2 £1.30. 7 x 5 x 2½ £1.45. 8 x 6 x 2 £2.20. 10 x
7 x 3 £2.50. 12 x 5 x 3 £2.30. 12 x 8 x 3 £2. 20. 10 x
7 x 3 £2.50. 12 x 5 x 3 £2.30. 12 x 8 x 3 £2.

BRIDGE RECTIFIER 200V PIV 4 amp £1.50. 8 amp £2.50.
TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p.
RESISTORS. 10Q to 10M. ¼W, ½W, 1W, 1p: 2W 10p.
HIGH STABILITY. 4w 2% 10 ohms to 1 meg. 8p.
Ditto 5%. Preferred values, 10 ohms to 1 meg. 8p.
PICK-UP CARTRIDGES SONATONE 9 TAHC £2.50.
BSR Stereo Ceramic SC7 Medium £2. SC8 High £2.

BSR Stereo Ceramic SC7 Medium £2. SC8 High £2.
PHILIPS PLUG-IN HEAD. AU1020 (G306 - GP3 10 - GP233

-AG3306 - AG3310) £2.
LOCKTITE SEALING KIT DECCA 118. Complete £1.
SOLDERING IRON 2404 40W £2.75.
VALVE OUTPUT Transformers (small) 90p.

CAR SPEAKERS on Baffles 7 × 4½ × 1½in. deep, 4 ohms. Twin Units Bass and Treble 10 watts, RMS, Door Mounting, Stereo pair £14.

IN-CAR GRAPHIC EQUALISER. Power Booster. Stereo 20 watts RMS per channel, 5 sliders Graphic Equalisation 5½ wide x 7½ deep x 2 in. high. 12 volt D.C. suitable for Car Radio or Cassette £30.



MINI-MULTI TESTER

Deluxe pocket size precision movi coil instrument, jewelled bearings 2000 o.p.v. Battery included. 11 instant ranges measure: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0-100mA. Continuity and resistance 0-1 meg ohms in two ranges.
Complete with Test Prods and instruction book showing how to measure capacity and inductance.

D C VOLTS

£6.50 Post 65p

PANEL METERS £4 each

50µа 100µа 500µа,

1ma, 5ma, 50ma, 25 volt, 50 volt, VU Meter. Facia 2% × 1¾ × 1½ in. Fixing hole 11/2 in. dia.

Lighting kit 6 or 12v 90p extra. 1ma (240° scale) 21/4in. sq. £5 Post 65p

RCS SOUND TO LIGHT CONTROL KIT

Kit of parts to build a 3 channel sound to light unit
1,000 watts per channel. Suitable for home or disco.
Easy to build. Full instructions supplied. Cabinet
24.50 extra. Will operate from 200MV to 100 watt signal.
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco
Lights, Edison Screw. 6 for £4, or 12 for £7.50. Post 65p.

"MINOR" 10 watt AMPLIFIER KIT £14

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available. Mono, £14, Stereo, £20, Post 65p. Specification 10W per.channel; input 100mV; size 9½ x 3 x 2in. approx. SAE details. Full instructions supplied. AC mains powered: Input can be modified to suit guitar.

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp.
Inputs for high, medium or low imp per channel, with volume
control and PC Board

£2.95 £2.95

	The second of th	. 001 001			
١	MAINS TRANSFORMERS	Post			
١	250-0-250V 70mA, 6.5V, 2A	£2 00			
	250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A				
	350-0-350V 250mA, 6.3V 4A, 4A CT, 5V 2A £12.50	£2 50			
١	300-0-300V 120mA, 2×6.3V 2A C.T.; 5V 2A	£2 50			
1	220V 45mA, 6.3V 2A £2.50	£1.00			

GENERAL PURPOSE LOW VOLTAGE

2 amp. 3. 4. 5. 6. 8. 9. 10, 12, 15, 18, 25 and 30V amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 amp. 6, 8, 10, 12, 100mA amp. 61, 300 amp. 20V, 40V, 60V, 1a, 12V, 3a, 12V, 3a, 12V, 3a, 12V, 3a, 12V, 3a, 12V, 3a, 13V, 5a and 17V:0-17V, 2a amp. 64, 60 amp. 62, 60 amp. 64, 6 3 amp. 6. 8, 10, 12, 10, 12, 100mA £1.30 80p 12V, 150mA £2.00 80p 10-0-10V2a £3.00 £1 30V, 5a and 17V-0-17V 2a £4.00 £2 0.5 8, 10, 16V, ½a £2.50 80p 0V 3a £3.50 £1 £4.50 £1 £1.50 80p £11.00 £2.50 £3.50 £1 £1.50 80p £11.00 £2.50 £12 £2.50

6V 1/2a 15-0-15V, 2a 9V, ¼a 32-0-32V, 6½a 500W AUTO TRANSFORMERS. 115V to 40V 150W ES Post £2.

CHARGER

OPUS COMPACT SPEAKERS FLUTED WOOD FRONTS TEAK VENEERED CABINET 11×8½×7in 50 to 14,000 cps. 15 watts 8 ohm

£20 pair Post £2

LOW VOLTAGE ELECTROLYTICS
ALL 10p
1 m/d, 2 m/d, 4 m/d, 8 m/d, 10 m/d, 16 m/d, 25 m/d, 30 m/d, 50
m/d, 100 m/d, 250 m/d, All 15 vgts. 22 m/d /6v/10v; 25
m/d /6v/10v; 47 m/d/10v; 50 m/d/6v; 68 m/d/6v/10v; 25
m/d /6v/10v; 100 m/d/10v; 150 m/d/6v/10v; 200 m/d/10v/
16v; 220 m/d /4v/10v/16v; 330 m/d/4v/10v; 500 m/d/6v/
16v; 220 m/d /4v/10v/16v; 330 m/d/4v/10v; 500 m/d/6v/
16v; 100 m/d/6v/10v/16v; 2200 m/d/6v/10v; 3300 m/d/6v/
1700 m/d/6v/10v/16v; 2200 m/d/6v/10v; 3300 m/d/6v;
1700 m/d/6v/10v/15p; 25v 20p; 50v 30p.
1000mF 12v 30p; 25v 35p; 50v 50p; 100v 70p.
2000mF 6v/25p; 25v 42p; 40v 60p; 1200mF 76v 80p.
2500mF 50v 70p; 3000mF 50v 65p; 2000mF 100v £1.
4500mF 64v £2. 4700mF 63v £1.20. 2700mF /76v £1.

HIGH VOLTAGE ELECTROLYTICS

| High Vol.| Add Elect | 1907 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908 | 1908

32/350V 50p 50+50/300V 50p 80+40/500V £2

TRIMMERS 10pF, 30pF, 50pF, 5p. 100pF, 150pF, 15p.

CERAMIC, 1pF to 0.01 mF, 5p. Polystyrene 2 to 5000pF, 5p.

PAPER 350V-0.1 7p; 0.5 13p; 1mF 150V 20p; 2mF 150V
20p; 500V-0.001 to 0.05 12p; 0.1 15p; 0.25 25p; 0.47 35p.

MICRO SWITCH SINGLE POLE CHANGEOVER 20p.

SUB-MIN MICRO SWITCH, 25p. Single pole change over.

TWIN GANG, 120pF 50p; 500pF £1.

GEARED TWIN GANGS 25pF 95p, 365pF £1.

GEARED 365 + 365 + 25 + 25pF £1.

TRANSISTOR TWIN GANG, Japanese Replacement 50p.

NEON PANEL INDICATORS 250V 30p.

ILLUMINATED ROCKER SWITCH. Single pole. Red 65p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 15p

CASSETTE MOTOR, 6 volt £1

CASSETTE MECHANISM. 12v Stereo Playback only £5

BAKER LOUDSPEAKERS "SALE PRICES"

WATTS TYPE
30 HI-FI
15 HI-FI
30 HI-FI
45 HI-FI
45 PA
75 PA
100 PA
100 PA
100 DISCO DELUXE MK II

BAKER 50 WATT AMPLIFIER



£69 Post £2 Ideal for Halls/PA systems, Discos and Groups. Two inputs. Mixer, Volume Controls, Master Bass, Treble and Gain Controls. 50 watts r.m.s. Three loudspeaker outlets 4, 8, 16 ohms.

BAKER 150 WATT MIXER/POWER AMPLIFIER

Professional 4 inputs with volume controls. Will mix mics, decks, musical instruments, etc.

Slave version available £75 100 Volt Line £14 extra. Post £2.

FAMOUS LOUDSPEAKERS "SPECIAL PRICES"

PRICE £7.50 £4.00 £10.50 £7.50 £10.50 £10.50 £9.50 £8.50 £8.50 £8.00 £14.00 £14.00 £20.00 MID-RANGE MID-RANGE MID-RANGE FULL-RANGE FULL-RANGE SEAS SEAS GOODMANS GOODMANS GOODMANS AUDIOM 8p AXIOM SEAS GENERAL AUDIOM PG PP12 AUDIOM P £24.50 £20.00 £27.50 £25.00 GR12 GOODMANS AUDIOM P

BATTERY ELIMINATOR MAINS to 9 VOLT D.C.

Stabilised output, 9 volt 400 m.a. U.K. made in plastic case with screw terminals. Safety overload cut out. Size 5 x 3½ x 2½in. Transformer Rectifier Unit. Suitable Radios, Cassettes, models, £4.50. Post 65p

DELUXE SWITCHED VOLTAGES

MODEL STABILISED
3-6-7½-9 volt 400ma DC max. Universal output plug and lead Pilot light, mains switch, polarity switch £7.50. Post 65p.

TEAK VENEERED HI-FI SPEAKER CABINETS

TEAK VENEERED HI-FI SPEAKER CABINETS
For 13x8in. or 8in. speaker
£10.50 Post £1.50
For 6½in. speaker and tweeter
Many other cabinets in stock. Phone your requirements.
SPEAKER COVERING MATERIALS. Samples large S.A.E.
LOUDSPEAKER CABINET WADDING 18in wide 25p ft.

CROSSOVERS. TWO-WAY 3000 c/s 3 or 8 or 15 ohm £1.90. 3-way 950 cps/3000 cps, £2.20. LOUDSPEAKER BARGAINS

25 ohm, 3in, 5in, 7x4in, £1.50; 6½in, 8x5in, £3; 8in, £3.50. 8 ohm, 2%in, 3in, 5in, £1.50; 6½in, £3; 8in, £4.50; 12ir, £6. 15 ohm, 3½in, 5x3in, 6x4in, £1.50. 25 ohm, 3iv, in, 5x3in, 7x4in, £1.50. 120 ohm, 3¼in dia. £1.50. MOTOROLA PIEZO ELECTRIC HORN TWEETER £6.50

BLACK PLASTIC CONSTRUCTION BOX with brushed aluminium facia. Sturdy job. Size 61/4 x 43/4 x 2in, £1.50

ECHO CHAMBER

play tape cartridge. Stationary play heads ensure good repro-duction and echo variance is achieved by changing tape speed. Input imp: 50k and 600 ohms. Power: 240 volts A.C. £68. Post £2 Spare tape £5.



ALUMINIUM HEAT SINKS. FINNED TYPE.

ALUMINIUM HEAT SINKS. FINNED TYPE.
6½"×2"×2"% "65p.
JACK PLUGS Mono Plastic 25p; Metal 30p.
JACK PLUGS Mono Plastic 30p; Metal 35p.
JACK SOCKETS. Mono Open 20p; Closed 25p.
JACK SOCKETS Stereo Open 25p; Closed 30p.
FREE SOCKETS — Cable end 30p.
2.5mm and 3.5mm JACK SOCKETS 15p.
2.5mm and 3.5mm JACK SOCKETS 15p.
DIN TYPE CONNECTORS
Sockets 3-pin, 5-pin 10p. Free Sockets 3-pin, 5-pin 25p.
Plugs 3-pin 20p; 5-pin 25p.
PHONO PLUGS and SOCKETS ea. 10p.
Free Socket for cable end ea. 15p.
Screened Phono Plugs ea. 15p.
TV CONVERGENCE POTS 15p each
Values = 10, 20, 50, 100, 200, 250, 470, 2000 ohms.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy

Stereo 20 watts RMS per cnanner, o silders drapnic Equalisation 5½ wide x 7½ deep x 2 in. high. 12 volt D.C. suitable for Car Radio or Cassette £30.

CASSETTE MOTOR. 6 volt £1

CASSET

TELEPRINTER TYPE 7B: Pageprinter 24v. d.c. power supply. Speed 50 bauds per min. S/hand, good cond. (no parts broken), £28.75. OR G.P.O. MODEL, as above except motor, 110/230v. a.c., £34.50. Carriage either type £9.50. Send S.A.E. for list of Teleprinter spares available.

TS.147 RADAR TEST SET Combination Sig. generator and frequency meter and power meter. Provides C.W. and F.M. signals, 115v. a.c., £225. Carr. £7.

HEWLETT PACKARD Signal Generator HP608B. Freq. 10-400MHz C.W. and A.M. Output 1 microvolt to 8v, 50. Mod. 400-1000Hz. 230v. a.c., £225. Carr. £10.

TRANSISTORISED 3cm. RADAR AMPLIFIER SWITCH: with 24v. waveguide switch, 9 × 4cm ins. with crystal CV. 2355 and spark gap VX 1046, £17.95 + £1 post. INSULATION TEST SET 0 to 10KV, negative earth, with Ionisation Amplifier, BC-221 FREQUENCY METER: 125-20,000kc/s, complete with original calibration charts, £24.15 + carr.

charts, £24.15 + carr.

ROTARY INVERTER TYPE: PE218E: Input 24-28v DC, 80 amps, 4,800r.p.m. Output 11v AC, 13 amp 400 c/s. 1Ph.P.F.9. £23+carr.

RESONATOR PERFORMANCE CTC 424 8.5 to 9.0 kmc/s 3 cm, £80.50 + post £2. INVERTER 24v. DC input 400 cycles 1pH 6600 r.p.m. 200v, peak, £8.05 + £2 post. OXYGEN BOTTLE 1800lb, wp. £11.50 × carr.

NOISE SOURCE UNIT with CV.1881 noise source mount. Produces thermal poise 15.5dB 200/250v. AC. £80.50.

H\$33 HEADSET. Low imp. £5.35 + 75p post.

MUIRHEAD DECADE OSCILLATOR TYPE 890D, £92 + carr. £5.

SIEMENS POWER METER REL3U/84/Alb: 0-12kmHz 1mw 500mw 6 ranges. 0.17dB 50 ohms, £92 + carr.

SIEMENS POWER METER REL3U/84/AID: U-12kmr12 11hw 300hw o ranges. 0.17db 50 ohms, 592 + carr.
CV.1596 CATHODE RAY TUBE: (09D, 09G), 4in. screen, green electrostatic base B12B. HT1200 volts, heater 4 volts, £11.50.
VACUUM AND PRESSURE DEAL TEST EQUIPMENT: complete with 2 × 4in. gauges indicating 0.20lb. p.s.i. 0.30lb. vacuum. With stand, hand pump, etc., £34.50 + carr.
TELEPRINTER MODEL 75, available with perforator attachment, £74.75 + £10 carr.

riage.

DIGITAL CLOCKS MODEL 304 with automatic recorder. Printout system model 301.

£86.25 + £10 carriage.
SPERRY TRANSISTORISED SERVO-AMPLIFIERS TYPE C1 with circuit diagram, £11.50 + £1.50 post. X-Y PLOTTER, £74.75 + £7 carriage

> BARGAIN MAPS Large stocks of unused U.S.A.F. surplus maps, weather charts, etc. including:

ONC-E1 — U.K. in full and part N.W. Europe. Scale 1:1,000,000. JNC-9N — N. Europe, U.K., Scandinavia. Scale 1:2,000,000. JN-21N — Europe (Mediterranean). Scale 1:2,000,000. SIZE 58" × 42". colour. Many others, Please send S.A.E. for list. Price each 75p (inc. P&P) 25 × Maps (either same type OR assorted), £10 + £1.60 P&P. 10 × Maps (either same type OR assorted), £6.50 (in. P&P).

All prices include VAT at 15% Carriage quotes given are for 50-mile radius of Herts.

W. MILLS

The Maltings, Station Road SAWBRIDGEWORTH, Herts. Tel: Bishop's Stortford (0279) 725872

ELECTRONIC VALVES WANTED

announcement of the community of the com

All Types Receiving, Transmitting, Industrial

PL504 - PL802 - PCL805 - CV131 - CV136 -CV138 — CV329 — CV345 — CV450 — 805 — 807 — 813 — 2K25, Etc.

Phone/write to:

PYPE HAYES RADIO LTD. 606 Kingsbury Road Birmingham B24 9PJ 021-373 4942

WW - 070 FOR FURTHER DETAILS



LOW VOLTAGE POWER DRILLS **AND ACCESSORIES**

Ilustration shows Titan Drill and Stand (Price £27 inc. VAT and Postage) which is One of the combinations which can be purchased from our comprehensive range of Drills and Accessories Prices from £8.34 (Reliant Drill only) inc. VAT and Postage.

Send 25p for Catalogue.

A. D. BAYLISS & SON LTD.

PFERA WORKS, REDMARLEY
GLOUCESTER GL19 3JU

Tel. Bromesberrow (053 181) 273

PRINTED CIRCUITS

FOR WIRELESS WORLD PROJECTS

1	U.h.f. television tuner—Oct. 1975—1 d.s.	CO EO
п	Surpline I.I. power amn—Sent 1975—1 de	05.00
ı	Audio compressor/limiter—Dec. 1975—1 s.s. (stereo)	£5.00
ı	F.m. tuner (advanced)—April 1976—1 s.s. (stereo)	£4.25
ı	Cassette recorder May 1976 1 as	£5.00
ı	Cassette recorder—May 1976—1 s.s.	£5.00
ı	Audio compander—July 1976—1 s.s.	£4.25
ı	Time code clock—August 1976—2 s.s. 3 d.s.	£15.00
ı	Date, didili, b.S.t. SWITCH—June 1977—2 de 1/e e	CO EO
я	Audio preamplifier—November 1976—2 e e	
ı	Additional Circuits—October 19 / /1 e e	04.00
ı	Oteleo Codel — April 19//— I de 7 e e	£8.50
ı	Wiolse Reypodic and memory—January 1077—2 d.c	20.00
ı	(logic board 10 4in, x 5in.) (keyboard and matrix 13in, v 10in.)	£14.00
ı	Low distol tion disc amplifier (steren)—Sentember 1077 1 a a	
П	Low distortion audio oscillator - September 1977 - 1 e e	C2 EA
ı	Symulesized Lill, transceiver—November 1077 2 d c 1 c c	040 00
П	Morsemaker—June 1978—1 d.s.	£12.00
	Metal detector—July 1978—1 d.s.	£4.50
	Oscilloscope waveform store—October 1978—4 d.s.	£3.75
	Widehard poice reduces News 1978—1 s.s.	
ě	Wideband noise reducer—November 1978—1 d.s.	
ı	Versatile noise generator—January 1979—1 s.s.	£5.00
	200MHz frequency meter—January 1979—1 d.s.	£7.00
	High performance preamplifier—February 1979—1 s.s.	£5.50
	Distortion meter and oscillator — July 1979 — 2 s s	
	woving coil preamplifier—August 1979—1 s s	
	Wulti-mode transceiver—October 1979—10 d s	C2E 00
	Amplification system —October 1979—3 preamp 1 poweramp	
	Digital capacitanas mater A. (14000 (£4.20 each)	C10 00
۱	Digital capacitanes mater A. il 1000	E 10.00

ligital capacitance meter—April 1980—2 s.s. Colour graphics system—April 1980—2 s.s.
Audio spectrum analyser—May 1980—3 s.s.
Multi-section equalizer—June 1980—2 s.s. £18.50 £10.50 Floating-bridge power amp - Oct. 1980 - 1 s.s. (12V or 40V) £4.00 Nanocomp — Jan. 1981 — 1 d.s. 1 s.s. Logic probe — Feb. 1981 — 2 d.s. £9.00 £6.00 Boards are glassfibre, roller-tinned and drilled. Prices include V.A.T. and U.K. postage.

Airmail add 20%, Europe add 10%, Insurance 10%. Remittance with order to:

M. R. SAGIN, 23 KEYES ROAD, LONDON, N.W.2

WW - 040 FOR FURTHER DETAILS

Digitel Video Noise Measurement System

The Digitel D4060 Noise Measurement System offers an accurate and economical method of measuring video signal to noise ratio on broadcast or industrial TV systems.



Accurate to ± 1.5dBs from 20dBs to 60dBs

- Measures signal to noise ratio down to 65dBs SNR
- Field interval SNR measurements are possible with the
- SNR measurement is possible in the presence of sync pulses, some
- Visual display on oscilloscope ensures measurement confidence
- Full CCIR weighting filter sets are available

DIGI-TEL ELECTRONICS

20 Trenches Road

WW - 075 FOR FURTHER DETAILS



+ PUBLIC TELEPHONE EQUIPMENT

CABLES + TERMINAL EQUIPMENT

TRANSMISSION + SWITCHING AND ROUTING

+ FACSIMILE +

ANTENNAS

+ LASERS + FIBRE OPTICS TELETEXT + SATELLITES + MICROWAVE TELETEXT + SATELLITES + MICROWAVE TELETEXT + SATELLITES + MICROWAVE

RIVATE TELEPHONE EQUIPMENT

+ GENERATORS + COMPUTERS

NOBILE RADIO + RADIO PAGING +

POINT-TO-POINT RADIO

Complete, detach and post to:

Terry Brandon, Sales Manager

Industrial and Trade Fairs Limited

Radcliffe House, Blenheim Court

Solihull, West Midlands B91 2BG

Tel: 021-705 6707 Telex: 337073

Communications 82 is organised by

Industrial and Trade Fairs Limited for

Tony Davies Communications

England

WIRELESS WORLD APRIL 1981

Communications

National Exhibition Centre Birmingham, England 20-23 April 1982

Your Opportunity to Sell Communications **Equipment** and Systems

Communications 82 will be the sixth in a biennial series of expositions - now recognised as the World's leading international events for selling communications equipment and systems. It comprises a major international exhibition and integral conference plus a programme of social events with guest speakers of international stature.

Communications 82 will be a total communications exposition, covering all systems, equipment and components used in communications, including transmission, switching and terminal equipment as well as associated products and services for recording, testing and maintenance.

Communications 82 will be total also in user appeal, spanning the boundaries between civil and military, public and private, industry and commerce, fixed and mobile, in the same way as do the technologies involved.

Communications 82, therefore, offers a unique opportunity for you to sell your products to potential customers from all over the world - at Communications 80 there were well over 16,000 visitors from 70 countries.

If you manufacture or sell communications equipment and systems nationally or internationally, you cannot afford not to participate in Communications 82 - the total communications exposition.

I am interested in exhibiting at Communications 82 Please send me the full Data Pack.	

Name		 				 •								
Position														



P&P 1.00 1.00 1.20 1.44 1.60 1.60 1.72 1.96 1.84 OA OA

P&P .50 1.00 .50 .60 .95 1.20 .50 1.00 1.20 1.20 1.20 1.20

2.90 3.93 6.35 7.39 8.79 10.86 12.29 16.45 18.98 21.09 24.18 32.40

30 VOLT RANGE (Split Sec)

SCREENED MINIATURES Pri 240V

AUTO TRANSFORMERS

230, 240, Voltages for step up or step down.

Ref. VA (Watts) TAP'S £ P&P

113' 15 0-115-210-240V 2.73 1.00

64 80 0-115-210-240V 4.41 1.20

4 150 0-115-200-220-240V 5.89 1.20

67 500 "12.09 1.84

20.84 1000 20.84 2.20

93 1500 "25.61 0A

95 2000 "38.31 OA

73 3000 "65.13 OA

80s 4000 0-10-115-200-220-240 84.55 OA

"0.115, 220, 240 Step Up or Step Down

*0, 115, 220, 240 Step Up or Step Down

NEW RANGE TRANSFORMERS

Volts £
3-0-3 2.83
0-6, 0-6 3.14
9-0-9 2.35
0-9, 0-9 2.19
0.8-9, 0.8-9 3.05
0.8-9, 0.8-9 3.05
0.8-9, 0.8-9 3.08
0.15, 0-15 2.19
12-0-12 2.88
0.20, 2-20 3.75
0-15-20, 0-15-20 5.09
0-15-27, 0-15-27 6.64

110	WINELESS WORLD AFRIC 15
TTL by TEXAS	Second Column
NEW RETAIL SHOP	Please add 30p P&P & VAT 15%. TECHNOMATIC LTD.
1 0000	Coverage Colleges etc. Orders assented. 17 RURNI EV ROAD LONDON NW10

CALLERS WELCOME

Government, Colleges, etc. Orders accepted

367 Edgware Road, W2



WIRELESS WORLD APRIL 1981

copper spring clip retained inside each precision tu contact. These contacts are now fitted into NEW temperature, solvent resistant polyester open-fram

INCREASED RANGE from 6 to 64 ways D.I.L. and t 32 ways S.I.L. pin counts. We offer a choice of SELECTIVE GOLD PLATING on the inner spring with LOW COST TIN PLATING as an alternative.
Add to this RELIABILITY insured by unique fully

automated assembly and test facilities giving controlled insertion/withdrawal forces. Tested up to a 1,000 operations. Another useful feature is the VERY LOW

PROFILE and 0.1 inch grid stackability.

To complement the ranges of flow-solder and wrap sockets, there are now 4 different pin types of matching **HEADERS** in D.I.L and S.I.L configurations.

Made in the U.K. by

Harwin Engineers SA, Fitzherbert Road, Farlington, Portsmouth, PO6 1RT, Hants. Tel: 0705 370451, Telex 86125

WW - 067 FOR FURTHER DETAILS

			ANSF			
	MAINS ISO		RS	JS RA	TINGS 12 or	
	Pri 0-120, 0-100-120V (12	20, 220,	240V) Sec	Separa	te 12V w	vinc
	60, 55-0-55 60 twice, to gir 120, 125, 175, 180, 220, Ref. VA (Watts)	-		Ref.	12v 0.5	0
M	07★ 20	4.84	P&P 1.20	213 71	1.0	0
10	149 60 150 100	7.37 8.38	1.20	18 85	4.0	2
- 11	151 200 152 250	12.28	1.72	70	5.0 6.0	3.
	153 350	18.07	2.12	108 72	8.0 10.0	5.
	155 750	22.52 32.03	2.20 OA	116	12.0 16.0	6. 8.
	156 1000 157 1500	40.92 56.52	OA OA	115 187	20.0	11
	158 2000 159 3000	67.99 95.33	OA OA	226	60.0	30
	*115 or 240v sec				OLT R	
	required. Pri. 0.220	-		Pri 220	0-240V. Vo	Itag 8, 2
	50 VOLT RAN	IGE (SI	olit Sec).	-	0, 12, 15, 1 an Am p	d 15
	Pri 220-240V. Voltages ava 15, 17, 20, 25, 30, 33, 4 25V-0-25V.	0 or 20V	-0-20V and	Ref. 112	30v .5	18
	Ref. 50v 25v	£	P&P	79 3	1	
	102 .5 1	3.75	1.20	20	2 3	
	103 1 2 104 2 4	4.57 7.88	1.20 1.44	21 51	4 5	1
	105 3 6 106 4 8	9.42	1.60 1.72	117 88	6	1
	107 6 12	16.37 22.29	1.84	89	10	2
	119 10 20	27.48	2.20 OA	90	12 15	3
	109 12 24	32.89	SCREE	92 NED 8	20 IINIAT	4
	60 VOLT RAN Pri 220-240V (Split S	ec.)	Ref. n	nA .	Volts	U
	Voltages available 6, 8, 10 18, 20, 24, 30, 36, 40, 48 24V-0-24V and 30V-0-	, 12, 16, 3, 60V, or	238 20 212 1A	0 , 1A	3-0-3 0-6, 0-6	3
	24V-0-24V and 30V-0- Amps	30V	13 10 235 33	0 0, 330	9-0-9	
	Ref. 60v 30v £	P&P	207 50	0, 500	0-8-9, 0	-8-9
	126 1 2 6.50	1.20	236 20	, 1A 0,200	0-8-9, 0 0-15, 0-	-15
ن ا السحد	127 2 4 8.36 125 3 6 12.10			MA 0,300	12-0-12 0-20, 2-	
	123 4 8 13.77 40 5 10 17.42			0 (DC) , 1A	20-12-0 0-15-20	
201	120 6 12 19.87 121 8 16 27.92	2.04	203 50	0, 500 , 1A	0-15-27 0-15-27	, 0-
	122 10 20 32.51	OA			RANS	
- V	189 12 24 37.47		Voltages a	available	105, 115 for step u	, 19
	MAINS ISOLATIN	G	Ref. VA	(Wati	is)	TAF
	Pri 200/220 or 400/ Sec 100/120 or 200/		113° 19	0-115-	210-240\ 210-240\	/
	VA Ref. £ 60 243 7.37	1.20	67 500	0-115-	200-220-	2.40
	250 246 4.61 350 247 18.07	2.04	84 1000 93 1500			
GOOF	500 248 22.52	OA	95 2000 73 3000) "		
	CASED AUTO	, OA	80s 4000	0-10-1	5-200-22	20-2
	240V cable input USA 115V outlets		57s 5000		240 Step	o Up
	VA P&P Ref. 20 £6.55 .95	ьбW	N	EW RAN	GE TRAF	VSF
	75 £8.50 1.20 150 £11.00 1.44	64W 4W	0-36-48	twice to g	120; (120 ive 72V o	
	200 £12.02 1.44 250 £13.38 1.44	65W 69W	2A £13.3 3A £16.1	5 PP £1	.22 4	A
	500 £20.13 2.04 1000 £30.67 2.20	67W - B4W	BE7 0-110			
llium	2000 £54.97 OA	95W	P&P 32p +			
rned	O15V CT (7.5-0-7.5	RMER	Pri. 0-115		BIN TRA	
high		P&P	24-30. To	give 3, 4,	5, 6, 8, 1	0,
ne	171 500MA 2.30 172 1A 3.26 173 2A 3.95 174 3A 4.13	.52	30, 2 Amp Multimete	r (20KΩ\	/) with co	omb
	Ref. Amp Price 171 500MA 2.30 172 1A 3.26 173 2A 3.95 174 3A 4.13 175 4A 6.30	.90	oscillator a DC curren	t to 500m	na resistan	ice
up to .		1.10	97 × 40m	m £8.50	. P&P £1	+ \
clip,		HTC	ER PR	ODI	UCT	5
	AVO TEST METI		Satellite N		AVIGATI	
	Latest Model 8 Mk. 5 £1 71 Electronics	43.10	2900 seri	ies. Mari	ne receiv	ers

BE7 0-110-120 220 240V Sec 20V 1 Amp €1.62. P&P 32p + VAT. SPLIT BOBBIN TRANSFORMER SPLIT BOBBIN TRANSFORMER
Pri. O-115; 0-115 (Ref. 70010), Sec. 0-12-15-20-24-30. To give 3, 4, 5, 6, 8, 10, 12, 15, 18, 20, 24, 30, 2 Amps. £4.65 P&P £1.10 + VAT. Special Offer Multimeter (20ΚΩV) with combined audio IF test oscillator at 1 KHz and 465KHz AC / DC to 1000 volts DC current to 500ma resistance to 1 M. Size 160 × 97 × 40mm £8.50. P&P £1 + VAT.

HER PRODUCTS

AVO TEST MI	ETERS
Latest Model 8 Mk. 5	£106.40
71 Electronics	£43.10
73 TV Service	£58.60
MM5 MINOR	£36.90
WEE MEGGER	£87.00
DA211 LCD Digital	47.00
DA212 LCD Diital	£67.00
DA116 LCD Digital	£108.90
Megger 70143 500v	87.00
Avo Cases and Acce	essories
P&P £1.32 VAT	15%

	BRID	GE RE	CTIFIER	łs
	200v	2A	45p	
	400v	1A	25p	
	400v	2A	55p	
	100v	25A+	£2.10	
	200v	4A	65p	
	400v	4A	85p	
V	400v	6A	£1.40	
	500v	12A	£2.85	
1	P	&P 20p.	VAT 15%	
	Ser	d 15p for	catalogue	

RADIO NAVIGATIONAL AIDS
Satellite Navigational Systems e.g. Wherefinder II;
2900 series. Marine receivers and accessories.
(Agents for P&O Radio Services). Also available RF
cable and UHF connectors. ANTEX SOLDERING IRONS 5W £4.58. 25W £4.58
Stand for above £1.90. P&P 53p. VAT 15%

ı	PARELI	METERS
ļ	43mm x 43mm	82mm x 78mm
۱	0-50μΑ £6.20	0-50µA £6.70
ì	0-500μA £5.95	0-500μΑ £6.70
i	0-1mA £5.95	0-1mA £6.70
-	0-30V £5.95	0-30V £6.70
ł	VU Panel Ind. 48 x 45mm	, 250µA FDS £2.60
ı	Carriage 76p	
1		

U4315 Budget Meter 20KΩ/V. Rangers to 1000V 2.5A AC/DC 500KΩ. Res in steel case £15.85. P&P £1.32. VAT 15%

METAL OXIDE RESISTORS £1/100 Special Offer 5% ¼W. Use instead of carbon film (in 100s only). TR4 Electrosil.

390Ω - 470Ω - 510Ω - 560Ω - 820Ω - 1K - 1K1 - 1K2 - 1K6 - 1K8 - 2K - 2K4 - 3K - 16K - 20K - 22K - 24K - 47K - 82K - 100K - 130K - 180K - 220K - 270K - 300K - P&P 30p + VAT

Barrie Electronics Ltd. 3,THE MINORIES, LONDON EC3N 1BJ TELEPHONE: 01-488 3316/8 NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST.

WW - 020 FOR FURTHER DETAILS

17 BURNLEY ROAD, LONDON NW10

(2 minutes Dollis Hill tube station) (ample street parking) **Tel: 01-452 1500/01-450 6597 Telex: 922800**

112

3 unigor multimeters for the price of 2

> approved by international research companies taut band suspension

52 measuring ranges

overload protection

JOHN MINISTER INSTRUMENTS LTD. 137/139 SANDGATE ROAD, FOLKESTONE, KENT CT20 2DE Telex 965418

Telephone 0303 41598


WW - 078 FOR FURTHER DETAILS



The 'SERIES TWO' MESSAGE REPEATER

with 4-track capability, using all four tracks to provide separate or simultaneous playback

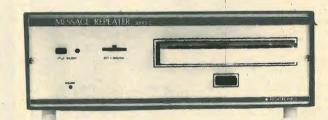Send for details of any item, and our full brochure of the comprehensive Reditronics range of sound communications equipment.





REDIFFUSION REDITRONICS LTD., La Pouquelaye, St Helier, Jersey, Channel Islands Tel: Jersey (0534) 30321 Telex: 4192341

U.K. DEPOT: River View Road, Bitterne, Southampton, Hampshire, U.K. Tel: Southampton (0703) 555566

Distributors for Greater London and Home Counties: Musitune Ltd., 388 Green Lanes, London N4 1 DW Tel: 01-802 1163

To obtain further details of any of the coded items mentioned in the **Editorial or Advertisement pages** of this issue, please complete one or more of the attached cards entering the reference number(s). Your enquiries will be passed on to the manufacturers concerned and you can expect to hear from them direct in due course. Cards posted from abroad require a stamp. These Service Cards are valid for six months from the date of publication.

Please Use Capital Letters

If you are way down on the circulation list, you may not be getting the information you require from the journal as soon as you should. Why not have your own copy?

To start a one year's subscription you may apply direct to us by using the card at the bottom of this page. You may also apply to the agent nearest to you, their address is shown below.

OVERSEAS SUBSCRIPTION **AGENTS**

Australia: Gordon & Gotch (Australasia) Ltd, 380 Lonsdale Street, Melbourne 3000, Victoria

Belgium: Agence et Messageries de la Presse, 1 Rue de la Petite-ILE

Canada: Davis Circulation Agency, 153 St. Clair Avenue West, Toronto 195,

Cyprus: General Press Agency Ltd, 131 Pro-dromou Street, P.O. Box 4528, Nicosia

Denmark: Dansk Bladdistribution. Hovedvagtsgade 8, Dk. 1103 Kobenhavr

Finland: Rautakiria OY. Koivuvaarankuja 2, 01640 Vantaa 64, Finland.

France: Dawson-France S.A., B.P.40, F-91121,

Greece: Hellenic Syngrou Avenue, Nea Smyrni, Greece.

Holiand: Van Ditmar N.V., Amsterdam 1004

India: International Book House, Indian Mercantile Mansion Ext, Madame Cama Road, Bombay 1

Iran: A.D.A., 151 Khiaban

Agency Ltd, Citrus House, P.O. Box 628, Tel Aviv

Japan: Western Publica-tions Distribution Agency, 170 Nishi-Okubo 4-chome, Shinjuku-Ku, Tokyo 160

Lebanon: Levant Distri-butors Co., P.O. Box 1181, Makdesi Street, Halim Hanna Bldg, Beirut

Malaysia: Times Distributors Sdn. Bhd., Times House, 390 Kim Seng Road, Singapore 9. Malaysia

Continental Ltd, 18a Scots Street, Valleta New Zealand: Gordon & Gotch (New Zealand) Ltd, 102 Adelaide Road, Wellington 2

Malta: W. H. Smith

Nigeria Ltd, 3 Kakawa Street, P.O. Box 139,

Norway: A/S Naivesens Kioskompani, Bertrand Narvesens vei 2, Oslo 6

Portugal: Livaria Bertrand s.a.r.l Apartado 37, Amadora

South Africa: Central News Agency Ltd, P.O. Box 1033, Johannesburg

Spain: Comercial Atheneum s.a. Consejo de Ciento, 130-136 Barcelona

Sweden: Wennegren Williams A B. Fack S-104, 25 Stockholm 30

Switzerland: Naville & Switzerland: Naville 8 Cie SA, Rue Levrier 5-7, CH-1211 Geneve 1 Schmidt Agence AG, Savogelstrasse 34, 4002 Basle

U.S.A.: John Barios, IPC Business Press, 205 East 42nd Street, New York, N.Y. 10017 Postage will be paid by Licensee

Do not affix Postage Stamps if posted in Gt Britain, Channel Islands, N Ireland or the Isle of Man

BUSINESS REPLY SERVICE Licence No 12045

WIRELESS WORLD Reader Enquiry Service 429 Brighton Road South Croydon Surrey CR2 9PS

Enquiry Service for Professional

ww.... ww.... ww...

ww.... ww.... ww....

ww.... ww.... ww....

ww.... ww... ww...

WIRELESS WORLD Wireless World, April 1981 WW 164 Please arrange for me to receive further details of the products listed. the appropriate reference numbers of which have been entered in the snace provided PUBLISHERS A/E No. of employees at this establishment I wish to subscribe to Wireless World

Wireless World: Subscription Order Form

To become a subscriber to Wireless World please complete the reverse side of this form and return it with your remittance to:

Subscription Manager, **IPC Business Press,** Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH, England

WIRELESS WORLD

Enquiry Service for Professional

ww.... ww.... ww...

ww.... ww.... ww...

Readers ONLY.


LOOK!

Wireless World, April 1981 WW 164

Please arrange for me to receive further details of the products listed,

the appropriate reference numbers of which have been entered in the

ANALOGUE

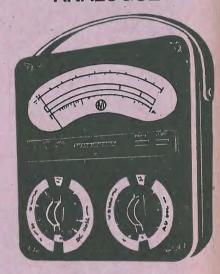

OR DIGITAL



MULTIMETERS

ex stock from:



International


FARNELL INTERNATIONAL INSTRUMENTS LTD WETHERBY.WEST YORKSHIRE.LS22 4DH

for brochures and price lists use the Wireless World Product Reply Service number below:

WW 003 for further details

WIRELESS WORLD APRIL 1981

The New Scopex 14D-10

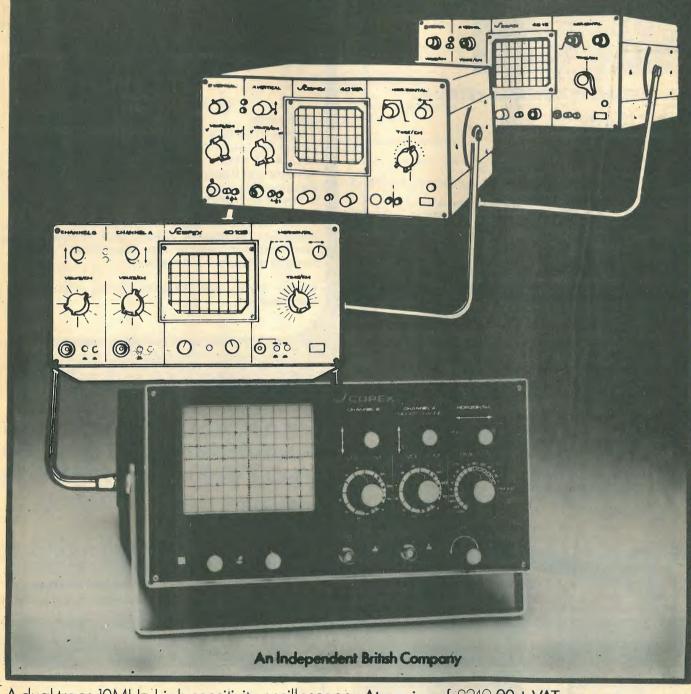

A dual trace 10MHz high sensitivity oscilloscope At a price of £240.00 + VAT. incorporating all the latest high technology developments to bring you all these outstanding features as standard.

- 10cm x 8cm display.
- 2mV sensitivity on both channels.
- Add and invert facility.
- Probe compensation.
- Push button X-Y.
- Trace locate.
- 10MHZ (-3dB) over full display.
- Complete with probes.

Ensures British leadership in the low cost high

performance oscilloscope market.

Distributors required in certain countries

COPEX	Please send me full details of the 14
ore Avenue, Letchworth, s SG6 1JJ. Tel: (04626) 72771.	Name
BARCLAYCARD *	Company
to pay by Barclaycard/Trust Card.	Address

WW - 8 FOR FURTHER DETAILS

My Barclaycard/Trust Card No. is

Please charge to my account.

Professional ASCII Keyboards





THE 'APPLE' COMPUTER KEYBOARD

- 52 key 7-bit ASCII Coded
- Positive Strobe, +5v -12v
- Full ASCII Characters
- Parallel output with Strobe.
- Power Light on Control National MM5740 Chip, TTL Output
- Superbly made, size 12x5,5x1,5in.
- Black keys with white legends
- Escape, shift, return and reset keys Complete with Circuit and Data

Ideal for use with TANGERINE, TRITON, TUSCAN, APPLE and most computers.

Ex-stock from Henry's.

This is definitely the BEST BUY. Supplied BRAND NEW in manufacturer's original packing (ANTI-STATIC). Just post remittance, total £35.95 (incl. VAT & Post).







404 Edgware Road, London W2 1ED, England I.E.D. 01-402 6822

FACTORY CLEARANCE SERVICES CO.

A GRAND CLEARANCE SALE OF NEW COMPU-TER SPARES WILL BE HELD AT OUR CODICOTE **WAREHOUSE ON** SATURDAY, 4th APRIL AND SATURDAY, 11th

COMPRISING OF:

APRIL

_____ from £10 Keyboards **Teletype Printers Type 35** Power Supply units, 5v, 10v, 12v, 18v, 24v, 1-amp to 20-amp...... from £7.50 10-Tonne of Electric Motors from 50p ea. Fans and Blowers from £2 5-Tonne of Transformers from £1

Plus: Resistors, Capacitors, Semiconductors, Rectifiers, Solenoids, Relays and thousands of electrical and mechanical assemblies. Jumbo bags of mixed components£5

Come along and browse, bring your own sandwiches!

A. R. DAVIES (FACTORY CLEARANCE)
28 ST ALBANS ROAD, CODICOTE
NR. OLD WELWYN, HERTS

TEL: STEVENAGE (0438) 833417-820686

WW-074 FOR FURTHER DETAILS

THE PRINTER SCOOP OF THE YEAR, SAVE OVER £1400 THE LOGABAX Z80 MICROPROCESSOR CONTROLLED

A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its recent cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities with all electronics on one plug in PC.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS ★ Full ASCII character set ★ Standard ink ribbon ★ RS232/V24 serial interface - 7 xtal

controlled baud rates up to 9600 \star Parallel ports interface \star Handshakes on serial and parallel ports \star 4 Type fonts, italic script, double width, italic large, standard \star Internal buffer \star Internal self test \star 170 CPS \star Variable paper tractor up to 17.5" wide ★ Solid steel construction ★ All software in 2708 eproms easily reconfigured for custom fonts etc. All this and more, not refurbished but BRAND NEW

At Only £525 + carriage and ins. £18.00 + VAT

OPTIONAL EXTRAS ★ Lower case £25.00 ★ 16K buffer £30.00 ★ Second tractor for simultaneous dual forms £85.00 ★ Teak finished floor stand £35.00 (+£8.50 carriage) * Logabax maintenance P.O.A. All prices subject to VAT – AVAILABLE ONLY FROM:

64-66 Melfort Rd, Thornton Heath Croydon, Surrey. 01-689 7702/6800 RPPRECIATION



86 High Street, Bletchingley

MAINS INTERCOM £37.99

+ VAT £5.70 per pa NO BATTERIES, NO WIRES. Made to high Safety and Telecommunications Standard. The modern way of letecommunications Standard. The modern way of mistant 2-way communications. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 44 mile on the same mains phase with call buzar and light indicator. On-off switch. Volume control. Useful as inter-office in-tercom between office and warehouse, in surgery and in homes, between house and garage. Also use-ful as burglar alarm. 6 months' service guarantee. P&P £1.95. Also F.M. 2-channel model £55.95 + VAT £8.40 + P&P £2.15 per pair.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER



10 days' price refund quarantee Barclaycard and Access welcome WEST LONDON DIRECT SUPPLIES (WW)
169 KENSINGTON HIGH STREET, LONDON W8 65N. TEL. 01-937 5548

TV TUBE REBUILDING

Faircrest Engineering Ltd., manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers'

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

Willis Road, Croydon, CRO2XX. 01-684 1422/01-684 0246

WW - 073 FOR FURTHER DETAILS

WIRELESS WORLD APRIL 1981

B. BAMBER ELECTRONICS

Туре	Price	Туре	Price	Туре	Price	Туре	Price	Туре	Price	Г
AC107	0.25	BC207	0.15	BFX84	0.24	TIS34	0.35			
AC126	0.33	BC208	0.15	BFX85	0.24	ZT20	0.10	21/2906	0.35	
AC128	0.34	BC212	0.10	BFX86	0.25	ZT62	0.47	2N2915	0.55	
AC141	0.25	BC212A	0.15	BFX87	0.25	ZT2270	0.30	2N2925	0.10	
AC142K	0.32	BC213	0.10	BFX88	0.25	ZT3053	0.30	2N2926	0.10	
AC165	0.62	BC214	0.12	BLY36	8.99	ZTX107	0.10	21(3053	0.30	
AC188	0.32	BC239	0.10	BSV64	0.89	ZTX108		21/3054	0.65	
ACY17	0.34	BC327	0.18	8VS68	0.40	ZTX109	0.10	2113055	0.65	1
ACY18	0.72	BC337	0.15	BSX20	0.25		0.10	2113137	0.76	10
ACY19	0.72	BC360	0.35	BSX21	0.25	ZTX196 ZTX212	0.20	2N3114	0.25	
	0.65	BCW35	0.25			ZIXZIZ	0.15	2N3242A	0.15	
ACY20	0.65	BCX32	0.24	BSY27	0.27	ZTX300	0.14	2N3478	0.65	
ACY21	0,73	BCY30	1.34	BSY38	0.20	ZTX312	0.39	2W3583	1.97	10
ACY44	0.32	BCY31	1.34	BSY95A	0.24	ZTX313	0.39	2N3632	8.69	
AD143	0.85	BCY33	1.34	BSY248	0.68	ZTX314	0.43	21/3703	0.15	100
ADYZ3	1.92	BCY34		BSX504	0.84	ZTX320	0.76	2113704	0.15	10
ADY26	7.60		1.60	BU105	1.84	ZTX321	0.76	21/3705	0.15	
AF114	0.50	BCY70	0.18	BU108	1.84	ZTX502	0.18	2W3706	0.15	
AF124	0.38	BCY71	0.20	MP3731	3.29	26210	8.46	2N3707	. 0.15	
AFZ11	5.57	BCY72	0.18	OC16	2.52	26220	8.46	2N3708	0.15	
AFZ12	5.57	BCY87	5.35	0019	2.52	26221	8.46	2N3715	2.97	
ASY52	0.80	BCY88	3.99	0020	2.52	26371	0.97	2N3716	3.27	
ASZ15	2.15	BCY89	3.99	0C22	2.52	211404	0.81	2N3766	1.28	U .
ASZ16	2.12	B0116	0.92	0023	2.52	211441	7.60	2N3790	4.40	
ASZ21	0.80	BD121	1.85	9C24	2,52	2N456A	3.60	2N3819	0.25	·
AUY10	1.29	B0144	1.40	0C25	2.52	2N696	0.35	2N3866	1.20	
BC107	0.10	BDYII	0.87	0028	2,52	211697	0.35	2113904	0.12	
BC107B	0.12	B0Y60	2.90	0029	2.52	2N706	0.21	2N3935	0.12	
BC108	0.10	BOY93	2.30	0035	1.99	2N7D8	0.48	2114126	0.26	
PBC108A	0.12	BF115	0.30	0C42	0.30	2N711	0.35	204236	0.28	1
BC1068	0.12	BF152	0.25	0C44	0.35	2N711A	0.86	2114427		
BC109	0.12	8F158	0.20	0C45	0.40	2N918	0.80	2N5038	3.25	
BC113	0.18	BF159	0.20	0070	0.56	211930	0.32	2N5089	2.45	
BC115	0.17	BF160	0.22	0071	0.47	2N1100	3.31	2N5100	0.25	
BC125	0.16	BF164	0.20	0072	0.47	2N1164	2.97	2N5199 2N5296	0.90	
BC136	0.14	# BF173	0.27	0074	0.47	-2N1302	0.78	2N5459	0.55	
BC143	0.24	BF17B	0.27	0C75	0.47	2N1303	0.69	280459	0.55	
BC147	0.10	BF185	0.27	9C76	0.35	2N1304	0.67	· 2N5461	0.55	1 '
BC147B	0.10	BF194	0.10	0077	0.58	2N1307	0.90	2N5486	0.63	
BC148	0.10	BF196	0.10	OCB1	0.37	2N1489	0.90	2N5687	0.54	
BC153	0.15	BF197	0.10	0C82	0.60	2N1531	7.41	2N6246	2.97	
BC154	0.15	BF200	0.28	0083	0.60	2N1554	8.59	28001	1.34	
BC157	0.13	BF2448	0.32	0C83N	0.60			28025	7.21	
BC158	0.12	BF257	0.32	0C84	0.65	2N1555	8.62	28033	2.93	
80138	0.12	BF258	0.25	0084	0.83	211613	0.25	2S95A	1.34	
BC171	0.12	BF258 BF259	0.25	00139	2.05	201893	0.65	2\$102	1.32	
BC171A	0.16	BF263	0.52	00170	1.26	2N2082	9.25	2\$301	2.26	
BC172B	0.12			00171	1.35	2N2193	0.55	28304	2.04	
BC177	0.18	BF576	0.60	0C200	2.60	2N2219	0.45	2\$324	2.04	
BC178	0.18	BFR80	0.28	0C201 0C202	2.60	2N2220	0.14	28502	2.34	
BC178A	0.20	BFW10	0.80	00202	2.60	2N2222A	0.22	28701	11.12	·
BC179	0.20	BFY50	0.25	00203	2.60	2N2366	0.65	28703	13.52	
BC182L	0.12	8FY51	0.25	0C204	2.60	2N2369	0.18	28711	2.62	1
00100	0.19	BEV52	0.25	00071	0.00	0110470		000.0		

CAMPORE LONG TERM

DISPOSABLE ELECTRODES

MONITOR CATHODE RAY TUBES M28-233 GH, M38-100LG, M28-13W. All brand-new and boxed. £10 each

MAINS ISOLATING

TRANSFORMERS TRANSFORMERS
500VA 240v in 240v C.T. Output. Enclosed in metal boxes, used but in good condition.
£15 each

MAINS TRANSFORMERS 40v in 24v at 25A output. Ideal for sold £15 each

COLOUR T.V. MAINS INPUT FILTER CHOKES

HELLERMAN HEAT SHRINK

Size LVR95 10mm. Colour black, length 150M

LARGE QUANTITY OF USED LIN BINS

PYE ATU4 AERIAL TUNER UNIT 2-9mhz, tapped coil, input via SO239. Totally enclosed in metal box 13in x 5in x 7in. BRAND NEW. Only £8 each

FERRANTI MICROSPOT CATHODE RAY TUBES

Type 3H/1010, suitable for photographic multi-channel recorder systems. Fitted with a mounting collar and prism cemented to the faceplate, screen aluminised, Phosphor P. The tubes are also fitted with mounting units type MU1053 and deflection coil type SC48A. Few only at £55 each

AVO 8 MOVEMENTS COMPLETE

WITH SCALE

RIBBON CABLE

Dept. WW, 5 STATION ROAD, LITTLEPORT, CAMBS, CB6 1QE Telephone: ELY (0353) 860185 (2 lines) Tuesday to Saturday

TELESCOPIC RADIO AERIALS

VIDICON SCAN COILS (Transistor type, but no data)

PYE WESTMINSTER

W30AM, low band, sets only, no control gear complete and in good condition. £45 each

PYE WESTMINSTER

W15AM low bands, sets complete and in good condition but are less speakers, mikes, cradles and LT leads. (Sets only.)

PYE BASE STATION

Prices from £220 each

A.C. ADAPTOR (Battery Charger) 120vac input, 5.8 vdc at 200mA output. USA type mains plug to 3.5mm jack plug, brand new and boxed.

A.C. ADAPTOR (Battery Charger) 117 vac input, 4.5 vdc at 150mA output. USA type mains plug to 2.5mm jack plug. Brand-new and boxed.

ISEP SLOTTED HORIZONTAL

RAIL Available in 9ft lengths.

WATCH STRAPS Black stainless steel, 50p each. Black plastic 25p each, watch spring bars 10p each. Discount for quantity.

DATA DYNAMICS MODEL ASR

240v operation, complete with punch and reade good condition

CB ACCESSORIES

S.a.e. for catalogue and price list.

TERMS OF BUSINESS: Cheques or P.O. with order, made payable to B. Bamber Electronics, or phone your Access or Barclaycard No. Please add 15% VAT on all goods advertised after adding postage as applicable.

CARRIAGE: Orders under £5 nett invoice add 75p. Orders over £5 but less than £20 add 50p. Orders over £20 at cost. Callers welcome.

WW-063 FOR FURTHER DETAILS

READ ALL ABOUT IT — all the latest on home entertainment equipment and ideas in . . .


HI FI YEARBOOK AND HOME **ENTERTAINMENT 1981**

Published again in November, this new 1981 edition in larger magazine size means more comprehensive coverage of the whole range of home entertainment equipment, from aerials to headphones, from microphones to video recorders and from radios to electronic organs.

Backed by authoritative articles on developments in the world of Hi Fi, plus details of stockists, Hi Fi Yearbook and Home Entertainment 1981 is essential reading for enthusiasts and buffs.

Available from leading newsagents and bookshops from 1st November 1980. Price £3.00.

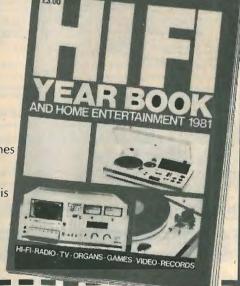If you have difficulty in obtaining your copy order direct from the publishers @ £3.50 inclusive.



ORDER FORM

To: General Sales Manager, Room 205, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Please send me. copy/copies of the Hi Fi Yearbook and Home Entertainment 1981 @ £3.50 including postage and packing. Cheque/postal order should be made payable to IPC Business Press Ltd.

Name Address

Registered in England No. 677128.

State Mil some

STOCK SOFTY

EPROM BLOWER

200 NS 16KX1 DYN. 8 for £19-95 300 NS 1KX4 ST. 2102L-3 650 NS 1KX1 ST. 8 for £ 5-50
TMS4030JL 300 NS 4KX1 DYN 8 for £ 9-95 2708 Ex Equip £2-25

TELETYPE ASR33



minal. Many features including: ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and diculously cheap and reliable data storage. Sup-

ICL TERMIPRINTER 300 BAUD TERMINALS



£325 + CAR

Made under licence from the world famous GE Co The ICL Termiprinter is a small attractive unit with so many features it is impossible to list them in the so many features it is impossible to list them in the space available! Brief spec. as follows; RS232 serial interface, switchable baud rates 110, 150, 300, (30 cps), upper and lower case correspondence type face, standard paper, almost silent running, form feed, electronic tab settings, suited for word processor applications plus many more features. Supplied in good condition and in working order. Limited quantity.



Brand new and boxed only + carriage £7.50 + VAT. £97.50 + VAT.

Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMS or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. £115 + carr. + VAT. Optional 2716, 2716 Function Card £40 + VAT. PSU £20 + £1.50 carr. + VAT. Write or phone for more details Write or phone for more details. 3K × 8 STATIC RAM CARDS

BRAND NEW PCB organised as a 3K × 8 page memory with 24 socketed 2102-L 650ns Rams, 4 Eprom Sockets and 16 TTL Chips for decoding. All IC's guaran-

£24.50 + £1.75 P.P. Dimensions 264 × 195mm. 0.1" connector.

OP PRESS - STOP PRESS - STOP PRESS - ST STEP INTO THE 80's

WITH TOMORROW'S WORLD TECHNOLOGY TODAY

The "TANTEL" Post Office approved PRESTEL-VIEWDATA ADAPTOR

At last this amazing piece of micro technology is available at a price you can afford. Just connect to the aerial socket of any colour or black and white domestic TV receiver and to your Post Office installed jack socket and you are into the exciting world of PRESTEL. Via simple push button use you are able to view a staggering 170,000 pages of up to the minute information on many services and utilities, order goods from companies, even play games!! All this and more without ever leaving your armchair!

ONLY £170 + £1.75 carr + VAT Send £197.50p

Note: When ordering please give the address and telephone number where the Tantel adaptor is to be used, we will arrange all details with the Post Office for installation of the jack socket (normally within 7 days).

MANUFACTURERS

ONLY

100,000 EX STOCK Miniature

relays continental series by Keyswitch, etc. all contact

CALL FOR QUOTES

NOW ONLY

£499 + Carr

JUST IN

Secondhand chassis 9" Blue-best mains powered video monitors, composite video input with inbuilt 5v 3 amp DC P.S.U. Tested, but unguaran-

£39.99 + £7.50 carriage

Complete with circuit.

WE'VE BOUGHT ANOTHER SHIPMENT SAVE OVER £1300!! DZM 180 CPS HIGH SPEED **MATRIX PRINTERS**

This must be one of our greatest bulk deals, this fabulous printer is listed at over £1800 and judging by the construction we are not surprised. Made under license from the LOGABAX Co. the DMZ180 is an exceptionally sturdy high speed 180 cps matrix printer, capable of printing up to 132 characters per line on standard "Fan Fold" sprocket fed paper. A

precision 7 × 7 matrix head using ruby bearings, gives a clear concise type font. Many other features include internal buffer for high throughput, standard ink ribbon, software controllable form and tab functions, standard "CENTRONICS" ASCII parallel interface

Optional extras Floor Stand £30.00 + VAT, Paper Stand £18.00 + VAT

Dept. W.W. 64-66 Melfort Rd., Thornton Heath, Croydon, Surrey. Tel: 01-689 7702 or 01-689 6800 Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimur order value £2.00. Prices and Postage quoted for UK only. Where post and packing not indicated please add 60p per order. Bona Fida account orders minimum £10.00. Export and trade enquiries welcome. Orders despatched same day where possible. Access and Barclaycard Visa welcome.

MAIL ORDER INFORMATION

effective 5v @ 7 amp supply.

Supplied complete with circuit at only £10.95 + £1.75pp.

Believed working but untested, unguaranteed.

I/O TERMINALS



Fully fledged industry standard ASR33 data ter

EQUIPMENT CASES



Superb professional fully enclosed, made for the G.P.O. to the highest standard, offered at a fraction of their original cost they feature aluminium sides, hinged removable front panel, which can be secured by 2 screws to prevent prying fingers. All are finished in two tone G.P.O. grey and although believed brand new may have minor scuff marks/scratches due to bad storage.

CLOCK MODULE

★12 HOUR * ALARM



★ 50/60 HZ The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" × 1½" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am pm, alarm set, power fail indicator, flash-ing seconds cursor, modulated alarm output etc. Supplied brand new with full data only Suitable transformer £1.75.

'GRAB BAGS'

50 + BAG £2.95 100 + BAGS £5.15

ELECTRONIC & EQUIPMENT

DISCOUNT

don't have sufficient stocks of any one item to nclude in our ads., we are packing all these items nto the "BARGAIN PARCEL OF A LIFETIME" pay plus we always include something from our ads. for unbeatable value!! Sold by weight

2.5kds £ 4.75+pp £1.25 5kds £ 6.75+pp £1.80

Keep your equipment Cool and Reliable with our tested ex-equipmen "Muffin Fans" almost salent running and easily mounted. Available is two voltages. 110 V.A.C. £5.05+pp 90p OH 240v A.C. £6.15+pp 90p OH 240v A.C. £6.15+pp 90p OH 240v A.C. £6.15+pp 90p OHMENSIONS 4½" x 4½" x 1½".

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistor Relays, Cap's., P.C.B.'s, Sub-assemblies, Switche

10kds £11.75+pp £2.25 20kds £19.99+pp £4.75

WW-081 FOR FURTHER DETAILS

These latest designs from the drawing board of John Linsley-Hood, engineered to the very highest standard, represent the very best that is available on the kit market today. The delicacy and transparency of the tone quality enable these amplifiers to outperform, on a side-by-side comparison, the bulk of amplifiers in the commercial market-place and even exceed the high standard of the bulk of a property of the commercial market-place and even exceed the high comparison, the 'bulk of amplifiers in the commercial market-place and even exceed the nign standard set by his earlier 75-watt design. Three versions are offered, a 30-watt with Darlington output transistors, and a 35- and 45-watt both with Mosfet output devices. All are of identical outside appearance which is designed to match and stack with our Linsley-Hood cassette recorder 2. As with all Hart kits the constructors interests have been looked after in a unique way by reducing the conventional (and boring) wiring almost to the point of extinction. Any of these kits represents a most cost-effective route to the very highest sound quality with the extra bonus of the enjoyment of building a sophisticated piece of equipment. 30-watt Darlington amplifier, fully integrated with tone controls and magnetic pick-up facility. Total cost of all parts is £81.12. Special offer price for complete kits £72. 35-watt Mosfet amplifier. Total cost of parts £98.41. Special offer price for complete kits £87.40. HART TRIPLE-PURPOSE TEST CASSETTE TC1. One inexpensive test cassette enables you to set up \UV level, head azimuth and tape speed. Invaluable when fitting new heads. Only £2.70 plus V.A.T. and 50 p postage.

LINSLEY-HOOD 300 SERIES AMPLIFIERS

MICROPHONE AMP FOR LHCR 2. A completely self-contained and screened stereo microphone amplifier is now available for the Linsley-Hood cassette recorder 2 deck. This useful unit may of course be used for any application requiring a low-noise high-quality microphone input. Gain may be independently set on both channels to suit many different types of transducer. Input is by stereo jack socket. Complete kit of parts only £8.70 plus V.A.T. and post.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £2.70 plus V.A.T. and 50p postage.

MICROPHONE AMP FOR LHCR 2

A completely self-contained and screened stereo microphone amplifier is now available for the Linsley-Hood cassette recorder 2 deck. This useful unit may, of course, be used for any application requiring a low-noise high-quality microphone input. Gain may be independently set on both channels to suit many different types of transducer. Input is by stereo jack socket. Complete kit of parts only £8.70 plus V.A.T. and post.

Reprints or original Articles from Hi-Fi News, 50p. Post free. No V.A.T. Reprints of MOSFET article 25p. No V.A.T. Post free.

TOP LOADING HI-FI CASSETTE DECK. Very limited quantity of British-made Thorn 4499 top loading decks fitted with stereo R/P head. 3 digit re-settable counter. 12-volt electronic speed-controlled motor and auto stop read.

Very special price £12.99 complete with top cover and cassette door. Post, etc., £1.50. V.A.T.

LINSLEY-HOOD PEAK DRIVE INDICATOR. A very useful device, connected to loudspeakers giving a 4-digit readouts of peak power delivered for the protection of both the loudspeaker and the perceived quality of sound, Gives instant indication even for peaks of only 5 microseconds duration. Unit uses CMOS technology, is self-contained and battery powered. Complete kit except batteries only £17.48 hijs V A T batteries, only £17.40 plus V.A.T.
Reprint of Article 250. No V.A.T. Post free.

CASSETTE HEADS

HS16 SENDUST ALLOY SUPER HEAD. Stereo R/P. Longer life than Permalloy. Higher out	put than
Ferrite, Fantastic frequency response. Complete with data	£8.20
HC20 Stereo Permalloy R/P head for replacement uses in car players, etc	£4.25
HM90 Stereo R/P head for METAL tape. Complete with data	£7.20
H561 Special Erase Head for METAL tape	£4.90
H524 Standard Ferrite Erase Head	£1.50
4-Track R/P Head. Standard Mounting	£7.40
R484 2/2 (Double Mono) R/P Head. Std. Mtg.	£4.90
ME151 2/2 Ferrite Erase. Large Mtg.	£4.25
CCE/8M 2/2 Erase, Std. Mta.	£7 90
CCE/ DIVI Z/Z E1886. DIQ. IVIIQ	L/.JU



Thurlby

Part Cost of Post, Packing and Insurance

A bench power supply system that meets today's needs

P&P Export Orders—Postage or shipping at cost plus

LINSLEY HOOD CASSETTE RECORDER 2

Our new improved performance model of the Linsley Hood Cassette Recorder incorporates our VFL 910 vertical front mechanism and circuit modifications to increase dynamic range. Board layouts have been altered and improved but retain the outstandingly successful mother-and-daughter arrangement used on our Linsley-Hood Cassette Recorder 1.

This latest version has the following extra features: Ultra low wow-and-flutter of .09% — easily meets DIN Hi-Fi spec. Deck controls latch in rewind modes and do not have to be held. Full Autostop on all modes. Tape counter with memory rewind. Oil damped cassette door. Latching record button for level setting. Dual concentric input level controls. Phone output. Microphone input facility if required. Record interlock prevents rerecording on valued cassettes. Frequency generating feedback served drive motor with built-in speed control for thermal stability. All these desirable and useful features added to the excellent design of the Linsley-Hood circuits and the quality of the components used makes this new kit comparable with built-up units of much higher cost than the modest, £94.90 + V.A.T. we ask for the components

LINSLEY-HOOD CASSETTE RECORDER 1

We are the Designer Approved suppliers of kits for this excellent design. The Author's reputation tells all you need to know about the circuitry and Hart expertise and experience guarantees the engineering design of the kit. Advanced features include: High-quality separate VU meters with excellent ballistics. Controls, switches and sockets mounted on PCB to eliminate difficult wiring. Proper moulded escutcheon for cassette aperture improves appearance and removes the need for the cassette transport to be set back behind a narrow finger trapping slot. Easy to use, robust Lenco mechanism. Switched bias and equalisation for different tape formulations. All wiring is terminated with plugs and sockets for easy assembly and test. Sophisticated modular PCB system gives a spacious, easily-built and tested layout. All these features added to the high-quality metalwork make this a most satisfying kit to build. Also included at no extra cost is our new MS15 Sendust Alloy record/play head, available separately at £7.60 plus V.A.T. but REPRINTS of the 3 articles describing this design 45p. No V.A.T.

Please send 9 × 4 S.A.E. or telephone for lists giving fuller details and

Instant easy ordering, telephone your

requirements and credit card number to us on

Oswestry (0691) 2894

Personal callers are always welcome but please note we are closed all day Saturday

Thurlby PL Series Single, Dual and Triple Output Units Prices from around £100

Simultaneous digital metering of voltage and current.

- Twin 3¾ digit (4000 count) meters with ½" LED displays. 0.1% accuracy, Resolution of 0.01 volts and 0.001 amps.
- True constant voltage or constant current operation.
- Current Limit can be set precisely without shorting the output.
- Remote sense facility for maintained precision at high currents. Designed to rigorous quality and safety standards.

Full data and distributor list from Thurlby Electronics Ltd. Coach Mews, St. Ives, Cambs. PE17 4BN Telephone: 0480 63570

WW - 054 FOR FURTHER DETAILS

£235 + CAR

Options: Floor stand £12.50 + VAT
Sound proof enclosure £25.00 + VAT

GIVE YOUR M.P.U A HOME ONLY

£9.95 unerb professional fully enclosed, made for the

NATIONAL MA1012 LED



SEMICONDUCTOR

Amazing value mixed semiconductors, include transistors, digital, linear I.C.'s, triacs, diodes, bridge recs. etc. All devices guaranteed brand new, full

COMPONENTS

DIRECT TO YOUR MICRO

Made by the "BALL MIRATEL" CORPORATION USA the CD12 is a self contained, mains powered chassis professional monitor. All controls are inbuilt on a single PCB with exception of the brightness control which can be brought out for external use. Many features such as composite video, quoted bandwidth of 19 Mhz, superb linearity and definition make this a must for any MICRO/CCTV application.

SCOOP PURCHASE

12" VIDEO MONITORS

HURRY WHILE STOCKS LAST

MEMOREX/BASF 7 MB HARD DISK **DRIVES**

Model 630-1B disk drives by Memorex BASF, TTL signals in and out, high speed, IBM 2311 compatible. Sold in good condition but unguaranteed.

£175.00 + VAT **BUYERS COLLECT**

"THE MULTIVOLT PSU"

The PSU to end all your MPU/LAB requirements, made by "Weir" Electronics at over £200.00. The supply features full regulation, current limit, and

overvoltage protection on all 7 outputs, just look at the spec.
+5v@12 amps, +5v@4.5 amps, +5v@4 amps,

+30v @2 amps, +12v @2.5 amps, -12v @2.5 amps and -9v @1 amp.
A superb unit supplied in two grades, complete

Brand New, Fully Tested Used and Untested

f39.99 Carriage and Insurance RGA FULLY CASED ASCII CODED



Straight from the U.S.A made by the world femous R.C.A. Co., the VP500 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of million operations. The keyboard has a host of other features noluding full **ASCII** 128 character set, user definable keys,

upper/lower case, rollover protection, single SV rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee. VP601 7 bit fully coded output with delayed

VP611 Same as VP601 with numeric pad. VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates.


VP616 Same as VP606, with numeric pad, ost, Packing and Insurance. ORDER NOW OR SEND FOR DETAILS

£59 99

5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.; 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12 x 5 x 3 x. The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp. IM323 K regulator to give an lators or a further 3 amp LM323K regulator to give an

www.americanradionistory.com

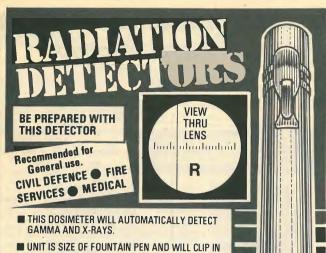

TOP POCKET. ■ PRECISION INSTRUMENT, METAL CASED,

WEIGHT 2 oz. ■ CONTAINS 3 LENSES. ■ RUGGED CONSTRUCTION

■ MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH.

British design and manufacture. Tested, calibrated and guaranteed. Ex-stock delivery by return.

Be prepared, uy whilst available.

404 EDGWARE ROAD, **LONDON W2 1ED**



Standard model

0-5 or 0-50R

ONLY

Post & Packing 60p

£6







Visual monitoring of anything, anywhere, by phone, in seconds, with Robot Phoneline TV.

Robot's Phoneline TV systems provide a low-cost, efficient solution to the problem of visually monitoring remote installations, meters, gauges, traffic, weather, water levels, or any subject, large or small. The Phoneline TV equipment works well with standard CCTV equipment and converts the broadband video signal from the camera to narrow band audio tones for transmission via the dial telephone network or voice grade radio, then to a video signal again for display on a monitor at the camera to a video signal again for display on a monitor at the camera to a video signal again for display on a monitor at the camera to a video signal experience and The agriculture process takes as little as 8.5 seconds and costs. grade radio, then to a video signal again for display on a monitor at the receiving end. The entire process takes as little as 8.5 seconds and costs only the amount of the phone call.

Since one or more cameras can be fed to one or more monitoring stations for viewing sequentially or simultaneously, and since the system can be fully automated, there is a almost infinite number of PLTV system configurations possible.

Permanent storage is available by recording the transmissions on audio cassette tapes.

For fast, uncomplicated, inexpensive visual monitoring of any subject anyplace, Robot Phoneline TV is the answer.

Write or call for more information and descriptive literature.

Robot (UK) Ltd., Building 33, East Midlands Airport Castle Donington, Derby DE7 2SA Tel: (0332) 812446. Telex: 37522

World Leaders in Phone Line Television and Image Processing Systems

WW - 048 FOR FURTHER DETAILS



Range includes

Mica capacitors

Teflon capacitors

Polyester capacitors

the best in electronics

Multiplate ceramic capacitors

Ceramic chip capacitors

Polypropylene capacitors

Polycarbonate capacitors

Polysulphonate capacitors

Microwave chip capacitors

Close Encounters of the Capacitor kind

The Eurofarad close tolerance Capacitors are worthy of your close examination and consideration. They are quality precision components made for the professional market. (Eurofarad is a CECC approved manufacturer) and Pascall, as UK agent, offers the full Eurofarad range of professional capacitors. Send for details today to:

Pascall Electronics Limited Hawke House, Green Street, Sunbury-on-Thames, Middlesex TW16 6RA

Telephone: (09327) 87418 Telex: 8814536

WW - 083 FOR FURTHER DETAILS

ALWAYS G RANGE OF OSCILLOSCOPES, COMPUTERS, TER-

WIRELESS WORLD APRIL 1981

36 MARCONI STANDARD SIGNAL
72MHZ
37 SCHLUMBERGER/SOLARTRON AUTOMATIC COUNTER type FB2602
£150 72WHZ
72WHZ
73 SCHLUMBERGER/SOLARTRON AUTOMATIC GOOTHERT/SPECIAL STATEMENT OF THE STATEMENT HEWLETT PACKARD AC CONVERTOR type 3461A
11 MUIRHEAD WAVE ANALYSER K-134-A 30-310HZ
22 PHILIPS COMPARATOR 278KHZ
33 HEATHKIT CAPACITOR CHECKER IT-28
43 HEATHKIT CAPACITOR CHECKER IT-28
44 HEWLETT PACKARD DIGITAL VOLTMETER type 3440A
45 HEWLETT PACKARD FREQUENCY CONVERTOR type 8729A
46 RACAL AUTO FREQUENCY CONVERTOR type 803R 500MHZ
47 AIRMEC ELECTRONIC VOLTMETER type 314A 5T1A TB.
98 HEWLETT PACKARD MEMORY DISPLAY 5480A with 5486A Contrad 5485A two channel input and 5485A two channel input 99 E.H.T. Unit 230 Volts 50 cs 25VA 7.5KV 100 AVO VALVE CHARACTERISTIC METER

VARIAN RUBIDIUM FREQUENCY STANDARD 100KHZ/1MHZ/5MHZ

49 KEITHLEY INSTRUMENTS REGULATED HIGH VOLTAGE SUPPLY TYPE

48 VARIAN RUBIDIUM FREQUENCY STANDARD 100KHZ/1MHZ/5MHZ

49 KEITHLEY INSTRUMENTS REGULATED HIGH VOLTAGE SUPPLY TYPE
241 Accuracy +/- 0.55% or 1mV
250

50 T.O.A. ELECTRONIC POLYRECORDER type EPR-2T
51 STODDARD AIRCRAFT Radio Interference and Field Intensity Meter type
NM-52A 375-1000MHZ (2 pieces)
52 TAYLOR ADARD AIRCRAFT Radio Interference and Field Intensity Meter type
NM-52A 375-1000MHZ (2 pieces)
52 TAYLOR VALVET ESTER type 45D
53 RHODE & SCHWARZ UHF TEST RECEIVER BN1523 280-940MHZ
(4850MHZ)
54 R & S 2-8 DIAPRAPH 300-2400 MHZ BN3562
55 R & S UNDSIGNED STANDARD STANDARD
56 R & S 2 WHE-UHF FREQUENCY METER 30-3000MHZ BN442
56 R & S 2-8 DIAPRAPH 300-2400 MHZ BN3562
57 R & S DIAPRET STANDARD
58 B & K HETRRODNIN COLTMETER 1985201
59 B & K HETRRODNIN COLTMETER 198201
50 B & K HETRRODNIN COLTMETER 1992 2005
60 HOWLETT PACKARD CLIP ON DC MILLIAMPMETER type 428A with 100 MHZ
61 DO 100 MHZ BN3562
62 SOLARTRON IDIGITAL VOLTMETER type 1420.2 with Mean AC Unit 255
63 SOLARTRON IDIGITAL VOLTMETER type 1867
64 MARCONI SINGLIF ALVOLTMETER TYPE 1867
65 JARROLD SWELE GENERATOR 1995BA/3/S (CT402)
65 SOLARTRON IDIGITAL VOLTMETER 199 1867
65 JARROLD SWELE GENERATOR 1995BA/3/S (CT402)
66 COSSOR NOISE LEVEL METER 199 1001
67 COSSOR NOISE LEVEL METER 199 1001
68 COSSOR NOISE LEVEL METER 199 1001
69 COSSOR NOISE LEVEL METER 199 1001
60 COSSOR NOISE LEVEL METER 199 1001
67 MARCONI VARIABLE ATTENUATOR 199 F1073A/S (CT421)
68 HEATHKT DEACAD FRESIST ANCE BOX DRIU
69 MARCONI SRABLE ATTENUATOR 199 F1073A/S (CT421)
69 MARCONI SWELE SECILLATOR 199 C1344 0.1HZ-10MHZ
60 HEWLETT PACKARD CONTRETER 199 6001
61 MARCONI SWELEPS ASSORDMENT 199 5001
62 SIGNAL GENERATOR 199 C7344 0.1HZ-10MHZ
63 ST.C. LEVEL METER 199 6000 MS
64 ASTICLE ASSORDMENT 199 5001
65 COSSOR SWEP OSCILLATOR 199 C7340
67 MARCONI SWELEPS ASSORDMENT 199 5001
68 COSSOR NOISE LEVEL METER 199 6001
69 COSSOR NOISE LEVEL METER 199 6001
60 COSSOR NOISE LEVEL METER 199 6001
60 COSSOR NOISE LEVEL METER 199 6001
60 COSSOR NOISE LEVEL METER 199 6001
61 MARCONI SWELEPS ASSORDMENT 199 5001
62 C

CONVERT THIS UNIT TO A

SUPER BATTERY CHARGER

Attractive green ministry quality case with remova ble top and bottom plates – heavy duty powe switches, high powered resistors to control current

good quality centre mounted amp meter, strip of wing nut terminals on front panel which can be used for connecting leads. All this for £3.50. P&P £2. Four units £12. Carriage £5.

STEPPING MOTORS 6/12 position with additional where the rotor is coils. Device can be used as a tacho. Diagram supplied. Will actually work on 5 volts. 12/24 recommended.

£1.50 each P&P 75p or 5for £5 P&P £1.50.

STEPPING MOTORS

KEYBOARD PAD

Size 3x2/2x2" high with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank. £4 each, P&P £1, or 5 for £15 P&P £2.

MINIATURE KEYBOARD octs, marked 0-9 and A-F and 3 optional function keys. £1.75 each.

CRYSTALS 50p each. Flat metal case — 19.2KHZ; 844.8KHZ; B7G — 10MHZ.

LOUDHAILERS. Transistorised hand-held. no leads. Standard internal batteries supplied. How! Switch £20 ea. P&P £2 INFRA RED QUARTZ LAMPS. 230V 620 Watts. Size 13\2" x \8" dia. £1.50 ea. 240V 1650 Watts. Size 22\3" x \2" dia. £3

ea.
BRIDGE RECTIFIER. 2 Amp 50p ea.
PHOTODIODE DETECTOR 4" fly leads, 25p ea.
AMPHENOL. 17-way chassis mount edge connectors 0.1

AMPHENOL. 17-way chassis mount edge connectors 0.1 spacing, 15p ea.
I.E.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre offset) 60p ea.
FANS. 115V 13 Watts. Size 3½4 x 3½4 x 1½" BRAND NEW. £4.50 ea. Secondhand £2.50 ea.
DELAY LINE. 50 nanosecs. 3 connections — ground-in-out Size 2x 7½6.65/16" New 25p ea.
MOTOR 12V DC with pulley and integral semiconductor. Speed Control. New £1 ea.
LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly, 15p.eae.

15p ea.
DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10way Printed Circuit Mount. New 10p ea. 100 for £7.50

oz/in. torque, 12/24 volt input 4-wire £12 each. P&P £1.50

SOME TEKTRONIX 500

RANGE OSCILLOSCOPES with Single Trace Plug-ins. Working. From £100. Phone for details

PLEASE CHECK AVAILABILITY BEFORE ORDERING

DIODES All new full spec. devices IN3063 BAX 13. 1S44, 1N4148; 1N3470; 1N4151. 100 off £1.50, 1,000 off £10

INFRA RED IMAGE **CONVERTER Type 9606** (CV 144)

CREED MODEL 75

Printer with keyboard. Late model Still the cheapest way to get a printout from your microprocessor. Basic data and connections supplied.

ONLY £25 each

As new, Ministry boxed £40 each

RACAL SA520

£15 each

1¾in diameter. Requires single low current 3KV to 6KV supply individually boxed. With data.

£12.50 each Infra Red Lamps also advertised

FERRET A.T.E. £650 Phone for details

VARIAN RUBIDIUM STANDARD Model R20, 5mhz, 1mhz, 0,1mhz £600

EX-MINISTRY SOLID STATE
400 HZ INVERTOR
28 VDC input, 115V output. Size 7 x 2½ x
15in approx. Connection details supplied.
£18 each. P&P£2

TRANSISTOR INVERTOR

115V AC 1.7 Amp Input. Switching is at 20Khz. Output windings from Pot Core. Can be rewound to suit own purpose or unit can be broken for host of components. Circuits supplied.
£1.25 each. P&P £2.

PULSE TRANSFORMER. Sub min. Size ½2 x 5/16 x ½4". Secondary centre tapped. New 20p ea. REMO TV TYPE MULTIPLIER. Two high voltage outputs and focus, £1 each. HANCES. Use the proper EHT CABLE, 10p per metre or £7.50 per 100 metre/drum. P&P £2. PHOTOGRAPHIC LAMPS. Pearl 230V 500 watt. Screw cap 75p ea. Box of 12 £55.9 P&P £1.50. RAPID DISCHARGE capacitors 8mfd 4kV £5 each. P&P £2. MYSTERY (C PACK. Some 40 pin — good mixture — all new devices. 25 (Cs for £1. P&P 50p. DECOUPLING CAPACTORS 0.05mfd 10V; 0.01mfd; 0.047mfd 250V; 33K, 330pf. All values 100 for £1.50. 75325 SN15862 MC4028 7417 7441 74C86 74C161

MOTOROLA DUAL in Line 6 pin Opto Co plate tester version 50p each. plate tester version bup each. EPROMS 2708 £5.50 each. ELECTROSTATIC VOLTMETER. 7.5KV £8 ea. P&P £1.50.

Other ranges available — please enquire.

FRIMMERS. Sub min. 0.25 to 1.25 pf. 1 to 4.5 pf. 7 to 45 pf. All .H.T. Capacitor 500pf 8KV 20p each. 0-way MULTI COLOUR RIBBON CABLE. New 40p per metre. 10-way MULTI COLOUR RIBBON CABLE. New 40p per meu e. 10 metres for £3.
GEC UHF 4-button tuner £1.50 each.
CENTAUR 115V FANS 4/2 x 4 x 1/2" £4.50 ea.
EX-USED equipment, tested, 60p each.
CONTACTORS. Heavy Duty 24V DC 5 make £1 each.
GEC UHF/VHF 6-button tuner £2 each.
S11A PHOTO MULTIPLER £2 each. P&P £1.
RANCO 250V 18A THERMOSTATS, with Control knobs calibrated fib. 200 degree £2.50 each.

THINMIERS. Subminion of the state of the sta

winkat DRE PC MOUNT SLIDE SWITCH. 2 pole 2 way 10peach.
4 D1GIT 7 SEGMENT per digit plus a figure one to the left plus
a centre minus sign to the left of the figure one with decimal
places between digits. Good brilliance at 1.5V. 15 connections
22.50 each. Some E.H.T. Transformers and Capacitors available. Please enquire.
FELEPHONES 706 style black; grey or blue £5.50 ea; 746 style
black or grey £7.50. Older style black £2.50 each. Discoloured
grey 706 £4 sa P&P.E1.50 per telephone.
DC SERVO MOTOR 110V 2.5Amp continuous. Double shaft.
Brand new. 4 wire. 4 brush £25 ea. Plus carriage.
PC Mount POTS. Wire wound with knob 200 ohm & 10ohm.
10p-ea.

PC Mount POTS. Wire wound with knob 200 ohm & 10ohm. 10p ea.
MiN. RELAY 24V. 2 pole c/o. Brand new. 75p each.
TIME DELAY RELAY 0.1 to 10 secs. 115V AC. DPDT. £5 each.
CAPACITORS at 5p each. 0.1uf 400V. Small rec. block PC
Mount German class; 3300pf; 220nf250V; 0.01 mfd 160V.
MISERT can be used as Microphone/Earpiece (Like used as insert in telephone but superior quality) Ex-Min. Brand new wrapped 75p each. or 10 for £6.
TOROIDAL TRANSFORMERS. Input 0-120-240 Volts. Output 0-12V; 0-12V. 10VA per winding. Encapsulated — identical to R.S. Components at £8.90. OUR SPECIAL PRICE £5 ea. P&P £1.50.

£1.50.
TANTALUM CAPACITORS – All at 10p each – 100 off £7.50.
22mfd 6V; 39mfd 10V; 22mfd 35V; 1mfd 35V.
MINIATURE SLIDE SWITCHES. Single pole 2 way 10p each, 10.6f \$2n.

10 off 90p.

HEAVY DUTY RHEOSTAT. 7.50hm 5.5Amp. Diameter 5".

Standard 1/4" shaft £2.50 each. P&P £1.50.

LARGE EX-MINISTRY SPEAKERS. OUTSIDE 15 ohm o 500 ohm. Tested. £25 each or 5 for £100.

MINIMUM ORDER £3 VALUE OF GOODS. MINIMUM P&P £1.50 — where P&P not stated please use own discretion — excess refunded. £5 CARRIAGE ON ALL UNITS. P&P or CARRIAGE and VAT at 15% on total MUST BE ADDED TO ALL ORDERS. CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc. BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

RANCO 250V 18A THERMOSTATS with Control knobs cali-brated 50-200 degree C£2.50 each. SOLID STATE UHF TUNERS. 30 acs £1 each. BRAND REX blue wire wraps. 30 metres for £1. P&P 25p. SLIDER CONTROL 500K Log. Single track. Complete with knob Length 32′″. 25p each. TRANSFORMERS

TRANSFORMERS
AUTO 240V input 115 V. 1 Amp output £1.25 each. P&P £1.25.
240V input . Soc. 6V. 1.86A. Size 2 \(^1\)2 \(^2\)2 \(^2\)2 \(^2\)2 \(^3\) (good quality.
£1.50 ea. P&P £1.
240V input Soc. 12V 0.92A. Size 2 \(^1\)2 \(^2\)2 \(^2\)2 \(^3\)2 \(^3\)0 (good quality.
£1.50 ea. P&P £1.
240V input 12V 100MA. Size 60 \(^4\)40 \(^3\)40 \(^3\)40 \(^3\)40 \(^3\)40 \

50p.
115V input. Sec 10-0-10V1A. Size 2½ x 2 x 2", 2 for £1.50.
SEMICONDUCTORS
1N4005 – 5p; 1N4002 – 3p.
4K5 paech.
BC147, BC288, BC157, BC158, BC237, BF197, OA90, OA81,
BA154, BA243.

At 25p each: TIP31, TIPA1A, 2N5£96, AF139, 2TX341. BY127 10p. BF181 20p; BD239 49p; BD241 40p; MA343AT 49p; BD28 50p; BD233 & BD234 Comp Pair 25W — 80p per

49); 80226 307) - 8050 8 80234 Comp Pair 2507 - 809 per pr. at 50p each. REGULATOR TBA625 8to 20V in -- 5V out 100MA TO5 Con. 50p each BF2566 20p. TV AMPLIFIER TBA 120 20p each.

NORWOOD ROAD, READING

TELEPHONE NO. READING 669656

2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel"

VALVES VAT **VALVES** Minimum | QQV03-20A | GAB7 | | QQV03-25A | GAG5 | | QQV06/40A | GAK5 | | QQV03-12 | 4.20 | GAK5 | | QQV03-12 | 4.20 | GAK5 | | QQV03-12 | 4.20 | GAL5 | | SC1/400 | 4.50 | GAL5 | | SC1/400 | 4.50 | GAL5 | | SC1/400 | 4.50 | GAM6 | | TT21 | 16.50 | GAM6 | | U25 | 1.15 | GAQ4 | | U26 | 1.15 | GAQ5 | | U191 | 0.85 | GAS6 | | U27 | 1.15 | GAQ5 | | U191 | 0.85 | GAS6 | | U301 | 0.65 | GAM6 | | U301 | 0.66 | GAM6 | | U301 | 0.67 | GAM6 | | U301 | 0.68 | GAM6 | | U301 | 0.68 | GAM6 | | U301 | 0.90 | | U3 0.70 6X5GT 1.15 6Y6G 0.60 6Z4 1.165 787 0.60 9D2 0.60 9D2 0.60 9D2 0.60 9D2 0.85 10C2 4.20 10F18 1.50 10P13 2.50 11E2 3.440 12AG 1.00 12AT7 1.15 12AU6 0.80 12AX7 1.80 12AX7 0.80 12BH7 0.85 12EBH7 0.85 12EBH7 0.85 12EBH7 0.85 12EBH7 0.85 12ESGT 0.80 12ESGT 0.90 12E 0.85 954 0.90 955 0.70 956 0.70 956 1.75 957 1.25 1625 0.70 1629 2.90 2051 0.70 5842 1.50 5881 1.50 6967 0.070 5842 1.50 6067 0.070 6067 0.070 6067 0.070 6067 0.085 6064 0.085 6064 0.085 6066 0.085 6066 0.085 6067 0.085 6067 0.085 6067 0.085 6067 0.085 6068 0.085 6069 0.090 6068 0.090 6068 0.090 6068 0.090 6069 0.090 6069 0.090 6069 0.090 6069 0.090 607 0.090 607 0.090 607 0.090 607 OV03-12 SC1/600 SC1/60 VALVES 4CX 1000A 4CX 5000A BM 25L BW 153 DM 25LB YL 1420 YL 1430 YL 1440 GXU 6 CV1597 CV2116 4CX 1500B BR 189 BR 179 CV 6131 GMU 2 TY4-500 BK485/5552A MIL 5948/175 Z759 Z749 Z800U Z801U Z803U Z900T 1A3 1L4 1R5 1S4 1S5 1T4 1U4 1X2B 2D21 2K25 2X2 2X2 3A4 3A72 3D6 3D22 3E29 3S4 4B32 5B/255M 5B/255M 5C22 5R4GY 5V4G 5Y3GT 5Z4G 5Z4GT 6/30L2 SN74L73N 0.38 SN74474N 0.30 SN7485N 0.30 SN74B5N 1.10 SN7491AN 0.32 SN74913N 0.42 DM74123N 0.48 SN75033N 0.42 SN7603N 1.80 SN7603N 1.80 SN7603N 1.95 MCSB00P 8.20 MCSB800P 9.80 MC14511BA1 2.95

VALVES AND TRANSISTORS elephone enquiries for valves, transis etail 749 3934, trade and export 743 0899.

PRICES MAY VARY

TEST SET FT2 FOR TESTING Transceivers A40, HARNESS "A" & "B" CONTROL UNITS "A" "R"

"J1" "J2," Microphones No 5, 6, 7 connectors, frames, carrier sets, etc.

DRUM CABLE continuous connection YC 00433.

The Forge, Lucks Green, Cranteigh

Surrey GU6 7BG Tel. 04866 5997

COLOMOR

(ELECTRONICS LTD.) 170 Goldhawk Rd., London W.12

FIELD TELEPHONES TYPE "J" Tropical, in metal cases

SWITCHBOARD. Can work with every type of magneto tele-

POSTAGE: £1-£3 45p; £3-£5 55p; £5-£10 60p; £10-£15 75p; £15-£20 90p; over £20 free.

Tel. 01-743 0899 or 01-749 3934 **Open Monday to Friday** 9 a.m.-5.30 p.m.

METALFILM RESISTORS 1k1 1k2 1k5 1k6 1k8 2k2 2k7 3k3 3k6 3k9 4k7 5k6 6k8 7k5 8k1 110R 120R 130R 130R 150R 180R 220R 220R 220R 230R 330R 330R 330R 470R 510R 560R 620R 680R 750R 820R 820R 1% Tolerance, 1/4 Watt 330k 470k 560k 820k **ONLY 3p EACH** Special Offer: 5 PCS of EACH (445 RESISTORS) ONLY £11.50. High Quality High Stability, Huge Minimum 5 pcs per value 89 Values (E24) Strength. VAT inclusive. Add £1.00 p&p all areas. ORION SCIENTIFIC PRODUCTS LTD.

Memories	8085 & Z80
2708	
2716	£4.75 8085A£6.80
2732£1	1.00
2114L ceramic 200ns	4.79
2114L ceramic 450ns	4.30 00714
2112A 45ns	£5.60
0110L 200ns	
(2K × 8 CMOS RAM, I data hold = 50μA)	8255A-5£4.99
4116 ceramic 200ns	22 50 8257-5£10.40
8264-15 150ns*£2	
(64K dynamic RAM)	8279-5£10.00
CRT Controller, µPD 3301*£3	7700
Flanny Diag Controller - PD700	7.73 700 700
Floppy Disc Controller, µPD765*£2	Z80-CTC£5.75
* Please phone for stock situation	Z80-DMA£19.95
Quantity discounts available on 10+ of one device.	Z80-SI0/2 £29.95
the state of the s	200-310/2 3.29.93

10 Wardour St., London W1

Please add P. & P. 30p to orders under £15. Add V.A.T. to total.

BDS Microsystem Designs Ltd. 28 Pinewood Close, St. Albans, Herts., AL4 0DS Telephone: St. Albans (0727) 31831

Belle Vue Radio and **Electronics Exhibition**

in the LANCASTER HALL on SUNDAY, MARCH 29, 1981

Doors open at 11 a.m.

The North's Premier Amateur Radio and Electronics Event

Features-

Inter-Club Quiz Construction Contest R.S.G.B. Bookstall

Grand Raffle Amateur Computer Stands

Radio Society's Stands and Trophy Morse Code Challenge


Home Office and Raynet Stands Belle Vue has ample car parks

F.M. talk-in on GB3NRS & G8NRS/A on 145MHz Chs S.22, R2, R6, and on 433MHz Chs SU8, RB4 & RB14

ADMISSION 40p – BY RAFFLE TICKET AND EXHIBITION PLAN ENTER AT REAR OF BELLE VUE OPP. MAIN CAR PARK OFF HYDE ROAD A57

FREQUENCY COUNTERS-OFF/AIR

PPM3

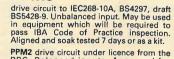

PPM2 drive circuit under licence from the BBC. Balanced inputs. Approved for critical programme monitoring by IBA, EBU and BPO.

SUM AND DIFFERENCE changeover board to suit PPM2 or BBC ME12/9.

PPM BOXES Illuminated mains powered single and twin versions. ERNEST TURNER high quality movements 640, 642, 643 and TWIN with flush-mount-

ing adaptors and illumination kits from stock.

Exhibiting at APRS: Stand 31, June 10-12 Peak Deviation Meter * Programme and Deviation Chart Recorders * Stereo Disc Amplifier 2 and 3 * Moving Coil Preampli-fier * 10 Outlet Distribution Amplifier * Stabilizer * Fixed Shift Circuit Boards.

RECEIVERS 250MHz 801 B £250 Crystal

OFF/AIR RECEIVER **TYPE 103** PRICE £135

50MHz 6 Digit £130 250MHz 8 Digit £250 520MHz 8 Digit £325 1-2GHz 8 Digit £550

20 models available including LED versions



RCS ELECTRONICS WOLSEY ROAD ASHFORD, MIDDX. Phone 53661

WW-082 FOR FURTHER DETAILS

Appointments

Advertisements accepted up to 12 noon Monday, 23 March, for May issue, subject to space being availDISPLAYED APPOINTMENTS VACANT: £12 per single col. centimetre (min. 3cm) LINE advertisements (run on): £2 per line, minimum three lines. BOX NUMBERS: £1 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 4AS.)

PHONE: IAYNE PALMER, 01-661 3033

Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.

ELECTRONIC OPPORTUNITIES £5,000-£15,000 Microprocessors - Minicomputers - Digital -Analogue - HF - VHF - UHF - Microwave

Where does your skill and interest lie?

Design? Test? Sales? Service? Systems? or perhaps Software?

- * Our clients are drawn from all sectors of industry: There are opportunities for Managers, Project Leaders, Engineers and Technicians.
- * Most UK locations and some Overseas
- * Make your first call count Contact MIKE GERNAT on 076-384-676/7 (24 hours)

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED 148-150 High St., Barkway, Royston, Herts SG8 8EG.

(691)

THE PAPUA NEW GUINEA UNIVERSITY OF TECHNOLOGY DEPARTMENT OF ELECTRICAL AND COMMUNICATIONS

PRINCIPAL OR SENIOR **TECHNICAL OFFICER**

(DIGITAL/MICROPROCESSOR)

Applications are invited for the above-mentioned position in the Department of Electrical and Communications Engineering

Applicants will be required to have appropriate qualifications and to be experienced in the fields of digital electronic equipment. Preference may be given to applicants with particular experience in microprocessor development.

Salary: K12450 - K15275. (K=£Stg. 0.6636). Appointment level will depend upon qualifications and experience

The initial contract will be for three years; other benefits include a gratuity of 24% taxed at 2%, appointment, repatriation fares, leave fares for the staff member and family after 18 months of service, settling-in and out allowance, six weeks' paid leave per year, education fares and assistance towards school fees, free housing. Salary continuation and medical benefit schemes are

Detailed applications (two copies) with curriculum vitae, together with the names and addresses of three referees, should be received by the Registrar, Papua New Guinea University of Technology, P.O. Box 793, Lae, Papua, New Guinea, by 30 March, 1981. Applicants resident in the United Kingdom should also send an additional copy to the Association of Commonwealth Universities (Appts), 36 Gordon Square, London WC1H OPF.

A division of SOS Bureau Ltd

The SOS Group

Trading as:

SOS Staff Bureau SOS Industrial Staff

SOS Senior Appointments

The following are a selection of the many vacancies currently on

FIELD SERVICE TECHNICIAN! £6,000! CAR! COMPUTER SYSTEMS! W. LONDON! A.T.E. ENGINEER! £8,000! ATLAS PROGRAMS! AVIONIC SYSTEMS! TEST TECHNICIAN! £7,000! CMOS EXPERIENCE USEFUL! COMMISSION PROTOTYPE! TEST EQUIPMENT! TEST TECHNICIAN! £6,000! VHF, UHF EX-PERIENCE! MICRO COMMUNICATIONS! EQUIPMENT AND TRACKING CONTROLS SERVICE SUPPORT ENGINEER! £9,000! ORGANISE MAINFRAME AND PERIPHERAL! INSTALLATION! SALES ENGINEER! \$9,000! CAR! NORTH ENGLAND! RELOCATION PACKAGE! TELECOMMUNICATIONS!

For information on these and other vacancies nationwide please contact: Lee Wood, 71 The Mall, Ealing, London W5 5LS.

(1009)

Company Communications Controller c.£10.000

As a major name in aviation and communication services for the world, maintaining and upgrading our own lines of communication is vital; customers and suppliers, for instance, are constantly in contact through telex, telephone, data transmissions and post. The task of our Company Communications Controller is to supervise both the technical and human aspects of the existing network and to advise on the introduction of new computer based information handling systems throughout the group. He or she will work from Southall, liaising with suppliers and with service staff on maintaining equipment. There is also a large amount of advisory and analytical work involved, in order that existing systems may

Candidates should possess an HNC in telecommunications engineering and should have worked for at least five years with a manufacturer, major telecomm. user, or in Post Office telecommunications. They should understand business communication problems, and ought to be capable of expressing technical solutions clearly to nontechnical management.

Benefits include a staff restaurant, a pension and life assurance scheme, relocation expenses where applicable and 5 weeks' holiday plus bonus. Please apply, in writing, to John Callow, IAL, Aeradio House, Hayes Road, Southall, Middx, quoting Ref. K/024. Tel: 01-843 2411.



THE HIGH TECHNOLOGY TASK FORCE

COMMUNICATIONS SYSTEMS COMPUTER SYSTEMS AND SERVICES AVIATION SYSTEMS AND SERVICES - WORLDWIDE

UMIST

EXPERIMENTAL OFFICER FOR SILICON DEVICE MANUFACTURE

REF: EEE/25. A new facility is being assembled in the Solid-State Electronics Group of the Department of Electrical Engineering and Electronics, for the manufacture and testing of semiconductor components in ultra-clean conditions. Within a large clean area there will be a total of 60 linear feet of ultra-clean beach beginning in the seminary and decayance of equal to the seminary and carried seminary and be a total of 60 linear feet of ultra-clean bench housing a wide range of equip-ment. The Experimental Officer will be responsible for the day-to-day running of this facility, overseeing its use by undergraduate and postgraduate stu-dents, and will be responsible for the maintenance of the equipment, includ-ing the air filtration plant. He/she may also be required to assist staff of the Solid-State Electronics group in any re-seach which involves semiconductor seach which involves semiconductor processing. A wide range of skills is re-quired, together with the necessary ex-perience and confidence to allow unsu-pervised working.

Salary will be in range of £4795-£9595 per annum (under review).

Requests for application forms, quoting the above reference, should be addressed to the Registrar, Room BB, UMIST, PO Box 88, Manchester M60 1QD. The closing date is March 31, 1981.

TOP JOBS IN **ELECTRONICS**

Posts in Computers, Medical Comms, etc. ONC to Ph.D. Free

Phone: 01-906 0251

(8994)

NORTHERN REGIONAL HEALTH AUTHORITY **ELECTRONICS TECHNICAL ASSISTANT (2 POSTS)**

Required for Regional Engineer's Division, based at Walkergate, New-

The appointments will be at Technical Assistant Grade 1. Salary £6,633

The posts offer technologically interesting and varied work, with excellent working conditions and well-equipped laboratories, and involve visits to hospitals throughout the Region, for which financial reimburse-

Applicants must be of high calibre and have had considerable and broad experience with modern electronic equipment.

Minimum qualifications: HNC or City and Guilds Full Technological Certificate in Electronic Engineering or equivalent.

Application form and job description available from the Regional Personnel Officer, Northern Regional Health Authority, Benfield Road, Newcastle-upon-Tyne NE6 4PY.

Closing date: 1 April, 1981.

Please telephone or write to Janet Findlay for further details. Roger Squire's

ELECTRONIC

SERVICE ENGINEERS

NORTH LONDON - ILFORD

Our company specialises in both sales and servicing of Disco-

theque Sound and Lighting Equipment. We currently have vacancies for engineers who have had previous experience of either HiFi, Studio PA or similar equipment. Good salary, plus

Commission and Bonus.

Barnet Trading Estate Park Road Barnet Herts EN 5 5SA Telephone: 01-441 1919

PHILIP DRAKE ELECTRONICS LTD.

PROJECT ENGINEER

to work in the Project Department. The job includes project discussion with customers, the detail design of systems, test supervision, and the compilation of system handbooks. Experience in the broadcast audio industry is essential and a formal qualification is desirable.

ASSISTANT TEST ENGINEER

to test primarily the custom-built products, mainly intercommunication systems, along with the standard product range. Some experience in the testing of audio and digital circuits and in the design of test jigs is desirable.

DRAUGHTSPERSON/TRACER

to work primarily in the Project Department, to prepare handbook drawings and design system metalwork, and also to prepare circuit diagrams and standard products. Experience in control panel layouts and broadcast audio requirements is

The company offers a 37½-hour week with 20 days' holiday minimum. Experience in the broadcast industry and/or suitable qualifications are desirable for all positions. Salary negotiable dependent on experience.

Apply by telephone or writing to: ALAN BRILL, PHILIP DRAKE ELECTRONICS LTD. 23 REDAN PLACE, LONDON, W2 4SA - Tel: 01-221 1476



CAPITAL HOUSE 29-30 WINDMILL LONDON W1P 1HG TEL: 01-637 5551

THE UK'S No. 1 ELECTRONICS AGENCY

Design, Dev. and Test to £10,000 Ask for Brian Cornwell

SALES to £12,000 plus car Ask for Ken Sykes

FIELD SERVICE to £10,000 plus car Ask for Maurice Wayne

We have vacancies in ALL AREAS of the UK

Telephone: 01-637 5551 (3 lines)

Sony Broadcast success story means even more career opportunities!

Tremendous growth and success has created the need for even more first class staff at the Basingstoke International Headquarters of one of the world's leaders in professional television broadcast equipment.

UK Sales Manager/ess – TV Production Houses

£ neg + car

This is a new position created as part of our planned expansion programme. The successful candidate should possess experience of either Production or Engineering Operations within a broadcast television environment. A knowledge of professional VTR's, editing systems and cameras is necessary whilst previous sales experience is desirable, though not essential.

Sales Engineers/Technical Support Engineers for Western Europe

Competent engineers experienced in video cameras and/or VTR's are sought to join our sales team. Successful candidates are likely to be in the age range 25-35 and should be highly motivated and able to work on their own initiative. Experience in dealing with customers would be an advantage as would knowledge of a second European language. Travel within the western European area will be necessary

Engineers -

information.

Commercial/Sales Applications Openings exist, at various levels for engineers with a wide experience of the TV Broadcast Industry, to utilize

their knowledge in a dynamic commercial environment. The selected candidate will be self motivated, capable of working with a minimum of supervision, and will be appointed to our Proposals/ Quotations section. He or she will have the ability to prepare detailed and concise customer presentations/

Previous commercial/sales experience desirable, however not considered essential

quotations complete with pricing

Systems Project Engineers

For our young and enthusiastic Special Projects Team. They will be involved in the design, manufacture and commissioning of static and mobile television systems, and in modifications and accessories. The successful applicants will have a thorough knowledge of sound and television principles. Ideally, he or she should have experience in operational television or its allied manufacturing industry.

Product Specialists

Opportunities exist for young engineers from a broadcast television background to be involved in all aspects of development, marketing and support of our entire product

We would be particularly interested to hear from you if you are currently working with professional VTR's/ VCR's, cameras or microprocessor controlled post production systems and would like to further develop your technical and commercial skills in a challenging environment.

Field Service Engineers

Currently, openings exist at Engineer and Senior Engineer levels for personnel with experience of working on professional VTR's and cameras probably in a Broadcasting organisation or TV Broadcast Equipment Manufacturer. The Engineer level position should appeal to applicants with limited relevant experience who are now seeking a progressive environment in which to broaden their careers. Both positions offer the opportunity for some UK and overseas travel

R & D Engineers

Sony is now established as the world leader in digital video recording technology. Development is still in the

formative stages but rapidly progressing to the new era of the 'All Digital Studio'. The R & D Section is involved in long term investigations into the application of high speed digital techniques to video processing, and in conventional product design. Being part of an international R & D team, the successful applicant may expect occasional opportunities for overseas travel. Applications are invited from engineers offering experience in high speed digital processing or video engineering. Alternatively, a well qualified recent graduate could be considered.

Lecturer

The Lecturer will join our training team and after a suitable familiarisation period will be required to conduct theoretical and practical training courses on our major products, and/ or write circuit descriptions and produce training manuals with lucid block diagrams. Ideally, candidates should have had experience of video tape recorders, digital circuits and a practical up-to-date knowledge of the broadcast industry. Knowledge, or an ability to master the techniques of video cameras, digital audio equipment and the application of microprocessors to broadcast equipment will be an advantage although we are prepared to provide the necessary additional training. Promising young graduates may also apply for consideration as a Trainee

If you like the thought of enjoying the success of world leadership then write in strict confidence to Barry White, Personnel Manager, Sony Broadcast, now! And please don't forget a CV.



Sony Broadcast Ltd.

City Wall House Basing View, Basingstoke Hampshire RG21 2LA United Kingdom

(968)

Challenging positions at home and abroad

RADIO TECHNICIANS COMMUNICATIONS **ENGINEERS**

EAE Limited install and maintain communications systems for the oil industry, at home

Due to rapid and continuing expansion in our activities, we constantly require Radio Technicians, with experience of HF, MF, VHF and UHF, and Engineers (preferably qualified to HNC level or above) in the fields of Microwave, Multiplex and Tropospheric Scatter.

In the North Sea, earnings are in the range £9,000 to £12,000 p.a. Overseas earnings could be up to £20,000 - plus tax concessions and generous home leave.

The work is demanding, but rewarding, offering you the chance to use your skills and your initiative to the full.

The company is based in Great Yarmouth, with offices in Aberdeen and Lerwick - but where relocation is necessary, we will give generous assistance with removal, legal and temporary accommodation expenses.

Please apply, with details of your career to date, to: Personnel Manager, EAE Limited, Dept WW, Offshore House, 284/285 Southtown Road, Gt. Yarmouth, Norfolk NR31 OJB Telephone 0493 58541

EAELimited

The following personnel are required by a radio manufacturer in South Africa. Successful applicants will need to be stable and not short term contract work.

Radio development engineers with experience of domestic radio. Salary R1500 per month. Radio technicians, preferably with

factory experience. Salary R1000

per month.

Draughtsmen, preferably with radio cabinet design experience.
Salary R1000 per month.
Radio or cabinet assembly line foreman or chargehands. These applicants must be prepared to train experience. train operators. Salary dependent on experience.

on experience.

Injection moulding machine setters. Salary R1000 per month.

Must be prepared for shift work.

PHOTO - STAFF CONSULTANTS LIMITED

133 OXFORD STREET LONDON W1R ITD

Telephone: 01-439 1821 (10 lines) Telex 263 231 FOSTAF G

(990)

DIGITAL EXPERIENCE?

FIELD, SUPPORT AND PRODUCTION. VACANCIES IN COMPUTERS, NC, COMMS., MEDICAL, VIDEO, ETC.

For free registration ring 01-290 0267



FLECTRONICS RECRUITMENT SERVICE

INNER LONDON EDUCATION AUTHORITY

Learning Materials Service

Television Centre, Thackeray Road, London, SW8

MOBILE SECTION ENGINEER ST3

The mobile section operates colour broadcast standard television facilities including a three camera (Link 120) mobile control room and battery portable equipment (Sony BVP, BVU). The main function of the section is to make observational classroom recordings for use in teacher education both in London and nationally. All members of the crew share rigging duties and driving of vehicles. A current driving licence is highly desirable and training will be provided leading to an HGV test.

The engineer will join a team of three other engineers who are jointly responsible for the operation and maintenance of the section's equipment. This involves lighting, vision control, microphone rigging, sound mixing and V.T. operation. Experience in one of the fields is essential; however as training in others will be given, it is important that candidates have appropriate academic qualifications and a thorough knowledge of current broadcast engineering practices. Candidates must also possess

Hours of work will be in accordance with the requirements of the service (the normal working week being 35 hours).

Further details available from the Mobile Videorecording Section, tele-

Salary within the scale £8,115 - £8,709 (plus an irregular hours allowance of £156 per annum).

Application forms available from the Education Officer (EO/Estab 1c), Room 365, County Hall, London, SE1. Telephone 633 7456/7546. Closing date: 14 days from appearance of advert.

SENIOR ENGINEER

ENG/OB Maintenance Salary: £11,406 p.a.

Independent Television News Limited has vacancies for two Senior Engineers in their expanding ENG/OB Maintenance Section at ITN House, London, W.1

The successful candidates would be members of a small team responsible primarily for the maintenance of ENG equipment including Sony BVU series U-matics, RCA Tk76C and Sony BVP330 cameras, TBCs and associated portable equipment. The section is also responsible for the long-term maintenance of our two camera Outside Broadcast Unit.

The work would occasionally involve travel with ENG teams to remote locations.

Previous maintenance experience with U-matic equipment and/ or lightweight cameras is essential

Generous pension scheme, free life insurance

Please telephone the Personnel Office on 01-637 3144, quoting reference number 30301 for an application form

(966)

SULTANATE OF OMAN

RADIO AND TV BROADCAST ENGINEERING **VACANCIES**

The Sultanate of Oman operates a modern colour television and radio broadcasting service with studio centres situated in the North and South of the country, the two centres being linked by satellite. High power VHF and low power UHF transmitters are employed to provide a 625 PAL TV service to populated areas of the Sultanate. The radio broadcasting service uses HF, MF and VHF transmitters of various powers. Both services are managed by the Ministry of Information and Youth Affairs.

Due to expansion of the service vacancies for a variety of posts have arisen and applications are invited from suitable qualified persons.

TRANSMITTER ENGINEERS

For maintenance of high power VHF TV transmitters and low power UHF transposers, high power MF, HF and VHF FM sound transmitters. The work will involve travel and in some cases overnight stops away from base. The transmitters operated within the Sultanate are manufactured by Siemens, Philips, Marconi and Continental Inc., U.S.A.

STUDIO ENGINEERS

For maintenance on cameras, vision mixers, S.P.G.S., vision distribution systems, telecine machines and video monitors, etc. There will also be operational work, particularly on outside broadcasts.

The equipments employed are Philips LDK15 cameras, Bosch Fernseh KCU40 and KCP cameras, vision mixer units by C.D.L. and Bosch Fernseh, telecine by Rank Cintel and Bosch Fern-

SOUND MAINTENANCE ENGINEERS

To maintain a wide range of high quality sound broadcasting equipment.

VTR ENGINEERS

For maintenance on Ampex VR1200B and Bosch Fernseh BCM40 machines. There will also be some operational work. During the forthcoming year it is intended that 1in. "C" Format VTR machines will be installed

PLANNING AND PROJECT ENGINEERS

To carry out planning for a wide range of transmitter installations for both TV and radio. Planning and Systems Engineers are also required for work on new radio studios to be constructed over the next few years.

Successful applicants will be expected to be directly involved with the nuts and bolts of the installation work, in some cases in remote areas. Applications are also invited for a number of senior positions in the transmitter, studio groups and electro-mechanical services groups. If you feel you can apply your knowledge and expertise to the efficient running of these groups we will be pleased to hear from you.

Applicants should be qualified to degree or HND level and have not less than six years' relevant experience. The senior positions require considerably more years of varied but relevant experience. In most cases a knowledge of Arabic —although not essential — would be useful.

Salaries, which are paid in Rials Omani, are fully remittable and tax-free and range from pounds sterling 1100 to 1300 per month upwards. The senior positions start at pounds sterling 1500 to 1700 per month (depending upon current rate of exchange).

Married accommodation is provided together with free air passage at beginning and end of contract for family. Air tickets are also provided for leave after the first year of service.

Applicants should write stating age, nationality, qualifications and full details of experience to:

Ministry of Information and Youth Affairs, Post Box 600, Muscat, Sultanate of Oman, marking the envelope "Technical Office" in top left-hand corner.

NORTH-EAST LONDON POLYTECHNIC FACULTY OF ENGINEERING BARKING PRECINCT LONGBRIDGE ROAD

Development Engineers in Digital Electronics

We have an important client in the Cambridge area who is about to embark upon a major development programme incorporating projects valued at several million pounds. Over the last few years they have been developing and exploiting a specialised area of telecommunications, and to complete the highly specialist and skilled teams which are involved in breaking new ground in digital development, two experienced Engineers are needed immediately.

They will ideally have experience of both hardware and software gained in a development environment where high standards and iminent deadlines are the norm. A Degree standard of education is less important than experience on design and development and they will have the opportunity of seeing a prototype design right through to

Our client offers in return the opportunity to become involved in a thriving organisation which offers excellent terms and conditions of employment, good career prospects and, most important, an opportunity to take digital electronics to new frontiers.

> Please apply in confidence, quoting Ref. KR77, to: **Andrew Millhouse Ketchum Recruitment Limited** 52 Bedford Row, London, WC1R 4LX. 01-405 1260

SCHOOL OF CHEMICAL & SYSTEMS ENGINEERING

DAGENHAM, ESSEX

SENIOR **TECHNICIAN**

T5 REF: 83/E/80

required to control and supervise technicians working within the microprocessor laboratory, under the supervision of the Principal Technician. Other duties will include planning and progression of progress and financial reports, and development, including design assistance, of equipment within the laboratory. Candidates should hold a full technological certificate and/or HNC/HND qualifications, and have had 5-10 years' experence in a technical environment.

The inclusive annual salary will be on a scale from £7,233 to £7,695 according to age, qualifications

For further details and application forms please contact the Personnel Office (R), North East London Polytechnic, Asta House, 156/164 High Road, Chadwell Heath, Romford, Essex, RM6 6LX. Telephone 01-590 7722, Ext. 3121 or 3135, quoting the above refer-

CLOSING DATE FOR RECEIPT OF APPLICATIONS: April 3, 1981.

IF THIS IS RECESSION **WE LIKE IT**

AT LAST ELECTRONIC ENGINEERS ARE BEING PAID WELL AND THEIR WORK IS APPRECIATED .

We have hundreds of vacancies which include

SYSTEMS ENGINEERS: for new company specialising in secure computers based on DEC 11/23 and Z80. Knowledge of image processing and pattern recognition an advantage. To £13,000. SURREY.

RESEARCH ENGINEER/MANAGER: for a group providing support to an international company engaged in research on precious metal refining, cancer research, pollution monitoring, etc. Broad based experience. To

R.F. ENGINEERS: for small dynamic company engaged on telemetry and remote monitoring instruments for the off-shore industry — tankers, gas rigs, etc. To £10,000. LONDON.

HARDWARE AND SOFTWARE ENGINEERS: to work on a new generation of Printers and Data Terminals based on Z80 Intel 8080 and 8008. To £11,000. BERKS.

PRINCIPAL AND SENIOR MICROWAVE ENGINEERS: for development of V.C.O.s, frequency multipliers, amplifiers and fitters. Good salary but confidential MIDLANDS.

YOUNG ENGINEER: with 8085 HW/5W experience to join a high flying team working on novel controls for the automotive industry. To £8,500.

DESIGN ENGINEER: broadcast TV equipment including character generators and teletext terminals. To £8,000. SURREY/HERTS. BORDER.

SENIOR ENGINEER: to design and develop special modules for users of a large international computer network based on ICL 1900 and PDP11. To.

DESIGN ENGINEER: mini and micro computer based control equipment and systems for the heavy mechanical electro mechanical industry. Z80 HW/SW experience essential. To £8,000. NORTH-EAST ENGLAND.

COMPUTER ENGINEERS: vacancies throughout UK in systems test, field

For further details, please contact:

Charles Airey Associates

PROBABLY THE BEST KNOWN SUPPLIER OF ELECTRONIC ENGINEERS IN THE COUNTRY. Financial T

ONE IN A MILLION?

chance that one - perhaps two - is destined to make a significant

That person's first decision might well be to join QUAD in Huntingdon. At school, he or she will have realised that amplifier design is not just a matter of having a listen or a fiddle with standard circuits and their variations. Later will have come an adolescent stage of great discoveries. "Increase the rise time to eliminate TIM" power supply for better imaging'

Following on from such childish things will have come an ability to distinguish between the characteristic impedance of the medium and the third row of the dress circle and between peak flux density and the rather gooey substance fed by spoon to small children. He or she will, nevertheless, be sufficiently down to earth to know that one newton is about the weight of the average apple.

Well, drop us a line anyway.

Mr. P. J. Walker

THE ACOUSTICAL MANUFACTURING COMPANY

30 St. Peter's Road, Huntingdon, Cambs. PE18 7DB

DEPARTMENT OF NUCLEAR PHYSICS

ELECTRONICS TECHNICIAN

Salary £5249-£6129 rising wef July, 1981, to £5695-£6650

Applications are invited for the post of electronics technician in the Department of Nuclear Physics for interesting and challenging work. The post involves assisting in the development and maintenance of a variety of equipment incorporating fibre-optic data links, 8 and 16-bit and bit-slice microprocessors, as well as some analogue circuitry. Some experience is essential, as are willingness and ability to learn quickly.

Applications in writing together with the names of two referees should be sent as soon as possible to the General Administrator, Department of Nuclear Physics, Keble Road, Oxford OX1 3RH. (967) THE LEADING TELEVISION FACILITIES COMPANY

REQUIRES

DIRECTOR OF OPERATIONS

EXCELLENT SALARY + CAR + PENSION + BUPA + PROFIT SHARE

The position of DIRECTOR OF OPERATIONS requires a person with drive, initiative and clear thinking, to be able to deal with the day-to-day demands of this high technology Television Facilities Company providing Studio, VTR and O.B. services to its Clientele.

Loyalty, hard work and the ability to lead, will be rewarded by a career in the fast-moving TELEVISION SERVICE and the Operations Director and his/her colleague Directors will have the opportunity of long-term future career development. The Company will be looking forward to one of the senior Directors becoming the next Managing Director.

The applicant must have Engineering ability and have worked or be working in a Broadcasting organisation and have high level Management experience plus that special "something" of being able to lead and drive for the achievement of the Company's policies.

The position of Director of Operations will be a Company Board appointment.

Please apply to the Sole Recruitment Agents in the strictest confidence quoting "OPS DIR 1981":



PERSONNEL & ELECTRONICS LTD.

Triumph House

Telephone: 01-573 8333 1096 Uxbridge Road Hayes

Telex: 934271 Middlesex UB4 8QH

England

(1005)


Can you develop our potential?

department has been extensively reshaped with new laboratories being built with a view to expansion. We can now offer Test Equipment Development Engineers and Technicians a real opportunity to become involved in the latest technology coupled with positive career development.

Test equipment development engineer £6500-£7500


Working closely with our Senior Engineers and outside companies you will primarily assist the Design Engineers in developing Test Equipment Design. In addition, you will develop systems and units from outline specifications through to building prototype units.

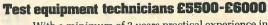As the department is still in its early stages you will have the opportunity to make a positive contribution to its formation and you will also be expected to attend comprehensive training seminars and



With a minimum of 2 years practical experience in a repair environment and an HNC or C&G in Electronics, you will undertake the repair and calibration of Proprietary and Purpose-Built Test Equipment

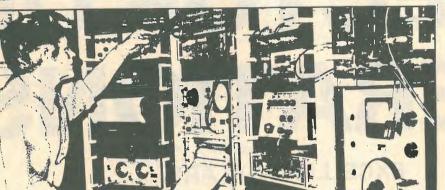In addition to 5 years practical experience in repair and calibration, you should have the ability to communicate with Senior



For both positions we offer outstanding career prospects with a company that is looking to the future. Apart from competitive salaries, we offer a sports & social club, 23 days holiday, contributory pension scheme and a subsidised restaurant. For further information, please telephone Julie Foreman on 578 0081 or write to her at:



Ultra Electronic Communications Ltd 419 Bridport Road Greenford Trading Estate

Technicians/Junior Engineers (Broadcasting Coverage)

If you like an outdoor life with plenty of travel all over the UK and are qualified to ONC/TEC level in electrical engineering (or a related subject), we may have just the career opportunity for you.

Working as a member of a small team, you would be involved in carrying out tests and surveys for our future television and local radio transmitter sites. A current driving licence is essential. Previous working experience should have involved testing or taking measurements.

Starting salary will be within the range £4,280-£5,980 per annum, according to experience. Further progression to a maximum of £7,360 per annum is possible after a period of experience.



INDEPENDENT BROADCASTING AUTHORITY

Please write or telephone for an application form quoting Ref: WW/575cc to Glynis Powell, IBA, Crawley Court, Winchester, Hampshire, SO21.2QA. Telephone: 822270.

(These posts are open to men and women).

UNIVERSITY OF SURREY

Audio Visual Aids Unit

Television Engineers

ONCE IN A DECADE CHANCE!

Join a small and lively team providing television services for teaching and research. Now converting to high quality Video 80 colour system, studio based but versatile and mobile. Photo-

graphy, film, graphics and instrument workshop services available within the Unit. Salaries according to experience and qualifications on scales between £4,870 and £7,873. Further training

available where appropriate. Write or telephone now: Staff Officer, University of Surrey, Guildford GU2 5XH. Telephone

Guildford 71281, ext. 776 for full information, quoting reference

THE OPEN UNIVERSITY **FACULTY OF** SCIENCE

Electronics

Technician

Applications are invited for a technical vacancy in the Chemistry Discipline. The main duties of the post will be to maintain and upgrade spectroscopic instru-ments and other apparatus, including ments and other appearatis, including mini-computers, an to take responsibility for the operation of a Varian Electron Resonance Spectrometer. An ability to contribute to the design, particularly in the computer interface area, of electronic equipment would be an ad-

vantage. Candidates should possess HNC (Electronics) or equivalent qualification and have 9-10 years' relevant exper

ience. Starting salary will be within the Grade echnician salary scale £6020-£7191 (£6,532-£7,802 p.a. from 1st July,

p.a. (£6,532-£7,802 p.a. from 1st July, 1981). Further details and application forms are available from the Assistant Secretary Science (3440/1), The Open University, Walton Hall, Milton Keynes MK7 6AA, or vvaiton Hall, Militon Keynes MK7 6AA, or telephone Militon Keynes (0908) 653481: there is a 24-hour answering service of 653868. Closing date for applications: 14th April, 1981.

TELEPHONE ENGINEER ABU DHABI

A Telephone Engineer is urgently required with experience on Siemens ESK 3000E or similar crosspoint exchange.

TELECOMMUNICATIONS TECHNICIANS

We also have vacancies for Radio Techs. able to take up appointments at

Comprehensive c.vs should be airmailed immediately to:

Mr. George Fee, General Manager AL MARIAH UNITED CO. P.O. Box No. 206, Abu Dhabi U.A.E.

Telex: 22323 Phone 326017 giving contact U.K. telephone

T.V./Video **Engineers Media Librarian**

*Salary range 5230-5625 Saudi Riyals per month

for the King Faisal Specialist Hospital and Research Centre Riyadh, Saudi Arabia

If you are well qualified in either of these areas, here is an excellent opportunity to make a break for 2 years and work in one of the world's most advanced Hospital and Research Centres. Working conditions are first class and all equipment and systems are the most modern available.

We need experienced T.V./Video Engineers to help maintain the hospital's sophisticated television network (mostly Sony equipment). You will be working with a five channel closed circuit system which is used for patient monitoring, training and medical/surgical recording, and in addition provides entertainment programmes for the hospital's surrounding residential and services complex.

Applicants should be able to operate test equipment and be familiar with PAL, SECAM and NTSC systems. Some previous experience of studio production (telecine and electronic editing systems) would be an advantage.

We also need a male Media Librarian to take overall control of the hospital's film and photographic library and operate the alv equipment lending pool.

These are married status posts and successful applicants will be offered a 2 year contract (extendible by mutual agreement) with generous leave periods, air conditioned accommodation subsidised meals and education assistance for eligible dependants. There are excellent facilities for sport and

*Sterling exchange rate at the time of going to press 8.0

Please apply in writing with career details, quoting ref. no.

Jim Hawkins Hospital Corporation International 49 Wigmore Street

Employment Agency reg. no. SE(A) 4698

HOSPITAL CORPORATION

UNIVERSITY POST GRADUATE STUDY

ELECTRONICS RESEARCH AT THE UNIVERSITY OF ESSEX

Graduates who have (or final year students who expect to obtain) a first or upper second-class honours degree are invited to apply for research leading to a higher degree (M.SC., M.Phil. or Ph.D.) in the following areas

Audio (high quality audio systems, music synthesis), Circuit Design (computer-aided design, filters), Computer Systems (architectures, languages, man-computer interaction, microprocessor systems), Optical Communications, Acousite Noise and Vibration Cancallation, Satellite Communication Systems, Microwave and Millimetre Wave Propagation, Telecommunications Transmission (data transmission, filters, PCM, DPCM),
Telecommunications Switching Systems and Software (computer control, traffic studies, network configurations), Visual Displays and Television Engineering (computer graphics, 3-D and colour TV), Picture Coding and Processing (feature extraction) tion, digital filtering, perception).

Further information and application form available from:
Professor K. W. Cattermole, Department of Electrical Engineering Science (Ref. JAN/2), University of Essex, Wivenhoe Park, Colchester CO4 3SQ.

Appointments

Professional Careers in Electronics



All the others are measured by us...

At Marconi Instruments we ensure that the very best of innovative design is used on our range of communications test instruments and A.T.E. We have a number of interesting opportunities in our Design, Production and Service Departments and we can offer attractive salaries, productivity bonus, pension and sick pay schemes together with help over relocation. If you are interested to hear more, please fill in the following details:-

NameAddress	Age
Telephone Work/Hon	ne (if convenient)
Years of experience	0-1 1-3 3-6 Over 6
Present salary £3,500 £4,500	£4,500- £5,500- over £5,500 £6,500 £6,500
Qualifications None	C&G HNC Degree
Present job	
	WW1 1

Return this coupon to John Prodger, Marconi Instruments Limited, FREEPOST, St. Albans, Herts, AL4 0BR. Tel: St Albans 59292



GEC MARCONI ELECTRONICS COMPANY

National Heart and Chest Hospitals **Brompton Hospital**

Medical Physics Technician Grade IV or III (ELECTRONICS)

We require a technician to work in a small but busy department which provides a comprehensive medical electronics/physics service to this leading cardio-thoracic

Within the department the technician will be engaged mainly in electronics work but other scientific or engineering skills would be an advantage. In addition the technician will be required to work in clinical areas trouble shooting and

advising staff in the use of equipment. Salary within the range of £4931-£7277 inclusive depending on experience. For further information contact Chief Technician, Mr. P. Butler, ext. 4252.

For application forms and job description contact Personnel Manager, Miss J. A. Jenks, Brompton Hospital, Fulham Road, London, SW3. Tel. 01-352 8121 ext. 4357.

MANCHESTER POLYTECHNIC

MANCHESTER POLYTECHNIC.

Department of Communication Arts and Design

SENIOR TECHNICIAN

required for the School of Film and Television. Experience required in operation and maintenance of electronic equipment, preferably CCTV and/or sound equipment. An appropriate qualification such as ONC or City and Guilds would be an advantage. A Union Membership Agreement is in operation under which new employees are required to join a recognised union. Salary scale: T3/4 £5,268-£6,651. For further particulars and application form (returnable by 3 April 1981) send a self-addressed envelope marked A/353 to the Secretary. Manchester Polytechnic, All Saints, Manchester. M15 6BH. (988)

TESTERS, TEST TECHNICIANS, TEST ENGINEERS. Barn what you're really worth in London working for a World Leader in Radio & Telecommunications. Phone Len Porter on 01-874 7281, or write: REDIFON TELECOMMUNICATIONS Ltd., Broomhill Road, Wandsworth London, SW18 (985)

EXACT TIME?

MSF CLOCK is ALWAYS CORRECT —
NEVER GAINS OR LOSES, SELF SETTING AT SWITCH-ON, DIGITS
SHOW Date, Hours, Minutes and
Seconds, auto GMT/BST and leap
year, also parallel BCD output for computer or alarm and audio to record and
show time on playback, receives
Rugby 60KHz atomic time signals,
built-in antenna, 1000Km range, ABSOLUTE ACCURACY, £54.80.
V.L.F.7 10-15KHz Receiver £13.70.
60KHZ RUGBY RECEIVER, as in MSF
Clock, serial data output, £15.70.
Pach funt-o-build kit includes all parts,
printed circuit, case, postage etc
money-back assurance so GET yours
NOW.

CAMBRIDGE KITS, 45 (WR) Old School Lane, Milton, Cambridge (965)

BUILDING RAMS?

Why waste time hand-wiring RAMS? This 5.3 x 2.5 inch professional plated thru PCB mounts on your prototyping board, looking like an 8K byte TTL compatible static RAM. 13 address lines, 8 data I/O, write enable, 2 eg and 1 positive card selects.

Assembled with sockets, pins and caps, just plug in 16,2114's and 1,74LS138 £21 plug in 16 2114's and 1 /4L51. Bare board £15, no VAT, post paid.

Ibix Electronic Design 56H Norris Hill Drive Heaton Norris Stockport, Cheshire

ENCAPSULATING, coils, transform encapsulating, coils, transformers, components, degassing, silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment low cost, used and new. Also for CRT regunning metallising. Research & Development. Barratts, Mayo Road, Croydon, CRO 2QP. 01-684 9917. (9678

ARTICLES FOR SALE

memory bargains. Low price guaranteed devices. Eprom programming service. SAE for information, T.D.S., 57 Westmead, Woking, Surrey, GU21 3BS. (907

CLEARANCE PARCELS: Transistors, CLEARANCE PARCELS: Transistors, resistors, boards, hardware, 101bs only £5.80: 1,000 Resistors £4.25, 500 Capacitors £3.75. BC 108, BC 171, BC 204, BC 230, 2N 5061, CV7497 Transistors, 10-70p, 100-£5.80. 2N 3055, 10 for £3.50. S.a.e. lists: W.V.E. (3), 15 High Street, Lydney, Glos. (444)

LAB CLEARANCE: Signal Generators: Bridges: Waveform, ators; Bridges; Waveform, transistor analysers; calibrators; standards; millivoltmeters; dynamometers; KW meters; oscilloscopes; recorders; Thermal, sweep, low distortion true RMS, audio FR, deviation. Tel. 040-376236. (8250

deviation. Tel. 040-376236. (8250

BRAND NEW VERO RACKS 19in x
5½in, complete with 20 off 40 way
edge connectors (only 6 used), 20
card slides and locking front panel
(12in long). P.S.U. insitu on card
slides having 110/240v input, on/
off switch and power on indicator.
Output is +5v at 5 amps and
-10v at 5 amps, fully stabilised.
(Can be converted to +12v at 5
amps). Price £35 P/P and VAT
inclusive. Rushmoor Electronics
Ltd, 43 Queens Road, Farnborough.
Hants. Telephone 0252 515373. (975)

AIRCRAFT BAND Xtal controlled Receiver Type Lowe AP-12, £95.— Telephone Derby 760809. WANTED. Sweep generator in HF range. (980

AVELEY CYBERVOX reel to reel language laboratory. Type AERC4 recorders, various items control unit, headsets, desks, offers invited for whole or part. Further details, Language Centre, Exeter University, Exeter EX4 4QH. Telephone Exeter 77911, extension 775. (981)

TELETYPE KSR33 with stand £100. Scopex 4D10A dual 10 MHz oscillo-scope with probes, £150. — Tele-phone Cambridge 46504. (987

ARTICLES FOR SALE

TO MANUFACTURERS, WHOLESALERS & **BULK BUYERS ONLY**

Large quantities of Radio, T.V. and Electronic Compinents.

RESISTORS CARBON & C/F 1/4, 1/4, 1/2, 1/3. 1 Watt from 1 ohm to

RESISTORS WIREWOUND. 1½, 2, 3, 5, 10, 14, 25 Watt. CAPACITORS. Silver mica, Polystyrene, Polyester, Disc Ceramics, Metalamite, C280, etc.

Convergence Pots, Slider Pots, Electrolytic condensors, Can Types, 'Axial, Radial, etc.

Transformers, chokes, hopts, tuners, speakers, cables, screened wires, connecting wires, screws, nuts, transistors, ICs, Diodes, etc., etc. All at Knockout prices. Come and pay us a visit. Telephone 445 2713

BROADFIELDS & MAYCO DISPOSALS
21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho Corner (9461)

RACAL COMMUNICATIONS RECEIVERS. 500kc/s 30mc/s in 30 bands 1MHz wide. RA17 £1.50. RA17L £200. Or a few as new £250. RA17E £300, all air tested, supplied with full manual, dust covers, in fair condition, new metal louvred case for sets £25. RA98A SSB-ISB adaptors, new and boxed with manual £75. RA96D used with manual, £75. RA218 SSB-ISB adaptors and fine tune units for RA117 £65. MARCONI TF801D/88, £150.

MARCONI R.F. RADIATION & POWER METER. OA1430 (CT477), as new, in grey metal case with full manual, power meter FX range, 10mc/s to 10gc/s, complete with X-S-L band aerials, £50.

MUIRHEAD FACSIMILE EQPT. TX D901 D/S £50. RX D900 D/S or P/D £75 each.

WEATHER SATELLITE. RX D900 S/1A or S/2A £125 each with manual

EXTEL TRANSTEL MATRIX PRINTERS. 5 level Baudot Code. Accepts speeds up to 300 bauds. Supplied set to 50 and 75 bauds switched. Tested with manual, £165.

All items are bought direct from H.M. Government, being surplus eapt. Price is ex-works. S.A.E. all enquiries. Phone for appointment for demonstration of any item. JOHNS RADIO, 424 BRADFORD ROAD, BATLEY, YORKS. TEL: 0924 478159 (9.30 a.m.-1 p.m.).

TEKTRONIX 465 oscilloscope, min condition, calibrated, other test equipment. — Phone, 0582-425721.

DIGITAL WATCH TESTER. Placing a digital watch on the sensor pad gives immediate readout of timekeeping. Accurate, attractive instru-ment uses. Built-in off-air frequen-cy standard. Offers invited for full manufacturing data, including pre-sentable prototype. 073 088 317.

GRUNDIG SATELLIT 2100. Multi band radio. £180. — Southend-on-Sea 588359. ASR 33 data terminal good condition including paper tape I/O, stand and all operator manuals, £240.— Telephone 01-946 3464. (998

6800 PARTS: 6802 MPU £6.50; PARTS: 6802 MPO 25.50; 6825 PARTS: 6850 ACIA £2.50; 2716J-8 UV £5.00. All to full spec. Postage £0.40. — M. S. Alexander, 83 Strachan Avenue, Dundee DD5 1RF. (994

ADVANCE SWITCH MODE SUP-PLIES, unused 5V at 40A £175. 24V at 15A £225. 5V at 20A £135. Tele-type 33 keyboard punch reader £250. Prowest 24in 5A B/W monitor £150. — Telephone Chesham (02405) 71432 evenings. (996

COSSOR 75MHz PORTABLE DUAL TRACE SCOPE, delayed sweep, ex-cellent condition with handbook, £295. — Phone (02556) 6540, Frin-

BREAKER BREAK, Build your own CB rig (27 MHZ transceiver), full circuit diagram and parts list. All components available in UK. Send a large SAE and £2.95 to P. Sherwood. 89 Aylestone Walk, Manchester M10 9NU, I'm on the side.

RET INTO TELEPHONE ANSWER-SET INTO TELEPHONE ANSWER-ING SERVICING. Telstor (old model) operational manual, £4.50. Autophone manual £3.75. Old model Telstor spares available. SAE en-quiries. G. Hay, 189 West Hendon Broadway, London NW9, 01-202 3344 (Callers by appointment please).

VÁCUUM EQUIPMENT. Edwards 12in coating unit. Also 140 L/S. Ion pump and chamber. Ion gauge, Fleet 3266. (1012

NEW 1981

MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL

by Markus

Price: £32.50

RADIO AMATEUR HANDBOOK by ARRL 1981 ed. Price: £8 THE ART OF ELECTRONICS by P. Price: £13.50 Horowitz WORLD RADIO TV HANDBOOK,

Price: £10.50 **ELECTRONIC PRINCIPLES 2nd ed.** Price: £4.35 by A. P. Malvino MANUAL OF ELECTRONIC SER-VICING TESTS AND MEA-VICING TESTS AND SUREMENTS by R. Genn Price: £10

INTRO. TO DIGITAL FILTERS by T.

MICROPROCESSORS AND MICROCOMPUTERS FOR ENG. STUDENTS AND TECHNICIANS by Price: £5.65 B. Wollard USING CP/M A SELF-TEACHING GUIDE by J. Fernandez Price: £6.75

> *ALL PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO.

Specialist in Scientific & Technical Books

19-21 PRAED STREET **LONDON W2 1NP**

Phone 402-9176

Closed Sat. 1 p.m.

G.W.M. RADIO LTD, 40/42 Portland Road, Worthing, Sussex. Telephone 34897 for surplus, wholesale and retail. Ex-Government and Marine retail. Ex-Government and Marine Communications receivers for callers. Changing stocks of test equipment, part exchanges, etc. Radio telephone equipment supplied to the trade. Model 7 Avometers £32 incl. Some Avometer movements available for selection by callers. Dashboard watches by Golay £35 each incl. WAMTED end lots and runs for shop and mail order. Test equipment Large or small lots of factory surplus. R/T sets and systems. systems.

VIDEO FOR SALE. Philips N1700 VCR LP plus six tapes 23 hours each. Excellent condition. Little used. £245. Private sale. Tel: office hours 01-460 6174. Also, 5C/450A valves. Two for sale. Any offers.

TELETEXT TEXAS XMII decoder module complete with infra red, remote control and data, £65. Phone Mirfield 499298 evenings. (983)

manufacturer has surplus test equipment and components for sale, large SAE for list. R. Dutton, 80 Wheatland Lane, Wallasey, Merseyside L44 7EH.

WIRELESS WORLD APRIL 1981

EXCLUSIVE OFFER

RACK MOUNTING CABINETS HIGHEST QUALITY 19" Ref PE LL10 TT Over 60 types available from 12 to 90 high. Also twins, triples and consoles. Above are only a fev types. Please send for full list.

AUDIO AND INSTRUMENTATION-TAPE RECORDER-REPRODUCERS

RECORDER-REPRODUCERS

Ampex FR1300 7 track 12" UHER 4000 1/4"

Consolidated 3800 7 track 12" UHER 4000 1/4"

Plessey ID33 Digital Units 7 track 12"

Plessey B5500 Digital Units 7 track 12"

Plessey B6500 Digital Units 7 track 12"

Ampex FR-1100. 6 speeds, stereo 1/4"

Ampex FR600. 4 speeds, 7 track 12"

D.R.I. RC-I. 4 speeds, 4 tracks 1/4", 1/2", 1"

Min-com CMF-100. 6 speeds, 7 tracks 1/4", 1/2", 1"

Min-tom CMF-100. 6 speeds, 7 tracks 1/4", 1/2", 1"

Prices of above £70 to £500 Also Transport Decks only availab

We have a large quantity of "bits and pieces" we cannot list — please send us your requirements. We can probably help — all enquiries answered.

×	Racal RA 117 Complete stations Leak Stereo 20 Amplifiers GEC TT-100 Valves Ink Jet Recorders Racal MA-796 Drive Units	£390.	00
3	CEC TT 100 Volume	£30.	00
h	Ink let Recorders	£190	00
4	Racal MA-796 Drive Units	£180.	nn
4	Optron Optical Encoders	£80 (nn
â	Ampex Bulk Erasers	£95.0	00
*	Eimac 6156 Valves	£21 (na
*	Clare Flash testers Advance Signal Generators H1E-J1	£50.0	00
*	Advance Signal Generators H1E-J1	£30.0	00
*	Bradley CT 471B VT Multi Meters Westrex Multi Cellular H.F. lens Horns	£60.0	00
×	Westrex Multi Cellular H.F. lens Horns	£40.0	00
×	General Electric 200/600 KHz 500 watt transmitters	S-	•
4	mitters Plessey PR-1556 filter Modulators Marconi HR-23 ISB Receivers K.B. Discomatic Domestic Juke Boxes	£245.0	טע
4	Marconi HR-23 ISR Receivers	£220 (20
Ŧ	K.B. Discomatic Domestic Juke Boxes	£90.0	'n
÷	SUR-025 WIRE Detectors in chests	. + 40 C	m
*	Hewlett Packard 400H VTVM Motors	COE C	'n
\star	Hewlett Packard 211A Sq. Wave Gen Astrodata & Ikor Meteorological Equipmen	£80.0	00
×	Astrodata & Ikor Meteorological Equipmen	t	
×	Ion Pump E.H.T. Power Supplies	£60.0	00
×	Ion Pump E.H.T. Power Supplies		
4	G R Kalas Flutter Motors Model 1740D	£14.U	10
2	Tektronix 551 Scopes	£160.0	'n
£	Tektronix 555 Scopes	£180.0	io
줖	Telegnic VR2M Sweeps	CAED O	2
×	Hell Schriber RC-28 Lenkurt Model 26D Data Sets. Aerial Multicouplers from Marconi TF 1168 Disc Oscillators	£75.0	O
×	Lenkurt Model 26D Data Sets	£90.0	0
×	Aerial Multicouplers from	£25.0	0
×	Marconi TF 1168 Disc Oscillators	£90.0	0
Ā	Hughes Memoscopes Nems Clarke 1306 VHF Receivers	£120.0	0
Σ			
Σ	Helix Aerials 11" & 18" and Reflectors Textronix 543A Oscilloscopes Textronix 561A Oscilloscopes mon Mobile 80 foot Tower Hydraulic 80ft ex 12" closed. Mounted on 4-wheel drive is	£1/5.U	'n
2	Textronix 543A Oscilloscones	£90.0	ň
7	Textronix 561A Oscilloscopes	£140.0	ŏ
Sir	mon Mobile 80 foot Tower Hydraulic 80ft ex	tended	i.
	12' 6" closed. Mounted on 4-wheel drive if	Bedfor	d
	Truck, self levelling, raised and lowered	in 1	0
	12 b" closed. Mounted on 4-wheel drive t Truck, self levelling, raised and lowered minutes. Used for servicing dish aerials. Racal RA-17 PReceivers (new). Collins KWT 6 Transmitter Receivers SSB 8 K 2407 Electronic Voltmeters. Winston "6" Band Spectrum Analysers. Advance Transistor Testers TT-15	P.U.F	₹.
Ξ	Colline VMT 6 Transmitter Baseines CCD	E/50.0	0
Σ	8 & K 2407 Flectronic Voltmeters	P.U.H	î.
2	Winston "5" Rand Spectrum Analysers	PUR	ĭ
2	Airmec 352 Sweep Generators D	£130.0	ö
À.	Advance Transistor Testers TT-15	£35.0	ŏ
*	Marconi TF 329 Magnification Meters	£140.0	0
T	Marconi IF 801/D/1 AM Signal Generators	E160.0	0
T	Marconi TF 801/D/1 AM Signal Generators: Ferranti 7.5KVa Auto Voltage Regulators Manson TFM-101 Multipliers	150.0	Ü
Ž.	Servemov 2lov Auto regulators	£190.00	0
Ž.	125ft Lattice masts 24" sides	PILE	
2	30ft, Lattice Masts, 15" sides	£115.00	Ö
È	10ft Light Lattice Sections, 6" sides	£18.00	0
k_	EMI 1/2" Audio Tape 3600ft 101/2" nab. New.	£4.50	0
).F	I.I. Model RC-1 Professional Tape Recorder-	Repro	-
	Manson TFM-101 Multipliers	eds	
	All reck mounting & Transisteries Monito	rScop	9
L	SEA/2R C R T a	250.00	
	Bacal 3 & 6 KCS S S R filters	£14.00	1
È	AVO CT 471A Electronic Multimeters	£60.00	í
÷	Stonorette L Tape Recorders	£29.00)
F	Uniselectors, 10 Bank 25-way	£3.50)
+	Multi-purpose Trolleys with Jacks 19 x 17	£16.00)
7	Advance 3KVA CV Transformers£	120.00)
7	SE4/2B C.R.T.s. Racal 3 & 6 KCS S.S.B. filters. AVO CT 471A Electronic Multimeters. Stonorette L. Tape Recorders. Uniselectors. 10 Bank 25-way. Multi-purpose Trolleys with Jacks 19 x 17. Advance 3KVA CV Transformers. Metal V.D.U. Tables 30" x 36" x 30".	£24.00)

We have a quantity of Technical Manuals and Periodicals of Electronic Equipment, not photostats. 1940 to 1960. British and American. No lists. Enquiries invited.

*	Data Efficiency Respoolers 240v	£28
	Belling Lee 100 Amp Interference Filters	
	Oscilloscope Trolleys from	
*	Racal MA1978 pre-Selectors	£65
*	Rack Mounting Operator Tables	£10
*	75ft. Aluminium Lattice Masts, 20" sides	£400
*	Racal MA-175 L.S.B. Modulators (new)	£45
*	Tally 5/8 Track Tape Readers track spooling	q £65
*	Racal RA-63 SSB Adaptors, new	£70
*	Racal RA 298 I.S.B. Transistorised Adaptor	s (nev
		£120

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on

PLEASE ADD CARRIAGE AND V.A.T. P. HARRIS ORGANFORD, DORSET BH16 6BR (0202) 765051

(8981)

ARTICLES FOR SALE

TELETEXT, TV SPARES & TEST EQUIPMENT. TELETEXT. Latest MK2 external unit kit incl. Mullard Decoder 6101VML and infra-red remote control £258, p/p £2,50 (further details on request). Also MK1 external unit kit incl. Texas XM11 decoder, special offer price £168, p/p £2,50. Both kits incl. UHF modulator, and plug into TV set aerlal socket. SPECIAL OFFER TEXAS XM11 Decoder, new and tested, limited quantity at ½ price, £65, p/p £1.40. Stab. power supply (5v) for Teletext decoders, £5.80, p/p £1. Thorn design XM11 interface unit, £1.80, p/p 80p. NEW SAW FILTER IF AMP PUS TUNER (complete & tested for sound & vision) £78.50 and \$20.000 MB. SAW FILTER IF AMP PLUS TUNER (complete & tested for sound & vision), £28.50, p/p £1. COLOUR BAR & CROSS HATCH GENERATOR KIT (MK4) PAL, UHF aerial input type, 8 vertical colour bars, R-Y, B-Y, grey scale, etc. P/B controls £35. Batt holders £1.50 or stab mains power supply kit £4.80, Deluxe case £5.20 or alum. case £2.90, p/p £1.40. Built & tested in De-luxe case (battery) £58, p/p £1.50. CROSS HATCH KIT UHF aerial input type also gives peak white & case (battery) £58, p/p £1.50.
CROSS HATCH KIT UHF aerial input type also gives peak white & black levels, batt. op. £11, p/p 45p.
Add-on GREY SCALE KIT £2.90, p/p 35p. De-luxe case £5.20. UHF SIGNAL STRENGTH METER KIT £17.50. Alum. case £1.80. De-luxe case £5.20, p/p £1.40. CRT TEST & REACTIVATOR KIT for colour & mono £22.80, p/p £1.70. THORN 9000 Touch Tune Remote control receiver unit plus transmitter handset £16, p/p £1.40. THORN 9000 Fascia incl. channel select. indicator, set controls, speaker, £5.80, p/p £1.60. TV SOUND IF TRANSTD. Tested, £6.80, p/p £5p. BUSH SURPLUS IF PANELS. A816 £1.80, TV312 (single I.C.) £5, Z718/BC6100 £5, A823 (Exp) £2.80, p/p 85p. BUSH Z718/BC6100 Line Time Base Panel 2904, incl. LOPT, EHT stick, Focus, etc., 18in or 22in, £15. p/p £1.60. BUSH 161 series TB panel £4.50, p/p £1.20. DECCA colour TV Thyristor Power supply £3.80, p/p £1.40. GEC 2010 series TB panel £4.50, p/p £1.20. PHILIPS. G6 S/S conv. panel £2.50, p/p £1.20. G8 Decoder panels for spares £1.80, p/p £1.20. G9 Signal panels for panel 24, 50, p/p 51.20. PHILIPS.
G6 S/S conv. panel £2.50, p/p £1.20.
G8 Decoder panels for spares £1.80,
p/p £1.20. G9 Signal panels for
small spares £3.80, p/p £1.20.
THORN 3500 Line TB panel £5, p/p
£1. 3000 ex-rental panels IF, VIDEO,
DECODER, £5, p/p £1.20. 8000/8500
TB salv/spares £4.80, p/p £1. 9000
Line TB (incl. LOPT) salv/spares
£7.50, p/p £1.60. COLOUR SCAN
COILS (Mullard or Plessey) £6, p/p
£1.80. Yoke £2.50, p/p £1. Blue Lat
75p, p/p 35p. Mono Scan Coils
(Thorn, Philips, Pye) £2.80, p/p £1.
VARICAP UHF TUNERS. Mullard
U321 £7.80, ELC1043/05 £5.50. G.I.
£3.50. Salv. (asstd) £1.50, p/p 45p.
Varicap UHF/VHF ELC2000S £8.50,
Bush (dual) £7.50, p/p 70p. TOUCH
TUNE CONTROL units, Bush (6
pos) £4.50, p/p 80p. VARICAP CONTROL UNITS 3 pos. £1.20, 4 pos.
£1.50, 5 pos. £1.80, 6 pos. £1.80, 6
pos. special offer £1, p/p 45p. UHF
transtd. Tuners (rotary) incl. s/m
drive £2.50, 4 pos. P/B £2.50, 6 pos.
P/B £4.20, p/p £1.20. (Special types
available, details on request).
DL50 Delay Line £2.50, p/p 50p.
Large selection of LOPTS, Triplers,
Mains Droppers, and other spares
for popular makes of colour &
monor receivers. PLEASE ADD 15%
VAT TO ALL PRICES. — MANOR
SUPPLIES, 172 WEST END LANE,
WEST HAMPSTEAD, LONDON,
N.W.6. SHOP PREMISES. Tel. 01794 8751. Easily accessible W.
Hampstead Jubilee Tube & Brit. N.W.6. SHOP PREMISES. Tel. 01794 8751. Easily accessible W. Hampstead Jubilee Tube & Brit. Rall N. London (Richmond-Broad St.) and St. Pancras-Bedford. Buses 28, 159, 2, 13. Callers welcome. Thousands of additional items not normally advertised available at shop premises. Open daily all week incl. Saturday (Thursday half day). MAIL ORDER: 64 GOLDERS MANOR DRIVE, LONDON NW11 9HT. PLEASE ADD 15% VAT all prices.

OSCILLOSCOPE H-P175A, delayed timebase, £250, Gould OS1000A £220. Telequipment D43 £50, S51 £60. S52 and D52 £70. All good working order, with manuals. Consider offers. 073088317 (Hants).

THE SCIENTIFIC WIRE COMPANY

ENAMELLED COPPER WIRE 1lb. 8oz. 4oz. 2.76 1.50 .80 3.20 1.80 .90 3.40 2.00 1.10 4.75 2.60 2.00 20z. .60 .70 .80 1.42 8 37 5 32 3 19 48 to 49 15.96 9.58 6.38 3.69 SILVER PLATED COPPER WIRE

14 to 30 6.50 3.75 2.20 1.40 14 to 30 3.38 2.36 1.34 .90
Prices include P&P. VAT and Wire Data
SAE for list. Dealer energial. TINNED COPPER WIRE

SAE for list. Dealer enquiries welcome. Reg Office: 22 Coningsby Gardens.

INVERTERS

High quality DC-AC. Also "no break" (2ms) static switch, 19" rack. Auto Charger.



Interport Mains-Store Ltd. POB 51, London W11 3BZ Tel: 01-727 7042 or 0225 310916

VIDEO CONVERSIONS

5-hour dual speed conversion to Philips N1700 VCR now available. Excellent picture and sound quality in kit versio £65; fitted £83.

1500-01-02 LP conversion too! Video in-out modifications

Evans Video Services Video Engineering Specialists Tel: 061-439 8696

PRINTED CIRCUITS. Make your own simply, cheaply and quickly! Golden Fotolak Light Sensitive Lac-Golden Fotolak Light Sensitive Lacquer — now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibre-glass Board approx. Imm thick £1.75 sq. ft. Post/Packing 60. — White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall. (714

EQUIPMENT WANTED

TO ALL MANUFACTURERS AND WHOLESALERS IN THE ELECTRONIC RADIO AND TV FIELD

BROADFIELDS & MAYCO DISPOSALS

will pay you top prices for any large stocks of

21 LODGE LANE NORTH FINCHLEY, LONDON N12 8JG Telephone Nos. 01-445 0749/445 2713 After office hours 958 7624

CAPACITY AVAILABLE

PRINTED CIRCUIT BOARDS. Conventional double and single sided PS boards. Fast prototype and production runs. Contact John Richards, Phototechnique, 11 Old Witney Road, Eynsham, Oxford. Telephone Oxford (STD - 0865) 880645.

ayed 000A speciality. PCB assemblies our speciality. Programmable auto-matic test equipment used to service your PCBs, fast efficient service. For quotation telephone Campbell & Campbell & Campbell & Shrewsbury (0743) 65748. (993

CAPACITY AVAILABLE

PCB ASSEMBLY CAPACITY AVAILABLE

Low or high volume, single or double sided, we specialise in flow line assembly of printed circuit boards.

Classified

Using the Zevatron flow soldering system and on line lead cutting, we are able to deliver high quality assemblies on time, and competitively priced. Test facilities available.

Find out how we can help you with your production. Phone or write. We will be pleased to call on you and discuss your

TW ELECTRONICS LTD.

120 NEWMARKET ROAD BURY ST. EDMUNDS, SUFFOLK TEL: 0284 3931

Sub-contract assemblers and wirers to the Electronics Industry

I.H.S. SYSTEMS

(9068)

Due to expansion of our manufacturing facilities we are able to under take assembly and testing of circuit boards or complete units in addition to contract development.

We can produce, test and calibrate to a high standard digital analogue and RF equipment in batches of tens to Telephone to arrange for one of our

engineers to call and discuss your requirements, or send full details for a prompt quotation

TEL. 01-253 4562 or reply to Box No. WW 8237

SMALL BATCH productions wiring assembly to sample or drawings. Specialist in printed circuits assembly. Rock Electronics, 42 Bishopsfield, Harlow, Essex 0279 33018.

ELECTRONIC DESIGN SERVICE.
Immediate capacity available for circuit design and development work, PC artwork, etc. Small batch and prototype production welcome.

— E.P.D.S. Ltd., 93b King Street, MAIDSTONE, Kent. 0622-677916.

(9667

PCB ARTWORK
with component and assembly Electrical Ltd,
Southwood Road, New Eltham SE9.

PRINTED CIRCUIT BOARDS. Quick deliveries, competitive prices. Quotation on request, roller tinning, drilling, etc. Speciality small batches. Larger quantities available. Boardraven Ltd, Lancaster Road, Carnaby Industrial Estate, Bridlington, North Humberside, YO15 3QY. For the attention of Mr J. Harrison. Tel: (0262) 78788.

P.C.B. DESIGNS on circuit diagrams, etc. Competitive hourly rates, quotes free, cheaper hourly rates for solder resists and legends. — Helstead Designs Ltd. Helstead. Tel: 0787-477408. (869)

compare our charges, quality and turnround for printed board attworks, assembly, test and prototype manufacture. Please phone Sharon Halfhide on Chelmsford 357935 or write to H.C.R. Artwork Designs, I Bankside, off New Street, Chelmsford, Essex. (557

TAIWAN OFFER PCBs AND ELECTRONIC COMPONENTS. Documents printing. Plastic molds and metal dies manufacture. Quick delivery, small to large batch, easy purchasing. — Hu Mou Enterprises Co, Rm 3, 6th Fl, 306 Kuang Fu S. Rd., Taipei, Taiwan. Cable: HUMOU Taipei. Telex: 28564 HUMOU.

P.C.B.s WIRING assembly looms, coils, instruments, quality design prototype and production service in house or on site. — Batvale Ltd, Ely (0353) 778756. (982

P.C.B. MANUFACTURE AND ASSEMBLY

Wave Soldering and inspection. High quality PCBs from your artwork. Prototype design. Artwork from your circuit. Fast turnaround.

Endean Communications Services Ltd., Baileys Mill, The Cliff, Matlock, Derbys. (0629) 4929. Tlx. 378267 ECS G. (859)

SMALL BATCH PCB's produced from your artwork. Also DIALS, PANELS, LABELS. Camera work undertaken. FAST TURNAROUND.

— Details: Winston Promotions, 9 Hatton Place, London ECIN 8RV. Tel. 01-405 4127/0960. (9794

P.C.B. PROTOTYPE and small batch production. Design layout, assem-bly and testing. Fast, relible ser-vice. Wye Valley Electronics, 13 High St, Lydney, Glos. Tel: Dean (0594) 41267. (365)

sheet Metal work, fine or chassis, covers, boxes, prototypes. 1 off or batch work, fast turnround. 01-449 2695. M. Gear Ltd., 179A Victoria Road, New Barnet, Herts. (812 Road, New Barnet, Herts.

ELECTRONIC DESIGN SERVICES.
MICROPROCESSOR HARDWARE and
SOFTWARE design facilities have
now been added to our established
expertise and comprehensive test
facilities previously available to
you for ANALOGUE and COMMUNICATIONS designs. — For fastest
results please phone Mr. Anderson,
Andertronics Ltd, Ridgeway, Hog's
Back, Seale (nr. Farnham), Surrey.
02518-2639. (275)

SERVICES

CIRCOLEC

THE COMPLETE ELECTRONIC MANUFACTURING SERVICE

We also provide a test, repair and modification service to suit your individual requirement.

For competitive prices and fast turnaround contact:

CIRCOLEC, 1 Franciscan Road, Tooting, S.W.17 Telephone: 01-767 1233

DESIGN DEVELOPMENT MANU-FACTURE. We can offer a high quality, professional service, cover-ing all aspects from original design to small batch production. Digital/ Analogue prototypes welcome. For competitive pricing and quick de-livery phone Mr. Flower, Digitalis Ltd., 9 Milldown Road, Goring-on-Thames, Oxfordshire, Tel: 0491 873162. (936

P.C.B. WIRING undertaken at a competitive rate. Can pick up and deliver. Write to Mr D. Pitt, 29 Bridgewood Close, Penge, London SE20 or phone 01-778 1374. (979

TURN YOUR SURPLUS Capacitors, transistors, etc, into cash. Contact COLES-HARDING & Co., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. (9509

DESIGN AND DEVELOPMENT.
ANALOGUE, DIGITAL, RF AND
MICROWAVE CIRCUIT AND
SYSTEM DESIGN, Also POB design,
mechanical design and prototype/
small batch production. — Adenmore Limited, Unit 103 Liscombe,
Bracknell, Berks. Tel: Bracknell
52023. (656

Let us realise all or any part of your project from prototypes to production, from artwork design and component sourcing, through assembly and test to final quality assurance, packing and delivery.

DESIGN SERVICE. Electronic Dephone 38030. (909)

Bright Service. Electronic Design Development and Production Service available in Digital and Analogue Instruments, RF Transmitters and Receivers for control of any function at any range. Telemetry, Video Transmitters and Monitors, Motorised Pan and Tilt Heads etc. Suppliers to the Industry for 16 years. Phone or write Mr. Falkner, R.C.S. Electronics, 6 Wolfers of Sey Road, Ashford, Middlesex. Phone Ashford 53661. (8341)

PRINTED CIRCUIT BOARDS

Manufactured, any quantity, competitive prices, roller tinned, photographic and artwork services available.

MAYLAND PCB CO. LTD. 4 The Drive Maylandsea, Chelmsford, Essex Tel: 0621 741560

P.C.B. INDIGESTION? Investigate cost of using hybrid modules to ease assembly problems and im-prove reliability. Contact D. L. Bradly, 43 Montague Road, Slough. Phone 38030. (969) Phone 38030.

ARTICLES WANTED

SPOT CASH

paid for all forms of electronics equipment and components.

F.R.G. General Supplies 550 Kingston Road London SW20 8DR Tel: 01-404 5011

Telex: 24224. Quote Ref. 3165

WANTED — National calculator chips I-C's, numbers MM5749N or MM5736N. Any quantity. — Telephone: 0204-27749. (977

REMITTANCE VALUE....

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap, any quantity. Prompt service and cash. Member of A.R.R.A.

M & B RADIO Bishopsgate Street Leeds LS1 4BB 0532-35649

storage space is expensive, why store redundant and obsolete equipment? For fast and efficient clearance of all test gear, power supplies, PC boards, components, etc., regardless of condition or quantities. Call 01-771 9413. (8209

CLASSIFIED ADVERTISEMENTS

Use this Form for your Sales and Wants

OSC MILES A CALL	
	VERTISEMENT INDICATED ON FORM BELOW
To "Wireless World" Classified Advertisen	ment Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5A
 Rate £2 PER LINE. Average six words per line. Minimum £10 (prepayable). 	NAME
 Name and address to be included in charge if used in advertisement. 	ADDRESS
Box No. Allow two words plus £1.	
Cheques, etc., payable to "IPC Business Press Ltd." and cross "& Co."	
Press Ltd." and cross "& Co."	***************************************

PLEASE WRITE IN BLOCK LETTERS. CLASSIFICATION.....

NUMBER OF INSERTIONS.....

ENCLOSED

WIRELESS WORLD APRIL 1981

RHODE & SCHWARZ

Selective UHF V/Meter, Bands 4 & 5, USVF Selectomat Voltmeter USWV £450. UHF Sig. Gen. type SDR 0.3-1GHz £750. UHF Signal Generator SCH £175.
XUD Decade Synthesizer & Exciter POLYSKOPS SWOB Land II Modulator / Demodulator BN 17950 / 2.

MARCONI

UHF Sig. Gen. type SCR. 1-1.9GHz.

TF2360R TV Transmitter Sideband Analyser. TM6936R UHF Converter for above. TF1101 RC oscillators £65. 6551 SAUNDERS. 1400-1700MHz. FM. TF1066B/1. 10-470MHz. AM/FM.
TF1152A/1. Power meter. 25W. 500MHz TF1370A RC Oscillator £135.

TF791D Carrier Deviation Meter **U.H.F. SIGNAL GENERATORS**

TF1066B/2 400-555MHz. Deviation to

TF1060/2 450-1250MHz.

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipots." Brand new with mounting structions. Only £2.50 each.

PRINTED CIRCUIT MOTORS 'Printed Motors Ltd' type G16M4. 60V DC. 5.5 amps. Continuous torque 140oz. in. 2350 rpm. Diameter 7.5". Depth 2.5". Shaft diam. 1/2 & 34". Price from Printed Motors is now over £150 ea. Supplied in good, used condition, tested & guaranteed £25 each (postage £3).

AUDIO & RF SIGNAL GENERATORS

ADVANCE types H1, H1E, C2, SG62B, J4A. TAYLOR 62A (AM/FM). AVO HF134. AIRMEC 352 Sweep Generator. MARCONI TF1066B/1 (AM/FM 10-

LABORATORY OVENS. — Gallenkamp 3 cu. ft. £145. Also Morgan Grundy 1 cu. ft. £55.

20-WAY JACK SOCKET STRIPS. 3 pole type with two normally closed contacts £2.50 each (+25p pp). Type 316 three pole plugs for above -20p ea. (pp free).

P. F. RALFE ELECTRONICS

10 CHAPEL STREET, LONDON, NW1 TEL: 01-723 8753



RANK KALEE 1742 Wow & Flutter Meter. AIRMEC 314A Voltmeter, 300mV (FSD)-300V AIRMEC Wave Analysers types 853 & 248A. DERRITRON 1KW Power Amplifier with control equipment

for vibration testing, etc. HEWLETT-PACKARD 8551B/851B Spectrum Analyser. 10Mhz-40GHz

HEWLETT-PACKARD tuned amp & null detector. TF2600 Voltmeter 1mV-300V fsd. RADIOMETER Distortion Meter BKF6 £125.

LABGEAR T.V. PATTERN GENERATORS 625-line cross-hatch/dot/grey scale £45 (£1 post). RANK SIGNAL STRENGTH METERS UHF Channels 20-60. Battery operated £30 (£1 post).

TELEVISION TEST EQUIPMENT

TEXSCAN VS-60B Sweep Generator. 0-1000MHz £250. TEXSCAN DU-88 X-Y Display units £95. TELONIC 2003 Sweep Generator System £225. TELONIC 101 X-Y Display units £75. TELONIC 1204 Sweepers 0-500MHz £150. TELONIC 121 X-Y Display units £95.

OSCILLOSCOPE SALE

SOLARTRON CD1400. D/Beam 15MHz £150. HEWLETT-PACKARD 1707A. 75MHz £450. TELEQUIPMENT D75. TELEQUIPMENT DM64 Storage scope. DYNAMCO D7100. HEWLETT-PACKARD 122A SB. Audio. AIRMEC 279. 4 Beam Display Scope. TEKTRONIX 581A. 545A & B. 544, 661, 515A.

NOTICE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry our three months' guarantee. Calibration and certificates can be arranged at cost. Overseas enquiries welcome. PLEASE ADD 15% VAT TO ALL PRICES.

DC POWER SUPPLIES APT 10459/8, 12-14V @ 5 Amps £25 (£2 p.p.)

APT 10459/8, 24V @ 5 Amps £25 (£2 p.p.)

APT 10459/8, 24V @ 5 Amps £25 (£2 p.p.)

We can supply the above power supply at any fixed voltage between 5V and 36V at 5A £25.

Mullard Dual supplies. Brand new with handbook. Pos & Neg 12V at 1A and 0.4A respectively. Dimensions 9x4x5ins. £10 + (£1 p.p.)

★FARNELL Current limited. Dimensions 7x5x4ins.

Following types available: 13-17 Volts @ 2A £15.

27-32 Volts @ 1A 5V £15. 5V @ 3A £15. (pp £1.50).

SPECIAL PURCHASE LAMBDA POWER SUPPLIES

Excellent LXS Series DC power units at less than a tenth of new price. The snag? — they're all 110V AC Input. Prices as follows: 5V at 24A. LXS D5 0V R. £25. (List £350). 15V at 12A, LXS D15 R, £20, (£339), 5V at 14A, LXS CC 5 0V, £20, (£258), 24V at 3.1A, LCS C 24, £15, (£223). Carriage each £2.50 extra

MODULATION METERS

AIRMEC 210 3-300MHz. AM/FM. £125 RADIOMETER AFM/1 3.5-320MHz. AM/FM. £145 RACAL 409 3-600MHz. AM/FM.

ROTRON INSTRUMENT

COOLING FANS Supplied in excellent condition, fully

tested: 115V, 4.5 × 4.5 × 1.5" **£4.50.** 230V £5. 115V, 3 × 3 × 1.5" £4 + postage ea. 35p.

CT212 RF Signal Generators. 85KHz-32MHz

BELL & HOWELL MICROFICHE VIEWERS

Type SR5. Screen size 9 × 5" New condition £75.

DIGITAL MULTI-METERS

DE FOREST ELECTRONICS TYPE MM200. DC V 0-1KV. AC V 0-700. DC 1.0-1A. AC 1.0-1A: Each in 4 ranges. Resistance 0-19.99 Mohms 5 ranges. LED Display 1999.
BRAND NEW. SPECIAL REDUCED PRICE OF

£39, INCLUDING VAT & P.P.

(ELECTRONICS) LTD. 9 & 10 CHAPEL ST., LONDON, NW1 01-723 7851 01-262 5125 ADJACENT TO EDGWARE ROAD MET. LINE STATION

PLEASE ADD 15% TO ALL ORDERS INC. CARR. CURRENT RANGE OF NEW L.T. TRANSFORMERS
OPEN TYPE TAG CONNECTIONS
ALL PRIMARIES 220-240v

ype	Secraps	Amps	Price	Carr	
1	24-30-40-48-60v	12	£36.50	£2.00	
2	24-30-40-48-60v	10	£31.50	£2.00	
3	24-30-40-48-60v	8	£27.50	£1.75	
4	24-30-40-48-60v	5	£16.75	£1.75	
5	24-30-40-48-60v	3	£11.50	£1.25	
6	24-30-40-48-60v	2	£7.50	£1.25	
	6-8-10-12	-16-18-20-2	24-36-40-48-60		
	CAN BE OBTA	INFO FROM	THE ABOVE RA	NGE	
	,, 22 021/				

7	19-25-33-40-50v	10	£27.50	£2.00
8	19-25-33-40-50v	6	£19.50	£1.75
9	19-25-33-40-50v	3	£9.25	£1.25
10	19-25-33-40-50v	2	£7.75	£1.25
	5-7-8-10-1	3-15-1	7-20-25-30-40-50v	
	OR 25-0-	25 v OF	20-0-20v CAN BE	
	OBTAINED	FROM	THE ABOVE RANGE	

12-15-20-25-30v 10 £18.50 12-15-20-25-30v 5 £10.50 12-15-20-25-30v 2 £6.25 3-4-5-6-9-10-12-15-18-20-24-30v OR 12-0-12v OR 15-0-15v CAN BE OBTAINED FROM THE ABOVE RANGE

12v 60A, 24v 30A £39.50 12v 30A, 24v 15A £19.50 12v 20A, 24v 10A £15.25 12v 10A, 24v 5A £8.75 12v 4A, 24v 2A £4.25

HEAVY DUTY OP TRANSFORMERS

Type OT28EL 100 watts, 3.75Ω, 7.5Ω, 15Ω, 1.75K CT, 4 EL34
2x25 m/a dc max. £15.50, P&P £1.25. Type OT29EL 50 watts,
3.75Ω, 15Ω, 3.5K CT, rated 2x125 m/a dc max £8.95, P&P £1.

AUTO STEPDOWN TRANSFORMERS
FOR AMERICAN EQUIPMENT
240/110 Volts. 80-2250 watts. Regular stock line. Types 801500 watts are fully shrouded. Fitted with American two or
three pin socket outlets and 3 core 240V mains lead. Types
1750 and 2250 watts are steel cased with two American
socket outlets. Neon indicator, three core mains lead and
carrying handle. Send SAE for price list and further details.
American sockets, plugs, adaptors also available.

GARDNERS UNIVERSAL LT TRANSFORMERS

Open frame top panel connections. PRI 120-240v secs 1v twice, 3v twice, 94 twice, separate windings, all at 6.4 amps. Conservatively rated. The following voltages can be obtained 1-13v, in steps of one volt twice and 1-0-1v = 13-0-13v in one volt steps, and 1-13v 12.84 £9.75 PRIP CT

SPECIAL OFFER OF HIGH GRADE EX-COMPUTER AUTO TRANSFORMERS Conservatively rated by famous makers, perfect condition, fraction of list price Open frame construction top panel connections. 4000 watts tapped 0-105-115-125-138-200, 215-230-240-260V £45, Carr. £4, 3000 watts £39.50, Carr. £4, 500 watt tapped 0-90-115-125-200-210-230-240-250 Volts. Conservatively rated 500 watts £8.75. P&P£2.

P&P £2.

LATEST PURCHASE. COMPUTER GRADE LT TRANSFORMERS. Conservatively rated. All Primaries 220-240V. No. 1 Secs. 27V 10A, 9V 3A, 15V/2A × 2. Separate windings. £8.50. P&P £2.

No. 2 sec. tapped 26-31-36V, 11.2A £12, P&P £2.

No. 3 sec. 36V 6A £6.50, P&P £1.50.

No. 4 sec. 43V 3A £4.75, P&P £1.50.

No. 5 sec. 24V 2A £2.75, P&P £1.25.

No. 6 sec. 27.5-0-27.5V 1.2A and 7-0-7V 0.75A £3.50, P&P £1.25.

No. 712.6V 6A C Core £5.50, P&P £1.25.

No. 813V 3A and 15V 1A £3.50, P&P £1.25.

No. 918V 2A £2.50, P&P £1.

No. 10 sec. 29-28-27-0-27-28-29V 350 M/A "C" Core £3, P&P £1.

No. 11 sec. 62-28-27-0-27-28-29V 350 M/A "C" Core £3, P&P £1.

No. 11 sec. 61-0-7-0-7-10V 0.6A and 29-21-0-21-28V 0.37A £3, P&P £1.

HEAVY DUTY LT C CORE TRANSFORMERS
PRI 110-220-240V sec. 12V 40A £22.50.
Carr. £4. PRI 110-220-240V secs 14V 3V
11/2 IV. Separate windings 40A each, 14-51-515-21-71-518-18/12-19-19/2V at 40A £25.
Carr. £4. PRI 220-240V sec. 140V CT (70-070V) 10A size 7 x 7 x 7 ins. top panel connections £29.50. Carr. £5.

HEAVY DUTY ISOLATION TRANSFORMERS 240-240V ex-computer equipment. Large selection available 10-15 amps. Fraction of maker price. Telephone for further details.

HEAVY DUTY MULTITAPPED TRANSFORMERS

TRANSFORMERS
Ex-computer equipment. Top panel connections, PRI 220-240V, secs. 36V 21A, 19.5V 23A, 47.5V 5A, 31.75V 9A, 19.5V 13A, 47.5V 5A, 36V 4A, 11.5V 12A, 36V 1A seven times. All separate windings, £35 carr.

HEAVY DUTY C CORE LT
TRANSFORMERS
PRI 220-240V sec. 18V 27A, 40V 10A, 40V 4A,
25V 4A, 52V 1A. All separate windings. £27.50.

PARMEKO CASED TRANSFORMERS
PRI 240V sec. 50V CTE 250 watts conservatively rated. Fitted mains on/off switch £10.
Carr. £3.
PRI 240V sec. 25V 60VA, fitted output sockets, PHI 240V sec. 25V 60VA, fitted output sockets, mains on/off switch and fuse, 26.50, P&P £2. PRI 240V sec. 12V 50VA, fitted input and output sockets. On/off switch and fuse, £7.50, P&P £2. Above transformers are designed for low voltage lighting. Supplied brand new at a fraction of maker's price.

HT TRÂNSFORMERS Fraction of maker's price. All primaries 230240V, Parmeko potted type 500-0-500V 120 M/A 6.3V 5A, 6.3V 3A, 5V 2A, £10.95. Carr. MFD

12.50, 400-300-0-300-400V 250 M/A, 6.6V 8A, 6.6V 0.25 0.25 0.400 0.25 0.400 0.25 0.400 0.25 0.400 0.25 0.400 0.400 0.400 0.400 0.400

265V 60 M/A, 6.3V 6A, 6.3V 1A, 5.V 2A £4.75, P&P 350-0-350V 80 M/A, 6.3V 3A, 5V 2A £4.75, P&P 61.50.
250V 100 M/A 6.3V 4.5A, 15V 1.2A £4, P&P 7.5
150

250V 100 M/A 6.3V 4.5A, 13V 1.2A 29, 160 170V 40 M/A, 6.3V 3.3A £3, P&P £1.25. C Core Type 370-390-410V 6 M/A £2, P&P 75p 250-0-250V 50 M/A 6.3V 1.5A £3.50, P&P £1.

LT CHOICES Potted types 100 M/H 2A £4.50, P&P £2. 130
M/H 1.15A £2.50, P&P £1.50. Open types 4.2
M/H 1.15A £2.50, P&P £1.50. Open types 4.2
M/H 1.0A £3.55, P&P £1.75. 2+2 M/H 12A
£4.50, P&P £2.50 M/H 4.4A £4.50, P&P £2.
Other types up to 40 amps available. Let us know your requirements.

DC WKG BLOCK CAPACITORS
10 MFD 600V DC WKG £2, P&P 35D, 2 MFD 600V DC WKG £0, P&P 35D, 2 MFD 600V DC WKG 50D, 1 MFD
Please add 20p per cap postage.

PARMERO HT CHOKES
Potted types 15H 250 M/A £4.50, P&P £2. 10H
180 M/A £3.75, P&P £2. 10H 120 M/A £3, P&P
1.50. 50H 50 M/A £1.50, P&P £1. 15H 75 M/A
£1.50, P&P £1. 50H 25 M/A £1.50, P&P £1.
Swinging type, 5H 40 M/A 44 250 M/A £3.75,
P&P £1.50. C-Core type 20H 180 M/A £3.75,
P&P £2. Open types 25H 60 M/A £2, P&P £1.
25H 25 M/A £1.50. 180H 24 M/A £4, P&P £2.

We are open all day Saturday. Hundreds of bargains for callers. Stockist of Switches, Relays, Caps, Resistors, etc. Please remember to add 15% VAT to all Mail Orders.

AEI 20 AMP CONTACTORS

Type	Coil	Contacts	Price
	voltage		
0652	415VAC	3M 18	£1.5
0655	415VAC	4M	£1.50
0648	110VAC	4M 48	£1.50
0650	110VAC	6M 28	£1,5
0653	110VAC	4M	£1.29
0654	110VAC	2M 28	£1.2
0651	110VAC	3M 18	£1.2
0649	42VAC	6M 28	£1.5
0647	42VAC	4M 48	£1.50

P&P 25p kg

HEAVY DUTY HT TRANSFORMERS
PRI 120-240V sec. tapped 150-168V. Conservatively rated at 3 amps, top panel connections,
£4.95, P&P £2.
C Core PRI 220-240V, sec. 250-0-250V £7.50,
P&P £2. 60 M/A 2.8-0-2.8V 28A, 5V 2A, 6.3V
3A, 24V 3A £7.50, P&P £2.

PARMEKO LT SAFETY TRANSFORMERS
Totally enclosed, fitted with mains on/off switch, spring type output terminals, mains 240V mains lead. Output 6 or 8V 8A. Ideal bench transformer. Brand new. Fraction of maker's price. £5.50. P&P £1.50. PARMEKO LT SAFETY TRANSFORMERS otally enclosed, fitted with mains on/of

AC WKG BLOCK CAPACITORS BY FAMOUS MANUFACTURERS

440 370 440 700 440 250 360 330 P&P up to 2.5 MFD 25p 2.7-15 MFD 50p

SPECIAL OFFER 12V DC CAR
ANTENNAS
Five sections, 1 metre fully extended.
Complete with dashboard control
switch, leads and mounting brackets.
These serials all need slight attention.
But motors are runners, £3.95, inc.

PARMEKO OLITPLIT TRANSFORMEDS PARMERO OUTPUT TRANSFORMERS
10 watts, PPI 80000 ct. Sec. 4.8-16Ω for 2 EL8
velves. Atlantic potted series £4.95. P&F
£1.50. Farnell multi-tapped Op Transformers,
type MR1/37 watts max. DC60 M/A 2/3Ω 7.5Ω
15Ω. Data sheet supplied £2.25, P&P 75p.

ARROW HEAVY DUTY SWITCHES 2 Pole make and 2 Pole break 250V AC 30 amp contacts, recessed, panel-mounting, £1.25, P&P 50p.

METWAY BAKELITE TERMINAL BLOCKS 2-way 30 amps packs of ten £4.50, P&P £1.50 inch 37-way cable socket ex-compute quipment £1.50. Post paid.

CRESALI RHEOSTATS

Type S150 4 inch dia. 5500 150 watts, new and boxed £3.50, P&F 75p. Berco 1 2in. dia. 15000 25 watt £1, P&P 50p, 5000 25 watt £1, P&P 50p.

HEAVY DUTY 240V DC
CONTACTORS
Single pole make 100 amp contact £2.50, P&P
£1. Two pole make 10 amp contacts and 2
pole make 5-amp contact £1.75, P&P 75p.

Standard open type relay single-hole fixing AC240V 3 CO 7-amps £1, 2 CO 7-amp 85p, AC 110V 3 CO 7 amps 85p, 48V DC 3 CO 85p, Plug-in type AC 12V 1 CO £1, P&P 25p per relay.

www.americanradiohistory.com

SWINDON, WILTS. SNZ 6J0

HEADLANDS TRADING ESTATE.




ANALYSERS TEKTRONIX 1L5 L.F. Spectrum Analyser Plug In. 50Hz-1MHz TEKTRONIX 1L10 Spectrum Analyser Plug In 1MHz-36MHz PARAMETRON 477 L.F. Spectrum Analyser 1MHz-50MHz	£700.00 £700.00 £800.00
BRIDGES GEN-RAD 1607A Transfer Function and Immittance Bridge, conwooden box MARCONI 868B Universal Bridge 1KHz-10KHz Source 1% MARCONI 1313 Universal Bridge 0.25% WAYNE KERR B.641 Auto Balance Bridge 0.1%	£300.00 £175.00 £350.00
COUNTERS HEWLETT-PACKARD 5245L + 5253B 8 Digit 500MHz MARCONI TF.2411 7 Digit DC-50MHz	£350.00 £85.00
DIGITAL MULTIMETERS KEITHLEY 130 3½ Digit D.M.M., NEW Case for above FLUKE 8100A 3½ Digit DC/AC Volts and Resistance	£7.00

B.641 Auto Balance Bridge 0.1%	£275.00
KARD 5245L + 5253B 8 Digit 500MHz 411 7 Digit DC-50MHz	£350.00 £85.00
TIMETERS 3½ Digit D.M.M., NEW ½ Digit DC/AC Volts and Resistance	£7.00
MARTIN ASSOCIATES	

RECEIVE	
METERS HEWLETT-PACKARD 3400A RMS Voltmeter 10Hz-10MHz	£295 00
DYMAR 711 Millivoltmeter	£65.00
MARCONI TF.791D Carrier Deviation Meter 4MHz-1024MHz	
MARCONI TF.791D Carrier Deviation Meter 4MHz-1024MHz.	C100.00
MARCONI TF.1020A R.F. Power Meter 250 MHz 100W 50 0hms	£100.00
MARCONI TF.2600 Sensitive Valve Voltmeter 10Hz-5MHz	£130.00
MARCONI TF.1245/46/47 "Q" Meter and 2 Oscillators 1KHz-300	UMHZ
	£750.00
HEWI FTT-PACK ARI) 130 L-C Meter 10H-3000H and 1DF-300P	Г
	£125.00
SIEMENS 3U84alb Thermal Milliwattmeter 1-500mW 12.5GHz	£120.00
DIEMETICO OCCIDIO TROCAMO INSTITUTO DE LA CONTRACTOR DE L	
OSCILLOSCOPES	
COSSOR CDU.150 D/Beam DC-35MHz 5mV/cm	£300.00
HEWLETT-PACKARD 141A D/Beam DC-20MH2 Storage	£350.00
MEWLETT-FACKARD 141A D/Deant DC-2014112 Storage	£230.00
NEW Oscilloscope Kikusui 5520 DC-20MHz Sens. 1mV/10MHz	6400.00
TEKTRONIX 432 Oscilloscope DC-25MHz Sens 10mV/div	. 2400.00
TELEQUIPMENT D.83 D/Beam DC-50MHz	1800.00
TEKTRONIX 603 Storage Monitor	£600.00
ν.	
PROBES	14
TEKTRONIX P.6105 X10 DC-100MHz	£40.00
TEKTRONIX P.6056 X10 DC-3.5GHz	
TEKTRONIX P.6057 X100 DC-1.4GHz	
TEKTRONIX P.6075A X10 200MHz	
TEKTRONIX P.6430 Temperature Probe —85°C to +150°C	£75.00
TEKTRONIX P.0450 Temperature Probe —65 C to 1 100 C	210.00
CYCNIAL COLIDOFO	
SIGNAL SOURCES	Inc
ADVANCE PG.52B Pulse Generator c/w P6:P1A:P2A: P3A Plug	CEED 00
100 things	. £330.00
AIRMEC 304 Power Oscillator 50KHz-100MHz 10V into 50 Ohn	C100.00
AMARIE OF THE CONTROL	. 2100.00
AIRMEC 365A AM/FM Generator 1-320MHz 50 and 75 Imp	£223.00
HEWLETT-PACKARD 606B H.F. Oscillator 50KHz-65MHz 50	Jnms
	. £500.00
HEWLETT PACKARD 8443A Tracking Generator Touring	-IIUMITZ
500hms	£900.00
MARCONI TF.801D/8S AM Signal Generator 10MHz-485MHz	£300.00
MARCONI TE 1101 R-C Oscillator 20Hz-200KHz	. £95.00
MARCONI TF.6700A Sweep Oscillator 8-12GHz	£1200.00
DECCA EP685AGB Pal Colour Bar Generator	£250.00
LABGEAR CM.6052/CB Pal Colour Bar Generator	£110.004
LADGEAR CWI.0002/CD Fai Colour Dai Generator	

WW - 071 FOR FURTHER DETAILS

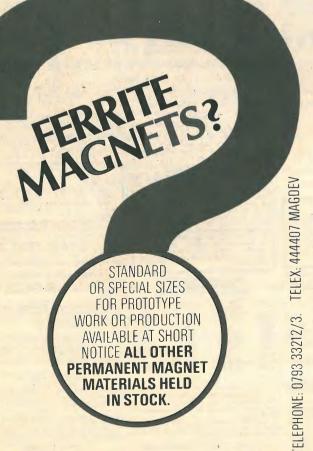

WORK OR PRODUCTION AVAILABLE AT SHORT NOTICE ALL OTHER PERMANENT MAGNET MATERIALS HELD IN STOCK.

MAGNET DEVELOPMENTS LIMITED

WW-079 FOR FURTHER DETAILS

FLOPPY DISK DRIVES New Low Prices! Unbelievable but True! Read On!

SIEMENS FDD - 100-8/FDD - 200-8

Fully Shugart Compatible Siemens 8" single and double sided disk drives are available now with unbeatable prices at single unit pricing.

Note these specifications:

TRACK 00 SENSING
ACTIVITY INDICATION
MECHANICAL END STOPS AT
TRACKS 00 AND 76
AUTO WRITE CURRENT
SWITCHING AT TRACK 43

★ WRITE PROJECT
CIRCUITRY

AUTO DISK EJECTION

FAIL SAFE INTERLOCK WHICH
PREVENTS THE COVER FROM
CLOSING ON A PARTLY
INSERTED DISKETTE

FD100-8 FD100-8
Capacity per disk unformatted
Bit Density inner track
Recording Method
Transfer Rate 400 K Bytes 3.2MBit

Settling Time Number of Recording

FD200-8 Same as above except Capacity per disk unfo Number of Recording SINGLE DENSITY

DOUBLE DENSITY

240V, 50HZ +24V @d 1.8 amps +5V @ 1.3 amps

800 KBytes 6 4MBIT

PRICING FDD-1008 FROM £249.95 EACH FDD-200-8 FROM £360.00 EACH

IRVINE BUSINESS SYSTEMS

WW - 088 FOR FURTHER DETAILS

The AIRAMCO Mikro 1000 -The Scottish Solution.

> The Mikro 1000 is a Scottish built micro-computer which combines State of Art technology with simplicity and durability to give a powerful small business system at a very competitive price.

> Driven by a 2.5 MHz or 4 MHz Z80 processing unit constructed around Industry Standard S100 Bus, the Mikro 1000 is designed to provide the ease of expansion necessary in a modern growing business or industry - memory is expandable from 32K to 256K, with up to 4 Megabytes of on-line disk storage.

The integral VDU has an 80 cols. x 24 lines screen, and incorporates a green phosphor CRT, while the 117 key keyboard can be used remotely from the main body of the machine, and may be programmed for user functions such as word processing commands.

As well as supporting all CP/M based languages, the Mikro 1000 has a full range of business software, including Sales, Purchase and Nominal Ledger, Inventory Control, and Payroll, as well as Word Processing (which is available at even lower cost as a separate system on the Mikro 1000 WP).

For further information on either Mikro 1000 system, please contact:



Unit A2, Longford Avenue, Kilwinning Ind. Est., Kilwinning, Ayrshire, KA22 8NP.

Tel: 0294 57755

Telex: 779808

WW-076 FOR FURTHER DETAILS

Who's Who and What's What in the Electrical Industry

Famous for its total coverage, detail and accuracy, the ELECTRICITY SUPPLY HANDBOOK usually sells out fast - so ensure your copy and post the coupon below, today!

 Over 2,000 names and locations of executive personnel in the Electricity Council, C.E.G.B., Area Boards and other organisations.

 Major authorities, government departments associated with the electrical industry.

 U.K. power stations, Area Board statistics, electricity tariffs, electrical associations.

• Pull out map of C.E.G.B. Regions, power stations and transmission lines.

Bound in maps of Area Boards.

PUBLISHED **MARCH 1981** Price £6.00 incl. postage

To: General Sales	Department,	Room 205	, Quadrant
House, The Qu	adrant, Sutte	on, Surrey,	SM2 5AS.

Please send me.....copy/ies of ELECTRICITY SUPPLY HANDBOOK 1981

Company registered in England No. 677128. Reg. Office: Quadrant Hous

PAGE

86 High Street, Bletchingley, Redhill, Surrey RH1 4PA. Tel: Godstone (0883) 843221

TELETYPE Model ASR 33 with 20 mA current loop or RS232 interface. 110 Baud, remote reader control (which may be disabled by insertion of a jumper), paper tape reader/punch & stand (when available) (rom £195).

POTTER Model LP-3000 High Speed (300 lpm) line printer
POTTER Model LP-3000 High Speed (300 ipm) line printer. E225 BCL Matrix printer. 120 cps with dual tractors and long platen (in excess of 300 col.), Unused
ODEC Model 4000 belt printer. 65 lpm. Parallel TTL interface. Manufactured 1980
ODEC Model 4000 ben printer. So Ipm. 1-251 pm.
10MEX Model 3404 disc drive. In higher a baseling with documentation and have the industry standard 200 tpi and 2200 bpi. These drives are complete with documentation and have the industry standard interface. IOMEC are no longer in business, nevertheless, electronic components are standard and we can interface. IOMEC are no longer in business, nevertheless, electronic components are standard and we can interface.
annual incomplete drives free of charge to blivers. Service is, in any case, appareilly available for lower
WANGO Model T 1222 disc drives, With one fixed and one top loading platter of 5 mByte capacity total.
WANGO Model 1 1222 disc drives, with one fixed and one top locating place 2500 rpm, industry standard interface £350
2500 rpm, industry standard interface
BURROUGHS disc drives, 2 x 2.5 mByte front loading Cartridge in Cartri
TREND Model HSR 350, 350 cps optical reader with TTL interface
PATA DYNAMICS Model 1114 high speed table punch. With parallel 112 interface. The recently serviced by DATA DYNAMICS. Price includes all documentation
Please note:
A VAT and carriage overs all items

★ VAT and carriage extra all items
★ Visitors welcome, but by appointment please
★ We are keen to bid competitively for all good used equipment

INDEX TO ADVERTISERS APRIL

Appointments Vacant Advertisements appear on pages 121-132

	PAGE		PAGE		INGL
					100
	77	Global Spec	30, 35	Northern Elec	103
Acoustical	04	GMT Elec	98	Northern Radio	120
Adcola	21	CD Industrial Flor I td			
Aero	125	Guide to Broadcasting Stations	106	OMB Electronics	34
Airamco	10 10	Guide to Broadcasting Stations		Orion	92, 120
Ambit International	18, 19				
Anglia Components	92		12	Pascal Electronics	. 12, 24, 118
AP Products	cover m	Hameg	102	PRRA I td	104
Aspen Electronics Ltd	22	Happy Memories	102	PM Components	18
Audio Electronics		Harris Electronics (London) Ltd	116	Powertran Electronics	93, 95
Avel Lindberg	102	Hart Flectronics	110	Pve IInicam	32, 33
Avo Inst	26	Horwin	111	Pype Hayes	108
11vo mot		Hanere Radio	114, 118		
		U: E: Veer Book		Radio Componzf Specialists	107
Bamber Electronics	115	Hilomaet	10	Ralfe, P. F	133
Rarnet Metal	92	House of Instruments	6	RCS Elec	120
Barrie Electronics Ltd	111	Tiouse of mistraments		Rediffusion Reditronics	112
Bayliss, A.D.	108	The state of the s		Rediffusion Rediffolies	118
BDS Microsystems Ltd	120	ILP Electronics Ltd	96, 97	Robot (UK)	
BDS Microsystems Ltd	cover iv	ILP Transformers Ltd	28		102
BIB Hi-Fi	00	ILP I ransformers Ltd	13	Safgan Electronics	100
Bull, J.		IMO	100	Sagin	108
- • 1		Integrex Ltd	24	Cameon	
	20 21	Interface Quartz	100	Courter E A	
Carston Electronics Ltd	20, 21	International Trade Fair		Science of Cambridge	
Chilton Flec		Iin-Design		Scopey Instruments td	
Chiltmead I td	119	ITA	103	Shure Electronics	
Clark Maets I td	10			Special Products Ltd	
Clef Products	98			Spender Audio	15
Colomor	120	Keithley Instruments	23	Strutt Electrical & Semel	98, 103, 105
Computer Appreciation	114, 136	Kalegy Acquetics		Surrey Electronics Ltd.	120
Court Search	28	Kirkham Amplifier	27	Surrey Electronics Ltd	
Crimson Elektrik	35	Kilkhani impinier			110
Crimson Elektrik				Technomatic	110
		Langrex	101	Tektronix (UK) Ltd.	63
Davies, A. R.	114	Levell Electronics	7	Teleconic Berkley	43
Digital	108	LJ Elec	105	Teleradio	70
Display Electronics	117	LJ Elec	16	Television	104
Display Electronics		Lowe Electronics		Teloman Products Ltd.	30
	102			Thurlby Electronics	116
Elec. M/Services	103	ar an in	134	Titan Transformers	22
Electricity Supply Hand Book		Magnet Design	11	THAIL THRISTOTHICLS	-
Electronic Brokers Ltd	,3,4,5,29,31	Maplin Electronic Supplies	24	Valradio Ltd.	24
Floatro Tech Comps I td		Marshall, A. (London) Ltd	124	valiatio Ltd	
Electrovalue		Martin Associates	134	Western-Whybrow Engineering	64
Elektor Publishers	17	Maile W/		West Hyde Developments Ltd	78
Everyday Electronics	92	Minetes T		West rivde Developments Ltd	114
Everyday Electronics		Manalith		West London Direct Supplies	01
T I S A T A	114	Mr. 11 J		Wilmslow Audio	
Faircrest Eng	201797 11 78	Mulainous Colders I to	Cover iv		1.4
Farnell Instruments	COVEL II, 20	Mura Electronics	26	Zaerix	14
Field Tech	29	Mula Electionics			

OVERSEAS ADVERTISEMENT

France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.

Hungary: Mrs Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget. Telephone: 225 008 – Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. — Servizio Estero, Via Mantegna 6, 20154 Milan. Telephone: 347051 — Telex: 37342 Kompass.

Japan: Mr. Inatsuki. Trade Media — IBPA (Japan), B.212. Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. ne: (03) 585 0581.

United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York. NY 10017 — Telephone: (212) 867-2080. Telex: 238327. Mr Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 — Telephone: (312) 62024

osu/4. Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA — Telephone (213) 821-8581 — Telex: 18-1059.

Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 4415 – Telephone: (216) 621 1919. Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 – Telephone (305) 532 7301. Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432. Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 – Telephone (713) 783 8673.

Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 — Telephone (416) 364 2269.

* Also subscription agents.

Printed in Great Britain by QB Ltd., Sheepen Place, Colchester, and Published by the Proprietors IPC ELECTRICAL-ELECTRONIC PRESS LTD., Quadrant House, The Quadrant, Sutton, Surrey SM25AS, telephone 01-661 3500. Wireless World can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co, CANADA: The Wm. Dawson Subscription Service Ltd, Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd: William Dawson & Sons (S.A.) Ltd. UNITED STATES: Eastern News Distribution Inc., 14th floor, 111 Eighth Avenue, New York, N.Y. 10011.

ADVENTURES ON THE IC'S



THE HOBBYIST For everyone who is keen on electronics

THE STUDENT A sound practical work programme for examination


A SPECIAL £6 OFF INTRODUCTORY OFFER FOR:-THE SERVICE ENGINEER To understand and keep up with modern progress

THE BUSINESS MAN Basic electronics to help understand the subject


ANYBODY CAN BUILD ELECTRONIC PROJECTS WITH EBBO BOARDS HERE'S HOW TO BUILD AN ELECTRONIC ORGAN.

Here's the Circuit Diagram 16 PROJECTS INCLUDE

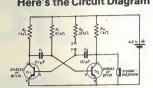PARKING LIGHT **BURGLAR ALARM** TWO TRANSISTOR RADIO CHIP RADIO COMPUTER COUNTER And many others



Here's how to build it on EBBO

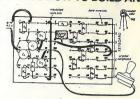

COMPONENTS INCLUDE

- 1 loudspeaker
- 1 variable capacitor midget potentiometer

Start with the resistors take resistor 1 (R1) and push it into hole numbers E23 and G5, take resistor 2 (R2) and push it into hole numbers A9 and A11 and do the same with all the other resistors. Then take transister 1 (TR1) and push it into hole number B8, C13 and D18, do the same with all the other components and you have a full working electronic organ. We even give you tunes to play.

What do you need



EBBO DISCRETE STARTER PACK Normal Price £6.67



ADVENTURES WITH ELECTRONICS
Normal Price £2.30

2 npn transistors (2N3053 or BFY51)

- 1 pnp transistor (ZTX500)
- field effect transistor (2N3819)
- 1 integrated circuit (ZN414)
- 1 photocell, e.g. ORP12
- 1 thermistor, e.g. TH3
- ... and many others

COMPLETE PACK OF COMPONENTS Normal Price £17.25

Total Price Normally £25 SPECIAL INTRO PRICE ONLY £19 inclusive of VAT and Post & Packing. Available from Watford Electronics, BI-PAK and all good component stockists.

DIP-DIP-DIP-DIP JUMPERS AP DIP JUMPERS ARE THE LOWEST PRICE IN THE UK



- **EX-STOCK DELIVERY**
- 5 STANDARD LENGTHS 6, 12, 18, 24, 36"
- WITH 14, 16, 24, 40 CONTACTS
- FULLY ASSEMBLED AND TESTED
- INTEGRAL MOULDED ON STRAIN RELIEF
- **LINE BY LINE PROBEABILITY**

SINGLE-ENDED			DOUBLE-ENDED all prices 1-9 off. Huge discounts for quantity					
	CONTACTS	24"	CONTACTS	6"	12"	18"	24"	36″
	14	£1.67	14	£2.11	£2.21	£2.31	£2.43	£2.63
	16	£1.89	16	£2.33	£2.45	£2.58	£2.66	£2.97
	24	£2.74	24	£3.45	£3.62	£3.78	£3.94	£4.30
	40	£4.38	40	£5.31	£5.61	£5.91	£6.22	£6.81

We can supply DIP, SOCKET, PCB, CARD-EDGE RS232, assemblies made-up, tested, ready for use, cheaper than you can buy the parts, ask for quote.

TEST-CLIP TEST-CLIP



Clip an AP TEST-CLIP over an IC and you immediately bring up all the leads from the crowded board into an easy working level.

22 NEW AP TEST-CLIPS TO PICK FROM

examples: TC 14 923695 £2.76 TC 16 923700 £2.91 TC 24 923714 £8.50

TC 40 923722 £12.88

POWERACE THE MOST EXPENSIVE BREADBOARD IN THE


WORLD



Three poweraces that give you th ultimate in breadboarding. Built in power supplies and a FREE logic probe is built into MODEL 102

POWERACE 101 923221 £61.30 POWERACE 102 923222 £95.80 POWERACE 103 · 923223

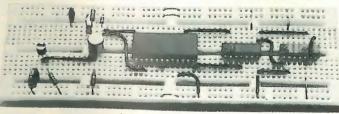SUPERSTRIP SS2 THE BIGGEST SELLING BREADBOARD IN THE WORLD



When you buy a SUPERSTRIP BREADBOARD you buy a breadboard to last you for ever, we give you a LIFETIME guarantee. SUPERSTRIP is the most used breadboard by hobbyists, professionals and educationalists because it gives you more for your money... With 840 contact points SUPERSTRIP accepts all DIP's and discrete components and with eight bus bars of 25 contact points each SUPERSTRIP will take up to nine 14-pin DIP's at any one time. You should only buy a breadboard once so buy the biggest seller with a lifetime guarantee SUPERSTRIP SS2 923252 PRICE INCL VAT £9.78

All prices shown are recommended retail incl. VAT In difficulty send direct, plus 50p P & P. Send S.A.E. for a free copy of colour catalogues detailing our complete range.

AP PRODUCTS, PO BOX 19, SAFFRON WALDEN, ESSEX, (0799) 22036



The biggest name in solder worldwide



Economy pack for general non-electrical use Replaces solid wire and stick solder. (B.S. 219 Grade L). Econopak 200g reel of 3mm dia. Size 16A. £4.14 per reel.







Toolbox Reels.

Multicore 5-core solder for general use. Suitable for electrical joints (B.S. 219 GradeG). 40/60 tin/lead. 1.6mm dia. Size 3. £3.91 per reel.

Multicore 5-core solder for radio, TV. and similar work. Reduces copper erosion. Suitable for service engineers and manufacturers using small quantities of solder. 1.2mm dia. Size 12. £3.91 per reel.



Multicore Wick. Multicore solder-wick for removing solder from

virtually any joint. 1.7mm dia. Size AB10. £1.38 per reel.

Products that help you make a better job of it.



Handy Disp	pensers	Perpacl
PC115	for printed circuits.	£1.15
SV130	for radio and T.V. repairs.	£1.61
AR140	for non-electrical applica-	
	tions, except aluminium	£1.38
SS160	for stainless steel and silver	
	jewellery.	£2.53
19A	for all electronic joints.	
	non-corrosive.	96p
AL150	for aluminium.	£1.93
BCA16	solder cream for stainless	
	steel, jewellery and house-	
	hold products (non-electrical).	£3.22
BCR10	solder cream for electronic	
	and electrical use.	£1.38
BCA14	all purpose solder cream,	
	non-electrical jointing and	
	repairing.	£1.38





Econopak.
Ersin Multicore 5-core solder. Contains non-corrosive flux for electrical applications.

1.2mm dia. 200g Econopak, Size 13A. £4.14 per reel.



Metal Soldering.
Arax Multicore 4-acid-core solder for metal fabrication (not aluminium) and repairs. 40/60 tin/lead. 1.6mm dia. Size 11. £3.91 per reel.



T.V. and Radio Soldering. Savbit Multicore for radio, T.V. and similar work. Reduces copper erosion. .2mm dia. Size 5. 90p per handy dispenser. Econopak. General purpose solder

suitable for all electrical joints. 40/60 alloy. 1.2mm dia. Size 6. 58p per handy

plastic dispenser.



Aluminium Soldering. Alu-Sol Multicore 4-core solder for soldering most types of aluminium. No extra flux needed. 1.6mm dia. Size 4. £6.90per reel.

Bib Hi-Fi Accessories Ltd., (Solder Division), Kelsey House, Wood Lane End, Hemel Hempstead, Hertfordshire HP24RQ Telephone: (0442) 61291.



Multicore soldering flux paste. Extra fast, non-corrosive, rosin-flux for electrical and general purpose

Rosin R.F.10. 35g net. 69p per pack.

Multicore soldering flux paste for soft metals (except aluminium) and stainless steel. Non-electrical. Arax A.F.14. 35g. 69p per pack.



Wire Stripper and cutter.

Wire stripper and cutter with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles. Ref: 9. £2.69 per pair.

All recommended retail prices shown are inclusive of VAT. If you have difficulty in obtaining any of these products send direct with 40p for postage and packing. For free colour brochure send S.A.E.