

wireless world

JULY 1981 60p


Australia A\$ 2.40
Canada C\$ 4.25
Denmark Dkr. 20.25
Germany Dm. 6.00
Greece Dra. 125.00
Holland Dfl. 5.75
Italy L. 2300
Norway Nkr. 21.00
Singapore M\$ 5.50
Spain Ptas. 180.00
U.S.A. \$3.75

**Upgraded micro
trainer**

Digital speech

**Long-distance
television**

**Low-loss
coaxial cable**

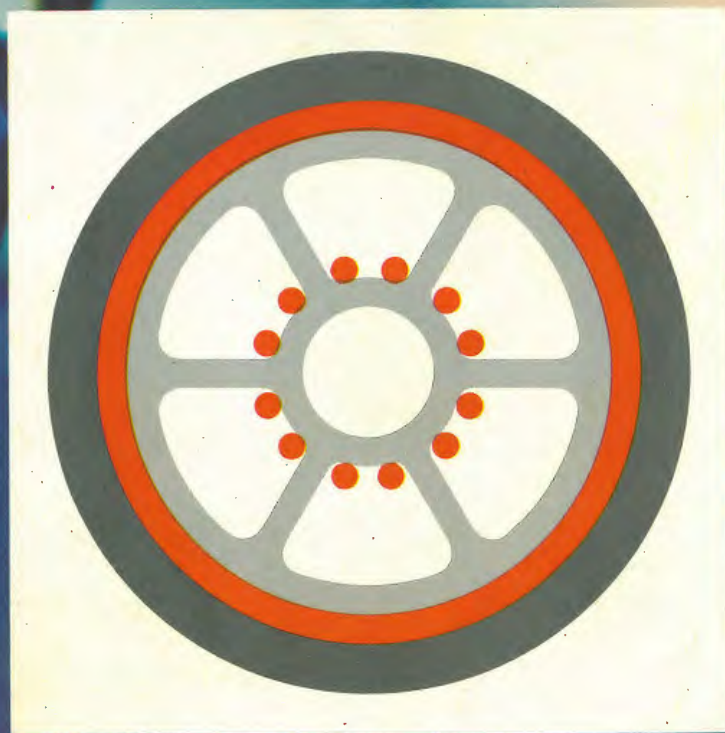

PROFESSIONAL TOOLCASES for Service Engineers

£43.70
inc. VAT

£39.90
inc. VAT



TL100 19" x 14" x 6"

Size TL99 17" x 12" x 6"

£13.75
inc. VAT



TLW4

The TL99 and TL100 are designed for the Professional Electronics, TV or Instrument Technician who needs to carry a large number of specialist tools. Constructed from hard wearing ABS with strong aluminium frames, twin handles and toggle locks. They offer a moulded tray in the base, a comprehensive 2 sided tool pallet that's reversible with space for up to 40 tools. — The TL100 will take quite a few more. There's space for documents and a heat sink for a hot soldering iron to prevent any damage being caused.

TLW4 Toolwallet measures 11" x 14" x 2½" when closed. Made from reinforced PVC with a heavy duty industrial zip. The TLW4 Toolwallet is a compact alternative when only tools are needed to be carried.

Mail Order

Please send

Enclosed my cheque **£** _____
(P&P £2.60 extra)

Name _____

Company _____

Address _____

Tools NOT included. British made.
Money back guarantee. Allow 7-21 days for delivery.

Teloman Products Ltd
Ermine House, Post St, Godmanchester, Cambs. PE18 8BA (0480) 65534

WIRELESS WORLD JULY 1981 VOL 87 NO 1546

wireless world

JULY 1981 60p


Australia AS 2.40
Canada C\$ 4.25
Denmark Dk 20.00
Germany Dm 6.00
Greece Dr 125.00
Holland Dfl 5.75
Italy L 2300
Norway Nkr 21.00
Singapore MS 5.50
Spain Pts 180.00
U.S.A. \$3.75

**Up-rated micro
trainer**

Digital speech

**Long-distance
television**

**Low-loss
coaxial cable**

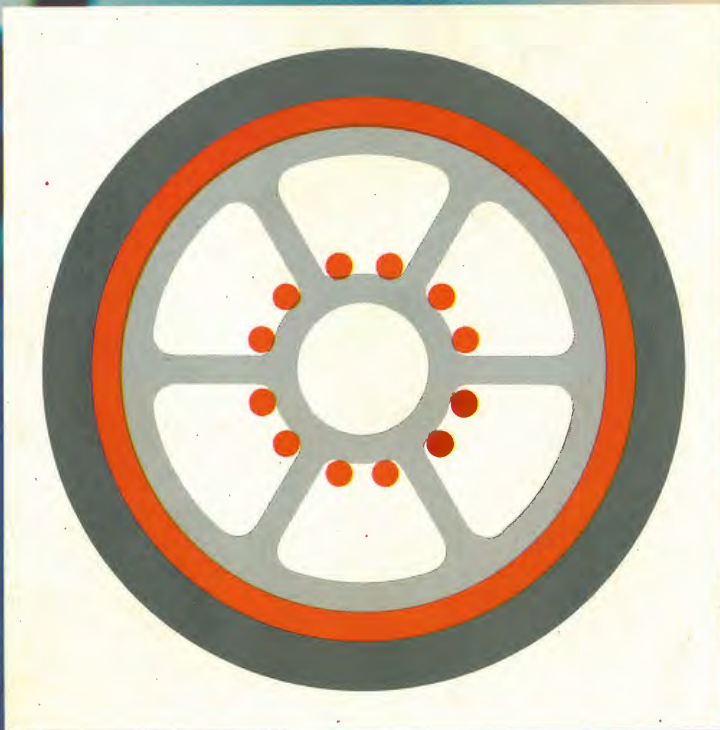



Autostore.

Low-cost voice-logging for people with more important things to do.

The problem: logging telephone and radio messages without spending a fortune on equipment or hiring an expensive technician to operate it.

The solution: the new Racal Recorders Autostore.

SIMPLICITY
With its automatic cassette-loading and fully automatic changeover from one deck to another, Autostore can—quite literally—be operated by whoever happens to be around.

And it provides over 24 hours of unattended continuous recording on eight channels.

VERSATILITY
Able to log radio and telephone messages simultaneously, Autostore can form part of a new system—or fit just as easily into an existing one.

And its uses vary from ambulance, fire, police and security applications to the recording of financial transactions, conferences, oil installation communications and taxi services.

Racal Recorders

Racal Recorders Limited, Hardley Industrial Estate, Hythe, Southampton, Hampshire SO4 6ZH, England.
Tel: (0703) 843265 Telex: 47600



RELIABILITY

Available in 4 or 8 channel versions, and with integral micro-processor controlled automatic Timesearch capability to enable rapid message retrieval, Autostore is engineered to the very highest standards by the company which pioneered air traffic control recording techniques.

FULL DETAILS

For full details of Autostore send off the coupon today.

I am interested in recording my communications accurately and reliably. Please:


- send me full details of Autostore
- arrange for a demonstration at my own premises

Name _____
 Position _____
 Company _____
 Address _____
 _____ Tel: _____

Racal Recorders Limited, Hardley Industrial Estate, Hythe, Southampton, Hampshire SO4 6ZH, England

ww

WW-001 FOR FURTHER DETAILS

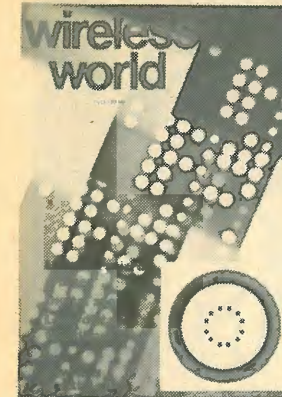

Front cover shows cross-section of the new type of coaxial cable described in this issue, superimposed on a photographic montage of punched tape symbolising the digital techniques in other articles. Photographer: Paul Brierley.

IN OUR NEXT ISSUE

Radio and the birth of the Universe. A review of the significance of the 3K cosmic microwave background in the Big Bang cosmological theory.

Electronics on the road. Broadly surveys electronic ignition, anti-lock brakes, cruise control, active suspension and other electronic systems; also social influences on design.

Correlator for angles. Measuring technique suitable for testing timing scatter in automobile ignition systems and other rotary mechanisms.

Current issue price 60p, back issues (if available) £1.00, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hop-ton Street, London SE1. Available on microfilm; please contact editor.

By post, currently issue 96p, back issues (if available) £1.50, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3500. Advertising 01-661 3129.

Telegrams/Telex: 892084 BISPRS G.

Subscription rates: 1 year £10.00 UK and \$33.80 outside UK.

Student rates: 1 year £5.00 UK and \$16.00 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3500.

Subscriptions: Oakfield House, Perrymount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Please notify a change of address.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd-class postage paid at New York.

© IPC Business Press Ltd, 1981 ISSN 0043 6062

wireless world

ELECTRONICS/TELEVISION/RADIO/AUDIO

JULY 1981 Vol 87 No 1546

29 Decline of the philosophical spirit

30 New development in h.f. coaxial cable
by S. C. Carter and H. M. Barlow

33 6809 evaluation system for £100
by R. Coates

38 World of amateur radio

39 Leap seconds
by L. Essen

41 Parallel tracking pickup arm modifications
by R. Cooper

45 Digital storage and analysis of speech
by I. H. Witten

49 Long distance television reception
by K. Hamer and G. Smith

51 Letters to the editor
Radio Amateurs' Examination/James Clerk Maxwell/Science and society

57 Wafer-scale integration
by I. Catt

60 Sound synthesis using Walsh functions
by A. A. Thomas

65 Which way h.f. broadcast receivers?
by Y-C Heng and R. C. V. Macario

70 News of the month
Frequency hopping radio/Broadcasting satellites report

73 The twins paradox of relativity
by I. McCausland

75 Circuit ideas
Low-noise m.c. pre-amp/Plotting c.r.o. waveforms

77 Designing with microprocessors - 9
by D. Zissos and G. Stone

81 Electrical and mechanical units
by D. A. Bell

83 New products



The Professionals

VALVES, SEMICONDUCTORS
& COMPONENTS for:-

Communications, Displays,
Radar, Computer,
Audio etc.

Hall Electric Limited,
Electron House,
Cray Avenue, St. Mary Cray,
Orpington, Kent BR5 3QJ.
Telephone: Orpington 27099
Telex: 896141

MIN DEF APPROVAL 0529/0531




DON'T GAMBLE WITH PERFORMANCE BUY LEVELL OSCILLATORS




FREQUENCY 1Hz to 1MHz in 12 ranges.
ACCURACY 0 to 1% fine control on TG200DMP.
 $\pm 1.5\% \pm 0.01\text{Hz}$ up to 100kHz.
 $\pm 2\%$ up to 1MHz.
SINE OUTPUT 7V r.m.s. down to $< 200\mu\text{V}$ with $R_s = 600\Omega$.
DISTORTION $< 0.05\%$ from 50Hz to 15kHz,
 $< 0.1\%$ from 10Hz to 50kHz, $< 0.2\%$
from 5Hz to 150kHz, $< 1\%$ at 1Hz and
1MHz.
SQUARE OUTPUT TG200D, DM & DMP only, 7V peak
down to $< 200\mu\text{V}$. Rise time
 $< 150\text{nS}$.
SYNC OUTPUT $< 1\text{V}$ r.m.s. sine in phase with output
SYNC INPUT $\pm 1\%$ freq. lock range per volt r.m.s.
METER SCALES TG200M, DM & DMP only: 0/2V
0/7V & -14/+6dBm.
SIZE & WEIGHT 260 x 130 x 180mm. 4.3kg with
batteries.

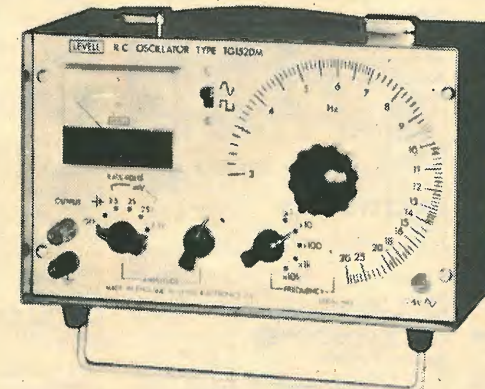TG200 TG200D TG200M TG200DM TG200DMP
£99 £108 £125 £130 £135



FREQUENCY 3Hz to 300kHz in 5 decade ranges.
ACCURACY $\pm 2\% \pm 0.1\text{Hz}$ to 100kHz.
Increasing to $\pm 3\%$ at 300kHz.
SINE OUTPUT 2.5V r.m.s. down to $< 200\mu\text{V}$
DISTORTION $< 0.2\%$ from 50Hz to 50kHz.
 $< 1\%$ from 10Hz to 200kHz.
SQUARE OUTPUT 2.5V peak down to $< 200\mu\text{V}$.
SYNC. OUTPUT 2.5V r.m.s. sine.
METER SCALES 0/2.5V & -10/+10dB on
TG152DM.
SIZE & WEIGHT 260 x 130 x 180mm. 3.4kg with
batteries.

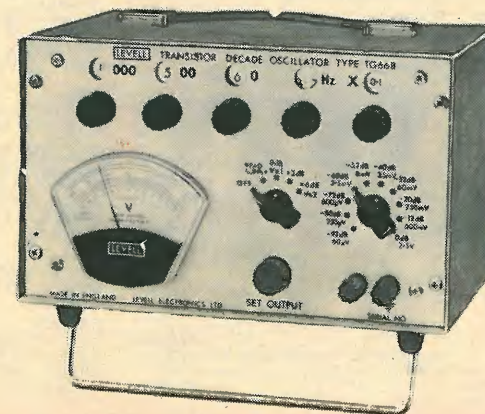TG152D TG152DM
Without meter **£80** With meter **£99**



FREQUENCY 0.2Hz to 1.22MHz on four decade
controls.
ACCURACY $\pm 0.02\text{Hz}$ below 6Hz.
 $\pm 0.3\%$ from 6Hz to 100kHz.
 $\pm 1\%$ from 100kHz to 300kHz.
 $\pm 3\%$ above, 300kHz.
SINE OUTPUT 5V r.m.s. down to $30\mu\text{V}$ with $R_s = 600\Omega$.
DISTORTION $< 0.15\%$ from 15Hz to 15kHz.
 $< 0.5\%$ at 1.5Hz and 150kHz.
METER SCALES 2 Expanded voltage and -2/+4dBm
SIZE & WEIGHT 260 x 180 x 180mm. 5.4kg.

TG66B TG66A
Battery model **£265** Mains & battery model **£280**

Prices are ex works with batteries. Carriage, packing and VAT
extra.
Optional extras are leather cases and mains power units.
Send for data covering our range of portable instruments.


LEVELL ELECTRONICS LTD.

MOXON STREET, BARNET, HERTS., EN5 5SD.
TEL: 01-449 5028/440 8686

CX80 COLOUR MATRIX PRINTER

At last a low-cost Colour Matrix Printer for Text, Graphics, Histograms, Colour VDU Dumps, etc.

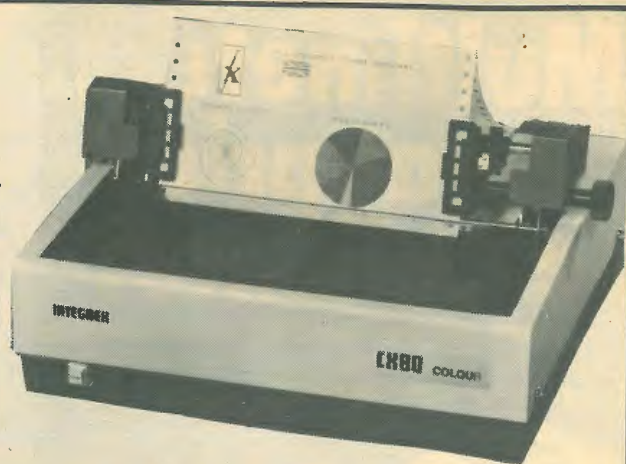Colour printout is quickly assimilated, makes graphics more understandable and is an ideal medium for the presentation of complex data or concepts.



Compatible with most microprocessors, prints in 7 colours – sophisticated internal programme makes the CX80 easy to use.

Dot Addressable + 15 user programmable characters, 96 ASCII and 64 graphics characters in rom. Centronics interface with RS232 and IEEE488 options.

The CX80 is a product of our own design and development laboratories. It represents a British breakthrough in colour printer technology. Colour brochure on request. OEM pricing available.

NRDC-AMBISONIC UHJ SURROUND SOUND DECODER



The first ever kit specially produced by Integrex for this British NRDC backed surround sound system which is the result of 7 years' research by the Ambisonic team. W.W. July, Aug., '77. The unit is designed to decode not only UHJ but virtually all other 'quadrophonic' systems (Not CD4), including the new BBC HJ. 10 input selections. The decoder is linear throughout and does not rely on listener fatiguing logic enhancement techniques. Both 2 or 2 input signals and 4 or 6 output signals are provided in this most versatile unit. Complete with mains power supply, wooden cabinet, panel, knobs, etc.

Complete kit, including licence fee **£57.70** + VAT or ready built and tested **£76.95** + VAT

INTRUDER 1 Mk. 2 RADAR ALARM

With Home Office Type approval

The original "Wireless World" published Intruder 1 has been re-designed by Integrex to incorporate several new features, along with improved performance. The kit is even easier to build. The internal audible alarm turns off after approximately 40 seconds and the unit re-arms. 240V ac mains or 12V battery operated. Disguised as a hard-backed book. Detection range up to 45 feet. Internal mains rated voltage free contacts for external bells etc.

Complete kit **£52.50** plus VAT, or ready built and tested **£68.50** plus VAT.

Wireless World Dolby noise reducer

Trademark of Dolby Laboratories Inc.




Complete Kit **PRICE: £49.95** + VAT (3 head model available)

Also available ready built and tested **Price £67.50** + VAT

Calibration tapes are available for open-reel use and for cassette (specify which) **Price £2.75** + VAT

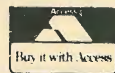Typical performance
 Noise reduction better than 9dB weighted.
 Clipping level 16.5dB above Dolby level (measured at 1% third harmonic content)
 Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%
 Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output
 Dynamic range >90dB
 30mV sensitivity




All kits are carriage free

INTEGREX LIMITED

Please send SAE for complete lists and specifications
**Portwood Industrial Estate, Church Gresley,
 Burton-on-Trent, Staffs DE11 9PT
 Burton-on-Trent (0283) 215432 Telex 377106**

Quartz Crystals

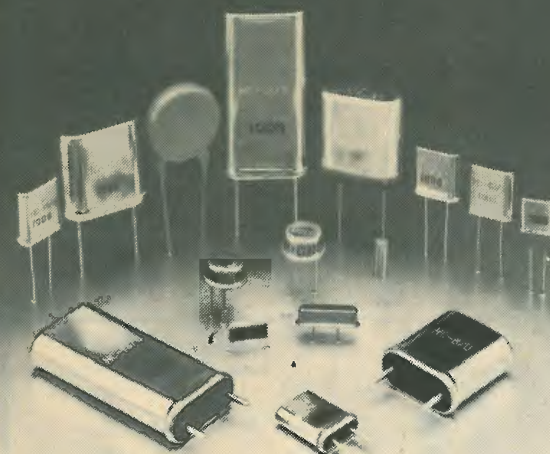

Stocks of standard items exceed a quarter of a million. Individual units to the tightest specification made to order.

Interface
 Quartz
 Devices
 Limited

This technology is available now from




29 Market Street
 Crewkerne
 Somerset TA18 7JU

Crewkerne (0460) 74433
 Telex 46283 infac g

WW - 034 FOR FURTHER DETAILS

MORE SPEC. FOR YOUR MONEY

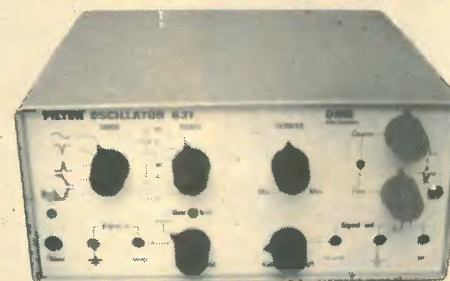

TYPE 631 FILTER OSCILLATOR

£112 & 2.50 carriage, ins. etc.

COVERS THE RANGE 0.1Hz to 100KHz

MODES -

ACCEPT	Q from less than 1 to over 300
REJECT	90 dB notch
HI and LO PASS	12 dB per octave
OSCILLATE	Sinewave and squarewave

TYPE 631LF - £118.13 & 2.50 carriage, ins. etc.

Low frequency version 0.01Hz to 10KHz

OMB ELECTRONICS, RIVERSIDE, EYNSFORD, KENT DA4 0AE
 Tel. Farningham (0322) 863567


Prices, which are CWO and ex-VAT, are correct at the time of going to press and are subject to change without notice.

FROM OMB ELECTRONICS

WW - 049 FOR FURTHER DETAILS

EXTENSIVE RANGE OF NEW FLUKE DMM'S FROM ELECTRONIC BROKERS

IMMEDIATE DELIVERY

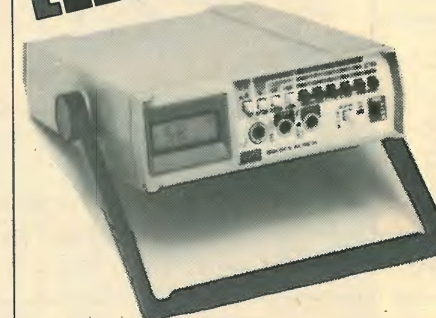

8050A 4 1/2 Digit LCD DMM with true RMS on AC volts and current DC volts 200mV-1KV, 10µV resolution AC volts. 200mV-750V, 10µV resolution. DC/AC current 200µA-2A, 0.01µA resolution resistance 200Ω-20MΩ, 0.01Ω resolution. Also reads dB direct referenced to 16 stored impedances. Conductance ranges 2mS and 200nS. **£245** mains model **£285** mains battery

8012A 3 1/2 Digit LCD DMM with true RMS on AC volts and current. DC volts 200mV-1KV, 100µV resolution. AC volts 200 mV-750V, 100µV resolution. DC/AC current 200µA-2A, 0.1µA resolution. Resistance 200Ω-20MΩ, 0.1Ω resolution Low resistance 2Ω and 20Ω, 1mΩ resolution Conductance ranges 2mS-20µS-200nS

£218.00 mains model **£244.00** mains battery.



8010A 3 1/2 Digit LCD DMM Same spec as 8012A plus a 10amp AC/DC current range, but no low resistance range.

£167.00 mains model **£193.00** mains battery.

8024A 3 1/2 Digit hand held LCD DMM with peak hold Level Detector and continuity tester. DC volts 200mV-1KV, 100µV resolution.

AC volts 200mV-750V, 100µV resolution. DC/AC current 2mA-2A, 1µA resolution. Resistance 200Ω-20MΩ, 0.1Ω resolution. Conductance 200nS. Peakhold of AC or DC volts and current. Level detector operates around +0.8V reference. Audio tone on level and continuity, **£155.00**, carrying case **£8.00** extra.

8020A 3 1/2 Digit hand held LCD DMM. spec as per 8024A with extra conductance range of 2mS but no peak hold, level or continuity ranges. Complete with carrying case. **£125.00.**



8022A 3 1/2 Digit hand held LCD DMM. Spec as per 8020A but no conductance ranges and slight reduction in accuracy, **£89.00** carrying case **£8.00** extra.

Also available a range of accessories including current shunts, EHT probe, rf probe, Temperature probe and touch and hold probe. Full details on request.

The warranty period on all items shown is 1 year other than the 8020A which is 2 years.

Electronic Brokers

61-65 King's Cross Road
 London, WC1X 9LN
 Tel: 01-278 3461 - Telex 298694

Prices do not include carriage or VAT.

WW - 054 FOR FURTHER DETAILS

New! Sinclair ZX81 Personal Computer. Kit: £49.⁹⁵ complete

Reach advanced computer comprehension in a few absorbing hours

Built: £69.⁹⁵ complete

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. At £99.95, the ZX80 offered a specification unchallenged at the price.

Over 50,000 were sold, and the ZX80 won virtually universal praise from computer professionals.

Now the Sinclair lead is increased: for just £69.95, the new Sinclair ZX81 offers even more advanced computer facilities at an even lower price. And the ZX81 kit means an even bigger saving. At £49.95 it costs almost 40% less than the ZX80 kit!

Lower price: higher capability

With the ZX81, it's just as simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASICROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, or to select a program off a cassette through the keyboard.

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!


The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

Proven micro-processor, new 8K BASIC ROM, RAM – and unique new master chip.

Kit or built – it's up to you!


The picture shows dramatically how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

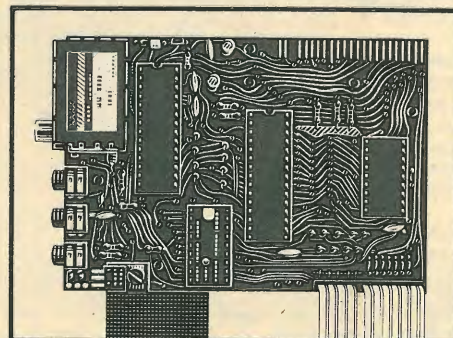Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



New Sinclair teach-yourself BASIC manual

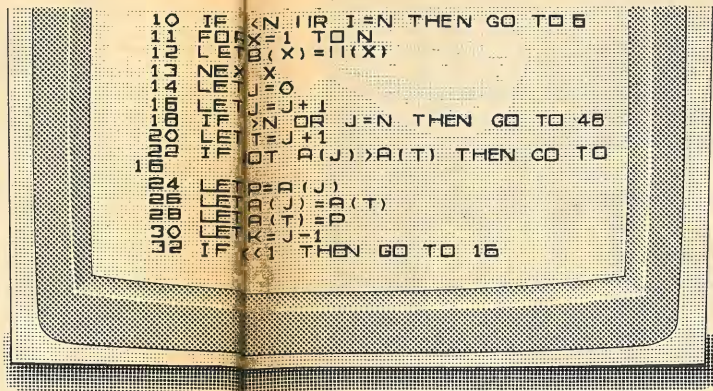Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs. You need no prior knowledge – children from 12 upwards soon become familiar with computer operation.



New, improved specification

● Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.

● Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.

● Unique syntax-check and report codes identify programming errors immediately.

● Full range of mathematical and scientific functions accurate to eight decimal places.

● Graph-drawing and animated-display facilities.

● Multi-dimensional string and numerical arrays.

● Up to 26 FOR/NEXT loops.

● Randomise function – useful for games as well as serious applications.

● Cassette LOAD and SAVE with named programs.

● 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.

● Able to drive the new Sinclair printer (not available yet – but coming soon!)

● Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.

sinclair ZX81

Sinclair Research Ltd, 6 Kings Parade, Cambridge, Cambs., CB2 1SN. Tel: 0276 66104. Reg. no: 214 4630 00

If you own a Sinclair ZX80...

The new 8K BASIC ROM used in the Sinclair ZX81 is available to ZX80 owners as a drop-in replacement chip. (Complete with new keyboard template and operating manual.)

With the exception of animated graphics, all the advanced features of the ZX81 are now available on your ZX80 – including the ability to drive the Sinclair ZX Printer.

Coming soon – the ZX Printer.

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alphanumeric across 32 columns, and highly sophisticated graphics. Special features include COPY, which prints out exactly what is on the whole TV screen without the need for further instructions. The ZX Printer will be available in Summer 1981, at around £50 – watch this space!



16K-BYTE RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.



How to order your ZX81

BY PHONE – Access or Barclaycard holders can call 01-200 0200 for personal attention 24 hours a day, every day. BY FREEPOST – use the no-stamp-needed coupon below. You can pay by cheque, postal order, Access or Barclaycard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option, of course. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST 7, Cambridge, CB2 1YY.				Order
Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack(s).	18	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95
TOTAL £				

Please tick if you require a VAT receipt

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ _____

*Please charge to my Access/Barclaycard/Trustcard account no. _____

*Please delete/complete as applicable. Please print.

Name: Mr/Mrs/Miss _____

Address _____

FREEPOST – no stamp needed. WRW07


ORDER BY POST OR TELEPHONE WITH BARCLAYCARD/ACCESS ELECTRONIC TEST EQUIPMENT SPECIALISTS ALL PRICES INCLUDE VAT

AUDIO ELECTRONICS

ALL MODELS ON DISPLAY RETAIL - MAIL ORDER - EXPORT - INDUSTRIAL OPEN SIX DAYS A WEEK CALL IN AND SEE FOR YOURSELF


SCOPES

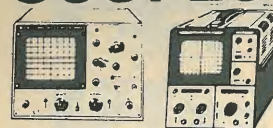A range of Scopes in stock from 5mHZ Single Trace to 50mHZ Dualtrace Mains and Battery/Mains portables. Many on demonstration



SINGLE TRACE (UK c/p etc £2.50) 3030 15mHZ 5LV 6.6x6.6cm. display plus component test £166.75

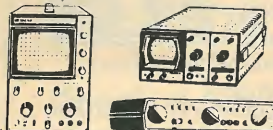
DUAL TRACE (UK c/p etc £3.50) CS1566A 10mHZ, 10mV 5" display £267.00



SAFGAN DUAL TRACE C/P UK £2.50 10mHZ £194.95, 12mHZ £201.25, 15mHZ £216.20

GENERATORS

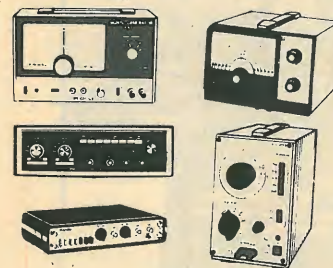UK c/p £1.75 A range of Signal Generators to cover Audio, RF and Pulsing. Mains operated.



RF SG402 100 KHZ-30mHZ with AM modulation £68.00 LSG16 100KHZ (300mHZ on Harmonics) £63.25

'PRO' MULTIMETERS

(UK c/p £1.20) M1200 100K/Volt 30 range plus AC/DC 15 amp £67.00

SWR/FS AND POWER METERS


UK C/P 85p Range in stock covering up to 150mHZ and up to 1K/watt power PL259 sockets. Also 25 mHZ Grid Dipmeter.

LOGIC PROBES/MONITORS

Logic probes indicating high/low, etc., states that scopes can miss. All circuit powered for all ICs.

DIGITAL MULTIMETERS

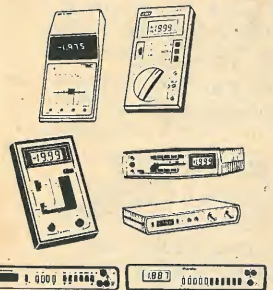A range of LED and LCD Bench and Hand DMMs battery operated with optional Mains Adaptors, some with optional Nicads. All supplied with batteries and leads.



HAND HELD (UK post etc 85p) GL35C 3 1/2 Digit LCD in AC/DC with case £37.50

BENCH PORTABLES


(UK c/p £1) DM235 3 1/2 Digit LED 21 ranges, 0.5% AC/DC 2A £60.38

MULTIMETERS

(UK c/p 75p) KRT101 1K/Volt 10 range pocket £4.60

FREQUENCY COUNTERS

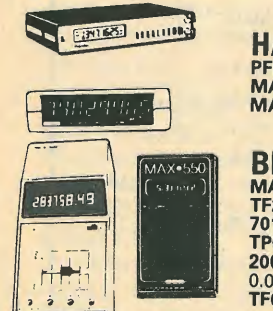Portable and Bench LCD and LED Counters up to 600mHZ. Prices include batteries and leads.



HAND HELD (UK post etc 85p) PFM200 20HZ to 200mHZ 8 Digit LED £57.27

CLAMP METERS/ INSULATION TESTERS

(All multirange except K2303)



K2303. 30 AMPS. 500 VAC. £21.95 3101. 300 AMPS. 600 VAC. 1K OHM £32.95

AT1020 20K/Volt 19 range de luxe plus hfe test £16.95

TV GENERATORS

(UK c/p £1.50) LCG-393V PAL 8VHF 6 patts £143.75

Stockists of electronic equipment, speakers/kits, PA equipment plus huge range of accessories UK carriage/packing as indicated Export - prices on request

AUDIO ELECTRONICS

Cubegate Limited 301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TELEPHONE 01-724 3564

FREE CATALOGUE! Send large SAE (20p UK) Schools, Companies, etc. free on request.



FAST ERECTING CLARK MASTS

Here is the expertise you can depend on-

25 years in this specialist field

When you choose a mast from the comprehensive Clarke range you are assured of a high standard of Engineering and operational reliability.

Why compromise?

Extended heights 4 metres-30 metres, capable of lifting headload 1 kg.-200 kgs. Sectional or telescopic air operated for field or vehicle mounting. Write or phone us for details today.

CLARK W.T.16 vehicle-mounted in a Saviem-Renault. An air-operated telescopic mast mainly used for raising heavy antennas and instruments. Extended heights 3.2m. to 30.5m.



CLARK MASTS LTD. Binstead, Isle of Wight, PO33 3PA, England. Telephone: Ryde (0983) 63691, Telex: 86686.



MICROCOMPUTER COMPONENTS

LOWEST PRICES - FASTEST DELIVERY

Table with columns: DEVICE, PRICE, DEVICE, PRICE, DEVICE, PRICE. Lists various microcomputer components like CPUs, support chips, memories, regulators, etc.

OFFICIAL ORDERS WELCOME QUANTITY DISCOUNTS AVAILABLE MIDWICH COMPUTER CO. LTD. All prices exclude post and packing on orders under £10 (50p) and VAT (15%)

The EP4000 is not just an EPROM Programmer . . .

Not only does the EP4000 copy, store, program and duplicate the 2704/2708/2716(3)/2508/2758/2716/2516/2532 and 2732 EPROMs without personality cards or modules, but also includes a video output for memory map display to make the powerful editing facilities really useful (and this is in addition to the in-built LED display for stand-alone use), but it also comes as standard with comprehensive input/output – RS232, 20mA loop, TTL, parallel handshake, cassette, printer and direct memory access. Now the programming power can be expanded with our range of add-on accessories listed below.



Made in the U.K.

. . . but also a Real Time EPROM Emulator . . .

Real time EPROM Emulation is the second major function of the EP4000. This facility allows the machine to directly replace your in-circuit EPROMs during the process of program development – the EP4000 can be configured to look like any EPROM it is capable of programming. The press of a button isolates

the external system so that data changes, entries, editing and downloading can be implemented. When the program is complete and working, the simulator cable can be replaced by an EPROM programmed by the EP4000.

. . . with real technical back-up and service.

The EP4000 comes with a technical manual describing every aspect of the machine – its purpose, its use, and how to use it. It also has a section describing the whole process of program development.

And if you ever need technical help or advice, you can now dial direct to our technical department for instant attention – Tel. (0803) 863380.

Finally, a full range of accessories is now available – these include Bipolar programming

modules, multi-EPROM simulator adaptors, buffer pods, EPROM Erasers, video monitors, 2764/2564 programming satellite, printer and production programmers. The EP4000 is ex-stock. Price – £545 + VAT (+£12 for DATAPOST delivery). Telephone, telex, write or call for full data and Distributor list, or place your order for immediate despatch – Overseas customers, please telex or write for quotation and terms. Agents in some countries, and distributors in Britain required.

G.P. Industrial Electronics Ltd.

Unit 6, Totnes Industrial Estate Totnes, Devon TQ9 5XL

Tel. Sales (0803) 863360. Technical (0803) 863380

Telex: 42596 GPELEC

ONE UP ON THE COMPETITION.

Introducing the first 4½ digit handheld DMM in a market that's been the exclusive domain of 3½ digit models. Until now . . .



The new Keithley 135.

Combining outstanding specification with impeccable performance. And confirming Keithley's position as a major innovator in D.M.M. technology:

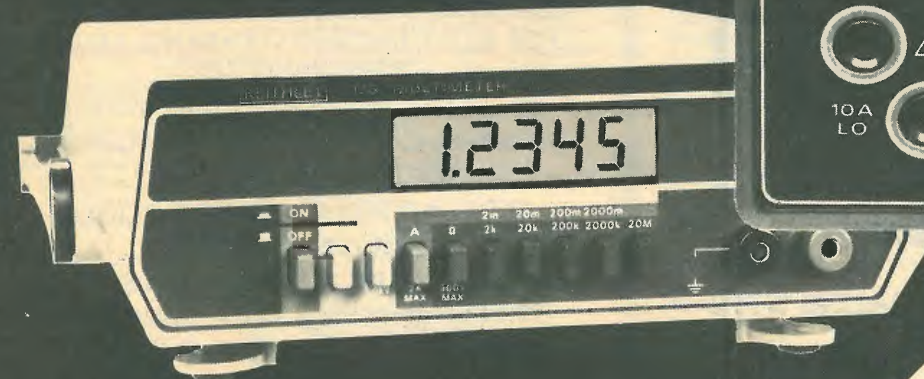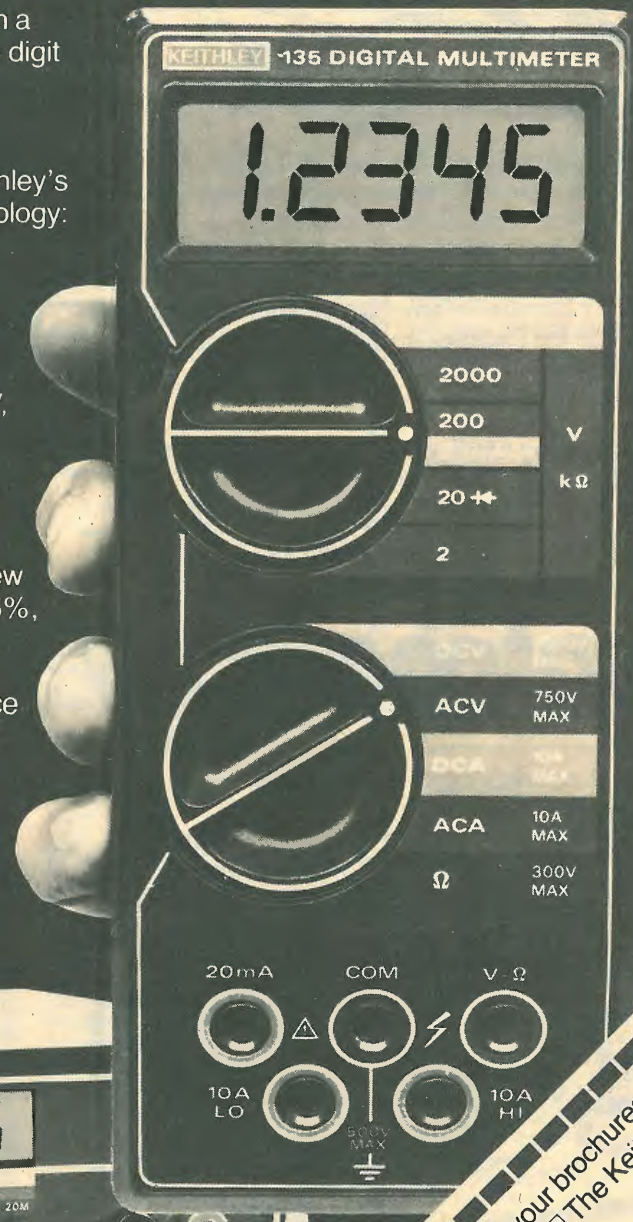- 0.05% DCV accuracy
- Five functions
- Low battery indicator
- Full overload protection: 1000V max DCV, 1000V peak ACV, 300V max Ohms
- 10 amp range
- ACV bandwidth to 20 kHz

Need a bench unit? Then take a look at the new Keithley 176. Five functions, 4½ digits, ±0.05%, DCV accuracy, and full function annunciators. Built up to a standard – not down to a price. Yet the 176 gives quality, 4½ digit performance at a cost some 3½ digit manufacturers would dearly love to match.

To find out more, fill in the coupon. And see what keeps Keithley one step ahead.



KEITHLEY

Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telephone (0734) 861287
Telex 847047

I'm interested. Please send me your brochures on

The Keithley 135 The Keithley 176 The Keithley Range


Name _____ Position _____

Company _____

Address _____

Tel _____ WWW7

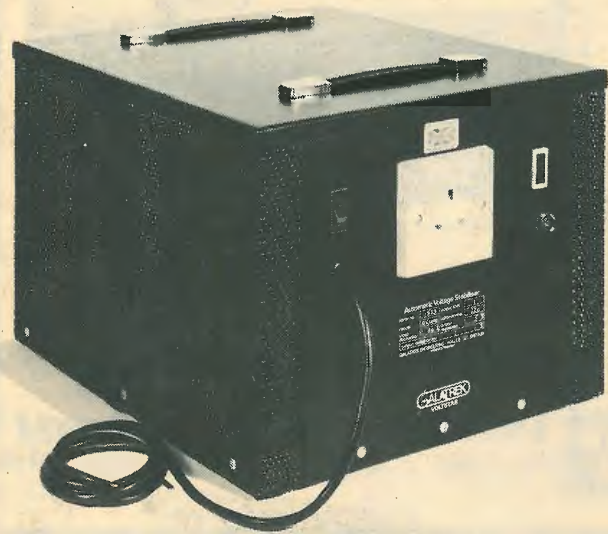Voltstab[®] The simple answer to your current problem.



If you are experiencing random faults and failures in your microprocessor-based equipment, they are probably caused by voltage irregularities. Even dedicated supplies may not be the answer - they will still suffer from momentary voltage transients and power supply breaks.

Galatrek have the simple answer. A plug-in VOLTSTAB Constant Voltage Transformer. Reliable, efficient and economical, the Galatrek VOLTSTAB offers you:

- Output stabilisation to $\pm 1\%$ from mains input fluctuations of $\pm 20\%$
- Transient attenuation
- Momentary power back-up

Available ex-stock from regional stockists in a choice of power ratings from 250VA to 5KVA, the Galatrek VOLTSTAB will keep your sensitive electronic equipment running smoothly. Both the factory and the regional stockists throughout the UK will assist you technically to ensure you match the VOLTSTAB unit exactly to your requirements.

Mr R Koffler, Galatrek International, Scotland Street, Llanrwst, nr Colwyn Bay, Gwynedd LL26 0AL, North Wales, Great Britain.
Tel No: 0492-640311/641298 Night Service: 0492-30592
Telex: 617114 A/B Galahu

Voltstab is the Registered Trademark of Galatrek International




Please send me the 18 page Galatrek VOLTSTAB catalogue, which includes details of your Mains Filters and Standby Power Supplies.

Name: _____
Position: _____
Company: _____
Address: _____

Tel No: _____

Trade OEM (please tick where appropriate) ww

WW - 021 FOR FURTHER DETAILS

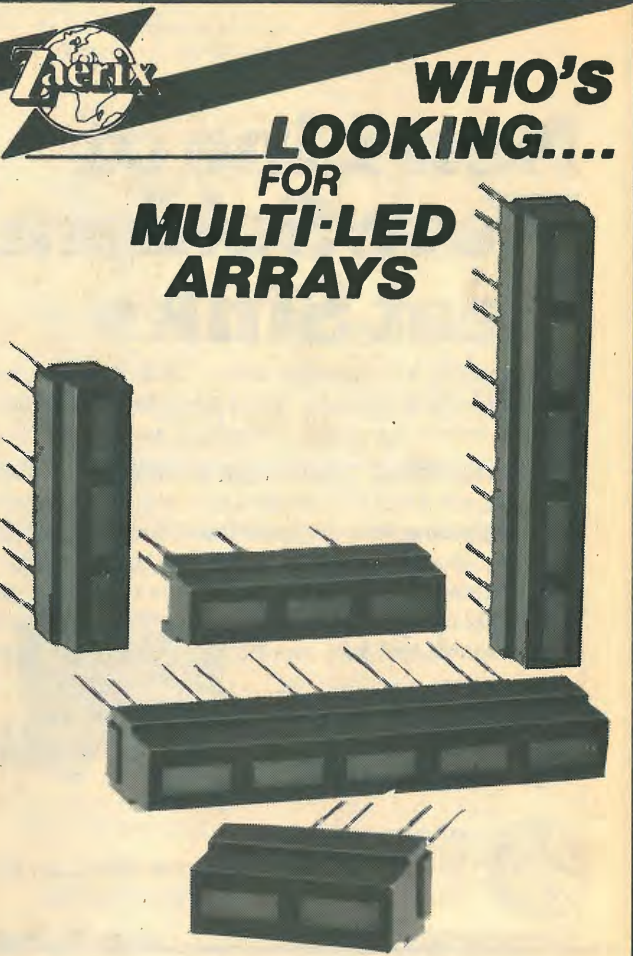

WHO'S LOOKING.... FOR MULTI-LED ARRAYS

OUR OFF THE SHELF RANGE OFFERS

...any combination and sequence of Red(GaP), Green(GaP) or Yellow (GaAsP/GaP) colours incorporated in one array,

...fully end-stackable, 2, 3, 4 or 5 segment options thereby enabling displays encompassing any number of segments to be created,

...black bezels as standard with white bezels to special order,

...push-fit mounting into correctly dimensioned panel cut-out,

...wide operating temperature range of -40°C to $+80^{\circ}\text{C}$.

So if you are into
TREND INDICATORS
BAR GRAPHS
or
EVENT DISPLAYS
Look at our

MULTI-LED ARRAYS

Our prices won't make your eyes water

Zaerix Electronics Limited

46 Westbourne Grove, London W2 5SF, England
Tel: 01-221 3642 Telex: 261306

WW - 014 FOR FURTHER DETAILS

MAPLIN make it easy...



in
SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)

in
HAMMERSMITH
159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)

For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our CATALOGUE

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!

Don't miss out on your copy.

On sale now in all branches
WH Smith price £1.

In case of difficulty check the coupon below.

make it easy... with MAPLIN

The
Maplin Matinée

Amazing value for
only £299.95 plus £99.50
for cabinet if required

Easy to build,
superb specification.

Comparable with organs selling for up to £1,000. Full construction details in Electronics & Music Maker commencing March, 1981 issue. Back numbers available.



MAPLIN ELECTRONIC SUPPLIES LTD.

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911

WW - 017 FOR FURTHER DETAILS

by MAIL ORDER

A fast service
You can rely on

- * Same day service on in-stock lines
- * Very large percentage of our stock lines in stock
- * All prices include VAT
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components—no rejects—no re-marks
- * Competitive prices
- * Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name: _____
Address: _____

(WW7/81)

The Brewster Family help put it together

S&R BREWSTER LIMITED
MANUFACTURE A WIDE RANGE OF
SOLDERING IRONS TO CATER FOR MOST TYPES OF
JOBS FOR HOBBIES, PROFESSIONAL & INDUSTRIAL USE.

MODEL K200
The largest standard
soldering iron in
our range
Power 200 Watts
Bit size 1 1/4"
£19.55
inc. VAT
Postage 93p extra

MODEL K500TC
A Temperature
controlled version
of the Model K200
Power 500 Watts
Bit size 1 1/4"
£25.30
inc. VAT
Postage 93p extra

MODEL H70
Our medium sized
general purpose
soldering iron with
interchangeable bits
6mm Bit fitted
Power 70 Watts
£11.50
inc. VAT
Postage 56p extra

MODEL H150TC
A temperature controlled
version of the H70
Power 150 Watts
£17.36
inc. VAT
Postage 56p extra
Spare bits for H series
£1.27 each inc. VAT
Postage 10p extra
Sizes available
4.5mm
6.0mm
9.5mm
11.0mm

All our range of soldering irons
are available in 100/110 volts and
220/240 volts. The type 1 and
model D are also available in
11/12 volts. (Please specify
when ordering)

The TYPE 1
The original
MIGHTY MIDGET
18 Watt
soldering iron
Fitted with
No. 20 (3mm) bit
£4.95
inc. VAT
Postage 28p extra
Spare Bits 69p
inc. VAT and postage
Sizes available
1.5mm (No. 19)
3.0mm (No. 20)
4.5mm (No. 21)
6.0mm (No. 22)
Special Bit
No. 78 I.C. Desoldering Bit
£1.27 inc. VAT
Postage 12p extra



MODEL D50
The smallest
temperature
controlled soldering
iron in our range with
interchangeable bits
Power 50 Watts
£12.07
inc. VAT
Postage 28p extra
Spare bits for model D
52p each inc. VAT
Postage 10p extra
Sizes available 1.5mm
3.0mm (fitted as standard)
4.5mm 6.0mm

Universal
**SOLDERING
IRON SAFETY
STAND**
Suitable for most
soldering irons
up to 50 watts

SOLDER
Postage
Savbit 22 S.W.G. 20ft. **70p 12p**
Savbit 22 S.W.G. 10ft **40p 8p**
Low Melt 145°C 20 S.W.G. 10ft
(Suitable for white
metalkits) **80p 12p**
£4.49
Postage 80p extra. Inc. VAT



FROM YOUR LOCAL RETAILER OR DIRECT FROM MANUFACTURERS.

S&R BREWSTER LTD

86-88 UNION STREET PLYMOUTH PL1 3HG ENGLAND
Tel: (0752) 665011 Telex: 45311

Retail, wholesale & industrial enquiries welcome

CECO
Vari-Stat



Precisely on time.


The Model 4401 Frequency Standard by Global Specialties: for precision and value, it's a source whose time has come.

The heart of the 4401 Frequency Standard is a unique 10MHz precision temperature controlled crystal oven oscillator (TCXO). Boasting an accuracy of ±0.5ppm (±0.00005%) from 0 to 40°C, it offers exceptional long term stability—aging 1ppm per year. And it's directly traceable to the National Bureau of Standards via factory calibration to WWVB.

Two short-circuit protected 50-ohm BNC outputs are capable of driving 10 TTL loads into matched 50Ω lines, providing square waves from 0.1Hz to 10MHz in 9 decade steps, with LED indication of the decade in use. And a frequency multiplier switch (1X, 2X, 5X) enables you to select fractional frequencies in each decade.

Our new 4401 Frequency Standard sets a new *value* standard.

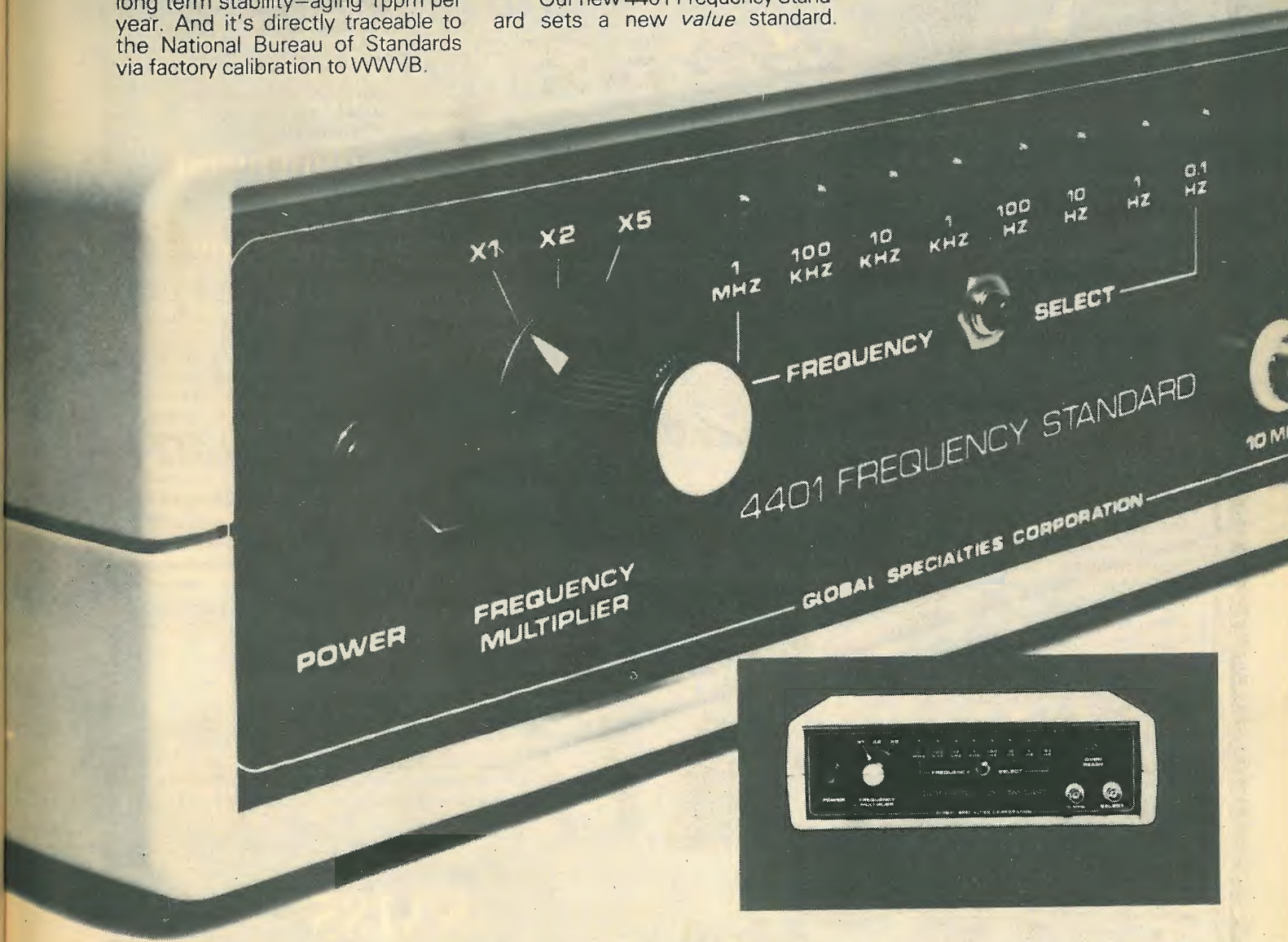Giving you an exceptionally accurate, stable source for oscilloscope timebase calibration, frequency counter calibration, laboratory time-keeping and other high-precision timing applications... so whatever your application, the Global 4401 Frequency Standard is precisely £118.



GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 7R
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: Saffron Walden (0799) 21682.
Telex: 817477.

G.S.C. (UK) Ltd., Dept 7R, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model 4401	FREQ STANDARD	Unit price inc P&P 15% VAT £138.58	Qty	_____
Name _____		Address _____		
I enclose cheque/P.O. for £ _____ or debit my Barclaycard/Access/ American Express card no. _____ exp. date _____				
FOR IMMEDIATE ACTION - The G.S.C. 24 hour, 5 day a week service. Telephone (0799) 21682 and give us your Barclaycard, Access, American Express number and your order will be in the post immediately.			For Free catalogue tick box <input type="checkbox"/>	

wireless world

Decline of the philosophical spirit

Ampère's *Théorie mathématique des phénomènes électro-dynamiques* (1826) is still worth reading. It is known as the principal founding source of electrodynamics, but other features are just as instructive. It begins with an extensive homage to 'Newtonian philosophy', and continues with a long mixture of physical theory, mathematical analyses and reports of experimental procedures. Ampère sought not merely methods of explaining and calculating effects; he wanted to find out how the phenomena actually occurred. Indeed, in the naive tradition sometimes followed at the time, he thought of his theory as a truth, 'uniquement déduite de l'expérience', to complete the title of his book.

Ampère is remembered now only for this work, but in fact it was a small part of his output. He was a polymath, whose activities were unified by his philosophical spirit. This spirit informed all his writings and came to its zenith in his *Essai sur la philosophie des sciences* (1834). But he was an outsider in philosophical thought, for the 1830s also saw the rise of positivism in the hands of some of his former students at the Ecole Polytechnique: Auguste Comte, and engineer-scientists such as Dupin and Poncelet. Associated closely at that time with educational and social causes, positivism became one of the dominant philosophies of the 19th century and has maintained its influence, directly and indirectly, until today. Knowledge without metaphysics; rejection of abstract intellectual objects; even a lack of attention to the way in which mathematics is used in physics. It is a strange contrast to read Ampère's *Essai*, with its Kantian concern with phenomena and their causes, with man's knowledge and his cognitive power to know.

It was through movements such as positivism that philosophy and science became separated. Positivism and its cousins (mechanism, materialism, instrumentalism, behaviourism, and so on) do not solve philosophical problems so much as ignore them. Yet scientists accept

positivist tenets without much thought: facts are facts are facts; theories are useful *only* for predicting new facts; mathematics is just a fiction which *in principle* has nothing to do with physical reality; the aim of science is consensus (as a noted FRS contentedly put it on television recently); the history of science is bunk — and, above all, philosophising about science is time-wasting nonsense. At the same time philosophy itself has become an enclosed profession, largely concerned with footling 'puzzles' in ordinary language; its practitioners rarely know anything beyond the writings of their professional colleagues. There are exceptional figures in the communities of both science and philosophy; but they stand out as such, often nervously.

Meanwhile the real world seems to have remained the same as it was in Ampère's day, especially with regard to the phenomena studied in physics. Thus the objects of scientific study remain basically unchanged, and so does the need for philosophical as well as technical skill. We now know far more about the technicalities of electricity and magnetism than did Ampère and his contemporaries; but we no longer bring to our theoretical studies the sensitivity to philosophical questions which Ampère, and others of his time, could show. He and his contemporaries were not really scientists in the way that we understand the term; they often called themselves 'natural philosophers', enquirers into the nature around them and into the powers of man to think up theories about it. They may have fallen into optimistic naiveties such as the allegedly immediate deduction of theories from facts; but they did not succumb to our reflex dismissals of the non-experimental and our inattention to the place of mathematics in scientific knowledge. The imperatives which informed not only Ampère but also his contemporaries such as Faraday and Ohm, and successors like Kelvin and Maxwell, have faded; the traditions of natural philosophy have long been broken; reflection has given way to 'research'.

new SM 85 PRO TECH SOUND

brings a new dimension
to a hand-held
condenser microphone

This new high technology Shure microphone will change the way people think of condenser microphones. The SM85 is designed especially for on-stage, hand-held use. Its sound is unique — far more tailored to the special needs of the vocalist: sizzling highs and a shaped mid-range for superb vocal reproduction, and a gentle bass rolloff that minimizes handling noise and "boominess" associated with close-up use. Ultra-low distortion electronics make the SM85 highly immune to stray hum fields. An integral, dual-density foam windscreen provides built-in pop protection.

What's more, the SM85 Condenser Microphone must pass the same ruggedness and dependability tests required of Shure dynamic microphones. As a result, the SM85 sets a new standard of reliability for hand-held condenser microphones.

The SM85 is *extremely* lightweight, beautifully balanced — it feels good, looks good on-stage, on-camera, on-tour. Ask your dealer for a demonstration of the new SM85 PRO TECH Sound, or write to us (ask for AL664) for full details.

SM85
Cardioid Condenser
Hand-Held
Professional Microphone

The Sound of the Professionals®

® **SHURE** ®

Shure Electronics Limited Ecclestone Road
Maidstone ME15 6AU
Telephone: Maidstone (0622) 59881

WW - 077 FOR FURTHER DETAILS

Editor:
TOM IVALL, M.I.E.R.E.

Deputy Editor:
PHILIP DARRINGTON
01-661 3039

Technical Editor:
GEOFF SHORTER, B.Sc.
01-661 3500 X3590

Projects Editor:
MIKE SAGIN
01-661 3500 X3588

Communications Editor:
MARTIN ECCLES
01-661 3500 X3589

News Editor:
DAVID SCOBIE
01-3500 3587

Drawing Office Manager:
ROGER GOODMAN

Technical Illustrator:
BETTY PALMER

Advertisement Manager:
BOB NIBBS, A.C.I.I.
01-661 3130

DAVID DISLEY
01-661 3500 X3593

BARBARA MILLER
01-661 3500 X3592

Northern Sales
HARRY AIKEN
061-872 8861

Midland Sales
BASIL MCGOWAN
021-356 4838

Classified Manager:
BRIAN DURRANT
01-661 3106

JAYNE PALMER
01-661 3033

BRIAN BANNISTER (*Make-up and copy*)
01-661 3500 X3561

Publishing Director:
GORDON HENDERSON

New development in h.f. coaxial cable

Structure offers lower losses and improved power handling

by S. G. Carter, M.Sc., Cable and Wireless and H. M. Barlow, F.R.S., University College, London

Recently it has become possible to make a high-frequency cable which is a cross between the conventional coaxial design and waveguides, a type of structure that exhibits much lower losses than is usual when based on attenuation per unit of cross-sectional area. This cable transmits in the dipole mode, well known for its application in optical fibres, and consists of an outer screen, as in the ordinary coaxial cable, with a group of parallel wires forming a concentric cylindrical structure for the inner in place of the more usual solid metal wire or tube.

At very low frequencies the guided transmission of telecommunication signals over long distances can be carried out by a single wire, using an earth return, or by pairs of parallel wires in space. However, as the frequency is increased the lack of electrical balance of the wires and the unrestricted spread of the field from them begins to present interference problems and a change has to be made to a screened transmission system. Up to the present, this has almost invariably taken the form of either TEM transmission in a coaxial cable or propagation in a hollow metal waveguide. Both of these arrangements have their own advantages and disadvantages but, as expected, signal attenuation has always been a major factor influencing system design. Any reduction of attenuation can lead to lower transmitted powers, small cables, an improved system noise performance and increased repeater spacing, either separately or in combination, according to design.

In the structure shown in Fig. 1, the currents set up the inner multi-wire structure are such as to provide for electric

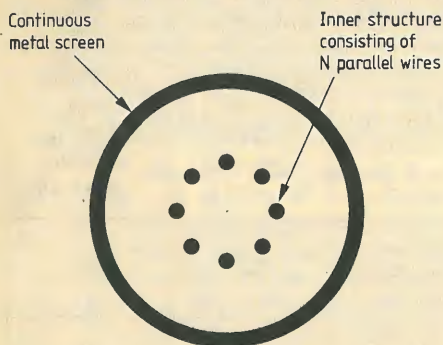


Fig. 1. Cross-sectional view of basic form of dipole-mode cable.

field across a diameter as well as a circumferential field: thus the arrangement supports a wave in the dipole mode. As a rule, a large part of the transmitted power is located within the wire-grid structure while, outside the grid, the field decays rapidly. In these circumstances the outer metal tube functions primarily as a screen and normally only produces a small perturbation of the field, even when its radius is reduced to about double that of the inner wire grid. Consideration of the operating conditions show that the inner multi-wire structure at u.h.f. behaves very much like the optical fibre at infra-red frequencies, where transmission is in the same HE_{11} mode with the power largely confined to the core and a rapid decay of field in the cladding. Further, like the large core-diameter optical fibre, the dipole mode cable can in principle support many different modes of propagation (as many as there are separate conductors) but, in practice, provision is made to ensure that only the lowest order dipole mode is carried. There is, however, one significant distinction between the behaviour of multi-conductor coaxial cable and optical fibre. Any attempt to screen a dielectric rod transmitting in the dipole mode in the u.h.f. region results in destruction of the field and inhibition of propagation in that mode. This is because the boundary conditions on the inside of the screen cannot be satisfied at such frequencies. The wire-grid coaxial cable suffers no such limitation. As with ordinary TEM transmission in conventional coaxial cables (and unlike tubular metal waveguides), the dipole-mode cable does not exhibit frequency cut-off and, in principle, can therefore be operated at any part of the spectrum down to d.c. However, it is in the high u.h.f. and s.h.f. regions that the losses are so much lower than those obtainable with current-day coaxial cables.

Cable structure

While Fig. 1 shows the basic structure of the dipole-mode cable, comprising a number of parallel wires to form a cylindrical grid, coaxial with an outer metal screen, it is of course necessary to support the inner conductors and separate them from the outer. Although regularly spaced disc insulators or beads may, when the cable is straight, keep the wires of the inner in position and also help to reduce the amount of dielectric employed, the

need for a flexible cable tends to demand a continuous dielectric tube to support the wires. So far two different types of cable structure have been developed experimentally and these are illustrated in Fig. 2. The polythene tube is extruded to include the group of parallel wires attached either to the outside or the inside of the tube and this inner structure is then, as a whole, located within the outer screen by one of the methods employed in the construction of ordinary low-loss coaxial cables; for example, a dielectric membrane helixed around the inner or, alternatively, a cartwheel-type dielectric spacer. For experimental purposes the method chosen was to support the inner structure by thin p.t.f.e. discs with a hole in the centre through which the inner cable structure was inserted. These supports were spaced approximately every 8 cm.

The cable attenuation is dependent not only on the number of wires included in the inner structure but also on their diameter. In general, the loss decreases as the number of wires increases and as more of the circumference of the inner is covered by metal. However, capacitive circumferential current is necessary for HE_{11} mode propagation and consequently the wires must always be spaced far enough apart to maintain this dipole mode at an adequate power level. Clearly, there are practical problems in fabricating a cable with a large number of very thin wires or strips of metal and therefore the experimental work was limited to structures having not more than 16 wires.

Cable terminations

Instruments and components available today for measurements all employ conventional, coaxial connectors and cables, so that the introduction of this new form of multi-conductor, dipole-mode cable requires special arrangements. Not only is a connector required to maintain the continuity of the multi-wire system, but transducers are necessary to convert the TEM waves of the supply to dipole-mode configuration prior to launching the wave on the cable. This operation has to be carried out with minimum loss and over as wide a band of frequencies as possible.

One method of launching into a dipole mode cable is to take the output from a conventional coaxial supply and, using a power divider, split it into as many parts as there are separate wires in the inner

structure of the dipole-mode cable. At the same time the amplitude and phase of each input is adjusted so that when superimposed they comprise the required dipole mode field distribution. This has been tried experimentally but it was found to be difficult to establish and maintain the precise amplitudes and phases required.

A more practical method of launching the required dipole mode from a TEM source is to use either electric or magnetic coupling into the multi-conductor cable. In general, transverse electric field coupling as shown in Fig. 3 gives more effective transfer of power but this tends to be at the expense of bandwidth when compared with the corresponding magnetic coupling shown in Fig. 4. In the electric field coupler (Fig. 3) a transverse wire fed from the coaxial input is located at approximately a quarter of the signal wavelength from a short-circuit termination formed by connecting together all the inner wires and the outer screen. Matching from the char-

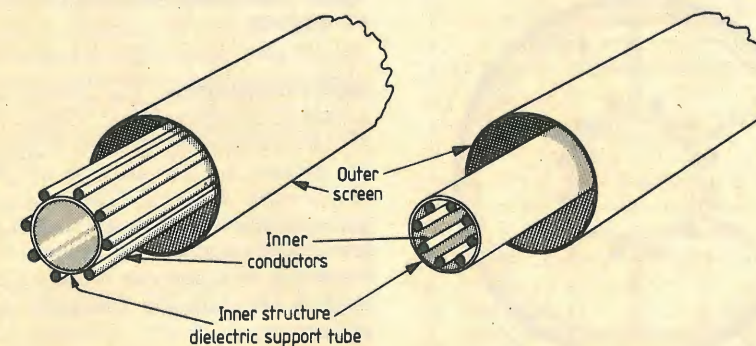


Fig. 2. Two different forms of dipole-mode cable.

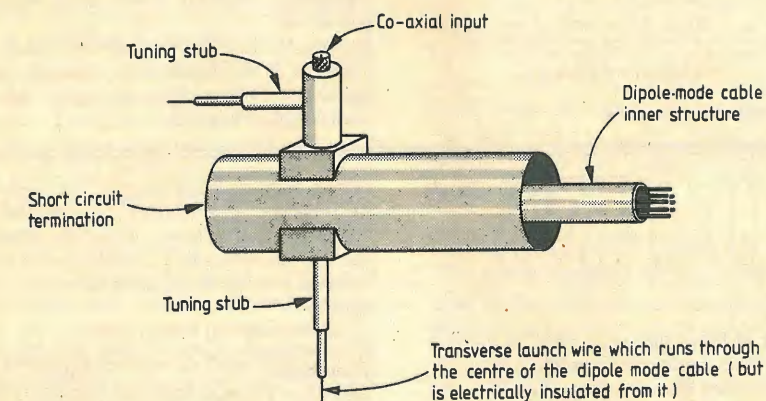


Fig. 3. TEM-to-dipole-mode transducer, using transverse-electric field coupling.

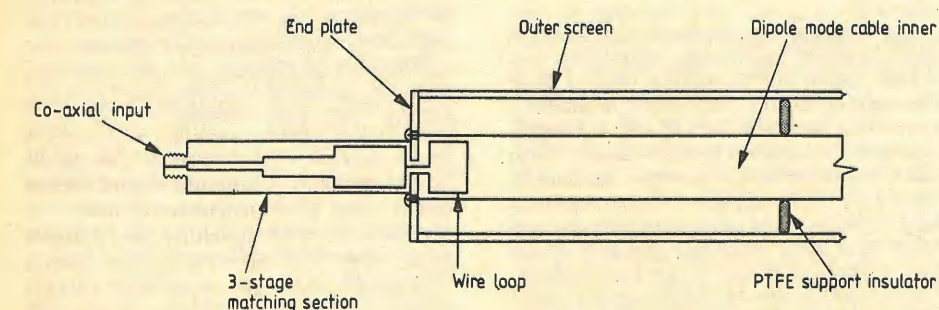


Fig. 4. Cross-section of dipole-mode launcher using magnetic coupling.

acteristic impedance of the coaxial feed to the dipole mode cable is obtained by suitably adjusting the series and shunt pistons shown in the diagram. The magnetic launcher (Fig. 4) is typified by a small loop of wire inserted into the end of the dipole mode cable and extending a short distance from the short-circuited end. A three-section matching unit is used to transform the impedance of the coaxial input down to the very low impedance of the loop. Table 1 shows the loss and bandwidths achieved in practice with these two different types of launcher.

Cable attenuation

Particular interest in dipole mode cables centres on the fact that their attenuation has been shown to be considerably lower than that of an equivalent, conventional coaxial cable. Furthermore, the dipole-mode cable has no cut-off frequency and, unlike a hollow metal waveguide, can be used satisfactorily at quite low frequencies.

Attenuation measurements having been made at various frequencies on two different dipole mode cable structures, both mounted inside a 2.22 cm-diameter copper tube. A simple substitution method was employed, consisting of a direct comparison between the loss of a known length of the cable with that of a back-to-back connexion between two dipole-mode launchers. Joints were made in the cable by employing short, thin, brass tubes to interconnect the individual wires and a sleeve was placed over the break in the outer.

The measured losses are shown in Fig. 5 and, while these display the very low attenuation obtainable, a more interesting result is a direct comparison between dipole mode and TEM losses in the same cable. The dipole-mode cable can be made to operate in the TEM mode, simply by joining them together, at each end, all the inner structure wires and then feeding between them jointly and the outer, as in a conventional coaxial cable. The use in TEM transmission of an inner structure, comprising parallel wires rather than a solid metal conductor, only causes between 7% and 10% increase in attenuation. The results of such a comparison made at a

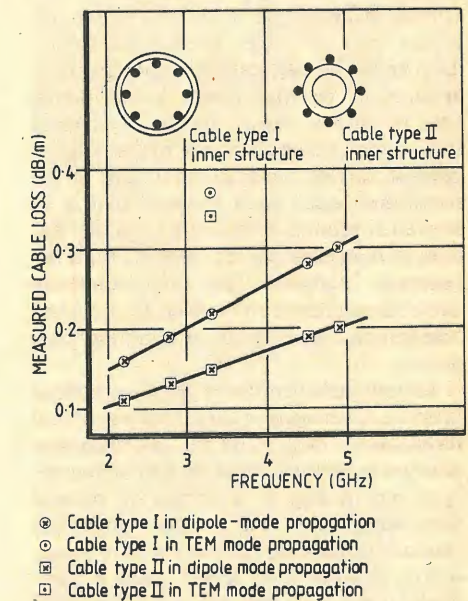


Fig. 5. Measured losses of multi-conductor cable in dipole-mode and TEM-mode transmission.

Table 1. Comparison of available bandwidth and losses for dipole-mode launchers shown in Figs. 3 and 4.

Launcher type	Bandwidth (between 3dB points) MHz	Nominal loss (TEM to dipole mode) dB
Magnetic coupling (see Fig. 4)	500	3.5
Electric coupling (see Fig. 3)	150	0.26

frequency of 3.3GHz on five different forms of cable are shown in Table 2. From these results it is clearly seen that when using an inner structure with a radius of about half that of the outer the losses are reduced to about 50% of those of the same cable operated in the TEM mode.

Practical applications

Optical-fibre transmission seems destined to take a large share of long-distance tele-communications and in due course to displace many of the coaxial line systems. However, there will always be a large number of circumstances in which conventional coaxial cable remains applicable and it is in these areas that the dipole-mode cable could find a useful place. The reduced attenuation characteristics of this cable reflects the more uniform energy-density distribution over the cross-section and the effective use made of the area occupied by the inner structure. Since the breakdown voltage of a cable is directly related to the uniformity of energy-density distribution within the cable, the expectation is that the power-handling capacity of dipole-mode cable will prove superior to that of the corresponding ordinary coaxial cable.

A typical example where this factor, together with the lower attenuation behaviour, could be particularly important is in application to high-power u.h.f. aerial feeders, such as those carrying the output from a television transmitter to the point of radiation. Here the size and weight of the transmitter equipment requires that it be located at ground level while the aerial has to be as high as possible consistent with the coverage required. The interconnecting cable has therefore to be both of considerable length and capable of handling high power.

Various structures have been considered over the development period for a practical dipole-mode cable, and the one that now emerges as likely to be of particular success is shown in Fig. 6. This has 12 parallel wires spiralled around an inner polythene tube and supported centrally within a concentric flexible outer screen using a 'cart-wheel' type dielectric spacer. This cable can be expected to exhibit the required low-loss characteristics while remaining flexible enough for all normal purposes. Joining the cable can be performed in a number of ways, ranging from the simple technique of soldering the individual wires together with small metal sleeves to the construction of a connector arrangement similar to that employed in conventional coaxial cables but with plug-in joints for each of the inner wires. An alternative joining technique has been used in which the separate wires are laid in metallized grooves cut longitudinally in a small length of dielectric tube.

In this new form of coaxial cable, transmitting in a wave mode not previously applied to such a purpose, an important development is foreseen, offering much lower losses, coupled with high-power operation at frequencies up to and including the bottom end of the

Table 2. Comparison of dipole-mode and TEM losses for five different types of cable contained within 2.22cm diameter outer screen.

Cable type number	Wire size (s w g)	Cross sectional view of inner structure	Measured losses at 3.3GHz (in dB/m)	
			Dipole mode	TEM mode
I	18		0.22	0.37
II	18		0.15	0.34
III	22		0.27	0.45
IV	18		0.29	0.39
V	22		0.20	0.36

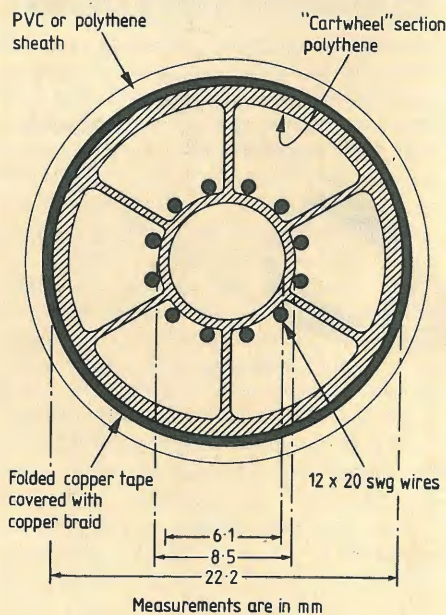


Fig. 6. Dipole-mode cable.

BOOKS

Handbook of Fiber Optics, Edited by Helmut T. Wolf. 558pp, hardback. Granada, £25.00. Ten authors from Germany, Japan and America, collaborated to produce this book, which is on the use of optical fibres in communications: applications for fibres conducting unmodulated light are largely ignored, except in the case of endoscopy.

The book is a concentration of a large body of widely scattered information, and is thus a convenient survey of the subject, with a large number of references. Each author undertakes a review of a particular facet of optical communications (the book was first published in 1979) and there are reviews of research activities in Europe, the USA and Japan. The writing is at a level which would be suitable for engineers and scientists in other disciplines who need to use optical fibres, and could be used by students. For the worker already involved, it is a useful reference source and guide to further reading.

After a long introduction to the subject by the

editor, four chapters describe the components of a system — waveguides, sources, detectors, connectors and switches. These are followed by sections on economics, applications in communication systems and a piece on medical endoscopes.

Acknowledgements. The authors are indebted to Professors A. L. Cullen and E. A. Ash of University College, London, for the facilities made available in the pursuit of this work. They also acknowledge with gratitude the most valuable collaboration provided by Cable & Wireless Ltd., in seconding for a year one of us (S.G.C.) to work full-time in the University on the project.

References

- Barlow, H. M. & Nouri, M., 'New forms of waveguide', *Wireless World*, February, 1976, p.p. 38-40.
Barlow, H. M., 'Multi-conductor coaxial cables operated in the dipole-mode and their possible applications', *Jour. Phys. D: Appl. Phys.*, Vol. 12, 1979, p.p. 321-333.

editor, four chapters describe the components of a system — waveguides, sources, detectors, connectors and switches. These are followed by sections on economics, applications in communication systems and a piece on medical endoscopes.

Ferromagnetic Core Design and Application Handbook, by M. F. DeMaw. 256pp., hardback. Prentice-Hall International, £12.95. The emphasis in the title of this book ought, perhaps, to have been on the applications of cores rather than on their design, since the majority of the text is devoted to very practical information on the specification and use of inductors which employ iron or ferrite cores.

Properties of materials and the physics of cores are covered in the first chapter, the succeeding three being concerned with the use of cores in the forms of rods and bars, toroids, beads, sleeves and pots. Chapter 5 deals with permanent magnetic materials. A good bibliography, a list of references and a number of appendices complete a most helpful book. The circuit diagrams used throughout the book to illustrate the use of cores, and reference to commercial cores by type number are especially useful, though the references are to American components.

6809 evaluation system for £100

Upated Nanocomp and cassette interface

by R. Coates

The 6809 is a recent 8-bit microprocessor which uses a 16-bit architecture to considerably improve the performance available from an 8-bit device. Because development of conventional 16-bit processors is accelerating, many designers think that the 6809 represents the practical limit for an 8-bit device.

Unfortunately, few potential users have been able to evaluate this processor because there is very little hardware available at present and information is still scarce. This design is based on the well-tried and tested Nanocomp (Jan. 81) and provides a useful low-cost evaluation system for the 6809.

The 6809 is the most recent addition to the M6800 family of microprocessors, and provides a much more advanced architecture than the 6802. Internally the device is a 16-bit processor, which can perform 16-bit operations, with several extra registers and other improvements. However, because the device retains an 8-bit external data bus, the hardware is very similar to the 6802 and can therefore be used with a slightly modified Nanocomp.

The improved performance of the 6809 is attributable to several factors besides the potential of 16-bit operations. An important advantage is the addition of extra and more powerful addressing modes which enable the processor to recognize 1464 different variations of instructions and addressing modes from a basic instruction set of 59. Despite this large number of instructions, the improved architecture makes the device easier to program.

To preserve software compatibility with earlier Motorola microprocessors, the 6809 is compatible at source-code level with the 6800 so all but a few of the existing mnemonics are included. Exceptions such as INX have been excluded to maintain as rigidly as possible the regularity of the architecture. Extra addressing modes have been provided for the existing instructions and new instructions, unique to the 6809, have been added. Therefore, source programs written for the 6800 can be re-assembled using the 6809 op-codes. (not all are the same as the 6800) and existing software can be transferred. All mnemonics excluded from the 6809 can be performed by new instructions. Although it may seem pointless to transfer existing software to a more powerful processor, it allows users to upgrade their systems with-

Table 1. Revised memory map

eprom	monitor	7FFF
	user	7C00
	eprom	7800
		7400
		7000
2114 rams	pia	4003
		4000
		13FF
	display buffer	13FA
	monitor workspace	13E0
		13D0
	monitor stack	13B0
	user stack	
	program ram	1000
pia	4000 output/data direction register A	
	4001 output/data direction register B	
	4002 control register A	
	4003 control register B	

out having to re-learn completely.

Branch instructions have been improved by adding 16-bit 2's complement offsets as well as 8-bit. This permits a branch to be made from anywhere to anywhere in the full 64K address range, which makes the writing of position independent programs much easier.

Circuit modifications

The block diagram of this design is identical to the original version except that the 6809 does not have an on-chip r.a.m. and the 128 bytes at address 0000 to 007F are not available. The circuit diagram in Fig. 1 is almost identical to the original and, apart from the obvious change of c.p.u. chip, the main difference is that the 74LS00, which generated the VMA.E signal, is omitted. This i.c. is not required because there is no valid memory address signal on the 6809, and invalid memory addresses are forced to FFFF. The E output can be used directly in place of VMA.E. Another alteration is the provision of an extra interrupt input, the fast interrupt request FIRQ. This input is not used in the present design, but is brought out to a pin for possible future use. Reset on the 6809 has a Schmitt-trigger input which, with capacitor C₉, provides automatic power-on reset. Because the c.p.u. on-chip r.a.m. is not available, the

memory map has been revised and is shown in Table 1. The monitor workspace is now positioned at the top of the 1K memory and therefore about 40 bytes are lost for user programs. All other aspects of the circuit and testing are as described for the 6802 version.

Operation

Operation is more or less the same as the 6802 version. As the monitor software listing now includes cassette-tape handling routines, the full 1K allocated to the monitor program, 7C00-7FFF, is now used. These routines use the L and P keys and are described later. The main alteration to the monitor is the register display command R which has been revised to take account of the increased number of c.p.u. registers. This command is automatically entered after a SWI, but may be re-entered with the R key. The condition-code register contents are first displayed with the right-hand digit denoting the register being displayed as shown,

- C = condition-code register
- A = acc A
- B = acc B
- D = direct page register
- X = X register (index)
- Y = Y register
- U = user stack pointer
- P = program counter
- S = hardware stack pointer

The I key will increment through the various registers, and their contents will be shown on the left four digits. After displaying S, the unit automatically returns to the monitor start. The two new software interrupt instructions, SW12 and SW13, are not used by the monitor but, with the hardware interrupts, the program can jump to and continue from a specified address in certain memory locations. These are listed in Table 2.

When an interrupt occurs, the continuation address is fetched, which is usually the interrupt service routine, and proces-

Table 2. Interrupt jump locations

When an interrupt occurs, an address is fetched from the memory shown and processing continues from that address.

Interrupt	Address
SW13	13E5/6
SW12	13E7/8
FIRQ	13E9/A
NMI	13F2/3
IRQ	13F4/5

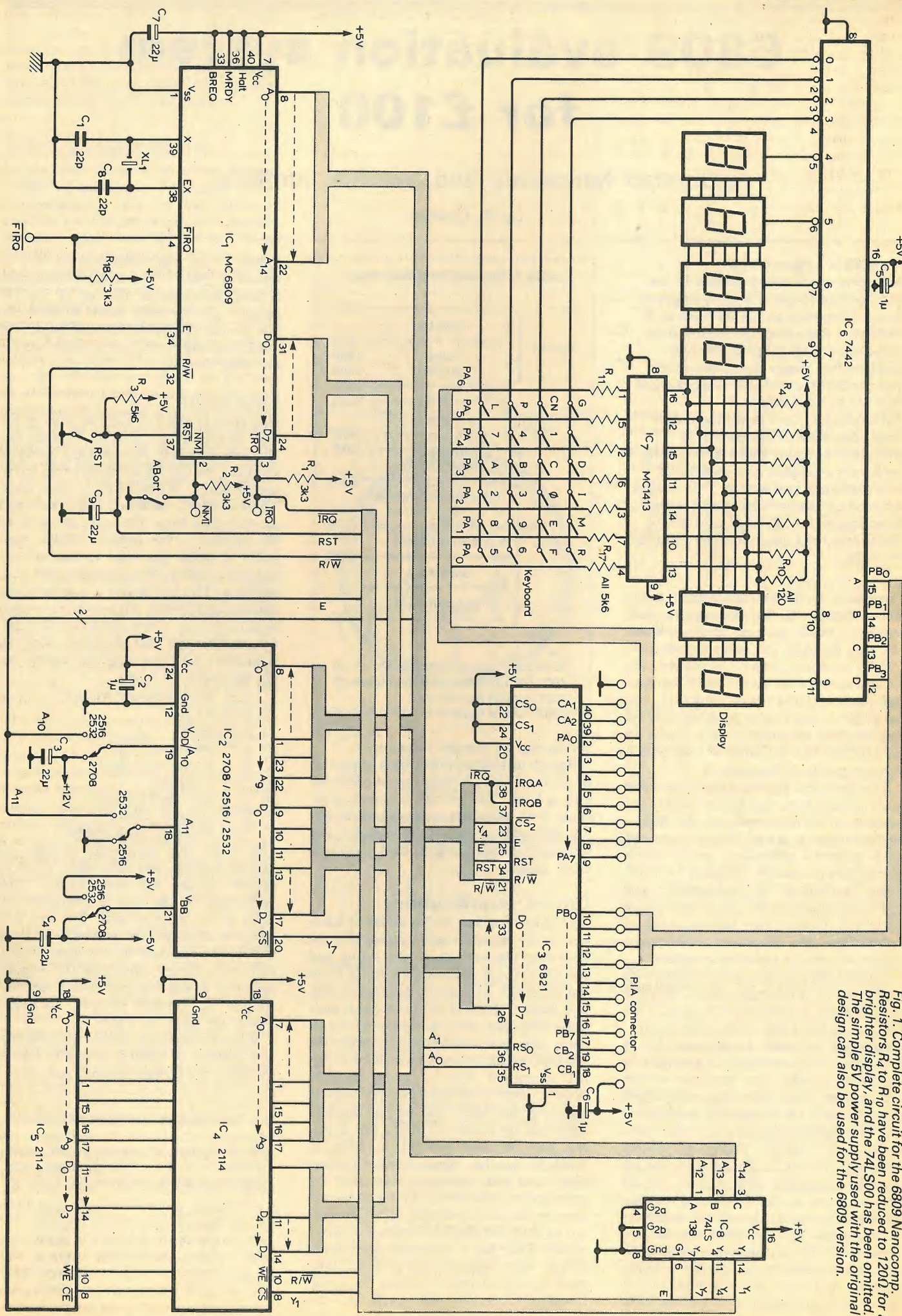


Fig. 1. Complete circuit for the 6809 Nanocomp. Resistors R₁ to R₁₀ have been reduced to 120Ω for a brighter display, and the 74LS00 has been omitted. The simple 5V power supply used with the original design can also be used for the 6809 version.

single continues from that point. The NMI input, however, is used for the abort key and its jump address is set automatically when a reset occurs, but it may be modified for other purposes by a users program. The monitor has been written to ensure that the useful monitor subroutines, listed in Table 2 of the original article, function identically and have the same entry address points. The re-entry point to the monitor from a user program is 7D97, which also applies to the 6802 version.

The four original programs can be included if a 2 or 4K e.p.r.o.m. is used. The start address for hex-decimal/decimal-hex converter is 7800, duckshoot - 7940, branch calculator - 7A00 and mastermind - 7A80. For duckshoot, the speed is set at location 1000 and 1 because there is no memory at 0000 in the 6809 version. Two's complement offsets used by the branch instructions of the 6802 are limited to 8 bits but the 6809 also uses 16-bit offsets, therefore the branch calculator program now caters for these. In addition to requesting the start and destination addresses, the program requests the number of bytes in the instruction, b in the right-hand display, which must be entered. If an instruction has only two bytes, it must be an 8-bit offset so an 8-bit value is given or two dashes if it is out of range.

An instruction which requires a 16-bit offset must be three bytes or more, so a 16-bit answer is displayed if a byte value of three or greater is given.

Programming

Because programming information for the 6809 is not widely available yet, a brief description of the architecture is given together with the instruction set and programming details. However, for serious programming, Motorola's MC6809 Preliminary Programming Manual is essential.

A programming model of the 6809 is shown in Table 3, and details of the registers are given below.

Accumulators (A, B, D)

The A and B registers are general purpose 8-bit accumulators for arithmetic calculations and data manipulation. Some instructions link the registers to form a

single 16-bit accumulator (D) with A as the most significant byte.

Direct page register

The direct addressing mode in the 6800 allows a shorter form of instruction to be used for accessing the bottom 256 bytes of memory. This facility has been enhanced in the 6809 so that the 8-bit direct page register is used as the most significant byte for direct addressing. This allows the direct mode to be used under program control at any place in memory.

Index registers (X, Y)

These are the same as the single 6800 register. The 16-bit address in the register takes part in the calculation of effective addresses and can be used to point to data directly. The address can also be modified by an optional constant or register offset. The 8-bit constant offsets are supplemented with 5 and 16-bit offsets. All four pointer registers (X, Y, U, S) can be used as index registers.

Stack pointers (U, S)

The hardware stack pointer, S, is used by the processor during subroutine calls and interrupts, and points to the top of the stack instead of the next free location as in the 6800.

The user stack pointer, U, allows arguments to be passed to and from subroutines. Both stack pointers can also be used as index registers, and have additional Push and Pull instructions which can operate on any or all of the registers (except themselves).

Program counter

Used by the processor to point to the address of the next instruction to be executed.


Condition code register

This register, also known as the flag register, defines the state of the processor at any time. The register comprises C (bit 0) CARRY. Indicates that a carry occurred on the last ALU operation, or a borrow from subtraction instructions. V (bit 1) OVERFLOW. Set by an operation which causes a two's complement arithmetic overflow.

Z (bit 2) ZERO. Set if the result of the previous operation was zero.

N (bit 3) NEGATIVE. Contains the m.s.b. from the result of the preceding

Table 3. Programming model of the 6809

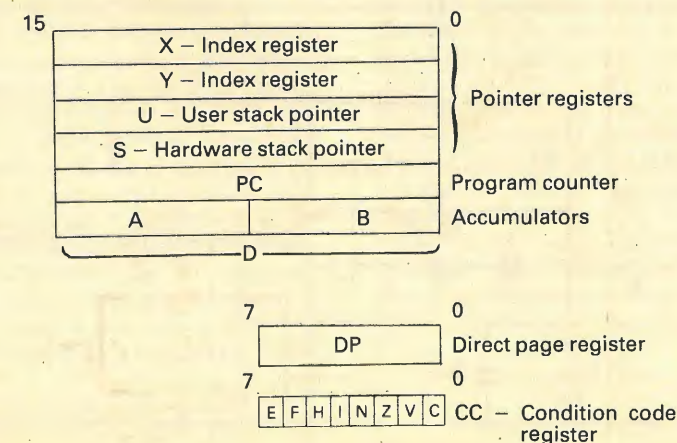

operation. Therefore, a negative two's complement will leave N set.

I (bit 4) IRQ mask bit. Interrupts on this line will not be recognised if I is set. NMI, FIRQ, IRQ, RESET and SWI all set the I bit, but SW12 and SW13 do not affect it. H (bit 5) HALF CARRY. Indicates a carry from bit 3 in the ALU after an 8-bit addition. Used by the decimal adjust instruction to perform the b.c.d. decimal add adjust operation.

F (bit 6) FIRQ mask bit. Interrupts on this line will not be recognised if I bit is set. NMI, FIRQ, SWI and RESET set the F bit. IRQ, SWI and SW13 do not affect it. E (bit 7) ENTIRE FLAG. Used to indicate whether all the registers were stacked or a subset (PC and CC) performed by a FIRQ. The E bit of the stacked condition code register is used on return from interrupt (RTI) to determine the extent of unstacking.

The main improvement offered by the 6809 is the proliferation of addressing modes which are summarised below.

INHERENT. In this mode the opcode contains all necessary address information (single byte instruction).

IMMEDIATE. The data to be used by the instruction immediately follows the opcode in memory. Can be an 8-bit or 16-bit value depending on the instruction.

EXTENDED. The contents of the two bytes following the opcode specify the 16-bit effective address used by the instruction.

EXTENDED INDIRECT. A special case of indexed addressing where one level of indirection is added to extended addressing, ie, the two bytes following the postbyte of an indexed instruction contain the address of the address of the data.

DIRECT. Similar to extended but only the lower 8 bits of the effective address are specified in the byte following the opcode. The upper 8 bits of the effective address are supplied by the direct page register. Therefore, programs using this mode rather than extended will use less memory.

INDEXED. The most complex addressing mode. In all indexed addressing, one of the pointer registers (X, Y, U, S and sometimes PC) is used in a calculation of the instruction. The postbyte of an indexed instruction specifies the basic type and variation of addressing mode, and the pointer register to be used. Table 4 gives the details necessary for calculating the postbyte opcode for all forms of indexed addressing. The five basic types of indexing are Zero Offset. The selected pointer register contains the effective address of the data to be used by the instruction.

Constant Offset. A two's complement offset and the contents of one of the pointer registers are added to produce the effective address of the operand. The pointer register's initial content is unchanged by the addition.

Three sizes of offset are available, ± 4-bit (-16 to +15), ± 7-bit (-128 to +127) and ± 15-bit (-32768 to +32767). The 5-bit offset is included in the postbyte, whereas 8-bit and 16-bit offsets require 1

Table 4. Indexed addressing modes

Type	Forms	Non indirect				Indirect			
		Assembler form	Postbyte op-code	+	#	Assembler form	Postbyte op-code	+	#
Constant offset from R (signed offsets)	no offset	R	1RR00100	0	0	[R]	1RR10100	3	0
	5-bit offset	n, R	0RRnnnnn	1	0	defaults to 8-bit			
	8-bit offset	n, R	1RR01000	1	1	[n, R]	1RR11000	4	1
	16-bit offset	n, R	1RR01001	4	2	[n, R]	1RR11001	7	2
Accumulator offset from R (signed offsets)	A - register offset	A, R	1RR00110	1	0	[A, R]	1RR10110	4	0
	B - register offset	B, R	1RR00101	1	0	[B, R]	1RR10101	4	0
	D - register offset	D, R	1RR01011	4	0	[D, R]	1RR11011	7	0
Auto increment/decrement R	increment by 1	,R+	1RR00000	2	0	not allowed			
	increment by 2	,R++	1RR00001	3	0	[,R++]	1RR10001	6	0
	decrement by 1	,-R	1RR00010	2	0	not allowed			
	decrement by 2	,--R	1RR00011	3	0	[,--R]	1RR10011	6	0
Constant offset from PC	8-bit offset	n, PCR	1XX01100	1	1	[n, PCR]	1XX11100	4	1
	16-bit offset	n, PCR	1XX01101	5	2	[n, PCR]	1XX11101	8	2
Extended indirect	16-bit address	-	-	-	-	[n]	10011111	5	2

R = X, Y, U or S X = 00 Y = 01 X = don't care U = 10 S = 11
+ and # indicate the number of additional cycles and bytes for the particular variation

or 2 bytes respectively after the postbyte for the offset.

Accumulator Offset. Similar to constant offset indexed except that the two's complement value in one of the accumulators (A, B or D) is used as the offset, the postbyte specifies which. Neither register is altered by the operation.

Auto Increment/Decrement. Similar to zero offset, but with auto increment. After the pointer register is used it is incremented by 1 or 2 and then used.

Indexed Indirect. All indexing modes, except auto increment/decrement-by-one and 5-bit offset, can have an additional level of indirection. This means that the effective address is contained at the location specified by the content of the index register plus any offset.

RELATIVE. Branch instructions use the relative addressing mode, i.e. the byte(s) following the branch opcode is a signed offset which is added to the program counter. If the branch condition is true, the calculated address (PC + signed offset) is loaded into the program counter. Execution then continues from the new address. Short branches require a 1-byte offset and long branches require 2 bytes.

PROGRAM COUNTER RELATIVE. Another type of indexed addressing where the program counter is used as the pointer, with an 8 or 16-bit offset. This is very useful for pointing to blocks of data in a program which must be relocatable, i.e. runs anywhere in memory. The Load Effective Address instruction makes use of this mode. For example, to point the X register to a block of data by specifying an offset, relative to the current PC position, where the data block resides. This offset

will remain constant wherever the program is run, whereas with a LDX instruction the absolute address must be specified. An additional level of indirection is available with this mode.

New instructions

PSH/PUL. These instructions allow any combination of registers to be pushed onto or pulled off the hardware (S) or user (U) stack. Which registers are pushed or pulled is defined by an immediate byte

after the opcode. Each bit in the byte specifies a register.

C C = bit 0
A, D = bit 1
B, D = bit 2
D P = bit 3
X = bit 4
Y = bit 5
U, S = bit 6
PC = bit 7

TFR/EXG. Any register may be transferred or exchanged with any other register of the same size, i.e. 8-bit to 8-bit or 16-bit to 16-bit. Also, a 16-bit register can be transferred to an 8-bit. The registers to be

Fig. 2. Cassette interface. This circuit is powered from the Nanocomp via the p.i.a. connector.


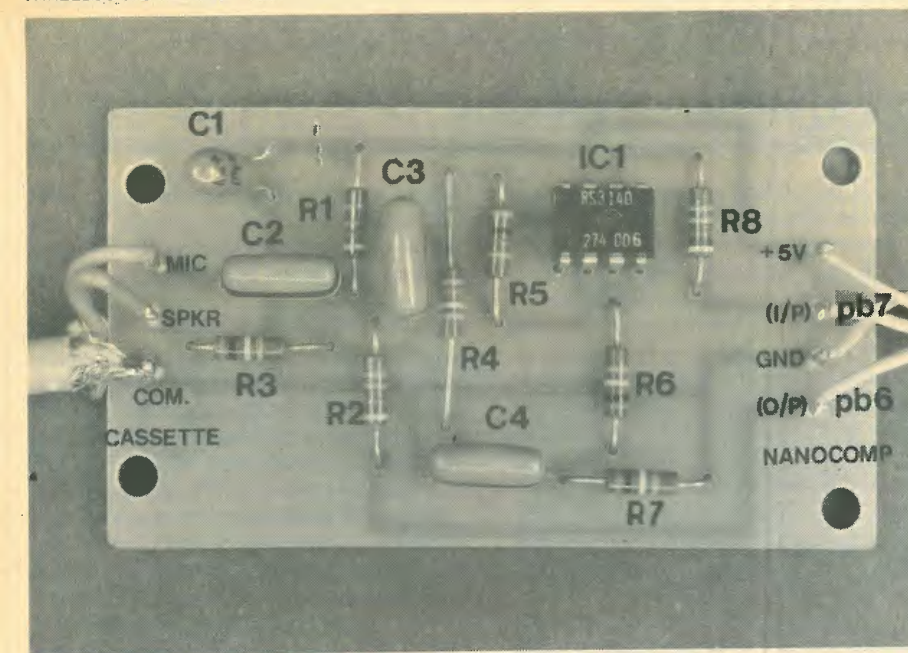
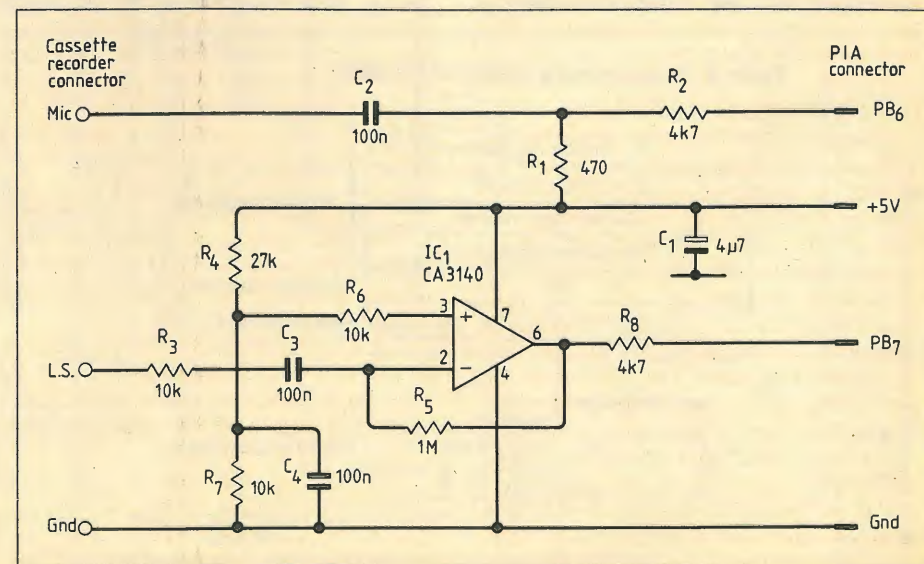


Fig. 3. Layout and component placement for the cassette interface.

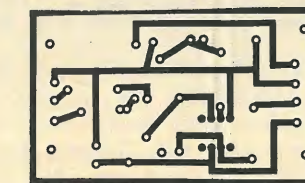

transferred are specified in an immediate byte. A code contained in the most significant four bits specifies the first register and the least significant four bits specify the second.

The register codes are

0000 = D
0001 = X
0010 = Y
0011 = U
0100 = S
0101 = PC
1000 = A
1001 = B
1010 = CC
1011 = DP

MUL. Multiplies the unsigned binary numbers in the A and B accumulators and places the unsigned result into the 16-bit D accumulator.

Although this short account of the 6809 is by no means complete, it should enable the constructor to start programming this very powerful processor.

Cassette tape interface

One facility which is more or less essential with any computer system is a means of storing programs. The cheapest convenient method of storage is a cassette tape and, as most users will have access to a cassette recorder, all that is required is the appropriate interface and software. This simple interface can be used with either version of the Nanocomp and will load the 1K memory in about 15s. An important part of the tape storage system is a set of routines, so readers using the original monitor will need to reprogram their e.p.r.o.m.

Data to be stored is transmitted to the recorder from a p.i.a. output line in the usual asynchronous serial format of a start

stranded wire can be used and soldered onto the connector.

Operation

The L and P keys are used to load and dump data respectively. To save a program, key P and the display will request the start address of the memory block to be saved S, followed by the finish address F. Transmission will start immediately the last key is released, so the recorder should be started before this. When the recording is finished, F will appear in the left of the display which indicates that the recorder can be stopped. Abort or Reset will return the monitor prompt.

To load a program, key L and start the recorder just before the beginning of the program. To provide a form of feedback, the top and bottom segments of the lefthand display are turned on as data is received. When a 1 is received, the top segment is on and when a 0 is received, the bottom segment is on. If the program is loaded correctly, when the end-of-file code is received F is displayed. Abort or Reset returns the prompt. If a checksum error is encountered in one of the data blocks, a C is displayed and loading is stopped. If this occurs the tape must be rewound and restarted.

With some experimentation the record and playback levels can be optimised although, with a reasonable recorder, they are not critical. It should be noted that the requirements for recording data on a cassette tape are high so only high quality audio cassettes or, preferably, certified data quality should be used. Also, a worn recorder which does not give an acceptable performance with speech or music is unlikely to produce reliable data recordings. Auto record-level machines may also cause problems because their circuits are not designed to be used with a low mean-to-peak ratio square wave.

Although the Nanocomp was originally intended as a microprocessor trainer, many constructors may want to update the unit as shown, and interface the circuit to other systems. We intend to support this design with a further article describing extra peripheral devices such as a-to-d and d-to-a converters and a simple e.p.r.o.m. programmer.

The original monitor/utility program has been revised to remove a potential bug in the master mind program, and to improve the performance if poor quality keys are used. A hex list of the new monitor, which also contains the cassette interface software, can be obtained from the editorial office by sending a large s.a.e. clearly marked 6802 or 6809.

A set of p.c.b.s for the 6809 Nanocomp (power supply and logic board) will be available for £9.00 and a cassette interface board for £1.50, inclusive of v.a.t. and UK postage, from M. R. Sagin, 23 Keyes Road, London N.W.2.

Technomatic Ltd, 17 Burnley Road, London N.W. 10, 01-452 1500, and Magenta Electronics Ltd, 135 Hunter Street, Burton-on-Trent Staffs, 0283-65435, will be offering a kit of components. Both companies will also reprogram e.p.r.o.m.s for both versions of the Nanocomp.

+5V 7a
0V 2a
PB6 12a
PB7 12b

If a ribbon cable is not available, ordinary

WORLD OF AMATEUR RADIO

CB — so close to 28MHz

One factor arising from the Home Office's draft 'performance specification' for 27MHz f.m. equipment, for what is now officially termed the "Citizens Band Radio Service", will be viewed with some dismay by many radio amateurs: the minimal frequency gap between "Channel 40" (27.99125MHz nominal carrier frequency) and the 28.000MHz low-frequency end of the 28MHz amateur band. This represents an unexpectedly savage turn-down of the RSGB request that any such service should not be located close to an amateur band.

It can be argued of course that if c.b.ers stick to the proposed conditions — for example that all equipment must be covered by a licence of which it will be a condition that "the apparatus fulfils, and is maintained to, certain minimum technical standards" — then there may be few problems. But there seem certain to be "social problems" when licensed c.b.ers find, as almost certainly they will, that their low-power, low-cost rigs cannot be expected to function satisfactorily when one of their neighbours is legally running a 28MHz amateur transmitter at 150 watts d.c. input or 400 watts p.e.p. output only a few kHz away from the c.b. channel!

Although the latest Home Office plans have received a good deal of criticism one cannot help feeling that if the same proposals had been made several years ago they would have been warmly welcomed by almost all those interested in the development of c.b. What remains to be seen is whether the proposed regulations will be obeyed or enforced.

For example, it is difficult to imagine even an otherwise conscientious c.b. operator actually taking care to insert a 10dB attenuator when using a high aerial!

Amateur television

The latest issue of *CQ-TV*, journal of the British Amateur Television Club, reports an increasing number of television contacts with Continental amateurs. Andrew Emmerston, G8PTH, of Canterbury mentions his successful reception of lockable SE-CAM colour transmissions from F1EDM at Le Havre. Several British amateurs are experimenting with video transmissions on the 1.3 and 10 GHz bands. In Melbourne, Australia a television repeater accepts signals on 440MHz and retransmits them on 579MHz and can thus be received on unmodified domestic television receivers. In the USA the FCC is continuing to permit a handful of amateurs to experiment with "medium scan television" on 29.150MHz with a maximum bandwidth of 36kHz. This concession is resulting in the exploitation of a number of novel techniques, including frame grabbing at an eighth of the 60 fields per second of standard American television. It has been found that at least

7.5 fields per second are needed to give a reasonable illusion of movement. One of the amateurs concerned in this work (W3EFG) was the originator, several years ago, of the General Electric (USA) "Sampledot" narrow-band system and plans are now being made to use some of the original Sampledot equipment in conjunction with a digital scan converter and frame grabbing to provide a 7.5 rather than 60 Hz field rate.

Slow-scan land and sea image data with a format of 256 by 256 pixels and 16 grey levels with digital transmission on the beacon signal at 145.825MHz are among the facilities that will be provided by the British amateur satellite UOSAT (University of Surrey) due to be launched in a few months time. UOSAT will carry an earth-pointing c.c.d. two-dimensional imaging array.

Amateurs at British Telecom's research centre at Martlesham are planning tv transmissions both for local "news" and for regular contacts with Holland. BATC deserves congratulations on the new "Amateur-Television Handbook" edited by John Wood, G3YQC and Trevor Brown, G8CJS. This excellent 96-page booklet is packed with eminently practical information and designs provided by some 20 amateurs and covering principles, aerials, receivers, transmission, vision sources, video processing and colour television (non-members £2 plus 35p postage from I. Pawson, 14 Lilac Avenue, Leicester LE5 1FN).

IARU Region 1 Conference

The many sessions of the IARU Region 1 Conference at Brighton, at which the national amateur radio societies of some 36 countries were represented among the 150 or so delegates, resulted in many recommendations that in the coming years should help to make as effective as possible both operating and technical investigations. But less happily this conference will also be remembered for the deaths of two of the delegates: Peter Balestrini, G3BPT and the Dutch amateur PAoOK. Peter Balestrini was the 1980 President of the RSGB and was attending the conference in his capacity of RSGB Emergency Communications Manager. Professionally engaged with Port of London Authority telecommunications, he was for many years one of the leading enthusiasts who built up the "Raynet" emergency system.

Although there can be few amateurs who did not wish the Conference well, some criticism has been expressed of the Home Office decision to permit the use of a special call sign, GB1IARU, since the use of "four-letter" call signs is not specified in the international Radio Regulations. However the Home Office clearly regarded

this as a very special "special event" and even gave blanket permission for the station to be operated by foreign delegates not holding a reciprocal British licence.

April solar storms

Highly disturbed h.f. propagation conditions were experienced during April, particularly during the periods April 7 to 13 and April 21 to 27, following intense solar flares. On some days F2 critical frequencies remained abnormally low and on April 13 between 0600 and 1700 hours the F2 layer was not detectable at The Appleton Laboratory, and the amateur h.f. bands remained virtually unusable during much of the day. A considerable number of severe h.f. blackouts and auroral conditions were experienced during the month. Such ionospheric disturbances tend to take place most frequently during the early decreasing phase of a sunspot cycle, but the events of April were unusual by almost any standard.

Observations made on 3.5MHz by G3XRJ and VK7AE in Tasmania, Australia during an eclipse of the sun on February 4 around 2030 hours showed a very marked enhancement of this low h.f. path between England and Australia during the total eclipse period. The effect, during the Australian "dawn", was to keep the path open almost an hour longer than normal, although there was a very rapid fadeout of signals after the sun re-emerged.

In brief

A weekend 'Hamfest' from Friday to Sunday, 26-28 June, is being organized by the Leeds & District Amateur Radio Society, opening with a "welly disco" and with arrangements for overnight camping and caravan facilities. A demonstration station, GB2WYR, will operate . . . The RSGB's v.h.f. national field day, probably now the biggest UK contest event of the year, is on July 4 to 5 . . . Mobile rallies include three on June 28: Longleat Park, Warminster, Wilts; Rolls Royce Sports and Social Club, Barnoldswick; and Crawfordsburn Scout Camp, Crawfordsburn County Park, near Bangor, Co. Down; July 12 Droitwich High School, Droitwich; July 19 Brighton Raceground, Brighton and Cornwall Technical College, Pool, Camborne. . . Abuse of the South London 144 MHz repeater continues, including the weekend of the Brixton disturbances . . . J.T. Dolan of Seattle, USA, was fined \$750 for operating the pirate broadcast station "RX4M Voice of Clipperton" after FCC engineers traced him using sophisticated mobile direction finders. In California, David Lee Grimm was fined \$1500 for illegal c.b. operation after repeated warnings and equipment valued at about \$8000 seized, including four linear amplifiers, two amateur radio transceivers and one c.b. radio transceiver. **PAT HAWKER, G3VA**

Leap seconds

Story of the transfer from astronomical to atomic time


by L. Essen, D.Sc., F.R.S.

Most people now know that all time measurements and time signals throughout the world are based on atomic clocks but the need to adjust them by one second at the end of the year is not well understood. It follows from the fact that the signals must not only give precise uniform intervals of time but must also give the time of day which is determined by the non-uniform rotation of the earth. The transfer from astronomical to atomic time and the co-ordination of the two systems was an important step in the advance of science and it is surprising that the full story has never been told. The requirements of radio engineers were always prominent in the discussions.

The time of day is not required very accurately for civil purposes — it is changed by an hour, twice a year — but for navigation at sea it should be fairly close to the time scale based on the position of the stars, known as UT1. Time intervals, on the other hand, are required to be as precise and uniform as possible, particularly for air navigation and the control of the frequencies of radio transmitters. For these applications the actual time or epoch of the signals is irrelevant.

These two requirements are so different that it might be asked why two separate sets of signals are not used, giving astronomical time for sea navigation and civil purposes and atomic time for everything else. This was indeed suggested by Dr G.M. Clemence of the US Naval Observatory who proposed that two units of time should be defined, adding, probably not very seriously, that the atomic unit should be called the Essen. The fundamental objection to this is that it would constitute a duplication of one of the basic units of measurement; and a practical objection is that the use of two time scales would undoubtedly lead to confusion, as our experience with standard frequency transmissions had shown. It was therefore worth while to make an effort to construct a single time scale, which would give the full accuracy of the atomic clock and the time of day as accurately as needed. This principle was accepted but it took 16 years to get international agreement on the details.

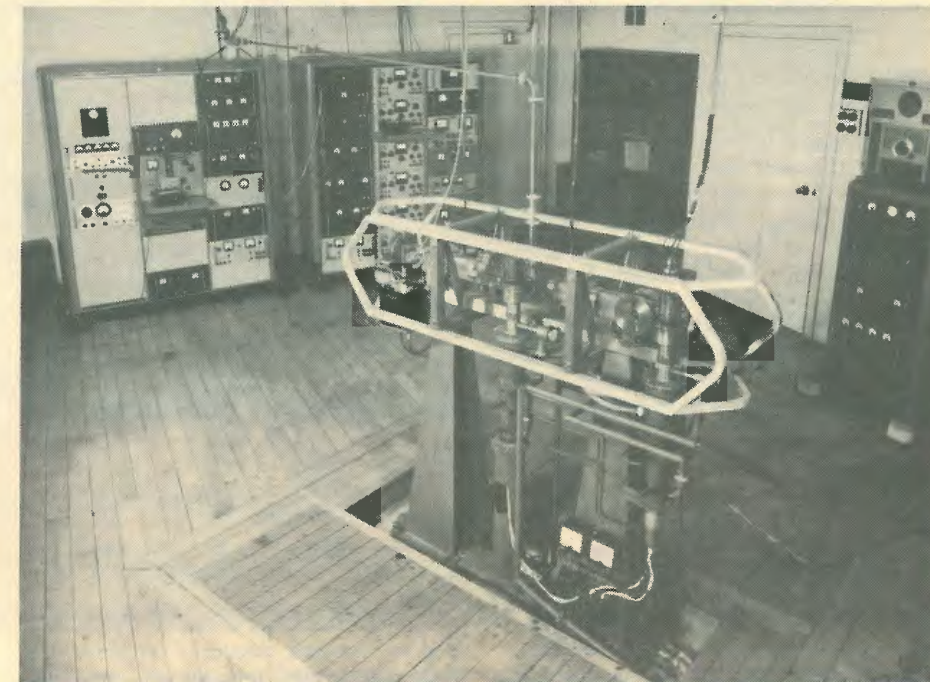The first caesium atomic clock was put into operation at the National Physical Laboratory, Teddington, in June 1955; and it was immediately obvious to us that



The original caesium resonator, designed at the NPL by the author and J. V. L. Parry, which led to the development of the atomic standard of time.

the necessary checks on its performance under different conditions could not be made in terms of astronomical time. A provisional atomic unit was defined and an atomic scale maintained by quartz clocks checked by the atomic clock, under standard conditions, as often as necessary.

It happened that the International Astronomical Union was meeting in Dublin that summer and through the courtesy of the Astronomer Royal, Sir H. Spencer Jones, I was able to attend this meeting to describe the clock and the initial results. One of the main topics of discussion at the meeting was a proposal to redefine the unit of time, making it in effect a fraction of the time of revolution of the earth round the sun instead of a fraction of the time of rotation on its axis. It was believed that this unit, the second of ephemeris time (ET) would be more constant than the second of universal time (UT1). It is difficult to measure it and the value being

recommended was in effect the average value of the second of UT1 over a period of 200 years. Such a unit might be useful for astronomical work but it is not of the slightest use to the physicist and radio engineer. I suggested that it might be wise to delay a decision until agreement was obtained on the definition of an atomic unit which would certainly be required in the future.

However, the proposal to change to ET was adopted and was confirmed at the General Conference of Weights and Measures in 1956. It was a strange decision and it meant that from 1956 until 1967, when an atomic unit was defined, the definitive unit of time existed only on paper. The unit used in practice was the second of UT1; and at the NPL this was defined in terms of the provisional atomic unit, which was made available throughout the world by our standard frequency transmissions and their 1s timing pulses derived from the standard. These were used at the International Bureau de l'Heure to smooth out the irregularities of the astronomical signals.

Although the atomic clock had a luke-warm reception at the Dublin meeting an important resolution was passed with the advocacy of Dr W. Markowitz. It was agreed that when the relationship between the atomic frequency and the second of ET had been established the atomic clock

The next leap second will be on 30th June 1981 in the last minute of the day. The minute before midnight will contain 61 seconds instead of 60 seconds.

would be used to make ET available. We planned together a programme of measurements to obtain this relationship: the time interval between certain agreed signals about a month apart was to be measured at the NPL in terms of the atomic clock and at the USNO in terms of ET. Markowitz had developed a method of obtaining ET more quickly than by direct observations of the sun; but even so the measurements were continued for three years before it was decided that further averaging was not likely to improve the accuracy of the result which was therefore announced. The result expressed as the frequency of the caesium atomic transition in terms of the second of ET was:

$$9192631770 \pm 20 \text{ cycles}$$

The second of atomic time was therefore the time occupied by 9192631770 cycles of the caesium line, the limits of error being omitted since they were due almost entirely to the astronomical measurements. This value was used at the NPL in place of the provisional value, from 1958, in accordance with the Dublin resolution.

There was still strong opposition from astronomers to the formal adoption of the atomic unit. They regarded the atomic clock as a kind of superior quartz clock which could be used to smooth astronomical time, and ignored the fundamental difference between them. The quartz clock is simply a stable oscillator which can be adjusted to have any frequency by altering its dimensions, whereas the atomic clock has a frequency determined with great precision by natural constants. It is reproducible anywhere in the world and provides a unit of time which is immediately and readily available. It is ideally suited to be a definitive standard of measurement. It must be admitted, as was often pointed out, that unlike the earth, it does sometimes stop, but this is an academic point of no practical significance. When one clock stops it can be reset by reference to one that has not, with a precision enormously greater than any astronomical mea-

surement. And even if they all stop they can be reset by reference to the stars so that one is no worse off.

It must be remembered too that the major observatories, including the Royal Greenwich Observatory, were founded with the specific object of providing the navy and merchant ships with time. Their responsibility was later extended to providing a uniform time scale for scientific purposes. The determination of astronomical time became a complex operation, the measurement made at many observatories being correlated at the Bureau de l'Heure which published the definitive corrections to time signals about 12 months in arrears. There was a considerable vested interest in retaining astronomical time as the definitive system. As several of those concerned jokingly said, there was no doubt that we must change to atomic time, but not before we retire, please.

Another question to be settled was the type of atomic clock to choose. In spite of the known performance of the caesium standard at the NPL and then at laboratories in Canada, the USA, and Switzerland, clocks based on the same spectral line of hydrogen and thallium were possible contenders. A lot of attention was also devoted to the study of a spectral line of ammonia; and although this was never a serious contender as a time standard it led to the development of the maser and the laser. The advantages of the caesium clock prevailed and in 1967 it was accepted for defining the unit of time, with the value given above.

The co-ordination of the 1s pulses carried on standard frequency transmissions with astronomical time signals presented some awkward problems. The first step was taken when they were made to coincide on 1st January 1958. It was realised that they would diverge because of the variations in the rate of rotation of the earth, and the question to be resolved was the amount of divergence that could be tolerated. The first figure suggested was

0.1s and to keep within this tolerance the actual frequency of the transmissions was offset from its nominal value by a stated amount each year, and in addition occasional step adjustments of 0.1s had to be made to the timing pulses. A further move towards co-ordination was made in 1960 when it was agreed with the RGO that all time signals transmitted from the UK would have the same epoch.

It was of course rather illogical to offset the constant unit in order to accommodate the variations of the astronomical unit and strong efforts were made to end this situation particularly through the International Scientific Radio Union. A satisfactory solution became possible when astronomers agreed that the signals could diverge by as much as 0.7s from astronomical time UT1. The frequency offset was eliminated, standard frequency transmissions operated on their true nominal values and the timing pulses on them gave true atomic time intervals. The divergence of the pulses from UT1 was compensated by a step adjustment of precisely 1s, when necessary on 30th June or 31st December. This enabled the pulses to continue undisturbed but the marker distinguishing the 1 minute pulse was moved along by 1s. The use of these leap seconds enables the time signals to be maintained within 0.7s of UT1, and for those who need it, the difference from UT1 is given more accurately by a code or Morse announcement. The only inconvenience caused to those measuring time interval is the need to check whether there have been any leap seconds if the interval extends through June or December. The astronomer no longer had to struggle to derive a uniform time scale from the complex and non-uniform periodicities of the solar system, but could measure these periodicities in terms of the atomic clock.

If I may finish on a personal note, I often think how lucky I was to work in a branch of science which was advancing rapidly, which exploited many different techniques and in which there was full international co-operation. The problem being tackled at the NPL when I joined in 1929 was the measurement of radio frequencies. The first solution was to measure them in terms of a tuning fork maintained in continuous oscillation. The accuracy achieved was 1 part in 10^7 which was considered by the Radio Research Board to be adequate for the foreseeable future, making further financial support unnecessary. The next advance was the quartz clock, which proved to be much more stable than the observatory pendulum clocks and gradually replaced them. They revealed an annual periodic change of 1 part in 10^8 in the rate of rotation of the earth. It was clear that any further improvement was prevented by the uncertainty in the value of the astronomical second. In 1945 I.I.Rabi, at Columbia University, suggested that the atomic beam magnetic technique might be adapted to form the basis of an atomic unit of time. The atomic clock has not only made the measurement of time and frequency far easier but has increased its accuracy by about one million times.

Parallel-tracking pickup arm modifications and improvements



Construction is not as difficult as you might think: "precision assembly is simply not required"

By Rod Cooper

A working model of the parallel-tracking pick-up arm, first described in the December 1979 and January 1980 issues, drew widespread interest at a recent exhibition as well as several constructive proposals for improvements, some of which are detailed in this article.

Two curious facts emerged from a showing of the parallel-tracking arm at the last Breadboard exhibition. Firstly, many people expressed doubts about their ability to construct an arm with sufficient accuracy, even when building from a kit of parts. This problem seems to have magnified out of all proportion. The parallel-tracking arm is far more tolerant of mechanical shortcomings in construction because of the "cleaning-up" effect of the servo system, and because of this particular design of gimbals, the inherent advantages of which were explained in the original article.

In addition, as the basic accuracy of the servo system is ± 0.2 degrees which represents about 1mm at the stylus, precision assembly is simply not required. The human eye is very good at detecting parallelism and it is therefore not at all difficult to set up the reference arm and parallel track to well within this limit using an ordinary set-square and a straight rule.

Moreover, the parts have specifically been designed to be adjusted — they are

not pre-set — and so any error in assembly can be adjusted out. The wear points such as bearings and pivots have been given particular attention in design so that any slack introduced by wear can also be adjusted out. It is salutary to compare this to the lack of serviceability and the built-in obsolescence of much of the equipment on the market today.

The second emergent fact was that the principle of parallel tracking had been dismissed out-of-hand, even by those who had read the original article and the analysis by Randhawa on the grounds that "it only saves 0.7% distortion, which isn't audible anyway". Nothing could be further from the truth! There is in fact not one isolated advantage to this technique but a package of benefits as listed below.

- Reduction of tracking distortion, as already mentioned.
- Reduction of stereo delay-distortion with elliptical styli.
- Capability for re-centering eccentric records. This deserves some comment as the design is the only one, as far as I know, which permits rapid and accurate correction of eccentricity. There are two important effects of eccentricity. On some types of music, the "wow" introduced by this defect is audible. That re-centering makes an audible difference I know to be true, from results obtained from my record collection. Also, the eccentric record is constantly levering the arm to the left and right every revolution, working against the

inertia of the arm and the friction of the pivots. Unfortunately the audible effects of wear from this source cannot yet be quantified, but the loading on the record surface can be calculated in a similar manner to that given later in this article for record warp, and is not negligible.

●Low inertia of the arm means that seriously warped records, eg 6mm warp, can be tracked. The benefits gained by low inertia are similar to those achieved from re-centering the record — reduced wow and record wear. Again, the audible effects of wear are not quantifiable, but an analysis of the loading due to inertia is given at the end of this article.

While the reduction in tracking distortion is probably not audible on its own to most people, when it is added to the audible effects of the other three points, the result is noticeable. Add to this the increased "trackability" and reduction in record wear, and the parallel tracking technique can be justified on all grounds except that of cost. And the cost factor can be reduced to a minimum by building your own!

Improvements

Pivot system. On the original design, the cup-type horizontal pivot tended to be a natural collector of dust. By inverting the cup and placing the pivot pin underneath, this problem can be avoided. However it is then no longer possible to use the pivot height adjustment to help correct for neu-

Louis Essen was born in 1908 and educated at High Pavement School in Nottingham and Nottingham University College, gaining a London external degree. Joining the NPL in 1929, he worked with D. W. Dye on tuning-fork and quartz oscillators and has continued to investigate frequency standards throughout his career. Working with A. C. Gordon-Smith from 1946 to 1950, he was able to establish, using a cavity resonator, a new value for the velocity of light, which is still accepted.

Taking up a proposal by I. I. Rabi in the United States, Dr Essen collaborated with J. V. L. Parry at the NPL to produce, in 1955, the first atomic caesium frequency standard: a later design now serves as the British national standard. Work in this field brought an involvement with relativity, which led to a belief that Einstein was wrong in one important respect and to a different interpretation of the Michelson-Morley experiment.

Dr Essen gained a Ph.D in 1941, a



D.Sc. in 1948 and was elected FRS in 1960. He was awarded the Popov Gold Medal of the USSR Academy of Sciences in 1959 and, in the same year, the OBE.

tral equilibrium as suggested in the January 1980 article because the effective height of the tracking arm above the horizontal pivot cannot now be altered. This is not so important as it might seem because the majority of modern cartridges can be set up for neutral equilibrium without having to resort to adjusting the horizontal pivots. With heavier-than-usual cartridges which cannot be set up by adjusting the vertical pivot, filing away some metal from the underside of the counterweight will help.

Light slit. The light slit is also the cue rest, but it can also be adapted to perform a third function as dust bug. It is in the perfect position to do this as a brush attached to the light slit will clean the record just in advance of the stylus. It can be raised for cleaning simply by cue-ing the arm, and as it is earthed can be used to remove static by incorporating carbon fibres in the brush.

Lead-out wiring. Litz wire can be used to greater effect than first realised. Because individual strands of litz wire are insulated it is possible to conduct most of the signals in just a couple of wires. The soldering technique for such fine wire is more demanding, but the unwanted forces introduced by the lead-out wires at the point where they exit from the tracking arm are reduced, considerably.

Tracking arm. The diameter of the duralumin tube used for the tracking arm has been increased to 9.5mm. The original smaller-diameter tubing performed well with most types of cartridge, but with the increased use of moving-coil cartridges I felt that a much stiffer tube was needed. A comparison of the new arm with a conventional arm is given at the end of this article.

Slider (part 19). The material now recommended for this part is Nylon 66, which is a high-tensile grade of nylon and has far superior low-friction and low-wear properties compared with the original brass/steel

arrangement. It is also very easy to cut to shape.

Drive cords. A superior material has been found in the form of round-section expanded neoprene cord. This is a soft, resilient cord which has excellent vibration absorbing properties, and which is designed to be joined with cyanoacrylate "super-glue" to form a fitted drive band.

Acoustic isolation of the servo motor and gearbox was neatly solved by the introduction of Sorbothane. This is a remarkable visco-elastic compound (modestly described by the manufacturer as "a significant advance in polymer technology") which can recover from deformations of more than 500% and which is very lossy to any mechanical excitation, typically 90% absorption. The texture is somewhere between that of plasticene and soft rubber. Used as mounting pads for the servo assembly in place of the rubber grommets first specified, it gives superior results. It is also an excellent material for decoupling the counterweight.

Gimbals. On the original model, if the horizontal pivot of the gimbals was knocked off the support pillars, there was nothing to stop them from going completely adrift. The design of the support pillars has therefore been modified to incorporate the pivot pins in a U-shaped recess so that this cannot happen. The improved design is shown on page 43.

Fast traverse. The criticism most often voiced concerned the two-minute return time, which was found by many to be inconveniently long, even for transcription purposes. This simple modification has been developed for a traverse time of just a few seconds. It can be retro-fitted to existing machines.

The modification consists of a second motor which drives the lead screw at speed without the assistance of the servo motor. Several constructors appear to have tried this method already, by driving the lead


Modifications and improvements shown on page 43 include simplified side supports and pivots, new tracking arm, and fast traverse action and slipping clutch, as well as a suggested alternative parallel track (bottom). The track, which uses two steel rods instead of a long slot in a strip of aluminium alloy, is easier to make if you have a drilling stand for an electric drill. Accuracy of the assembled track depends on the straightness of the steel rods and not so much on the accuracy of drilling (drill both plates together); this simplifies the task of producing a well-true track. Precision-ground steel rod of 1/4in diameter is readily available from engineers merchants and is not expensive. The rods are fixed into the end plates with Loctite, which is allowed to set with the assembly resting on a flat surface such as a piece of plate glass.

screw direct and simply slipping the drive band from the servo motor —not good practice because of the stretching and generally increased wear of the drive band. It also puts an unfair strain on the miniature gears in the worm gear transmission. A much more acceptable method is to drive the lead screw indirectly as on page 43.

By using a double-groove pulley wheel with a slipping clutch on the output shaft of the servo gearbox, the drive bands are operated within their limits, and the slipping clutch relieves the gear wheels inside the gearbox of excessive strain. Such a slipping clutch is easy to construct from a couple of wavy-type spring washers and set collars, as shown on page 43.


The servo motor now has to overcome the magnetic drag of the second motor during normal operation, if this second motor is a permanent-magnet type. This is avoided by applying a small bias current to the second motor of a value that will overcome the drag but not make the motor revolve. This can be done by a suitable resistor via the switching network. Alternatively, a motor with a field coil can be used, avoiding this requirement altogether. But whichever type of motor is used, it needs to be sufficiently powerful to overcome the slipping clutch and drive the lead screw, without the advantage of the reduction gearbox that the servo motor employs. There is no requirement for it to be vibration-free or quiet running like the servo motor, so a relatively robust and inexpensive motor can be used.

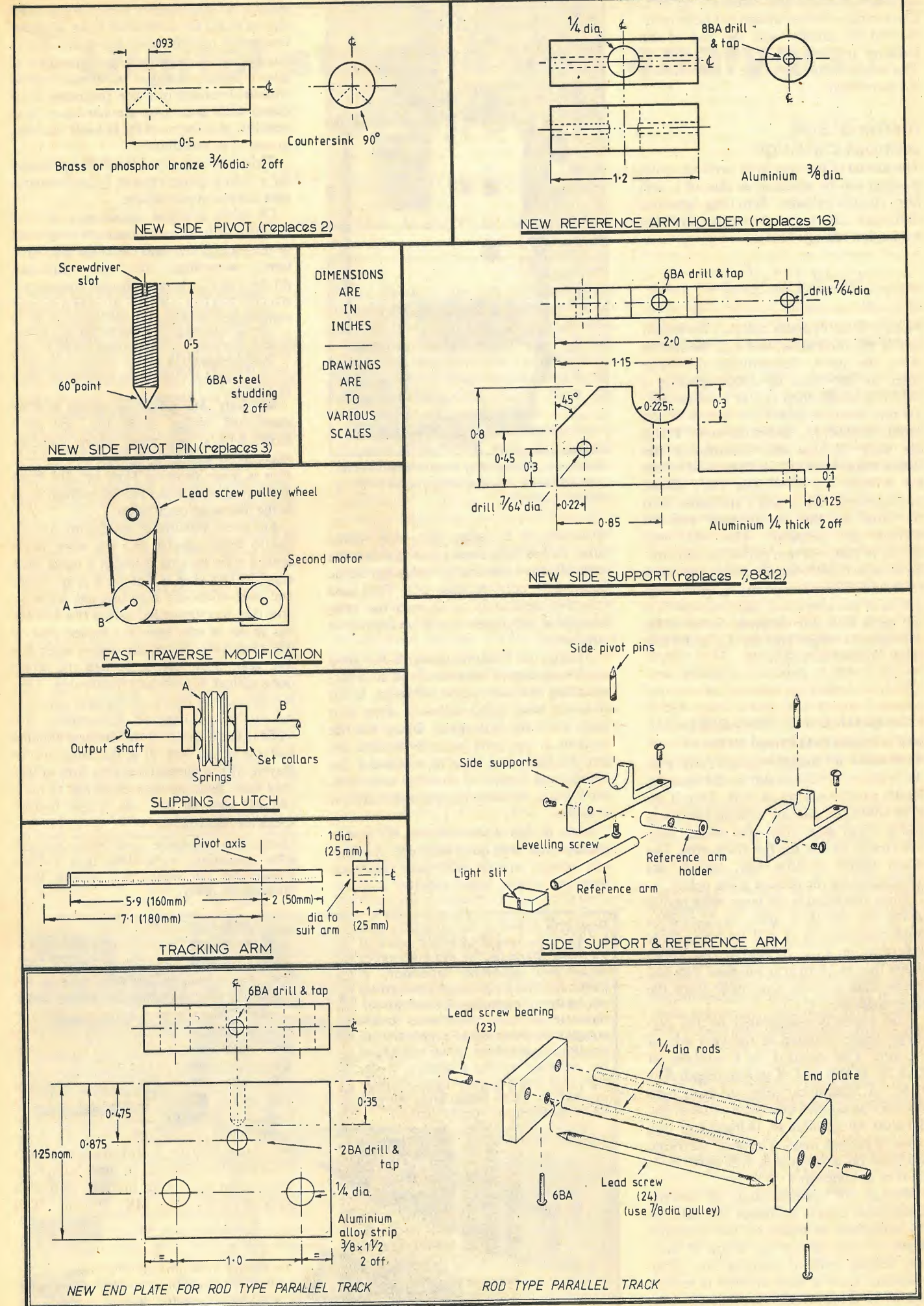The new arm is of the same aluminium alloy as the Mk 1, HT30TF, which is a hard alloy fully heat-treated and cannot be manipulated (eg drawn, bent or compressed) in the usual way without cracking. The diameter of the 9.5mm tube was chosen to give an increase in overall stiffness over the Mk 1 arm. Wall



DIMENSIONS ARE IN INCHES
DRAWINGS ARE TO VARIOUS SCALES

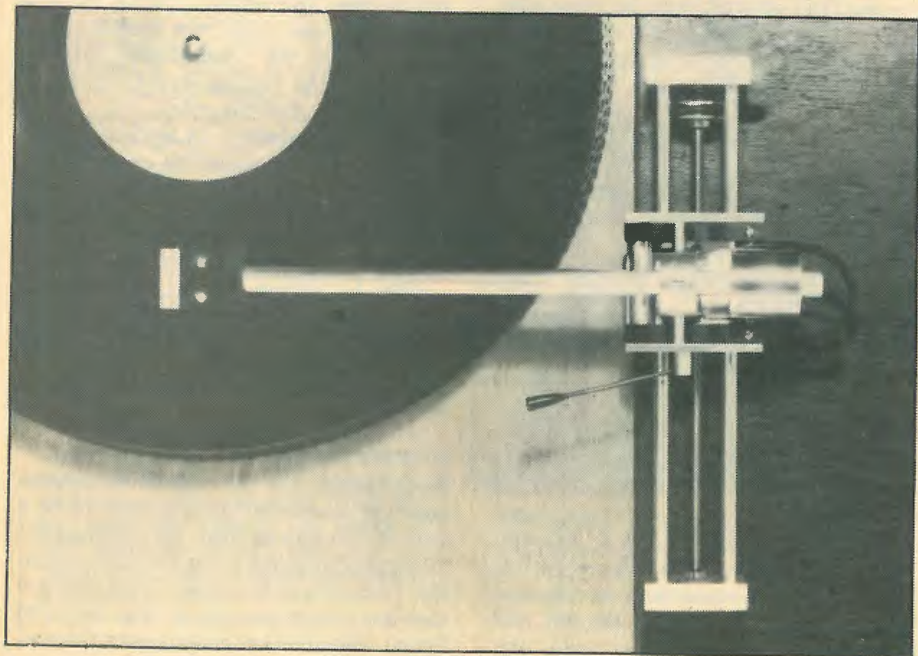Alternative to original parallel track comprising two steel rods is easier to make if you have an electric drill and stand.



thickness remains the same at 22s.w.g. The cartridge holder design has been modified to fit directly onto the end of the tracking arm instead of sliding along it. The weight of 100cm of the 9.5mm tubing is a mere 55gm.

Inertia of arm without cartridge

The inertia of the arm from pivot to stylus position can be assumed as that of a uniform circular cylinder 18cm long, ignoring difference in mass between cartridge holder and tubing. This is

$$I_{\text{arm}} = M \left(\frac{a^2}{4} + \frac{l^2}{3} \right)$$

where a is the cylinder radius, l the length and M the total mass, and I_{arm} the inertia about the pivot. Substituting the value 10gm for M , 18cm for l and ignoring a (which is small) then I_{arm} is 1080gm cm². To this must be added the inertia of the counterweight, I_{cw} , about the pivot. Using the same formula and substituting the values 80gm for M , 2.5cm for l and 1.2cm for a then I_{cw} is 185gm cm². These measurements for a and l are taken with the arm in the equilibrium position without the cartridge. Thus the total inertia is 1080+185gm cm²=1265gm cm². Now $M_e = I_{\text{tot}}/R^2$, where M_e is the mass referred to the stylus point, I_{tot} is the total inertia of the arm about the pivot and R is the pivot to stylus distance. Substituting the values 1265gm cm² for I_{tot} and 18cm for R , then M_e is 3.9gm.


Comparison of new arm with conventional arm

As R and l are roughly equal in any arm, the terms in R^2 cancel out in the equation for M_e which becomes $M_e \propto M$. Thus if the same tubing is used for both an 18cm arm and a 23cm arm, then the overall mass will clearly be less for the 18cm arm. The actual figure is 22% less, but is not meaningful for the reasons given below.

More important is the large reduction in inertia for the 18cm arm. As $I_{\text{arm}} \propto R^2$ a small reduction in R will lead to a large reduction in I_{arm} . A simple calculation shows that an 18cm arm will have 39% less inertia than a 23cm arm made from the same material.

This effect is exaggerated by the cartridge being mounted at the very end of the arm. The inertia I_c of a cartridge of mass M_c at the end of an arm length R is $M_c R^2$. A typical cartridge of mass 5gm mounted at the end of an arm of 18cm has therefore an I_c value of 1620gm cm² due solely to its own mass. The same cartridge mounted on a 23cm arm will have an I_c value of 2645gm cm²!

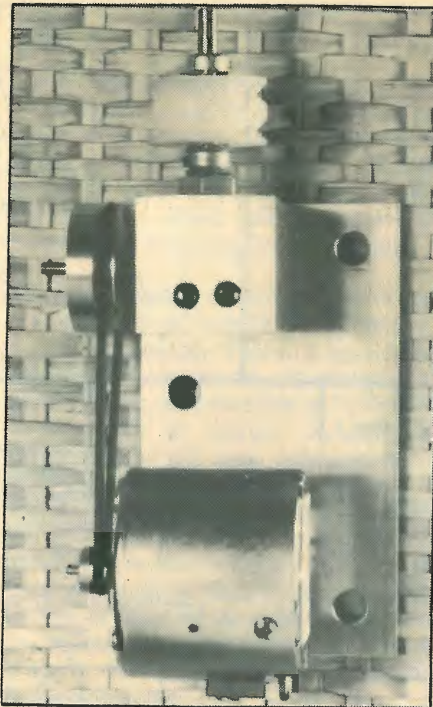Because the manufacturers of conventional arms cannot influence the mass of the cartridges as made by the specialist firms, or even reduce the length of their arm designs without running into other problems, most of them attempt to reduce inertia by using exotic materials for con-




One way of achieving faster traverse is to use a second, inexpensive, motor with slipping clutch.

struction, or by using ultra-thin walled tube. As has been shown above, this is the least effective method of reducing inertia because it only reduces M . The most effective method is to shorten the arm, because of the presence of R^2 in the inertia equations.

Making use of exotic materials has good marketing appeal because of the aura surrounding titanium, carbon fibre etc. but it does not make good economic sense as it costs a lot for little gain. Using thinner sections is not good practice because the arm becomes less able to withstand the knocks and bumps of everyday use. Also, the thinner the material, the more likely it is to flex.

In the design of the new arm, the design principle has been quite different. A relatively robust straight stiff tube has been specified to give good rigidity. A light-

Born and raised in Birmingham, Rod Cooper now lives in Lichfield, working as Sales Manager for the electronics repair and calibration laboratory of DMR Ltd of Nottingham. A mechanical engineering background and an interest in applying electronics to the solution of mechanical problems undoubtedly contribute to the success of his parallel-tracking pickup arm design (not forgetting the mercury pickup switch, April 1980) and, coming soon, an electronic ignition circuit.

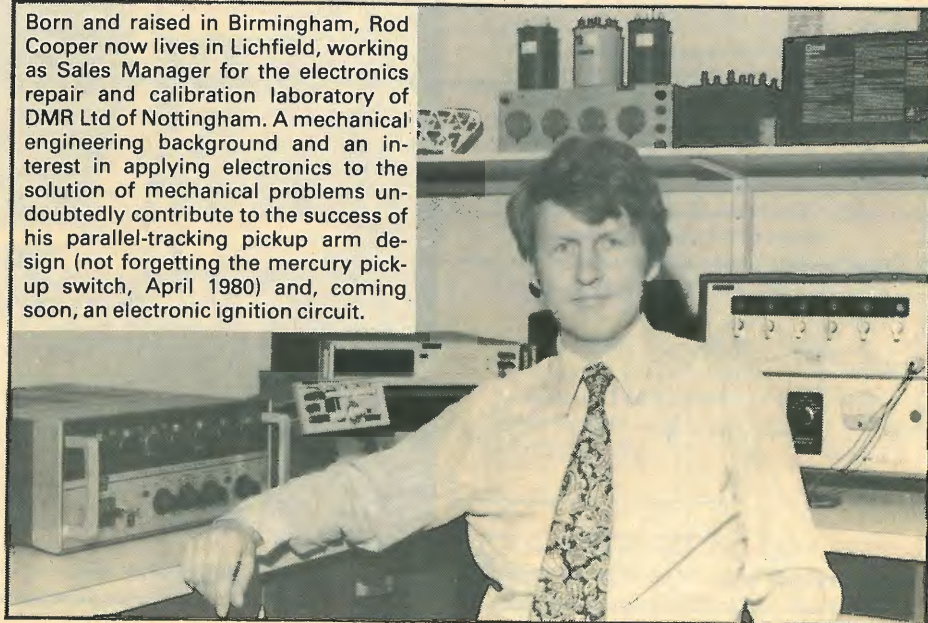

weight but inexpensive material has been chosen to get the economics right, and give reasonable overall mass. But more important, the arm length has been specified to give a large reduction in overall inertia without running into the problems associated with arms that are too short (e.g. stability, and the need for fail-safe tracking in case of servo failure).

This approach provides all the potential for a radical improvement in performance over the conventional arm.

Of what practical importance is M_e ? Firstly it influences the resonant frequency of the pickup arm and cartridge combination, according to the equation $f_0/2\pi\sqrt{M_e C}$ where C is the compliance of the stylus. With modern high-compliance cartridges a low value of M_e is a prime requirement for avoidance of resonance problems. (See page 64 of April 1978 *Wireless World* for an analysis of these problems.)

Secondly, M_e influences record wear as mentioned earlier. Take the case of a record with a 1mm warp, which is not an uncommon amount even on a new record. This is taken to mean 1mm up and 1mm down from the mean record surface level in the following calculation.

For every revolution the record surface has to work against M_e , the work done against g by moving distance d being $M_e d$ ergs. In this case d will be 0.2cm. Now, one state-of-the-art conventional tracking arm that has just appeared on the market has an M_e of just 9gm. If a typical disc of 650 grooves is played say once a week for five years with this arm then the work done against M_e will be 315,900 ergs. This is equivalent to lifting a 63kg man approximately 5cm into the air. Remember, this work is being done by the delicate playing surfaces of the record! If the same disc is played with a parallel-tracking arm of M_e only 4gm, then the work done will be only 140,400 ergs, or 56% less. These figures speak for themselves.

Carbon fibre, neoprene cord, Nylon 66, and other components are available from J. Biles Engineering, 120 Castle Lane, Solihull, West Midlands B92 8RN.

Digital storage and analysis of speech

1 - Storing waveforms digitally

by Ian H. Witten, M.A., M.Sc., Ph.D., M.I.E.E. University of Calgary

One of the difficulties with digital speech storage and analysis is that new signal-processing techniques have been developed to handle digital signals. Since these only appeared recently, and are rather mathematical, they are not understood very widely. Concepts like the z-transform, the discrete Fourier transform, and digital filters are quite unfamiliar to many practising electronic engineers. Although there are several textbooks on the subject, nearly all of them treat it in a frighteningly theoretical and abstract way. The aim of this article is to introduce some of these ideas in a down-to-earth manner by putting them in the practical context of the speech waveform.

Computer-generated speech is still a rather esoteric subject, despite the explosive growth in practical applications that we are witnessing. Texas Instrument's Speak 'n Spell toy - now about three years old - is probably the best example of a consumer device that uses speech output. But there are others. Cheap speech synthesizers intended for hobby computers have been on the market for several years now, as has a talking calculator. Digital transmission of speech is used in the telephone network, and the new System X exchange developed by the Post Office uses messages stored in digital form to guide the user and tell him what is happening to his call. Note that analogue storage of speech has been used in the telephone service for many years, for the speaking clock, weather forecasts, and even bedtime stories.

Analogue storage of speech. The most familiar device that produces speech output is the ordinary tape recorder. However, this is unsuitable for speech output from computers. One reason is that it is difficult to access different utterances quickly: although random-access tape recorders do exist, they are expensive and subject to mechanical breakdown because of the stresses associated with frequent starting and stopping.

Storing speech on a rotating drum instead of tape offers the possibility of access to any track within one revolution time. For example, the IBM 7770 Audio Response Unit, employs drums rotating twice a second which are able to store up to thirty-two 500 ms words. These can be accessed randomly, within half a second at

most. Although one can arrange to store longer words by allowing overflow on to an adjacent track at the end of the rotation period, the discrete time-slots provided by this system make it virtually impossible for it to generate connected utterances by assembling appropriate words from the store.

The Cognitronics Speechmaker has a similar structure, but with the analogue speech waveform recorded on photographic film. Storing audio waveforms optically is not an unusual technique, for this is how soundtracks are recorded on ordinary films. The original version of the "speaking clock" of the British Post Office used optical storage in concentric tracks on flat glass discs. This was developed in the mid 1930s, and synchronization of utterances with real time was achieved in an intriguing manner. A 4 Hz signal from a pendulum clock was used to supply current to an electric motor, which drove a shaft equipped with cams and gears that rotated the glass discs containing utterances for seconds, minutes and hours at appropriate speeds!

A second reason for avoiding analogue storage is price. It is difficult to see how a random-access tape recorder could be incorporated into a talking pocket calculator or child's toy without considerably inflating the cost. Solid-state electronics is much cheaper than mechanics.

But the best reason is that, in many applications of speech storage, it is necessary to form utterances by linking together separately recorded parts. It is totally infeasible, for example, to store every possible telephone number as an individual recording! And utterances that are formed by linking individual words which were recorded in isolation, or in a different context, do not sound completely natural. For example, in an experiment performed in 1960, individual words were recorded on acoustic tape, which was spliced with the words in a different order to make sentences. The result was played to subjects who were scored on the number of key words which they identified correctly. The overall conclusion was that while embedding a word in normally spoken sentences increases the probability of recognition (because the extra context gives clues about the word), embedding a word in a constructed sentence, where intonation and rhythm are not properly rendered, decreases the probability of recognition. When the speech was uttered

slowly, however, a considerable improvement was noticed, indicating that if the listener has more processing time he can overcome the lack of proper intonation and rhythm.

Nevertheless, many present-day voice response systems do store what amounts to a direct recording of the acoustic wave. However, the storage medium is digital rather than analogue. This means that standard computer storage devices can be used, providing rapid access to any segment of the speech at relatively low cost - for the economics of mass-production ensures a low price for random-access digital devices compared with random-access analogue ones. Furthermore, it reduces the amount of special equipment needed for speech output. One can buy very cheap speech input/output interfaces for home computers which connect to standard hobby buses. Another advantage of digital over analogue recording is that solid-state r.o.ms can be used for hand-held devices which need small quantities of speech. Hence this article begins by showing how waveforms are stored digitally, and then describes some techniques for reducing the data needed for a given stretch of speech.

Digital storage. When an analogue signal is converted to digital form, it is made discrete both in time (sampling) and in amplitude (quantizing). Much of the theory of digital signal processing investigates signals which are sampled but not quantized (or quantized into sufficiently many levels to avoid inaccuracies). The operation of quantization, being non-linear, is not very amenable to theoretical analysis, since it introduces issues such as accumulation of round-off noise in arithmetic operations, which, although they are very important in practical implementations, can only be treated theoretically under certain somewhat unrealistic assumptions (in particular, independence of the quantization error from sample to sample).

Sampling

A fundamental theorem of telecommunications states that a signal can only be reconstructed accurately from a sampled version if its highest component frequency is less than half the frequency at which the sampling takes place. Figure 1(a) shows how a component of slightly greater than half the sampling frequency can masquerade, as far as an observer with access only to the sampled data can tell, as a compo-

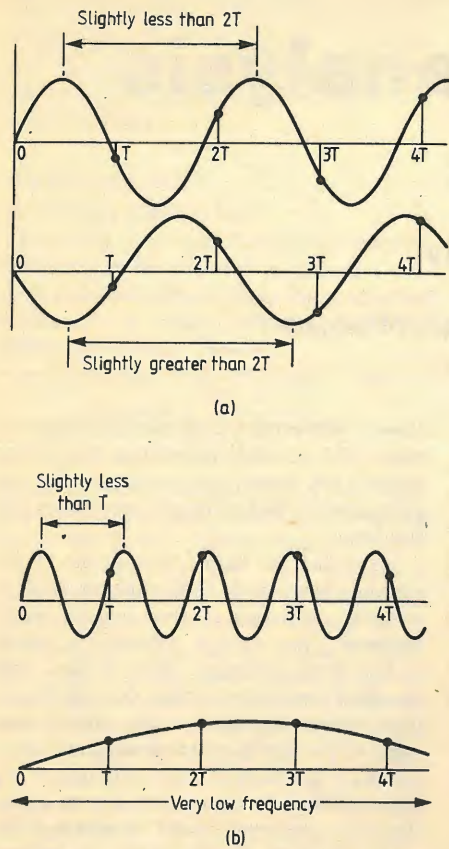


Fig. 1 Different sine waves which appear the same when sampled (a) components near half the sampling frequency (b) a component at just under the sampling frequency and its low-frequency equivalent

nent at slightly less than half the sampling frequency. Call the sampling interval T seconds, so that the sampling frequency is $1/T$ Hz. Then components at $1/2T + f$, $3/2T - f$, $3/2T + f$ and so on all masquerade as a component at $1/2T - f$. Similarly, components at frequencies just under the sampling frequency masquerade as very low-frequency components, as shown in Fig. 1(b). This phenomenon is often called "aliasing".

Thus the continuous, infinite, frequency axis for the unsampled signal, where two components at different frequencies can always be distinguished, maps into a repetitive frequency axis when the signal is sampled. As depicted in Fig. 2, the frequency interval $[1/2T, 2/2T]^*$ is mapped back into the band $[0, 1/2T]$, as are the intervals $[2/2T, 3/2T]$, $[3/2T, 4/2T]$, and so on. Furthermore, the interval $[1/2T, 1/2T]$ between half the sampling frequency and the sampling frequency, is mapped back into the interval below half the sampling frequency; but this time the mapping is backwards, with frequencies at just under $1/2T$ being mapped to frequencies slightly greater than zero, and frequencies just over $1/2T$ being mapped to ones just under $1/2T$. The best way to represent a repeating frequency axis like this is as a circle.

* Intervals are specified in brackets, with a square bracket representing a closed end of the interval and a round one representing an open one. Thus the interval $[1/2T, 2/2T]$ specifies the range $1/2T < \text{frequency} < 2/2T$.

Figure 3 shows how the linear frequency axis for continuous systems maps on to a circular axis for sampled systems. For present purposes it is easiest to imagine the bottom half of the circle as being reflected into the top half, so that traversing the upper semicircle in the anticlockwise direction corresponds to frequencies increasing from 0 to $1/2T$ (half the sample frequency), and returning along the lower semicircle is actually the same as coming back round the upper one, and corresponds to frequencies from $1/2T$ to $1/T$ being mapped into the range $1/2T$ to 0.

As far as speech is concerned, then, we must ensure that before sampling a signal no significant components at greater than half the sample frequency are present. Furthermore, the sampled signal will only contain information about frequency components less than this, so the sample frequency must be chosen as twice the highest frequency of interest. The telephone network aims to transmit only frequencies lower than 3.4 kHz. This region will contain the information-bearing formants, and some - but not all - of the fricative and aspiration energy*. Transmitting speech through the telephone system degrades its quality very significantly, probably more than you realize since everyone is so accustomed to telephone speech - try the dial-a-disc service and compare it with high-fidelity music for a striking example of the kind of degradation suffered.

Since speech contains significant amounts of energy above 3.4 kHz, it should be filtered before sampling to remove this. Otherwise, the higher components would be mapped back into the baseband and distort the low-frequency information. Because it is difficult to make filters that cut off very sharply, the sampling frequency is chosen to be rather greater than twice the highest frequency of interest; for example, the digital telephone network samples at 8 kHz. The pre-sampling filter should have a cutoff frequency of 4 kHz; aim for negligible distortion below 3.4 kHz; and transmit negligible components above 4.6 kHz - for these are reflected back into the band of interest, namely 0 to 3.4 kHz. Figure 4 shows a block diagram for the input hardware.

Quantization

Before considering specifications for the pre-sampling filter, let us turn from sampling in time to amplitude quantization. This is performed by an a-to-d converter

*See "The Chatterbox," *Wireless World* 84 and 85 (December 1978 and January 1979), for a simple explanation of formants, frication, and aspiration.

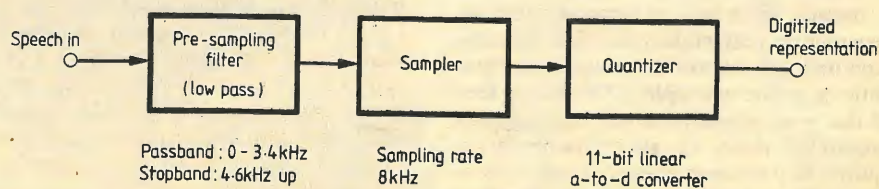


Fig. 4 Block diagram of input hardware for speech digitization

(analogue-to-digital), which takes as input an analogue voltage (produced by the sampler) and generates a corresponding binary value as output. The simplest correspondence is *uniform* quantization, where the amplitude range is split into equal regions by points termed "quantization levels", and the output is a binary representation of the nearest quantization level to the input voltage. Typically, 11-bit conversion is used for speech, giving 2048 quantization levels, and the signal is adjusted to have zero mean so that half the levels correspond to negative input voltages and the other half to positive ones.

It is, at first sight, surprising that as many as 11 bits are needed for adequate representation of speech signals. Research on the digital telephone network, for

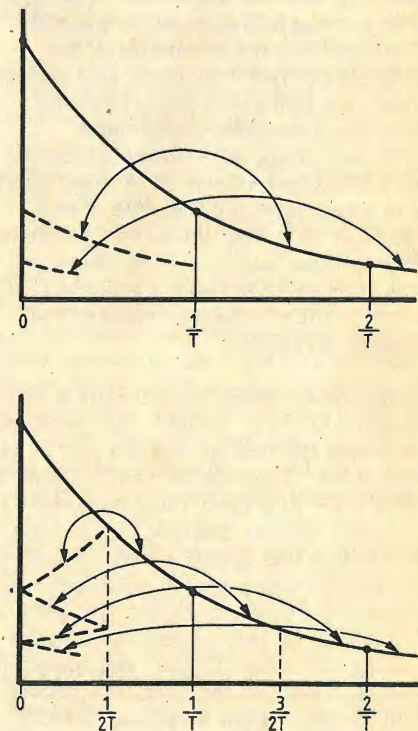


Fig. 2 How sampling "folds" the frequency spectrum

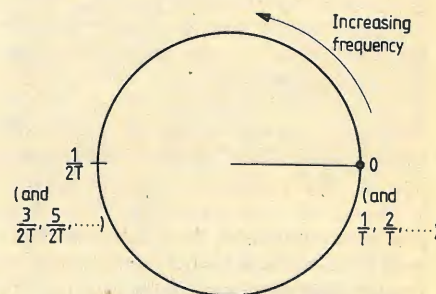


Fig. 3 The circular frequency axis of sampled systems

example, has concluded that a signal-to-noise ratio of some 30 dB is enough to avoid poor speech quality, loss of intelligibility, and listener fatigue for speech at a normal level. But 11-bit quantization seems to give a very much better signal-to-noise ratio than this figure. To estimate its magnitude, note that for N -bit quantization the error for each sample will lie between

$$-1/2 \cdot 2^{-N} \text{ and } +1/2 \cdot 2^{-N}.$$

Assuming that it is uniformly distributed in this range - an assumption which is likely to be justified if the number of levels is sufficiently large - leads to a mean-squared error of

$$\int_{-2^{-N-1}}^{2^{-N-1}} e^2 p(e) de,$$

where $p(e)$, the probability density function of the error e , is a constant which satisfies the usual probability normalization constraint, namely

$$\int_{-2^{-N-1}}^{2^{-N-1}} p(e) de = 1.$$

Hence $p(e) = 2^N$, and so the mean-squared error is $2^{-2N}/12$. This is $10 \log_{10}(2^{-2N}/12)$ dB, or around -77 dB for 11-bit quantization.

This noise level is relative to the maximum amplitude range of the conversion. A maximum-amplitude sine wave has a power of -9 dB relative to the same reference, giving a signal-to-noise ratio of some 68 dB. This is far in excess of that needed for telephone-quality speech. However, look at the very peaky nature of the typical speech waveform given in Fig. 5. If clip-

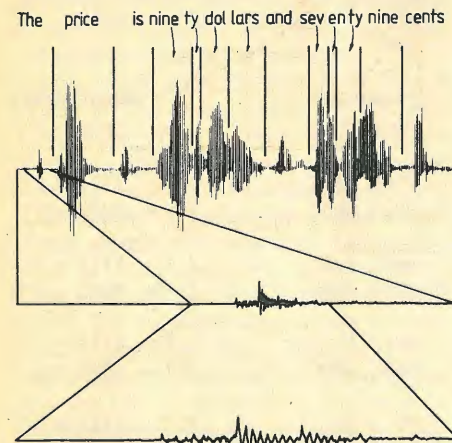


Fig. 5 Typical speech waveform

ping is to be avoided, the maximum amplitude level of the a-to-d converter must be set at a value which makes the power of the speech signal very much less than a maximum-amplitude sine wave. Furthermore, different people speak at very different volumes, and the overall level fluctuates constantly with just one speaker. Experience shows that while 8- or 9-bit quantization may provide sufficient signal-to-noise ratio to preserve telephone-quality speech if the overall speaker levels are carefully controlled, about 11 bits are generally required to provide high-quality representation of speech with a uniform quantization. With 11 bits, a sine wave whose

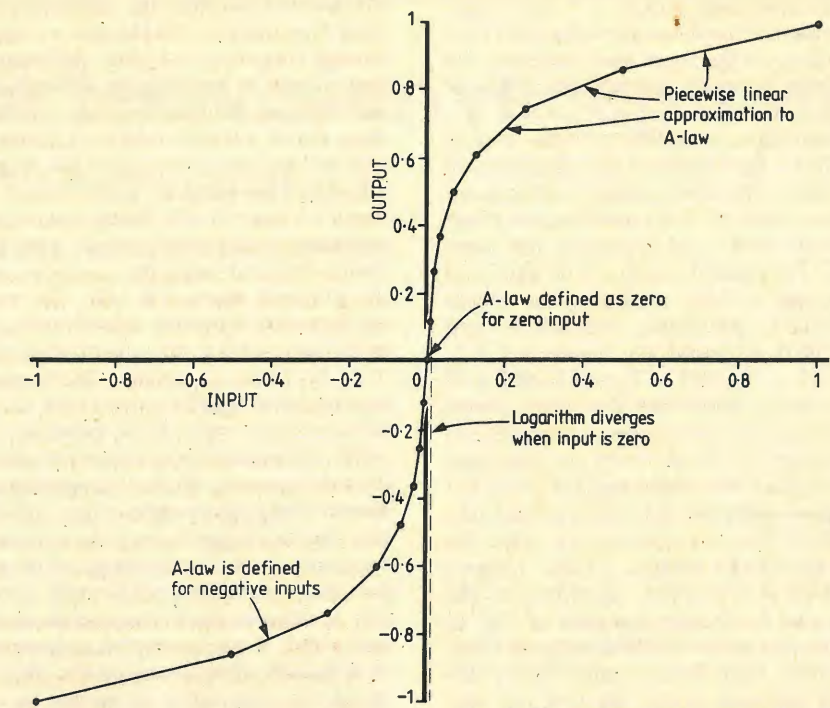


Fig. 6 Piecewise linear approximation to the A-law input/output relationship

amplitude is only 1/32 of the full-scale value would be digitized with a signal-to-noise ratio of around 36 dB, which is not much greater than the figure mentioned above for adequate quality. Even then it is useful if the speaker is provided with an indication of the amplitude of his speech: a traffic-light indicator with red signifying clipping overload, orange a suitable level, and green too low a value, is often convenient for this.

Logarithmic quantization

For the purposes of speech processing, it is essential to have the signal quantized uniformly. This is because all of the theory applies to linear systems, and nonlinearities introduce complexities which are not amenable to analysis. Uniform quantization, although a nonlinear operation, is linear in the limiting case as the number of levels becomes large, and for most purposes its effect can be modelled by assuming that the quantized signal is obtained from the original analogue one by the addition of a small amount of uniformly-distributed quantizing noise, as in fact was done above. Usually the quantization noise is disregarded in subsequent analysis.

However, the peakiness of the speech signal illustrated in Fig. 5 leads one to suspect that a non-linear representation, for example a logarithmic one, could provide a better signal-to-noise ratio over a wider range of input amplitudes, and hence be more useful than linear quantization - at least for speech storage (and transmission). And indeed this is the case. Linear quantization has the unfortunate effect that the absolute noise level is independent of the signal level, so that an excessive number of bits must be used if a reasonable ratio is to be achieved for peaky signals. It can be shown that a logarithmic representation like

$$y = 1 + k \log x,$$

where x is the original signal and y is the value which is to be quantized, gives a signal-to-noise ratio which is independent of the input signal level. This relationship cannot be realized physically, for it is undefined when the signal is negative and diverges when it is zero. However, realizable approximations to it can be made which retain the advantages of constant signal-to-noise ratio within a useful range of signal amplitudes, one widely used approximation being called the A-law. The idea of non-linearly quantizing a signal to achieve adequate signal-to-noise ratios for a wide variety of amplitudes is called "companding", a contraction of "compressing-expanding". The original signal can be retrieved from its A-law compression by antilogarithmic expansion.

Figure 6 shows one common 8-bit coding scheme which is a piecewise linear approximation to the A-law. This provides an 8-bit code, and gives the equivalent of 12-bit linear quantization for small signal levels. It approximates the A-law in 16 linear segments, 8 for positive and 8 for negative inputs. Consider the positive part of the curve. The first two segments, which are actually collinear, correspond exactly to 12-bit linear conversion. Thus the output codes 0 to 31 correspond to inputs from 0 to 31/2048, in equal steps. (Remember that both positive and negative signals must be converted, so a 12-bit linear converter will allocate 2048 levels for positive signals and 2048 for negative ones.) The next segment provides 11-bit linear quantization, output codes 32 to 47 corresponding to inputs from 16/1024 to 31/1024. Similarly, the next segment corresponds to 10-bit quantization, covering inputs from 16/512 to 31/512. And so on, the last section giving 6-bit quantization of inputs from 16/32 to 31/32, the full-scale positive value. Negative inputs are converted similarly. For signal levels of

less than $32/2048$, that is 2^{-8} , this implementation of the A-law provides full 12-bit precision. As the signal level increases, the precision decreases gradually to 6 bits at maximum amplitudes.

Logarithmic encoding provides what is in effect a floating-point representation of the input. The conventional floating-point format, however, is not used because many different codes can represent the same value. For example, with a 4-bit exponent preceding a 4-bit mantissa, the words 0000:1000, 0001:0100, 0010:0010, and 0011:0001 represent the numbers 0.1×2^0 , 0.01×2^1 , 0.001×2^2 , and 0.0001×2^3 respectively, which are the same. (Some floating-point conventions assume that an unwritten "1" bit precedes the mantissa, except when the whole word is zero; but this gives decreased resolution around zero - which is exactly where we want the resolution to be greatest.) Table 1 shows the 8-bit A-law codes, according to the piecewise linear approximation of Fig. 6, written in a notation which suggests floating point. Each linear segment has a different exponent except the first two segments, which as explained above are collinear.

Logarithmic encoders and decoders are available as single-chip devices called "coders" (for "coder/decoder"). Intended for use on digital communication links, these generally provide a serial output bit-stream, which should be converted to parallel by a shift register if the data is intended for a computer. Because of the potentially vast market for coders in telecommunications, they are made in great quantities and are consequently very cheap. Estimates of the speech quality necessary for telephone applications indicate that somewhat less than this accuracy is needed - 7-bit logarithmic encoding was used in early digital communications links, and it may be that even 6 bits are adequate. However, during the transition period when digital networks must coexist with the present analogue one, it is anticipated that a particular telephone call may have to pass through several links, some using analogue technology and some being digital. The possibility of several successive encodings and decodings has led telecommunications engineers to standardize on 8-bit representations, leaving some margin before additional degradation of signal quality becomes unduly distracting.

Unfortunately, world telecommunications authorities cannot agree on a single standard for logarithmic encoding. The A-law, which we have described, is the European standard, but there is another system, called the μ -law, which is used universally in North America. It also is available in single-chip form with an 8-bit code. It has very similar quantization error characteristics to the A-law, and would be indistinguishable from it on the scale of Fig. 6.

The pre-sampling filter

Now that we have some idea of the accuracy requirements for quantization, let us discuss quantitative specifications for the pre-sampling filter. Figure 7 sketches the

characteristics of this filter. Assume a sampling frequency of 8 kHz and a range of interest from 0 to 3.4 kHz. Although all components at frequencies above 4 kHz will fold back into the 0-4 kHz baseband, those below 4.6 kHz fold back above 3.4 kHz and are therefore outside the range of interest. This gives a "guard band" between 3.4 and 4.6 kHz which separates the passband from the stopband. The filter should transmit negligible components in the stopband above 4.6 kHz. To reduce the harmonic distortion caused by aliasing to the same level as the quantization noise in 11-bit linear conversion, the stopband attenuation should be around -68 dB (the signal-to-noise ratio for a full-scale sine wave). Passband ripple is not so critical, for two reasons. Whilst the presence of aliased components means that information has been lost about the frequency components within the range of interest, passband ripple does not actually cause a loss of information but only a distortion, and could, if necessary, be compensated by a suitable filter acting on the digitized waveform. Secondly, distortion of the passband spectrum is not nearly so audible as the frequency images caused by aliasing. Hence one usually aims for a passband ripple of around 0.5 dB.

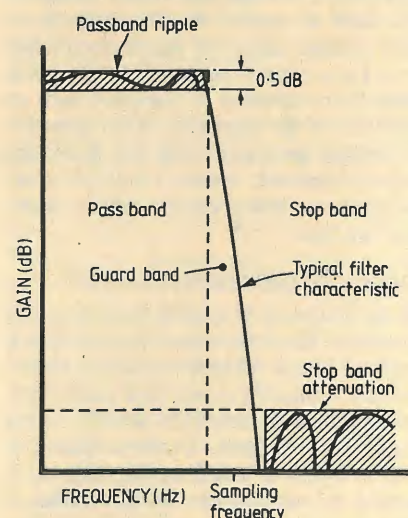


Fig. 7 General characteristics of the pre-sampling filter

The pass and stopband targets we have mentioned above can be achieved with a 9th order elliptic filter. While such a filter is often used in high-quality signal-processing systems, for telephone-quality speech much less stringent specifications seem to be sufficient. Figure 8, for example, shows a template which has been recommended by telecommunications authorities. A 5th order elliptic filter can easily meet this specification. Such filters, implemented by switched-capacitor means, are available in single-chip form. Integrated c.c.d. filters which meet the same specification are also marketed. Indeed, some codecs provide input filtering on the same chip as the a-to-d converter.

Instead of implementing a filter by analogue means to meet the aliasing specifications, digital filtering can be used. A high sample-rate a-to-d converter, operating at,

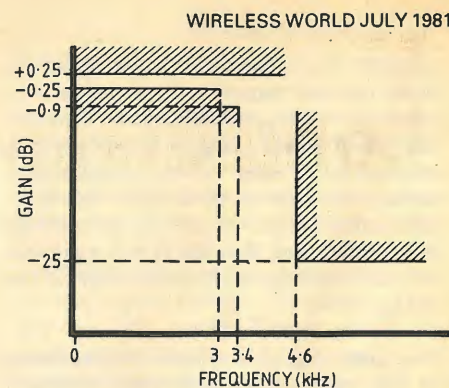


Fig. 8 Specifications of the pre-sampling filter for telephone-quality speech

say, 32 kHz, and preceded by a very simple low-pass pre-sampling filter, is followed by a digital filter which meets the desired specification, and its output is subsampled to provide an 8 kHz sample rate. While such implementations may be economic where a multichannel digitizing capability is required, as in local telephone exchanges where the subscriber connection is an analogue one, they are unlikely to prove cost-effective for a single channel.

continued on page 59

Table 1. 8-bit A-law codes, with their floating-point equivalents.

8-bit codeword			interpretation
sign bit	exponent	mantissa	
0000	0000	0000	$.0000 \times 2^{-7}$
0000	1111	0000	$.1111 \times 2^{-7}$
0001	0000	0000	$2^{-7} + .0000 \times 2^{-7}$
0001	1111	0000	$2^{-7} + .1111 \times 2^{-7}$
0010	0000	0000	$2^{-6} + .0000 \times 2^{-6}$
0010	1111	0000	$2^{-6} + .1111 \times 2^{-6}$
0011	0000	0000	$2^{-5} + .0000 \times 2^{-5}$
0011	1111	0000	$2^{-5} + .1111 \times 2^{-5}$
0100	0000	0000	$2^{-4} + .0000 \times 2^{-4}$
0100	1111	0000	$2^{-4} + .1111 \times 2^{-4}$
0101	0000	0000	$2^{-3} + .0000 \times 2^{-3}$
0101	1111	0000	$2^{-3} + .1111 \times 2^{-3}$
0110	0000	0000	$2^{-2} + .0000 \times 2^{-2}$
0110	1111	0000	$2^{-2} + .1111 \times 2^{-2}$
0111	0000	0000	$2^{-1} + .0000 \times 2^{-1}$
0111	1111	0000	$2^{-1} + .1111 \times 2^{-1}$
1000	0000	0000	$-.0000 \times 2^{-7}$
1000	1111	0000	$-.1111 \times 2^{-7}$
1001	0000	0000	$-2^{-7} - .0000 \times 2^{-7}$
1001	1111	0000	$-2^{-7} - .1111 \times 2^{-7}$

Negative numbers treated as above, with a sign bit of 1

Long distance television reception

1 - An introduction

by Keith Hamer and Garry Smith

In these occasional articles, the authors will introduce readers to the hobby of long-distance television reception, or DX-tv as it is often called, and pass on their experiences as dedicated amateurs. This first part discusses how tv signals are affected by weather and atmospheric conditions, basic tv set requirements, simple aerials and signal identification.

There are many factors, such as transmitter powers and terrain, which will influence the range over which a television signal can be reliably received, but in general, the strength of the signal becomes weaker as the distance between the transmitter and receiver increases. Reliable reception is normally limited to approximately 70 miles from the transmitter.

Readers have probably noticed that the strengths of signals from the more distant transmitters vary during certain weather conditions. Distant signals, which are normally very weak, may become comparable in strength to that of the local transmitter for a matter of hours, or even days.

Sometimes a distant signal will be received on the same channel as the local transmitter. This is termed 'co-channel reception' (or interference, depending on whether you are an enthusiast or a viewer). These temporary extensions in the range of distant signals are connected with variations in the troposphere, which extends from the earth's surface to about 20,000ft above. For example, when an anticyclonic weather condition exists, together with a cold front stretching between Scandinavia and the UK, a temperature inversion in the troposphere usually takes place. Temperature inversions enhance long-distance television reception.

Fortunately for the average viewer, but not for the DX-tv enthusiast, widespread interference on u.h.f. television caused by tropospheric conditions of the type described above is relatively rare. Enhanced reception on Bands I and III is also associated with these conditions.

Ionized patches in the E layer of the atmosphere often cause interference on Band I frequencies between early May and September. The E layer is between about 60 and 80 miles above the earth's surface. Before BBC 1 transmissions were duplicated on u.h.f., viewers had to rely on 405-line UK Band I transmissions, on which sporadic E signals would cause quite

a lot of interference. This interference often manifested itself as a herringbone pattern superimposed on the picture which could last for up to several hours. At times, the BBC 1 picture was totally obliterated. Viewers relying on channel 2 might also have experienced a loud buzz on the sound channel from the video signal of foreign transmissions on the same frequency. Unfortunately, there was little the viewer could do apart from switch over to ITV or turn off the set! Later, in some areas, the BBC duplicated their BBC 1 transmissions on higher frequencies in Band III to help overcome the problem.

If the viewer was curious enough to tune through the Band I frequencies while sporadic E signals were present, he/she would obtain video information resembling a mass of unlocked white lines without the sound channel. At other frequencies, a distorted sound signal may have been present. The reason for the unlocked video is fairly simple: The 405-line system, as used on the v.h.f. channels in the UK, employs positive video modulation whilst most Continental countries employ a 625-line system with negative video modulation. This is in some ways similar to our own 625-line system but with different sound and vision spacings and channel bandwidths. Also, most Continental countries employ the 625-line system on both v.h.f. and u.h.f. channels, unlike our own system which is only used on the u.h.f. channels. We will cover the difference in transmission standards in greater detail in a subsequent article.

Some readers will have already realised that, as the European 625-line system is similar to our own, we should, at certain times, be able to resolve u.h.f. television signals from the Continent on a standard u.h.f. receiver designed for use in the UK. This is precisely the case and if your existing u.h.f. receiving aerial is already directed towards the Continent, you should be able to receive Continental transmissions when the right atmospheric conditions exist. It is unlikely that the sound channel will be received because of the different sound and vision spacings in use but good quality colour pictures may be received. It is possible to re-tune the sound stages of the receiver but, unless you are well versed in foreign languages, there is little point.*

Resolving signals enhanced by sporadic

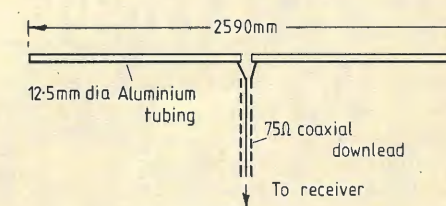


Fig. 1. A simple dipole for frequencies around 55MHz.

E in Band I is slightly more difficult due to the greater differences in transmission standards. We have already said that a 625-line signal received under sporadic E conditions will show up as a mass of unlocked white lines when displayed on the screen of a British receiver operating on 405-lines v.h.f. To resolve these signals the receiver will need to operate on the 625-line system but with the tuner covering v.h.f. frequencies. Fortunately the problem can be overcome in several ways.

Certain portables are available which were originally intended for the European market. These sets have 625-line coverage on Bands I and III and this is probably the easiest way round the problem.

If an old dual-standard receiver is on hand it may be modified so that band selection, that is u.h.f. to v.h.f., is independent of the system switch setting. The system switch is left permanently in the 625-line position.

If a single-standard receiver is available, it is possible to fit an additional inexpensive tuner and incorporate a change-over switch at the i.f. input to select the output from the existing u.h.f. tuner or the additional v.h.f. tuner. The latter two suggestions will of course depend on the competence of the individual to carry out such modifications.

Another way is to employ a frequency converter which is connected directly to the aerial input of a single-standard receiver. Such converters are sometimes used in conjunction with communal aerial distribution systems, in which translated u.h.f. signals are distributed at v.h.f. frequencies, to minimise cable losses, and a converter at the receiver converts the signals back to u.h.f. Hence, if we feed the input of the converter with a DX signal in Bands I or III, the unit will translate the signals to a u.h.f. frequency to enable a single-standard receiver to be used for both systems. Suitable converters may be obtained from aerial suppliers currently advertising in various magazines.

* On Dutch television many programmes are in English with Dutch subtitles. - Ed.

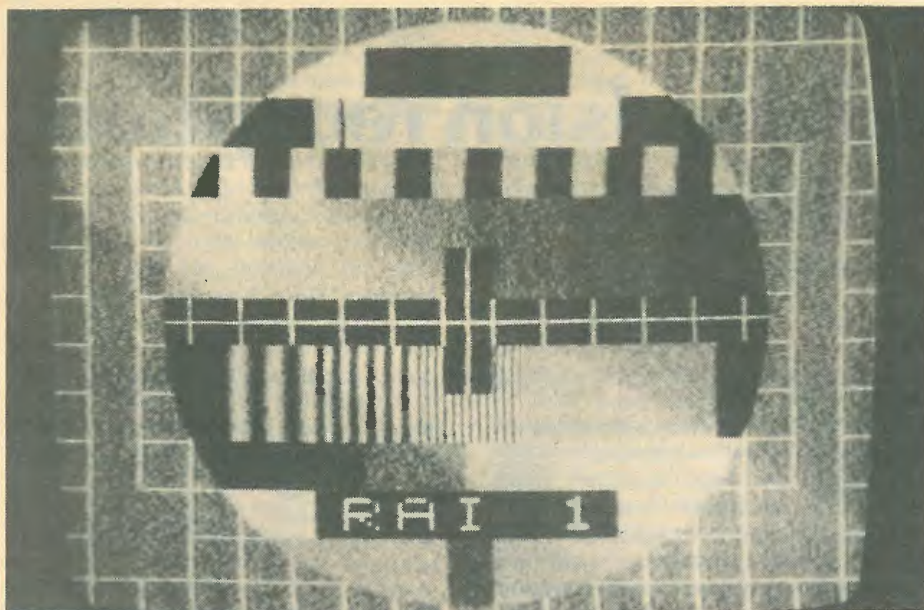


Fig. 2. The Philips PM5544 electronically generated test pattern. This photograph, taken directly from the screen, shows typical reception quality of the Italian RAI under sporadic E conditions.

Aerials

In the minds of most people, the very mention of receiving television signals from other countries conjures up an elaborate array of aerials atop an enormous lattice mast. This need not be the case. Sporadic E enhanced signals can attain very high signal strengths, especially during an intense opening, and consequently the simplest of aerials will suffice.

It should be noted that for serious DX work and the reception of weak signals, an outdoor multi-element system should be considered. Use can be made of the directional properties of the aerial if some method of rotation is used. As the majority of Continental transmissions are horizontally polarized, the receiving aerial should be mounted in the same plane, i.e. with its elements horizontal.

A simple aerial system for the beginner can consist merely of a half-wave dipole, as shown in Fig. 1, mounted outside for best results. The rods can be cut to suit a frequency in the centre of Band I, i.e. around 55MHz. As a horizontal dipole will be directional to some degree, best results will be obtained if the aerial can be rotated.

Signal identification

After a distant signal has been received, one will automatically want to identify its source. This can be difficult if the source happens to be a programme, but if a test pattern is received the chances of identification are greatly improved.

Until fairly recently there were many different test patterns in use throughout the world and almost every country had its own design. Unfortunately a growing number of broadcasting organizations have introduced similar electronically generated test patterns and at present there are two main types; the Philips PM5544 and the FuBK-type as shown in Figures 2 and 3 respectively. But most services now incorporate some form of station identification and so during sustained reception it is relatively easy to identify the country of origin and sometimes even the transmitter.

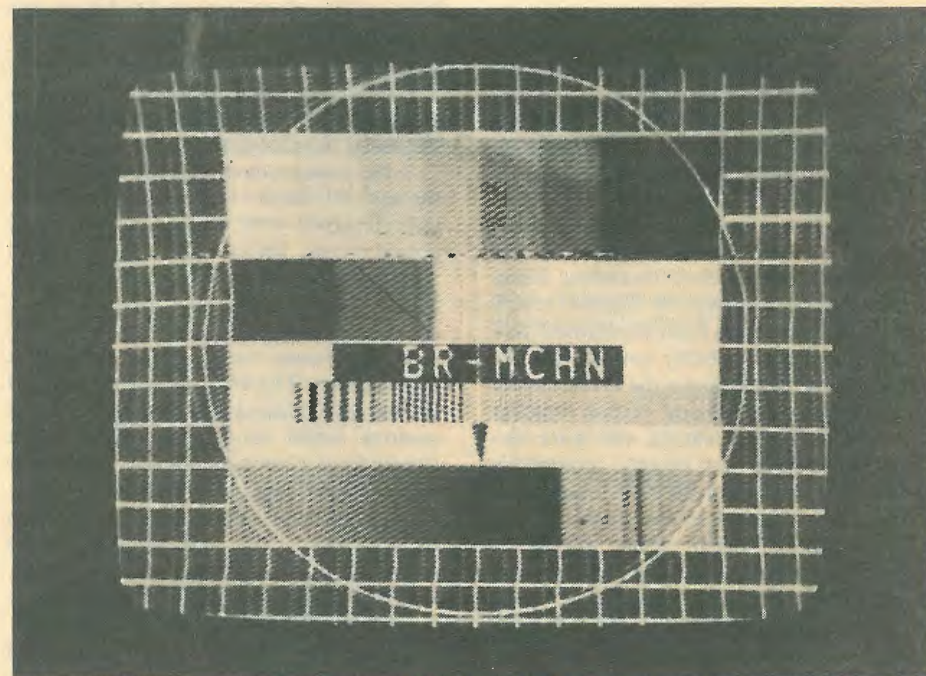


Fig. 3. A photograph of the FuBK electronically generated test pattern used by the West German Bayerischer Rundfunk. This signal was also received under sporadic E conditions.

Books

Until recently there was very little information available for the would be television DXer, but the situation has now changed. One publication which should be of interest to both the beginner and the established DXer is 'Long Distance Television Reception For The Enthusiast' by Roger Bunney, published by Babani. Other books and publications which may be of interest to television DXers will be mentioned in due course.

The authors will be pleased to hear from readers with experiences of long-distance television reception and will hopefully be able to assist with any identification problems. Reception reports and any photographic examples of DX reception will be welcomed. □

Readers wishing to respond to the authors' invitation should write to them c/o WW editorial dept.

Literature received

Application note 757-4, from Ailtech, describes the use of the Ailtech 757-57 GPIB Interface Unit in conjunction with their 757 spectrum analyser. Copies are available from Eaton Ltd, EID, Sherwood House, High Street, Crowthorne, Berkshire. WW405

Reference guide to HBM strain gauges, which lists hundreds of types and presents information on mounting adhesives and accessories, can be had from Carl Schenck (UK) Ltd, Stonefield Way, Ruislip, Middlesex HA4 0JT. WW406

A great many housings and accessories from the UK and overseas, together with tools, instruments and small components are described in the new West Hyde catalogue, which is obtainable from West Hyde Developments Ltd, Unit 9, Park Street Industrial Estate, Buckinghamshire HP20 1ET.

LETTERS TO THE EDITOR

CB PIRATES – OR PROTESTERS?

In your editorial in the May issue you were rather hard on the c.b. pirates. If a reasonable request is unreasonably refused it is unreasonable to expect the applicant to accept the decision. The applicant therefore has a moral right to ignore the decision and the blame for the consequences lies with the person who made the wrong decision.

You admit that the request for a citizens' band service was reasonable and that the initial refusal of the Home Office was unreasonable. The blame for the effects on the community therefore rests with the negligent robots in the Home Office, and the pirates have every reason to grumble at the expense of changing to the new system. Indeed, if logic ruled the world the officials in the Home Office would be made to pay for the new equipment out of their own pockets. That would teach them to be reasonable in the future.

S. Frost
Edinburgh 2

JAMES CLERK MAXWELL

Mr Wellard's recent two-part appreciation of James Clerk Maxwell published in your March and May issues was rather forceful in depreciating the work of Albert Einstein. Undoubtedly it will evoke reaction from the disciples of Relativity but, in my view, Wellard is to be applauded for his forthright contribution. It was indeed deplorable that the 1979 celebration of the centenary of Einstein's birth did not take into account the memory of Maxwell who died in the same year. More to the point, however, it is fitting to note that in 1980 experimental proof showing that the ether can assert a force was reported in *Nature* (G. M. Graham and D. G. Lahoz, *Nature*, 285, 154 (1980) and it was Maxwell and not Einstein that was supported.

I hope we will see further acceptance of Maxwell's principles in the years ahead, perhaps in regard to the third of the four alternative empirical laws of electrodynamics presented in Maxwell's treatise. This particular law is an inverse-square law of attraction with force acting directly between like charged bodies when moving at the same velocity. It can, therefore, give physical basis to Newton's law of gravitation and may even extend to provide accord with the equations, but not the underlying philosophy, of General Relativity (H. Aspden, *J. Phys. A*, 13, 3649 (1980)).

H. Aspden
Chilworth
Southampton

It pains me to find two glaring fallacies in M. G. Wellard's discussion in the March issue of the Michelson-Morley aether-drift "experiment", as it is generally termed. The first, that a mirror may function as a frequency-changer, is probably peculiar to Mr Wellard alone; the second, that the Doppler effect may be produced by the movement of the medium across the source, appears to be quite widely held.

With respect, I would merely comment on the first fallacy by saying that a fortune awaits the inventor of so simple a means of providing superheterodyne radio reception; for the second

fallacy, may I perhaps be granted a slightly more comprehensive comment? For our argument we require confidence in one assumption, however: that energy manifested in a simple coherent wave train may be represented by a set of uniform material objects, which may be arranged in a regular pattern in space and in particular in a line representing the line of advance of the wave, each object standing for either a peak, zero-crossing or other phase-state. We could construct a mechanical model, then, with a launcher which rolls a series of balls at regular intervals onto a straight level track, along which they would propel themselves at a steady velocity to a reception device with a counting mechanism, which would be matched by a similar counter on the launcher. We could then say what is the frequency of dispatch, and of arrival at the receiver, and how many balls are in transit. Now suppose that the track is the surface of a continuous transporter-belt, and that this is set to run steadily towards the launcher (to match Mr Wellard's example); what would then have changed? Not necessarily either the rate of dispatch or arrival at the end of the track. The balls would be more closely spaced along the track, in accordance with its speed, but they would travel between launcher and receiver more slowly in a compensating measure. Would we expect to detect the equivalence of the Doppler-effect in this model?

Now suppose the belt to be halted, but either the launcher or receiver to be moving along it. What would be changing in this case? Not necessarily the rate of dispatch. But the rate of reception would have to change, because the number of balls in transit would be constantly changing in proportion to the speed with which the effective track-length was either increasing or decreasing. Now could we be said to recognise the change of frequency at the receiver of this model as the equivalent of the Doppler effect?

Surely the implication of this, and of Mr Wellard's discussion (erroneous though it may be in some details) is that the designers of the aether-drift "experiment" were suspending their principles of scientific method. If this were so, the members of the scientific faculties have been somewhat slow in offering criticism of this lapse. Perhaps it is pertinent to mention here that Fizeau's aether-drag "demonstration" should be subjected to closer inspection; the use of a "control" beam of light propagated in static water, to be compared with its "twin" in water flowing in either one or the other direction relative to the light's direction would, I rather suspect, provide indications against the drag hypothesis.

To conclude, could I suggest, with all due respect, that criticism be always welcome, as is needed if the scientific ideal is to be upheld, but that criticism should be more critically examined before publication? And that applies to this, if it is considered worthy of print!

If by trial and error we may learn, then let us by all means make errors – and then learn to recognise them!

C. B. V. Francksen
Farnborough
Hants

The author replies:

In C. B. V. Francksen's working model of the Michelson and Morley experiment the balls represent the energy of consecutive cycles of a

light wave, the launcher the source of light and the semi-transparent mirror, the receiver represents the reflecting mirror, and the stationary or moving track represents the stationary or moving ether. The model can be improved by allowing the launcher and receiver to change positions when the light beam is reflected in the experiment. In the fourth paragraph of the letter the receiver's changed rate of reception is analogous with the frequency changing effect of the moving reflecting mirror.

Mr Francksen need have no fear that his letter is unworthy of print. In the fifth paragraph he has pinpointed the basic flaw in the reasoning that gave rise to the experiment. The history of this experiment is dealt with by Dr Berkson in his "Fields of Force" from page 261 onwards. Fresnel had explained the phenomenon of stellar aberration by assuming the ether did not interact with the Earth. When Arago discovered that this phenomenon did not occur when light passed through a prism, Fresnel said that the ether was trapped within the volume of the prism and dragged along the light. Fresnel calculated his 'dragging coefficient', and by passing light through a moving column of water Fizeau proved Fresnel's 'dragging coefficient'. The moving volume of water dragged along the light wave. Stokes had already proposed an alternative theory to explain stellar aberration – the ether was dragged along by the moving Earth – and Stokes' theory cannot explain Fresnel's 'dragging coefficient'.

Michelson and Morley ignored Fresnel and Fizeau and accepted Stokes' theory that the Earth created an ether wind. If the Michelson-Morley experiment is repeated, effectively immersed in a flowing volume of water, their interferometer will show signs of interference.

M. G. Wellard

TELEVISION FOR NO-SIGNAL AREAS

Mr Osborne's case history of a practical application of an 'active deflector' system (May issue) was read with great interest but with some apprehension. This article could well give the impression that such schemes are very simple and demand little more than redundant aerials, salvaged coaxial cables and modified standard television distribution amplifiers employed with ingenuity by an experienced amateur.

My company has become very involved with 'self help' schemes and supplies standard, and specialised equipment together with engineering advice and assistance where necessary. As a result of our involvement and experience, I would like to make the following points:

1. Communities forced to consider 'self help' systems, usually of populations less than 200, are entitled to the best possible television reception, with a target of standards comparable to well-engineered cable systems.
2. Cable systems should be used whenever possible with the advantages of multi television channels, v.h.f./f.m. radio, teletext operation and provision for future channel services.
3. Active deflector systems should be engineered to the same standard as cable systems, where we comply with BS 5603 and CTVR/1. Due regard must be paid to filtering of received channels, minimum transmitter power, and cal-

gineers should be redoubling their efforts to make maximum use of their limited budgets.

Jack Anderson
Dunmurry
Belfast

I do hope that the proportion of letters in favour of your editorial "Microchips and megadeaths" in the November 1980 issue is typical of your postbag and of engineers in general.

I am sorry to recall that, for two years after leaving university, I too worked in 'defence' projects for a leading electronics manufacturer. However, engineers and computer scientists are fortunate in having a wide range of job opportunities available. I would encourage anyone who is employed on 'defence' work (especially projects for other countries which help to fuel wars in which Britain has no interest!) to look for more useful employment. When one leaves defence projects it is a great joy to be able to talk freely about one's work, and to contemplate its use without envisaging catastrophe.

Could *Wireless World* take matters further by publishing one or more detailed articles listing the firms students should avoid when looking for employment? The Campaign Against Arms Trade (5 Caledonian Road, Kings Cross, London N1 9DX, tel: 01-278 1976) would be only too happy to supply information to any other interested readers.

David Bailey
Manchester 16

OPTO-ELECTRONIC CONTACT BREAKER

Your article on opto-electronic contact breakers (April issue) suggests that they can be fitted to any make of distributor. My own Hillman Hunter uses a distributor in which vacuum advance moves one of the contacts of the contact breaker and, as you can see from the enclosed pages of the maintenance manual, all vacuum advance would be lost if the contact breaker were changed as the author suggests.

M.D. Samain
University of Salford

The author replies:

Mr Samain is, of course, correct in saying that the opto-electronic contact breaker is not suitable for sliding contact type distributors. This type of contact breaker is designed to extend contact life by spreading the area of contact erosion, but must be regarded as a palliative rather than a cure for the well known problems of conventional ignition systems. It is particularly unfortunate that no proprietary devices are available to replace such a contact breaker, for the same reasons which rule out my own device.


On re-reading the article as published I could not, however, see where it was suggested that any make of distributor was suitable for conversion.

J.R. Watkinson

DIVIDING BY FRACTIONS

Referring to the article by Gilbert Pearson in your April 1981 issue, which described a method of division from PAL sub-carrier frequency to line frequency by digital counters, I would like to suggest a simpler way to accomplish this.

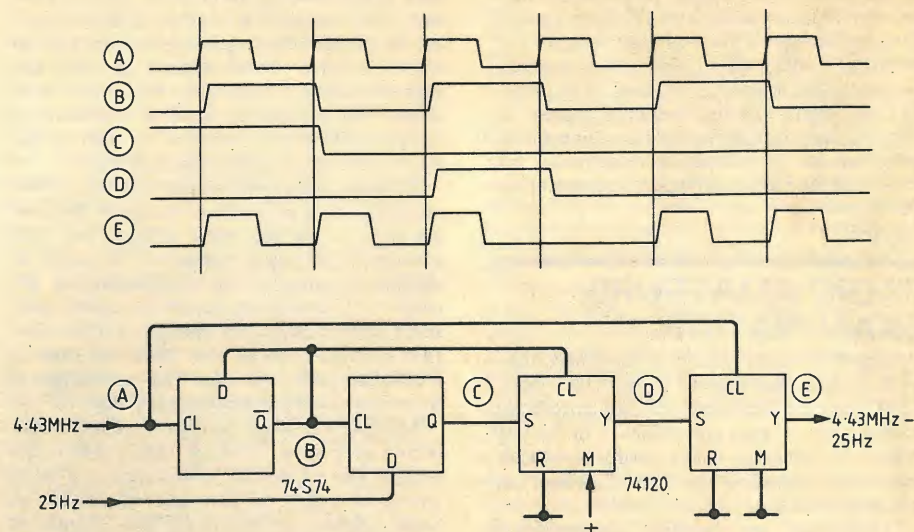By using the dual pulse synchronizer SN74120 together with a dual D flip-flop SN74S74, you can easily "remove" a single period of the 4.43MHz signal 25 times per second. After counting down by 1.135 you have a frequency of 3906.25Hz with very low jitter. Using a simple phase locked loop, either a



4MHz master clock or a 31250Hz double line frequency is easily produced.

Looking at the signal diagram and the 74120's truth table, you can see how the circuit works with only two digital integrated circuits.

Knut A. Lyster,
Lyster Elektronik
Royken
Norway

With reference to the article "Dividing by fractions" in your April 1981 issue, I would like to draw your attention to a more general method of generating a sequence of p pulses, as regularly spaced as possible in q clock periods. The technique is described in a paper 'The use of digital techniques in television waveform generation' presented at the 1974 International Broadcasting Convention and it is the subject of British Patent No. 1 455 821.

A particular feature of this method is that it generates a 'residue' function, which represents the time difference (jitter) between each output pulse and its ideal position. This residue can be added with appropriate polarity, amplitude and timing to the control loop of a voltage-controlled oscillator in such a way as to eliminate the need to filter any of the systematic jitter components in the phase-locked loop.

This technique is used in commercial equipment (such as the HP 8662A Synthesised Signal Generator described in February 1981 *Hewlett-Packard Journal*) and the associated counting methods are used frequently in digital television processing when a line harmonic clock rate is used to handle signals related to PAL subcarrier, whether or not it is 'mathematically' locked.

John Chambers
BBC Research Department
Tadworth
Surrey

ETHICS IN ACTION

There is no escaping the moral responsibility placed on all of us to examine our role and function in society (June letters). We should see whether we are contributing directly or indirectly to the design and manufacture of armaments, or other socially unacceptable products, and then reconcile this role with our conscience, ethics, religious beliefs, or whatever standards we live by, and then act upon the outcome. All my life I have refused to work on anything whatsoever to do with armaments or warfare, and any price I may have paid has been trifling in comparison to the degree of sympathy and respect I have encountered, often from the most

unexpected quarters.

Western civilisation and technology cannot continue much longer without facing the facts and realising that there will be consequences arising directly from its actions - mostly, I fear, very unpleasant ones - but faced they must be, and your courageous editorials will do much to start electronic engineers thinking.

Robin H. Mann
C.E.G.B.
Barnet
Herts

PICKABACK SPARKS

Regarding Mr A.R. Churchley's remarks in April letters, it may be of interest to refer to the paper in the *Journal of the Institution of Electrical Engineers*, vol. 93, part IIIa, no. 5, 1946, "The development of triggered spark gaps for high power modulators" by J.D. Craggs, M.E. Haine and J.M. Meek. This paper describes the development of triggered spark gaps, during the war years, for use in short pulse modulators for magnetrons for radar applications.

The pulses generated by the discharge of artificial transmission lines were one or two microseconds in duration and up to a few megawatts power. Repetition frequencies up to 2,500Hz were achieved. Early work was on three electrode spark gaps in air. Later this was extended to similar gaps sealed in glass vessels containing a pressure of up to three atmospheres of a mixture of argon with a 6-7% oxygen; the latter to suppress the long lived metastable state in argon which inhibited deionisation. The ratio of the trigger pulse energy to that of the main pulse was 10^3 - 10^4 to 1.

The transmission lines were charged from a d.c. source through a choke. At first this was done at the resonant frequency of the choke and the transmission line capacitance, so that the line charged to twice the direct voltage. To achieve a variable frequency system a series diode allowed the line to charge to twice the direct voltage and then await the occurrence of the trigger pulse. However, it was later found that, without the diode, the frequency could be increased to any value above the resonant frequency and still give the doubling of voltage. The charging waveform then tends to a linear rise.

It may be of interest that patents were applied for and granted only for the sealed systems. The open air gaps system was rejected by the Patent Office because of a similar system patented in the last century for a lightning arrester.

M.E. Haine
Much Hadham, Herts



flexible

The SSG520 10 to 520MHz synthesized signal generator is flexible enough to meet your need

REMOTE PROGRAMMING

This option simplifies remote control of all major functions

IEEE488 INTERFACE

Add-on module for low cost microcomputer controlled A.T.E. Switching module and other IEEE488 accessories available

TRANSMITTER TESTING

Compatible with TTS520 transmitter test set for complete testing of base stations, mobile or fixed radios up to 100 watts rating, pocketphones, pagers, etc.

Send for our comprehensive folder of r.f. test equipment NOW!




Farnell

FARNELL INSTRUMENTS LIMITED
SANDBECK WAY · WETHERBY
WEST YORKSHIRE LS22 4DH
TEL. (0937) 61961 · TELEX 557294
OR HARPENDEN · TEL. (05827) 69071

WW - 075 FOR FURTHER DETAILS



AMCRON INDUSTRIAL MUSCLE

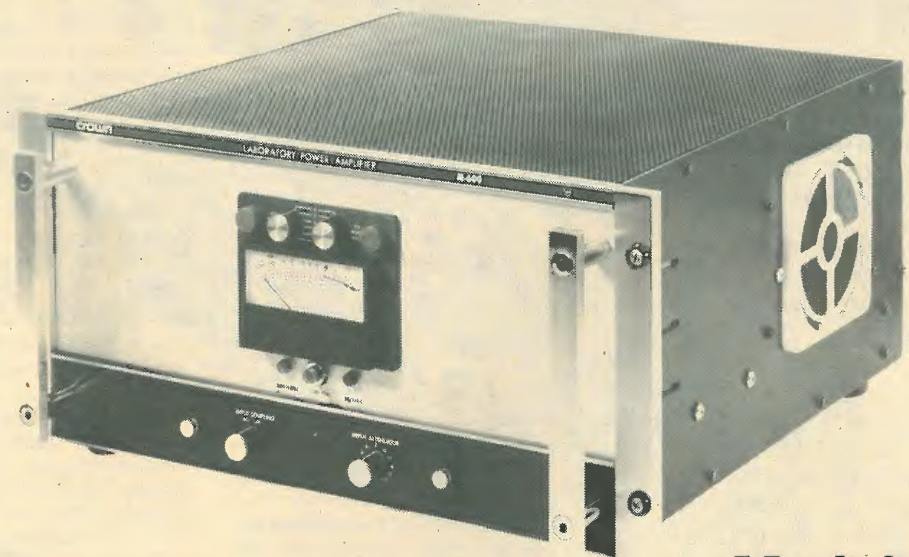

Model — M600

- ★ POWER RESPONSE DC — 45KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5KW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.).
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KVA.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS.
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.
- ★ UNITS AVAILABLE FROM 100VA-12KVA.

For full details on all Amcron Products write or phone Chris Flack



Analogue Associates

PROFESSIONAL AUDIO AND INDUSTRIAL ELECTRONICS

P.O. BOX 3
ATTLEBOROUGH
NORFOLK NR17 2PF
Tel: 0953-452477

WW — 031 FOR FURTHER DETAILS

Wafer-scale integration

Reducing costs by using i.c. chips on the wafer

by Ivor Catt
Microprocessor Applications Project, Watford College

Much of the cost of manufacturing electronic equipment with integrated circuits lies in making connections to the chips and interconnecting them. Considerable reduction in this cost is claimed for the method proposed here in which memory chips are used while they are still on the semiconductor wafer, the whole of which is permanently built into equipment. On the wafer, a chain of good chips is formed under external control to produce a long serial memory. Any bad chips are automatically by-passed without requiring programming of the metallization that interconnects them or advance knowledge of the distribution of the bad chips on the wafer.

The traditional method of manufacture of a "silicon chip" microcircuit is as follows. A wafer of pure silicon material several inches in diameter is sent through a series of furnaces where hot gases are diffused into selected areas of the surface, creating some 500 identical two-dimensional microcircuits ("chips") on the surface, half of them perfect and half of them faulty. At this stage, a minute fraction, perhaps 1%, of the total manufacturing cost of a complete computer system has been spent.

The microcircuits are tested using a wafer probe and marked to distinguish the good from the bad. The wafer is then cut up into individual microcircuits measuring perhaps one tenth of an inch square, and each good one individually packaged in a one inch long black box with about fourteen contacts. The black boxes are tested and assembled into printed circuit boards. Then the boards are tested and assembled into systems which are also tested (see Fig.1).

What is being called "the microelectronics revolution" is the successful attempt to reduce the cost of all these stages by squeezing more and more circuitry into each microcircuit (or black box) so that a complete deliverable system can be made with fewer of them. However, more circuitry on a chip means that each chip must be larger and more likely to be useless as a result of its including a faulty spot on the wafer. This leads to lower yield and increased cost, and the practical limit to the size of a chip is in the region of one or two tenths of an inch square. Also, as the complexity of a microcircuit increases, the cost

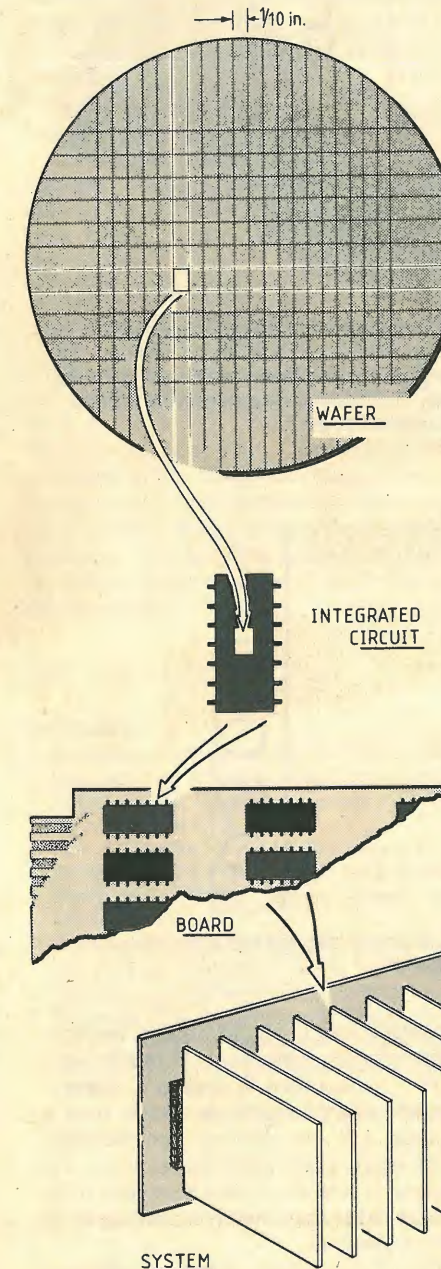


Fig. 1. Main steps in the construction of electronic equipment from the conventional silicon chip.

of testing escalates in geometric proportion, so that even today's conventional, relatively simple microprocessors and r.a.m.s are expensive because of appalling testing problems.

Wafer scale integration is an alternative approach to the above. Although nominally divided up into "chips", the

wafer is never dissected, and there are built-in interconnections between chips. The full wafer, including faulty chips, is installed in the final electronic system. All the costly conventional manufacturing stages — testing the wafer, dicing, packaging, testing, interconnection, testing — are omitted.

The wafer is conventional except that metallization overlaps between chips to give the inter-chip connections mentioned above. Grids of metallization lines across the wafer distribute voltage supplies and clocks. Crossovers between grids are achieved by two layer metallization. An array of fusible links on the grids localizes the effect of any shorts between voltage supplies. Each chip contains bonding pads for voltage supplies and clock inputs, but only a small number of these pads are connected to the outside.

There are four classes of w.s.i. as shown in the chart in Fig.2. Of these, two were tried and abandoned or found wanting. One is a possible dream for the future. That leaves the fourth, "fault tolerant w.s.i." Now that everyone realizes that the more complex microcircuits already on the market are untestable, it is coming to the fore as the main contender for further advance in microelectronic technology.

The "fault tolerant" interconnection approach is based on the fact that today's "chip" contains a massive quantity of circuitry — more than 5,000 transistors — the same amount of logic as was contained in a complete general purpose computer in the 1960s. The process of getting rid of bad chips and linking up good chips into a perfect machine is delayed until after the wafer has been installed in a working machine, and even after the machine has been switched on for use in the morning. Further, the interconnections between good chips are "broken" when the machine is switched off, so that every time it is switched back on the machine is rebuilt from virgin circuitry during the first five minutes of operation. A very small proportion (some 5%) of the circuitry in each chip is devoted to this reconstruction process after switch on. The reconstruction is under the control of a control board containing logic of conventional design (100 packages which could of course be integrated into a single microcircuit). This control board is called "chip Z". The rest of this article describes the author's approach to fault tolerant w.s.i.

The aim is to build up on the wafer a

spiral of interconnected good chips which avoids the bad chips. This is achieved by a gradual growth process, shown in Fig.3, where additional chips (for example F) are added to the growing spiral, one by one; the latest chip being tested and discarded if found by chip Z to be faulty. Chip Z communicates with it *via* the good chips ABCDE already in the spiral.

We end up with one or more spirals of perfect tested chips (Fig.4), which for architectural purposes might just as well lie on a straight line.

In the simplest machine, of which the working model has already been built under Russell C. Aubusson at the Middlesex Polytechnic, the wafer accommodates one (or more) shift registers which can usefully replace computer disc memory and get rid of the inconvenience of rotating parts.

The next machine in the family has the addition of a fast (or control) line to the previous slow (or data) line, as shown schematically in Fig.5. Serial commands travel rapidly down the spiral along the fast line, checking the address field in each chip they pass and completing a read or write with the appropriate word. The addition of the fast line speeds up memory access from 20 milliseconds to about 5 microseconds, a speed approaching that of conventional random access memory. Although somewhat slower than r.a.m. of conventional design it is attractive because of its extremely low cost, between 10 and 100 times cheaper than what conventional fabrication can achieve, and also because it is self-repairing. If a fault develops, it is only necessary to switch off the machine and the memory will be repaired on switch-on, the newly failed chip being avoided when the new spiral is formed. Because of cost reduction and reliability improvement, computers could be expected to incorporate r.a.m.s using w.s.i. as a matter of course when the memory size is 256,000 words or more.

The rest of this article outlines the opportunities open to us via w.s.i. once we break out of the stranglehold of the Von Neumann computer architecture, an archaic design more than a third of a century old which has set the pattern for all computers, microprocessors and microcomputers up to the present time (see editorial, February 1981 issue, p.31).

Over the years the idea has become entrenched that electronic computers are 'information processing' devices, a phrase which implies sequential processing in the same way as a doctor sees his patients sequentially, forgetting all about one patient when he turns to the next. To develop the analogy further, it has become accepted that the doctor should have no recollection of what the patient's third finger looked like when he examines the fourth, and so on. Before moving on to examine the fourth finger, the doctor notes down in the record the state of the third finger, and then forgets all about it.

It is remarkable, and in my opinion unfortunate, that the conventional, schizoid computer is regarded as able to make a reasonable showing at performing quite complex tasks in spite of its being virtually

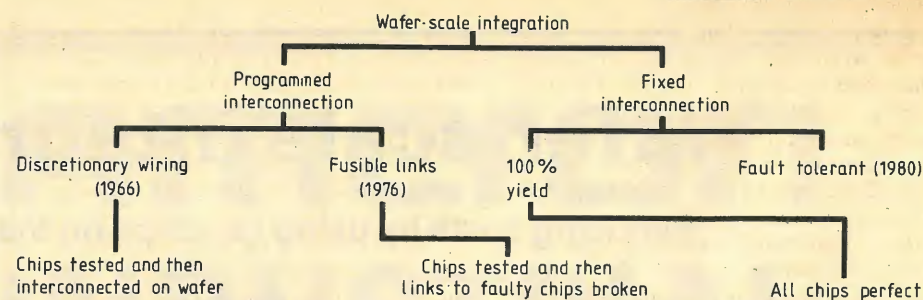


Fig. 2. Chart showing variants of wafer-scale integration and the condition of the chips resulting from these methods.

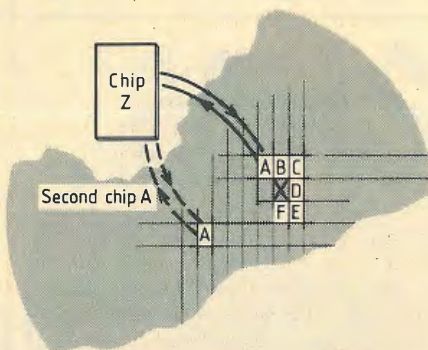


Fig. 3. Process of building up a spiral (or spirals) of chips on a wafer by adding contiguous good chips and avoiding faulty chips. This is done by external control via the external chip Z.



Fig. 4. Schematic of a spiral built up on a wafer.

completely split down the middle, between memory and processing. However, my book "Computer Worship" lists a number of applications in which such a machine will not perform satisfactorily. These are generally applications where it is required to operate on data according to its content rather than merely according to its address location.

Wafer scale, fault tolerant hardware leads us to the possibility of a very cheap, reliable machine of a different kind. It is clear that more sophisticated operations than "read" and "write" could easily be performed in a processing node. For instance, the data field on the fast line in Fig.5 could be added to the data field on the slow line rather than merely replace it. That is, we could have an "add" command instead of a "write" command. This is the first step towards operating on more than one word in the store at the same time—that

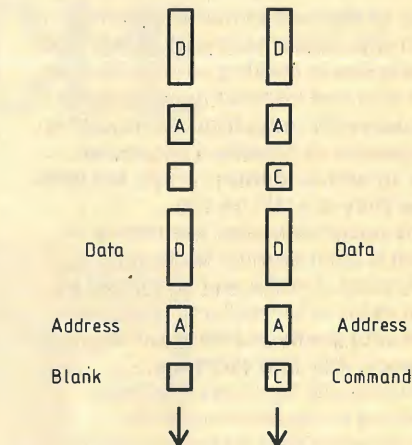


Fig. 5. Schematic of a more advanced system in which a fast, or control, line is added to the slow, or data, line. This fast line carries commands to the data line and allows more rapid memory access than with the simple memory system.

is, towards distributed processing (a much misused phrase). A number coming down the fast line can be added to more than one word in memory at the same time.

A major break with tradition should be noted. Whereas a word in memory has traditionally been addressed (accessed) by its physical location, words in this kind of memory are addressed by one field within the word. That is, each word carries its address around with it. We actually have a content addressable memory (=associative memory) masquerading as a r.a.m.

We can consider moving forward towards even more powerful, more complex machines. Basic principles are sketched in Fig.7. It is possible to send a "loop" com-

mand down the fast line, with the result that all words get trapped in tiny loops rather than continuing in a "follow my leader", barrelling mode. Further, a "mixed mode", or "precess" command can be sent down the fast line, causing words of one class to loop while words not of that class barrel.

The "mixed mode" makes it possible for any word in memory to have rapid access to all other words in the memory. For example, in the case of a machine used to monitor aircraft circling above an airport, one word, containing the co-ordinates of one aircraft, could be caused to barrel past the records of all other aircraft stacked up waiting to land, so that co-ordinates could be compared and a collision risk by that aircraft foreseen.

The next step in sophistication comes when we realise that when a barrelling word passes by a looping word, the situation is similar to a word on the fast line passing a word on the slow line. It is possible to cause barrelling words to act as commands and operate on looping data words so that the overhead on the fast line is reduced.

Methods have been worked out whereby segments of the slow line behave as auto-


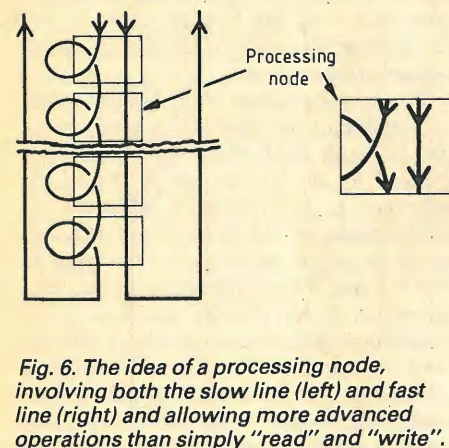


Fig. 6. The idea of a processing node, involving both the slow line (left) and fast line (right) and allowing more advanced operations than simply "read" and "write".

Fig. 7. Different modes of processing: (left) "follow-my-leader" or barrelling mode; (middle) mode in which words are trapped in tiny loops; (right) mixed mode in which some words loop and others barrel.

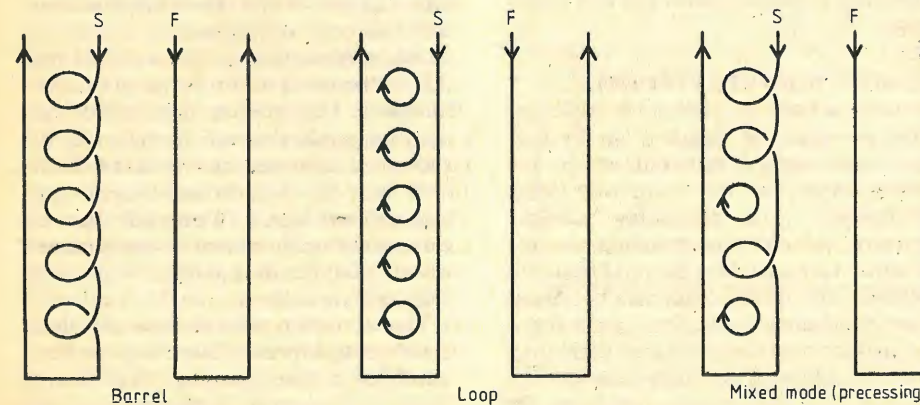

nomous subroutines, the relevant words leaping past each other like a line of children, and flagging when a computational task is completed. We can get an extremely powerful machine which performs many processes at the same time although the hardware is very cheap and self-repairing.

The first project based on the principles described here proved the feasibility of the microelectronics aspects of the subject. With E.A. Newman as its technical head, ACTP (Advanced Computer Technology Project, a section of the Department of Industry) financed the project in the Microelectronics Centre at the Middlesex Polytechnic, where it was led by Dr R.C. Aubusson. ACTP then funded projects to develop a computer architecture. These were at Brunel University under R.M. Lea, and at Prestwick Circuits Ltd.

The Royal Signals and Radar Establishment, Malvern, has funded two projects on the airborne digital signal processing implications of the computer architecture. This work, at Prestwick Circuits Ltd, is led by Ken Wood. Burroughs Corporation, Cumbernauld and San Diego, is now investing in the development of both the microelectronics and of the computer architecture. This work is led by Dr Malcolm Wilkinson. Wafers designed at Cumbernauld, processed in San Diego and then tested in Cumbernauld have successfully generated spirals of more than 200 chips on an imperfect wafer. This lays to rest any technological doubts about the overall feasibility of the invention.

References

1. Aubusson, R. C. and Catt, I. "Wafer-scale integration - a fault-tolerant procedure", *IEEE Journal Solid-State Circuits*, vol. SC-13, no. 3, June 1978.
2. Catt, I. German Patent Application no. P 23 39 089.8-53. US Patent no. 3913072. British Patent no. 1377859. British Patent no. 1525048.
3. Sutherland, I. E. and Mead, C. A. "Microelectronics and computer science", *Scientific American*, September 1977, pp. 210-228.
4. Manning, F. B. "An approach to highly integrated, computer-maintained cellular arrays", *IEEE Trans. Comput.*, vol. C-26, pp. 536-552, June 1977.
5. Catt, I. "Computer Worship," Pitman, London 1974.

Digital storage and analysis of speech

continued from page 48

Reconstructing the analogue waveform

Having digitized and stored a signal, it needs to be passed through a d-to-a converter (digital-to-analogue) and low-pass filter when replayed. D-to-a converters are cheaper than a-to-d ones, and the characteristics of the low-pass filter for output can be the same as those for input. However, the desampling operation introduces an additional distortion, which has an effect on the component at frequency *f* of

$$\frac{\sin(\pi f/f_s)}{\pi f/f_s}$$

where *f_s* is the sampling frequency. An "aperture correction" filter is needed to compensate for this, although many systems simply do without it. Such a filter is sometimes incorporated into the codec chip.

For telephone-quality speech, existing codec chips, coupled if necessary with integrated pre-sampling filters, can be used, at a remarkably low cost. For higher-quality speech storage the analogue interface can become quite complex. Comprehensive studies of the problems as they relate to digitization of audio, which demands much greater fidelity than speech, have identified the following sources of error:

- slow-rate distortion in the pre-sampling filter for signals at the upper end of the audio band;
 - insufficient filtering of high-frequency input signals;
 - noise generated by the sample-and-hold amplifier or pre-sampling filter;
 - acquisition errors because of the finite settling time of the sample-and-hold circuit;
 - insufficient settling time in the a-to-d conversion;
 - errors in the quantization levels of the a-to-d and d-to-a converters;
 - noise in the converters;
 - jitter on the clock used for timing input or output samples;
 - aperture distortion in the output sampler;
 - noise in the output filter as a result of limited dynamic range of the integrated circuits;
 - power-supply noise injection or ground coupling;
 - changes in characteristics as a result of temperature or ageing.
- Care must be taken with the analogue interface to ensure that the precision implied by the resolution of the a-to-d and d-to-a converters is not compromised by inadequate analogue circuitry. It is especially important to eliminate high-frequency noise caused by fast edges on nearby computer buses.

To be continued

Sound synthesis using Walsh functions

Simple introduction to the synthesis of complex vibration modes

by Alan A. Thomas

An experimental approach to additive synthesis employing digital techniques is described. The system enables an infinite number of waveshapes to be generated by a basic fixed Walsh function generator feeding a set of digitally programmed attenuators. By mathematical analysis of known waveshapes the system may be used as a source of sound for music synthesis, provided that a voltage-controlled oscillator and filter are added to the basic system. Using additional hardware, time-dependent spectrum changes are possible.

A sound may be represented by a series of sinusoidal components of particular frequency, amplitude and phase. The lowest frequency component is referred to as the fundamental, first mode, or first partial. Remaining components are then related to this fundamental frequency by simple ratios. Such a relationship is termed harmonic. Not all musical sounds are entirely composed of harmonically related partials; non-harmonic components, that is partials which do not bear simple direct integral ratios to the fundamental, may also be present. This is the reason that simple harmonic analysis may result in a synthesized sound which lacks some of the character of the original, even though care is taken to mimic all other basic properties.

In harmonic analysis, each partial is given the corresponding value of N in the harmonic series; the fundamental is the first harmonic. For a sound composed of frequencies in the ratios 1: 3: 5 for example, the second and fourth harmonics have zero amplitude, and it follows that the frequencies three and five may be referred to as the non-zero coefficients in the harmonic series of the sound under analysis.

Consider now a further sound composed of frequencies in the ratios 6: 12: 15. Can this series be termed harmonic? It is always possible to find a fundamental frequency of which a given series are harmonics; in this example the ratios are all multiples of three and can therefore be regarded as the second, fourth and fifth harmonics respectively of a fundamental frequency, three. In this case both the fundamental and third harmonic are said to have zero coefficients. The fundamental of a harmonic series need not necessarily be present; if the fundamental is present it

should be considered as a non-zero coefficient in the normal manner. An interesting point is that if frequencies of 6, 12 and 15Hz were combined, the resulting complex function would repeat exactly three times per second although the fundamental has zero amplitude. In general therefore, any collection of frequencies can be arranged to fit into a harmonic series, although the fundamental may not be present.

A second important point which must now be made is that there is only one characteristic phase and amplitude for each harmonic which will result in the desired waveshape being realised. How therefore can a harmonic series be set down such that both phase and amplitude information is given for all non-zero coefficient harmonics? A wave of arbitrary phase can be represented as the sum of a sine and cosine wave both of zero phase with amplitudes given by the phase relationship of the original. It follows that a complex periodic function may be represented by a series of sine and cosine functions whose amplitude and period are dependant variables. All that remains is to derive some method whereby the relevant amplitudes may be located. This is Fourier analysis and was first formalized from the basic ideas of other workers by Fourier in 1822 during his work on heat flow. The series of terms derived by Fourier analysis for a particular function is termed the Fourier series and indicates the magnitude of the sinusoidal components. In short, a complex periodic function such as a musical sound may be represented by a series of sine and cosine functions. But first it is necessary to perform harmonic analysis of the waveform to locate the non-zero coefficient sinusoidal components and then apply the Fourier analysis to determine the amplitude of the individual sine and cosine terms.

Fourier sound synthesis

By using a bank of quadrature oscillators—the frequency of which is set by harmonic analysis and amplitude set by the Fourier series of the waveform to be synthesized—a reasonably accurate synthetic sound corresponding to the mode of vibration may be produced. To maintain the same characteristic sound when fundamental frequency is changed the frequency of the generated harmonics must be altered proportionately. In practice this requirement has been the

death knell of Fourier synthesis in commercial electronic instruments. For accurate synthesis, a large number of oscillators are required and the task for the electronic engineer, while not impossible, is complex since it is necessary to arrange that all oscillators remain in quadrature and track each other accurately in frequency while maintaining constant amplitudes.

Clearly some method is desirable whereby the attributes of Fourier analysis as applied to sound synthesis may be maintained but the method of waveform generation altered to remove the inherent practical limitations. The method discussed removes these limitations by transformation of the sine and cosine functions associated with the Fourier series to the rectangular functions of the Walsh closed normal orthogonal set.

The transformation from Fourier series to Walsh/Fourier series for a given function is purely mathematical, and has been detailed by K. Simens and R. Kitai, see reference 1. The principal advantage in transforming to the Walsh/Fourier series as far as sound synthesis is concerned is that the bank of quadrature oscillators employed in direct Fourier synthesis is replaced by a single master oscillator controlling an appropriate digital function generator. Thus by using a single voltage-controlled oscillator the facility to play tunes is realised and the analogous Walsh harmonics, derived within the function generator, automatically track the master oscillator maintaining the characteristic sound of the synthesized mode of vibration, independent of pitch.

Properties of Walsh functions

Walsh functions were first investigated by J. L. Walsh in 1923 and are of purely mathematical origin². Collectively, they form a closed set of orthonormal functions. The functions are defined on a basic interval, in this case time. The sequence may then be repeated to form a set of periodic functions. During each interval the functions may only take on the values of ± 1 and are thus rectangular in form. If the basic interval is subdivided into 2^n equal segments where n is an interger, then the corresponding number of Walsh functions which may be incorporated within the basic interval is $2^n - 1$.

The recursion relationship governing the form of individual functions has been translated to the appropriate digital form by H. F. Harmuth³. Harmuth has shown

that once Walsh functions have been converted to zero and one logic levels, the recursion relationship reduces to modulo-two addition, the logical exclusive-or function.

Certain Walsh functions are analogous to a further set of mathematical functions: Rademacher functions. Rademacher functions are a set of square waves in simple geometrical progression, the recursion relationship for Rademacher functions, and hence the analogous Walsh functions, once translated in a similar manner to the appropriate digital form reduces to modulo-two counting, the logical binary function. It follows that a digital representation of the complete Walsh orthonormal set for a given value of n may be produced by a logic system comprising of exclusive-or gates and binary counters driven from a master oscillator.

Before producing a suitable function generator it is necessary to decide on a suitable value of n . If harmonic followed by Fourier analysis is performed to obtain the appropriate Fourier series for a given function, the resulting series tends toward infinity; that is, the number of sine and cosine functions should ideally be infinite for perfect harmonic representation.

It is no surprise that when the parallel mathematical analysis is performed to obtain the Walsh/Fourier series the number of Walsh functions required for perfect representation also tends toward infinity. This implies that the greater the value chosen for n , the more accurate the final waveform synthesis. In practice n must be limited to a value which is a compromise between acceptable accuracy of synthesis and the amount of hardware involved in the function generator. The effect of limiting n to a finite value will be considered in more detail later.

Basic Walsh function generator

Given $n=5$ a generator will produce $2^5 - 1$ Walsh functions and the number of Rademacher functions will be equal to n , that is 5. The first requirement is to produce the five Rademacher functions. This is achieved by a simple five-bit synchronous binary down counter driven by the master oscillator. The analogous Walsh functions thus produced are wal31, wal15, wal7, wal3 and wal1 at consecutive outputs of the binary counter. The remaining Walsh functions are formed by performing modulo-two addition of the functions so far derived in the appropriate order. Wal2 for example is formed by modulo-two addition of wal1 and wal3. The three functions lying between wal7 and wal3 are formed as follows: wal6 is formed by modulo-two addition of wal7 and wal1; wal5 is formed by modulo-two addition of wal7 and wal2 and wal4 is formed by modulo-two addition of wal7 and wal3. The sequence is straightforward from the examples given. The table lists the complete arrangement for all 31 Walsh functions when $n=5$. The system may be extended for higher orders of n if desired by simply increasing the number of counter sections and exclusive-

Generation of first 32 Walsh functions (wal0 excluded) using binary counters and exclusive-or gates.

Function	Modulo - 2 Division	Modulo - 2 Addition	Function	Modulo - 2 Division	Modulo - 2 Addition
wal31	Oscillator		wal15	wal31	
wal30		wal31, wal1	wal14		wal15, wal1
wal29		wal31, wal2	wal13		wal15, wal2
wal28		wal31, wal3	wal12		wal15, wal3
wal27		wal31, wal4	wal11		wal15, wal4
wal26		wal31, wal5	wal10		wal15, wal5
wal25		wal31, wal6	wal9		wal15, wal6
wal24		wal31, wal7	wal8		wal15, wal7
wal23		wal31, wal8	wal7	wal15	
wal22		wal31, wal9	wal6		wal7, wal1
wal21		wal31, wal10	wal5		wal7, wal2
wal20		wal31, wal11	wal4		wal7, wal3
wal19		wal31, wal12	wal3	wal7	
wal18		wal31, wal13	wal2		wal3, wal1
wal17		wal31, wal14	wal1	wal3	
wal16		wal31, wal15			

or gates and using the same basic sequence.

Synthesis of functions using Walsh harmonic bank

To synthesize a function it is necessary to resolve the Walsh/Fourier series. The non-zero coefficient functions of the series which lie within the range of the generator are then selected and mixed in the proportions indicated by the series.

For example, the non-zero coefficient functions in the range 0 to 31 for the triangular wave given by the Walsh/Fourier series are wal2, wal6, wal14 and wal30. Their relative amplitudes are +0.5, +0.25, +0.125 and +0.0625 respectively. Thus, by selecting these four functions from the Walsh harmonic bank and summing them in the relevant proportions, a triangular wave is synthesized.

The frequency of the waveform depends on the basic interval chosen for the Walsh functions which is in turn determined by the frequency of the master oscillator. If the waveform is to have a frequency f , then the master oscillator frequency must be $2^n f$, where n is as previously defined.

Perfect harmonic synthesis is only possible when an infinite number of Walsh functions are employed. When a finite number is used the synthesized waveform appears in a sampled form, the sample rate being 2^n per period. This results in the wave having 2^n discrete levels within each period. To remove this appearance, it is necessary to integrate the function; in practice this can usually be achieved by simple low-pass filtering. Fig. 1 shows the appearance of the triangular wave just discussed before low-pass filtering. Naturally the number of samples and

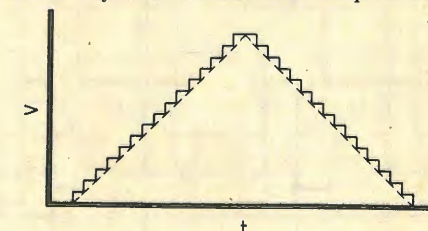


Fig. 1. Triangular wave is synthesized by selecting four functions, wal2, wal6, wal14 and wal30, and summing in relevant proportions

therefore the accuracy of the waveform can be increased by employing a higher order of n but at the expense of more hardware.

Summing of the various Walsh functions may be performed by a standard virtual-earth operational amplifier arrangement, the proportions of mix being scaled to best suit the practical device.

If the master oscillator is made voltage-controlled the frequency of synthesized waveform may be adjusted in the traditional manner. If large variations of frequency are required, the low-pass filter must also be voltage-controlled.

Digitally programmable attenuators

If each of the Walsh functions are fed to a digitally programmable attenuator the outputs of which are then mixed an entirely flexible system is produced which can produce virtually any desired waveshape. This, coupled with a voltage-controlled master oscillator and filter, enables a musical device with infinite tonal qualities to be realised. Further, by altering the program of the attenuators during the life of the wave, the spectrum may be made time-dependent, enabling wave shapes such as that of the piano to be synthesized.

An experimental system is shown in Fig. 2. Referring to this figure, a voltage-controlled oscillator generates a rectangular waveform at a frequency 2^n times higher than the frequency desired for the synthesized waveform. A Walsh function generator comprising binary counters and exclusive-or gates then generates, under control of the v.c.o., $2^n - 1$ Walsh functions. Each Walsh function is then fed to a digitally programmable attenuator (d.p.a.); only one path is shown in Fig. 2. The d.p.a. is controlled by a read-only memory (r.o.m.) which stores up to 32 eight-bit digital words. This enables up to 256 levels of attenuation to be programmed, any 32 of which may then be selected by addressing the appropriate digital word. The order in which the digital words are selected is controlled by a sequencer which comprises of JK flip-flops and logic gates; the sequencer may also be made programmable if desired. The voltage-controlled oscillator which

feeds the Walsh function generator also feeds a divide-by-*n* counter. In this manner the period over which the coefficient of the particular Walsh function is varied is controllable. Once again, the counter cycle is made programmable.

The output of each d.p.a. is then summed in a traditional virtual earth summing amplifier, the output of which is fed to a voltage-controlled filter (v.c.f.), this being controlled by the same control voltage which controls the v.c.o. Thus, the v.c.o. and v.c.f. track together. The total system results in a waveform being synthesized in which the spectrum may be altered in a programmable manner, both in terms of type and rate of spectrum change. In practice the sequence is initiated by the keyboard controller.

Polyphonic waveform synthesis

By the application of appropriate Walsh/Fourier series both triangular and sawtooth waveforms may be synthesized in a manner compatible with existing organ divider techniques.

The principle by which polyphonic operation is achieved in electronic organs is well known. Briefly, pitches ratioed in accordance with the scale of equal temperament are generated for the highest octave; either 12 independent oscillators are employed or a single master oscillator working in conjunction with a digital function generator. Lower octaves of each scale member may then be generated by the use

of binary dividers, as tones spaced at octave intervals have a 2:1 frequency ratio. By this method, any number of pitches may be generated polyphonically, while the number of oscillators required need not exceed 12. Being of digital form the method has the disadvantage that only one waveshape is directly available at the divider outputs, namely a squarewave. For reasonable additive sound synthesis a minimum of two additional waveshapes should also be simultaneously available: triangular and sawtooth waves.

If the organ dividers are arranged to be of the form shown in Fig. 3, the signals present at the various outputs become not only octave-related but also take the form of useful Walsh functions and may be employed in direct Walsh/Fourier synthesis, enabling a practical circuit for the simultaneous generation of square, triangular and sawtooth waveforms to be constructed.

Referring to Fig. 3, given that the index *n* = 5, five Walsh functions are directly available from the divider chain wal31,

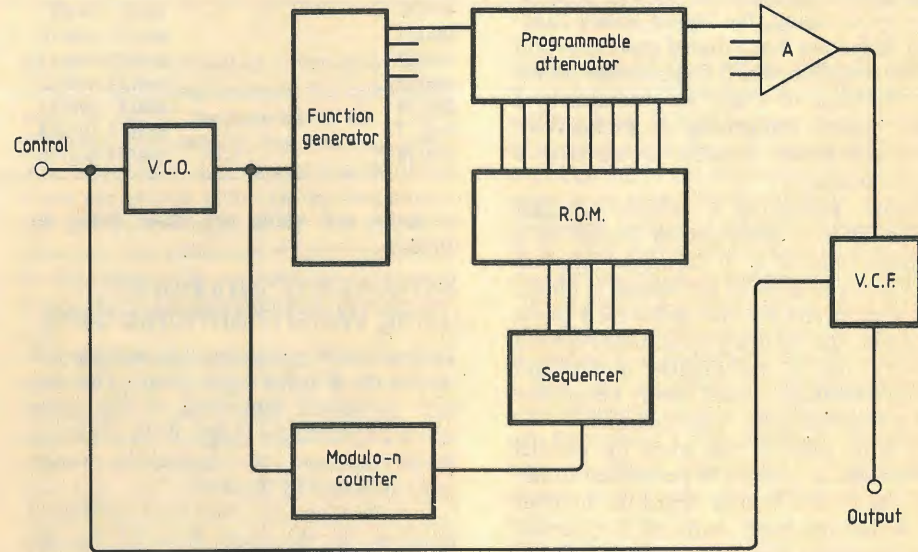


Fig. 2. If each of the Walsh functions are fed to a digitally programmable attenuator and the outputs mixed virtually any waveshape can be produced.

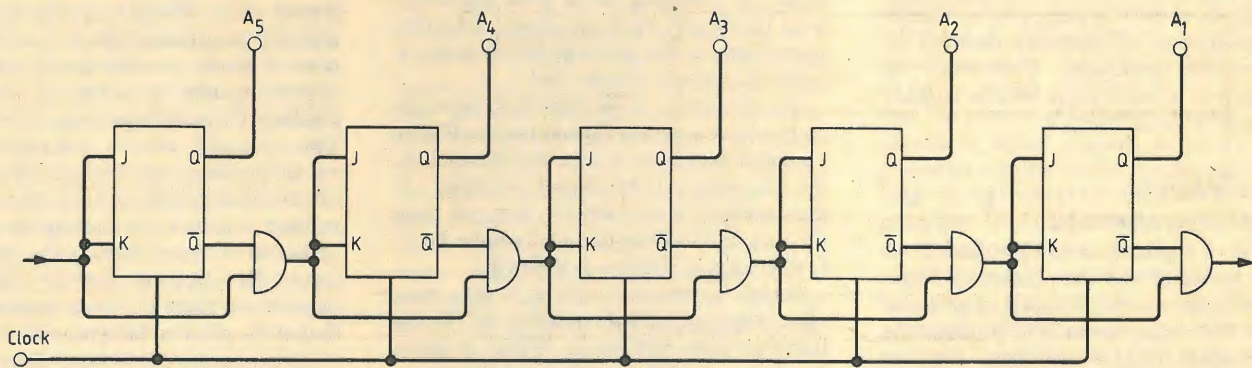


Fig. 3. Binary divider chain providing wal31, wal15, wal7, wal3 and wal1 at consecutive outputs.

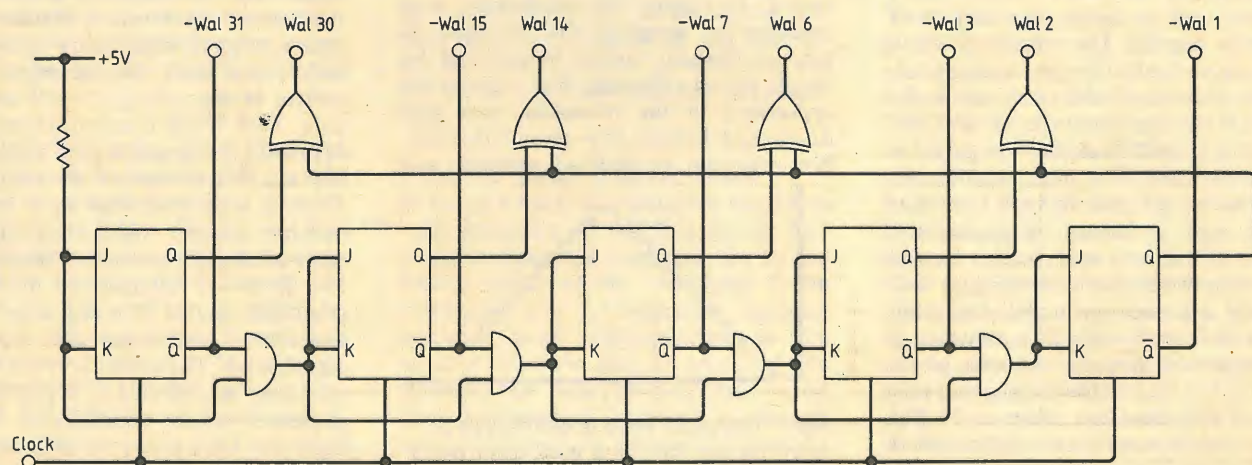


Fig. 4. By adding inverters and four exclusive-or gates triangle and sawtooth waveforms can be synthesized.

wal15, wal7, wal3 and wal1 at consecutive outputs of the divider. The Walsh/Fourier series of a sawtooth waveform, limited to the first 32 functions applicable when *n* = 5 is as follows

$$-1wal1, -0.5wal3, -0.25wal7, -0.125wal15, -0.0625wal31.$$

The negative signs in the series are interpreted as function inversion for practical purposes. All the necessary functions for sawtooth waveform synthesis are directly available from the divider outputs, provided function inversion is taken into account.

Now consider the Walsh/Fourier series of a triangular waveform:

$$+0.5wal2, +0.25wal6, +0.125wal14, +0.0625wal30.$$

None of these four functions are directly available at the divider outputs. But the table shows that these four functions may be derived by the use of only four exclusive-or gates. The complete arrangement for deriving all the necessary function for synthesis of both triangular and sawtooth waveforms is detailed in Fig. 4.

To sum these functions accurately in the relevant proportions they are rewritten in more familiar binary-weighted form:

$$+2^4wal2, +2^3wal6, +2^2wal14, +2^1wal30.$$

and for the sawtooth wave:

$$-2^4wal1, -2^3wal3, -2^2wal7, -2^1wal15, -2^0wal31.$$

By applying the functions to the appropriate inputs of two d-to-a converters, accurate summation of the functions may be realised. Although of higher cost, d-to-a converters have two distinct advantages over operational amplifier summators. Firstly, as the output of a converter is in binary-weighted proportion to a single reference voltage or current, the accuracy of summation becomes independent of any variations in the logical 1 or 0 levels present at the outputs of the dividers or exclusive-or gates. Secondly, high accuracy summation resistors need not be fabricated.

Fig. 5 shows a practical circuit developed for evaluation of the system using readily available integrated circuits. For economy, the facility for simultaneous waveform generation has been dropped during evaluation; only a single d-to-a converter is employed together with some additional data selection logic.

Digital-to-analogue conversion

The d-to-a converter is the six-bit Motorola MC1406L, whose digital inputs are compatible but inverting which must be taken into account when selecting appropriate outputs from the dividers. The device requires an external reference for its operation and, as the output is in the form of a current ratio, current-to-voltage conversion is also necessary in this particular application. The reference for the MC1406L device, IC₈, consists of the tem-

perature-compensated zener diode with a current of 7.5mA supplied through R₁, with C₁ providing a.c. decoupling. Because the negative reference input (pin 13) of IC₈ is the high impedance node of the internal reference amplifier, buffering is not necessary. The device requires its reference in the form of a current, determined by resistors to pin 12 and the reference voltage. With the potentiometer set to mid-position, the values are selected to produce a reference current of -2mA. The value of R₃ is selected so that both reference input points have the same source impedance, to reduce reference current error and temperature drift. The internal reference amplifier also requires compensation to maintain stability; with the values selected for the input resistances, the compensation capacitor C₂ must have a minimum value of 180pF to maintain an acceptable phase margin.

The output of IC₈ (pin 4) provides a current which is a linear product of a six-bit digital word and an analogue reference voltage. The output current is negative and is defined from the equation

$$-I_o = I_{ref} \left(\frac{A_1}{2} + \frac{A_2}{2^2} + \frac{A_3}{2^3} + \frac{A_4}{2^4} + \frac{A_5}{2^5} + \frac{A_6}{2^6} \right)$$

where *I*_{ref} is the reference current and A₁ through to A₆ are the digital inputs, m.s.b. through l.s.b. respectively, A_{*n*} = 0 if the input is at logical 1, and A_{*n*} = 1 if the input is at logical 0. As the voltage at the

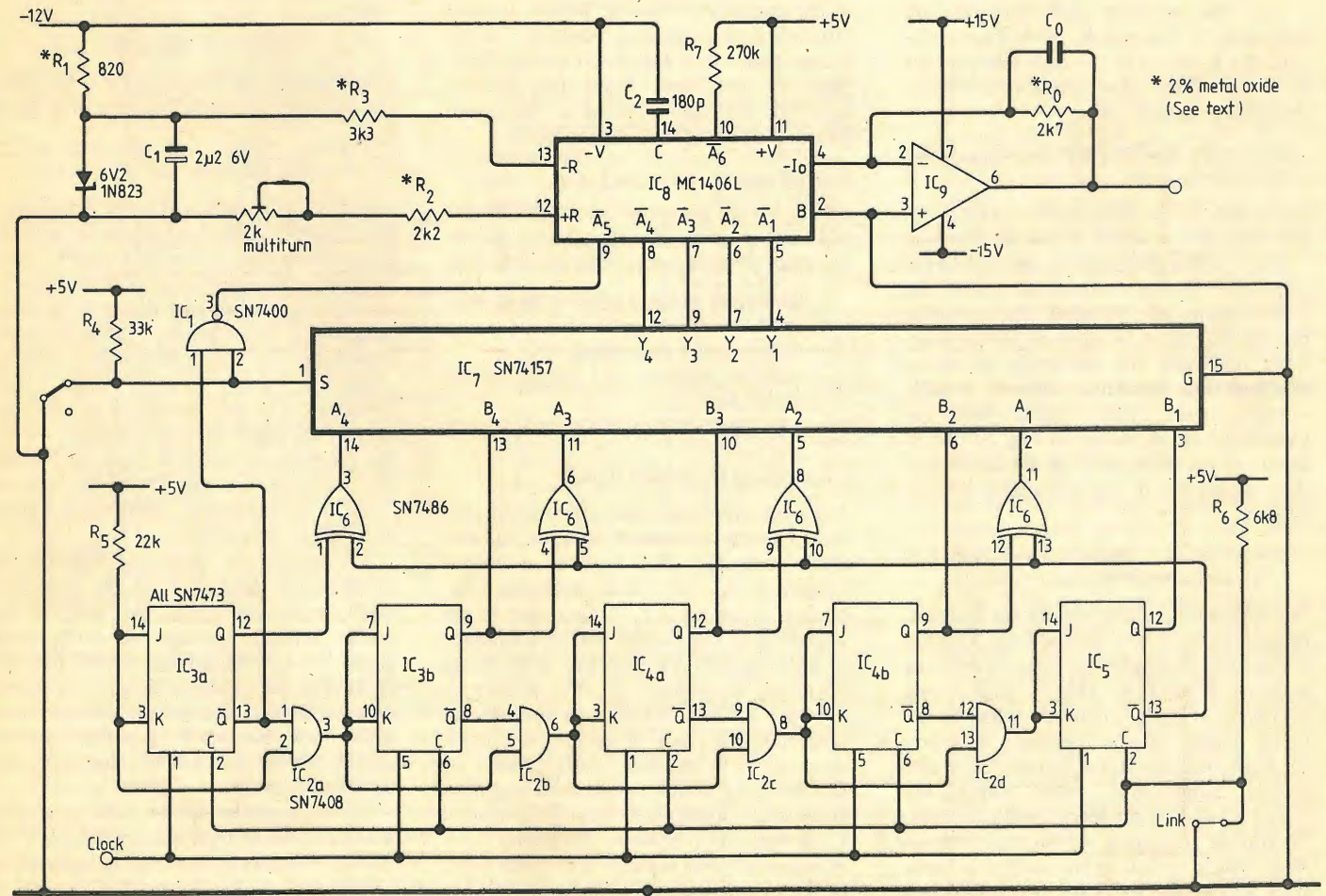


Fig. 5. Practical circuit for system evaluation omits simultaneous waveform generation for economy.

output must not rise above $\pm 0.4V$ for accurate conversion, simple resistive current-to-voltage conversion is not practical and an op-amp converter IC₉ is used. The virtual-earth effect of the amplifier maintains the voltage at pin 4 of IC₈ within the permitted value, while the output voltage ($-I_o R_o$) may be set to any reasonable value by the suitable selection of R_o . With R_o set at $2.7k\Omega$, the output voltage may be set to a peak value of $+5V$ by adjustment of the reference current control. Capacitor C_o provides low-pass filtering of the output waveform; the operational amplifier is a 741 general-purpose device.

Digital function generation and selection logic

Although the MC1406L device is a six-bit d-to-a converter, only five-bit conversion is required in this application. To maintain maximum accuracy during conversion, the input corresponding to the least-significant-bit is dropped and disabled by connecting to $+5V$ through R_7 . The remaining most-significant-bits are supplied through data selection gates. The four most-significant-bits are supplied with an SN74157N, quadruple 2-to-1-line data selector, IC₇. Hence either of two functions may be presented to each of these inputs as required. The least-significant fifth-bit is a special case, since it is not required during triangular waveform synthesis if the desired sample-rate is defined on the time axis. This bit is therefore supplied through a simpler nand-gate arrangement, IC₁.

The data selectors and nand-gate are controlled by the switch. With it open-circuit, the B-inputs of the data selectors are allowed to their respective d-to-a conversion points, namely:

wal1 to A₁, wal3 to A₂, wal7 to A₃, and wal15 to A₄.

In the case of the least-significant fifth-bit, the nand-gate is allowed and the function -wal31 is inverted and transferred to the respective d-to-a conversion point A₅. After taking into account the inversion provided by the d-to-a inputs, all the functions necessary for sawtooth waveform synthesis are presented, namely -wal1, -wal7, -wal15, and -wal31. With the switch closed, as shown in Fig. 5, the A-inputs of the data selectors are allowed to their respective d-to-a conversion points, namely:

-wal2 to A₁, -wal6 to A₂, -wal14 to A₃, and -wal30 to A₄.

In the case of the least-significant fifth-bit, the nand-gate is now disabled and a logical 1 is applied to disable the respective d-to-a conversion point A₅. Hence, after taking into account the inversion provided by the d-to-a inputs, all the functions necessary for triangular waveform synthesis are presented, namely wal2, wal6, wal14, and wal30. Dropping the least-significant fifth-bit during triangular waveform synthesis must result in this wave having a lower peak amplitude than that of the sawtooth wave. The amplitude variation is only around 3%, and is sufficient to warrant the

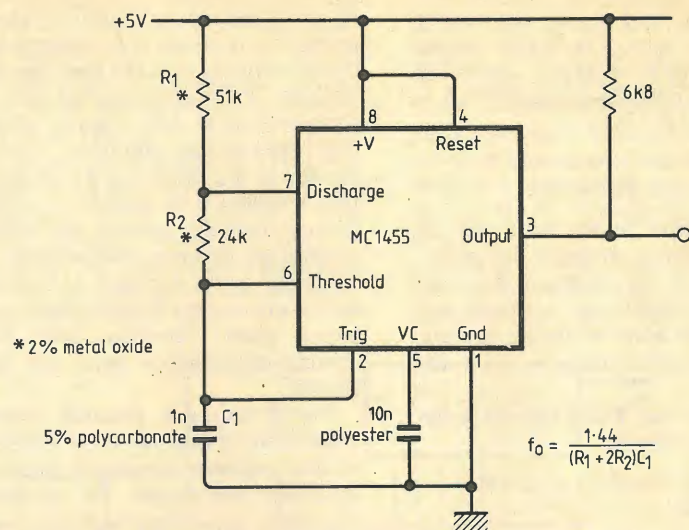


Fig. 6. Clock generator frequency is set to $2^5 f$ for testing dynamic operation of Fig. 5.

otherwise necessary switching of the current reference.

The divider, comprising IC₃, IC₄ and IC₅, is a series of individually clocked master/slave flip-flops controlled appropriately at their JK inputs via and-gates IC₂. Collectively they constitute a five-bit synchronous ripple-through gated binary down-counter which generates the control of a clock-generator, five basic Walsh functions. Four true functions are supplied to the appropriate B-inputs of the data selectors, while a fifth and inverse function is supplied to the nand-gate as required. Four true functions are also fed to the exclusive-or gating where, in conjunction with a common function -wal1, the necessary four additional inverse functions are generated. These four inverse functions are then supplied to the appropriate A-inputs of the data selectors.

Setting-up procedure

Setting up the generator is straightforward and only requires the adjustment of the reference potentiometer. The procedure is

- set switch to open position as in sawtooth waveform synthesis
- fit temporary link shown
- monitor positive d.c. output of the generator
- adjust potentiometer to set d.c. output to $+5V$
- remove temporary link.

The generator may now be tested for correct dynamic operation using a suitable clock generator, Fig. 6. For an output frequency f_o , the clock generator frequency is set to $2^5 f_o$. Using the values suggested in Fig. 6, the output frequency is approximately 440Hz. Maximum operating frequency of the divider is around 5MHz, while the maximum operating frequency of the d-to-a conversion section is predominantly limited by the slew-rate of the operational amplifier current-to-voltage converter. The value of C_o depends on the output frequency f_o . It is suggested that initially the $-3dB$ point of the operational amplifier is set to $2^5 f_o$. Thus $C_o = 1/2\pi 2^5 f_o R_o$. This gives a value of $4.7nF$.

Practical extension for full polyphonics

By applying appropriate Walsh functions to separate summators any number of different waveshapes may be synthesized simultaneously at a given frequency. But for full polyphonics, simultaneous multi-frequency generation of these waveshapes must also be arranged. As an aid to locating functions which form a useful geometrical progression in frequency, an analogy with sine and cosine notation is again useful. Designating the odd and even indexed functions sal and cal respectively, one obtains

$$sal(a') = sal(2a+1)$$

where the sal function of index a' has twice the frequency of the sal function of index a , and

$$cal(b') = cal(2b)$$

where the cal function of index b' has twice the frequency of the cal function of index b . From this it may be deduced that the functions at consecutive outputs of the divider are octavely related and form a geometrical progression in frequency. For multi-octave generation of the functions -wal31, -wal15, -wal7, -wal3, and -wal1 therefore, it is only necessary to select the correct extended-divider outputs. -wal1, for synthesis purposes at pitch $A_2(880Hz)$ for example, is the identical function -wal3, for synthesis purposes at pitch $A_1(440Hz)$, and so forth.

To extend the generator scheme for multi-octave generation of the functions wal30, wal14, wal6, and wal2 however requires separate groups of exclusive-or gates. For correct frequency, wal2 at pitch $A_2(880Hz)$ for example should be formed by modulo-two addition of the functions wal1 and wal3 at pitch A_2 , giving frequencies of 880Hz and 1760Hz for wal1 and wal3 respectively.

Thus extension of the basic generator scheme to full polyphonic capability, while viable, requires a formidable amount of hardware in m.s.i. form. With a view to

continued on page 82

Which way h.f. broadcast receivers?

Proposals for the development of s.w. sets

by Y.-C. Heng and R. C. V. Macario, University College of Swansea

With a vast number of shortwave receiver sets around the world, estimated as being over 100 million sets in regular use, and with a majority of listeners with little or no technical knowledge, using their sets in a wide variety of environments, it is worth taking a look at methods for improving the design of h.f. sets. The use of digital tuning techniques and the incorporation of microprocessors are discussed.

According to conservative estimation, there exist in the world today between 200 and 300 million radio sets capable of shortwave broadcast reception. A regular audience approaching 100 million is also estimated. The figure must surely encourage shortwave broadcasters, but also indicates how important is the function of shortwave broadcasting. It is also estimated that there are one million amateur radio enthusiasts (class A) around the world, but as this is only 1% of the suggested audience clearly the majority of shortwave broadcast listeners have relatively little technical interest or perhaps background and accept comparatively inexpensive receivers. In addition, listeners operate their sets either in an environment with a high level of man-made noise or have a very inefficient aerial. On the other hand, they are usually hampered by difficult tuning operation, undefined signal reception, and poor receiver stability, yet form the majority of shortwave broadcast listeners. This article therefore sets out to discuss which way a shortwave broadcast receiver designer might go with regard to alternative design approaches and the discussion is supported by practical demonstrations. The possibility of applying microprocessors in popular shortwave broadcast receiver designs must also be considered and views on this approach are also included.

What is required?

In this section, difficulties of both manufacturers and users of shortwave broadcast receivers are mentioned, but firstly requirements of users and recommendations of broadcast unions are also set down.

In order to bring out the difficulties facing the shortwave service, it is reasonable to know the distribution of shortwave broadcast frequencies in the radio spectrum. It seems that the arrangement of radio spectrum has never been able to

TABLE 1. Current proposals of h.f. broadcasting service

PRESENT FREQUENCY ALLOCATION	PROPOSAL FROM E.B.U. (1)	PROPOSAL FROM U.K. (2)	PROPOSAL FROM A.B.U. (1)
3900 to 3950 (2)	3900 to 4060	2300 to 2495 3200 to 3400 (except 3260 to 3265)	3900 to 3950 (2) 3950 to 4000 (2)
3950 to 4000 (2)	4750 to 4995 (2)	3900 to 4000 4750 to 5060 (except 4995 to 5005)	4750 to 4995 (2) 5005 to 5060 (2)
4750 to 4995 (2)	5005 to 5060 (2)	5740 to 6200 7100 to 7500 9400 to 9900 9400 to 9800 11600 to 12000 13360 to 13560 15100 to 15600 17500 to 17900 21450 to 21850 25600 to 26100	5950 to 6200 7100 to 7300 9500 to 9775 11700 to 11975 13600 to 14000 15100 to 15450 17700 to 17900 21450 to 21750 25600 to 26100

- (1) E.B.U.: European Broadcast Union
U.K.: United Kingdom
A.B.U.: Asian-Pacific Broadcast Union
(2) Shared with other services
(3) Frequency in kHz

TABLE 2. Present and proposed h.f. broadcasting frequency spectrum

CURRENT HF BANDS	WARC PROPOSAL (AFTER 1982)
3.900 to 4.000 (2)	3.200 to 3.400 (2) BAND 1
4.750 to 4.995 (2)	3.950 to 4.000 (2) BAND 2
5.005 to 5.060 (2)	4.750 to 4.850 (2) BAND 3
5.950 to 6.200	4.850 to 4.995 (2) BAND 3
7.100 to 7.300 (2)	5.005 to 5.060 (2) BAND 4
9.500 to 9.775	5.950 to 6.200 BAND 4
11.700 to 11.975	7.100 to 7.300 BAND 5
15.100 to 15.450	9.500 to 9.900 BAND 6
17.700 to 17.900	11.650 to 12.050 BAND 7
21.450 to 21.750	13.600 to 13.800 BAND 8
25.600 to 26.100	15.100 to 15.600 BAND 9
	17.550 to 17.990 BAND 10
	21.450 to 21.850 BAND 11
	25.670 to 26.100 BAND 12

- (1) Frequencies are in MHz
(2) Shared with other services

shortwave from the Asian Broadcasting Union (ABU), the European Broadcasting Union (EBU) and the United Kingdom before the 1979 World Administration Radio Conference (WARC) are listed on Table 1. At WARC 1979, the frequency allocations in Table 2 were agreed and these will be available for allocation from January 1982. Table 2 also lists the present band planning. A glance at Table 2, and Table 1 for that matter, shows that the broadcast bands are scattered between 3 and 27MHz, with no simple arithmetic relation among them.

Design difficulties

Despite the general difficulties faced by radio receiver designers, there are some distinct problems for a popular low-cost shortwave receiver design.

In 1959, there were only a few transmitters with transmitting powers of over 200kW, but during the last 20 years, their number has increased to about 400. They generate tens, in some cases hundreds, of millivolts at the antenna terminals when received. The trouble caused in the receiver is that strong signals generate a large number of intermodulation products, strong enough to give the appearance of liveliness, yet masking weak wanted signals. How to distinguish the wanted weak signal from massive strong unwanted signals is always a major technical task.

totally satisfy any shareholder of the spectrum. "How to best share the radio spectrum for each different service?" will always be a difficult technical and political exercise. Shortwave broadcasting in particular is briefly considered here.

In the past twenty years, the total shortwave broadcasting service (including in-band and out-of-band) has grown up from 11,000 to 27,000 daily frequency hours¹, and the problem of congestion is well understood. Re-allocation and expansion suggestions of the broadcast bands on

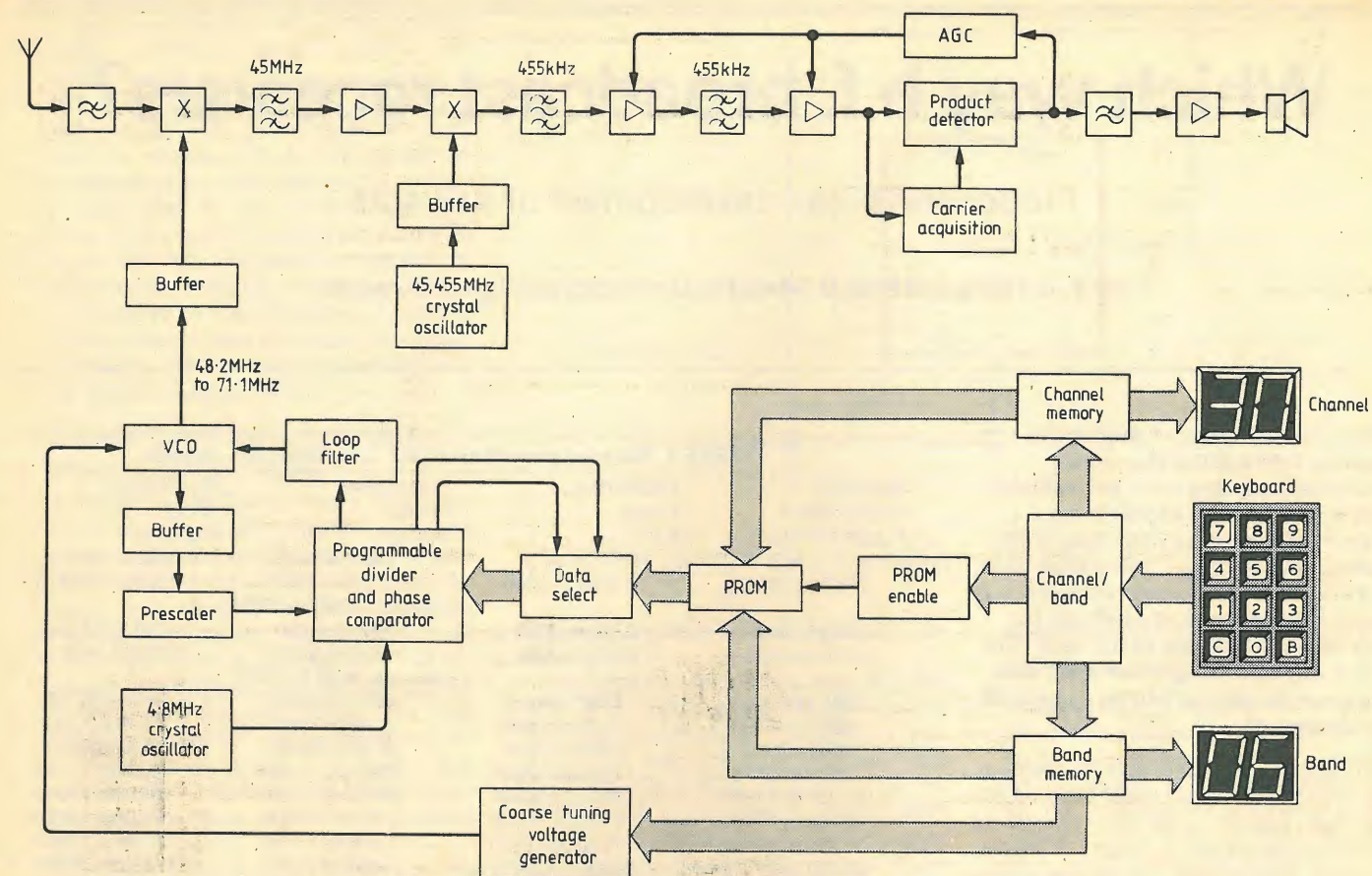


Fig. 1. First approach for a functional system.

A free-running local oscillator in a superhet receiver is always troublesome, especially when the first intermediate frequency is set to a high frequency to improve image rejection ratio.

Even with the most sophisticated mechanical tuning dial design, a resolution of 10Hz at 30MHz can really never be achieved. One can therefore imagine the outcome of the accuracy of a normal popular shortwave broadcast receiver.

Good shaping of the selectivity curves of the r.f. and i.f. stages offer a direct way of rejecting unwanted signals, but cost is a factor when seeking good selectivity curves.

Due to skywave transmission, a fading phenomenon is inherent with shortwave broadcast reception; a way to conquer this problem should always be considered.

User's difficulties and requirements

No need to say, as often as not the designer's difficulties mentioned above are overcome in a popular-model shortwave broadcast receiver design by being transferred to user operation and reception difficulties.

Difficulties to tune to a desired station, and maintain that listening station from drifting, unavoidable interference and spurious signals due to poor linearity and selectivity, audio output variations due to fading effects, are some of the major difficulties facing users. What do the users want? The users simply want easy operation, good performance and low cost re-

ceivers, requirements of course, in almost direct conflict with manufacturers.

After a joint meeting between representatives of national receiver and transmitter manufacturers associations and an EBU study group concerned with h.f. broadcasting², a brief and pertinent description was suggested for a popular shortwave broadcast receiver design: it should be reasonably-priced, stable with product demodulator and easy-tuned.

Following this suggestion, the design philosophy is divided into four sections: easy operation, high stability, low cost and good performance.

One way and better way to relieve the difficult task of mechanical tuning is to apply a digital tuning technique. Digital tuning can make it possible to tune quickly and accurately over a large number of shortwave broadcast stations. Incorporation by means of frequency synthesizer circuits is discussed below.

Tuning a station can be achieved by keying in frequency information, wavelength information, or a pre-assigned code. Before the idea of programme-labelling^{3,4,5} can be widely implemented, listeners still need to look up from a handbook or simply memorize the identity information of a station. It is tiresome to find out station identity information from a handbook each time, but it is also impractical to memorize such things as 5.339MHz or 56.19 meters of more than a few stations. Therefore a station assignment plan similar to the m.f. could be considered^{10,11}. For instance, one plan is to divide the whole shortwave broadcast spectrum into several "fre-

quency bands". Then in each band, stations with agreed channel spacing are given unique channel numbers. For example, the above-mentioned station could now have a pre-assigned code such as Band 3, Channel 79. With a station identity information simpler than a telephone number and using a keyboard entry technique, the user could tune to a favourite programme station easily and accurately.

After tuning to a given frequency, an ideal shortwave broadcast receiver should stay tuned to that frequency without readjustment over an extended period. By applying the frequency synthesis technique, the ideal condition can be approached.

A frequency synthesizer can generate a very large number of local oscillator frequencies by programming and have the stability and accuracy equal to that of a single master crystal oscillator. Today, a crystal oscillator stability of 1 part in 10⁶ is easily achieved in a non-ovened but room-type environment; this implies remaining within ± 5 Hz when tuned to 10MHz. Many interesting synthesizer devices are now appearing on the open market, not necessarily originally developed for shortwave receivers, but which can be readily adapted for such purposes. In this article the Philips LN 123 and Plessey NJ 8811 synthesizers are used in two different design approaches.

To keep receiver cost down is almost mandatory. In general, manufacturing cost can be subdivided into material cost, testing cost and assembly cost. By using cheaper components, such as integrated

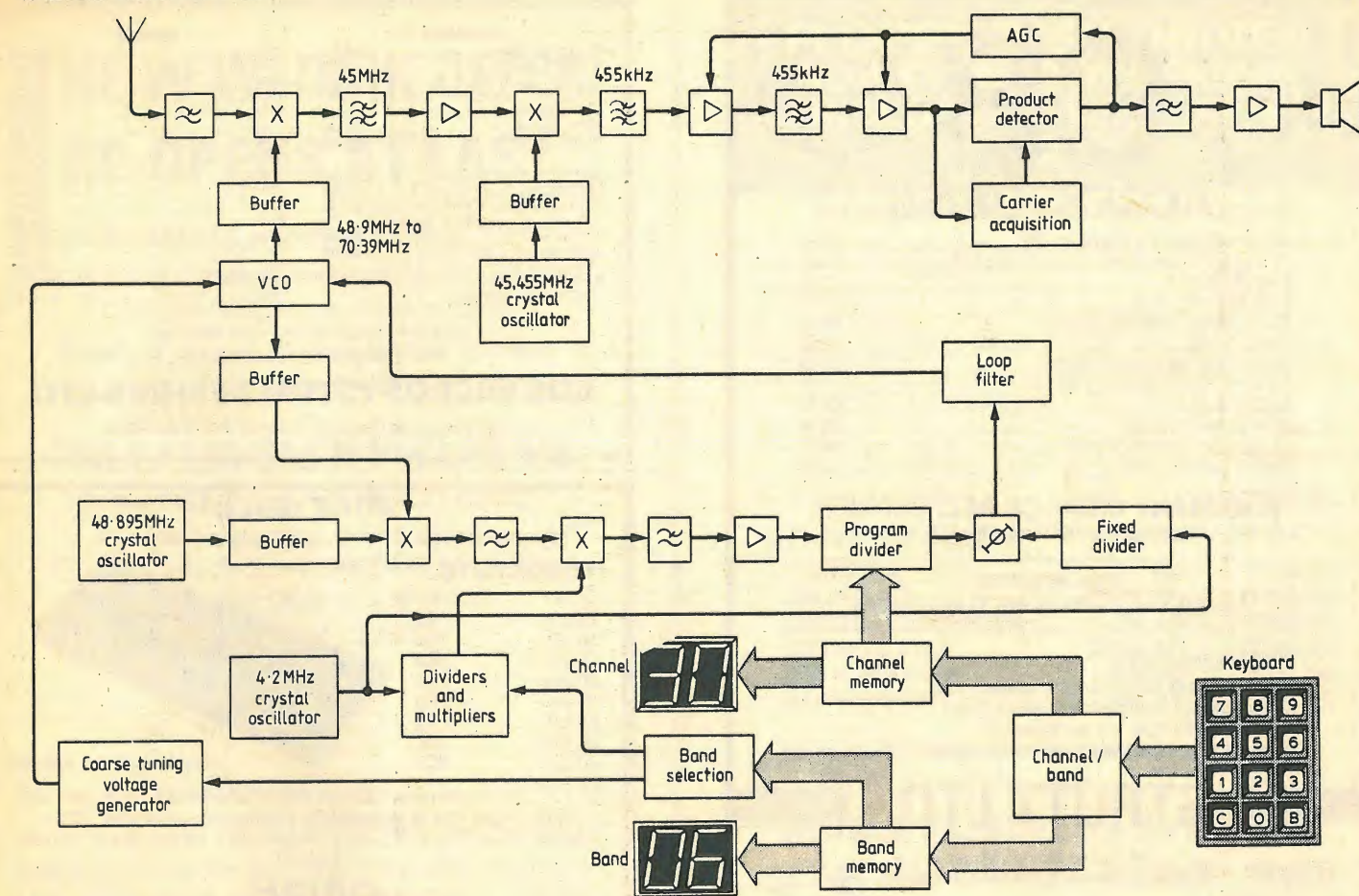


Fig. 2. Second approach for a functional system.

circuits, ceramic filters, etc., not only the material cost, but also the testing and assembly costs can be reduced. A suggested frequency allocation proposal which can reduce the price of the receiver system design is given in design approach 2.

Good performance and low cost are not easy to reach at the same time by a designer, sometimes the two requirements are in direct conflict, but this does not mean a low cost receiver need not have good performance. To some extent, the art is how to distribute the expense over the design. Nevertheless, some specifications which should be considered as a "must be good" are listed here:

- (1) Linearity
- (2) Sensitivity
- (3) Selectivity
- (4) Image rejection ratio
- (5) Frequency stability

H.f. Receiver Design Approaches

Having just specified the design requirements, we now describe two designs which achieve the requirements, but which are based on quite different approaches.

Fig. 1 shows a system block diagram. In this first system design approach, frequency allocation is based on the WARC 1979 new agreement, listed in Table 2. The whole frequency spectrum is arranged to have 12 frequency bands and a channel spacing of 5kHz is assumed. Under this scheme, a broadcast station with a transmitting frequency at 9.645MHz would now have an identity code: Band 6;

Channel 30. To tune to this station, the operator presses the key 'B' first, opening the gate to the band memory unit and at the same time closing the gate to channel memory unit. The number '6' is then pressed and the memory display unit then shows this band number. The user then presses key 'C' reversing the above gate switch functions and then the number '30'. The channel display unit should then show this channel number. The actual digits stored in the band and channel memory units are b.c.d. coded. These b.c.d. numbers are then used as address codes to fetch the correspondent set of words from the eeprom to program the programmable divider. The vco (voltage-controlled oscillator) output, via a buffer and prescaler stages, is divided down in the programmable divider and then sent to the phase comparator unit to compare with the reference frequency signal. If a different of frequency or phase exists, an error voltage is generated through the loop filter to correct v.c.o. frequency or phase in the usual way. With the correct v.c.o. frequency, the receiver is tuned to the wanted station frequency.

The antenna r.f. signal is selectable by converting to the i.f. frequency. An up-conversion superhet system with a first i.f. of 45MHz and second i.f. of 455kHz has been adopted so as to ensure a high image rejection ratio. Double-balanced modulators are used in these two conversion stages to improve various interference characteristics such as intermodulation products, spurious noise, etc. New low-voltage high-level balanced modulators, with which the

manufacturers claim a third-order intermodulation of -60dB and a 1dB compression point of 15dBm, are currently available.

Although at the forthcoming WARC HF conference in 1983, any possible planning of the shortwave broadcasting bands will be based on a double-side band (d.s.b.) sound broadcasting system, the introduction of single-side band (s.s.b.) transmissions has to be taken into account². A carrier reduction in excess of 6dB, with respect to peak envelope power, is also likely. A residual carrier is necessary for the operation of automatic-gain-control circuits in the receiver and for frequency-locking or carrier acquisition purposes. On the other hand, a 12dB reduction makes for a sensible reduction of transmitter power consumption and running costs⁸.

The upper-side band (u.s.b.) transmitting mode is likely to be used in the future shortwave broadcast s.s.b. transmission, therefore only u.s.b. detection is considered in the s.s.b. detector design. As indicated a regenerated carrier signal from the carrier acquisition circuit mixes with the received carrier signal in the product detector stage. The audio information is then amplified after a low-pass filter to the required level through audio amplifiers. The nature of possible carrier acquisition circuits is not discussed here for two reasons. Firstly such circuits are not easy to devise and secondly they deserve a long separate discussion.

continued on page 80

CB

ACCESSORIES

THE BIG DUMMY'S GUIDE TO CB.....£2.50
 DV 27 ANTENNA FROM.....£4.40
 K-40 ANTENNA.....£27.99
 MAG MOUNTS K-40.....£8.80
 S.W.R./POWER METERS FROM.....£6.10
 PATCH LEADS.....£2.00
 2 AMP POWER SUPPLY FROM.....£10.12
 3-5 AMP POWER SUPPLY FROM.....£11.80
 ROGER-BLEEP.....£4.75
 POWER MIKE FROM.....£8.44
 EXTENSION SPEAKERS from.....£2.77
 AM/CB CONVERTER.....£7.29

AND MANY MORE CB ACCESSORIES
 All prices exclude Carriage and V.A.T.

OPENING HOURS:
 Mon.-Sat. 8 a.m. - 5.30 p.m. Sun. 10 a.m.-12.30 p.m.

Just give us a ring on:
 Tavistock 0822-5865, ask for Transistor Kid.
 Tavistock 0822-5247, ask for Silicon Chip
 London 01-520 7236, ask for Rifleman.
 Bognor Regis 0234 828473, ask for Big Daddy

STRUTT LTD.

3d Barley Market Street
 Tavistock, Devon PL19 0JF. Telex 45263

WW-037 FOR FURTHER DETAILS

MEMORIES		MICROS	
8 x 4116, 250ns.....	£9.00	8035L.....	£3.50
8 x 4116, 200ns.....	£9.50	8243.....	£2.00
2716.....	£3.00	8085A.....	£5.00
2732.....	£7.00	8085A-2.....	£6.00
2114L, 200ns.....	£1.50	8155.....	£6.00
6514, 200ns.....	£4.00	8155-2.....	£7.00
6116L, 200ns.....	£20.00	8251A.....	£4.00
µPD765 (8272).....	£20.00	8253-5.....	£3.50
µPD7002 (A-D converter).....	£3.00	8255A-5.....	£3.50
TTL delay lines, 100ns-10ns taps.....	£4.00	8257-5.....	£8.00
TTL delay lines, 200ns, 20ns taps.....	£4.00	8259-5.....	£5.00
Crystals - 5, 6 and 10MHz.....	£2.00	8279-5.....	£5.00
All components guaranteed new, full specification devices.		Z80.....	£4.00
		Z80 PIO.....	£4.00
		Z80 CTC.....	£4.00
		Z80 DMA.....	£15.00
		Z80 SIO/0, SIO/2.....	£19.00

All above are special offers while stocks last
 Please add P&P 30p. Add VAT to total

BDS MICROSYSTEM DESIGNS LTD.
 28 Pinewood Close, St. Albans, Herts. AL4 0DS

PURE GOLD!

Top-quality, low-profile, gold-plated contacts,

IC SOCKETS

8 pin	8p
14 pin	14p
16 pin	16p
18 pin	18p
20 pin	20p
22 pin	22p
24 pin	24p
28 pin	28p
40 pin	40p



Unbeatable value!

Minimum Order £10. Add £1 P.&P.
 500 + and one type less 5%. 1,000 + any mix less 10%.
 Special offer 10 x 8 pin, 20 x 14 pin, 20 x 16 pin. 5 x all others
 £11.50

ORION

Orion Scientific Products Ltd., 10 Wardour St., London, W.1

WW - 042 FOR FURTHER DETAILS

THE W.W. DISK OFFER RE-OPENS AT LAST

We have obtained a limited stock of European single sided drives so please get orders in soon

Circle the enquiry number for data
 Total U.K. price including VAT at 15% and carriage, CWO

ONLY £155 EACH INCLUSIVE

(Drive £132, P and P £2.78, VAT £20.22)

Please make cheques and P.O.s payable to
W.W. Disk Offer and send to:
W.W. DISK OFFER
 49 Milford Hill
 Batford
 Herts

Please call **0582-429122** to check on availability before ordering.

Allow 21 days for delivery. This offer applies to U.K. only and is subject to availability. For non U.K. orders send SAE for quotation

WW - 020 FOR FURTHER DETAILS

FLOPPY DISK DRIVES NOW EVEN LOWER PRICES UNBELIEVABLE BUT TRUE! READ ON!

SIEMENS FDD - 100-8/FDD - 200-8

Fully Shugart Compatible Siemens 8" single and double sided disk drives are available now with unbeatable prices at single unit pricing.

Note these specifications:

★ TRACK 00 SENSING	★ WRITE PROTECT CIRCUITRY
★ ACTIVITY INDICATION	★ AUTO DISK EJECTION
★ MECHANICAL END STOPS AT TRACKS 00 AND 76	★ FAIL SAFE INTERLOCK WHICH PREVENTS THE COVER FROM CLOSING ON A PARTLY INSERTED DISKETTE
★ AUTO WRITE CURRENT SWITCHING AT TRACK 43	

FDD 100-8 Single Sided	Single 250 K	or	Double Density 500 K	FROM
				£249.95
FDD 200-8 Double Sided	Single 500 K	or	Double Density 1 MByte	FROM
				£349.95

OTHER PRODUCTS C.W.O. 30 DAYS

CP/M 2.2	71.50	75.00
BASIC 80	156.75	165.00
BASIC COMPILER	175.75	185.00
WORD STAR	218.50	230.00
MAIL MERGE	66.50	70.00
SUPERSORT	94.05	99.00

Full range of SD SYSTEMS S-100 CARDS & KITS ALSO AVAILABLE

Send S.A.E. for further details

IRVINE BUSINESS SYSTEMS

P.O. BOX 5
 IRVINE, Ayrshire
 TEL: (0294) 75000
 TELEX: 777582




SIEMENS


A quiet word from Siemens

Siemens produces a range of electronic teleprinters and printer terminals which are quiet, rugged and require little maintenance thanks to a plug-in fault diagnosis and modular design and construction.

TELEPRINTERS are available in various configurations with, or without, paper tape facilities or keyboard, or with magnetic tape attachments that will take the place of a tape reader and punch and provide a convenient method of storing messages.

The Model 1000 Teleprinter uses a plastic type wheel for high print quality, whereas the PT80-5 is a version of the PT80 but using the ITA (No 2) telegraphy code can be supplied with either needle or ink-jet matrix printing. Military orientated versions of the Model 1000 Teleprinter (1000V) are available for specialised applications along with the Teleprinter 1000 CA crypto teleprinter and ancillary equipment covering error correction and modulation and demodulation.

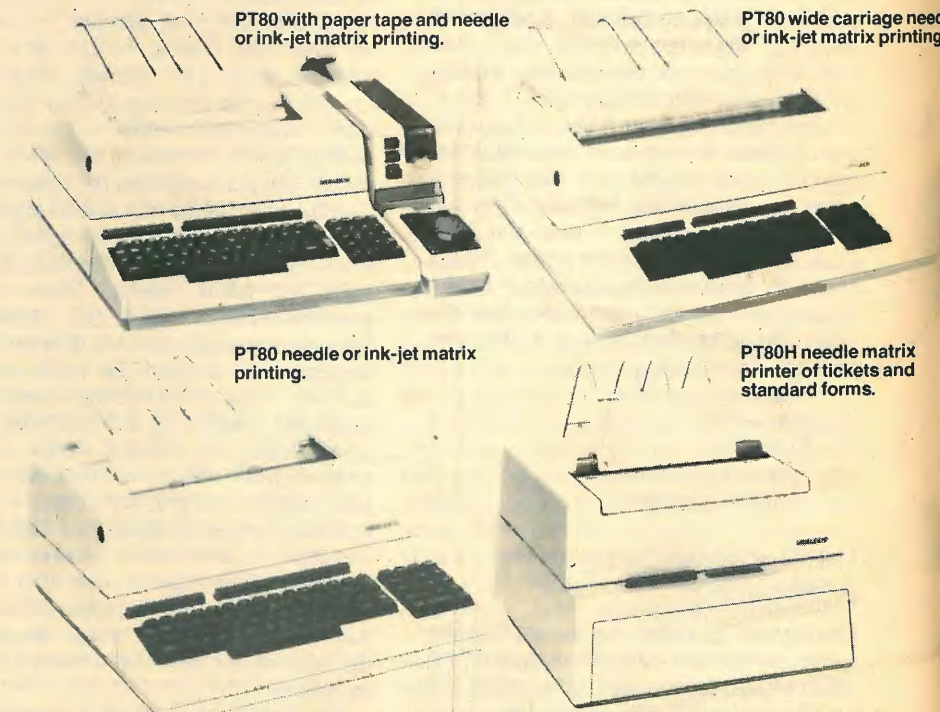PRINTER TERMINALS using the ITA (No 5) code, which is used with most computer installations can be




supplied with full tape facility with, or without, a keyboard, or either needle or ink-jet matrix printing.

The PT80i is a special high-speed bi-directional ink-jet matrix printer producing good quality prints at speeds of up to 4,800 Baud. This machine can be supplied with or without a key pad and with either serial or parallel connections.

Ink-jet printing is a method of printing in which Siemens has had a large involvement. It operates at very low noise levels (less than 50 dB) using plain paper.

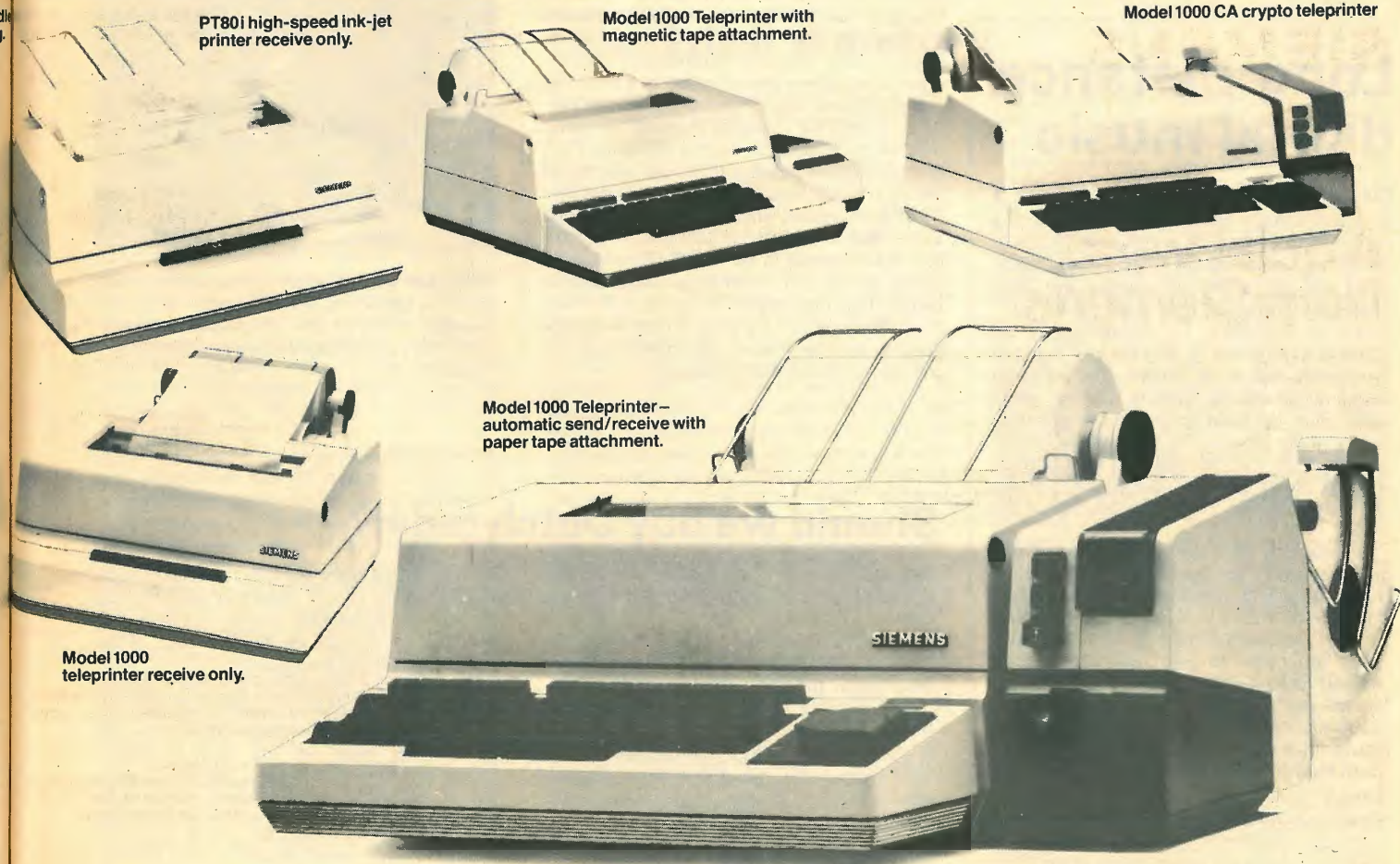For complete details contact:
 Siemens Ltd., Siemens House, Windmill Road,
 Sunbury-on-Thames, Middlesex TW16 7HS
 Tel: Sunbury-on-Thames (09327) 85691
 Telex: 8951091



Model 1000 teleprinter receive only.

All models available for OEM as complete units or modules; also floppy disc drives.

WW - 007 FOR FURTHER DETAILS

Siemens-printer terminals are our business

NEWS OF THE MONTH

Frequency-hopping military radio produced

A British firm, Racal-Tacticom Ltd, claims to be the first in the world to go into production with a frequency-hopping military radio. Some of the first models, which operate at v.h.f., have been ordered by the Ministry of Defence for evaluation by the British Army. Some are going to other NATO member countries and, according to the company, will be in service in Europe within the next few months. The purpose of frequency-hopping (an "electronic counter-countermeasure" in military jargon) is to avoid the unwelcome attention of jamming or interception of messages (known as "electronic countermeasures"). Instead of operating continuously in one channel, the radio communication system is designed so that the frequency, of both transmitter and receiver, automatically jumps about from channel to channel in a random sequence. The equipment developed by Racal-Tacticom is a speculative commercial venture which they have been working on for only three years. Gerry Whent, chairman and managing director of the company, says confidently that sales of the product, which includes vehicle and manpack versions, "throughout the 1980s are likely to run into hundreds of millions of pounds from our traditional markets alone".

Parts of the v.h.f. band from 30 to 88MHz are available for use by military communications.

Long distance digital music

Casually switching on my tuner to Radio 3 around lunchtime on the 17th May, I heard a superb performance of a Vaughan Williams symphony. Consulting the *Radio Times*, I discovered that the music was coming live from Shanghai as part of a tour made by the BBC Symphony Orchestra. The second half of the concert consisted of Beethoven's Fifth Symphony, and as an encore, the orchestra played a rip-roaring bravura Chinese piece called 'How the good news was brought from Peking to the villages'. All through the concert one was aware that the quality of the transmission was superb and it astonished me to realise that it was coming from the other side of the world.

On checking with the BBC, I learned that they had used for the first time NICAM-3 (Near Instantaneously Companded Audio Multiplex) which converts the stereo signals to digital form and then compresses them so that up to three stereo pairs may be sent over conventional 2048kbps digital telephone systems. The signal was encoded at Shanghai, sent through a radio link to Peking, transmitted again via the geostationary Intelsat over the Indian Ocean, received at the British Telecom station at Madley, sent through 'conventional' circuits to the BBC where it was decoded and retransmitted to us. It took about a quarter of a second for sound made in China to reach our ears at home in the U.K.


Within this range nine 6.4MHz bands have been selected by Racal for frequency hopping; and within a chosen 6.4MHz "hop band" the frequency hops among 256 channels, each 25kHz wide. The method of achieving this, and the necessary synchronization between transmitter and receiver, were outlined in our earlier report on the prototype (December 1979 issue, p.85). The hopping rate is described by the maker as "medium", which means somewhere between 50 and 500 hops per second. Some idea of the spread-spectrum character of the transmission can be gained from the spectrum analyser display here. The horizontal, frequency axis represents the extent of one "hop band" of 6.4MHz. The small peaks are signal spectra and are a record of the successive frequency positions of the signal in about 35 of the 256 channels over a fraction of a second. The large-amplitude peak in the middle of the screen is the spectrum of a strong jamming signal, and it can be seen how this is avoided by most of the positions of the frequency-hopped communication signal.

Up to 50 "hopping nets", each using a different hopping code, can be operated in the same hop band simultaneously — and possibly up to about 200 if they are not all working at the same time. Fixed frequency nets can also be operated in a hop band. The system can function with one third of the available channels occupied by other signals, such as fixed frequency, other hopping transmissions or jammers. Transceivers are controlled by a keyboard (see photo) and three rotary switches. The keyboard is used for changing the mode of operation, for entering codes and for checking. Day-to-day operation requires the use of only two of the rotary switches. Transmission modes are: F3 simplex, voice, analogue information, and digital data at rates up to 16kbit/s. To protect certain frequencies in the hop band, or to avoid strong signals, up to 16 frequencies may be barred from the hopping sequence in any hop band. Racal say that the price of their frequency hopping radio set is about 20% higher than that of a conventional military transceiver.


Should we buy Dutch radar?

Although the value of the defence industry may be questioned in its ability to actually defend us against any potential enemies, one thing in its favour is that it provides work for the manufacturers of defence equipment. All the more puzzling then is the proposal by the MoD to purchase missile tracking radar from the Netherlands. The radar would be used in place of the Marconi GWS25 Seawolf tracker. The MoD seems to be willing to accept a degraded performance and a lower environmental standard in exchange for lighter weight.

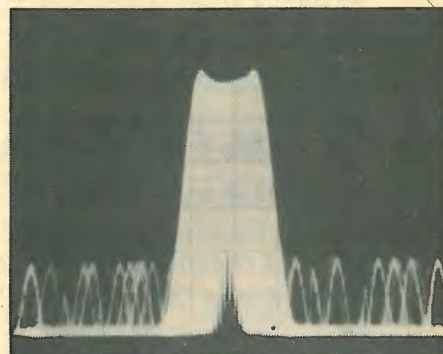Marconi Radar Systems are, understandably, upset about this; the Seawolf has been in use



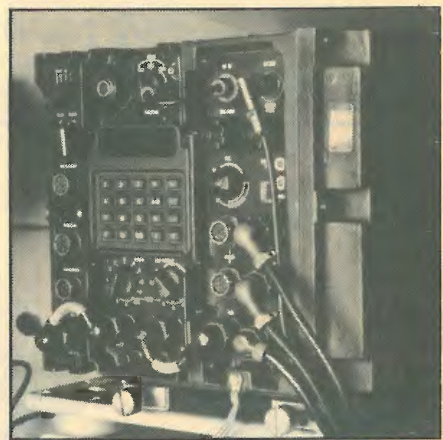Spectrum analyser display shows a frequency hopping signal (small peaks) spread out over a 6.4MHz hop band. The large amplitude signal in the middle is from a jammer.



A 50-watt vehicle station. The central unit, with the keyboard, is the transceiver (output 10mW or 4W) which is common to both the vehicle station and the manpack version.

with the Royal Navy and is in full-scale production. Over the past 35 years they have built up an expertise in tracking systems and have been working to enhance the performance of the system against low level missiles.

Marconi have proposed a series of modifications to make the Seawolf lighter while retaining the performance improvements at a comparable price. They point out that such equipment would also have considerable export potential, but if the Navy's decision goes against them there would follow the destruction of the design team and loss of employment in various factories.

TV direct by satellite

It seems that we are going to need to learn another set of initials to denote yet another medium for telecommunications. This one is DBS, for direct broadcasting by satellite. The Home Office has issued a report on the options available and a possible strategy for instituting a system.

Under a plan drawn up by the International Telecommunications Union (ITU) in 1977, the UK has been allocated five DBS channels which could be beamed towards the UK from a geostationary satellite of 31° west. Each channel would be capable of providing one tv service or a number of radio services with national coverage. Reception could be by individual households, in which case an antenna and the appropriate converter would cost around £150 to £200; alternatively there could be a community receiving station, distributed to households by cable.

Various satellite systems are discussed in the document and their likely cost. For instance, a two channel system using ESA's European Communications Satellite would cost about £15m per channel per year over a ten-year period; a five-channel system broadcast via the L-Sat, ESA's large satellite would cost about £10.5m per channel. Cost could be reduced by starting with a pre-operational system with a spare satellite held for launching, though if there were a breakdown in the operational satel-

Component supplies

It is annoying to need a particular component and not to be able to find a supplier. We have received two catalogues from new suppliers and any new source is always welcome. Anglia Components originally started as a supplier of spare parts to retail radio and tv repair shops they have now expanded into a general component and tools supplier and still have some emphasis (a whole separate section) on tv replacement parts. They have installed a computer and offer to deliver all catalogued items by return of first class post. They can cater for low and high volume orders and can offer regular deliveries to high volume users. The newest issue of the catalogue describes in its 110 pages resistors, capacitors, semiconductors and industrial integrated circuits, opto-electronics, electromechanical components, tools, test equipment and linear i.c.s. The catalogue is available from Anglia Components, Burdett Road, Wisbech, Cambs PE13 2PS.

Another catalogue, from M.S. Components, also emphasises that all catalogued parts are dispatched on the day that the order is received. The catalogue is of a similar size to that from Anglia; it contains some 2,500 separate items and it is promised that there will be a new edition soon which will be increased to over 3,000 items. Among the many products one particular service worthy of note is a transformer prototyping service. M.S. can supply, within 48 hours, transformers within the range 3 to 50VA with the secondary voltage and current specified by the customer, with a set price for each transformer of £5.99. Another notable point is that M.S. encourage the amateur constructor. You do not need to be an account holder and can buy components over the counter on a Saturday morning, if you can get to M.S. Components, Zephyr House, Waring Street, West Norwood, London SE27 9LH.

lite, there would be no service until the replacement was launched.

Also discussed at length is the content and quality of any proposed DBS service. With a worldwide reputation or the high quality of our domestic tv services and any new service should maintain that standard. Competition for the sake of audience figures can lead to a reduction in the range and quality of programmes available to the public. With the introduction of the fourth tv channel in the UK and the pilot cable services recently announced, there could be many channels available to the public. Another possibility is the extension of cable tv to a national service to provide broadcast programmes and other telecommunications services to the home. Bearing all this in mind, the report suggests that a modest start would be preferable, with perhaps only two channels.

The report goes on to discuss some of the programme options. The BBC has proposed that it should provide television programme services on two channels, one would be a subscription films, and other BBC special productions, opera, drama, music and extended coverage of sporting events; all these would be to run in the normal schedules. This service would not be financed from the net revenue of the tv licence fees. The second BBC DBS channel would be used for a service of retransmissions of 'the best of BBC-1 and BBC-2' especially for those who are unable to view the programmes at the time of the original transmission. Another proposal for a subscription chan-

nel has come from the Granada group to consist principally of recent feature films. The Open University has proposed that priority should be given to an educational channel and this idea has been supported by a number of other organisations. Teletext and information services are also mentioned.

As regards the kinds of DBS serves that might be provided, the general consensus seems to be for a 625-line standard tv signal with the possibility of adding additional sound channels for stereo, sound tracks in different languages or separate radio services.

Financing such a service poses major problems and it is suggested that it may be operated by a separate body acting as a common carrier which leased the individual channels to the broadcasting bodies. The establishment of the system would require considerable initial capital outlay, and there is the continuing running cost. Licensing and subscription and advertising revenues are some of the possible sources.

Finally there are environmental aspects of DBS to be discussed. The receiving antennae are likely to have some visual impact on our skylines although a dish as small as 40 to 50cm in diameter might be possible under favourable conditions. A community reception centre with cable distribution to the individual household might be preferable. For transmission to the satellite only one transmission station would be needed compared with the 1,000 or so, currently in use for the terrestrial service.

EBU proposes a world digital television standard

Western European broadcasters, through their organization the European Broadcasting Union, have proposed a set of parameters as a digital television standard for studio equipment. They hope it will be adopted throughout the world. It will in fact be submitted to the final meeting of CCIR study groups on this subject due to be held in September this year in Geneva. The need for such a standard has arisen because more and more television studio equipment is going digital and compatibility between different units is desirable. The EBU says that an agreed world standard would "mean less expensive equipment, because of the economies of scale, and benefit international programme exchange. It would have important financial advantages for users and manufacturers, lead to improvements in the technical quality of programmes shown in a country with a different television system from the originating country, and assist the international exchange of technical information on television production".

The EBU standard is based on coding of the separate components of the colour tv signal rather than the other possible approach, coding of the composite PAL, SECAM or NTSC colour signal. (Both of these methods have been studied by broadcasters for several years.) In the EBU proposal the luminance signal component is sampled at a frequency of 13.5MHz and the two colour-difference signals are each sampled at 6.75MHz. Thus the standard is called "13.5:6.75:6.75" in shortened form. The EBU hopes these parameters will be applicable to both 525-line and 625-line television systems and hence that the number of samples per television line

will then be very similar. Because of the different field rates, of course, the number of samples per picture will be different.

The need for a worldwide standard in this field was the subject of a recommendation by all the unions at the 3rd World Conference of Broadcasting Unions held in Tokyo in 1980. In the USA the SMPTE has been studying the problem for some years, and the EBU has coordinated its work with the investigations of this society. There are now indications of support for the EBU proposal from several of the broadcasting unions. For example, the Organización de la Televisión Iberoamericana (OTI) has already given its support and this is particularly significant because both 525-line and 625-line countries exist in the OTI area. Encouraging reactions are also said to have come from the North American National Broadcasters Association and the Union of National Radio and Television Organizations of Africa.

● Another digital standard soon to be established in the field of television is for viewdata terminals — but in Europe only. Its purpose is to standardize television sets as far as public viewdata is concerned so that a common set of integrated circuits can be used with any of the different viewdata systems, such as Prestel in the UK, Bildschirmtext in West Germany and Teletel in France. At the time of writing the standard is expected to be ratified in June by the central organization of the European telecommunication authorities, the Conférence Européenne des Postes et des Télécommunications (CEPT) at Bern.

Technologists detained in USSR

Two professional workers in the field of electronics have been arrested in the USSR after unsuccessful attempts to obtain exit visas to enable them to emigrate from the country. Both are Jews. Kim Fridman, an electronics engineer, was head of the test department in the Kiev Radio Works. Viktor Brailovsky, a computer scientist, was a senior research fellow in the Institute of Electronic Control Machines, Moscow.

Both men appear to have run foul of the Soviet authorities by holding cultural and scientific seminars in their homes, in spite of the fact that these meetings were conducted on strictly legal lines and had no political content. Kim Fridman's wife Henrietta, who visited these offices recently, told us it is common practice for "Refuseniks"* to hold such seminars, mainly to continue their scientific education and keep their professional knowledge up to date. The charge against Fridman is "parasitism";

*"Refuseniks" are Soviet Jews who, having been consistently refused permission to emigrate to Israel, are harassed by the KGB, usually dismissed from their work, and live in fear of arrest and trumped-up charges resulting in imprisonment.

that against Brailovsky "defaming the Soviet state and public order".

Kim Fridman voluntarily left his job in October 1969 in anticipation of a three-year wait before he would be allowed to submit his application to emigrate. The official reason for refusing him permission to leave the USSR is "secrecy" — presumably it was considered he had knowledge of Soviet radio technology which might be useful to an enemy of the state. Considering the date he left his job, *Wireless World* has expressed scepticism on the validity of this reason, which seems more like an excuse; and on the strength of our view the UK Foreign Office is arranging to have the Fridman case heard at the Madrid conference. Up to the time of his arrest in March 1981, Kim Fridman had been doing temporary, unskilled work but had been finding it more and more difficult to obtain employment.

Viktor Brailovsky asked for an exit visa in 1972. This was refused in 1973 and shortly afterwards he was dismissed from his post at the Institute of Electronic Control Machines. It is thought that his arrest, in December 1980, resulted from his editing of a cultural journal "Jews in the USSR", but the charge of defaming the Soviet state appears to be contrived



because the journal, which ceased publication in June 1979, was not political. After his arrest, other scientists tried to go to his home for further seminars, at the invitation of his wife Irina, also a computer scientist, but were turned away by KGB officers. Some time in 1981 the IEEE expects to publish a paper by Brailovsky in their *Transactions on Pattern Analysis and Machine Intelligence*.

All professional workers in electronics will be distressed to hear of the way these colleagues in the USSR are being treated by the authorities and will hope for success in the efforts currently being made to help them.

New satellite earth station

British Telecom are to build a new satellite communications earth station in Wiltshire. An 87-acre site at Stert, near Devizes, has been purchased, and the first dish aerial is expected to be operating by early 1986. About six aerials should be working on the site by 1990. This is BT's third satellite tracking station, and has become necessary because capacity of Goonhilly Downs and Madley is limited. There will soon be further Intelsat satellites placed into geostationary orbits. Apart from these, Inmarsat, the international maritime satellite communication system, which the new station will also serve, is expected to grow rapidly in the next few years, becoming operational in early 1982.

At the time of writing Intelsat V-B, the second of a new series of nine international communications satellites, was scheduled to be launched on May 21 from Cape Canaveral. Like its predecessor, Intelsat V-B weighs 1,928 kg and has almost double the communications capability of early satellites in the Intelsat series — 12,000 voice circuits and two colour television channels. It will be positioned in geosynchronous orbit over the Atlantic Ocean as the main satellite to provide communications services between the Americas, Europe, the Middle East and Africa.

Dennis Baker has been awarded the Martlesham Medal for 1981. Given by British Telecom to present or former members of its staff, the medal is awarded for 'outstanding achievement in telecommunications science and engineering.' Mr Baker was responsible for introducing silicon transistors into submarine cable repeaters. He developed a system for bonding the extremely thin wires used in transistors onto the silicon chip. The repeater amplifiers used may be at depths of three miles with pressures of up to three tonnes per square inch. They need to have a guaranteed life of 25 years. The transistors developed by Mr Baker and his team have been in use in cables all round the world without failure for the past ten years. Mr Baker is also involved with integrated circuits and computer logic. He leads the team which is credited with coining the word 'microprocessor', and is currently working on small geometry circuits for the System X telephone exchanges, and on computer-aided design for large-scale integrated circuits. He is shown here holding microphotographs of the metal-to-silicon bonds used in the submarine amplifier transistors.

The twins paradox of relativity

A composite reply to correspondence arising from Professor Dingle's October article

from Professor Ian McCausland

Department of Electrical Engineering, University of Toronto

I am grateful for the opportunity to reply to various letters that have been sent to the Editor in response to Professor Herbert Dingle's article¹. I shall start with Dr Tom Wilkie's letter (June issue), since it was in response to discussion with him that the article came to be written.

I am sorry if Dr Wilkie feels that he has been singled out in an undesirable way by Dingle's article. I understand that Dingle had planned to rewrite the article in more general terms, without specific reference to Dr Wilkie, but he did not live to do this. I did think of making such alterations myself, but I was reluctant to tamper with what Dingle had written.

Since Dr Wilkie describes his conviction that Dingle is wrong as being "unshakable", there is little that I can reply to him; but I would like to make some comments about his letter which may say something to others who may view the question as being still open.

In reply to Wilkie's comment that "most academic journals have for some years rightly viewed the matter as settled and regarded more discussion of it as a waste of paper", and his final plea to "let it rest", I would simply observe that he was the one who published the item entitled "The Twin Paradox revisited" in *Nature* in 1977, which led directly to the writing of Dingle's paper¹.

One of the interesting features of the responses to Herbert Dingle's criticisms of special relativity has been the variety of attempts to answer Dingle's question about the relative rates of the equatorial and polar clocks mentioned by Einstein in his original paper. Wilkie's answer is to say that it may be that there is an error or ambiguity in this example in Einstein's paper, and he later states that original papers may not be definitive because "second thoughts may change the author's mind". It is interesting to note that, in the very example mentioned, we do have Einstein's second thoughts available to us. If one studies that example in the generally-accepted English version of Einstein's first paper² (translated from the text in a German collection published in 1922), one finds a footnote which excludes the case of pendulum clocks, but that footnote does not appear in the originally published version of the paper. The later addition of the footnote seems to me to confirm that Einstein did mean exactly what he said, and also confirms that the statement about the slowing of the equatorial clock was intended to refer to a real slowing, not merely something that depended on the point of view of the observer.

According to Wilkie, Max Born answered in technical terms whose meanings were precise and well-defined. As an example of Born's precision, consider the following statement, referring to the special theory³: "The simple fact that all relations between space co-ordinates and time expressed by the Lorentz transformation can be represented geometrically by Minkowski diagrams should suffice to show that there can be no logical contradiction in the theory." Since the Lorentz transformation is contained in the special theory, but is not the whole theory, it is illogical to claim that any property of the Lo-

rentz transformation is a sufficient condition for the whole theory to be free of logical contradiction.

With reference to Wilkie's statement that the language of relativity is geometry, not English or German, Dingle did not question the impeccability of the mathematics of special relativity. But the theory is based on postulates expressed in words, and the mathematics is not the whole theory; it was the theory as a whole that Dingle criticized, not its geometry.

I agree with Dr Wilkie that some of Dingle's critics have tripped themselves up by their use of words. However, this is not always because of the difficulty of expressing abstruse technical matters in words. Consider, for example, a case that I have documented elsewhere⁴, in which, in *The Listener* in 1971, one scientist stated that the results of the Hafele-Keating experiment supported special relativity, and another stated that the experiment had no relevance whatever to the special theory. Now, a statement that the results of a certain experiment support a certain theory is a perfectly simple factual statement (however abstruse and technical may be the reasoning that led to that conclusion), and the same applies to the contrary statement. The fact that the two statements are contraries of one another (they cannot both be true, though they might both be false) shows that one or other of the scientists (or both) misunderstood either the theory or the experiment (or both). Or it might mean that there is a contradiction in the theory.

In the note mentioned above⁴, I documented several other unsatisfactory statements that have been published by defenders of the theory. These cannot be dismissed as being merely poorly worded, since most of them were uttered by scientists who are prolific authors of books and who may therefore be reasonably expected to be able to write what they mean. I think we should keep in mind the words of the anonymous diplomat (quoted by Sir Bruce Fraser in his revision of Sir Ernest Gowers' *The Complete Plain Words*) who said: "What appears to be a sloppy or meaningless use of words may well be a completely correct use of words to express sloppy or meaningless idea."

Wilkie's paragraph about all the scientists who did not choose to seek fame by dethroning Einstein is very interesting, but totally devoid of scientific basis. The pursuit of scientific truth is not aided by statements such as: "That no young student over the last 20 years has seen the chance to make his name by developing Professor Dingle's ideas is eloquent testimony to the erroneousness of these ideas."

Several other letters were received by the Editor with varying degrees of relevance to the problem at hand. Before dealing with individual letters, examine the nature of the problem. According to Dingle⁵ a paradox arises when, from the same premises P, two (or more) apparently contradictory conclusions X and Y seem inescapably to follow. It can be resolved only if one of the following four things can be shown: (1) the conclusions are not in fact contradictory; (2) conclusion X does not follow; (3) conclusion Y does not follow; (4) the premises P contain an internal contradiction.

Furthermore, if we start with a pair of contradictory premises, then, as Popper⁶ has pointed out, we can infer any conclusion we like using valid rules of inference.

How does this apply to our problem? Suppose that we have a set of premises P, and suppose that one scientist (D) deduces from those premises a conclusion X, and that another (E) deduces from the same premises a conclusion Y, which is directly contradictory to X. Each scientist may believe that he has shown by his own deduction that the other's deduction is faulty, but in fact both deductions might be perfectly valid deductions from premises P which contain an internal contradiction. Furthermore, even if hundreds of supporters of E come forth, each with a different argument showing that Y does in fact follow from P, these do nothing whatever to show that D's deduction of X from P is faulty. To refute D's argument it is necessary to examine that argument itself and show that there is an error in it — in other words, to show that conclusion X does not follow from the premises P.

In reading the literature on the twin paradox, one finds many articles showing ingenuity, with varying degrees of originality, and picturesque detail, that asymmetrical ageing can be deduced from Einstein's theory. Many of these articles present the arguments in such a way as to imply that they refute the deduction of the opposite conclusion (symmetrical ageing), when in fact their results merely contradict the opposite result and, for the reasons discussed above, contradiction does not imply refutation unless it is first proved that the theory from which the contradictory results have been derived is itself free from contradiction.

For example, one of the correspondents, T. de Limelette, writes: "But I agree that the solutions to the paradox found in some texts are not all one could wish. I propose here my own. It is contained entirely within the special theory." I think it is clear from the foregoing that yet another presentation of the derivation of asymmetrical ageing, without showing what is wrong with the other argument, is not a solution to the problem that Dingle raised. T. de Limelette also comments on Dingle's article as follows: "I wonder where Professor Dingle picked up the strange idea that two different observable descriptions of the same events are not permissible. A description requires observers, apparatus and measurement procedures before it can be observed. These are not left unchanged by a change in the reference coordinate system. So why should the results of the measurements have to remain the same?" I am not quite sure that is the point of this comment, unless it is to suggest that the rather bizarre set of observations envisaged by Dingle are in fact feasible.

N. Thomas comes closer to dealing with Dingle's argument. The relevant paragraph of his letter is as follows:

The situation according to Special Relativity is as follows (for instance, see Introduction to Relativity by L. Marder, Longmans 1968). According to Paul the outward and return journeys take 1½ days each, whilst according to Peter they take 15 years each. Thus Peter judges Paul's clock to be running slow by the factor $15 \times 365 / 1.5 = 3650$. According to Paul, Peter's clock runs slow by the same factor, and at the end of his outward journey Paul says that 35½ seconds have elapsed on Peter's clock whilst 1½ days have elapsed on his own clock. Now suppose that Peter had previously placed a stationary clock synchronized with his own at the point where Paul reverses his journey. Both Peter and Paul will say that this clock reads 15 years at the end of the outward journey, and this is how Peter assigns a duration of 15 years to the outward journey. However, be-

cause he is moving relative to Peter, Paul says that this additional clock is not synchronized with Peter's own clock but rather leads it by 15 years minus 35½ seconds: this is an example of the relativity of simultaneity. As soon as Paul reverses direction he judges that Peter's clock now leads the local clock (which reads 15 years) by 15 years minus 35½ seconds. Paul measures 1½ days on his own clock for the return journey (making a total of 3 days) whilst he judges that only a further 35½ seconds elapse on Peter's clock (making a total for the trip of 30 years). According to Paul, Peter's clock therefore races forward by 30 years minus 71 seconds during the reversal; as discussed by Einstein this can be explained using General Relativity. (Alternatively, since Paul changes inertial frames it can be attributed within Special Relativity to a change in his definition of simultaneity). Special Relativity does not therefore predict that Paul is rejuvenated at the beginning of the return journey, and Dingle's refutation of the theory on this basis is not valid.

It seems to me that his is not a satisfactory answer to Dingle's article. It should be recalled that Dingle was discussing Einstein's own resolution of the twin paradox, and that this resolution required the use of general relativity. (Einstein's article takes the form of a discussion between a relativist and a critic; the discussion of the paradox starts from special relativity but the critic asks for a resolution that satisfied the general theory, and it was that resolution that Dingle discussed in his article¹.) This seems to me to suggest that Dingle's argument must be met in terms of the general theory, not the special theory.

The other point to be noted about Einstein's resolution is that he agreed that it is perfectly valid to consider Paul to be fixed throughout the whole course of events, provided that the appropriate fields of force are invoked. This means that we could rephrase a passage in N. Thomas's letter as follows: "Now suppose that Paul had previously placed a stationary clock synchronized with his own at the point where Peter reverses his journey. Both Peter and Paul will say that this clock reads 15 years at the end of the outward journey, and this is how Paul assigns a duration of 15 years to the outward journey." (In case it may be argued that the fields of force associated with the initial parting of Peter and Paul might upset the synchronization of that clock, one can assume that Peter and Paul are moving uniformly relative to one another at the start of the process, so that no fields of force are needed at the original parting.)

W. James writes that "Dingle gives a wholly spurious symmetry to the problem by assuming that the Universe is empty but for the two clocks in his analysis (although in the statement of the problem he also refers to the earth.)" I can find no such assumption stated; in fact Dingle talks about the earth and a distant planet, whereas Einstein's statement of the same problem defines it wholly in terms of reference frames. Einstein's article does not use any other objects except the travelling twins to resolve the paradox, except that later in his paper, when his supposed critic suggests that the gravitational fields are fictitious, he states that "all the stars in the firmament can be conceived as participating in the creation of the gravitation fields". I do not think that Dingle would have objected to this statement, and the fact that Dingle did not happen to mention all the stars in the firmament can scarcely be taken as equivalent to an assumption on his part that the universe is empty except for the two clocks.

W. James also states: "The clock paradox of special relativity is stated in McCausland's

article 'if there are two clocks in uniform relative motion the special theory of relativity requires each clock to run faster than the other' . . .". In fact my article⁸ does not even mention the clock paradox, much less state it. In the relevant context I quoted a passage from Davies⁹, and then suggested that passage provided strong support for Dingle's claim that "if there are two clocks in uniform relative motion, the special theory requires each clock to run (not merely seem to run) faster than the other." If the passage I quoted from Davies does not support that claim of Dingle's, then I think that someone should state clearly what it does mean.

I. M. Crann states that Dingle tacitly assumes some form of universal time, and that this assumption of "absolute" time guarantees that contradictory results will be obtained. I do not think that Dingle makes such an assumption, any more than Einstein did. Einstein stated quite clearly, in the passage Dingle quoted, that retardation of a clock during one phase of the experiment was over-compensated by faster working during another phase, and that a clock works faster if located at a point of higher gravitational potential. I think that Dingle merely followed Einstein's argument to its inevitable conclusion.

K. Burnett (May letters) asks "Am I the only reader of *Wireless World* with an interest in physics who finds the long series of articles on special relativity somewhat boring?" After making some interesting comments about theories of modern physics, he ends his letter by writing: "When a new more inclusive theory arises, which will embrace quantum mechanics and general relativity, I suspect that few 'anti-relativists' will like the result. But boring it won't be."

I do not know the grounds on which Burnett bases his suspicion that few anti-relativists would like such a result. There seems to me to be a suggestion here that those who criticize relativity are like Luddites longing for a retreat to pre-Einstein physics, whereas in fact they are trying to suggest that it is time for the scientific world to consider the possibility of moving on to post-Einstein physics.

Some correspondents, such as W. James, M.H. de la Rica, R. V. Harvey, and A. B. Starks-Field, present alternative resolutions, or partial resolutions, of the clock paradox. For the reasons given in my earlier comments, I believe that they do not meet Dingle's argument, because they do not identify a fault in his reasoning. M.M. Albahari (February letters) suggests a new experiment to test the validity of relativity by a test of the constancy of the velocity of light, using time intervals four orders of magnitude greater than those in the Michelson-Morley experiment. A.H. Winterflood states that Dingle is wrong in believing that the mathematics of special relativity is impeccable; he states that the mathematics of the theory is wrong, and refers to his recently-published book "Einstein's Error". Other correspondents, such as C.L. Thomson, W.T. Morris, J. de Pièrre, F. Allen and J.A. MacHarg, contributed interesting comments and suggestions, and V. Halsall contributed a discussion relating to Dr Essen's article in *Wireless World* dated October 1979.

There is another letter which I think requires comment, namely a letter by J.H. Fremlin, which appeared in *New Scientist* last year¹⁰. Some of the comments below were made in a letter that I sent to the editor of *New Scientist* in October 1980, but to the best of my knowledge my letter has not been published.

Professor Fremlin stated that he would "like very much to refute the suggestion that opponents of the theory of relativity find it difficult to get a proper hearing". He might like to refute the suggestion, but his letter certainly does not do so. The only evidence he presents in support

of his "refutation" is about things that were published, whereas the suggestion that he claims to refute is related to the fact that papers have been denied publication. There is no contradiction between the fact that some papers have been published and the fact that others have been denied publication. Unfortunately few people, except those who have direct experience, are aware of the difficulty of having any paper published if it is critical of relativity. Part of the problem is that almost all the evidence about papers that have been rejected is hidden from public view.

To take a specific example, Professor Dingle's paper¹ was rejected by another journal before his death. I have in my possession a copy of the relevant correspondence (which spanned a period of several months) between Dingle and the journal, but the journal has refused my request for permission to publish its part of the correspondence.

Professor Fremlin's letter also dealt with his own personal correspondence with Dingle, and his (Fremlin's) demonstration of the difference to be expected between the ages of the pair of twins in the twin paradox. Although it is difficult to comment on this without seeing all of the relevant correspondence, I suspect that Dingle considered the finding of an error in Fremlin's analysis to be a non-existent problem. He was convinced that the special theory contained an internal contradiction, and he knew that meant that it was possible, using valid rules of inference, to deduce from the theory any conclusion that one wished.

Dr Wilkie did not think it was wise to publish Professor Dingle's article, because Dingle is unable to defend himself. As I pointed out in my note accompanying the article, Professor Dingle sent the article to me in the hope that it would eventually be published. I am conscious of the inferiority of my qualifications as a defender of Herbert Dingle, but perhaps I may excuse my attempts by quoting a sentence from his last book, *The Mind of Emily Brontë*: "To disinter from a mass of diverse writing a common substratum demands penetration of a far higher order, and the only ground on which I claim justification for attempting the task is the absence of competitors."

In fact there is a significant number of scientists dissatisfied with the special theory of relativity. Anyone who doubts this should read the August 1979 and October 1980 issues of the journal *Speculations in Science and Technology*. I happen to believe that Herbert Dingle was right in his thesis that the special theory is untenable, but I would not be so rash as to claim that I have an "unshakable conviction" on this. I am, however, firmly convinced that the problems raised by Professor Dingle have not been satisfactorily solved.


References

1. Dingle, H. The "twins" paradox of relativity. *Wireless World*, vol.86, October 1980, pp. 54-6.
2. Einstein, A. On the electrodynamics of moving bodies, in *The Principle of Relativity* by H. A. Lorentz et al, Methuen, 1923.
3. Born, M. Special theory of relativity. *Nature*, vol.197 1963, p. 1287.
4. McCausland, I. Science on the defensive. *Canadian Electrical Engineering Journal*, vol.5, April 1980, pp. 3/4.
5. Dingle, H. Science at the Crossroads. Martin Brian & O'Keefe, 1972, p. 185.
6. Popper, K. R. Conjectures and Refutations. Harper Torchbooks, 1968, p. 319.
7. Einstein, A. Dialog über Einwände gegen die Relativitätstheorie. *Naturwissenschaften*, vol.6, 1918, pp. 697-702.
8. McCausland, I. Why not discuss relativity. *Wireless World*, vol.86, October 1980, p.55.
9. Davies, P. C. W. Space and time in the modern universe. Cambridge University Press, 1977, p.39.
10. Fremlin, J. H. Special theory. *New Scientist*, vol.87, 25 September 1980, p. 950.

CIRCUIT IDEAS


Low noise moving-coil preamp

Noise performance of this design is about 3dB below many similar commercial units, and the high-frequency response is -1dB at 150kHz without the 3n3 output capacitor. The output clips at about 500mV and, below 150mV, distortion is caused solely by the push-pull input stage. Cartridges with high impedances will give lower distortion. High quality components must be used throughout and the circuit layout should be neat with no long connections. The circuit shown has been optimised for an Ortofon moving-coil cartridge, but other types should also be suitable.

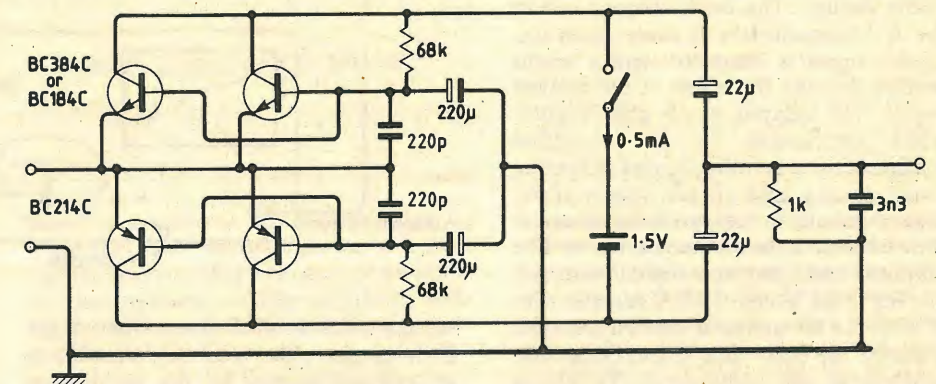

Performance

Voltage gain	35dB
Input impedance	20Ω
Output harmonic distortion (mainly 3rd)	
400mV	3Ω R _s 6Ω
150mV	0.13% 0.32%
100mV	0.1% 0.056%
50mV	0.05%
Noise (unweighted 10Hz to 15.7kHz) referred to input (includes hum)	
o.c.	74nV
s.c.	52nV 4 transistors as shown
	74nV 2 transistors only
Frequency response	
-1dB at 15Hz	
-3dB at 50kHz (see text)	
R. Lee	
Bradford	

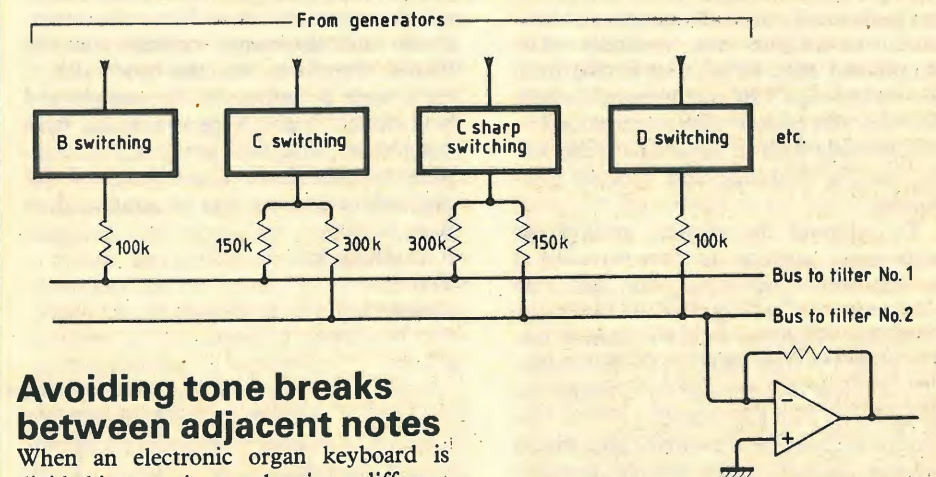

Avoiding tone breaks between adjacent notes


When an electronic organ keyboard is divided into sections each using a different filter, as described by Dr Pykett, there is a noticeable change in tone when a single-note step is made from one filter to the next. This can be overcome very effectively by grading the change. In the diagram, note B drives filter no. 1, note C drives 66% filter 1 and 33% filter 2, note C sharp drives 66% filter 2 and 33% filter 1, and note D drives only filter 2. The change

from one filter to the next is therefore spread between four notes and the abrupt change of tone is eliminated. Mixing from the notes driving one filter should be at a low impedance input to avoid signals being fed back.
J. H. Asbery
Wembley
Middx.

Video summing amplifier

A simple video summing amplifier and limiter with an adequate bandwidth for modest c.c.t.v applications can be built using one LM318 op-amp. Because a sharp cut-off is required, to avoid overloading the monitor, the emitter-base junction of a transistor is used as a limit sensing element. Emitter current is $(\beta+1) \times$ base current provided by the clip-level potentiometer, which reduces the limiting slope by the factor β .

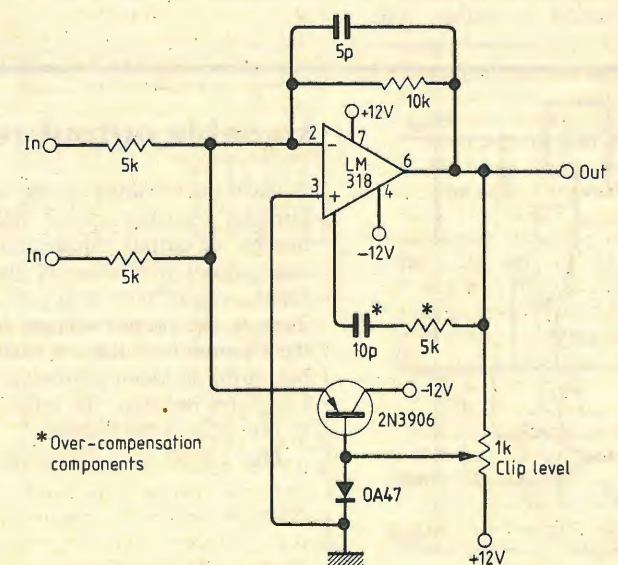The circuit can be assembled on Veroboard provided that tracks to the op-amp are kept short. It is recommended that the 10kΩ feedback resistor is mounted across the top of the i.c. and the 5pF capacitor mounted underneath the board. The LM318 can drive directly into a 75Ω load.
P. Newman
Glasgow




Plotting oscilloscope waveforms

This system enables a display to be plotted from an oscilloscope which has a delayed sweep facility. The oscilloscope is set in the A-intensified-by-B mode so an unknown signal is displayed with a bright portion showing the extent of the delayed sweep. The delayed sweep gate, a pulse which corresponds to the intensified portion of the waveform, is used to operate a sample and hold circuit whose output voltage is equal to the waveform voltage at the end of the delayed sweep interval. The output is measured by a digital voltmeter and fed to the Y axis of a X/Y recorder. An X drive for the plotter is derived from the wiper of the delay-time multiplier potentiometer in the oscilloscope. To plot a waveform, the potentiometer is rotated through its full range, which drives the pen horizontally while the sample and hold circuit drives the pen vertically. The sample and hold circuit can be fed from the oscilloscope ChI out terminal, which provides the plotter with vertical deflection features such as adjustable scale factor, ac/0/dc coupling, and variable positioning.

To calibrate the plotter, ground the scope input, position the trace vertically at an appropriate reference point and scan horizontally using the delay-time multiplier control to write a reference line. The plotter is then adjusted for full deflection, i.e. one inch for one c.r.t. horizontal division. As with any sampling system, the waveform must be repetitive, and trigger jitter on the oscilloscope will blur the plotter waveform.

This arrangement can form the basis of a powerful computer controlled waveform acquisition system. In this case, the position of the B gate pulse is set by a control voltage from the computer.

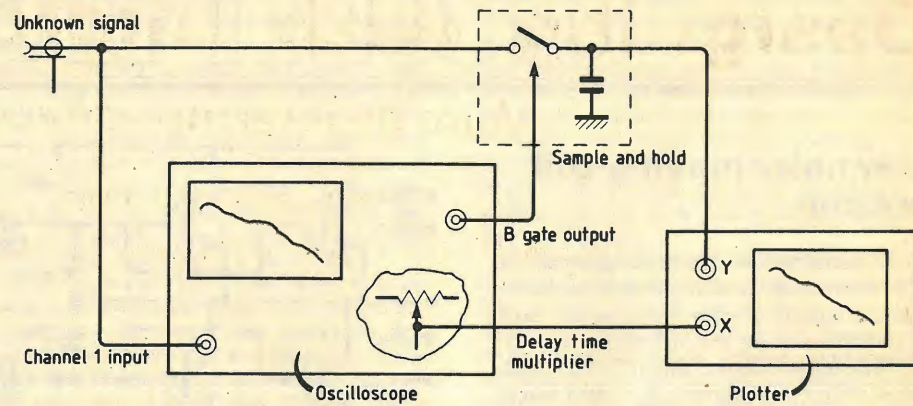
As the waveform samples are digitized by the computer, the control voltage is increased and the sampling position is scanned across the waveform. Although this is a slow data acquisition system, the progress of digitization is visible. The





voltage which controls the position of the B sweep gate pulse must be derived from an external source, so the oscilloscope needs to be slightly modified.

The computer can determine many waveform parameters such as peak, mean, r.m.s. and harmonic content via the Fourier transform, but the bandwidth of the system is limited by the sample and hold circuit. A prototype system has been constructed using two ports in a PET computer to control the converters, and the digitization process was programmed in Basic.

P. D. Hiscocks
Toronto
Canada

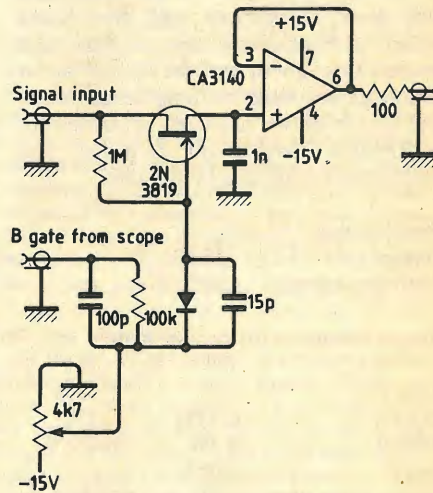

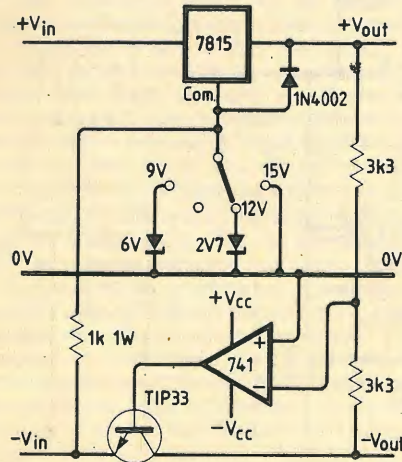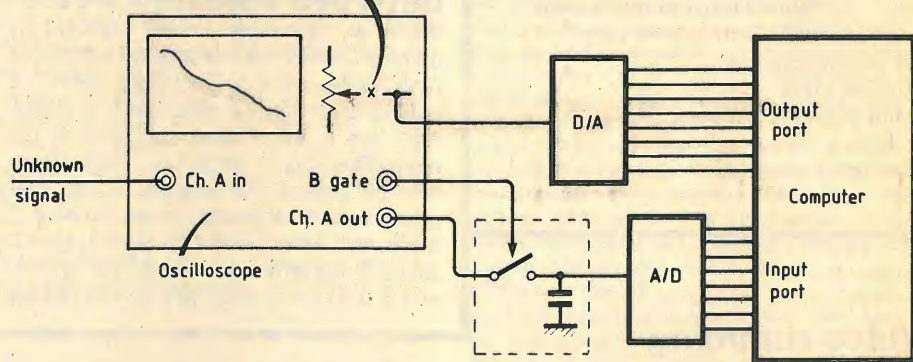Lead from delay time multiplier pot broken and connected externally.



Variable output regulator

A small modification to the normal three terminal regulator circuit will provide a number of output voltages and retain the short-circuit protection of the regulator. Many designs have been published which increase the output voltage by returning the common terminal to a positive pedestal but, if the common terminal is returned to a negative pedestal, the output is reduced by the value of the pedestal.

This circuit uses Zener diodes to pro-

vide switched outputs below 15V, however, the diodes could be replaced by an adjustable low power regulator. A 1N4002 protects the regulator from reverse voltage if the output is shorted. Dual supplies can be provided by adding the op-amp and transistor shown, but the negative rail is not protected.

J. McDonald
Portsmouth
Hants.

Designing with microprocessors

9 - More on interrupt-driven circuits

by D. Zissos and G. Stone

Department of Computer Science, University of Calgary, Canada

Procedures for the step-by-step design and implementation of interfaces in interrupt-driven microprocessor-based systems are described in this article. The authors show that the interface hardware is the same for both vectored and non-vectored interrupts, and that it is almost independent of the microprocessor chip used. Fully-worked out examples, using the Intel 8080 and the Motorola 6800 chips are used to demonstrate these statements.

As explained in the first article on this subject (June issue), interrupt-driven circuits are used when sensitivity to the environment is needed. This would be the case with equipment and/or processes which, when they malfunction, require fast corrective action to avoid catastrophes that may result in damaging equipment, shutting down systems and so on.

The concepts we used to develop such systems are straightforward, involving basically the equipment or the process signalling the micro-processor when it wishes to communicate with it, and waiting for the microprocessor to respond. This resulted in the development of an uncomplicated interrupt configuration, whose block diagram is shown in Fig. 7 in the June article. For ease of reference this diagram is reproduced here as Fig. 1.

The function of the interrupt controller in Fig. 1 is to generate the interrupt request signal, IRQ, when one or more flags are present, and to provide the microprocessor, when it responds to the interrupt request, with some meaningful information which allows it to vector to the appropriate service routine. The meaningful information is denoted variable *i*. The design and implementation of interrupt controllers and a review of support chips implementing their function will be considered in a later article.

Interface hardware

Although at first sight the design and implementation of the interface hardware might appear complex (particularly to the uninitiated), in practice it turns out to be a straightforward process, as we shall demonstrate next. Our starting point is Fig. 1, which clearly indicates that the interface hardware is a logic circuit whose function is to monitor the status signals of the peripheral (which may be either equip-

ment or a process) and generate flag f_n when the status signals indicate to it that the peripheral wishes to communicate with the microprocessor. The interface then simply waits for the microprocessor to respond electronically.

Note that the flag simply requests a response from the microprocessor, which may well be ignored, if masked by the programmer. To avoid blocking microprocessor responses to emergencies, an interrupt pin, which cannot be disabled by software, is also provided in most cases. The interrupt signal using this pin is referred to as a **non-maskable interrupt**, to discriminate it from **maskable interrupts**, which represent requests rather than commands for microprocessor responses.

When the microprocessor responds, it generates the electronic 'go ahead' signal which, as explained in the June article, consists of i/o signal(s) associated with predetermined i/o address(es) - see Fig. 1. The nature of the 'go ahead' signal is described in detail in article 5, published in the October 1980 issue. On receipt of the i/o signal(s), the interface generates the command signals that drive the peripheral. In order to prevent the flag from continuously interrupting the microprocessor, the interface must clear the flag.

Since the interrupt controller does not send a signal back to the interface, it follows that interrupt interfaces are independent of the nature of the interrupt controllers. That is, the interface hardware in


interrupt systems depends only on the peripheral and not on whether vectored or non-vectored interrupts are being used. Furthermore, because the microprocessor response consists of i/o signals, whose nature does not vary greatly from microprocessor to microprocessor, the interface hardware is almost identical for all types of microprocessors.

Interrupt interfaces, in common with all other interfaces, are designed and implemented using well-established procedures that always work¹. We shall demonstrate the simplicity of the design procedures and lack of complexity of their implementation by means of a design problem, after we describe the nature of the interrupt software.

Interface software

As in the case of the interface hardware, the interrupt software is relatively uncomplicated and should present no difficulty to the reader who possesses some knowledge of programming. In the author's experience, the primary cause of misoperation in practice is lack of proper initialization procedures, which results in unwanted signal spikes (glitches) that are generated on interrupt lines during hardware and/or software initialization of interrupt in-

Fig. 1. Basic configuration of an interrupt system (a repeat of Fig. 7 in the June issue).

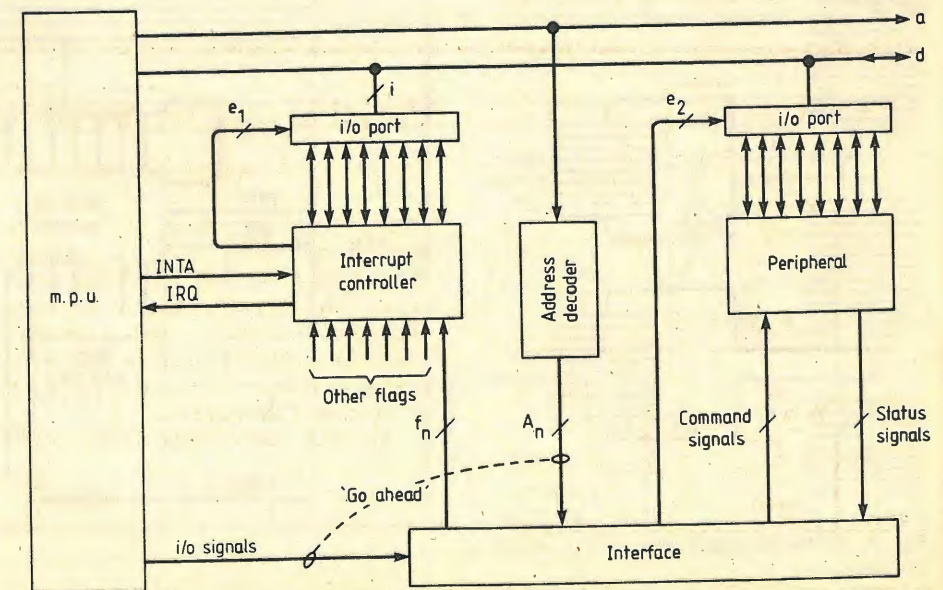

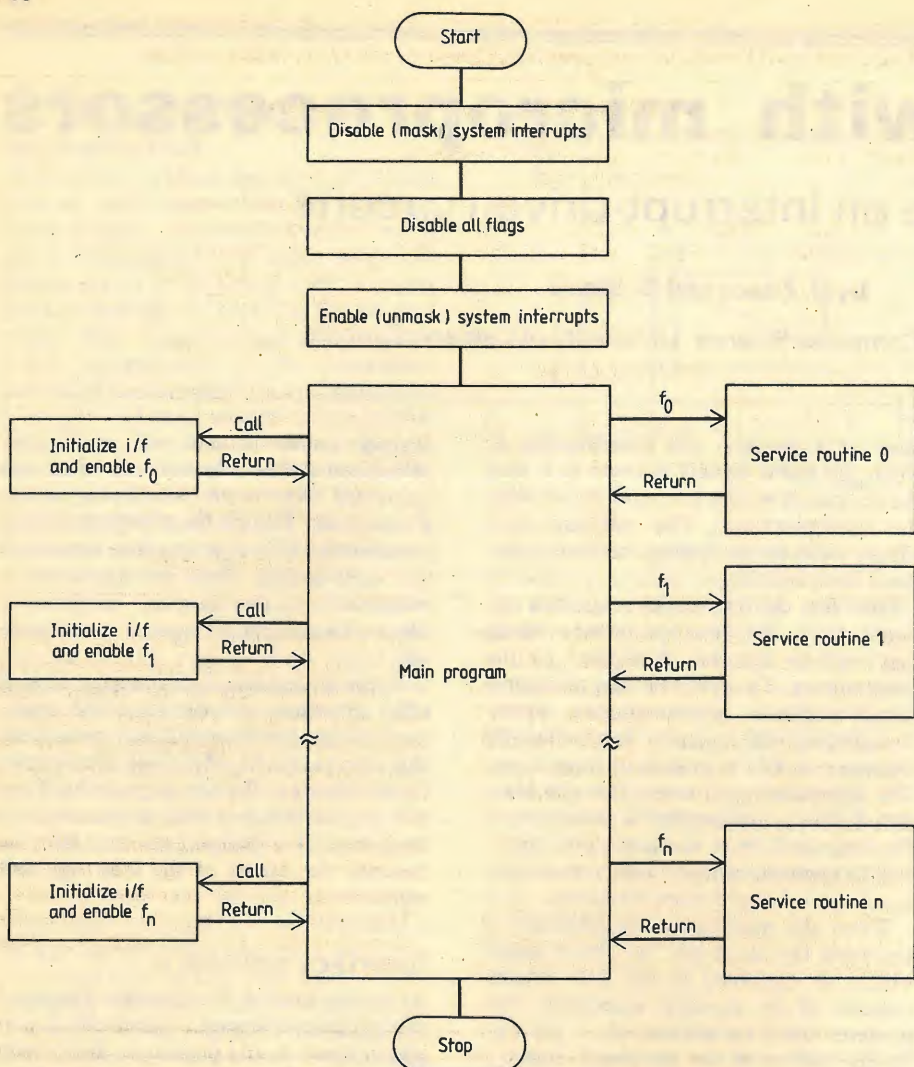


Fig. 2. System initialization.

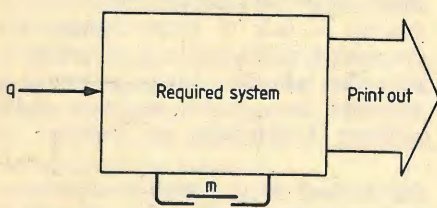


Fig. 3. Block diagram of the event counter.

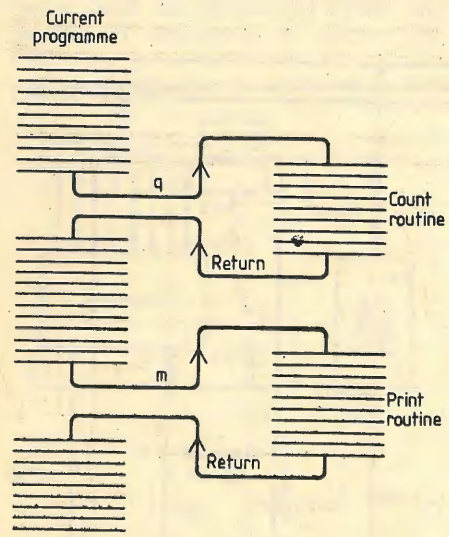


Fig. 4. Software responses of the event counter.

interfaces. An initialization procedure that avoids this problem is flowcharted in Fig. 2. As an additional precaution, all interfaces that are not being used should be disabled.

We mentioned earlier that during a program interruption, the re-entry point, consisting of

1. The return address;
2. The condition flags, and;
3. The working registers;

must be preserved during program interruption. In practice this information is stored in stack, which is a block of consecutive locations in r.a.m. that can be accessed from one end on a last-in-first-out (lifo) basis. A stack is established in r.a.m. by loading a base address into the stack pointer. Every time a new item is put on stack the stack pointer is 'advanced' (decremented) and everytime an item is removed the stack pointer is 'retarded' (incremented)². This means that the base address points to the highest location in stack.

PUSH, POP and RETURN instructions, explained earlier, refer to explicit operations in which information is transferred between the microprocessor chip and locations in stack specified by the stack pointer.

In summary, for the purpose of writing the interface software the only system feature that one has to know, is the vectoring address associated with each of the interrupt flags one is generating.

We shall now give an example to demonstrate the steps used to design and implement interrupt-driven microprocessor systems.

Design example - an event counter

Pulses representing events arrive randomly on line *q* in Fig. 3. Our problem is to design an interrupt-driven system that would allow a print-out of the event-count to be produced each time switch *m* is activated. Activation of the switch, which can be assumed to be infrequent, resets the count.

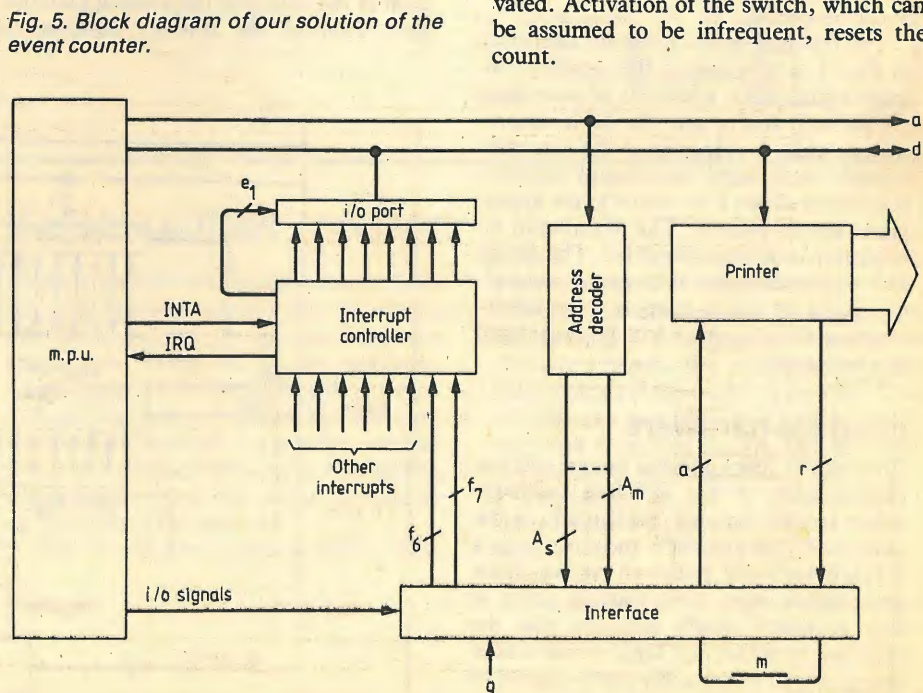


Fig. 5. Block diagram of our solution of the event counter.

Table 1: Mnemonic and hex listings of the count and print routines used in the event counter

INTEL 8080				MOTOROLA 6800				COMMENTS
Code	Mnemonics	Operands	Machine code	Code	Mnemonics	Operands	Machine code	
COUNT ROUTINE				COUNT ROUTINE				
PUSH	PSW		F5	INC	COUNT		7C 06 50	Save program status
INR	C		0C	STA	A	F002 B7	F0 02	Increment count
OUT	62		D3 62	CLI			0E	Clear count flag
POP	PSW		F1	RTI			3B	Restore program status
EI			FB					Enable interrupts
RET			C9					Return to interrupted program
PRINT ROUTINE				PRINT ROUTINE				
PUSH	PSW		F5	LDA	A	COUNTB6	06 50	Save program status
MOV	A	C	79	STA	A	F003 B7	F0 03	Copy word count into A
OUT	63		D3 63	CLR	COUNT		7F 06 50	Print and clear flag
MVI	C	00	0E 00					Clear count
POP	PSW		F1					Restore program status
EI			FB					Enable interrupts
RET			C9					Return to interrupted program

We will implement the design using an action/status printer, and either the Intel 8080 or the Motorola 6800.

Solution

Step 1: aim of the design. To demonstrate the steps used in designing and implementing interrupt interfaces.

Step 2: resources. A microprocessor-based system and an action/status character printer.

Step 3: our solution. Our solution consists of evoking a COUNT routine when an



event is detected, and a PRINT routine each time switch *m* is activated, as shown in Fig. 4. The COUNT routine will be given a higher priority than the PRINT routine should signals *q* and *m* be both present before the program is interrupted. The block diagram of our solution is shown in Fig. 5.

8080 implementation

Step 4: hardware design. Reference to Fig. 5 shows that the basic functions of the interface hardware is to generate interrupt

flag *f₆* when switch *m* is activated and signal *f₇* when a pulse is received on terminal *q*, and allow them to be cleared under program control. The most straightforward method of implementing these two functions is to use two JK flip-flops, as

Fig. 6. (a) Interface hardware of the event counter problem using the Intel 8080 microprocessor; (b) interface hardware of the event counter using the Motorola 6800. Note that the two interfaces are almost identical.

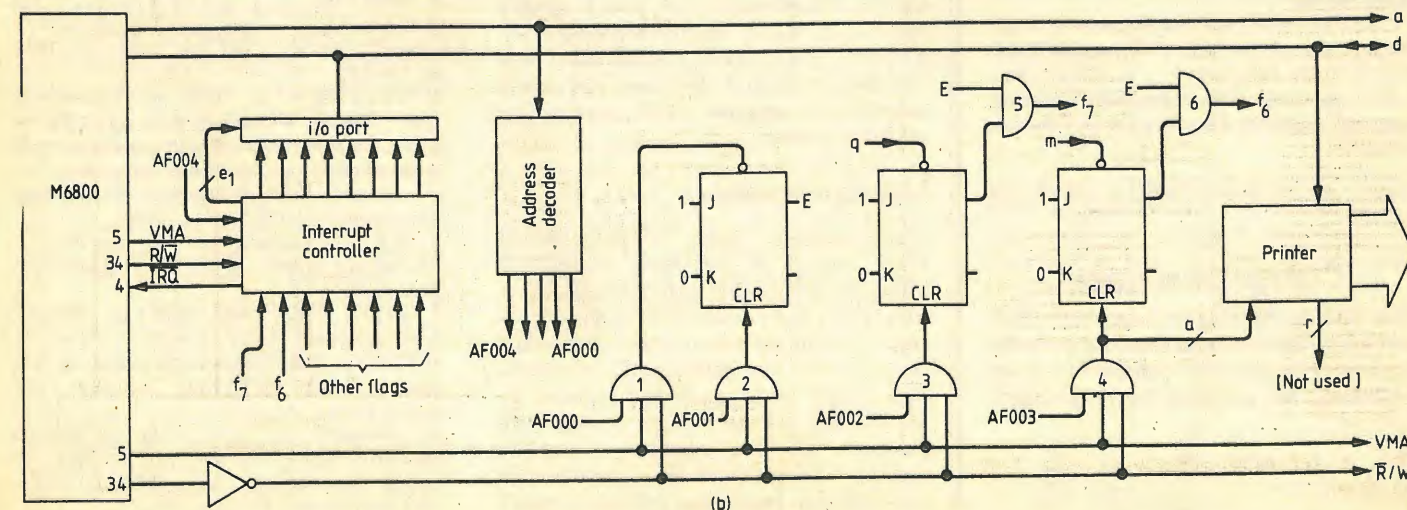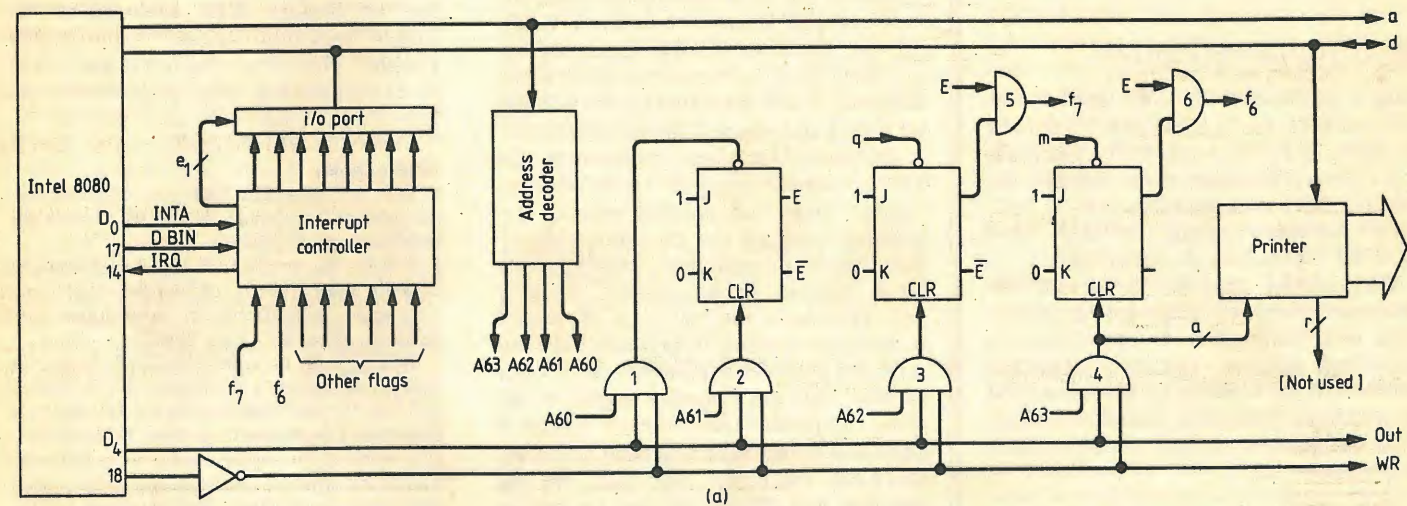

shown in Fig. 6(a). Switch m is connected directly to the clock terminal of flip-flop 6, allowing it to be set each time switch m is pushed and released. Similarly the output of the sensor is connected directly to the clock terminal of flip-flop 7, which also allows it to set each time the sensor generates a pulse.

We can allow the programmer to reset the two flip-flops by simply routing software-generated i/o pulses to their clear terminal. For this purpose, we can use two AND gates, 3 and 4, as shown in Fig. 6(a). The i/o addresses 63 and 62 are used for this purpose. That is, flip-flop 6 is reset by executing an OUT instruction with address 63 and flip-flop 7 by executing also an OUT instruction with address 62.

To allow the programmer to enable or disable the interface, we can introduce a third JK flip-flop which is set by executing an OUT instruction with address 60, and reset by executing an OUT instruction with address 61, as shown in Fig. 6(a). We use the output E of this flip-flop to AND flags f_6 and f_7 .

The final function of the interface is to activate the printer. We can either use a separate OUT instruction for this purpose or simply connect the output of gate 4 to the action terminal of the printer. This causes execution of OUT 63 both to clear f_6 and activate the printer at the same time. This, in addition to saving an extra gate, also avoids using an extra i/o instruction.

Step 5: software design. The COUNT and PRINT routines are shown in Table 1.

6800 implementation

Step 4: hardware design. We use the same procedures to derive the interface hardware of the Motorola 6800. The reader's attention is drawn to the fact that the two interfaces are almost identical.

Step 5: software design. The PRINT and COUNT routines are shown in Table 1.

Well-defined steps for the design and implementation of interrupt interfaces have been demonstrated. Specifically, it has been shown that the interface hardware is the same for both vectored and non-vectored interrupts and that it is almost independent of the microprocessor chip used.

References

1. Zissos, D. "Problems and Solutions in Logic Design," Edition 2, Oxford University Press, 1979.
2. Duncan, F. G. "Microprocessor Programming and Software Development", Pentice-Hall, 1979.

The next article in the series will deal with interrupt controllers.

Correction note

Data store by running average, May 1981, contained three incorrect hex bytes in the machine-code list. The correct values are underlined. We apologise for these errors.

Address		
02E4	<u>B5</u>	28
036D	<u>B0</u>	<u>E5</u>
03D0	<u>A6</u>	26

Which way h.f. broadcast receivers

continued from page 67

The prescaler and prom devices used in the first system approach design are quite expensive at present. A 'direct entry without calculation' method could be used to replace the prom devices, but the cost reduction would be balanced out by adding twelve different crystal oscillators due to the fact that no simple arithmetic relation exists among the shortwave broadcasting bands. An alternative approach is, however, to ask whether a rearranged frequency allocation plan could end up with a cheaper system design. Fig. 2 shows the system functional block diagram. The suggested frequency allocation proposal is listed in Table 3. The amount of spectrum allocated is the same; but the band edge starting frequencies are slightly offset from the current and proposed WARC frequencies.

TABLE 3. Suggested proposal

rf (MHz)	osc (MHz)	offset (MHz)
3.900 to 4.390	48.900 to 49.390	48.895
4.600 to 4.945	49.600 to 49.945	48.895 + 0.700
4.950 to 5.440	49.950 to 50.440	48.895 + 1.050
6.000 to 6.490	51.000 to 51.490	48.895 + 2.100
8.100 to 8.590	53.100 to 53.590	48.895 + 4.200
10.200 to 10.690	55.200 to 55.690	48.895 + 6.300
12.300 to 12.790	57.300 to 57.790	48.895 + 8.400
14.400 to 14.890	59.400 to 59.890	48.895 + 10.500
16.500 to 16.990	61.500 to 61.990	48.895 + 12.600
20.700 to 21.190	65.700 to 66.190	48.895 + 16.800
24.900 to 25.390	69.900 to 70.390	48.895 + 21.000

Prior to the programmable divider, the v.c.o. output is converted down twice, first by a fixed 48.895MHz frequency signal, then by a correspondent band offset frequency signal generated from a one signal source and selected through multiplier or dividers. After these conversions, the v.c.o. frequency is equal to the channel number times and channel spacing frequency; therefore the programmable divider can be programmed directly by the b.c.d. number in the channel memory unit. Because of the low v.c.o. frequency at the input terminal of programmable divider, no prescaler is required. After comparison with the reference signal in the phase comparator unit, an error voltage is generated through the loop filter to correct the v.c.o. frequency. The fact that the prescaler and PROM devices are not required, the whole system cost is greatly reduced because of the frequency allocation. The r.f., i.f. signal amplification and selection, sideband detection and audio amplification are the same as the first system approach.

Microprocessors

Microprocessors have invaded almost every branch of electronic technology which includes radio communications as well. There is no doubt about some advantages of using microprocessors in product design, such as: "intelligent" products, easy design modification and reduced assembly and testing cost, is a long-term prospect. To see whether a popular shortwave broadcast receiver could benefit from this new technology or not, we check

the necessity of using microprocessors against the basic requirement of the majority shortwave broadcast listeners.

(1) Easy operating: microprocessors could be used to replace Ch/Band switching unit, memory unit and prom unit.

(2) Good performance: no improvement after using microprocessors unless a sophisticated self-adaptive receiver⁶ design is implemented.

(3) Low cost: one of the disadvantages of using microprocessors is the requirement of reinvestment for new tools and resources and possible re-training in production engineering. Although the unit cost of the microprocessor is low, the overall unit receiver cost could be the same as when a specially developed l.s.i. device is produced for a large number receiver market⁹.

Today, due to the advanced integration technique, most parts of the system block diagram could be integrated as a few l.s.i. modules, and consequently the assembly and testing cost could also be reduced. Therefore, unless a multi-functional receiver is demanded^{6,7}, we do not see a desire to use microprocessors in popular shortwave broadcast receiver design.

Conclusion

Two system approaches have been described for a popular shortwave broadcast receiver design. Both demonstrate the simple "tuning by channel" operating philosophy. They also bring out realization of an easy-operating, good performance and low-cost shortwave broadcast receiver.

References

1. E.B.U. Document SPB 108, "Statistics on the present occupancy of the h.f. bands for broadcasting", Sept. 1979.
2. E.B.U. Document SPB 130, "joint meeting between representatives of national receiver and transmitter manufacturers' associations and EBU sub-group R1", Feb. 1980.
3. PEEK, J. B. H. and SCHMIDT, J. M., "A station programme identification (s.p.i. system for f.m. sound broadcasting)", International Broadcast Convention, No. 166, 1978, pp.321-323.
4. The P.I. System, leaflet issued by the Swedish Telecommunication Administration, 1979.
5. WHYTHE, D. J. and ELY, S. R., "Data and identification signalling for future radio receivers", IEE/IBC Conf. No. 166, Sept. 1978, pp.324-326.
6. WINN, R. F. E., "H.f. radio communication", Wireless World, Jan. 1980, pp.54-58.
7. FUKUK, et al., "Portable all-band radio receiver using microcomputer controlled PLL synthesizer", IEEE Transactions on Consumer Electronics, Vol. CE-26, Aug. 1980.
8. E.B.U. Document SPB 66, Appendix 2, "Economic aspects of s.s.b. Transmitters", June 1978.
9. SYED, I. A., "Simplified l.s.i. Design", New Electronics, Jan. 27th, 1981.
10. Long- and medium-wave Broadcasting Conference, Geneva 1975, EBU Document 140F, Annex 1.
11. Macario, R. C. V., "An all digitally operated receiver for the new medium frequency broadcasting plan", IEE/IBC Conference No 166, Sept 1978, pp 330-332.

Electrical and mechanical units — are they the same?

by D. A. Bell, F.Inst.P., F.I.E.E.

SI units, with L,M,T,Q dimensions, provide a single consistent set for both mechanical and electrical applications. The presence of the Q dimension distinguishes electrical from purely mechanical phenomena.

"Units of the world unite: you have nothing to lose but your dimensions!" If scientists used slogans as politicians do, this might have been the call for the introduction of SI (Système International) units which unify electrical and mechanical units. As far as electrical units are concerned, they appear to involve little change from MKS units, though there is a change in the status of those odd but essential constants, ϵ_0 and μ_0 . The change is more drastic in mechanical units, which might be said to have been brought into line with electrical practice. In particular, it is now recognised that heat and mechanical energy are within limits interchangeable, something which was demonstrated by Rumford in 1798 and first quantified by Joule in 1842. The result is that heat energy is in future to be measured in joules* instead of in calories. The equivalence is 'within limits' because the experiments of Rumford and Joule were concerned with the transformation of mechanical energy into heat; but the converse transformation is subject to Carnot's law, that the proportion of heat which can be transformed to mechanical energy cannot exceed $(T_1 - T_2)/T_1$ where T_1 and T_2 are the upper and lower temperatures, e.g. temperatures of boiler and condenser of steam plant. It is this limitation which gives rise to the allegation that electric power stations have an "efficiency" of only about one-third.

To return to electrical units, we now have only one set of units instead of three: for example current is now measured only in amperes, discarding the c.g.s. electromagnetic unit of current which was equal to ten amperes and the c.g.s. electrostatic unit which was equal to one-third of a nanoampere. (The reason for the ratio between electromagnetic and electrostatic c.g.s. units being numerically equal to the velocity of light will appear later.) A separate idea which has been absorbed via MKS into the SI system is that of rational-

* For large quantities of heat energy, which have often been expressed in tonnes of coal equivalent or tonnes of oil equivalent, the unit much bigger than a megajoule is the *exajoule* (EJ) which is 10^{18} joules.

ised units. This idea is that a factor involving π can reasonably be expected in circumstances involving spherical or circular geometry, e.g. the electric field around a charged sphere or the capacitance between concentric cylinders, but not where the geometry is planar, e.g. the capacitance between two parallel plane electrodes. (C.g.s. formulae are exactly the reverse of this.) The simplest electrical formula is that for the potential V at distance r from a point charge q :

$$V = \frac{q}{4\pi\epsilon_0 r} \quad (1)$$

4π is the rationalising factor, since the system has spherical symmetry; and if q is in coulombs and r in metres, then V is in volts. How does this happy coincidence of units come about?

Through choice of a suitable value of ϵ_0 of course! So the first function of ϵ_0 is to be of the right size as a unit-forming constant. Mechanical units also are brought in through the formula for the force F between two charges:

$$F = \frac{q_1 q_2}{4\pi\epsilon_0 r^2} \quad (2)$$

The force F will be in Newtons. It is convenient also to introduce the idea of an *electric field* E such that $F = qE$ and E in volts per metre is given by

$$E = \frac{q}{4\pi\epsilon_0 r^2} \quad (3)$$

So far it has been assumed that nothing else is present apart from the charges represented in the formulae, i.e. that the charges are in a vacuum. (The results are very nearly the same if they are in air.) Now suppose the charges are immersed in a fluid having a property described as relative permittivity ϵ_r (relative to a vacuum) which is none other than what we have long known as "dielectric constant": its value is usually dependent on frequency and temperature, but is around 2.3 for benzene, 7 for porcelain and 80 for water at low frequency and room temperature. It is an experimental fact that equation (2) now becomes

$$F = \frac{q_1 q_2}{4\pi\epsilon_r \epsilon_0 r^2} \quad (2a)$$

and so (3) is changed to

$$E = q/4\pi\epsilon_r \epsilon_0 r^2 \quad (3a)$$

In order to obtain a quantity which depends only on q and r , not on the surrounding medium, (3a) is transposed into the form

$$\epsilon_r \epsilon_0 E = q/4\pi r^2 = D \quad (3b)$$

The new quantity D was originally called the flux of electric induction. It has the useful property that the integral of D over any closed surface is equal to the charge enclosed (Gauss's theorem in rationalised units): this is obvious in (3b) if the charge is imagined to be surrounded by a sphere of radius r and therefore surface $4\pi r^2$. D is measured in coulombs per square metre in SI units. Note that ϵ_0 , as well as ϵ_r , has been transferred to the left-hand side of (3b); and ϵ_0 , which we originally introduced as a constant serving to give the right size of unit, is commonly called "the permittivity of free space", which is where the controversy begins. Some physicists argue that permittivity is a property of matter, and therefore free space cannot have a permittivity. Accordingly, they claim that the c.g.s. system of units is inherently correct in putting $\epsilon_0 = 1$, because in free space D must then be the same as E , not merely numerically equal to it. Engineers find it convenient to distinguish between D and E because engineering is concerned with the behaviour of material objects.[†] (It is also a link with displacement current, but that is another story.) However, there is also a conceptual argument that D is a causal property of charge and that E is an effect which may be modified by the interposition of a material medium having the property described by the constant ϵ_r ; and ϵ_0 is not necessarily a pure number but is the constant factor relating effect E to cause D . This makes D appear to be more fundamental than E , though in practice it may be difficult to say which is the hen and which is the egg!

It is now known that magnetic phenomena are manifestations of *currents*, which can usually be identified with charges in motion. The relevant formulae look more complicated because a current, unlike a static charge, has direction as well as magnitude; and the equations therefore have to be in vector form. Most of them, however, can be obtained from the analogous

[†] Perhaps one should qualify this as "old-fashioned engineering", since there is now talk of "software engineering".

electrostatic equations by the rule-of-thumb procedure "replace scalars and scalar operations by vectors and vector operations and replace $1/\epsilon_0$ by μ_0 ." Thus the magnetic equation analogous to (3) is

$$d\mathbf{B} = \mu_0 i d\mathbf{l} \times \mathbf{a}_r / 4\pi r^2 \quad (4)$$

and the analogue of (2) is

$$d\mathbf{F} = \mu_0 i d\mathbf{l} \times i' d\mathbf{l}' \times \mathbf{a}_r / 4\pi r^2 \quad (5)$$

Because the different parts of the current (circuit) may be at different distances from the point of observation, equation (4) gives only the contribution $d\mathbf{B}$ to the total magnetic effect \mathbf{B} at a given point, the contribution being that due to a short element $i d\mathbf{l}$ of the current, which is at distance r from the point. The quantities in bold type are vectors, the symbol \times here represents vector multiplication and \mathbf{a}_r is a unit vector in the direction of r . Equation (4) means that the direction of $d\mathbf{B}$ is at right-angles to both the direction of current flow and the direction of r . (This is part of the definition of 'vector multiplication'.) Note that an equation for \mathbf{B} has been offered as analogous to the one for \mathbf{E} , a consequence of replacing $1/\epsilon_0$ by μ_0 . In fact \mathbf{H} is the property of current which is independent of surrounding medium (the analogue of Gauss's theorem for \mathbf{D} is that the line integral of \mathbf{H} round a closed circuit is equal to the current enclosed) and therefore analogous to \mathbf{D} . This time we are accustomed to regarding \mathbf{H} as a cause and \mathbf{B} as its effect. Initially μ_0 also can be regarded as a unit-forming constant, the function of which is to ensure that the force between two currents comes out in Newtons.

So much for units; but what of "dimensions"? It is familiar that all mechanical units can be related back to the fundamentals of length, mass and time: for example, force = mass \times acceleration leads to a dimensional relation $[F] = [MLT^{-2}]$. Some quantity additional to L, M and T may be needed for electrical phenomena and in the c.g.s. system this was taken as either ϵ or μ so that every quantity had two sets of dimensions as well as two sizes of unit. What can be demonstrated experimentally, by giving a capacitor a charge which is measured in c.g.s. electrostatic units and discharging it through a meter which measures the current in c.g.s. electromagnetic units, is that the ratio of numerical values in the two sets of units is equal to the numerical value of the speed of light. It is, moreover, implicit in Maxwell's equations that the velocity of propagation of electromagnetic radiation is $1/(\mu\epsilon)^{1/2}$ from which it is deduced that the inverse of the product of μ and ϵ has the dimensions of the square of velocity.

There is no certain method of dividing the dimensions $L^{-2}T^2$ between μ and ϵ . But it seemed a plausible conjecture (no more) that since magnetic effects are due to charges in motion the dimensions of velocity squared should be associated with equation (5). Since current = charge/time, the current-length product $i d\mathbf{l}$ is equivalent to a charge-velocity product; and if μ_0 has dimensions which differ from those of

ϵ_0 by $L^{-2}T^2$ then μ_0 will cancel out the velocities in $i d\mathbf{l}$ and $i' d\mathbf{l}'$ and we shall have force related to charge²/distance² in both (5) and (2). It is tempting to suggest that if μ_0 has only the dimensions of velocity⁻² and ϵ_0 is purely numeric, then the dimensions of charge can be expressed in terms of L, M, T through either equation. But this could be a trap for the unwary. It is equally possible that there is an electrical dimension which appears equally in μ_0 and $1/\epsilon_0$ and therefore cancels out in the product $\mu\epsilon$. It is equally plausible, however, the electrical phenomena must involve more than the purely mechanical dimensions of length, mass and time. In SI units, therefore, one takes the reasonable step of taking Q as a further dimension to add to L, M, T . On this basis it is found from equations (2) and (5) that ϵ_0 and μ_0 have dimensions $L^{-3}M^{-1}T^2Q^2$ and LMQ^{-2} respectively. M and Q cancel out in the product $\mu_0\epsilon_0$, leaving the dimensions $L^{-2}T^2$ of velocity⁻². One might wonder how this squares with the specification of ϵ_0 and μ_0 in units of farads per metre and henries per metre respectively. The fact is that both farads and henries involve all four L, M, T, Q dimensions (as can be seen from the fact that $1/2 CV^2$ and $1/2 Li^2$ are energies) so that these specifications are still valid in the self-consistent system of SI units. The important difference between the MKS and SI systems is the SI postulate that Q should be taken as the electrical 'dimension', in contrast to both the c.g.s. and MKS systems, though the MKSA system (A for ampere) was half-way there. But incidentally, ϵ_0 and μ_0 now have dimensions which are contrary to the c.g.s.-based argument that D and E are identical in free space. I wonder how long the matter will be allowed to rest there. □

Literature received

Engineering Bulletin 3539A from Sprague describes a range of Tanite chip capacitors with conformal plated terminations. The capacitors are of the solid-electrolyte type, for use in hybrid circuits. The bulletin can be obtained from the UK distributor, Hy-Comp Ltd, 7 Shield Road, Ashford Industrial Estate, Ashford, Middlesex TW15 1AV. WW401

Catalogue of components and instruments is available from HRS Components, Ltd, Brasshouse Passage, Birmingham B1 2HR. WW402

Short catalogue describing a range of plastic-film capacitors with values in the range 100pF to 20 μ F can be obtained from Ashcroft Electronics Ltd, 28 Somerford Road, Cirencester GL7 1TW. WW403

Leaflet on the 3M Videodata communication system for installation in buildings is available. This is nothing to do with a videotext system, but is concerned with the use of coaxial cables instead of multicore types to carry video and data throughout a building. The system is broadband, which allows the connexion of new equipment relatively cheaply. Copies from Mike Bellamy, Interactive Systems Group, 3M (UK) Ltd., 3M House, PO Box 1, Bracknell, Berkshire RG12 1JU. WW404

Sound synthesis using Walsh functions

continued from page 64

i.s.i. implementation, interested readers may like to consider the application of computer-generated Walsh functions. Clearly a microprocessor-based system could be realised enabling the software implementation of fully polyphonic musical sounds.

Effects of relative phase of harmonics

If a sine wave oscillator is set to a frequency of 220Hz and its output summed after passing through a variable phase shift network with that of a second sine wave oscillator of frequency 440Hz, the resulting waveshape, displayed on an oscilloscope, alters as the relative phase of the two components is varied. If the waveform is also listened to however no apparent change in sound is perceived by the ear, regardless of the phase relationship. Therefore as far as steady-state sounds are concerned, the relative phase of the individual partials in direct Fourier synthesis is irrelevant.

With regard to Walsh harmonics, B. A. Hutchins, whose work first prompted my interest in Walsh synthesis, has conducted synthesis experiments using different Walsh/Fourier series for the same waveform and has demonstrated differences in tone colour which are directly attributable to the use of different phase relationships. The effect is connected with the problem of monaural phase.⁴ Interested readers may like to generate the triangular wave mentioned earlier using the Walsh/Fourier series than quoted, and compare the sound perceived when the alternative Walsh/Fourier series +0.5wal1, -0.25wal5, -0.125wal13, -0.063wal29 is used.

Acknowledgment. The concept of using Walsh functions for musical synthesis was first suggested by Dr C. Frederick of the Centre for Radiophysics and Space Research, Cornell University. □

References

- 1 K. Siemens and R. Kitai, Digital Walsh/Fourier analysis of periodic waveforms, *IEEE Trans.*, vol. IM-18, December 1969, p. 316.
- 2 J. L. Walsh, Closed set of normal orthogonal functions, *American Journal of Mathematics*, vol. 45, 1925, p. 5.
- 3 H. F. Harmuth, Transmission of Information by Orthogonal Functions, 2nd Edition, Springer-Verlag DDR 1972, pp. 90, 91.
- 4 V. Lozhkin, Monaural phase effects, *Soviet Physics Acoustics*, vol. 17, no. 1, July-Sept 1971.

NEW PRODUCTS

LCR bridge

Combined inductance/capacitance, resistance and Q are the LCR Data-bridge 410's three manually selectable function ranges. On the LC range the bridge distinguishes between inductors and capacitors and gives the value and the appropriate units automatically. All four functions have overridable auto-ranging through eight decades. Measuring frequencies of 100Hz and 1kHz are selected manually, but an indication is given when the component under test can be measured more accurately using the frequency not selected. A similar indication is given for series and parallel measurement modes when the best mode for a given component is not selected. Range limits are 1m Ω to 100M Ω , 0.1 μ H to 9999H, 0.1pF to 9999 μ F and 0.1 to 99 for Q measurements, all with a basic accuracy

of 0.25%, ± 1 digit. Six push-buttons are the only controls and the reading, obtained within one second of insertion of the component, is given on a 4-digit i.e.d. display. The unit of measurement is indicated by one of nine i.e.ds, except in the case of the Q range when all range i.e.ds are extinguished. Input protection, a switchable polarizing voltage for electrolytics and a socket for external test leads or fixtures are also provided. Internally, a Z80 microprocessor carries out the control functions. An option is available with digital outputs for use with limits comparators, and the standard version costs £495. AIM Cambridge Ltd, Burrei Rd, Indust. Est., St Ives, Huntingdon, Cambs PE17 4LF.

WW301



Video editing interface

Trigger Happy is designed to help organisations who have a U-matic edit pair of video recorders but who want to use material shot on low-gauge cassette or open-reel format. Built to a Fantasy Factory specification, it "bridged the editing gap between consumer and U-matic formats", allowing fast editing from 1/2in feed decks (VHS, Beta, Sony 3670, National 3150) direct onto a 3/4in U-matic edit deck via a normal edit controller.

Trigger Happy obviates the need for a transfer first onto U-matic with a resulting loss of quality, or for tedious stop-watch editing. It contains two counter-displays, one which counts control track pulses from the feed deck, the other which is preset to a number specific to the edit controller being used. A start pulse causes the U-matic edit deck to roll down to the edit point at precisely the right time.

According to its designer,



WW303



A.m./f.m. signal generator

A fully programmable microprocessor-controlled signal generator covering the range 10kHz to 1024MHz has been introduced to the market by Marconi Instruments Ltd. The manufacturers claim that the 2017 gives signals that are completely free from non-harmonic spurious additions from 4 to 1024MHz, ± 1 dB level accuracy, 4V output across the complete frequency range and a sideband noise figure better than -136dB/Hz at 20kHz offset in the range 256 to 512MHz. A slow-sweep facility provides an analogue sweep between any two frequencies on one of nine carrier ranges so that spurious responses within a receiver can

easily be found. The carrier frequency can be stepped up or down in steps of any size and the total shift at any point indicated on depression of a key. Two methods of manual control are used: one digital using a keyboard, and one analogue using rotary controls. Programming via a general purpose interface bus (IEEE-488) extends the range of applications to include a.t.e. systems. The 2017 is said to be simple to use and a memory facility is provided so that up to ten frequencies can be stored for later use. Marconi Instruments Ltd, Longacres, St Albans, Herts AL4 0JN.

WW302

Richard Monkhouse of Costronics, Trigger Happy Mk2 is easy to interface as modification data and kits are provided (state feed deck and controller), no mechanical modifications being needed except for fitting sockets. Price is £440 from sole distributors Fantasy Factory Video Ltd (a registered charity company), at 42 Theobalds Road, London WC1 8NW.

WW303

High-temperature thermistors

The range of thermistors available from Electrautom has been expanded by the inclusion of the Mid-Temp series for temperatures from 200 to 600°C. These devices can be used as temperature sensing elements in cookers, soldering irons and photo-copier fuser rollers. Electrautom Ltd, Etom House, Queens Rd, Maidstone, Kent ME16 0JG.

WW304

Microcomputer


Both a microcomputer for business and personal use and applications software are available from LSI Computers Ltd. The standard M Three computer, manufactured in Great Britain, is based on the Z80 microprocessor with 64K r.a.m., two double-density 51/4in floppy disc drives, v.d.u. and keyboard with 109 keys, fourteen of which are programmable.

Versions with the two 51/4in disc drives replaced with two 8in double-density drives and Centronix matrix printers for use with the system can also be supplied. A CP/M operating system is included as standard. The basic system costs under £3000, excluding v.a.t. LSI Computers Ltd, Copse Rd, St Johns, Woking, Surrey GU21 15X.

WW305

IEEE data bus connectors

Up to fifteen programmable measurement or instrumentation devices can be interconnected using the Amphenol terminated cable assemblies to IEEE 488 interface standards. Each assembly comprises a 24-core screened cable and two rack and panel type connectors, i.e. connectors with combined plug and socket, which can be mounted upon each other in 'piggy-back' fashion. Of the 24 conductors, 16 are used for signal lines and eight for logic ground returns and shielding. Celdis Ltd, 37 Loverock Rd, Reading, Berks RG3 1ED.

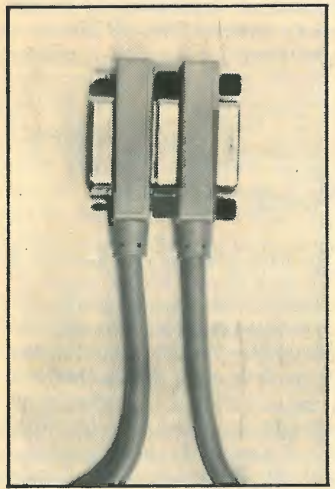

WW306

Power supplies

Voltage stabilized, current limited power supplies ranging from 2.5A, 10-15V internally adjustable units to '19in' laboratory types capable of delivering more than 15A from 0 to 65V are available in the UK through Big Ears (seriously). EA-Produktion, the German manufacturers, claim that the complete range consists of more than 150 models, each of which has a two year guarantee. The latter type mentioned above has fine and




WW305

coarse controls for both current and voltage, 40mV maximum output variation from 0 to 100% mains variation, an output temperature coefficient of 0.01%/°K and resistor or voltage programmable output voltage and current. All laboratory types have s.c.r. pre-regulation for low dissipation and can be supplied with either l.c.d. or analogue meters. Plug-in supplies for covering 5-24V and 0.5-10A, converters for 12V d.c. to 220V a.c. and combined variable a.c. and d.c. supplies are included in the range. As far as we know, all these supplies are designed for 220V±10% mains operation. Four 'low-price' units were tested by us using a 240V mains supply, and found to perform well under all loads. Two weeks delivery is quoted for units that cannot be supplied from stock. Big Ears, 68 Narborough Rd, Leicester.

WW307

Brushless d.c. motor

Drive electronics of the GAE 43.14 brushless Hall effect controlled d.c. motor are mounted on the stator for compactness. This unit, measuring 56×30mm, can produce up to 2Ncm torque and has a nominal running speed of 2000 r.p.m. which can be varied using an external control circuit. Supply voltages range from 18 to 30V; for a 24-volt version the supply current is 200mA. Ball bearings are used on the 4mm diameter drive shaft for the dynamically balanced high inertia rotor. Papst Motors Ltd, Parnell Court, East Portway, Andover, Hamps SP10 3LX.

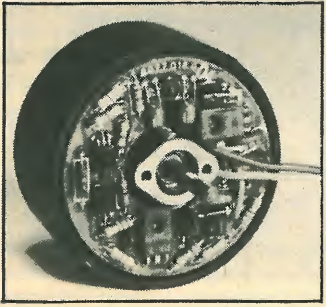


WW308

Four-layer p.t.h. board for prototypes

A four-layer plated-through printed circuit board suitable for prototypes or small production runs has been introduced by Logiclaver, a subsidiary of ICL. The p.c.b., known as Multiboard, is arranged as a matrix of 60×88 drilled pads spaced at 0.1in. The component side, or X tracking, has pads connected at regular intervals in columns, and the underside, or Y tracking, has different pads connected at regular intervals in rows. Sandwiched between the X and Y layers are a ground or 0V layer, and a power supply layer which provides two interleaved supply rails. The ground and supply rails are connected to three sets of pads regularly spaced throughout the board.

To assemble a circuit, the components are placed in their optimum positions and they are then interconnected by linking and cutting tracks on pads using isolated pads where necessary.


Multiboard is manufactured in a standard Eurocard size, 233.4×160mm, and will accept DIN connectors at the front or rear. The board has a characteristic impedance of 50Ω which is maintained after customising. When a completed board has been tested, Logiclaver can produce a production run of customised boards from layout drawings or cut and link information supplied with pad addresses. Logiclaver, Plymouth Grove, Manchester M13 9LN.

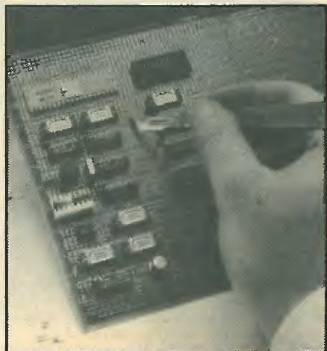

WW309

R.f.i. suppression filters


Negligible d.c. and low frequency voltage drop coupled with high insertion loss for a wide range of frequencies are features quoted for the 1.5 and 5nF radio-frequency interference filters from Oxley Developments Co. Ltd. Minimum insertion losses from 200MHz to 1GHz are 45dB for the 1.5nF type and 50dB for the 5nF type. Maximum limits of these pi-section ceramic devices are 350V d.c., 10A d.c. or low-frequency a.c. and -55 to 85°C operating temperature. Both the FLTM/P/1500 (1.5nF) and FLTM/P/5000 (5nF) types have stud mounting packages with M5 threads. Versions with 12UNEF threads are also available. Oxley Developments Co. Ltd, Ulverston, Cumbria LA12 9QG.

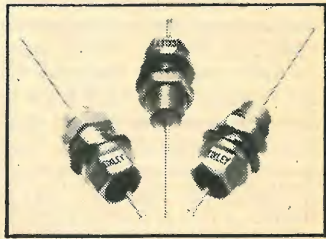

WW310

Silicone-free thermal grease


In applications where silicone contamination from thermal grease causes problems, Thermalcote II could provide an alternative. This grease, which at 36°C provides a minimum thermal conductivity of 16.7×10^{-4} cal/s cm°C, is said not to dry out, melt or give migration problems. A high-lubricity oil base is used which permits the compound to flow into small gaps and the working temperature is 165°C (200°C max). The manufacturers, Thermalloy, have also introduced a 1/2in high heat sink, for mounting on top of T03 transistor packages, which can be used on its own or combined with existing p.c.b. mounting heat-sinks for additional cooling. MCP Electronics Ltd, 38 Rosemont Road, Alpertown, Wembley, Middx HA0 4PE.

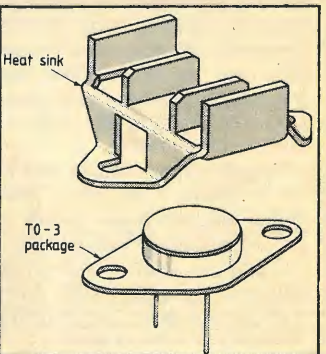

WW311

TRANSCENDENT 2000 single-board synthesizer

Complete Kit £168.50

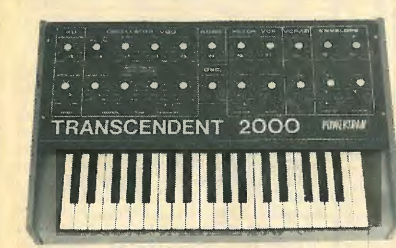

Designed by consultant Tim Orr (formerly synthesizer designer for EMS Ltd.) and featured as a constructional article in ETI, this live performance synthesizer is a 3-octave instrument transposable 2 octaves up or down giving sweep control, a noise generator and an ADSR envelope shaper. There is also a slow oscillator, a new pitch detector, ADSR repeat, sample and hold, and special circuitry with precision components to ensure tuning stability amongst its many features.

The kit includes fully-finished metalwork, fully assembled solid teak cabinet, filter sweep pedal, professional quality components (all resistors either 2% metal oxide or 1/2% metal film), and it really is complete - right down to the last nut and bolt and last piece of wire! There is even a 13A plug in the kit - you need buy absolutely no more parts before plugging in and making great music! Virtually all the components are on the one professional quality fibreglass PCB printed with component locations. All the controls mount directly on the main board, all connections to the board are made with connector plugs and construction is so simple it can be built in a few evenings by almost anyone capable of neat soldering! When finished you will possess a synthesizer comparable in performance and quality with ready-built units selling for many times the price.

Comprehensive handbook fully describes construction and tells you how to set up your synthesizer with nothing more elaborate than a multi-meter and a pair of ears!

TRANSCENDENT DPX MULTI-VOICE SYNTHESIZER Complete Kit £299



The Transcendent DPX is a really versatile 5 octave keyboard instrument. These are two audio outputs which can be used simultaneously. On the first there is a beautiful harpsichord or reed sound - fully polyphonic, i.e. you can play chords with as many notes as you like. On the second output there is a wide range of different voices, still fully polyphonic. It can be a straightforward piano or a honky tonk piano or even a mixture of the two! Alternatively you can play strings over the whole range of the keyboard or brass over the whole range of the keyboard or should you prefer - strings on the top of the keyboard and brass on the lower end (the keyboard is electronically split after the first two octaves) or vice versa or even a combination of strings and brass sounds simultaneously. And on all voices you can switch in circuitry to make the keyboard touch sensitive! The harder you press down a key the louder it sounds - just like an acoustic piano. The digitally controlled multiplexed system makes practical touch sensitivity with the complex dynamics law necessary for a high degree of realism. There is a master volume and tone control, a separate control for the brass sounds and also a vibrato circuit with

variable depth control together with a variable delay control so that the vibrato comes in only after waiting a short time after the note is struck for even more realistic string sounds.

To add interest to the sounds and make them more natural there is a chorus/ensemble unit which is a complex phasing system using CCD (charge coupled device) analogue delay lines. The overall effect of this is similar to that of several acoustic instruments playing the same piece of music. The ensemble circuitry can be switched in with either strong or mild effects.

Although the DPX is an advanced design using a very large amount of circuitry, much of it very sophisticated, the kit is mechanically extremely simple with excellent access to all the circuit boards which interconnect with multiway connectors, just four of which are removed to separate the keyboard circuitry and the panel circuitry from the main circuitry in the cabinet. The kit includes fully finished metalwork, solid teak cabinet, professional quality components (all resistors 2% metal oxide), nuts, bolts, even a 13A plug!

PORTWAY INDUSTRIAL EST.
ANDOVER, HANTS, SP10 3MM

POWERTRAN
WORLD LEADERS IN
ELECTRONIC KITS

Our Catalogue is FREE!
Write or phone now!
ANDOVER (0264) 64455

DE LUXE LINSLEY HOOD 75W STEREO AMPLIFIER



Complete Kit
£85

This easy-to-build version of our world-wide acclaimed 75W amplifier kit based upon circuit boards interconnected with gold plated contacts resulting in minimal wiring and construction delightfully straightforward. The design was published in Hi-Fi News and Record Review and features include rubber filter, variable scratch filter, versatile tone controls and tape monitoring while distortion is less than 0.01%.

MPA 200 100W. (rms into 8 ohms) MIXER/AMPLIFIER

COMPLETE KIT
£49.90



Featured as a constructional article in ETI, the MPA 200 is an exceptionally low priced - but professionally finished - general purpose high

power amplifier. It features adaptable input mixer which accepts a wider range of sources such as microphone, guitar, etc. There are wide range tone controls and a master volume control. Mechanically the MPA 200 is simplicity itself with minimal wiring needed making construction very straightforward. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. - complete down to the last nut and bolt.

COMPLETE KIT
£64.90

SP2-200 2-CHANNEL 100W. AMPLIFIER



The power amplifier section of the MPA 200 has proved not only very economical but very rugged and reliable too. This new design uses two of these amplifier sections powered by separate power supplies fed from a common toroidal transformer. Input sensitivity is 775mV. Even simultaneously driven, each channel delivers over 100W rms into 8 ohms. The kit includes fully finished metalwork, fibreglass PCBs, controls, wire, etc. - complete down to the last nut and bolt!

NEW KITS!

Programmed from a synthesizer, our latest design to be featured in ELECTRONICS TODAY INTERNATIONAL, the 1024 COMPOSER controls the synth. with a sequence of up to 1024 notes or a large number of shorter sequences e.g. 64 of 16 notes all with programmable note length. In addition a rest or series of rests can be entered. It is mains powered but an automatically trickle charged Nickel-Cadmium battery supplying the memory, preserves the program after switch off. The kit includes fully finished metalwork, fibreglass PCB, controls, wire, etc. - Complete down to the last nut and bolt!

1024 COMPOSER Complete Kit £89.50



DJ90 DISCO SYSTEM - COMING SHORTLY!

READ ALL ABOUT IT!
In Electronics Today International July issue




All kits also available as separate packs (e.g. PCB, component sets, hardware sets, etc.). Prices in our FREE CATALOGUE.

PRICE STABILITY: Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement until August 31, 1981, if this month's advertisement is mentioned with your order. Errors and VAT rate change excluded.

EXPORT ORDERS: No VAT. Postage charges at actual cost plus £1 handling and postal documentation.
U.K. ORDERS: Subject to 15% surcharge for VAT. NO charge is made for carriage.

SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit.
SALES COUNTER: If you prefer to collect your kit from the factory. Call at Sales Counter. Open 9 a.m. to 12 noon, 1 to 4.30 p.m. Monday to Thursday.

V.A.T. NOT INCLUDED IN PRICES

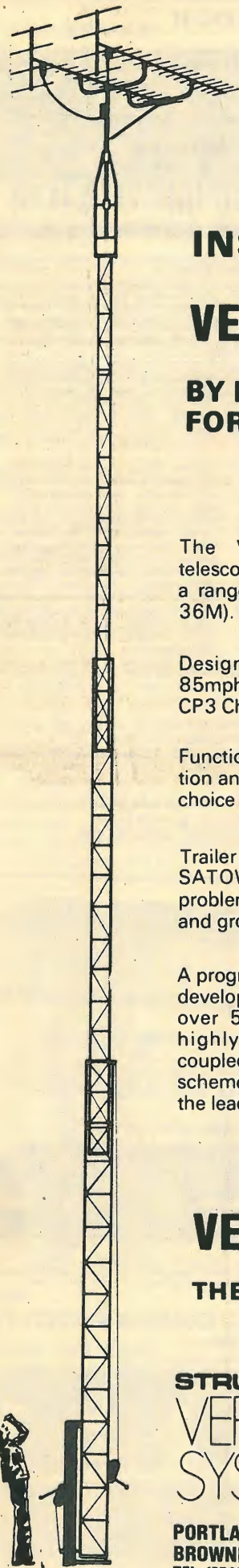

INSIST ON VERSATOWER

BY PROFESSIONALS—FOR PROFESSIONALS

The VERSATOWER range of telescopic and tilt-over towers cover a range of 25ft to 120ft (7.5M to 36M).

Designed for Wind Speeds from 85mph to 117mph conforming with CP3 Chapter V, part 11.

Functional design, rugged construction and total versatility make it first choice for telecommunications.

Trailer mounted or static, the VERSATOWER solves those difficult problems of antenna support, access and ground level maintenance.

A programme of continuous product development has led to a range of over 50 models, all available at highly competitive prices. This coupled with our quality assurance scheme ensures that we maintain the leader position we enjoy today.

VERSATOWER THE PROFESSIONALS' CHOICE

STRUMECH VERSATOWER SYSTEM

PORTLAND HOUSE, COPPICE SIDE BROWNHILLS, WEST MIDLANDS
TEL: (05433) 4321. TELEX: 335243 SEL

WW-067 FOR FURTHER DETAILS

MAINS INTERCOM NEW IMPROVED

£37.99
 + VAT £5.70 per pair
NO BATTERIES, NO WIRES. Made to high Safety and Telecommunications Standard. The modern way of instant 2-way communications. Just plug into power socket. Ready for use. Crystal clear communications from room to room. Range 1/4 mile on the same mains phase with call buzzer and light indicator. On-off switch. Volume control. Useful as inter-office intercom between office and warehouse, in surgery and in homes, between house and garage. Also useful as burglar alarm. 6 months' service guarantee. P&P £1.95. Also F.M. 2 channel model £55.95 + VAT £8.40 + P&P £2.15 per pair.

NEW! AMERICAN TYPE CRADLE TELEPHONE AMPLIFIER

ONLY £18.95
 + VAT £2.85 + P&P £1.65
 New improved battery operated Telephone Amplifier with detached plug-in speaker. Placing the receiver on to the cradle activates on/off switch for immediate two-way conversation without holding the handset. Many people can listen at a time. Increases efficiency in office, shop, workshop. Perfect for conference calls, leaves the user's hands free to make notes, consult files. No "holding on", save money and long-distance calls. Volume control. Model with conversation recording facilities. Price £20.95 + VAT £3.15, post and packing for either model £1.65.
 10 days' price refund guarantee.
 Barclaycard and Access welcome.

WEST LONDON DIRECT SUPPLIES (WW)
 169 KENSINGTON HIGH STREET, LONDON W8 6SN. TEL: 01-937 5548.

FOTOLAK

POSITIVE LIGHT SENSITIVE AEROSOL LACQUER

Enables YOU to produce perfect printed circuits in minutes!
 Method Spray cleaned board with lacquer. When dry, place positive master of required circuit on now sensitized surface. Expose to daylight, develop and etch. Any number of exact copies can of course be made from one master. Widely used in industry for prototype work.

FOTOLAK	£2.00	Pre-coated 1/16" Fibre-glass board	
Developer	30p	204mm x 114mm	£1.50
Ferric Chloride	50p	204mm x 228mm	£3.00
		408mm x 228mm	£6.00
		467mm x 305mm	£9.00

Plain Copper-clad Fibre-glass.	Single-sided	Double-sided
Approx. 3.18mm thick sq. ft.		£1.50
Approx. 2.00mm thick sq. ft.	£2.00	
Approx. 1.00mm thick sq. ft.	£1.50	£1.75
Clear Acetate Sheet for making master, 260mm x 260mm		12p

Postage and packing 80p per order. VAT 15% on total
G. F. MILLWARD ELECTRONIC COMPONENTS LIMITED
 P.O. Box 19, Praa Sands, Penzance, Cornwall. Telephone GERM0E (073-678) 2329

WATCH OUR **TELEVISION**

...the only magazine in Britain that gives the amateur enthusiast and professional engineer alike a comprehensive up-to-date coverage of TV technology. Coverage includes the latest developments in circuitry, video and long distance television...with a special emphasis on servicing and fault finding.
 Regular construction articles have included test equipment, monochrome & colour receivers, monitors and a video camera.

THIS MONTH
VIDEO EFFECTS GENERATOR
 A versatile monochrome studio set-up for the amateur TV programme maker.

ELECTRONIC AERIAL SWITCHING
 Roger Bunney's latest ingenious design.

COLOUR PORTABLE PROJECT - part 3

SERVICING THE GEC HYBRID COLOUR SETS

ON SALE NOW 70p

Well worth a closer look

TELEVISION

ELECTROVALUE

BEST SELLERS...

Rechargeable Cells by SANYO-CADNICA. Size AA 99p; C 2.27; D 3.76; PP3 4.10. With tags: AA 1.06, C 2.43, D 3.99
 Chargers PP3 4.75, AA 4.95, A.C.D 7.60. Plastic boxes PB1 116 x 77 x 35mm 62p.
 Breadboards Euro 5.70N, Veroblock 3.63, Bimboard 8.03, Buzzer 6-15V 80p.
 CAPACITORS Polystyrene 47-4700pF ea 7p, C280 .01 6p, 1 7p, 22 9p (full range). Polyester (PCM 7.5mm), .001 6p, .0047 7p, .056 8p, 1 9p, (PCM 10mm) 1uF 26p. (Many more values in this range). Variable Dilecon 100pF 2.08, 500pF 3.21.
 ELECTROLYTICS Full range.
 CONNECTORS - 1/4" jack plug 32p, skt 12p, 3.5mm jack plug 17p, skt 14p, 2.5mm 12p, DIP header 14 pin 38p, 16 pin 43p. Quick test mains block 5.25.
 Fuse holders 20mm panel 22p, chassis 6p. Hall-effect devices from 1.80N.
 Heat sinks Power 1.25°C/W 2.85, finger type 103 25p, T0220 25p.
 INTEGRATED CIRCUITS - Hundreds of types 741 18p, 555 23p, CA3140E 40p, LM380N 99p, LM3914N 2.68, S566B 2.14, TCA965 1.20. IC holders 8 pin 9p, 14-40 pin 1p per pin. Knobs, screw fitting 1/4" from 16p. Loudspeakers 2 1/2" 8 or 64 ohms 93p. Magneto resistors from 1.60N. Meters, panel 60x45mm 50uA-1A ea 4.80. Opto LEDs red 7p, yellow 9p, green 11p, ultrabright 21p all colours. LED drivers UAA170/UAA180 ea 1.52.
 POTENTIOMETERS - Carbon 20mm dia, 100R-2M 1in, 220R-4M 7 log scale 29p, 1K-2M 2in, 4K7-2M 2 log duals, ea 81p. Add 51p if required with switch. Sliders mono 72p, stereo 1.18, bezel 34p. Wirewound 25R-10K, 3watt ea 1.50.
 PRINTED CIRCUIT MATERIALS
 300 x 150mm S/S SRBP 1.25, 1/gl 1.90, 500gm ferric chloride lab grade 3.40. Positiv 20 photo resist 74ml 1.65. Etch resist pen 1.05, silver paint 3g 4.14N. Relays 12v coil 3P2W 10A contacts 2.90. Resistors 1/3W, 1/2W, 3/4W 5% ea 2p. Metal oxide TR5 2% 5p, film MR25 5p. Semiconductors 1N4007 6p, 1N4148 3p, RCA2N3055 70p, BC107-9 family 14p, BC182/212 family 3p, BFR34A 63p, BFT65 1.19, C106D1 45p, TIP31A/32A ea 44p, TIP41A/42A ea 45p, TIP2955/TIP3055 ea 55p. Solder 500gm 60/40 20SWG 7.30N. Irons Antex C, CCN, CX or X25 ea 4.40N. Oryx50 temperature controlled 11.50N. ISO-TIP cordless with charger 24.00N.
 SWITCHES - Slider DPDT min 18p, std 20p. Wavechange 1P12W, 2P6W, 3P4W, 4P3W ea 40p. Time Switch 13A 3on/3off per day 14.68N. Min toggles silver contacts SPDT 57p, DPDT 80p, 3PDT 1.64, 4PDT 2.75. DIL gold plated 4PST 95p, 10PST 2.10.
 Miniature drills - 12Vdc TITAN 10.28N. TITAN kit 17.06N. Stand 12.00N. Tools CK pliers 4.70, cutters 6.10, strippers 4.95. Vero wiring system kit 4.42, wire 1.17. Computer Nascom 1 built £140.00N.
 NASCOM
 2 kit £295.00 complete (less 8X4118's £225.00N). P/S kit, 3amp 32.50N, 16K RAM kit 110.00N.
 Add VAT at 15% to all prices.
 Small order surcharge 40p if under 5.75. No inland P&P on CWO orders.

ELECTROVALUE LTD. DEPT. WW6, 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 (STD 0784. London 87). Telex 264475.
 Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

BEST SERVICE
 FOR KEEN BUYERS!
 S.A.E. brings comprehensive price list (Valid 3 mths). Covering catalogue '81
 Access and Barclaycards accepted
 Everything brand new & guaranteed
 Hard to find items
 Keen prices & discounts
 Special quantity discounts
 Speedy turn round on orders
 No P/P charges on U.K. C.W.O. orders over £5.75. (Add handling charge of 40p if under)
 Please add 15% V.A.T. to total value of all orders
 Shop hours: 9-5.30; Sats. to 9-1p.m.

SALE BY AUCTION

Due to a shift in concentration and production, the machines, assembly lines and also the entire plant and business equipment of a works are available. On behalf of the management of the firms GTE/Sylvania and Schwarzwälder Elektronik Werk I am selling by auction the plant of the firm.

SABA - Werk III
 Aussere Ailinger Strasse 14
 7990 Friedrichshafen, West Germany

Tuesday, 7th July, 1981, 10 a.m.
Wednesday, 8th July, 1981, 9.30 a.m.

For auction:
 Flow soldering plant with immersion bath, armament lines, ceiling circular conveyor, paint spray stations, drying kilns, ultrasonic degreasing plant, assembly lines, modern electroplating equipment, winding machines, de-insulating presses, bending and cutting automatic machines, testing compartments, transformers, hydraulic and pneumatic punches and presses, (Lifetestwagen) spot welding machines, rotary heat kiln, aerosol recovery plant, freon degreasing plant, mixer, Wolfram welding equipment, continuous heating kiln, hydrogen hatch kiln, eight and ten head lock and seal machines for 90° and 110° colour tubes as well as shelves, canteen equipment, machine tools, fork lift truck and over 1,000 items measuring and testing equipment for many more items.

Viewing: Monday, 6th July, 1981, from 10.00 to 17.00 hours; Tuesday, 7th July, 1981, from 8.00 to 9.45 hours; Wednesday, 8th July, 1981, from 8.00 to 9.15 hours. Preview can be arranged by telephone call. Catalogue with over 3,000 items on request.


HORST F. G. ANGERMANN HAMBURG
 VEREIDIGTER U. ÖFFENTLICH BESTELLTER VERSTEIGERER
 SCHÄTZER FÜR IMMOBILIEN, MASCHINEN UND INDUSTRIEANLAGEN
 2000 Hamburg 11 · Mattentwiete 5
 Telefon: (040) 36 76 91-93 · Telex: 02-13 303 · 02-15 272

10 OUT OF 10.— IT'S ELEKTRIK!

- Whose amplifiers sound audibly superior?
- Who supplies the BBC, IBA, top loudspeaker manufacturers international recording studios etc?
- Which power amplifier modules feature high speed, electronic protection, virtually zero TIM, negligible THD, 110dB S/N ratio, and a range of power outputs from 60-300 WRMS?
- Which amplifiers are guaranteed unconditionally stable thermally, electrically and mechanically?
- Whose reputation for back-up, service and friendly advice is second to none?
- Who makes amplifiers OEM capable of driving motors, magnets, vibrators etc?
- Who offers a complete hi-fi kit amplifier at half the cost of any comparable units?
- Who also specialise in active amplification?
- Who offers a complementary range of ancillary equipment such as heatsinks, bridge drivers and toroidal power supplies etc?
- Who is the leading name in innovative and proven amplification?

CrimsonElektrik

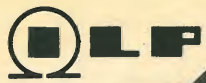If you would like further details on our complete range send a 7" x 10" sae + 50p cheque or PO for our comprehensive users / application manual to:
CRIMSON ELEKTRIK, (WW), 9 CLAYMILL ROAD, LEICESTER LE4 7JJ. Telephone 0533 761920 Telex 34694 CRIMLEK



SIMPLY AHEAD
and staying there

The range grows bigger... better...

New Profile Amplifiers - Two New Series



HY120



HY60

MOSFET

CHOOSE AN I.L.P. MOSFET POWER AMP when it is advantageous to have a faster slew rate, lower distortion at higher frequencies, enhanced thermal stability, the ability to work with complex loads without difficulty and complete absence of cross-over distortion. I.L.P.'s exclusive encapsulation technique within fully adequate heatsinks has been taken a stage further with specially developed computer-verified 'New Profile' extrusions. These ensure optimum operating efficiency from our new MOSFETS, and are easier to mount. Connection is via five pins on the underside. **I.L.P. MOSFETS ARE IDENTICAL IN PERFORMANCE TO THE CHEAPEST AMPLIFIERS IN THIS EXCITING NEW CATEGORY BUT ARE ONLY A FRACTION OF PRICES CHARGED ELSEWHERE.**


Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
MOS120	60W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£25.88 + £3.88
MOS200	120W into 4-8Ω	0.005%	20V/μs	3μs	100dB	£33.46 + £5.02

BIPOLAR


(Standard O-P Transistors)

CHOOSE AN I.L.P. BIPOLAR POWER AMP where power and price are first consideration while maintaining optimum performance with hi-fi quality and wide choice of models. From domestic hi-fi to disco and P.A., for instrument amplification, there is an I.L.P. Bipolar to fill the bill, and as with our new Mosfets, we have encapsulated Bipolars within our New Profile extrusions with their computer-verified thermal efficiency and improved mounting shoulders. Connections are simple, via five pins on the underside and with our newest pre-amps and power supply units, it becomes easier than ever to have a system layout housed the way you want it.

Model	Output Power RMS	Distortion Typical at 1KHz	Slew Rate	Rise Time	Signal/Noise Ratio DIN AUDIO	Price & VAT
HY30	15W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£7.29 + £1.09
HY60	30W into 4-8Ω	0.015%	15V/μs	5μs	100dB	£8.33 + £1.25
HY120	60W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£17.48 + £2.62
HY200	120W into 4-8Ω	0.01%	15V/μs	5μs	100dB	£21.21 + £3.18
HY400	240W into 4Ω	0.01%	15V/μs	5μs	100dB	£31.83 + £4.77

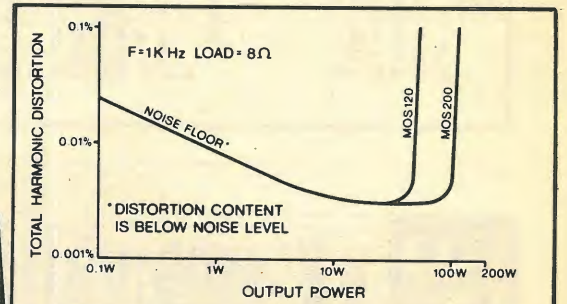

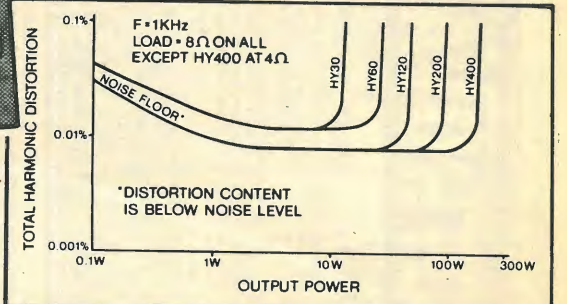Load impedance both models 4Ω - ∞ Input impedance both models 100KΩ
4Ω - ∞ Input sensitivity both models 500mV Frequency response both models 15Hz-100KHz - 3dB



Load impedance all models 4Ω - ∞ Input impedance all models 100KΩ
Input sensitivity all models 500mV Frequency response all models 15Hz-50KHz - 3dB



THE NEW PROFILE EXTRUSIONS
The introduction of standard heatsink extrusion for all I.L.P. power amplifiers achieves many advantages:— Research shows they provide optimum thermal dissipation and stability. Slotted shoulders allow easy mounting; standardisation enables us to keep our prices competitive. Surfaces are matt black, anodised for higher thermal conductivity. Extrusions vary in size according to module number.

NEW PRE-AMPS

HY6 (mono) and HY66 (stereo) are new to I.L.P.'s range of advanced audio modules. Their improved characteristics and styling ensure their being compatible with all I.L.P. power-amps both MOSFET and BIPOLAR, giving you chance to get the best possible reproduction from your equipment. HY6 and HY66 pre-amps are protected against short circuit and wrong polarity. Full assembly instructions are provided. Mounting boards are available as below.
Sizes - **HY6** - 45 x 20 x 40 mm. **HY66** - 90 x 20 x 40 mm. Active Tone Control circuits provide ±12dB cut and boost. **Inputs Sensitivity** - Mag. PU. - 3mV; Mic - selectable 1-12mV; All others 100mV. **Tape O/P** - 100mV; **Main O/P** - 500mV; **Frequency response** - D.C. to 100KHz - 3dB.

HY6 mono £6.44 + 97p VAT Connectors included
HY66 stereo £12.19 + £1.83 VAT Connectors included
B6 Mounting Board for one HY6 78p + 12p VAT
B66 Mounting Board for one HY66 99p + 15p VAT

NEW POWER SUPPLY UNITS

Of the eleven power supply units which comprise our current range, nine have toroidal transformers made in our own factory. Thus these I.L.P. power supply units are space-saving, more efficient and their better overall design helps enormously when assembly building. All models in the range are compatible with all I.L.P. amps and pre-amps with types to match whatever I.L.P. power amps you choose.

PSU30 ±15V at 100mA to drive up to 12 x HY6 or 6 x HY66 £4.50 + 0.68p VAT
● **THE FOLLOWING WILL ALSO DRIVE I.L.P. PRE-AMPS**
PSU36 for use with 1 or 2 HY30's £8.10 + £1.22 VAT
● **ALL THE FOLLOWING USE TOROIDAL TRANSFORMERS**
PSU50 for use with 1 or 2 HY60's £10.94 + £1.64 VAT
PSU60 for use with 1 HY120 £13.04 + £1.96 VAT
PSU65 for use with 1 MOS120 £13.32 + £2.00 VAT
PSU70 for use with 1 or 2 HY120's £15.92 + £2.39 VAT
PSU75 for use with 1 or 2 MOS120 £16.20 + £2.43 VAT
PSU90 for use with 1 HY200 £16.20 + £2.43 VAT
PSU95 for use with 1 MOS200 £16.32 + £2.45 VAT
PSU180 for use with 1 HY400 or 2 HY200 £21.34 + £3.20 VAT
PSU185 for use with 1 or 2 MOS200 £21.46 + £3.22 VAT

★ Freepost facility


When ordering or writing about I.L.P. products, you do not need to stamp the envelope. Mark it FREEPOST plus the code shown in the address below. We pay the postage for you.

★ TO ORDER

Send cheque or money order payable to I.L.P. Electronics Ltd and crossed. Or pay by ACCESS or BARCLAYCARD. Cash payments must be in registered envelope; if C.O.D. payment is wanted, please add £1.00 to TOTAL value of order.

* See also our ad. on page 101

COMPATIBLE WITH ALL I.L.P. MODULES

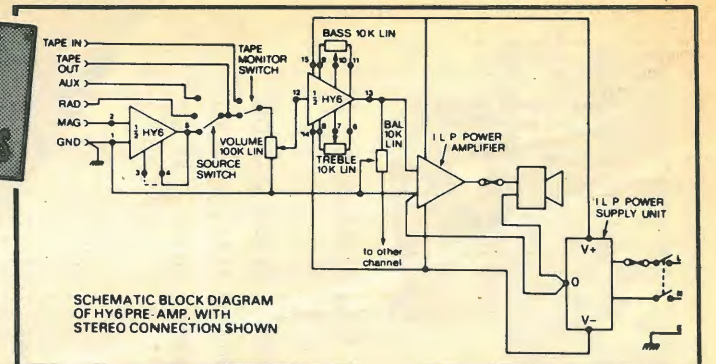

- DISTORTION TYPICALLY 0.005%
- S/N RATIO - 90dB (Mag. P.U. - 68 dB)
- 38 dB overload margin on Mag. P.U.
- LATEST DESIGN HIGH QUALITY CONNECTORS
- ONLY POTS, SWITCHES AND PLUGS/SOCKETS NEED ADDING
- NEEDS ONLY UNREGULATED POWER SUPPLY ±15 to ±60v

IN A RANGE OF 11 MODELS USING LATEST TOROIDAL TRANSFORMERS

We want to know

We have always maintained good working relations with our customers, and therein lies a large measure of the company's success and growth. Now that we are running our most exciting programme yet, we would like to have your comments about our current products and any others you would like to see coming from I.L.P. Send us your letter (with your age, job, etc., if you don't mind) to: Customer Liaison, I.L.P. Electronics Ltd., FREEPOST, Roper Close, Canterbury CT2 7EP (No stamp required).

BRITAIN'S FOREMOST QUALITY MODULE SUPPLIERS

To: I.L.P. ELECTRONICS LTD, CANTERBURY CT2 7EP

Please supply Total purchase price £

I enclose Cheque Postal Orders International Money Order

Please debit my Access/Barclaycard Account No.

NAME

ADDRESS

Signature WW7

NO QUIBBLE 5 YEAR GUARANTEE
7-DAY DESPATCH ON ALL ORDERS
BRITISH DESIGN AND MANUFACTURE
FREEPOST SERVICE



I.L.P. ELECTRONICS LTD.

FREE POST 5 Graham Bell House, Roper Close, Canterbury, Kent CT2 7EP.
Telephone (0227) 54778 [Technical (0227) 64723] Telex 965780

Available also from MARSHALLS, WATFORD ELECTRONICS and certain other selected retailers

WW - 074 FOR FURTHER DETAILS

ALL U.K. ORDERS DESPATCHED POST FREE

TEST INSTRUMENTS

- THANDAR- DIGITAL MULTIMETERS (LED) - PDM35 £39.68 DM235 £60.38 DM350 £83.38 DM450 £136.85...

PRODUCTION TESTING DEVELOPMENT SERVICING

POWER UNITS Now available with 3 OUTPUTS



Type 250VRU/30/25

OUTPUT 1: 0-30v, 25A DC OUTPUT 2: 0-70v, 10A AC OUTPUT 3: 0-250v, 4A AC

ALL Continuously Variable

VALRADIO LIMITED, BROWLES LANE, FELTHAM MIDDLESEX TW13 7EN Telephone: 01-890 4242/4837

WW - 047 FOR FURTHER DETAILS

LANGREX SUPPLIES LTD Climax House, Fallsbrook Rd., Streatham, London SW16 6ED RST Tel: 01-677 2424 Telex: 946708 RST

SEMICONDUCTORS

Table listing semiconductor components including diodes, transistors, and thyristors with their respective part numbers and prices.

VALVES

Table listing vacuum tubes (valves) such as 6X4, 6X5, 6X6, etc., with their specifications and prices.

BASES

Table listing various electronic bases and their prices.

CRTS

Table listing cathode ray tubes (CRTs) and their prices.

INTEGRATED CIRCUITS

Table listing integrated circuits and their prices.

Table listing various electronic components and their prices, including resistors and capacitors.

Many more instruments available in the LEADER and TMK ranges Send for catalogue 30p (including postage) Cash with order

DAROM SUPPLIES

Open: Monday to Friday 9 a.m.-5.30 p.m. 4 Sandy Lane, Stockton Heath WARRINGTON, WA4 2AY, CHESHIRE Telephone: (0925) 64764

WW - 048 FOR FURTHER DETAILS

B. BAMBER ELECTRONICS COMMUNICATIONS HOUSE

5 STATION ROAD, LITTLEPORT, CAMBS. CB6 10E PHONE: ELY (0353) 860185 (TUESDAY TO SATURDAY)

RADIO TELEPHONES

Pye Westminster W15AM high band and low band available. Sets complete and in good condition but are less speakers, mikes, cradles and LT leads (sets only) £80.00 ea.

Pye Westminster W15AM Mid Band crystalized and converted to 129.9MHz, 130.1MHz and 130.4MHz. Very good condition £140.00 ea.

Pye Westminster W15AMB (Boot Mount) low band complete with control gear and accessories. Good condition £92.00 ea.

Pye Westminster W30AM low band, sets only no control gear, complete and in good condition. £55.00 ea.

Pye Base Station F30AM low and high band, with and without remote and T/T. Prices from £220.00

Pye RTC Controller Units, for remotely controlling a VHF or UHF fixed station radiotelephones over landlines. £35.00 ea.

Pye PC1 Controller Units, similar to above but more modern. £100.00 ea.

Pye Olympic M201 Multi Channel AM sets complete but less mike, speaker and cradle. £120.00 ea.

Pye Reporter MF6AM High band mobile, very good condition. £175.00 ea.

Pye Motophones MF5AM high band and low band available. Sets complete and in good condition. £55.00

Pye Cambridge AM10B Dash Mount sets complete and in good condition but untested. £40.00 ea.

Pye Cambridge AM10B Boot Mount sets, high band 12.5kHz. sets only, no control gear, good condition. £25.00 ea.

Please note all sets are sold less crystals unless otherwise stated. Sets can be crystalized on your frequency at £20 per channel extra.

AMATEUR RADIO

Yaesu FRG7700 0.15-30MHz general coverage receiver, AM/FM/SSB/CW £309.00 Yaesu FRG7 0.5-30MHz. general coverage receiver AM/SSB £199.00 Yaesu FT707 1400m, 100w PEP, SSB, AM, CW, variable IF bandwidth digital 8 bander £529.00...

CB ACCESSORIES

K40 Antenna £31.00 Avanti 6' Moonraker (Mag.) £49.95 Avanti 6' Moonraker (Mag.) £28.56...

POWER SUPPLIES

Bremi 3/5 amp 13.8v £14.24 Bremi 3/5 amp Deluxe 13.8v £17.70 Bremi 5/7 amp 13.8v £19.90 Bremi 10 amp 13.8v £47.80

LINEARS (BURNERS)

Skipmaster 100w AM 180w SSB £118.90 Skipmaster 150w AM 190w SSB £137.00

ACCESSORIES

PA Horns (large) £12.50 PA Horns (medium) £9.22 RP20 RF Pre-Amplifier £16.45

TRANSISTORS

2SC495 £1.10 BA521 £4.16 2SC496 £1.31 LA4031P £3.21 2SC1096 £1.72 LC7120 £5.87 2SC1173 £1.69 LC7130 £5.93...



Hameg Oscilloscope HN307 bandwidth DC to 10MHz with component tester, 7cm dia. CRT, an ideal service instrument. £170.00 Standard C8800 2m FM mobile, digital readout, two speed scan rate for memories in 5 or 25kHz steps. 150w RF output £1.41

THE TELECOMMUNICATIONS SPECIALISTS

WW - 063 FOR FURTHER DETAILS

WW - 036 FOR FURTHER DETAILS

Terms of business: CWO. Postage and packing valves and semiconductors 40p per order. CRTs £1. All prices include VAT. Price ruling at time of despatch. In some cases prices of Mullard and USA valves will higher than those advertised. Prices correct when going to press. Account facilities available to approved companies with minimum order charge £10. Carriage and packing £1 on credit orders. Over 10,000 types of valves, tubes and semiconductors in stock. Quotations for any types not listed. S.A.E.

Telephone 01-677 2424/7 Telex 946708 E. & O.E. Open to callers Monday-Friday 9 a.m.-5 p.m.

Table with columns for VALVES, Minimum Order £1, and VALVES VAT IS INCLUDED. Lists various valve types and their prices.

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc. retail 749 3934, trade and export 743 0899.

COLOMOR (ELECTRONICS LTD.) 170 Goldhawk Rd., London W.12

FIELD TELEPHONES TYPE "J"

Tropical, in metal cases. MAGNETO SWITCHBOARD. Can work with every type of magneto telephones.

POSTAGE: £1-£3 45p; £3-£5 55p; £5-£10 60p; £10-£15 75p; £15-£20 90p; over £20 free.

Tel. 01-743 0899 or 01-749 3934 Open Monday to Friday 9 a.m.-5.30 p.m.


TV TUBE REBUILDING

Faircrest Engineering Ltd. manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono.

Willis Road, Croydon, CR0 2XX. 01-684 1422/01-684 0246

THE COMPLETE SOLUTION TO STRAIN GAUGE AMPLIFICATION

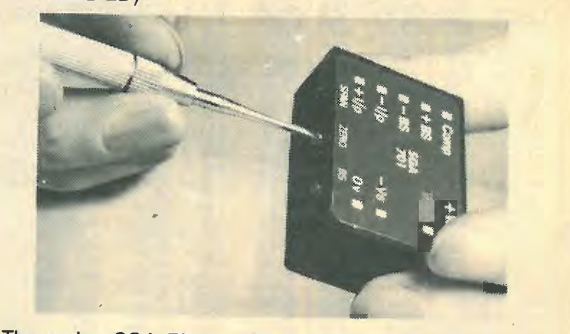- COMPLETE WITH BRIDGE SUPPLY
COMPLETE WITH ALL ADJUSTMENTS (SPAN ZERO BRIDGE VOLTAGE)
COMPLETE (NO EXTERNAL COMPONENTS NEEDED)



The series SGA 700 provides the complete solution to Strain Gauge Amplification. Simply connect the bridge, connect the power supplies and the SGA 700 does the rest.

CIL Electronics Ltd 14 Willowbrook Road, Worthing, Sussex BN14 8NA. Tel: Worthing (0903) 204646

WW - 052 FOR FURTHER DETAILS

TV TUBE REBUILDING

Willis Road, Croydon, CR0 2XX. 01-684 1422/01-684 0246

WW - 069 FOR FURTHER DETAILS

Table listing Mullard Modules (LP1171 Plus, LP1179, LP1186) and Ultrasonic Transducers (40KC/S).

HEWLETT-PACKARD DISPLAYS Half-inch red common anode. Definitely the brightest will replace (DL707).

VERO COMPUTER FRAMES 19 x 8in. with 64 runners and guides. NATIONAL 4116 Dynamic (16K RAM) 200 N/seconds, £1.95.

SCOOP ONLY £29.95 + V.A.T. BRITISH MADE 52 KEY 7 BIT ASCII CODED POSITIVE STROBE.

Professional ASCII Keyboards The 'CHERRY' Computer Keyboard Ideal for use with TANGERINE, TRITON, TUSCAN, APPLE and most computers.

404 Edgware Road London W2, England. 01-723 1008

COMPUTER WAREHOUSE NOW OPEN MONDAY-SATURDAY 9.30-5.30

In stock now test equipment, microprocessors, teletypes, transformers, power supplies, scopes, sig. gen's, motors, peripheral equipment, I.C.'s, tools, components, variacs, keyboards, transistors, microswitches, V.D.U.'s sub-assemblies + thousands of other stock lines.

Table listing RAM and EPROM prices: 2716 5v Rail £7.50, 2716 3 Rail £8.50, 2708 450 NS £4.50, 2708 Ex Equip £2.25.

TELETYPE ASR33 I/O TERMINALS From £195 + CAR + VAT
ICL TERMIPRINTER 300 BAUD TERMINALS
SCOOP PURCHASE 12" VIDEO MONITORS

CONNECT DIRECT TO YOUR MICRO Made by the "BALL MIRATEL" CORPORATION USA the CD12 is a self contained, mains powered chassis professional monitor.

EQUIPMENT CASES GIVE YOUR M.P.U. A HOME ONLY £9.95 + 1.85 pp

THE PRINTER SCOOP OF THE YEAR THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX180L MATRIX PRINTER

NATIONAL MA1012 LED CLOCK MODULE 12 HOUR ALARM 50/60 HZ

MAJOR SAVINGS HARD DISK DRIVES Another major purchase allows us to bring you the professional technology of hard disk drives at a price you can now afford.

SEMICONDUCTOR 'GRAB BAGS' Amazing value mixed semiconductors, include transistors, digital, linear I.C.'s, triacs, diodes, bridge recs. etc.

MUFFIN FANS Keep your equipment Cool and Reliable with our tested ex-equipment "Muffin Fans" almost silent running and easily mounted.

66% DISCOUNT Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains.

ELECTRONICS Dept. WW. 64-66 Melfort Rd., Thornton Heath, Croydon, Surrey. Tel: 01-689 7702 or 01-689 6800

WW - 076 FOR FURTHER DETAILS

STEP INTO THE 80's WITH TOMORROW'S WORLD TECHNOLOGY TODAY

THE TANTEL PRESTEL-VEWDATA ADAPTOR At last this amazing piece of micro technology is available at a price you can afford.

OPTIONAL EXTRAS Lower case £25.00 + 16K buffer £30.00 + Second tractor for simultaneous dual forms £85.00

IDEAL - TANGERINE, OHIO ETC. FULLY CASED ASCII CODED KEYBOARDS

Straight from the U.S.A. made by the world famous R.C.A. Co. the VP600 Series of cased freestanding keyboards meet all requirements of the most exciting user, right down to the price!

5v D.C. POWER SUPPLIES Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.



L.E.D.s .125 and .2

1N4148 Diodes	1+	100+	1000+	RED	1+	100+	1000+
	.02	.016	.013	Y. or G.	.08	.069	.058
					.11	.10	.09

CARBON FILM RESISTORS E12 SERIES

Prices per 100. Larger and Mixed. Quantity prices available.

	.25W	.5W
100 off one type	.70	.90
500 off one type	.62	.78
1000 off one type	.54	.68

LOW PROFILE I.C. SOCKETS

	TEXAS			SCANBE		
8 pin	1+	100+	500+	1+	100+	1000+
14 pin	.075	.068	.06	.059	.049	.044
16 pin	.09	.082	.073	.082	.07	.064
18 pin	.125	.113	.10	.104	.089	.081
20 pin	.14	.126	.113	.12	.10	.092
22 pin	.15	.135	.12	.143	.122	.111
24 pin	.15	.135	.12	.146	.132	.116
28 pin	.16	.145	.125	.155	.14	.12
40 pin	.24	.215	.19	.23	.195	.176

Please add £1.50 handling charge and 15% V.A.T.

We also stock Microprocessors, CMOS, TTL, Transistors, Capacitors, Potentiometers, Connectors, etc. Free catalogue available to trade customers only. Enquiries welcome.

Harrison Bros.

Electronic Distributors
22 Milton Road, Westcliff-on-Sea
Essex SS0 7JX, England
Tel: Southend-on-Sea (0702) 32338

WW - 035 FOR FURTHER DETAILS

TELEPRINTER TYPE 7B: Pageprinter 24v. d.c. power supply. Speed 50 bauds per min. S/hand, good cond. (no parts broken), £28.75. OR G.P.O. MODEL, as above except motor, 110/230v. a.c., £34.50. Carriage either type £9.50. Send S.A.E. for list of Teleprinter spares available.

TS.147 RADAR TEST SET Combination Sig. generator and frequency meter and power meter. Provides C.W. and F.M. signals, 115v. a.c., £225. Carr. £7.

HEWLETT PACKARD Signal Generator HP608B. Freq. 10-400MHz C.W. and A.M. Output 1 microvolt to 8v.50. Mod. 400-1000Hz. 230v. a.c., £225. Carr. £10.

TRANSISTORISED 3cm. RADAR AMPLIFIER SWITCH: with 24v. waveguide switch, 9 x 4cm ins. with crystal CV. 2355 and spark gap VX 1046, £17.95 + £1 post.

INSULATION TEST SET 0 to 10KV, negative earth, with Ionisation Amplifier, 100/230 volts a.c., £48.87 + carr.

BC-221 FREQUENCY METER: 125-20,000kc/s, complete with original calibration charts, £24.15 + carr.

ROTARY INVERTER TYPE: PE218E: Input 24-28v DC, 80 amps, 4,800r.p.m. Output 11v AC, 13 amp 400 c/s. 1Ph. P.F. 9. £23 + carr.

RESONATOR PERFORMANCE CTC 424 8.5 to 9.0 km/c/s 3 cm. £80.50 + post £2.

INVERTER 24v. DC input 400 cycles lPh 6600 r.p.m. 200v, peak, £8.05 + £2 post.

OXYGEN BOTTLE 1800lb. w.p. £11.50 + carr.

NOISE SOURCE UNIT with CV.1881 noise source mount. Produces thermal noise 15.5dB 200/250v. AC. £80.50.

SIEMENS POWER METER REL3U/84/Alb: 0-12kmHz 1mw 500mw 6 ranges. 0.17db 50 ohms, £92 + carr.

CV.1596 CATHODE RAY TUBE: (09D, 09G), 4in. screen, green electrostatic base B12B. HT1200 volts, heater 4 volts, £11.50.

VACUUM AND PRESSURE DEAL TEST EQUIPMENT: complete with 2 x 4in. gauges indicating 0.20lb. p.s.i. 0.30lb. vacuum. With stand, hand pump, etc., £34.50 + carr.

TX-RX RADAR UNIT, 3cm, complete with magnetron, pulse transformers, crystals, waveguides, blower unit, etc. £126.50 + carr.

MARCONI RF POWER METER, 1020A/1 dualrange 50 or 100W £69 + carr.

HEWLETT PACKARD POWER METER Type 431C, £75.50 + carr.

TWENTY MILLION MEGOMETER, £95 + carr.

GAUSS METER Type G1, 3 ranges, 5,000/10,000/25,000. £85 + carr.

SPERRY TRANSISTORISED SERVO-AMPLIFIERS TYPE C1 with circuit diagram, £11.50 + £1.50 post.

X-Y PLOTTER, £74.75 + £7 carriage.

C.C.T.V. EHT UNIT, 50kV, £75 + £10 carr.

C.C.T.V. CABLE, 22-Way, 500 metres, £650 + carriage.

BARGAIN MAPS

Large stocks of unused U.S.A.F. surplus maps, weather charts, etc. including:

- ONC-E1 — U.K. in full and part N.W. Europe. Scale 1:1,000,000.
- JNC-9N — N. Europe, U.K., Scandinavia. Scale 1:2,000,000.
- JN-21N — Europe (Mediterranean). Scale 1:2,000,000.
- SIZE 58" x 42" colour. Many others. Please send S.A.E. for list.

Price each 75p (inc. P&P)

25 x Maps (either same type OR assorted), £10 + £1.60 P&P.

10 x Maps (either same type OR assorted), £6.50 (in. P&P).

All prices include VAT at 15%
Carriage quotes given are for 50-mile radius of Herts.

W. MILLS

The Maltings, Station Road
SAWBURIDGEWORTH, Herts.
Tel: Bishop's Stortford (0279) 725872

RADIATION DETECTORS

BE PREPARED VIEW THRU LENS

Ideal for the experimenter

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture.
Tested and fully guaranteed. Ex-stock delivery.



01-723 1008/9

404 EDGWARE ROAD, LONDON W2 1ED

FREE RECHARGE SERVICE AFTER PURCHASE

£6.95
inc. VAT Post & Pack 60p

COMPLETE WITH DATA

REGULATED POWER SUPPLIES

Protection: All models internal foldback, overload, thermal and short circuit protected. Fully fused.

Type AD12-AD24 (Illustrated) TYPES AVAILABLE

MODEL NO.	AD12	AD24	AD24I2	ADV30
OUTPUT CURRENT	8 amp	8 amp	16 amp	5 amp
NOMINAL OUTPUT VOLTS	12	24	12	0 to 30
INPUT VOLTS	15-230-250	115-230-250	24 DC	115-230-250
TOLERATED MAINS VARIATION	15% 50 cycles a/c	15% 50 cycles a/c	15%	15% 50 cycles a/c

PRICES

1 off — AD 12-AD24	£68.50	1 off—ADV30	£118.00
1 off — AD 24I2	£54.00		

All subject to VAT @ 15%

2-YEAR GUARANTEE

SOUTHERN ELECTRONICS

6 WESTCLIFF ARCADE, RAMSGATE, KENT
TEL. THANET (0843) 57888

WW - 060 FOR FURTHER DETAILS

Patronics VHF FREQUENCY COUNTERS

SUPER VALUES!

For quality of construction, un-failing efficiency and sheer good value this

200MHz, 7 digit D.F.M.

is unequalled for direct readings up the mobile radio VHF Band. Will operate on mains or 12v supply, making it ideal for use with mobile equipment. Manufactured and guaranteed by Catronics Ltd.

Model DFM5 £119.55
+ £5 carr + 15% VAT Write for illustrated leaflet

HIGH STABILITY OVENED VERSION with better than 1 in 10⁷ reference oscillator DFM 5/S also available at £154.35 + £5 carr. + 15% VAT
Our popular 500 MHz Counter still available at only £142.50 + £5 carr. + 15% VAT

In addition to our famous 250MHz and 500MHz counters we have also produced a

200MHz COUNTER KIT
SPECIALLY FOR HOME CONSTRUCTORS

- Our new KF200 counter, although small is a no-compromise design. It offers:
- ★ A full 8-digit LED display
 - ★ A frequency range of 10Hz to 200MHz
 - ★ An accuracy of 10Hz at 30MHz, 50Hz at 150MHz in normal home environments
 - ★ 5/6-volt operation from batteries or mains PSU (not supplied)
 - ★ Power consumption of only 1W maximum
 - ★ Small size 4" x 2" x 1"
 - ★ Assembled in about 2 hours
 - ★ Full illustrated instructions
- The KF200 is supplied as 1 PCB assembly, which may be split, if required, to give a separate display unit. (Suitable for direct driving an 8 digit common cathode display.) The unit is available in kit or assembled/tested module form. Prices (INCLUDING V.A.T.):
- Counter Kit £72 Module £85
(Add 75p for Post and Packing)

Barclaycards & Access Welcome. Please quote card no.

Patronics
COMMUNICATIONS HOUSE,
20 WALLINGTON SQUARE,
WALLINGTON, SURREY SM6 8RG
Tel. 01-669 6700

WW - 009 FOR FURTHER DETAILS

ALWAYS A CHANGING RANGE OF OSCILLOSCOPES, COMPUTERS, TERMINALS ETC.

- Item No.
- 1 TEKTRONIX STORAGE OSCILLOSCOPE Type 434. Current Model. As new. 12 months warranty (No warranty £1,400) £1,850
 - 2 TEKTRONIX STORAGE OSCILLOSCOPE type 564 with 3A6 & 3B4 £350
 - 3 HAMEG OSCILLOSCOPE type 412. Dual Trace 20 MHz £250
 - 4 TELEQUIPMENT OSCILLOSCOPE type D61A. Dual Trace 10MHz £280
 - 5 SCOPEX OSCILLOSCOPE type 4D10. Dual Trace 10MHz £170
 - 6 HEWLETT PACKARD OSCILLOSCOPE type 120B. (X-Y) £120
 - 7 MARCONI WAVE ANALYSER TF2330. Good condition £150
 - 8 AVO UNIVERSAL BRIDGE B150 with adaptor A151 £80
 - 9 ADVANCE SIGNAL GENERATOR type E2 100KHz-100MHz £50
 - 10 B & K AUTO VIBRATOR EXCITER CONTROL type 1018 £20
 - 11 SOLARTRON Digital Voltmeter type LM1450 £40
 - 12 SOLARTRON PULSE GENERATOR type G0101.2 £40
 - 13 ADVANCE V.H.F. Millivoltmeter type VM79 — No probes £35
 - 14 ADVANCE A.F. SIGNAL GENERATOR type J2 £25
 - 15 KNIGHT RF Sig Gen KG686 with Sweep Marker Gen KG687. The Pair £90
 - 16 ADVANCE Audio Signal Generator HIE 15Hz to 50KHz £45
 - 17 BEULAH VIDEO MONITOR £50
 - 18 LYONS PULSE GENERATOR type PG-2E £45
 - 19 COSSOR SINE SQUARE WAVE GENERATOR 20Hz-1MHz £40
 - 20 AVO UNIVERSAL BRIDGE Type 1 £75
 - 21 P.S.I. RMS VOLTMETER type A1301 £90
 - 22 LABGEAR 625 COLOUR MATCH GENERATOR CM 6004-PG £30
 - 23 ADVANCE LF OSCILLATOR type S085A £75
 - 24 TAYLOR AMF/M SIGNAL GENERATOR type 62A Mk II £125
 - 25 MARCONI UNIVERSAL BRIDGE type TF1313 1/4% £200
 - 26 MARCONI WIDE RANGE OSCILLATOR type TF1370 10Hz-10MHz £90
 - 27 SOLARTRON TRUE RMS VOLTMETER type VM1484 £75
 - 28 RANK V.H.F. SIGNAL STRENGTH INDICATOR £25
 - 29 RACAL COUNTER ELECTRONIC FREQUENCY 32MHz type 836 £75
 - 30 WAYNE KERR CAPACITANCE BRIDGE type B541C £40
 - 31 WAYNE KERR COMPONENT BRIDGE type B121 £45
 - 32 HEWLETT PACKARD DC CURRENT SOURCE type 6181B 0-100V; 0-250mA £175
 - 33 MARCONI SAUNDERS LEVELLING AMPLIFIER type 6587 £175
 - 34 TEKTRONIX PRE TRIGGER PULSE GENERATOR type 111 £85
 - 35 RACAL H.F. SELECTIVE ANALYSER type 9056 £375
 - 36 MARCONI STANDARD SIGNAL GENERATOR type TF144H 10KHz-72MHz £225
 - 37 SCHLUMBERGER/SOLARTRON AUTOMATIC COUNTER type FB2602 £150
 - 38 BRANDENBURG PHOTOMULTIPLIER POWER UNIT 0-2500Volts £70
 - 39 SCHLUMBERGER/SOLARTRON COMPUTING VOLTMETER type JM1776 £90
 - 40 HEWLETT PACKARD AC CONVERTOR type 3461A £90
 - 41 MUIRHEAD WAVE ANALYSER K-134-A 30-310Hz £90
 - 42 PHILIPS COMPARATOR 278KHz £75
 - 43 HEATHKIT CAPACITOR CHECKER IT-28 £25
 - 44 HEWLETT PACKARD DIGITAL VOLTMETER type 3440A £60
 - 45 HEWLETT PACKARD FREQUENCY CONVERTOR type 8729A £130
 - 46 RACAL AUTO FREQUENCY CONVERTOR type 803R 500MHz £35
 - 47 AIRMEC ELECTRONIC VOLTMETER type 314A £75

- 48 VARIAN RUBIDIUM FREQUENCY STANDARD 100KHz/1MHz/5MHz £600
- 49 KEITHLEY INSTRUMENTS REGULATED HIGH VOLTAGE SUPPLY TYPE 241 Accuracy +/- 0.05% or 1mv. £250
- 50 T.O.A. ELECTRONIC POLYRECORDER type EPR-2T £90
- 51 STANDARD AIRCRAFT Radio Interference and Field Intensity Meter type NM-52A 375-1000MHz (2 pieces) £275
- 52 TAYLOR VALVE TESTER type 45D £45
- 53 RHODE & SCHWARZ UHF TEST RECEIVER BN1523 280-940MHz (400MHz) £120
- 54 R & S G DIAPHRAGM 300-2400 MHz BN3562 £285
- 55 R & S Unbalanced Standard ATTENUATOR BN18042/50 £45
- 56 R & S VHF-UHF FREQUENCY METER 30-3000MHz BN442 £60
- 57 R & S DIRECT CAPACITANCE METER BN5201 £75
- 58 WAYNE KERR UNIVERSAL BRIDGE type B521 (CT375) £50
- 59 B & K HETERODYNE VOLTMETER type 2005 £250
- 60 HEWLETT PACKARD CLIP ON DC MILLIAMPMETER type 428A with probe £70
- 61 SOLARTRON DIGITAL VOLTMETER type LM1420.2 £30
- 62 SOLARTRON DIGITAL VOLTMETER type 1420.2 with Mean AC Unit. £35
- 63 SOLARTRON DIGITAL VOLTMETER type 1867 £30
- 64 MARCONI SIGNAL GENERATOR type TF995A/3/S (CT402) £225
- 65 JARROL SWEEP GENERATOR 20-112 MHz £40
- 66 HEWLETT PACKARD VALVE VOLTMETER type 412A £35
- 67 HATHFIELD SELECTIVE LEVEL METER type 1001 £18
- 68 COSSOR NOISE LEVEL METER CT454 £35
- 69 HEATHKIT DECADE RESISTANCE BOX DR1U £10
- 70 MARCONI VARIABLE ATTENUATOR type TF1073A/S (CT421) £40
- 71 ROCHAR UNIVERSAL COUNTER TIMER type A1149 £80
- 72 WAYNE KERR UNIVERSAL BRIDGE type B521 £50
- 73 WAYNE KERR AF SIGNAL GENERATOR type S121 10Hz-120KHz £80
- 74 SIGNAL GENERATOR type CT344 0.1Hz-10MHz £30
- 75 CLARE FLASH TESTER type Q103B £15
- 76 MARCONI RF ATTENUATOR type TF1073A £35
- 77 HATHFIELD TRANSDUCER SELECTIVE LEVEL METER AV-3U £90
- 78 TELONIC SWEEPER 450-900MHz £55
- 79 COSSOR SWEEP OSCILLATOR type CT202 £35
- 80 DEIR DIGITAL VOLTMETER type 500 Mk 3 £20
- 81 AIRMEC AM/FM SIGNAL GENERATOR type 204 1-320MHz £130
- 82 HATHFIELD TRANSDUCER SELECTIVE LEVEL METER SPO 7820 £90
- 83 S.T.C. LEVEL MEASURING SET type 74309B £90
- 84 AVO TRANSISTOR ANALYSER type CT446 £30
- 85 SIEMENS SUPERHET RECEIVER 30Hz-1MHz £35
- 86 R & S MICROWAVE POWER METER BN2412/50 0-3200MHz £80
- 87 ADVANCE SIGNAL GENERATOR 848 100KHz-100MHz £25
- 88 HEWLETT PACKARD DIGITAL RECORDER type 5050B £25

JUST IN

B. & K. LEVEL RECORDER type 2305. 50db Potentiometer Brand New. With accessories. £9.50 ea.

HEWLETT PACKARD X-Y RECORDER type 7015B..... £600 ea.

GENERAL RADIO type 1360-B Microwave Osc. 1.7-4.1Ghz... £750

GR type 1142-A Frequency/Discriminator Meter 0-1.5Mhz... £225

GR type 1807 DC Microvoltmeter/Nanoammeter 1.5Kv maz/175 GR OSCILLATORS type 1209-C, 1209-OL; 1215-C (50-900MHz) with Power Unit type 1269-A..... £225

PLEASE CHECK AVAILABILITY BEFORE ORDERING

CONVERT THIS UNIT TO A SUPER BATTERY CHARGER

An active green ministry quality case with removable top and bottom plates — heavy duty power switches, high powered resistors to control current, good quality centre mounted amp meter, strip of wing nut terminals on front panel which can be used for connecting leads. All this for £3.50. P&P £3. Four units £12. Carriage £6.

STEPPING MOTORS

6/12 position with additional where the rotor is coils. Device can be used as a tacho. Diagram supplied. Will actually work on 5 volts. 12/24 recommended.

£1.50 each P&P 75p
or 5 for £5 P&P £1.50.

STEPPING MOTORS

200 Steps. 20 oz/in. torque, 12/24 volt input 5-wire

£12 ea, P&P £1.50

KEYBOARD PAD

Size 3x2 1/2x2 1/2" with 12 Alma Reed Switches. Blue keys marked in green 0-9 and a star with one blank.

£4 each. P&P £1, or 5 for £15 P&P £2.

MINIATURE KEYBOARD

Push contacts, marked 0-9 and A-F and 3 optional function keys. £1.75 each.

CRYSTALS 50p each

Flat metal case — 19.2KHz; 844.8KHz; B7G — 10MHz.

PULSE TRANSFORMER. Sub min. Size 1/2 x 5/16 x 1/4". Secondary centre tapped. New 20p ea.

REMO TY TYPE MULTIPLIER. Two high voltage outputs and fuses. £1 each.

DON'T TAKE CHANCES. Use the proper EHT CABLE. 10p per meter or £7.50 per 100 metre drum. P&P £2.

PHOTOGRAPHIC LAMPS. Pair 230V 500 watt. Screw cap. 75p ea. Box of 12 50p. P&P £1.50.

INFRA RED QUARTZ LAMPS. 230V 620 watts. Size 1 1/2" x 1/8" dia. £1.50 ea. 240V 1650 watts. Size 2 3/4" x 1/2" dia. £3 ea.

BRIDGE RECTIFIER. 2 Amp 50p ea.

PHOTODIODE DETECTOR 4" fly leads, 25p ea.

AMPHENOL. 17-way chassis mount edge connectors 0.1 spacing. 15p ea.

I.E.C. Standard MAINS LEAD. Moulded (3 vertical flat pins centre offset) 60p ea.

FANS. 115V 13 watts. Size 3/4 x 3/4 x 1 1/2" BRAND NEW. £4.50 ea. Secondhand £2.50.

DELAY LINE. 50 nanoseconds. 3 connections — ground-in-out. Size 2 x 7/16x5/16" New 25p ea.

SOME TEKTRONIX 500 RANGE OSCILLOSCOPES

with Single Trace Plug-ins Working.

From £100. Phone for details

DIODES

All new full spec. devices IN3063 BAX 13, 1544, 1N4148, 1N3470, 1N4151

100 off £1.50, 1,000 off £10

MULTIMETER Russian Type 4324 AC/DC volts; AC/DC current; Ohms, etc.

Brand New, boxed.

£12.50 each
P&P £2.50

METROHM INSULATION AND CONTINUITY TESTER 500 volts

Portable, Battery Operated, Standard P.P.7 (Battery not supplied). Complete with carrying case.

As new £40 each
Used but good condition £25 each.
P&P £3.

MOTOR 12V DC with pulley and integral semiconductor. Speed Control. New £1 ea.

LEDEX ROTARY SOLENOIDS. 115V DC. No switch assembly. 15p ea.

DIAMOND H CONTROLS ROTARY SWITCH. Single pole 10-way. Printed Circuit Mount. New 10p ea. 100 for £7.50

RAPID DISCHARGE capacitors 8mf4 4kV 5p each. P&P £2.

DECOUPLING CAPACITORS 0.05mf 10V; 0.01mf; 0.047mf 250V; 33k, 330pf. All values. 100 for £1.50.

E.H.T. Capacitor 500pF 8KV 20p each.

10-way MULTI COLOUR RIBBON CABLE. New 40p per metre. 10 metres for £3.

GEC UHF 4-button tuner £1.50 each.

CENTAUR 115V FANS. 4 1/2x4 1/2x1 1/2". £4.50 ea. Ex-equipment, tested 60p each.

CONTACTORS. Heavy Duty 24V DC 5 make £1 each.

GEC UHF/VHF 6-button tuner £2 each.

931A PHOTO MULTIPLIER E2 each. P&P £1.

RANCO 250V 18A THERMOSTATS with Control knobs calibrated 50-200 degrees C £2.50 each.

SOLID STATE UHF TUNERS. 38MHz. £1 each.

BRAND REX blue wire wraps. 30 metres for £1. P&P 25p.

TRANSFORMERS

AUTO 240V input 115V. 1 Amp output £1.25 each. P&P £1.25.

240V input. Soc. 6V, 1.86A. Size 2 1/2x2x2". Good quality £1.50 ea. P&P £1

240V input Soc. 12V 0.92A. Size 2 1/2x2x2". Good quality. £1.50 ea. P&P £1

240V input 12V 100MA. Size 60x40x42mm 50p each.

240V input. Soc. 1C 0-12V 50MA. Size 53 x 45 x 40mm. £1 ea.

115V input. Soc. 5V 250MA. Size 1 1/16 x 1 1/8 x 1 1/4. 2 for 50p.

115V input. Soc. 10-0-10V1A. Size 2 1/2 x 2 x 2 1/2. For £1.50.

SEMICONDUCTORS 1N4005 — 5p; 1N4002 — 3p.

At 5p each:
BC147, BC157, BC158, BC237, BF197, OA90, OA81, BC148B, BA154, BA243.

At 25p each:
TIP31, TIP41A, 2N5636, AF139, 2TX341.

BY127 10p. BF181 20p; BD239 49p; BD241 40p; MA343AT 49p; BD228 50p; BD233 & BD234 Comp Pair 25p — 80p per pair, at 50p each.

REGULATOR TBA625 8 to 20V in - 5V out 100MA T05 Con. 50p each BF256C 20p.

TV AMPLIFIER TBA 120 20p each.

CREED MODEL 75

Printer with keyboard. Late model. Still the cheapest way to get a printout from your microprocessor. Basic data and connections supplied.

Used, good condition

ONLY £25 each

MINIATURE VARIAC 0.6 AMP

In an attractive Blue Case with Carrying Handle. Size 10 1/4 x 6 1/4 x 6 1/2". With 20 good quality screw terminals with integral 4mm socket giving multiple voltage and current outputs.

As new condition. Individually Boxed.

£15 each. P&P £2

RADAR AERIALS

Rotary, complete with Waveguide Couplers. These are brand new, Ministry boxed. Very impressive. Dish diameter 27 inches.

£85 each. Carriage £5

EX-MINISTRY MASTS

40ft. HEAVY DUTY

With guys, etc. In transit case

£50 each. Carriage £5

INVERTOR, TYPE 350


Input 115 Volts DC. Output 115 Volts AC 400Hz, 3-Phase. Supplied with connection details.

Tested, good condition. £30 each

Tested but scruffy. £15 each
Carriage £5

INFRA RED IMAGE CONVERTER Type 9606 (CV 144)

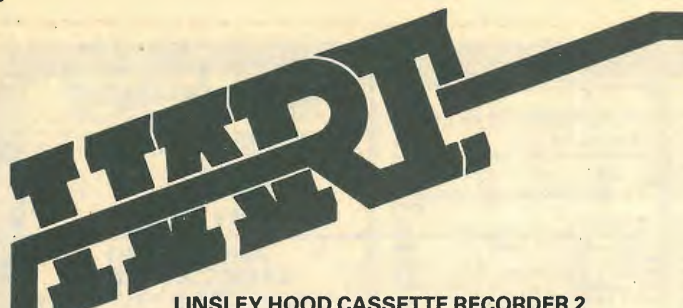1 3/4in. diameter. Requires single low current 3KV to 6KV



LINSLEY-HOOD 300 SERIES AMPLIFIERS

These latest designs from the drawing board of John Linsley-Hood, engineer to the very highest standard, represent the very best that is available on the kit market today.

Three versions are offered, a 30-watt with Darlingtone output transistors, and a 35- and 45-watt, both with Mosfet output devices. All are of identical outside appearance which is designed to match and stack with our Linsley-Hood cassette recorder 2.

Reprints of original Articles from Hi-Fi News 50p. Post free. No VAT. Reprints of MOSFET Article 25p. No V.A.T. Post free.

LINSLEY HOOD CASSETTE RECORDER 2



Our new improved performance model of the Linsley Hood Cassette Recorder incorporates our VFL 510 vertical front mechanism and circuit modifications to increase dynamic range.

LINSLEY-HOOD CASSETTE RECORDER 1



We are the Designer Approved suppliers of kits for this excellent design. The Author's reputation tells all you need to know about the quality and the experience guarantees the engineering design of the kit.

Part Cost of Post, Packing and Insurance

Order up to £10 - 50p Orders £10 to £49 - £1 P&P Export Orders - Postage or shipping at cost plus £2 Documentation and Handling Over £50 - £1.50

Please send 9 x 4 S.A.E. or telephone for lists giving fuller details and price breakdowns.

Instant easy ordering, telephone your requirements and credit card number to us on Oswestry (0691) 2894

FEED YOUR MICRO BYTES WITH OUR SOLENOID CONTROLLED CASSETTE DECK



Front loading deck with full solenoid control of all functions including optional search in fast wind modes. 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £2.70 plus V.A.T. and 50p postage.

CASSETTE HEADS

- HS16 SENDUST ALLOY SUPER HEAD. Stereo R/P. Longer life than Permalloy. Higher output than Ferrite. Fantastic frequency response. Complete with data. £8.20

All prices plus VAT

HART ELECTRONIC KITS LTD OSWESTRY SHROPSHIRE phone (0691) 2894 Telex 35661 Hartel G

Large table of electronic components including resistors, capacitors, diodes, and integrated circuits with their respective part numbers and prices.

RECHARGEABLE BATTERIES PRIVATE & TRADE ENQUIRIES WELCOME Full range available to replace 1.5 volt dry cells and 9 volt PP type batteries, SAE for lists and prices. £1.45 for booklet, "Nickel Cadmium Power," plus catalogue.

10 OUTLET DISTRIBUTION AMPLIFIER 2 STABILIZER FOR HOWL REDUCTION, BALANCED AND UNBALANCED VERSIONS BOXED OR RACK MOUNTING PUBLIC ADDRESS: SOUND REINFORCEMENT

NEW RETAIL SHOP 305 Edgware Road, W2 Open: 9.30 - 5.30 CALLERS WELCOME Please add 30p P&P & VAT 15%.

SPEECH SYNTHESISER (A Project by TEXAS INSTRUMENTS LTD) Superb major solid state speech project for under £100. Promises to have a dramatic impact on State-of-Art Electronics now, and for generations to come.

TECHNOMATIC LTD. 17 BURNLEY ROAD, LONDON NW10 (2 minutes Dollis Hill tube station) (ample street parking) Tel: 01-452 1500/01-450 6597 Telex: 922800

HERE IT IS! THE BRAND NEW 8022A HAND-HELD DMM

Consider the following features:
 6 resistance ranges from 200 ohm-20 ohms
 8 current ranges from 2mA-2A AC/DC
 10 voltage ranges from 200 mv-1000v DC-200 mc-750V AC
 Pocket size — weighing only 370 gms.
 Full overload protection — will withstand 6kv spikes
 Rugged construction — virtually indestructible
 Meets tough military specs — drop proof
 In line, pushbutton operation for single-handed use
 Incorporates low power CMOS chip for low power consumption
 All this plus a 2-year full guarantee

For only £89 + VAT **SOFT CARRYING CASE £7 extra**
 Carriage and Insurance £3

Even more sophisticated the Fluke 8020A
 Identical in most respects to the 8022A but in addition incorporates a conductance range from 2mS-200nS.

Price £125
 Carriage and insurance £3.00
 A handsome soft carrying case is included (this model only)

Y7206 EN
 20,000 OPV
 AC Volts: 0-10, 50, 250, 500, 1000.
 DC Volts: 0-0.5, 5, 25, 125, 250, 500, 1000.
 DC Current: 0-0.05, 5, 250mA.
 Resistance 0.3k ohms, 300k ohms, 3 meg ohms.
 Decibels — 20 — +63dB
 Dims 127 x 90 x 32mm.
£14.95 (inc. VAT)
 P&P £1

TMK500
 30,000 OPV
 A sturdy and reliable instrument. Has internal buzzer.
 AC Volts: 0 to 2.5, 10, 25, 100, 250, 500, 1000
 DC Volts 0 to 0.25, 1, 2.5, 10, 25, 100, 250, 1000
 DC Current: 0 to 50 µA, 5 ma, 50 ma, 12 amp.
 Resistance: 0 to 6K, 60K, 6 meg, 60 meg.
 Decibels: — 20 to +56dB.
 Short test: Internal buzzer.
 Size: 160 x 110 x 55 mm.
£27.95 (inc. VAT)
 P&P £1

OFF THE SHELF DELIVERY ON THESE

FLUKE

DIGITAL MULTIMETERS BRAND NEW FROM FLUKE!!! NOW AVAILABLE THE 8024A HAND HELD DMM

This model incorporates all the features of the 8020A but in addition has:
 A peak hold switch which can be used in AC or DC for volts and current functions.
 Audible continuity testing and level detection for sensing logic levels.
 A temperature (°C) range for use with a thermocouple. **£155**
 Carriage and Insurance £3

The following accessories are in stock now

Y8008 Touch and Hold Probe £29
 80K-40 High Voltage Probe £51
 81RF RF Probe to 100 MHz £35
 80T-150C Temperature Probe (C) £86
 801-800 Clamp-on AC Current Probe £61

8010A AND 8012A BENCH MODEL D.M.M.s

The 8010A is a general purpose, bench/portable digital multimeter with more functions and features than ever offered for such a low price. Its companion, the 8012A, has identical characteristics except that it has two additional low resistance ranges, 2Ω and 20Ω to replace the 8010A's 10 ampere current range.

The 8010A and 8012A feature:
 10 voltage ranges from 200mv - 1000v dc, 200mv - 75v ac.
 3 conductance ranges from 2mS - 200 nS.
 8 resistance ranges from 200Ω - 20mΩ - the 8012A has two additional resistance ranges 2Ω and 20Ω.
 10 current ranges from 200µA - 2A AC/DC - the 8010A has two additional current ranges 10A AC and 10A DC.

8010A £167 **8012A £218**
 Carriage and insurance £3

The 8010A is also available with two rechargeable Nicad size C batteries installed in option 8010 at £193.00.

LOW COST, AUTORANGING MULTI-FUNCTION COUNTER MODEL 1900A

- Autoranging in both frequency and period measurement modes
- Wide Frequency range — 5 Hz to 80 MHz
- High sensitivity — 25 mV, typically 15 mV
- Six digit LED display with leading zero suppression, automatic annunciation and overflow
- Optional internal battery pack providing 4 hours continuous operation
- Autoreset on all gate times, all function switches
- Four manually selected gate times providing resolution to 0.1 Hz
- Event counting to 10⁶ events with overflow indicator
- Signal input conditioning with switchable 1 MHz low pass filter and attenuator
- Rugged moulded case with convenient tilting/carrying handle
- Optional parallel data output with decimal point and annunciation
- Traditional high Fluke quality
- Self check

£235 Carriage and Insurance £3

PLEASE ADD 15% VAT TO ALL ORDERS EXCEPT WHERE ITEMS MARKED "VAT INCLUDED." CALLERS WELCOME

We are open 9 a.m. - 6 p.m. Monday-Saturday

We carry a very large selection of electronic components and electro-mechanical items. Special quotations on quantities

ROTARY STUD SWITCH
 PLESSEY 30-way, 2 bank.
 Single pole. Contacts 1 amp 240V, AC/DC. 0050 res.
 Make before break. Stop infinitely adjustable allowing for any desired arc of travel. Ideal for instrument and model switching. Size 2 3/4" dia overall x 2 1/2" deep plus 1 1/4" x 1/4" dia spindle.
£3.75 (inc. VAT)
 P&P 50p

BENDIX MAGNETIC CLUTCH
 Superb example of electro-mechanics. Main body in two sections, coil section fixed with 3/4" sleeve, drive section rotating on outer perimeter. Uniting plate has 3/8" ID bearing concentric with main section and 18-tooth cog wheel. Extremely powerful transmission. 24V D.C. 240 m/a.
£4.75 (inc. VAT)
 P. & P. 75p

ELECTRO-TECH COMPONENTS LTD.
 364 EDGWARE ROAD, LONDON, W.2. TEL: 01-723 5667

Happy Memories

4116	200ns	£1.70
2114	200ns	£2.95
2708	450ns	£3.35
2114	450ns	£1.95
2716	5 volt	£3.70

Soft-sectored mini-discs for PET, TRS-80 etc. Supplied in FREE LIBRARY CASE, £19.95 per 10


Low Profile I.C. Sockets by "Texas"
 Pins 8 14 16 18 20 22 24 28 40
 Pence 10 11 12 16 17 20 21 28 37

Memory Upgrade Kits for Apple, 2020, TRS-80, etc., from £13.60, please phone. Quantity prices available on request. Government and Educational Orders welcome. Trade accounts opened

All prices include VAT. Postage FREE on orders over £15, otherwise add 30p
 Access and Barclaycard welcome

HAPPY MEMORIES, DEPT. W.W.
GLADESTRY, KINGTON
HEREFORDSHIRE HR5 3NY
Tel. (054422) 618

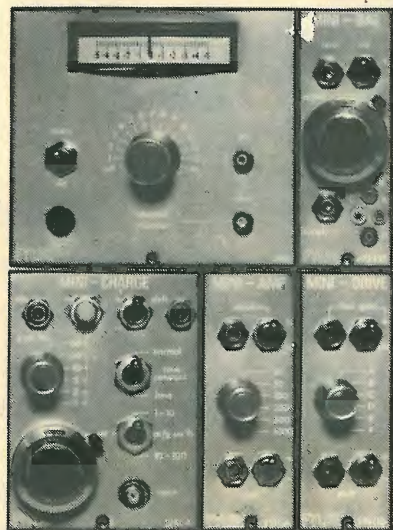FYLDE
TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. Individually powered modules— mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE Fylde Electronic Laboratories Limited.
 49/51 Fylde Road Preston PR1 2XQ
 Telephone 0772 57560

WW-072 FOR FURTHER DETAILS

P.&R. COMPUTER SHOP

EPSON MX-80 80.GPs DOT MATRIX PRINTER WITH SPECIAL INTERFACES. 3982 IBM I/O PRINTERS. VDUS, ASCII KEYBOARDS, ASR, KSR, TELETYPE, PAPER TAPE READERS, PAPER TAPE PUNCHES, SCOPES, TYPEWRITERS, FANS 4" 5" 6". POWER SUPPLIES, STORE CORES, TEST EQUIPMENT AND MISCELLANEOUS COMPUTER EQUIPMENT. OPEN: MONDAY TO FRIDAY 9am-5pm SATURDAY TILL 1pm.

COME AND LOOK AROUND
 SALCOTT MILL, GOLDHANGER ROAD
 HEYBRIDGE, ESSEX.
 PHONE MALDON (0621) 57440

WW - 024 FOR FURTHER DETAILS

CLEF ELECTRONIC MUSIC

PIANOS SPECIALISTS SINCE 1972 DOMESTIC & STAGE TYPES KITS OR MANUFACTURED

The most advanced form of Touch Sensitive action simulating piano key inertia by patented technique. Four mixable voices for serious tone variation plus electronic chorus and flanger effects. See lists for Cabinets, P.A. and Manufacture.

£79 KIT **£114 Built**

Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carr. & Ins. and we operate Telephone BARCLAYCARD. Visit our Showroom.

CLEF PRODUCTS (ELECTRONICS) LIMITED
 Dept. W, 44a Bramhall Lane South
 Bramhall, Stockport, Cheshire SK7 1AH
 061-439 3297

WW - 025 FOR FURTHER DETAILS

LLP TRANSFORMERS
 INCREASED PRODUCTION CAPACITY BRINGS LOWER PRICES

TOROIDAL IN A RANGE OF 76 TYPES FROM 30VA TO 500VA AND IN CHOICES OF THREE PRIMARIES 110V, 220V or 240V.

TYPE	SERIES No.	SECONDARY RMS Volts	CURRENT	PRICE
30VA 70x30mm 0.45 Kg	1X010	6+6	2.50	£4.48 +0.87p P/P +0.80p VAT
	1X011	9+9	1.66	
	1X012	12+12	1.25	
	1X013	15+15	1.00	
	1X014	18+18	0.83	
	1X015	22+22	0.68	
	1X016	25+25	0.60	
50VA 80x35mm 0.9 Kg	2X010	6+6	4.16	£4.93 +£1.10 P/P +0.90p VAT
	2X011	9+9	2.77	
	2X012	12+12	2.08	
	2X013	15+15	1.66	
	2X014	18+18	1.38	
	2X015	22+22	1.13	
	2X016	25+25	1.00	
80VA 90x30mm 1 Kg	3X010	6+6	6.64	£5.47 +£1.43 P/P +£1.04 VAT
	3X011	9+9	4.44	
	3X012	12+12	3.33	
	3X013	15+15	2.66	
	3X014	18+18	2.22	
	3X015	22+22	1.81	
	3X016	25+25	1.60	
120VA 90x40mm 1.2 Kg	4X010	6+6	10.00	£6.38 +£1.43 P/P +£1.17 VAT
	4X011	9+9	6.66	
	4X012	12+12	5.00	
	4X013	15+15	4.00	
	4X014	18+18	3.33	
	4X015	22+22	2.72	
	4X016	25+25	2.40	

TYPE	SERIES No.	SECONDARY RMS Volts	CURRENT	PRICE
160VA 110x40mm 1.8 Kg	5X012	12+12	6.66	£8.44 +£1.43 P/P +£1.48 VAT
	5X013	15+15	5.33	
	5X014	18+18	4.44	
	5X015	22+22	3.63	
	5X016	25+25	3.20	
	5X017	30+30	2.66	
	5X018	35+35	2.28	
225VA 110x45mm 2.2 Kg	6X014	18+18	6.25	£10.06 +£1.73 P/P +£1.77 VAT
	6X015	22+22	5.11	
	6X016	25+25	4.50	
	6X017	30+30	3.75	
	6X018	35+35	3.21	
	6X026	40+40	2.81	
	6X028	110	2.04	
300VA 110x50mm 2.6 Kg	7X016	25+25	6.00	£11.66 +£1.73 P/P +£2.01 VAT
	7X017	30+30	5.00	
	7X018	35+35	4.28	
	7X026	40+40	3.75	
	7X025	45+45	3.33	
	7X028	110	2.72	
	7X029	220	1.36	
500VA 140x60mm 4 Kg	8X017	30+30	8.33	£15.53 +£2.05 P/P +£2.64
	8X018	35+35	7.14	
	8X026	40+40	6.25	
	8X025	45+45	5.55	
	8X033	50+50	5.00	
	8X028	110	4.54	
	8X029	220	2.27	

+ A NEW SERIES OF P.C.B MOUNTING LAMINATED TYPES

TYPE	SERIES No.	SECONDARY RMS Volts	CURRENT	PRICE
3VA	P2401	3+3	0.50	0.92p +24p P/P +17p VAT
	P2402	4.5+4.5	0.33	
	P2403	6+6	0.25	
	P2404	7.5+7.5	0.20	
	P2405	9+9	0.17	
	P2406	12+12	0.12	
	P2407	15+15	0.10	
6VA	P3401	3+3	1.00	£1.91 +£30p P/P +33p VAT
	P3402	4.5+4.5	0.67	
	P3403	6+6	0.50	
	P3404	7.5+7.5	0.40	
	P3405	9+9	0.33	
	P3406	12+12	0.25	
	P3407	15+15	0.20	
12VA	P4401	3+3	2.00	£2.09 +58p P/P +40p VAT
	P4402	4.5+4.5	1.33	
	P4403	6+6	1.00	
	P4404	7.5+7.5	0.80	
	P4405	9+9	0.66	
	P4406	12+12	0.50	
	P4407	15+15	0.40	

ABOUT THE NEW LAMINATES

I.L.P. LAMINATED
 I.L.P. printed-circuit mounted mains transformers have two independent primary windings which can be connected in series for 240V or parallel for 120V operation. The two independent secondaries can also be connected in series or parallel to give a wide range of output voltage/current configurations. All are wound on split bobbins, eliminating need for an inter-winding screen. Breakdown tested to 2000 VAC minimum.
 Regulation — 3VA typically 21%; 6VA typically 15%; 12VA typically 10%

GOODS DESPATCHED WITHIN 7 DAYS OF RECEIPT OF ORDER

FOR SINGLE AND SMALL QUANTITY ORDERS.

★ Now turn to our ads. on pages 88 and 89

- * CUSTOMER DESIGN ENQUIRIES INVITED. QUANTITY PRICE LIST AVAILABLE.
- * FREEPOST FACILITY (U.K. only). Simply send your order in envelope to FREEPOST to address below. NO STAMP REQUIRED.
- * TO ORDER Enclose cheque/Postal Order/Money Order payable to I.L.P. Electronics Ltd or quote your ACCESS or BARCLAYCARD account No. To pay C.O.D. add £1 extra to TOTAL value of order.
- * Also available from ELECTROVALUE and MARSHALLS.

LLP TRANSFORMERS (A DIVISION OF I.L.P. ELECTRONICS LTD)

FREEPOST 5, GRAHAM BELL HOUSE, ROPER CLOSE
 CANTERBURY CT2 7EP - Phone (0227) 54778 - Technical (0227) 64723 - Telex 965 780

WW - 055 FOR FURTHER DETAILS

BULK EPROM PROGRAMMING


2-YEAR WARRANTY



This unit provides simple, reliable programming of up to 8 EPROMS simultaneously. It has been designed for ease of operator use — a single "program" key starts the self check — blank check — program — verify sequence. Independent blank check & verify controls are provided along with mode, pass/fail indicators for each copy socket and a sounder to signal a correct key command & the end of a programming run. Any of the 2704/2708/2716 (3 rail) & 2508/2758/2516/2716/2532/2732 (single rail) EPROMS may be selected without hardware or personality card changes. PRICE £545 + VAT. Postage paid

BULK EPROM ERASING

EX-STOCK

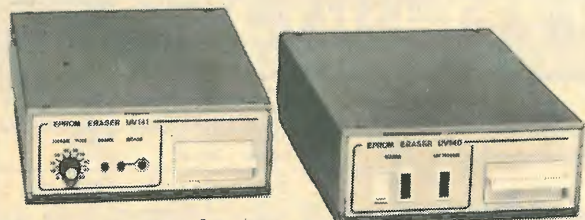

MODEL UV141 EPROM ERASER

- 14 EPROM capacity
- Fast erase time
- Built-in 5-50 minute timer
- Convenient slide-tray loading of devices
- Safety interlocked to prevent eye and skin damage
- Rugged construction
- MINS & ERASE indicators
- Price £78 + VAT postage paid.

MODEL UV140 EPROM ERASER

Similar to Model UV141 but without timer. Price £61.50 + VAT post paid

BULK EPROMS

EX-STOCK

	1-9	10-24	25-49	50-99	100 up
2716 (450ns) (single rail)	£5.00	£4.50	£4.00	£3.55	£2.95
2708 (450ns)	£3.90	£3.50	£3.10	£2.90	

Postage and Packing is included in all prices. ADD VAT at 15%. All our EPROMS are manufactured by leading companies and are fully guaranteed, branded and to full specification.

WRITE OR TELEPHONE FOR FURTHER DETAILS OR SEND OFFICIAL COMPANY ORDERS/CHEQUES TO:

Overseas customers, please telex or write for quotation and terms.

GP INDUSTRIAL ELECTRONICS LTD.

Unit 6, Burke Road, Totnes Industrial Estate, Totnes, Devon
Telephone: Totnes (0803) 863360 sales, 863380 technical
Telex: 42596
DISTRIBUTORS REQUIRED - EXPORT ENQUIRIES WELCOME

WW - 039 FOR FURTHER DETAILS

The new name in power operational amplifiers

Apex Microtechnology of Tucson Arizona, whose products are available through Pascall, offer a comprehensive range of hybrid power op amps with high input sensitivity and high voltage and current outputs.

High voltage—up to 280 volts output swing

PA 08 PA 08A — Fet input
PA 83 PA 83A — High accuracy

Applications Features

- High voltage instrumentation
- Programmable power supplies up to 300V
- Electrostatic deflection
- Test equipment
- Wide supply range - ±15V to ±150V
- Programmable output current limit up to 300V (PA08 only).
- Low bias current
- Protected output stage—Thermal shutoff
- Fully protected input - Up to ±150V (PA83 only)



Send for full product listings of Apex Microtech's exciting product range

Pascall Electronics Limited, Hawke House, Green Street, Sunbury-on-Thames, Middlesex TW16 6RA Telephone: (09327) 87418 Telex: 8814536

Def Stan 05-31 / BS9000 / CECC approved

WW - 065 FOR FURTHER DETAILS

reprints

If you are interested in a particular article/special Feature or advertisement published in this issue of

WIRELESS WORLD

why not take advantage of our reprint service.

Reprints can be secured at reasonable cost to your own specifications providing an attractive and valuable addition to your promotional material. (Minimum order 250.)

For further details contact Martin Bloomfield, IPC Electrical-Electronic Press Ltd. Phone 01-661 3036 or simply complete and return the form below.

To Martin Bloomfield, Reprints Department, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS

I am interested in copies of the article/advertisement headed featured in

WIRELESS WORLD

on page(s) in the issue dated

Please send me full details of your reprint service by return of post.

Name

Company

Address

Tel. No.

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

BSR DE LUXE AUTOCHANGER

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge. AC 200/250V. Size 13½-11¼in. 3 speeds. Above motor board 3¼in. Below motor board 2½in. with Ceramic Stereo cartridge.



£20 Post £2
Ready cut Mounting Board £1 extra

HEAVY METAL PLINTHS

Cut out for most BSR or Garrard decks. Silver grey finish. Size 16x13¼in. £4

WOOD PLINTH, TEAK EFFECT with board cut for B.S.R. (Post £1) £4

PIONEER and J.V.C. etc. TEAK VENEERED PLINTH 19 x 14¼in. with Plastic Cover 17¼ x 13in £10.50 Post £2

TINTED PLASTIC COVERS

Post £1.50
Inside sizes: 14½ x 12½ x 3in. £4. 18¼ x 12½ x 3in. £6. 18 x 13¼ x 4in. £6. 17¼ x 9½ x 3½in. £3.

BSR SINGLE PLAYER DECKS

BSR P200 2 speeds flared aluminium turntable. "S" shape arm, cueing device, Less cartridge £27 Belt Drive Post £2.
BSR P172 RIM DRIVE QUALITY DECK Manual or automatic play. Three speeds. Precision ultra slim arm. Cueing device. Bargain price £20 Post £2



BSR P207 BUDGET SINGLE PLAYER

ideal for disco or small two-speed Hi-Fi system with stereo cartridge and cueing device. £17 Post £2

GARRARD 6-200 SINGLE PLAYER DECK

Brushed Aluminium Arm with stereo ceramic cartridge and Diamond Stylus, 3-speeds. Manual and Auto Stop/Start. Large Metal Turntable. Cueing Device and Pause Control. Ready cut mounting board £1 extra. £22 Post £2

ELAC HI-FI SPEAKER

8in. TWIN CONE £5.95
Large ceramic magnet. 50-16,000 c/s. bass resonance 40 c/s. 8 ohm impedance, 10 watts



10in. TWIN CONE £7.95

Post 99p

POTENTIOMETERS Carbon Track

5kΩ to 2MΩ. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5k. SP 45p. Sliders Mono 85p. Stereo 85p.

EMI 13½ x 8in. LOUDSPEAKERS

With tweeter and With tweeter and crossover. crossover, 10 watt. 8 ohm. 15 watts, 3 or 8 ohm. £9.50 Post 99p
Bass woofer, EMI £10.95 Post 99p
15 ohm. 20 watt. £10.95 Post 99p
SUITABLE BOOKSHELF CABINET £10.50. Post £2

THE "INSTANT" BULK TAPE ERASER Suitable for cassettes, and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead. £8 Post 99p
Will also demagnetise small tools Head Demagnetiser only £5

RELAYS, 12V DC £1.25, 6V DC 95p, 18V £1.25, BLANK ALUMINIUM CHASSIS, 6 x 4-£1.20; 8 x 6-£1.50; 10 x 7-£1.90; 12 x 8-£2.20; 14 x 9-£2.50; 16 x 6-£2.40; 16 x 10-£2.70. All 2½in. deep. 18 swg. ANGLE ALL, 6 x 3¼ x 3¼in. 18 swg. 25p. ALUMINIUM PANELS, 18swg. 6 x 4-30p; 8 x 6-60p; 14 x 3-80p; 10 x 7-80p; 12 x 8-90p; 12 x 5-60p; 16 x 6-90p; 14 x 9-£1.20; 12 x 12-£1.30; 16 x 10-£1.40. PLASTIC AND ALL BOXES IN STOCK. MANY SIZES ALUMINIUM BOXES. 4 x 4 x 1½ £1. 4 x 2½ x 2 £1. 3 x 2 x 1.80p. 6 x 4 x 2 £1.30. 7 x 5 x 2½ £1.45. 8 x 6 x 3 £2.20. 10 x 7 x 3 £2.50. 12 x 5 x 3 £2.30. 12 x 8 x 3 £3. All 18swg. BRIDGE RECTIFIER 200V PIV 4amp £1.50. 8amp £2.50. TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p. RESISTORS, 100 to 10M, ¼W, ½W, 1W, 1p, 2W 10p. HIGH STABILITY, ¼w 2% 10 ohms to 1 meg. 8p. Ditto 5%. Preferred values, 10 ohms to 10 meg. 3p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 15p PICK-UP CARTRIDGES SONATONE 9TAHC £2.50. BSR Stereo Ceramic SC7 Medium £2. SC8 High £2. PHILIPS PLUG-IN HEAD. AU1020 (G306 - GP310 - GP233 - AG3306 - AG3310) £2. LOCKTITE SEALING KIT DECCA 118. Complete £1. SOLDERING IRON 240V 40W. 5mm bit £2.95.

CAR SPEAKERS on Baffles 7 x 4½ x 1½in. deep. 4 ohms. Twin Units Bass and Treble 10 watts, RMS. Door Mounting. Stereo pair £14. Complete with black/silver fronts.

IN-CAR GRAPHIC EQUALISER. Power Booster. Stereo 20 watts RMS per channel, 5 sliders Graphic Equalisation 5½ wide x 7½ deep x 2in. high. 12 volt D.C. suitable for Car Radio or Cassette £30. Post £1.50.

MINI-MULTI TESTER

Deluxe pocket size precision moving coil instrument. Impedance + Capacity — 2000 o.p.v. Battery included. 11 instant ranges measure: DC volts 10, 50, 250, 1000. AC volts 10, 50, 250, 1000. DC amps 0-100mA. Continuity and resistance to 1 meg ohms in two ranges. £6.50 Post 65p
De-Luxe Range Doubler Model, 50,000 o.p.v. £18.50. 7 x 5 x 2in. Post £1

PANEL METERS £4 each

50µa 100µa 500µa, 1ma, 5ma, 50ma, 100ma, 25 volt, 50 volt, VU Meter. Facia 2⅝ x 1¾ x 1½in. Fixing hole 1½in. dia. Lighting kit 6 or 12v 90p extra. 1ma (240° scale) 2¼in. sq. £5 Post 65p

RCS SOUND TO LIGHT CONTROL KIT

Kit of parts to build a 3 channel sound to light unit 1,000 watts per channel. Suitable for home or disco. £15 Post 95p
Easy to build. Full instructions supplied. Cabinet £4.50 extra. Will operate from 200MV to 100 watt signal. 200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights, Edison Screw, 6 for £4, or 12 for £7.50. Post 65p.

"MINOR" 10 watt AMPLIFIER KIT £14

This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. Post 65p. Specification 10W per channel; input 100mV; size 9½ x 3 x 2in. approx. SAE details. Full instructions supplied. AC mains powered. Input can be modified to suit guitar.

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp.

Inputs for high, medium or low imp per channel. with volume control and PC Board £2.95 Post 65p
Can be ganged to make multi-way stereo mixers

MAINS TRANSFORMERS

250-0-250V 70mA, 6.5V 2A	£4.50	Post £2
250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A	£5.00	£2
350-0-350V 250mA, 6.3V 4A, 4A CT, 5V 2A	£14.50	£2
300-0-300V 120mA, 2x6.3V 2A C.T.; 5V 2A	£10.00	£2
220V 45mA, 6.3V 2A	£2.50	£2

GENERAL PURPOSE LOW VOLTAGE

1amp. 3A, 5, 8, 9, 10, 12, 15, 18, 25 and 30V	£6.00	£2
2amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60	£8.00	£2
3amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60	£9.50	£2
5amp. 6, 8, 10, 12, 15, 18, 20, 24, 30, 36, 40, 48, 60	£12.50	£2
12v, 100mA	£1.30	80p
12v, 750mA	£2.00	80p
10-0-10V 2a	£3.00	£1
30v, 5a and 20v, 1a	£4.00	£2
0.5, 8, 10, 15V, 1/2a	£2.80	80p
9v, 3a	£3.50	£1
25-0-25V 2a	£4.50	£1
30v, 1 1/2a	£3.50	£1
6V, 1/2a	£2.00	£1
15-0-15V, 2a	£3.75	£1
12v, 3a	£3.50	£1
10v, 30v, 40v, 2a	£3.50	£1
2 of 28 volt 1a	£5.00	£2
20v, 1a	£3.00	£1
9-0-9V 50ma	£1.50	80p
2 of 18v, 6a	£11.00	£2
12-0-12V, 2a	£3.50	£1
9v, 1/2a	£1.50	80p
32-0-32V, 6½a	£11.00	£2

AUTO WOUND 115V to 240V 150W £8

400W £10 500W £12 £2

CHARGER TRANSFORMERS Post RECTIFIERS Post

6-12 volt 3a	£4.00+£2	6-12 volt 2a	£1.10+80p
6-12 volt 4a	£6.80+£2	6-12 volt 4a	£2.00+80p

OPUS COMPACT SPEAKERS

FLUTED WOOD FRONTS
TEAK VENEERED CABINET
11x8½x7½in. 4 or 5 to 14,000 cps. 15 watts 8 ohm
£20 pair Post £2

LOW VOLTAGE ELECTROLYTICS

ALL 100
1 mf, 2 mf, 4 mf, 8 mf, 10 mf, 25 mf, 30 mf, 50 mf, 100 mf, 250 mf. All 15 volts. 22 mf/6V/10v; 25 mf/6V/10v; 47 mf / 10v; 50 mf / 6v; 68 mf / 6v / 10v / 16v / 25v; 100 mf/10v; 150 mf/6V/10v; 200 mf/10v/16v; 220 mf/4V/10v/16v; 330 mf/4V/10v; 500 mf/6v; 680 mf/6V/10V/16V; 1000 mf/2.5V/4V/10V; 1500 mf/6V/10V/16V; 2200 mf/6V/10V; 3300 mf/6v; 4700 mf/4V. ALL 10p.

HIGH VOLTAGE ELECTROLYTICS

8/450V 45p 8+8/450V 75p 32+32+16/350V 90p
8/800V £1.20 8+16/450V 75p 100+100/275V 65p
16/350V 45p 20+20/450V 75p 150+200/275V 70p
32/500V 75p 32+32/350V 50p 220/450V 95p
32/350V 50p 32+32/500 £1.80 80+40/500V £2
50/500V £1.20 50+50/300V 50p

VALVE OUTPUT Transformers (small) 90p, TRIMMERS 10pF, 30pF, 50pF, 5p, 100pF, 150pF, 15p.

CAPACITORS Various 10pF to 100,000pF 5p.
PAPER 350V-0.1 7p; 0.5 13p; 1mF 150V 20p; 2mF 150V 20p;
500V-0.001 to 0.05 12p; 0.1 15p; 0.25 25p; 0.47 35p.
MICRO SWITCH SINGLE POLE CHANGEOVER 30p.
SUB-MIN MICRO SWITCH, 30p. Single pole changeover.
TWIN GANG, 120pF 50p; 500pF £1.
GEARED TWIN GANGS 25pF 95p, 365pF £1.
GEARED 365 + 365 + 25 + 25pF £1.
TRANSISTOR TWIN GANG, Japanese Replacement 50p.
NEON PANEL INDICATORS 250V 30p.
ILLUMINATED ROCKER SWITCH, Single pole. Red 65p.
CASSETTE MOTOR, 6 volt £1
CASSETTE MECHANISM, 12v Stereo Playback only £5
U.H.F. COAXIAL CABLE SUPER LOW LOSS, 25p yd.
COAX PLUGS 20p. COAX SOCKETS 20p.

BAKER LOUDSPEAKERS

"SALE PRICES"

MODEL	INCHES	OHMS	WATTS	TYPE	Post £2 ea. PRICE
MAJOR	12	4-8-16	30	HI-FI	£12
DELUXE MK II	12	8-16	15	HI-FI	£12
SUPERB	12	8-16	30	HI-FI	£20
AUDITORIUM	12	8-16	45	HI-FI	£20
AUDITORIUM	15	8-16	80	HI-FI	£34
GROUP 45	12	4-8-16	45	PA	£12
GROUP 75	12	4-8-16	75	PA	£20
GROUP 100	12	8-16	100	PA	£20
GROUP 100	15	8-16	100	PA	£28
DISCO 100	12	8-16	100	DISCO	£20
DISCO 100	15	8-16	100	DISCO	£28

BAKER 50 WATT AMPLIFIER

£69 Post £2
Ideal for Halls/PA systems, Discos and Groups. Two inputs. Mixer, Volume Controls, Master Bass, Treble and Gain. Special offer

BAKER 150 WATT MIXER/POWER AMPLIFIER

Post £2
Professional 4 inputs 4 volume controls. Will mix mics, decks, musical instruments, etc. £89

100 watts Mobile 24 volt DC & 240 volt AC mains. Input 3 mikes + 1 music. 4-8-16 ohm + 100 volt line £95 (PP £2).

FAMOUS LOUDSPEAKERS "SPECIAL PRICES"

MAKE	MODEL	SIZE	WATTS	OHMS	Post £2 ea. PRICE
SEAS	TWEETER	4in	50	8	£7.50
GOODMANS	TWEETER	3½in	25	8	£4.00
AUDIOAX	TWEETER	3¾in	60	8	£10.50
SEAS	MID-RANGE	4in	50	8	£7.50
SEAS	MID-RANGE	5in	80	8	£12.00
SEAS	MID-RANGE	4½in	100	8	£12.50
GOODMANS	FULL-RANGE	5½in	15	8	£6.50
GOODMANS	FULL-RANGE	8in	30	8	£9.50
GOODMANS	AUDIOM 8p	8in	15	15	£8.50
SEAS	WOOFER	8in	30	8	£14.00
CELESTION	DISCO	10in	20	8	£11.50
CELESTION	DISCO	10in	60	8/16	£21.50
RIGONDA	GENERAL	10in	15	8	£5.50
GOODMANS	AUDIOM PG	12in	60	8	£20.00
GOODMANS					

Superior Quality Precision Made NEW POWER RHEOSTATS

New ceramic construction, heavy duty brush assembly, continuously rated.

25 WATT 10/25 50 100/150/250/500/1k1 1.5kΩ £2.80. Post 30p (£3.56 inc. VAT & P).

100 WATT 1/5/10/25/50/100/250/300/500/1k1/1.5kΩ/2.5kΩ/5kΩ/7.5kΩ £6.90. Post 75p (£8.80 inc. VAT & P).

SOLID STATE E.H.T. UNIT Input 230V A.C. Fully isolated, approx. 15KV. Built-in 10 sec. timer.

Miniature SOLENOID FLUID VALVE 12V DC 150ohm coil normally closed.

METERS (New) - 90mm DIAMETER AC Amp. Type 62T2, 0-1A, 0-5A, 0-10A, 0-20A.

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES 4ft 40 watts £6.70.

SANGAMO WESTON TIME SWITCH Type S251 200/250 AC 2 on/2 off every 24 hours.

VEEDER-ROOT PRE-SET COUNTER Type MG 1636 3 fig. countdown any number from 999 to 001.

AC GEARED MOTORS DC MOTORS MICROSWITCHES RELAYS REED SWITCHES SOLENOIDS

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT 0-260V

200W 1 amp inc. a.c. voltage £14.50 0.5 KVA (2 1/2 amp MAX) £18.00 1 KVA (5 amp MAX) £24.00

3-PHASE VARIABLE VOLTAGE TRANSFORMERS Dual input 200-240V or 380-415V.

LT TRANSFORMERS

13.0 13V at 1 amp £2.80 P&P 75p (£4.08 inc VAT).

WATER PUMP Mfg. by S.P.A. Astairis of Italy. 220/240V AC 50 Hz. 2800 R.P.M.

HY-LIGHT STROBE KIT Mk IV Approx. 4 joules. Adjustable speed. Price £27 + £2 P&P.

INSULATION TESTERS (NEW) 500 VOLTS 500 megohms £49.00 P&P £2.00.

TIME SWITCH VENNER TYPE ERD Time switch 200-250V a.c. 30 amp contact 2 on/2 off.

SUB-MINIATURE PRECISION BUILT GEARED MOTOR 3-9v. D.C. Operation. Speed 2-6 R.P.M.

FROM STOCK AT PRICES THAT DEFY COMPETITION

SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB, 01-995 1560

TRANSFORMERS CONTINUOUS RATINGS

Table of transformer ratings for mains isolators, 12 or 24-volt, and 30 volt range (split sec).

50 VOLT RANGE Pri 220-240V. Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 25, 30, 33, 40 or 20V-0-20V and 25V-0-25V.

60 VOLT RANGE Pri 220-240V (Split Sec). Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V.

SCREENED MINIATURES Pri 240V. Ref. mA Sec Volts £ P&P

500 VOLTS 500 megohms £49.00 P&P £2.00

60 VOLTS RANGE Pri 220-240V (Split Sec). Voltages available 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60V.

MAINS ISOLATORS 400/440 to 200/240

CASED AUTOS 240V cable input USA 115V Flat pin outlets

CONSTANT VOLTAGE TRANSFORMERS ±1% For 'clean' mains to computers, peripherals.

SPLIT BOBBIN TRANSFORMERS Pri 0-115; x2 (70010). Sec voltages available: 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V.

OTHER PRODUCTS AVO TEST METERS Latest Model 8 Mk. 5 £116.40

AVO TEST METERS (continued) 71 Electronics £45.80 73 TV Service £63.90

BRIDGE RECTIFIERS 200v 2A 45p 400v 1A 25p 400v 2A 55p

TELEPHONES - Latest model 746, brand new, boxed, 2 tone grey £11.50, Ivory £12.50, PP £1.20 + VAT.

METAL OXIDE RESISTORS £1/100 Special Offer TR4 5% (100s only). Use in place of c.film.

3000v 2A £2.85 P&P 20p. VAT 15%

Barrie Electronics Ltd. 3, THE MINORIES, LONDON EC3N 1BJ TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & LIVERPOOL ST

MICRO TIMES

19 Mill Street, Bideford, North Devon, EX39 2JR Telephone Bideford (023-72) 79798 Dept. WWI

MEMORIES 2114 450ns 1+ 25+ £1.35 £1.30 4116 150ns £1.45 £1.40 HM 6116P-3 (16k 150ns) £15.50 £15.25

6809 Single Board Computer ★kit★ Complete kit £160 plus 15% V.A.T. £1 P. & P.

THYRISTORS C106D 28p

LINEAR ICs NE555 18p NE556 50p RC4136 65p

CPU's 6502 £5.45 6504 £7.25 6802 £5.85 6809 £15.00

JUST ARRIVED FROM VERO S100 Prototyping Boards

FLOPPY DISC CONTROLLERS FD1771 £19.50

COMBO CHIPS Intended for Z80 Usage

ENCODER/TRANSMITTER LM1871 £1.90

RECEIVER/DECODER LM1872 £1.90

VOLTAGE REGULATORS 7805 5V 55p 7812 12V 55p


ULTRONIC FLY REPELLER A must for campers

ELECTRONIC WHEEL OF FORTUNE Fun Kit Easy to assemble. Case included. Wonderful game. £5

ORDERING INFORMATION Please add 50p P. & P. Plus 15% V.A.T. to all orders.

PRINTED CIRCUITS FOR WIRELESS WORLD PROJECTS

Table of printed circuit projects: Stripline r.f. power amp—Sept. 1975—1 d.s. £5.00, Audio compressor/limiter—Dec. 1975—1 s.s. (stereo) £4.25, etc.

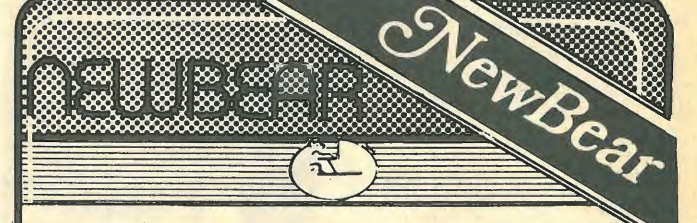

SEND/PHONE FOR EXTENSIVE special offer LISTS 74LS, 6800, 6502, Z80, 6809 CONNECTORS, CRYSTALS, SWITCHES, DISK DRIVES, MEMORIES "LOW PRICES" Fast Delivery

NEW! Thurlby 1503 high resolution multimeter £139

Greater resolution, greater accuracy, and greater versatility + VAT

- 4½ digits (±32,768 counts)
- 10uV, 10mΩ, 1nA resolution
- 0.05% basic DCV accuracy
- LCD, fully field portable
- 7 functions including Frequency
- Outstanding price/performance ratio



available ex-stock.

Full data and distributor list from **Thurlby Electronics Ltd.**
Coach Mews, St. Ives, Huntingdon, Cambs.
PE17 4BN. ENGLAND. Tel: (0480) 63570

WW-062 FOR FURTHER DETAILS

SWITCHCRAFT XLR CONNECTORS

Line Female A3F	£1.07	Chassis Female D3F	£1.34
Line Male A3M	£0.93	Chassis Male D3M	£0.77

4, 5 and 6 pin versions and large selection audio adaptors available

NEUTRIK XLR CONNECTORS

Latchless Chassis NC3-FZ	£0.67	Latchless Chassis Male NC3-MZ	£0.59
Line Female NC3-SC	£1.34	Line Male NC3-MC	£1.15
Female Chassis NC3-FP	£1.65	Chassis Male NC3-MP	£0.87

4, 5 and 6 pin versions and large selection of Audio Audio Adaptors available

XLR LINE MAIN SERIES

XLR LNE 11C	£3.87	XLR LNE 12C	£3.76
XLR LNE 32	£2.89	XLR LNE 31	£4.14

BELCLERE AUDIO TRANSFORMERS

EN6422 Ratio 1 + 1.2 + 2. Freq. 40Hz-35KHz. PRI 150/600Ω, sec. 600/2 4KΩ. £3.64
EN6423 Ratio 1 + 1.6:45 + 6:45. Freq. 40Hz-25KHz. PRI 150/600Ω, sec. 6.25K/25KΩ. £3.64
SKT-723 MuMetal Screening can, 38dB reduction 50Hz ext. field. £1.05

Trade enquiries welcome; quantity discounts available. All prices subject to V.A.T. Call, write or phone. Min. order £10. Please add £1 postage. Access, Amex, Barclaycard.

KELSEY ACOUSTICS LTD.


28 POWIS TERRACE, LONDON W11 1JH
01-727 1046

WW - 023 FOR FURTHER DETAILS

Wirewound Ceramic Resistors

Axial or vertical mounting
5w-17w OR5-39K
from £9.35 per 100

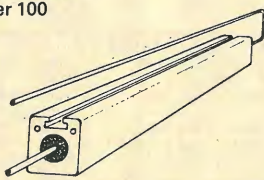QUICK ACTING & ANTI SURGE CARTRIDGE FUSES
from £3.15 per 100.



Cable Sleeves and Markers from £1.38 per 1,000.
Crimp Terminals from £9.60 per 1,000.
Audible Warning Devices. Buzztone, Bleepstone, Banshee, Bedlam, etc. from £1.14 each.
Self-adhesive Pcb guides from £5.04 per 100.

PBRA LTD.

Golden Green, Tonbridge
Kent TN11 0LH
Hopfield (073274) 345
Member Crystalate Group

WW-068 FOR FURTHER DETAILS

Cotswold Electronics Toroidal Power Transformers

Budget range for the amateur and professional



Type	VA	Secondary		Dimensions		Weight Kg	Price
		Volts RMS	Current RMS	Dia.	Height		
C1000	30	6+6	2.50	70mm	30mm	0.45	
C1001	30	9+9	1.67	70mm	30mm	0.45	£4.55
C1002	30	12+12	1.25	70mm	30mm	0.45	
C1003	30	15+15	1.00	70mm	30mm	0.45	(+£1.10 p.p.)
C1004	30	18+18	0.83	70mm	30mm	0.45	+ 0.84 VAT)
C1005	30	22+22	0.68	70mm	30mm	0.45	
C1006	30	25+25	0.60	70mm	30mm	0.45	
C1007	30	30+30	0.50	70mm	30mm	0.45	

C1010	60	9+9	3.33	87mm	33mm	0.75	
C1011	60	12+12	2.50	87mm	33mm	0.75	£4.86
C1012	60	15+15	2.00	87mm	33mm	0.75	
C1013	60	18+18	1.67	87mm	33mm	0.75	(+£1.43 p.p.)
C1014	60	22+22	1.36	87mm	33mm	0.75	+ 0.94 VAT)
C1015	60	25+25	1.20	87mm	33mm	0.75	
C1016	60	30+30	1.00	87mm	33mm	0.75	
C1017	60	110	0.55	87mm	33mm	0.75	
C1018	60	220	0.27	87mm	33mm	0.75	
C1019	60	240	0.25	87mm	33mm	0.75	

C1020	100	12+12	4.17	88mm	40mm	1.00	
C1021	100	15+15	3.33	88mm	40mm	1.00	£5.70
C1022	100	18+18	2.78	88mm	40mm	1.00	
C1023	100	22+22	2.27	88mm	40mm	1.00	(+£1.43 p.p.)
C1024	100	25+25	2.00	88mm	40mm	1.00	+ £1.07 VAT)
C1025	100	30+30	1.67	88mm	40mm	1.00	
C1026	100	110	0.91	88mm	40mm	1.00	
C1027	100	220	0.45	88mm	40mm	1.00	
C1028	100	240	0.42	88mm	40mm	1.00	

Type	VA	Secondary		Dimensions		Weight Kg	Price
		Volts RMS	Current RMS	Dia.	Height		
C1030	160	18+18	4.44	108mm	42mm	1.5	
C1031	160	22+22	3.64	108mm	42mm	1.5	£8.40
C1032	160	25+25	3.20	108mm	42mm	1.5	
C1033	160	30+30	2.67	108mm	42mm	1.5	(+ £1.73 p.p.)
C1034	160	35+35	2.29	108mm	42mm	1.5	+ £1.52 VAT)
C1035	160	110	1.46	108mm	42mm	1.5	
C1036	160	220	0.73	108mm	42mm	1.5	
C1037	160	240	0.67	108mm	42mm	1.5	

C1040	230	25+25	4.60	115mm	50mm	2.2	
C1041	230	30+30	3.83	115mm	50mm	2.2	£10.20
C1042	230	35+35	3.29	115mm	50mm	2.2	
C1043	230	40+40	2.88	115mm	50mm	2.2	(+ £1.73 p.p.)
C1044	230	110	2.09	115mm	50mm	2.2	+ £1.79 VAT)
C1045	230	220	1.05	115mm	50mm	2.2	
C1046	230	240	0.96	115mm	50mm	2.2	

C1050	330	25+25	6.60	130mm	52mm	2.8	
C1051	330	30+30	5.50	130mm	52mm	2.8	£11.90
C1052	330	35+35	4.71	130mm	52mm	2.8	
C1053	330	40+40	4.13	130mm	52mm	2.8	(+ £1.90 p.p.)
C1054	330	45+45	3.67	130mm	52mm	2.8	+ £2.07 VAT)
C1055	330	110	3.00	130mm	52mm	2.8	
C1056	330	220	1.50	130mm	52mm	2.8	
C1057	330	240	1.38	130mm	52mm	2.8	

C1060	530	30+30	8.83	145mm	60mm	3.8	
C1061	530	35+35	7.57	145mm	60mm	3.8	£15.80
C1062	530	40+40	6.63	145mm	60mm	3.8	
C1063	530	45+45	5.89	145mm	60mm	3.8	(+ £2.05 p.p.)
C1064	530	50+50	5.30	145mm	60mm	3.8	+ £2.68 VAT)
C1065	530	110	4.82	145mm	60mm	3.8	
C1066	530	220	2.41	145mm	60mm	3.8	
C1067	530	240	2.21	145mm	60mm	3.8	

NOTE: All types normally supplied with 240 V primary 110 V, 220 V or other voltage supplied on request.

24 hour answering service: You may telephone your order throughout 24 hours quoting your Access or Barclaycard number. Phone number 0242-41313.

Cotswold Electronics Ltd Cheltenham GL51 9NX

Type	Mains Voltage	Secondary Volts	VA	Qty

FREEPOST(UK) only: We pay postage on all enquiries and orders. Address your envelope: Dept W Cotswold Electronics Ltd, FREEPOST, Cheltenham Glos. GL51 1BR (No stamp required)

I enclose Cheque P.D. Money Order

Access/Barclaycard No. []

Name []

Address []

Postal Code []

Telephone No. []

WW - 016 FOR FURTHER DETAILS

LOW VOLTAGE POWER DRILLS AND ACCESSORIES

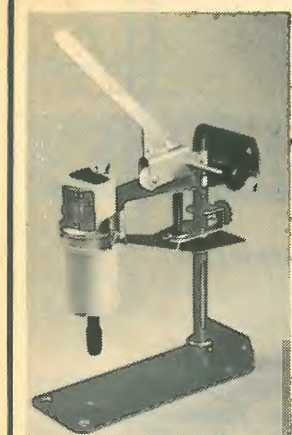


Illustration shows Titan Drill and Stand. (Price £27 inc. VAT and Postage) which is One of the combinations which can be purchased from our comprehensive range of Drills and Accessories.
Prices from £8.34 (Reliant Drill only) inc. VAT and Postage.
Send 25p for Catalogue.

A. D. BAYLISS & SON LTD.

PFERA WORKS, REDMARLEY
GLOUCESTER GL19 3JU
Barclaycard, Access Welcome

Tel. Bromesberrow (053 181) 273

Stockists: Richards Electric, Gloucester
D & D Models, Hereford
Hoopers of Ledbury
Hobbs of Ledbury

CHERRY E61

sub-miniature micro switches. 5 amp, 250 volt no/nc, 100 pcs, £15; 500 pcs £67.50; 1,000 pcs £125; 5,000 pcs £550; 10,000 pcs £1,000

GRAMPIAN h/duty telescopic p/a speaker stands, £60 ea.; 5 for £287.50; 10 for £550; 50 for £2,500.

GRAMPIAN 100 watt, cast all, finned heatsinks, drilled to take five, T0.3 driver devices, £7.50 ea.; 5 for £35; 10 for £65; 50 for £300; 100 for £550. Size L292, W153, D32. Weight 4lb. 1oz. approx.

RECORD LEVEL METERS, EDGE TYPE. W35, H21, D32. Resistance 500Ω, £1.50 ea.; 10 for £14; 100 for £125; 500 for £550; 1,000 for £950.

COMPUTER GRADE ALUMINIUM ELECTROLYTIC. 7500 µf + 7500µf 25 volt - 10 + 50%. H80, D40 £1.25 ea.; 10 for £12; 100 for £110; 500 for £500; 1,000 for £900; 2,000 for £1,700.

MINIATURE TOGGLES. 6A 125v. a.c. D.P.D.T. with centre "off" position, £1 ea.; 10 for £9; 50 for £42.50; 100 for £80; 500 for £350.

100V. LINE TRANSFORMERS. Tapped 0.5-1.3 watts into 16 Ω speaker fitted with 6-way terminal block for easy connections, £2.50 ea.; 10 for £24; 50 for £112.50; 100 for £220; 500 for £1,050; 1,000 for £2,000.

Terms c.w.o. Add 5% to all orders for p. and p. + 15% V.A.T. Export enquiries welcome.

ELECTRONIC EQUIPMENT CO.

Syngfield House
Tyssen Street, London E8 2ND
Telephone: 01-249 5217
Telex: 8953906 EECO.G

Are you having problems in obtaining components at the right prices? If so let us have your enquiry. We probably have it in stock.

WW - 073 FOR FURTHER DETAILS

CHILTERN ELECTRONICS

BCM BOX 8085, LONDON WC1N 3XX. TEL. 0494 714483

VIDEO MONITOR BARGAIN

Due to bulk surplus purchase, we are able to offer these professional video monitors brand new in original boxes at a fraction of their original cost.

- ★ 12-inch screen, green phosphor with anti-glare shield.
- ★ Ideal for graphics or alphanumeric display.
- ★ Standard composite video in, 240 volt operation.
- ★ Extremely attractive anodised aluminium case.
- ★ Auxiliary Power Supply for keyboard.
- ★ Resolution better than 600 lines.
- ★ Ideal for home use - just plug into your micro system.
- ★ As used by many large mainframe computers.

We believe these are the finest monitors available anywhere at any price. Full data and cables included. Only £75. Please phone for cost of carriage.

ASCII KEYBOARDS

Top quality 84-key ASCII keyboards, with numeric and control key clusters. Brand new, but may have minor scratches and no circuit, so only £15. Postage £2.

TELETYPES

The famous model 33 Teletypes, ASCII coding with 20mA loop interface, in good working order, now available at these very low prices. As sold elsewhere for up to £500.
KSR Model 33 £65. ASR Model 33 £120 with pedestal.

DEC PDP8 COMPUTERS

PDP8E. Latest version with TTY and DMA cards, fully overhauled. £450. Complete with 8K Core expandable up to 32K.
PDP8L. Earlier version of above, with TTY interface. Only £120.

ICL TERMIPRINTERS

Letter quality silent printing terminals, ideal for word processors. Upper and lower case ASCII, RS232 interface. 30 ch/sec. New £250. Used from £100.

CENTRONICS LINE PRINTERS

(Model 101A)

The heavy duty professional line printers, 165 ch/sec. Only £250.

DISKS & MAGTAPES

Diablo/DRI Series 30 2.5 MByte Cartridge drives available ex-stock. Fully overhauled. Exchangeable £500. Fixed cartridge £425.
Fixed 5 MByte disk with controller for 8080 system £350.
PERTEC Industry Standard Magnetic Tape Drives: 7 Track £120. 9 Track £450.
We stock a large amount of DEC equipment, please telephone for details. All equipment may be viewed at our office near High Wycombe.
Prices exclude VAT, heavy items must be collected.

WW-066 FOR FURTHER DETAILS

Children know more about computers than their parents. True or False?

Well, true enough for Practical Computing to propose a twinning scheme for schools and businesses, bringing pupil brainpower to bear on business problems. Read all about it in the July issue.

Also in this issue of Practical Computing:
Reviews of Explorer 85, a modular system which can be built up from a single board to a full disc configuration. And Gemini - a large capacity business system.
Prokit - a package of subroutines to ease data entry on the Pet.

How a freight forwarding company started with an Apple but ended up with an IBM mini.
Business software - first of a four-part series on how to write your own.
Education. How to write a Pet program to provide a framework for multiple choice tests.

All this plus the usual Apple, Tandy, Pet and ZX80 advice pages in the July issue of Practical Computing.
Price 80p. At your newsagent or complete the coupon:

To Marketing Department, IPC Electrical-Electronic Press, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Please send me Practical Computing for one year. I enclose Cheque/P.O. for £10 (U.K.)/£16 (overseas) made payable to IPC Business Press Ltd.

Name []

Address []

40 years

DANAVOX

DANAVOX (GT. BRITAIN) LTD.
1 CHEYNE WALK,
NORTHAMPTON NN15PT
TEL. NORTHAMPTON (0604) 36351

of research... "on components and accessories for dictating machines, tele-communications, hearing aids and electroacoustic equipment etc."




STETOCLIP JUNIOR 60 HEADSET




STETOCLIP LIGHT WEIGHT HEADSET




SENIOR STETOCLIP HEADSET

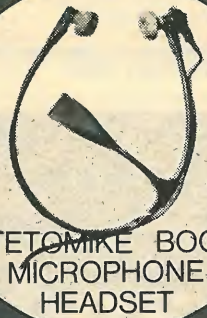

STETOMIKE BOOM MICROPHONE HEADSET

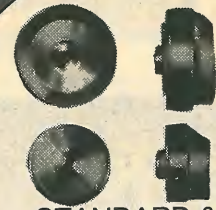

STANDARD & SUB-MINOR EARPHONES

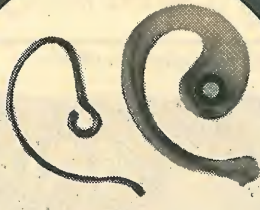


PLASTIC EARHANGERS



DANAMIC FIDELITY EARSET



STETOTUBE HEADSET

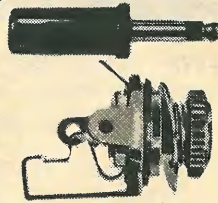


2.5 mm and 3.5 mm JACK PLUGS & SOCKETS



DANASOUND HEADSET



DANASONIC INDUCTION AUDIO LOOP RECEIVER

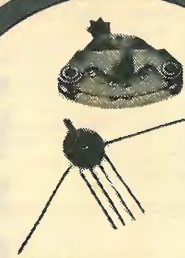

SUBMINIATURE SWITCHES

WW-079 FOR FURTHER DETAILS

Memories	Price
2114L-300ns	£2.10
4116-200ns	£1.89
2708-450ns	£3.15
2716-450ns	£4.99

74LS series	Price
74LS240	£1.54
74LS243	£1.54
74LS244	£1.54
74LS245	£1.70

Bridge Rectifiers	Price
25 Amp 50 volt	£0.74
25 Amp 100 volt	£0.94
25 Amp 200 volt	£1.26
25 Amp 400 volt	£1.68
25 Amp 600 volt	£2.10
25 Amp 800 volt	£2.63

Please add 50 pence for carriage.
All prices EXCLUDE VAT
Please send s.a.e. for price list.

STRUTT LTD.
ELECTRONIC COMPONENT DISTRIBUTORS
ETC.
3c BARLEY MARKET STREET, TAVISTOCK
DEVON, ENGLAND PL19 0JF
Tel. Tavistock (0822) 5439/5548. Telex: 45263

WW-038 FOR FURTHER DETAILS

SCOOP ONLY £29.95 +VAT

Professional ASCII Keyboards

The 'CHERRY' Computer Keyboard



BRITISH MADE
52 KEY 7 BIT ASCII CODED
POSITIVE STROBE
+5V - 12V
FULL ASCII CHARACTERS
PARALLEL OUTPUT WITH STROBE
POWER LIGHT ON CONTROL

CHIP BY GENERAL INSTRUMENT (G.I.)
TTL OUTPUT
SUPERBLY MADE SIZE 13 x 5.5 x 1.5 ins.
BLACK KEYS WITH WHITE LEDGENS

ESCAPE. SHIFT. RETURN & RESET KEYS
CONTROL REPEAT & BELL
Complete with DATA

Ideal for use with TANGERINE, TRITON, TUSCAN, APPLE and most computers. Ex-Stock from HENRY'S
This is definitely the BEST BUY. FULLY GUARANTEED. Supplied BRAND NEW in manufacturers original packing. Just post remittance total £35.95 (incl. V.A.T. & Post)

The 'Apple' Power Supply Suitable for use with most computers

A PROFESSIONAL BUILT & TESTED, CASED & VENTILATED POWER UNIT WITH BUILT IN OVERLOAD & CUT OUT PROTECTION CIRCUITS

Specifications
Input voltage: 210-250v
Supply voltages: +5.0, +11.8, -12.0, -5.2
Power consumption: 60 watts max. (full load)
Full load power output: +5v: 2.5 amp; -5v: 250ma; +12v: 1.5 amp; -12v: 250ma
Size: 10" x 3 3/4" x 2 1/2"
Weight: (Approx.) 3 lbs

Complete with full data & information - Supplied brand new

The Apple Power Supply is a high-voltage 'switching' power supply. While most other power supplies use a large transformer with many windings to convert the input voltage into many lesser voltages and then rectify and regulate these lesser voltages, the Apple Power Supply first converts the AC line voltage into a DC voltage, and then uses this DC voltage to drive a high-frequency oscillator. The output of this oscillator is fed into a small transformer with many windings. The voltages on the secondary windings are then regulated.

PREVENTS DAMAGE & RETURNS UNIT TO NORMAL WORKING CONDITIONS



LIST PRICE £60
OUR PRICE £32.50 +VAT
Just post remittance £39.50 (includes VAT, post & packing) on delivery by return.

'Cherry' Add-on Keypad


A COMPACT 12 BUTTON KEYPAD SUITABLE FOR USE WITH CHERRY KEYBOARD TO EXTEND ITS FUNCTIONS PLUS FOUR EXTRA KEYS.
SUPPLIED BRAND NEW WITH DATA
A 3 x 4 non-encoded single node keyboard in sloped format

LIST PRICE £22.00
OUR PRICE £10.95 PLUS VAT



HENRY'S COMPERKIT DIVISION
404 Edgware Road, London, W2, England
Telephone: 01-402 6822
Telex: 262284 Mono Transonics

Has it with Access VISA

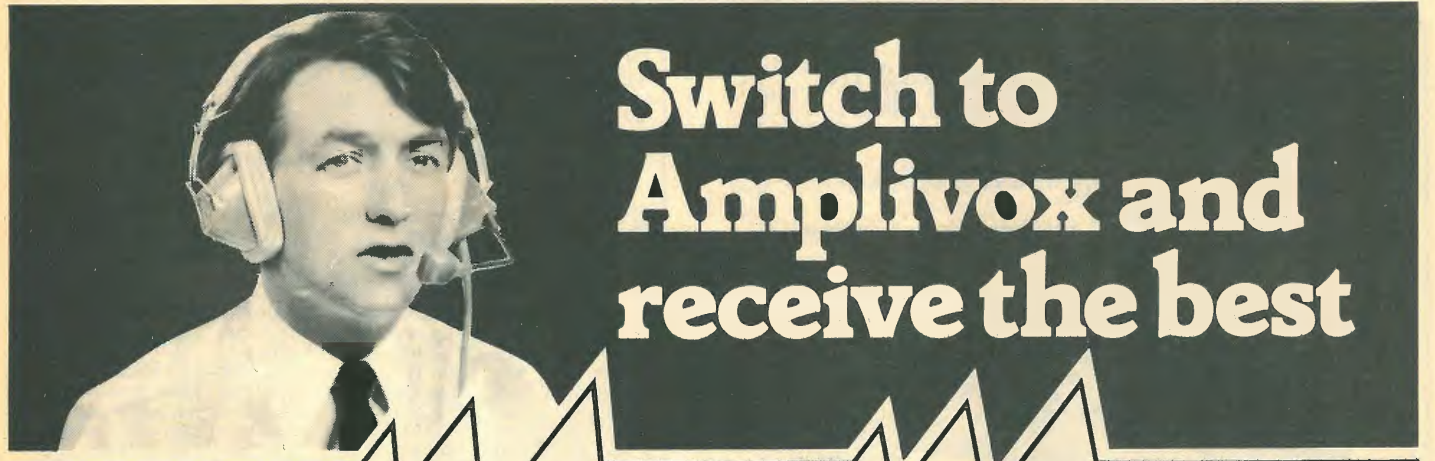


Switch to Amplivox and receive the best

The advanced design of the 410 Headset has placed the product far ahead in the world of radio communications. Its light weight, low ear pressure and trim design make the headset ideal where long periods of continued use are required. A pliable sliding headpad reduces head-pressure to an absolute minimum and as the earpads are constructed of non-hardening tropicalised material they give an excellent low pressure seal as well as providing optimum comfort whilst in use. The headband is constructed of nylon covered stainless steel spring wire and will prevent any form of wire snagging and also carries the receiver signal. Tinsel wiring has been incorporated to give extended electrical life under high vibration movements. Special features can usually be incorporated to meet specific requirements.

The first name in Audiometric Equipment.
Amplivox Limited
Amplivox Limited, 13A Station Field Ind. Est., Kidlington, Oxford, England OX5 1LJ.

Model 410 Specifications

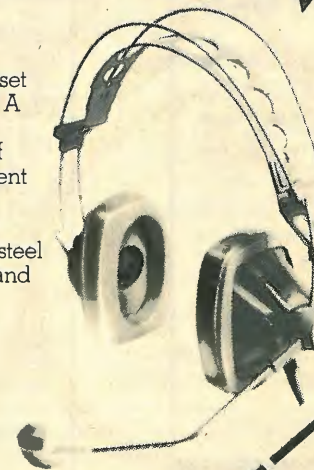- Receive IMP 400 OHMS
- Microphone Imp 200 OHMS
- Mic Sensitivity at 800Hz in respect to 80dB Input - 30dB
- Weight 350 grams



Please send me details of the Amplivox 410 Headset

Name _____
Company _____
Address _____

Amplivox Limited
13A Station Field Ind. Est.
Kidlington OXFORD
OX5 1LJ.

WW-071 FOR FURTHER DETAILS


RUBBER DUCK TO LOGI BAIRD-SAY GOOD BUDDY, WHERE DO I GET TRANSISTORS AND I.C.'s FOR C.B. AND R.F. APPLICATIONS?

'ANGLIA' OF COURSE !! THEY ARE THE UK'S LEADING SUPPLIER OF MOTOROLA & JAPANESE TYPES!

ANGLIA COMPONENTS
 BURDETT ROAD, WISBECH
 CAMBS PE13 2PS
 TEL : 0945 63281
 TELEX 32630

Anglia is a franchised distributor with a wide product range. Our catalogue is available to all professional users

MEASURE UP TO YOUR NEEDS WITH GROTECH

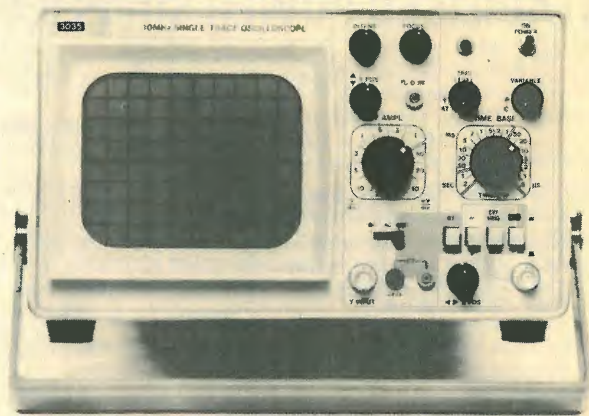


TYPE 3035

DC-10MHz Bandwidth
 5mV/div sensitivity
 200ns/div to 0.2s/div timebase
 Triggering to 20MHz
 5" Bright CRT

Triggered and automatic sweep
 Regulated internal supplies
 10 x 8 div display
BUILT-IN COMPONENT TESTER £165*

If your need falls between 10MHz and 30MHz then we can measure up to it, including battery operated models. Every scope in the range is designed to meet our basic design philosophy of building in that extra benefit. The 3035 has a full 10MHz scope specification, plus a Component Tester which displays the characteristics of both active and passive components. While the 3337 is a complete 30MHz instrument with signal delay, plus a 10KV CRT for a bright display normally reserved for much wider bandwidth scopes.

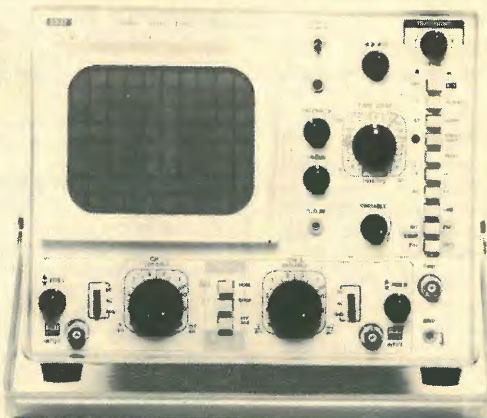

TYPE 3337 *U.K. LIST EXC VAT

DC-30MHz Bandwidth
 11.7ns Risetime
 5mV/div sensitivity
 Signal Delay
 Algebraic addition and subtraction

Full X-Y operation
 Triggering to 50MHz
 Composite trigger mode
 40ns/div - 1s/div Sweep speeds
 C.R.T. 10KV PDA
£355*

For your copy of the Grotech catalogue just telephone Reading (0734) 866945

Grotech Instruments Limited
 5 Nimrod Way, Elgar Road, Reading, Berks. RG2 0EB.

To obtain further details of any of the coded items mentioned in the Editorial or Advertisement pages of this issue, please complete one or more of the attached cards entering the reference number(s). Your enquiries will be passed on to the manufacturers concerned and you can expect to hear from them direct in due course. Cards posted from abroad require a stamp. These Service Cards are valid for six months from the date of publication.

Please Use Capital Letters

If you are way down on the circulation list, you may not be getting the information you require from the journal as soon as you should. Why not have your own copy?

To start a one year's subscription you may apply direct to us by using the card at the bottom of this page. You may also apply to the agent nearest to you, their address is shown below.

OVERSEAS SUBSCRIPTION AGENTS

- Australia:** Gordon & Gotch (Australasia) Ltd, 380 Lonsdale Street, Melbourne 3000, Victoria
- Belgium:** Agence et Messageries de la Presse, 1 Rue de la Petite-ILE Brussels 7
- Canada:** Davis Circulation Agency, 153 St. Clair Avenue West, Toronto 195, Ontario
- Cyprus:** General Press Agency Ltd, 131 Prodromou Street, P.O. Box 4528, Nicosia
- Denmark:** Dansk Bladdistribution, Hovedvagtsgade 8, Dk. 1103 Kobenhavn.
- Finland:** Reutakirja OY, Koivuvaarankuja 2, 01640 Vantaa 64, Finland.
- France:** Dawson-France S.A., B.P.40, F-91121, Palaiseau
- Germany:** W. E. Saarbach GmbH, 5 Koln 1, Follenstrasse 2
- Greece:** Hellenic Distribution Agency, P.O. Box 315, 245 Syngrou Avenue, Nea Smyrni, Greece.
- Holland:** Van Diltmar N.V., Oostelijke Handelskade 11, Amsterdam 1004
- India:** International Book House, Indian Mercantile Mansion Ext, Madame Cama Road, Bombay 1
- Iran:** A.D.A., 151 Khaban Soraya, Tehran
- Israel:** Stelmatsky's Agency Ltd, Citrus House, P.O. Box 628, Tel Aviv
- Italy:** Intercontinental s.a.s. Via Veracini 9, 20124 Milano
- Japan:** Western Publications Distribution Agency, 170 Nishi-Okubo 4-chome, Shinjuku-Ku, Tokyo 160
- Lebanon:** Levant Distributors Co., P.O. Box 1181, Makdesi Street, Halim Hanna Bldg, Beirut
- Malaysia:** Times Distributors Sdn. Bhd., Times House, 390 Kim Seng Road, Singapore 9, Malaysia.
- Malta:** W. H. Smith Continental Ltd, 18a Scots Street, Valletta
- New Zealand:** Gordon & Gotch (New Zealand) Ltd, 102 Adelaide Road, Wellington 2
- Nigeria:** Daily Times of Nigeria Ltd, 3 Kakawa Street, P.O. Box 139, Lagos
- Norway:** A/S Narvesens Kioskparti, Bertrand Narvesens vei 2, Oslo 6
- Portugal:** Livaria Bertrand s.a.r.l Apartado 37, Amadora
- South Africa:** Central News Agency Ltd, P.O. Box 1033, Johannesburg
- Spain:** Comercial Athenum s.e. Consejo de Ciento, 130-136 Barcelona 15
- Sweden:** Wennegren Williams A.B. Fack S-104, 25 Stockholm 30
- Switzerland:** Naville & Cie SA, Rue Levrier 5-7, CH-1211 Geneve 1
- U.S.A.:** John Barrios, IPC Business Press, 205 East 42nd Street, New York, N.Y. 10017

Postage will be paid by Licensee

Do not affix Postage Stamps if posted in Gt Britain, Channel Islands, N Ireland or the Isle of Man

BUSINESS REPLY SERVICE
 Licence No 12045

WIRELESS WORLD
 Reader Enquiry Service
 429 Brighton Road
 South Croydon
 Surrey CR2 9PS

Enquiry Service for Professional Readers

WIRELESS WORLD Wireless World, July 1981 WW 167

Please arrange for me to receive further details of the products listed, the appropriate reference numbers of which have been entered in the space provided.

WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW

Name

Name of Company

Address

Telephone Number

PUBLISHERS USE ONLY		A/E		
---------------------	--	-----	--	--

Position in Company

Nature of Company/Business

No. of employees at this establishment

I wish to subscribe to Wireless World

VALID FOR SIX MONTHS ONLY

Wireless World: Subscription Order Form

To become a subscriber to Wireless World please complete the reverse side of this form and return it with your remittance to:

**Subscription Manager,
 IPC Business Press,
 Oakfield House, Perrymount Road,
 Haywards Heath, Sussex RH16 3DH,
 England**

It's easy to complain about advertisements.

The Advertising Standards Authority. If an advertisement is wrong, we're here to put it right.

ASA Ltd., Brook House, Torrington Place, London WC1E 7HN.

Please arrange for me to receive further details of the products listed, the appropriate reference numbers of which have been entered in the space provided.

Name

Position in Company

Name of Company

Address

Telephone Number

Nature of Company/Business

No. of employees at this establishment

VALID FOR SIX MONTHS ONLY

CUT HERE

Postage will be paid by Licensee

Do not affix Postage Stamps if posted in Gt Britain, Channel Islands, N Ireland or the Isle of Man

BUSINESS REPLY SERVICE
Licence No 12045

WIRELESS WORLD
Reader Enquiry Service
429 Brighton Road
South Croydon
Surrey CR2 9PS

CUT HERE

Wireless World Subscription Order Form Wireless World, July 1981 WW 167


UK subscription rates	USA & Canada subscription rates
1 year: £10.00	1 year: \$33.80
Overseas 1 year: £13.00	

Please enter my subscription to Wireless World for 1 year


I enclose remittance value made payable to **IPC BUSINESS PRESS Ltd.**

Name

Address

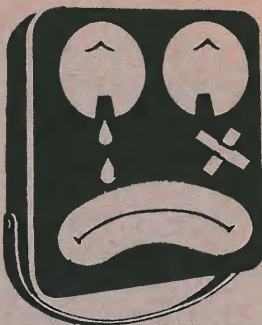

BEFORE

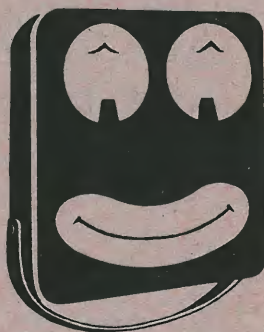

AFTER!

PUT A SMILE BACK ON
YOUR OLD AVOMETER!

Send it now for estimate,
repair or recalibration

Quick turn round
on estimates/repairs

Large stocks of new
AVOMETERS

Avo Sales and Service




Farnell International Instruments Ltd.,
Sandbeck Way, Wetherby
West Yorkshire LS22 4DH

Tel 0937 63541 Telex 557294 Farist G

WW-004 FOR FURTHER DETAILS

The New Scopex 14D-10

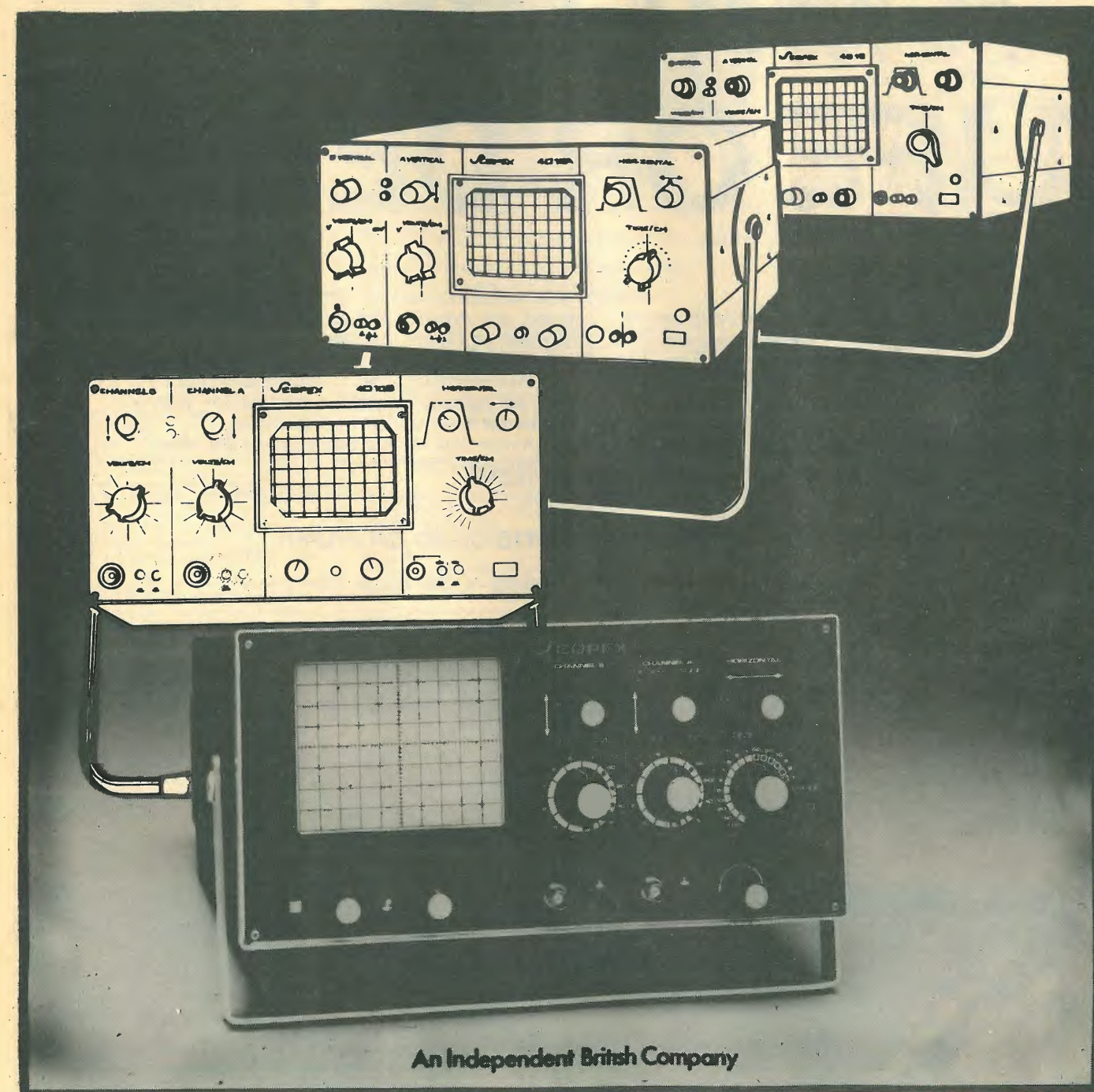


An Independent British Company

A dual trace 10MHz high sensitivity oscilloscope incorporating all the latest high technology developments to bring you all these outstanding features as standard. At a price of £240.00 + VAT. Ensures British leadership in the low cost high performance oscilloscope market. Distributors required in certain countries

- 10cm x 8cm display.
- 2mV sensitivity on both channels.
- Add and invert facility.
- Probe compensation.
- Push button X-Y.
- Trace locate.
- 10MHZ (-3dB) over full display.
- Complete with probes.



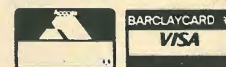Pixmore Avenue, Letchworth,
Herts SG6 1JJ. Tel: (04626) 72771.



I wish to pay by Barclaycard/Trust Card.
Please charge to my account.
My Barclaycard/Trust Card No. is

Please send me full details of the 14D10.

Name

Company

Address

Tel:

WW - 028 FOR FURTHER DETAILS

A MATTER OF LIFE OR DEATH

When an accident occurs involving severe electric shock, people on the spot may be suffering from a kind of shock themselves. The realisation that one has literally only seconds to save a life can itself be momentarily paralysing. That's why *Electrical Review* has completely re-styled its *Electrical Shock Chart*. The new chart, prepared in consultation with St. John's Ambulance Brigade, highlights the main points

in red, and explains and illustrates the actions to be taken so clearly that they can be grasped instantaneously even in a crisis. It also includes vital instruction on what to do if the casualty does not respond to artificial respiration—with a section on external heart compression. Action this second could save a life. Post this coupon NOW.

VIVID RED AND BLACK. PLASTIC, CARD OR PAPER.
SIZE 19 in × 13½in (474mm × 346mm)

ELECTRIC SHOCK ACT AT ONCE — DELAY IS FATAL


make sure it is safe to approach

If the casualty is not clear of the source of the shock break the contact by switching off the current, removing the plug, or wrenching the cable free. If this is not possible, stand on dry insulating material (rubber, wood, brick, thickly folded news-
paper, books) and try to push or pull the casualty clear of the contact using similar insulating material (such as a broomstick) as a lever. Do not touch him with bare hands.

if the casualty is breathing

Place the casualty in the recovery position and give first aid.

recovery position

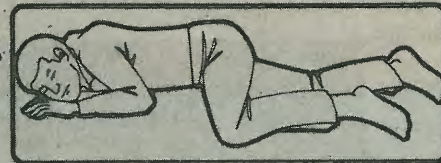

if the casualty is NOT breathing

Give full medical aid while you perform artificial respiration—speed is essential


3. Take a deep breath. Pinch casualty's nostrils together with your fingers. Seal your lips around his mouth and blow air steadily into his lungs. Watch his chest rise.



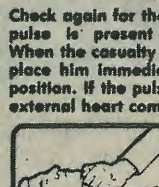4. Remove mouth and watch chest fall. 5. Repeat and continue inflations at your natural rate of breathing. When casualty starts breathing place him immediately in the recovery position.

if the casualty does not respond to artificial respiration

Take care! Too small a thump will be ineffective but too large a thump could injure the casualty. Assess the casualty—a thin person will require less force than a fat person.



Check again for the carotid pulse. If the pulse is present continue inflations. When the casualty breathes on his own, place him immediately in the recovery position. If the pulse is still absent start external heart compression.



normal
dilated

Check the pulse again. If it is present continue with inflations until casualty breathes on his own, then place him immediately in the recovery position. If the pulse is absent repeat the 15 compressions and two inflations until there is a response from the casualty.

doctor:-

phonet:-

ambulance:-

phonet:-

hospital:-

phonet:-

nearest first aid:-

phonet:-

on recovery continue to watch casualty carefully as breathing may stop. If it does, turn casualty on his back and start artificial respiration again. Cover casualty with one blanket only.

Prepared in co-operation with St. John Ambulance.

electrical review
Direct House, Stamford St. London, SE1 1JU

Electrical Review SHOCK FIRST AID CHART

To General Sales Dept., Room 205 Quadrant House, The Quadrant, Sutton, Surrey.
Please send me the copies of the Electrical Review First Aid Chart indicated below:

..... paper charts at 70p each
..... Plastic charts at £2.10 each
..... card charts at £1.40 each

I enclose cheque money order for

Name _____
Address _____

All prices include postage and packing. Cheques should be made payable to Electrical Review Press Ltd.
51

RHODE & SCHWARZ

Selective UHF V/Meter. Bands 4 & 5. USVF Selectomat Voltmeter USWV £450.
UHF Sig. Gen. type SDR 0.3-1GHz £750.
UHF Signal Generator SCH £175.
XUD Decade Synthesizer & Exciter.
POLYSKOPS SWOB I and II.
Modulator/Demodulator BN1 7950/2.
UHF Sig. Gen. type SCR. 1-1.9GHz.

MARCONI

TF995B/2 AM/FM Signal Generator.
TF2500 Audio power meter
TF1101 RC oscillators £65.
6551 SAUNDERS. 1400-1700MHz. FM.
TF1066B/1. 10-470MHz. AM/FM.
TF1152A/1. Power meter. 25W. 500MHz.
£50.
TF1370A RC Oscillator £135.
TF791D Carrier Deviation Meter.

U.H.F. SIGNAL GENERATORS

TF1066B/2 400-555MHz. Deviation to 300KHz.
TF1060/2 450-1250MHz.
TF1058 1.6-4000MHz.

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipot." Brand new with mounting instructions. Only £2.50 each.

PRINTED CIRCUIT MOTORS

'Printed Motors Ltd' type G16M4. 60V DC. 5.5 amps. Continuous torque 140oz. in. 2350 rpm. Diameter 7.5". Depth 2.5". Shaft diam. ½ & ¾". Price from Printed Motors is now over £150 ea. Supplied in good, used condition, tested & guaranteed £25 each (postage £3).


AUDIO & RF SIGNAL GENERATORS

ADVANCE types H1, H1E, C2, SG62B, J4A.
TAYLOR 62A (AM/FM). AVO HF134.
AIRMEC 352 Sweep Generator.
MARCONI TF1066B/1 (AM/FM 10-470MHz).

LABORATORY OVENS. — Gallenkamp 3 cu. ft. £145. Also Morgan Grundy 1 cu. ft. £55.
20-WAY JACK SOCKET STRIPS. 3 pole type with two normally closed contacts £2.50 each (+25p pp). Type 316 three pole plugs for above — 20p ea. (pp free).

P. F. RALFE ELECTRONICS

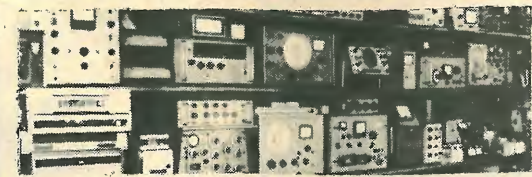10 CHAPEL STREET, LONDON, NW1
TEL: 01-723 8753



RANK KALEE 1742 Wow & Flutter Meter.
AIRMEC 314A Voltmeter. 300mV (FSD)-300V.
AIRMEC Wave Analysers types 853 & 248A.
DERRITRON 1KW Power Amplifier with control equipment for vibration testing, etc.
HEWLETT-PACKARD 8551B/851B Spectrum Analyser. 10MHz-40GHz.
HEWLETT-PACKARD tuned amp & null detector.
HEWLETT-PACKARD 331A Distortion Meter
RADIOMETER Distortion Meter BKF6 £125.

TELEVISION TEST EQUIPMENT

TEXSCAN VS-60B Sweep Generator. 0-1000MHz £250.
TEXSCAN DU-88 X-Y Display units £95.
TELONIC 2003 Sweep Generator System £225.
TELONIC 101 X-Y Display units £75.
TELONIC 1204 Sweepers 0-500MHz £150.
TELONIC 121 X-Y Display units £95.

OSCILLOSCOPE SALE

ADVANCE OS250. Dual Beam 10MHz £185
HEWLETT-PACKARD 1707A. 75MHz £450.
TELEQUIPMENT D75.
TELEQUIPMENT DM64 Storage scope.
DYNAMCO D7100.
HEWLETT-PACKARD 122A SB. Audio.
AIRMEC 279. 4 Beam Display Scope.
TEKTRONIX 581A, 545A & B, 544, 661, 515A.

NOTICE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry our three months' guarantee. Calibration and certificates can be arranged at cost. Overseas enquiries welcome. PLEASE ADD 15% VAT TO ALL PRICES.

DC POWER SUPPLIES

★APT 10459/8, 12-14V @ 5 Amps £25 (£2 p.p.)
★APT 10459/8, 24V @ 5 Amps £25 (£2 p.p.)
★We can supply the above power supply at any fixed voltage between 5V and 36V at 5A £25.
★Mullard Dual supplies. Brand new with handbook. Pos & Neg 12V at 1A and 0.4A respectively. Dimensions 9x4x5ins. £10 + (£1 p.p.)
★FARNELL Current limited. Dimensions 7x5x4ins. Following types available: 13-17 Volts @ 2A £15.
27-32 Volts @ 1A 5V £15. 5V @ 3A £15. (pp £1.50).

SPECIAL PURCHASE LAMBDA POWER SUPPLIES

Excellent LXS Series DC power units at less than a tenth of new price. The snag? — they're all 110V AC Input. Prices as follows:
5V at 24A. LXS D5 0V R. £25. (List £350).
15V at 12A. LXS D15 R. £20. (£339).
5V at 14A. LXS CC 5 0V. £20. (£258).
24V at 3.1A. LCS C 24. £15. (£223).
Carriage each £2.50 extra

MODULATION METERS

AIRMEC 210 3-300MHz. AM/FM. £125
RADIOMETER AFM/1 3.5-320MHz. AM/FM. £145
RACAL 409 3-600MHz. AM/FM.

ROTRON INSTRUMENT COOLING FANS

★ Supplied in excellent condition, fully tested:
★ 115V, 4.5 × 4.5 × 1.5" £4.50. 230V £5. 115V, 3 × 3 × 1.5" £4 + postage ea. 35p.
★ CT212 RF Signal Generators. 85KHz-32MHz. £55.

BELL & HOWELL MICROFICHE VIEWERS

★ Type SR5. Screen size 9 x 5in. New condition. £50.


DIGITAL MULTI-METERS

★ DE FOREST ELECTRONICS TYPE MM200. DC V 0-1KV. AC V 0-700. DC 1.0-1A. AC 1.0-1A. Each in 4 ranges. Resistance 0-19.99 Mohms. 5 ranges. LED Display 1999.
★ BRAND NEW. SPECIAL REDUCED PRICE OF £39, INCLUDING VAT & P.P.

Who's Who and What's What in the Electrical Industry

Famous for its total coverage, detail and accuracy, the ELECTRICITY SUPPLY HANDBOOK usually sells out fast — so ensure your copy and post the coupon below, today!

- Over 2,000 names and locations of executive personnel in the Electricity Council, C.E.G.B., Area Boards and other organisations.
- Major authorities, government departments associated with the electrical industry.
- U.K. power stations, Area Board statistics, electricity tariffs, electrical associations.
- Pull out map of C.E.G.B. Regions, power stations and transmission lines.
- Bound in maps of Area Boards.

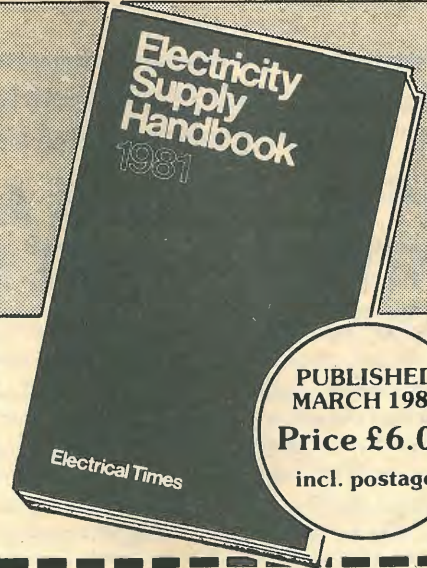

To: General Sales Department, Room 205, Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Please send me.....copy/ies of ELECTRICITY SUPPLY HANDBOOK 1981

Name _____

Address _____

Company registered in England No. 677128. Reg. Office: Quadrant House, The Quadrant, Sutton, Surrey, SM2 5AS.

Guide to Broadcasting Stations

18th Edition

Around the world some thousands of radio stations are sending signals. If you're receiving, this standard guide will tell you who's where. It lists stations broadcasting in the long, medium, short wave and vhf bands, dealing with them by frequency, geographical location and alphabetical order. Sections are helpfully cross referenced. The Wireless World Guide to Broadcasting Stations is the eighteenth edition of a publication which has sold over 270,000 copies. In addition to the stations data, it includes much useful information on aerials, propagation, signal identifications and reception reports.

£3.25 inc. postage.

Wireless World

Guide to Broadcasting Stations

18th Edition

Over 270,000 copies sold

To: General Sales Dept., Room 205
Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

Please send me _____ copy/ies of the Wireless World Guide to Broadcasting Stations (18th edition) @ £3.25 a copy inclusive, (U.K.), \$8 overseas, remittance enclosed. Cheque/P.O. payable to IPC Business Press Ltd.

Name _____
(please print)
Address _____

Registered in England No. 677128
Registered Office: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

Appointments

Advertisements accepted up to 12 noon Monday, June 29, for August issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £12 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £2 per line, minimum 5 lines (pre-payable).
BOX NUMBERS: £1 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 4AS.)
PHONE: JAYNE PALMER, 01-661 3033 (DIRECT LINE)
Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.



ALWAYS AHEAD WITH THE BEST!

£5,000-£15,000

PDP 11: NOVA: ECLIPSE: Z80: 8080: 6800: BIT-SLICE: TTL: ECL: RADAR: SONAR: SATCOM: Phototypesetters: Wordprocessors: Flight Simulators: ATE: Electro-Medical: Teletext: Data-Comms: Automation: Microwave?

Where does your skill and interest lie - Design? Test? Service? Software? Consultancy? or perhaps Research?

- * Our clients are drawn from all sectors of industry:
- * There are opportunities for Managers, Project Managers, Engineers and Technicians.
- * Most UK locations and some Overseas.
- * Make your first call count - Contact MIKE GERNAT on 076 384 676/7 (usually until 8 p.m.)

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
148-150 High St., Barkway, Royston, Herts SG8 8EG.

(1118)

APPOINTMENTS IN ELECTRONICS to £15,000

MICROPROCESSORS
COMPUTERS - MEDICAL
DATA COMMS - RADIO

Design, test, field and support engineers - for immediate action on salary and career advancement, please contact:

Technomark
Engineering and Technical Recruitment
11, Westbourne Grove
London W2. 01-229 9239 (9257)

DIGITAL EXPERIENCE?

FIELD, SUPPORT AND PRODUCTION. VACANCIES IN COMPUTERS, NC, COMMS., MEDICAL, VIDEO, ETC.

For free registration ring
0453 883264
01-290 0267

LOGEX

ELECTRONICS RECRUITMENT SERVICE
LOGEX HOUSE, BURLEIGH, STROUD
GLOUCESTERSHIRE GL5 2PW
TEL. 0453 883264, 01-290 0267 (921)

Electronic Engineers - What you want, where you want!

TJB Electrotechnical Personnel Services is a specialised appointments service for electrical and electronic engineers. We have clients throughout the UK who urgently need technical staff at all levels from Junior Technician to Senior Management. Vacancies exist in all branches of electronics and allied disciplines - right through from design to marketing - at salary levels from around £4000 to £12000 p.a.

If you wish to make the most of your qualifications and experience and move another rung or two up the ladder we will be pleased to help you. All applications are treated in strict confidence and there is no danger of your present employer (or other companies you specify) being made aware of your application.

TJB ELECTROTECHNICAL PERSONNEL SERVICES,
12 Mount Ephraim,
Tunbridge Wells,
Kent. TN4 8AS.

Tel: 0892 39388



Please send me a TJB Appointments Registration form:

Name

Address

(861)

Service & Installation Engineers

An Electronic Defence Systems company in the South of England is seeking Service & Installation Engineers to be engaged on the installation and technical support of complex medical electronic equipment, both at home and abroad.

They are looking for adaptable self-reliant engineers who are prepared to spend periods of up to approximately four months overseas. The successful candidates will have a good knowledge of semi-conductor circuitry, be qualified to H.N.C. or equivalent standard and will preferably have worked on such equipment as modern high-power radar systems.

Please write quoting ref: WW/386 giving full details of career to date, listing any companies to whom you do not wish your application forwarded, to: John Maines, Riley Advertising (Southern) Limited, Old Court House, Old Court Place, Kensington, London, W8 4PD.

A member of the Rex Stewart Group
LONDON BIRMINGHAM BRISTOL EDINBURGH GLASGOW
LIVERPOOL MANCHESTER NEWCASTLE NOTTINGHAM PERTH

Confidential Reply Service
Riley

(1164)

APPOINTMENTS
IN
ELECTRONICS
to £12,000 +

MESSAGE SWITCH
DATA COMMS-TELEMETRY
TELEGRAPHY-RF COMMS

Interesting and varied opportunities, U.K. and overseas. For immediate action on salary and career advancement, contact:

Technomark
Engineering and Technical Recruitment
11, Westbourne Grove
London W2. 01-229 9239 (1080)

Electronics R&D

£7,999

Join us in the forefront
of technology

Take your pick

HF-VHF-UHF

Microwave Optics & Acoustics
A challenging and full career in
Government Service

Candidates, normally aged under 30, should have a good honours degree or equivalent in a relevant subject, but any candidates about to graduate may be considered.

Appointments as Higher Scientific Officer (£6,075-£7,999) or Scientific Officer (£4,805-£6,480) according to qualifications and experience. Promotion prospects.

Please apply for an application form to the Recruitment Officer (Dept I.E.1), H M Government Communications Centre, Hanslope Park, Milton Keynes MK19 7BH.

(1028)

TECHNICIAN (MOBILE RADIO)

£6500-£7500 Western Home Counties

This subsidiary of a world-wide group markets a diverse range of electrical and electronic products throughout the UK.

They are looking for a Technician to install and service a range of radio telephone products. The successful candidate will be responsible for the service support needed by the Sales Team and may also be called upon to develop a contribution to the customer training programme.

Applications are invited from candidates qualified by experience of installation and service work in the mobile radio telephone field and with the ability to develop as a member of a dynamic team.

Candidates should be prepared to travel widely in the course of these duties, a mobile workshop being provided.

The benefits package includes a contributory pension scheme, life assurance plus generous relocation assistance.

Please write with full career details or telephone for an application form in strict confidence quoting ref WW/546 to: Ray Diamond

GERRARDS

Gerrard Recruitment Service,

10 Argyll Street, London W1V 2BQ. Tel: 01-437 6816

COLOUR VIDEO SERVICES

have a vacancy for an enthusiastic

BROADCAST VIDEO ENGINEER

Experience in maintenance and operation of 2in. quad VTR is essential. Knowledge of 1in. "C" format VTR would be very useful. There would be opportunities to gain experience on flying spot telecine and other equipment on the station. Salary between £6,427 and £8,246 according to experience.

Applicants please telephone:

Mr. F. H. Weinel
on 01-486 2881, or write to:
COLOUR VIDEO SERVICES LIMITED
22-25 Portman Close, Baker Street, London, W.1

(1183)

UNIVERSITY OF OXFORD
DEPARTMENT OF PSYCHIATRY

ELECTRONICS TECHNICIAN

Electronics Technician required for varied and challenging post in medical research. Duties include the design and construction of equipment used in psychological and physiological experimentation. Applicant must be thoroughly conversant with discrete components, micro circuit amplifiers, TTL and c.mos techniques and be able to design both analogue and digital circuits. Knowledge of microprocessors an advantage.

Salary scale: Whitley Council Medical Physics Technician III £5223-£6750 or II £6291-£7845 p.a., dependent on age and experience.

Further details from Dr. D. Johnston, Psychological Treatment Research Unit, The Warneford Hospital, Oxford OX3 7JX (Tel. Oxford 45651, extension 218).

(1152)

URGENT ELECTRONICS ENGINEERS FOR HUNDREDS OF VACANCIES INCLUDING...

SENIOR SOFTWARE ENGINEER for rapidly expanding company, involved in mpu based instrumentation for quality control. 8080/8085 Machine Code, Assembler and Basic. W. LONDON, to £10,000.

YOUNG ENGINEERS for applied research connected with sonar, radar, RF microwave, signal processing and opto-electronic circuitry. SOUTH COAST, to £8,000.

VIDEO ENGINEERS complex projects associated with moving picture processing and transmission, complex signal processing, frame and picture storage techniques. BERKS, to £10,000.

DES/DEV ENGINEERS for data communications projects including: network management systems and colour graphics. BUCKS, to £10,000.

Charles Airey Associates

4 Hammersmith Grove, London W6 0NA. Tel: 01-741 4011 (1175)

GOVERNMENT OF DUBAI DUBAI RADIO AND COLOUR TELEVISION TELEVISION ENGINEERING DEPARTMENT

Applications are invited from suitably qualified Engineers with several years' proven experience in the field of Television Engineering to fill the following vacancies:

1. TELEVISION STUDIO ENGINEER

To be responsible to the Chief Engineer for the maintenance of all equipments within the Television Studio Complex and Outside Broadcast Units. Candidates should preferably have some experience of Memory Modulated Lighting Systems. All studios are equipped with EMI 2005 Cameras and Richmondhill Laboratory Mixers. LDK 14 Cameras are used in the Eng. Unit and Ampex BCC-20 Cameras in the OB Unit.

Salary shall be sterling £13,000-£14,000 depending on experience.

2. V.T.R. ENGINEER

To be responsible to the Chief Engineer for the maintenance of all VTR Equipments within the Studio Complex and Outside Broadcast Unit. Candidates should preferably have experience in AMPEX 1200B, AVR2, VPR2 and VPR20 machines.

Salary shall be sterling £13,000-£14,000 depending on experience.

3. LIGHTING DIRECTOR

To be responsible to the Chief Engineer for the lighting of all drama and light entertainment productions and shall act in the capacity of Technical Manager.

Salary shall be sterling £17,000-£18,000 depending on experience.

Salaries quoted are annual and are tax-free. The initial contract shall be for a period of 2 years and further details regarding conditions of service may be obtained from Mr. J. Billett, Falcon Television, 7a Grafton Street, London, W1X 3LA. Tel. 01-629 6848.

Applications, which shall be treated with the strictest confidence, should be sent, accompanied with full c.v. and U.K. telephone contact, to:

Chief Engineer - Television
DUBAI RADIO AND COLOUR TV
P.O. Box 1695
Dubai, United Arab Emirates

(1179)

Technicians in Communications

GCHQ We are the Government Communications Headquarters, based at Cheltenham. Our interest is R & D in all types of modern radio communications - HF to satellite - and their security.

THE JOB All aspects of technician support to an unparalleled range of communications equipment, much of it at the forefront of current technology.

LOCATION Sites at Cheltenham in the very attractive Cotswolds and elsewhere in the UK; opportunities for service abroad.

PAY Competitive rates, reviewed regularly. Relevant experience may count towards increased starting pay. Promotion prospects.

TRAINING We encourage you to acquire new skills and experience.


QUALIFICATIONS You should have a TEC Certificate in Telecommunications, or acceptable equivalent, plus practical experience.

HOW TO APPLY For full details on this and information on our special scheme for those lacking practical experience, write now to

Robby Robinson, Recruitment Office
GCHQ, Oakley, Priors Road, Cheltenham
Glos. GL52 5AJ
or ring
0242 21491
ext 2269

(666)

GCHQ

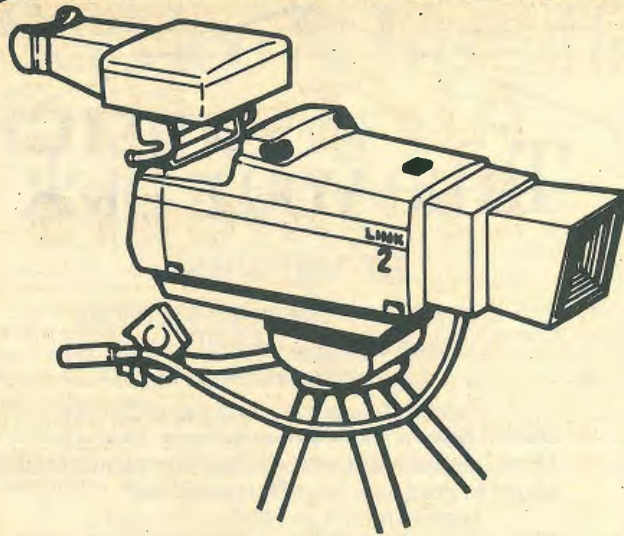

LINK

As a well-established designer and manufacturer of equipment to TV broadcast companies worldwide, we urgently require experienced engineers to fill the following demanding positions, both of which offer a high degree of job satisfaction.

SALES SUPPORT ENGINEER - VISION MIXERS

We need an electronic engineer with a background in TV studio engineering to work on the commissioning, acceptance, demonstration and after-sales activities of broadcast standard vision mixers. Direct experience of mixers, whilst not essential, would be a definite advantage. Alternatively you should have worked on video switching systems and be familiar with the performance requirements of modern colour TV routing and switching.

Considerable involvement with customers will be necessary and the position would necessitate occasional travel within the U.K. Minimum age would be 28.

DESIGN AND DEVELOPMENT ENGINEER - VIDEO

Experienced engineers, to be involved in the design of TV studio products, including a new range of colour cameras, using the very latest analogue and digital techniques. You will have the opportunity to see your designs made in volume production, fulfilling the high technology requirements of the '80s.

We are looking for engineers, minimum age 25, who are qualified to degree level and who have at least four years' experience of electronic equipment. A knowledge of microprocessor techniques and video engineering would be added advantages.

Salaries offered are extremely competitive and are backed by free life and health insurance plus a contributory pension scheme. Generous financial assistance with relocation will be given where appropriate to help successful candidates move to this pleasant rural part of Hampshire which offers easy access to London and major towns in the South of England.

Please phone Jacqui Cornall at Andover (0264) 61345 and ask her to send you an application form or, alternatively, let us have full details of your background and experience.

LINK

ELECTRONICS

Walworth Industrial Estate,
Andover, Hampshire, England Telephone: Andover (0264) 61345

(1151)

PRODUCTION ENGINEER

We have a vacancy for an Engineer with experience of quartz crystal production. The successful applicant will be responsible for manufacturing methods and the maintenance of top standards in our Southampton factory.

Education to H.N.C. standard is desirable, a practical approach and the ability to work without supervision is essential.

Above-average salary for the right applicant, plus relocation allowance if necessary and normal company benefits.

Apply in writing to:
The Personnel Director
IQD CRYSTAL ELECTRONICS
29 Market Street, Crewkerne
Somerset, TA18 7JU



(1180)



CAPITAL

APPOINTMENTS LTD.

THE UK'S No. 1 ELECTRONICS AGENCY

Design, Dev. and Test to £10,000
Ask for Brian Cornwell

SALES to £12,000 plus car
Ask for Maurice Wayne

FIELD SERVICE to £10,000 plus car
Ask for Paul Wallis

We have vacancies in ALL AREAS of the UK

Telephone: 01-637 5551 (3 lines)

(291)

CAPITAL HOUSE
29-30 WINDMILL
STREET
LONDON W1P 1HG
TEL: 01-637 5551

Gresham Executive Appointments

D.E.C. EXPERIENCE?

Real Time Mini/Micro Applications.
Industrial Computer Systems.
Experience and your personality create progression in the following areas:

- SALES ENGINEER
- SENIOR SOFTWARE ENGINEER
- APPLICATIONS ENGINEER
- DEVELOPMENT ENGINEER

Contact Keith Diprose on 021-643 5231
GRESHAM EXECUTIVE APPOINTMENTS
5th Floor, New Street Chambers
67a New Street, Birmingham

(1163)

The Middlesex Hospital, London W1N 8AA

JUNIOR MEDICAL PHYSICS TECHNICIAN

Applications are invited for the above post in the Department of Clinical (Physiological) Measurement. Applicants should have 2 GCE 'A' levels or at least 4 'O' levels, three of which must be in scientific subjects, as well as two years' technical experience in electronics or some allied scientific subject. The job is essentially that of a junior technician in the electronics laboratory but a suitably motivated candidate may be required to take part in patient-monitoring activities in the Intensive Care Unit and the Operating Theatres. Day Release may be available for those studying for approved qualifications. Salary: £3614-£4523 p.a. Further information is available from Miss B. Smith, Personnel Officer, The Middlesex Hospital, Mortimer Street, London W1N 8AA. Tel: 01-636 8333 Ext. 7462.

(1165)

DEVELOPMENT OPPORTUNITIES

COMMUNICATIONS WEST SUSSEX

Our Research & Development Laboratories in Crawley, West Sussex, are actively involved in developing the Communications technology and equipment of the future.

To meet the demands of our expanding programme, we are currently seeking additional R & D personnel with proven expertise in any of the following areas:

- HF Transmitters and Linear Wideband Amplifiers
- VHF/Mobile Radio Systems
- Signal Processing & Control
- Communications Hardware/Software

All positions are at Senior/Principal Engineer level and we offer highly competitive salaries together with attractive benefits.

If you are seeking a progressive Development opportunity, make this your next move.

For further details and application forms, please telephone or write to:

David Bird, Personnel Department,
Rediffusion Radio Systems Limited,
Broomhill Road, London, SW18 4JQ.
Telephone: 01-874 7281



REDIFFUSION

Radio Systems

... great to communicate with

Trent Polytechnic RESEARCH ASSISTANT/ DEMONSTRATORS

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Good honours graduates desirous of working for a higher degree are invited to apply for research posts in the following areas:

- 1) Three-dimensional television.
- 2) Photovoltaic cells using organic semiconductors.
- 3) Bipolar charging of powders for use in electrostatic powder coating.
- 4) Low frequency noise in instrumentation systems.

Salary Currently: £4683-£4884-£5085 rising to £5034-£5250-£5466 from 1 September, 1981.

Further details of project and form of application available from The Assistant Director (Administration) Trent Polytechnic, Burton Street, Nottingham NG1 4BU. Applications to be returned as soon as possible.

(1153)

ARTICLES WANTED

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap, any quantity. Prompt service and cash. Member of A.R.R.A.

M & B RADIO
86 Bishopgate Street
Leeds LS1 4BB
0532-35649

WE BUY FOR CASH: Components, PCBs, etc. Good prices paid. Quick decision, money by return. Ring (0703) 785862. (1172)

SPOT CASH

paid for all forms of electronics equipment and components.

FRG General Supplies Ltd.
Unit 3
Longhill Industrial Estate
March, Cambridgeshire
Tel: March 56614
Tel: 01-404 5011
Tel: 24224. Quote Ref. 3165 (8742)

STORAGE SPACE is expensive, why store redundant and obsolete equipment? For fast and efficient clearance of all test gear, power supplies, PC boards, components, etc., regardless of condition or quantities. Call 01-771 9413. (8209)

Air Traffic Engineers

The Civil Aviation Authority has vacancies for men and women as Air Traffic Engineers Grade 2 in its Telecommunications Division offering a variety of work on a wide range of electronic systems and specialised equipments.

Air Traffic Engineers Grade 2 are involved in the installation and maintenance of radio, radar, air navigational and landing aids, and data processing systems. Staff are employed at some Civil Airports, Air Traffic Control Centres and Radar Stations and other locations throughout the UK but at present most of the vacancies are likely to be in the South of England with a few vacancies elsewhere in the UK.

Qualifications and Experience

You should be at least 20 years of age and have obtained either the O.N.C. (Eng.) with an electronic bias or C. & G. Telecommunications Technician T3 Certificates or other similar technical qualifications.

Skilled working experience in radio, radar or data processing is essential.

Salary

Salaries are on an incremental scale £5,683-£8,783. Posts in the London area attract an additional allowance (Inner London £1,082 - Outer London £452). Grade 1 posts (maximum salary £10,610) are normally filled by promotion from Grade 2.

For full details and an application form complete and send the coupon to: CAA, Personnel (Tels), Room T 1206, CAA House, 45-59 Kingsway, London, WC2B 6TE.

Name.....
Address.....
..... WW



Civil Aviation Authority

(1125)

R & D OPPORTUNITIES. Senior level vacancies for Communications Hardware and Software Engineers, based in West Sussex. Competitive salaries offered. Please ring David Bird at Rediffusion Radio Systems on 01-874 7281. (1182)

UNIVERSITY OF OXFORD. ELECTRONICS TECHNICIAN. Electronics technician required for work on mass spectrometers and other equipment in the Department of Geology and Mineralogy, under the technical direction of the Electronics Group in the Physics Department. Applicants should have wide experience in fault-finding and building of modern electronic equipment. Appointment in the first instance until July 31, 1985. Salary range, from July 1, 1981, £6,532-£7,802. Applications with full personal and professional details as soon as possible, to the Administrator, Department of Geology, Parks Road, Oxford OX1 3PR. (1168)

£25,000?

1. REAL TIME SOFTWARE ENGINEERS. Avionic applications. £11,000. Herts.
2. DEVELOPMENT MANAGER, working with microprocessor-based detection systems. £12,000. Middlesex.
3. SALES ENGINEERS, selling range of microprocessor-based test equipment. £10,000 plus car. Various.
4. SENIOR DESIGN ENGINEERS, to work on Z80-based systems, for entertainment industry, £10,000. Middlesex.
5. DESIGN ENGINEER to work on Digital/Analyse Systems. Some microprocessor. £8,500. Surrey.
6. PRODUCT SUPPORT ENGINEER microcomputers. Experience of Z80 or 8080 Software. £9,000 plus car. London.

HUNDREDS OF OTHER ELECTRONICS AND COMPUTER VACANCIES TO £25,000

Phone or write:
ANTHONY GILES, M.Sc., C. Eng., M.I.E.E.
CLIVEDEN CONSULTANTS
87 St Leonard's Road, Windsor, Berks
Windsor (07535) 57818
24-hour Ansaphone (1119)

CLIVEDEN

TOP JOBS IN ELECTRONICS

Posts in Computers, Medical, Comms, etc. ONC to Ph.D. Free service.

Phone: 01-906 0251 (8994)

By order of Rank Television Limited
Plant & Equipment surplus to requirements

IMPORTANT 4-DAY SALE BY AUCTION

TELEVISION MANUFACTURER'S
EXCELLENT MODERN MACHINERY & EQUIPMENT

at the works ERNESETTLE LANE, PLYMOUTH at 10 a.m. each day

DAY ONE

TUESDAY, 30 JUNE, 1981
WIRE WOUND COMPONENTS
MANUFACTURING PLANT

- including:
AUMANN WPA 70 12-STATION SEQUENTIAL WINDERS
UNIVERSAL 3LS & 1980 GORMAN 920A TOROID WINDERS
ROTAWINDER SEQUENTIAL CHOKE WINDER, LESSONA 104 COIL
WINDERS
BENCH COIL WINDERS by Ko-lectric, Avo & Douglas, ARTOS WIRE
CUTTERS AND STRIPPERS
1980 ZEVATRON TL3 DIP SOLDER MACHINE, FLOW SOLDER MACHINES
GENERAL ENGINEERS VACUUM IMPREGNATION PLANTS
BARLOW WHITNEY ELECTRIC CURING OVENS & WAX
IMPREGNATION PLANTS
DALE 255 KVA DIESEL GENERATOR, BROOMWADE V300F2 AIR COMP-
RESSOR
LANSING-BAGNALL 2000LB ELECTRIC FORK LIFT TRUCK
FLOOR & OVERHEAD CONVEYOR SYSTEMS, DEXION SPEEDLOCK PAL-
LET RACKING
FLOOR CLEANING EQUIPMENT, BENCHES, STORAGE BINS & FACTORY
FURNITURE
EXTENSIVE RANGE OF MODERN CANTEEN FURNITURE AND KITCHEN
EQUIPMENT

DAY TWO

WEDNESDAY, 1 JULY, 1981
TELEVISION MANUFACTURING PLANT
MACHINE TOOLS, OFFICE FURNITURE
FORK LIFT TRUCKS & MOTOR VEHICLES

- including:
BLAKELL PALLETISER with SIGNODE STRAPPING EQUIPMENT
NIKON PROFILE PROJECTOR, KURTZ RT25 CABINET FOILING MACHINE
TOP & BOTTOM CARTON STAPLER, SILK SCREEN PRINTER
FRY 75 FLOWSOLDER MACHINE with chain conveyor & 3 solder bath
lines
POWER BELT, GRAVITY ROLLER AND GLIDEWHEEL CONVEYOR
SYSTEMS
LOW LEVEL CAROUSEL CHAIN CONVEYORS
Q&S 10" HACKSAWING MACHINE, SS&SC LATHES by Kerry & Wyvern
BEAVER VBRP TURRET MILL, UNIVERSAL MILLS by Adcock & Shipley
and Parkson
BENCH & PILLAR DRILLS by Arboga, Kerry, Meddings, Progress and
Webo
EDWARDS SHEET METALWORKING MACHINERY, GUYSON SAND
BLAST CABINET
TRENKJAEGER COLD SAW, VIRAX 604 PIPE THREADER, CHAIN HOISTS
SEYMOUR 2000LB VERTICAL PLASTICS INJECTION MOULDING
MACHINE
AEW ELECTRIC MUFFLE FURNACES, SPRAY BOOTHS,
AVERY WEIGHING MACHINES
BTH 330 KVA DIESEL GENERATOR, BROOMWADE V500 AIR COMPRES-
SOR
PERMUTIT CTP WATER TREATMENT PLANT, DEXION SPEEDLOCK PAL-
LET RACKING
SAFES, AIR CONDITIONER, KITCHEN EQUIPMENT & EXTENSIVE RANGE
OF OFFICE FURNITURE
ROVER 3.5 AND JAGUAR 3.4 AUTOMATIC SALOON CARS
FORD GRANADA 2.3L AND CITROEN CX2000 & GLS PALLAS SALOON
CARS
FORD CORTINA 1.6 & 2.0 GLESTATE CARS
FORD 2817 ARTIC UNITS, D1311 RIGID AND TRANSIT COMMERCIAL
VEHICLES
ELECTRIC & LPG FORK LIFT TRUCKS & PALLET CONVEYORS by BT
Rolatrac, Coventry Climax, Lansing Bagnall, Linde and Montgomerie
Reid

ON VIEW: Monday 22 to Friday 26 June, 1981; Monday 29 June and mornings of sale.
Catalogues, when ready, from the Agents:

Weatherall
Green & Smith
Chartered Surveyors

22 Chancery Lane, London WC2A 1LT
01-405 6944. Telex 22446

29 King Street, Leeds LS1 2HP
(0532) 442066 Telex 557544

Auctioneers and Valuers of Industrial Property, Plant and Machinery

London Leeds Paris Frankfurt Munich New York

TO MANUFACTURERS, WHOLESALE &
BULK BUYERS ONLY

Large quantities of Radio, I.V. and Electronic Components.
RESISTORS CARBON & C/F 1/8, 1/4, 1/2, 1. 1 Watt from 1 ohm to
10 meg.
RESISTORS WIREWOUND. 1 1/2, 2, 3, 5, 10, 14, 25 Watt.
CAPACITORS. Silver mica, Polystyrene, Polyester, Disc Ceramics,
Metalumite, C280, etc.
Convergence Pots, Slider Pots, Electrolytic condensers, Can Types,
Axial, Radial, etc.
Transformers, chokes, hopts, tuners, speakers, cables, screened wires,
connecting wires, screws, nuts, transistors, ICs, Diodes, etc., etc.
All at Knockout prices. Come and pay us a visit. Telephone 445 2713.
445 0749.

BROADFIELDS & MAYCO DISPOSALS
21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tolly Ho Corner (9461).

THE
ART OF
ELECTRONICS

by Horowitz & Hill
Price £13.50

THE PPL SYNTHESIZER COOK-
BOOK, by H. Kinley Price: £5.25
THE MC6809 COOKBOOK, by C. D.
Warren Price: £5.00
DIGITAL ICS... HOW THEY WORK
AND HOW TO USE THEM, by A.
W. Barber Price: £5.75
ELECTRONIC DESIGN WITH OFF
THE SHELF INTEGRATED CIR-
CUITS, by Z. H. Meiksin Price: £6.25

EXPERIMENTER'S GUIDE TO
SOLID STATE ELECTRONICS PRO-
JECTS, by A. W. Barber Price: £5.50
COMPLETE GUIDE TO READING
SCHEMATIC DIAGRAMS, by J.
Douglas-Young Price: £5.50
PRACTICAL SOLID STATE CIR-
CUIT DESIGN, by J. E. Oleksy Price: £6.50

WORLD RADIO/T.V. HANDBOOK,
by J. M. Frost Price: £10.50
1981 THE RADIO AMATEUR'S
HANDBOOK, by A.R.R.L. Price: £8.00

ALL PRICES
INCLUDE POSTAGE

THE MODERN BOOK CO.

Specialist in Scientific
& Technical Books
19-21 PRAED STREET
LONDON W2 1NP
Phone 402-9176
Closed Sat. 1 p.m. (8974)

SHADED POLE MOTORS for im-
mediate disposal, complete plant
and cooling capable of producing
over 5,000 shaded pole motors per
week, 2 pole and 4 pole. Tel:
053181 273. (1177)

TEKTRONIX OSCILLOSCOPES in
tip-top condition. 545A DC-15MHz
£120. 545B DC-33MHz £180. D/trace
amplifiers. CA £80. LA2 £120. Sup-
plied calibrated with full hand-
books. Prices inclusive. Carriage
extra. Bournemouth (0202) 472376/
291481. (1157)

FR DX-400 AMATEUR BAND
RECEIVER. 160m to 2m including
CB and 4m. AM. FM. SSB with
matching speaker, mint condition.
£185. Telephone Swanley (Kent)
63968. (1067)

ENCAPSULATING, coils, transform-
ers, components, degassing, sili-
cone rubber, resin, epoxy. Lost
wax casting for brass, bronze, sil-
ver, etc. Impregnating coils, trans-
formers, components. Vacuum
equipment low cost, used and new.
Also for CRT regunning met-
allising. Research & Development.
Barratts, Mayo Road, Croydon,
CRO 2QP. 01-684 9917. (9678)

BUGGED? UNDER
SURVEILLANCE?

THE BUGGING GAME
is a unique, previously restricted book describ-
ing modern counter-surveillance and eavesdrop-
ping techniques. A virtual encyclopedia of "hid-
den knowledge" it tells ALL YOU NEED TO
KNOW about professional and secret service
methods! PART 1 - TELEPHONE SYSTEMS.
PART 2 - RADIO & MICROPHONE SYSTEMS.
PART 3 - ELECTRONIC SURVEILLANCE &
COUNTERMEASURES. 300 pages of unobtain-
able information! DON'T WAIT! ... this book
could easily disappear from the market. Price £9
per set plus £1 p. & p. CYBERSCAN INTERNA-
TIONAL 35 Dell Farm Road, Ruislip, Middlesex
HA4 7TX. Tel. (089 56) 73265. (1034)

TIME WRONG?

MSF CLOCK IS ALWAYS CORRECT
- never gains or loses. SELF-SET-
TING at switch-on, 8 digits show
date, hours, minutes and seconds,
can expand to years, months and
milliseconds, auto GMT/BST and
leap year, also parallel BCD and au-
dio outputs, receives Rugby 60KHz
atomic time signals, built-in an-
tenna, 1000Km range, ABSOLUTE
TIME. £54.80.
V.L.F. 7 10-150KHz Receiver £13.70.
60KHz RUGBY RECEIVER, as in MSF
Clock, serial data output, £15.70.
Each fun-to-build kit includes all
parts, printed circuit, case, postage,
etc. money back assurance so GET
yours NOW.

CAMBRIDGE KITS
45 (WU) Old School Lane
Milton, Cambridge (1156)

SURPLUS STOCK

Omron Relays, Crouzet
Timing Motors, Crouzet Micro
Switches, Bulgin Lep and
Panel Lampholders, Transfor-
mers -

For details please write to or phone:
Mr. P. Givens
c/o R. G. MITCHELL LTD.
HEATHROAD, SKEGNESS, LINCS.
TEL: 0754 67373 (1184)

Belling & Lee L3000 Screened
Room, dimensions 24ft. x 16ft. x
12ft. Air conditioned with double
door and four shielded fluorescent
lights complete with 8 x 60 amp
filters and flooring, £1,000. Re-
erection can be arranged. Contact:
R. A. UPTON, F.C.A., 325 Clifton
Drive South, Lytham St. Annes,
Lancashire FY8 1HN. (1178)

HAVE YOU SEEN THE GREEN LIST?

1000s of components (radio, audio, CB
and electronic) and electronic items
and accessories at unbelievably low
prices, something for everyone. Send
25p for list and receive FREE RECORD
SPEED INDICATOR.
MYERS (Dept. W.W.)
14-16 Clifton Grove, Harehills, Leeds 9
(1167)

500 MHz SCOPE £100. HP185 samp-
ling scope, dual beam with high-z
probes, circuit diagrams, etc. Tel:
Bracknell 59435 (evenings). (1159)

RACAL COMMUNICATIONS RECEIVERS.
500kc/s 30mc/s in 30 bands 1MHz wide. RA17
£1.50. RA17L £200. Or a few as new £250.
RA117E £300, all air tested, supplied with full
manual, dust covers, in fair condition, new metal
louvered case for sets £25. RA98A SSB-USB adap-
tors, new and boxed with manual £75. RA98D
used with manual, £75. RA218 SSB-USB adaptors
and fine tune units for RA117 £65.
MARCONI SIGNAL GENERATOR TF801D/1 TO
8S £85 to £150.
MARCONI R.F. RADIATION & POWER METER.
OA1430 (CT477), as new, in grey metal case with
full manual, power meter FX range, 10mc/s to
10gc/s, complete with X-S-L band aerials, £50.
FERROGRAPH TAPE RECORDERS SERIES 4-5-6
and 7 - Mono and stereo. Series 4 to £6 £10 to
£20 ea. Series 7 £100 to £200 ea. Collected.
EXTEL TRANSEL MATRIX PRINTERS. 5 level
Baudot Code. Accepts speeds up to 300 bauds.
Supplied set to 50 and 75 bauds switched.
Tested with manual, £165.

All items are bought direct from H.M. Govern-
ment, being surplus eqpt. Price is ex-works.
S.A.E. all enquiries. Phone for appointment for
demonstration of any item. JOHNS RADIO,
WHITEHALL WORKS, 64 WHITEHALL ROAD,
BIRKENSHAW, BRADFORD. TEL. BRADFORD
684007 (9.30 a.m.-1 p.m.). (848)

THE SCIENTIFIC
WIRE COMPANY

ENAMELLED COPPER WIRE				
SWG	lb.	oz.	4oz.	2oz.
8 to 29	2.75	1.50	80	60
30 to 34	3.20	1.80	90	70
35 to 40	3.40	2.00	1.10	.80
41 to 43	4.75	2.60	2.00	1.42
47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	6.50	3.75	2.20	1.40
TINNED COPPER WIRE				
14 to 30	3.38	2.36	1.34	.90

Prices include P&P. VAT and Wire Data
SAE for list. Dealer enquiries welcome.
Reg Office: 22 Coningsby Gardens. (9063)

INVERTERS
High quality DC-AC. Also "no
break" (2ms) static switch,
19" rack. Auto Charger.



COMPUTER POWER SYSTEMS
Interport Mains-Store Ltd.
POB 51, London W11 3BZ
Tel: 01-727 7042 or 0225 310916 (9101)

LAB CLEARANCE: Signal Gener-
ators: Bridges: Waveform
transistor analysers: calibrators:
standards: millivoltmeters: dvna-
mometers: KW meters: oscillo-
scopes: recorders: Thermal, sweep.
low distortion true RMS audio FR.
deviation. Tel. 040-376238. (8250)

LAB TEST EQUIPMENT Clearance.
Environmental oven, Digivision
VDU, remote recording thermo-
meter, related instruments and
accessories, channel analyser trans-
ducer and thermocouple indicators.
View at Melksham Court, Stinch-
combe, Dursley, Glos. 0453 46446. (1161)

IBM MT 72 WORD PROCESSORS.
Incorporating a golf ball I/O type-
writer and magnetic tape cassette
memory module. Stop code search
and edit functions, margin control.
£375 plus VAT. Other ex-word pro-
cessor printers available. Autotype.
Tel: Haywards Heath (0444) 414484. (1176)

OSCILLOSCOPES, signal gener-
ators, DVMS, analysers, etc. for sale.
Real savings on new cost. Cash
also paid for good test equipment.
Tel: Hertford 50427. (1158)

TEKTRONIX 465 oscilloscope, mint
condition, calibrated, other test
equipment. Phone 0582-425721.

WIRELESS WORLD 1949 to 1979
inclusive good condition, offers.
Phone Stevenage (Herts) 2171. (1160)

Quartz Crystal Units
ACCURATE
RELIABLE
Private enquiries, send 13p in stamps for brochure
THE QUARTZ CRYSTAL CO. LTD.
J.C.C. WORKS, WELLINGTON CRESCENT,
NEW MALDEN, SURREY. 01-942 6334 & 2988.
(8492)

TELETEXT, TV SPARES & TEST
EQUIPMENT, TELETEXT. Latest
external unit kit incl. Texas XM11
Decoder 6101VML and infra-red
remote control £248, p/p £2.80 (fur-
ther details on request). Also MK1
external unit kit incl. Texas XM11
decoder, special offer price £168
p/p £2.80. Both kits incl. UHF
modulator, and plug into TV set
aerial socket. SPECIAL OFFER
TEXAS XM11 Decoder, new and
tested, limited quantity at 1/3 price,
£60 p/p £1.40. Stab. power supply
(5v) for Textext decoders, £5.80,
p/p £1. Thorn design XM11 inter-
face unit, £1.80, p/p 80p. NEW
SAW FILTER IF AMP PLUS TUNER
(complete & tested for sound &
vision), £28.50, p/p £1. COLOUR
BAR & CROSS HATCH GENERATOR
KIT (MK4) PAL, UHF aerial input
type, 3 vertical colour bars,
R-Y, B-Y, grey scale, etc. P/B con-
trols £35. Batt holders £1.50 or stab.
mains power supply kit £4.80. De-
luxe case £5.20 or alum. case £2.90,
p/p £1.40. Built & tested in De-luxe
case (battery) £58 (mains) £70, p/p
£1.60. CROSS HATCH KIT UHF
aerial input type also gives peak
white & black levels, batt. op. £11,
p/p 45p. Add-on GREY SCALE KIT
£2.90, p/p 35p. De-luxe case £5.20
UHF SIGNAL STRENGTH METER
KIT £17.50. Alum. case £1.80. De-
luxe case £5.20, p/p £1.40. CRT
TEST & REACTIVATOR KIT for
colour & mono £24.40, p/p £1.80.
COLOUR PANELS, large selection of
tested panels for popular makes
(part-ex in shop). TV SOUND IF
TRANSD. Tested, £6.80, p/p 85p.
BUSH SURPLUS IF PANELS. A816
£1.80. TV312 (single I.C.) £5. Z718/
BC6100 £5. A823 (Exp) £2.80, p/p
85p. BUSH 161 series TB panel A634
£2.80, p/p £1.20. GEC Series 1 mono
panels, £1.80, p/p £1.30. GEC 2040
CDA panel £4.50, p/p £1.20. PHILIPS
G6 S/S conv. panel £2.50, p/p £1.20.
G8 Decoder panels for spares £1.80,
p/p £1.20. G9 Signal panels for
small spares £3.80, p/p £1.20.
THORN 3500 Line TB panel £5, p/p
£1. 3000 ex-renal panels IF, VIDEO,
DECODER, £5, p/p £1.20. 8000/8500/
9000 Decoders Salvaged £7.50, p/p
£1.60. 9000 Line TB (incl. LOPT)
salv/spares £7.50, p/p £1.60.
VARICAP UHF TUNERS. Mullard
U321 £6.80. ELC1043/06 £6.80.
ELC1043/05 £5.50. G.1. £3.50. Salv.
(asstd) £1.50, p/p 60p. Varicap UHF/
VHF ELC2000S £8.50. Bush (dual)
£7.50, p/p 70p. TOUCH TUNE CON-
TROL units. Bush (6 pos) £4.50, p/p
80p. VARICAP CONTROL UNITS 3
pos. £1.20, 4 pos. £1.50, 5 pos. £1.80,
6 pos. £1.80, 8 pos. special offer £1,
p/p 45p. UHF transd. Tuners
(rotary) incl. s/m drive £2.50, 4
pos. P/B £2.50, 6 pos. P/B £4.20,
p/p £1.20. (Special types available,
details on request). DL50 Delay
Line £2.50, p/p 50p. Large selection
of LOPTS, Triplers, Scancells, Mains
Droppers, and other spares for
popular makes of colour and mono
receivers. PLEASE ADD 15% VAT
TO ALL PRICES. MANOR SUP-
PLIES, 172 WEST END LANE, WEST
HAMPSTEAD, LONDON, N.W.6.
SHOP PREMISES, Tel. 01-794 8751,
794 7346. Easily accessible W.
Hampstead Jubilee Tube & Brit.
Rail N. London (Richmond-Broad
St.) and St. Pancras-Bedford. Buses
28, 159, 2, 13. Callers welcome.
Thousands of additional items not
normally advertised available at
shop premises. Open daily all week
incl. Saturday (Thursday half day).
MAIL ORDER: 64 GOLDERMANOR
DRIVE, LONDON, NW11 9HT.
PLEASE ADD 15% VAT to all
prices. (60)

ARTICLES FOR SALE

MARCO TRADING TRANSFORMERS

Table with 5 columns: Primary, Secondary, Current, 1+, 10+, 100+. Rows include 240v, 240v, 240v, 240v, 240v.

EUROPEAN ADAPTORS

Manufacturers note: We can supply FROM STOCK 1,000+ quantities of the above transformers.

Table with 5 columns: Ref., DC Voltage, Current, 1+, 10+, 100+. Rows include EOB, EM3, EO9, ET4.

Manufacturers/Suppliers please note. We can supply from stock 1,000 and quantities of the above European adaptors.

MARCO TRADING

Dept. WW1, The Old School, Edstaston, Wem, Shropshire, SY4 5RJ. Tel. Whixall (094872) 464/465

F.R.G. GENERAL SUPPLIES LTD.

March 27, 1981. HP740R. DC standard/differential voltmeter, designed for calibrating digital voltmeters.

BRAND NEW VERO RACKS

5 1/2in, complete with 20 off 40 way edge connectors (only 6 used), 20 card slides and locking front panel.

SERVICES

FACILITIES AVAILABLE

- Circuit Design & Development
Digital and Analogue
Artwork Layout
Free prototype bd. (non PTH)

One or all services available, no order too small. Please telephone Chelmsford 357935 or write to H.C.R. 1 Bankside, off New Street, Chelmsford, Essex.

CAPACITY AVAILABLE

PCB ASSEMBLY CAPACITY AVAILABLE

Low or high volume, single or double sided, we specialise in flow line assembly of printed circuit boards.

Using the Zevatron flow soldering system and on line lead cutting, we are able to deliver high quality assemblies on time, and competitively priced.

Find out how we can help you with your production. Phone or write. We will be pleased to call on you and discuss your requirements.

TW ELECTRONICS LTD.

120 NEWMARKET ROAD BURY ST. EDMUNDS, SUFFOLK TEL: 0284 3931

Sub-contract assemblers and wireers to the Electronics Industry (9068)

ELECTRONIC DESIGN SERVICE. Immediate capacity available for circuit design and development work, PC artwork, etc.

COMPARE our charges, quality and turnaround for printed board artworks, assembly, test and prototype manufacture.

SERVICES

CIRCOLEC

THE COMPLETE ELECTRONIC MANUFACTURING SERVICE. Let us realise all or any part of your project from prototypes to production.

Free Offer! Ring for details of a free introductory offer to our sub-contract PCB assembly service.

CIRCOLEC FREEPOST (no postage required) London SW17 8BR Telephone: 01-767 1233

P.C.B. MANUFACTURE AND ASSEMBLY

Wave Soldering and inspection. High-quality PCBs from your artwork. Prototype design. Artwork from your circuit.

SMALL BATCH PCB'S produced from your artwork. Also DIALS, PANELS, LABELS. Camera work undertaken. FAST TURNAROUND.

ELECTRONIC DESIGN SERVICES. MICROPROCESSOR HARDWARE and SOFTWARE design facilities have now been added to our established expertise.

PROTOTYPE ELECTRONIC design, development, construction. One-off and small batch production to drawings.

I.H.S. SYSTEMS

Due to expansion of our manufacturing facilities we are able to undertake assembly and testing of circuit boards or complete units in addition to contract development.

We can produce, test and calibrate to a high standard digital analogue and RF equipment in batches of tens to thousands.

Telephone to arrange for one of our engineers to call and discuss your requirements, or send full details for a prompt quotation.

TEL. 01-253 4562

or reply to Box No. WW 8237 (8237)

PCB ARTWORK DESIGN SERVICE with component notation masters and assembly drawings. PADS Electrical Ltd, 01-850 6516, 45 Southwood Road, New Eltham SE9. (7905)

BATCH PRODUCTION wiring and assembly to sample or drawings. McDeane Electricals Ltd, 19b Station Parade, Ealing Common, London W5. Tel: 01-992 8976. (169)

P.C.B.s WIRING assembly looms, coils, instruments, quality design prototype and production service in house or on site. - Batvale Ltd Ely (0353) 778756. (982)

BOARDRAVEN LTD.

PRINTED CIRCUIT BOARDS

Manufactured to your specifications. Single/double sided. Very speedy deliveries on prototypes and quantity. Master layouts if required.

SHEET METAL WORK, fine or general front panels chassis, covers, boxes, prototypes. 1 off or batch work, fast turnaround. 01-449 2695. M. Gear Ltd., 179A Victoria Road, New Barnet, Herts. (812)

DESIGN AND DEVELOPMENT. ANALOGUE, DIGITAL, RF AND MICROWAVE CIRCUIT AND SYSTEM DESIGN. Also PCB design, mechanical design and prototype/small batch production.

NOT JUST a PCB assembly service specialising in large boards, carrying upwards of 500 components, but a broad based manufacturing facility that includes control panel fabrication using any combination of technologies from "chips" and triacs to relays and motor contactors.

BUSINESS FOR SALE

FOR SALE

Long Established

FULLY EQUIPPED TV TUBE REBUILDING PLANT

Own Freehold Factory Building. Customs delivery van, land for expansion. Would suit group buyers, or rental company, to produce own tubes of following types Colour, Delta - Inline - Mono - 20mm Portable. Present stock of tubes. Owner wishes to retire. No reasonable offer refused.

Replies: Box No. 1041 (1041)

EQUIPMENT WANTED

TO ALL MANUFACTURERS AND WHOLESALERS IN THE ELECTRONIC RADIO AND TV FIELD

BROADFIELDS & MAYCO DISPOSALS

Will pay you top prices for any large stocks of surplus or redundant components which you may wish to clear. We will call anywhere in the United Kingdom.

21 LODGE LANE NORTH FINCHLEY, LONDON N12 8JG Telephone Nos. 01-445 0749/445 2713 After office hours 958 7624 (9123)

SERVICES

PRINTED CIRCUIT BOARDS

Manufactured, any quantity, competitive prices, roller tinned, photographic and artwork services available.

MAYLAND PCB CO. LTD. 4 The Drive Maylandsea, Chelmsford, Essex Tel: 0621 741560 (997)

PRINTED CIRCUIT MANUFACTURE. Very fast, reliable service. Lowest prices. Prototypes welcome. Inhouse photography. Phone 0674-573 for instant quote or write to AKRONICS Ltd., 42/44 Ford Street, Moretonhampstead, Devon. (9857)

Phone your Classifieds

to JAYNE PALMER

on 01 661 3033

COURSES

CCAT CAMBRIDGESHIRE COLLEGE OF ARTS AND TECHNOLOGY

Courses in Electronics

BSc IN ELECTRONIC ENGINEERING

A four year part-time degree course for mature students. Of particular interest to those engaged in Digital, Telecommunications or Control Systems.

CEI PART II

One year full-time or two years part-time course in preparation for the CEI Part II examination which is the present academic qualification for Chartered Engineers.

Further details and application forms are available from the Information Office, Room H268, Cambridgeshire College of Arts and Technology, Cambridge, CB1 2AJ. Telephone (0223) 63271. (1026)

CLASSIFIED ADVERTISEMENTS

Use this Form for your Sales and Wants

PLEASE INSERT THE ADVERTISEMENT INDICATED ON FORM BELOW

To "Wireless World" Classified Advertisement Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS

- Rate £2 PER LINE. Average six words per line. Minimum £10 (prepayable).
Name and address to be included in charge if used in advertisement.
Box No. Allow two words plus £1.
Cheques, etc., payable to "IPC Business Press Ltd." and cross "& Co."

Table with 10 columns and 10 rows for advertisement classification and insertion tracking.

PLEASE WRITE IN BLOCK LETTERS. CLASSIFICATION NUMBER OF INSERTIONS. REMITTANCE VALUE ENCLOSED

SAFGAN presents **DT-400** series from **£169 + VAT**
 HIGH-QUALITY **DUAL TRACE** OSCILLOSCOPES
A BRITISH PRODUCT EVERYONE CAN AFFORD

Model DT-410 DUAL TRACE 5mv/div 10MHz @ **£169 + VAT**
 Model DT-412 DUAL TRACE 5mv/div 12MHz @ **£175 + VAT**
 Model DT-415 DUAL TRACE 5mv/div 15MHz @ **£188 + VAT**

SPECIFICATION FOR ALL MODELS

- * CH1, CH2: 5mv/div - 20v/div in 12 col 1-2-5 steps. Input impedance 1MΩ + 22pF
- * BANDWIDTH: 10MHz (DT-410), 12MHz (DT-412), 15MHz (DT-415)
- * TIME BASE: 0.5μs/div - 200ms/div in 18 cal steps
 X5 Expansion to 100 ns/div
 X5 Multiplier to 15/div
- * XY FACILITY: Matched Inputs X = CH1, Y = CH2
- * TRIGGER: Level Control, ± Slope, Bright Line AUTO, NORMAL, TV Triggering CH1, CH2 0.5 div, EXT Trig 100mv
- * Z Modulation
- * Cal output/probe compensation.
- * Graticule blue ruled 8 × 10 div (6.4 × 8cm²)
- * SIZE: H215mm W165mm D280mm Weight 4.5 kg.
 PROBE (X1-REF-X10) **£11.50 + V.A.T.**

Orders to: **SAFGAN ELECTRONICS LTD.** (Goods + 15% + £3.50 P&P). Or £6.50 parcel service
56 Bishop's Wood, St. John's, Woking, Surrey, GU21 3QB Tel: Woking 69560 or Woking 66836
 London Stockist: Audio Electronics, Edgware Road, London. Tel. 01-724 3564

DT-400 Series

WW - 050 FOR FURTHER DETAILS

INDEX TO ADVERTISERS JULY

Appointments Vacant Advertisements appear on page 119-127

PAGE	PAGE	PAGE
Ambit International 22, 23	Galatrek International 24	Pascal Electronics Ltd. 102
Amplivox Ltd. 109	Global Specialties Corporation 27	PBRA Ltd. 106
Analogue Associates 56	G P Industrial Electronics Ltd. 18, 102	PM Components Ltd. 95
Anglia Components 112	Guide to Broadcasting Stations 118	Powertran Electronics 85
Antex Electronics Cover iii		Practical Computing 107
ASA Ltd. 112	Hall Electric Ltd. 2	P&R Computershop 101
Audio Electronics 16	Happy Memories 100	Racal Recorders Cover ii
Avel Lindberg Ltd. 106	Harris Electronics (London) Ltd. 22	Radio Component Specialists 103
Bach-Simpson (U.K.) Ltd. 116	Harrison Brothers 96	Ralfe, PF Electronics 115
Bamber, B. Electronics 90	Hart Electronic Kits Ltd. 98	Reprints 102
Barrie Electronics Ltd. 105	Hasbrook Trading 110	RST Valve 91
Bayliss, A.D. and Sons Ltd. 107	Henry's Radio 92, 96, 109	
B D S Microsystem Designs Ltd. 68	Horst F.G. Angermann 87	Safgan Electronics Ltd. 128
Brewster, S&R Ltd. 26	HiFi Yearbook 1981 116	Sagin, M. R. 104
Carston Electronics Ltd. 21		Sandwell Plant Ltd. 98
Catronics Ltd. 96	ILP Electronics Ltd. 88, 89	Scopex Instruments 113
Chiltern Electronics 107	ILP Transformers Ltd. 101	Service Trading Co. Ltd. 28
Chilmead Ltd. 97	IMO 13	Shure Electronics Ltd. 68, 69
CIL Electronics Ltd. 20, 92	Interface Quartz Devices Ltd. 11	Siemens Ltd. 14, 15
Clark Masts Ltd. 17	Intergrex Ltd. 10	Sinclair Research Ltd. 20
Clef Products (Electronics) Ltd. 101	Irvine Business Systems 69	Sonimag 19 96
Colomor Electronics Ltd. 92		Southern Electronics 94
Crotech Instruments Ltd. 112	Keithley Instruments Ltd. 19	Sowter, E. A. Ltd. 94
Crimson Elektrik 87	Kelsey Acoustics Ltd. 106	Special Products Distributors Ltd. 86
CT Electronics (Acton) Ltd. 111, 117	Langrex Supplies Ltd. 91	Strutt Ltd. 68, 109, 116
Darom Supplies 90	Levell Electronics Ltd. 3	Surrey Electronics 98
Danavox (Gt. Britain) 108	Maplin Electronic Supplies Ltd. 25	Technomatic Ltd. 99
Digi-Tel Electronics 94	Marshall, A. (London) Ltd. 20	Television 86
Disk Offer 69	MCP Electronics 23	Teloman Products Ltd. Cover iv
Display Electronics 93	Micro Times 105	Tempus 110
Dutchgate Ltd. 110	Midwich Computer Co. Ltd. 17	Thurby Electronics Ltd. 106
Electronic Brokers 4, 5, 6, 7, 9, 11	Mills, W. 96	Titan Transformers 12
Electronic Equipment Co. 107	Milward, G.F. Electronic Components Ltd. 86	
Electro-Tech Components Ltd. 100	MTL Microtesting Ltd. 20	Valradio Ltd. 90
Electrovalue Ltd. 87		West Hyde Development Corp. 9
Electricity Supply Hand Book 1981 115	Newbear 104	West London Direct Supplies 86
Electrical Review Shock Charts 114	Northern Electronics 22	Wilmslow Audio 8
Faircrest Engineering Ltd. 92	OK Machine and Tool UK Ltd. 12	Zaerix Electronics Ltd. 24
Farnell Instruments Ltd. 55, Reader Card	OMB Electronics 11	
Fyde Electronic Laboratories Ltd. 100	Orion Scientific Products Ltd. 22, 68	

OVERSEAS ADVERTISEMENT AGENTS:
France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.
Hungary: Mrs Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget.
 Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE
Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan.
 Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106.
 Telephone: (03) 585 0581.
United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 - Telephone: (212) 867-2080. Telex: 238327.
 Mr Jack Farley Jr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone: (312) 63074.
 Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.

Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone: (216) 621 1919.
 Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone: (305) 532 7301.
 Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432.
 Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.
Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.
 * Also subscription agents.

Plugin* for Fingertip Control!

take the heat out of a delicate situation.

Ready to use Antex new model XS-BP soldering iron comes with a fitted plug, ready to switch on.

The new handle in extra-tough material features a detachable finger-guide for precise control in operation and a hexagonal moulding to prevent the iron rolling on the work bench.

We have retained our well-proven heating element. Efficiency of heat transfer and ease of fitting slide-on, slide-off bits make this the professional's choice of soldering instrument. The iron is also available for 115, 50, 24 or 12 volt.

* fitted with the NEW safety plug.

Send now!

ANTEX (ELECTRONICS) LIMITED
 MAYFLOWER HOUSE, ARMADA WAY, PLYMOUTH, DEVON TELEPHONE 0752 667377 · TELEX 45296

R S P MODEL X5-BP (25 WATTS £5.30)
 MODEL CS-BP (17 WATT £5.30 + VAT)

Please send the ANTEX New Range full colour brochure to: NAME _____

ADDRESS _____

WW7

WW-002 FOR FURTHER DETAILS

PROFESSIONAL TOOLCASES for Service Engineers

£43.70
inc. VAT

£39.90
inc. VAT

Size TL100 19" x 14" x 6"



The TL99 and TL100 are designed for the Professional Electronics, TV or Instrument Technician who needs to carry a large number of specialist tools. Constructed from hard wearing ABS with strong aluminium frames, twin handles and toggle locks. They offer a moulded tray in the base, a comprehensive 2 sided tool pallet that's reversible with space for up to 40 tools. — The TL100 will take quite a few more. There's space for documents and a heat sink for a hot soldering iron to prevent any damage being caused.

TLW4 Toolwallet measures 11" x 14" x 2½" when closed. Made from reinforced PVC with a heavy duty industrial zip. The TLW4 Toolwallet is a compact alternative when only tools are needed to be carried.

Size TL99 17" x 12" x 6"

£13.75
inc. VAT

Mail Order

Please send

Enclosed my cheque **£** .
(P&P £2.60 extra)

Name _____

Company _____

Address _____

Tools NOT included. British made.
Money back guarantee. Allow 7-21 days for delivery.



TLW4

Teloman Products Ltd
Ermine House, Post St, Godmanchester, Cambs. PE 18 8BA (0480) 65534