

Wireless
Special

AUGUST 1992 70p

wireless world


**Receiving
Meteosat II**

**Computing
insertion loss**

**Circuit
modelling by
home computer**

Australia A\$ 2.30
Canada C\$ 3.25
Denmark DKK 28.25
Germany DM 6.50
Greece DRG 160.00
Holland Dfl. 8.00
Italy L 3100
Norway Nkr. 24.00
Singapore S\$ 5.50
Spain Ptas 240.00
Switzerland Fr. 6.50
U.S. \$ 3.75

wireless world

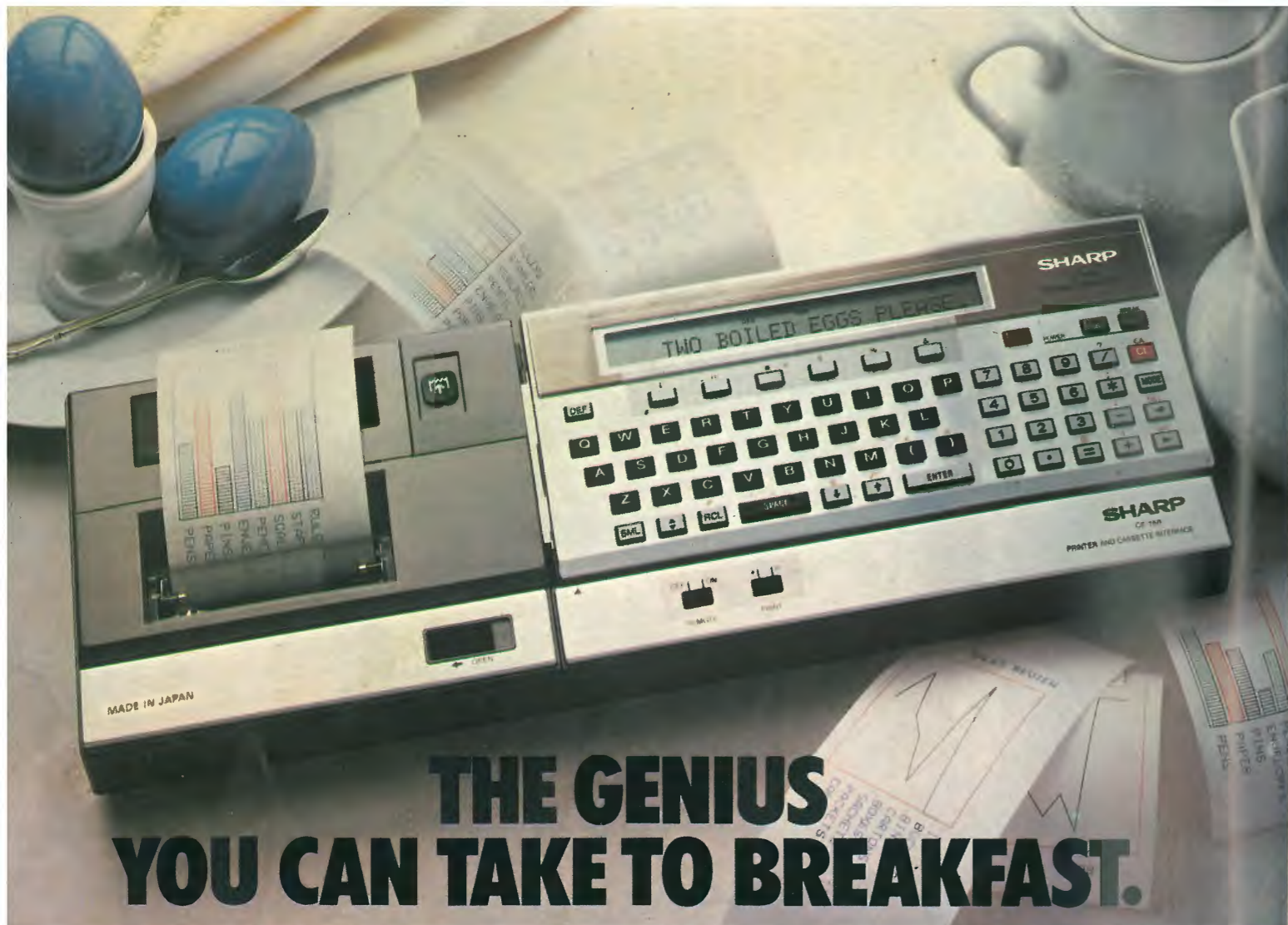

THE GENIUS YOU CAN TAKE TO BREAKFAST.

Now, at last, real portable computer power. The new Sharp PC 1500 pocket computer. A pocket-sized genius that will travel with you to conferences, seminars and business breakfasts.

The PC 1500 has the capacity and BASIC language usage that is very nearly that of the desk-size Personal Computer. When fitted with the optional 4-colour graphic printer, it is one of the most powerful pocket computers on earth.

Chores can be handled swiftly and accurately any time of day, wherever you happen to be. Estimates, records and charts of sales, billings and other important data can be re-programmed, calculated and summoned

at the touch of a button. It can even play blackjack, analyse your biorhythms or give you a beeped reminder of a scheduled meeting.

Large memory capacity, up to 11.5K bytes. 4-colour print-out. Six user-programmable keys. The incredible new PC 1500. A revolution in pocket computers.

From Sharp. Where great ideas come to life.

SPECIFICATIONS PC 1500 Pocket Computer

CPU	C-MOS 8-bit CPU
Capacity	ROM: 16K bytes RAM: 3.5K bytes to 11.5K bytes

CE 150 Colour Graphic Printer/Cassette Interface (Optional)

Printing Digits	Standard 18 digits (36,18,12,9,7,6,5,4 digits selectable)
Printing System	X-Y axis plotter system
Printing colours	Red, blue, green, black
Printing directions	Right, left, up, down
Cassette Interface	Up to two cassette tape recorders can be connected.

Please send details of the Sharp PC 1500

Type of application: _____

Name: _____

Address: _____

The world of
SHARP
where great ideas come to life.

Sharp Electronics (UK) Ltd, Computer Division, Sharp House, Thorp Road, Newton Heath, Manchester M10 9BE. Telephone: 061-205 2333



Design and specifications subject to change without notice.

WW-003 FOR FURTHER DETAILS

WIRELESS WORLD AUGUST 1982 VOL 88 NO 1559

Receiving Meteosat II

Computing insertion loss

Circuit modelling by home computer

Australia \$2.40
Canada \$2.50
Denmark DKK 28.25
Germany DM 6.50
Greece DRG 160.00
Holland GFL 8.00
Italy L 3100
Norway NKR 24.00
Singapore S\$ 5.50
Spain Ptas 240.00
Switzerland FR 6.50
U.S.A. \$3.75



Autostore.

Low-cost voice-logging for people with more important things to do.

The problem: logging telephone and radio messages without spending a fortune on equipment or hiring an expensive technician to operate it.

The solution: the new Racal Recorders Autostore.

SIMPLICITY
With its automatic cassette-loading and fully automatic changeover from one deck to another, Autostore can—quite literally—be operated by whoever happens to be around.


And it provides over 24 hours of unattended continuous recording on eight channels.

VERSATILITY
Able to log radio and telephone messages simultaneously, Autostore can form part of a new system—or fit just as easily into an existing one.

And its uses vary from ambulance, fire, police and security applications to the recording of financial transactions, conferences, oil installation communications and taxi services.

Racal Recorders

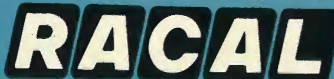Racal Recorders Limited, Hardley Industrial Estate, Hythe, Southampton, Hampshire SO4 6ZH, England.
Tel: (0703) 843265 Telex: 47600



RELIABILITY
Available in 4 or 8 channel versions, and with integral micro-processor controlled automatic Timesearch capability to enable rapid message retrieval, Autostore is engineered to the very highest standards by the company which pioneered air traffic control recording techniques.

FULL DETAILS
For full details of Autostore send off the coupon today.

I am interested in recording my communications accurately and reliably. Please:

- send me full details of Autostore
- arrange for a demonstration at my own premises

Name _____
Position _____
Company _____
Address _____
Tel: _____

Racal Recorders Limited, Hardley Industrial Estate, Hythe, Southampton, Hampshire SO4 6ZH, England.

WW

WW-001 FOR FURTHER DETAILS



Front cover is a montage of an electronic watch circuit superimposed on an Aztec calendar wheel. Picture by Paul Brierley.

NEXT MONTH

Eprom emulator/programmer – enables program evaluation without constant alteration of eprom. When testing is finished, emulator transfers its contents to eprom.

Selective call for c.b. radio – allows keypad-generated data frame to modulate c.b. carrier and call designated receiver.

Simple low-frequency oscilloscope – suitable for audio work. Vertical bandwidth is 1MHz at 50mV/cm – triggered or free-running sweep. Costs around £40.

Current issue price 70p, back issues (if available) £1, at Retail and Trade Counter, Units 1 & 2, Bankside Industrial Centre, Hopton Street, London SE1. Available on microfilm; please contact editor.

By post, current issue £1.6p, back issues (if available) £1.50, order and payments to EEP General Sales Dept., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Editorial & Advertising offices: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.

Telephones: Editorial 01-661 3500. Advertising 01-661 3130.

Telegrams/Telex: 892084 BISPRS G. **Subscription rates:** 1 year £12 UK and £15 outside UK.

Student rates: 1 year £8 UK and £10 outside UK.

Distribution: Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. Telephone 01-661 3500.

Subscriptions: Oakfield House, Perry-mount Road, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Please notify a change of address.

USA: \$39 surface mail, \$98.30 airmail. US subscriptions from IPC B.P. Subscriptions Office, 205 E. 42nd Street, NY 10017.

USA mailing agents: Expeditors of the Printed Word Ltd, 527 Madison Avenue, Suite 1217, New York, NY 10022. 2nd-class postage paid at New York.

© IPC Business Press Ltd, 1982 ISSN 0043 6062

ELECTRONICS
BROADCASTING
AUDIO

wireless world

COMMUNICATIONS
COMPUTING
VIDEO


AUGUST 1982 Vol 88 No 1559

- 27 BY ANY OTHER NAME**
- 28 80-100w MOSFET AUDIO AMPLIFIER**
by J. L. Linsley Hood
- 33 DISC DRIVES**
by J. R. Watkinson
- 37 ELECTROMAGNETIC ANALOGY**
by W. A. Scott Murray
- 40 CIRCUIT MODELLING BY MICROCOMPUTER**
by R. I. Harcourt
- 43 DIGITAL DIVIDERS WITH SYMMETRICAL OUTPUT**
by Cornelius van Kolten
- 47 DIGITAL FILTER DESIGN**
by B. M. C. Cheetham and P. M. Hughes
- 53 MICROCOMPUTER LINE PRINTER**
by P. L. Woods
- 57 LETTERS**
- 61 METEOSAT HIGH-RESOLUTION IMAGES**
by M. L. Christleson
- 65 NEWS OF THE MONTH**
- 68 CIRCUIT IDEAS**
- 70 COMMUNICATIONS**
- 72 NETWORK ANALYSIS WITH A ZX81**
by L. E. Weaver
- 75 COST-EFFECTIVE ELECTRONIC IGNITION**
- 76 DESIGNING WITH MICROPROCESSORS**
by D. Zissos and Jane Pleus
- 79 ELECTRIC FIELDS IN SOLENOIDAL COILS**
by F. S. Chute and F. E. Vermeulen
- 81 NEW PRODUCTS**



AMCRON INDUSTRIAL MUSCLE

- ★ POWER RESPONSE DC - 45KHz ± 1dB.
- ★ OUTPUT POWER IN EXCESS OF 1.5KW INTO 2.75 Ohm LOAD (CONTINUOUS R.M.S.)
- ★ D.C. OUTPUT 20 AMPS AT 100 VOLTS OR 2KVA.
- ★ HARMONIC DISTORTION LESS THAN 0.05% DC-20KHz AT 1kW INTO 6 OHMS.
- ★ PLUG-IN MODULES: CONSTANT VOLTAGE/CURRENT, PRECISION OSCILLATORS.
- ★ UNIPOLAR AND BIPOLAR DIGITAL INTERFACES, FUNCTION GENERATORS, AND MANY OTHERS.
- ★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD.
- ★ FULL OPEN AND SHORT CIRCUIT PROTECTION GUARANTEED STABLE INTO ANY LOAD.
- ★ TWO UNITS MAY BE CONNECTED TO PROVIDE UP TO 4kW.
- ★ INTERLOCK CAPABILITY FOR UP TO EIGHT UNITS.
- ★ 3-YEAR PARTS AND LABOUR WARRANTY.
- ★ UNITS AVAILABLE FROM 100VA-12KVA.

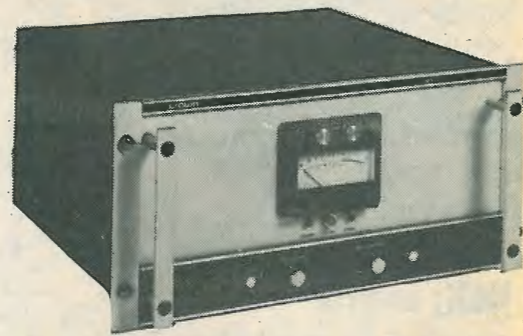

Model - M600

For full details on all Amcron Products write or phone Chris Flack

P.O. BOX 3
ATTLEBOROUGH
NORFOLK NR17 2PF
Tel: 0953-452477

Analogue Associates

PROFESSIONAL INDUSTRIAL ELECTRONICS

WW - 026 FOR FURTHER DETAILS

INSTANT PRINTED CIRCUITS!!

Make your own - to professional standards - within minutes using either "Fotolak" Light-sensitive Aerosol Lacquer or Pre-coated board. No Darkroom or Ultra-violet source needed!

Fotolak aerosol £2.50 (30p) Developer £0.30 (15p)
Ferric Chloride £0.60 (45p) Acetate Sheet £0.15 (15p)

Copper-clad Fibre-glass Boards: Single-sided £2 ft. sq. (45p)
Double-sided £2.25 ft. sq. (60p)

Pre-coated Fibre-glass Board:
8'x4 1/2' £1.75 (25p) 16'x9' £7 (60p) 24'x18' £18 (£1.70)
8'x9' £3.50 (45p) 24'x12' £13 (£1.20) Eurocard £1.25 (25p)

Double-sided Board (all sizes) add 20%
Postage individual items in brackets. Maximum charge £2 per order.

WHITE HOUSE ELECTRONICS
P.O. Box 19, Praa Sands, Penzance TR20 9TF
Telephone: Germoe (073-676) 2329

TV TUBE REBUILDING

Faircrest Engineering Ltd. manufacture a comprehensive range of equipment for processing all types of picture tubes, colour and mono. Standard or custom built units for established or new businesses. We export world-wide and have an excellent spares service backed by a strong technical team.

Full training courses are individually tailored to customers' requirements.

For full details of our service contact Neil Jupp

FAIRCREST ENGINEERING LTD.

4 Union Road, Croydon, CR0 2XX
01-684 1422/01-684 0246

WW - 059 FOR FURTHER DETAILS



L&J COMPUTERS

192 HONEYPOT LANE, QUEENSBURY, STANMORE, MIDDX HA7 1EE. 01-204 7525

THE "PET" SPECIALISTS

4016 16K Computer	£460
4032 32K Computer	£575
2031 171K Single Drive Floppy Disk	£350
4040 343K Dual Floppy Disk	£575
4022 Tractor Feed Printer	£350
8032 32K Computer	£750
8096 96K Computer	£995
8050 950K Dual Drive Floppy Disk	£750
8023 Tractor Feed Printer	£750
8422 22 Megabyte Winchester Disk	£3250
9000 SuperPet 134K Multilanguage Computer	£1295

WE HAVE A DAZZLING ARRAY OF CONNECTIONS WITH THE OUTSIDE WORLD! D TO A CONVERTERS (8, 12 & 16 BIT) A TO D CONVERTERS RESOLUTIONS X/Y PLOTTERS (A3 SIZE UPWARDS) DIGITAL INPUTS/OUTPUTS RS 232: IEEE: CENTRONIC INTERFACES

AS WELL AS BUSINESS SOFTWARE, WE ALSO CAN SUPPLY ENGINEERING REQUIREMENTS, LIKE: DATA ANALYSIS/STATISTICAL PACKAGES TAPEPREP FOR ONC MACHINE TOOLS SECTION CALCULATIONS FOR DRAWING OFFICES ANALYSIS FOR CONTROL SYSTEMS

COME AND SEE THE NEW VIC-20 £165



FULLY WORKING AND OPERATIONAL ASK US ABOUT ALL THE ADD-ON-GOODIES THAT GO WITH THE VIC

MASSSES OF BOOKS ON THE PET & VIC + INTERFACING & CONTROL

SEND US A LARGE STAMPED ADDRESSED ENVELOPE (12x9) AND WE WILL BE DELIGHTED TO SEND YOU ALL OUR CURRENT INFORMATION!


* PRICES DO NOT INCLUDE VAT

ALL GOODS SENT SAME DAY WHEREVER POSSIBLE
LARGE S.A.E. FOR LISTS ETC.



WW - 035 FOR FURTHER DETAILS

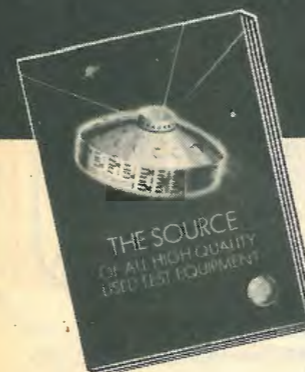THE SOURCE OF ALL HIGH QUALITY USED TEST EQUIPMENT



Electronic Broker's new catalogue of current Used Test Equipment is hot off the press. Send for your FREE copy now!

Name

Company

Address


Position

Department Tel No

Post To: Electronic Brokers Ltd., 61/65 Kings Cross Road, London WC1X 9LN, Tel: 01-278 3461. Telex 298694


WW-200
FOR FURTHER DETAILS

Hilomast Ltd

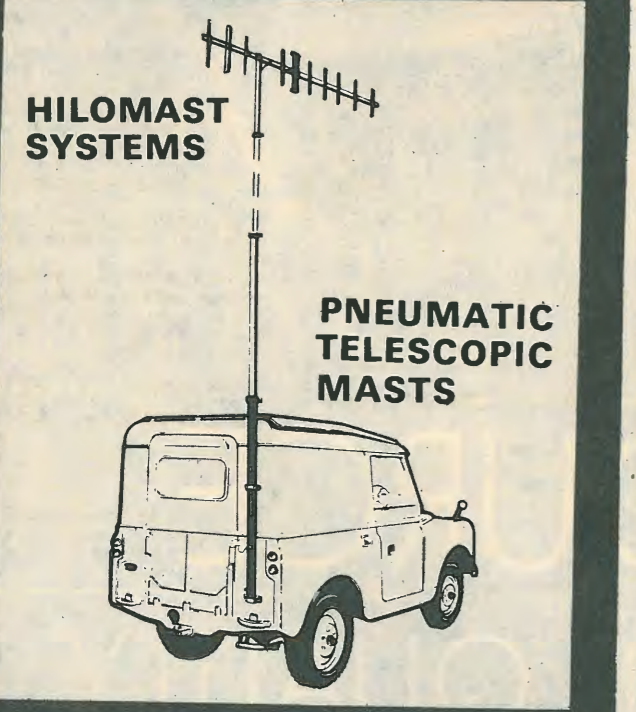

HILOMAST SYSTEMS

PNEUMATIC TELESCOPIC MASTS

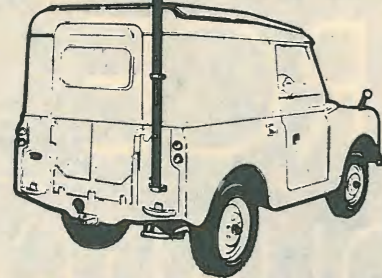

HILOMAST LIMITED
THE STREET HEYBRIDGE — MALDON
ESSEX CM9 7NB ENGLAND
Tel. MALDON (0621) 56480
TELEX NO. 995855

WW - 015 FOR FURTHER DETAILS

Toroidal Transformers

THE COTSWOLD "BUDGET RANGE" OFFERS BUILT-IN QUALITY COUPLED TO A RELIABLE DELIVERY SERVICE MOST TYPES FROM STOCK

IEC 65
VDE 0550
BS 415
TO ORDER

PHONE
TELEX, WRITE
FOR DATA SHEET
AND PRICE LIST

Budget Range Stockist
BARRIE ELECTRONICS LTD.
3 The Minories, London EC3N 1BJ. 01-488 3316

Cotswold Electronics LTD.

Unit T1, Kingsville Road, Kingsditch Trading Estate, Cheltenham GL51 9NX
Tel: 0242-41313 Telex: 897106

WW - 040 FOR FURTHER DETAILS

RADIATION DETECTORS

BE PREPARED VIEW THRU LENS

Ideal for the experimenter

- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH
- 0-5 R

British design & manufacture.
Tested and fully guaranteed. Ex-stock delivery.
As supplied to Fire Services/Civil Defence

HENRY'S Official Orders welcome
01-723 1008/9

CALLERS: 404 EDGWARE ROAD, LONDON W2 1ED
Mail Orders/Export Enquiries to: 11-12 Paddington Green, London W2

£6.95
FREE RECHARGE SERVICE AFTER PURCHASE
Add. VAT, Post & Packing Costs
COMPLETE WITH DATA

CLEF ELECTRONIC MUSIC

PIANOS SPECIALISTS SINCE 1972 DOMESTIC OR STAGE SIX OR 7 1/4 OCTAVES KITS OR MANUFACTURED

The most advanced form of touch-sensitive action simulating piano key inertia by patented technique.

Four mixable voices for serious tone variation plus electronic chorus and flanger effects.

Component Kits include Keyboard.

Full Kits further contain: Cabinets, Harness, Power Amp and Speaker.

Domestic Prices

£	SIX	7 1/4
Comp	234	266
Full	398	442
MFD	620	695

Kit £314
Mfd £439

BAND-BOX An Electronic Backing TRIO. Drums, Bass & Chord Instrument. User Programmable for 50-100 scores, using microprocessor.

MASTER RHYTHM User Programmable DRUM MACHINE. Twenty-four patterns. Eight parallel tracks. Twelve instruments sequence operation.

Write or Phone for full details of our range of high quality Kit and manufactured Electronic Musical Instruments. Prices include V.A.T., Carr., & Ins. and we operate Telephone BARCLAY-CARD/ACCESS.

Competitive EXPORT Quotations given.

CLEF PRODUCTS (ELECTRONICS) LIMITED
Dept. W. 44a Bramhall Lane South
Bramhall, Stockport, Cheshire SK7 1AH
061-439 3297

WW - 044 FOR FURTHER DETAILS

TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

★ 294 TYPES TO CHOOSE FROM!
★ ORDERS DESPATCHED WITHIN 7 DAYS OF RECEIPT FOR SINGLE OR SMALL QUANTITY ORDERS
★ 5 YEAR NO QUIBBLE GUARANTEE

TYPE	SERIES No.	SECONDARY Volts	RMS Current	PRICE
30 VA 70x30mm 0.45Kg Regulation 18%	1x010	6+6	2.50	£5.12 +p/p £1.04 +VAT £1.92 TOTAL £7.08
	1x011	9+9	1.66	
	1x012	12+12	1.25	
	1x013	15+15	1.00	
	1x014	18+18	0.83	
	1x015	22+22	0.68	
	1x016	25+25	0.60	
1x017	30+30	0.50		
50 VA 80x35mm 0.8Kg Regulation 13%	2x010	6+6	4.16	£5.70 +p/p £1.30 +VAT £1.05 TOTAL £8.05
	2x011	9+9	2.77	
	2x012	12+12	2.08	
	2x013	15+15	1.66	
	2x014	18+18	1.38	
	2x015	22+22	1.13	
	2x016	25+25	1.00	
80 VA 90x30mm 1 Kg Regulation 12%	3x010	6+6	6.64	£6.08 +p/p £1.67 +VAT £1.16 TOTAL £8.91
	3x011	9+9	4.44	
	3x012	12+12	3.33	
	3x013	15+15	2.66	
	3x014	18+18	2.22	
	3x015	22+22	1.81	
	3x016	25+25	1.60	
120 VA 90x40mm 1.2 Kg Regulation 11%	4x010	6+6	10.00	£6.90 +p/p £1.67 +VAT £1.29 TOTAL £9.86
	4x011	9+9	6.66	
	4x012	12+12	5.00	
	4x013	15+15	4.00	
	4x014	18+18	3.33	
	4x015	22+22	2.72	
	4x016	25+25	2.40	
160 VA 110x40mm 1.8 Kg Regulation 8%	5x011	9+9	8.89	£7.91 +p/p £1.67 +VAT £1.44 TOTAL £11.02
	5x012	12+12	6.66	
	5x013	15+15	5.33	
	5x014	18+18	4.44	
	5x015	22+22	3.63	
	5x016	25+25	3.20	
	5x017	30+30	2.66	
225 VA 110x45mm 2.2 Kg Regulation 7%	6x012	12+12	9.38	£9.20 +p/p £2.00 +VAT £1.68 TOTAL £12.96
	6x013	15+15	7.50	
	6x014	18+18	6.25	
	6x015	22+22	5.11	
	6x016	25+25	4.50	
	6x017	30+30	3.75	
	6x018	35+35	3.21	
300 VA 110x50mm 2.6 Kg Regulation 6%	7x012	15+15	10.00	£10.17 +p/p £2.00 +VAT £1.83 TOTAL £14.00
	7x014	18+18	8.33	
	7x015	22+22	6.82	
	7x016	25+25	6.00	
	7x017	30+30	5.00	
	7x018	35+35	4.28	
	7x026	40+40	3.75	
500 VA 140x60mm 4 Kg Regulation 4%	8x016	25+25	10.00	£13.53 +p/p £3.35 +VAT £2.38 TOTAL £15.76
	8x017	30+30	8.33	
	8x018	35+35	7.14	
	8x026	40+40	6.25	
	8x025	45+45	5.55	
	8x033	50+50	5.00	
	8x042	55+55	4.54	
625 VA 140x75mm 5 Kg Regulation 4%	9x017	30+30	10.41	£16.13 +p/p £2.50 +VAT £2.79 TOTAL £21.42
	9x018	35+35	8.92	
	9x026	40+40	7.81	
	9x025	45+45	6.94	
	9x033	50+50	6.25	
	9x042	55+55	5.68	
	9x028	110	5.88	
800 VA 140x90mm 6 Kg Regulation 4%	9x029	220	2.84	£16.13 +p/p £2.50 +VAT £2.79 TOTAL £21.42
	9x030	240	2.60	

IMPORTANT: Regulation - All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain full load voltage.

The benefits of ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:
For 110V primary insert "0" in place of "X" in type number.
For 220V primary (Europe) insert "1" in place of "X" in type number.
For 240V primary (UK) insert "2" in place of "X" in type number.

How to order Freepost:
Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.
Also available at Electrovalue, Maplin and Technomatic.

Please send _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

Post to: ILP Electronics Ltd., Freepost 5, Graham Bell House, Roper Close
Canterbury CT2 7EP, Kent, England.
Telephone Sales (0227) 54778; Technical (0227) 64723; Telex 965780.

ILP TRANSFORMERS (a division of ILP Electronics Ltd)

WW - 027 FOR FURTHER DETAILS

New Fluke 4 1/2 Digit Hand-held D.M.M.s

Now in Stock

Basic dc accuracy 0.04%; 10 μV, 10 nA and 10 MΩ sensitivity.
Display annunciators for low battery (BT) and special functions: frequency (kHz), dB, continuity (---, ||) and relative reference (REL).
Autoranging MΩ measurements from 2 MΩ to 300 MΩ.
Conductance functions for resistance measurements to 10,000 MΩ.
Separate constant-current source diode-test function for checking semiconductor junctions.
Full range capability for voltage, current, resistance (200 μA, 200 mV and 200 Ω ranges).
Wideband True RMS AC measurements to 100 kHz.
Overload protection to 750 VAC or 1000 VDC on voltage inputs and 500 V on resistance. Protection on current inputs provided by a 2A/250V fuse in line with a heavy-duty 3A/600V fuse.
Sophisticated self-diagnostics provided for all range and function selections plus LCD display, battery and CMOS circuitry.
Fluke's 8062A makes many of the same measurements as the 8060A, at a lower price.
Continuity and relative reference functions identical to 8060A.
True RMS measurements to 30 kHz.
Basic dc accuracy 0.05%; 10 μV, 10 nA and 10 MΩ sensitivity.

Fluke 8060A **£275.00**
Fluke 8062A **£210.00**

Fluke 8022B With 2 year warranty **£85.00**
Fluke 8021B With 2 year warranty **£95.00**
Fluke 8020B With 2 year warranty **£125.00**
Fluke 8024B With 2 year warranty **£155.00**
Fluke 8050A Mains Model **£255.00** Mains Battery **£285.00**
Fluke 8012A Mains Model **£229.00** Mains Battery **£257.00**
Fluke 8010A Mains Model **£175.00** Mains Battery **£203.00**

ACCESSORIES

A81-230 Battery eliminator **£14.00**
C90 Carry case for hand held **£10.00**
801-600 Amp clamp **£68.00**
80J-10 Current shunt 10A **£22.00**
80K-40 H.V. probe 40kV **£56.00**
80K-6 H.V. probe 6kV **£40.00**
80T-150 Temperature probe **£72.00**
80T-H Touch hold probe **£36.00**
83RF R.F. probe 100MHz **£40.00**
85RF R.F. probe 500MHz **£69.00**
Y8102 Thermocouple probe **£41.00**
Y8103 Bead thermocouple **£18.00**
Y8104 K type thermocouple termination **£8.00**
Y8133 Deluxe test leads **£14.00**

Full Specs. on Request.
The above prices do not include carriage or VAT (15%).

EXPRESS DELIVERY SERVICE

Simply Phone or Telex your order for immediate dispatch.

Electronic Brokers Ltd
61/65 Kings Cross Road
London WC1X 9LN
Telephone: 01-278 3461
Telex: 298694 Elebro G

WW - 201 FOR FURTHER DETAILS

Electronic Brokers

**Superior Quality Precision Made
NEW POWER RHEOSTATS**



New ceramic construction, heavy duty brush assembly, continuously rated.
25 WATT 10/25 50 100/150/250/500/1kΩ 1.5kΩ
 £3.10 + 30p P&P. (£3.91 inc. VAT).
50 WATT 250Ω £5.50 + 50p P&P. (£6.90 inc. VAT).
100 WATT 1/5/10/25/50/100/250/300/500/1kΩ/1.5kΩ/2.5kΩ/
 5kΩ/3.5kΩ £7.25 + 75p P&P. (£8.20 inc. VAT).
Black Silver Skirted Knob calibrated in Nos. 1-9, 1/2in dia. brass bush. Ideal for above Rheostats 24p ea. + VAT.

SOLID STATE E.H.T. UNIT
 Input 230V A.C. Fully isolated. Approx. 15KV. Built-in 10 sec. Timer. Easily modified for 20 sec. 30 sec. to continuous operation. Size 155x85x50mm. Price £5 + 75p P&P. (£6.61 inc. VAT).



N.E.C. Geared Motor. 152 rpm, 200lb.in. 230V AC 50Hz. Ratio 9.2 to 1. Non-reverse. Incl. capacitors. Fraction of maker's price. Price: £37.50 + £4 p&p. (total incl. VAT £47.73). N.M.S.

240V A.C. SOLENOID VALVE
 Designed for Air/Gas at 0-7. Water 0-5 psi. Inlet/outlet 3/8". Forged brass body. Manuf. Dewarswitch Asco. Price: £5.50 + 75p P&P. (£7.10 inc. VAT). n.m.s.

METERS (New) - 90mm DIAMETER
 AC Amp. Type 62T2: 0, 1A, 0-5A, 0-10A.
 AC Volt. 0-150V, 0-300V.
 DC Amp. Type 65C5: 0-5A, 0-10A, 0-50A, 0-100A. DC Volt. 15V, 30V. All types £3.80 ea. + P&P 75p (£5.00 inc. VAT) except 0-50A DC, 0-100A DC. Price £5.00 plus 75p P&P (£6.61 inc. VAT).
 *Except



ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES
 4ft 40 watt £8.70 inc. VAT £10.00 (callers only).
 2ft 20 watt £3.20. Post £1.25 (£5.57 inc. VAT & P).
 (For use in standard bi pin fittings).
 12in 9 watt £3 + P&P 45p (£3.97 inc. VAT).
 9in 6 watt £2.50 + P&P 45p (£3.39 inc. VAT).
 6in 4 watt £2.50 + P&P 45p (£3.39 inc. VAT).
 Complete ballast unit for either 6V, 9V or 12V tube 230V AC op. £5.50 Post 55p (£6.96 inc. VAT & P). Also available for 12V DC £5.50 Post 55p (£6.96 inc. VAT & P).

BLACK LIGHT BULBS
 Self-ballasted Mercury U.V. 175W Bulbs. Available for either B.C. or E.S. fitting. Price incl. p&p + VAT £11.50.
 Black Light U.V. Tubes from 6in to 4ft from stock. Foolsap s.a.s. for details.
 400W UV LAMP AND BALLAST complete £38.00 Post £3.50 (£47.73 inc. VAT & P). 400W UV LAMP only £14.00. Post £2.00 (£16.40 inc. VAT & P).

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT 0-260V
 200W 1 amp inc. a.c. voltmeter £19.00
 0.5 KVA (2/2 amp MAX) £19.00
 1 KVA (5 amp MAX) £25.00
 2 KVA (10 amp MAX) £41.00
 3 KVA (15 amp MAX) £49.00
 5 KVA (25 amp MAX) £73.00
 10 KVA (50 amp MAX) £174.00
 15 KVA (75 amp MAX) £270.00



3-PHASE VARIABLE VOLTAGE TRANSFORMERS
 Dual input 200-240V or 380-415V. Star connected
 3 KVA 5 amp per phase max £108.00
 6 KVA 10 amp per phase max £182.00 Carriage, packing & VAT extra
 10 KVA 16 amp per phase max £329.00

LT TRANSFORMERS
 13.0 13V at 1 amp £2.80 P&P 75p (£4.08 inc. VAT).
 0.15V at 24 amp, 0-30V at 12 amp £20.40 P&P £2.3 (£26.11 inc. VAT & P).
 0.6V/12V at 20 amp £16.20 P&P £2.00 (£19.43 inc. VAT & P).
 0.12V at 20 amp or 0.24V at 10 amp £14.90 P&P £2.00 (£19.43 inc. VAT & P).
 0.6V/12V at 10 amp £9.10 P&P £2.00 (£11.78).
 0.6V/12V/17V/18V/20V at 20 amp £20.50 P&P £2.00 (£26.68 inc. VAT & P).
 0.10V/17V/18V at 10 amp £11.55 P&P £2.00 inc. P&P (£15.58 inc. VAT).

INDUSTRIAL STROBE. Suitable for both industrial and educational purposes. Kit when assembled produces a variable speed 1 to approx. 70 flash per second. Light output approx. 0.5 joules. Price, less case, £27 + £2 P&P (total incl. VAT £33.36). Suitable case £11 + £2 P&P (total incl. VAT £14.95).

FROM STOCK AT PRICES THAT DEFY COMPETITION!

- | | |
|------------------|--------------------|
| AC GEARED MOTORS | C.F. BLOWERS |
| DC MOTORS | AC CAPACITORS |
| MICROSWITCHES | STROBE KITS |
| RELAYS | FLASHTUBES |
| REED SWITCHES | CONTACTORS |
| SOLENOIDS | SYNCHRONOUS MOTORS |
| PROGRAMME TIMERS | |

Phone in your enquiries

EPROM ERASURE KIT

Why waste money? Build your own EPROM ERASURE for a fraction of the price of a made-up unit. Complete kit of parts less case, to include 12" 8 watt 2537 Angstrom Tube, Ballast unit, pair of bi-pin leads. Neon indicator, safety microswitch, on/off switch and circuit.
 LESS CASE. Price: £13.80 + 75p P&P. (Total incl. VAT £16.50).
 Warning: Tube used in this circuit is highly dangerous to the eyes. Unit MUST be fitted in suitable case.

REVERSIBLE MOTOR. 42 RPM 110V A.C. 100lb.in. Will operate on 230V A.C. Speed remains at 42 rpm but torque reduces by 50%. Price £16.50 + £2.50 P&P (Total incl. VAT £21.28).
 5 rpm or 15 rpm pole non-reversible Motor. Either type. £5.50 each + 50p P&P. (Total incl. VAT £6.88). N.M.S.

BRAND NEW CASSETTE TYPE MOTORS. Three types. 6V, 7.2V, 12V. Price, any three, for £2 + 50p. P&P (incl. VAT £2.88) N.M.S.
38.3 rpm GEARED MOTOR. Torque 35 lb.in. reversible 115V AC inc. start capacitor. Price: £10.50 + £2.00 P&P (total incl. VAT £14.38). Suitable Transformer 230V AC operation. Price £6.50 + 50p P&P (total incl. VAT £8.05). N.M.S.

ROTARY CARBON VANE VACUUM & COMPRESSOR

Direct coupled to 1/3 hp. 110/115V AC Motor 4.2 amp. 1380 rpm. Motor manuf. by A.E.I. Pump by Williams. Max. Vac. 2586 H.G. Max. pressure cont. 10 p.s.i. int. 15 p.s.i. Max. airflow 3 c.f.m. at 60066 H.G. Price £30 + P&P £4 (£39.10 inc. VAT). N.M.S.
 Suitable transformer 240V op. £10 P&P £2 (£13.80 incl. VAT). N.M.S.

WATER PUMP
 Mfg. by S.P.A. Astalasi of Italy. 220/240V AC 50 Hz. 2800 R.P.M. approx. 1/3hp. Centrifugal pump with 1/2" inlet/outlet. Delivery approx. 40 gals per min. at 10lbs head. (Non-self-priming). Price £16.50. P&P £2.50 (£21.85 inc. VAT). N.M.S.

HY-LIGHT STROBE KIT Mk IV
 Approx. 4 joules. Adjustable speed. Price £27 + £2 P&P. (Total incl. at £33.36). Case and reflector price £11 + £2 P&P (Total incl. VAT £14.95). Foolsap s.a.s. for further details inc. Super Hi-Light. N.M.S.

INSULATION TESTERS NEW
 500 VOLTS 500 megohms £49.00 P&P £2.00 (£58.85 inc. VAT & P) 1000 VOLTS 1000Ω £55.00 P&P £2.00 (£65.55 inc. VAT & P). SAE for leaflet.




TIME SWITCH VANNER TYPE ERD
 Time switch 200-250V a.c. 30 amp contact 2 on/2 off every 24 hrs. at any manually pre-set time 36 hour spread reserve and day omitting device. Built to highest Electricity Board Specification. Price £11.50 P&P £1.50. (£14.95 inc. VAT). R&T.

SANGAMO WESTON TIME SWITCH
 Type S251 200/250 AC 2 on/2 off every 24 hours. 20 amps contacts with override switch. Diameter 4" x 3". Price £9.50 P&P £1 (£12.08 inc. VAT). Also available with solar dia. R&T.
 Also available Sangamo Weston 60 amp and AEG 80 amp. Phone for details.

Type S288 1 on, or 1 timed c/o every 24 hours, day omitting device. Price £11 + £1 P&P. (£13.80 inc. VAT). N.M.S.
 Type S388. As above, plus 36 hours spring reserve. Less perspex cover. Price: £13 + £1 P&P (£16.10 inc. VAT). N.M.S.

N.M.S. - New Manufacturers' Surplus. R&T - Reconditioned and Tested.

METER PROBLEMS?

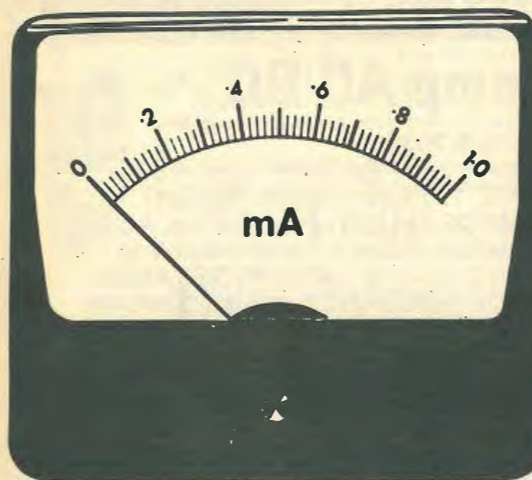

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

HARRIS ELECTRONICS (London)
 138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937
 Telex: 892301 HARTRO G

WW - 011 FOR FURTHER DETAILS

10 OUTLET DISTRIBUTION AMPLIFIER 3



A compact mains-powered unit with one balanced input and ten a.c. and d.c. isolated floating line outputs.

- ★ Exemplary R.F. breakthrough specifications giving trouble-free operation in close proximity to radio telephones and links
 - ★ Excellent figures for noise, THD, static and dynamic IMD
 - ★ Any desired number of outlets may be provided at microphone level to suit certain video and audio recorders used at press conferences
 - ★ Meets IEC65-2, BS415 safety and I.B.A. 'signal path' requirements
- Also available as a kit of parts less the case and all XLR connectors for one or ten outlets.
- Broadcast Monitor Receiver 150kHz-30MHz ★ Stereo Disc Amplifier 2 and 3 ★ Moving Coil Preamp/Amplifier ★ Illuminated PPM Boxes ★ PPM Drive Boards and Ernest Turner Movements ★ Stabilizer and Frequency Shifter Boards ★ Peak Deviation Meter ★ Programme and Deviation Chart Recorders.

SURREY ELECTRONICS LIMITED
 The Forge, Luicks Green
 Cranleigh, Surrey GU6 7BG
 Tel: 04866 5997

ELECTRONIC VALVES WANTED


All Types Receiving, Transmitting, Industrial

- PL504 - PL802 - PCL805 - CV131 - CV136 - CV138 - CV329 - CV345 - CV450 - 805 - 807 - 813 - 2K25, etc.

Phone/write to:
PYPE HAYES RADIO LTD.
 606 Kingsbury Road
 Birmingham, B24 9PJ
 021-373 4942

WW - 018 FOR FURTHER DETAILS

**We supply
HAMEG
for Industry**

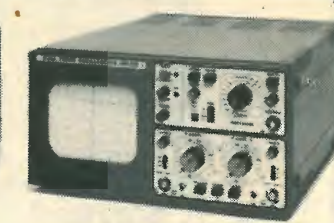

HM 203 PORTABLE OSCILLOSCOPE

Dual Trace. DC to 20MHz. 8 x 10cm display. Risetime 17.5ns. Sensitivity 5mV/cm-20V/cm. Timebase 0.5µs-0.2S. x 5 magnifier. X-Y operation. Auto or variable trigger. Channel 1, Channel 2, line and external. Coupling AC, or TV low pass filter. Weighs only 6Kg. Size (m.m.) H. 145, W. 285, D. 380 £220.00

HM 307 OSCILLOSCOPE

Single trace. DC to 10MHz. Risetime 35ns. 5mV/cm to 20V/cm. Timebase 0.5µs-0.2S. Built in component tester. LPS technique provides stable and reliable triggering up to 30MHz £138.00



HM412-5

Dual Trace. DC to 20MHz 8 x 10cm display with internal graticule. Rise time 17.5ns. Variable input 2mV-20V/cm. Add and invert modes. Timebase 0.5µs-0.2S with sweep delay 100ns-1S x 5 expansion. X-Y operation. XY modulation. Trigger CH1, CH2, CH1/2, Line or EXT. £350.00

HM705


Dual Trace DC-70MHz 8 x 10cm display with internal graticule. Risetime 5ns. Variable input 2mV-20V. Add and invert modes. 95ns Signal Delay Line. Timebase 50ns-1S/cm with Sweep delay 100ns-1S x 10 expansion. XY operation. Z modulation. Trigger CH1, CH2, CH1/2 line or EXT. £580.00

The above prices do not include carriage or VAT (15%).

Simple Phone or Telex your order for immediate dispatch.

Electronic Brokers Ltd
 61/65 Kings Cross Road
 London WC1X 9LN
 Telephone: 01-278 3461
 Telex: 298694 Elebro G

WW - 202 FOR FURTHER DETAILS

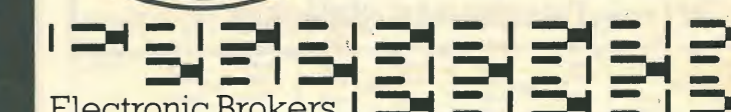

SERVICE TRADING CO


57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB, 01-995 1560
 ACCOUNT CUSTOMERS MIN. ORDER £10

Personal callers only. Open Saturdays

9 Little Newport Street
 London WC2H 7JJ
 Tel: 01-437 0576

WW - 005 FOR FURTHER DETAILS

**HABED
PARABOLIC DISHES**

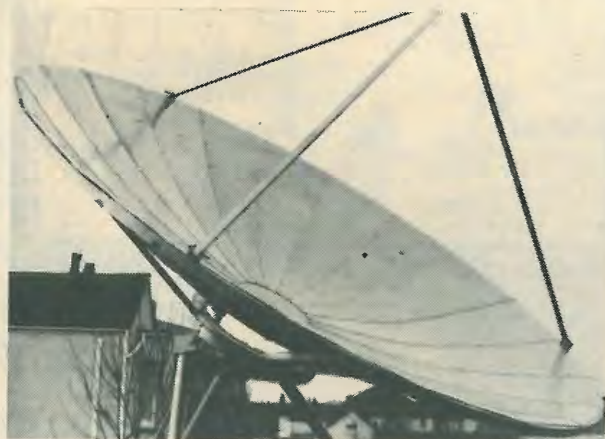

6ft dia. for use in satellite reception and microwave transmissions. Please send S.A.E. for full details and data sheet.

Harrison Bros.

Electronic Distributors

22 Milton Road, Westcliff-on-Sea, Essex SS0 7JX
 Tel. Southend (0702) 332338

WW - 008 FOR FURTHER DETAILS

NEW...Essex Tiny Basic System



- * RS232 Interface 48 I/O Lines
- * Powerful Tiny Basic Processor
- * Autostart Operation with Watchdog Timer
- * Up to 16K Byte EPROM EPROM Programmer
- * Accommodates Instant ROM Modules

The Essex Tiny Basic Computer is an ideal choice for data acquisition and process control systems. Its crystal controlled timer and interrupts provide accurate timing and fast response to critical events, while the watchdog timer ensures reliable operation. Programs can be entered and tested from an RS232 terminal, and then be copied into EPROM. Alternatively, Instant ROM modules may be used both during development and for program storage.

*INSTANT ROM is the trademark of Greenwich Instruments

PRICE EXCLUDING VAT: £185 - CARRIAGE WITHIN THE UK £2 - PLEASE SEND FOR FULL INFORMATION

Essex Electronics Centre
 University of Essex, Colchester, CO4 3SQ.
 Telephone: Colchester (0206) 865089

WW - 042 FOR FURTHER DETAILS

hi! performance hi! competitive hi!

FULL HOUSE OF MULTIMETERS

Bench Models DL 705, 706, 720 and DF 760

TRIO

- 3½ and 4½ digit LED
- Rugged and Reliable
- 2 YEAR GUARANTEE
- Simple Operation - Auto Ranging
- Mains or Battery
- 7 Digit Frequency Counter
- Resolutions 1 and 0.1 mV
- DCV, ACV, DCA, ACA and Ohms
- Basic accuracy 0.8, 0.25, 0.1 and 0.05%
- Prices from £92 include FREE batteries, hand book and Test Leads



KEITHLEY

Hand Held Models 128, 130, 131 and 135
Bench Models 169 and 176

- 3½ and 4½ digit Large LCDs
- State of the Art - Full One year warranty
- DCV, ACV, DCA, ACA, Ohms, Temp and Comp Tester
- Switched 'AUDIO' beep with variable threshold
- Basic accuracy 0.5, 0.25 and 0.05%
- Rotary Controls = single hand operation
- Non skid feet and Tilt stand
- 10 AMP capability - High MTBF
- Many optional accessories
- Prices from approx £89 inc FREE Batteries and Test Leads



BBC GOERZ METRAWATT

Models MA 1D, 1H, 2D, 2H, 3D, 3E and 5D

- Digital and Analog - Hand Held and Bench
- Huge LCDs - Many Safety Features
- Black, Rugged and Reliable
- 1 Year Guarantee
- 3½ and 4½ Digits
- Variable Viewing Angle - Hand free operation
- 20 Amp capability
- DCV, ACV, DCA, ACA, Ohms, Capacitance, Temp and Level in dBs
- Meet DIN 40050, 43780, 57410 or 57411 Requirements
- Prices from approx £26 inc FREE Batteries, Manual and Test Leads



HC

Hand Held Models HM 101 and 102, HC 601 and 703

- 3½ digit LCD and Analogue
- Colour coded front panel and edge switches
- High impact ABS with Tilt stand
- Safety features meets UL 1244
- Basic accuracy 0.6 and 0.2%
- Full Range of DCV, ACV, DCmA, ACmA and Ohms
- FREE Battery, Manual and Test Leads
- Analogue from approx £5 - Digital from approx £37



House of Instruments
Clifton Chambers, 62 High Street
Saffron Walden, Essex CB10 1EE
Tel: (0799) 24922 Telex: 818750



hi!

House of Instruments Ltd.

WW - 016 FOR FURTHER DETAILS

P.M. COMPONENTS LTD

VALVE & COMPONENTS SPECIALISTS

INTEGRATED CIRCUITS

AN124 2.50	ML231B 1.75	TA7120P 1.85	TBA651 1.75	TD42540 2.15
AN214Q 2.50	ML232B 1.75	TA7130P 1.50	TBA720A 2.45	TD42541 2.15
AN240P 2.50	ML237B 1.95	TA7203 2.95	TBA750Q 1.85	TD42581 1.15
BA521 3.35	ML238B 1.95	TA7204P 2.15	TBA800 9.89	TD42582 1.15
ET1601E 1.75	ML239 1.42	TA7205AP 1.80	TBA810AS 1.35	TD42590 2.95
HA1151P 2.50	ML28 1.65	TA7222AP 1.80	TBA8200 1.45	TD42591 2.95
HA1366V 1.95	MSM5807 6.75	TA7227P 4.25	TBA890 2.50	TD42593 2.95
LA4031P 1.50	PLLOZA 5.75	TA7310P 1.80	TBA920 1.55	TD42610 2.50
LA4102 2.95	SAA1025 7.25	TA7313AP 2.95	TBA950 2.35	TD42611 1.95
LA4400 4.15	SAA500A 8.05	TA7313AP 2.95	TBA950/2K 2.35	TD42640 2.80
LA4422 2.50	SAS560S 1.60	TA7320 1.10	TBA990 1.49	TD42650 1.35
LC120 3.50	SAS570S 1.80	TA7320P 1.80	TBA990 1.49	TD42650 1.35
LC130 3.50	SL490 1.95	TA7320P 1.80	TBA990 1.49	TD42650 1.35
LC137 3.50	SL901B 4.85	TA7320P 1.80	TBA990 1.49	TD42650 1.35
LM324N 0.45	SL917B 6.65	TA7320P 1.80	TBA990 1.49	TD42650 1.35
LM330P 0.75	SL1310 1.80	TA7320P 1.80	TBA990 1.49	TD42650 1.35
LM383T 2.95	SL127 1.10	TA7320P 1.80	TBA990 1.49	TD42650 1.35
LM390N 1.95	SL1327Q 1.10	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MS1513L 2.30	SN76003N 1.65	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MS1515L 2.95	SN76013N 1.65	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1307 1.50	SN76013N 1.65	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1307P 1.50	SN76013N 1.65	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1327 0.95	SN76033N 1.65	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1327P 0.95	SN76101N 0.89	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1330P 0.75	SN76131N 1.30	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1349P 1.20	SN76227N 1.05	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1350P 0.75	SN76532N 1.40	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1351P 1.50	SN76533N 1.30	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1352P 1.00	SN76544N 1.30	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1485 3.00	SN76560N 1.05	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1401BPC 0.32	SN76660N 0.70	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC1723 0.50	TA7061AP 3.95	TA7320P 1.80	TBA990 1.49	TD42650 1.35
MC3357 2.25	TA7108P 1.00	TA7320P 1.80	TBA990 1.49	TD42650 1.35

SEMICONDUCTORS

AA12 0.25	BC172C 0.10	BD139 0.32	BF336 0.34	R2322 0.58
AC126 0.22	BC173B 0.10	BD144 1.10	BF337 0.29	R2323 0.66
AC127 0.20	BC174 0.09	BD159 0.85	BF355 0.37	RC1633A 0.90
AC128 0.20	BC174A 0.09	BD166 0.48	BF362 0.38	RCA61635 0.80
AC128K 0.20	BC177 0.19	BD179 0.72	BF363 0.38	SK5EF 1.45
AC141 0.24	BC178 0.15	BD201 0.83	BF371 0.20	TIP29 0.40
AC141K 0.38	BC182 0.10	BD202 0.85	BF457 0.23	TIP30C 0.43
AC142K 0.30	BC182LB 0.10	BD203 0.78	BF458 0.28	TIP31C 0.42
AC158K 0.20	BC183 0.12	BD204 0.70	BF459 0.38	TIP33B 0.75
AD142 0.30	BC183L 0.09	BD223 0.48	BF459 0.38	TIP34B 0.75
AD143 0.82	BC184LB 0.09	BD223 0.48	BF459 0.38	TIP34B 0.75
AD149 0.70	BC204 0.10	BD225 0.48	BF459 0.38	TIP34B 0.75
AD161 0.39	BC207B 0.13	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC209B 0.13	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC212L 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC212LA 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC213 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC213L 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC214 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC214C 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC214L 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC217 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC217A 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC217B 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC218 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC218L 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC219 0.12	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC251A 0.12	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC252A 0.15	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC258 0.39	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC258A 0.39	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC284 0.30	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC300 0.30	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC302 0.26	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC303 0.26	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC307 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC307A 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC307B 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC308 0.10	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC308A 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC309 0.10	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC309A 0.09	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC309B 0.10	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC309C 0.10	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC347A 0.13	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC461 0.35	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC478 0.79	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC527 0.20	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC547 0.10	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC548 0.10	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC549A 0.08	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC550 0.08	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC557 0.08	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC557A 0.08	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC557B 0.08	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC558 0.08	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC558A 0.08	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BC558B 0.08	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BCY33A 1.60	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BD115 0.30	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BD116 0.30	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BD124P 0.55	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BD131 0.32	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BD132 0.35	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BD133 0.40	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BD134 0.28	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BD137 0.28	BD232 0.35	BF459 0.38	TIP34B 0.75
AD162 0.39	BD138 0.30	BD232 0.35	BF459 0.38	TIP34B 0.75

DIODES

AA119 0.08	BY206 0.14	IN4001 0.04
BA102 0.17	BY208-800 0.33	IN4002 0.04
BA103 0.17	BY210-800 0.33	IN4003 0.04
BA105 0.17	BY223 0.90	IN4005 0.06
BA145 0.16	BY298-400 0.22	IN4006 0.06
BA148 0.17	BY299-800 0.22	IN4007 0.06
BA154 0.06	BYX10 0.20	IN4148 0.02
BA155 0.15	BYX36-150P 0.20	IN4448 0.02
BA156 0.15		IN5401 0.12
BAX13 0.04		IN5402 0.14
BAX16 0.06		IN5403 0.12
BB105B 0.30		IN5404 0.12
BT151 0.79		IN5405 0.13
BY127 0.10		IN5406 0.13
BY127 0.11		IN5407 0.16
BY133 0.15		IN5408 0.16
BY154 0.45		IT44 0.04
BY176 1.20		
BY179 0.63		
BY184 0.35		

CRT TUBES

A selection of tubes available. Prices available on request.

3BP1	D14-260GH
5BKP1	D14-250GH
13BP4	DH7-11
1768	DP7-11
CV429	M17-151GVR
D10-210GH	M38-121GH/R
D13-450GH	O1SE4DP7
D13-481GM	XP2020
D14-1206GH	XP5449GM

PHONE
0474 813225
3 LINES


P. M. COMPONENTS LTD
SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX
965966
WEST ST G

A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714 18.50	E2807 7.50	EF92 2.50
A1998 11.50	E288CC 7.50	EF93 0.85
A2087 11.50	E298CC 7.50	EF94 0.85
A2134 17.50	E3107 13.50	EF9

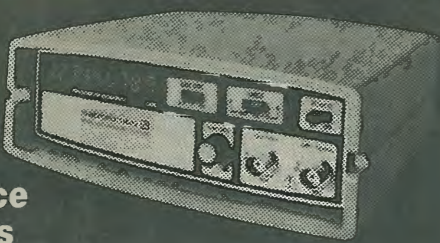An entire range of low-cost high-performance instruments



sabtronics

'Making Performance Affordable'

*2010A	3 1/2-Digit L.E.D. Bench DMM	5020A	1Hz-200KHz Function Generator
*2015A	3 1/2-Digit L.C.D. Bench DMM	*8110A	100MHz 8-Digit Frequency Meter
2020	3 1/2-Digit L.E.D. Bench DMM with Microcomputer Interface	*8610A	600MHz 8-Digit Frequency Meter
2033	3 1/2-Digit L.C.D. Hand DMM	*8610B	600MHz 9-Digit Frequency Meter
*2035A	3 1/2-Digit L.C.D. Hand DMM with Temp.	8000B	1GHz 9-Digit Frequency Meter
*2037A	3 1/2-Digit L.C.D. Hand DMM with Temp.	8700	10MHz Universal Frequency Counter/Timer
LP-10	10MHz Logic Probe	PSC-65	800MHz Prescaler
		9005	5MHz Single Trace Oscilloscope

* Also available in kit form.

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices - no-one can beat our price/performance ratio.

Full colour illustrated brochure and price list from:

BLACK STAR LTD.,
9a Crown Street, St. Ives,
Cams. PE17 4EB
Tel: (0480) 62440. Telex 32339



WW - 033 FOR FURTHER DETAILS

meet the metrics

A great variety of tools and sets to help you turn most any Metric fastener or adjusting screw you're likely to encounter... hex socket set screws and cap screws, hex nuts, hex head cap screws, and whatever.

All tools precision made for exact fit. Bright nickel chrome nutdriver shafts and protective black oxide finished hex socket screwdriver blades. Plastic (UL) handles shaped for perfect grip and balance.

FIXED HANDLE NUTDRIVERS

COMPACT SETS

NUTDRIVER SHANKS & HEX SOCKET SCREWDRIVER BLADES

REPLACEMENT BLADES AND SHANKS

SETS

Full catalogue available on request

Replacement Blades and Shanks

Separately available for 99 Series

Sets

Full catalogue available on request

Replacement Blades and Shanks

Separately available for 99 Series

Sets

Full catalogue available on request

Replacement Blades and Shanks

Separately available for 99 Series

Sets

Full catalogue available on request

Replacement Blades and Shanks

Separately available for 99 Series

Sets

Full catalogue available on request

Replacement Blades and Shanks

The lightweight mast with 101 applications

25 years in this specialist field



The smoothly operated QTM Mast comes fitted with handpump or can be vehicle mounted with 'Power Pack' for extension and retraction. Available in a range of heights up to 15 metres, the QTM mast can provide the ideal answer for:

- Mobile Radio Telephone
- Environmental - gas sampling collector
- Police Mobile HQ (UHF)
- High level photography
- Field Telecommunications
- Meteorology
- Floodlighting
- And a host of other uses
- Anemometer and Wind Measurement

CLARK MASTS

Find out more about the QTM series by writing or phoning:-

U.K.
CLARK MASTS LTD. (W.W.)
Evergreen House, Ringwood Road,
Binstead, Isle of Wight,
England PO33 3PA
Tel: Isle of Wight (0983) 63691
Telex: 86686

EUROPE
GENK TECHNICAL PRODUCTS N.V. (W.W.)
Woudstraat 21, 3600 Genk,
Belgium.
Telefoon 011-380831
Telex 39354 Genant B.

WW-041 FOR FURTHER DETAILS

TEST COMPONENTS ON THIS NEW OSCILLOSCOPE



USE READER CARD FOR DETAILS

WW - 039 FOR FURTHER DETAILS

D.I.L. MINIATURE ON-OFF SWITCHES Gold-plated contacts. Sealed base. Ideal for programming. 6-position at less than half manufacturer's price. ONLY 75p Will fit into 14-pin DIL socket. Ten at 65p ea; per 100 55p ea.	HONEYWELL PROXIMITY DETECTOR Integral amplifier, 0v. D.C. £3.50 ea. PHOTO CONDUCTIVE CELL £1.25. High-power Cds cell, 600mW, for control circuits. Resistance 800 ohm to 4K. Max. volts 240. Size 1/2 x 1/2in. RIBBON MICROPHONE with pre-amp. on chassis. £1.75.	MULLARD MODULES LP1171 AM, FM IF Strip Front end Pair £5.75 LP1180 varicap Med. & Long Tuner £2.50 LP1157 CRYSTALS COLOUR TV 4.433619 mc/s £1.25 Miniature type sealed	ULTRA SONIC TRANSDUCERS 40KC/S. Complete on 18in. Screened cable. £1.75 each; pairs £2.95. ULTRA SONIC TRANSMITTER Complete unit (encased requires 1.5V). £3.25. FOSTER DYNAMIC MICROPHONES 200 ohm impedance. Moving coil. Complete on chassis. £1.75 pair.
U.H.F. MODULATOR Latest type, adjustable, ideal for computers, with data circuit. Size 3x2x1 inch. Only £3.50 In screened case	LM380 Amplifier 85p LM318N Hi-Slew Op. Amp. £1.50 LM323K, 5v. 3-amp. reg. £3.50 LM310N Volt. Follower Amp. £1.20 LM311H High Perf. Volt. Comparator £1.00 LM384N, 5-watt Amp £1.20 LM393N Dual Com. 60p 7905 Reg. -5v. 75p	MINIATURE HIGH-QUALITY FANS "Whisper Model" by Roton. Low-power consumption (less than 10 watts). Silent running. 115v. (two in series for 230v.). 50/60Hz. Size 4 1/2 x 4 1/2 x 1 1/2in. ONLY £6.50 EACH incl. V.A.T. BRAND NEW 50% less than manufacturer's price	STEREO CASSETTE MECHANISMS 6 or 12 volt. Complete with Heads + Erase and Solenoid. Brand new £5.50 ea.
MINIATURE EDGE INDICATOR METERS With illuminated dial scale 0-10. F.S.D. 100 microamp. Size 1 1/2 x 1 1/2 x 1/2 deep. Only £1.65.	MONSANTO Half-inch +1 Display High Intensity £1 each set of 4 £3.50 Common anode 14 Pin DIL Package	HEWLETT-PACKARD DISPLAYS 5082-7650 HIGH EFFICIENCY AND VERY BRIGHT. Only £1.00 each Set of 6 for £5 Half-inch red common anode will replace DLT7/14-pin DIL.	TV CENDERENCE POTS (LIN) 50 ohm ALL 50p 100 " 200 " 5K " 50 "
BRIDGE RECTIFIER 800 PIV 35 amps 1 1/2 x 1 1/2 x 1/2in. £3.50	STEREO CASSETTE TAPE HEADS. Quality replacement for most recorders with mounting plate. Record/Replay £2.80 MARRIOTT TAPE HEADS Quarter track. Type XRP518 Record/Replay (each) £2.00 XRP536 Record/Replay (each) £3.00 XES11 Erase (each) £1.00	EX-MOTOROLA 5 + 5-WATT CAR STEREO AMPLIFIERS Complete and tested units. Medium and Long Wave. Supplied as two built units (5 x 2 x 2in.) with circuit and data. Only £5 pair. Includes pre-amp.	
NATIONAL P.8080A Chips £2.95 6216 £1.75 IN4148 DIODES Full spec. but no polarity band. Per 1,000 £10 MINIATURE M.P.C. POTENTIOMETERS Model M2. High-quality, 5% tolerance, 2-watt, with lin. spindles. All values, 47 ohms-47k only 60p each per 10; 50p each per 100; 40p each.	RECHARGEABLE BATTERIES VARTA 3.6 volts DEAC M/AH 225 £1.50 DRYFIT 6-volt, 4.5 amp. £7.50 XTAL FILTER 10.7 mc/s; 12.5dB separation, 1 1/2 x 1 1/4 x 1 inch £7.00 100KC/S + 1 meg. 3-pin £2.00	"CHERRY" ADD-ON KEYPAD A compact 12-button keypad suitable for use with Keyboard extend its functions plus four extra keys. Supplied brand new LIST PRICE £22.00 OUR PRICE ONLY £7.50 incl. V.A.T.	

QUANTITY DISCOUNTS on ALL items (unless stated), 15% per 10, 20% per 50, 25% per 100. All items BRAND NEW (unless otherwise stated). DELIVERY from stock - Add post 35p per order.

HENRY'S EXPORT enquiries invited
01-723 1008/9

Callers to: 404 EDGWARE ROAD, LONDON W2 1ED
ALL MAIL ORDERS/EXPORT ENQUIRIES 11/12 PADDINGTON GREEN, LONDON, W2

WIRELESS WORLD AUGUST 1982

THE CASE FOR I.L.P.



It's the chance every constructor wants

Did you know

It's something you have always wanted....something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U.'s, the range will shortly be extended to house any other modular projects.

POWER AMPS



P.S.U.'s



PRE-AMP MODULES

WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN. It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, FREE. You don't even have to stamp the envelope if you address it the way we tell you.

I.L.P. are the world's largest designers and manufacturers of hi-fi audio modules?

I.L.P. pioneered encapsulated power amps and pre-amps for enhanced thermal stability, mechanical protection and durability?

There are TWENTY power amplifiers from 15 to 240 watts RMS including the very latest super-quality Mosfets to choose from?

TWENTY pre-amp modules allow you to incorporate exciting professional applications to your equipment never before available to constructors and experimenters?

I.L.P. are suppliers to the B.B.C., I.B.A., N.A.S.A., British Aerospace, Marconi, Racal, Ferranti, G.E.C., Rolls Royce etc?

Goods are despatched within 7 days of your order reaching us and covered by our 5 year no-quibble guarantee?



FREEPOST 5
GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP
Telephone Sales (0227) 54778 Technical Only (0227) 64723 Telex 965780

FREEPOST
Mark your envelope clearly FREEPOST 5 and post it WITHOUT a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

SEND COUPON (NO STAMP NECESSARY) FOR YOUR FREE I.L.P. CATALOGUE AND OPEN UP TO A NEW WORLD OF QUALITY & VALUE

To: I.L.P. ELECTRONICS LTD.
PLEASE SEND ME I.L.P. CATALOGUE, POST PAID BY RETURN

Name: _____
Address: _____

I HAVE/HAVE NOT PREVIOUSLY BUILT WITH I.L.P. MODULES

I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford.

WW - 024 FOR FURTHER DETAILS

WIRELESS WORLD AUGUST 1982

BY ORDER OF B. BAMBER ELECTRONICS AND OTHERS

SALE BY AUCTION

TO BE SOLD BY

ANGLIA INDUSTRIAL AUCTIONS

SPECIALIST AUCTIONEERS TO THE RADIO AND ELECTRONICS INDUSTRY

LOTS INCLUDE:

Resistors, capacitors, pots, connectors, switches, diecast boxes, plastic project boxes, vero board, transformers, relays, bulbs and neons, tools, transistors, valves, panel meters, digital watches, calculators, car radio speakers, intercom units, multimeters, cable, test equipment, radio telephones and spares, amateur radio transceivers, Weller spares.

Over 900 lots - Catalogues available

TO BE HELD ON WEDNESDAY, AUGUST 18, 1982

ON THE PREMISES OF

B. BAMBER ELECTRONICS
5 STATION ROAD
LITTLEPORT
CAMBS. CB6 1QE
TEL: ELY (0353) 860185

WW-068 FOR FURTHER DETAILS

THE MOST ECONOMICALLY - PRICED PROFESSIONAL EPROM PROGRAMMERS AROUND

SUITABLE FOR EPROMS:
2708, 2516, 2716, 2532, 2732, 2732A
plus option for 2564, 2764

DATAPROM

STARTING AT £395 + VAT
Albetros (Products) Limited Frances Road Basingstoke Hampshire RG21 3DA
Telephone (0256) 57551

WW - 032 FOR FURTHER DETAILS

ELECTRON GUNS TV TUBE COMPONENTS

If you are Rebuilding or Manufacturing TV Tubes - We are the leading suppliers of Electron Guns and TV Tube Components to the TV Tube Industry. We specialise in all aspects of Electron Mount Technology. Our product range includes more than 250 gun types for Colour, In Line, Mono and Display Tubes along with Mount Parts, Bases, Getters, Sealoffs, and all other associated items for TV Tube Production. A Full Technical Back-up and Advisory Service is available to all customers Worldwide.

Please request our current catalogues and Data Information.

GRIFTRONIC EMISSION LTD
2 SWAN STREET
ALCESTER
WARWICKSHIRE
B49 5DP
ENGLAND

Telephone: (0789) 764852/764100. Telex: 312354 Grifem G

WW - 045 FOR FURTHER DETAILS

NOW!
FROM SESCOM

ORDER YOUR FAVOURITE AUDIO ACCESSORIES BY MAIL

SEND FOR YOUR FREE COPY OF OUR 1982 CATALOG



48 PAGES
8 1/2" x 11"

OVER 250 ITEMS
INCLUDING DIRECT BOXES, MIC-SPLITTERS,
SIGNAL PROCESSING, AUDIO MODULES,
TRANSFORMERS & MANY OTHER ACCESSORIES
WITH TECHNICAL DATA & USE DIAGRAMS

We Ship the fastest & most convenient way for you! Most Shipments From Stock



SESCOM, INC.
RETAIL SALES DIVISION
1111 Las Vegas Blvd. North
Las Vegas, NV 89101-1197 U.S.A. TWX (910)397-6996

WW - 048 FOR FURTHER DETAILS

WIRELESS WORLD AUGUST 1982

AUDIO ELECTRONICS

RETAIL-MAIL ORDER-EXPORT INDUSTRIAL-EDUCATIONAL

TEST EQUIPMENT CENTRES

CALL IN AND SEE FOR YOURSELF OPEN SIX DAYS A WEEK ALL MODELS ON DISPLAY

ALL PRICES INCLUDE VAT

DIGITAL MULTIMETERS

- All models complete with leads and batteries
- | | |
|---|--|
| Hand Held Models 3 1/2 digit LCD (UK C/P 65p) | Bench Models 3 1/2 digit LCD unless stated (UK C/P 90p) |
| 601 26 range push button 2A AC/DC Basic 0.5% £36.50 | 2010A LED 31 range, 10A AC/DC basic 0.1% (Sabtronics) £81.50 |
| 2033A Similar to above by Sabtronics £39.95 | TM353 LCD 27 range 2A AC/DC basic 0.1% (Sinclair) £86.25 |
| 703 As 601 but 0.2% basic £54.00 | 2015A LCD 31 range 10A AC/DC basic 0.1% (Sabtronics) £89.50 |
| 188m/6011A 15 range + Hfe tester push button 10A DC £43.50 | TM351 LCD 29 range 10A AC/DC basic 0.1% (Sinclair) £113.85 |
| 189m 30 range plus Hfe tester. Rotary switch 10A AC/DC £69.95 | 2001 LCD 28 range plus 5 range capacitance meter 10A AC/DC Basic 0.1% (Pantec) £108.00 |
| 2035A 28 range 0.1% basic 2A AC/DC push button (Sabtronics) £71.00 | 1503A 4 1/2 digit LCD 30 ranges 10A AC/DC 4 MHz counter, 4 KHZ osc. 0.05% basic (Thurby) £171.00 |
| 2037A As 2035A plus 2-temp. ranges £77.00 | 1503HA As above but 25A and 0.03% basic £189.75 |
| 129 25 range 0.8% basic 10A AC/DC rotary switches (Keithley) £79.35 | |
| 130 As model 129 but 0.5% basic £102.35 | |
- ACCESSORIES**
AC Adaptors (2010A & 2015A only) £5.69 Cases TM351/353 £6.84
2001 £7.50 1503 £20.45 Touch and hold probe THP20 £14.95



- ### GENERATORS
- R-C Pulse RF Function: Audio (UK C/P £1)
- All models 220/240 V AC AUDIO (20 HZ - 200 KHZ 4 band. Sine/SQ 0-P) £222.00
- TE220 Max distortion 1% £68.95
- LAG27 Max distortion 0.5-1% (LEADER) new model £86.25
- AG202A Max distortion 0.5-1% (TRIO) £78.20
- LAG120A 5 band 10 HZ - 1 MHz. Sine/SQ 0.05-0.8% dist. £146.00
- LAG125 As LAG120A but 0.02% dist. (LEADER) £273.00
- AG203 10 HZ - 1 MHz 5 band 0.1% Sine/SQ (TRIO) £126.50
- RF (All with Int/Ext mod. variable output) £59.95
- TE200 100 KHZ - 100 MHz 5 band (300 MHz harm) £59.95
- LS617 As above made by LEADER new model £71.30
- SG402 100 KHZ - 30 MHz 6 band (TRIO) £68.00
- FUNCTION (All sine/SQ/Triangle/TTL etc.) £68.00
- 5020A 1 HZ - 200 KHZ (SABTRONICS) £90.00
- T6100 1 HZ - 100 KHZ (THANDAR) £90.85
- T6102 0.2 HZ - 2 MHz (THANDAR) £166.75
- PULSE T6105 5 HZ - 5 MHz Various outputs (THANDAR) £97.75

- ### INSULATION AND CLAMP METERS
- Multi-range clamps all with resistance range, carry case and leads. Also digital and DC clamp in stock. (UK C/P 75p)
- ST300 300A, 6000V AC, 9 ranges. £28.95
- K2606 300A, 6000V AC, 8 ranges. (Optional temp. probe £13.80) £49.50
- K2903 900A, 750V AC, 9 ranges. £77.50
- Battery operated complete with carry case. (UK C/P £1)
- YF501L 500V/100 Meg. Plus 0-100 ohm £65.00
- K3103 600V/100 Meg. Plus 0-2.6K ohm £109.00
- K3106 500V & 1000V, 1000 & 2000 Meg. £119.00
- K4101 Earth resistance tester £149.00
- M500 Hand cranked insulation tester 500V/100 Meg. £79.50
- K8031 110V/600V phase tester £23.50

- ### ELECTRONIC INSULATION TESTERS
- Multi-range clamps all with resistance range, carry case and leads. Also digital and DC clamp in stock. (UK C/P 75p)
- ST300 300A, 6000V AC, 9 ranges. £28.95
- K2606 300A, 6000V AC, 8 ranges. (Optional temp. probe £13.80) £49.50
- K2903 900A, 750V AC, 9 ranges. £77.50
- Battery operated complete with carry case. (UK C/P £1)
- YF501L 500V/100 Meg. Plus 0-100 ohm £65.00
- K3103 600V/100 Meg. Plus 0-2.6K ohm £109.00
- K3106 500V & 1000V, 1000 & 2000 Meg. £119.00
- K4101 Earth resistance tester £149.00
- M500 Hand cranked insulation tester 500V/100 Meg. £79.50
- K8031 110V/600V phase tester £23.50

- ### AMATEUR RADIO AND CB TESTING
- (Full lists send S.A.E.)
- KDM6 1.5 to 250 MHz 6 range DIP meter (illus) £47.95
- RC1000 0/10/100/1000 watts. SWR etc. 150 MHz max. (illus) £45.00
- CB20 SWR/Power twin meter to 30 MHz 1KW (illus) £8.95
- HM20 20K/Volt multirange multimeter. Plus SWR/Power meter 150 MHz £22.95
- LPM880 RF Power meter 5/20/120W. 1.8 - 500 MHz £84.00
- LPM885 SWR/Power. 20/200/1000W. 1.8 - 54 MHz (illus) £54.00

- ### HAVE A BANANA!
- Low cost reliable meters (All supplied with batts/leads) (UK C/P 55p)
- BANANA 15 range pocket 20K/Volt plus cont. buzzer (illus) £20.64
- KRT101 10 range pocket 1K/Volt £4.95
- T10L 12 range 1K/Volt + overload £5.75
- NH55 10 range pocket 2K/Volt £6.50
- ST5 11 range pocket 4K/Volt £7.50
- NH56R 22 range pocket 20K/Volt £11.50
- YN360TR 19 range plus Hfe test 20K/Volt £14.95
- KRT5001 16 range 10 amp DC range double 50K/Volt £17.95
- ST303TR 21 range plus Hfe Test 20K/Volt £18.95
- TMK500 23 range plus 12A DC plus cont. buzzer 30K/Volt £24.50
- T10L 12 range 1K/Volt + overload £5.75
- NH55 10 range pocket 2K/Volt £6.50
- ST5 11 range pocket 4K/Volt £7.50
- NH56R 22 range pocket 20K/Volt £11.50
- Choose from UK's largest range

AUDIO ELECTRONICS CUBEGATE LIMITED
301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564
ALSO AT HENRYS RADIO, 404/406 EDGWARE ROAD, LONDON W2
WE ARE OPEN 6 DAYS A WEEK - CALL IN AND SEE FOR YOURSELF!

OSCILLOSCOPES

- TRIO CS1566A 20 - 20 MHz dual trace triggered sweep. 5mV/0.5 us/CH2 inV/x 10 mag. 19 sweep ranges. Limited offer. WAS £363.40 NOW £320.00 (UK C/P £4.00)
- HM307 Single trace 10 MHz 5mV/0.5 micro sec. Plus built in component tester 6 x 7cm display (HAMEG) £158.70
- Optional case £18.40
- 3030 Single trace 15 MHz, 5mV/0.5 micro sec. Plus built in component tester. 95mm tube. Trig. to 20 MHz (CROTECH) £172.50
- 3035 Single trace 15 MHz, 5mV. Trig to 20 MHz plus built in component tester 0.2 uSec. 130mm Tube (CROTECH) £189.75
- HM203 Dual 20 MHz. Trig to 30 MHz 5mV/0.5 micro sec. 8 x 10cm display. (HAMEG) £253.00
- CS1562A Dual 10 MHz 10mV. 1 uSec. 140mm tube (TRIO) £267.95
- 3131 Dual trace 15 MHz trig. to 35 MHz 5mV/0.5 micro sec. 130mm tube. plus component tester. £276.00
- CS1575 Dual 5 MHz 1mV 0.5 uSec. 140mm tube. Phase display audio scope (TRIO) £312.80
- CS1560AII Dual 15 MHz 10mV. 0.5 uSec. (TRIO) £341.55
- 3034 Battery-mains dual trace 15 MHz. trig to 20 MHz built in Nicads. 5mV. 0.5 uSec. (CROTECH) £356.50
- (Eliminator charger optional £28.75)
- UK C/P Single track £3 ea. Safgan £3 ea. Dual track £4 ea. SC110 £1.00
- HM412-5 Dual 20 MHz delayed sweep: trig to 40 MHz, 5mV/0.1 micro sec 8 x 10cm display (HAMEG) £402.50 (Optional case £21.85)
- SC110A New Model 10 MHz battery portable. 10mV/0.1 uSec. 2" trace. 140mm tube. (TRIO) £171.00
- (Options: Carry case £6.84, AC Adaptor £5.69, Nicads £8.63)
- CS1820 Dual 20 MHz 2.5mV/0.1 uSec. Delay sweep. 140 mm tube (TRIO) £483.00
- CS1577A Dual 35 MHz 2mV. 0.1 uSec. Single sweep facility. 140mm tube. (TRIO) £523.25
- CS1830H Dual 30 MHz 2mV. 0.2 uSec (fitted delay line). Delay sweep. 140mm tube (TRIO) £626.75
- HM705 Dual 10 MHz delayed sweep: Single sweep: Delay line: Trig to 70 MHz; 2mV/0.1 micro sec. 8 x 10cm display (HAMEG) £667.00
- Range of low cost Dual Trace Scopes mains operated. Made in UK to exacting standards. Available as 10 MHz, 15 MHz, or 20 MHz. All feature 5mV sensitivity. 0.5 micro sec. 6.4 x 8cm display. (SAFGAN)
- OPTIONS HM203/412/705 View Hoods £6.90
- Component Tester £28.75
- DT410 Dual 10 MHz £205.85
- DT415 Dual 15 MHz £217.35
- DT420 Dual 20 MHz £228.85
- Scope probes all models - see below.

- ### FREQUENCY COUNTERS
- (All models battery operated) (UK C/P £1)
- PFM200A Pocket 8 digit LED 200 MHz 10 mV (THANDAR) £67.50
- 8110A 8 digit LED 2 range 100 MHz. Bench (SABTRONICS) £77.00
- 8610A 8 digit LED 3 range 600 MHz Bench (SABTRONICS) £94.00
- 9610B 9 digit LED 3 range 600 MHz Bench (SABTRONICS) £113.85
- 9000B 9 digit LED 3 range 1000 MHz Bench (SABTRONICS) £178.00
- TF400 8 digit LCD 40 MHz (500 MHz with TP600) (THANDAR) £126.50
- TF200 8 digit LCD 2 range 200 MHz (600 MHz with TP600) (THANDAR) £166.75
- TP600 600 MHz prescaler (THANDAR) £43.13
- OPTIONS TF series carry case £6.84 AC adaptors £5.69 'B' series AC Adaptors £5.69 All models probe kits £7.95

- ### TOP QUALITY ANALOGUE MULTIMETERS
- (UK C/P £1.20)
- All featuring AC/DC Volts/Current and Ohms ranges.
- MAJOR 20K 29 range 20K/V. £33.90
- 2 1/2 AC 12 1/2 AC (PANTEC) £40.25
- MAJOR 50K 29 range 50K/V. 2 1/2 AC 12 1/2 AC (PANTEC) £49.95
- M1200 30 range 100K/V. 15A AC/DC. 200 Meg. (ROBIN) £18.50
- PAN3001 34 range 40K/V. 5A AC/DC. 50 Meg. (PANTEC) £59.80
- Also 500KHZ - 500 MHz signal injector and 3 range cap. meter. £66.70
- PAN3003 42 range 1 Meg/V. 5A AC/DC. 1 uA FSD
- (NOTE 3001 & 3003 Electronic Protection Mirror Scales)
- K1400 26 range large scale 20K/Volt: 10A AC/DC. 20 Meg ohm. 5KV AC/DC £95.00
- K200 39 range 10 Meg. ohm input. 25 HZ - 1 MHz £105.00

- ### DIRECT READ HV PROBE
- (UK C/P 65p) 0/40 KV: 20K/Volt £18.40
- ### OSCILLOSCOPE PROBE KITS
- (UK C/P 50p per 1 to 3)
- BNC plug X1 £7.95
- X10 £9.45
- X1 - X10 £10.50
- X100 £16.95
- ### DECADE BOXES
- RSB2 32 value Resis. box. 1 ohm to 4 Meg. £18.50
- CSB20 20 Value Cap. box. 470 pf to 1 uF £21.00
- ### PORTABLE TV COUNTER GENERATOR
- MC101 8 patterns/dots/lines etc. Built in Nicads. Pat B UHF only. Complete with charger, case and leads. £162.50

- ### VARIABLE POWER SUPPLIES
- Mains input - Volts/Amps meter (UK C/P £1)
- PP241 0/12, 12/24 Volt. £35.00
- 0/1 amp
- PP243 0/12, 12/24 Volt. £59.95
- 0/3 amp
- ### 'SCOPE ADD ON UNITS
- LTC905 Semiconductor curve tracer (illus) (LEADER) £95.45 (UK C/P 85p)
- H265 Component tester (HAMEG) (UK C/P 65p) £27.95

- ### DIRECT READ TEMPERATURE
- TH301 -50°C to +750°C LCD readout. Complete with battery and thermocouple. £68.43
- ### LOGIC PROBES/MONITOR
- Sabtronics LP10 10 MHz £28.50
- GSC LP2 1.5 MHz probe £19.95
- LEADER LDP076 50 MHz (with case) £56.90
- GSC LM1 monitor (8 to 16 pin IC) £33.00
- GSC DPL Digital pulsar. Single/100 pps £58.50

ALL PRICES INCLUDE VAT

FREE CATALOGUE

Order by Post with CHEQUES/ ACCESS/VISA or Telephone your order

Allow up to 10 days for delivery (unless advised)


Send large SAE (20p UK) Schools, Companies, etc. Please write in.

WW - 010 FOR FURTHER DETAILS

WIRELESS WORLD AUGUST 1982

10 into 1 Does Go.

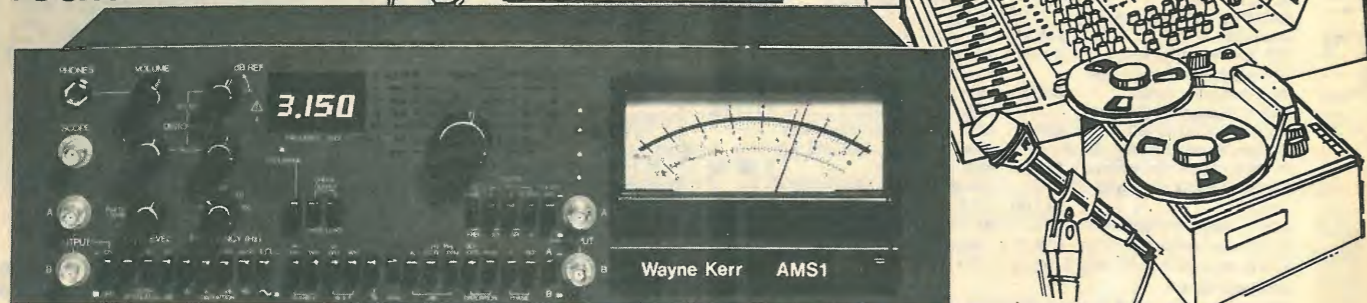Complete audio measuring system see the 10 features...



1. Freq. Counter, 2. Oscillator, 3. Noisemeter, 4. Wow & Flutter meter, 5. Level Meter, 6. Distortion,
7. Phase, 8. Power, 9. Drift, 10. Rumble.

Already in use from the small service workshop to Audio Equipment manufacturers to professional studio to IBA Broadcast station to the "BBC". AMS1 provides the solution.

Saves time, saves space, saves capital equipment cost, saves earthing problems. Transportable and easy to use. This low cost comprehensive audio workshop meets the latest specifications for Audio Measurement with accuracies equivalent to many of its stand alone counterparts.

10 Instruments, 15 Measurements for the price of One. That's the AMS1... from Wayne Kerr.

Belgium - Simac Electronics SPRL. Tel: 022192453. Telex: 23662. France - Tekelec Airtronic. Tel: 5347535. Telex: 204552. Netherlands - C.N. Flood B.V. Tel: 996360. Telex: 31238. Sweden - Scandia Metric AB. Tel: 20400. Telex: 10766. West Germany - Keithley Instruments GmbH. Tel: 7144065. Telex: 5212160. Italy - Telav International SRL. Tel: 4455741. Telex: 312627. Spain - Unirtronics SA. Tel: 2425204. Telex: 22596. Eastern Europe, USSR, China - Data Loop Ltd. Tel: 0306 81166. Telex: 859417. South Africa - Telkor Pty Limited. Tel: 011 489740. Telex: 4-22171.

WAYNE KERR
WKR Limited Durban Road
Bognor Regis
West Sussex PO22 9RL England
Tel: (0243) 825811 Telex: 86120

WW - 029 FOR FURTHER DETAILS

ELECTROVALUE

A SPECIAL SUMMER PROMOTION

FREE VOUCHERS TO SAVE YOU UP TO £2.10

Send for Catalogue 82 before August 31 (60 pages, A4-70p post paid) and we give you THREE 70p REFUND VOUCHERS FREE valid for spending singly at any time on any one C.W.O. order minimum list value £10 to quickly save you a total of £2.10. Send 70p now for your EV Catalogue 82 + 3 free vouchers by return... and all in addition to the other benefits (discounts, guarantees to spec., brand new stock, etc) you enjoy by buying from Electrovalue.

+ USUAL DISCOUNTS + FREE POSTAGE

DISCOUNTS
5% on orders over £23 (inc. V.A.T.)
10% on orders over £57.50 (inc. V.A.T.)
on most catalogue items but not on payments by credit cards.
POSTAGE
Not charged on U.K. orders over £5.75 (inc. V.A.T.). If under, add 40p handling charge.

★ SEMICONDUCTORS/ICs/OPTRONICS
★ COMPUTERS/SOFTWARE, etc
★ CAPACITORS/RESISTORS
★ CONNECTORS/SWITCHES/KNOBS
★ POTS/FERRITES/METERS
★ BOOKS/SOLDER TOOLS

and more and more and more

ELECTROVALUE LTD. 28A St. Jude's Road, Englefield Green, Egham, Surrey TW20 0HB. Telephone Egham 33603 (London 87 33603; STD 0794 33603) Telex 264475 Northern Branch (Shop service only) 680 Burnage Lane, Manchester M19 1NA. Telephone 061-432 4945.

EV88 - A low-cost evaluation system for the 8088 microprocessor

EV88 is a single board microcomputer that is ideal for evaluating the 8088 8-bit/16-bit microprocessor. EV88 can also be used as a powerful controller, and, with a suitable cross-assembler running on a standard microcomputer, and an EPROM programmer, for low-cost development of 8088-based systems.

EV88 is supplied fully assembled and tested, with comprehensive documentation, and a copy of The 8086 Book, by Rector and Alexy. All you need is a 5V 1A power supply and a terminal or a suitable microcomputer.

- ★ 8088 microprocessor in minimum mode (software compatible with the 8086 16-bit microprocessor).
 - ★ Comprehensive monitor in 2K EPROM.
 - ★ 2K CMOS RAM.
 - ★ Cassette interface.
 - ★ 24 lines of I/O.
 - ★ Eight levels of interrupt.
 - ★ RS-232 compatible serial interface (300 baud to 9600 baud).
 - ★ Three-channel counter/timer.
 - ★ Buffered data, address and control lines.
 - ★ Double Eurocard.
 - ★ On-board expansion to 16K EPROM/RAM (sockets provided).
 - ★ Breadboarding area.
 - ★ All bus signals available on 64-way DIN 41612 connector.
 - ★ Single 5V supply.
 - ★ Price £300 plus VAT. Includes delivery.
- 8088/8086 design service available (software and hardware).

LFH Associates Ltd.
40A High Street
Stony Stratford
Milton Keynes
(0908) 566660

WW - 065 FOR FURTHER DETAILS

PRINTED CIRCUITS FOR WIRELESS WORLD PROJECTS

Audio compressor/limiter—Dec. 1975—1 s.s. (stereo)	£4.25
Cassette recorder—May 1976—1 s.s.	£5.00
Audio compander—July 1976—1 s.s.	£4.25
Audio preamplifier—November 1976—2 s.s.	£8.50
Additional circuits—October 1977—1 s.s.	£4.00
Stereo coder—April 1977—1 d.s. 2 s.s.	£8.50
Low distortion disc amplifier (stereo)—September 1977—1 s.s.	£2.00
Low distortion audio oscillator—September 1977—1 s.s.	£3.50
Synthesized f.m. transceiver—November 1977—2 d.s. 1 s.s.	£12.00
Morsemaker—June 1978—1 d.s.	£4.50
Metal detector—July 1978—1 d.s.	£3.75
Oscilloscope waveform store—October 1978—4 d.s.	£18.00
Regulator for car alternator—August 1978—1 s.s.	£2.00
Wideband noise reducer—November 1978—1 d.s.	£5.00
Versatile noise generator—January 1979—1 s.s.	£5.00
200MHz frequency meter—January 1979—1 d.s.	£7.00
High performance preamplifier—February 1979—1 s.s.	£5.50
Distortion meter and oscillator—July 1979—2 s.s.	£5.50
Moving coil preamplifier—August 1979—1 s.s.	£3.50
Multi-mode transceiver—October 1979—10 d.s.	£35.00
Amplification system—Oct. 1979—3 preamp 1 poweramp	£4.20 each
Digital capacitance meter—April 1980—2 s.s.	£7.50
Colour graphics system—April 1980—1 d.s.	£18.50
Audio spectrum analyser—May 1980—3 s.s.	£10.50
Multi-section equalizer—June 1980—2 s.s.	£8.00
Floating-bridge power amp—Oct. 1980—1 s.s. (12V or 40V)	£4.00
Nanocomp 6802 or 6809—Jan, July, 1981—1 d.s. 1 s.s.	£9.00
Cassette interface—July, 1981—1 s.s.	£1.50
Eprom programmer—Jan., 1982—1 d.s.	£4.50
Logic probe—Feb., 1981—2 d.s.	£6.00
Modular frequency counters—March, 1981—8 s.s.	£20.00
Opto electronic contact breaker (Delco)—April, 1981—2 s.s.	£4.00
CB synthesiser—Sept. 1—1 d.s.	£6.00
Electronic ignition—March, 1982—1 s.s.	£4.00

Boards and glassfibre roller-tinned and drilled. Prices include VAT and UK postage. Airmail add 30%, Europe add 10%. Insurance 10%. Remittance with order to:

M. R. SAGIN, NANCARRAS MILL, THE LEVEL CONSTANTINE, FALMOUTH, CORNWALL

WW - 037 FOR FURTHER DETAILS

SAFGAN DT-400 Series BRITISH MAKE DUAL TRACE 'SCOPES



NEW 20MHz

LOW COST

DT-410 £175*
DT-415 £185*
DT-420 £195*
* Ex V.A.T.

RELIABLE WITH 18 months GUARANTEE

DT-410, 10 MHz	DT-415 15MHz	DT-420 20MHz
★ CH1, CH2: 5mv/div—20v/div.	★ External Trigger	★ Z-Modulation.
★ Time Base: 1 sec/div—100ns/div.	★ CAL output 1v 1kHz.	★ Graticule blue ruled 8x10 div. (4in. CRT).
★ XY Facility: Matched XY inputs.	★ Size: H215mm, W165mm, D280mm.	★ Weight: 4kg.
★ Trigger: Level control, ± Slope selection.		
★ Auto, Normal, TV Triggering.		

PROBE (XI-REF-X10) £11.50

SAFGAN ELECTRONICS LTD.
OMEGA ROAD, WOKING, SURREY TEL WOKING (04862) 69560
Carriage: England & Wales £7.50 + V.A.T.; Scotland £10.50 + V.A.T.
London Stockist: Audio Electronics - Tel: 01-724 3564
North-West Stockist: Darom Supplies, Warrington, Ches. - Tel: Warrington 64764
Avon Stockist: L. F. Hanney, Bath - Tel: Bath 24811
Cardiff Stockist: Steve's Electronics Supply Co., Cardiff - Tel: (0222) 41905
Cheshire Stockist: Kay's Electronics, Chesterfield - Tel: (0246) 31695
Newcastle Stockist: Aikman Bros. & Co., Newcastle - Tel: 0632 26728
Birmingham Stockist: P.A.T.H. Electronic Services - Tel: 021-327 2339
Derby Stockist: RTS, Derby - Tel: (0332) 41235

WW - 055 FOR FURTHER DETAILS


ACTIVE COMPONENTS MAIL ORDER SPECIALISTS

Lowest Prices — Fastest Delivery

DEVICE	PRICE	DEVICE	PRICE	DEVICE	PRICE	DEVICE	PRICE
MEMORIES		REGULATORS		4520	0.69	LOW PROFILE—	
2114 Low power	0.80	7805	0.39	4526	0.70	GOLD	
200ns	2.79	7812	0.39	4528	0.70	8-pin	0.22
2708 450ns	2.79	7815	0.29	4541	0.99	14-pin	0.29
2716 450ns	2.29	7816	0.29	4543	0.99	16-pin	0.31
(+5v)		7818	0.29			18-pin	0.33
2716 350ns	3.59	7815	0.29	74LS SERIES		20-pin	0.35
450ns	5.95	7905	0.55	74LS00	0.10	22-pin	0.40
2732 450ns	3.90	7912	0.55	74LS01	0.11	24-pin	0.42
2732 350ns	4.40	7915	0.55	74LS02	0.12	28-pin	0.54
2532 450ns	3.90	LM309K	0.99	74LS03	0.12	40-pin	0.81
4116 200ns	0.70	LM317K	3.20	74LS04	0.12		
4118 200ns	0.84	LM323K	4.95	74LS05	0.13		
4184 200ns	4.65			74LS08	0.12		
4516/4816	3.25	280 FAMILY		74LS09	0.12		
100ns	3.25	280A CPU	3.49	74LS10	0.12	DIL JUMPERS	
5516 200ns	3.38	280A CTC	3.99	74LS11	0.12	24in Cable single	
6116 200ns	5.10	280A CTC	2.99	74LS12	0.12	ended 14-pin	1.40
150ns	7.61	280A DART	5.70	74LS13	0.22	24in Cable single	
		280A DMA	11.95	74LS14	0.12	ended 16-pin	1.80
		280A P10	2.85	74LS15	0.12	24in Cable single	
		280A P10	3.15	74LS16	0.12	ended 24-pin	2.35
		280A P10	11.99	74LS17	0.15	24in Cable double	
		280A P10	3.15	74LS18	0.15	ended 40-pin	3.25
		280A P10	11.99	74LS19	0.15	6in Cable double	
		280A P10	11.99	74LS20	0.12	ended 16-pin	1.90
		280A P10	11.99	74LS21	0.12	6in Cable double	
		280A P10	11.99	74LS22	0.15	ended 24-pin	3.10
		280A P10	11.99	74LS23	0.15	6in Cable double	
		280A P10	11.99	74LS24	0.12	ended 40-pin	4.85
		280A P10	11.99	74LS25	0.33	12in Cable double	
		280A P10	11.99	74LS26	0.39	ended 14-pin	2.00
		280A P10	11.99	74LS27	0.39	12in Cable double	
		280A P10	11.99	74LS28	0.39	ended 16-pin	2.15
		280A P10	11.99	74LS29	0.39	12in Cable double	
		280A P10	11.99	74LS30	0.39	ended 24-pin	3.25
		280A P10	11.99	74LS31	0.39	12in Cable double	
		280A P10	11.99	74LS32	0.39	ended 40-pin	5.10
		280A P10	11.99	74LS33	0.39	16in Cable double	
		280A P10	11.99	74LS34	0.39	ended 14-pin	2.05
		280A P10	11.99	74LS35	0.39	18in Cable double	
		280A P10	11.99	74LS36	0.39	ended 16-pin	2.25
		280A P10	11.99	74LS37	0.39	16in Cable double	
		280A P10	11.99	74LS38	0.39	ended 24-pin	3.40
		280A P10	11.99	74LS39	0.39	18in Cable double	
		280A P10	11.99	74LS40	0.39	ended 40-pin	5.25
		280A P10	11.99	74LS41	0.39		
		280A P10	11.99	74LS42	0.39		
		280A P10	11.99	74LS43	0.39		
		280A P10	11.99	74LS44	0.39		
		280A P10	11.99	74LS45	0.39		
		280A P10	11.99	74LS46	0.39		
		280A P10	11.99	74LS47	0.39		
		280A P10	11.99	74LS48	0.39		
		280A P10	11.99	74LS49	0.39		
		280A P10	11.99	74LS50	0.39		
		280A P10	11.99	74LS51	0.39		
		280A P10	11.99	74LS52	0.39		
		280A P10	11.99	74LS53	0.39		
		280A P10	11.99	74LS54	0.39		
		280A P10	11.99	74LS55	0.39		
		280A P10	11.99	74LS56	0.39		
		280A P10	11.99	74LS57	0.39		
		280A P10	11.99	74LS58	0.39		
		280A P10	11.99	74LS59	0.39		
		280A P10	11.99	74LS60	0.39		
		280A P10	11.99	74LS61	0.39		
		280A P10	11.99	74LS62	0.39		
		280A P10	11.99	74LS63	0.39		
		280A P10	11.99	74LS64	0.39		
		280A P10	11.99	74LS65	0.39		
		280A P10	11.99	74LS66	0.39		
		280A P10	11.99	74LS67	0.39		
		280A P10	11.99	74LS68	0.39		
		280A P10	11.99	74LS69	0.39		
		280A P10	11.99	74LS70	0.39		
		280A P10	11.99	74LS71	0.39		
		280A P10	11.99	74LS72	0.39		
		280A P10	11.99	74LS73	0.39		
		280A P10	11.99	74LS74	0.39		
		280A P10	11.99	74LS75	0.39		
		280A P10	11.99	74LS76	0.39		
		280A P10	11.99	74LS77	0.39		
		280A P10	11.99	74LS78	0.39		
		280A P10	11.99	74LS79	0.39		
		280A P10	11.99	74LS80	0.39		
		280A P10	11.99	74LS81	0.39		
		280A P10	11.99	74LS82	0.39		
		280A P10	11.99	74LS83	0.39		
		280A P10	11.99	74LS84	0.39		
		280A P10	11.99	74LS85	0.39		
		280A P10	11.99	74LS86	0.39		
		280A P10	11.99	74LS87	0.39		
		280A P10	11.99	74LS88	0.39		

Marconi Type R1020 Hinged antenna column.

Easy to raise Easy to lower

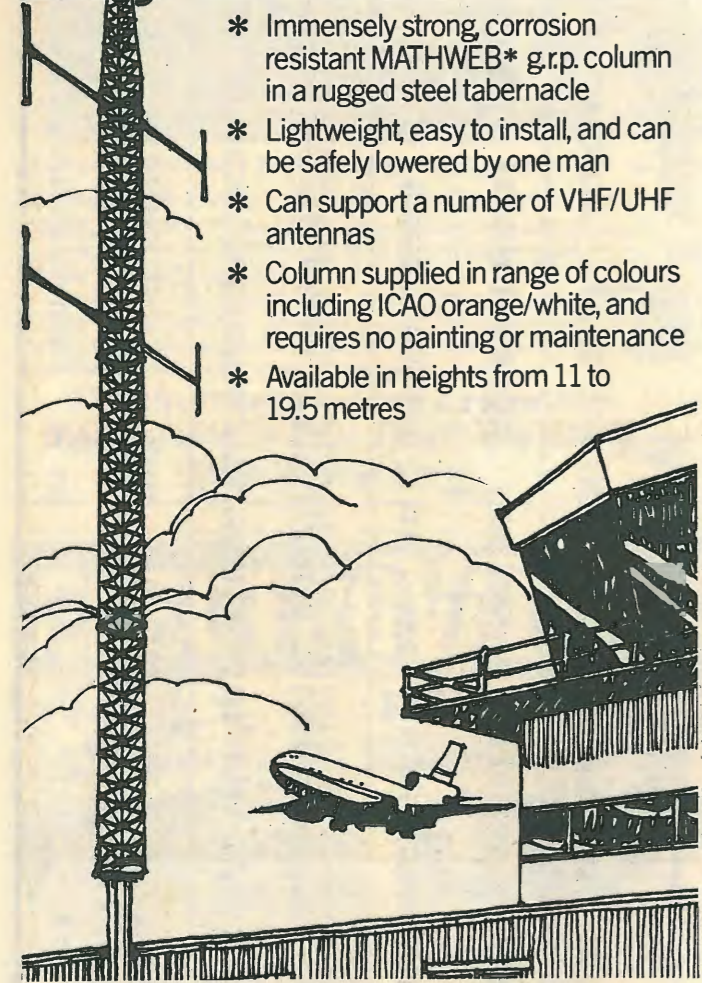

- * Immensely strong, corrosion resistant MATHWEB* g.r.p. column in a rugged steel tabernacle
- * Lightweight, easy to install, and can be safely lowered by one man
- * Can support a number of VHF/UHF antennas
- * Column supplied in range of colours including ICAO orange/white, and requires no painting or maintenance
- * Available in heights from 11 to 19.5 metres

OTHER MARCONI SUPPORT STRUCTURES

Include the MATHWEB* Lattice Antenna Mast Type R1010, and the Triangular Section Tubular Steel Self Supporting Tower Type R1060.

For details of these and other Marconi Antennas products please contact Chris Pettitt, Marketing Manager, Antenna Systems Division.

*MATHWEB is a registered trademark of the BP Group

Marconi Antennas

Marconi Communications Systems Limited
Lane Works, Waterhouse Lane, Chelmsford CM1 2QX, England
Tel: 0245 67111 Telex: 99108

A GEC-Marconi Electronics Company

WW - 014 FOR FURTHER DETAILS

VALVES			Minimum Order £1	VALVES VAT IS INCLUDED							
A1065	1.40	EL821	8.20	SC1/600	4.50	6AN8A	0.80	12AU7	0.80	6146	4.95
A2293	8.90	EL222	9.95	SP61	1.90	6A04	3.40	12AV6	0.95	6146B	5.20
A2900	13.75	EM80	0.85	TT21	23.00	6A05	1.00	12AX7	0.85	6360	2.85
AR8	0.75	EM87	1.30	TT22	18.50	6A05B	1.80	12BA6	0.90	6550	6.60
ARP3	0.70	EY51	0.95	U25	1.15	6A56	1.15	12BE6	1.25	6870	14.00
ATF4	0.60	EY81	0.65	U26	1.15	6AT6	0.90	12BH7	1.95	8552	8.20
B124	3.90	EY86/87	0.20	U27	1.15	6AU6	0.60	12BY7A	0.70	1299	2.85
CV31	1.40	EY88	0.65	U191	0.85	6AV6	0.85	12C8	0.85	3P1	11.00
DAF96	0.70	EZ80	0.70	U281	0.70	6AX4GT	1.30	12E1	18.95	5FP7	18.00
DET72	28.95	EZ81	0.70	U301	0.65	6AX5GT	1.30	12J5GT	0.55	4EP1	32.00
DF96	0.70	GM4	5.90	UB01	11.50	6BA6	0.55	12K7GT	0.70	88J	14.00
DH76	0.75	GY501	1.30	UB01	0.90	6BE6	0.60	12K8GT	0.80	88L	14.00
DL92	0.60	GZ32	1.05	UBC41	1.20	6BG6G	1.20	12Q7GT	0.80	CV1526	16.00
DY86/87	0.65	GZ33	4.20	UABC80	0.75	6BJ6	1.30	12SC7	0.85	DG7-32	34.80
DY802	0.70	GZ34	2.75	UAF42	1.20	6BQ7A	0.85	12SH7	0.85	DG7-36	36.00
E5L	14.90	GZ37	3.95	UBF80	0.70	6BF7	4.80	12SL7	0.70	DM9-11	38.40
EB8CC	1.80	KT66	8.30	UBF89	0.70	6BW6	6.20	12SQ7	1.45	DP3-33GM	41.80
EB8CC/01	3.10		9.20*	UBL21	1.75	6BW7	0.90	12SQ7GT	0.85		
E92CC	2.80	KT88	8.95	UCC84	0.85	6C4	0.50	12Y4	0.70	* spec Q	
E180CC	4.20		13.80*	UCC85	0.70	6C8	0.55	13D3	0.70		
E190F	7.75	MH4	2.50	3CF90	1.90	6CH6	6.20	13D5	0.90		
E182CC	6.25	ML6	2.50	UCH42	1.85	6CL6	2.75	13D6	0.80	PLUMBICON	
EA76	2.25	MX10/01	21.50	UCH81	0.75	6CX8	3.80	14S7	1.15	P800 3LF	
EABC80	0.80	N78	9.90	UCL82	0.95	6CY5	1.15	19A05	0.85	P800 IR	
EB91	0.60	OA2	0.70	UF4	1.35	6D5	0.70	19G3	11.50	P800 IB	
EB33	1.15	OB2	0.80	UF80	0.95	6F6	1.80	19G6	8.50	XQ1020R	
EB30	0.90	PAB80	0.60	UF85	0.95	6F6GB	1.10	19H5	39.55	XQ1020B	
EBF80	0.60	PC85	0.75	UL84	0.95	6F7	2.80	20D1	0.80		
EBF83	0.60	PC86	0.85	UM80	0.90	6F8G	0.85	20F2	0.85	SPECIAL V	
EBF89	0.60	PC88	0.90	UM84	0.70	6F12	1.50	20E1	1.30	4CX1000A	
EC32	0.65	PC97	1.20	UY82	0.70	6F14	2.05	20P1	0.85	4CX5000A	
EC91	4.40	PC900	0.90	UY85	0.85	6F15	1.30	20P3	0.75	YL 1420	
EC92	0.85	PCC84	0.50	VR105/30	1.25	6F17	3.20	20P4	1.25	YL 1430	
EC81	0.85	PCC89	0.65	VR150/30	1.35	6F23	0.75	20P5	1.35	YL 1440	
EC32	0.60	PCC189	0.85	XG6	0.95	6F24	1.75	25LGT	0.95	BW 153	
EC33	0.85	PCF32	1.90	XG1M	1.70	6F33	10.50	25Z4G	0.75	DM 25LB	
EC34	0.60	PCF82	0.70	XR1-6400A	6FH8	4.20	30C15	0.50	YL 1420		
EC35	0.60	PCF84	0.75		82.90	6GA8	1.95	30C17	0.50	YL 1430	
EC36	1.70	PCF86	1.50	Z759	19.00	6GH8A	0.95	30C18	2.45	YL 1440	
EC37	0.80	PCF87	0.50	Z768	0.75	6H6	1.15	30F5	1.15	GXU6	
EC38	0.95	PCF200	1.45	Z800U	3.45	6I4	1.35	30F12	1.40	CV1597	
EC39	0.90	PCF201	1.85	Z801U	3.75	6I4WA	2.00	30F12	1.25	CV2116	
EC40	0.85	PCF800	0.50	Z803U	16.00	6J5	2.30	30F14	2.15	BR 178	
EC41	0.65	PCF801	1.75	Z900T	2.45	6J5GT	0.90	30L15	1.10	CV6131	
EC42	0.85	PCF802	0.70	1A3	0.65	6J6	0.90	30P12	1.15	GMU 2	
EC43	3.25	PCF802	1.10	1L4	0.50	6J6W	0.90	30P12	1.15	TY4-500	
EC44	1.70	PCF808	1.45	1R5	0.60	6J6EC	2.95	30P13	1.25	BK485/5552A	
EC45	2.10*	PCH200	1.35	1S4	0.45	6J6C	2.95	30P14	2.45	MIL 5948/1754	
EC46	1.20	PCL81	0.75	1S5	0.45	6K7	0.80	35L6GT	1.40	IC	
EC47	0.70	PCL82	0.95	1T4	0.45	6K6	3.35	35L7	1.30	SN5402N	0.28
EC48	0.80	PCL84	0.90	1U4	0.80	6L6M	2.80	35Z4GT	0.80	SN5410F	2.32
EC49	0.70	PCL86	0.75	1X2B	1.40	6L6G	2.50	60C5	1.15	SN5470F	0.48
EC50	0.75	PCL805/85	0.95	2D21	1.10	6L6GC	2.10	50C6G	1.35	SN54196J	1.20
EC51	1.40	PD500/510	3.40	2K25	1.85*	6L6GT	1.25	75B1	1.25	SN7407N	0.28
EC52	0.85	PFL200	1.10	2K26	16.95	6L7G	1.85	75C1	1.70	SN7408N	0.18
EC53	0.80	PFL200	2.80*		24.50*	6L18	0.70	76	0.95	SN74453P	1.10
EC54	1.15	PL36	1.10	2X2	1.15	6L06	2.95	78	0.95	SN7407N	0.28
EC55	2.25	PL81	0.85	3A4	0.70	6LD20	0.70	80	1.70	SN7408N	0.18
EC56	0.65	PL82	0.70	3AT2	2.40	6K6GA	2.70	85A2	1.40	SN74453P	1.10
EC57	1.75	PL83	0.90	3D7G	0.30	6J5	1.00	807	1.25	SN7453N	0.18
EC58	0.60	PL84	0.95	3D22	23.00	6SA7	1.00	807	1.25	SN7473N	0.38
EC59	0.75	PL504	1.00	3E29	19.00	6S7	1.15	813	1.90*	SN7474N	0.30
EC60	1.05	PL508	1.95	3S4	0.60	6S7J	1.05	813	19.32	SN7474N	0.30
EC61	1.50	PL509	3.20	4B32	18.25	6SK7	0.95	829B	68.50*	SN7485N	0.95
EC62	2.90	PL510	5.95*	5B/254M	16.90	6SL7GT	0.85	829B	14.00	SN7485N	0.95
EC63	0.65	PL519	3.95	5B/255M	14.50	6SN7GT	0.80	832A	8.90	SN7491AN	0.32
EC64	0.60	PL519	6.10*	5B/258M	12.50	6SR7	1.10	866A	3.80	SN74123N	0.42
EC65	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC66	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC67	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC68	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC69	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC70	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC71	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC72	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC73	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC74	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC75	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC76	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC77	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC78	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC79	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EC80	0.80	PL802	3.20	5C22	29.90	6SQ7	0.95	866E	6.25	DM74123N	0.38
EL1	2.45	PY809	6.45	6/30L2	0.90	7B7	1.75	2051	2.80	MC14511BA	
EL2	0.70	PY801	0.80	6AB7	0.70	8B8N	2.95	5763	4.20	B1702AL	3.30
EL3	0.80	QV03/10	7.50	6AC7	1.15	9D2	0.70	5842	7.50	MM6300-LJ	
EL4	0.95	QV03-20A	6A4G	0.75	6V6GT	0.90	1625	1.80	MC6800P	5.80	
EL5	1.00		21.50	6AH6	1.15	10C2	0.85	5933	6.80	MCM6810AP	
EL6	4.20	QV03-25A	6AK5	0.65	10F18	0.70	6057	2.20	2.20	3.80	
EL7	0.80		38.50	6AK8	0.80	10P13	1.50	6060	1.95	MCM6810AP	
EL8	1.70	QV06/40A	6ALE	0.60	11E2	19.50	6064	2.30	6340-1J	3.60	
EL9	5.90		16.10	6ALSW	0.85	12A6	0.70	6065	3.20	6340-1J	3.60
EL10	3.95	QV03-12	4.20	6AM5	4.20	12AT6	0.70	6067	2.30	MIC945-5D	0.22
EL11	1.70	SC1/400	4.50	6AM6	1.50	12A7B	0.65	6080	5.30	MIC936-5D	0.22

VALVES AND TRANSISTORS
Telephone enquiries for valves, transistors, etc: retail 749 3934, trade and export 743 0699.
D10 CABLE FIELD TELEPHONES
Geiger Muller Tubes GM4, MX12/01 and others.

TEST SET FT2 FOR TESTING Transceivers A40, A41, A42 and CPR26.
HARNESSES "A" & "B" CONTROL UNITS "A" "R" "J1" "J2" Microphones No 5, 6, 7 connectors, frames, carrier sets, etc.
DRUM CABLE continuous connection YC 00433.

Signal Generators MARCONI TF 144H/4S; TF144H/6S 10 kHz-72MHz
Prices on application

COLOMOR (ELECTRONICS LTD.)
170 Goldhawk Rd., London W.12
Tel. 01-743 0899 or 01-749 3934
Open Monday to Friday
9 a.m. - 5.30 p.m.

ScheTronics Limited

For repair and calibration of test equipment. We also have the following second user LF/HF equipment for sale.

Siemens including Pegamat - W & G - H.P. - Hatfield
Anritsu - Marconi - Fluke - STC - etc...


Unit 10, Dunstall Estate
Crabtree Manorway
Belvedere, Kent DA17 6AW
Telephone: 01-311 9657

WW - 066 FOR FURTHER DETAILS

STOP WASTING TIME TESTING BOARDS

MD will pin-point microtroubles in seconds. Portable and simple to use by non-technical staff in the REPAIR SHOP or on the PRODUCTION LINE, MD tests ROM, RAM & I/O and prints diagnostic reports. MICRODOCTOR can be plugged into an unknown system to perform a general diagnostic and print a MEMORY-MAP. The ENGINEER may enter specifics of CHECKSUMS and RAMTESTS, READS and WRITES to specific MEMORY and I/O locations, SHORTING tests on DATA and ADDRESS LINES, PRINT-OUTS of memory in ASCII or HEX. These sequences are retained in CONTINUOUS MEMORY, available always at the push of a key.

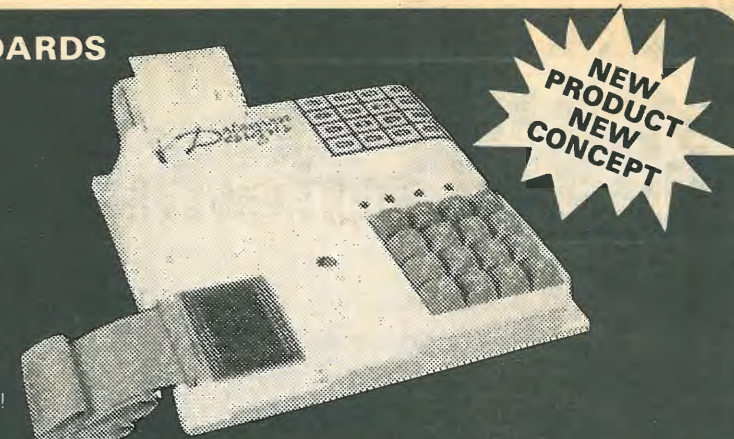★ FREE Z80 DISASSEMBLER with each MD (other disassemblers soon to retrofit at low cost). Get a DISASSEMBLER LISTING of ROM in any microsystem! MICRODOCTOR — £295.00




NEW PRODUCT NEW CONCEPT

INTELLIGENT EPROM PROGRAMMER

Good tools need not

HART

LINSLEY HOOD CASSETTE RECORDER 2

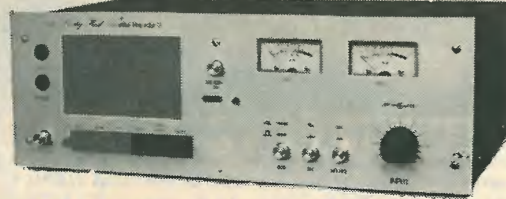

Our new improved performance model of the Linsley Hood Cassette Recorder incorporates our VFL 910 vertical front mechanism and circuit modifications to increase dynamic range. Board layouts have been altered and improved but retain the outstandingly successful mother-and-daughter arrangement used on our Linsley-Hood Cassette Recorder 1. This latest version has the following extra features: Ultra low wow-and-flutter of .09% - easily meets DIN Hi-Fi spec. Deck controls latch in rewind modes and do not have to be held. Full Auto-stop on all modes. Tape counter with memory rewind. Oil damped cassette door. Latching record button for level setting. Dual concentric input level controls. Phone output. Microphone input facility if required. Record interlock prevents rerecording on valued cassettes. Frequency generating feedback servo drive motor with built-in speed control for thermal stability. All these desirable and useful features added to the excellent design of the Linsley-Hood circuits and the quality of the components used makes this new kit comparable with built-up units of much higher cost than the modest, £94.90 + V.A.T. we ask for the complete kit.

LINSLEY HOOD CASSETTE RECORDER 1



We are the Designer Approved suppliers of kits for this excellent design. The Author's reputation tells all you need to know about the circuitry and Hart expertise and experience guarantees the engineering design of the kit. Advanced features include: High-quality separate VU meters with excellent ballistics. Controls, switches and sockets mounted on PCB to eliminate difficult wiring. Proper moulded escutcheon for cassette aperture improves appearance and removes the need for the cassette transport to be set back behind a narrow finger trapping slot. Easy to use, robust Lenco mechanism. Switched bias and equalisation for different tape formulations. All wiring is terminated with plugs and sockets for easy assembly and test. Sophisticated modular PCB system gives a spacious, easily-built and tested layout. All these features added to the high-quality metalwork make this a most satisfying kit to build. Also included at no extra cost is our latest HS 16 Sendust Alloy super head, available separately at £8.20 but included free with the complete kit at £75 plus VAT. Reprints of the 3 original articles describing this design 45p. No VAT. Reprint of the subsequent postscript article 30p. No VAT.

PRACTICAL WIRELESS 'WINTON' TUNER

Brilliant new Ted Rule designed Tuner with everything! Gives you fantastic stereo f/m reception with pilot cancelling decoder i.c., fluorescent display, digital frequency readout along with clock and timer functions. In addition to f.m. covers l.w., m.w., s.w. and even TV sound. Further details are in our lists; send for your copy.

Part Cost of Post, Packing and Insurance
Order up to £10 - 50p
Orders £10 to £49 - £1
Over £50 - £1.50

P&P Export Orders - Postage or shipping at cost plus £2 Documentation and Handling

Please send 9 x 4 S.A.E. or telephone for lists giving fuller details and price breakdowns.

Instant easy ordering, telephone your requirements and credit card number to us on Oswestry (0691) 2894.

ERASERS FOR THE DEVELOPMENT LAB



UVIT
Powerful, compact unit to erase up to six EPROMs quickly and safely. 10-60-minute electronic timer.
£59.13 + V.A.T.

UVIB
As above but without timer.
£46.95 + V.A.T.

Carriage paid (U.K.)

Send cheque or official order for prompt delivery.

Also available in London from:
Technomatic Ltd
Henrys Radio
Ambit International

IN USE IN DESIGN LABS & EDUCATIONAL ESTABLISHMENTS AROUND THE WORLD

NORTHERN ELECTRONICS

51 Arundel Street, Mossley, Lancashire Tel: Mossley (04575) 4119

WW - 047 FOR FURTHER DETAILS

LINSLEY-HOOD 300 SERIES AMPLIFIERS



These latest designs from the drawing board of John Linsley-Hood, engineered to the very highest standard, represent the very best that is available on the kit market today. The delicacy and transparency of the tone quality enable these amplifiers to outperform, on a side-by-side comparison, the bulk of amplifiers in the commercial market-place and even exceed the high standard set by his earlier 75-watt design. Three versions are offered, a 30-watt with Darlington output transistors, and a 35- and 45-watt, both with Mosfet output devices. All are of identical outside appearance which is designed to match and stack with our Linsley-Hood cassette recorder 2. As with all Hart kits the constructors interests have been looked after in a unique way by reducing the conventional (and boring) wiring almost to the point of extinction. Any of these kits represents a most cost-effective route to the very highest sound quality with the extra bonus of the enjoyment of building a sophisticated piece of equipment. 30-watt Darlington amplifier, fully integrated with tone controls and magnetic pick-up facility. Total cost of all parts is £81.12. Special offer price for complete kits £72. 35-watt Mosfet amplifier. Total cost of parts £98.41. Special offer for complete kits, £87.40. 45-watt Mosfet amplifier. Total cost of parts £104.95. Special offer price for complete kits £94.80.

[Reprints of original Articles from Hi-Fi News 50p. Post free. No VAT. Reprints of MOSFET article 25p. No V.A.T. Post free.

FEED YOUR MICRO BYTES WITH OUR SOLENOID CONTROLLED CASSETTE DECK



Front loading deck with full solenoid control of all functions including optional read in fast wind modes. 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £2.70 plus V.A.T. and 50p postage.

CASSETTE HEADS

HS16 SENDUST ALLOY SUPER HEAD. Stereo R/P. Longer life than Permalloy. Higher output than Ferrite. Fantastic frequency response. Complete with data..... £8.20
HC20 Stereo Permalloy R/P head for replacement uses in car players, etc..... £4.25
HM90 Stereo R/P head for METAL tape. Complete with data..... £7.20
H51 Special Erase Head for METAL tape..... £4.90
H524 Standard Ferrite Erase Head..... £1.50
4-Track R/P Head. Standard Mounting..... £7.40
R484 2/2 (Double Mono) R/P Head. Std. Mtg..... £4.90
ME151 2/2 Ferrite Erase. Large Mtg..... £4.25
CCE/6M 2/2 Erase. Std. Mtg..... £7.90

All prices plus VAT

HART

HART ELECTRONIC KITS LTD
OSWESTRY
SHROPSHIRE
phone (0691) 2894
Telex 35661
Hartel G

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTITIES OF COMPONENTS BECOME REDUNDANT. WE ARE CASH PURCHASERS OF SUCH MATERIALS AND WOULD APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE. WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner

Telephone 445 2713/0749

(9461)

WW - 043 FOR FURTHER DETAILS



Bigger and Better for 1982
the colourful Wilmslow Audio brochure
- the definitive loudspeaker catalogue!

Everything for the speaker constructor - kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort of our ★ two listening lounges (Customer operated demonstration facilities)
- ★ Ample parking ★

Send £1.50 for catalogue (cheque, M.O. or stamps - or phone with your credit card number)

★ Access - Visa - American Express accepted ★ also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

Lightning service on telephoned credit card orders!

WW - 007 FOR FURTHER DETAILS

RADIOCODE CLOCKS

are powerful and comprehensive instruments which receive, decode and analyse time-coded standard frequency transmissions to provide accurate, secure and completely automatic time/calendar or synchronisation systems.



Applications


- Automatic master clock and slave controller.
- Synchronisation of separate equipment and events.
- Programmable energy management system.
- Computer clock/calendar with battery backup.
- Data logging and time recording.
- Process and equipment control.
- Broadcasting, Astronomy, Navigation.
- Satellite tracking.

If you have a time or synchronisation problem, write or phone for further details of our portable and new microcomputer-controlled Radiocode Clocks.

Circuit Services, 6 Elmbridge Drive Ruislip, Middlesex. Ruislip 76962

WW - 034 FOR FURTHER DETAILS

The Keithley 179A

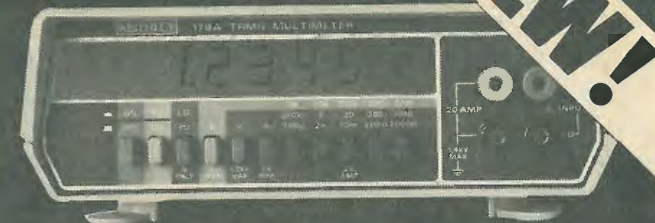

A MEASURE OF ACHIEVEMENT.

Specification... Versatility... Accuracy... Price. In almost every major area the new 179A - a 4 1/2 digit bench/portable DMM - from Keithley Instruments sets some pretty impressive standards:

- 20 amp capability
- Full function: 27 ranges including true RMS AC Measurement
- Year's guarantee on spec
- 0.04% DC accuracy
- IEEE option
- Large display and 10µV dc resolution.

For those requiring 10 times more sensitivity and an analogue output there's the 177, a unit with similar specification to the 179A. Both models are part of a vast range of test equipment from one of the world's leading manufacturers.

For more information fill in the coupon at the bottom of the page.

Alternatively, phone our Instant Information Service on 0734 864784 now.

KEITHLEY

Keithley Instruments Ltd
1 Boulton Road Reading Berkshire RG2 0NL
Telephone (0734) 861287
Telex 847047

I'd like to know more...

Name _____

Position _____

Company _____

Address _____

Telephone _____

(WW/8)

WW - 028 FOR FURTHER DETAILS



The over and outperformer

SHURE

You simply can't make it
any clearer.

For the address of your nearest dealer together with full details of the Shure Microphone range, write to:
Shure Electronics Ltd., Eccleston Road, Maidstone ME15 6AU or telephone: 0622 59881.

WW - 050 FOR FURTHER DETAILS

wireless world

... By any other name ...

In a recent Letter to the Editor, a reader described his feelings at seeing a copy of *Wireless World* for the first time after a long interval. On seeing the content, he felt impelled to write and suggest that the journal might benefit from a change of title, to take account of the fact that the World is now rather more computer-shaped than it was when wireless was the current miracle.

The letter constitutes cast-iron evidence to support the assertion, made by *WW* staff for seventy years, that one simply cannot produce a journal like this — the whole thing is logically impossible. Philosophy and printed boards, audio amplifiers and microcomputers, exposure meters and clocks do not, it must be admitted, appear to share much common ground. Neither, indeed, do the types of reader to whom our articles are addressed: the enthusiast making an amplifier on the corner of the kitchen table experiences but modified rapture at the prospect of an article on Rademacher-Walsh functions, though he may read it and be interested. The professional engineer does not require instruction in the design of an a-to-d converter, but he might want to build the digital voltmeter to which the article is an introduction. And one of the continuing arguments on basic physics possibly leaves both of them glassy-eyed, but nonetheless entertained.

The fact is, of course, that *Wireless World* is a hybrid in so many senses that it almost defies description. Both professionals and amateurs read it; the articles it contains are theoretical, or practical, or both; its topics cover the field from logic design to a discussion of the best material with which to stuff loudspeaker enclosures and from

descriptions of optical-fibre communications systems to a design for an electronic cat-door.

In all this, the one common factor is electronics, in its wider sense. It leads us into any subject in which it is used — optics, chemistry, motoring, aviation — in addition to the more familiar area of telecommunications. Computers happen to be an important manifestation of electronic engineering and are therefore completely within our field of interest. "Wireless" as a word disappeared in the forties or thereabouts, at around the time when "electronics" was born. But even then, *Wireless World* had been in existence for thirty-five years and its title was far too well known for Iliffe to risk causing an outcry by changing it.

Forty years on, computers, microprocessors and a mass of other digital circuitry have edged out the more traditional forms of electronic design — even sound reproducing is becoming digital in form. As this happens, it is clear that the content of the journal must change to meet new requirements, which is why a newcomer glancing at our contents page immediately after a look at the *Wireless World* logo might justifiably feel puzzled. If, however, a change of name after thirty-five years was felt to be too much of a shock for readers to bear, how much more of a jolt would it be after seventy-one?

The name is unimportant, except inasmuch as it sometimes misleads the casual bookstall browser and, perhaps, the not very well informed advertising agent. What is important is that the content should treat all aspects of electronics, which it will continue to do, no matter in what unexpected directions the subject leads us.

Editor:
PHILIP DARRINGTON

Deputy Editor:
GEOFF SHORTER, B.Sc.
01-661 8639

Technical Editor:
MARTIN ECCLES
01-661 8638

News Editor:
DAVID SCOBIE
01-661 8632

Drawing Office Manager:
ROGER GOODMAN

Technical Illustrator:
BETTY PALMER

Advertisement Manager:
BOB NIBBS, A.C.I.I.
01-661 3130

DAVID DISLEY
01-661 8641

BARBARA MILLER
01-661 8640

Northern Sales:
HARRY AIKEN
061-872 8861

Midland Sales:
BASIL MCGOWAN
021-356 4838

Group Classified Manager:
BRIAN DURRANT
01-661 3106

IAN FAUX
01-661 3033

Production:
BRIAN BANNISTER
(Make-up and copy)
01-661 8648

80-100W MOSFET AUDIO AMPLIFIER

The final section of this three-part article describes the complete amplifier circuit in detail, with the addition of a loudspeaker protection circuit.

by J. L. Linsley Hood

In the earlier parts of this article I discussed some of the design requirements of power mosfet audio amplifiers and described the evolution of a high-gain, symmetrical, class 'A' driver stage suitable for use with a power mosfet output. Inevitably, the final design of the gain stage, as shown in the completed power amplifier circuit of Fig. 14, shows some minor differences in comparison with the basic voltage-amplifier circuit, which underlines the point that any final design represents only the small tip of a large submerged iceberg of design effort. Unless one is lucky, or one's target performance is relatively modest, or one has considerable experience with closely similar designs, there is always a large amount of work necessary to convert a reasonably satisfactory basic design into a final version having, as nearly as possible, a blameless performance under all conceivable test conditions.

Design considerations

The choice of output power rating for any power amplifier is, inevitably, somewhat arbitrary and depends on the voltage ratings of the available components, and on the cost of the power transformer, smoothing capacitors and heat sinks which one is

prepared to afford. However, in practical terms, the major considerations which limit the possible output power are the voltage ratings of the output devices, and of the available electrolytic reservoir capacitors.

The output power mosfets I decided to use are the complementary n-channel and p-channel devices from Hitachi, since they are readily available, are reasonably inexpensive, appear to be adequately rugged, and have useful power ratings. These particular mosfets are available in peak working voltages up to 160V. However, there are other similar devices, either available now or promised in the near future, from Fairchild, Motorola, Ferranti, Supertex, International Rectifier and Intersil, so it seems likely that a design based on complementary power mosfets will not restrict the user to a single source of components.

Some earlier experiments with mosfet-output audio amplifiers had shown that the

Fig. 14. Complete circuit diagram of the 100W amplifier.

r.m.s power output could be related to the available supply voltage in the manner shown in Fig. 15, over the range 25-100 watts. Since it had been decided, for various reasons, to use a symmetrical positive and negative supply, 63V electrolytic capacitors on each half would allow a safe working voltage, overall, of 120 volts, equivalent to a $\pm 60V$ supply. In practice, the limited regulation of a simple rectifier-capacitor power supply is likely to reduce this, on load, to some $\pm 55V$, giving an overall power output of 80 watts.

This output power requires a voltage swing of 25.3V r.m.s. across an eight ohm load, and if it is desired to drive this from an input voltage of '0VU' - which in audio-engineering terms implies 0.775V r.m.s. at a 600 ohm source impedance - the gain will require to be 32.6, which gives a suitable feedback resistor combination of 33k and 1041 ohms - though, in the event, for other considerations, it was decided to make this 1012, made up from a 1k and an 12 ohm series chain.

In the interests of d.c. symmetry, the input-circuit resistance should be also of the order of 33k. The values suggested are adequately close to this.

The performance of any feedback ampli-

fier under transient (step-function or square wave) input conditions is helped if the input rise time can be limited. This can be done most easily by an input RC integrating network, R_2C_2 , which gives a -3dB point at about 30kHz, allowing an adequate bandwidth for audio use.


A 470 ohm trimmer potentiometer in the emitter circuit of the input long-tailed pair allows accurate d.c. balance to be obtained with transistors having normal commercial spreads in V_{be} values and current gain. This is bypassed by a 100 μ F tantalum bead capacitor to avoid loss of open-loop a.c. gain. The output d.c. potential may be adjusted by means of this potentiometer to 0V, $\pm 20mV$.

Circuit performance depends strongly on the characteristics of the 'tail' of the 'long-tailed pair'. For correct operation of any such circuit, the dynamic impedance of the tail should be very large in comparison with the impedance as seen at the emitters of Tr_1 and Tr_2 . Also, ideally, to minimize common-mode problems, the current from this source should be largely independent of the dynamic emitter potentials. Finally, the tail circuit should provide an adequate isolation from unwanted signal components on the supply line. A junction fet satisfies all these requirements very fully, and also allows, as explained above, control of the operating current in the second-stage class A amplifier. To allow a wider range of negative supply-line voltages, the negative-line supply to this fet is derived from a Zener-diode-stabilized -12 volt source. The use of a separate power supply for the driver stages is of considerable assistance in avoiding the performance degradation which can occur due to the intrusion of distorted signal potentials from the high-current output stage.

The second stage, class 'A', voltage amplifier is similar to that shown earlier in Fig. 13, except that conventional, two-transistor, constant-current sources are used as the loads for each half, and that a small amount of a.c. positive feedback is derived from the output of Tr_5 , through R_8 and R_7 , in addition to the current stabilizing d.c. negative feedback path through R_9 to Tr_3 . The positive feedback restores the open loop a.c. gain to the 500,000 figure, over the frequency range 100Hz-3kHz, obtainable from the less d.c. stable configuration of Fig. 12.

The output power mosfets require a quiescent current value of 100mA for optimum performance - although it is difficult, because of the efficient operation of the n.f.b. loop, to see any significant change in the distortion residues, as this is adjusted, at any frequency below 10kHz - and this quiescent current is largely independent of the output device temperature. The 'amplified diode' circuit of Tr_{10} is not, therefore, used to sense the output transistor temperature, but used simply to generate a reasonably constant voltage drop.

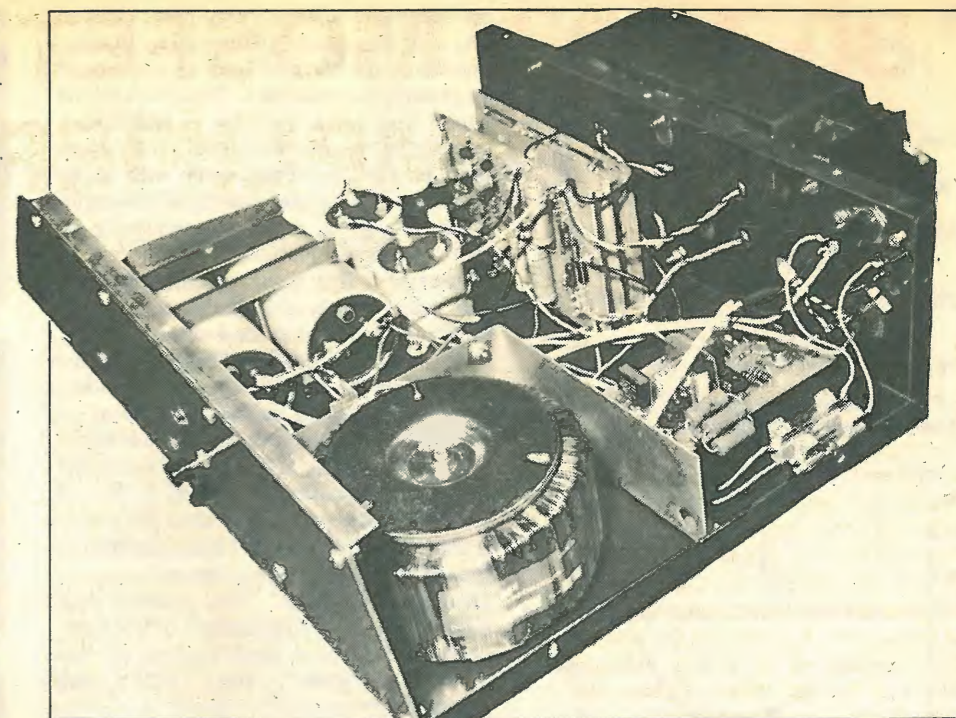Although the output devices present a very high l.f. input impedance, the effect of the 1200pF total gate-source capacitance cannot be ignored, and the current



Prototype amplifier. Loudspeaker protection circuit is at rear right.

through Tr_6 - Tr_7 must be enough to avoid any slew-rate limiting within the rise-time levels allowed by the input CR network, (R_2C_2). A current of 7mA is adequate for this, and permits worst-case dissipations of 900mW for $Tr_{4,7}$ and 450mW for $Tr_{5,6}$, which are within their limits.

Since the Hitachi output devices are not protected by internal Zener diodes, it is unnecessary to exclude the possibility of reverse gate biasing, provided that this is within the $\pm 14V$ gate-source breakdown voltage limits. This gate breakdown protection can therefore be provided by a pair of back-to-back 8V zeners, while the gate-source capacitance and the 680 ohm gate 'stopper' resistor will exclude the possibility of very rapid extraneous noise pulses which could escape Zener limiting due to lead inductance or turn-on time delays. Ideally, $R_{17,19}$ and the Zeners should be mounted close to the power mosfet pins.

Feedback loop, and loop stability

Although the use of a two-stage voltage amplifier will not automatically guarantee, under all load conditions, that the internal phase shift will not approach 180° until the open-loop gain is negligible, the necessary conditions for an adequate phase margin, at unity gain, are very much easier to contrive in circuits in which only two successive gain stages are employed - provided that the additional phase shift of any other element in the feedback path is small enough to be neglected.

Unfortunately, in the case of the conventional junction-transistor Darlington or compound (p-n-p/n-p-n.) emitter follower this additional phase shift is significant, even at a few hundred kilohertz where the loop gain is still high, so this loop gain must be artificially reduced at higher frequencies to preserve closed-loop stability. Two basic methods exist for this, of which the first, and simpler, is simply to connect an external capacitor across the whole of the gain stage so that this acts as an inte-

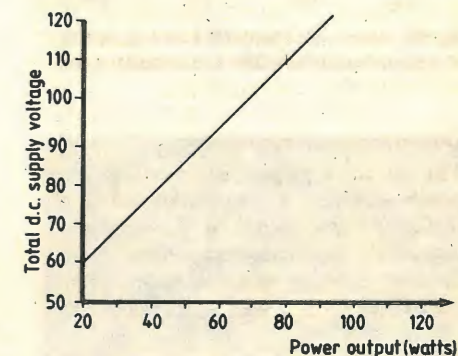


Fig. 15. Amplifier output power as function of supply voltage.


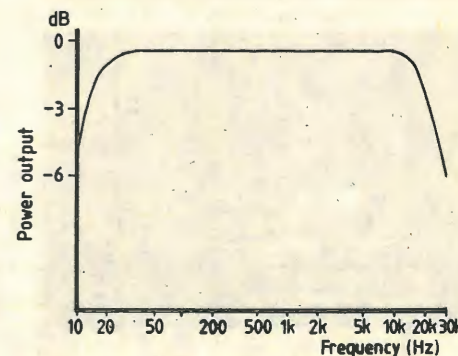


Fig. 16. Power bandwidth of amplifier.

gration network with a gain decreasing linearly by 20dB/decade from some l.f. break point. This has the advantage of allowing a wide phase margin of stability, and predictable performance characteristics. The second method is to tailor the h.f. performance so that it is maintained at as high a level as possible up to the point at which the loop phase shift approaches 180°, and then to reduce the gain rapidly, in a manner chosen not to exceed the 180° stability threshold, until it is less than unity.

This method is commonly employed in

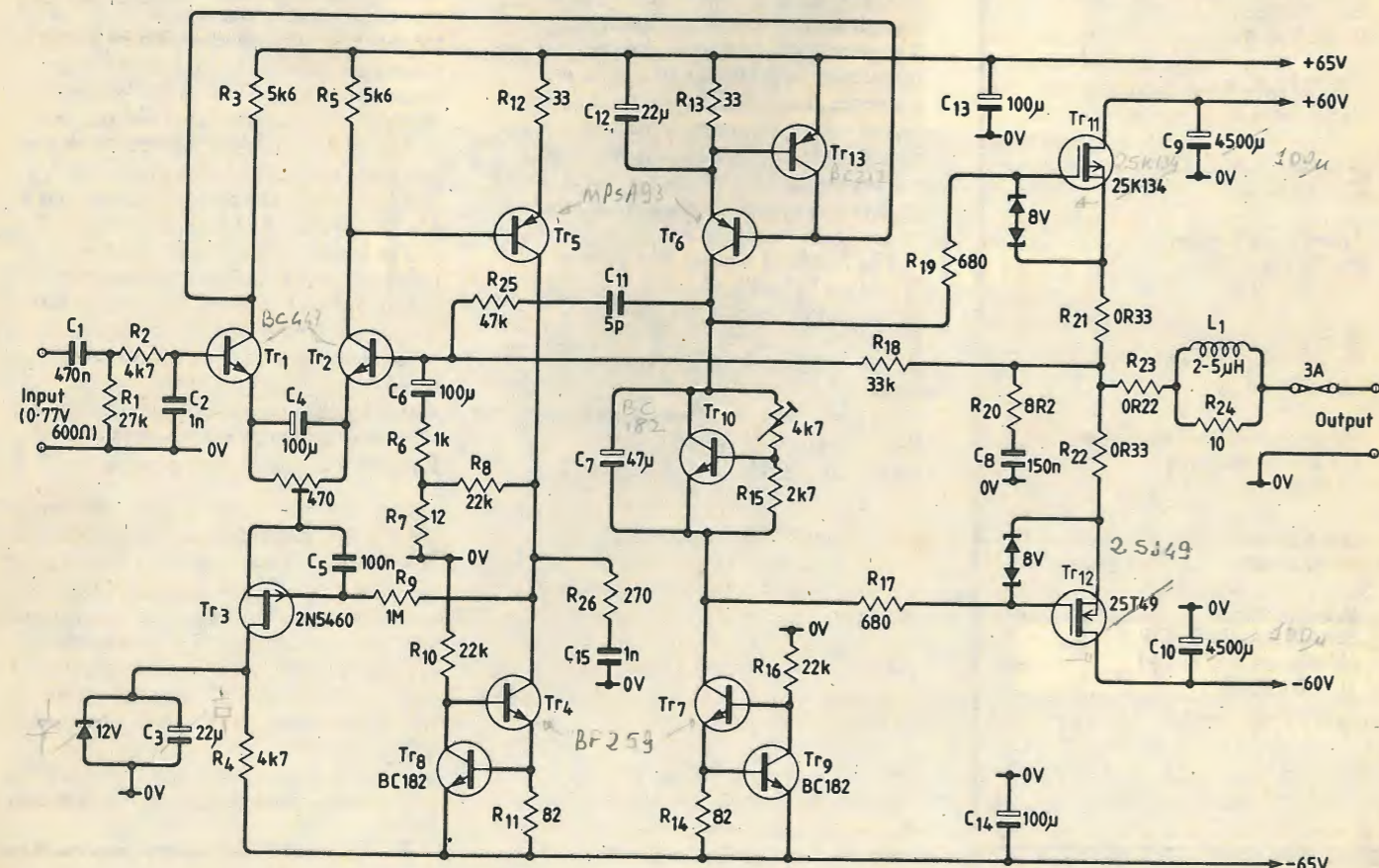

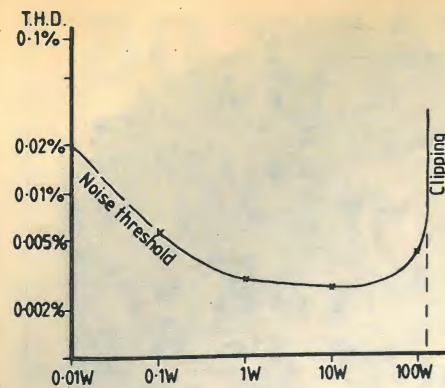


Fig. 17. Harmonic distortion as a function of output power (1kHz, 8Ω load).

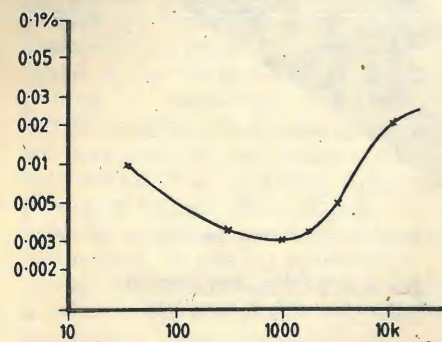


Fig. 18. Harmonic distortion as a function of output frequency (80W, 8Ω load).

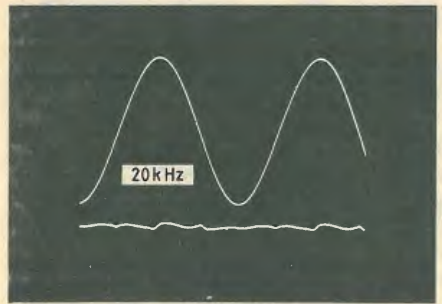
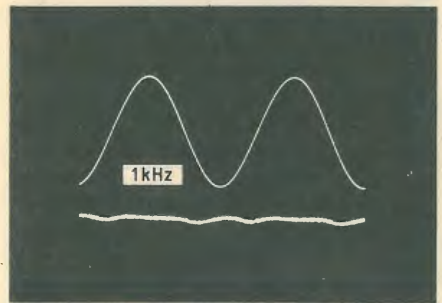
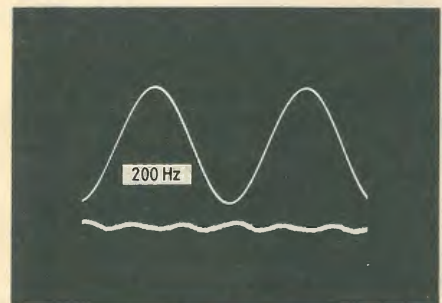


Fig. 19. Harmonic distortion residues at 80W/8Ω for 200Hz, (0.004% mainly second harmonic), 1kHz (0.0025%) and 20kHz (0.025%).

commercial transistor amplifier designs, often by the simple artifice of a capacitor between collector and base of the second stage amplifier transistor, because it allows better h.f. t.h.d. figures — and consequently better reviews in the 'Hi-Fi' journals. It does, however, carry with it the penalty that the phase margin of the amplifier is less good, with a consequently inferior transient response — manifest in respect of a less good 'settling time' — and a less predictable performance with differing loudspeaker load characteristics. In addition, the internal slew-rate limiting imposed by the second-stage collector-base capacitance (which is the mechanism by which the h.f. gain is reduced) leads to the predictable problem that signals accompanying large transient inputs will be blotted out during the period in which the amplifier is slew-rate limited. This is the phenomenon called 'Transient Intermodulation Distortion' by Otala⁷. This problem does not exist with the first method of h.f. compensation. A very good analysis of this problem was given by Jung⁸ (with a small addendum by myself⁹).

The biggest advantage, in this respect, conferred by power mosfet output devices, is that the inherent phase-shift of the output emitter-follower impedance conversion stage is sufficiently small that it may be neglected up to the megahertz region. This means that, with care, feedback audio amplifiers having high orders of negative feedback (open-loop gain) can be designed without the need for any external control of h.f. gain, and which will exhibit the desirable characteristics given by systems in which the gain decreases with frequency at 20dB/decade, and the loop phase shift does not significantly exceed 90°.

Influence of negative feedback

The use of negative feedback is, unfortunately, not as well understood, even among electronics engineers, as one might sometimes wish, and this misunderstanding has spilled over into the more emotive, and less logical, realm of the 'Hi-Fi' fraternity, where the ill effects attendant upon the improper use of this technique have encouraged the attempt to design amplifiers believed by their authors to employ no negative feedback whatever — a case of discarding the baby along with the bath water, if there ever was one.

The necessary conditions which must be satisfied if the potential benefits are to be gained have been examined both by Baxandall^{10,11,12}, in his series on audio amplifier design in this journal, and also, from a different angle, by *Wireless World's* own Cathode Ray¹³. The message from all these contributions, if I may presume to precis, is that the amplifier in question must be made as linear as possible before negative feedback is applied; that the gain — at the frequency under consideration — must be enough, or the customary simplification of the mathematics will be inappropriate; and that a small amount of n.f.b., by injecting into the input an additional distorted signal, will worsen the harmonic distortion which would have been present without it.

Translated into design requirements,

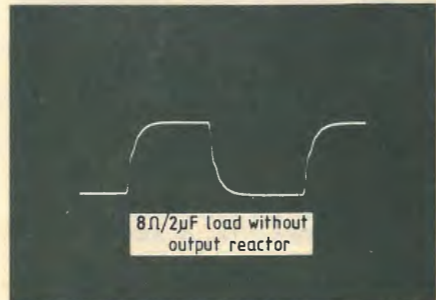
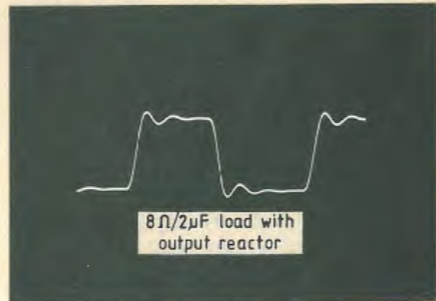
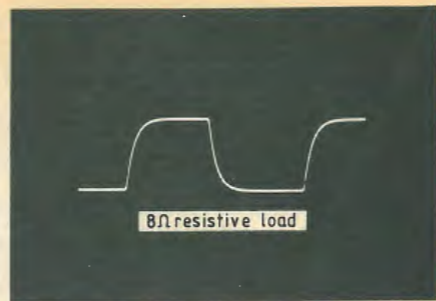


Fig. 20. Response of amplifier to 10Vp-p 100kHz square wave on resistive and reactive loads, with and without output inductor.

this implies that a high stage gain, coupled with good linearity and the lowest practicable phase shift, is the necessary design objective — most easily attained if not more than two gain stages are employed. The inclusion of a positive feedback path within the overall n.f.b. loop as a means of increasing the loop gain brings with it some supplementary requirements. These are that the phase shift within the positive feedback loop must be very small over the range of interest, since the p.f.b. will worsen it, and that the linearity of this part of the circuit must be much better than that of the remaining circuit outside the p.f.b. loop, or the benefits will be negated. Looked at in this light, the use of a bootstrapped driver load in an audio amplifier is not well advised, since the loop containing the 'bootstrap' will include the output devices whose linearity it is desired to improve.

In the particular case of the feedback loop built around Tr₂, Tr₅, R₈ and R₇, the linearity of this is very good because it is only driving a high-value resistive load, and the dominant phase shifts are those due to C₆ at the l.f. end, and the circuit stray capacitances in Tr₅ collector circuit at the h.f. end of the pass band. This gives a phase-linear bandwidth which is greater than that of the overall n.f.b. gain loop, and therefore satisfies the conditions for

improving the overall amplifier performance.

Because of the capacitive nature of the load presented to Tr₆ by the gate-source capacitance of the power mosfets, the h.f. loop gain of the amplifier falls below unity at about 30MHz, which is sufficient to give an adequate margin of stability, while still allowing some 60dB of negative feedback at 30kHz, the chosen upper operating frequency limit. No additional h.f. roll-off components are required.

Stability with capacitive loads

A minor problem associated with power mosfets, discussed by Hitachi in their design note¹⁴ is that the very high-frequency — 3dB point of the mosfet used as a source follower (typically 30-40MHz for the Hitachi devices) allows the inductance of the internal gate-contact lead — some 70nH — to produce a negative resistance condition, with consequent parasitic oscillation, under conditions of small capacitive load (0.01μF-0.22μF). Oscillation, under these conditions, but due to other causes, is not uncommon in audio amplifiers, and can be the cause of amplifier failure when used with the so-called low-impedance loudspeaker cables, even when the amplifier is completely stable under the 8ohm/2μF load combination frequently chosen by reviewers. Needless to say, this possibility of parasitic oscillation should be avoided and this is most easily done in this type of design by the inclusion of a small inductor of some 5μH inductance, (20 turns of 24s.w.g. enamelled wire, wound round the case of a 10ohm, 1watt carbon-rod resistor) in the output lead to the loudspeaker load.

This output inductance has two practical effects, apart from the avoidance of parasitic oscillation. The first of these is to reduce the total harmonic distortion of the circuit, as measured at the output at high audio frequencies, simply because it acts as an output low-pass filter. The second effect, due to the same cause is a 'ripple' on the square-wave/reactive-load test waveform, which is an inevitable effect of any steep-cut, low-pass filter. Without this output inductor, the 8ohm/2μF test waveform is smoothly rounded and free of any overshoots.

Output stage protection

Because of the freedom of power mosfets from secondary breakdown, and because they have an inherent positive temperature coefficient of resistance, output stage protection can be much simpler than is the case with normal junction transistors, and a simple fuse in the output circuit is quite adequate. This has a practical advantage over many of the electronic protection methods normally employed, in that it avoids hard clipping under dynamic conditions when the amplifier is required to drive fast h.f. transients into loudspeakers having a low h.f. impedance.

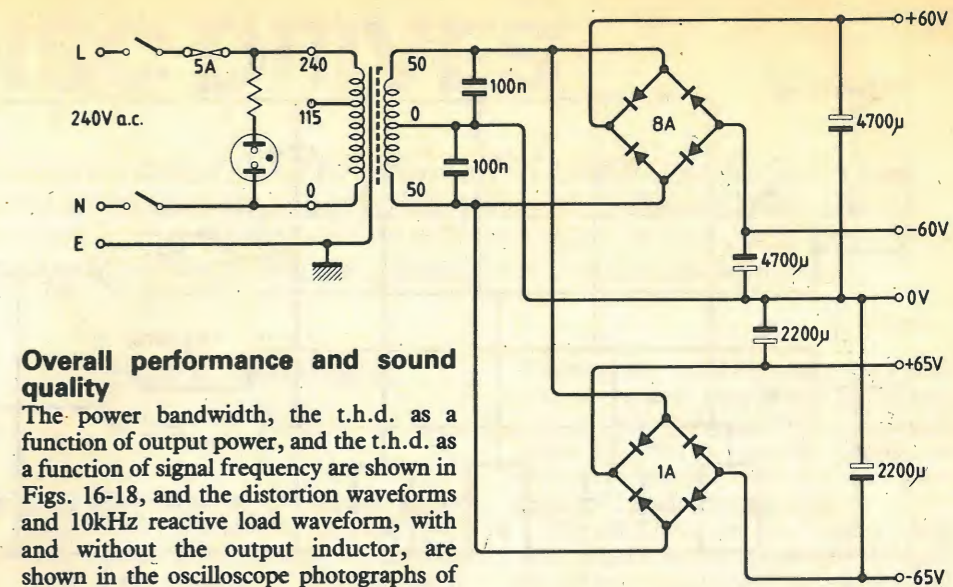


Fig. 22. Power supply used in prototype.

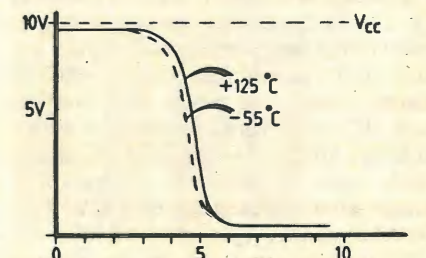


Fig. 23. Typical transfer characteristic of c.m.o.s. gate.


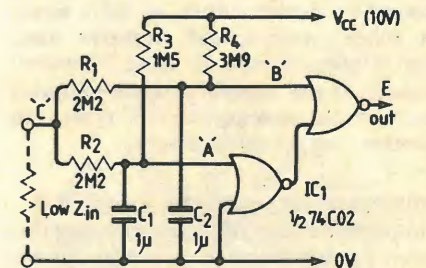


Fig. 24. Input d.c. level monitor using c.m.o.s. Nor.

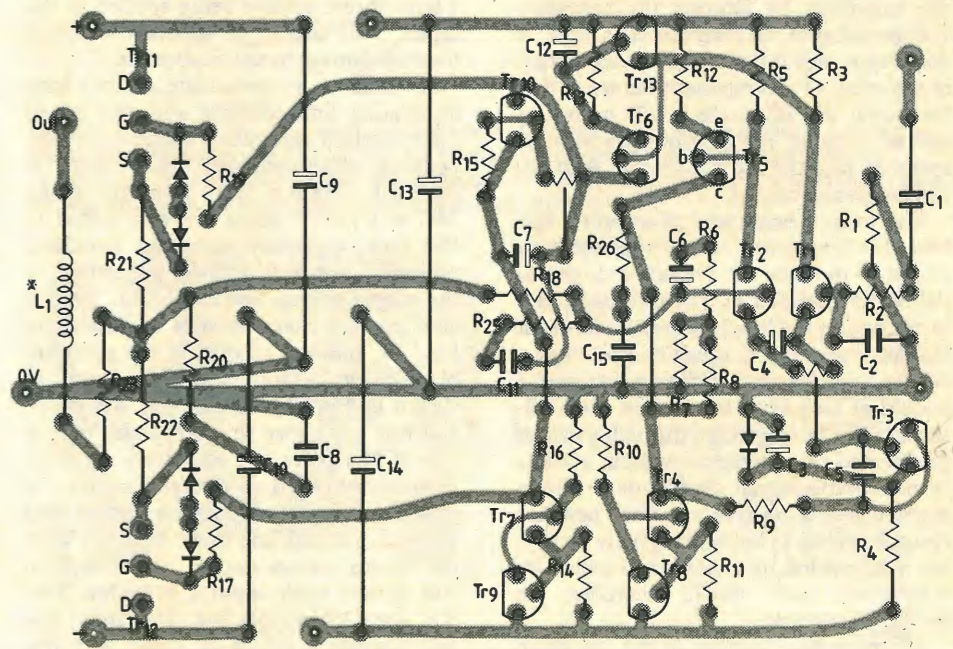

* L₁ is wound on R₂₄

Fig. 21. Printed-board for power amplifier.

DISC DRIVES

When a read/write head's position is determined by information on the disc surface, data-storage capacity can be greatly increased. As shown here, there are different methods of applying this technique which, in the case of a drive with ten discs in one pack, can increase the storage capacity four times despite a loss of 5% in data storage area.

by J. R. Watkinson
B.Sc., M.Sc.,

During track following, the correct position for the servo head is with half of each type of track beneath it. The read/write heads will then be correctly centred on their respective data tracks. This relationship is illustrated in Fig. 4.

The amplitude of dibits from A tracks with respect to the amplitude of dibits from B tracks depends on the relative areas of the servo head which are exposed to the

pulse will be negative. In addition, the A-track dibits are shifted by one half cycle with respect to the B-track dibits. The width of the magnetic circuit in the servo head is equal to the width of a servo track.

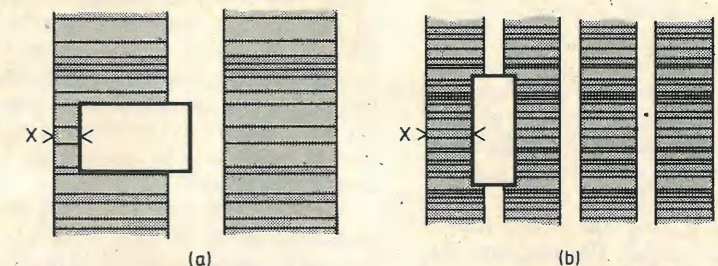


Fig. 1. At (a), misalignment x has little effect on the output signal, but at (b), the same misalignment in a system using four times greater track density causes unacceptable errors in the read signal. Distance x is not to scale.

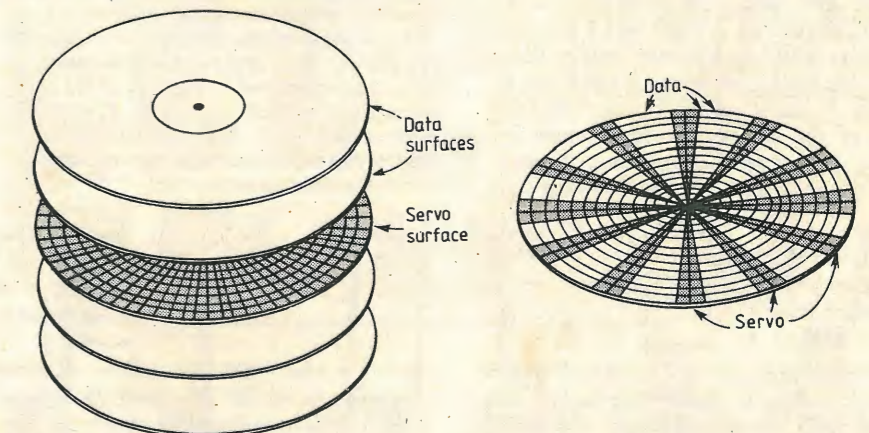


Fig. 2. In a multi-platter disc pack, one surface is dedicated to servo information, left, but as the number of platters in a pack falls, the percentage of data storage area lost to servo information rises. For this reason, some discs have servo information embedded in the data on the same side, as in the case of the single platter, right.

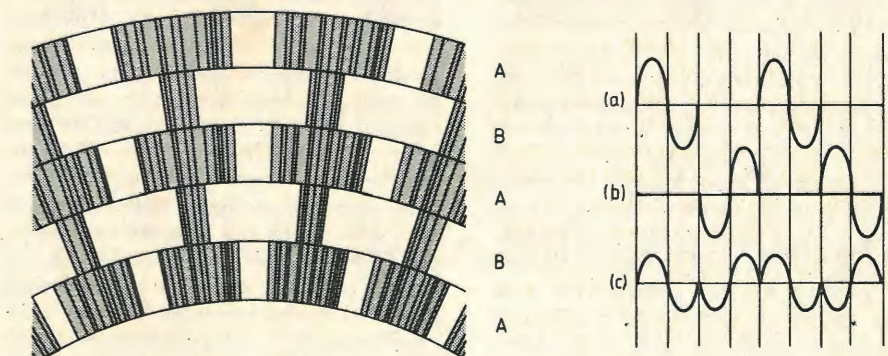


Fig. 3. The servo surface, left, has two types of track, A and B, which are 180° out of phase with each other and have opposite polarities. Waveform (a) results when the servo head is directly above track A, and waveform (b) appears when the head is above track B. When the head is correctly positioned, waveform (c) results.

Possibly the most significant event in the history of disc storage was the introduction of the servo-surface drive. Through the virtual elimination of thermal effects on head positioning, servo-surface drives, in which the head's position relative to the disc is determined by information on the disc surface, allow great increases in data storage density.

Changes of temperature in relatively simple disc-drive positioners, such as those discussed in the June issue of *Wireless World*, do not only affect accuracy through expansion and contraction in mechanical components such as head cantilevers. Thermal drift in the cylinder transducer and associated circuits also causes problems. How temperature changes limit the number of tracks on a given disc is illustrated in Fig. 1.

Because the position-error signal in a servo-surface disc drive is derived from a head reading the disc, these problems are drastically reduced. In a multi-platter drive, one surface of the pack holds servo information, which is read by the servo head. All of the read/write heads move with the servo head. In a ten-platter pack, this means that 5% of the usable data storage area is lost, but this is unimportant since the track density in a drive with a servo surface can be typically four times greater than in a drive without one.

Using one side of a single-platter cartridge for servo information would be unacceptable as it represents 50% of the usable data storage area so, in this case, servo information is interleaved with sectors on the read/write surfaces. Disc drives using this technique are usually referred to as 'embedded servo' drives.

Figure 2 shows the essential features of these two main categories of servo-surface drive, which will be described in turn.

Servo surface

As stated, one surface of the disc pack contains information to control the positioner. This surface is written when the disc is manufactured and, should it become corrupted, must be rewritten on special machine known as a servo writer.

The key to the operation of the servo surface is the way in which it is recorded by the servo writer. Recorded transitions are in adjacent pairs known as dibits, separated by a space, and Fig. 3 shows that there are two distinct types of servo track. On an A-type track, the first transition of the pair will cause a positive pulse on reading, whereas on a B-type track, the first

Digital Equipment Co.

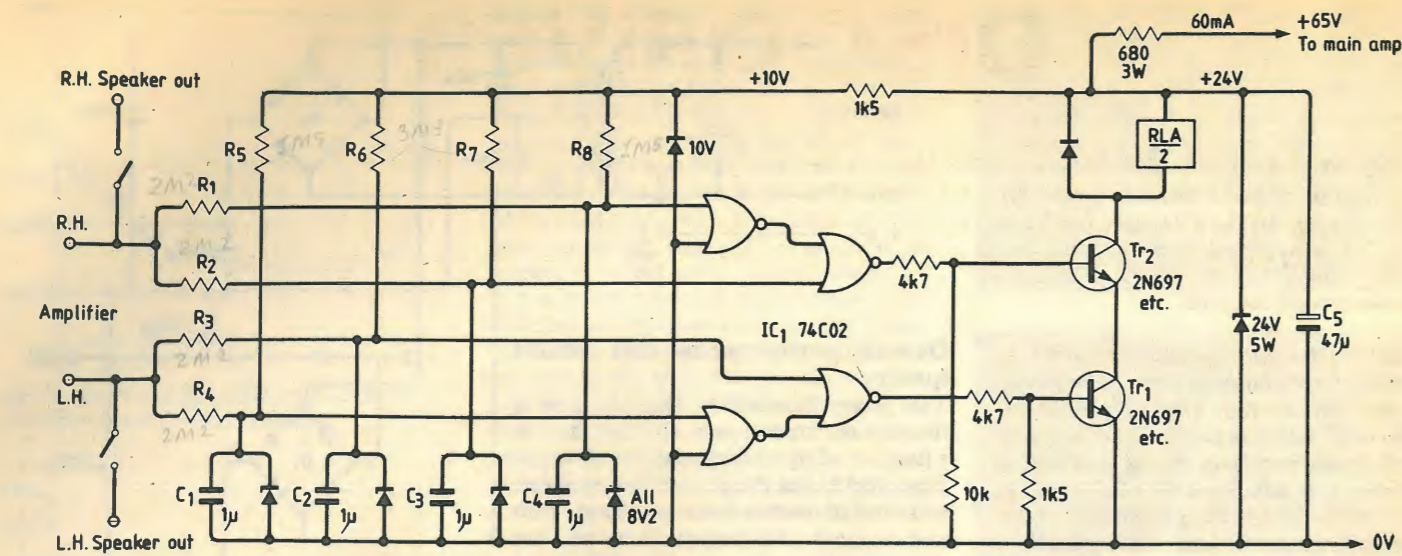


Fig. 25. Complete two-channel loudspeaker protection circuit with switch-on delay.

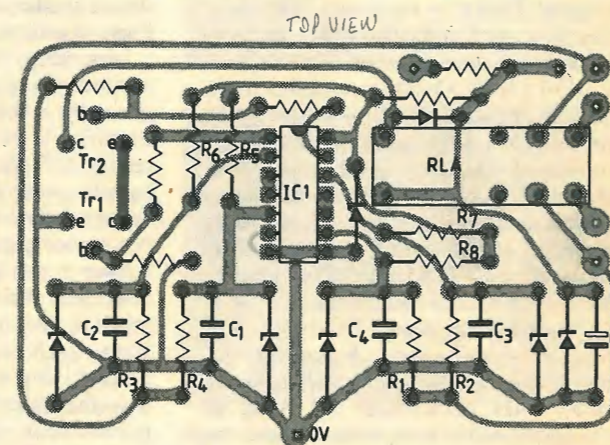


Fig. 26: Layout of printed board for circuit of Fig. 25.

Power supply

A suitable power supply circuit is shown in Fig. 22. As mentioned above, the output power of the amplifier depends almost entirely on the supply line voltages, and the original design was based on a conventional 'E' and 'I' cored transformer with a nominal 50-0-50 secondary winding, which gave a quiescent output d.c. voltage, after rectification, of $\pm 62V$. This was subsequently replaced by a 250VA 50-0-50V toroidal cored unit, in the interests of a lower residual 50Hz field, and this gave a d.c. output of ± 65 volts, and increased the power output, at 1kHz across an 8ohm, water-cooled, resistive load, from 83watts/channel to some 105watts/channel. It was thought prudent to uprate the reservoir capacitors to 80V types, but no other changes are necessary.

Loudspeaker protection circuit

Although the use of direct coupling between loudspeaker and amplifier output, together with the use of split positive and negative h.t. rails, undoubtedly helps in the economical design of high-powered audio amplifiers by limiting the necessary voltage rating of the reservoir capacitors, it does carry with it the implicit hazard that, in the event of a component failure within the power amplifier, the whole output of one or other of the supply lines may be switched into the output circuit, with expensive consequences.

The most elegant way of avoiding this hazard is to employ a small supplementary circuit to monitor the average d.c. potential of the amplifier output terminals, and to disconnect the loudspeakers in the event that an averaged d.c. offset of more than a volt or so is detected. Experiments over a period of time have shown that the loudspeaker can be connected through a pair of gold-plated relay contacts without audible or measurable signal degradation. Silver-plated contacts are excellent when new and clean, but tend to become partially rectifying if sulphided by exposure to urban atmospheres, and should therefore be avoided if possible.

An inevitable problem in the use of an 'average d.c. potential' monitoring circuit is the necessity for some compromise be-

tween speed of response, in disconnection following a fault condition, and the need not to diagnose a large but legitimate v.l.f. signal - especially if asymmetrical - as such a fault. My own choice is an integrating time-constant of about 2 seconds. This ignores all the normal l.f. signal components, at least at the largest signal levels I have so far used, but allows a switch-off in better than 80 milliseconds in the event of a large direct voltage being applied to the input. This should be adequate to avoid thermal damage to the loudspeaker.

In order to accommodate a fairly long integrating time-constant with the use of non-polarized capacitors, a high-input-impedance offset-detection logic circuit is essential. C.m.o.s. logic elements of the 74C or CD4*** series are well suited to this task, especially since the switching potentials are well defined in relation to the supply voltage line employed. Typical gate transfer characteristics are shown in Fig. 23. Because of this, if the gates are biased by an input resistor chain, as shown in Fig. 24, so that one sits below and one sits above this threshold level, a pair of Nor gates will effectively act as an input-threshold d.c. monitor circuit, in which the output will only be high so long as input A is high and input B is low. With the resistor values quoted, this condition will be met while input C is within $\pm 2V$ d.c., for a 10V supply line. The circuit also will provide a switch-on delay of a few seconds while C_1 charges up through R_3 to a potential above the $\frac{1}{2}V_{cc}$ level.

The complete, two-channel, loudspeaker protection circuit based on this arrangement needs only one Quad 2-input Nor gate, and a pair of switching transistors. The final circuit is shown in Fig. 25. It is 'fail-safe' in the sense that the relay contacts are normally open, and can only operate if the h.t. supply is present and both transistors are energized. The relay used is an RS Components p.c.b.-mounting, 24V unit, with 5A, 250V a.c.-rated gold-plated contacts, of d.p.d.t. operation. H.t. supply for this is best obtained from the output stage +65 volt line.

References

- Linsley Hood, J. L., *Wireless World*. Letters. Jan. 1975 p18.
 - Otala, M., *Trans. I.E.E.E.* AU-18, pp 234-239.
 - Jung, W. G., *Hi-Fi News and Record Review*. Nov. 1977, pp 115-123.
 - Linsley Hood, J. L., *Hi-Fi News and Record Review*. Jan. 1978, pp 81-83.
 - Baxandall, P. J., *Wireless World*. Ju. ly 1978, pp 76-79.
 - Baxandall, P. J., *Wireless World*. Dec. 1978, pp 53-56.
 - Baxandall, P. J., *Wireless World*. Feb. 1979, pp 69-73.
 - 'Cathode Ray', *Wireless World*. Oct. 1978, pp 47-50.
 - Hitachi Ltd., Design Note DE 1A. Feb. 1979. (Central Res. Lab.)
- Editor's note: We understand that a kit of components for the amplifier is to be made available by Hert Electronic Kits, Ltd, Oswestry, Shropshire. A preamplifier design to match the mosfet power amplifier will be described later in the year. □

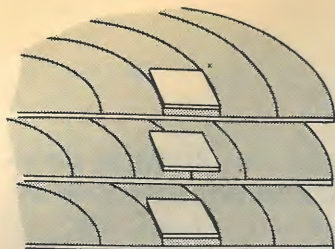


Fig. 4. When the servo head is straddling two servo tracks, the data heads are correctly aligned with their respective tracks.

respective tracks. As the servo head has only one magnetic circuit, it will generate a composite signal whose components will change with respect to one another as the position of the servo head changes. Figure 5 shows several composite waveforms obtained at different positions of the servo head. The composite waveform is processed by using the first positive and negative pulses to generate a clock. From this clock are derived clamping signals which permit only the second positive and second negative pulses to pass through. This resultant waveform has a d.c. component which, when filtered, gives a voltage proportional to the distance from the track centre. The position error reaches a maximum when the servo head is entirely above one type of servo track and further movement will cause it to fall. The next time the position error falls to zero will be at the centre line of the adjacent cylinder.


Cylinders with even addresses (l.s.b. = 0) will be those where the servo head is detented between an A track and a B track. Cylinders with odd addresses will be those where the head is between a B track and an A track. It can be seen from Fig. 5 that the sense of the position error becomes reversed on every other cylinder. Accordingly, an inverter has to be switched into

the track-following feedback loop in order to detent on odd cylinders. This inversion is controlled by the l.s.b. of the cylinder difference at the beginning of a seek, such that when the heads arrive at the target cylinder, the sense of the feedback will be correct.

Seeking across the servo surface results in the position error signal rising and falling in a sawtooth. This waveform can be used to count down the cylinder difference which controls the seek. As with any cyclic transducer there is a problem in finding an absolute position. This difficulty is overcome by making all servo tracks outside cylinder zero type A, and all servo tracks inside the innermost cylinder type B. These areas of identical servo tracks are called guard bands, and Fig. 6 shows the relationship between the position error and the guard bands. During a head load, the servo head generates a constant-maximum positive position error in the outer guard band. This drives the carriage forward until the position error first falls to zero. This, by definition, is cylinder zero. Some drives, however, load heads by driving the carriage at low speed across the disc until the inner guard band is detected, and then find cylinder zero by performing a full-length reverse seek.

Another, less common form of servo surface is shown in Fig. 7. In this type, there is a common sync. bit in both tracks,

Fig. 5. Waveforms resulting from several positions of the servo head in relation to the disc. Amplitudes of waveforms (a) and (b), components of the actual waveform (c), are proportional to the area of the servo head over the track concerned. A position-error signal, (d), is obtained by comparing the second positive and negative peaks in the composite waveform, (c).

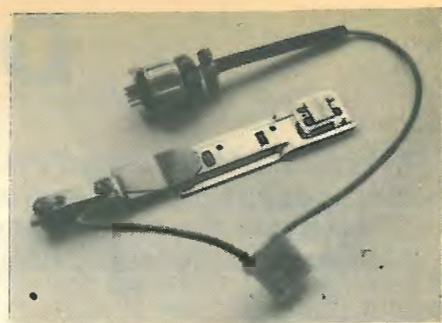

Servo head from a multi-platter disc drive. The rectangular plug is for mechanical support only.

and subsequent servo bits at different times afterwards. The position error is derived by opening sample and hold gates at different delay times after the sync. bit. As three distinct transitions can be seen in one cycle, the resultant waveform is known as a tritbit signal.

We have seen that a position error and a cylinder count can be derived from the servo surface, eliminating the conventional cylinder transducer. The carriage velocity could also be derived from the slope of the position error, but unfortunately such a signal is only available while the servo head is above the disc, and velocity feedback is needed when the heads are retracted. Some form of velocity transducer is still therefore necessary.

As there are exactly the same number of dibits on every track, it is possible to describe the rotational position of the disc simply by counting them. All that is required is a unique pattern of missing dibits once per revolution to act as an index point, and the sector transducer can also be eliminated.

Unlike the read/write circuits, the servo circuits are active during a seek as well as

when track following, and so must be constructed in such a way that they do not suffer interference from pulse-width modulated e.m.a. drivers. The main problem comes when the index is due, where the presence of a noise pulse during a "missing" dibit could inhibit recognition of the index. There are two solutions to this problem. In the first, a preamplifier i.c. is incorporated in the servo-head cantilever, so that the servo signal leaves at high level and low impedance, making it noise immune. In the second approach, the sector counter predicts when an index pattern is due, by counting slightly less than the number of dibits in one revolution, and inhibits switching in the e.m.a. driver until index has been detected.

An advantage of deriving the sector count from the servo surface is that the number of sectors on the disc can be varied. Any number of sectors can be accommodated for by feeding the dibit-rate signal through a programmable divider, so the same drive may be used for storing, say, 22 sectors of 16-bit data for a minicomputer or 20 sectors of 18-bit words when connected to a main-frame (2 disc words are the same as 1 memory word).

In a non-servo disc drive, the write clock is usually derived from a crystal oscillator. As the disc speed can vary with supply voltage fluctuations, a tolerance gap has to be left at the end of each disc block to cater for the highest anticipated speed, to prevent overrun into the next block on a write. In a servo-surface disc drive, the write clock is obtained by multiplying the dibit-rate signal with a phase-locked loop. The write clock thus obtained is locked to the disc speed, and the recording density will be independent of supply fluctuations.

Most servo surface disc drives offer an offset facility, where a register written into by the system controls a d-to-a converter, which injects a small voltage into the track-following loop. The action of the servo is such that the heads move away from the theoretical track centre line until the position error is equal and opposite to the offset voltage. The position of the heads about the track centre line is thus program controlled, Fig. 8. Offset is only employed for the purpose of reading, if a write is attempted, the drive will return to the track centre line.

Head alignment. The servo-surface technique is also used for head alignment. On the data surfaces of the alignment disc, dibit patterns are written at the reference cylinder. A special test box is required for head alignment, and this usually contains an exact copy of the circuit board used by the drive to obtain a position error signal from a dibit signal. The module in the test box is fed not by the servo head, but by the data head to be adjusted. The position-error output drives a centre-zero meter which gives a direct reading of the head misalignment in micro inches. The selected head is adjusted radially in the carriage until the meter reading is within the specification. Precautions are taken to ensure that the alignment disc is not written over.

Program-controlled head-alignment measurement. In some test boxes, the posi-

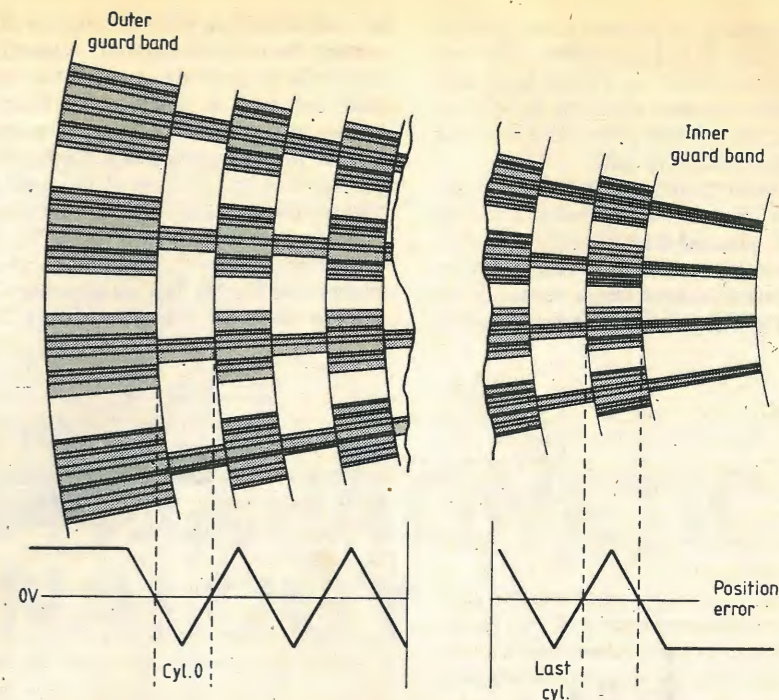


Fig. 6. The servo surface's working area is defined by the inner and outer guard bands, at which the position error signal is maximum.

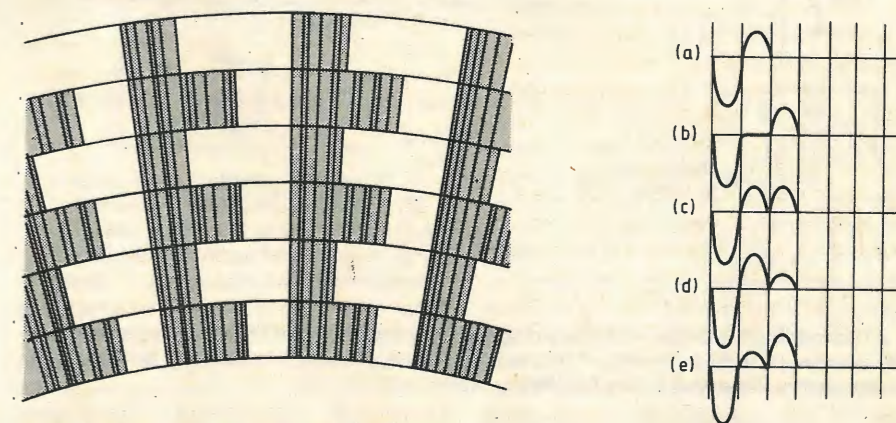


Fig. 7. The 'tritbit'-type servo surface in which the position-error signal is derived from pulses from two types of track following a common negative synchronization pulse. (a) and (b) are obtained when the servo head is directly above one or other of the tracks, (c) is the correct waveform, and (d) and (e) show typical off-track waveforms.


tion-error signal from the selected data head is compared with zero volts, to create a binary signal depending on the head position relative to the track centre line. This signal is fed back into the disc-control logic and becomes a bit in a register accessible to the system, known as 'sign change'. Under program control, the positioner is set to maximum offset, and then brought back until the sign-change bit changes state. The amount of offset needed to cancel the alignment error is equal to the error itself, Fig. 9. After sequentially testing all of the heads, the program can print out a table of the alignments. By comparison with the specification, an engineer can decide which, if any, heads need adjustment. The head alignment can also be checked at further reference tracks on both the innermost and outermost cylinders, as a check on carriage alignment accuracy.

Embedded-servo drives

In drives with few platters, the use of an entire surface for servo information gives a

high percentage loss of data recording area. In the embedded-servo drive, servo information is interleaved with data on the same surface, causing a smaller loss of data storage area.

The embedded-servo drive heads will be reading data at some times and alignment information at others as the disc rotates. A sector transducer is required to generate a pulse which is true when the head is reading servo information and false when reading or writing data. Figure 10 shows the principle. On all disc drives, the width of the read/write head is less than the track spacing to prevent crosstalk. As the servo head is also the read/write head here, it is slightly narrower than the spacing of the servo information. This has the harmless effect of rounding off the peaks of the triangular position-error waveform. During the pulse from the sector transducer, the head sees alignment information, and the servo circuit develops a position-error signal in much the same way as any servo drive. Within the servo area there are two sets of alignment patterns, the second be-

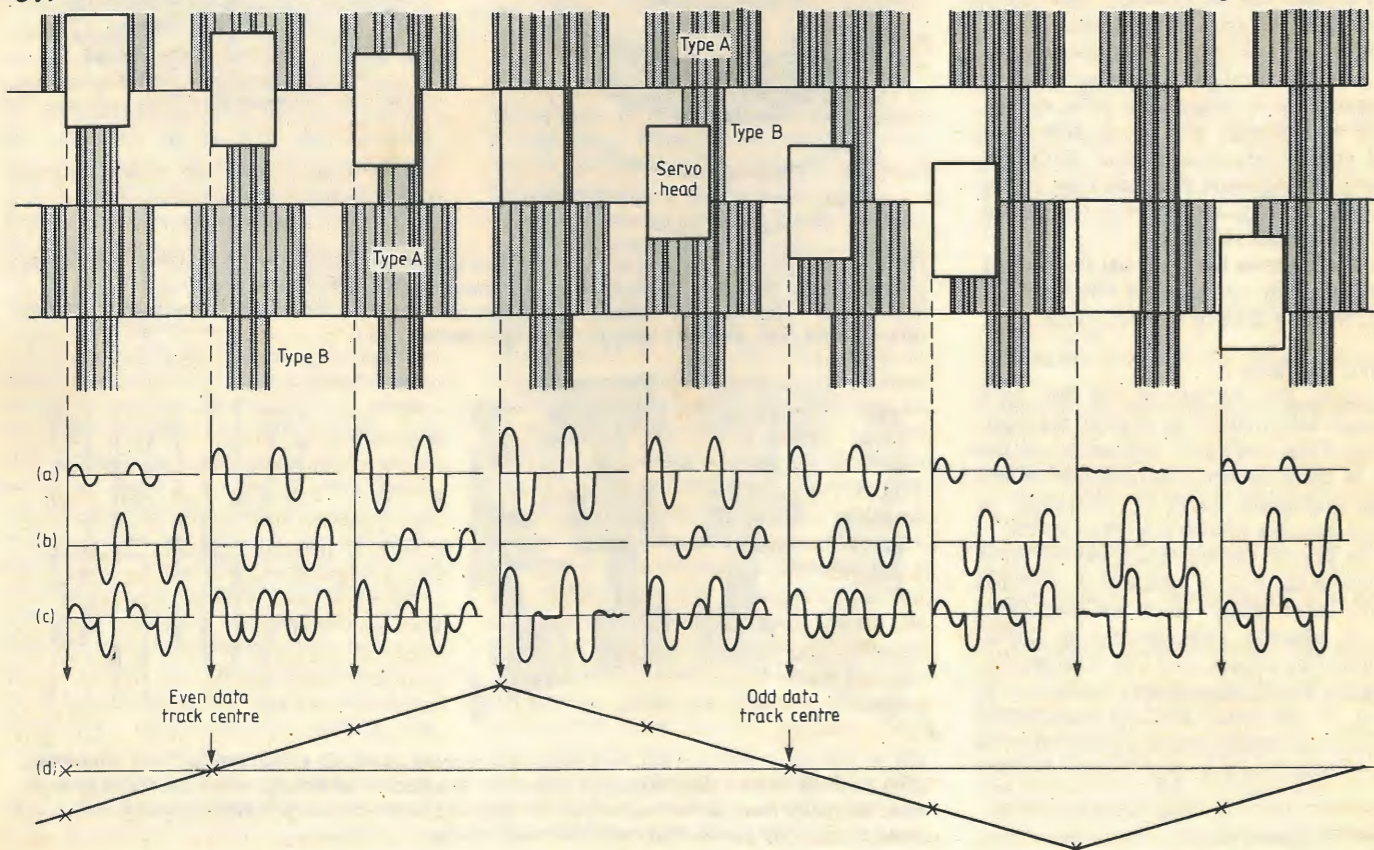

ing positioned to a position error of zero when the first is at a maximum. The two bursts of information are known as S1 and S2. Sample-and-hold circuitry is used to carry over the position error when the head is traversing read/write data.

The discontinuous nature of servo information means that cylinder crossing cannot be counted directly during a seek, as the positioner is fast enough to cross several tracks between servo bursts. With reference to Fig. 11, the cylinder crossings

are established as follows. During the S1 period, the position error is compared with zero volts to generate one data bit, whose state depends on whether the head was inside or outside the S1 null point. A similar process takes place during the S2 period, and the position of the head relative to the servo pattern is described as being in one of four places by the two bits. These bits are stored, and at the next servo bursts, two further bits are generated, describing the new position of the head.

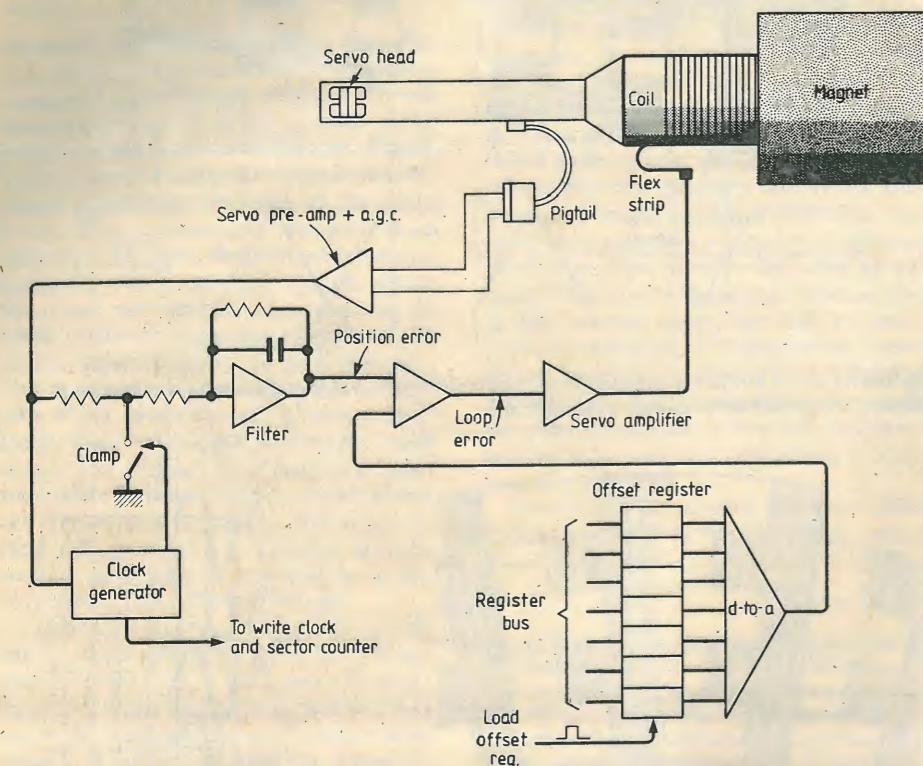


Fig. 8. Representation of servo-surface disc drive's feedback loop. The offset register drives a d-to-a converter which can modify the feedback loop, allowing the heads to be offset from the track centre line under control of the operating system.

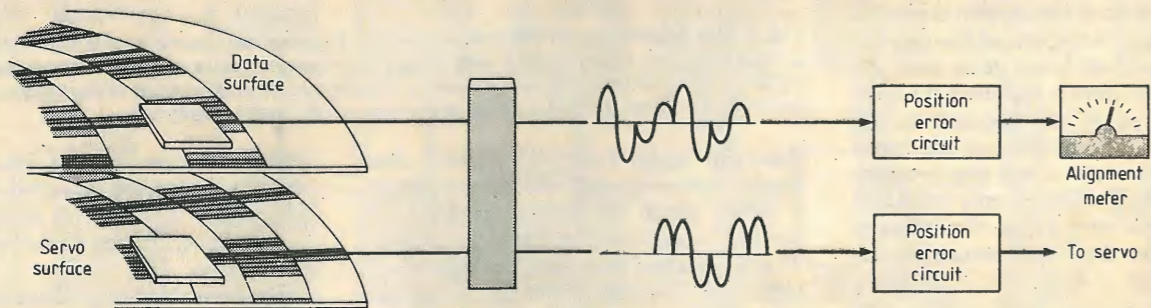


Fig. 9. Head alignment. An alignment disc with 'dibits' on its data surfaces is used in conjunction with a duplicate of the position-error circuit driving a head-alignment meter. Using offset, the program can move the servo head off track until the read/write head is in the correct position. The amount of offset necessary to achieve this is equal to the alignment error.

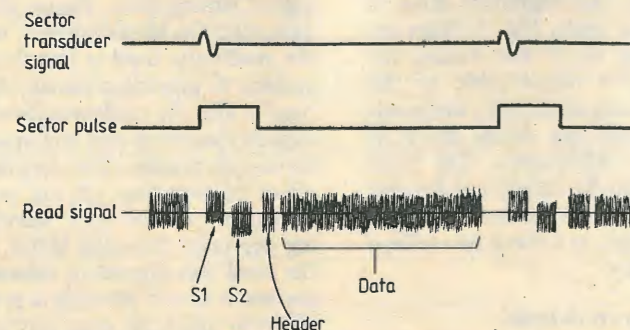


Fig. 10. In an embedded-servo drive, the same head is used for both servo information and data. During a sector pulse, the read signal is treated as servo information.

Figure 12 shows that there are a number of cases which can satisfy the same initial and final conditions. The only difference between the cases is the carriage velocity, so the output of the carriage-velocity transducer is digitized and used to resolve the ambiguity.

At every sector pulse, the two bits from the previous bursts, the two bits from the current bursts and the digitized velocity are fed into a rom which is pre-programmed to return the theoretically cor-

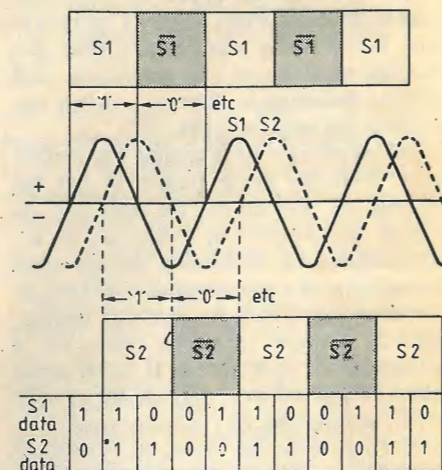


Fig. 11. There are two basic types of servo track, S1 and S2, recorded in two different positions and staggered. During S1, a position error signal is generated from the relative areas of the two types of track (S1 and $\bar{S1}$) under the head as in the conventional servo-surface drive. This position-error value is stored in a sample and hold circuit. For track counting, the position error value is compared with 0V to obtain a data bit. During S2, another position error signal and data bit are generated. The four possible combinations of the two bits are shown here in relation to the two position errors.

rect number of cylinders which must have been crossed for all combinations of inputs. This number is then subtracted from the cylinder difference counter which controls the seek. The calculation will only be valid for one disc rotational speed, so the disc motor requires a speed control. This is achieved by counting controller-clock pulses during the time between sector pulses, and developing a loop error by comparison with the desired number of pulses.

As the cylinder crossing count is deductive, there will be the odd occasion when the count is in error and the positioner comes to the wrong cylinder. In a conventional disc drive, this would be a mispositioning error which would warrant an

continued on page 46

A Heretic's Guide to Modern Physics

- 1 Theories and Miracles
- ▶ 2 Electromagnetic Analogy
- 3 Impact of the Photon
- 4 A more realistic Duality?
- 5 Quantization and Quantization
- 6 Waves of Improbability
- 7 Limitation of Indeterminacy
- 8 Haziness and its applications
- 9 The State of Physics Today

THE ELECTROMAGNETIC ANALOGY

In his second article Dr Murray takes a dispassionate look at Victorian electromagnetic theory and finds that, contrary to popular belief and textbook wisdom, it had begun to go decidedly green around the edges before it was thirty years old — a fact that many otherwise worthy men have preferred to ignore.

by W. A. Scott Murray
B.Sc., Ph.D.

The earliest organized investigation of the physical properties of light was undertaken in the seventeenth century by Sir Isaac Newton. Despite the evidence of some of his own experiments, Newton himself remained convinced throughout his life that light consisted of showers of particles, or "corpuscles". His authority among scientists was such that much philosophical argument arose before Thomas Young's famous experiment — on the mutual interference of light rays after passing through a double slit — was accepted as conclusive evidence for the wave nature of light, largely through the mathematical ingenuity of Fresnel. Incidentally, the most convincing demonstration that I know of in favour of "light waves" is due directly to Fresnel, and lies in the fact that the shadow of a one-penny piece has a bright spot at its centre.

That light behaves as a wave system is one of the most thoroughly researched and supported conclusions in all science. By assuming waves of a definite wavelength one can calculate numerically how light will behave in optical apparatus of any complexity one chooses and, lo and behold, that is precisely the way light does behave in practice. The accuracy of the prediction seems to be unlimited, and to depend only on the accuracy with which we can measure the result. I want to place special emphasis on the precision with which the wave theory describes the behaviour of light as observed in Nature, because it is primarily that precision which makes the wave theory of light so convincing. As long as we stick to light which is bright enough to be seen, and of ordinary visible wavelengths, the theory works perfectly every time.

The next major step in the wave theory

was taken in 1862 by James Clerk Maxwell, on the basis of his formulation of Michael Faraday's ideas of electricity and magnetism. Faraday had come to interpret his observations in terms of electric and magnetic fields of force, which Maxwell found could be expressed by exact analogy with the mathematical formulations of hydrodynamics — that is, the behaviour of incompressible fluids. Faraday's field concept conveniently bypassed the fundamental problem of action-at-a-distance. (namely, how can one electric charge repel another when there is no connecting rod between them?). It suggested that the electric field permeated everything and everywhere, like a fluid throughout all space, so that such actions really took place locally, within the field, rather than "at a distance".

By this means action-at-a-distance came to be regarded as a non-problem, the first of many difficulties so handled in physical science. Note that the non-problem technique does not solve the philosophical problem to which it is addressed, but evades it. It is clearly legitimate as a technique, to permit us to maintain our momentum and get on with the next phase of the job, provided we put up a marker flag to remind ourselves that we have left behind us a fundamental problem unsolved. It is philosophically dangerous to omit this precaution. For example, there are those who have specialized in field theory so strongly that they believe in an electric field, as if it were a physical entity having an independent physical existence in its own right — like an electron perhaps, or a

filing cabinet. Such folk do not envisage an electric field merely as a convenient mathematical trick for integrating a set of inverse-square-law forces.

I am discussing this concept of a "force field" at some length because it is the first instance we have encountered where an attractive product of romantic imagination has come to be treated, with no basis of experimental evidence whatsoever, as though it corresponded to an established or even a self-evident truth. It is in this romantic, unscientific way that doctrines arise in physics. (When a doctrine is subjected to criticism that it cannot withstand it usually turns into a dogma; it is then to be believed by faith rather than by evidence). In the present case the truth is that we know nothing of how or why one electric charge should be influenced by the distant presence of another, but only that it is so influenced and by precisely how much. It is another miracle.

These ideas may seem far removed from waves and light, but the connection between them was Maxwell's very great invention: he showed that a particular combination of his changing electric and magnetic fields, which can be written, down mathematically in the form of a "wave equation", would propagate through space at the velocity of light. Thence it needed but one further, obvious step to the postulate

"Light consists of electromagnetic waves".

That step was taken. Combining as it did the three topics of electricity, magnetism, and light under the single concept of wave motion, it was extraordinarily satisfying aesthetically and it seemed to remain true when tested to any depth. It came to be

believed by all scientists at the turn of the century and it is still believed by nearly all scientists today. Heinrich Hertz went on to cap it by generating radio waves electrically and showing that they belonged to the same family of phenomena.

Thus at the end of the "classical" period in physics all appeared superficially tidy. It was generally accepted that the entire spectrum of light from long-wave radio through and beyond the ultraviolet was a manifestation of electromagnetic waves of defined, invariant velocity c , whose "colours" were determined by their frequencies and corresponding wavelengths in accord with the general axiom of wave motion, frequency \times wavelength = c . Those must have been happy days of self-satisfied Victorian complacency before the storms broke...

A couple of minor points arose. First, the physical energy transported by the light waves, which propagated at the speed of light, was taken to be the energy contained in the electromagnetic field as described by a simple formula of the theory. Once launched into space, this energy had an independent existence even though its source, a star for instance, should later explode as a supernova. So here one had an electric field and a magnetic field, neither of which (according to the theory itself) could exist without continuous connection to a source and a sink of fluence, while their combination, the *electromagnetic* field, did have an independent existence. These static and dynamic fields were therefore quite different in their intrinsic natures, yet there was nothing in Maxwell's equations to suggest that one type of field was more physically "real" (that is, had any more independent, objective and existence) than the other.

Second, and on a slightly larger scale of discrepancy, Maxwell's formulation of electric and magnetic fields was mathematically equivalent to the behaviour of incompressible fluids, as has been mentioned already; yet the waves in his *electromagnetic* field were *transverse* waves, of a type which in the mechanical case require a solid substance to transmit them and will not propagate in a fluid medium. Thus the medium involved, which became known as the ether, was required to exhibit physical properties which differed from moment to moment, according to whether the field it was supporting was static or in motion. This gave rise to much trouble.

In view of the intellectual triumph of Maxwell's work it would indeed have been churlish to have raised such apparently insignificant points as these at the time. Yet in retrospect one can see that they were real discrepancies whose incidence formed part of a pattern of discrepancy in electromagnetic theory. (Remember, please, that we are not attacking the theory, but examining a miracle: a physical occurrence for which we can offer no physical explanation). For physical waves as normally understood are mechanical waves; they are waves in *something* — in air, or water, or at the air-water interface, or in solid rock, or what-have-you. Their

velocity is determined in relation to the medium in which they travel. Hence a careful measurement of the velocity of light in the laboratory, coupled with the assumption of the constancy of light velocity in its ether medium should, it was believed, reveal the velocity of the laboratory through the ether.

That experiment was duly performed, most famously by Michelson and Morley in a basement in the University of Chicago in 1887. The date is most interesting, being 25 years after the first publication of Maxwell's postulate of the electromagnetic nature of light, and 18 years before the publication by Einstein of the special relativity theory with which it is usually connected. That connection is something of a myth. Einstein did not refer to the Michelson-Morley experiment at all but assumed the velocity of light to be universally constant as a fact of nature (*it was not tested* in Michelson-Morley!). His other starting-point, the principle of relativity in the form of the denial of absolute motion, was in no sense new but had appeared in Newton's *Principia* just 200 years before.

Thus for contemporary thinkers the really shocking implication of Michelson and Morley's result was not that it might lead towards a new relativity theory some two decades later, but that it asserted, unmistakably and immediately, that *there was no ether* for the electromagnetic light waves to undulate in. It was of secondary importance that the medium in which electromagnetic waves travelled did not reveal any frame of reference of zero motion, or absolute rest. It was an equally red herring to say that it was merely the postulated electromagnetic waves that had no ether, because the experiment as performed was a straightforward experiment in light, having no reference to electricity or magnetism. The really crucial experimental result was that light waves, whatever their form, could not be waves in a physical medium. And if they were not waves in a physical medium, how could they be said to be waves at all? The answer to that question is *not* straightforward.

There was an immediate and almost instinctive reaction against the Michelson-Morley result. Some physicists (like Sir Oliver Lodge) simply refused to accept it, while others up to the present day have repeated the experiment with progressively more refined apparatus in the hope of proving it wrong. All such attempts so far have failed. Most of those experimenters believed themselves to be taking issue with Einstein and special relativity; only a discerning few have understood that they were really trying to save the electromagnetic theory, and with it the whole of the concept of fields of force of nineteenth-century physics. The Michelson-Morley experiment denies the existence of an ether, and there is no doubt about its finding: space is empty. There is nothing there.

In view of the admittedly overwhelming evidence that light consisted of waves (and very probably electromagnetic waves), physics at the turn of the century refused to face the consequences of the Michelson-

Morley result. Two lines of experimental evidence that seemed to be equally valid seemed also to be in absolute mutual conflict. The philosophical crisis was acute, and it has never been resolved. One approach has been to ignore the problem in the hope that in due course and in the light of later knowledge it will go away — this is the "don't care" or "too busy" reaction, which really means "too difficult" — but unfortunately this is a problem that *doesn't* go away. Another approach is to ask why a physical ether should be necessary for the waves to propagate in: why do they demand a *physical* medium? The answer would seem to be that according to the theory these "waves" carry physical energy in readily measurable amounts, so that they must be physical waves; and physical waves cannot be waves in nothing, unless we are to believe in miracles...

Then there are the semantic approaches, which seek to show that the problem is one of wording only and has no philosophical depth. "Very well", it has been said, "we have been denied a luminiferous ether; let us call the medium in which the waves travel 'space', or 'an inertial frame of reference'". The trouble with such proposals is that space, insofar as we can *measure* its properties, is empty, a vacuum, having no physical content. (Do not let us get bogged down with arguments about the "permittivity" or "im-

Summary

History of the scientific concepts of light: Newton (corpuscles), Young and Fresnel (waves), Faraday (fields of force), Maxwell (electromagnetic theory). The philosophical problem of "action-at-a-distance" was not solved but bypassed, setting a precedent; this raised the question of the nature of a field theory and led to the emergence of related doctrine and dogma. Some minor discrepancies were inherent in electromagnetic theory as propounded: depending on scenario its fields possessed differing degrees of physical reality, and differing properties were required of the medium, or ether, in which the electromagnetic phenomena occurred. A major problem arose in consequence; when the issue was put to the test, the famous Michelson-Morley experiment unequivocally denied the existence of a physical ether for electromagnetic waves to undulate in. Attempts were made to evade this philosophical crisis by ignoring it, by semantic arguments, and by attributing physical properties to non-physical, mathematical equations. The last of these ideas, which began to take root in the 1890s, re-introduced mysticism into natural philosophy after a banishment of only 350 years. An alternative approach (which was not acceptable in the climate of those times) might be to regard electromagnetic theory as an analogy of Nature which although often extremely useful may not always be a perfect analogy.

pedance" of empty space, which are artifacts of electromagnetic theory). We cannot manufacture a physical medium having physical properties out of nothing merely by coining phrases or by re-defining space.

Yet another approach — and this one had far-reaching philosophical consequences — arose from the remark that the *mathematics* of wave propagation predicted results in accord with observation even though the physical requirements for wave propagation were not satisfied. The temptation became very strong to say that these light waves were not physical waves at all, but *mathematical* waves. Here at a stroke one seemed to have a potential solution satisfying both aspects of the experimental evidence: (a) light consists of waves (*c.f.* Young and Fresnel, and perhaps also Maxwell and Hertz), while at the same time (b) the waves are not physical waves in a physical ether (*c.f.* Michelson and Morley), but of a purely mathematical nature.

This was the first move in the takeover, by default, of theoretical physics by the Mathematicians' Union. It wasn't a complete takeover until the 1930s when the mathematics of the new quantum mechanics became so obscure and esoteric that the ordinary physicist gave up trying to follow the wilder ramifications of the theory. The nature of the physicists' default was their failure to insist sufficiently strongly on the physical reality of the physical world. In the case of light, energy is

transmitted at a definite speed through a vacuum, and this energy is a physical entity which gives rise to measurable physical effects at its destination. Mathematical waves, being abstract and non-physical, cannot give rise to physical effects. If we accept mathematical waves as the basis for light, we are accepting miracles; for by our definition a miracle is a physical occurrence for which we can offer no *physical* explanation.

Mathematical explanations of physical events *will not do*. For those who believe that mathematics can take the place of physics, or who have merely failed to think about the suggestion deeply enough, I offer the following little mnemonic: Nobody ever became sunburnt as a result of exposure to a differential equation!

Thus in addition to being the first move in the general mathematical takeover, this was the beginning of the return of mysticism into Natural Philosophy after a banishment which had lasted no longer than 350 years. The evidence we shall put together will show that the process has continued steadily, until today the whole fundamentals area has become so permeated by mysticism that one can scarcely distinguish where the physics ends and the metaphysics begins. There is a way of making the distinction, but it calls for a certain old-fashioned ruthlessness in complying with physical discipline and rejecting unsupported mathematical speculation, however superficially attractive the latter

may appear. The process will become easier and more sure as our long-neglected critical faculty is gradually re-developed and applied to these problems.

What other alternatives do we have for dealing with the quandary in which the Michelson-Morley result has placed us? There is one approach which always carried a budding promise, although in the face of the mystical takeover it has received little more than lip-service. It is that light does not in fact consist of electromagnetic waves but *behaves like* a system of electromagnetic waves. The distinction here between "is" and "behaves like" is not merely tautological or semantic, but fundamental. It tells us to treat the great electromagnetic theory as an analogy or mathematical model of nature, which probably reflects some features of physical reality but not necessarily all features, and which may prove to be a more accurate model of nature in some circumstances than in others. Therefore we do not say that electromagnetic theory is wrong; indeed, we make use of it successfully every day of our lives. We simply say that the area of its applicability may be limited.

Armed with that kind of philosophical background, which is much more restrained and cautious than that of our predecessors at the turn of the century, we are far better placed than they were to withstand the next shock to physical thinking, which was about to be delivered (in 1899) by Max Planck. □

Next month

2Kbyte eprom emulator/programmer

A design for an emulator for 2516/2716 eproms, in which a ram, loaded with software by keypad, carries out the function of a rom and allows a program to be run and tested without the need for eprom reprogramming. Ram contents are easily modified, and the emulator plugs into the system eprom socket. When the program is satisfactory, the emulator transfers to eprom the tested ram contents.

Selective call for c.b. radio

To call any one of 64K similarly equipped c.b. receivers, enter a number on a keypad to generate a 16 data-bit frame to modulate the carrier. Only the selectively called receiver will respond. The device is easily modified for high-security applications, such as remote access and data interrogation.

Simple, low-frequency oscilloscope

A very simple design, using a surplus radar tube. It uses easily obtained components, is straightforward and costs only around £40.

Vertical bandwidth is up to 1MHz at 50mV/cm and the timebase is either astable or triggered.

Op-amp development

As a preliminary to a full description of his new, modular preamplifier, John Linsley Hood traces the development of the operational amplifier, from the early 741 types to the mosfet-input CA 3140 and the bipolar/fet TL071/2/4/ series, designed for use in audio work.

On sale August 18.

CIRCUIT MODELLING BY MICRO-COMPUTER

The small-signal a.c. properties of a circuit may be modelled on a computer. Here the implementation of a program uses techniques to reduce the computing time by 77%, or more, and to plot graphs of the frequency and phase responses.

A previous article on this subject¹ led me to implement circuit modelling on my home computer. I prefer to reserve the word 'analysis' for analytical, normally algebraic, methods such as complex variable theory. As home computers cannot do algebra, I have called the process 'circuit modelling'.

For the design of a 16-node active filter, I used a program to plot frequency responses on a printer, giving simultaneously phase and gain curves. The reduction of the infinite admittance determinant to a two-by-two was done for 50 frequencies in order to obtain enough points for a good curve. At first this took nearly two hours to run on my 4MHz Z80A microcomputer. The table shows a breakdown of the number of operations in Basic.

Operation Type	Number of Operations Originally	No. after Optimising Code
FOR X = ..	700	700
FOR P = ..	6650	6650
FOR Q = ..	74550	21150
ADDS	223650	43400
SUBTRACTS	298200	29800
DIVIDES	149100	14900
MULTIPLIES	745500	61000
ARRAY REFS.	1341900	86800
IF... THEN	0	28500
TOTAL	2840250	292900

Clearly any operation contained in the FOR...NEXT Q loop is carried out a far greater number of times than in any other position. The first step in reducing the running time is to move as many operations as possible outside this loop. The second step is to reduce the number of array references, as these take the longest time. Thirdly to eliminate any unnecessary computations: the determinant being evaluated is normally sparse because few nodes are interconnected. This causes many zero entries to appear and the computer dutifully subtracts zero for each unused node. This can be avoided by including a test for zero. For a typical 16-node circuit, these changes have reduced the number of computations ten-fold. The Basic interpreter code used is shown under. It uses the notation of A. S. Beasley's article¹ and cuts the time for a 50 frequency graph to 27 minutes, a saving of 77%. Note that the use of the exponentiation operator (**) has been avoided. I have used $A=Y1*Y1+Y2*Y2$ in place of $A=Y1**2+Y2**2$. Exponentiation is slower than multiplication and less accurate.

Further optimisation will be machine dependent, and the use of a Basic compiler

By R. I. Harcourt

```
FOR X=N TO 3 STEP -1
Y1=YR(X,X)
Y2=YI(X,X)
A=Y1*Y1+Y2*Y2
IF A=0 THEN 1600
FOR P=0 TO X-1
Y3=YR(P,X)
Y4=YI(P,X)
IF (Y3 = 0 AND Y4=0) THEN 1300
FOR Q=0 TO X-1
Y5=YR(X,Q)
Y6=YI(X,Q)
IF (Y5 = 0 AND Y6=0) THEN 1200
B=Y3*Y5-Y4*Y6
C=Y5*Y4+Y6*Y3
YR(P,Q)=YR(P,Q)-(B*Y1+C*Y2)/A
YI(P,Q)=YI(P,Q)-(C*Y1-B*Y2)/A
1200 NEXT Q
1300 NEXT P
1400 NEXT X
RETURN
1600 PRINT "NODE "X;" UNUSED"
GOTO 1400
```

such as that produced by Microsoft is the simplest method. I did not use Fortran because it is rather hard to plot graphs using the Fortran Format statements. It is also much harder to write a proper command decoder using Fortran rather than Basic. However, rather than spending money on a Basic compiler, I decided to re-code the FOR...NEXT Q loop, using assembler, and call the machine code subroutine from the Basic. I will not describe the assembler code in detail as it depends on the computer in use; but I will describe the macro-codes I used. Provided a Macro-assembler is available, the macro-code will be the same for any computer.

Macro-codes

A macro is a block of code which is invoked whenever the macro call is used. The macro-assembler sees the name of the macro called, and automatically inserts in its place the block of code defined. This would be useful even if it just saved typing, but the technique really comes into its own when the macro can have arguments.

If I define a macro for multiplication, called, say, MPY, then I shall need to specify a multiplier, a multiplicand and a place for the answer. The macro MPY is used as follows:

MPY X,Y,Z is equivalent to $Z=X*Y$
It is defined by saying:
MPY MACRO A,B,C

*(code is entered here)

ENDM

The code for the multiplication is not shown but whenever MPY is used that

code replaces the macro-call. The real arguments X, Y and Z are substituted in place of the dummy arguments A, B and C. It is now possible to use expressions like:

MPY X,Y,Z
MPY Z,W,Z

which is the equivalent of $Z=W*X*Y$, and $MPY X,X,X$

this is the same as (LET) $X=X**2$

The macro-codes for use in the FOR...NEXT Q loop are shown in the appendix.


Graph plotting

Here is a Basic program for plotting gain and phase shift simultaneously on a line-printer or v.d.u. Examples are shown. It should be noted that both frequency and gain are plotted using logarithmic scales. Gain and phase axes are drawn so as to completely fill a page, with automatic scaling of axes. A gain point is plotted as a letter G, a phase point as a P, but if both coincide the letter B is used at that point. The code is as follows:


```
REM PLOT A GRAPH
INPUT "HEADING":C#
INPUT "FROM WHAT FREQUENCY":F1
INPUT "TO WHAT FREQUENCY":F2
INPUT "IN HOW MANY STEPS":NF
RA=EXP(LOG(F2/F1)/(NF-1))
LPRINT CHR$(12)
LPRINT TAB(30);"FREQUENCY RESPONSE CURVE - :C#"
LPRINT
MN=1E38 : MX=-1E38 : F=F1/RA
A1=-90 : A2=90
FOR I=1 TO NF
F=F*RA
FR(I)=F
GOSUB 20000
GOSUB 21000
GOSUB 22000
GOSUB 23000
IF MX<G THEN MX=G
IF MN>G THEN MN=G
IF A1<A THEN A1=A
IF A2>A THEN A2=A
GG(I)=G
AA(I)=A
NEXT I
RN=MX-MN
RA=A1-A2
ST=RN/20
SA=RA/20
LPRINT
LPRINT "GAIN dB (G) : "
FOR I=0 TO 20
LPRINT TAB(16+I*5) :
LPRINT USING "###.#":(MN+ST*I)
NEXT I
LPRINT
FOR I=1 TO NF
LPRINT USING "#####.#" : FR(I) :
LPRINT " Hz" : TAB(20) :
GS=INT(100*(GG(I)-MN)/RN)
AS=INT(100*(AA(I)-A2)/RA)
IF GS>AS THEN S1=AS : C1$="P" : C2$="G" : S2=GS-AS-1
IF GS<AS THEN S1=GS : C1$="G" : C2$="P" : S2=AS-GS-1
IF GS=AS THEN S1="B" : S2=1 : C2$=""
LPRINT SPC(5) :
LPRINT C1$ :
LPRINT SPC(5) :
LPRINT C2$ :
NEXT I
LPRINT
LPRINT "PHASE DEGREES : "
FOR I=0 TO 20
LPRINT TAB(16+I*5) :
LPRINT USING "###.#":(A2+SA*I)
NEXT I
RETURN
```

All the print statements can be seen to be LPRINT statements and a 132 column printer was used. If v.d.u. output is required, then PRINT statements should be substituted and the graph should be scaled according to the width available.

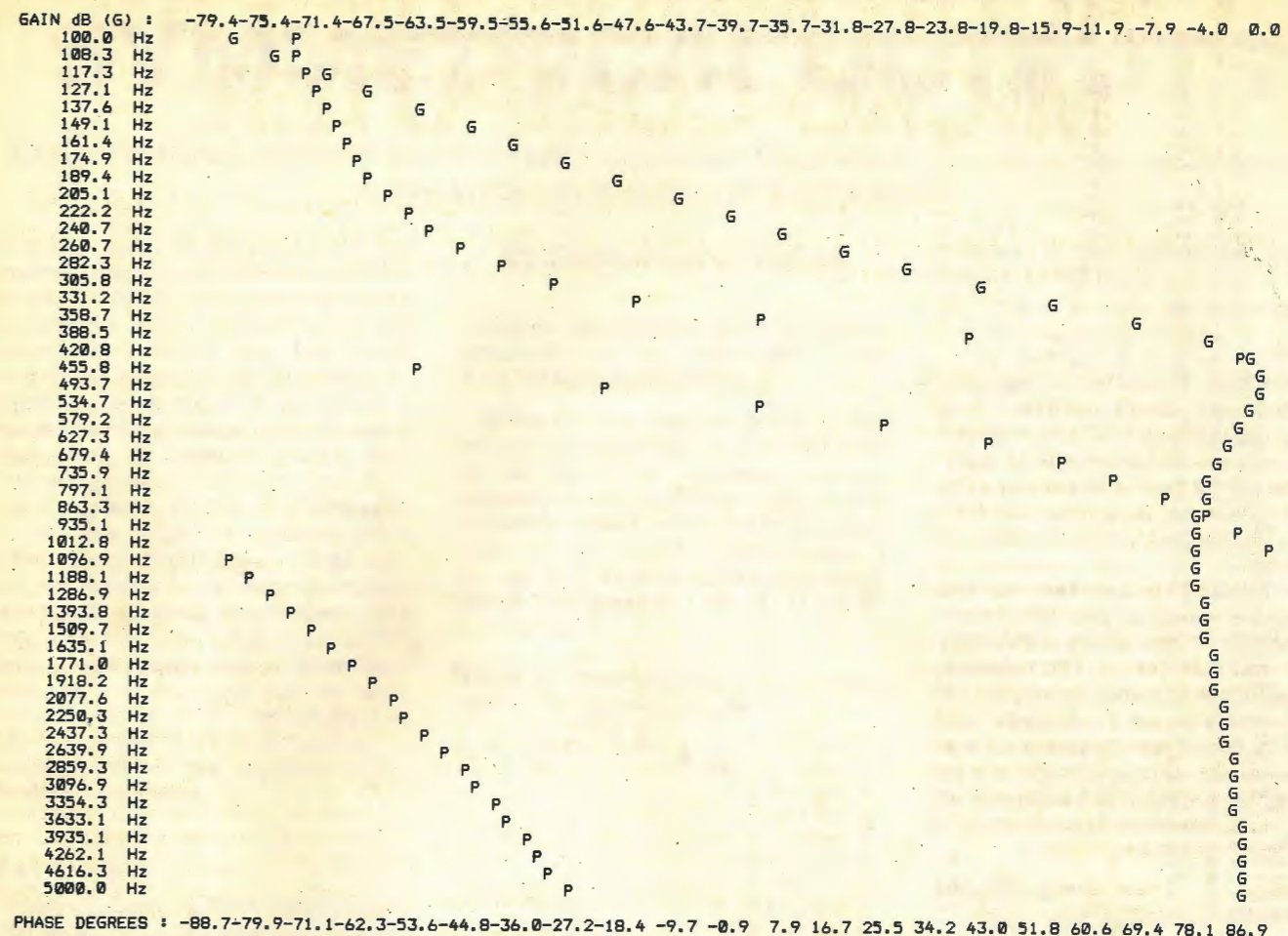
FREQUENCY RESPONSE CURVE - FIFTH ORDER LOW-PASS FILTER



FREQUENCY RESPONSE CURVE - LCR NETWORK

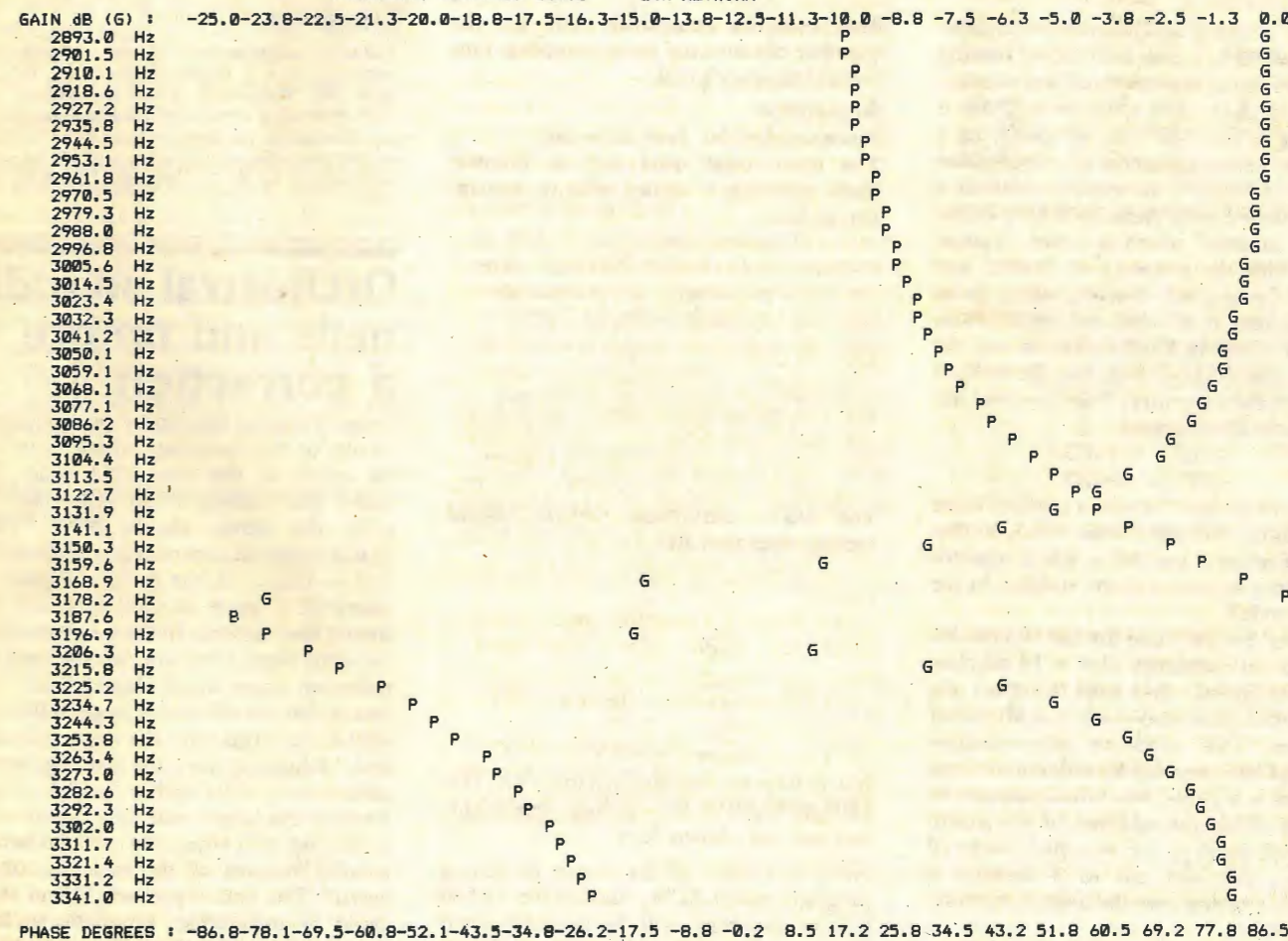

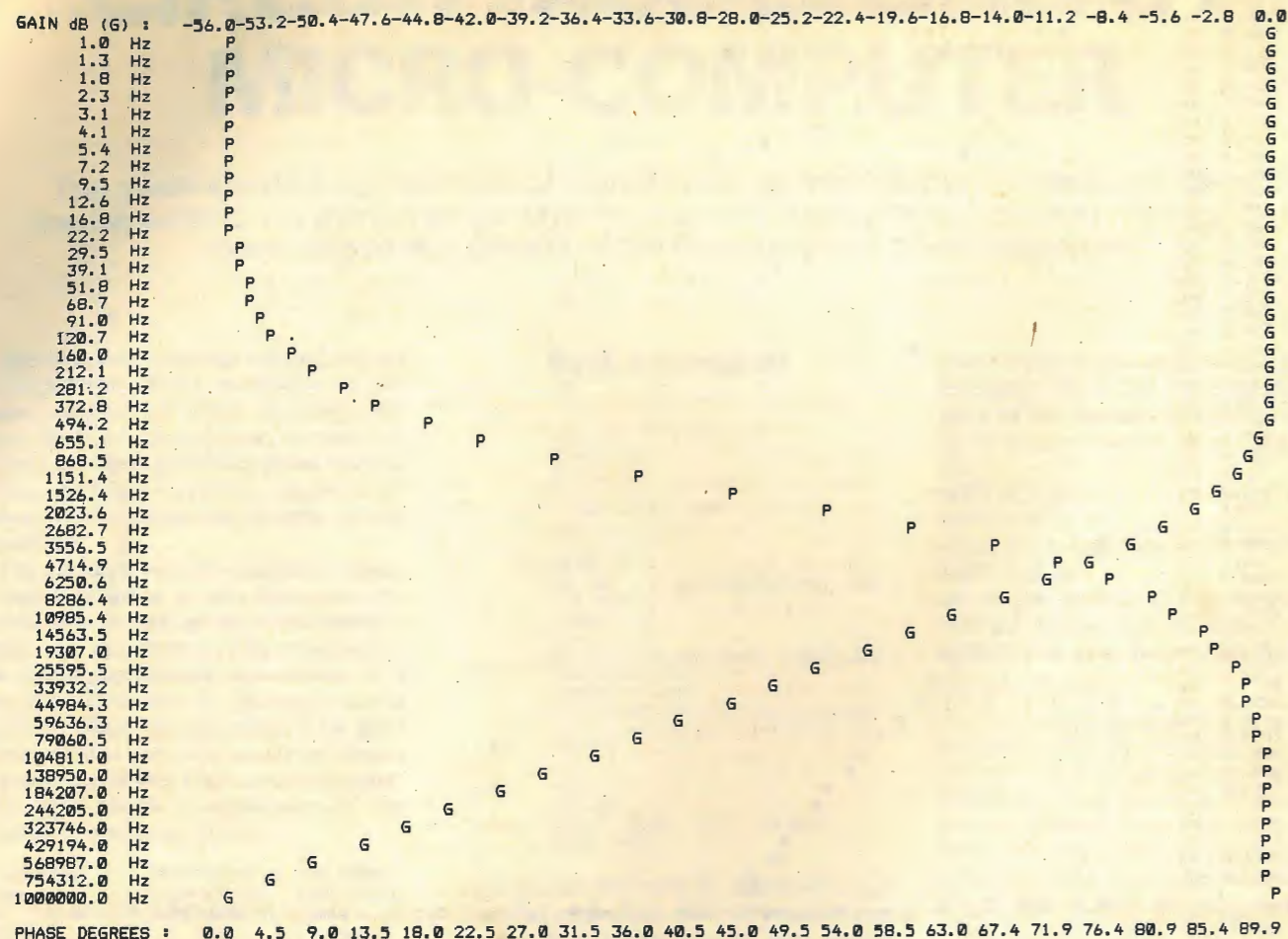PHASE DEGREES : -86.8-78.1-69.5-60.8-52.1-43.5-34.8-26.2-17.5 -8.8 -0.2 8.5 17.2 25.8 34.5 43.2 51.8 60.5 69.2 77.8 86.5
Graphs produced by the program. The frequency axis is vertical, so the curves may make more sense if viewed from the side.



While working on loudspeaker crossovers, I wanted to model a crossover feeding two drive units, one of which was connected out of phase. For speakers in phase it was easy to find the sum by specifying a summing network, but for an out-of-phase speaker, I found it necessary to invent a non-existent circuit element. I have called this an 'inverter' which is a two terminal device with the property of 'losing' any current flowing into it while taking in an equal current at its other end which is also lost. This violates Kirchhoff's law and the charge conservation laws, but the method works on the computer. The 'inverter' has admittance determinant:

$$\begin{vmatrix} +1E5 & +1E5 \\ +1E5 & +1E5 \end{vmatrix}$$

and the value used (always a positive value added to the YR array) was +1E5, so that the net effect was of a small resistor connecting an out-of-phase speaker to the output node.

Having cut the time for our typical 16-node circuit frequency plot to 16 minutes from two hours, I then tried the effect of a BASIC compiler and used the Microsoft compiler. This produces true machine code and the time for 50 reductions from 16 nodes to a 2-by-2 was now 2 minutes 48 seconds. With the addition of the macro assembler codes to the two inner loops (P and Q), this was cut to 2 minutes 6 seconds, a saving over the original running time of 98%.

So it can be seen that with a little effort, much time can be saved. The purchase of a

Basic compiler compatible with the interpreter can turn the home computer into a useful designer's tool.

Appendix
Macro-codes for fast reduction
The macro-code used was as follows: Each operation is shown with its equivalent in Basic:

```

MSB  Y3,Y5,Y4,Y6,B  :B=Y3*Y5+Y4*Y6
MAD  Y5,Y4,Y6,Y3,C  :C=Y4*Y5+Y6*Y3
MAD  B,Y1,C,Y2,D    :D=B*Y1+C*Y2
MSB  C,Y1,B,Y2,E    :E=C*Y1+B*Y2
DIV  D,A,D          :D=D/A
DIV  E,A,E          :E=E/A
SUB  YRPQ,D,YRPQ   :YR(P,Q)=YR(P,Q)-D
SUB  YIPQ,E,YIPQ   :YI(P,Q)=YI(P,Q)-E
RET
END
    
```

The macro definitions, which should precede their use, are:

```

MAD  MACRO  M1,M2,M3,M4,ANS
      MPY   M1,M2,T1
      MPY   M3,M4,T2
      ADD   T1,T2,ANS
      ENDM

MSB  MACRO  M1,M2,M3,M4,ANS
      MPY   M1,M2,T1
      MPY   M3,M4,T2
      SUB   T1,T2,ANS
      ENDM
    
```

All other macro definitions (ADD, SUB,MPY,DIV) are machine dependant, and are not shown here.

Note: A version of the circuit modelling program, called ACM, suitable for TRS80 micro-computers, will be available from Molimerx Ltd, 1 Buckhurst Road, Town Hall Square, Bexhill-on-Sea, E. Sussex.

References

This article is an extension of "Circuit analysis by small computer," by A. S. Beasley, *Wireless World*, Feb. and April 1980. Photocopies of this are available from WW, Editorial, at a price of 90p inclusive. An interesting discussion of the theory may be found in "Two-port representation of multi-mode networks by matrix partitioning," by R. T. Kennedy, *J.I.E.R.E.* Feb. 1969.

Orchestral sounds, halls and timbre - a correction

Denis Vaughan has kindly pointed out to us one or two misprints which crept into his article in the May 1982 issue: Just under the heading 'First reflections' on p.32, the phrase should read: "Their timing is exactly controlled by the width (1 foot ≈ 1ms)." In the middle of page 33, reference is made to Guildford and this should read Gilford. In the third column of the same page, there are two references to reflection times which should read: "this means that the effectively larger reflections start about 81ms after the original sound". and; "Kingsway has quite a lot of powerful reflections to offer within the first 105ms. Because the larger reflections continue to return up to 147ms, the substantial and lengthy support of the musicians is assured". The figures printed (18 and 14ms) could be misleading, especially to those interested in modelling electronically the initial reflection pattern of the hall.

DIGITAL DIVIDERS WITH SYMMETRICAL OUTPUTS

The author uses Johnson counters with controlled feedback to give symmetrical even and odd-numbered divisions of a clock pulse.

By Cornelius van Holten

Time and again, in literature on digital circuitry, ideas are published on the problem how to obtain a 50% duty cycle when a regular pulse train is divided by an odd number. Some clever (and less clever) methods are proposed, e.g. the use of exclusive-or gates in the clock pulse lines, a separate flip-flop with a delay of half a pulse period, the output of which is combined with the normal flip-flops, etc.

In my opinion, the use of EXOR-gates in clock lines should be avoided, since spikes on the output-signals of the flip-flops may occur; a better way is to combine the outputs signals of the flip-flops. The ideas, found in Refs. 3 and 4 are broadened in this paper, and a generalized scheme is proposed which may be easily expanded. Moreover, the control input is pure binary and there is no attempt to change the (odd or even) sequence length. Standard i.cs are used.

The Theory

When a Johnson or Möbius ring counter is fed back, a sequence length of n or 2n is derived, depending on whether a straight or twisted loop is used. The maximum sequence-length is 2n for n bits, and sequences of 2(n-1) etc, are derived when outputs, other than the last, are chosen. When two adjacent outputs are fed back via an AND-gate and negated, (Fig. 1.) any length between 2n and 2 may be obtained.

If an auxiliary flip-flop is connected to the chain and is switched on the opposite pulse edge, the output is shifted over 1/2T, where T is the clock pulse period. It is necessary for the incoming pulse train to have a duty cycle of 50%; if not, a divider is needed which will halve the frequency. In Fig. 2, the outputs of 2 flip-flops, FF₁, the last in the chain, and FF₂, the extra flip-flop, are combined in an OR-gate to

Table 1. Feedback signals and sequence length.

Feedback	Sequence/length
A	2
AB	3
B	4
BC	5
C	6
CD	7
D	8
DE	9
E	10
EF	11
F	12
FG	13
G	14
GH	15
H	16

obtain an odd sequence length (9) with a symmetrical output. In this case, D and E are fed back (see Table 1).

When an even sequence length is chosen, a symmetrical output is derived from the last flip-flop in the chain, only one (negated) output is fed back and no OR process is needed. In the Table 2, a list is given of all possible combinations; I through VIII are the controls signals which switch the (negated) I for A, II for B, ... VIII for H.

Table 2. Control inputs and corresponding sequence lengths.

Control inputs	Output (*T)
I	1 + 1 = 2
1 1	1 1/2 + 1 1/2 = 3
1	2 + 2 = 4
1 1	2 1/2 + 2 1/2 = 5
1	3 + 3 = 6
1 1	3 1/2 + 3 1/2 = 7
1	4 + 4 = 8
1 1	4 1/2 + 4 1/2 = 9
1	5 + 5 = 10
1 1	5 1/2 + 5 1/2 = 11
1	6 + 6 = 12
1 1	6 1/2 + 6 1/2 = 13
1	7 + 7 = 14
1 1	7 1/2 + 7 1/2 = 15
1	8 + 8 = 16

Complete circuit

In Fig. 3, the complete diagram is given, consisting of 8 flip-flops (a shift register), a pulse circuit, an output, feedback gates controlled by the inputs I to VIII, and a decision making circuit with 4 full adders for odd and even lengths.

The latter operates as an EXOR-gate with 8 inputs: Y = I ⊕ III ⊕ IV. ... ⊕ VIII and therefore Y = '1' for odd and '0' for even lengths; the unused input of the full adder at the bottom is permanently held at a logical '1' level.

In the output circuit, the function H + YZ is realized. For Y = 0, the output

becomes H (for even length sequences) and for Y = 1, the output is H + Z (for an odd length) as shown in the time charts in Fig. 4a and 4b respectively.

The flip-flops A to H are D flip-flops, operating in the leading clock pulse edge and Z (auxiliary flip-flop) reacting on the trailing edge of it. The P flip-flop is needed when the input pulses are not symmetrical, and a buffer gate is used for amplification. The correction and enabling circuit is described in the Appendix. In normal circumstances, this circuit is inoperative and the shift register is loaded with all zeros by the enabling input, and cycles via 10000000, 11000000, 11100000, ... through 11111111, 01111111, etc. back to the all zero condition. This is the "normal" sequence, 1 out of the 16 possible cycles. Of course, other values of n than 8 are possible, this number has been chosen for comparison with the circuit described by Girolami and Bamberger².

Modification

In Fig. 3(a), there are 8 control inputs which are used separately (for even lengths) or in groups of adjacent pairs (for odd lengths). If one wishes to control the sequence length via a binary weighted control input, a decoder is needed as described in Table 3.

In Fig. 3(b), a read only memory is programmed as a decoder, and the input 1 may be used to control the output circuit: even or odd; the output function is H +

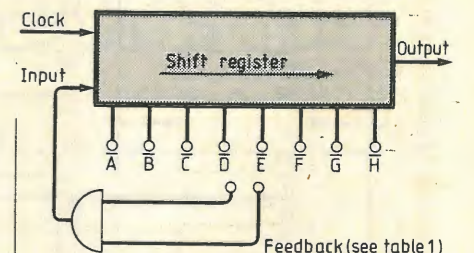


Fig 1. Basic principle of a variable length counter.

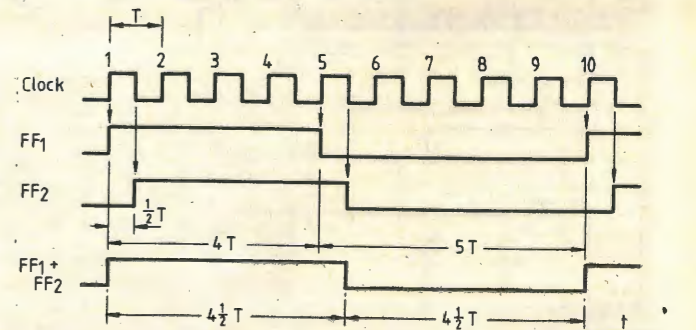


Fig 2. The addition of two asymmetrical flip-flop outputs leads to a symmetrical output.

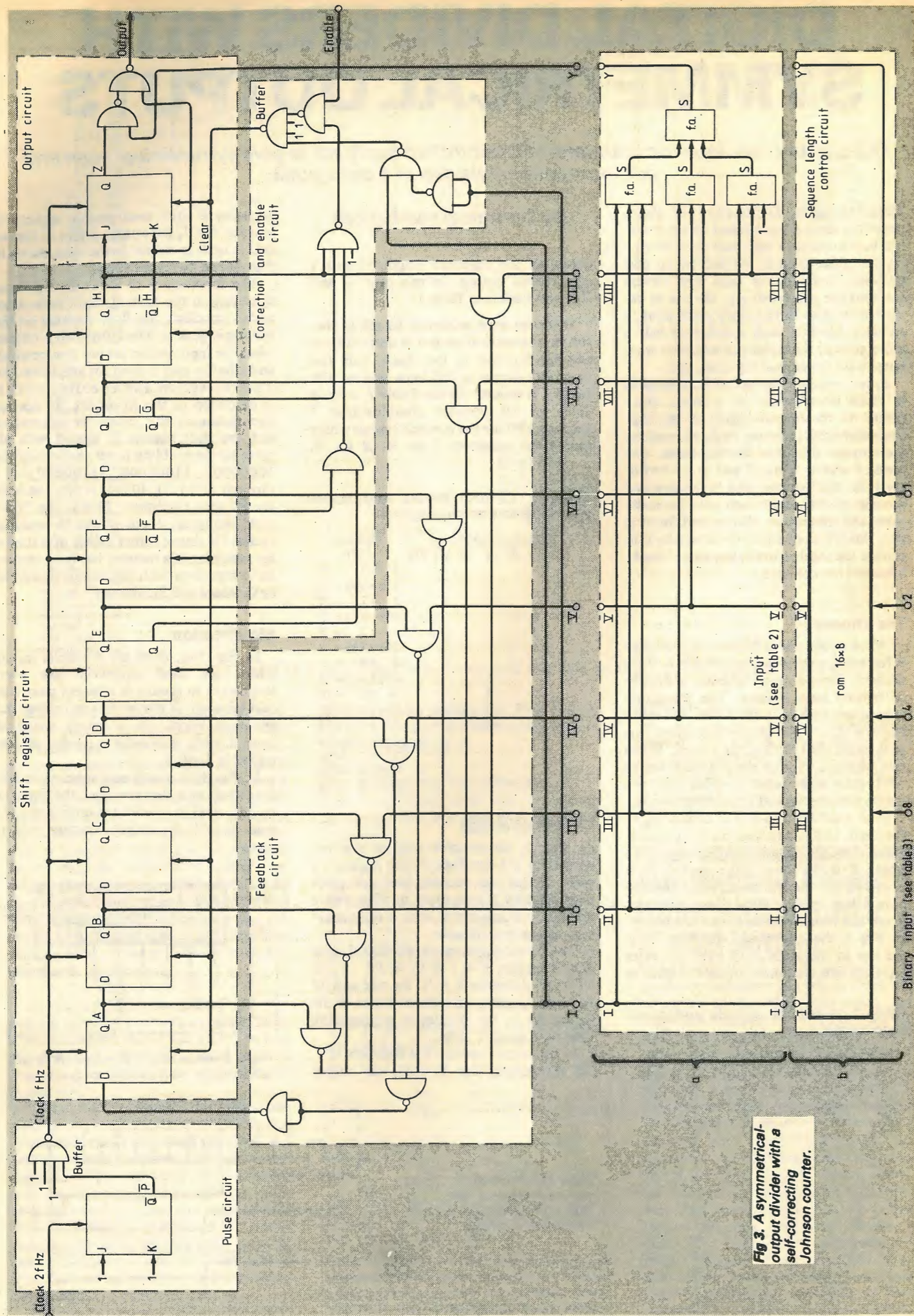


Fig 3. A symmetrical-output divider with a self-correcting Johnson counter.

Table 3. Binary weighted control inputs and corresponding signals and sequence lengths.

Input	I	II	III	IV	V	VI	VII	VIII	Sequence length
8 4 2 1									
0 0 0 1				no sense					—
0 0 1 0	1	0	0	0	0	0	0	0	2
0 0 1 1	1	1	0	0	0	0	0	0	3
0 1 0 0	0	1	0	0	0	0	0	0	4
0 1 0 1	0	1	1	0	0	0	0	0	5
0 1 1 0	0	0	1	0	0	0	0	0	6
0 1 1 1	0	0	1	1	0	0	0	0	7
1 0 0 0	0	0	0	1	0	0	0	0	8
1 0 0 1	0	0	0	1	1	0	0	0	9
1 0 1 0	0	0	0	0	1	0	0	0	10
1 0 1 1	0	0	0	0	1	1	0	0	11
1 1 0 0	0	0	0	0	0	1	0	0	12
1 1 0 1	0	0	0	0	0	1	1	0	13
1 1 1 0	0	0	0	0	0	0	1	0	14
1 1 1 1	0	0	0	0	0	0	1	1	15
0 0 0 0	0	0	0	0	0	0	0	1	16

YZ, realized by NAND gates via the formula $H \cdot YZ$

Conclusion

A method is proposed by which in a straightforward manner any sequence length may be chosen via a binary weighted input. The circuits are normal s.s.i. or m.s.i. i.cs; for an 8 bit integrated shift register, the clock input is buffered as is the clear input. The buffers may be left out. The output is symmetrical and no spikes occur, since the Johnson principle is in fact a Gray code of sorts, changing only 1 output per clock pulse.

The number of flip-flops is $\frac{1}{2}n$, when n is the sequence length, whereas for a normal counter $\log_2 n$ flip-flops are needed. There is little disadvantage, however, with low prices. In both cases the sequence is nonbinary.

Appendix

With $n = 8$, there are 256 possible zero-one bit patterns, of which only 16 (8×1 and 8×0 in groups of 8) are valid. All



Cornelius van Holten holds an honours degree in electrical engineering from the Technical College at Rotterdam and a degree from the Delft University of Technology. He is in charge of a digital engineering laboratory for undergraduates in the Applied Physics Department of the Delft University, and lectures in measurement methodology.

He has written a self instruction course in digital circuitry and some 20 papers in periodicals.

other sequences have to be detected and corrected; since 00000000 is a valid combination, resetting of all flip-flops is an easy way to correct.

If one wishes to correct any invalid combination immediately, a rather complex circuit is needed; it turns out, however, that with certain combinations, the register may be reset; within 16 clock pulses any error will be removed.

In the normal sequence, no '0' is present between '1's; so 101 looks a good bit pattern to detect. However, not all sequences contain this combination; 1001 also occurs.

To check these sequences we write down any non-normal sequence, economizing space by writing the notation in a row, as follows:
e.g. 1110110100010010

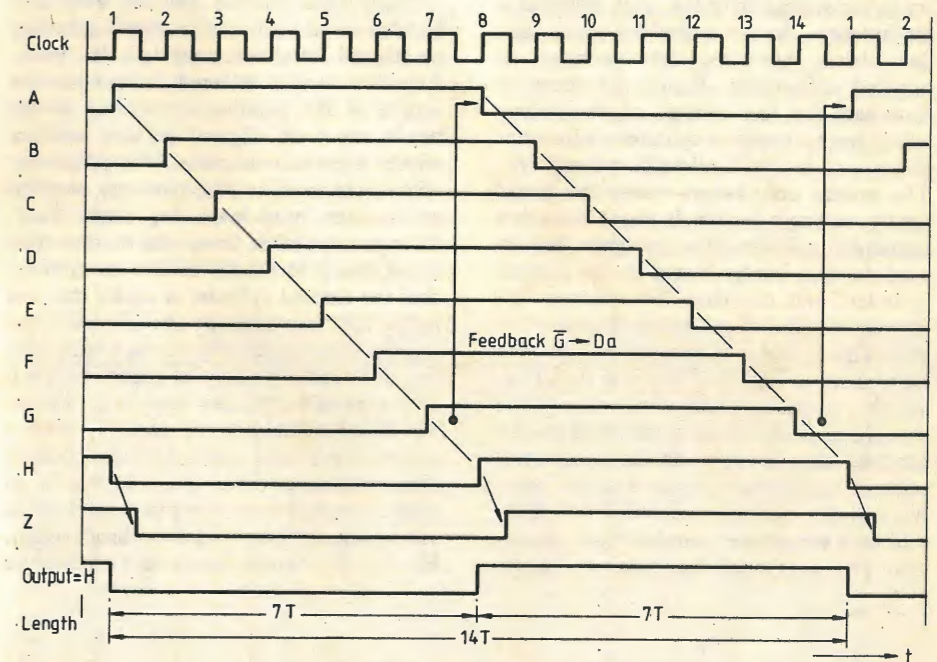


Fig 4a. Time chart for an even-numbered division (e.g. 14).

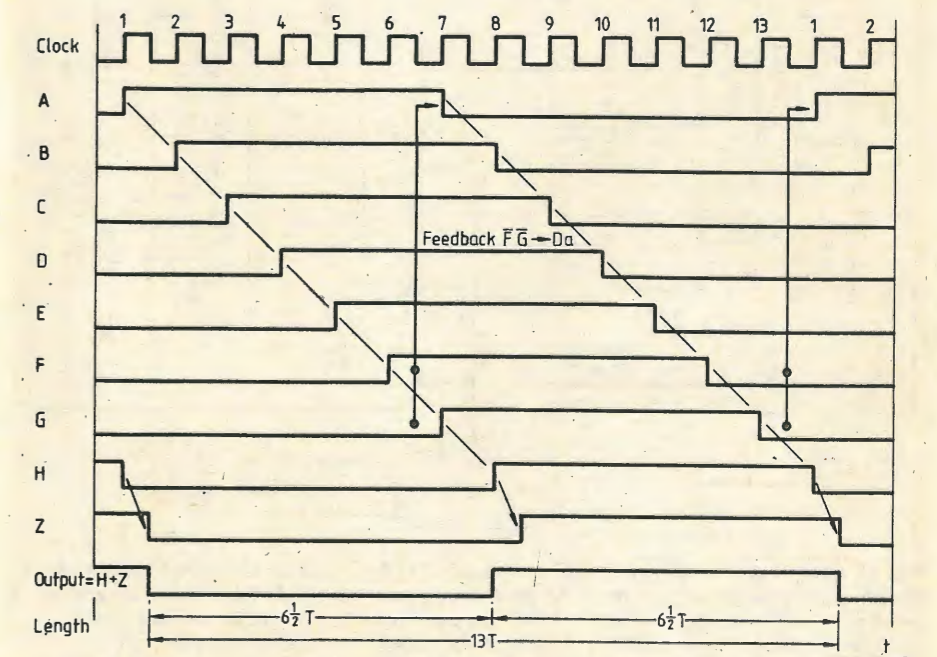


Fig 4b. Time chart for an odd-numbered division (e.g. 13).

The ends are in fact connected, so by checking 101 and 1001 "over the edge" if needed, the result is:

101: (3x) and 1001: (1x)
This means that FGH and EFGH have to be used; simplification gives:
 $(EF + F) \bar{G}H = (E + F) \bar{G}H$ or rewritten in NAND-form:

$\overline{E.F.GH}$
Since reset is a '0' signal, we invert this to: $\overline{E.F.GH}$; a buffer and an external enable (normally '1') signal results in the circuit as show in Figs. 3 and 4.

For a sequence of 2, however, this correction has to be corrected itself by an

I.II signal (I is 1, II = 0) since this short sequence the detection patten occurs.

A	B	C	D	E	F	G	H
0	1	1	0	0	0	0	0
0	0	1	1	0	0	0	0
1	0	0	1	1	0	0	0
1	1	0	0	1	1	0	0
0	1	1	0	0	1	1	0
0	0	1	1	0	0	1	1
1	0	0	1	1	0	0	1

Detection and correction follows: there is no reason, to choose EFGH; any group of 4 consecutive outputs is valid. The reset is asynchronous, i.e. not controlled by the

clock pulse, but within one period T the counter is ready and starts again, whatever the sequence length may be. □

References

1. L. E. Getgen. Divide symmetrical clock pulses by odd numbers, get a symmetrical output. *Electronic Design*, 5, March 1, 1980, p.110.
2. G. Girolami, P. Bamberger, Symmetrical-output dividers, *Wireless World*, February 1982, p.53, 54.
3. R. M. M. Oberman. *Electronic Counters*. Macmillan, London, 1973, p.151ff.
4. M. Morley. Two IC's restore symmetrical output to a ring counter. *Electronic Design*, February 18, 1982, p.206. □

continued from page 36

try in the system error log, as it indicates a malfunction. In the embedded-servo surface drive, however, the condition is handled differently. Figure 13 shows a flowchart for the control of the drive, which has no absolute cylinder-address register, and in which all seeks are relative. The system only knows where the heads are by reading a header. In order to reach a particular cylinder, the program has to read the first header it sees on the current cylinder, and calculate the cylinder difference required to get to the desired cylinder. This cylinder difference, which may be positive or negative, is sent to the drive, which performs a deductive seek. When this is complete, the program again reads a header. Most of the time the header will contain the desired cylinder address, proving that the seek was successful, but in the odd case where the cylinder count deduction was in error, the program simply

loops and calculates a new difference value until the correct cylinder is reached.

Since each surface has its own embedded-servo information, the heads may be aligned using a normal data disc pack. As a new head is selected, it becomes the source of the position error, and as the heads are only aligned to one another within a certain tolerance, the positioner will adjust itself to eliminate any position error when head switching takes place. This process takes time, and further time is necessary to read a header to confirm that the desired cylinder is under the new head. The time taken by this process is the same as that needed to perform a one cylinder seek, such as might be necessary when all tracks of a cylinder have been written but there is still data to transfer. With a conventional disc drive format, both of these processes would cause the loss of an entire revolution of the disc, waiting for sector zero to come under the heads again. Having abandoned the concept of absolute

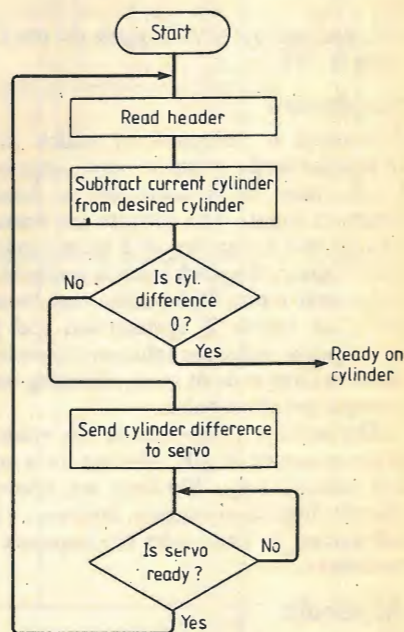


Fig. 13. Flow chart for an embedded-servo positioner system. An absolute cylinder-address register is not used, so all seeks are relative. Seek errors simply cause an extra execution of the loop.

cylinder addressing, which made it necessary to read headers to discover the head position, it is also possible to abandon the fixed index concept, as the sector number is contained in every header read. There is no index point on the disc, and all of the sector pulses are identical. The format of adjacent tracks is displaced to allow enough time for a seek or head change, and for a header to be read to confirm the position, before sector zero of the new track comes around. In the case of a long data transfer of many blocks, a significant transfer-time reduction is achieved, since rotational latency is eliminated.

It is possible to build two versions of the drive. In the first, only the position error developed during S1 is used for track following. In the second, the position error from S1 is used for track following on even cylinders, and that from S2 used on odd cylinders. The second version obviously has twice as many cylinders as the first, but in other respects is basically the same.

Winchester technology and floppy discs and their drives are discussed in the next part of this series. □

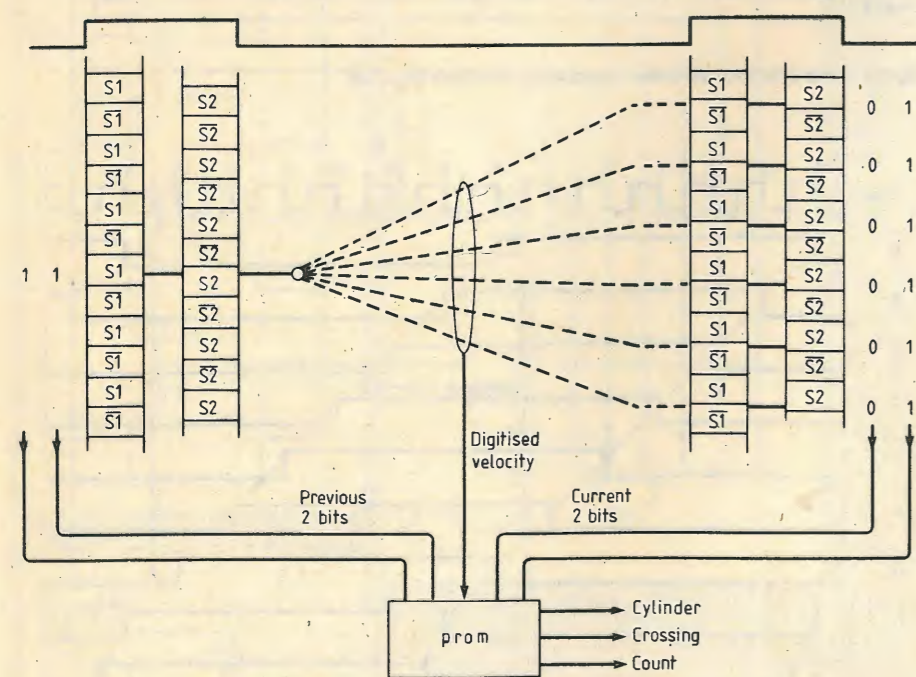


Fig. 12. Here, a seek is being carried out and value 11 from a servo sector has been stored for comparison with two bits from the next servo sector. As can be seen, there are many positions on the subsequent sector where the positioner appears to be on the correct cylinder. To avoid this ambiguity, digitized information from the carriage velocity transducer together with the two stored bits and two bits currently being read address a prom which returns the cylinder crossing count.

DIGITAL FILTER DESIGN

Fast numerical operations using limited precision fixed-point arithmetic are now being provided by new types of microprocessors and l.s.i. circuits. This third article in a series of four outlines some of the problems of using fixed-point arithmetic and gives a brief survey of the new devices, concentrating on the Intel 2920.

by B. M. G. Cheetham and P. M. Hughes

Three types of operation are required for digital filters: multiplication of samples by constant coefficients, addition, and temporary storage for delaying samples. The digital filter shown in Fig. 1, a bi-quadratic section, represents the sequence of mathematical operations that must be carried out for each input sample x_n referred to as X to produce an output sample y_n referred to as Y. The sequence of operations may be summarized as

1. Calculate W by adding W multiplied by $-b_1$ and W' multiplied by $-b_2$ to X. (W and W' are values of W stored during previous executions of this algorithm - see steps 3 & 4).
2. Calculate the output Y by adding W times a_1 and W' times a_2 to W.
3. Set W' to the number currently stored in W for next time.
4. Set W equal to the number currently stored in W.

Recursive digital filters are generally implemented as cascades of biquadratic sections i.e. the required transfer function $H(z)$ is expressed as the product of second-order transfer functions $H_1(z), H_2(z) \dots$ each being realised by a distinct digital filter section of the type illustrated. A practical digital filter, therefore, would be a device or devices capable of performing the calculation sequence listed above for all biquadratic sections, for each input signal sample x_n . These calculations must be carried out accurately and within the time-span available between samples in real-time applications. Before looking at real-time digital filters, however, consider briefly their implementation on general-purpose digital computers.

Real-time processing

Although digital filters have been studied for many years, their use has until recently been mainly confined to research applications and computer simulations. This is likely to change rapidly with the development of special-purpose microprocessors and v.l.s.i. devices for signal processing. Such devices essentially execute the type of program discussed in the panel, but if the programmed filter is to be used for continuous signals sampled in the Nyquist rate, all numerical calculations must be completed for each input sample before the next one becomes available; otherwise an increasing backlog of samples would be built up. This imposes a speed requirement which is not present when processing blocks of stored data on a general purpose computer. Such processing would normally use the highly accurate floating-point arithmetic operations provided by high level languages but at great cost in processing time, typically 100µs per

multiply or add. The necessary increase in processing speed required for real-time filtering is currently possible only at the expense of accuracy through the use of fixed-point arithmetic. It is thus necessary to represent all samples, coefficients and results of additions and multiplications by binary numbers of limited wordlength with the equivalent of the decimal point, i.e. the binary point, assumed fixed at some position within the word.

For example, the 16-bit number 0.11000000001101 with fixed binary point represents the decimal number 0.75040 correct to about five significant figures, whereas 0.0075040 must be written as 0.00000011110110 which gives


only about three significant figures of precision. In contrast to floating-point numbers, the accuracy to which a fixed-point number represents a given number depends on its magnitude. Care must be exercised in positioning the binary point lest the addition of two numbers be allowed to overflow, producing a result too large for the chosen format. Negative numbers may be represented in two's complement form with a value obtained by subtracting 1.XXX... from the fractional part of the binary number. In this representation, the fixed-point numbers outside the range ± 1 are not allowed and all numbers likely to appear within a digital filter would have to be scaled accordingly.

The use of fixed-point number representations clearly introduces complications in the design of digital filters and introduces

Programming on general purpose computers

Digital filters are often programmed in high-level languages such as Fortran or Basic and run on general-purpose computers or microcomputers to process blocks of signal samples stored as data arrays. This approach may be used to analyse experimental data where unwanted effects must be filtered out or where particular features must be extracted; you may have used the "trapezoidal rule" for numerical integration $y_n = y_{n-1} + (x_n + x_{n-1})/2$, without realizing that the formula represents a type of digital filter.

Programming a digital filter on a desk-top computer is a very useful way of testing its design before building it. In this application the programmed filter is a simulation of the system to be built, which may be tested by feeding in special test signals generated or captured as blocks of data by the computer. Programming digital filters in high-level languages is straightforward and a good way of learning about their capabilities.

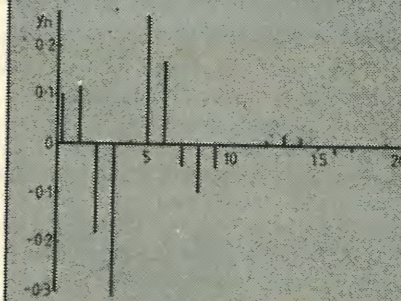

As an example, a Basic program for a fourth-order digital filter is given in the first listing. The filter consists of two biquadratic sections with transfer functions

$$\frac{1-2z^{-1}+z^{-2}}{1-1.0524z^{-1}+0.6232z^{-2}}$$

$$\text{and } \frac{1+2z^{-1}+z^{-2}}{1-0.1665z^{-1}+0.5348z^{-2}}$$

This filter has a Butterworth type band-pass response (passband 0.125f_s to 0.25f_s, where f_s is the sampling frequency), as designed in the previous article. Each biquadratic section is implemented by calling a subroutine (GO-SUB 800) with coefficients a_1, a_2, b_1, b_2 , stored in the Jth elements of arrays A1, A2, B1, B2; J is 1 for the first biquadratic section and 2 for the second. The subroutine simply follows steps 1 to 4 derived from Fig. 1 with the Jth elements of arrays W1 and W2 holding W and W' as required for subsequent calls to the subroutine. Arrays W1 and W2 are zeroed before the first call to the subroutine. Variables X and Y are the input to and output from the programmed biquadratic section. For this example, an array X loaded with 21 samples of the discrete time impulse δ_n is used as an input signal. Output samples are stored in a second array Y and are also printed out. Graph shows the output obtained from this program. This method may be generalised to digital filters of any order with input and output data arrays of much larger dimension.

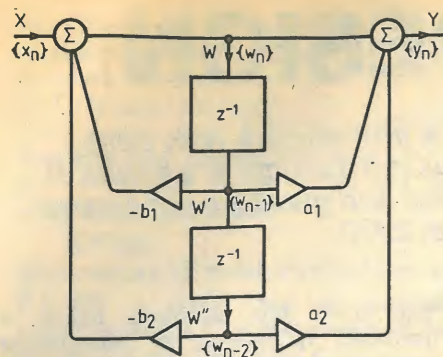


Fig. 1. Recursive digital filters are generally implemented as cascades of biquadratic sections, above. Diagram shows sequence of mathematical operations that must be carried out for each input sample $\{x_n\}$ to give output sample $\{y_n\}$.

innaccuracy which will tend to degrade performance as compared with the theoretical ideal. Some of the most important effects are next considered.

Quantization noise. The conversion of an analogue signal into digital form introduces a degree of distortion as a result of representing the sampled voltages as fixed-point binary numbers. This distortion effectively adds on error signal known as quantization noise to the original signal, as illustrated in Fig. 2. The level of this unwanted noise signal is determined by the wordlength available and the dynamic range allowed for the analogue signal i.e. its expected maximum and minimum voltages. It may be shown that an n-bit analogue-to-digital conversion (with $n > 4$) results in a quantization noise signal of r.m.s. value $\Delta/2\sqrt{3}$, $\Delta = (V_{max} - V_{min})/2^n$, is known as the quantization step. In theory, the noise is spread evenly over the frequency spectrum 0 to $f_s/2$. For a zero-mean input of r.m.s. value σ , the signal to quantization noise ratio is

$$20 \log_{10}(2\sqrt{3}\sigma/\Delta) \\ = 20 \log_{10}(2\sqrt{3}\sigma \cdot 2^n/2V_{max}) \\ \approx 6n + 10.8 + 20 \log_{10}(\sigma/V_{max}) \text{ dB.}$$

For this formula to be valid, input signal must not exceed the prescribed dynamic range. Ensuring that $\sigma \leq V_{max}/4$ achieves this to reasonable accuracy for noise-like signals, giving a maximum s-n ratio of

$$6n + 10.8 + 20 \log_{10}(0.25) = 6n - 1.2 \text{ dB}$$

This formula may be used as a rule-of-thumb for a wide range of different types of input signal although higher ratios may be obtained by reducing σ/V_{max} for specific signals such as sinusoids. Clearly the maximum value depends on the number of bits in the digital representation, and increasing this number improves the figure by 6dB per bit.

Data wordlength. With fixed point number systems both the range and precision of the numbers which can be represented is limited. For convenience it is usual to think of all the signals within a digital filter as being in the range -1 to 1. Such signals require only one bit in front of the binary point, this being used as the sign bit to differentiate between positive

and negative numbers. The precision of the number representation is determined by the number of bits available for storing data. A sixteen-bit data word, for example, with one bit used for the sign, gives a quantization step size of 2^{-15} . All data must therefore be rounded to the nearest integer multiple of 2^{-15} . In practice it is difficult to determine exactly how many bits are needed to satisfy particular performance requirements. The present generation of special-purpose signal processing devices employ basic wordlengths of between 16 and 25 bits.

Coefficient quantization. When a digital filter is implemented in real time its coefficient values as well as its samples must be quantized and stored to limited precision. The effect is to degrade the frequency response as illustrated in Figure 3. A wordlength of about 12 bits is typically used for coefficients. The second program listed calculates the amplitude-frequency response of a digital filter with original unquantized coefficients and with quantized values as they would be represented in the filter. The maximum difference over the relative frequency range 0 to 0.5 is printed out as a measure of the degree of degradation suffered.

Dynamic range limitations. Signal overflow, which occurs when the result of an addition or multiplication within a filter is out of range, will cause incorrect operation. The errors generated can cause self-sustaining oscillation of large amplitude which are highly undesirable. The simplest way of avoiding overflow is to multiply the input to each biquadratic section by a suitable scaling factor S. The aim is to reduce the input signal level sufficiently to ensure that the largest internal number likely to be generated is within range. For a sinusoidal input, S may be set equal to $1/G_{max}$ where G_{max} is the maximum gain between the unscaled input and any point in the second-order section. This ensures that no internal signal exceeds the input in amplitude. In practice, it is sufficient to examine only the overall gain of the section $G(\omega)$, and the gain $G_1(\omega)$ between the input and the internal signal W . It can be shown that

$$G_{max} \leq 2 \max\{G(\omega), G_1(\omega)\} = 2M \\ 0 \leq \omega \leq \pi$$

with $G(\omega) = |H_2(e^{j\omega})| =$

$$\left| \frac{1 + a_1 e^{-j\omega} + a_2 e^{-2j\omega}}{1 + b_1 e^{-j\omega} + b_2 e^{-2j\omega}} \right|$$

$$\text{and } G_1(\omega) = \left| \frac{1}{1 + b_1 e^{-j\omega} + b_2 e^{-2j\omega}} \right|$$

M may be calculated by evaluating $G(\omega)$ and $G_1(\omega)$ over the range $0 \leq \omega \leq \pi$ and searching for the maximum modulus.

A Basic program for doing this is provided, see third listing. Choosing $S = 1/2M$ will eliminate the possibility of overflow for sinusoidal signals, and in practice will normally prove satisfactory for other types of signal. In many cases this result may be unduly pessimistic and larger scaling factors S may be used depending on the particular filter being implemented and the

type of arithmetic used. If G_{max} is significantly greater than the maximum value of $G(\omega)$ (overall gain) it may be necessary to scale up the output of a section to bring the overall passband gain to unity. Scaling factors are often approximated to the nearest power of two so that the required multiplication may be carried out by simply shifting the signal representation an appropriate number of bits to the left or right.

Example. Consider the scaling required for the first section of the bandpass filter whose impulse response is shown in the panel opposite. The coefficients a_1, a_2, b_1, b_2 for this section are -2, 1, -1.0524, 0.6232 respectively. By means of the program the maximum values of $G(\omega)$ and $G_1(\omega)$ are found to be 2.57 and 3.56 and hence $G_{max} \leq 2M = 7.12$. A suitable scaling factor is therefore $1/7.12 \approx 0.1404$. This would often be approximated to 2^{-3} , the nearest power of two, requiring the input to be shifted three bit positions to the right. As $G_1(\omega)$ is greater than $G(\omega)$ in this example, it would be necessary to scale up the output signal if a maximum gain of unity were required for the whole section.

Microprocessor implementation

In addition to its filtering task, a microprocessor may be required to control a-d and d-a converters, or alternatively interface with other digital devices as a means of signal input and output. When controlling converters it is necessary to provide some means of accurately maintaining a fixed sampling frequency.

The choice of microprocessor type depends mainly on the required sampling rate. The present generation of general purpose eight-bit microprocessors can provide digital filters with sampling frequencies of at most a few hundred hertz; the more powerful 16-bit microprocessors¹ enables this to be increased to about 5 kHz.

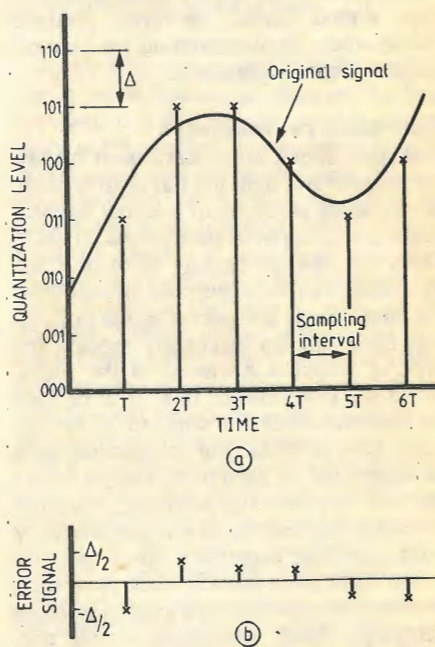


Fig. 2. Conversion of an analogue signal into digital form produces an error signal (quantization noise) which, in effect, is added to the original.

For the real-time filtering of audio bandwidth signals at sampling rates of about 8kHz and above, it has until recently been necessary to employ bit-slice microprocessors² or custom-designed hardware circuits which incur a high component count and circuit board complexity. The introduction in August 1980 of a microprocessor specifically designed for digital signal processing, the Intel 2920, significantly changed this position and marked the start of a new trend in digital signal processing. This is now being continued and emphasized by the introduction of a digital signal processor by NEC³ and the fad⁴, an l.s.i. digital filter designed by British Telecom. Details of other microprocessors intended for digital signal processing have been published⁵ by Texas Instruments and Bell Laboratories.

The Intel 2920 incorporates both a-d and d-a converters on-chip and when programmed as a typical eighth-order digital filter has a sampling rate of approximately 30kHz. As such, the device can be used simply as a one-chip replacement for audio-bandwidth analogue filters. More recent devices differ from the Intel 2920 in that they do not incorporate the converters, but provide the means for interfacing with external converters. These provide more powerful arithmetic facilities than the 2920, including fast high precision multiplication. Large program and data memories are provided by the NEC, Texas and Bell devices which should allow them to implement not only fixed filters, but also adaptive digital filters which automatically modify their frequency response as the characteristics of the input signal change.

The Plessey/British Telecom fad (filter and detect) is not strictly a microprocessor, but sacrifices flexibility for simplicity of operation. It contains on one chip all the circuitry necessary to implement the biquadratic filter section shown in Fig. 1. Used as a single second-order section, the device can operate at a sampling rate of 64000 samples per second, with each input and output sample being up to 16 bits in length. The fully programmable filter coefficients are supplied in serial form by external memory. As an alternative to act-

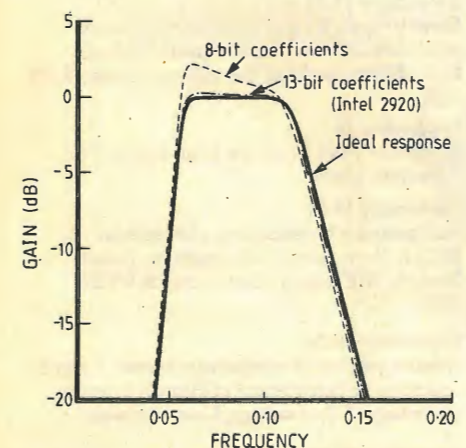


Fig. 3. Amplitude response of an eighth-order Butterworth bandpass filter shows effect of coefficient quantization.

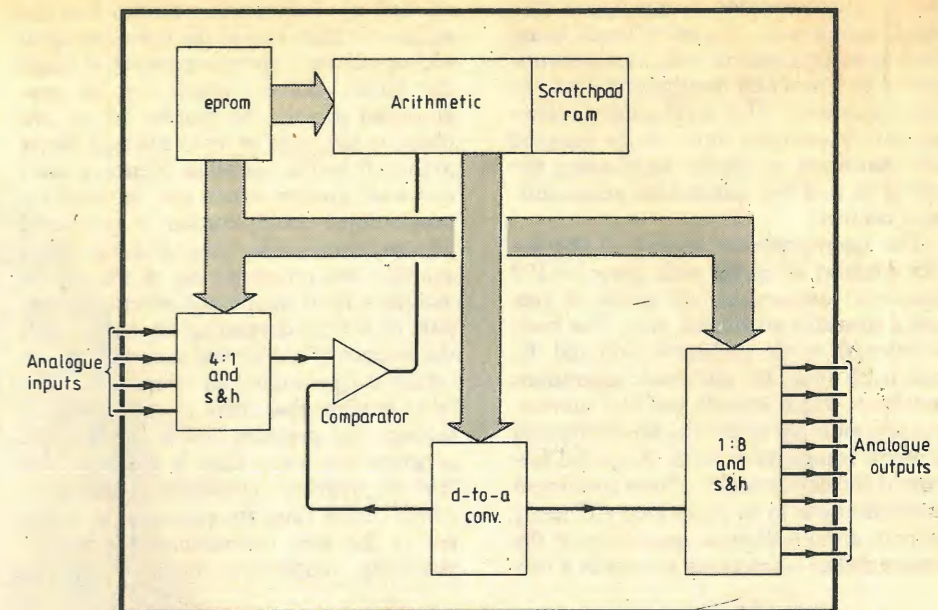


Fig. 4. Intel 2920 is basically a high-speed microprocessor connected to a nine-bit d-to-a converter, with eight multiplexed output channels under software control.

ing as a single second-order section, by using on-chip memory, the fad can be used in a multiplexed fashion to implement a cascade of eight second-order sections, providing a sixteenth-order filter with a sampling rate of 8000 samples per second. Cascades of between two and seven second-order sections can be implemented by modifying external connections.

To illustrate the full capabilities of microprocessor-implemented digital filters and to demonstrate how the techniques described may be applied to their design, consider in more detail the use of the Intel

2920. This device is now generally available, at gradually decreasing cost, and may be programmed by Intel users with a knowledge of digital filters without recourse to expensive design packages.

Intel 2920

Shown schematically in Fig. 4, the Intel 2920 consists basically of a high-speed microprocessor connected to a 9-bit d-to-a converter. The output is connected to a one-to-eight line multiplexer which is under software control. Eight signal output channels are therefore available. The out-

Program to implement fourth-order digital filter on general-purpose computer used in example on page 47

```

10 DIM P(100),Q(100)
20 PRINT "NO. OF SECTNS:"
30 INPUT N
40 PRINT "IDEAL COEFFS:"
50 GOSUB 170
60 FOR I=0 TO 100
70 P(I)=Q(I) @ NEXT I
80 PRINT "QUANTISED COEFFS:"
90 GOSUB 170
100 PRINT "FREQUENCY IDEAL AC
    TUAL(DB) @ N=0"
110 FOR I=0 TO 100 @ F=I/200
120 PRINT USING "0.DDD,7D,2D,6D,
    2D" ; F,P(I),Q(I)
130 M1=ABS(P(I)-Q(I))
140 IF M1>M THEN M=M1
150 NEXT I @ PRINT "MAX DIFF=";M
160 STOP
170 FOR J=1 TO N @ K=J+J
180 PRINT J;" A1,A2,B1,B2="
190 INPUT C1(K-1),C2(K-1),C1(K),
    C2(K) @ NEXT J
200 FOR I=0 TO 100
210 W=PI*I/100 @ Q(I)=0
220 FOR J=1 TO 2*N
230 X=(1+C1(J)*COS(W)+C2(J)*COS(
    2*W))^2+(C1(J)*SIN(W)+C2(J)*
    SIN(2*W))^2
240 IF X<1.E-20 THEN X=1.E-20
250 Q(I)=Q(I)+(-1)^J*10*LG(X)
260 NEXT J @ NEXT I @ RETURN

5 DISP "A1,A2,B1,B2 ?"
10 INPUT A1,A2,B1,B2 @ A=1
15 GOSUB 35
20 DISP "MAX GAIN G(W) =" ; G
25 DISP "MAX GAIN G1(W) =" ; G1
30 END
35 G=-1 @ G1=-1
40 FOR F=0 TO .5 STEP .01
45 W=2*PI*F @ W2=2*W
50 R2=COS(W2) @ I1=-1*SIN(W)
55 I2=-1*SIN(W2) @ R1=COS(W)
60 N0=A+R1*I1+R2*I2 @ N=A1*I1
65 N1=N+A2*I2 @ D=1+B1*R1+B2*R2
70 D0=D @ D1=B1*I1+B2*I2
75 I=NUM(N0+J N1)
80 I=DEN(D0+J D1)-CVT TO EUL
85 N=N0*N0+N1*N1 @ N=SQR(N)
90 D=D0*D0+D1*D1 @ D=SQR(D)
95 H0=N/D @ H1=1/D
100 IF H0>G THEN G=H0
105 IF H1>G1 THEN G1=H1
110 NEXT F
115 RETURN

```

Program left compares responses of recursive filter with ideal and with limited wordlength coefficients. That above calculates maximum values of $G(\omega)$ and $G_1(\omega)$ for a biquadratic section.

put is also connected to one input of a signal comparator, the other input being derived from a sample and hold network driven by one of four multiplexed analogue input channels. This arrangement allows up to four analogue inputs to be sampled and converted to digital form using the converter and the comparator under software control.

The microprocessor section of the device contains an eeprom with space for 192 processor instructions, 40 words of ram and a specialist arithmetic unit. The basic wordlength of the arithmetic unit and the ram is 25 bits. All arithmetic operations provided, which include add and subtract but not multiply or divide, are performed in two's complement form. A special feature of the device which allows coefficient multiplications to be performed efficiently without a multiplication instruction is the binary shifter (sometimes known as a bar-

rel shifter). Before being loaded into the arithmetic unit, one of the operands in an add or subtract operation passes through the binary shifter, which can be programmed to shift the number up to two places to the right or up to thirteen places to the left in one operation. Hence, a 'shift and add' process which can be used for programmed multiplication is combined into one instruction. Other features which simplify the programming of the device include a fixed instruction execution time (600 or 800 ns depending on device) and the absence of conditional jumps which are replaced by conditional operations. The latter ensures that there is only one path through the program and hence that the program execution time is constant. An 'end of program' instruction is included, which causes program execution to transfer to the first instruction in memory, providing continuous repetition of the

program. As the input signal is normally sampled on each pass through the program, the sampling interval is equal to the product of the number of instructions and the instruction execution time. For example, a program containing 40 instructions run on a 600 ns device produces a sampling interval of 24µs i.e. a sampling rate of approximately 41666 samples per second giving a signal bandwidth of almost 21 kHz. This represents the theoretical upper limit and it is prudent in a practical system to allow some measure of oversampling and limit the signal bandwidth to say one third of the sampling frequency.

A technique based on the canonical signal digit code used for coefficient multiplications on the 2920 together with details of digital filters implemented using this device will be given in a subsequent article. □

References

1. Digital filter implementation on 16-bit microcomputers by H. T. Nagle & V. P. Nelson, *IEEE Micro*, February 1981, pp. 23-41.
2. Microprogrammable digital filter implementation using bipolar microprocessors, by M. E. Woodward *Microelectronics (GB)* vol. 10, September-October 1979, pp.23-31.
3. NEC µPD7720 data sheet, NEC Microcomputers, Inc., 1981.
4. Digital filtering using a custom designed device, by R. H. Macmillan & P. Millar, IEE Colloquium on Implementation of Digital Signal Processing Algorithms using Microprocessors, London November 1981.
5. Microcomputer with 32-bit arithmetic does

high-precision number crunching, by K. McDonough *et al*, *Electronics*, 24 February 1982, pp. 105-10. *Bell System Technical Journal*, September 1981, vol. 60, part 2 (various papers).
6. 2920 Design Handbook, Intel Corporation 1980.

References in June article

1. Oppenheim A. V. and Schaffer, R. W. Digital Signal Processing, Prentice Hall, 1975.
- Terrell, T. J. Introduction to Digital Filters, Macmillan 1980.
- Peled, A. and Liu, B. Digital Signal Processing Theory, Design and Implementation, Wiley, 1976.

2. Rader C. M. and Gold, B. Digital filter design techniques in the frequency domain, *Proc. IEEE*, vol. 55 1967, pp. 149-71.
3. Ackroyd, M. H. Digital Filters, Butterworth, 1973.
4. Constantinides, A. G. Spectral transformations for digital filters, *Proc. IEE*, vol. 117, 1970, pp. 1585-90.

Appendix to June article

To calculate \sqrt{x} where $x=a+jb$.
Convert x to Euler form $x=re^{j\theta}$, where
 $r=\sqrt{a^2+b^2}$, $\theta=\arctan b/a$.
Take square root $\sqrt{x}=\sqrt{r} e^{j\theta/2}$.
Convert \sqrt{x} to Cartesian form
 $\sqrt{x}=\sqrt{r}(\cos \theta/2+j \sin \theta/2)$.

EVENTS

- August 5-6**
Computational physics on the distributed array processor. Institute of Physics Conference at the University of Glasgow. Details from the Institute of Physics, 47 Belgrave Square, London SW1X 8QX.
- August 14-17**
Harrogate International Festival of Sound and Video at the Harrogate Exhibition Centre and at various hotels close by.
- August 21-27**
15th International Congress on high speed photography and photonics. San Diego, California, USA. Organised by the International Society for Optical Engineering, Washington 98227, USA.
- August 26-September 5**
Firato 82. Biennial exhibition and trade show for consumer electronics. At the RAI Exhibition Centre, Amsterdam.
- September 2-6**
SIM HI FIVES: International exposition of music and high fidelity has been extended this year to include a video and consumer electronics section. Milan Fair Centre, Italy.
- September 6-7**
Seventh annual microprocessor workshop at the University of Liverpool Computer Laboratory.
- September 6-10**
Annual Meeting of the British Association for the Advancement of Science. To be held at the University of Liverpool. BAAS, 23 Savile Row, London W1X 1AB.

- September 6-9**
Enrolment for course for the Radio Amateurs examination. Brixton College for Further Education, Brixton Hill, London SW2.
- September 6-10**
Microcoll 82: Seventh Colloquium on microwave communication. Budapest. Sponsored by the International Union of Radio Sciences and the Hungarian Academy of Sciences. Details from Microcoll, 1252 Budapest, 114, PO Box 15, Hungary.
- September 7-10**
6th International conference on computer communication. London. Details from ICC 82, PO Box 23, Northwood Hills, Middlesex HA6 1TT.
- September 7-8**
Semiconductor 82: Exhibition at the Bingley Hall, Birmingham.
- September 7-9**
Compec Scotland: Exhibition of computers, systems, peripherals and software. Sponsored by *Computer Weekly*. City Hall, Glasgow.
- September 9-10**
Microprocessors and their applications. Symposium at Bristol Polytechnic, Ashley Down Road, Bristol BS7 9BU.
- September 9-12**
The 5th Personal Computer World Show. Barbican Centre, London.
- September 8-10**
Eurographics '82: International congress for computer graphics. UMIST. Conference details from Andrew Yates, University of Manchester

- Institute of Science and Technology, PO Box 88 Manchester M60 1RD.
- September 13-16**
12th European solid state device research conference, Munich. Details from Dr Zerbst, Siemens AG, Otto Hahn Ring 6, D-8000 Munchen 83, FRG.
- September 13-17**
12th European microwave conference, Finlandia Hall, Helsinki, Details from Microwave Exhibitions, 43 Dudley Road, Tunbridge Wells, Kent TN1 1LE.
- September 14-16**
ElectroWest; West of England electronics exhibition, Bristol. Exhibitions for Industry Ltd, 157 Station Road East, Oxted, Surrey RH8 0QF.
- September 18**
Computer Fair; Prestatyn High School PTA, Prestatyn, Clwyd.
- September 18-21**
International broadcasting convention: IBC82, Metropole Hotel, Brighton. Details from the IEE, Savoy Place, London WC2R 0BL.
- September 19-24**
Human aspects of computer systems: A short course at the Department of Human Sciences, University of Technology, Loughborough.
- September 19-24**
Industrial digital and microprocessor-based control systems. IEE vacation school at Baliol College, Oxford.



No hangover!


Hangover, a rather loose term to describe the stored energy resonance in a loudspeaker, the principal cause of colouration that immediately tells you you're listening to a loudspeaker.

Take it away and there's a new world – the loudspeakers have nothing more to say – instead there's just the orchestra and the magic of the music.



Perhaps even something to celebrate about.

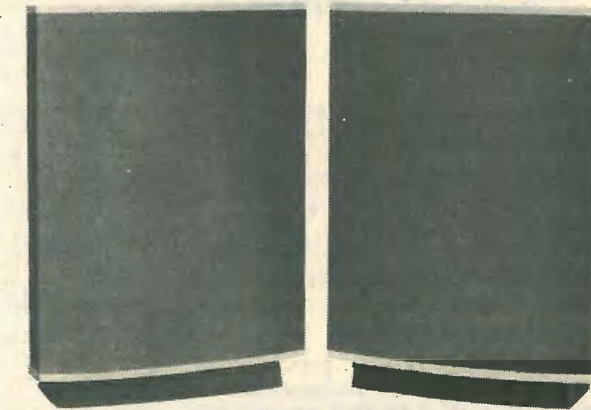For further details and the name and address of your nearest Quad ESL-63 retailer write or telephone The Acoustical Manufacturing Co. Ltd., Huntingdon, Cambs., PE18 7DB. Telephone: (0480) 52561.



QUAD
for the closest approach to the original sound

EP4000 EPROM EMULATOR PROGRAMMER



The microprocessor controlled EP4000 will emulate and program all the popular EPROMs including the 2704, 2708, 2716(3), 2508, 2758, 2516, 2716, 2532 and 2732 devices. Personality cards and hardware changes are not required as the machine configures itself for the different devices. Other devices such as bipolar PROMs and 2764 and 2564 EPROMs are programmed with external modules.

The editing and emulation facilities, video output and serial/parallel input/output provided as standard make the EP4000 very flexible to allow its use in three main modes:

- As a stand alone unit for editing and duplicating EPROMs.

Items pictured are: ● EP4000 Emulator Programmer - £545 + £12 delivery; ● BSC buffered simulator cable - £39; ● MESA 4 multi EPROM simulator cable - £98; ● 2732A Programming adaptor - £39; ● 2764 Programming adaptor - £64; ● 2564 Programming adaptor - £64; ●

- As a slave programmer used in conjunction with a software development system or microcomputer.
- As a real time EPROM emulator for program debugging and development (standard access time of the emulator is 300ns).

Data can be loaded into the 4k x 8 static RAM from a pre-programmed EPROM, the keypad, the serial or parallel ports and an audio cassette. Keypad editing allows for data entry, shift, move, delete, store, match and scroll, and a 1k x 8 RAM allows temporary block storage. A video output for memory map display, as well as the built-in 8 digit hex display allows full use of the editing facilities to be made.

BP4 (TEXAS) Bipolar PROM Programming module - £190
 Also available (not shown): ● VM10 Video monitor - £99; ● UV141 EPROM Eraser with timer - £78; ● GP100A 80 column Printer - £225; ● PI100 interface for EP4000 to GP100A - £65.
 VAT should be added to all prices

DISTRIBUTORS REQUIRED ● **EXPORT ENQUIRIES WELCOME**

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
 Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

WW - 023 FOR FURTHER DETAILS

MICROCOMPUTER LINE PRINTER

This is the second of two articles describing an interface for driving a 40-column dot-matrix printer mechanism from Z80 signals. With the mechanism, addressing and interrupt sections covered, the author explains the controller i.c., power circuits, running the printer and modifications required to drive a 12V mechanism.

by P. L. Woods

Turning now to Fig. 3, the rest of the controller circuit can be considered. IC₂ is a bidirectional buffer designed to isolate the controller-board internal data bus from any noise on the system data bus, and vice versa. It is enabled only when the controller board is addressed, and the direction in which it passes data is determined by the \overline{WR} line buffered by IC_{1a} and IC_{3a}. To reduce noise problems, IC_{1a} is a Schmitt trigger, and similar buffers are used on the other control bus lines.

The control bus is connected to the printer controller chip, IC₁₄, and through three-state buffers, IC₁₃, to the status outputs of the controller i.c. It is also connected to IC₉, the interrupt reply byte circuit. Note that D0 from IC₉, pin 18, should go to D0 on IC₂, pin 2, and so on up to D7, pin 9 on IC₂ to pin 9 on IC₂.

A 6.0MHz clock for the controller i.c. is provided by an HC18/U or HC25/U crystal, XL₁. IC₁₄ contains the character generator for the printer, and the output

for the currently selected character appears on PS1 to PS7 (pins 27 to 33 respectively). High-voltage open-collector line drivers, IC₁₆ and IC₁₇, are used to send the signal to the solenoid drivers.

Two additional signals have to be sent to the printer; one is a paper advance signal, FS (at pin 21 of IC₁₄), the other is to turn the drive motor on and off, MT (pin 34).

Three status signals are needed back from the printer for correct operation. The first of these comes from a timing coil which allows the controller to correctly space the dots for each character. If no


timing pulses are found within 0.2s after the motor is turned on, the circuit assumes that the motor has stalled, so an error status is set (Error at pin 22), and the motor stopped to prevent it from burning out.

The second signal is from a reed relay which indicates when the printer carriage has reached the 'home' position, and that the motor may be stopped as it has finished printing a line.

The third status line is from a normally-closed pushbutton, connected to ground, which serves two functions. If the switch is depressed (open) when the Reset line goes high then the controller enters a test mode and prints lines of characters until the switch is closed. Otherwise, pressing the switch when the printer is idle advances the paper through the mechanism.

Solenoid and motor drivers
 Figure 4 shows a solenoid drive circuit. Seven of these circuits are required for the

Fig. 3. Controller i.c. and buffers. Mr Woods informs us that the controller, IC₁₄, is not the DPC-2 as given here and in last month's parts list, but is the DPC-4.

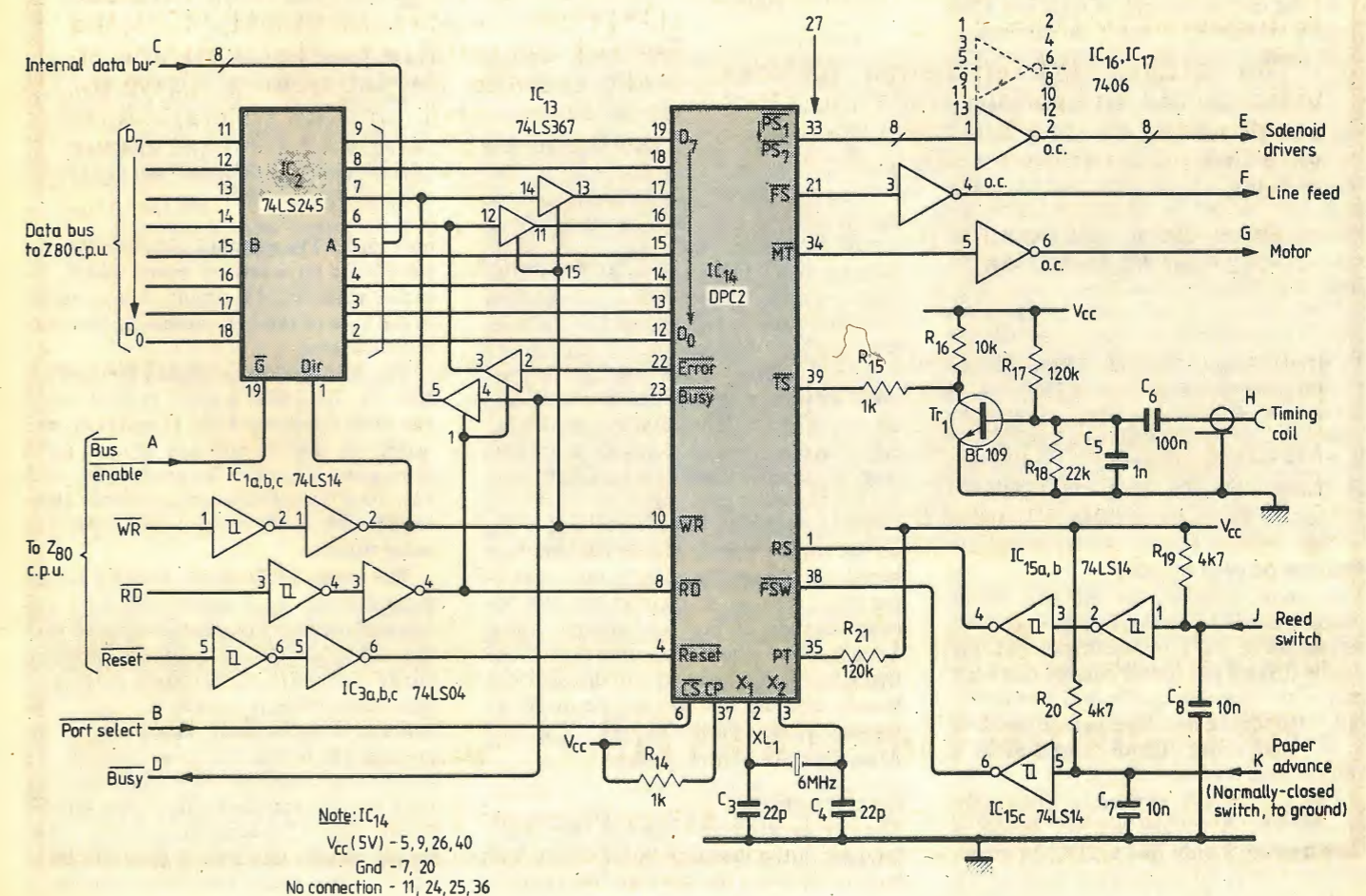

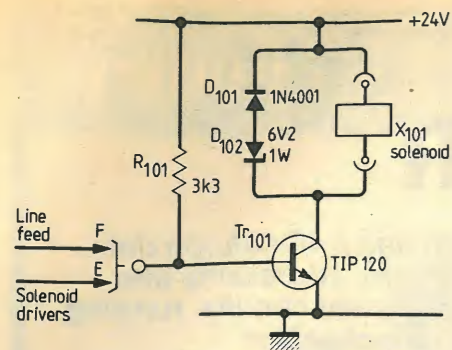


Fig. 4. Eight of these solenoid driver circuits are required, one for each of the seven needle drives and one for the line-feed solenoid. Tr₁₀₁ is a power Darlington transistor.

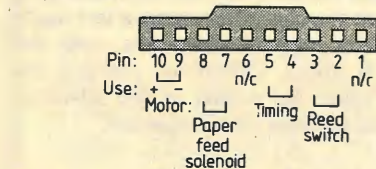
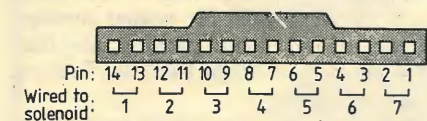


Fig. 7. Edge connector diagrams for the printer mechanism.

head solenoids and one for the line-feed solenoid.

As the circuit consists of only one Darlington transistor, it needs no discussion. One point worth mentioning though is that, should the circuit's input become open, as happens when the cable between the interface and printer board is disconnected, the solenoid is turned on. The effects of this will be explained later. No heat sink should be needed because, although the peak current is high (3.2A), the duty cycle is low. Diodes D₁₀₁ and D₁₀₂ are used to protect the transistor.

The driver for the motor is shown in Fig. 5, and is a little more complex because dynamic braking (through TR₂₀₄) is used to stop the motor at the end of each line. A Darlington transistor, Tr₂₀₃, is used to power the motor and will need a small heat sink. As with the solenoids, the motor will be turned on when the circuit's input is open.

Printer power supply

The circuit diagram for the two power supplies needed is shown in Fig. 6. Careful separation of the interface logic from the needle drivers has the advantage that each part of the circuit requires only one power rail. That for the interface logic (Figs 2 and 3) is 5V at about 300mA, supplied by a 7805 voltage regulator, IC₃₀₁.

The 24V supply requires a little more explanation. A voltage doubler circuit is used because I only had a 12V, 2A transformer; a 24V, 1A transformer used with a

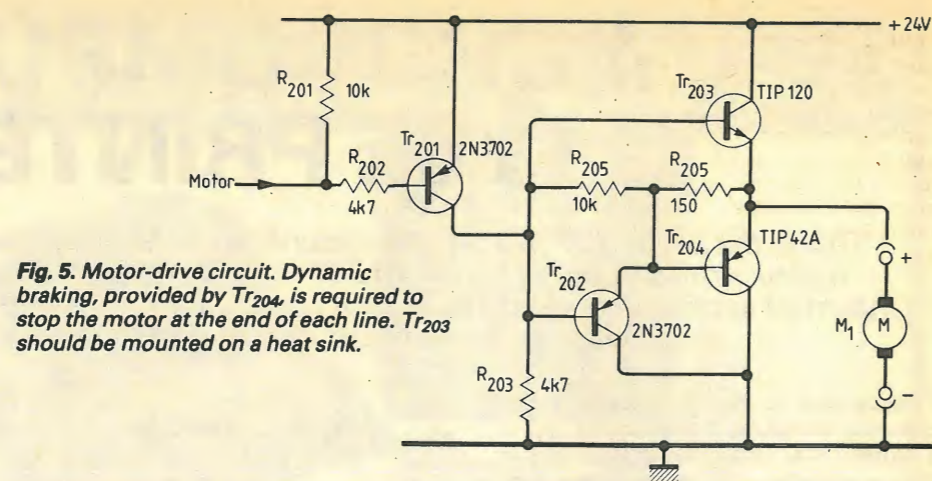


Fig. 5. Motor-drive circuit. Dynamic braking, provided by Tr₂₀₄, is required to stop the motor at the end of each line. Tr₂₀₃ should be mounted on a heat sink.

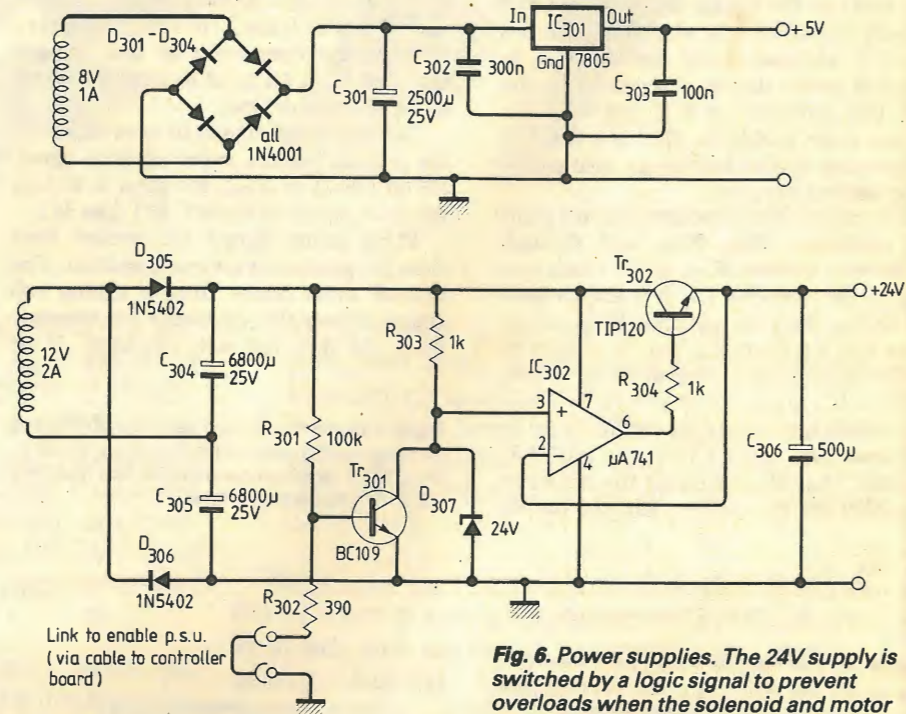


Fig. 6. Power supplies. The 24V supply is switched by a logic signal to prevent overloads when the solenoid and motor driving circuit inputs are open. The author had a 12V transformer in his 'junk box', hence the voltage doubler. Heat sinks are required for IC₃₀₁ and Tr₃₀₂.

bridge rectifier would perform equally well.

If the action of Tr₃₀₁ is ignored, then the circuit is an op-amp, IC₃₀₂, connected as a voltage regulator, with Tr₃₀₂ as the series pass element. The purpose of Tr₃₀₁ is to shut down the 24V rail should the control cable from the interface board to the solenoid drivers become disconnected. As mentioned above, in this event all the solenoid drivers, together with the motor driver, turn on. The resulting prolonged 30A current demand is sufficient to destroy the rectifier diodes, as happened during testing of the prototype.

So the link to enable the 24V rail is not on the supply board, but on the interface board, and two of the wires in the connecting cable are used to connect the link between the base of Tr₃₀₁ and ground. Using a multipole connector ensures that if the flying lead is not plugged into the interface board, then the link will not be made, so turning off the 24V supply. Both IC₃₀₁ and Tr₃₀₂ will require heat sinks.

Construction

The circuit was constructed in two parts: the first is the interface board which was built to fit into a slot in one of the compu-

ter's cards. The solenoid and motor drivers were built on a second board which, together with the 24V supply, was mounted in the base of the box containing the printer mechanism.

The interface board should be carefully laid out, i.e., with a good ground mesh, and with the ground pin of each i.c. connected to that of the i.c.s around it. A decoupling capacitor is needed for each i.c., 10µF tantalum-bead capacitors alternating with 10nF ceramic disc capacitors being suitable.

The layout of the driver board is a little more difficult as it carries both t.t.l. signals and the heavy currents associated with the solenoids. Because of the solenoid surge currents mentioned earlier, a substantial cable is needed to connect the emitter of each driver transistor to the ground side of the 24V power supply. To avoid noise caused by the solenoids getting back into the interface, the digital ground return should be separate from the 24V-supply return, although it need not be as heavy. Once again, everything should be

Table 1: Program to display printer character set. This program was written to demonstrate the operation of the printer, and act as a confidence test for it. It is loaded at location 4000 (hex.) in memory, and should be entered, after the stack pointer has been set up, using a CALL instruction. This listing was produced on the printer described in this article, as was its result, shown in Table 2.

```

1 ; LISTING ONE.
2 ;
3 ; DISPLAY PRINTER
4 ; CHARACTER SET.
5 ;
6 ; COPYRIGHT.
7 ; PL WOODS. 1982.
8 ;
9 MAIN: EQU 4000H
10 ORG MAIN
11 LOAD MAIN
12 ;
13 ; PRINTER PORT ADDR.
14 PRT: EQU 11H
15 ;
16 ; RESET PRINTER
17 4000 CD5E40 CALL RESET
18 ; VALUE OF FIRST
19 4003 3E20 LD A,32
20 ;
21 ;
22 ; PRINT 14 LINES, EAC
23 ; BEGINNING WITH THE
24 ; VALUE OF THE CHAR
25 ; IN HEX. EACH LINE
26 ; CONSISTS OF FOUR
27 ; GROUPS EACH OF FOUR
28 ; CHARACTERS.
29 4005 060E LD B,14
30 4007 CD3140 LINE: CALL PRTHX
31 400A CD6540 CALL SPACE
32 ; SET UP FOR GROUPS.
33 400D C5 PUSH BC
34 400E 0604 LD B,4
35 4010 CD6540 GROUP: CALL SPACE
36 ; SET UP FOR EACH

```

Table 2: The printer's character set. This listing shows the result of running the program in Table 1. The first four lines (values 20 to 5F inclusive) are an upper case ASCII character set, while the last six lines (from A0 to FF) are a Kata Kana (Japanese) character set. The middle four lines are not specified for the controller chip used and so represent 'noise'.

```

20 ! " # $ % & ' ( ) * + , - . /
30 0 1 2 3 4 5 6 7 8 9 : ; < = > ?
40 @ A B C D E F G H I J K L M N O
50 P Q R S T U V W X Y Z [ \ ] ^ _
60 ` a b c d e f g h i j k l m n o
70 p q r s t u v w x y z { | } ~
80
90
A0
B0
C0
D0
E0
F0

```

well decoupled for best performance, using 20µF, 36V electrolytic capacitors connected between the 24V side of each solenoid and ground. Connexions to the matrix printer itself are through a pair of non-reversible connectors, the mating halves of which are supplied with the printer. One of the connectors is 14 way and supplies the solenoids, while the other is 10 way and carries the motor, paper feed and timing signals (Fig. 7).

```

37 ; CHARACTER.
38 4013 C5 PUSH BC
39 4014 0604 LD B,4
40 4016 CD6540 CHAR: CALL SPACE
41 ; PRINT CHARACTER.
42 4019 CD4C40 CALL PUTPRT
43 ; NEXT CHARACTER.
44 401C 3C INC A
45 ; END OF GROUP?
46 401D 10F7 DJNZ CHAR
47 ; END OF LINE?
48 401F C1 POP BC
49 4020 10EE DJNZ GROUP
50 ; TERMINATE LINE.
51 4022 CD2940 CALL NEWLIN
52 ; ALL LINES DONE?
53 4025 C1 POP BC
54 4026 10DF DJNZ LINE
55 ;
56 ; ALL DONE.
57 4028 C9 RET
58 ;
59 ; START A NEW LINE.
60 4029 F5 NEWLIN: PUSH AF
61 402A 3E0A LD A,0AH
62 402C CD4C40 CALL PUTPRT
63 402F F1 POP AF
64 4030 C9 RET
65 ;
66 ; PRINT 'A' AS TWO
67 ; HEX DIGITS.
68 4031 F5 PRTHX: PUSH AF
69 ; HIGH DIGIT.
70 4032 0F RRCA
71 4033 0F RRCA
72 4034 0F RRCA
73 4035 0F RRCA
74 4036 CD3E40 CALL PRTHX
75 ; LOW DIGIT.
76 4039 F1 POP AF
77 403A CD3E40 CALL PRTHX
78 403D C9 RET
79 ;
80 ; PRINT LOW 4 BITS OF
81 ; 'A' AS A HEX DIGIT.
82 403E F5 PRTHX: PUSH AF
83 ; MASK BITS
84 403F E60F AND 0FH
85 4041 B7 OR A
86 ; CONVERT TO ASCII
87 4042 27 DAA
88 4043 C6F0 ADD A,0FH
89 4045 CE40 ADC A,04H
90 4047 CD4C40 CALL PUTPRT
91 404A F1 POP AF
92 404B C9 RET
93 ;
94 ; PRINT THE CONTENTS-
95 ; OF THE 'A' REG.
96 404C F5 PUTPRT: PUSH AF
97 ; LOOP UNTIL PRINTER
98 ; READY.
99 404D DB11 PRLP: IN A,(PRT)
100 ; CHECK ERROR STATUS.
101 404F CB67 BIT 4,A
102 4051 2808 JR Z,PRterr
103 ; BUSY BIT.
104 4053 CB57 BIT 2,A
105 4055 20F6 JR NZ,PRLP
106 ; SEND CHARACTER.
107 4057 F1 POP AF
108 4058 D311 OUT (PRT),A
109 405A C9 RET
110 ;
111 ; HERE IF THERE IS
112 ; A PRINTER ERROR.
113 405B 76 PRterr: HALT
114 405C 18FD JR PRterr
115 ;
116 ; RESET PRINTER
117 ; CONTROLLER.
118 405E F5 RESET: PUSH AF
119 405F 3E11 LD A,11H
120 4061 D311 OUT (PRT),A
121 4063 F1 POP AF
122 4064 C9 RET
123 ;
124 ; PRINT A SPACE.
125 4065 F5 SPACE: PUSH AF
126 4066 3E20 LD A,' '
127 4068 CD4C40 CALL PUTPRT
128 406B F1 POP AF
129 406C C9 RET
130 END

```

Conversions for a 12V printer mechanism

After this article had been completed, a version of the printer mechanism for use with a 12V supply, the DP-824F-12, and associated controller, the DPC-4A, were introduced; this section describes modifications required to accommodate these.

Pin connexions on the 12V mechanism are exactly the same as those on the 24V model. The DPC-4A i.c. can be used to control either version of mechanism by altering the signals on certain pins.

On the 12V mechanism, the solenoids require a 730µs pulse, as opposed to 400µs for those of the 24V version. This pulse length is determined by the controller and depends on the logic state at pin 35, the 'printer type' terminal (PT). When this pin

is tied to the +5V rail, as shown in Fig. 3, the pulse length is 400µs. For the 12V mechanism, R₂₂ must be changed to 1kΩ and wired to ground instead of +5V.

Current requirements for the 12V mechanism's solenoids and motor are higher because of the lower supply voltage, hence, R₁₀₁ of Fig. 4 should be reduced to 2.2kΩ in all eight solenoid-driver circuits, and R₂₀₂ of Fig. 5 reduced to 3.3kΩ.

Finally, the voltage doubler used in the 24V supply, Fig. 6, can be replaced by a bridge-type rectifier and single smoothing capacitor (say, 10 000µF, 25V). The zener diode, D₃₀₇, should be replaced by a 12V type.


Both the 24V and 12V mechanisms mentioned are friction-feed types but sprocket-feed versions, available from the same manufacturer, may be used.

Demonstration program

Table 1 is a program, written in Z80 assembly language, which is designed to test the printer by causing it to display its complete character set. The results of this program are shown in Table 2. The program is loaded into memory at 4000 (hex.), a convenient location in my system, and is entered from a system monitor which first sets up the stack pointer (SP register), and then pushes a return address onto the stack (e.g. by the use of a CALL 4000 instruction). The test program ex-

Table 1 is a program, written in Z80 assembly language, which is designed to test the printer by causing it to display its complete character set. The results of this program are shown in Table 2. The program is loaded into memory at 4000 (hex.), a convenient location in my system, and is entered from a system monitor which first sets up the stack pointer (SP register), and then pushes a return address onto the stack (e.g. by the use of a CALL 4000 instruction). The test program ex-

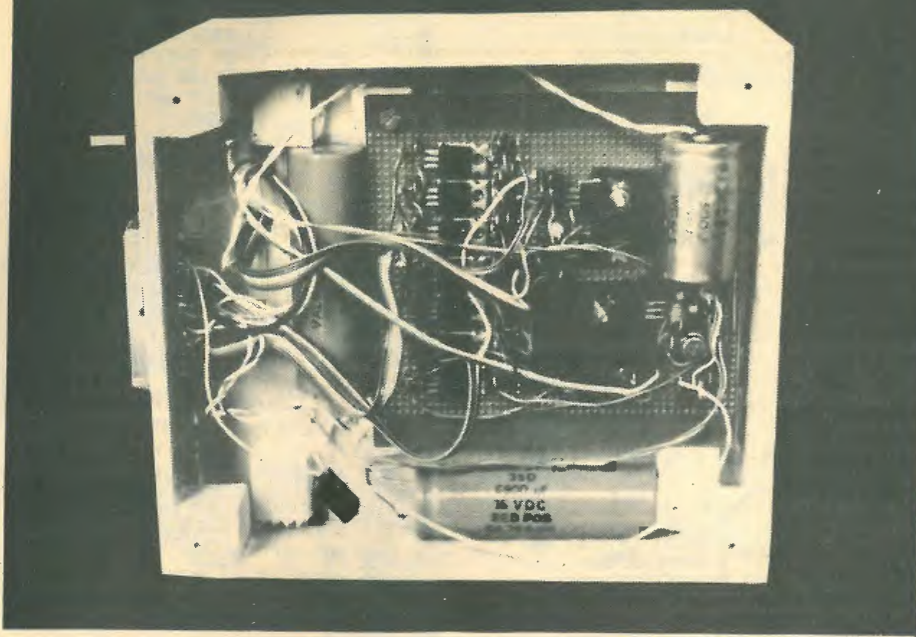Solenoid driver board. Mounted in the base of the printer box is a driver for each of the matrix needles, the paper advance relay and motor. There is also a 24V power supply.



cuts a RET instruction when finished.

This article is not the place to introduce assembly language programming, and so instead of a detailed description of the program, notes are given to assist those wishing to use all, or part, of the program for their own purposes.

The port address of the printer is declared in an EQU pseudo instruction at line 14. This address must correspond with the address used by the hardware.

There are three interface driver routines of interest, namely RESET, PUTPR and NEWLIN. Starting at line 118 is a subroutine called RESET. The purpose of this is to 'set' the printer controller should a previous program error have left it in an unacceptable state. The same effect may be achieved by using the RESET bus signal. As good practice, a CALL to RESET should be made at the start of each program which accesses the printer. No

registers are modified by this subroutine.

The second subroutine of note, PUTPR at line 96, may be regarded as causing the character sent to it from the 'A' register to be printed. PUTPR waits until the printer is ready, then transfers a character from the 'A' register to a print buffer in the printer controller i.c. If the printer error bit is set, the subroutine will halt at address 405B. Normally this point would contain a code to alert the operator to a printer problem. If there is no error the subroutine returns, leaving all registers unmodified.

The third and final subroutine to inspect is NEWLIN, at line 60. The purpose of this is to cause printing of the line in the controller print buffer, which it does by sending an OA character (line feed) to the printer. Once again, this routine does not change any registers. It should be noted that this subroutine must be called at least once every 40 characters to avoid the print buffer becoming full, in which case, overflow characters will be lost.

Conclusion

In this article it has been shown that it is possible to build a low-cost printer for a home-computer system. Although this design was originally intended as a means of printing programs from a Z80-based system, it may easily be adapted to make it compatible with any popular microprocessor and for use in any application where a permanent printed record is required, such as data logging. That the controller only allows upper-case graphics characters to be printed is not a problem for the majority of applications. □

BOOKS

Computing

From Hardware to Software

by Graham Lee
454 pages, paperback/hardback
MacMillan, £8.95/£16.00

This is an introductory text, albeit an extremely thorough one, and covers both equipment and programming at a level suitable for A level or first-year university courses. The author has used a computer model - the Simple Digital Computer - throughout, with which to illustrate his points more generally than would have been possible with a commercial design.

Advanced 6502 Interfacing

by J. M. Holland
190 pages, paperback
Prentice-Hall, £9.05

This book is practical in its approach to the subject of persuading 6502 microprocessors to perform useful functions in timing, control, data acquisition and high-current load driving. It is written for those who are already familiar with microprocessors.

Introduction to 6800/6802 Microprocessor Systems

by R. J. Simpson and T. J. Terrell
238 pages, paperback
Newnes £6.95

For readers who may not be versed in the language of logic and binary arithmetic, the authors have included a useful first chapter on basics before embarking on a description of the 6800/6802 devices and their use. This is followed by chapters on programming and on input/output signals, the practical approach being the province of the final two chapters on the MEK6802D5 evaluation system, with some investigations to carry out with its help.

Microcomputer Data Communications Systems

by F. J. Derfler, Jr.
129 pages, paperback
Prentice-Hall, £9.70

Microcomputers can serve as terminals in a data communication network to provide information at home, as an alternative to what the author calls the 'time tyranny' of radio, television and newspapers. The book describes such systems, including sections on modems and terminals, and going on to show how Apples, TRS-80s and others can be employed in this way. There is also a piece on using the CP/M disc operating system with S-100 bus computers and others.

Video

Video-Tape Recording

by J. F. Robinson, revised by S. Howe
362 pages, hardback
Butterworth, £12.00

The third edition of a well known text, this covers the whole field of professional and domestic video tape recorders from the engineering point of view. New information is presented on the helical B and C formats, and the domestic type of machine, with additional coverage of timebase correction. Those familiar with television engineering are led easily into the subject by the way of a first chapter on tape recording in general terms.

Video Techniques

by G. White
299 pages, hardback
Butterworth, £10.95

Although the blurb says that this is for the engineer or technician in television or ancillary industries, it hardly seems detailed enough for that purpose. It is a descriptive book, which is well suited to readers in other fields who want to obtain a working knowledge of television, both broadcast and recorded, studio equipment, transmission, reception (including teletext and viewdata) and digital techniques.

LETTERS

BRITISH HI-FI

I'm informed by John Crabbe of *Hi-Fi News/Record Review* that the Acoustical manufacturing company's claim that the QUAD FM4 brings 'Home the world's best broadcasting system at the touch of a button' is ethically justified, as Acoustical, in contributing to the support of the Philharmonica, helps to pay the piper.

Most other British high fidelity manufacturers do not, and subsist upon music making of all kinds parasitically, and thus have no prestige or reputation internationally amongst serious consumers of reproduced music.

By and large, British high-fidelity products are not materially competitive or competitive in terms of dazzling or convenient features. But they are perhaps more competitive qualitatively. Unhappily, however, recognition of their qualities is pretty well reserved to engineers, technicians, and 'hi-fi fans'. Most serious consumers of reproduced music, here and abroad, don't know about them, and have precious little opportunity to learn.

Thus, while the programming and technical quality of the world's best broadcasting system is revered - and envied - internationally, British high-fidelity products are known about and coveted only by the membership of tiny audiophilic cults, here and abroad.

I have at hand No 1 of the 1982 Edinburgh Festival newsletter. It's publication was apparently entirely supported by the advertisements of hoteliers, restaurant-keepers, one or two insurance companies, and a bank or two. Many people who will attend Festival events, or wish to, and many who - due to privation or remoteness - are dependent upon broadcast reception and recordings for musical enjoyment during most of the year, will remain in ignorance of the products of Linn, Syrinx, Strathclyde Transcription Devices, the makers of the Systemdek, and even Tannoy - not to mention KEF, B&W, Sugden, Castle, Celef, Mitchell, Acoustical, Naim, Riga, C&J Walker, MB Creek, Boothroyd, Stuart-Meridian, and even Wharfedale, south of the border.

It would be too charitable to say that the British high-fidelity industry has its head in the sand. A harsher but more appropriate judgement would suggest that it is contemplating its own navel from the inside, is unwholesomely involved and beguiled subjectively by its own entrails.

John F. Withey
Pollockshields
Glasgow

SCIENTIFIC COMPUTER

Please could you note in your records that I am the new Editor of The Sci. Comp. 80 monthly newsletter for users of the scientific computer designed by John Adams, M.Sc., details of which were published in your magazine.

Any of your readers who built the SC80, who are not members of the group, would find it well worth joining. Back issues, still available, contain a plethora of hardware, software and firmware. Mr Adams contributes articles monthly, and has developed no less than five versions of the BURP high level language, an excellent 64K d.o.s. (CP/M compatible), a standard Basic interpreter and some excellent hardware improvements. These include a 32K

dynamic memory expansion, 64K mapping circuits, interrupt vector circuits, ASCII character generator modification and a floppy disc controller p.c.b. Details of all these are in the newsletter. One year's subscription is £6.50 for U.K. members, £8 for the continent, and £8.50 for elsewhere. Cheques sent to the address below.

I would like to take this opportunity to thank Mr Philip Probetts for the past two years of excellent newsletters under his editorship. I hope I can do as well.

John Hodson
189 Trent Valley Road
Oakhill
Stoke-on-Trent, ST4 5LE

AMATEURS AND CB

C. G. Howard's comments in the June issue of *WW* under 'Amateurs and c.b.' highlighted the indifference of the Home Office towards illegal c.b. amateur operations. But what about the specific identifiable violations where the Home Office attitude is downright irresponsible?

I am referring to the illegal pirate radio stations that flagrantly operate in the v.h.f./f.m. broadcast band. There are a number of them, but two examples serve to illustrate the general case - 'Thameside Radio' and 'Liberation Radio'.

I asked British Telecom why these stations were not closed down and imagine my surprise, as a legal broadcasting operator, when I was told that the Home Office would not give the necessary authorization for British Telecom to do so. Must a campaign be mounted privately to ensure that the law of the land is upheld when a government department refuses to do so? Continual violation of the law in this way is a form of anarchy, in principal every bit as bad as other, more subversive, movements.

The Home Office, in supporting the violation of statutory laws by its non-action is encouraging further escalation. This is yet another of a growing number of examples of where government legislation controls the actions of responsible citizens but not those who chose to flout the law of the land.

H. Clayton
Northwood
Middlesex

CARTRIDGE ALIGNMENT

Referring to P. E. Cryer's letter in the June 82 issue, I found some difficulty in understanding the layout instructions in his second paragraph together with the associated diagram on the next page. However, it is of course quite true, as he says, that it makes no difference to the geometry whether you think of the stylus traversing over the record, or the record traversing under the stylus; all that matters is the relative moment of the two.

Two or three points seems to warrant comment: firstly, there is nothing particularly new or useful in finding out that the proportion of tracking angle errors depends on the choice of setting radii - of course it does. It is necessary, in the interests of minimizing tracking error distortion, for the angular error to vary inversely with radius, and as Cryer's figures indicate, this is exactly what does happen. The relationship of tracking angle errors at both outer and inner radii to the error at the radius for minimum

angle (my R_{min}) depends on the amount of dip in the curve of angle across the record, as is obvious from my Fig. 1.

Secondly, I cannot understand Cryer's statement that my own factors "would place B on the other side of the datum line". If the datum line is defined as a line through the two points where the stylus cuts the circles having radii p and q as in his diagram, then obviously the intersections at both inner and outer record grooves (his B and A) must necessarily lie on one side of the said datum line, and none of my 'factors' can alter this condition.

Thirdly, Cryer's roundabout method of calculating p and q as described in his last paragraph, cannot work. The expression $p/q/p=(p+q)-p$, is meaningless, a mere identity which reduces to $q=q$. Obviously it cannot be used to separate q from p when $(q+p)$ is known. The whole point of my final paragraph in the Oct '81 issue, was to show that one did not need to go through the whole procedure based on formula 4(b) every time, in the light of the linear $y=a+bx$ relationship ascertained at middle of paragraph. The final outcome, which cannot be simplified or improved, was to evaluate p and q (my r_0 and R_0), from the empirical expression $R_0=79+hC/84$ and $r_0=12+hC/71$ or ideally L^2-C^2/R_0 . For the recommended overhang value of $h=2600/C$, this reduced further to $R_0=110$ and $r_0=49$ (ideally 48.81, but the 0.19 discrepancy is insignificant in practice).

If one uses a protractor, or my setting gauge, as in the November 1981 article, there is no need to evaluate the offset angle O (my B), but if desired it can be very easily obtained, within about 0.1° accuracy, from my empirical expression 4380/C.

R. J. Gilson
Winchester
Hampshire

HERETIC'S GUIDE TO MODERN PHYSICS

I was delighted to see you are still providing a forum for open and constructive criticism of modern theory.

That Dr Murray should need to assure his colleagues that he has "no wish to cause you offence" is a sad comment on the state of physics. Doubtless his article is the result of a long and critical investigation of modern theory, and he would welcome any constructive criticism of his article. Equally doubtless, a few of his colleagues know his investigation is a deliberate attempt to revive the flat earth theory and Maxwell's wave theory of light - an insult to Newton's corpuscular theory of light.

I predict Dr Murray will soon learn to appreciate the truth of the supreme investigator, Michael Faraday's bitter response to the hostility to his theories of the self-satisfied mathematicians of his day - "A man who makes assertions, or draws conclusions, regarding any given case, ought to be competent to investigate it."

Many Nobel prizes were awarded for contributions to the basic premise of relativity - that nothing in the universe can travel faster than the speed of light. Cerenkov received the 1958 prize for his experimental proof that "when charged atomic particles pass through water or other media at a speed in excess of that of light itself, a bluish light is emitted."

Aspden, Dingle, Essen, MacCausland and other critics of relativity are dismissed as cranks and crackpots by the Establishment. Is there any member of the Establishment competent to investigate the strange case of why the crank Cerenkov received a Nobel prize?
M. G. Wellard
Kenley
Surrey

WALSH FUNCTIONS

I write with respect to the recent articles on Walsh Functions by Mr T. Roddam (WW Dec. 1981, pp 31 et seq. and WW Jan. 1982, pp 47 et seq.) to raise the following points.

The Rademacher functions, shown in Fig. 4 of this series correspond to Wal (1,0), Wal (3,0), Wal (7,0), Wal (15,0) . . . The associated intermediate Walsh functions may be derived by "exclusive Or" processing all combinations of the Walsh functions. Thus, for example referring to Fig. 3, the Wal (2,0) function is derived from Wal(3,0)⊕Wal(1,0) and should be inverted in the Figure. Several other derived Walsh functions have been inverted in Fig. 3. A correctly-signed set is enclosed for reference.

There is also an error in Fig. 5.

$$\text{Wal}(5,0) = \text{Wal}(2,0) \oplus \text{Wal}(7,0)$$

which does not hold for this diagram. I enclose a modified diagram which will satisfy this requirement. Incidentally, the paper by Barratt, Gordon and Brammer also contains these errors.

I mention these slips since many people seem to be becoming interested in these functions that valuable introductory articles, such as Mr Roddam's are worth these small corrections in the interests of accuracy.

R. T. Irish
Swindon,
Wilts.

Mr Irish enclosed an amended set of functions, which we have regretfully been obliged to omit for reasons of space. They can be obtained from this office - Ed.

FUNCTION OF FUNCTIONS

With reference to Mr Sutherland's letter (June), I think that the view of sidebands as mathematical fiction is not entirely unfounded. I believe that a periodic complex waveform and its Fourier series expansion are not one and the same thing in the sense of somehow being freely interchangeable without the active involvement of suitable physical devices to perform the complex series and conversion and vice versa. On this view a modulated radio transmission propagates in its complex form and there is no need to postulate any sidefrequencies at the transmitter end. The sidefrequencies are generated at the receiving end by tuned circuits. These have the capability to store energy and thus perform integration, thereby generating the continuous waves known as Fourier series components or sidefrequencies. The physical process by which a sidefrequency is generated can be understood by considering the following experiment:

Suppose that a high "Q" tuned circuit is adjusted for resonance at 110kHz and placed near a 100kHz oscillator. Clearly, the tuned circuit will not begin to oscillate since any such oscillations would move in and out of phase with the oscillator, thus receiving just as much help as hindrance. However, should the amplitude of the oscillator be decreased whenever out of phase with the tuned circuit and increased when in phase, then the tuned circuit would receive more help than hindrance and would build up oscillations. It would oscillate at 110kHz whilst receiving its energy in burst of 100kHz. Assuming a very high "Q", the inertia of the tuned circuit would be large enough to smooth out any amplitude variations and it would appear to receive a continuous wave input (i.e. one of the sidefrequencies). In fact it would be generating the continuous wave.

For the above process to take place the amplitude of the oscillator would have to be altered (i.e. modulated) at 10kHz which is, of course, the appropriate modulating frequency for the

110kHz sidefrequency.

It is interesting to note that it would not be essential to alter the amplitude of the oscillator in order to generate the 110kHz response. The same effect could be achieved by alternating the phase of the oscillator at 10kHz, which suggests how sidefrequencies are generated in the case of suppressed carrier, frequency and phase modulation systems.

So, although the sideband concept is a very useful, even essential part of radio theory, it is not necessary to assume that sidefrequencies have physical existence prior to the complex waveforms arriving at the receiving equipment. As explained by the *Wireless World* contributor Cathode Ray (September 1955, under the heading "Fourier - Fact or Fiction") continuous sinewaves are not the only possible form into which complex waveforms may be "decomposed", and hence it makes sense to assume that the sine form occurs simply because of the sine-wave nature of oscillations in tuned circuits at the receiving end of transmitter - receiver link.
G. Berzins
Frimley
Surrey

REMOTE CONTROL FOR HI-FI

I read Mr. Kirby's article on a remote control hi-fi system (WW, March 1982) with some interest, as I was at that time busy designing a similar system. I too used the Mullard voltage-controlled potentiometers for control of the audio signal path, but found a much simpler and cheaper remote control system.

The major drawback of Mr Kirby's system seem to be the fact that the Plessey receiver (ML 922) only has three analogue control outputs; hence the need to use a 'stepped' volume control. The Motorola remote control system (MC 14497 - transmitter and MC 6203 - receiver) has four analogue channels and a host of other useful features. For example, toggle action volume mute and a single button operation which sets three of the analogue channels to 50% and the fourth to 30%.

This system is the same as that used on Grundig remote control television and so the modifications for hi-fi applications are quite simple. I wondered whether Mr Kirby was aware of this possibility and if not, and he was interested, I could send him some details.

D. F. Lovely,
Bioengineering Unit,
University of Strathclyde.

The author replies:

It seems from Dr Lovely's comments that we are heading in opposite directions. I regard the use of the two analogue outputs on the Plessey ML 922 as a necessary evil! I would much rather have used all digital tone level setting controls. The reason I did not was my inability to design a stereo bass and treble control circuit using less than four of the Analog Devices AD7110 chips. These cost around £8 each and the extra expense compared to the use of the Mullard analogue tone control i.c. seemed unwarranted.

I chose the Plessey remote control chip set (after looking at several alternatives) because of the analogue and digital outputs available on the ML922, and their use of an infrared photodiode to logic level integrated preamp, which saves much trouble with discrete high gain amplifiers.

Also a whole family of receiver chips are available, including one with a 5 bit latched output for a microcomputer interface, all operated by the same transmitter.

There is a toggle output on the ML922; this is used to switch the loudspeaker headphones relay, a quite effective mute control. In practice the 3/8 full scale normalised level of the analogue outputs is not a disadvantage; I rarely alter the tone by more than 1/8 of the scale.

My choice of the AD7110 was for the relative simplicity of driving it from a single chip microcomputer (the Zilog Z80), which can be programmed in Basic, as well as machine code. Then the interface between the controlling computer, and the controlled preamp/tuner/record deck can be some simple buffers. All the decoding from the received codes to the sequences necessary to drive, say, a synthesising tuner could be handled in software. This would make it easily adaptable to the various units commercially available. The prom decoding and sequencing logic used in the published design are an interim solution.

D.C. INPUT OR R.F. OUTPUT?

In "Amateur radio" for June, 1982, Pat Hawker laments the replacement of "d.c. input power" regulations by new limitations on "dBW carrier power" in the revised Amateur Licence Schedule. While I tend to agree that the dBW is not particularly welcome, the change to an "r.f. output" criterion is long overdue.

"D.c. input" was firmly rooted in the days of valve transmitters and constant-carrier modes, when both h.t. voltage and anode current were metered, and the meter needles would stay still to be read! For most radio amateurs - like it or not - those days are gone. Either our transmitters tend to be solid-state and have only r.f.-output metering, or they are primarily designed for s.s.b. In both cases it makes more sense to measure r.f. output, and this can be done with acceptable accuracy for the Amateur Service. At low powers, the accuracy requirement is minimal (at least for regulatory purposes), and at higher powers either commercial power meters can be used, or extremely simple homemade equipment, such as an existing s.w.r. meter can be calibrated accurately by transfer.

Although a d.c.-input limit does encourage high-efficiency amplifiers, is that what we really need? In today's crowded bands, the most important characteristic of a signal is its quality, and an r.f.-output limit allows amateurs to operate their transmitters in a more linear, though less efficient, manner.

The demise of d.c.-input limits is a welcome advance, but other relics of the past remain in the new Schedule: for example, the 6dB difference between the power limits for c.w. (A1A/B) and for s.s.b. (J3E). Can anyone explain how a c.w. signal with a well-shaped keying waveform differs significantly in interference potential from an s.s.b. (J3E) signal of the same peak envelope power, and why the power limits for the two modes should not be the same? The 6dB penalty against c.w. is a legacy of the transition to s.s.b. from plate-and-screen modulation, and has no current relevance. In any further revisions of the Schedule it deserves a decent burial, alongside d.c. input limits.

Ian F. White, G3SEK
Abingdon
Oxfordshire

THE NEW ELECTRONICS

It is at least eight years since I shared the responsibility for selecting graduates for employment in an electronics development laboratory, and I read with interest and dismay Mr Jaques' article in the January issue.

I was interested in that some of Mr Jaques' questions were similar to the ones I put to interviewees, and dismayed because the responses he obtained mirrored so closely those that I obtained all too often. True, my own efforts were rewarded by the occasional interviewee who did *understand* some of the principles with which he had been presented and could perhaps even describe his final-year project clearly and accurately! Indeed a few such went on to become much respected colleagues.

However, it is not Mr Jaques' article which prompts the writing of this letter, but rather the contradictions and inconsistencies in the letters about this article which appeared in the March and April issues. In a letter of reasonable length I can only draw attention to a few of these.

There is much to agree with in Mr Graham's letter - I too would reach for my text books to deal with Tensor analysis etc., etc., etc., and must agree entirely with his reference to "learning by rote" - but what is the relevance to Mr Jaques' article?

Mr Jaques' questions are all of an elementary nature - for example, surely a qualified electronics engineer might reasonably be expected to derive the expression for the gain of the amplifier configuration in thirty seconds flat, even if didn't remember " $-R_2/R_1$ ". Does it really require a text book on op-amps to deal with this? (Why does it have to be an op-amp anyway?)

Perhaps Mr Graham would tell us - I really would love to know - which text book does he reach for when he wishes to remind himself about Ohm's Law?

Surely the point is that an elementary *understanding* of circuit theory and device fundamentals is all that is required to answer most of Mr Jaques' questions? That is, are they not nearly all designed to avoid testing the mere ability to recall tabulated data from the candidate's memory?

Even if a graduate cannot recall a precise expression governing the current/voltage relationship for a semiconductor device, is it not reasonable to expect him to understand that it is a function of temperature, for example?

On the subject of final year projects, my experience was that students got involved in much too complex systems without any hope of fully understanding them in the limited time available! Whilst I am sure that Exeter students have written many good final year reports, does Mr Graham really believe that the result of a few weeks project work is to produce an "expert specialist"?

Turning to Mr Wehner's letter, I will ignore the first part as being totally irrelevant, and in any case, highly suspect. However, he goes on to make my point for me very well. He takes Mr Jaques to task for not drawing his (Mr Wehner's), "standard" amplifier circuit. One might quibble with the precision of Mr Jaques' "the gain between X and Z" but there is no ambiguity. Mr Wehner wants to define the gain referred to some point not even present in the circuit - why? Even if "input impedance" is not given its normal meaning, the circuit shown does have an infinite "source" impedance - so

why the complication?

Whilst I do not see any ambiguity in Mr Jaques' Figure 2, surely a graduate might be reasonably expected to spot and question any such ambiguity?

It is my own belief that extraordinary progress in electronics has led to the very thing that Mr Graham objects to: learning and examination by rote. Inadequate emphasis is given to understanding and applying fundamentals. This may not matter for certain systems "designers". However, one would hope that some of the electronics engineers we are educating might actually be capable of designing the "guts" of those fascinating multilegged black boxes we all love so dearly. New processes, new devices, new circuits, all require an understanding of, and an ability to use, the fundamentals of which Mr Graham is so scornful - or have we already left it to the Americans and the Japanese?

Whilst writing this letter, I asked my son (who graduated with first class honours in Electronics Engineering and Physics about five years ago), to read and comment on your contributor's article and letters as I thought it appropriate to obtain a perhaps more modern view than my own. (Although I do not actually qualify for Mr Graham's unnecessary reference to "Grandpa".) My son's reaction was not inconsistent with my own, but I feel inclined to give him the "last word". He recalled a comment he made to his examiners - "I could have done better if I had spent more time simply memorizing information rather than trying to understand it all . . . the examination questions all too often merely required the regurgitation of chunks of lecture notes . . . a computer programmed to do the same in response to a few key words, could have got a degree."

C. W. Ward,
Yelverton,
Devon


THE DEATH OF ELECTRIC CURRENT

After Dermond O'Reilly's second blistering attack, May 1982, perhaps Ivor Catt should slink away with his tail between his legs.

When discussing a TEM wave, it is common practice to use the formula O'Reilly objects to, $E/H = \sqrt{\mu/\epsilon}$. See for instance Bell, *Wireless World*, August 1979, page 44, and also A. F. Kip, "Electricity and Magnetism", page 332, equation 12.34. Kip uses the popular convention, where vectors are written in bold type and the amplitudes of vectors are written in faint type. In *Wireless World*, July 1979, page 73, the diagram immediately above my equation (a) that O'Reilly objects to makes it clear that amplitudes are being discussed.

Para. 3. Where is it said by anyone but O'Reilly that a wave is called transverse EM because displacement current flows across it? On the contrary, a wave is described as TEM because E (not dD/dt) and M are transverse. dD/dt has nothing to do with it, and will not even exist in the case of a steady TEM signal. O'Reilly makes this very point earlier in the same paragraph, that the bulk of a steady TEM wave contains no displacement current.

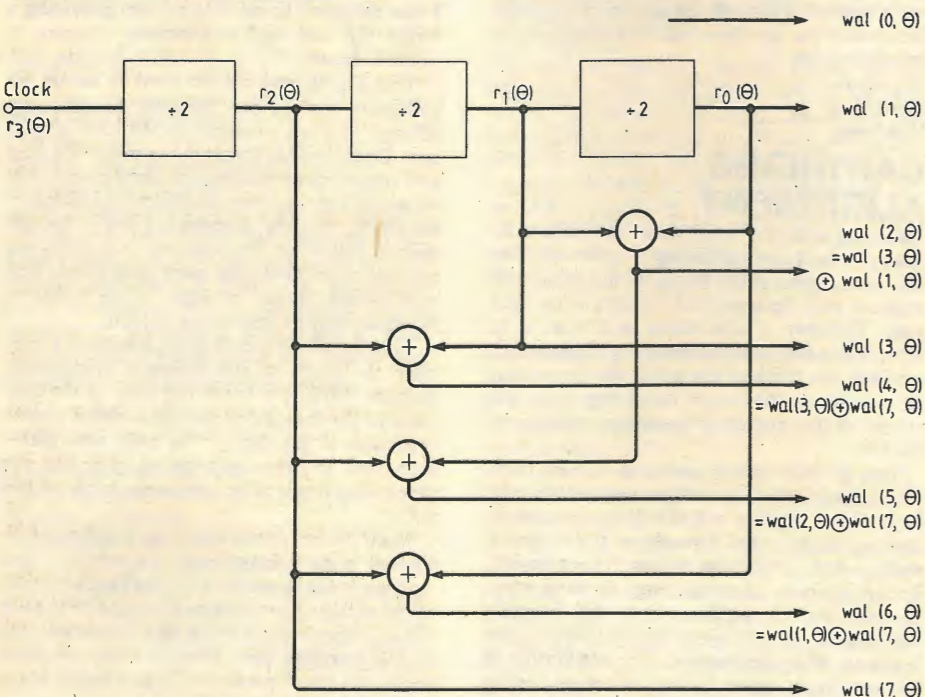Following your publication in the December 1980 issue of my article 'Death of electric current', you published a letter by R. T. Lamb and my reply to his letter, both in the March 1981 issue. The following quotations from my reply show that I found Lamb's letter muddled;



"I think Mr Lamb has reversed physicists and engineers."

"Lamb seems to call Theory N 'the current model' and Theory H 'e-m theory'."

Lamb himself wrote, among other things; "This is a broad generalization and, like all such, has exceptions, so please don't rush to quote them at me!"

You then published R. T. Lamb's reply to my reply in September 1981. Here the plot really thickens. For instance, I have no idea what "principal assertion" he refers to in his first sentence:

"I was pleased to note that Ivor Catt, in his reply to my letter (March issue), gave yet another example of the truth of its principal assertion."

Presumably he is promoting a particular philosophical position in the matter of theory, fact, hypothesis, truth and so on. If he is, then he should give us references to the originator of his philosophical view, or if it originates with himself, he should state it clearly.

Which model of Kepler's is he discussing in his second paragraph, September 1981, when he says:

"Kepler's problem was that the central construct of his model . . . ?"

There should have been more information, or reference to the literature where the particular activity of Kepler is discussed. Lamb may be talking about the ellipse, or the Harmony of the Spheres, or something else. Again, we see Lamb's ability to pitchfork confusion into a discussion.

In the December 1981 issue, you published my reply to Lamb's September letter. Then in April 1982 you published his reply. Again, Lamb confuses the issue. Even though in my latest reply, December 1981, I wrote, "If Lamb thinks (unlike me) that a mere model is in dispute, why the tenacity?", Lamb comes back with the reply, April 1982; ". . . [Ivor Catt] seems to acknowledge that we are discussing models of reality and not reality itself."

A dialogue, or debate, between two parties is of little value if the debaters ignore what the other man is saying.

Lamb's apparent assertion in paragraph three that it can be experimentally established that RC discharge current does not continue for ever I find astonishing. Also, in the last sentence of that paragraph, what does he mean by "an e.m. wave model"? Is that phrase yet another misnomer for a theory of mine? I don't know. I always name my theories clearly.

In his second paragraph, April 1982, it is unacceptable, because muddling, if he does not clearly specify which "other correspondents" have shown that the "insurmountable difficulties" introduced by ρ and J exist only in Mr Catt's mind." No one has retrieved classical electromagnetism from the death-blow dealt to it by the question in my letter of August 1981. It is of crucial importance to establish whether classical electromagnetism collapsed in August 1981, so I am sending a personal request to each of the following experts to submit an answer to *Wireless World*; Professors Mott, Dirac, Salaam, Brown, Lindsay, Bleaney, Gosling and Mr G. G. Scarrott.

The internal contradiction in classical electromagnetism is contained within this set of axioms;

1) A transverse electromagnetic wave (TEM) travels without change at the speed of light in a vacuum, guided by two perfect conductors.

2) Lines of electric flux terminate on electric


charge. (This is one of Maxwell's equations.)

3) Electric charge cannot be created or destroyed.

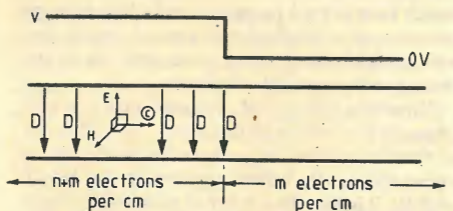4) Electric charge travels slowly in a conductor significantly slower than the velocity of light in a vacuum.

Now consider a TEM voltage step travelling to the right between two perfect conductors.

Behind the step, the D lines from the upper (more positive) conductor terminate in electrons, n per cm length of conductor, in (on) the lower conductor. These electrons are in addition to the electrons, m per cm, which neutralise the holes in the molecules of the lower conductor.



Ahead of the voltage step, m electrons per cm length of lower conductor are present, neutralising the holes. During the next $\frac{1}{30}$ nanosecond, the voltage step moves forward by 1 cm (approx.), so that n new electrons appear in this section of the lower conductor, to terminate the newly appearing tubes of D flux between the two conductors. Where do they come from? Not from the upper conductor, because by definition, displacement current is not the flow of electrons. Not from somewhere to the left, behind the voltage step, because such electrons would have to travel at the speed of light in a vacuum.

Ergo, classical electromagnetism, which for this purpose includes both Theory N and Theory H, is dead.

Ivor Catt
C.A.M. Consultants
St. Albans

AMATEURS AND BAND 1

My attention has just been brought to the fact that the BBC is intending to use band I frequencies, channels B1 and B2, for schools broadcasting. As a radio amateur with a keen interest in the 50MHz band I find this very unsettling. It leads me to believe that there really is something wrong with the way frequencies are allocated in the UK, since if the whole 88 to 108 MHz band were available for broadcast, the BBC could have far more suitable channels tunable on existing receivers with existing antennae.

I had very much hoped that radio amateurs in the UK would eventually get an allocation at 50MHz. We would not require a band MHz wide; 50 to 50.5MHz would be quite adequate. If, however, the BBC intends to use these frequencies, I would ask that they leave a "listening hole" from 50.0 to 50.2 at least, and 50.5MHz if possible, since these frequencies are of scientific value.

I and many others have spent a lot of time, money and effort in the study of this most interesting part of the spectrum, and propagation there is not confined to the sunspot maximum: only the other week I was able to hear the PYZAA beacon in Brazil for the first time.

Therefore it would be very sad indeed if all of

our efforts were to come to nothing and we were unable to even listen on 50MHz in future.

BBC please take note.

Mr G. M. Pheasant
Great Wyrley
Walsall

BLUMLEIN AND STEREO

I have followed with interest the correspondence in your columns relating to the invention of stereophonic disc recording.

It now seems that the earliest existing stereophonic discs are by Arthur Keller at Bell labs in America made using dual groove techniques in December 1932.

The earliest known orthogonal monogroove stereophonic discs were cut at EMI for A. D. Blumlein in 1933 and early 1934. This work was covered by his classic patent 394.325 which was applied for in December 1931.

On recording this document I was drawn to the conclusion that Blumlein probably had carried out research on stereophonic disc recording before its application was made. As a result I have made some effort to find whether work was done by Blumlein before the merger of the Columbia Gramophone Co and the Gramophone Co to form EMI in 1931. Unfortunately I found that his co-workers at Columbia are no longer with us and EMI were unable to confirm or deny the possibility of such earlier work. There are however to my knowledge seven references to such work and among these there are which I feel are important.

One by James Moir was based on a discussion between Moir and Blumlein during World War II and the other by Clark, Dutton, Vanderlyn who were co-workers of Blumlein. H. A. M. Clark worked with Blumlein at Columbia from 1929 and was therefore in a position to write with authority.

I have found it most frustrating that the work of probably Britain's finest electronic engineer is not proclaimed to the world at large and that his long promised biography has not yet appeared.

It does no credit to EMI that they have done so little to publicise the work of Blumlein whose efforts so enriched our knowledge in such fields as sound recording, television, radar, measurements, and electronic circuitry that we still make use of his ideas forty years after his tragic death.

References

1. H. A. M. Clark, G. F. Dutton, P. B. Vanderlyn. 'The Stereoscopic Recording and Reproducing System'. *IEE Proc.* Vol 104 pt. B 1957. Reprinted July/August 1957 IRE Transactions.
2. James Moir 'Hifi News & RR' Tape recorders & Stereo Pt 2 the Audio Fair 1957 p483.
3. Donald Aldous 'Hifi News & RR' Supplement 1977 '100 years Recorded Sound' Chronology p85.
4. H. Burrell-Hadden 'Practical Stereophony' 1946 p20.
5. H. W. Hellyer 'Stereo Sound' 1974 p10.
6. Gordon J. King 'The Practical Hifi Handbook, 1959 p20.
7. Percy Wilson. 'The Gramophone Handbook' 1957 p211.

R. Maude
Dalton
Huddersfield

METEOSAT HIGH-RESOLUTION IMAGES

Enhancements for receiving high-resolution pictures from Meteosat II on a home-built station. The original weather-satellite receiver, designed for Tiros-N high-resolution images, was described towards the end of last year.

by M. L. Christieson

This article describes additional equipment required to receive Meteosat primary data on the basic Tiros high-resolution receiving system outlined in a recent article.¹ Meteosat-2, which is in geosynchronous orbit at zero degrees longitude, transmits digital data in shared time with the analogue Wefax service.

The Wefax service transmits data by means of an amplitude modulated 2400Hz f.m. subcarrier, and the reception of this has been described before.² It is, however, important to understand how the Meteosat system as a whole operates, and how each service fits in. The spacecraft has a mirror radiometer similar to that used in the Tiros series, but because of its stationary position, the mechanics of the scan system are different. The spacecraft spins about its vertical axis at a rate of 100 rev/min. The radiometer looks out of the side of it and thus the spin provides the line scan. The frame scan is obtained by tilting the mirror from south to north over a period of about 25 minutes. There are five sensors; two are infra-red, two are visible-light sensitive, and one is sensitive in the water-vapour band. Their spectral bands are

visible (vis.)	0.4 to 1.1 μ m
infra-red (i.r.)	10.5 to 12.5 μ m
water vapour (w.v.)	5.7 to 7.1 μ m

Since the amount of data that may be transmitted in 25 minutes is limited, only one of each type of sensor, or one infrared and two visible-light sensors may be used at once. The basic image format is

infra-red	2500 lines \times 2500 pixels
water vapour	2500 lines \times 2500 pixels
visible	2500 lines \times 2500 pixels or 5000 lines \times 5000 pixels

This data, called the raw image, is sent in digital form to the Meteosat ground computer system at the European Space Operations Centre (ESOC) at Darmstadt in West Germany. Here it is stored and certain processing carried out, such as the registration of the two visible channels. The images are then sectored and retransmitted using Meteosat's S-band transponders as analogue Wefax data for secondary data-user stations (s.d.u.s.), and as full-resolution digital data to p.d.u.s.

There are two types of digital images sent from ESOC - 'A formats' which cover the full earth disc, and 'B formats' which cover the eastern Atlantic and Europe. Both A and B formats are sent at regular times throughout the day according to the current Meteosat dissemination

Feedback Instruments Ltd

schedule³ and contain, at various times, data from all the sensors. The transmissions are coded on the schedule by A or B followed by the sensor data that they contain; for example AI contains full-disc infra-red data and BIV contains the sectorized data from the infra-red and both visible sensors. BIVW contains infra-red and only one visible channel because the water-vapour image is also transmitted.

Transmission duration varies, depending on the amount of data being sent, from a few minutes to 29 minutes. The shortest format at present is BIW and the longest AV. In general terms BIV and AI are sent every half hour during daylight, with water vapour replacing visible during darkness. AV is sent four times a day. This schedule is however subject to changes. These transmissions can occupy up to six consecutive four-minute slots in the schedule and normally take place on only one of the transponder channels. The general characteristics of the p.d.u.s. transmissions are shown in Table 1.

Antenna and receiver design

The basic receiver described for a.v.h.r.r. is used with some modifications.¹ The frequency is very close to that of the h.r.p.t. from NOAA-6, and in the prototype station the down-converter and demodulator are common to both systems. Suitable crystals are used to retune the down-converter to either of the Meteosat frequencies. Both frequencies are available because an s.d.u.s. demodulator is used to receive Wefax formats in addition to the p.d.u.s. data. It is useful to have the We-

fax facility in order to receive ESOC administration notices.

A completely separate antenna and pre-amplifier are used and system selection is by means of a coaxial relay at the input to the down-converter. The preamplifier design is similar to that used on the h.r.p.t. system, except that the combiner section is not required since a single dish antenna is used. Due to the removal of combiner loss, the noise figure can be reduced to around 1dB. This corresponds to a noise temperature of 75K. The antenna noise temperature is the same as before, 70K, so the value of the system noise temperature, T_{sys} , is approximately $70 + 75 = 145K$. The recommended G/T for a p.d.u.s. is 11.5dB/K, so the antenna gain, G, should be $21.6 + 11.5 = 33dB$.

The gain of a parabolic dish is given by approximately

$$G = \frac{4\pi AE}{\lambda^2}$$

where A = aperture area, E = efficiency (usually about 0.5) and λ = wavelength.

Rearranging this, to obtain a gain of G (expressed as a real number), the required diameter is

$$\sqrt{\frac{G\lambda^2}{E\pi^2}}$$

or for this frequency, approximately $0.0766\sqrt{G}$ metres. For a gain of 33dB this gives a diameter of 3.4 metres.

This size of dish is recommended for commercial use, but a significantly smaller one may be used without a large increase in error rate. The prototype uses a 2.1 metre dish, which gives a gain of about 29dB, ($G/T = 29 - 21.6 = 7.4dB/K$).

The exact design of the prime feed for

Table 1. General characteristics of the p.d.u.s. transmissions.

Transmission frequency	— (ch.2) 1691.0MHz (analogue and digital) — (ch.1) 1694.5MHz (analogue only)
Polarization	— linear
Effective radiated power	— 18.2dBW
Modulation type	— digital split-phase-L
Modulation index	— 1.2 radians
Bit rate	— 166.66kbit/s
Bandwidth	— 1MHz
Bits/word	— 8
Words/frame	— 364
Frames/subframes	— 8 (A formats), 4 (B formats)
Frame sync.	— first three words
Recommended G/T	— 11.5dB/K

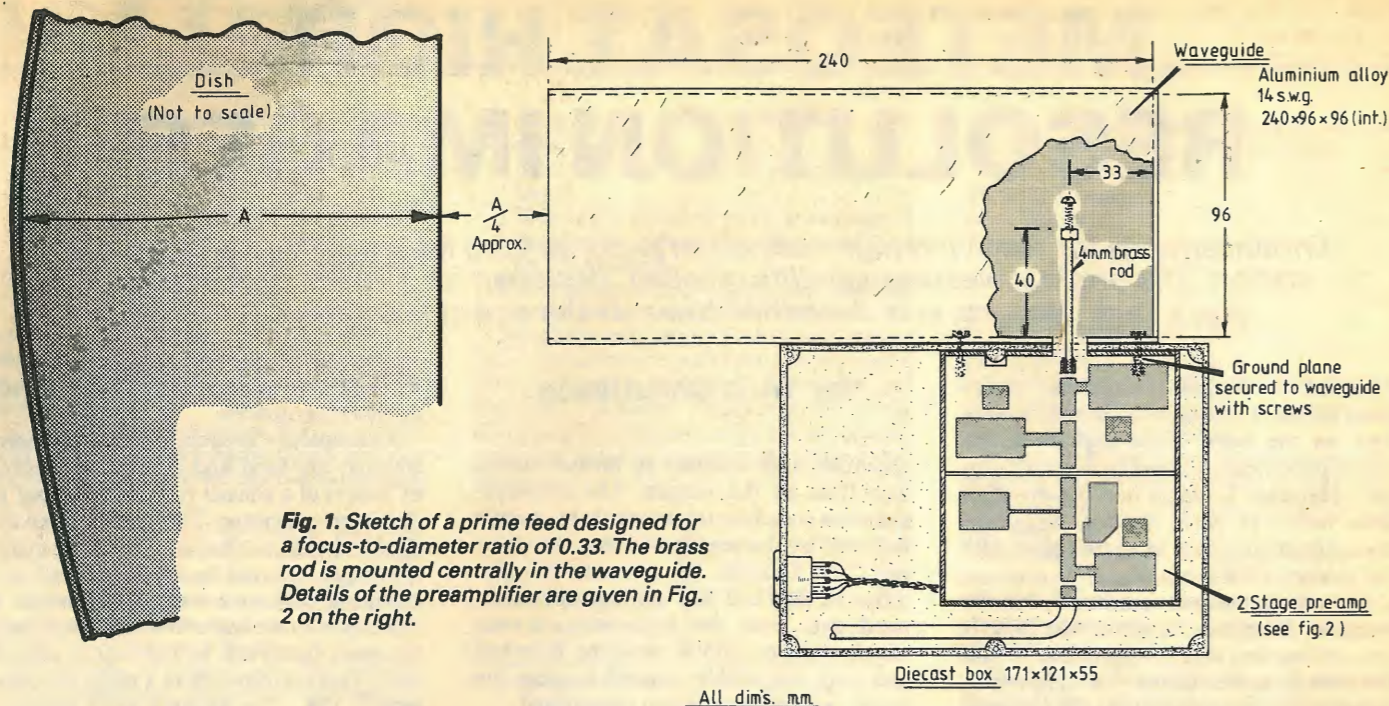


Fig. 1. Sketch of a prime feed designed for a focus-to-diameter ratio of 0.33. The brass rod is mounted centrally in the waveguide. Details of the preamplifier are given in Fig. 2 on the right.

the dish will depend on the focus-to-diameter ratio which determines the beam width that will fully illuminate the dish, but without spill-over. Figures 1 and 2 show a design which was optimized for a f/d ratio of 0.33. A smaller ratio presents an almost impossible design problem. A square section wave guide was used rather than a circular one because a slightly wider beam width can be obtained before the wave guide becomes too small to support wave transmission. If a dish with a larger f/d ratio were used a suitable circular section, sometimes known as a 'beer can feed' could be used. Construction of the pre-amplifier is identical to that used on the Tiros h.r.p.t. station except that the small receiving element is connected immediately before the first chip capacitor. The length of the element is adjusted, by means of the brass screw in the top, for optimum noise performance by pointing the waveguide, without the dish, in the general direction of Meteosat and adjusting it

using the s.d.u.s. transmissions. A usable but rather noisy facsimile picture could be obtained on the prototype.

The dish mounting may be rigid because the beam-width is not narrow enough for the satellite to move off beam during its daily movement of about two degrees. A reasonably unobstructed view of the sky must be available and the direction may be estimated from a nomograph or calculated.⁴ Once the signal has been acquired, final adjustment of direction, focus and polarization may be achieved.

Conversion to 10.7MHz is by the same converter system used for h.r.p.t. which was in turn based on one for Meteosat s.d.u.s. Careful adjustment of the interdigital filter is needed if it is required to pass h.r.p.t., as well as the Meteosat transmissions, without significant differences in performance on the four frequencies.

If the maximum benefit is to be gained from the lower bandwidth of the Meteosat transmission, the i.f. bandwidth should be

reduced to about 1MHz. The simplest way to do this is to remove the 2.2k Ω damping resistor across the tuned circuit in the mixer mosfet drain. The remainder of the wideband i.f. amplifier may be used without modification.

Phase demodulator

The method of modulation and the modulation index are identical to those used on the h.r.p.t. transmission and so the phase-locked loop demodulator may be used without change. The base bandwidth of the p.d.u.s. signal is considerably lower than the h.r.p.t., for which the post-detection filter was designed, and therefore a further filter must be added before the signal is applied to the p.d.u.s. decoder. This filter is placed after the existing filter output, in parallel with the existing connection to the h.r.p.t. decoder, and has a 3dB cut-off point of 280kHz, Fig. 3.

Data decoding

At this point in the system it is convenient to separate the p.d.u.s. chain from the h.r.p.t. system because the differences between the two become progressively more extensive. As before, the next step is to convert the s.p.l. data to n.r.z. and clock, in a manner that avoids most of the noise. The principle of s.p.l. decoding was covered before and the same definitions apply here. The h.r.p.t. system uses a digital integrator as a bit conditioner, and although this method could have been used again, because of the lower data rate a more conventional analogue implementation was used. Far simpler methods could be used to decode s.p.l., but it is well worth making the extra effort at this point because the decoder and front-end performance determines the overall error rate.

A complete circuit diagram of the decoder is shown in Fig. 4, and it operates as follows. Raw s.p.l. data is divided into two chains, one of which is clipped, and both positive and negative transitions used to regenerate the clock by pulsing a tuned

Table 3. The 24-word frame label broken down.

Word number	Meaning
1&2	Number of frames per subframes
3&4	Number of subframes in transmission
5&6	Current subframe number
7&8	Image line number (headers are zero)
9-12	Image number from mission start
13	Format indicator, A=00 B=FF (hex)
14	Vis 1 indicator } 00 = Data not present F0 = 1st half line present
15	Vis 2 indicator } 0F = 2nd half line present
16	IR indicator } 00 = Data not present
17	WV indicator } FF = Data present
18	Grid, 00 = No grid present
19	Reserved (00 on current operations)
20	Scan direction (normally 00 = S-N/E-W)
21-24	Spare (all zeros)

circuit at twice the data rate. Two c.m.o.s. phase-locked loop i.cs provide logic level clocks both in phase, and at 90° to the s.p.l. 'bits'. Two D-type flip flops generate clocks at data rate both in phase and at 90° to the incoming data. The two clock dividers can be initialized externally by the clock-error signal which goes high if a phase error is detected by the frame synchronizer. The clock signals are gated to produce the enable and reset pulses that operate the integrators and sampling circuits. At the end of each data bit the integrated values of both associated s.p.l. bits are held at the inputs of a comparator, the output of which is clocked into a further D-type flip flop. This forms the n.r.z. output. Both 180° and 90° clocks are used by the sync. detector. The waveforms marked on the circuit diagram are timed over a single data bit.

P.d.u.s.-frame format

Like the h.r.p.t. from Tiros the data stream is divided into blocks of words called frames. Each frame consists of 364, eight-bit words and the first three words of each frame are always the same; they form the synchronizing sequence. The transmission is structured as a number of sets of the frames, each set containing four frames in a B format and eight in an A format. These



One of eight registered primary data users, Mike Christieson, at his station. From left to right are colour-display electronics, computer-terminal and v.d.u. with colour monitor above it showing p.d.u.s. full-disc image, and the PDP9 mini-computer with four tape drives. The white panel below the tape drives is the satellite interface.

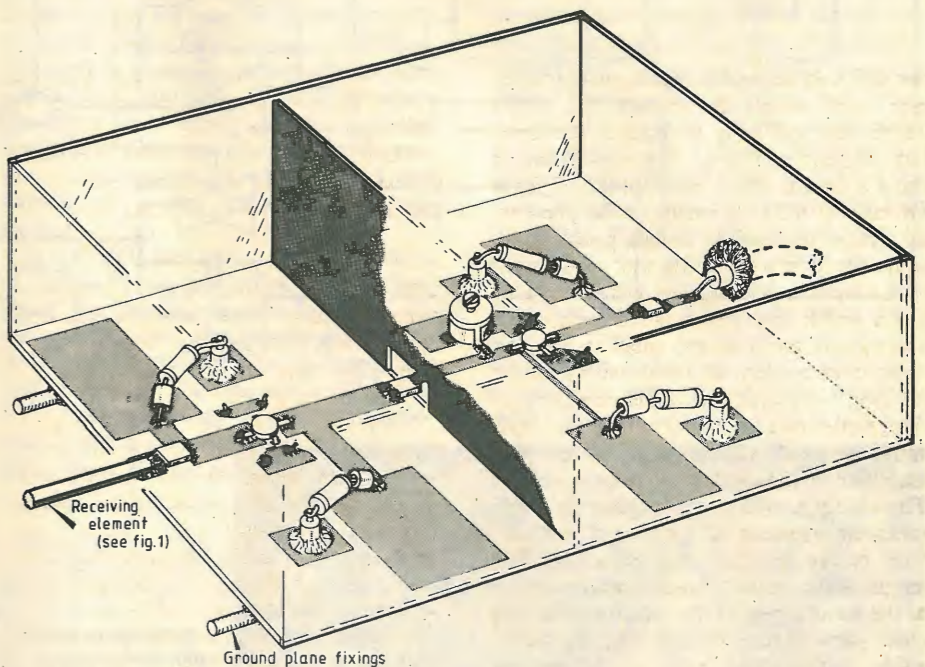


Fig. 2. Details of the two-stage preamplifier shown in Fig. 1. This is a slightly modified version of the one designed for receiving h.r.p.t. using the signal from NOAA-6, as described in the November 1981 issue of Wireless World.

Table 2. P.d.u.s. frame format. The first three words of each 364-word frame are always the same.

3 words	1 word	24 words	Spare		Data
Sync.	Format ident	Frame number 0000	40 words in 'A'	8 words in 'B'	
Sync.	Format ident	0001	Data, radlance values sent m.s.b. first		
etc.	etc.	0010	Data		
1 Sub-frame All syncs. are 3 words 00000101 00001100 11011111 Most significant 4 bits 0111 = A format 0011 = B format		0011	Data 202 words	Further data in 'A' formats 158 words grid in 'B'	
		0100	Data (only exists in 'A' formats)		
		0101	Data Note: IR & WV have 8 bit resolution v.i.s. is 6 bit (to l.s.b.s filled by zeros)		
		0110	Data		
		0111	Data 44 words	Grid, 316 words (2500 grid bits plus 28 spare)	
4 words			360 words		

Background

The launch of Meteosat-2 on 19 June, 1981, began a new era of European space exploitation. It was the major part of the first active payload for Ariane, the European Space Agency's launch vehicle. After launch, the satellite was placed in a transfer orbit and then lifted into a near geosynchronous orbit by the apogee boost motor. On 20 June it was 86° W and drifting slowly eastwards at a rate of 2.8° per day. During the drift-phase, test transmissions were carried out and by the time it arrived on station on the morning of 21 July, most of the telecommunications system had been checked out. The first image scan in visible light was performed at 1030 GMT on 28 July, and in infrared on 30 July. The scheduled We-fax analogue service commenced on 17 August and the primary-data user station (p.d.u.s.) service on 15 September.

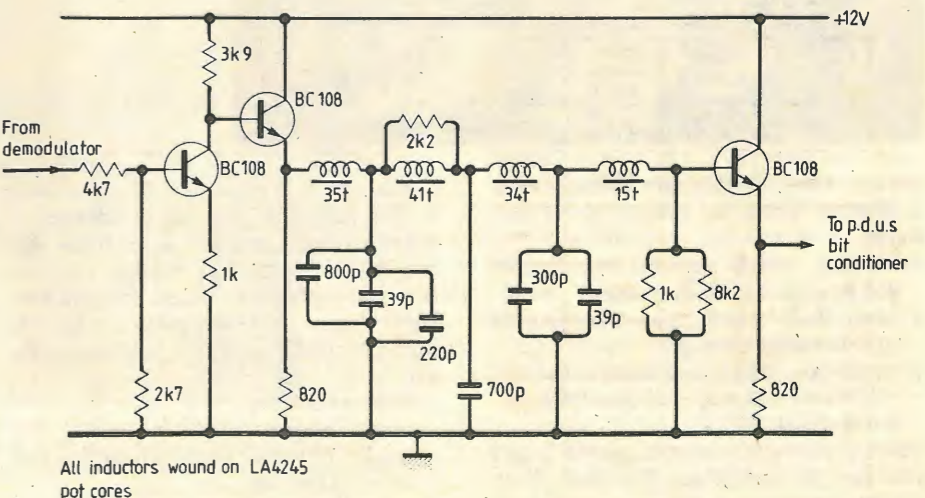


Fig. 3. Post-detection filter for p.d.u.s. with 3dB cut-off point of 280kHz.

Communications crisis

A pressure group, consisting members of companies and associations connected with the communications industry, has been set up to try and persuade the Government to speed up their liberalization of telecommunications. Many of the companies have invested money in anticipation of the liberalization and are now suffering financial hardship. The group calls itself the Communications Crisis Committee and its members include; Professor Lou Schnurr of the Chelmer Institute of Higher Education; The Mobile Radio Trade Association (MRTA); The Independent Telephone Supplies Association (ITSA); The Federation of Communications Services (FCS); The Mobile Radio Users' Association and the National Committee for the Legalization of Citizen's Band Radio (NATCOL-CIBAR).

They have put their opinions together into a document called the Report of the Communications Crisis Committee which consists of contributions from each of the corporate members of the Committee.

Professor Schnurr sets the scene by decrying the self-perpetuating monopoly of the present system. Even where free enterprise agreements exist, they are bound by licensing and technical approval procedures. A particular area for discontent is the allocations of the radio-frequency bands, especially the constraints on commercial development of the spec-

trum "controlled by an organization insensitive to market demand and without the philosophy of optimizing available spectral bandwidth for the purpose of services development. So long as such practices are contained within the moated walls of establishment privilege and internal decision making, the marriage of telephony and wireless cannot exist". This, he implies, impedes the whole of the diffusion of information technology throughout commerce.

Contributions from the other committee members also press for the liberalization of the use of British Telecom's network; to give access to mobile radio users, so that advanced data services for communication to mobile traffic. MRUA suggests that mobile services should have access to frequencies below 1,000MHz, frequencies above that being reserved for radio location and navigation. They also press for private network communications which would also have access to the public switched networks.

In a specific case study, Godfrey Wilson of Digital Paging Ltd bitterly complained about the inability to gain from BT the exchange facilities required for direct dial-in capability, available on his companies paging service. The unrealistic pricing of BT's radiopaging service; the "extortionate delays in obtaining services, and servicing from BT; excessive delays from the

Home Office in obtaining frequencies." Wilson feels it is unacceptable to be forced to compete with the body that issues the licences.

In conclusion, the committee puts forward several points for "direct, immediate action": Government departments should be asked to take steps to break the cycle of "time wasting tactics by BT and the Home Office Radio Regulatory Department; licensing powers should be transferred from BT to the Department of Industry; BT management to give fair and equitable access to BT competitors of the same facilities enjoyed by BT's own services and at the same price; require BT to set up self-accounting in all areas where there may be competition, ensuring public accountability. Pending the division of such areas, BT should suspend further commercial development; The Cabinet Office should take action to allocate some 60MHz of the radio frequency spectrum below 960MHz for private sector mobile radio services in conformity with the allocations of the 1979 WARC. There should be support and funding available to a private sector coordinating group. This would assist the administration and allocation of radio communications services, enabling medium-term commercial development of information technology and telecommunications services.

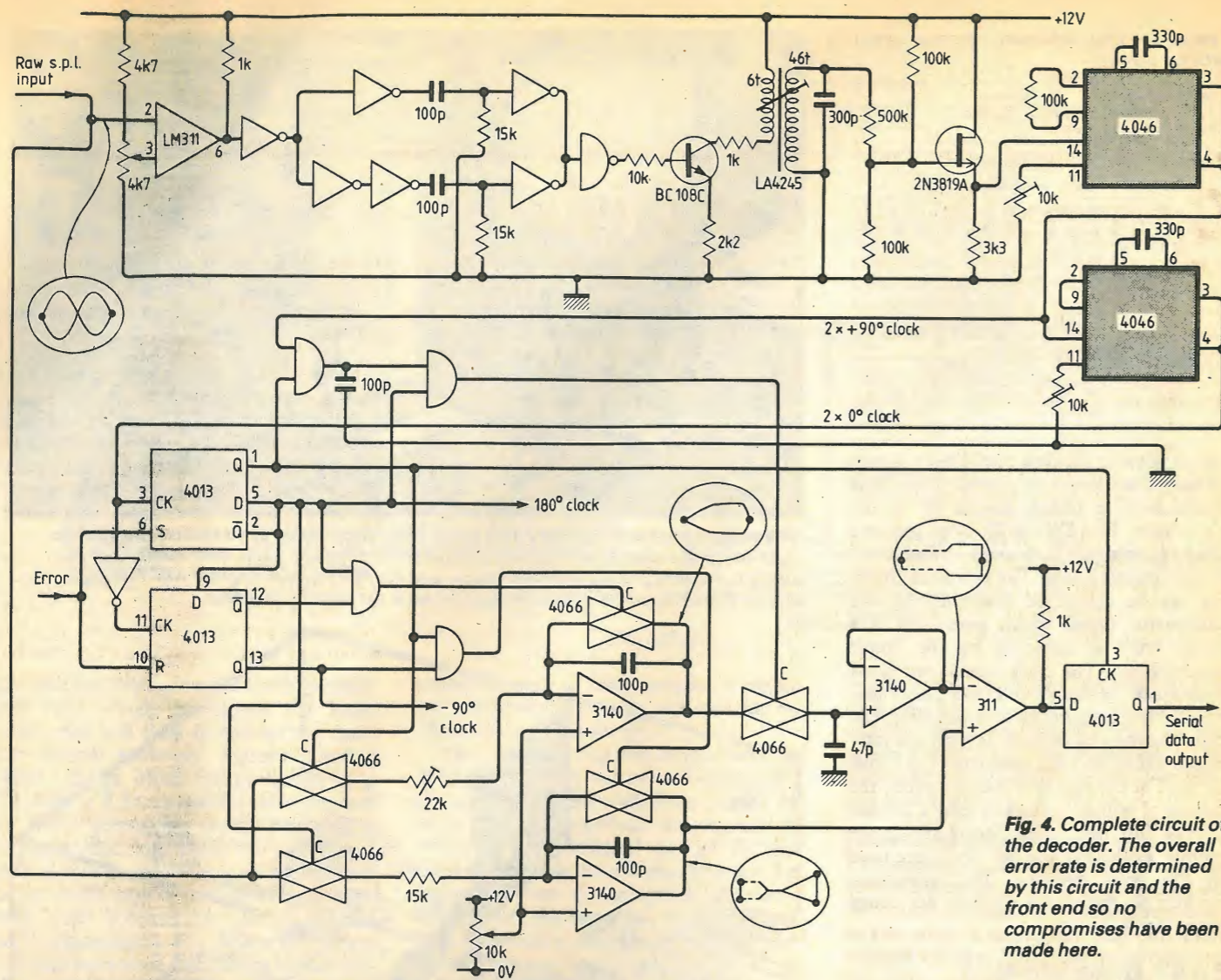


Fig. 4. Complete circuit of the decoder. The overall error rate is determined by this circuit and the front end so no compromises have been made here.


Note that when both visible channels are scheduled and only one channel is available, lines are duplicated.

All digital transmissions are preceded by a series of frames containing random data (with the label zero) to synchronise the receiver. The heading is then repeated 42 times in an A format and 84 times in a B format. Data then follows and the sequence is ended by one or two conclusion sub-frames. There is insufficient space here to describe fully the contents of the identification and the reader is referred to the ESA publications for this essential information.^{5, 6, 7, 8.}

References

- 1 High-resolution weather satellite pictures, M. L. Christieson, *Wireless World*, Nov., Dec. 1981, Jan. 1982
- 2 Meteosat earth station, M. L. Christieson, *Wireless World*, June, July 1979
- 3 Meteosat dissemination schedule, (published regularly) ESA.
- 4 *Meteosat dissemination news letter*, No 81/2, July 1981, ESA
- 5 Meteosat high-resolution image dissemination, ESA
- 6 Definition of h.r. format interpretation data, M. Jones, 79 06 11, ESA
- 7 Meteosat calibration reports, (published occasionally) ESA
- 8 Special response data for Meteosat-2, Meteosat systems guide annex B1, ESA

To be continued

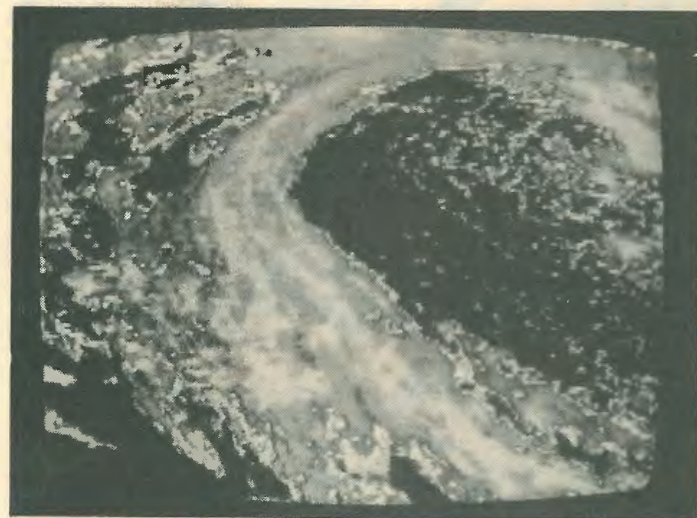

A depression in the eastern Atlantic scanned by one of the satellite's two visible-light sensors

sets are rather confusingly referred to as subframes. There are three types of subframes

- heading, which contain identification and interpretation information
- data, which contain the image, and the grid-coastline bit map
- conclusion, which are similar to heading subframes but may contain updated information.

Table 2 shows the construction of a data subframe for both A and B formats. Each subframe has a 'label', consisting of 24

words, and its contents are shown in Table 3. The data from one line of infra-red or water vapour is sent in one subframe, but one line of visible data requires two consecutive subframes. When formats containing more than one image are sent the lines are interleaved in the following priority

- infra-red line one
- visible line one
- visible line two or water-vapour line one
- infra-red line two
- visible line three, etc.



Arthur C. Clarke, on the right, is receiving the Marconi Fellowship Award for 1982 from HRH Prince Claus of the Netherlands. Arthur Clarke was awarded the prize particularly for his pioneering ideas in the field of satellite communication. He originated proposals for the use of 'Extra-terrestrial relays', first published in an article in *Wireless World* in October 1945. Since then he has worked in similar proportions in both science fact and science fiction.

Old brain, new hat?

First announced as long as two years ago, the "hand-held" Newbrain personal computer emerged recently under the new parentage of Grundy Business Systems. Following Newbury Laboratories dropping of the project in 1980 - itself then only three years old - Bob Smith and colleagues left to seek new backing, ending up with a Grundy:BTG share arrangement of 70:30%. At the same time, the specification of the machine was improved so that Grundy now claim it is designed for "business, scientific and educational use as well as home computing". Now with its resident random-access memory increased to 32K (plug-in modules of 64, 128, 256 or 512 can take it to 2M) and 28K of read-only memory, it is designed to operate with a range of interchangeable and expandable program modules, or firmware. The hand-held claim is based on the built-in 16-character 14-segment vacuum fluorescent display together with optional one-hour battery module of the AD version, designed chiefly to occupy minimum desk space. But an MDB model with on-



board nickel-cadmium cells will allow display in its editing mode for four hours and preserve memory for 20 hours and should be available in six months time. The cheapest version, model A at £199 + vat, comes without this display but with tv and monitor ports instead, as well as dual cassette port, RS232/V24 printer and bidirectional ports. The screen display can provide, unusually, 40 or 80 characters per line and a resolution of 250 dots vertically by up to 640 dots, and may be mixed with a separately scrollable character-mode

display. The 512 character font includes viewdata mosaics, upper and lower case Greek letters, arc, and line drawing graphics, as well as the 96 ISO printing characters.

Firmware consists of interchangeable modules, communicating via hardware-independent interfaces, and may be expanded without interference with the hardware. The enhanced-ANSI Basic allows for user proofing of programs, direct interrupt handling, device-independent i/o, chaining and external calls. The

screen editor claims novelties for a microcomputer: backwards scrolling, multi-screen ability and direct cursor addressing. The operating system provides for peripheral device drivers to the processors — the cassette device involves a second processor which uses a learning algorithm to accommodate tape speed fluctuations. Additional rom slots are available in a buffer expansion module that accepts Z80 assembler, Comal structured Basic, statistics and text processing packages. The buffer module also has memory paging circuitry, parallel i/o ports, analogue ports, two multi-speed V24 ports, as well as rom space, which will be included on-board in the M models available later. Proprietary software packages may be used from cassette or *via* disc under control of the CP/M module, available September. A communications module, also available September, contains 32 V24 ports to give flexibility in sharing peripheral devices and connecting computers together. Unfortunately, a videotext module takes only low priority, and is planned for "some time next year".

Meeting Grundy's price targets meant adopting n.m.o.s. circuits instead of the more expensive c.m.o.s. types. Switch-off circuitry was incorporated to keep the circuits cool and power consumption within reasonable limits. "Other machines do have problems in this respect," says Grundy's Mike Wakefield, who is pleased to be able to claim a 0 to 45° C temperature range.

Welsh Dragon

The Dragon 32 computer is the first product of a new company, Dragon Data Ltd, a subsidiary of the toy manufacturers, Mettoy. Aimed at the first user, Dragon Data have concentrated their publicity in marketing a 'family home computer' where the children might use it for learning and games playing while the parents can compute family budgets, or index a collection.

The Dragon 32 is based on a Motorola 6809E which has an internal architecture so designed that it needs far fewer instructions to operate it than many other microprocessors and is very fast. It has a 16K rom with extended Microsoft colour Basic, which gives high-resolution graphics of up to 256 x 192 pixels: there is a modulated output to a domestic tv and there is also a monitor output. The basic computer includes a Centronics-type interface, so a 'professional' printer may be plugged in directly. The keyboard is similar to that used on DEC equipment and offers typewriter-style keys, guaranteed for 20 million key depressions. There is a 32K ram with the ability to expand to 64K. In addition there is a games cartridge slot with sockets for two joystick controls for the playing of games;



cartridges for the more popular amusement arcade games, space invaders, a 'Pacman'-type game and others, are available. Programmes may be stored on cassette tape. Dragon Data say that they have paid particular attention to the cassette interface so that the computer will work with a wide range of cassette recorders.

Some software on cassette is already available, particularly the Dragon Special Selection tapes which are games programs which explain how they work and so give some insight into their programming.

Especially useful for educational programs is the ability to switch sound from a cassette player through to the tv sound. Program and a sound commentary can be included on the same cassette. A language lesson could show the words on the screen while they are spoken through the speaker. The Dragon can also generate sound with five octaves of musical notes with selectable duration and volume. This too comes out through the tv speaker.

Future expansions and developments include a disc operating system, an RS232 port, a second microprocessor and an operating system together with Prestel and

Banking on video

Barclays Bank has found that the best way to keep their staff informed is through video programmes, shown on tv sets at the place of work. They have invested in a £1M recording studio and insist that their programmes should be of the highest quality both in content and presentation. So they have hired tv producers and popular tv performers to make the programmes look as much like the programmes the staff might watch at home, as possible. Such subjects as 'How to spot fraudulent use of Barclaycard' or the implications to the staff on the opening of the banks to the public on Saturday mornings, have been produced and are examples of the training and information functions. In order to generate enough copies of the video films for distribution, Barclays have a computer-controlled copying suite with quality monitoring also controlled by computer.

The next phase of the video network is to extend it to 2,300 outlets. Barclays have awarded a £3.5M contract to Soundcraft Network Video to install 700 additional Type 5 Sony U-Matic video cassette recorders and 1,900 Trinitron monitors, and to maintain the whole system.

Mike Pogson, the managing director of Soundcraft, told us that his company had made considerable investment in providing servicing back-up for such a system. He described the lack of fully-trained broadcast engineers who were necessary to diagnose as well as rectify any faults in the field. He saw the role of his company as removing all the technical problems from

teletext facilities. Other operating languages can be added, including Pascal, 'C' and Basic compilers.

Program cassettes and cartridges are planned for a wide range of applications. The Dragon is all British, designed by Dragon Data with the co-operation of the PATs Centre, and Motorola, whose chips, manufactured in Scotland are used in the computer.

Comparisons are always difficult but the nearest competitor to the Dragon is the Sinclair ZX Spectrum. The Dragon 32 has more memory and a particular advantage in having a 'professional' keyboard. The Centronics interface is also a big advantage. The Sinclair has more colours available at high resolution and the big (so far theoretical) advantage of the Microdrive; the miniature, low cost disc memory. However, there is a big difference in 'feel' with the ZX Spectrum feeling like a toy computer and the Dragon and its keyboard with the touch of a 'real' computer.

The Dragon 32 is in production at the Mettoy factory in Swansea, it will be on sale in the High Street early in August for just under £200.

the client's shoulders so that they can 'get on with producing and distributing the programmes'.

The Soundcraft deal is claimed to be the biggest contract by a corporate organization in Europe.

New technology and the graduate

The Department of Education and Science has approved the co-operation between the Science and Engineering Research Council and the Open University for a series of programmes of 'technological topping-up' courses. It is intended to provide a re-education for those graduates who have been working in industry for periods of 5 to 15 years. The SERC became aware of a need for such courses and have commissioned the OU to produce them.

The courses will use the OU's techniques for home study with tutorial support and study centre facilities for practical work. Two areas in particular have been identified for priority treatment, which are computer applications (including real-time monitoring and control systems), and manufacturing.

The computer applications course is expected to consist of a 'foundation' module on software engineering, computer systems architecture, and operating systems. This would be followed by a number of 'core' modules on monitoring systems, systems modelling, control systems and project management. There would also be optional modules on robotics, man/machine interactions, and computer-aided design. The full course will be

the equivalent of one year's full time study. Certificates would be awarded for each module of the course and a diploma for the successful completion of the whole course. Students may then be able to undertake a further project in a related area which would lead to an M.Sc.-level qualification.

Telecom showcase

British Telecom's new exhibition centre is not a museum, stressed Peter Benton, the Deputy Chairman of BT, although it does trace the history of telecommunications from the early days of telegraphy. The centre's full title is Telecom Technology Showcase and in addition to the historical aspect which is well covered with many working examples of, for example, a Strowger telephone exchange of 1940s vintage, there is an exhibition of BT's latest equipment and techniques. Currently these include many digital techniques, displays about optical fibres and satellite telecommunications with examples of some of the latest equipment. It is planned to change the displays regularly to keep them up-to-date.

The Showcase is situated in Queen Victoria Street, London, in part of BT's Baynard House and is next door to the Mermaid Theatre. Lord Miles, formerly Sir Bernard Miles, officially opened the showcase and pointed out the role that the Mermaid's Molecule Club had played in educating young people in science and technology. He hoped that the Showcase would also contribute towards the edification of the young. He also looked forward to the micro revolution which he felt would release us from the 'work ethic' and allow us to get on with living, without the encumbrance of work.

Projects Editor

Wireless World needs a Projects Editor, who will be responsible for running the laboratory.

The work consists of design and development of equipment subsequently to be described in *Wireless World*, commissioning articles on construction and testing pieces of commercial equipment.

The successful applicant will be experienced in both analogue and digital techniques and will be able to express himself clearly in writing.

If the post appeals to you, please write to the Editor, Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS or telephone 01-661 3128.

CIRCUIT IDEAS


Extended addressing for the Z80

Current 40-pin memory-mapping i.cs are expensive and difficult to obtain. As this circuit shows, it is possible to extend the addressing capability of a Z80 to more than 16 bits using readily available 74S189, 64-bit t.t.l. rams.

The microprocessor's four most significant address lines are not used for memory access, but instead address one of 16 stores of eight or 12 bits which are used as most significant address lines; in essence the same function as carried out by dedicated memory-mapping i.cs.

Each store is loaded using an OUT(C),r instruction which, with the Z80, results in the contents of the B register being placed on the upper half of the address bus. To load a particular store, the program has to put the eight address bits into the A (or D, E, H or L) register, the store addressing the top four bits of B, then load C with the i/o address of the mapping circuit and issue an OUT(C),A (or D, E, H or L) instruction. If 12 address bits are to be generated, the top four bits must also be placed in the bottom four positions of B.

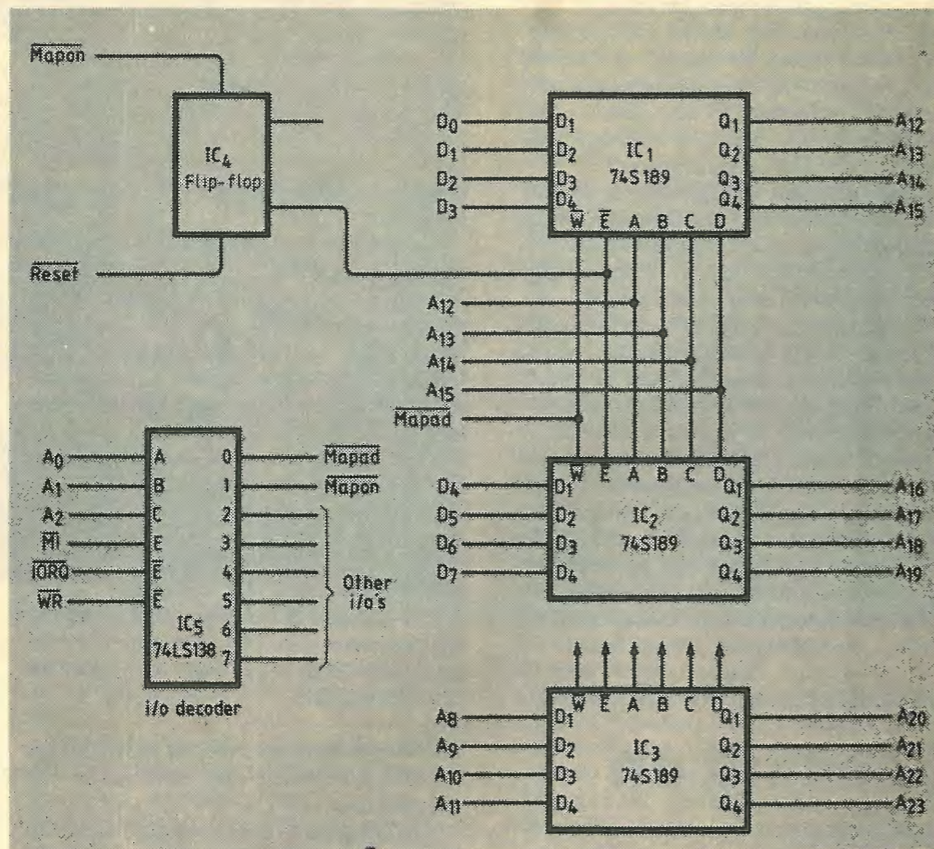Sixteen different stores are used so that various parts of the program can be allocated one or several locations, allowing each store to work on its own ram. For example, interrupt routines may be run without upsetting background pointers.



Initially, bistable IC₄ disables the stores, whose outputs are held high by resistors until a switch-on signal is generated using a spare i/o line. This gives a fixed value on

start up while the initializing program loads the 16 stores.
Brian Dillon
Dublin

Low-current voltage regulator

Standby consumption and output rating of this low-power regulator are 50µA and greater than 10mA respectively. Current limiting is included, brought about by gate-to-source voltage starvation in the 4007, and the output is short-circuit proof. Components used are cheap and readily available.

With the components shown, the output voltage is 12.78V, given by

$$V_{out} \approx V_{BR}(Tr1) + V_R$$


where $V_R = V_S - V_T$ and $V_T \approx 1.5V$. And

$$V_{RA} = V_F(D1) + V_{BR}(Tr1) - V_T$$

such that $V_{out} = V_{RA} + V_{RB}$. In this case, assuming a typical BC109 breakdown voltage of 8.2V for $Tr1$, a forward voltage for $D1$ of 0.4V and a threshold voltage of 1.5V, $V_{RA} = 7.1$ and $V_{RB} = 5.68$. Therefore $V_{out} = 12.78V$.

With a maximum input voltage of 20V, with V_R at around 4V, the c.m.o.s. device will be operating at around 16V which is inside its rating.

D. Roffey
Bromley

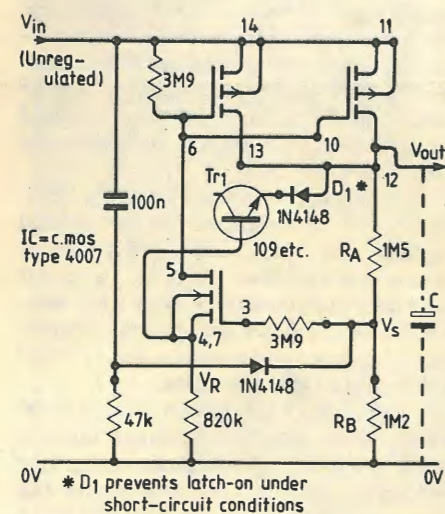


* $D1$ prevents latch-on under short-circuit conditions


Programmable frequency divider

The 74163 4-bit binary counter may be used to divide the clock frequency by N, where $2 \leq N \leq 16$, by applying binary (16-N) to the data inputs and connecting the load input to the inverted carry output.

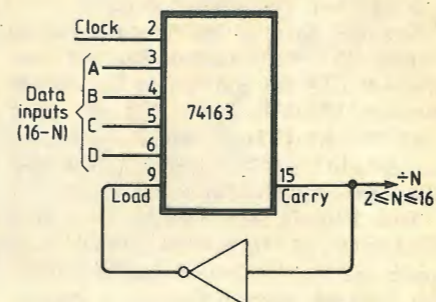N. H. Sabah
American University of Beirut



WIRELESS WORLD AUGUST 1982

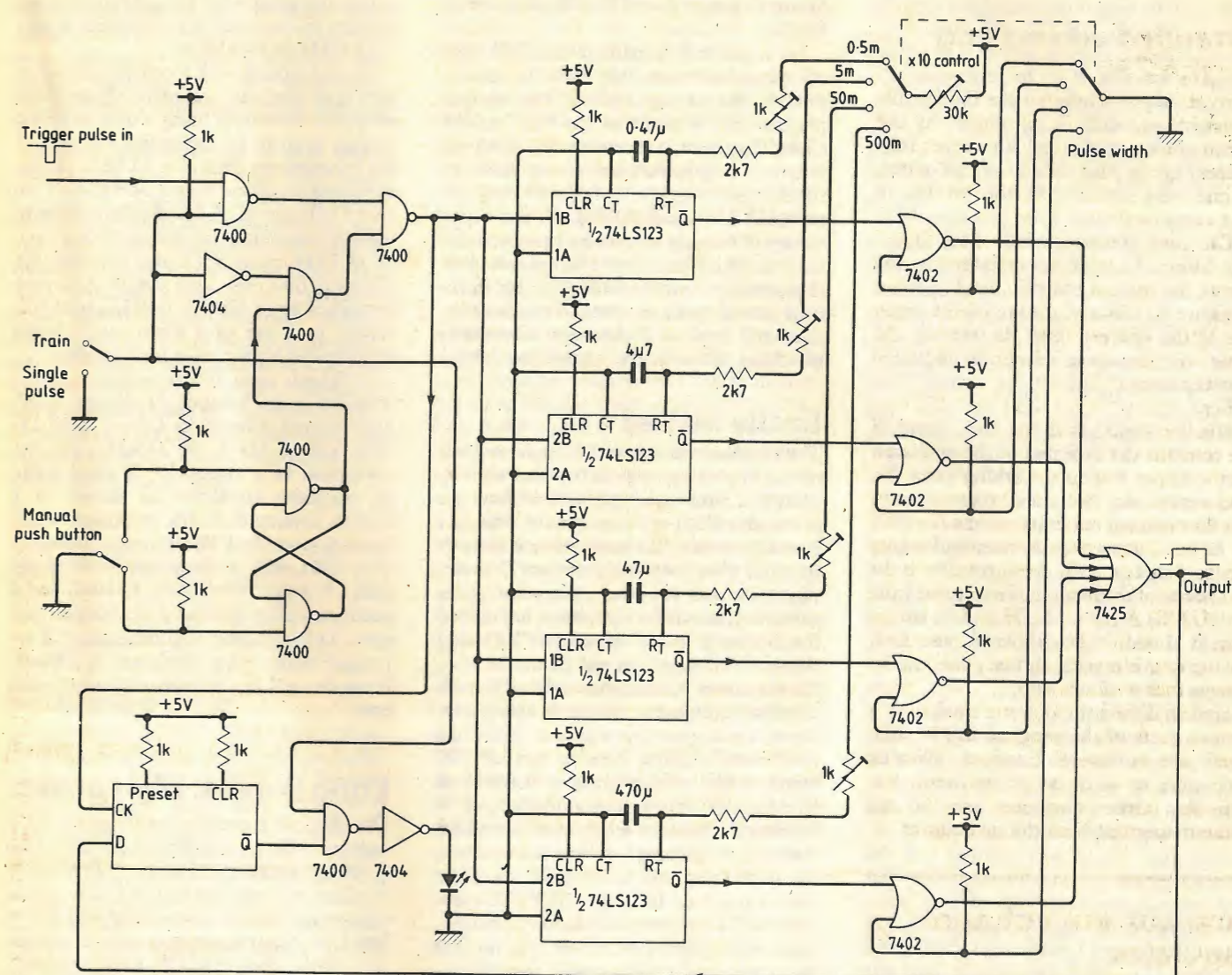

Pulse-generation using t.t.l.

Variable-pulse control using t.t.l. i.cs is not unusual, but most circuits use non-retriggerable monostables since they are less prone to false triggering from noisy supply lines and stray signals. However, when a 100% duty cycle is reached, output jitter occurs and above 100%, the pulse repetition frequency is reduced.

This circuit uses separate retriggerable monostables and is not prone to false triggering. Jittering near the 100% duty cycle does not occur and at and above 100%, an l.e.d. lights and the output becomes static. Further stages may be added.

A. R. Millichope
Birmingham


WIRELESS WORLD AUGUST 1982

Window discriminator

Two op-amps and numerous close-tolerance resistors used in conventional window discriminators are replaced by this circuit at the expense of convenient adjustment.

Designed to lift the pen of an X-Y recorder when the Y input exceeded the range 0.5 to 4.5V, the circuit uses the 555's control-voltage input to trim the trigger level. A potential divider was used at the input to change the voltage range to between 0.4 and 3.6V. Predictable operation is ensured by tying the threshold input to the positive rail and if a t.t.l. output is required, the open-collector output, pin 7, can be used in the conventional manner.

R. M. Jones
County Durham

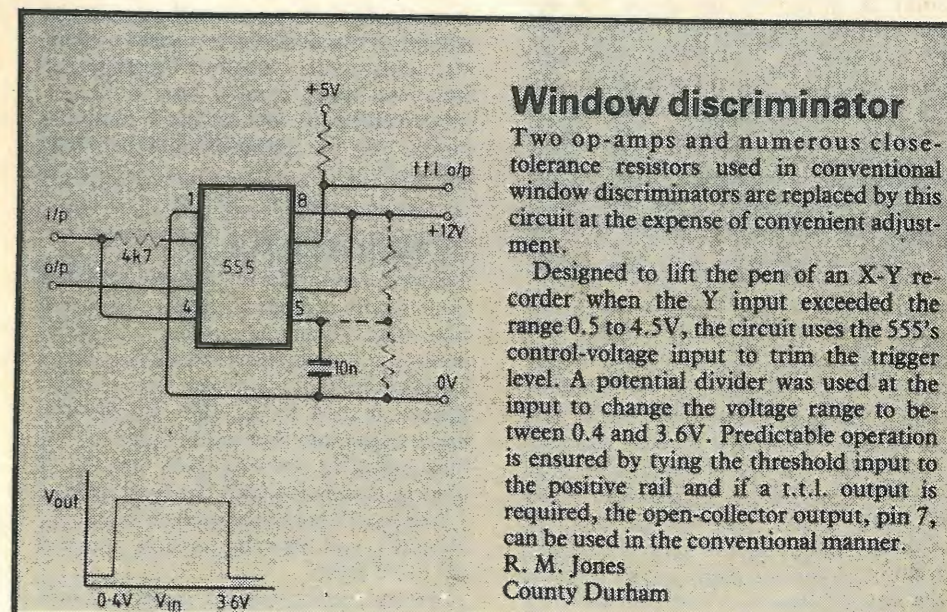

COMMUNICATIONS

Howard Hughes

I watched the recent two-part EMI film on Howard Hughes (BBC 2) with interest — though it seemed a great pity that so much emphasis was placed on his extraordinary idiosyncrasies, so little on the remarkable contributions made to technology by the companies controlled by his secret telephone calls in the middle of the night. Hughes was undoubtedly the fruitiest of fruit-cakes — though if he had been born in Chipping Sodbury, rather than Houston, Texas, he might have passed as the last of the great eccentrics. Fruit-cake or eccentric he has the distinction of being one of the few men ever to take on and defeat the European telecommunications "establishment" led by the British Post Office.

Wireless World has always been proud of the fact that the potential of the geostationary orbit as a unique parking place for microwave and broadcast relay stations was first pointed out in its columns in 1945 by Arthur Clarke. But the means of implementing this in 1963 by a transfer orbit and position-keeping jets were entirely the work of the Hughes Aircraft team led by Harold Rosen, Tom Hudspeth and Don Williams. An equally difficult job was to convince the Post Office. BPO were ranged solidly behind the concept of a series of station-keeping satellites some 12,000 miles above the Earth, involving all the problems of tracking and hand-over. The Post Office engineers attacked the geostationary orbit on the grounds of excessive time delay and pointed out the impracticability of conversation between two nervous speakers reduced to a hopeless tangle by the delays. Indeed the first transatlantic call I made over Early Bird (Intelsat 1) in 1965 did seem to bear out their gloomy prognostications — it was only later, when they had virtually admitted defeat, that it emerged that the real villain of the piece was the inadequate design of echo-suppressor then in use. It is often forgotten that it was not until well after the launching of Early Bird in 1965 (following the experimental ATS series) that Intelsat/Comsat became firmly committed to the synchronous orbit. In the struggle, which lasted some 3-4 years, Hughes Aircraft was not adverse to using the lavish hospitality that had earlier brought Howard Hughes before a Congressional Committee. I have to declare an interest as I was a bemused member of a party of European journalists taken to Culver City, Los Angeles and the fabulous Hughes Research Laboratories out at Malibu Beach — a trip that remains indelibly in the memory as one of the most lavishly endowed press parties of all time! I can plead only that it was not the trip that subverted me to support the geostationary orbit but a previous more modest meeting with Harold Rosen, at the conclusion of

one of his many efforts to convince European PTT organizations that their future was to be found 22,300 miles above Earth.

No mention was made in the EMI film of communications satellites or lasers though the dying recluse was shown playing with a model of the CIA-backed Global Explorer, the remarkable deep-sea recovery ship which came very near to success and which one day may itself be recognized as contributing to the technology of reaping a richer harvest from the sea bed. In his later days Hughes was close to madness — but as an old-style entrepreneur he did more to advance communications and aviation technology than whole battalions of eminently sane bureaucrats!

Easily nicked

The emphasis on lightweight, microminiature complex equipment in communications and broadcasting is not without its problems. High-cost equipment that can be easily carried, can easily be carried away by other than the rightful owners. It is not without reason that e.n.g. (electronic news gathering) television equipment has earned the sobriquet "easily nicked gear". During the past few years several crews have returned minus many thousands of pounds worth of equipment. Nor is it only portable electronic gear that vanishes. In April a BBC crew in South London lost £25,000 worth of film equipment from the back of an estate car while taking a lunch break in Stockwell. Another anonymous company has been advertising (under a box number) for information on a loss of a complete Sony e.n.g. unit including BVP330P camera, BVU110P recorder, battery charger, radio microphone, etc. This was not the first e.n.g. unit to disappear in the UK.

Communications equipment — professional, amateur and c.b. — has become very vulnerable to car thieves. But the thieves need to be careful in their choice of vehicle. I heard of a case recently where what looked like a standard broadcast car radio was taken from a Special Branch police vehicle. It was in fact a disguised control unit for a boot-mounted two-way radio!

Stable at s.h.f.

Although semiconductor devices, including Gunn diodes and Impatt diodes, make possible relatively simple self-excited oscillators at s.h.f., it remains essential for many applications to provide some form of stabilization. A good deal of effort, for example, has been put into developing cavity resonators, including low-cost types that can be used in association with the front-ends of 12 GHz satellite receivers where the circuit elements may take the form of punched out metal sheet.

Recently much interest is being shown

in small dielectric resonators which can be used in connection with cavity resonators to improve greatly the temperature characteristics or, for example, to stabilize monolithic GaAs fet oscillators.

In conjunction with a conventional cavity it is claimed that commercially available dielectric resonators using a disc of doped barium titanate in the cavity can reduce the temperature drift of a 10 GHz cavity-stabilized oscillator from 3 MHz per °C to only 3 kHz per °C. A new Mullard range of dielectric-stabilized oscillators within the 4 to 16 GHz frequency range includes the facility to tune over 1 per cent of the lowest frequency limit without degrading stabilization, or 8 per cent when rather lower stability and higher noise is acceptable.

A French team at Laboratoires d'Electronique et de Physique Appliquée (LEP) has reported (*Electronics Letters*, April 15, 1982 Vol 18 No 8, pp 345-347) the development of a monolithic X-band GaAs fet oscillator stabilized by means of a barium titanate dielectric resonator which delivers more than 30mW output power at 10.8 GHz with a frequency drift better than 1 p.p.m/K from -20°C to 80°C, and a maximum chip efficiency of about 20 per cent. The oscillator chip measures 1.2 by 1.4mm² with a chip thickness of 300µm. It can be used as a voltage-controlled oscillator.

Long waves, high power

The BBC is currently carrying out a £2-million refit to the Droitwich 200 kHz (1500 m) long-wave station at Droitwich, taking the opportunity to increase transmitter output power from 400 kW to 500 kW. The transmitters now in use are two of the four 200 kW units originally supplied by Marconi for the special wartime 800 kW station near Hull. The use of the Marconi "Pulsam" high-efficiency technique will make the higher power units more economical to run.

500 kW is a long way from the first long-wave (1600m) BBC station at Daventry. This was completed in 1924 and had a power of 25 kW following tests on a Marconi 15 kW long-wave transmitter in the Chelmsford factory. At that time the intention was to supplement the local regional transmitters (1.5 kW plus 0.12 kW relays) by a single transmitter providing "a reasonable field strength over most of the British Isles" — as indeed it appears to have done at a time when most listeners used outdoor aerials, electrical interference was reasonably low and there were none of those infuriating signals emanating from the line time-bases and switched-mode power supplies of colour television sets. Indeed in the 1930s it was firmly recognised in the UK that high-power stations of the order of 500 kW "may be a doubtful blessing".

American broadcasters, who have never used the long-wave broadcast band, have been limited even on medium-wave "clear channels" to a maximum of 50 kW and yet have traditionally achieved extensive and excellent night-time coverage using directional aerials to minimize mutual interference.

However this coverage is now under severe threat from Cuba who have stated an intention to install two 500 kW transmitters with omnidirectional aerials, plus over 180 other transmitters of various powers — and have withdrawn from a key Region 2 planning conference. It could be argued that the Americans have brought this problem on themselves by their intention to transmit programmes to Cuba on medium-waves — yet another example of how it is often external broadcasting for government agencies that has been the prime cause of the transmitter power race and excessive interference.

AMATEUR RADIO

Satellite scene

Several of the balloon flights being organized this year by the South African Radio League as a preliminary to an amateur satellite project have been completed successfully, including two flights to 100,000 ft with simple recovery beacons and a 10-hour flight to this height carrying a linear transponder as well as telemetry and recovery beacons. During the flight about 20 amateur operators had s.s.b. and morse contacts through the beacon over distances of several hundred kilometres. A later flight will be aimed at keeping a transporter at 100,000 ft over an extended period with power derived from solar panels. The whole project is enjoying the full co-operation of a number of universities and electronics firms.

During April, a false command initiated by the main computer on board the University of Surrey's UOSAT satellite inadvertently switched on both the 145 MHz and the 432 MHz beacons at the same time, resulting in desensitizing both command receivers so that the satellite was no longer under ground control. The normal fail-safe software in the computer had previously been temporarily over-written, with the result that the malfunction persisted for an extended period.

Ron Broadbent, G3AAJ, secretary of Amsat-UK, has complained of the many demands directed to the society, stemming not from radio amateurs but from school and university staffs seeking detailed information on what they regard as a "British Schools Satellite".

Vintage valves

A few months ago the turning over by Mullard Ltd of their Blackburn factory from the manufacture of domestic valves to other products led to nostalgic backward glances to the heyday of the "red" EF50 of wartime radar, the EF39 used in many communications receivers, and other once familiar small-signal valves.

Across the Atlantic the process of closing down production lines of "vacuum tubes" has been going on for several years, without many tears being shed. But surely a note in *QST* will touch the hearts of every old-time amateur and professional communications man: RCA have discontinued manufacture of a further batch of glass-envelope transmitting valves including such famous types as the 807, 811A, 813, 829B — valves that found their way into innumerable transmitters since they were first introduced well over 40 years ago — and still do yeoman service in many transmitters even today, although presumably the demand for replacements has dipped. Transmitters needed to be large to accommodate them and the ceramic types with (often noisy) forced-air cooling were displacing them, years before the semiconductor era began to deliver the knock-out blow. The 813 needs a hefty 5 amps at 10 volts just to keep the filament energized; but was — and remains — a magnificent workhorse for Class C service. Show me a transistor that will provide a comfortable 300 watts r.f. output at 20 MHz with a similar freedom from parasitic oscillation and ease of design — but until then many will regret the gradual passing of the thermionic era.

Perhaps not quite passing — Mullard, for example, tell me they have no plans to discontinue their range of transmitting valves, including near equivalents of a number of the axed RCA types. Indeed I hear rumours of European manufactured valves being sent across to the States and then returning to find sockets in European transmitters.

Here and there

The regulations introduced by the FCC on January 1, 1981, limiting the amount of r.f.i. generated by new computing devices marked for the home to limits calculated not to interfere with broadcast reception are having an effect on manufacturers. Although initially many manufacturers applied for waivers, the regulations must be complied with by October 1983, and recently the FCC laboratory has been rejecting less than 15 per cent of devices compared with 25-30 per cent in early 1981. FCC are now investigating the amount of interference produced by other digital devices including digital clocks using synthesized speech.

A number of candidates who took the

Radio Amateur's Examination in May appear to have been less than happy with the multichoice paper and support the view, expressed on a number of previous occasions in this column, that the City & Guilds Institute should carefully consider updating the aims and scope of the examination — and contributing to the reduction of the administrative time it takes in the UK to sit the exam and acquire a licence.

With the help of a small grant from the Science Research Council, the R.S.G.B. Propagation Studies Committee is to assist in the collection over the next four to five years of data on Sporadic E propagation on frequencies above 100 MHz. North/south propagation paths on 50 MHz were open on many occasions during March and April 1982. An unusually large number of South African stations were received in the U.K. on April 12.

In brief

The boom in walkabout audio tape cassette players has encouraged the marketing in Japan of miniature 50 MHz "walkie-talkie" units, such as the Standard "Talkman" with headphones and miniature boom microphones. In future someone "talking to themselves" in the street may or may not be a first sign of madness . . .

David Adams, VE3BHF (G4NWA) of Sutton West, Ontario has been walking the length of Britain, from the Scilly Isles to the Orkneys with a backpack that includes a 144 MHz hand-held transceiver . . . Callsign of the 70.05 MHz beacon transmitter on Harpur Hill, near Buxton, Derbyshire has changed from GB3SU to GB3BUX as part of the plan to use two-letter GB callsigns for repeaters and three-letter ones for beacons. Similarly, for example, the beacon high on the IBA's concrete aerial support tower at Emley Moor, West Yorkshire has changed from GB3EM to GB3MLE . . . Tropospheric 10 GHz contacts across the English Channel to amateurs in France and Holland continue to be reported over distances up to about 250 km . . . A "very slow rise" in membership is reported by the R.S.G.B. who state that of members resigning "the vast majority gave the present economic climate and unemployment as the main reason" . . . Forthcoming mobile rallies include: July 25, Anglian Mobile Rally, Stanway School, Colchester; Scarborough A.R.S. at Spa Ocean Room. August 1, R.S.G.B. National Mobile Rally at Woburn. August 8, 25th annual Derby Mobile Rally, Lower Bemrose School, off Derby Ring Road. August 15, Preston A.R.S. at Walton-le-Dale County High School, Brindle Road, Bamber Bridge, Preston. August 22, Bromsgrove A.R.C. picnic at Avoncroft Art Centre, Bromsgrove.

PAT HAWKER, G3VA

NETWORK ANALYSIS WITH A ZX81

Extensive insertion loss and group delay computations of ladder filters are faster with an inexpensive microcomputer than with a programmable calculator

The specification of the ZX81 reveals that it is also potentially a 'super-calculator' capable of handling much more extensive programs at a far higher computing speed than, for example, the Texas TI59. The 9½-digit accuracy is admittedly less but nevertheless perfectly adequate for a wide range of practical problems. The program described was written not only to fulfil a professional requirement, but also to test the capabilities of the ZX81 fitted with the 16K ram.

The menu it provides is as follows.

- Compute and display the insertion loss and group delay of a passive ladder network with up to 10 branches, excluding the terminations. For a frequency base in MHz the group delay is computed over an increment of 1kHz.
- Each branch can consist of a single inductor or capacitor, or a series or parallel tuned circuit. More complex structures can be handled by means of a simple device.
- A chosen value of dissipation can be assigned to the components.
- Component values entered can be listed and corrections made before computation starts.
- At the end of a calculation, individual frequencies and element values can be modified without re-starting the program from the beginning. This is invaluable for estimating the effect of component tolerances or for 'zooming in' on any particular area of the network response.
- Up to five group-delay equalizer sections can be added and the total resultant delay displayed. The display is in the form of the zero-frequency delay, followed by the differences from that value at the other points.
- Because the group delay values of the network are held in an auxiliary array, re-computation of the group-delay response after changes to the equalizer parameters is fast.
- Added loss due to dissipation in the equalizer can be displayed.

To give an idea of the running time, the ZX81 in the fast mode displays the insertion loss and group delay of a seventh-order elliptic-function filter at 15 points in around 75 seconds. Each successive attempt at group-delay equalization takes around 12 seconds, not including the time taken to enter values.

Because many users will not need the

by L. E. Weaver

group-delay equalization routine, the procedure for use is conveniently divided into two portions.

Computation of network response

First some general remarks. As I am principally concerned with video filters, the units chosen are Ω , μF , μH , MHz and μs . These can be replaced by any other self-consistent set, but obviously minor changes to the print statements will be needed.

It is assumed that the network is unbalanced and contains no bridged-T sections. The group-delay equalizers are dealt with quite differently. The branches are numbered from the input to the output, and the component values are entered in the same order so that for example, the fourth branch will contain L(4) and C(4), or perhaps L(4) or C(4) alone. As shunt and series branches alternate in a ladder network it is only necessary to specify the nature of one of these. This is chosen to be the branch facing the input termination.

The dissipation is expressed by D, which is the reciprocal of the Q factor, and must be specified at some frequency. This will often be the cut-off frequency or possibly one of the points of nominally infinite rejection. Because of the simplification in the expressions for the impedances, the standard device is employed of assuming that both the inductors and capacitors have the same dissipation, and that in a resonant circuit D is the sum of these. However, experience shows that provided D is less than about 0.02 ($Q > 50$) the individual dissipations do not need to be equal. It follows that if the capacitors can be considered as dissipationless, D can be taken as one half of the value which would otherwise apply. This may not sound very satisfactory but in practice it works surprisingly well.

With such a long program and only 16K of storage the display prompts necessarily have to be kept very short, so it seems desirable to set out the procedure in detail. Each input will, of course, be followed by NEW LINE.

Prompts	Inputs
FO?	Starting frequency
FM?	Maximum frequency
DF?	Frequency step
D?	Dissipation constant
FD?	Dissipation frequency (if

D=0 then a nominal positive value must be entered)

RI?	Input termination
RO?	Output termination
NO. OF BRANCHES?	Total excluding terminations
L+C? N=1	YES for a resonant circuit, NO for a single resistor or capacitor
SER OR PAR?	When previous input was YES, input SER for a series and PAR for a parallel resonant circuit
L? N=1	Enter L(1)
C?	Enter C(1). If only one L or C the other must be entered as zero



L. E. Weaver, B.Sc., M.I.E.E. is the author of three well-known works on television measurements, and of a number of monographs and papers both on that subject and on aspects of network design. Now a television engineering consultant, he was previously head of the measurements laboratory in the BBC designs department. While in that position he also used the experience previously gained in network design at STCs transmission laboratory to produce high-quality video filters, some of which have been commercially manufactured on a considerable scale.

This process will continue until the last branch has been entered. Then

SHUNT IN? YES for a shunt input, NO for a series
GOTO CHECK. This will then list the entered values. Modify by, for example, LET L(4) = 5.25. Do not enter RUN or CONT. When satisfied enter GOTO LOSS, which starts computation. After completion values can be modified and the network re-calculated by again using GOTO LOSS.

Group delay equalization

The insertion loss of a filter is usually required over a frequency range wide enough to cover both the pass and stop bands, but with delay equalization the situation is totally different. As a rough guide the important area in that instance lies between zero frequency and the 6dB point for a lowpass network, and between the 6dB points for a bandpass. It follows that a new set of frequencies must be selected up to the allowable total of 15, achieved by entries such as LET FM = 6 and LET FD = 0.5. The initial computation is then repeated by means of GOTO LOSS, which takes very little time as the component values do not have to be re-entered. The read-out must be completed, indicated by a 9 code.

The program allows for one first-order equalizer section followed by up to four second-order. Alternatively, up to five second-order sections may be used. Each is defined by a resonant frequency and a shape factor K, which must be made zero for the first-order section. The first-order section, if present, must be entered before the others.


The procedure is then as follows.

Prompts	Inputs
9/1590	CONT
V?	Total number of sections
FR? M=1	Resonant frequency of first section
K?	K-parameter of first section
FR? M=2	Resonant frequency of second section
K?	K for second section

As soon as the parameters for M=V have been entered the computation starts.

The initial attempt is not likely to be successful, so it will then be necessary to modify the equalizer parameters by inputs of the form LET F(2) = 2.2 and LET K(3) = 1.2. This must be followed by GOTO EQU, which repeats the calculation with the new values.

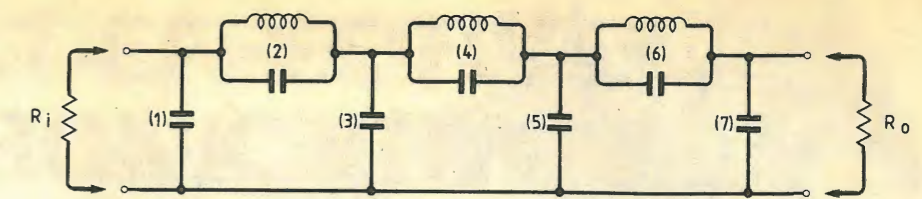At the end of the equalization process, GOTO DISS will provide a read-out of the equalizer dissipation corresponding to the value of D. This does not need to be the same as the D used for the insertion loss but may be re-entered before calling up the DISS routine.



Loss section								UNITS: Ω , μH , μF , MHz
$R_i=R_o=75$								
N	1	2	3	4	5	6	7	
L	0	1.58	0	3.09	0	1.67	0	
C	315.5 E-6	53.8 E-6	655 E-6	150 E-6	564 E-6	379 E-6	126 E-6	
Group delay equalizer								
M	1	2	3					
FR	2.0	3.0	4.5					
K	0	1.3	0.7					

Fig. 1. Component values of a 5MHz elliptic function lowpass filter in the form recommended for program entry. Suggested initial parameter values are included for a three-section group delay equalizer.

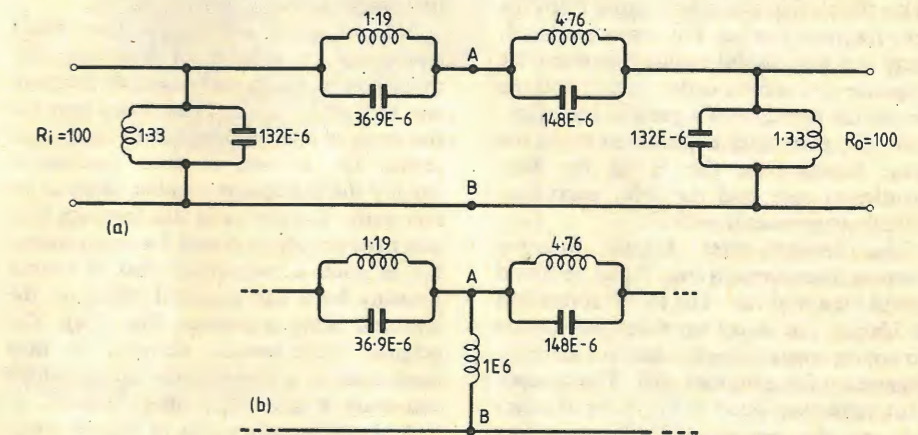


Fig. 2. Use of a dummy shunt branch where a series arm contains more than two components. Values shown are for a 10MHz bandpass filter with midband frequency 12MHz and rejection points at 6 and 24MHz. Original configuration at (a), dummy shunt branch inserted at (b).

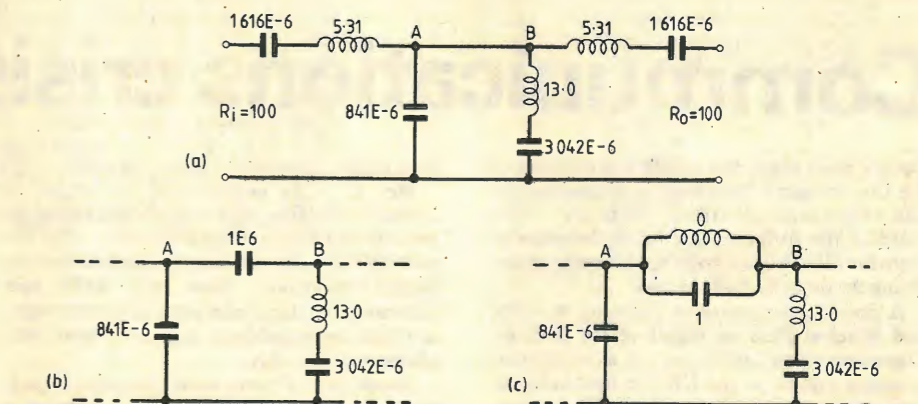


Fig. 3. Use of a dummy series branch where a shunt arm contains more than two components. Values shown correspond to a 3MHz bandpass filter with midband frequency 2MHz and a single rejection point at 0.8MHz. Original configuration at (a), dummy series branch suitable for bandpass structures only (b) and universally applicable dummy series branch (c).

In the absence of enough ram to run an optimization program, a graphical method has been found effective. This consists in plotting the combined group delay responses for successive parameter changes from some initial set of values, taking care not to try to deal with too many simultaneous changes. Some of these will inevitably be in the wrong direction, but one

quickly gets a feel for the way in which moves have to be made. Remember that the aim must be to minimize the absolute error, that is the positive and negative deviations must tend to equality, subject to the condition with video filters that the error may be allowed to increase with frequency. The display provides the deviations directly, which saves a great deal of

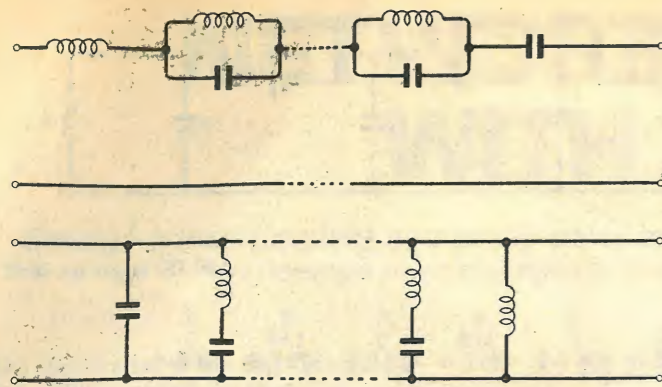


Fig. 4. Pair of canonical two-terminal reactance arms.

tedious plotting especially in the earlier stages of the process, since it is simple to note the maxima and minima at each stage without drawing the complete curve.

A brief guide to the shape of the delay equalizer responses may be found useful. The first-order network provides a group delay which falls steadily starting from the zero-frequency value. On the other hand, there is a very useful analogy between the response of a second-order section and the amplitude response of a parallel tuned circuit. The parameter K performs much the same function as the Q in the last-mentioned case, and the delay maximum roughly corresponds with FR .

The seventh-order elliptic function lowpass filter given in Fig. 1 may be found useful for a trial run. The loss is about 4dB at 5MHz. The delay equalizer parameters do not represent an optimum, but merely a suggestion for an initial trial. The component values are listed in the order of insertion into the program, with the capacitors provided in exponential notation, thus avoiding strings of zeros.

Before leaving the subject of insertion loss calculation, one still has to deal with the problem of network branches containing more than two reactances such as may be encountered in bandpass filters. In fact it can be very easily solved by the use of dummy branches as the following examples will make clear.

Fig. 2(a) shows a bandpass filter with a bandwidth of 10MHz, a mid-band frequency of 12MHz, and rejection frequencies at 8 and 24MHz. The series arm has the form of two parallel tuned circuits in series, i.e. a total of four reactances, usually the maximum number likely to be met with. The device in this instance is to add between points A and B a shunt inductor of such a magnitude that it cannot possibly have any practical effect on the loss and delay responses, Fig. 2(b). The original three-branch network is now converted to a five-branch ladder which can easily be handled by the program.

A shunt branch yields to similar treatment, as is illustrated by the bandpass filter of Fig. 3(a). This has a bandwidth of

3MHz with a mid-band frequency of 2MHz and a rejection frequency at 0.8MHz. Because it has a bandpass characteristic it is possible to employ the analogue of Fig. 2(b), that is the series insertion of a very large capacitor, Fig. 3(b). The resulting five-branch ladder can now be treated normally. In this instance, there is an alternative which applies equally to lowpass structures, that is the insertion of a parallel tuned circuit with a zero-valued inductor and a capacitor of any nominal size, Fig. 3(c).

It is worth stressing that the dummy branch technique can always be applied, subject to the limitation of a total of ten branches imposed by the present program. The justification for this is the theorem that a two-terminal reactance arm can always be transformed into one of the two configurations of Fig. 4 (ref. 1), for which reason they are sometimes called canonical networks. Of course, not all of the inductors and capacitors have to be present, so the two examples given above are obviously included. It will sometimes involve the transformation of one configuration into another, but this is comparatively simple provided a reference table of equivalent circuits is available².

References

1. R. M. Foster, Reactance theorem. *Bell System Technical Journal*, vol. 3, April 1924, pp. 259-67.
2. A. Zverev and H. Blinichikoff, Network transformations for wave filter design. *Electronics*, June 26 1959, pp. 52-4.

To be continued.

Communications crisis—a reply

On our news pages this month is a criticism of the Government's liberalisation programme for the telecommunications industry. John Butcher, the Parliamentary Under Secretary of State for Industry has made the following reply, listing the progress made to date.

A licence was granted in February to Cable and Wireless PLC on behalf of the Mercury Communications Limited to run a telecommunications system in the UK the first independent system of its kind outside North America. By the middle of next year the first subscribers should be connected to Mercury, surely an astonishing achievement in the time.

On the liberalisation of attachments progress has been remarkable. Already some 50 attachments, including about 25 telephones, 20 modems and five telex teleprinters can be supplied competitively which under the old regime would either have been completely unavailable or supplied only through BT.

November 1981 - Interim approved scheme for extension telephones from BT's special range. The latter have been added to since then and all of BT's special range telephones can now be supplied in competition with BT. The first approvals under this interim scheme have now

been made and more will follow shortly.

May 27 - An extension of this scheme to include callmakers, repertory diallers and apparatus incorporating integral modems. The Department is now considering applications for further evaluation. Now that BSI's new laboratory can undertake some of the test work, it should be possible to deal with more telephones more quickly.

March 31 - Orders made requiring apparatus to be marked to tell customers whether or not it is approved for connection to BT's networks. This is vital information for users if they are to choose apparatus that will not cause damage and produce inferior service.

Six draft standards have been written and made available for public comment in record time and further drafts will follow shortly. So far all standards are meeting their target dates.

May - The British Approvals Board for Telecommunications (BABT) was incorporated and will begin to accept applications for approval when the first standards are published.

The Department and BT have agreed on arrangements allowing BT's present suppliers of telex teleprinters to supply the models they now sell to BT direct to customers. This makes five

models available competitively if the manufacturers wish to take advantage of this arrangement.

"The Government has a duty" he continued "to make sure that apparatus connected to BT's network does not endanger consumers who use this equipment or BT's engineers and does not impair the quality of service that the network is able to provide to all. Much of the preparations that have been made over the past 12 to 18 months have been aimed at avoiding such dangers.

"In many cases little of this progress is visible to the outside observer but all of it is necessary if liberalisation is to be fair and to work. Critics do not do justice to the immense amount that has already been achieved."

"Since April private operators have been able to apply to the Department of Industry for a licence to provide services over the network. The provision of these value added network services (VANS) will help to satisfy the demand more quickly than at present and encourage the growth of a wider range of services, providing jobs and helping business in Britain to become more competitive.

COST-EFFECTIVE ELECTRONIC IGNITION

The popularity of Rod Cooper's ignition circuit design, published in the March issue, led to many requests for a component location diagram. In response, here is a component layout - regrettably held out of the last issue - designed to complement the board pattern originally given. A resistor and decoupling capacitors were omitted from the published circuit, so a corrected version is reproduced herewith, which now corresponds with the board design.

Printed boards to an alternative layout, with components horizontally arranged, is available from M. R. Sagin (see advertisement), who may also be able to supply wound transformers and discharge capacitors. Ferrite and bobbins are also available from Mullard stockists.

The graphs showing the relation between combustion efficiency and spark were originally published in an article entitled Ignition Design Trends by K. Garrett, in *Automotive Engineering*, April-May 1977. Oscilloscope traces were produced from equipment kindly loaned by Hewlett Packard.



Components for ignition circuit

Resistors

1	180
2	10k
3	180
4	33M
5	270
6	180
7	4.7k
8	2.2k
9	27k
10	2.2k
11	22k
12	1.2k
13	1.2k
14	330

Transistors


1	TIP3055,MJE3055
2	BFY52
3	2N3903
4	2N3903
5	TIP2955,MJE2955
6	BFY52

Capacitors

1	470n 1kV polypropylene (RS)
2	10n
3	1n 1kV polypropylene
4	470p
5	5n polyester
6	5n polyester
7,8	100 to 500µ10V electrolytic

Diodes

1	1N4001
2	1N4007
3	1N4007
4	1N4001
5	1N4148
6	1N4001
7	1N5402 or similar 3A rec.
Zeners 4.7 and 10V 400mW	

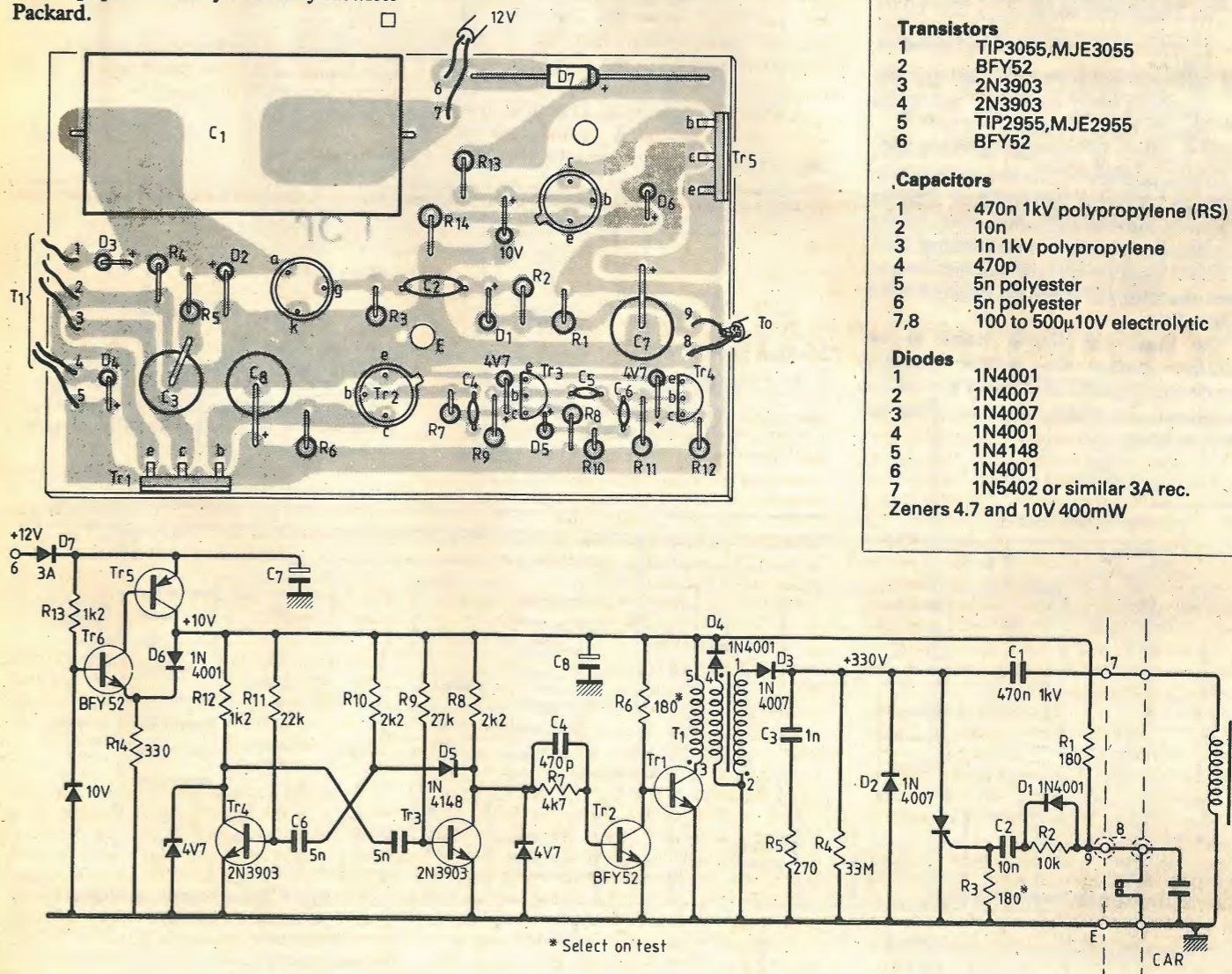

DESIGNING WITH MICROPROCESSORS

Step-by-step procedures for implementing microprocessor systems with commercially-available i/o chips – illustrated by a design problem – conclude this series of articles.

The most effective design strategy is to choose those i/o chips whose terminal characteristics can be programmed to match those of the peripheral in question. But such an objective however would be unrealistic because in practice the microprocessor system will have its own programmable i/o chips already interfaced to the microprocessor chip, as illustrated in Fig. 1. In situations like this a good starting point is to derive a simplified programming model of the i/o chip, omitting those features that are not likely to be used. Initially, a programming model should contain the ports, typically two per chip, the control and status registers. Programming models of the Intel 8155, p.i.a. and v.i.a. are shown in Fig. 2, 3 & 4.

The next items to be specified are

- 1 – how the interface initiates an m.p.u. read operation for moving data into a microprocessor (from peripheral 1 in Fig. 1)
- 2 – how the p.i.o. chip signals that the requested read operation has taken place to the interface.

For example in the case of the p.i.a., when programmed with control word 26 to move an item of information from a peripheral into the microprocessor, all the interface has to do is to pull terminal CA1 in Fig. 3 high. When the microprocessor reads the item the signal on terminal CA2 is pulled low.

The third and fourth items to be specified involve the reverse process, namely moving data from the m.p.u. into a peripheral, in which case the designer needs to know

by D. Zissos and Jane Pleus

- 3 – how the interface initiates an m.p.u. write operation for moving data from the microprocessor to a peripheral m.p.u. (peripheral 2 in Fig. 1)
- 4 – how the p.i.o. chip signals that the requested write operation has taken place.

In the case of the Intel 8155 chip, when programmed with control word 99 data is

requested from the m.p.u. by pulling the STROB terminal in Fig. 2 low when the m.p.u. responds when the requested item of information has been loaded into the 8155, the signal on terminal BBF changes to 1.

5 – the final item to be specified is the status flip-flop for each of the ports, as this is the signal looked at by the programmer in the test-and-skip mode.

For example in the case of the 8155, SFFA

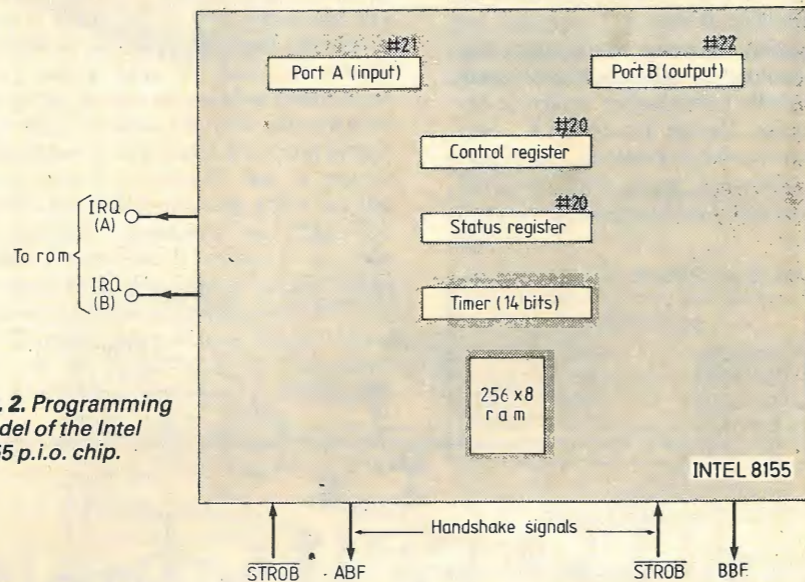


Fig. 2. Programming model of the Intel 8155 p.i.o. chip.

Control register (write only) #20						Status register (read only) #20							
Timer	EI (B)	EI (A)	Handshake signals	Data direction bit (B)	Data direction bit (A)	Not used	TMR	EI (B)	SFFB	IRQ (B)	EI (A)	SFFA	IRQ (A)

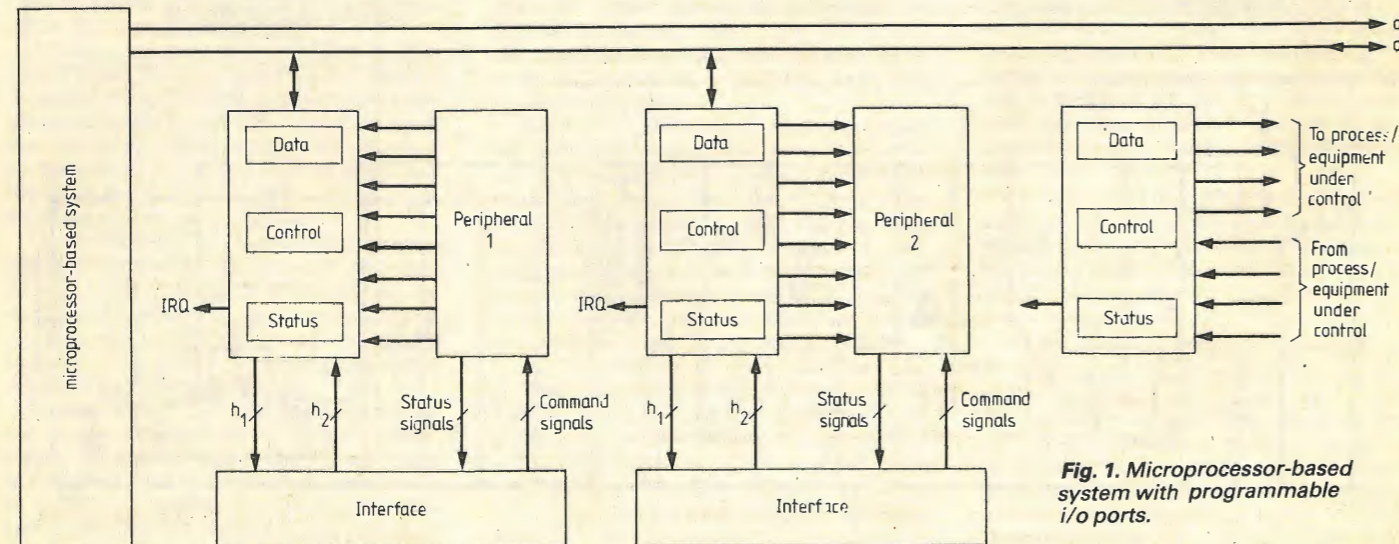


Fig. 1. Microprocessor-based system with programmable i/o ports.

Mnemonic and hex listings of the PRINT problems using programmable i/o chips and test-and-skip.

8085 & 8155				6800 & PIA				6502 & VIA				Comments	
Mnemonics	Machine code Address	Opcode	Operand Label	Mnemonics	Machine code Address	Opcode	Operand Label	Mnemonics	Machine code Address	Opcode	Operand Label		
LXI SP, 20C8	2020	31 C8	20									Initialize	
CALL IOPRT	23 CD	00 20		JSR IOPRT	0200	BD 01 00		JSR IOPRT	0300	20 00 02		--	
LXT H, 2080	26 21	80 20		LDX #0300	03 CE	03 00		LDX #00	03 A2	00		--	
MVI B, n	29 06	n		LDAB #n	06 C6	n		LDY #n	05 A0	n		--	
DCR B	2B 05		X0: DCRB	DEC B	08 5A		X0: DEY	07 88				Decrement character count	
JM X2	2C FA	3D 20		BMI X2	09 2B	13		BMI X2	08 30	11		If no more characters, go to X2	
IN 20	2F DB	20	X1: IN 20	LDAA F003	0B B6	F0 03	X1: LDA A00D	LDA A00D	0A AD	0D A0		Read status register port	
ANI 10	31 E6	10		ANDA #80	0E 84	80		AND #10	0D 29	10		Erase all but status flip-flops	
JZ XI	33 CA	2F 20		LDAA 00, X	12 A6	00		LDA 0400, X	11 BD	00 04		If data not printed, go to X1	
MOV A, M	36 7E			STAA F002	14 B7	F0 02		STA A000	14 8D	00 A0		Otherwise, get next character	
OUT 22	37 D3	22		LDAA F002	17 B6	F0 02						Print	
				INX H	39 23			INX	1A 08				Dummy clear to clear SFF of PIA
JMP X0	3A C3	2B 20	X2: RST 1	JMP X0	1B 7E	02 08		JMP X0	18 4C	07 03		Go to X0	
				RST 1	3D CF			SWI	1E 3F				Return to monitor

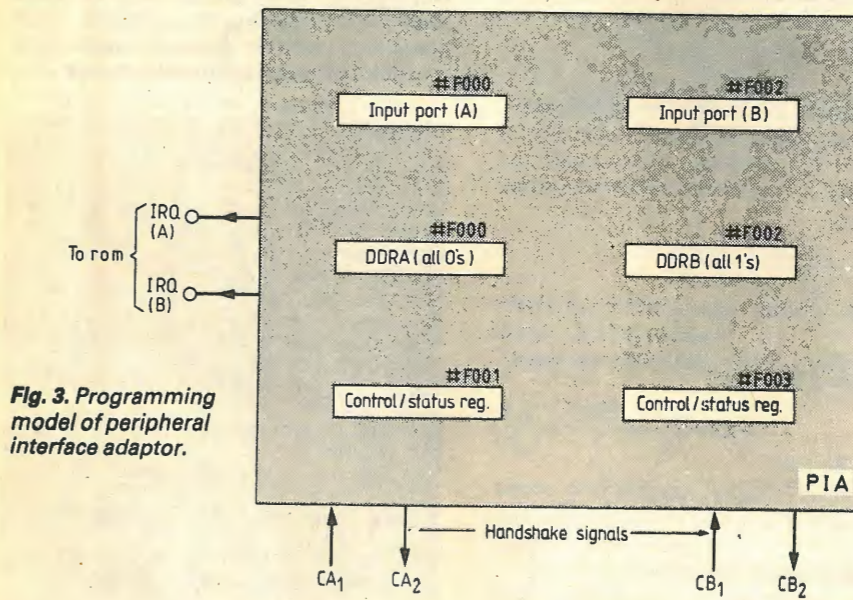


Fig. 3. Programming model of peripheral interface adaptor.

Control/status register A				Control/status register B			
Status ffs SFFA	CA2 control	DDRA access	CA1 control (EI)	Status ffs SFFB	CB2 control	DDRB access	CB1 control (EI)
Read only				Read only			

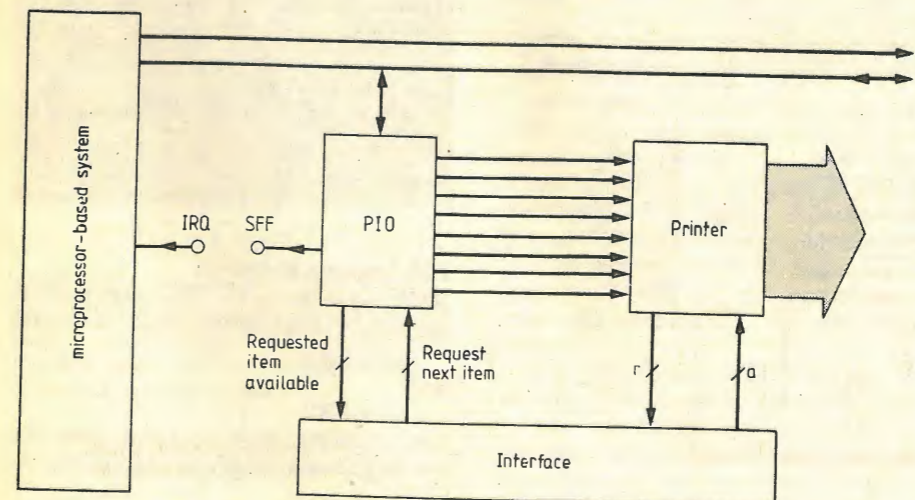


Fig. 4. Block diagram of the PRINT problem.

and SFFB are bits 1 and 4 of the status register – see Fig. 2. Status flip-flop signals are normally made available on terminals for use as interrupt flags if desired. Such flags can be disabled by program; bit 2 in Fig. 2, when 0 disables interrupt flag IRQ(A).

Programming models of the 8155, the p.i.a. and v.i.a. are shown in Figs 2 & 3.

Design problem

Objective: to consolidate the design steps described in the previous article.

Using programmable i/o chips, design a test-and-skip system that would allow the programmer to print a block of characters stored in consecutive memory locations. Implement the design using an action/status character printer and (a) the 8155 interfaced to the 8085 and (b) the p.i.a. interfaced to the Motorola 6800.

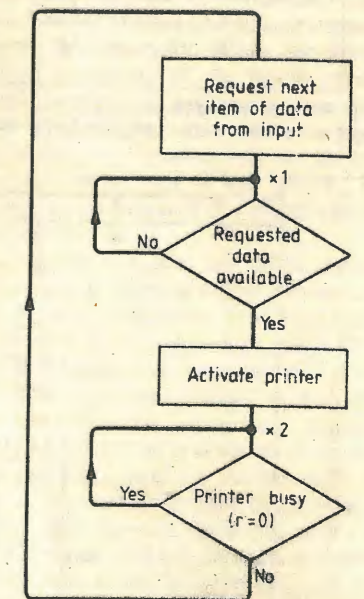


Fig. 5. Flow-chart of our solution to the PRINT problem.

Solution

Handshake signals Fig. 1

h1 - 1 indicates that the port is full (has new data) and 0 that the port is empty (data has been read).

h2 - 0-to-1 change requests an m.p.u. read cycle.

h3 - 0-to-1 change requests new data from the m.p.u.

A test-and-skip system that transfers blocks of data of specified length, byte-by-byte, from memory to a peripheral device through an i/o port using a microprocessor-based system with at least one programmable i/o port is shown in the

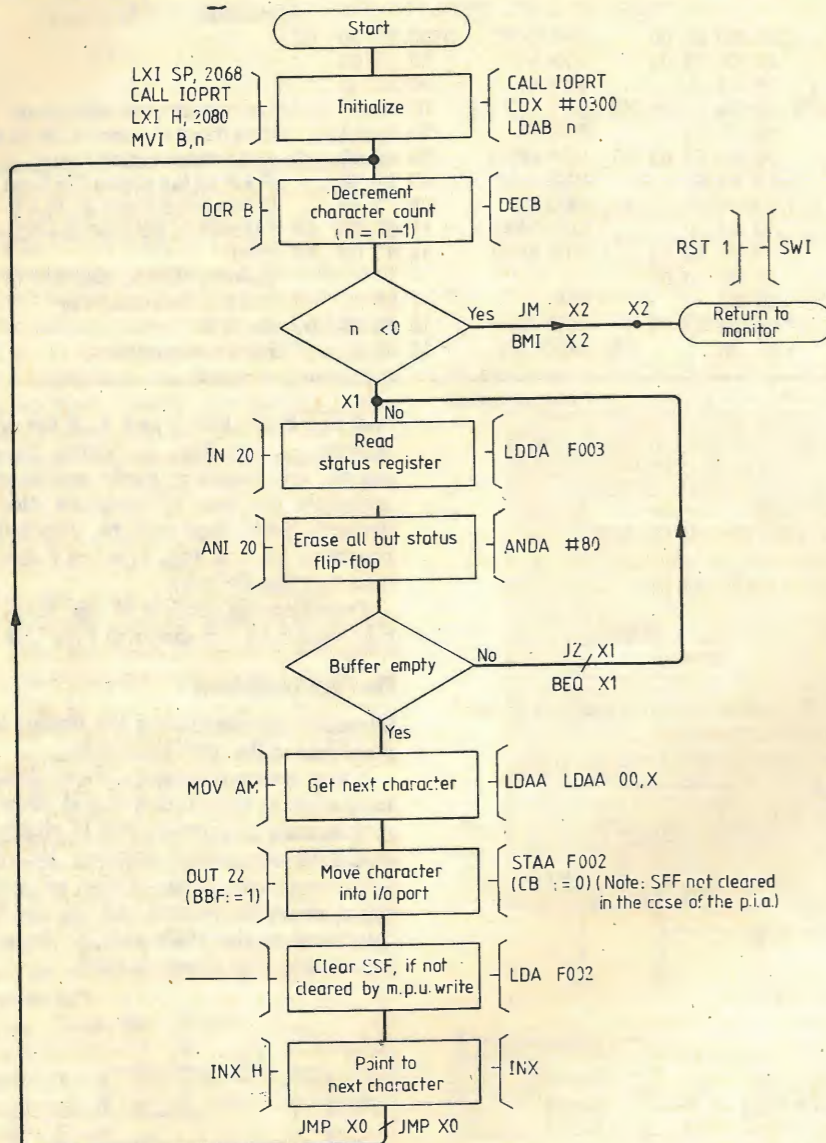


Fig. 6. Programming flowchart of the PRINT problem using programmable i/o chips and test-and-skip

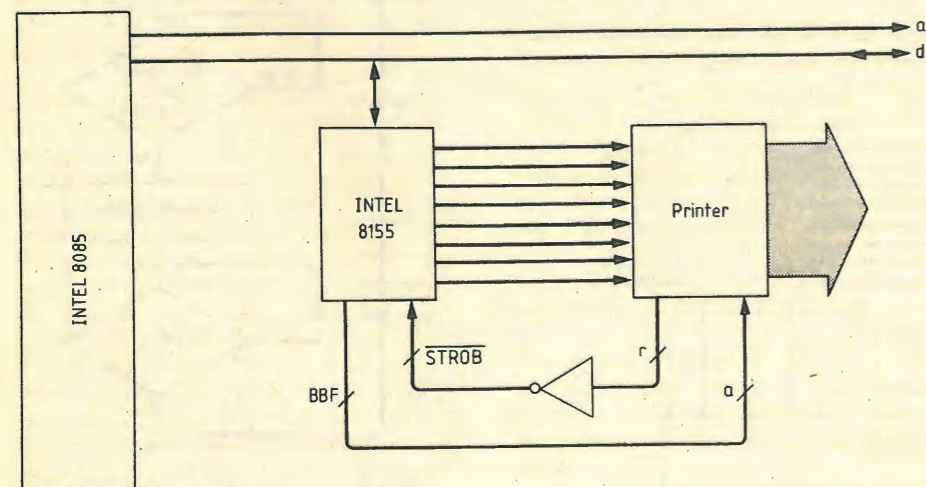


Fig. 7. 8155 implementation of the PRINT problem.

block diagram of Fig. 4, derived directly from Fig. 5 of the previous article. Its step-by-step operation is shown in the flow chart of Fig. 5. The hardware design consists of implementing the interface equations derived for each of the p.i.o. chips. The software design is the self-explanatory programming flow chart of Fig. 6. Ignore at this stage the statements to the sides of the boxes.

8155 implementation

By direct reference to the data sheet of the Intel8155 and to the definitions of handshake signals h1 and h2, we obtain

h1 = BBF
and
h3 = STROB.

The implementation of these equations constitutes the hardware component of our solution, Fig. 7.

Next refer to the 8085 instruction set to derive the mnemonic statements that implement the flowchart in Fig. 6. For ease of reference we list them to the left of each box. Finally, we tabulate these statements with the corresponding machine codes and comments on page 77.

8155 data

Programming model, Figure 2. The control word 0A disables the interrupt terminals and to program the 8155 i/o chip to function in the following way.

Section A - input port
An m.p.u. read is requested by a 1 to 0 change in STROB
When m.p.u. responds (reads) ABF* changes to 0
ABF pulled high by a 1 to 0 change on STROB
ABF pulled low by an m.p.u. read of port A
Status flip-flop (bit 1 of the status register)
set by a 1 to 0 change on STROB
reset by an m.p.u. read of port A

Section B - output port
New data requested from m.p.u. by a 1 to 0 change on STROB
When m.p.u. responds (writes) BBF* changes to 1
BBF* pulled high by an m.p.u. write operations
BBF pulled low by a 1 to 0 change on STROB
Status flip-flop (bit 4 of the status register)
set by an m.p.u. write operation
reset by a 1 to 0 change on STROB

*ABF = 1 indicates new data in input port
*BBF = 1 indicates new data in output port

PIA implementation

Referring to the p.i.a. data sheet and the definitions of handshake signals, we obtain

h1 = CB2
and

h2 = CB1.

Implementing these equations gives the pia implementation of our solution, Fig. 8.

continued on page 80

ELECTRIC FIELDS IN A SOLENOIDAL COIL

- often forgotten, more often misunderstood

The time-varying magnetic field in a coil gives rise to electric fields that in turn determine the terminal or circuit properties of the coil

*by F. S. Chute
and F. E. Vermeulen

Since the time of Michael Faraday's experiments, researchers have sought to understand the electromagnetic behaviour of the solenoidal coil, but a complete field solution has proved a difficult and elusive goal. While it is well known that the magnetic field within a long, multi-coil is predominantly axial and azimuthally symmetric, the associated electric fields are less clearly defined. However, a few fundamental points can be made regarding these electric fields without having to resort to a complete boundary-value solution.

When excited by an alternating current, the time variations of the axial magnetic field within the coil must, in accordance with Faraday's law of induction, produce an electromotive force around any closed loop linking the magnetic field. The result is an induced electric field in the circumferential direction, and it is just this field that gives rise to the eddy current that circulates whenever the coil is wound around a core of lossy material. However, the existence of this circumferential electric field at the surface of the coil causes a redistribution of charge along the helical conductor forming the coil, such that the negative charge is concentrated towards the opposite end of the coil. This separation of charge creates a secondary electric field that in the interior region of a long solenoid is predominantly axial. The redistribution of charge is precisely such that the sum of the magnetically induced circumferential electric field and the secondary axial electrical field arising from the charge separation is just equal to zero along the surface of the coil winding.

The relative magnitudes of these circumferential and axial components of the electrical field are easily estimated for a long solenoid of length l and radius a , comprised of N turns. If the magnetic flux linking a cross section of the coil of area πa^2 is defined as Φ , the electromotive force around a closed loop of radius a must in phasor form be given by

$$e.m.f. = j\omega\Phi$$

where ω is the angular frequency. An average value for the circumferential electric field at radius a can now be obtained by dividing this e.m.f. by the circumference of the coil. In other words,

$$E_{\phi a} = \frac{j\omega\Phi}{2\pi a}$$

where $E_{\phi a}$ is the average induced circum-

ferential electric field at the surface of the coil. Alternatively, since the terminal voltage, V , of the coil is just N times this e.m.f.

$$E_{\phi a} = \frac{V}{2\pi a N}$$

Neglecting end effects, an average value for the axial electric field, at radius a , can be obtained by dividing the terminal voltage by the length of the coil. Thus,

$$E_{za} = \frac{V}{l}$$

where E_{za} is the average value of the axial electric field at radius a . Taking the ratio of E_{za} and $E_{\phi a}$ yields

$$\frac{E_{za}}{E_{\phi a}} = \frac{2\pi a N}{l} = \frac{2\pi a}{d} = \cot\psi \quad (1)$$

where d is the separation between turns and ψ is commonly referred to as the pitch angle of the winding.

For coil configurations commonly used this pitch angle is only a few degrees and the secondary axial electric field is typically more than an order of magnitude greater than the circumferential electric field! Moreover, the axial field E_z is nearly independent of distance from the axis of the coil, whereas the circumferential electric field E_{ϕ} decreases to zero at the coil centre. At interior points then, the dominating influence of the axial electric field will be even more pronounced than near the surface of the coil winding.

All too often this surprising result is not fully appreciated although it was pointed out as early as 1928 by Townsend¹ in conjunction with an investigation of gaseous discharges, and again in 1969 by Contaxes². It is of interest to note that both of these authors comment, more than 40 years apart, that the existence of such a large axial electric field is remarkably unknown.

It is only by virtue of the fact that the secondary electric field of the coil (whose source is the charge distributed along the winding) is much larger than the circumfe-

rential electric field (produced directly by the time-varying magnetic field), that a unique value of potential difference between the terminals of the coil can be defined. For a loosely wound coil with a large pitch angle ψ , the magnitudes of the two fields are more nearly equal and no unique value will exist for the terminal voltage. In this case the measured value of potential difference will depend upon the placement of the leads of the voltmeter that is used to measure the voltage across the coil.

In some earlier work^{3, 4}, the authors have described a technique for visually displaying electrostatic fields and electromotive force by utilizing the heat-sensitive colour changes of cholesteric liquid crystals. In this technique, Mylar sheets coated with encapsulated liquid crystals are bonded to a sheet of Teledeltos resistive paper. Currents induced in the resistive paper in the presence of an electric field will cause heating, and produce a temperature variation that is characteristic of the distribution and intensity of the electric field vectors lying in the plane of the resistive paper. The apparent colour of the liquid crystal sheets used by the authors³ is black below about 25°C. Between 25°C and 30°C, the colour of the sheet changes with temperature from red, through yellow and green, to blue at about 30°C. Above 30°C, the apparent colour is again black. Regions of a uniform coloration represent regions of constant temperature or field intensity. While the limited thermal sensitivity of the liquid crystals and their nonlinear temperature response make serious quantitative measurement impractical, the liquid-crystal display does serve to provide the viewer with an immediate appreciation of the overall electric field distribution.

To display the axial and radial electric fields of a coil carrying a time-varying current, a sheet of resistive Teledeltos paper was bonded to a 3.2 mm thick, 60 x 60cm sheet of Perspex with spray adhesive. Four 30 x 30 cm sheets of liquid crystal were then similarly bonded to the resistive paper. This three-layer sandwich combination was then carefully drilled with 40 holes of 2.5 mm diameter to serve as a support plate for a 20 turn coil of No 14 A.W.G. copper wire. A continuous length of wire was then threaded through the holes in the support plate to create a coil of length 40 cm, diameter 10 cm, and turn spacing 2 cm, having a pitch angle so that $\cot\psi = 15.7$. The coil, which has an induc-

*Department of Electrical Engineering
University of Alberta

NEW PRODUCTS

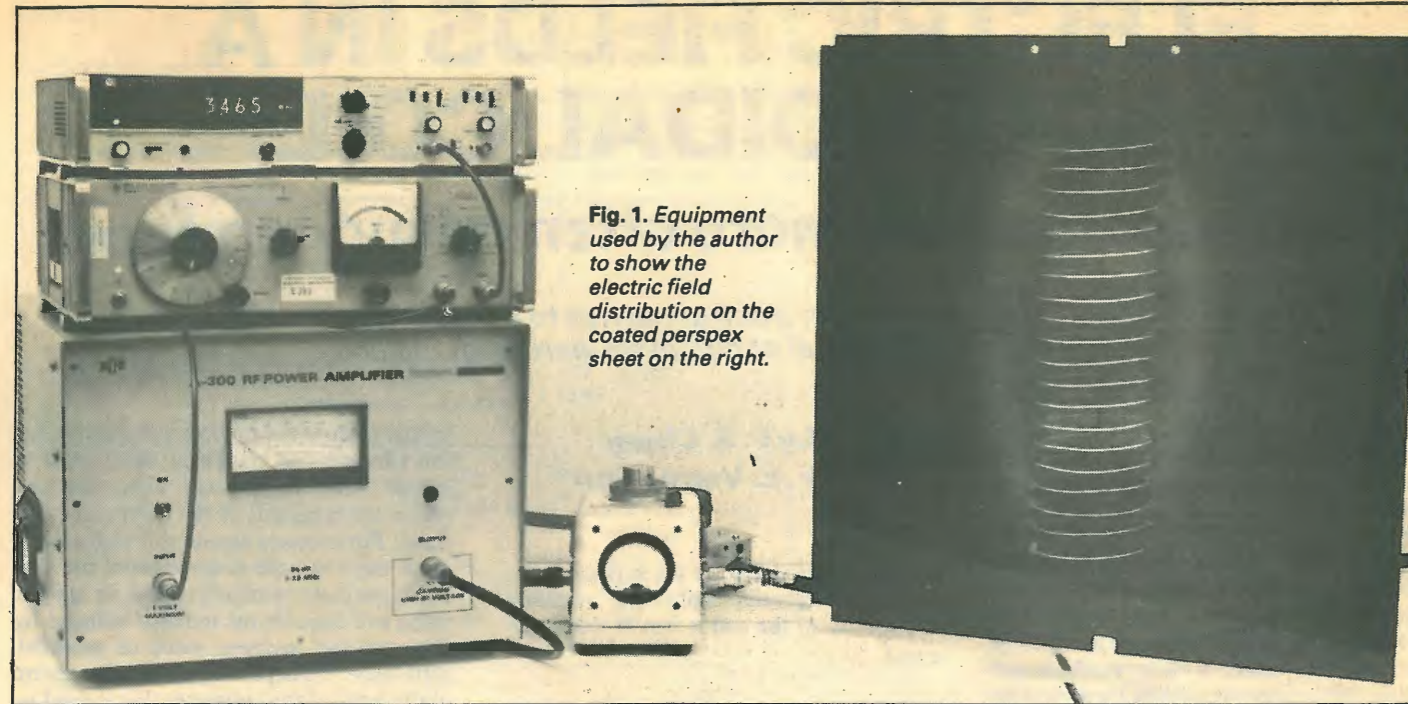


Fig. 1. Equipment used by the author to show the electric field distribution on the coated perspex sheet on the right.

tance of about $12 \mu H$, was series-connected to high-voltage capacitors to resonate at 3 MHz. The coil circuit was fed at 3 MHz from an Electronic Navigation Industries A-300 RF Power Amplifier driven by a Hewlett-Packard 651A Test Oscillator. Figure 1 is a photograph of the apparatus showing the distribution of the dominant secondary electric field surrounding the coil.

When the coil is energized, the liquid crystal sheets change colour almost instantly, in response to the current induced by the radial and axial electric fields around the coil, to produce the display.

The interior region is a uniform shade of blue except near the coil extremities, clearly indicating the uniform nature of the field within the coil. Indeed, the temperature differs by less than $2-3^\circ C$ over the entire central region of the photograph, which ranges through various shades of blue to shades of green in the original display. Near the ends of the coil, where all the field solutions quoted in this paper are modified by end effects, and hence, are only approximate, the axial electric-field intensity has decreased just enough so that not enough heating is produced to cause a perceivable liquid crystal response.

References

- 1 J. S. Townsend and R. H. Donaldson, "Electrodeless discharges," *Phil. Mag. J. Sci.*, vol. 5, pp. 178-191, 1928.
- 2 N. Contaxes and A. J. Hatch, "High frequency fields in solenoidal coils," *J. Appl. Phys.*, vol. 40, No. 9, pp. 3548-3550, 1969.
- 3 F. S. Chute and F. E. Vermeulen, "A visual demonstration of two-dimensional electrostatic fields," *Amer. J. Phys.*, vol. 24, pp. 1075-1077, Dec. 1974.
- 4 F. E. Vermeulen and F. S. Chute, "Visual demonstration of electromotive force and induced current," *Amer. J. Phys.*, vol. 45, pp. 309-310, Mar. 1977.

continued from page 78

The Motorola 6800 statements that implement the flow chart are obtained by referring to the 6800 instruction set (see Sept. 1980 issue). As in the case of the 8085, we list them in mnemonic form to the right of each box, and then tabulate them with their machine code, page 77.

Note that a write operation does not reset the status flip-flop, so in the case of the p.i.a. we need to execute a dummy read to clear SFF.

Invitation. Additional problems and solutions in this area are available from Professor D. Zissos, Department of Computer Science, University of Calgary, Calgary, Canada T2N 1N4.

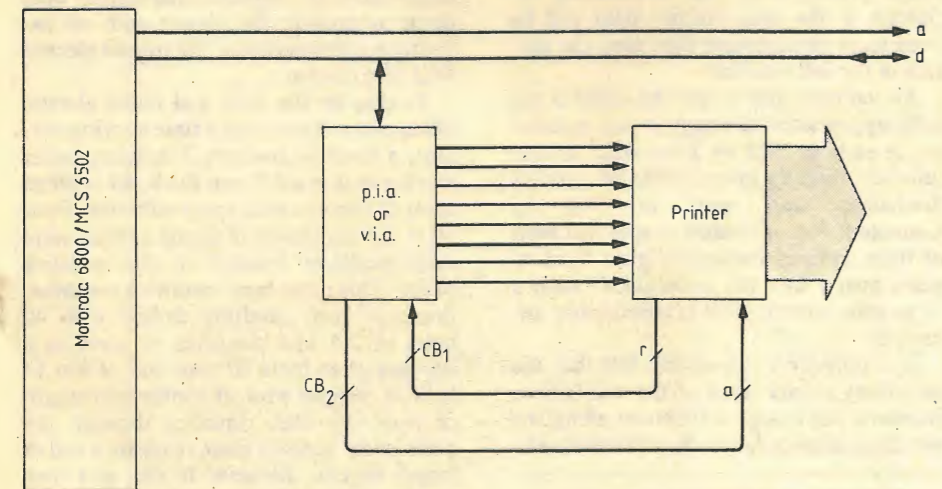


Fig. 8. PIA implementation of the PRINT problem.

PIA data

Programming model, in Fig. 3. Control word 26 for both sections disables the interrupt terminals and programs the PIA chip to function in the following way.

Section A - input port

An m.p.u. read is requested by a 0 to 1 change on CA1
When m.p.u. responds (reads) CA2 changes to 0
CA2 pulled high by a 0 to 1 change on CA1
CA2 pulled low by an m.p.u. read of port A
Status flip-flop (bit 7 of control/status register)
set by a 0 to 1 change in CA1
reset by an m.p.u. read of port A

Section B - output port

New data requested from m.p.u. by a 0 to 1 change of CB1
When m.p.u. responds (writes) CB2 changes to 1
CB2 pulled high by a 0 to 1 change on CB1
CB2 pulled low by an m.p.u. write into port B
Status flip-flop (bit 7 of control/status register)
set by a 0 to 1 change in CB1
reset by an m.p.u. read of port B

LOW-COST PRINTER FOR HOME COMPUTERS

Graphics and lower-case letters are possible on the Amber 2400 printer costing £69.95 excluding v.a.t. The unit prints 24 characters per line on a 58mm-wide plain-paper roll some 90 feet long. Data rates are selectable between 75 and 9600 bits/s. Four horizontally-aligned print solenoids oscillate from side to side, each covering $\frac{1}{4}$ of the paper width, under control of the unit's microcomputer, which also handles software routines and allows data input options. The 2400 is primarily intended for use with home computers. Amber Controls Ltd, Central Way, Watworth Industrial Estate, Andover.

WW301




WW301

FREQUENCY MEASURING D.M.M.

The main difference between this and Fluke's previous hand-held digital multimeters is the inclusion of a frequency measurement function - one of a number of additional facilities made possible by the inclusion of a Sharp 4-bit microprocessor and a CMOS measurement-processing circuit designed and manufactured 'in house'. Frequencies from 12Hz to 200kHz are measured on the 8060A in four automatically-selected

ranges, with 0.01Hz resolution on the lowest range (200Hz), and indicated on a 4½-digit l.c.d. Alternating voltages may be displayed directly in V r.m.s., in dBm (referred to 600 ohms), or in volts or decibels relative to a previously stored reference. This offset facility may be used with other measurement functions. Direct and alternating voltage, a.c. and d.c. functions are in five ranges, resistance in seven, and decibels in four. Basic d.c. accuracy is 0.04% and sensitivities are 10µV, 10nA and 10mΩ. A 200nS range may be used to measure resistances up to 10GΩ. Further functions include diode test, audible/visual continuity test and self test. Normally, input impedance on the direct-voltage ranges is 10MΩ, but on the 200mV and 2V ranges, an input impedance of greater than 1GΩ may be selected. Fluke (GB) Ltd, Colonial Way, Watford, Herts WD2 4TT.

WW302

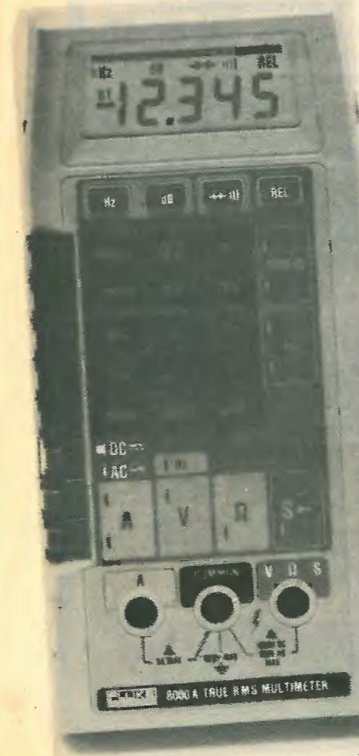

WIRELESS WORLD AUGUST 1982

the relay-contact ratings are 240V and 1A. CIL Microsystems Ltd, Decoy Road, Worthing, Sussex BN14 8ND.

WW303

64K EPROM PROGRAMMING ADAPTER


Any eprom programmer suitable for Texas 2532-type devices may be used to program 64K eproms by adding an adapter made by Elan

Digital Systems. The E6 adapter has a z.i.f. socket for 2564 or 2764 devices and a ribbon cable terminated by a plug which fits into the existing programmer. Each half of the 64K, selected by a switch, is programmed separately by the existing programmer in the usual manner. All automatic test or editing functions of the existing programmer are retained and an additional feature allows Intel 2732 or 2732A i.c.s to be read through the adapter. Elan Digital Systems Ltd, 16-20 Kelvin Way, Crawley, West Sussex RH10 2TS.

WW304


CMOS R.F. SWITCH

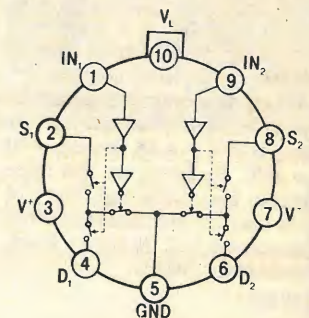The IH5341 is a dual-channel r.f. and video switch with t.t.l. and c.m.o.s.-compatible control inputs, manufactured by Intersil. Each channel has three switch elements, connected in a series/shunt formation, giving an $R_{DS(on)}$ of less than



75Ω, flat response from 0 to 100MHz and 70dB isolation at 10MHz in the off state. Isolation between the two channels is greater than 60dB at 10MHz. Supply current is less than 1µA and switching speeds are 150ns, on and 80ns, off, giving break-before-make operation. A TO-100 package is used. Intersil Datel Ltd, 9th Floor, Snamprogetti House, Basingstoke, Hants.

WW305

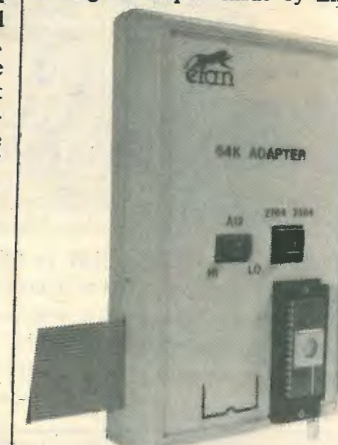

WW303



ANALOGUE/SWITCHING INTERFACE

This IEEE-bus-controlled interface, manufactured by CIL Microsystems, provides eight analogue inputs, four analogue outputs and four relay-activated change-over switches, for general-purpose control and monitoring applications in research and industry. A concise set of ASCII commands are handled by a 6502 microprocessor, which can also run specific operating programs loaded from the main computer into an optional 4K of ram. Two versions of the PCI 6000 are available, one with eight-bit resolution and one with 12-bit resolution. Facilities include differential inputs and programmable gain, and

NEW PRODUCTS

EPROM ERASER

Both models in Northern's eeprom eraser range cost under £60 excluding vat and can be used to erase up to six devices at once. The latest of these, the UV1T, is basically the same as the earlier UV1B, but with a 10 to 60-minute time switch fitted. Lamp life is quoted as being in excess of 3000h and all models, i.e., those mentioned for 220 to 240V operation and two others for 110 or 240V mains, comply with appropriate British Standards. Northern Electronics Ltd, 51 Arundel Street, Mossley, Lancs OL5 0LS.

WW306

CODED ROTARY SWITCHES

Miniature rotary switches with ten or 16 positions, giving b.c.d. or hexadecimal outputs, have been added to the Elma range of ceramic wafer switches marketed by Radiatron. Measuring 10 by 10 by 11mm, these switches can be obtained for mounting either horizontally or vertically on a p.c.b. and with either a screwdriver slot or spindle. Gold-plated contacts are used, giving a contact resistance of less than 50mΩ and the contact rating is 50V at 0.2A between -40 and 85°C. Radiatron say that these switches have a life expectancy of more than 10⁴ rotations. Radiatron Components Ltd, 76 Crown Road, Twickenham, Middx.

WW307

32 × 8 BIPOLAR PROM

A 'washed emitter' process has been used to produce two 256-bit Schottky bipolar proms with typical access times of 9ns. One, the 63S080 has open-collector outputs and the other, the 63S081 has three-state outputs. Applications of these 32 × 8-bit proms include address decoders, priority encoders and random-logic elements in high-speed systems. Monolithic Memories Ltd, Lynwood House, 1 Camp Road, Farnborough, Hants GU14 6EN.

WW308



DISPOSABLE TEMPERATURE INDICATORS

Adhesive dots and strips for recording maximum temperatures are available from Cobonic Ltd. Within a second of reaching the temperature marked on it in both °C and °F, one of five different areas on the labels, or one area on



the dots, changes irreversibly from white to black. There are 40 different temperature levels in the range, from 40 to 260°C, and each sensitive area changes colour at within 1% of the specified temperature. These products are useful for monitoring and recording maximum temperatures in hazardous and inaccessible areas. Cobonic Ltd, Lantern Yard, Ludlow Road, Guildford, Surrey GU2 5NW.

WW309

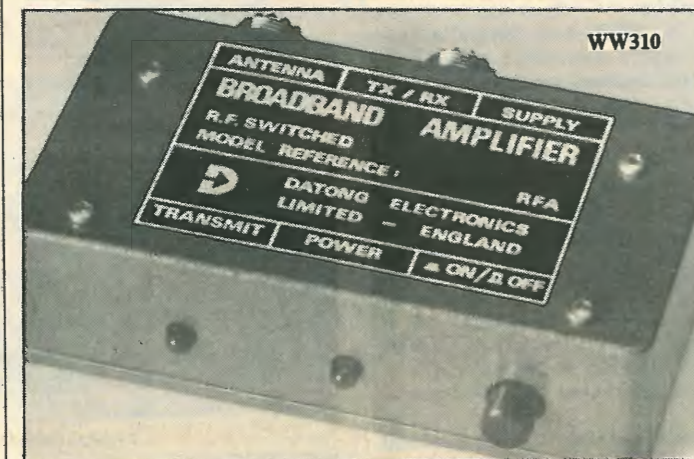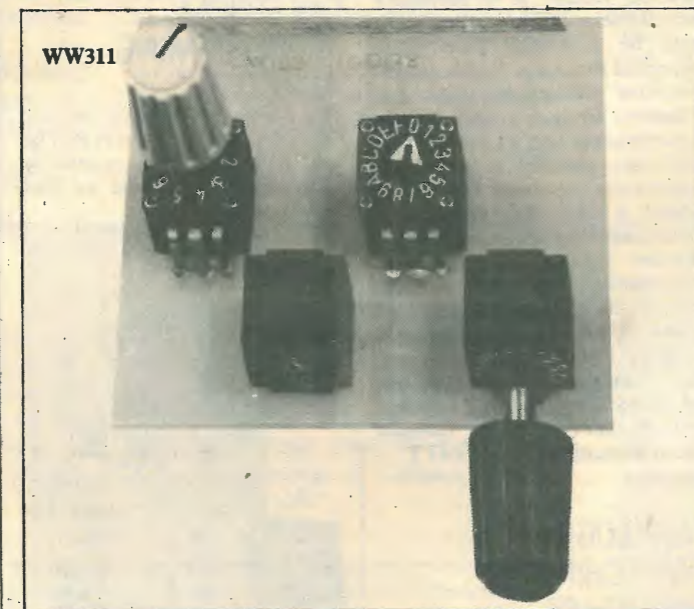

BROADBAND R.F. PREAMPLIFIER

An r.f. preamplifier providing 9dB gain and suitable for use with low-power transceivers in the range 5 to 200MHz can be obtained from Datong. Send/receive switching is automatic, using r.f. sensing and an internal bypass relay, and the unit is claimed to handle large signals well (intercept point + 20dBm). Applications of the model RFA include private mobile v.h.f. transceivers, marine and aeronautical band reception, scanning receivers and antenna-loss compensation. Datong Electronics Ltd, Spence Mills, Mill Lane, Bramley, Leeds LS13 3HE.

WW310

NON-INVASIVE X-RAY METER

An electronic system for non-invasive measurement of radiation intensity and exposure time in diagnostic X-ray equipment has been developed in Sweden by three researchers at the Chalmers Institute of Technology. The equipment,

produced by HB Innova Electronic and called Digi-X, consists of a measurement unit, with parameter, threshold and mode controls, and a detector which is attached to the patient. Peak kilovolt readings are indicated digitally and actual exposure time is calculated from previously stored threshold values selected by the operator. The system may also be used to check beam quality and, with an option, be used to calculate current and mAs values. HB Innova Electronic, Box 25062, S40031 Gothenburg, Sweden.

WW311


METALLIZED-FILM CAPACITORS

Extensions in Rifa's range of metallized polypropylene capacitors have been made to include the PHE425 series. These components, with values ranging from 1.5 to 135nF, are relatively small since they incorporate a 4μm-thick metallized film. Capacitance tolerances are 1%, 2%, or 5% and insulation resistance is claimed to be better than 200GΩ at 20°C, 10V. Working voltages, dependent on value, may be 200, 100 or 63V, direct. Rifa AB, Market Chambers, Shelton Square, Coventry.

WW312

T.T.L.-OUTPUT PATTERN GENERATOR

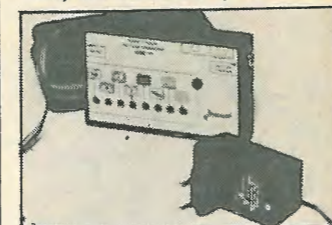A hand-held pattern generator providing t.t.l.-compatible red, green and blue signals for servicing monitors and video displays is manufactured by Sadelta. Eight patterns are produced, colour bars, red, green, blue and white rasters, grey scale, cross-hatch and vertical lines, and the unit may be used for




up to four hours from one battery charge. The RGB11 is intended for servicing of commercial and hobby v.d.us, including video games, and c.c.t.v. monitors. House of Instruments, Clifton Chambers, 62 High Street, Saffron Walden, Essex CB10 1EE.

WW313

Professional readers are invited to request further details on items featured here by entering the appropriate WW reference number(s) on the mauve reply-paid card.

The Professional Choice

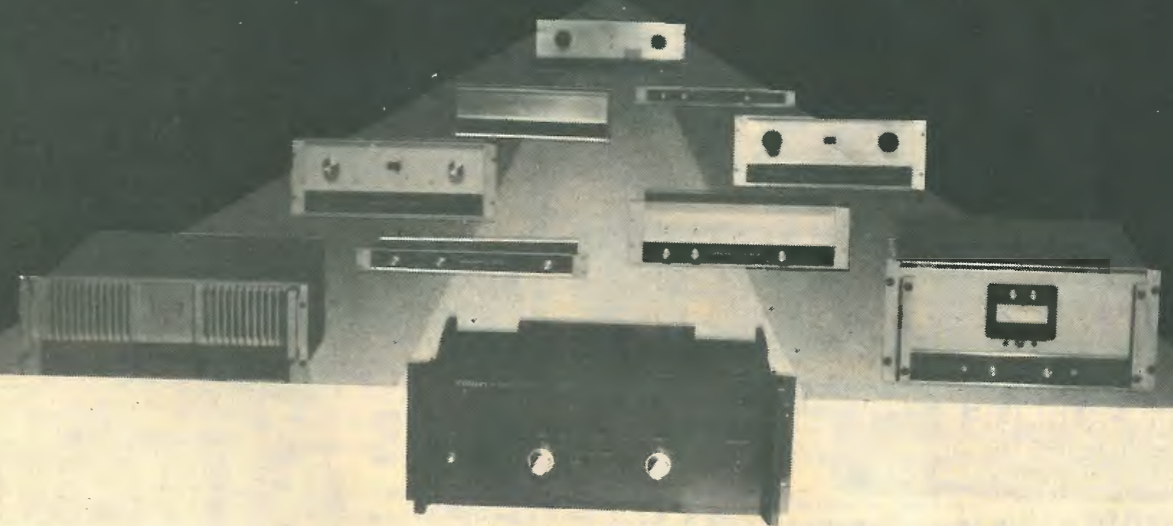

AMCRON 

Since the introduction of the DC300 in 1967, AMCRON amplifiers have been used worldwide - wherever there has been a need for a rugged and reliable amplifier. Their reputation amongst professional users, throughout industry, has made the name of AMCRON synonymous with power amplification. For power you can depend on - choose AMCRON, the professional choice.

For further details contact the UK Industrial distributor:

G.A.S.

G.A.S. ELECTRONICS

16, ST. ALFEGE PASSAGE, LONDON SE10

TELEPHONE: 01-853 5295

TELEX: 923393 LASFR G

U.K. RETURN OF POST MAIL ORDER SERVICE, ALSO WORLDWIDE EXPORT SERVICE

BSR DE LUXE AUTOCHANGER £20
Plays 12", 10" or 7" records, Auto or Manual. A high quality unit backed by BSR reliability. Stereo Ceramic Cartridge, AC 200/250V. Size 13 1/2 x 11 1/2 in. 3 speeds. Above motor board 3 3/4 in. Below motor board 2 1/2 in. Post £2 Cut Board £1 extra

HEAVY METAL PLINTHS Post £2
Cut out for most BSR or Garrard decks. Silver grey finish, black trim. Size 16x13 3/4 in. £4

DECCA TEAK VENEERED PLINTH Post £1.50
Superior finish with space and panel for small amplifier. Board is cut for B.S.R. 18 3/4 in. x 14 1/4 in. x 4 in. Black/chrome fascia trim. Also with boards cut out for Garrard £3. Tinted plastic cover £6

TINTED PLASTIC COVERS Post £2
17 1/2 x 13 1/2 x 3 1/4 in. £6
17 1/2 x 9 3/4 x 3 1/4 in. £5
13 3/4 x 12 x 2 1/4 in. £5
15 1/4 x 13 1/2 x 4 in. £6
17 x 12 1/2 x 3 1/4 in. £5

Callers Only (not suitable for post)
21 1/2 x 14 1/4 x 2 1/2 in. £6
23 3/4 x 14 x 3 1/4 in. £6

BSR SINGLE PLAYER DECKS
BSR P232 BELT DRIVE QUALITY DECK Post £24
Manual or automatic play. Precision ultra slim arm. Cueing device. Bargain price. With stereo ceramic cartridge

BSR P204 SINGLE PLAYERS SPECIAL OFFERS
Two speed 33/45 r.p.m. hi-fi decks with stereo cartridges, cueing device and snake arm. Ceramic - 240V AC £15 or 9V DC £19. Magnetic - 240V AC £20 or 12V DC £24

GARRARD 6-200 SINGLE PLAYER DECK £22 Post £2
Brushed Aluminium Arm with stereo ceramic cartridge and Diamond Stylus, 3-speeds. Manual and Auto Stop/Start. Large Metal Turntable. Cueing Device. Ready cut mounting board £1 extra.
GARRARD SP25 Mk 4. Less cartridge. Balanced arm. Few only. £30 Post £2
3-speed single player

BATTERY ELIMINATOR MAINS TO 9 VOLT D.C.
Stabilised output, 9 volt 400 m.a. U.K. made in plastic case with screw terminals. Safety overload cut out. Size 5 x 3 1/4 x 2 1/2 in. Transformer Rectifier Unit. Suitable Radios, Cassettes, models. £4.50. Post 65p.

DE LUXE SWITCHED MODEL STABILISED £7.50. Post £1.
1. 3-6-7-9 volt 400mA DC max. Universal output plug and lead. Pilot light, mains switch, polarity switch.

DRILL SPEED CONTROLLER/LIGHT DIMMER KIT. Easy to build kit. Controls up to 480 watts AC mains. £3. Post 65p.
DE LUXE MODEL READY-BUILT 800 watts. Front plate fits standard box. £5. Post 65p.

EMI 13 1/2 x 8 in. LOUSPEAKERS £9.50 Post £1.50
Model 450, 10 watts R.M.S. with moving coil tweeter and two-way crossover; 3 ohm or 8 ohm.
"Final Clearance"
SUITABLE BOOKSHELF CABINET £6.50. Size 18 x 11 x 6 in. Post £1.50.

RELAYS 6V DC 95p. 12V DC £1.25. 18V £1.25.
BLANK ALUMINIUM CHASSIS 6x4 - £1.45; 8x6 - £1.80; 10x7 - £2.30; 12x8 - £2.60; 14x9 - £3; 16x6 - £2.90; 16x10 - £3.20. All 2 1/2 in. deep. 18 swg.

ALUMINIUM PANELS 18swg. 6x4 - 45p; 8x6 - 75p; 14x3 - 75p; 10x7 - 95p; 12x8 - £1.10; 12x5 - 75p; 16x6 - £1.10; 14x9 - £1.45; 12x12 - £1.50; 16x10 - £1.75.

PLASTIC AND ALI BOXES IN STOCK. MANY SIZES ALUMINIUM BOXES. 4x4 x 1 1/2 in. £1. 4x2 1/2 x 2 in. £1. 3x2 x 1 in. £1. 6x4 x 2 in. £1. 7x5 x 3 in. £2. 8x6 x 3 in. £2. 10x7 x 3 in. £3. 12x5 x 3 in. £2. 12x8 x 3 in. £3. All with lids.

BRIDGE RECTIFIER 200V PIV 2A £1. 4A £1.50. 8A £2.50.
TOGGLE SWITCHES SP 30p. DPST 40p. DPDT 50p.
MINIATURE TOGGLES SP 40p. DPDT 60p.

RESISTORS. 10Ω to 10M. 1/4W, 1/2W, 1W, 2p: 2W 10p. HIGH STABILITY. 1/2w 2% to 10 ohms to 1 meg. 10p. Ditto 5%. Preferred values, 10 ohms to 10 meg. 3p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt 20p. PICK-UP CARTRIDGES SONOTONE 9TA £2.50.
BSR Stereo Ceramic SC7 Medium Output £2. SC12 £3.

PHILIPS PLUG-IN HEAD, Stereo Ceramic. AU1020 (G306 GP310 - GP233 - AG3306, E, A, D, C, QLM 30/3 Magnetic 25. LOCKTITE SEALING KIT DECCA 118. Complete £1.
ANTX SOLDERING KIT IBCN 240V 15W 3mm bit £5.25.

JACK PLUGS AND SOCKETS Plastic 25p; Metal 30p.
JACK SOCKETS Stereo Open 20p; Closed 25p.
JACK SOCKETS Stereo Open 20p; Closed 30p.
FREE SOCKETS - Cable end 30p. Metal 45p.

2.5mm and 3.5mm JACK SOCKETS 20p. Plugs 20p.
DIN TYPE CONNECTORS
Sockets 3-pin, 5-pin 10p. Free Sockets 3-pin, 5-pin 25p. Plugs 3-pin 20p; 5-pin 25p; Speaker plugs 20p; Sockets 15p.

PHONO PLUGS AND SOCKETS ea. 15p.
Free Socket for cable end 20p. Screened Phono Plugs 25p.
300 ohm TWIN RIBBON FEEDER 10p vd.
U.H.F. COAXIAL CABLE SUPER LOW LOSS 25p vd.
COAX PLUGS 30p. COAX SOCKETS 20p.
NEON INDICATORS 250V, round 30p. Rectangular 45p.
SOLID DIELECTRIC 100pf, 500pf £1.50.

POTENTIOMETERS Carbon Track
5kΩ to 2MΩ. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5K. SP 45p.

MINI-MULTI TESTER NEW
De luxe pocket size precision moving coil instrument. Impedance + Capacity 4000 Ω p.v. Battery included. 11 instant ranges measure: DC volts 5.25, 250, 500. AC volts 10, 50, 500, 1000. DC amps 0-250µa, 0-250mA. Continuity and resistance 0 to 600K ohms

De Luxe Range Doubler Model. 50,000 Ω p.v. £18.50. 7x5x2in. Post £1

NEW PANEL METERS £4.50
50µa, 100µa, 500µa, 1ma, 5ma, 50ma, 100ma, 500ma, 1 amp, 2 amp 25 volt, VU Meter. 2 1/4 x 2 x 1 1/4 in. Post 65p

RCS SOUND TO LIGHT CONTROL KIT £15
Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. Suitable for home or disco. Easy to build. Full instructions supplied. Post 95p
Cabinet £4.50 extra. Operates from 200W to 100W.
200 Watt Rear Reflecting White Light Bulbs. Ideal for Disco Lights, Edison Screw. 6 for £4, or 12 for £7.50. Post 65p. Suitable panel mounting holders 85p.

RCS "MINOR" 10 watt AMPLIFIER KIT £14
This kit is suitable for record players, guitars, tape playback, electronic instruments or small PA systems. Two versions available: Mono, £14; Stereo, £20. Specification 10W per channel; size 9 1/2 x 3 x 2 1/2 in. SAE details. Full instructions supplied. 240V AC mains. Post £1.

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board. Can be ganged to make multi-way stereo mixers £2.95 Post 65p

MAINS TRANSFORMERS Post
250-0-250V 70mA, 8.5V, 2A £4.50 £2
250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A £5.00 £2
350-0-350V 250mA, 6.3V 6A CT £12.00 £2
300-0-300V 120mA, 2x6.3V 2A C.T.; 5V 2A £13.00 £2
220V 45mA, 6.3V 2A £3.00 £1
250V 60mA, 6V 2A £3.75 £1

AUTO 115V to 240V 150W £9. 250W £10. 400W £11. 500W £12.00 £2

GENERAL PURPOSE LOW VOLTAGE
Tapped outputs available Price Post
2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £8.00 £2
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £10.50 £2
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £12.50 £2
3 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £18.00 £2
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £23.75 £1
5-8-10-16V, 1/2 amp. £2.00 £1
6V, 12 amp. £2.00 £1
6-0-6V, 1 1/2 amp. £3.50 £1
9V, 250ma. £1.50 80p
20-0-20V 1 amp £4.00 £2
9V, 3 amp £3.50 £1
9-0-9V, 50ma £1.50 80p
10-0-10V, 2 amps £3.00 £1
10-30-40V, 2 amps £3.50 £1
12V, 100ma £1.50 80p
12V, 750 ma £2.00 80p
12V, 3 amps £3.50 £1
12-0-12V, 2 amps £3.50 £1
20-0-20V 1/2a £10.00 £2

CHARGER TRANS Post RECTIFIERS Post
6-12 volt 3a £4.00+£2 6-12 volt 2a £1.10+80p
6-12 volt 4a £8.50+£2 6-12 volt 4a £2.00+80p

OPUS COMPACT SPEAKERS £22 pair Post £2
TEAK VENEERED CABINET
11x8 1/2 x 7 1/2 in. 15 watts
50 to 14,000 cps. 4 ohm or 8 ohm

OPUS TWO 15x10 1/2 x 7 3/4 in. 25 watt
2-way system £39 pair. Post £5

LOW VOLTAGE ELECTROLYTICS Wire ends 10p
1 mf, 2 mf, 4 mf, 8 mf, 10 mf, 16 mf, 25 mf, 50 mf, 100 mf, 250 mf. All 15 volts. 22 mf/6V/10v; 25 mf/6V/10v; 47 mf/10v; 50 mf/6v; 68 mf/6v/10v/16v; 25v; 100 mf/10v; 150 mf/6v/10v; 200 mf/10v/16v; 220 mf/4v/10v/16v; 300 mf/4v/10v; 500 mf/6v; 680 mf/6v/10v/16v; 1000 mf/2.5v/4v/10v; 1500 mf/6v/10v/16v; 2200 mf/6v/10v; 3300 mf/6v/10v/16v; 5000mf 12V 15p; 25V 20p; 50V 30p; 120mF 70V 88p.
1000mF 12V 20p; 25V 35p; 50V 50p; 100V 70p.
2000mF 6V 25p; 25V 42p; 40V 60p; 1200mF 70V 80p.
2200mF 63V 90p; 2500mF 50V 70p; 3000mF 50V 65p;
4500mF 64V £2; 4700mF 63V £1.20; 2700mF 76V £1.

HIGH VOLTAGE ELECTROLYTICS
2/500V 45p 8-8/450V 75p 32+32+16/350V 90p
8/450V 45p 8-8/500V £1 100+100/275V 65p
16/350V 45p 8-16/450V 75p 150+200/275V 70p
32/500V 75p 32+32/350V 50p 220/450V 95p
32/350V 50p 32+32/350V £1.80 50+50+32+32/325V 75p
50/450V 95p 50+50/300V £1.90 50+50+50/350V 95p

CAPACITORS WIRE END High Voltage
.001, .002, .003, .005, .01, .02, .03, .05 mfd 400V 5p.
.1Mf 200V 5p. 400V 10p. 600V 15p. 1000V 25p.
.22Mf 350V 12p. 600V 20p. 1000V 30p. 1750V 50p.
47Mf 1500V 10p. 400V 20p. 630V 30p. 1000V 60p.
VALVE OUTPUT TRANSFORMERS (small) 90p.
TRIMMERS 30pF, 50pF, 10p, 100pF, 150pF, 500pF 30p.
MICROSWITCH SINGLE POLE CHANGEOVER 40p.
SUB-MIN MICROSWITCH, 50p, Single pole changeover.
TWIN GANG, 120pF 50p, 500 pF 100p £1.
GEARED TWIN GANGS 25p 95p.
GEARED 365+365+25+25pF £1.
TRANSISTOR TWIN GANG, Japanese Replacement £1
SOLID DIELECTRIC 100pf £1.50, 500pf £1.50.

HEATING ELEMENTS, WAFER THIN
Size 11x9x1/4 in. Operating voltage 240V, 250V approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, Propagation, etc. Must be clamped between two sheets of metal or ceramic, etc.
ONLY 60p EACH (FOUR FOR £2) ALL POST PAID.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS £3.95. Post 65p.
All parts and instructions with Zener diode printed circuit, mains transformer 240V a.c. Output 6 or 7 1/2 or 9 or 12V d.c. up to 100mA or less. Please state voltage required.

NEW baker Star sound
high power full range quality loudspeakers produced to give exceptional reproduction. Ideal for Hi-Fi, music P.A. or discotheques. These loudspeakers are recommended where high power handling is required with quality results. The high flux ceramic magnet ensures clear response.

MODEL	INCHES	OHMS	WATTS	TYPE	PRICE	POST
MAJOR	12	4-8-16	30	HI-FI	£14	£2
DELUXE MK II	12	8	15	HI-FI	£14	£2
SUPERB	12	8-16	30	HI-FI	£24	£2
AUDITORIUM	12	8-16	45	HI-FI	£22	£2
AUDITORIUM	15	8-16	60	HI-FI	£34	£2
GROUP 45	12	4-8-16	45	PA	£14	£2
GROUP 75	12	4-8-16	75	PA	£18	£2
GROUP 100	12	8-16	100	Guitar	£24	£2
DISCO 100	12	8-16	100	Disco	£24	£2
GROUP 100	15	8-16	100	Guitar	£32	£2
DISCO 100	15	8-16	100	Disco	£32	£2

BAKER 150 WATT MIXER/POWER AMPLIFIER £89 Post £2
For Discotheque, Vocal, Public Address. Three speaker outlets for 4, 8 or 16 ohms. Four high gain inputs, 20 mv, 50K ohm. Individual volume controls "Four channel" mixing. 150 watts 8 ohms R.M.S. Music Power. Slave output 500 M.V. 25K ohm. Response 25 Hz - 20kHz ± 3dB. Integral Hi-Fi preamp separate Bass & Treble. Size - 16" x 8" x 5 1/2". Wt - 14lb: Master volume control. British made. 12 months' guarantee. 240V A.C. mains or 120V to order. All transistor and solid state.
MONO SLAVE VERSION £75. 100 Volt Line Model £104.
NEW Stereo Slave Model 150 + 150 watt £125. Post £4.
BAKER'S NEW PA150 MICROPHONE PA AMPLIFIER £28. PP £3.
4 channel 8 inputs, dual impedance, 500-600 ohm 4 channel mixing, volume, treble, bass. Presence controls, Master volume control, echo/send/return socket. Slave input/output sockets.

BAKER £69 Post £2
50 WATT AMPLIFIER
Ideal for PA systems, Discos and Groups. Two inputs, Mixer, Volume, Controls, Master Bass, Treble Gain.
RCS offers MOBILE PA AMPLIFIERS. Outputs 4-8-16 ohms
20-watt RMS 12v DC, AC 240v, 3 inputs. 50K £46 PP £2.
40-watt RMS 12v DC, AC 240v, 4 inputs. 50K 100v Line £75 PP £2.
Mic 1; Mic 2; Phono; aux. outputs 4 or 8 or 16 and 100v line
60-watt RMS, Mobile 24 volt DC & 240-volt AC mains. inputs 50K.
3 mics + 1 music. Outputs 4-8-16 ohm + 100 volts line £95 PP £2.
Battery only Shoulder PA Amplifier 10w max. Includes mike and speaker, OK for meetings, crowd control, stalls, fetes, traders, etc. Batteries included (6 of U2) £27.50 post £1.50.

FAMOUS LOUSPEAKERS "SPECIAL PRICES"

MAKE	MODEL	SIZE	WATTS	OHMS	PRICE	POST
SEAS	TWEETER	4in	50	8	£3.50	£1
GODDMANS	TWEETER	3 1/2 in	25	8	£4.00	£1
AUDAX	TWEETER	4in	30	8	£6.50	£1
SEAS	MID-RANGE	4in	50	8	£7.50	£1
SEAS	MID-RANGE	5in	80	8	£12.00	£1
SEAS	MID-RANGE	4 1/2 in	100	8	£12.50	£1
GODDMANS	HIFAX	7 1/2 x 4 1/4	100	4/8/16	£22	£2
GODDMANS	WOOFER	8in	25	4/8	£6.50	£1
GODDMANS	HE	8in	60	8	£12.50	£1
RIGONDA	GENERAL	10in	15	8	£5	£2
AUDAX	WOOFER	10in	50	8	£16.00	£2
GODDMANS	HPG	12in	120	8/15	£29.50	£2
GODDMANS	GR12	12in	90	8/15	£25.50	£2
GODDMANS	HPD	12in	120	8/15	£29.50	£2

SPEAKER COVERING MATERIALS. Samples Large S.A.E.
B.A.F. LOUSPEAKER CABINET WADDING 18in wide 35p ft.

MOTOROLA PIEZO ELECTRIC HORN TWEETER, 3 3/4 in. square £5
100 watts. No crossover required. 4-8-16 ohm, 7 1/2 x 3 1/4 in. £10.50

CROSSOVERS. TWO-WAY 3000 c/s 30 watt 8 or 15 ohm £3. 3-way 950 cps/3000 cps. 40 watt rating. £4. 3 way 60 watt £6.
LOUSPEAKER BARGAINS
3 ohm, 5in, 7x4in, £2.50; 6 1/2 in, 8x5in, £3; 8in, £3.50, 10in, £5.
8 ohm, 2 1/2 in, 3in, £2; 5in, £2.50; 6 1/2 in, £3; 8in, £4.50; 12in, £5.
15 ohm, 3 1/2 in, 5x3in, 6x4in, £2.50.
25 ohm, 3in, £2; 5x3in, 7x4in, £2.50, 120 ohm, 3 1/4 in dia. £1.
CASSETTE MONO REPLAY. Complete working £12.50
CAR CASSETTE MECHANISM. 12V Stereo Head £5

THE "INSTANT" BULK TAPE ERASER £9.50 Post 95p
Suitable for cassettes and all sizes of tape reels. AC mains 200/250V. Hand held size with switch and lead (120 volt to order). Will also demagnetise small tools.
Head Demagnetiser only £5.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS £3.95. Post 65p.
All parts and instructions with Zener diode printed circuit, mains transformer 240V a.c. Output 6 or 7 1/2 or 9 or 12V d.c. up to 100mA or less. Please state voltage required.

RELAY-A-QUIP PRODUCTS
Moat Lodge, Stock Chase
Maldon, Essex, UK
Tel: 0621 57242 10am-8pm Mon.-Sat.

TRADE P.O.A.
"SEIKO"
30w Iron
£2.95

RELAY-A-QUIP PRODUCTS
Moat Lodge, Stock Chase
Maldon, Essex, UK
Tel: 0621 57242 10am-8pm Mon.-Sat.

RELAY-A-QUIP PRODUCTS
Moat Lodge, Stock Chase
Maldon, Essex, UK
Tel: 0621 57242 10am-8pm Mon.-Sat.

Time's running out... for Ni-Cads!

NEW NEC SUPERCAPS
5 VDC
1.0 F
NN54

Available from stock NOW!
1.0 FARAD 1.0 FARAD 1.0 FARAD
SUPERCAP SUPERCAP SUPERCAP
+ 5101 + 1703 + 7507
C.MOS Programmable C.MOS
R.A.M. Tuner Chip Microcomputer

Only part of the Anglia range of NEC components
Burdett Road, Wisbech, Cambs, PE13 2PS
Telephone 0945 63281
Telex 32630 ANGLIA G

THE PARTS YOU NEED - fast!
WW - 062 FOR FURTHER DETAILS

19" Rack Mounting Cabinet - Or Free Standing
£23.95
£19.50
OFFER ENDS SOON

Front Panel 480x150 mm. Rear Case 425x250x140 mm
* Top, bottom and rear cover removable for access * Plates have heavy duty grey paint finish * Front panel is heavy gauge - 3mm aluminium * Strong, screwed, construction throughout - screws included * Heavy gauge chassis mounting plate is pre-drilled and has four mounting positions to choose from * Front panel is of brushed aluminium finish enhanced with heavily chromed handles *

ADD VAT AT STD. RATE & ORDERS UNDER £5. P&P 50p ABOVE ITEMS £1 P&P

Ask for our FREE Catalogue

SLIDE SWITCHES	PRICE
1P2T	10p
2P2T pcb	12p
2P2T	12p
2P3T	20p
1P4T pcb	26p
4P2T pcb	28p
4P3T pcb	35p
6P3T pcb	42p
4P4T pcb	45p

Bridge WO-005 16p

DIODES
1N4148 - 2p 1N4002 - 3p
1N4003 - 4p 1N4004 - 5p

RELAY-A-QUIP PRODUCTS
Moat Lodge, Stock Chase
Maldon, Essex, UK
Tel: 0621 57242 10am-8pm Mon.-Sat.


RELAY-A-QUIP PRODUCTS
Moat Lodge, Stock Chase
Maldon, Essex, UK
Tel: 0621 57242 10am-8pm Mon.-Sat.

TRANSFORMERS Despatch by return

MAINS ISOLATORS CONTINUOUS RATINGS: 12 or 24-VOLT RANGE
Pri 0-120; 0-100-120V, Sec 0-CT-115V x 2

Ref. VA (Watts)	£
-----------------	---

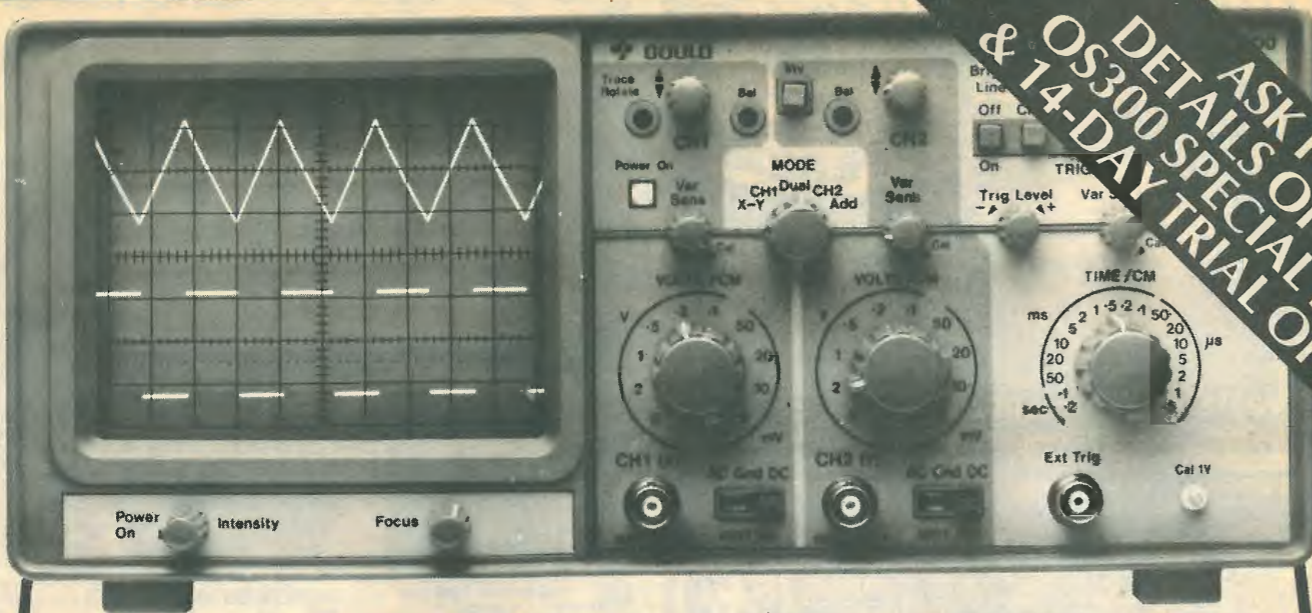GOULD OSCILLOSCOPES SET A HIGHER STANDARD



ASK FOR OUR PRICE & OS300 SPECIAL OFFERS. DETAILS OF OUR 14-DAY TRIAL OFFERS.

The new Gould OS300 Dual Trace 20MHz Scope

A tough, professional instrument you can trust - at a price you can afford! ★ Max. sensitivity 2mV/cm. ★ Stepped and continuously variable attenuator and timebase controls. ★ D.C. coupled triggering and "active" T.V. sync separator. ★ 'Add' and 'Invert' for differential measurements. ★ X-Y facility. Built to do more - safely, reliably and for longer.

Ask for our 8-page data sheet for full details and applications information.



Electronics & Electrical Products

Gould Instruments Division
Roebuck Road, Hainault, Ilford, Essex IG6 3UE.
Telephone: 01-500 1000. Telex: 263785

10619

<p>Item No. 1 HEWLETT PACKARD RMS VOLT METER type 3400A 1mV-300V, 10Hz-10MHz £150</p> <p>2 BOONTON SIGNAL GEN POWER AMPLIFIER type 230A 10-500MHz £50</p> <p>3 HEWLETT PACKARD AUDIO SIGNAL GENERATOR type 205AG £25</p> <p>4 CLAUDE LYONS AUTOMATIC VOLTAGE STABILISER 2.88kVA Compact £60</p> <p>5 TEKTRONIX AMPLIFIER type 1121 £40</p> <p>6 SES ABSORPTION WATT METER type TG2600 2-10000MHz, 100 Watts 50 ohm £100</p> <p>7 TEKTRONIX PLUG-IN type D Single Trace High Gain DC Differential £20</p> <p>8 TEKTRONIX PLUG-IN type E Single Trace Low Level AC Differential £25</p> <p>9 TEKTRONIX PLUG-IN type G Single Trace Wide Band DC Differential £25</p> <p>10 TEKTRONIX PLUG-IN type L Single Trace 30MHz High Gain £25</p> <p>11 TEKTRONIX PLUG-IN type M 4 Trace DC-20MHz £125</p> <p>12 TEKTRONIX PLUG-IN type O Transducer & Strain Gauge £75</p> <p>13 TEKTRONIX PLUG-IN type R Transistor Rise Time £75</p> <p>14 TEKTRONIX PLUG-IN type S Transistor Rise Time £125</p> <p>15 TEKTRONIX PLUG-IN type T Differential Comparator £75</p> <p>16 TEKTRONIX PLUG-IN type Z Differential Comparator £75</p> <p>17 HEWLETT PACKARD LCR BRIDGE type 4251A £125</p> <p>18 HEWLETT PACKARD AMPLIFIER type 4251A £135</p> <p>19 HEWLETT PACKARD DC CURRENT SOURCE type 6181B 0-100V, 0-250mA £35</p> <p>20 FAST RESPONSE RECORDER type H3020-3 (3 channel) Brand new £50</p> <p>21 HEWLETT PACKARD AUDIO OSCILLATOR type 200L £25</p> <p>22 HEWLETT PACKARD PULSE GENERATOR Model 212A £40</p> <p>23 HEWLETT PACKARD DC MICRO VOLT AMMETER type 425A £40</p> <p>24 HEWLETT PACKARD OSCILLOSCOPE 182A with 1809A and 1825A 75MHz Dual Trace Delayed Sweep £750</p> <p>25 AVO VALVE TESTER type CT160 (22 valve bases) £20</p> <p>26 AVO TRANSISTOR ANALYSER type CT446 £20</p> <p>27 MARCONI UNIVERSAL BRIDGE type TF88A £150</p> <p>28 GENERAL RADIO DIGITAL TIME & FREQUENCY METER type 1151-A £45</p> <p>29 MARCONI (SANDERS) MICROWAVE POWER METER type 6598 £150</p> <p>30 MARCONI UHF SIGNAL GENERATOR type TF1090 £30</p> <p>31 MARCONI FM SIGNAL GENERATOR type TF1071 18.7-102.5MHz £30</p> <p>32 MARCONI SUPPRESSED ZERO VOLT METER type TF1377 £115</p> <p>33 MARCONI VARIABLE ATTENUATOR type TF1073A/2S (CT421) £30</p> <p>34 ERNST TURNER 20KV ELECTROSTATIC VOLT METER 6 inch £180</p> <p>35 MARCONI AM/FM SIGNAL GENERATOR TF994/3S (CT402) 1.5-220MHz £180</p> <p>36 B & K ACCELEROMETER PREAMPLIFIER type 2620 £30</p> <p>37 B & K DEVIATION BRIDGE type 1503 £50</p> <p>38 B & K DEVIATION BRIDGE type 1504 £50</p> <p>39 B & K MICROPHONE AMPLIFIER type 2602 £35</p> <p>40 B & K MICROPHONE AMPLIFIER type 2605 £35</p> <p>41 B & K BEAT FREQUENCY OSCILLATOR type 1013 £95</p> <p>42 B & K BEAT FREQUENCY OSCILLATOR type 1018 £95</p> <p>43 B & K EXCITER CONTROL PRE AMPLIFIER type 1608 £20</p> <p>44 B & K EXCITER CONTROL PRE AMPLIFIER type 1608 £20</p> <p>45 HOUSTON INSTRUMENTS LOG VOLT METER-CONVERTOR Model HLVC150 £30</p> <p>46 POLAROID FIELD STRENGTH METER type FIM-B2 with RF Tuning Unit FIM-X2 7360-10,000MHz £35</p> <p>47 HEWLETT PACKARD DIGITAL VOLT METER type 3460B with AC CONVERTER type 3461A +/- 0.004% £100</p>	<p>Item No. 53 SANDERS OSCILLATOR type CLC-4 £75</p> <p>54 B & K ELECTRONIC VOLT METER type 2409 2Hz-200KHz £95</p> <p>55 GENERAL RADIO MICROWAVE OSCILLATOR type 1380B 1.7-4.1GHz £225</p> <p>56 GENERAL RADIO FREQUENCY/DISCRIMINATOR METER type 1142A 0-1.5MHz £26</p> <p>57 HEWLETT PACKARD MEMORY DISPLAY type 5480A with CONTROL type 5486B and Two Channel Input type 5485A £225</p> <p>58 GENERAL RADIO DECADE CAPACITOR 1413 with ANALOG LIMIT COMPARTOR 1182 and IMPEDANCE COMPARTOR 1854 £190</p> <p>59 STODDARD RADIO INTERFERENCE & FIELD INTENSITY METER type N-M 52A £195</p> <p>60 KEITHLEY REGULATED HIGH VOLTAGE SUPPLY type 241 £145</p> <p>61 BRANDENBURGH HIGH VOLTAGE GENERATOR type MRS0 £75</p> <p>62 BRANDENBURGH HIGH VOLTAGE P.U. Model 705 Metered 0-15KV +/- £100</p> <p>63 BELX POWER UNIT type CMT3001 +/- £40</p> <p>64 PLESSEY TELEGRAPH SIGNAL GENERATOR TSG10 with TDMS type 70. Speed 50-75-100 (2 units) £360</p> <p>65 As Above but SPEED 45.5-50-75 £300</p> <p>66 RACAL H.F. SELECTIVE ANALYSER type 9056 £235</p> <p>67 RACAL UHF FREQUENCY METER type 9839 10-500MHz £225</p> <p>68 RACAL 800MHz DECADE DIVIDER type 9010 £40</p> <p>69 RACAL AUTO FREQUENCY CONVERTOR type 9039 500MHz £20</p> <p>70 RHODE & SCHWAB NOISE GENERATOR SKTU BN4151/2/80 3-1000MHz £75</p> <p>71 R & S UHF TEST RECEIVER BN1523 280-940MHz £250</p> <p>72 R & S FREQUENCY METER VHF-UHF 30-300MHz type WD BN442 £40</p> <p>73 R & S ATTENUATOR type DPR BN1804/250 £25</p> <p>74 R & S RESONANCE FREQUENCY METER 30-500MHz WAM BN431/2 £30</p> <p>75 R & S WIDE BAND SIG GEN type SBF BN4081 10Hz-10MHz £30</p> <p>76 R & S SIGNAL GENERATOR type SMAR BN4123 30Hz-30MHz £50</p> <p>77 R & S CAPACITANCE METER BN5201 £50</p> <p>78 ISOLATING TRANSFORMER 240V Input 240V Output 1300 Watts £15</p> <p>79 AUTO TRANSFORMER 1.4 kVA Pri Volts 90-240 Sec Volts 115 £15</p> <p>80 DC SERVO MOTOR 110V 2.5A Cont. Double Shaft, 4 wire 4 brush. New £15</p> <p>81 ULT TRANSISTOR A.C. VOLTAGE REGULATOR Model TL-T1000-2S Rating 1000V £40</p> <p>82 WAYNE KERR AUTOBALANCE CAPACITANCE BRIDGE type B541 £75</p> <p>83 PHILIPS VIDEO COLOUR TEST GENERATOR type PM5522. No case £145</p> <p>84 PHILIPS FM STEREO GENERATOR type PM4656. Separate L & R Signals Carrier Free 100MHz +/- 1% RF O/P 30W pk-pk £30</p> <p>85 PHILIPS COMPARTOR 278KHz £30</p> <p>86 PHILIPS AUTOMATIC ELECTRONIC VOLT OHM METER type PM2405 £20</p> <p>87 B & K AUTOMATIC VIBRATION EXCITER CONTROL type 1016 £20</p> <p>88 HEWLETT PACKARD DC POWER SUPPLY type 6448B 0-500 Volts 0-1.5 Amps £250</p> <p>89 BRANDENBURG REGULATED HIGH VOLTAGE P.U. type 928R 0-100KV; 0-1MA £150</p> <p>90 ADVANCE PULSE GENERATOR type P650020 £20</p> <p>91 GAUMONT-KALEE FLUTTER METER type 1740 £30</p> <p>92 ADVANCE SIGNAL GENERATOR L.F. type 81A 15Hz-200KHz £20</p> <p>93 ADVANCE BATCH COUNTER type 4841 £20</p> <p>94 ADVANCE AUDIO SIGNAL GENERATOR type J1 £30</p> <p>95 ADVANCE SIGNAL GENERATOR type E2 100Hz-100MHz £45</p> <p>96 PVE SCALAMP 40KV RMS Max ELECTROSTATIC VOLT METER £35</p> <p>97 PVE SCALAMP 20KV RMS Max ELECTROSTATIC VOLT METER £35</p> <p>98 RANK ABENA E.H.T. METER 0-20KV £35</p> <p>99 SINE & SQUARE WAVE AUDIO GENERATOR type TE-22 20Hz-200KHz £85</p> <p>100 BLACK & WHITE 20" MONITOR by IKEGAMI type PM201TS. Solid State £26</p>	<p>MARCONI AM/FM SIGNAL GENERATOR type TF1066B/6S 10-470 MHz in 5 bands £250 each. Carriage £6.</p> <p>WAYNE KERR COMPONENT BRIDGE type B521 (CT 375) Resistance 1mOhm - 1000 MegOhm Capacitance 1pF - 5000Kuf Inductance 1µH - 500kH. With copy of manual ONLY £40 each. Carriage £6.</p> <p>AVO VALVE TESTER type CT160 (22 valve bases) with copy of manual £20 each. Carriage £6.</p> <p>AVO TRANSISTOR ANALYSER type CT446 with copy of manual £20 each. Carriage £6.</p> <p>AVO SIGNAL GENERATOR No. 2 AM/FM AM 0.45-225MHz; FM 20-100MHz with copy of manual £75 each. Carriage £6.</p> <p>MARCONI COUNTER/FREQUENCY METER TF1417/2 with Converter type TF 2400/TF17285 - 500MHz £35 each. Carriage £6.</p> <p>TELETYPE PRINTERS KSR33 - ASCII Keyboard £50. ASR 33 - as above with 8-bit Punch and Reader £75. Carriage £8 each unit.</p> <p>MULTIMETER Russian Type 4324 AC/DC volts; AC/DC current; ohms, etc. Brand new, boxed. £12.50 each. P&P £2.50</p> <p>ISOLATING TRANSFORMER 240V input 240V Output 1300 Watts £15 each. Carr. £6</p> <p>SINE & SQUARE WAVE AUDIO GENERATOR type TE-22, 20Hz-200KHz. Portable as new ONLY £35 each. P&P £4</p> <p>IKEGAMI MONITOR 20" Black & White Solid state. Video in, int. ext. Sync. £65 each. Carriage £6</p>
--	--	--

PLEASE CHECK AVAILABILITY BEFORE ORDERING COMPONENT LIST AVAILABLE S.A.E. OR PHONE

BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome. All units £6 carriage. Plus V.A.T. on total. CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc.

CHILTMHEAD LTD.
NORWOOD ROAD, READING
TELEPHONE NO. READING 669656
(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel")

INDUSTRIAL MUSCLE AT A REALISTIC PRICE

★ POWER BANDWIDTH DC to 100KHZ ± 1db
★ OUTPUT POWER IN EXCESS OF 500 WATTS PER CHANNEL INTO 2 OHMS
OR IN EXCESS OF 1KW SINGLE CHANNEL IN BRIDGE MODE INTO 6 OHMS
★ HARMONIC DISTORTION LESS THAN 0.01% DC TO 100KHZ AT 1KW INTO 6 OHMS
★ INTERFACE BOARDS CAN BE CUSTOM DESIGNED AND BUILT TO CATER FOR A WIDE-RANGE OF SPECIALISED USES
★ OUTPUT MATCHING TRANSFORMERS AVAILABLE TO MATCH VIRTUALLY ANY LOAD
★ UNCONDITIONALLY STABLE INTO ANY LOAD
★ BASIC PRICE INCLUDING BRIDGE MODE SWITCHING AND HANDLES £455

S & R AMPLIFICATION
6 Tanners Hill, London S.E.8
Telephone: 01-692 2009

WW - 064 FOR FURTHER DETAILS

SWITCHCRAFT XLR CONNECTORS

Line Female A3F £1.59 Chassis Female D3F £2.04
Line Male A3M £1.36 Chassis Male D3M £1.19

4, 5, 6 and 7-pin versions and large selection audio adaptors available

NEUTRIK XLR CONNECTORS

Latchless Chassis NC3-FZ £0.67 Latchless Chassis Male NC3-MZ £0.59
Line Female NC3-FCC £1.34 Line Male NC3-MC £1.15
Female Chassis NC3-FP £1.65 Chassis Male NC3-MP £0.87

4, 5-pin, PCB and black versions and large selection of audio adaptors available

XLR LINE MAIN SERIES

XLR LINE 11C £3.87 XLR LINE 12C £3.76
XLR LINE 32 £2.89 XLR LINE 31 £4.14

BELCLERE AUDIO TRANSFORMERS

EN6422 Ratio 1 + 1:8.45 + 6.45. Freq. 40Hz-35KHz. PRI 150/600Ω, sec. 600/2.4KΩ £4.15
EN6423 Ratio 1 + 1:8.45 + 6.45. Freq. 40Hz-25KHz. PRI 150/600Ω, sec. 6.25K/25KΩ £4.15
SKT-723 MuMetal Screening can, 39dB reduction 50Hz ext. field £1.30

Trade enquiries welcome: quantity discounts available. All prices subject to V.A.T. Call, write or telephone. Minimum order £10. Please add £2 postage. Access, Amex, Barclaycard.

KELSEY ACOUSTICS LTD.
28 POWIS TERRACE, LONDON W11 1JH
01-727 1046/0780

WW - 075 FOR FURTHER DETAILS

VIDEO TECHNIQUES

by Gordon White Price: £12.00

AN INTRO. TO THYRISTORS AND THEIR APPLICATIONS Price: £7.50
by M. Ramamoorthy
DIGITAL ICs - HOW THEY WORK AND HOW TO USE THEM Price: £6.50
by A. W. Barber
SERVICING RADIO, HI-FI AND TV EQUIPMENT Price: £7.50
by J. D. Lenk
H/B OF PRACTICAL ELECTRONIC CIRCUITS Price: £17.45
ELECTRONIC TEST EQUIPMENT OPERATION AND APPLICATION Price: £21.00
by A. M. Rudkin
ELECTRONIC COMPONENTS AND SYSTEMS Price: £13.50
by T. D. Towers
TOWERS' INTERNATIONAL TRANSISTOR SELECTOR Price: £10.50
by B. Grob
ELECTRONIC CIRCUITS AND APPLICATIONS Price: £17.00
INTRODUCTION TO RADIO FREQUENCY DESIGN Price: £22.00
by W. H. Hayward

★ PRICES INCLUDE POSTAGE AND PACKING ★
THE MODERN BOOK CO.
Specialist in scientific and technical books
15/21 PRAED ST., LONDON W2 1NP
PHONE: 01-402 9178 - Closed SATURDAY 1 p.m.
Please allow 14 days for reply or delivery

WW - 031 FOR FURTHER DETAILS

WW - 031 FOR FURTHER DETAILS

HF ANTENNAS

★ MODE; Full half wave operation.
★ BANDS; Up to 4 spot frequencies.
★ POWER; Receive to 800W (PEP).
★ SWR; Better than 1.5:1 on channel.

THE SMC TRAPPED DIPOLE ANTENNA
has been developed to satisfy the needs of commercial and military users. It is capable of operation between 2 and 30 MHz on as many as four spot frequencies - each capable of accommodating many channels. Excellent matching and efficiency with a single coaxial feed is offered by the use of SMC H1Q traps and the incorporation of a ferrite balun in a full half wave design. NB: Power absorbing terminating resistors are not employed. The antenna may be deployed using one or two support masts, installation (incorporating SMC light duty portable masts) can be easily effected by two people in half an hour.

FT180 "PIONEER" HF SSB TRANSCEIVER.
1.8-18MHz, 6 channels 100 watts RF output measuring only 95(H) x 240(W) x 310(D) mm and weighing 6kg. May be operated as a base or mobile transceiver, complementing our trap dipole and HW4 mobile aerials. Prices start at £500, making this unit not only very attractive but highly competitive.

SOUTH MIDLANDS COMMUNICATIONS LTD.
OSBORNE ROAD, TOTTEN SOUTHAMPTON SO4 4DN
Telex: 477351 SMCMM G
Tel: Totton (0703) 867333

WW - 063 FOR FURTHER DETAILS

YOUR PROBLEM SOLVED!

The WEZ Antistatic Circuit Board Holder

A unique Combination of Moulded Profile, retains P.C.B.s of different sizes on the bench, or in transit!!

One of the many ANTISTATIC answers from **TEKNIS**

Two boards; total cost £6 incl. p/p + V.A.T.

TEKNIS
TEKNIS HOUSE, MEADOW, GODALMING, GU7 3HQ
Telephone (04868) 5432 Telex 859585


WW - 074 FOR FURTHER DETAILS

STORE CLOSING SALE


Bargains

That will make you money.....

FANS - BLOWERS

- 
- Snail type blower with inset mains motor, Smiths Extractor fan, 5" Woods, ex computer £2.50
 - Tangential blower, 10 x 3" air outlet, Dual speed, Condenser operated - Mains motor £2.90

LIGHTING & POWER CABLES

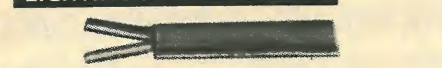- 
- Copper Clad, PVC sheathed, Made by Volex to BSS.
 - 1.5mm single per 100 metres £2.00
 - 1.5mm flat twin per 100 metres £3.50
 - 1.5mm flat 3 core & E per 100 metres £5.50
 - 4mm single per 100 metres £3.00
 - 6mm flat 3 core per 100 metres £27.50
 - 16mm flat twin & E per 100 metres £47.50
 - Telephone and multiway cables, Reliance as used by GPO £60.00
 - 15 core per 200 metres £40.00
 - 10 core per 200 metres £40.00

THERMOSTATS & HEAT SWITCHES

- Thermostat: 3 level contact type .30
- 10 amp appliance type thermostat, Spindle adjust .40
- Contact type with changeover, 10 amp switches, 0 - 100°C .58
- Wall mounting, metal case, c/o contacts low voltage £2.30

TIMERS & CLOCKS


- 
- Time and Set Switches, Smiths, Glass fronted 25 Amp, 230 volts £2.30
 - 24 Hour time switch, 100 amp Smiths with clockwork reserve, Ex Electricity Company, £5.50
 - Cooker clock switch, Smiths, 12 hour £1.00
 - Clockwork operated switches: 15 amp, 230 volt. On time up to: 10 minutes £1.37, 30 minutes £1.37, 120 minutes £1.37, 360 minutes £1.37
 - OMRON mini timer, ref STP NH £3.50



WIRES & CABLES

- 3 core and screened power flex cable: 3 cores each 50.025 (equiv. 2.5mm) per metre .40, 3 cores each 30.025 (equiv. 1.5mm) per metre .30, 3 cores each 24.02 (equiv. 1mm) per metre .20
- Armoured Cable 1.5mm, 3 core .40
- Extension lead, 3 cores, 5mm pvc covered /100 M. £9.50
- Ext. lead, twin, 5mm rubber covered /1000 metres £60.00
- Iron Flex, Woven cotton covered, rubber insulated 2 core 100 metre £12.50
- FIGURE 8 FLEX Heavy Duty .75mm, 600 metre £19.00
- Figure 8 Flex per 100 metres £3.00


BLEEPERS - SIRENS - BELLS - ALARMS - BUZZERS

- 
- Siren/Hooter - Delta 6 or 12v DC or 24v AC .37
 - Open type buzzer, ex GPO, 10 - 20v .30
 - Underdome bell, 4v - 9v .85
 - Fire alarm bell, 12" gong, heavy cast iron const. £12.00

PROJECT BOXES - CASES - CABINETS


- 
- Black plastic boxes, 2 7/8 x 4 1/8 x 3 deep .50
 - Ditto 3 5/8 x 2 3/4 x 1 3/4 deep .40
 - Ditto 3 7/8 x 3 3/8 x 1 deep .30
 - Plated metal box, 7 1/2 x 4 1/2 x 1 1/2 deep £1.00
 - Dark grey half boxes, May be joined to make three different depth boxes, 4 5/8 x 2 5/8 x 3/4 deep .20
 - 4 5/8 x 2 5/8 x 1 deep .25
 - White plastic box ideal for touch switch, transmitter, etc. .50
 - Through top is square hole, 3 1/2 x 3 1/2 x 3 1/2
 - Loudspeaker cabinet for 6 1/2" speaker .95
 - PORTABLE RADIO CASE - 5" speaker, size approx 6 1/4" x 3 3/4" x 2" deep £1.00

COUNTERS

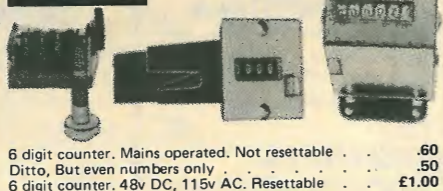
- 
- 6 digit counter, Mains operated. Not resettable .60
 - Ditto, but even numbers only .50
 - 6 digit counter, 48v DC, 115v AC, Resettable £1.00

SOLENOIDS - BATTERY & MAINS

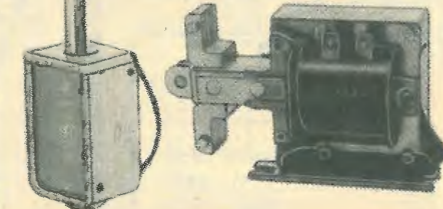- Mains operated with plunger, Round small .60
- Oblong small .75
- Oblong medium £1.00
- Large push or pull £3.50



MAINS TRANSFORMERS

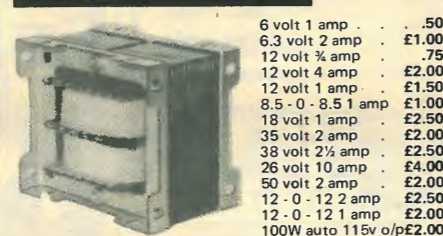- 
- 6 volt 1 amp .50
 - 6.3 volt 2 amp £1.00
 - 12 volt 1/2 amp .75
 - 12 volt 4 amp £2.00
 - 12 volt 1 amp £1.50
 - 8.5 - 0 - 8.5 1 amp £1.00
 - 18 volt 1 amp £2.50
 - 35 volt 2 amp £2.00
 - 38 volt 2 amp £2.50
 - 26 volt 10 amp £4.00
 - 50 volt 2 amp £2.00
 - 12 - 0 - 12 2 amp £2.50
 - 12 - 0 - 12 1 amp £2.00
 - 100W auto 115v o/p £2.00

MOTORS - MAINS & BATTERY


- 3 - 6 volt battery motor, very small .16
- 3 - 12 volt battery motor, very low current .20
- Mains motor with gear box: 5 rev minute £2.25, 80 rev minute £3.00, 110 rev minute £2.00, 200 rev minute £1.50
- Mains motor, double ended fan motor £1.20
- Ditto single ended fan motor £1.00
- Fan blade for the above .50
- Mains motor, double ended, very powerful 1 1/2" stack £1.50
- Mains instrument motors: 1 rev 24 hours £1.50, 1 rev 1 hour £1.50, 16 rev minute £1.50, 4 rev minute £1.50, 2 rev minute £1.50, 1 rev minute £1.50



- Motor, clockwork, set up to 1 hour .20
- Motor, clockwork, set up to 1 hour with ringer £4.25
- Mains motor 1/4 h.p. 1425 revs, ex computer £1.25
- Vent opening motor with end stop switches £1.50
- 12 volt motors, Smiths, single ended 1/4" spindle £2.25
- 12 volt motors, Smiths, double ended 1/4" spindle £1.75
- 12 volt motor, P Magnet type, single ended £5.00
- 1 1/2 h.p. motor 3450 rpm 100 volt, 50Hz, New

RELAYS & RELAY BASES

- Standard open relays 3 x 8 amp c/o contacts .50
- 6 volt dc coil .90
- 110 volt ac coil .50
- 24 volt dc coil .50
- 230 volt ac coil .50
- 1 x 8 amp changeover, 230 volt AC coil .40
- Enclosed plug-in round base relays - 3 changeover contacts 50 volt coil (ex fruit machine) .40
- 110 volt coil 2 changeover .40
- 12 volt coil 3 changeover .40
- 8 pin bases, Bases for 2 changeover relay .40
- 11 pin bases, Bases for 3 changeover relay .40
- Miniature Relays: 12 volt 2 changeover .40, 12 volt 4 changeover .40, 24 volt .40, 48 volt .40

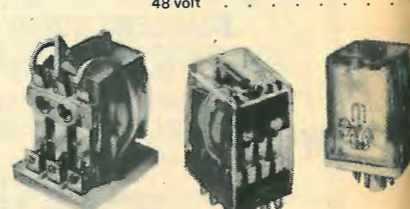


POWER SUPPLY UNITS

- In car, 12 volt for using 6 volt equipment .20
- Mains to 24 volt Mullard, Stereo .02
- Mains to 12 volt - 800 mA .03
- Mains to 50 volt 25cps for telephone ringing .05

INTERFERENCE SUPPRESSORS

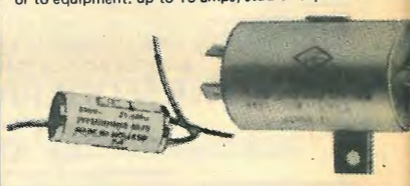- Suppressor .1 mfd 250v 50Hz side tag metal cased .25
- Condensors .1 mfd + 2 x .0005 mfd side tag metal cased .25
- .2 mfd + 2 x .0005 mfd metal cased .25
- Choke/condensator combination, stops mains interference or to equipment, up to 15 amps, stud or clip mount .25



Approximately 100 tons of stock has to be cleared right away from our big store, hence these very low price offers. Prices quoted are for bulk orders, minimum order £100, minimum any item £25. VAT and carriage are extra, although large orders not too far away will be delivered free. Contact us on this point.

Should you want a small quantity of any of the items as samples, for instance, then send listed price x 2, which will cover the VAT and postage on letter post items. For heavy items, add the amount you think, bearing in mind that the smallest parcel now costs £1.35 and a 10 kilo parcel £3.25.

We have managed to list most of the items in the store we have to empty. All goods are offered subject to being unsold and the conditions of sale are as stated, but should you want more information, please contact Mr. Bull or Mr. Stepany at Haywards Heath between 12 and 4pm. On Haywards Heath (0444) 454563.

J. BULL (Electrical) Ltd.

(DEPT. WW), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSEX RH16 3QU.

Established 30 YEARS


SWITCHES - ROCKER, TOGGLE, ETC.

- Rocker switches: white push into hole 1" x 7/16". All rated 10 amp, AC 250 volt. on/off .12, changeover centre off .15, on/off with neon .30, push to make spring return .20, push to break spring return .20
- Larger two circuit one on one off with mounting plate .20
- 13 amp rocker switch, Car Fastener (DoT) .15
- Pistol Grip Switch: with lock-on as in electric drills .30
- Interlocking Switch: blow heater, 3 rockers, 10 amp .30
- Micro switches, V3 types, 10 amp c/o contacts .20
- Mains button operated: 15 amp c/o contacts .25, 10 amp off/on .15, 15 amp off/on .15, Lever operated add .10, Lever with roller operation add .15
- Miniature types: Burgess V4T6 c/o .30
- Two mounted with roller operator .65
- Glass reed switches: 60 watt 10p, 40 watt 5p, flat multi stackable 60 watt .50
- Operating coils for reed switch multi voltage 3, 6, 9 or 12 .50
- Ceramic magnets Mullard .10
- Mini magnet .15

FERRITE RODS FOR AERIALS, ETC.

- Dia 1/2" - 4" long 15p 5" long 20p 8" long 30p
- Dia 5/16" - 5" long 20p 6" long 25p 8" long 30p
- Dia 3/8" - 4" long 20p 5" long 25p 8" long 30p
- Dia 1/2" - 6" long 35p 8" long 30p
- Ferrite slab - 3" long x 3/4" x 1/8" .20
- L & M coils for above, per set .20

TELESCOPIC AERIAL

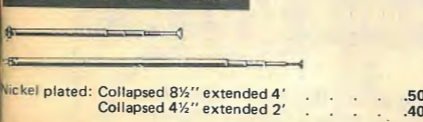- 
- Nickel plated: Collapsed 8 1/2" extended 4' .50
 - Collapsed 4 1/2" extended 2' .40

BULBS & LAMPS

- Torch bulbs, 3.5v MES Box of 25 .35
- Spot light bulbs 6.2v .3A 11mm Box of 50 £1.00
- 6.2v .3A 14mm Box of 10 .30
- 12v .5A 16mm Box of 10 .50
- Car Bulbs: 18 watt SBC .12, SBC Lamp holders .15


TAPE RECORDER PARTS

- track record/playback heads .25
- track record .45
- track erase .20
- track erase .40
- tape spool 1/2" tape .15

TRANSISTORS


- photo transistors, Mullards seconds 75% working, 100 for £5
- full wave rectifier, 440v 2 amp .20
- 50v Silicon diodes .02
- Germanium transistor 107, 109, etc. .03
- Germanium transistors .05
- Surface Barrier transistors .25

AMPLIFIERS

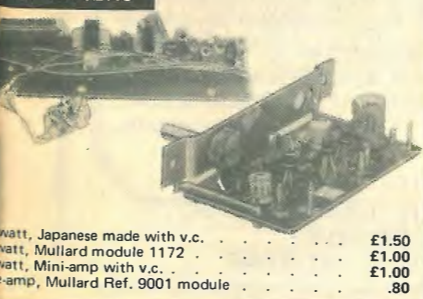- 
- 1 watt, Japanese made with v.c. £1.50
 - 1 watt, Mullard module 1172 £1.00
 - 1 watt, Mini-amp with v.c. £1.00
 - 1 watt, Mullard Ref. 9001 module .80

MISCELLANEOUS ITEMS

- 
- Neon Mains indicators, Standard .15
 - Extra small .25
 - Bench isolation mains in 230/240v output, 250W £4.50
 - Mains input, Porcelain removable fuse .20
 - Light operated switch 12 volt, Encapsulated £1.25
 - Insulating board, srpb etc. Approx 10 tons, Sheet size 4' x 4' or larger, Various thicknesses, price per lb. .50
 - Ditto, Tufnol, price per lb. £2.00
 - Aerosol can ICI Fluon lubricant .35
 - Varicap P.B. TV tuner .50
 - Battery Holder takes 6 U2 batteries, snap connector .25
 - Car Battery clips, as for charger, + and - per pair .10

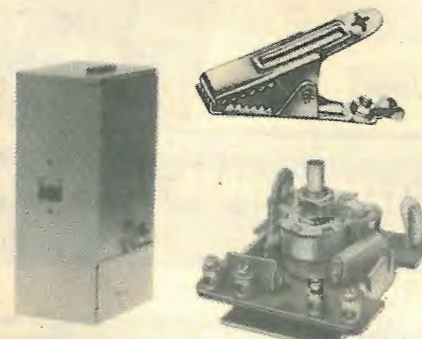


- BUY TIME SLOT METER, 10p gives 1 hour, boxed with lock and coin tray £2.00
- DIMMERS AND CONTROLLERS 1250W dimmer, Ultra ref SF20/5 £2.00

TOOLS:

- 8 ba button dies .15
- Screw driver, miniature for grub screw .10
- Small size, general purpose .08
- Solenoid mains operated AIR VALVE 200/230 volt model £2.30
- 100 volt model £1.15
- ULTRA SONIC Transmitters and receivers .25
- VALVE HOLDERS: B9A with skirt ceramic .15, B7G PTFE .25
- INSERT speaker/mike, balanced armature, 600 ohm Rewireable fuse and carrier MEM 20 amp 250 volt .28
- Magnetic Clutch, Zerex 1215494 PN 866 - 10 .90


PANEL METERS & INSTRUMENTS

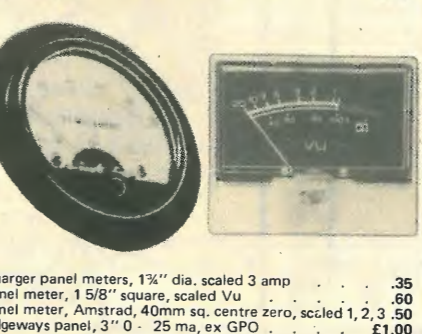
- Volt meter 0 - 200 volts 2 1/2" round £1.50
- milli amp meter, 500 ma 2 1/2" round £1.00
- amp meter, hot wire scaled 0 - 9 amps £1.20
- Ammeter, 2 1/2" round, centre zero, 500 ma £1.00




- Charger panel meters, 1 1/2" dia, scaled 3 amp .35
- Panel meter, 1 5/8" square, scaled Vu .60
- Panel meter, Armrad, 40mm sq, centre zero, scaled 1, 2, 3 .50
- Edgeways panel, 3" x 2" - 25 ma, ex GPO £1.00

SWITCHES

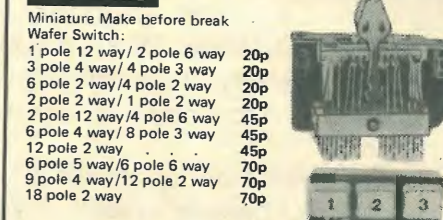- 
- Miniature Make before break Wafer Switch: 1 pole 12 watt / 2 pole 6 watt 20p, 3 pole 4 watt / 4 pole 3 watt 20p, 6 pole 2 watt / 4 pole 2 watt 20p, 2 pole 2 watt / 1 pole 2 watt 20p, 2 pole 12 watt / 4 pole 6 watt 45p, 6 pole 4 watt / 8 pole 3 watt 45p, 12 pole 2 watt 45p, 6 pole 5 watt / 6 pole 6 watt 70p, 9 pole 4 watt / 12 pole 2 watt 70p, 18 pole 2 watt 70p
 - Push/push table lamp type, better than average quality .15
 - 10 digit switch pad for telephone £1.00
 - Computer key switches, bank of 6 with knobs £1.25
 - Lever type, as used by Post Office .60
 - Push button switch bank, 9 push (6 interlocking, 3 independent locking) .40
 - 3 push switches, with integral knobs .40
 - PCB Mounting 2cm diameter 1 pole 4 watt .40

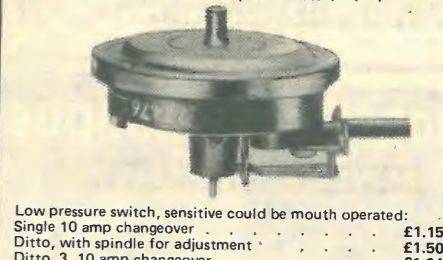

MOTORISED & AUTOMATIC SWITCHES

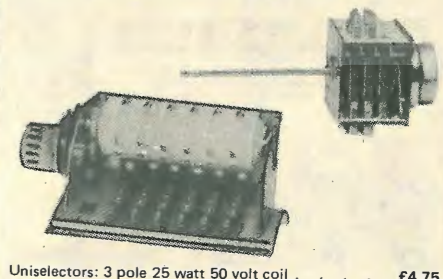- 
- Low pressure switch, sensitive could be mouth operated: Single 10 amp changeover £1.15, Ditto, with spindle for adjustment £1.50, Ditto, 3 10 amp changeover £1.64
 - Uniselectors: 3 pole 25 watt 50 volt coil £4.75, 4 pole 25 watt 50 volt coil £6.00, 2 pole miniature 25 watt £2.30
 - Motorised c/o Micro switches, Adjustable sw cams mains capacitor run motor: 4 switch £2.00, 6 switch £2.50, 8 switch £3.00, 12 switch £3.50
 - HUMIDITY SWITCH, spindle adjustable .50
 - DELAY SWITCH, A delay switch which can give delays of a few seconds to a few minutes, depending upon the voltage applied to its heater coil .50
 - WIRE WOUND POT, 25 watt 1K and 8 ohm .50



- 100K Multi turn pots .15
- Wire wound pot, with integral knob, available in values - 15 ohms, 33 ohms, 50 ohms, 100 ohms .15
- Miniature PRE-SETS, each .05

Machine Intelligence

In more ways than one, human intelligence and judgement are being built into software. Predictions from time series data, games strategies, pattern recognition... we look at these three examples of "intelligent" programs in our August issue, out now.

We review the Televideo 802 (a hard disc computer for businessmen), and the Sharp PC 1500 (a pocket micro for engineers and scientists).

And we examine stock control on an Apple and a portable version of the ever-popular Invaders game.

FOR ALL THIS AND MUCH MORE BUY PRACTICAL COMPUTING, BRITAIN'S LEADING PERSONAL COMPUTER MAGAZINE.

AUGUST ISSUE OUT NOW

80p AT YOUR NEWSAGENT'S - BUT HURRY

Practical Computing

80p

Hitachi Oscilloscopes

performance, reliability, exceptional value and immediate delivery!

Hitachi Oscilloscopes provide the quality and performance that you'd expect from such a famous name, in a range that represents the best value for money available anywhere.

V-152	15MHz Dual Trace	V-650	60MHz Dual Trace, Dual Timebase
V-202	20MHz Dual Trace	V-1050	100MHz Quad Trace, Dual Timebase
V-302	30MHz Dual Trace	V-209	20MHz Dual Trace, Portable
V-352	35MHz Dual Trace	V-509	50MHz Dual Timebase, Portable

Prices start from around £235 and we hold the range in stock for immediate delivery.

For colour brochures giving detailed specifications and prices, ring 0480 63570. Reltech Instruments, 46 High Street, Solihull, W. Midlands B91 3TB

WW - 60 FOR FURTHER DETAILS

RADFORD

Audio Measuring Instruments, Audio Amplifiers, Loudspeakers and Loudspeaker Components for the professional and enthusiast

RADFORD AUDIO LTD.

10 BEACH ROAD
WESTON-S-MARE, AVON BS23 2AU
TEL. 0934 416033

WW - 058 FOR FURTHER DETAILS

P.&R. COMPUTER SHOP

IBM GOLFBALL PRINTER 3982, £70

EPSON MX-80 80.GPs 3982 IBM I/O PRINTERS DOT MATRIX PRINTER WITH SPECIAL INTERFACES. VDUs, ASCII KEYBOARDS, ASR, KSR, TELETYPEs, PAPER TAPE READERS, PAPER TAPE PUNCHES, SCOPES, TYPEWRITERS, FANS 4" 5" 6". POWER SUPPLIES, STORE CORES, TEST EQUIPMENT AND MISCELLANEOUS COMPUTER EQUIPMENT. OPEN: MONDAY TO FRIDAY 9 a.m.-5 p.m., SATURDAY TILL 1 p.m.

COME AND LOOK AROUND
SALCOTT MILL, GOLDHANGER ROAD
HEYBRIDGE, ESSEX
PHONE MALDON (0621) 57440

WW - 049 FOR FURTHER DETAILS

SAMSONS

(ELECTRONICS) LTD.
9-10 Chapel Street, Marylebone
London NW1 5DN
21-23 Bell Street, London, NW1
01-262 5125 & 01-723 7851

MUFFIN FANS SPECIAL OFFER!!!

240v fans 4 1/2x4 1/2x1 1/8" £3.75 inc. VAT + postage.
110v fans 4 1/2x4 1/2x1 1/8" £4.75 inc. VAT + postage.
Radiospare price £14.50!!!

SPECIAL OFFER: VARIABLE TRANSFORMERS

Brand new, boxed, input 240V, output 0-265 volts 5 amps. Base or panel mounting with calibrated dial 0-265 volts and control knob. Price £28, inc. carr. and VAT.

SPECIAL OFFER: HIGH POWER AMPLIFIER TRANSFORMERS

Pri tapped 120-240V sec tapped 34-29-0-29-34V 6 amps and 46V 1A. Open frame type. Tag connection. Size 5x4 1/2x4ins. £3 inc. postage and VAT.

LATEST PURCHASE. COMPUTER GRADE TRANSFORMERS.

Conservatively rated. All Primaries 220-240V. No. 1 sec. 27V 10A, 9V 3A, 15V 12A x 2. Separate windings. £5.50, P&P £1.50.
No. 2 sec. tapped 26-31-36V, 11.2A £12, P&P £2.
No. 3 sec. 36V 6A £8.50, P&P £1.50.
No. 4 sec. 43V 3A £4.75, P&P £1.50.
No. 5 sec. 24V 2A £2.75, P&P £1.25.
No. 6 sec. 27.5-0-27.5V 1.2A and 7-0-7V 0.75A £3.50, P&P £1.25.
No. 7 17V 1A £2 P&P 75p.
No. 8 13V 3A and 15V 1A £3.50, P&P £1.25.
No. 9 18V 2A £2.50, P&P £1.
No. 10 sec. 29-28-27-0-27-28-29V 350 M/A "C" Core £3, P&P £1.
No. 11 sec. 10-7-0-7-10V 0.6A and 29-21-0-21-29V 1A £3, P&P £1.
No. 12 27V 1A 22V 1A 10V 1A, 4 separate windings "C" core type. £4.95, P&P £1.50.
No. 13. 65V 1A and 18-24V 1/2A £3.95, P&P £1.50.
No. 14. Tapped 12-15-27V 1A £2, P&P 75p.
No. 15. 6.3V 600M/A 6.3V 330M/A 6.3V 20 M/A 8V 500 M/A 50V 40 M/A £2, P&P £1.
No. 16. Tapped 14-15-16V 2A £2, P&P £1.
No. 17. Tapped 36-37-38-39-41-42-43V 1A "C" core £2.75, P&P £1.

CRESSALL RHEOSTATS

Type S 150 4 ins. dia. 650 ohms 150 watts new and boxed £1.90, P&P 95p, VAT 29p, 1500 ohms 25 watts 1 1/2 ins. dia. £1, P&P 50p, VAT 29p, 5000 ohms 2 1/2 ins. dia. £1, P&P 50p, 50 ohms 12 1/2 watt 3/4in. dia. £1, inc. post, VAT 15p.

ISOLATION TRANSFORMERS

Pri tapped 220-240V sec. 240V 500 watts Open frame type, top panel connections. Ex-equipment, but in perfect condition. £15 inc. carr. £3, VAT £2.70.

BERCO VARIABLE TRANSFORMERS

Type 42A panel mounting, input 240V, output 0-270V 2A with control knob. Ex-equipment, but in perfect condition, £10, P&P £2.50, VAT £1.88.

DC WKG BLOCK CAPACITORS

8 MFD 1000V DC WKG £3, P&P £1, VAT 25p, 8 MFD 350V DC WKG £1.25, P&P 50p, VAT 25p, 4 MFD 500V DC WKG £1, P&P 50p, VAT 22p, 2 MFD 600V DC WKG £0.90, P&P 20p, VAT 12p, 1 MFD 1000V DC WKG £0.50, P&P 20p, VAT 12p, 1 MFD 600V DC WKG 5 for £1.50, P&P 50p, VAT 30p, 0.25 MFD 500V DC WKG 5 for £1.25, P&P 50p, VAT 16p, 0.1 MFD 1500V DC WKG 5 for £1.25, P&P 50p, VAT 15p, 2 MFD 100V DC WKG 10 for £1.50, P&P 75p, VAT 33p, Tubular metalised paper caps 20 MFD 350V DC WKG with clip £3, P&P 50p, VAT 52p.

LOW CURRENT LT TRANSFORMERS

Open frame clamped type, split bobbin. All primaries 240V No. 1 sec tapped 12-15-20-24-30V 750 M/A £4, No. 2 sec. 9-0-9V 1A and 6.3V 200 M/A £2.50, No. 3 15-0-15V 600 M/A and 6.3V 200 M/A, No. 4 sec. 12-0-12V 750 M/A and 6.3V 200 M/A £4, No. 5 sec. 13V 1/2A £1.50, No. 6 sec. 8V 1/2A 6.3V 600 M/A, 6.3V 300 M/A 50V 40 M/A £2.50, No. 7 sec. 17V 1/2A (DC) £1.75, No. 8 sec. 16.5V 1/2A x 2 £1.75, No. 9 sec. 18V 2A £4, No. 10 sec. 24V 2A £4.50, No. 11 sec. 15V 2A £3.50. All prices include postage and VAT.

SPECIAL OFFER!!! PARVALUX GEARED MOTORS

Cap start 240V AC RPM 44. Torque 4lb./ins., fitted with small cog on output shaft. Ideal for garage door opener or curtain pulley. Our price £8.95 inc. carr. and VAT.

MONITORS

Ultronics 12" monochrome monitor 750 ohm Video in Video out circuit breaker protected, housed in stylish case with side mounted controls. A must for home computer users. Only a few left!! £45 inc. VAT. Callers only.

HIGH GRADE TRICKLE CHARGERS

Input 240V AC. Output 12V DC 2 Amps. With mains lead, red and black battery leads with attached clips. Completely fused. Housed in wall mounting, steel case size 6x4 3/4x4in. £4.50, P&P £1.50 plus VAT. Total £6.90.

BLOCK PAPER CAPACITORS

8 MFD 1000V DC WKG £3, P&P £1, 8 MFD 350V DC WKG £1, P&P 50p, 6 MFD 350V DC WKG £75, P&P 25p, 6 MFD 300V AC WKG £1.50, P&P 50p, 4 MFD 350V DC WKG 50p, P&P 25p, 2 MFD 350V DC WKG 40p, P&P 20p, 1 MFD 1000V DC WKG 50p, P&P 20p.

SPECIAL OFFER HEAVY DUTY TRANSFORMERS

Pri 240V sec 50V 15 Amps. Twice will give 100V CT or 50V 30A. Open frame type. Terminal block primary. Sec heavy wire leads. Frame size 8 1/2x7 1/2 inches. Screen winding between pri and sec. Brand new, fraction of list price. £32, carr. £5, VAT £5.55.

HEAVY DUTY LT C CORE TRANSFORMERS

Pri 110-220-240V. Secs 14V, 3V, 12V, 1V. Separate windings. All at 40 Amps. 14-15-15 1/2-17-18-18 1/2-19-19 1/2V can be obtained. £25, carr. £4, VAT £4.35.

IMPORTANT NEWS!!!

We would like to announce the opening of our new branch at 21-23 BELL STREET, NW1. It will, of course, stock our fantastic range of products that have made us famous over the past 25 years. PLUS!! many new ranges, i.e. computer and electronic components, test equipment, panel meters, multimeters, semi-conductors, ICs and a large selection of plugs and sockets.

WHY NOT PAY US A VISIT - IT COULD SAVE YOU POUNDS!!!

Pri tapped 220-240V sec. 240V 500 watts Open frame type, top panel connections. Ex-equipment, but in perfect condition. £15 inc. carr. £3, VAT £2.70.

HEAVY DUTY ISOLATION TRANSFORMERS

240-240V ex-computer equipment. Large selection available 10-15 amps. Fraction of maker price. Telephone for further details.

SPECIAL OFFER OF ERIE ELECTROLYTIC CAPACITORS

22,000 MFD 63V WKG £4.50 inc. postage and VAT, 6800 MFD 100V DC WKG £2.50 inc. postage and VAT, 3000 MFD 150V DC WKG £2.50 inc. postage and VAT, 10,000 MFD 16V DC WKG five for £2.50 inc. postage and VAT, 100 MFD 25V DC WKG 10 for £1, inc. postage and VAT, 4.7 MFD 50V DC WKG 10 for 75p, inc. postage and VAT, 22,000 MFD 10V DC WKG 5 for £2.50, inc. postage and VAT.

SPECIAL OFFER LT TRANSFORMERS


Computer grade Pri 115-230V sec 27V 10A, 9V 3A, 15V 0.5A, 15V 0.5A, 15V 0.5A, 17.5V 100 M/A. Separate windings, open frame type, top panel connections, £3.95, postage £2.40, VAT 94p.

LATEST PURCHASE. COMPUTER GRADE T TRANSFORMERS.

All primaries 240V. No. 1 sec. 26V 6A £8.50, carriage £1.50, No. 2 sec. tapped 26-31-36V, 11.2A £12, P&P £2.
No. 3 sec. 36V 6A £8.50, P&P £1.50.
No. 4 sec. 43V 3A £4.75, P&P £1.50.
No. 5 sec. 24V 2A £2.75, P&P £1.25.
No. 6 sec. 27.5-0-27.5V 1.2A and 7-0-7V 0.75A £3.50, P&P £1.25.
No. 7 17V 1A £2 P&P 75p.
No. 8 13V 3A and 15V 1A £3.50, P&P £1.25.
No. 9 18V 2A £2.50, P&P £1.

PLEASE ADD VAT

D MARKETING Ltd.

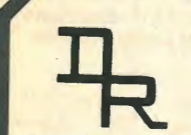

SERIES 600
The D&R SERIES 600 range of professional mixing consoles has found its way into hundreds of (hospital) broadcast studios, discotheques, clubs, entertainment and outdoor Public Address systems and recording studios. Available in 6, 12, 18 or 24 channel configuration with, as standard, separate balanced mic. and line inputs, insertion points, gain, three band tone controls, two auxiliary lines, pan-pot and linear fader, plus pre-fade-listening and overload LED per channel. The output section includes four master faders, echo return and phones controls and two large V.U. meters. Optional XLR-3 connectors, 48 volt phantom powering, stereo channels with R.I.A.A. correction, talkback, fader controlled start switches, balanced outputs and 24 volt D.C. mains powering are available.

D&R Electronica was founded over 10 years ago with the aim of developing and manufacturing high quality mixing consoles for the studio and entertainment industry with a special emphasis on value for money design engineering. The result is a range of five basic models with a large number of channel configurations and options. All models are highly flexible in use and give the best quality possible at today's state of technology.
SERIES 200 - A small mixer specially designed for four track recording.
SERIES 600 - A range of mixers for live amplification, broadcast studios and two track recording.
SERIES 400 - 'In-Line' mixing consoles for budget 4, 8 or 16 track recording.
SERIES 1000 - A range of comprehensive 'In-Line' consoles for professional recording studios.
SERIES 8000 - Top of the range 'In-Line' consoles with integral patch bay for top recording studios. A large number of ancillary signal processing units complement the D&R programme.

Please complete this coupon for further details:-

- D&R Series 200
- D&R Series 400
- D&R Series 8000
- D&R Series 600
- D&R Series 1000
- D&R Ancillary Equipment

- BULLET loudspeaker components
- VITAVOX loudspeaker equipment
- HELIOS mirror balls

NAME _____
ADDRESS _____

D.S.N. MARKETING LTD, Westmorland Road, London NW9 9RJ
Telephone: 01-204 7246. Telex: 895 4243.
Trade, Wholesale, O.E.M. & Export enquiries welcome.



WW - 070 FOR FURTHER DETAILS

DAROM SUPPLIES Dept. AW - Tel: (0925) 64764

4 Sandy Lane, Stockton Heath
Warrington, Cheshire, WA4 2AY

sabtronics

FREQUENCY METERS

8 digit:

- ★ Convenient single input for entire range
- ★ Big easy to read LED display
- ★ Excellent sensitivity
- ★ 10MHz crystal controlled timebase
- ★ Battery or mains operated
- ★ 3 switch selectable gate times
- ★ Leading zero suppression

8110A..... 20Hz-100MHz£67
8610A..... 20Hz-600MHz£82



9 digit:

- ★ 9 digit resolution for more precise readings
- ★ Excellent 30mV sensitivity up to 1Ghz
- ★ 3 switch selectable gate times
- ★ 10 MHz crystal controlled timebase
- ★ 2 separate inputs for added versatility
- ★ Front panel sensitivity control
- ★ Battery or mains operated

8610B..... 10Hz-600MHz£99
8000B..... 10Hz.....1000MHz.....£155

WW - 72 FOR FURTHER DETAILS

HANDHELD MULTIMETERS
High quality, precision 3 1/2 digit LCD DMMs with excellent price performance value



2033.....£36.75
AC/DC 100µV-1000V
AC/DC 10µA-2A
Ohms 1Ω-20MΩ
2035.....£62
AC/DC 100µV-1000V
AC/DC 0.1µA-2A
Ohms 0.1Ω-20MΩ

Add 15% V.A.T. on all prices - prices correct at 1-5-82 - E&OE cash with order or credit card - Carriage £5 for Express Delivery

VHF FM MOBILE RADIO

! And it's British !

MODEL CT210

- ★ APPROVED TO MPT 1301
- ★ MODULAR CONSTRUCTION
- ★ RANGE OF ACCESSORIES



MODEL CT210

- ★ MADE IN U.K.
- ★ COMPETITIVE PRICE
- ★ MULTI-CHANNEL CAPABILITY

Export and Dealer Enquiries Welcome

COM-TEK (MIDS) LTD. 506 Alum Rock Road - Birmingham B8 3HX

Telephone: 021-326 6343

Telex: 337000

WW - 061 FOR FURTHER DETAILS

UNITS

TYPE 9045	VMOS WIDEBAND LINEAR POWER AMPLIFIER. 30 KHz-60 Mhz. without tuning. 4 watts max. RF output. Increases power output by 10 times and may be used in series for more gain and lower drive level.	£49.50 £2.00
TYPE 9050	VMOS WIDEBAND LINEAR POWER AMPLIFIER. 20-200 Mhz. 4 watts max. RF output.	£49.50 £2.00
TYPE 9054	VMOS LINEAR POWER AMPLIFIER. 20 watts RF output. 1-250 Mhz.	£85.00 £4.00
TYPE 9030	WIDEBAND RF PREAMPLIFIER. 1 KHz-100 Mhz. without tuning. N.F. 3.0 dB. Gain 40 dB. Increases sensitivity of instruments by 100 times.	£29.50 £1.50
TYPE 9056	1500 Mhz. FREQUENCY DIVIDER BY 10. Divides input frequencies in the range 100-1500 Mhz. by 10.	£59.50 £1.50
TYPE 9025	RF PREAMPLIFIER. Aligned to your specified frequency in the range 1-250 Mhz. N.F. 1.0 dB. Gain 40 dB. adjustable - 40 dB. Masthead/lab. use.	£29.50 £1.50
TYPE 9025/FM BAND II	88-108 Mhz. N.F. 1.0 dB. Gain 40 dB. adjustable - 40 dB. masthead/lab. use.	£29.50 £1.50

COMPONENTS

GASFET Transistors NEC NE 72089 N.F. 0.6 dB. at 500 Mhz. 0.8 dB. at 1.3 Ghz. 1.3 dB. at 4 Ghz. £30.00
UHF Dual-Gate Mosfet BF 960 N.F. 2.8 dB. at 800 Mhz. Gain 18 dB. £3.50
RCA 40673 Mosfet 80p
Varicaps: Thomson-CSF BB204 80p
Motorola MV104 80p
Shottky Diodes: Motorola MBD101 60p
Pin Switching Diodes: Thomson-CSF BA182 50p
BA244 70p

Voltage Regulators: 12V. 1A. 7812..... 80p
12V. 5A. 78H12..... £6.00
15V. 5A. 78H15..... £6.00
Variable Voltage Regulator: 1.5A. 1.2 to 37V. LM317K..... £3.00

Synthesizer Signetics: HEF 4750VD..... £25.00
HEF 4751VD..... £25.00
Opto-isolators Darlington..... £1.50
Electronic Attenuators..... £1.00
Mullard 808 Film Dielectric Trimmers 2-22 pf..... 20p

Siliconix: U350..... £11.00
E430..... £3.50
E177..... £1.20
MC1590G..... £3.00
National: LM370..... £4.00
LM380..... £1.00

POST AND PACKING 50p - PLEASE ADD V.A.T. 15% ON TOTAL

ALL COMPONENTS AND UNITS ABOVE IN STOCK FOR IMMEDIATE DESPATCH
RESEARCH COMMUNICATIONS LIMITED
43A COURT STREET, FAVERSHAM, KENT ME13 7AL

WW - 020 FOR FURTHER DETAILS

LANGREX SUPPLIES LTD
Climax House, Fallsbrook Rd., Streatham, London SW16 6ED
RST Tel: 01-677 2424 Telex: 946708 RST

SEMICONDUCTORS			VALVES			INTEGRATED CIRCUITS						
AA119 0.12	AS215 1.38	BC172 0.13	E130L 19.39	EF86 1.74	GXU1 16.10	PC97 1.38	QY5-3000A 1.38	UL84 1.38	4B32 29.16	6CW4 8.83	12BE6 2.79	5670 5.18
AA300 0.20	AS216 1.27	BC173 0.13	E180CC 11.39	EF89 1.84	GXU2 28.43	PC90 1.38	QZ06-20 34.16	UM80 1.15	4B32 29.16	6DK6 3.00	12BH7 1.29	5675 21.47
AA320 0.48	AS217 1.15	BC177 0.32	E182CC 13.80	EF92 1.07	GXU4 32.77	PC84 1.15	R10 5.75	UY41 1.44	4CX250B 51.75	6D6B 4.49	12E1 19.26	5687 6.31
AA330 0.17	AS220 2.64	BC178 0.16	E188CC 9.40	EF93 1.15	GXU5 31.77	PC85 1.38	R18 1.89	UY85 1.20	4CX300A 80.50	6EA8 3.38	12E11T 19.26	5696 4.35
AA315 0.17	AS221 2.88	BC179 0.32	E201 25.88	EF95 1.22	GZ32 1.44	PC89 1.56	R19 1.38	XG1-2500 28.75	4X150A 24.41	6EB8 2.44	12E14 34.50	5725 5.62
AA217 0.17	AS222 2.88	BC182 0.13	E280C 9.02	EF98 1.67	GZ33 1.46	PC88 1.51	R20 1.66	XG2-6400 113.50	5B254M 23.72	6F6 1.73	13E1 123.05	5726 3.62
AC107 0.63	AUY10 2.88	BC183 0.13	E288CC 18.54	EF183 0.92	GZ34 2.46	PC89 1.51	RG-250 35.77	XG5-500 28.23	5B254M 23.72	6F6 1.73	14E1 28.75	5727 6.47
AC125 0.29	BA145 0.15	BC184 0.13	E300 12.58	EF184 0.96	GZ37 4.60	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC126 0.29	BA148 0.17	BC212 0.13	E300 12.58	EF185 1.25	KT61 4.62	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC127 0.29	BA154 0.12	BC214 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC128 0.35	BA156 0.12	BC238 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC141 0.32	BA155 0.13	BC237 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC141K 0.40	BA156 0.12	BC238 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC142 0.32	BA156 0.12	BC238 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC142K 0.40	BA156 0.12	BC238 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC176 0.35	BAW62 0.06	BC301 0.38	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC176 0.35	BAX13 0.07	BC303 0.39	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC107 0.18	BC308 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC188 0.32	BC108 0.18	BC327 0.14	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC109 0.18	BC328 0.14	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC114 0.17	BC338 0.14	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC115 0.21	BCY30 1.44	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC116 0.22	BCY31 1.73	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC117 0.26	BCY32 1.73	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC118 0.21	BCY33 1.27	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC119 0.21	BCY34 1.15	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC120 0.21	BCY39 3.91	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC135 0.17	BCY40 3.22	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC136 0.22	BCY42 0.35	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC137 0.22	BCY43 0.35	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC147 0.14	BCY58 0.22	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC148 0.14	BCY70 0.20	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC149 0.15	BCY71 0.21	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC157 0.15	BCY72 0.20	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC158 0.15	BCZ11 2.01	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC159 0.15	BCZ12 0.16	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC167 0.13	BD121 1.96	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC170 0.13	BD123 3.22	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AC187 0.32	BC171 0.12	BD124 2.30	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AD149 2.88	BC172 0.13	BD125 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AD161 0.40	BC173 0.13	BD126 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AD162 0.40	BC174 0.13	BD127 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51	RG-1250 63.94	XG2-6400 113.50	5B254M 23.72	6F6 1.73	14E1 28.75	5749 5.14
AF106 0.40	BC175 0.13	BD128 0.13	E300 12.58	EF185 1.25	KT66 11.50	PC88 1.51</						

Enquiry Service for Professional Readers ONLY.

WIRELESS WORLD Wireless World, August 1982 WW 268

WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW
WW	WW	WW

Please arrange for me to receive further details of the products listed, the appropriate reference numbers of which have been entered in the space provided.

Name

Position in Company

Name of Company

Address

Telephone Number

Nature of Company/Business

No. of employees at this establishment

VALID FOR SIX MONTHS ONLY

CUT HERE

Postage will be paid by Licensee

Do not affix Postage Stamps if posted in Gt Britain, Channel Islands, N Ireland or the Isle of Man

BUSINESS REPLY SERVICE
Licence No 12045

WIRELESS WORLD
Reader Enquiry Service
429 Brighton Road
South Croydon
Surrey CR2 9PS

CUT HERE

Wireless World Subscription Order Form Wireless World, August 1982 WW 268

UK subscription rates
1 year: £12.00
Overseas 1 year: £15.00

USA & Canada subscription rates
1 year: \$39.00

Please enter my subscription to Wireless World for 1 year

I enclose remittance value made payable to
IPC BUSINESS PRESS Ltd.

Name

Address



BEFORE



AFTER!

PUT A SMILE BACK ON YOUR OLD AVOMETER!

Send it now for estimate, repair or recalibration

Quick turn round on estimates/repairs

Large stocks of new AVOMETERS

Avo Sales and Service

Farnell International

Farnell International Instruments Ltd.,
Sandbeck Way, Wetherby
West Yorkshire LS22 4DH

Tel 0937 61961 Telex 55478 Farint G

WW-004 FOR FURTHER DETAILS

ELECTRIC SHOCK

2 WAYS TO RECOVERY

ACT AT ONCE - DELAY IS FATAL

ELECTRIC SHOCK ACT AT ONCE - DELAY IS FATAL

make sure it is safe to approach
If the casualty is not clear of the source of the shock break the contact by switching off the current, removing the plug or unscrewing the cable fuse. If this is not possible stand on dry insulating material (rubber mat, brick, thickly layered newspaper, bank) and try to push or pull the casualty clear of the contact using suitable insulating material (woolens, broomstick) or a long thin rod (push him with bare hands).

If the casualty is breathing
Place casualty in the recovery position and call medical aid.

If the casualty is NOT breathing
Get someone to call medical aid while you start artificial respiration - speed is essential

start artificial respiration - speed is essential

1. Check airway: Remove any obstruction. Tilt the head back and pull the chin up.
2. Press head well back with one hand and pull the chin up with the other.
3. Take a deep breath, pinch nostrils together with your fingers, seal your lips around his mouth and blow air steadily into his lungs. Repeat this every 5 seconds.
4. Remove mouth and watch chest fall. Repeat and continue inflations at your natural rate of breathing. When casualty starts breathing place him immediately in the recovery position.

IF AFTER FOUR INFLATIONS casualty does not respond to artificial respiration

Check correct pulse rate of the neck and pupils of eyes. If the pulse is absent the victim is dead and the pupils dilated this means that the casualty's heart has stopped beating. Give the casualty a decisive thumb on the lower part of the breastbone - right to the left with a clenched fist.

external heart compression

Feel for the lower half of the breastbone. Place the heel of your hand on this part of the bone slightly to the left, keeping palm and fingers all the time. Cover this hand with the heel of the other hand with arms straight, feet spread, pressing down on the lower half of the breastbone. Do this 15 times - once per second and then give the casualty five inflations.

Check the pulse again. If it is present continue with inflations until casualty breathes on his own. Then place immediately in the recovery position. If the pulse is absent start external heart compression.

on recovery continue to watch casualty carefully as breathing may stop. If it does turn casualty on his back and start respiration again.

Display the ELECTRICAL REVIEW shock first aid chart (356x508mm) supplied in thousands to destinations world-wide. Recent deliveries include consignments to companies in Papua New Guinea, Dubai, United Arab Emirates, The Philippines, apart from UK commercial and industrial, educational, Central Government, Local Authorities' orders.

Carry the ELECTRICAL REVIEW pocket-size shock card (92x126mm) designed to help safety and training officers, medical and welfare personnel; all who might find themselves called to save a life. Always pocket your card; there's a useful two-year calendar on the back.

GET IT - READ IT - PRACTISE 1-4
BE READY TO SAVE A LIFE.
SOMEONE MIGHT SAVE YOURS.

ACT AT ONCE - DELAY IS FATAL!

To IPC Electrical-Electronic Press Ltd.,
General Sales Department,
Room 205,
Quadrant House,
Sutton, SM2 5AS,
Surrey,
England.

Company registered in England
No 677128. Registered Office
Quadrant House, The Quadrant,
Sutton, Surrey SM2 5AS

Please send.....copy/copies as indicated

Pocket Card @ 70p each inc VAT

Paper Chart @ 70p each post free

Card Chart @ £1.40 each post free

Plastic Chart @ £2.10 each post free

Discounts: 100 + copies 10%
500 + copies 15%

(Overseas surface and air mail rates supplied on application.)

BRITAIN'S BETTER BARGAIN STILL IN WORLD-WIDE DEMAND

WIRELESS WORLD CIRCARDS at 1976 prices 10% discount for 10 sets! Most sets are still available even though the companion volumes CIRCUIT DESIGNS 1, 2 and 3 are out of print. (CIRCARDS SETS 1 to 30).

wireless world circard Set 14: Digital counters—1

Basic binary counters

Typical data
 $V_{CC} = 12V$
 $R_1, R_2 = 3.3k\Omega - 10^4$
 $R_3, R_4 = 2.2k\Omega - 10^4$
 $R_5, R_6 = 6.8k\Omega - 10^4$
 $C_1, C_2 = 100pF$
 $D_1, D_2 = PS10$
 Frequency 100kHz typically
 Trigger input $\approx 4V$
 Trigger input width $< 1\mu s$

Circuit operation

The bistable circuit is a T-type "flip-flop" in which the output changes state for a negative-going transition at the trigger input. If the base-drive current is arranged so that T_1 is in saturation, its collector voltage will be about 0.2V. This is too low to forward-bias the base-emitter junction of T_2 , about 0.7V, and hence T_2 will be off. This means its

as D_1 is forward-biased. The anode of D_1 is approximately at $V_{CC}/2$ and because its cathode is connected to a high potential via R_5 it is reverse-biased. Therefore T_1 collector current is reduced, causing a rise in its collector voltage, increasing base-drive current to T_2 . This causes T_2 collector voltage to drop and T_2 base current decreases causing a further increase in T_1 collector voltage. The process continues until the other stable state, T_2 conducting and T_1 off, is sustained. The next negative-going trigger pulse resets the circuit to its previous state. It produces one output pulse for every two trigger pulses. The interconnection of these bistable circuits to give a binary ripple counter demands that the

Q output of a previous flip-flop is connected to the trigger (or T-) input of the next flip-flop. This gives a natural count of 2^n where n is the number of stages, and 2^n is the number of states through which the counter progresses.

Circuit modification
 Range of R_1, R_2, R_3, R_4 to 47k Ω
 Frequency variation: 150 to 300kHz
 Range of C_1, C_2 330 to 3300pF
 Frequency variation: 140 to 90kHz
 Increase turn-on speed with capacitors across resistors R_5 and R_6 typically 5 to 20% of C_1, C_2 .
 Increased frequency of operation possible with additional diodes connected

- 1 Basic Active filters
- 2 Switching Circuits, comparators and Schmitts (But these gaps cannot be filled)
- 6 Constant current circuits
- 7 Power amplifiers
- 8 Astable circuits
- 9 Optoelectronics
- 10 Micro power circuits
- 11 Basic logic gates
- 12 Wideband amplifiers
- 13 Alarm circuits
- 14 Digital Counters
- 15 Pulse modulators
- 16 Current differencing amplifiers—signal processing
- 17 Current differencing amplifiers—signal generation
- 18 Current differencing amplifiers—measurement and detection
- 19 Monostable circuits
- 20 Transistor pairs
- 21 Voltage-to-frequency converters
- 22 Amplitude modulation and detection
- 23 Reference circuits
- 24 Voltage regulators
- 25 RC oscillators—1
- 26 RC oscillators—2
- 27 Linear cmos—1
- 28 Linear cmos—2
- 29 Analogue multipliers
- 30 Rms/log/power laws
- 31 Digital multipliers
- 32 Transistor arrays
- 33 Differential and bridge amplifiers
- 34 Analogue gate applications—1
- 35 Analogue gate applications—2.

To IPC Electrical - Electronics Press Ltd.
 General Sales Department,
 Room 205,
 Quadrant House,
 Sutton,
 Surrey SM2 5AS

Company registration in England
 Quadrant House, The Quadrant,
 Sutton, Surrey SM2 5AS
 Reg. No 677128

Please send me the following sets of
 Circards: £2 each,
 £18 for 10 post free.
 Remittance enclosed..... payable
 to IPC BUSINESS PRESS LTD.

Name (Please print).....
 Address (Please print).....

Fill gaps in your circuit files with these sets of 127 x 204 mm cards in plastic wallets. These unique circuit cards normally contain descriptions and performance data of 10 tested circuits, together with ideas for modifying them to suit special needs.

COMPUTER WAREHOUSE

THE 'ALLADINS' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Diablo/DRE Series 30 2.5 mb. fully refurbished DEC RK05 media and software compatible. Front load £550.
 Top load £295.
 PSU for 2 drives £125.
 Diablo-Dre 44A-4000A or 4000B 10 mb 5+5 removable pack new and refurbished from £995.
 CDC 80 mb removable pack DEC RM03 media and software compatible brand new from £2,950.
 Honeywell 5+5 10 mb drives £450 good s/h condition.
 For more information on controllers, expansions and ready to go sub systems contact sales office.

DISTEL ©

The UK's FIRST free of charge, 24 hr. public access data base. Get information on 1000's of stock items and order via your computer and credit card. On line now, 300 baud. CCITT tones, full duplex, fully interactive.
DON'T MISS THOSE BARGAINS CALL NOW, IT'S FREE!
 7 days per week 24 hrs. per day
01-683 1133

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU. Mains filtering and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing 1000's of pounds, and designed to run 24 hours per day. The PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The unit is fully enclosed with removable top lid, twin fan cooling, mains filtering, trip switch, 'power on' and 'run' LED's, aluminium front panel and rear cable entries. Give your system that professional finish for only £49.95 + £9.50 carr. — Dim. 19" wide 16" deep 10.5" high. Usable area 16" w. 10.5" h. 11.5" d. Units are in good but used condition 240 or 110 working—complete with data. Large stocks of PDP8 spares—enquire.

COOLING FANS

Keep your "Hot Parts" cool and reliable with our range of professional fans.
 ETRI 99XU01 Miniature equipment fan 240 vac working DIM 92 x 25 mm BRAND NEW complete with finger guard. Makers price £16 our price £9.95
 BUHLER 69.11.22 micro miniature 8-16 v DC reversible fan. Measures only 62 x 62 x 22 mm. Uses a brushless DC servo motor almost silent running ideal portable equipment, life in excess of 10,000 hours. BRAND NEW manufactures price £32.00 our price £12.95
 MUFFIN/CENTAUUR cooling fans DIM 120 x 120 x 38 mm tested ex equipment 240v £6.25 115v £4.95 + p&p £1.90
 KOOLTRONICS Powerful snail type blower gives massive air movement with centrifugal rotor DIM as a cube 8" x 8" x 6" air aperture 2.5" x 2.5" with flange fixing. BRAND NEW 110v 50Hz ac working ONLY £9.95 + £1.90 p&p




8" FLOPPY DISK DRIVES

Unbelievable value the DRE 7100 & 7200 8" disk drives utilise the finest technology to being our PRICE and the superb manufacturing quality. The 7100 single sided & 7200 double sided drive accept hard or soft sectoring, IBM or ANSI standard giving a massive 0.8 MB (7100) & 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMENS etc compatible. Supplied BRAND NEW with user manual and 90 day warranty.
 7100 single sided £225.00 + 9.50 + vat
 7200 double sided £295.00 + 9.50 carr + vat
 full technical manual £20.00 alone £9.00 with drive, refund of difference on purchase of drive.
 SHUGART s/h 800-2" Drive's 110v 50Hz motor £160 + £9.50 carr.
 Removed from working equipment but untested. SA120 Alignment disk's £9.95

9" Monitors

DT10 Monitor a complete MOTOROLA 9" video monitor housed in an attractive metal case DIM approx. 10" deep 16" wide and 11" high. The monitor has a 75 ohm composite video input with a bandwidth of 18 mhz. A separate internal PSU delivers 5v dc for external use and 12v DC for video monitor. The case has sufficient room inside for mounting other units such as 5" disk drives etc. Internal pots give full control over all monitor functions. Supplied in a tested, as new or little used condition. 240v AC operation £55.00 Carriage and Insurance £10.50
 MOTOROLA 9" open chassis monitor. Standard 240 v AC with composite 75 ohm video input, bandwidth in excess of 18 mhz. Monitors are ex equipment and although unguaranteed they are all tested prior to despatch, and have no visible burns on the screens. Dim approx. 9" x 9" x 9". Supplied complete with mains and input lead. Ideal ZX81 etc or giving the tele back to the family!! Black and white phosphor £35.00 + £9.00 Carr.

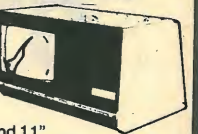

SUPER SCOOP



CENTRONICS 739-2
 The "Do everything Printer" at a price that will NEVER be repeated. Standard Centronics interface, full graphics, 4 type fonts with high definition & proportional spacing for word processor applications, 80-132 columns, single sheet, roll or sprocket paper handling plus much more. Available only from DISPLAY ELECTRONICS at a ridiculous price of only £299.00
 Options: carriage & insurance £10.00
 Interface Cable £10.00
 RS232 Converter £45.00
SAVE £250

TELETYPE ASR33 I/O TERMINALS

FROM £195 + CAR. + VAT
 Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry. RS232 serial interface. 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order
 Options: Floor stand £12.50 + VAT
 KSR33 with 20ma loop interface £125.00 + Sound proof enclosure £25.00 + VAT

SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator. Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only £169.00 pp £1.95 Data sheet on request


MAINS FILTERS

Professional type mains filters as used by "Main Frame" manufacturers. Ideal for curing those unerving hang ups and data glitches—fit one now and cure your problems.
 Suppression Devices SA5A upto 5 amp load £5.95
 Corcom Inc F1886 up to 20 amp load £9.50
 Corcom Inc F1900 upto 30 amp load £12.25

RECHARGEABLE BATTERIES

CYCLON type D001 sealed lead acid maintenance free 2v 2.5 ah. Will deliver over 300 amps on short circuit!! Brand new at only £2.95
 SAFT VR2C size 'C' 1.2v 2 ah. nickel cadmium £1.50 each 10 for £11.50

RCA FULLY CASED ASCII CODED KEYBOARDS

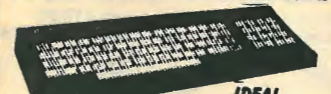

IDEAL TANGERINE OHIO ETC.
 Straight from the USA made by the world famous RCA Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback and a 1 year full RCA backed guarantee.
 VP601 7 bit fully coded output with delayed strobe, etc. £43.95
 VP611 Same as VP601 with numeric pad £54.95
 VP506 Serial, RS232, 20MA and TTL output with 6 selectable Baud Rates £64.26
 VP616 Same as VP606, with numeric pad £84.34
 Plug and cable for VP601, VP611 £22.25
 Post, Packing and Insurance £1.95
ORDER NOW OR SEND FOR DETAILS

D.C. POWER SUPPLY SPECIALS

Experimentors PSU Ex-GPO unit all silicon electronics. Outputs give +5v @ 2 amps, +12v @ 800 ma, -12v @ 800 ma, +24v @ 350 ma, 5v @ 50 ma. floating. Dim 160 x 120 x 350 mm. All outputs fully regulated and short circuit proof. Removed from working equipment, but untested. Complete with circuit. Transformer guaranteed. Only £14.50 + £2.50 pp.
POWER ONE CP143 super compact unit giving continuous output of 5v @ 5 amps. dim. 215 x 67 x 80 mm. BRAND NEW and guaranteed Only £21.00 + £1.50 pp.
CUSTOM POWER CO55 5v @ 3 amp. Very compact unit dim. approx 60 x 90 x 190 mm. Semi open chassis, full crowbar overvoltage protection. Tested Ex Equipment. £11.95 + pp £1.25
MINI SYSTEM PSU Ex equipment unit ideal for the small micro. Outputs give 5v @ 3 amps, +12v @ 1 amp and -12v @ 300 ma. Crowbar overvoltage protection and current limit. Fully tested. Dim 70 x 165 x 320 mm. Complete with Circuit only £12.95 + £2.00 pp.
PERIPHERAL SYSTEM SUPPLY. Fully cased unit supplied in a Brand new or little used condition. Outputs give 5v @ 11 amps, "+" 15-17v @ 8 amps, "-" 15-17v @ 8 amps and "+" 24v @ 4 amps. All outputs are crowbar protected and the 5 volt output is fully regulated. Fan cooled. Supplied tested, with circuit £35.00 + £8.50 carr.
MAIN FRAME SUPPLY. A real beefy unit designed for MINI or MAINFRAME use outputs give 5 volts @ 50 amps, +12v @ 5 amps, -12v @ 10 amps. All output are fully regulated with crowbar overvoltage protection on the 5v output. Supplied with circuit and tested. Ex-Equip. 110v AC input. Only £49.95 + carr. £10.50.

66% DISCOUNT ELECTRONIC COMPONENTS & EQUIPMENT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's, P.C.B.'s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME" Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads for unbeatable value!! Sold by weight.
 2.5kls £4.25 + pp £1.25
 10kls £10.25 + pp £2.25
 5kls £5.90 + pp £1.80
 20kls £17.50 + pp £4.75

300 BAUD DATA MODEMS

Join the communications revolution with our standard EX GPO 2a/b data MODEMS. Modem operates on standard CCITT tones with full auto answer facilities. Will switch to ANSWER or ORIGINATE. Standard RS232 I/O connections. Ideal networks. DISTEL etc. Complete with data. Untested but good condition £55.00 carr. £8.50.

1200 BAUD DATA PUMP MODEMS

Compact unit for use with private or "Dial up lines" Designed to work in pairs at any baud rate upto 1200 full duplex (4 wire circuit) or half duplex (2 wire circuit). Features include remote test facilities, RS232 I/O lines etc. Supplied with data in working order, but less case cover £65.00 + £4.50 carr.

OLIVETTI TE300 REDUCED TO CLEAR

Complete input output terminal with integral 8 hole paper tape punch and reader. Unit operates at 150 baud in standard ASCII. Ideal as a cheap printer for a MICRO etc. 120 columns, Serial data I/O. Supplied complete with data, untested, unguaranteed £65.00 + £11.50 carr.

Display ELECTRONICS

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00, Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies £20.00 Where post and packing not indicated please ADD 60p + VAT Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.
 64-66 Melfort Road, Thornton Heath, Near Croydon, Surrey
 01-689 7702 - 01-689 6800 Telex 27924

Appointments

Advertisements accepted up to 12 noon Wednesday, July 28th, for September issue, subject to space being available.

DISPLAYED APPOINTMENTS VACANT: £13.50 per single col. centimetre (min. 3cm).
 LINE advertisements (run on): £2.50 per line, minimum 5 lines. (Prepayable.)
 BOX NUMBERS: £1.50 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS.)
 PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to IPC Business Press Ltd.

AMPEX SYSTEM MAINTENANCE ENGINEER

to join a resident team at a site of EXCEPTIONAL INTEREST situated in the St. James's Park area of London. The team is responsible for round-the-clock maintenance of a large INFORMATION STORAGE AND RETRIEVAL SYSTEM WHICH COMBINES both VIDEO AND COMPUTER TECHNOLOGY.

Ampex requires an Engineer with:

- Sound knowledge of Electronics/HNC or equivalent
- At least three years' experience of maintaining ANALOGUE and/or DIGITAL electronic equipment
- Preferably, specific experience with: VIDEO equipment, such as cameras, VTRs, etc, and/or DIGITAL equipment such as disk/tape drives, mini computers.

Good salary plus generous shift allowance.

Company car plus travel allowance.

Pension and Life Assurance and Permanent Health Schemes.

Please write or phone for an application form from Maureen Brake, Reading (0734) 875200, Ampex Great Britain Limited, Acre Road, Reading, Berkshire.

(1729)

ST BARTHOLOMEW'S HOSPITAL, LONDON EC1A 7BE

Electronic Engineer

in Radiation Physics Department required

to assist in the servicing of a modern 20 MeV Linear Accelerator and a 6 MeV Linear Accelerator which is about to be installed and in the manufacture of dosimetry equipment and devices required for development and research. Experience in Radar or Radiation Physics would be advantageous but not essential as appropriate training will be provided. Support given to obtain relevant higher qualifications. Applicants should possess ONC/HNC (Electronics) or other appropriate qualifications and at least three years' relevant experience. Salary on Medical Physics Technician Grade III scale: £6,468 to £8,087 per annum inclusive. For application form and job description please write to the Personnel Department or telephone 01-600 9000 Ext. 2271. Ref. no. TG/10. Closing date, 4 August, 1982.

(1733)

National Broadcasting School

The National Broadcasting School, an independent organisation under the auspices of the IBA, provides training for Independent Radio. As well as running full-time engineering courses, the Engineering Department also teaches the non-technical courses and maintains 6 broadcast-capable studios and ancillary areas.

PART-TIME LECTURERS IN ENGINEERING

Two part-time lecturers are required to contribute to 3-month Engineering Course starting 21 September. They must have considerable experience in radio broadcasting and the ability to pass on that experience. Salary negotiable.


BROADCAST ENGINEER

A Broadcast Engineer with several years' experience in maintaining modern sound broadcasting equipment and a recognised technical qualification is required. In addition to the maintenance of the school's studios, the job includes teaching Broadcast Engineers. A desire to teach is therefore essential and previous experience in this and local radio would be an advantage. Salary negotiable.

Applications, which will be treated in confidence, should be made to the Chief Engineer, NBS, 14 Greek Street, London W1.

(1717)

14 Greek Street
 London W1
 01-434-2411

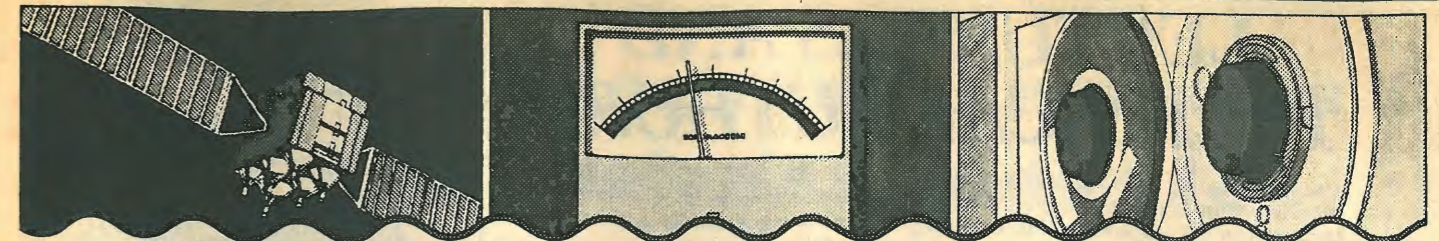

ELECTRONICS TECHNICIANS Total involvement across the spectrum of advanced communications

The Government Communications Headquarters at Cheltenham is one of the world's foremost centres for research, development and production in the fields of voice and data communications and communications security. Its comprehensive facilities, some of them unique, are geared towards producing creative solutions to complex communications problems using state-of-the-art techniques including computer/microprocessor applications.

There are currently opportunities for those with proven practical experience in electronics to become totally involved in complex systems spanning the whole spectrum of electronics technology. As a Telecommunications Technical Officer you will supervise a team of technicians involved in the management, construction, installation, testing, commissioning and maintenance of traditional and advanced technology communications and computer systems. Alternatively you will provide support for project engineers and scientists involved in the planning, research and engineering development of state-of-the-art systems.

You will work in one or other of the following fields:-

Telecommunications at HF, VHF and microwave frequencies, including satellite communications, computers and digital processing.

Data Transmission

Communications Security

Where necessary, in depth training will be provided and there are opportunities to attend familiarisation and management courses.

Posts are at two levels:-

At the lower level, the successful candidates will provide first line technical and supervisory control of a number of technicians involving work of a practical nature requiring 'hands on' participation. They may also undertake individual work of a highly technical nature with or without supervisory responsibilities.

The higher level posts involve the management of 2 or more teams as mentioned above. In many areas there is a close technical involvement requiring a high level of technical competence. Working as members of a multi-disciplinary team, the successful candidates will be expected to apply

their knowledge and experience to the broader fields of work planning and management, including the implementation of medium to large scale projects.

Cheltenham

A significant advantage for people working at GCHQ in Cheltenham is its location in this elegant Regency town set in the heart of the Cotswolds. You can choose to live in the town itself, or in one of the delightful villages that surround it. Either way, you will have easy access to good shops, schools, sports facilities and cultural amenities in Cheltenham and nearby Gloucester, and also enjoy fast road/rail links to London, the Midlands and the West Country. RELOCATION ASSISTANCE MAY BE AVAILABLE.

Qualifications


Candidates must possess a TEC/SCOTEC Certificate in Electronics, Telecommunications or similar discipline; or a City and Guilds Part II Telecommunications Technicians Certificate, or Part I plus Mathematics B, Telecommunication Principles B, and either Radio Line Transmission B or Computers B; or equivalent. Preference may be given to candidates with higher qualifications. Senior ex-service personnel with formal approved Service technical training may also be considered.

In addition, all candidates must have had appropriate training and will normally be expected to have about 4 years (lower level) or 7 years (higher level) experience in either radio communications transmitters or receivers, radar, data transmission, computers or similar electronic systems. High technical competence and/or proven managerial experience is also required.


Salaries up to £9085

Higher level posts: £8065 — £9085; lower level posts: £5980 — £8180. Level of appointment and starting salary according to qualifications and experience. There are good prospects of promotion to posts with salaries of up to £12,650.

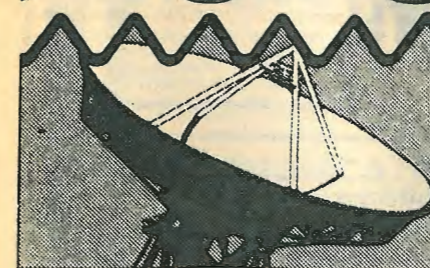For further information and an application form (to be returned by 12 August 1982) write to Civil Service Commission, Alencon Link, Basingstoke, Hants RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). Please quote ref: T/5792/2.



GCHQ in the heart of the Cotswolds

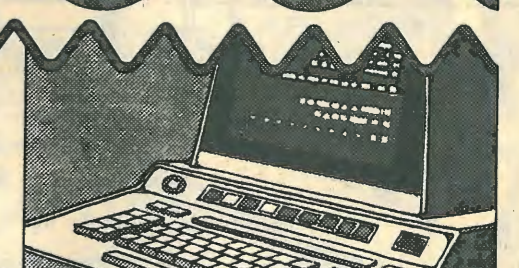

CCTV SERVICE ENGINEER

required to carry out repair and maintenance on all types of surveillance equipment. Salary commensurate with age and experience. Please write, with full C.V., to: BOX No. 1711

(1711)

2-WAY RADIO SERVICE TECHNICIAN

Experienced in servicing V.H.F. and U.H.F. Land Mobile Equipment, required for expanding COMMUNICATIONS COMPANY in STAINES. SALARY: Commensurate with experience.

CONTACT: Chris Turner,
FRANK CODY ELECTRONICS LTD
STAR HOUSE, GRESHAM ROAD,
STAINES, MIDDLESEX
 Or telephone Staines 62682 for an appointment.

(1701)

LECTURERS AND TECHNICAL AUTHORS

The Engineering Training Centre situated near Evesham in Hereford and Worcestershire, trains the Corporation's technical staff, both on first appointment and thereafter in the technology of broadcasting. The site is residential for students and some 400 BBC staff normally work or are in training there.

LECTURERS

Duties will involve contributing towards the operational training of Technical Staff in Television and/or Radio Broadcasting. This includes instructing Technical Operators who are responsible for sound coverage, audio mixing, camera work and lighting in Television or operating Network Continuity Suites in Radio. The Training Centre has Radio and Colour Television Studios using the latest broadcasting equipment.

Candidates, male or female, should have recent experience in some aspect of Technical Operations or Engineering in the Broadcast or Closed Circuit field and a good technical knowledge of audio or video equipment. They should preferably have a qualification of HNC, C & G Full Technological Certificate in Telecommunications, a pass in the examination of the Council of Engineering Institutions or equivalent. Consideration will be given to providing appropriate training to otherwise suitable applicants who do not hold these qualifications.

TECHNICAL AUTHORS

Engineering Training Department includes a Unit, consisting of one Senior Author and four Authors, which provides overall systems descriptions for major installations throughout the Corporation and publishes technical standards and procedures. The unit is supported in-house by a drawing office and printing facilities, together with computer based phototypesetting, word processing and graphics.

The technologies covered by Technical Publications Unit are Radio, Television, Transmission and, increasingly within these fields, computers. Authors have substantial personal responsibility to assemble and present their material accurately and in a form acceptable to users.

The successful applicant will hold a degree in electronics or a reasonable equivalent such as a Higher National Certificate, have good experience of technical documentation and a good grasp of a significant area of broadcasting technology or of a closely related field of electronics. Increasing versatility across the whole field will be expected as experience grows. Appropriate training, including areas of broadcasting technology, will be provided if necessary.

Salary on appointment, for both positions will be between £9,435 and £10,293 rising to £12,254.

Excellent welfare and club facilities. Pensionable posts. Relocation expenses considered.

For an application form and further information about the Technical Author vacancy please contact **Head of Training Section (Engineering), Mr J H Brooks**; those interested in the Lecturer vacancy, please contact **Head of Training Section (Operations), Mr D G Enoch**. BBC Engineering Training Centre, Wood Norton, Evesham, Worcs WR11 4TF. Telephone Evesham 45123.

Closing date for return of application forms is 14 days after publication.

BBC

(1723)

£25,000?

- DESIGN ENGINEER**
RF test equipment including VSWR test sets, frequency standards and RF measuring instruments for a small successful company. £ Negotiable - West Country.
- TEST ENGINEERS**
To test and service VHF and UHF transmitters and receivers - several clients. To £8,000 - Hants/Berks.
- RF DESIGN ENGINEERS**
To join a small team designing microprocessor-based signal sources. To £11,000 - Herts.
- PROJECT LEADER**
To head team engaged on microwave development, UHF/VHF techniques, microstrips and mixers. To £14,000 - Herts.
- ELECTRONIC ENGINEERS**
Development of digital-based intruder detection equipment. To £8,000 - Surrey.
- DESIGN ENGINEER**
To design all stages of microwave and satellite communication systems from base band to 6GHz. To £10,000 - Essex.

CLIVEDEN CONSULTANTS
87 St. Leonard's Road
Windsor, Berks.
Windsor (07535) 57818/58022
24-hour service (1640)

CLIVEDEN

UNIVERSITY OF EAST ANGLIA
Norwich

ELECTRONICS TECHNICIAN

Required to be responsible for the Electronics Workshop in the School of Mathematics and Physics. The workshop offers technical support to research and teaching in physics and electronics systems engineering. The successful applicant's responsibilities will include:

- the organisation and general supervision of the workshop;
- the design and construction of digital and analogue circuits;
- the repair and modification of electronic equipment including microcomputer systems.

Applicants must hold a suitable qualification in electronics, be able to work with minimum supervision and have substantial experience of modern electronic engineering techniques.

Salary on the Grade 7 scale £7,605-£8,542 per annum.

Application forms and further particulars can be obtained from the Senior Administrative Assistant, School of Mathematics and Physics, University of East Anglia, Norwich NR4 7TJ, to whom applications should be returned by 5 July, 1982.

1692

APPOINTMENTS
IN
ELECTRONICS
to £15,000

MICROPROCESSORS
COMPUTERS - MEDICAL
DATA COMMS - RADIO

Design, test, field and support engineers - for immediate action on salary and career advancement, please contact

Technomark
Engineering and Technical Recruitment

11, Westbourne Grove
London W2. 01-229 9239 (9257)

UNIVERSITY COLLEGE, CARDIFF
DEPARTMENT OF PHYSIOLOGY
**ASSISTANT
EXPERIMENTAL
OFFICER**

(ELECTRONIC INSTRUMENTATION)

CORRECTED ADVERTISEMENT

Applications are invited for the above post - design experience essential, degree in electronics an advantage. Salary range: OR Gr. IB £5,286-£8,925 p.a. - duties to commence as soon as possible.

Applications (two copies), together with the names and addresses of two referees, should be forwarded to the Vice-Principal (Administration) and Registrar, University College, P.O. Box 78, Cardiff CF1 1XL, from whom further particulars may be obtained. Closing date 11th August. Ref. 2428. (1728)

DIGITAL EXPERIENCE?
FIELD SUPPORT
R & D AND SALES
VACANCIES IN COMPUTERS
NC, COMMS., MEDICAL
VIDEO, ETC.

For free registration ring
0453 883264
01-290 0267

LOGEX

ELECTRONICS RECRUITMENT SERVICE
LOGEX HOUSE, BURLEIGH, STROUD
GLOUCESTERSHIRE GL5 2PW
TEL 0453 883264, 01-290 0267 (321)

TELECOMMUNICATION ENGINEERS
SAUDI ARABIA
C.£22,500 P.A. TAX FREE

SWITCHING SYSTEM ENGINEER
Exp. SPC switching system, analyse and evaluate tenders relating to electronic switching.

MOBILE TELEPHONE SYSTEM ENGINEER
Study requirements for new automatic mobile telephone system.

MARITIME TELECOMMUNICATIONS ENGINEER
Draw up tender specifications, coastal MF, HF, VHF stations.

COAXIAL CABLE SYSTEMS ENGINEER
Draw up tender specifications.

FREQUENCY MONITORING SPECIALIST
Study requirements for frequency spectrum management.

OUTSIDE PLANT NETWORK ENGINEER
Analyse and evaluate tenders and inspect contractors' work.

MICROWAVE SYSTEM ENGINEER
Study VHF, UHF and microwave link requirements and recommend appropriate system required.

Positions are offered on bachelor status. Candidates must be qualified to BSc. Age 35+. Leave is approx. 2 months per annum plus 3 economy excursion flights to UK. Telephone Montin (UK) Ltd on 0532-567141 for application form only or mail detailed résumé to Montin (UK) Ltd, Protection House, 83 Bradford Road, Pudsey, West Yorkshire LS28 6AT.

1700

Electronic Engineers salaries up to £13k

VIDEO is one of the World's fastest growing industries, and McMichael Ltd. is in the forefront of advanced video technology. We need young dynamic electronic engineers at all levels to join prestige high technology project teams.

As an analogue or digital video engineer, you would be involved in such projects as, video conferencing, broadcast effects, laser video transmission, precision displays, and other projects.


Our project teams are based at our new research and development Laboratories in Stoke Poges, Bucks., set in 37 acres of ground, with extensive sports and social facilities.

If you are experienced in high speed digital processing or analogue video, write or phone for an application form today.

McMICHAEL LIMITED

Sefton Park, Bells Hill, Stoke Poges, Slough SL2 4DY

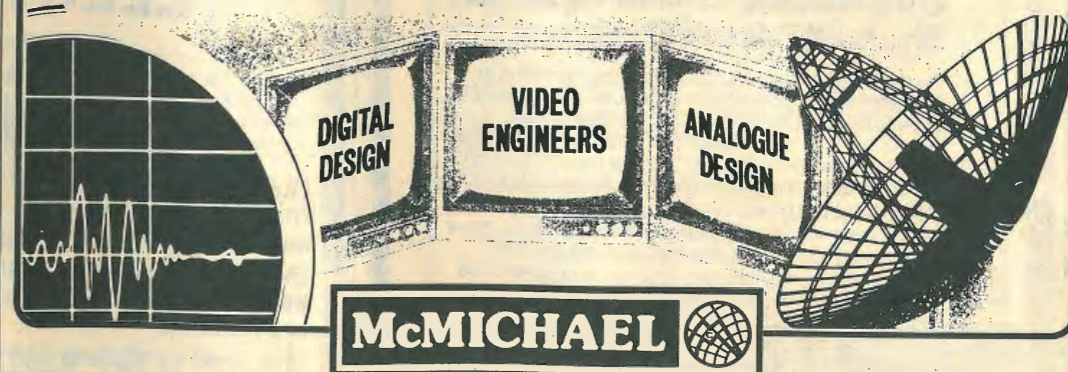Telephone Fulmer (02816) 2777 Telex 849212



McMICHAEL

ALWAYS AHEAD WITH THE BEST!

£5,000-£15,000

★ Experienced in:

Mini/Microprocessor Hardware and Software Digital and Analogue circuitry; RF and Microwave techniques?

★ **Where does your interest lie:**
Image processing; Automation; Datacomms; Radar Nav aids; Mobile Radio; Medical; Telemetry; Simulation; Satcom; Lans?

★ **There are opportunities in:**
Design; Test; Service; Sales; Systems; Production; Quality and Research.

★ **Make your first call count - Contact MIKE GERNAT on 076 384 676/7 (usually until 8 p.m.)**

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
148-150 High St., Barkway, Royston, Herts SG8 8EG.

(1734)

CAPITAL
APPOINTMENTS LTD.

THE UK's No. 1 ELECTRONICS AGENCY

Design, Development and Test to £14,000
Ask for Brian Cornwell

SALES to £15,000 plus car
Ask for Maurice Wayne

FIELD SERVICE to £12,000 plus car
Ask for Paul Wallis

We have vacancies in ALL AREAS of the U.K.

Ask for a Free Jobs List

Telephone: 01-637 5551 (3 lines)

(291)

Appointments

THE UNIVERSITY OF PAPUA NEW GUINEA SENIOR TECHNICAL OFFICER (ELECTRONICS)

Applications are invited from suitably qualified persons for the above position in the University of Papua New Guinea.

DUTIES:

The successful applicant will be expected to join a technical group involved in carrying out electrical/electronic maintenance to scientific departments and faculties within the University. A proven record of experience is required covering maintenance and servicing in a wide range of teaching and research instrumentation commonly used in Bio-Medical/Dental Sciences. The Department of Physics houses modern and well-equipped electronics and technical workshops to facilitate the work envisaged.

The successful applicant will be required to supervise and to provide on-the-job training to national Papua New Guinean technical staff.

QUALIFICATION:

Applicants should hold a Higher National Certificate in Electronics/Electrical Engineering or equivalent qualification. Possession of a current and valid driving licence will be desirable.

SALARY: K15625 per annum plus 24% gratuity.

Further details may be obtained from the Chief Technical Officer in Physics Department on telephone 245243 or the University of Papua New Guinea, P.O. Box 320, UNIVERSITY, Papua New Guinea.

Applications together with names and addresses of three professional referees should reach the Secretary, University of Papua New Guinea, P.O. Box 320, University Post Office, Papua New Guinea, not later than 9th July, 1982.

SECRETARY
UNIVERSITY OF PAPUA NEW GUINEA

Commissioning/Engineering Support Broadcast Television Equipment

Tremendous growth and success has resulted in an excellent career opportunity in the QA Department of Sony Broadcast, a world leader in professional broadcast television equipment. The Company has an expanding range of high technology products which include video cameras, VTRs and editing control systems.

An experienced engineer, who should ideally have a background in broadcast television equipment supported by a relevant qualification, is now required to join a small team responsible for the evaluation of product performance. Key activities will also include commissioning, assistance in product customisation and the establishment and maintenance of ATE, including software. Full product training will be given where necessary.

This position carries an attractive salary, first class conditions of employment and considerable prospects for personal development.

If you are interested, please write, giving brief details of career and present salary to Mike Jones, Senior Personnel Officer, Sony Broadcast Limited, City Wall House, Basing View, Basingstoke, Hants RG21 2LA. Tel: 55011.

SONY Broadcast
Sony Broadcast Ltd.
City Wall House
Basing View, Basingstoke
Hampshire RG21 2LA
Telephone (0256) 55011

(1731)

TRAINEE RADIO OFFICERS

First-class, secure career opportunities.

A number of vacancies will be available in 1982/83 for suitable qualified candidates to be appointed as Trainee Radio Officers.

If your trade or training involves Radio Operating, you qualify to be considered for a Radio Officer post with the Composite Signals Organisation.

Candidates must have had at least 2 years' radio operating experience or hold a PMG, MPT or MRGC certificate, or expect to obtain this shortly.

On successful completion of between 36 and 42 weeks specialist training, promotion will occur to the Radio Officer grade.

Registered disabled people may be considered.

SALARY & PROSPECTS

TRAINEE RADIO OFFICER: £4,357 at 19 to £5,203 at 25 and over. On promotion to Radio Officer: £5,968 at 19 to £7,814 at 25 and over. Then by four annual increments to £10,662 inclusive of shift working and Saturday and Sunday elements.

For full details please contact our Recruitment Officer on Cheltenham (0242) 21491 Ext. 2269 or write to her at:

Recruitment Officer, Government Communications Headquarters, Oakley, Priors Road, Cheltenham, Gloucestershire GL52 5AJ

(1631) **GCHO**

ELECTRONIC SERVICE ENGINEER

Due to the rapid growth of our In-Car Entertainment Division we seek an additional engineer to service our range of products.

Experience of both analog and digital systems is essential as complex microprocessor based units are handled.

The ideal candidate will have been employed for a minimum of 3 years servicing car audio or domestic Hi-Fi equipment, together with 2 years' microprocessor-based hardware experience. Due to the nature of our products, persons without this experience are unlikely to be suitable.

Some administrative capability would be considered an advantage.

Applications in writing with full c.v. to:
The Technical Manager

Autocar
ELECTRICAL EQUIPMENT CO. LTD

Chantry Road Industrial Estate
Kempston, Bedford MK42 7SD

(1693)

Engineers & Scientists

£9,126

Communications R & D...
...the leading edge

VIDEO ENGINEER

Rediffusion Consumer Manufacturing Ltd is seeking an experienced video engineer to join a progressive team engaged on a wide variety of stimulating projects associated with video cassette recorders, video cameras, video disc players and colour TV receivers and monitors.

Assessment reporting is an important part of this team's function and the ability to express oneself, both verbally and in writing, is essential.

Our Laboratories are situated in Chessington, within easy commuting distance of the Surrey countryside. An attractive salary and the usual big company benefits are offered to suitably qualified and experienced engineers. If you believe you can make an effective contribution to our future video projects please write to or phone:-

Mr Harry Brearley,
Rediffusion Consumer Manufacturing Ltd.,
Fullers Way South,
Chessington, Surrey KT9 1HJ. Phone: 01-397 5413

REDIFFUSION

(1715)

PICCADILLY
RADIO
261

Serving an area of four million people in and around Manchester, seeks a

Broadcast Engineer

for maintenance, operations, development and installation of studio equipment. A fascinating job working with a friendly and enthusiastic team.

Write with C.V. to:
Chief Engineer
Piccadilly Radio
P.O. Box 281
Manchester M60 1QU

(1698)

Appointments

At HM Government Communications Centre, we're applying the very latest ideas on electronics and other technologies to the problems of sophisticated communications systems, designed to enable and protect the flow of essential information.

The work is of the highest technical challenge, offering full and worthwhile careers to men and women of high ability, on projects covering the following areas of interest:-

RADIO - from HF to microwave, including advanced modulation systems, propagation studies, applications of Microcircuitry.

ACOUSTICS **SIGNAL ANALYSIS**
MAGNETICS **SYSTEMS ENGINEERING**

Applicants, under 30 years of age, should have a good honours degree or equivalent qualification in a relevant subject, but candidates about to graduate may also apply.

Appointments are as Higher Scientific Officer (£6,840-£9,126) or Scientific Officer (£5,422-£7,399) according to qualifications and experience. Promotion prospects.

For an application form, please write to the Recruitment Officer, (Dept. W/W8), HM Government Communications Centre, Hanslope Park, Milton Keynes, MK19 7BH.

Teleco Oilfield Services Ltd has pioneered a reliable shock-resistant Measurement-While-Drilling (M.W.D.) tool which saves drilling time and money, promotes safety and improves well-path accuracy in offshore drilling activities. Our dynamic growth has created a career opportunity for an

ASSISTANT ENGINEERING MANAGER (Electrical/Electronics)

This position is located in our facility in Aberdeen, and offers a stimulating environment with an excellent benefit package and an opportunity to grow with the company in this rapidly expanding industry.

The successful candidate, reporting to the Engineering Manager, will primarily be required to provide engineering support for the Electronic Maintenance department, to introduce new tools to the field and to exercise budgetary control over electrical and electronic activities.

Applicants should possess B.Sc./H.N.D. qualifications in Electrical/Electronic Engineering and a minimum of six years' experience in a maintenance or production environment. A knowledge of analogue and digital electronics as employed in a hostile environment would be an advantage.

A salary of c. £13,500 and a company car reflects the seniority of this position. Applicants should send a C.V. as soon as possible to:

The Personnel & Administration Manager
TELECO OILFIELD SERVICES LTD., Hareness Circle
Altens Industrial Estate, Aberdeen
Agency enquiries are not requested (1677)

TELECO

MICROCOMPUTER ENGINEER

Required by newly formed company working on innovative computer-based speech processing systems in central London. Applicants must have experience with digital hardware and will be expected to develop real-time applications for Intel 16 bit S.B.C.s and contribute to their software support.

This is an ideal opportunity to work with a small team and use the most advanced signal processing technology and computer support taking the product from design through to installation. It will be necessary to liaise with customers and implement a particular interface requirement.

Salary will depend on experience and be in the range of £8,000-£10,000. Please reply in writing, giving details of qualifications and career to date, to:

AUDIO MAGIC LTD.
105 Green Croft Gardens
London NW6 3PE

(1732)

FIELD SERVICE ENGINEER

LKB Instruments Limited, the U.K. subsidiary of a major international medical/scientific instrument company require a Field Service Engineer for their Customer Service Department.

Applicants should have a sound knowledge of digital and analogue electronics, with preferably some field experience in the scientific instruments world.

The work entails the repair and maintenance of instruments situated mainly in Hospitals and University Laboratories. Preference will be given to applicants living in the Gloucester to South Birmingham area.

Conditions of employment are excellent and in addition to a good basic salary and company car, the company have a profit sharing scheme, BUPA participation and 4 weeks annual holiday.

Contact Mrs S. Francis for application forms:-
LKB Instruments Limited,
232 Addington Road,
Selsdon,
South Croydon,
Surrey, CR2 8YD.
Tel: 01-651 5313

(1716)

MANY FIRMS ARE THROUGH THE RECESSION AND RECRUITING AGAIN

PROJECT MANAGER

VLF and LF equipment for helicopter systems control. Integration of program and cost data. Liaison with clients, etc. Experience in radio communications environment essential. Berks. To £12,500.

SOFTWARE ENGINEER

For new high technology computer peripheral equipment with a resident basic interpreter. Many advanced design concepts. Experience Z80/8080 SW essential. Berks. To £10,000.

YOUNG ENGINEERS

For designs associated with processing low-noise signals, displays and control circuitry for a new thermal imaging system. Essex. £6,000-£8,000.

RF ENGINEERS

To design non-broadcast TX up to 5 MHz 20 KW for very advanced medical diagnostic instrumentation. Greater London. To £11,000.

ASSISTANT COMMUNICATIONS MANAGER

For large international L Comms. network, including FDM, TDM, Facsimile and voice staff supervision and hardware development client liaison - European travel. London. To £12,000.

Whatever your experience send your CV or ring:

Charles Airey Associates

Tempo House, 15 Falcon Road, Battersea
London SW11 2PJ
Tel. 01-223 7662 or 228 6294

(1357)

A Professional Audio Company situated in central London require a

TECHNICAL ENGINEER

interested in working with a wide range of studio equipment from video to 24-track digital recorders. Previous experience is not necessary but a good practical knowledge of electronics including digital techniques is essential. Please write giving information about yourself and for further details.

BOX NO. 1727

(1727)

UNIVERSITY OF OXFORD
DEPARTMENT OF ENGINEERING SCIENCE

GRADUATE ENGINEER IN CHARGE OF THE ELECTRONIC SERVICES DIVISION

A graduate engineer is required to direct the Electronic Services Division, which provides the supporting services for the Department's research and undergraduate teaching. The person filling the post should have a proven knowledge and experience of advanced electronic technology, the ability to anticipate future developments in this field, to supervise the design of both analogue and digital electronics, including the hardware and software associated with the development of microprocessor-based instruments, and to advise research staff on how best to use this technology to advance their research.

The position also involves the management and administration of the electronic services staff, comprising at present three research assistants (Electronic Design Engineers) and five technicians, who are responsible for:

- (i) design and construction of electronic circuitry;
- (ii) servicing and modification of existing equipment;
- (iii) operation of the departmental electronic stores.

The person appointed will also be required to supervise any laboratory stewards working in this field, the safety checking of electrical equipment and the control of the electronic section of the inventory. He/she will be expected to contribute to the teaching and future development of the microprocessor laboratory.

The position is on the University Research Support Staff Grade II Scale with a salary range from £9,750-£12,860 with superannuation on the USS Scheme.

Application should be made to the Administrator, Department of Engineering Science, Parks Road, Oxford OX1 3PJ, enclosing a detailed curriculum vitae and the names and addresses of three persons to whom reference may be made.

(1699)

UNIVERSITY OF YORK

Department of Electronics

1 post of Technician Grade 6 2 posts of Technician Grade 3

Applications are invited for the above posts in the new Department of Electronics.

The Chief Technician (Grade 6) will be required to set up and run the Research Laboratories and will be responsible for the development, provision and maintenance of equipment and services needed by staff and students working in communications, control engineering and microelectronics. A degree, HNC or equivalent qualification is required, together with extensive experience of electronic engineering, including computers.

Salary for Grade 6 on Scale £6,532-£7,802 p.a. (under review). One Grade 3 Technician will be required to assist the Chief Technician in the research laboratories and the other Grade 3 Technician will assist the Senior Technician running the teaching laboratories. For appointments at this grade a degree or a minimum of 2 "A" levels plus some experience is required, but applicants with "A" levels without experience may be appointed at a lower grade and given training.

Salary for Grade 3 on scale £4672-£5473 p.a. (under review). Applications in writing, giving full details of age, education and experience, together with the names and addresses of two referees, should be sent to Mrs. E. D. Heavens, Senior Administrative Assistant, University of York, York YO1 5DD, by Friday, 13th August, 1982.

(1725)

R & D OPPORTUNITIES. Senior level vacancies for Communications Hardware and Software Engineers, based in West Sussex. Competitive salaries offered. Please ring David Bird at Redifusion Radio Systems on 01-874 7281. (1162)

SOUNDTRACS audio mixers require a test engineer for final product test. At least three years' experience of testing audio products in a production environment. The position entails final test, some sub-assembly approval, writing test specifications in conjunction with the design team and some post development work. Much of our sub-assembly is on semi-auto jigs. Up to £8,000 p.a. depending on experience, 26 days' holiday, BUPA and other normal benefits. Todd Wells, 01-399 3392 or write Soundtrac Laboratories Ltd., 91 Ewell Road, Surbiton, Surrey. (1710)

PART-TIME LECTURERS

Reqd. by private college to teach ELECTRONICS and/or PHYSICS up to A-level standard for between 7 and 15 hours per week (daytime only).

Contact City Tutorial College, 67/83 Seven Sisters Rd., London, N.7. Tel: 01-263 5937/8. (1718)

SITUATIONS VACANT

Lecture Theatre Manager

The Institution wishes to recruit a Theatre Manager to replace the present manager who will retire shortly. The Institution of Electrical Engineers arranges approximately 200 meetings, seminars, colloquia and conferences a year in its lecture theatres at Savoy Place, London.

These lecture theatres are equipped with modern lighting and audio visual aids. The latter includes large screen projection facilities for video tapes and projection facilities for films, slides and transparencies; sound reinforcement and recording facilities; radio microphones and audio loop transmission for the hard of hearing. The facilities are subject to periodic updating and improvement.

The Lecture Theatre Manager is responsible for managing all the lecture theatres in the broadest sense by satisfying both the needs of the audience and the speakers. Will be expected to

assist and advise the speakers through the correct choice and use of audio and visual aid equipment and to ensure that the audience obtain the maximum information from the lecture. Will be expected to maintain the equipment in first-class order and to make recommendations for changes and improvements, and will operate the equipment during lectures.


The Lecture Theatre Manager, in addition to being professionally and technically competent, should have a personality which inspires confidence in the lecturers.

We offer a competitive starting salary and other conditions of employment include: 35 hour flexible working week, generous leave entitlement, subsidised staff restaurant, and pension and life assurance scheme.

Candidates (male or female) should apply in confidence, detailing career and salary progression to the Director of Administration, Institution of Electrical Engineers, Savoy Place, London, WC2R 0BL.



THE INSTITUTION OF ELECTRICAL ENGINEERS

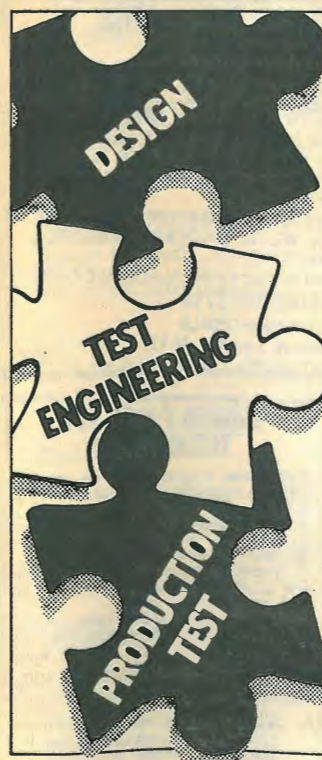

ELECTRONIC TEST ENGINEERING

Having introduced an extended new product range many of which are micro-processor based, Marconi Instruments has once again confirmed itself as Europe's leading manufacturer of measurement systems and automatic test equipment. Our products are selling throughout the world to all leading users in the electronics and aerospace industries and we are naturally developing further innovated designs.

A key role in our organisation is that of test engineering, where a group of professional engineers are responsible for the development of sophisticated methods and software for the manufacture of our products. We are now looking for experienced Engineers and are particularly interested if you have experience in the following disciplines:

IEEE Bus Control Systems • ATE Programming Test Techniques

Whatever your level of experience we would like to hear from you. We can offer an excellent salary plus a wide range of company benefits, including relocation expenses where appropriate.

For further details contact Mr. J. Prodger, Recruitment Manager, Marconi Instruments Limited, Longacres, St. Albans, Herts. Telephone: St. Albans (0727) 59292 ext. 369.

marconi instruments

ARTICLES FOR SALE

RACAL COMMUNICATIONS RECEIVERS

500 Kc/s - 30Mc/s 1Mhz wide. RA17L - £175. RA17E - £225. A few sets available as new at £75 extra. All receivers are air tested and calibrated in our workshop, supplied with full manual, dust cover, in fair used condition. New black metal covered cases for above sets £25 each. RAS9D - ISB - SSB - £75. RA218 - SSB - ISB and fine tune for RA17 - £50. TRANSMITTER DRIVE UNIT RA79. 1.5mc/s - 30mc/s - SSB - ISB - DSB - F5M - CW - £150. AERIAL TUNING UNIT and protection unit MA197B - £25 to £50. DECADE FREQUENCY GENERATOR MA350B Solid state synthesiser for MA79 or RA117 - RA217 - RA1217 - £150 to £200. MA250 - 1.6mc/s to 31.6mc/s - £150 (New). MA250G - precision frequency standard - 5mc/s to 100khz - £100 to £250. RACAL MA152 - Standing wave ratio indicator. FX2mc/s - 25mc/s Power up to 1000watts - 50 ohms - Auto trip switch - Transistor mains 100 - 250AC, new and boxed - £40. RACAL COUNTER 836 (9036) 32mc/s TTL circuit design - tested with manual - £30 to £75. OSCILLOSCOPES COSOR C0U150 - 35mc/s - Twin Beam - Solid State - £175 with manual. TEXTRONIC OSCILLOSCOPE 647 and 647A Solid State - 50mc/s and 100mc/s bandwidth - £250 and £350. Tested, circuit and instructions. AERIAL MASTS - we have three masts approx. 130ft high, complete with all fittings. Base - insulators, etc. Mast steel tube 8" all parts galvanised, supplied brand new, all items boxed - £1000 - or each complete mast - £400.

All items are bought direct from H.M. Government, being surplus equipment. Price is ex-works. SAE for all enquiries. Phone for appointment for demonstration of any item. John's Radio, Whitehall Works, 84 Whitehall Road East, Birkenshaw, Bradford BD11 2ER. Tel. (0274) 684007. V.A.T. and Carriage extra.

MARTIN ASSOCIATES (ELECTRONICS) LTD.

'PARTHA' BECKHAMPTON
Nr. MARLBOROUGH, WILTS.
TEL: Avebury (067 23) 219

ADVANCE OS.2000 Oscilloscope Dual Beam 20MHz..... £185
AIRMEC 209 20KV Ionisation Tester..... £75
DAWE 11918 600/300W Ultrasonic Cleaner..... £200
DYMAR 711 VHF Millivoltmeter..... £50
ELECTRONIC VISUAL EV.8000 Display Unit..... £500
B & K 2409 Electronic Voltmeter 2Hz-200kHz..... £125
B & K 2305 Level Recorder..... From £250
H-P 1335A X-Y Display Storage..... £350
H-P 1332A X-Y Display..... £300
BRYANS 20170 X-Y Recorder..... £35
BRYANS 2600/A3 X-Y Recorder..... £200
HAFSTROM Heat/Frig Oven -70° to +200°C..... £500
MARCONI TF.1370 R-C Oscillator..... £95
TELEQUIPMENT D.43 Dual Beam Oscilloscope DC-15MHz..... £125
TELEQUIPMENT D.75 Dual Beam Oscilloscope DC-50MHz NEW CRT..... £550
MARCONI TF.888B Universal Bridge 1%..... £100
MARCONI TF.2600 Sensitive Voltmeter 1mV-300V..... £100
PHILIPS PM.6456 Stereo Generator..... £195
KEITHLEY 130 Handheld Digital Multimeter..... £75
GALLENKAMP ASOV 150 No. 2 OVEN..... £95
TAYLOR SG.52A AM/FM Signal Generator..... £35
NARDA 3020A Bi-Directional Coupler 50-1000MHz..... £95
The above prices do not incl. carriage and VAT
URGENTLY REQUIRED: OSCILLOSCOPES ENVIRONMENTAL OVENS (1384)

ENCAPSULATING EQUIPMENT FOR coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment, low cost, used and new. Also for CRT regunning metallising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

OSCILLOSCOPES. 50 MHz, D. beam, D. timebase, N.P. Tek, etc. From £150. Marconi Sigen 2002B AM/FM £500. Marconi DFM 2331 £230. REI Schwartz capacitance bridge £100. Advance 5-volt 40-amp switched P.S.U. £80. Oscilloscope probes, Tek/HP, etc. Wayne Kerr "Midge" - 55 to 150C meter/probe £80. Please include VAT and postage. "Q" Services, 29 Lawford Crescent, Yateley, Camberley, Surrey, 0252 871048. (1695)

SCOOP PURCHASE new unused Cosor transistor testers, Model 1325, £37.50, including VAT, and postage/limited quantity/orders dealt with in strict rotation. Anchor Electronics, The Anchor, Eastwood, Notts (07737) 67281. (1694)

SAVE 33% on PCB 2H holders, in boxes of 15. Limited offer 30. Hurry and phone 0353 778756, 9 a.m. to 9 p.m. Save time. We represent over 30 leading manufacturers. Free index of hand tools and production aids. Batvale Mkt. Ltd., 50 High Street, Sutton, Ely, Cambs. Tel: (0353) 778756. (1667)

Video Engineers

Sony are looking for a high flier - do you fit the bill?

Everyone knows our reputation for high quality domestic TV, audio and VCR equipment, but that's only part of the Sony success story.

We also lead the field in industrial video and other commercial and industrial applications. Video cameras, professional and digital audio, dictating machines, language laboratories - these are just some of the areas in which Sony is out in front.

Products like these are amongst the most sophisticated on the market and the Engineers who provide the back-up service need to have the highest level of technical competence if they are to maintain the standard of service which our customers have come to expect - second to none!

We're expanding fast to meet the growth of our business and as part of that expansion, we now wish to recruit an additional Engineer for our National Service Centre at Feltham, Middlesex.

Although we provide initial and on-going product training, you must have several years good fault diagnosis experience on the kind of products we have described. In particular, experience of industrial video (U-matic format) is essential, as is qualification to at least City & Guilds 222 (with Colour Endorsement), 224 or equivalent.

If you are the high flier we're looking for, we'll offer you a very competitive salary and a range of benefits which is everything you would expect from a company which places great importance in looking after its staff.

For an application form, you should contact Rosemary Browne, Personnel Department, Sony (UK) Limited, Pyrene House, Sunbury-on-Thames, Middlesex. Telephone: Sunbury-on-Thames 81211.

SONY

**THE OPEN UNIVERSITY
FACULTIES OF
TECHNOLOGY AND SCIENCE
ELECTRONICS
COMMON FACILITY**

Assistant Electronics Design Engineer

Applicants are invited for an Assistant Electronics Design Engineer, to work on a wide variety of electronics work in the Interfaculty Electronics Facility.

The design will involve both analogue and digital circuitry, including a growing involvement in microprocessors and the associated software.

The work will appeal to someone with a keen interest in electronics, who is eager to learn new techniques and who already has some experience in design.

Qualifications required are minimum design experience of one year with at least TEC III or ONC and preferably working to a higher qualification. The salary will be on the T5 scale £5695-£6650.

Further particulars and an application form are available from: Mrs. B. McBrearty (498/1), Faculty of Technology, The Open University, Walton Hall, Milton Keynes MK7 6AA, or telephone Milton Keynes (0908) 653941: there is a 24-hour answering service on Milton Keynes (0908) 653868.

This is a re-advertisement and previous candidates do not need to apply.

Closing date for applications: 30th July. (1705)



**PHONE
YOUR
CLASSIFIEDS
TO
IAN FAUX
ON
01-661 3033**

80 x 24 VDU
All the electronics for a 24 lines by 80 characters visual display unit on one assembled and tested printed circuit board measuring 8.75 inch x 6.50 inch.
You provide: power supply +5v at 1.2 amps +12v/-12v at 25mA, ASC11 encoded keyboard, video monitor.
The VDU-1 will talk to the R.S.232 serial port on your computer, at up to 19,200 Baud 56 features including cursor (X, Y) addressing.
VDU-1 Assembled and tested PCB £135
PSU-1 VDU-1 power supply £32
All prices subject to £2.50 registered delivery, plus VAT.
SIRIUS CYBERNETICS
Comyn Lodge, 66 Holly Walk
Leamington Spa, Warwickshire.
Tel. (0928) 318110 (1645)

ARTICLES FOR SALE

**TO MANUFACTURERS, WHOLESALERS
BULK BUYERS, ETC.
LARGE QUANTITIES OF RADIO, TV AND
ELECTRONIC COMPONENTS FOR DISPOSAL**

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc.

ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, etc.

ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE
TELEPHONE: 445 0749/445 2713
BROADFIELDS & MAYCO DISPOSALS
21 Lodge Lane, North Finchley, London, N.12
(5 minutes from Tally Ho Corner) (1613)

TELETEXT (Ceefax/Oracle) or Viewdata (Pre-tele) add-on adaptors for your existing television or microcomputer. Discount prices. Mail order. Trade enquiries welcome. Avon Office Services (WW), FREEPOST, Bristol, BS10 6BR. (0272) 502008 any time. (1724)

BRIDGES, waveform/transistor analysers. Calibrators, Standards. Millivoltmeters. Dynamometers. KW meters. Oscilloscopes. Recorders. Signal generators - sweep, low distortion, true RMS, audio, FM, deviation. Tel. 040 376236. (1627)

PRINTED CIRCUITS. Make your own simply, cheaply and quickly. Golden Fotolak Light Sensitive Lacquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear Acetate sheet for master 14p. Copper-clad Fibreglass Board approx. 1mm thick £1.75 sq. ft. Post/Packing 60p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall. (714)

POWER V MOS-FET TECHNOLOGY
We specialise in all aspects of this important subject. A comprehensive service is offered to individual or OEM users, including:
★ Hitachi Supertex and RCA V MOS-FET from stock.
★ V MOS-FET power modules from stock.
★ Competitive prices (120 watt modules £15.45, 1 off).
★ Printed circuits and kits.
★ Data books and application notes.
★ Design, evaluation and advice service.
★ Catalogue/sample data sent free (50p stamp appreciated towards post and packing).
Phone 02514 22303 and ask Richard Walsh about your application requirement or write:
AUDIO TECHNOLOGY
Freeport, Church Crookham
Aldershot, Hants. GU13 0BR

WIRELESS WORLD AUGUST 1982

EXIDY SURPLUS SALE
We have thousands of these parts for 1/2 PRICE & UNDER
NO REASONABLE OFFER REFUSED
ALL ITEMS BRAND NEW
74LS04 74LS157 3130 OP AMP
74LS05 74LS373 8880 ACIA
74LS32 74LS373 6502 Processor
74LS10 74LS365 4027 RAM
7805 1 AMP 5V REG
LSI Breakout TV Game Chip
PCB for Breakout TV Game
4700 MFD 10V 1K Resistors 1/4W
Sockets: 40 PIN, 24 PIN, 20 PIN, 16 PIN, 14 PIN
Joystick Plastic Holders (Over 1,000 sets)
Transformers for Commodore Pet: 8:0:8 5AMP, 16V 1 AMP, 22V 1 AMP, 240V Primary
Telephone Answering Machines - All faulty
TEL: 01-440 7033 (1696)

GRAEPEL PERFORATORS LTD.
Unit 1-B, Charles Street, Dept. WS, Walsall, Staffs WS2 9LZ. Tel. 0922 611644/611414. Telex 335291.
Perforated Metals - Screens, Plastics, Wire Meshes, Sifting Media, Cable Tray, Gratings, direct from Manufacturer's Stock. We can cut to size.
We specialise in one-offs or large quantities.

THE SCIENTIFIC WIRE COMPANY
P.o. Box 30, London, E.4
ENAMELLED COPPER WIRE
SWG 1lb. 8oz. 4oz. 2oz.
8 to 23 2.76 1.50 .80 .60
30 to 34 3.20 1.80 .90 .70
35 to 40 3.40 2.00 1.10 .80
41 to 43 4.75 2.50 2.00 1.42
47 8.37 5.32 3.19 2.50
48 to 49 15.96 9.58 6.38 3.69
SILVER PLATED COPPER WIRE
14 to 30 6.50 3.75 2.20 1.40
TINNED COPPER WIRE
14 to 30 3.38 2.36 1.34 .80
Prices include P&P, VAT and Wire Data SAE for list. Dealer enquiries welcome. Reg Office: 22 Coningsby Gardens. (9063)

Texscan System Analyzer 9900 - 10-300 MHz £100; Tequipment Oscilloscope D43 double beam £100; Tequipment Oscilloscope calibrator £50; Hewlett Packard 430c power meter and head £75; Signal Generators: Marconi TF 1060/2 UHF 450-1200 MHz £150; Marconi 801D 10-460 MHz £125; Marconi 801 £40; Hewlett Packard 612A 450-1230 MHz £300. Wanted: Frequency Counter, at least 1.5 GHz. - Ashford, Middx. 53661 daytime. (1726)

NEW BOXED VALVES: 212E/£150, 304H/£40, 12A/£3, 2G/£2, 35T/£3, 46/£2, 5R4GY/£1, 6AL5/50p, 808/£4, 801Z/£3, 101D/£3, 1616/£2, C6A/£5, CV177/£15, DET10/£5, DET25/£10, EF50/£1, E91H/£1, E92CC/50p, EL81/£1, GT1E/£5, L57B/£3, L58/£3, PT15/£2, PEN25/£1, VT25/£3, TT11/£1. SAE catalogue or phone 0803 28489, Radel Electronics, 86 Union Street, Torquay. (1673)

ROTRON EQUIPMENT cooling fan 120mm x 120mm, new, boxed, 115 vac, 7 watts, 55 ofm. £7.50 inc. VAT, postage. ETRI equipment cooling fan, 160mm, new condition, 200 cfm, 250 vac, £18.50, inc. VAT, postage. Sealed lead acid batteries, 6v, 1.1 AH, new, boxed, £3.95, inc. VAT, postage. Field Electric Ltd., 3 Shenley Road, Borehamwood, Herts., 01-953 6009. (1714)

STYL ALL TYPES supplied, send SAE for price list. Watts Radio, 8 The Apple Market, Kingston, Surrey. (1709)

WORKBENCHES, secondhand. Ex-ITT TV factory. Open- or cubicle-style, need space. Details: 042 486 3464. 9a.m. to 9p.m. (Sussex).

RF DESIGNER WITH INVENTIVE FLAIR AND A TASTE FOR RURAL LIFE

Our clients are a small cheerful and highly motivated company who are sole manufacturers of a socially essential paramedical product. They are in the throes of moving to a Georgian manor house with eight acres of land, in rural England (with low housing costs). The need is for an engineer, probably between 25 and 45, with a genuinely radical and inventive approach to design and a sound knowledge gained in the radio frequency (ideally, low power) field. The successful candidate will work in a small specialist team. The potential and prospects attached to the position are second to none. Apart from a competitive, negotiable salary, the company offer excellent relocation expenses to this attractive low cost housing area. To discuss this position or any other specialist Communications vacancies we may have, telephone Paul Hecquet on 044 46 47301/2/3/4 or write with a brief C.V.

The Electronics Recruitment Company
18 Station Road, Burgess Hill, West Sussex RH15 9DE
04446 47301/2/3/4 (1629)
Communications Division

Electronic Engineers - What you want, where you want!

TJB Electrotechnical Personnel Services is a specialised appointments service for electrical and electronic engineers. We have clients throughout the UK who urgently need technical staff at all levels from Junior Technician to Senior Management. Vacancies exist in all branches of electronics and allied disciplines - right through from design to marketing - at salary levels from around £4000 to £12000 p.a.

If you wish to make the most of your qualifications and experience and move another rung or two up the ladder we will be pleased to help you. All applications are treated in strict confidence and there is no danger of your present employer (or other companies you specify) being made aware of your application.

TJB ELECTROTECHNICAL PERSONNEL SERVICES,
12 Mount Ephraim,
Tunbridge Wells,
Kent. TN4 8AS.
Tel: 0892 39388

Please send me a TJB Appointments Registration form:
Name
Address
..... (861)

ARTICLES FOR SALE

BRIDGES, waveform/transistor analysers. Calibrators, Standards. Millivoltmeters. Dynamometers. KW meters. Oscilloscopes. Recorders. Signal generators - sweep, low distortion, true RMS, audio, FM, deviation. Tel. 040 376236. (1627)

VHF AM/FM/VIDEO Sig. Gen. 4-300 MHz. ROHDE and SCHWARZ SMAF E200. A.F. Sig. Gen. XTAL controlled PLL £60. Both in excellent condition. Tel. Swindon (0793) 826416. (1706)

CLEARANCE. 40-metre reels of 38-way screened cable, £39 each. Computer spec. capacitors, 20,000 MSD at 55 volts, £2.50. Phone Mike at Mirage Lighting on Hitchin (0462) 73388 between 10 a.m. and 7 p.m. (1662)

COMPUTER APPRECIATION

86 High Street, Bletchingley, Redhill, Surrey RH1 4PA. Tel: Godstone (0883) 843221

APPLE II, Europlus microcomputer with 48K memory, integer card, twin disc drives and 12" monitor. software includes VISI CALC, APPLE PILOT and DOS 3.3. Purchased earlier this year and as new..... £385
APPLE II, Europlus microcomputer with 48K memory, colour card and modulator and disc controller card. With DOS 3.3. As new..... £535
NCR Model 81-30 commercial microcomputer system. With 64K memory, twin floppy disc drives, VDU and 180 cps matrix printer. System is under 2 years old and cost over £15,000. Full support available from NCR..... £2,500
RAYTHEON Model PTS 1200. Computer system comprising 64K byte MOS memory, 3 VDU terminals, DIABLO Series 30 2.5 megabyte disc drives, cassette drive and numerous multiplexor and option cards. Processor test set with integral cassette drive is included. The whole system is contained in 2 rack cabinets and was manufactured 1977/78..... £1,900
RAYTHEON Model 704 16 bit processor. With front panel and 12 KW memory..... £150
DTC MICROFILE MICROCOMPUTER. Compact 8080 based system with 56K bytes, dual serial interfaces and programmable front panel display. Machines are available with one PERSCI dual drive (Currently \$1,700 each). software includes operating system, powerful BASIC, assembler and letter writer..... £500
MEMOREX Model 277B VDU. These VDUs are equipped with a network interface operating via a single coaxial connector. Microprocessor controlled with firmware in 2/8 EPROM. Details available shortly..... £35
LICON VDU Keyboards. High quality attractive cased keyboards with cursor control and programmable functions keypads (total 29 extra keys). Manufactured 1979/80 and either new or nearly new..... £18.50
IBM Model 1053 Golfball Printer. Compact 15 cps high-reliability mechanical printer in fully refurbished condition. Exactly equivalent to 735 less keyboard. Can be driven from PIA (or similar) with addition of PSU and solenoid driver ICs (details available). Accepts standard office golfballs..... £35
TEXAS INSTRUMENTS Model 810. High speed (180 cps) matrix printer. With serial interface..... £495

DIABLO Series 30 removable DISC DRIVE. 2.5 megabyte with industry standard interface. These drives are hardware, software and media compatible with RK05, and PDP 11 interfaces are available from XYLOCICS at low cost..... £375
POWER SUPPLY. For above..... £50
DOCUMENTATION Model M600L compact card reader. CR11 compatible..... £250
SYSTEME RK05 compatible controller for PDP 11 UNIBUS. Solid complete with twin RK05 - compatible DIABLO series 30 front loading disc drives and all cables and power supplies..... £285
PERTEC. Miniature 9-track 800 c.p.i. tape drive..... £190
LASER ASSOCIATES Nd GLASS LASER. 1.06 micron wavelength. 1-2 J per pulse. A single pulse from this laser burns a hole through a steel rule. Complete with cooling system and output monitor. FULLY OPERATIONAL..... £500
FACT Model 4001. 1000 cps capacitive paper tape reader..... £100
TREND Model HSR 500 optical paper tape reader..... £100
EMS SYNTHESIZER Model SYNTHI. A complete AKS keyboard and DK2 keyboard. Current (Jan. '81) new price £1,921..... £275
GESTETNER Model FB12 plain paper photocopier with some supplies..... £150
NASHUA Model 1215 plain paper photocopier..... £150

Please note:
 * VAT and carriage extra all items
 * Visitors welcome but by appointment please
 * We are keen to bid competitively for all good used equipment

INDEX TO ADVERTISERS AUGUST

Appointments Vacant Advertisements appear on pages 100-111

PAGE	PAGE	PAGE
Acoustical Mfg. Co. Ltd. 51	Faircrest Engineering 2	Northern Electronics 24
Active Components 21	Farnell Instruments Ltd. 16, Reader Card	
Albetros (Products) Ltd. 18		
Analogue Associates 2		
Anglia Components 87		
Antex (Electronics) Ltd. Cover iii		
Armon Electronics Ltd. 8		
Audio Electronics 19		
Avel Lindberg (Cotswold Electronics) 4		
Bamber, B. Electronics 18		
Barrie Electronics Ltd. 87		
Black Star Ltd. 12		
Broadfield & Mayco Disposals 24		
Bull, J. (Electrical) Ltd. 90, 91		
Cambridge Kits 84		
Carston Electronics Ltd. 14, 15		
Chiltern Electronics 96		
Chiltmead Ltd. 88		
Circuit Services 25		
Clark Masts Ltd. 16		
Clef Products (Electronics) Ltd. 4		
Colomor Electronics Ltd. 22		
Computer Appreciation 112		
Com-Tek (Mid) Ltd. 94		
Darom Supplies 84, 94		
Dataman Designs 23		
Display Electronics 99		
DSN Marketing 93		
Electrical Review Shock Cards 97		
Electronic Brokers Ltd. 3, 5, 7, 9		
Electrovalue Ltd. 20		
Essex Electronics 6		
Happy Memories 8		
Harris Electronics (London) 7		
Harrison Bros Electronic Dist. 6		
Hart Electronic Kits Ltd. 24		
Hemmings Electronics and Microcomputers 84		
Henry's Radio 4, 16		
Hilomast Ltd. 4		
House of Instruments 10		
ILP Electronics Ltd. 5, 17		
Interface Quartz Devices Ltd. 9		
Keithley Instruments Ltd. 25		
Kelsey Acoustics Ltd. 89		
Langrex Supplies 95		
Levell Electronics 96		
LFH Associates Ltd. 20		
L&J Computers 2		
Marconi Communications Systems Ltd. 22		
Memotech 85		
Modern Book Co., The 89		
Monolith Electronic Co. 84		
Japan: Mr. Inatsuki, Trade Meria - IBPA (Japan), 8.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585 0581.		
United States of America: Ray Barnes, IPC Business Press, 205 East 42nd Street, New York, NY 10017 - Telephone: (212) 867-2080. Telex: 238327.		
Mr Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone: (312) 63074.		
Mr Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.		
Mr Jack Mentel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone: (216) 621 1919.		
Mr Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.		
Mr Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone: (404) 237 7432.		
Mike Loughlin, IPC Business Press, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.		
Canada: Mr Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269.		
* Also subscription agents.		

OVERSEAS ADVERTISEMENT

AGENTS:
France & Belgium: Norbert Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.

Hungary: Mrs Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget.
 Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan.
 Telephone: 347051 - Telex: 37342 Kompass.

Printed in Great Britain by QB Ltd., Sheepen Place, Colchester, and Published by the Proprietors IPC ELECTRICAL-ELECTRONIC PRESS LTD., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS, telephone 01-661 3500. Wireless World can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd, Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd. UNITED STATES: Eastern News Distribution Inc., 14th floor, 111 Eighth Avenue, New York, N.Y. 10011.

WE'RE MAKING A STAND FOR BETTER SOLDERING!

And including it in the **NEW Antex all-in-one pack!**

The new ST4 stand with the big sponge on it's own or in the SK5 and SK6 kits with the new CS and XS low-leakage soldering irons. These new models have tougher, cooler handles, detachable hooks, the well known Antex doubleshaft insulation, the big range of push-on bits and fitted with or without moulded-on safety plugs.

Model CS-BP - 17 Watts
 Fitted with safety plug 240 volts
 R.R.P. £5.45



SK5 Soldering Kit
 Contains Model CS230 iron and the ST4 stand. R.R.P. £6.25

SK6 Soldering Kit
 Contains Model XS230 and the ST4 stand. R.R.P. £6.35

SK5-BP and SK6-BP
 Soldering kits fitted with safety plugs.
 SK5-BP kit R.R.P. £7.10
 SK6-BP kit R.R.P. £7.20

Model XS-BP - 25 Watts
 Fitted with safety plug.
 240 volts

Model XS - 25 Watts
 Available for 240 and 115 volts
 R.R.P. £4.70
 50, 24 and 12 volts
 R.R.P. £4.80

Model CS - 17 Watts
 Available for 240 and 115 volts
 R.R.P. £4.60
 50, 24 and 12 volts
 R.R.P. £4.80

Model CCN - 15 Watts
 Ceramic shaft only 240 volts
 R.R.P. £5.00


Model C - 15 Watts
 Stainless steel shaft only.
 240 and 115 volts
 R.R.P. £4.60
 50 and 24 volts
 R.R.P. £4.80

TCSU1 Soldering Station
 for safe 24 volt temperature-controlled miniature soldering iron, variable tip temperature 65 - 430°C, antistatic earth connection, with XSTC or CSTC iron.
 R.R.P. £40.50



Model ST4 Stand.
 R.R.P. £1.60

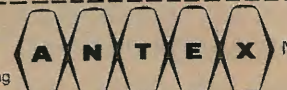Excluding V.A.T. (15%) and Postage & Packing



Made in England

ANTEX (Electronics) Ltd.,
 Mayflower House, Plymouth, Devon.
 Tel: 0752 667377 Telex: 45296


Please send literature and price list to:

Name _____ Address _____

_____ Tel _____

Our products are widely distributed by wholesalers and retailers throughout the U.K. Please try your local dealer. w/w/8

WW-002 FOR FURTHER DETAILS

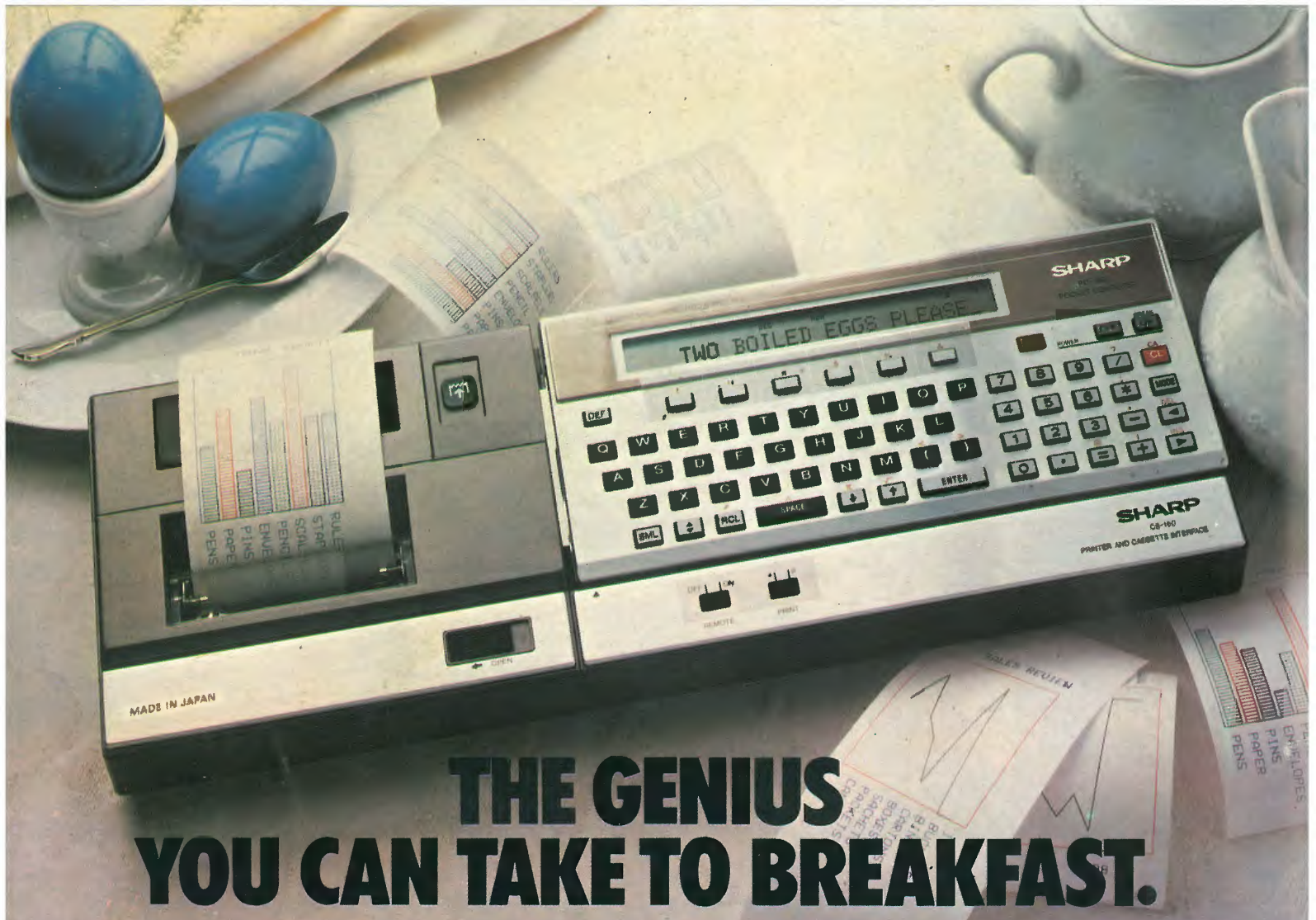

THE GENIUS YOU CAN TAKE TO BREAKFAST.

Now, at last, real portable computer power. The new Sharp PC 1500 pocket computer. A pocket-sized genius that will travel with you to conferences, seminars and business breakfasts.

The PC 1500 has the capacity and BASIC language usage that is very nearly that of the desk-size Personal Computer. When fitted with the optional 4-colour graphic printer, it is one of the most powerful pocket computers on earth.

Chores can be handled swiftly and accurately any time of day, wherever you happen to be. Estimates, records and charts of sales, billings and other important data can be re-programmed, calculated and summoned

at the touch of a button. It can even play blackjack, analyse your biorhythms or give you a beeped reminder of a scheduled meeting.

Large memory capacity, up to 11.5K bytes. 4-colour print-out. Six user-programmable keys. The incredible new PC 1500. A revolution in pocket computers.

From Sharp. Where great ideas come to life.

SPECIFICATIONS PC 1500 Pocket Computer

CPU	C-MOS 8-bit CPU
Capacity	ROM: 16K bytes RAM: 3.5K bytes to 11.5K bytes

CE 150 Colour Graphic Printer/Cassette Interface (Optional)

Printing Digits	Standard 18 digits (36, 18, 12, 9, 7, 6, 5, 4 digits selectable)
Printing System	X-Y axis plotter system
Printing colours	Red, blue, green, black
Printing directions	Right, left, up, down
Cassette Interface	Up to two cassette tape recorders can be connected.

Please send details of the Sharp PC 1500

Type of application: _____

Name: _____

Address: _____

The world of
SHARP
where great ideas come to life.

Sharp Electronics (UK) Ltd, Computer Division, Sharp House, Thorp Road,
Newton Heath, Manchester M10 9BE. Telephone: 061-205 2333



Design and specifications subject to change without notice.

WW-003 FOR FURTHER DETAILS

www.americanradiohistory.com