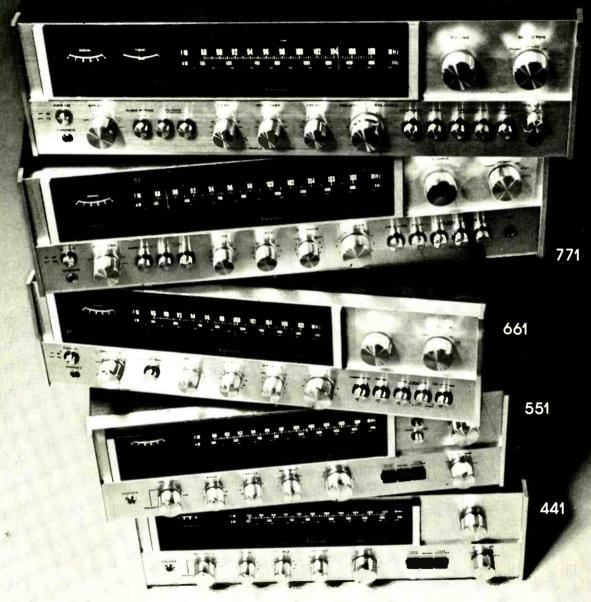


Tops all of ours and all of theirs too

the Sansui 881



SANSUI 881 is our finest hour.

The most advanced model in the long line of our already famous AM/FM stereo receivers and it's not only our best, it's the best on the market today.

Specs: 63 watts per channel minimum RMS into 8 Ohm load from 20 Hz to 20 KHz with no more than 0.3% total harmonic distortion. 1.8 microvolts sensitivity.

Hear the SANSUI 881 at your nearest SANSUI franchised dealer - and be sure to pick up your free copy of "The Sounds of SANSUI" or write directly to us.

SANSUI ELECTRONICS CORP.

Woodside, New York 11377 • Gardenia, California 90247 • SANSUI ELECTRIC CO. LTD. Tokyo, Japan SANSUI AUDIO EUROPE S.A. Antwerp, Belgium • ELECTRONIC DISTRIBUTORS (Canada) B.C. Circle 1 on reader service card


Sansui

ANOTHER DIMENSION

has been added to the world famous family of

Simpson® 260°

VOLT-OHM-MILLIAMMETERS

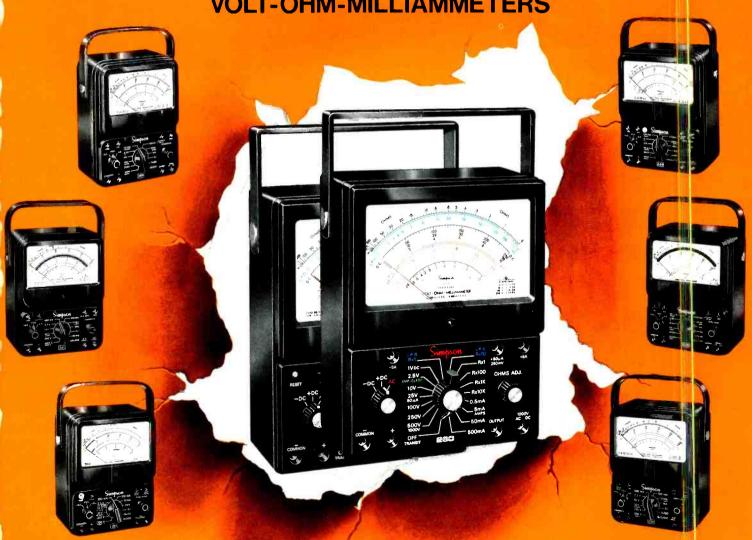

The pacesetters for over 40 years and still going strong!

Still the leader.

the time honored, ever popular

Simpson **SERIES 6**



- Direct dial reading of Amp-Clamp ranges
- External access battery and fuse compartment
- Clip-type fuse holder and extra fuse
- Optional 5 kV slip-on safety probe
- Multi-purpose, test leads with combination probe and alligator clips
- Only 2 batteries . . . one 9-volt NEDA 1604 and one 1.5-volt "D" cell NEDA 13F. Batteries supplied.
- Rugged taut band movement, varistor protected

Simpson Rx10,000 260 260-6 complete with hatteries

OLT - OHM - MILLIAMMETER 10 V BANGE ADD 17 DE 18 V BANGE ADD 26 DE 18 DE

ZERO DE POMIZ LEVEL

200-0, Complete with batteries.
test leads and manual\$75.50
260-6M, with mirror scale
260-6RT, in Roll Top Case\$84.00
260-6MRT, with mirror scale, in Roll Top Case \$87.00

RANGES:

DC Volts: 0-0.25; 0-1; 0-2.5; 0-10; 0-50; 0-250;

0-500; 0-1000

0-2.5; 0-10; 0-50; 0-250; 0-500; 0-1000 AC Volts:

DC Microamperes: 0-50 (250 MV Drop) DC Milliamperes: 0-1; 0-10; 0-100; 0-500

DC Amperes: 0-10 (250 MV Drop)

AC Amperes: Up to 250 with optional Model 150

Amp-Clamp Adapter

-20 to +10; -8 to +22; -6 to +36; +20 to +50DB Scale (1 MW 600 Ω

Reference):

Resistance: Rx1; Rx100; Rx10K

AND THE EQUALLY POPULAR, VERSATILE, CIRCUIT OVERLOAD-PROTECTED 260-6P



Reset pushbutton releases when overload exists. Will not reset until overload condition is eliminated.

260-6P, complete with bat-

teries, test leads and manual \$115.00

260-6PM, with mirror scale . . . \$118.00

260-6PRT, in Roll Top Case. \$124.00

And a broad line of Simpson Accessories are available for the Simpson 260 Family of VOMS

Model 150 Amp-Clamp Catalog No. 00532 complete with No. 00533 test lead \$29.50



30 kV DC Probe Catalog No. 00509 \$22.00



Grip-Tip Extension Probe



Vinyl Ever-Redy Case Catalog No. 00805 . \$20.50



Vinyl Sheath Case Catalog No. 01818 . \$16.75



The World Famous Simpson VOMS Is Available



260-6XL,	complete with batteries,	
test leads	s and marual	\$90.00
260-6XLM	M, with mirror scale	\$93.00

AND THE CIRCUIT OVERLOAD-PROTECTED 260-6XLP

Reset pusabutton releases when overload exists. Will not reset until overload condition is el minated.

260-6XLP, complete with batteries, test leads and manual \$125.00 **260-6XLMP**, with mirror scale **\$128.00**



5 kV DC Probe Catalog No. 00506 . . \$5.25



5 kV AC Probe Catalog No. 00505 .. \$5.25



And NOW... for the special needs of the

solid state electronics industry

Simpson SERIES 6 XL

- X for extra ranges and features
- for low-power ohms capabilities
- Extra shock and drop resistant construction High impact, custom-molded panel and case
- 33 ranges with extra voltage, current, resistance and low-power ohms functions
- Extra large viewing area with color-keyed scales
- Direct dial reading of Amp-Clamp ranges
- External access battery and fuse compartment
- Clip-type fuse holder and extra fuse
- Optional 5 kV slip-on safety probe
- Multi-purpose, test leads with combination probe and alligator clips
- Only two batteries . . . one 9-volt NEDA 1604 and one 1.5-volt "D" cell NEDA 13F. Batteries supplied.
- Rugged taut band movement, varistor protected

RANGES:

DC Volts:

0-0.250; 0-1; 0-2.5; 0-10; 0-25; 0-100; 0-250; 0-500; 0-10)0

AC Volts:

0-2.5; 0-10; 0-25; 0-100; (1-250; 0-500; 0-1000

DC Microamperes: 0-50 (250 MV Drop)

DC Milliamperes:

0-0.5; 0-5; 0-50; 0-500

DC Amperes:

0-5 (250 MV Drop)

AC Amperes:

6 ranges from 0-5 to 0-250 with optional Model 150 Amp-Clamp adapter

DB Scale (1 MW 600 \Omega Reference):

-20 to +10; -9 to +21;-1 to +29; +11 to +41, + 19 to + 49

Resistance (Standard Power):

Rx1 (6 Ω center scale), R> 100 (600 Ω center scale), Rx1K (601)0 Ω center scale), Rx10K (60, 100 Ω center scale)

Resistance (Low Power). Rx1 (20 Ω center scale), Ax10 (200 Ω center scale). Max open circuit voltage only 100 mV! Max measuring power only 0.125 mW!



SIMPSON PRODUCTS encompass a broad range of: Analog and Digital Panel Meters, Pyrometers, Elapsed Time Meters, Meter Relays and Controllers, Events Counters, Volt-Ohm-Milliammeters, Digital Instruments, Microtesters, Electronic Multimeters, Temperature Testers, Illumination Level Meters, Photo Tachometers, Noise and Sound Level Meters, Electrical Safety and Microwave Leakage Testers, Cathode Ray Oscilloscopes, Insulation Resistance Testers, Clamp Type Ammeters and VOA's, Chart Recorders, Signal Generators, Automotive Test Equipment, Digital Frequency Counters and Timers, Portable Secondary Standards, R-L-C Bridges, Custom Engineered Instruments and other Special Testing Apparatus.



Over 40 years of integrity in design, quality construction and easy availability has established Simpson as the leading supplier of highest quality test and measuring instruments. Through the years servicemen and technicians have become accustomed to expect long life and trouble-free performance from all Simpson products.

Electronic and electrical equipment distributors throughout the world carry Simpson products in stock for immediate delivery. Though seldom required, parts, repair service and calibration, when needed, are available through a large network of Authorized Service Stations.

For complete details on the entire Simpson 1975 product line, write for new 60-page Catalog 4400 or call your nearest Simpson Representative.

SIMPSON ELECTRIC COMPANY

853 Dundee Avenue, Elgin, Illinois 60120 • (312) 697-2260

CABLE: SIMELCO • Telex: 72-2416

IN CANADA: Bach-Simpson, Ltd., London, Ontario

IN ENGLAND: Bach-Simpson (U.K.) Ltd., Wadebridge, Cornwall IN INDIA: Ruttonsha-Simpson Private, Ltd., Vikhroli, Bombay



The first in a new series of **Audel® Service Guides—** "SERVICING RCA FOR 1975"

SERVICING RCA FOR 1975

by Stan Prentiss, is the forerunner of an entirely new series of specialized service manuals, developed by the Audel Division of Howard W. Sams & Co., Inc., to guide you in servicing the new products of the leading TV manufacturers.

Here under one cover is the first comprehensive directory of detailed servicing data and information for all '75 models of RCA Color TV, black and white TV, stereo, tape recorders, and radio. It is a complete guide for troubleshooting, schematics, replacement parts lists, and service tips, with full and accurate identification of all integrated circuits used, specific circuit writeups, and pertinent RCA training material. Invaluable for servicemen and do-it-yourselfers alike.

SERVICING RCA FOR 1975 will be followed shortly by 1975 service guides for other leading electronic home entertainment manufacturers.

SERVICING RCA FOR 1975 BY STAN PRENTIS:

TELEVISION

HOME TV-FM ANTENNAS by Paul Lawrence and Hansen Elroy

Tells and shows how to select the right antenna for the location, how to install, control, and adjust it for best reception. 208 pages, softbound.

No. 21076 \$5.95

CLOSED-CIRCUIT TELEVISION HANDBOOK 3rd Edition by Leon A. Wortman

Covers the use of CCTV in industry, education, medicine, and commerce. Includes equipment requirements, use of cassette and cartridge recorders and portable recorder units in CCTV. 288 pages, softbound. No. 21097 \$7.95

KNOW YOUR OSCILLOSCOPE 3rd Edition by Paul C. Smith

Revised by Robert G. Middleton

Explains the many applications of oscilloscopes, their circuits and functions, accessories, proper adjustments, and maintenance. 168 pages, softbound

No. 21102

HOW TO USE VIDEO TAPE RECORDERS by Harry Kybett

Video tape recorders are increasingly used in education, the medical profession, sales, and industry. This operational guide covers the problems and maintenance of vtr, and shows how to use vtr to record, play back, edit and copy. 264 pages, softbound.

No. 21085



RADIO

\$4.95

FIRST-CLASS RADIOTELEPHONE LICENSE HANDBOOK 4th Edition by Edward M. Noll

This best-seller is designed to help you acquire a first-class radiotelephone license and prepare you for the responsibility of operating and maintaining broadcast equipment. Covers transmitter, equipment, studio, master control, and remote equipment, and includes recently revised FCC rules and regulations. 416 pages, softbound.

No. 21144

SECOND-CLASS RADIOTELEPHONE LICENSE HANDBOOK 5th Edition by Edward M. Noll

Prepares the reader to pass FCC license

examination, and provides the practical data needed to maintain two-way radio equipment efficiently. All material is based on the FCC Study Guide and Reference Material, 448 pages, softbound

No. 21111

CB RADIO ANTENNAS 3rd Edition by David E. Hicks

A complete guide for those who want to improve the "reach" of their CB radio improve the "reach" of their CB radio equipment. No prior knowledge of antenna design and installation is needed to understand and follow this guide, 136 pages, softbound.

No. 21100 \$4.50



ELECTRONICS

LIGHT-BEAM COMMUNICATIONS by Forrest M. Mims, III

Covers the principles of light-beam communication, light sources and detectors, components, and optical communication systems. Discusses its early history, rapid development since the advent of the laser, and the potential for this relatively new method of communication. 160 pages, soft-

No. 21147

UNIQUE IC OP-AMP APPLICATIONS by Walter G. Jung

Many analog functions call for unique op-amp devices that allow applications not possible with standard op-amps. This book divides these unique op-amp applications into four general categories and explains and illustrates the operation of each. 144 pages, softbound. No. 21163



AUTOMOTIVE

SOLID-STATE IGNITION SYSTEMS by Rudolf F. Graf and George J. Whalen

An invaluable guide for the car owner who wants to install and service his own solidstate ignition system, as well as for the professional serviceman. Covers all types of solid-state ignition systems available today. 136 pages, softbound.

No. 21049



Order from your Electronics Parts Distributor, or mail to Howard W. Sams & Co., Inc.

Send books checked at right. \$_ Please include sales tax where applicable. Canadian prices slightly higher.

Send FREE 19	mer. 75 Sams Book Catalog	g.	21085
Name			- ☐ 21111 - ☐ 21100 ☐ 21147
Address			21163
City	State	Zip	_

HOWARD W. SAMS & CO., INC.

4300 West 62nd Street, Indianapolis, Indiana 46206

21076

21102

21097

a TV set only a TV technician could love.

Ultra-portable CK3000 Test Jig.Under 25 lbs.—easy to tote from job to job. The handle's not just for show!

Ready to use. Fully pre-tested. A complete unit including 13V in-line slotted-mask CRT with x-ray inhibiting glass.

Accessories included: Two 70° adapters; two 90° extensions; six yoke-programmer plugs; audio leads; four convergence ballast plugs; Set-Up and Instruction Manuals.

The big book. CK3000 Set-Up Manual lists over 7000 models, 49 brands. And we're constantly updating it. Just mail the registration card.

Adapters. You can buy kits for the seven most popular brands and discrete adapters for 42 more. Many old adapters can be used, too—don't throw them away!

30kV and more. A must for today's sets. Anode meter's big 50μA movement makes it easy to monitor voltages to 35kV—more than in any TV set you'll meet.

Patented yoke programmers let you match CK3000's yoke to six different deflection outputs. Three for tube and hybrid, two for transistor sweep, one for SCR sweep.

Dual focus connections. Built-inalternate focus supply for testing both 4.5kV and the new Black-Matrix 7.1kV.



See the CK3000 Test Jig at your Sylvania distributor's now!

GTE SYLVANIA

Radio-Electronics.

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

More than 65 years of electronics publishing

APRIL 1975 Vol. 46 No. 4

BUILD ONE OF THESE

- 33 **COSMOS Burglar Alarm Circuits** Use COSMOS IC's to build a variety of burglar alarms. by R. M. Marston
- **Accented Tick Timer** Solid-state timer is ideal for photo darkrooms. It's easy to build. by Frank H. Tooker
- TV Typewriter II Part III-Final instructions for completing your personal computer terminal. by Ed Colle

STEREO HI-FI **AUDIO**

Audio Signals You Never Heard Before Audio rectification can be a real problem. Learn how it happens and what you can do about it. by Len Feldman

GENERAL **ELECTRONICS**

- **Looking Ahead** Tomorrow's news today. by David Lachenbruch
- **Understanding Pseudo-Random Circuits** Useful in music synthesizers, here's a look at the circuits that generate these sequences. by Don Lancaster
- R-E's Replacement Transistor Guide 2N5784 through 2N6011. compiled by Elizabeth & Robert F. Scott

TEST EQUIPMENT


- **Equipment Report** Hickok model 246 color bar generator.
- 20 **Equipment Report** Telequipment D61 dual-trace scope.
- **Equipment Report** Castle "Master Subber" Mark V signal circuit analyst.
- **Equipment Report** Leader LCG-395 universal color bar generator
- 4-Channel Digital Scope Portable unit uses LED display array to analyze digital signal chains. by James B. Vice
- **Using The Curve Tracer** More ways to use curve tracers effectively. by Charles Gilmore

TELEVISION

- Add CCTV To MATV Systems 36 It isn't difficult, once you know how to do it. by James E. Kluge
- Step-By-Step Troubleshooting Charts IC's in vertical and horizontal countdown circuits. by Stan Prentiss
- 73 Service Clinic Electronic organs. by Jack Darr
- **Reader Questions** R-E's service Editor solves reader problems.

DEPARTMENTS

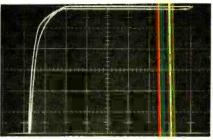- **Advertising Index**
- 93 **Books**
- 16 Letters
- **New & Timely**
- **New Literature**
- **New Products**
- **Next Month**
- 109 Reader Service Card



TYPICAL WAVEFORM PRODUCED BY A CURVE TRACER shows reverse characteristics of a small-signal silicon diode. It's just one of several interesting our re-tracer applications. ... see page 58

Hugo Gernsback (1884-1967) founde M. Harvey Gernsback editor-in-chief and publisher Larry Steckler, CET, editor Robert F. Scott, W2PWG, CET, technical editor Arthur Kleiman, associate editor Jack Darr, CET service editor I. Queen, editorial associate Leonard Feldman contributing high-fidelity editor David Lachenbruch, contributing aditor Karl Savon, semiconductor editor Barbara Schwartz, editorial assistant Vincent P. Cicenia, production manager Sarah Martin, production assistant: Harriet I. Matysko, circulation director Arline R. Bailey, advertising coordinator Advertising Sales Offices, see page 106

Cover photo by Walter Herstatt Cover design by Louis G. Rubsamen



Radio Electronics is a member of the Institute of High Fidelity and is indexed in Applied Science & Technology Index and Readers Guide to Periodical Literature.



Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-640. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$8.75. Pan-American countries, \$10.25. Other countries, \$10.75. Single copies 75c. © 1975 by Gernsback Publications, Inc. All rights reserved. Printed in IJ S.A. in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Boulder, CO 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this marjazine.

3

looking ahead

50-in-one

Peter Goldmark's latest gadget is a system which permits the transmission of 50 — count 'em 50 — visual and aural programs in the bandwidth of a single television channel. At press time, there had been no announcement of the system, known as RTS, but we've learned that it allows the multiplexing of 50 slow-scan "slide" programs with full audio for transmission on a television channel via microwave or broadcast. With a reduced number of programs, an FM subcarrier (SCA) could be used to send audio-visual information. Goldmark's company, Goldmark Communications Inc., is promoting the system for education and aiming it primarily at networks of community colleges. It's understood that the pilot project will be at Piedmont Central Community College in Charlotte, N.C.

For better UHF

More than 60% of Public Broadcasting stations are in the uhf band, so it's only natural for Public Broadcasting Service to be concerned about the problems - and future - of uhf. PBS President Hartford Gunn has urged educational television stations to mount a concerted campaign to help make uhf equal to vhf at both the transmitter and receiver levels, uhf, he noted, has achieved complete parity with vhf in Great Britain and other European countries, and the same could be accomplished here with proper legislation and FCC rules.

Gunn cited a special survey conducted for PBS by Hazeltine Research, which found that the addition of rf amplification and PIN diode attenuators to home receivers could effect an im-

provement comparable to doubling the transmitter power. The cost to manufacturers, he said, would be about three dollars per set, translating to nine dollars at retail. He urged public broadcasters to appeal to the FCC and Congress to mandate better receivers. At the same time, he called attention to a recent study of the PBS Engineering Committee, which recommended a minimum uhf station operating power of two megawatts and antenna height of not less than 1,000 feet above average terrain. These minimums, he said, are met by only six of 135 public TV stations surveyed.

Sony's home projector

A home version of Sony's industrial-educational projection television system is definitely scheduled marketing in the United States this fall. Like the current non-consumer version, it's expected to use a 12-inch Trinitron receiver as the projection source, but instead of the two-piece (projector and screen) approach, it's mounted in a single furniture-styled cabinet that looks like a secretary desk. The screen is in the upper portion and the TV projector and optical system are concealed in the hinged lower part when not in use. The screen is expected to measure about 30 by 40 inches, and the price will be between \$2,500 and \$3,000. The Sony unit will be the third projection color set on the consumer market. The others are the Advent Video-Beam two-piece system with a 52 by 69-in, screen and on assembled by Muntz Elman Manufacturing, which has a picture about the same size as the Sony.

Television injuries

Did you know that an esti-

mated 14,000 Americans checked into hospital emergency rooms in the year ending last June 30 with "television-related" injuries? That's the total projected by the Consumer Product Safety Commission on the basis of 710 actual cases reported through the National Electronic Injury Surveillance System. When you think of "television-related" injuries. you may conjure up visions of shocks, fires and implosions. But in the vast majority of cases reported, there was nothing wrong with the set at all. In fact, 97 percent of the injuries resulted from people bumping into television sets, dropping them on toes, and so forth. Nearly half of the victims were children under five.

In another development, the Consumer Product Safety Commission disagreed with Consumers Union on the question of safety of slide switches, commonly found on many brands of television. CU had rated one such set not acceptable on the grounds that someone pushing a coin or some other metal object into the slot could get a potentially lethal shock. The safety commission disagreed, a spokesman noting that the set in question met UL safety standards and that the commission had never received a report of injury from slide controls, which have been used in television sets for six years.

Latest on home VTR

The dream of a popular-priced home videotape recorder remains a dream. Various plans by manufacturers to introduce such an instrument have repeatedly been postponed — partly because of the unpropitious economic conditions today and partly because of extremely high costs. But this doesn't prevent the development of new home VTR systems, and we're seeing about

one new idea a month.

This month's new system represents an attempt by major Japanese manufacturers to establish a "standard," with complete interchangeability of tapes. The new system - being promoted by Matsushita (Pana-Toshiba, Hitachi, sonic). Mitsubishi and Sharp - is a variation of the standard cartridge videotape recorder used for industrial and educational purposes. The previous drawback of Japanese system had been the ability to record only one-half hour on a cartridge. The proposed new home system squeezes a full hour of playing time into the same single-reel cartridge of halfinch tape. It will be submitted this spring to the Electronic Industries Association of Japan for listing as a standard. Sony has been pushing for a different half-inch-tape system, but there have been no reports so far that any other Japanese or American manufacturers plan to adopt it. The new Sony system, originally scheduled for sale this year, no longer seems to have a definite timetable.


Calculator suit

Brewing for a long time, a major patent and anti-trust suit has erupted in the calculator industry. Bowmar Instruments has filed a \$240-million triple-damage action against its chip supplier Texas instruments, charging that TI went into competition with it in producing hand-held calculators using its confidential trade secrets. It also accuses TI of selling below cost to injure competitors and refusing to sell certain components to Bowmar and others. TI said the charges were "totally without merit."

by DAVID LACHENBRUCH CONTRIBUTING EDITOR

The new Mallory CA3 Intrusion Alarm.

Reliable.

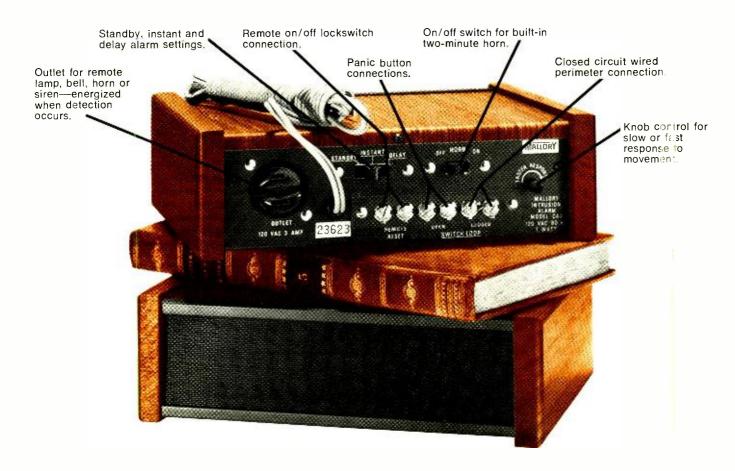

(And inconspicuous.)

This area-and-perimeter device creates and transmits an ultrasonic wavelength field for detection up to a distance of 20 feet. And because of its modern design and walnut-grain finish, the CA3 is attractive and inconspicuous enough to pass as a radio or stereo tuner.

Virtually any movement by an intruder (or a break in the perimeter circuit) activates the built-in horn and the remote outlet for two minutes. An automatic reset handles the possibility of a new or renewed intrusion. And special CA3 circuitry guards against false alarms from line transients and insects. A variety of companion indoor or outdoor accessory devices is available.

The Mallory CA3 Ultrasonic Intrusion Alarm. From the manufacturer of the most complete line of do-it-yourself security products. Another sound reason to see your Mallory distributor today.



MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC. Box 1284. Indianapolis, Indiana 46206; Telephone: 317-856-3731

Batteries • Capacitors • Controls • Security Products • DURATAPE* • Resistors • Semiconductors • SONALERT* • Switches • Timing Devices and Motors

DURACELL® DURATAPE® and SONALERT® are requisitered trademarks of P. R. Mallory & Co. Inc.

new & timely

Computer uncomplicates scoring at national gymnastic contest

Contestants and spectators at the NCAA 32nd National Gymnastics Championships, knew the exact scores and standings of individuals, teams and schools at all times during the meet, for the first time in 32 annual contests. An IBM 370/168 computer with a remote terminal on the gymnasium floor was the reason for the breakthrough.

The competition, which included 43 universities represented by more than 180 performers, requires some 5,000 scores to be tabulated during the competitive events. In pre-computer days,



SILENCE WAS AN ADVANTAGE of the Tektronix computer display terminal that was set up on the gymnasium floor of the NCAA National Gymnastics Championships at Penn State University. The gymnasts were able to perform absolutely without distraction, and the records of their performance were transmitted across the campus to the computer at the University's Computation Center.

this called for a small army of scorekeepers who worked all night—and sometimes several days—to total the scores, calculate the final standings and make up the tabulations.

The scoring is complicated by the necessity of showing the standings of individuals, teams and universities, all separately. Since some competitors are eligible for team medals only, others for individual events only, some for an all-around medal and a few eligible for

any combination of these, a second degree of complication is introduced.

The 370/168 was programmed with APL language, a tool execellently adapted to the collection and analysis of the complex scoring. The computer could on command immediately print out the standings in any given event, the team totals at any time and the complete record of any individual's performance during the meet, showing everything he had competed in and his standing in each event.

The computer was linked by telephone line to a terminal—a Tektronix 4013 computer display terminal—on the gymnasium floor. Three other terminals—Datel 1030's, which give a hard copy printout—kept the press, the coaches and the contestants abreast of the situation at all times.

DR. ADLER CITED BY CHICAGO IEEE



DR. ROBERT ADLER, FAMED INVENTOR and Zenith's vice president and director of research, was given the Outstanding Technical Paper award by the Chicago section of the IEEE, for a paper entitled "An Optical Video Disc Player for NTSC receivers."

Dr. Adler is best known to the television world for his invention of the ultrasonic remote control and the gated-beam tube for sound and color demodulation, as well as a widely used synchronizing circuit that improves color reception and a system of projection television that uses a laser beam modulated by ultrasonic diffreaction.

Among his other inventions are a highfrequency magnetostrictive oscillator and electro-mechanical filter and the low-noise beam-type amplifier known as the Adler tube.

New Marine backpack transceiver will have 280,000 radio channels

A far cry from the famous "walkie-talkie" of 30 years ago-which had a

useful range of only a few miles ("reliable" or minimum range, only 3 miles)



"MANPACK" COMBAT RADIO HAS 280,000 channels to select from. Using groundwave transmission for distances of a few thousand yards and skywave transmission for possible ranges in the thousands of miles, it will normally be used for distances ranging from local up to a few hundred miles.

and operated on a single frequency—the new "Manpack" radio offers the operator a choice of some 280,000 high-frequency channels, and can communicate over thousands of miles. (Normal working range would be from 50 to about 300 miles, plus short-range local traffic)

The new AN/PRC-104, being developed by the Hughes Aircraft Co. for the Marine Corps, is only 12½ inches wide, 11½ high and 2% thick. Its weight is 12½ pounds including battery, about one-third that of the famous SCR-300 walkie-talkie of 1944. It is so nearly automatic as to be called a "hands-off" transceiver. "The radioman simply goes into the transmit-receive mode, selects his frequency and hits the press-to-talk switch. Then the antenna is tuned, the set aligned, and the transmitter comes up immediately to full power," explains a Hughes communications manager.

The new Manpack is a single-sideband transceiver, producing 20 watts peak output power but using less than 5 watts average power. The battery operates 16 hours without recharging.

Production will be in two stages, a first step in which 37 radios and 10 vehicular mounts will be delivered to the Marine Corps for testing, then 5,000 sets to be delivered after the results of the Marine Corps' testing are incorporated into the equipment design and manufacture. (continued on page 12)

TUNER SERVICE CORPORATION





FEATURES

- A UHF Tuner with 70 channels which are detented and indicated just like VHF channels.
- A VHF Hi Gain Solid State Tuner.
- AC Powered.
- 90 Day Warranty.

Demonstrate the **SUBSTITUMER** to your customers and show improved reception with their TV sets.

You may place your order through any of the Centers listed below.

PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.



VHF OR UHF ANY TYPE (U.S.A. ONLY) \$ 995 UHF/VHF COMBINATION(U.S.A. ONLY) \$15 DO

- IN THIS PRICE ALL PARTS ARE INCLUDED.

 Tubes, transistors, diodes, and nuvistors are charged extra. This price does not include mutilated tuners.
- Fast, efficient service at our conveniently localed Service Centers.
- All tuners are ultrasonically cleaned, repaired, realigned, and air tested.

REPLACE

UNIVERSAL REPLACEMENT TUNER \$12.95 (Cana :a \$15.95)

- This price buys you a complete new tuner built specifically by Sarkes Tarzian Inc. for this purpose.
- All shafts have a maximum length of 10½" which can be cut to 1½".
- Specify heater type parallel and series 450 mA
 or 600 mA

CUSTOMIZE

- Customized tuners are available at a cost of only \$15.95. With trade-in \$13.95. (Canada \$17.95 and \$75.15)
- Send in your original tuner for comparison purposes to Franchises listed below.



WATCH US GROW

HEADQUARTERS BLOOMINGTON, INDIANA 47401 537 South Walnut Street Tel. 812-33	I-0411
ARIZONA TUCSON, ARIZONA 85713 P.O. Box 4534, 1528 S. 6th Ave. Tel. 602-76	
CALIFORNIA NORTH HOLLYWOOD, CALIF. 91601 10654 Magnolia Boulevard Tel. 218-76	
BURLINGAME, CALIF. 94010 1324 Marsten Road Tel. 415-34	
MODESTO, CALIF 95351 123 Phoenix Avenue Tel 200-5	
FLORIDA TAMPA FLORIDA 33606 1505 Cypress Street 7el 8/3 25	
HIALEAH, FLORIDA 33013	6-7078
GEORGIA ATLANTA, GEORGIA 30310 938 Gordon Street S.W Tel. 404 7	
ILLINOIS CHAMPAIGN, ILLINOIS 61820	
CHICAGO, ILLINOIS 60621	
SKOKIE, ILLINOIS 69976	5-0230
INDIANA RAMMOND, INDIANA 46323 6833 Grand Avenue 761, 219-84	5-2676
INDIANAPOLIS, INDIANA 46204	-3493
KENTUCKY LOUISVILLE KENTUCKY 40208 2920 Taylor Boulevard Tel. 502-63	
LOUISIANA SHREVEPORT, LOUISIANA 71104 3025 Highland Avenue Tel. 318-86	
MARYLAND BALTIMORE, MARYLAND 21215 5505 Reisterstown Rd., Box 2624 Tel. 301-35	4-1186
MISSOURI ST. LOUIS, MISSOURI 63132 10530 Page Avenue Tel 314-42	-0633
NEVADA LAS VEGAS, NEVADA 89102 1412 Western Avenue No. 1 Day 702-38	
NEW JERSEY TRENTOR NEW JERSEY 08638 901 North Olden Avenue el 609-39	-4233
FERSEY CITY NEW JERSEY 07207	-0999
JERSEY CITY, NEW JERSEY 07307	a-3/30
OHIO	1-5080
CLEVELAND, OHIO 44109	1-2314
OREGON PORTLAND, OREGON 97210 1732 N.W. 25th Avenus Tel. 503-22	≟-9059
TENNESSEE GREENEVILLE TENNESSEE 37743 1215 Snapps Ferry Road	¥-8451
MEMPHIST TENNESSEE 38111 3158 Barron Avenue	1-2355
TEXAS DALLAS, TEXAS 75218 11540 Garland Road Tel. 214-32	<u>"-</u> 8413
VIRGINIA NORFOLK, VIRGINIA 23513 3295 Santos Street 1804-35	i-2518
CANADAST. LAURENT, QUEBEC	
CALGARY, ALBERTA	

IF YOU WANT TO BRANCH OUT INTO THE TV TUNER REPAIR BUSINESS, WRITE TO THE BLOOMINGTON HEADQUARTERS ABOUT A FRANCHISE.

Where do the pros get their training?



Almost half of the successful TV servicemen have home study training and with them, it's NRI 2 to 1.

It's a fact! Among men actually making their living repairing TV and audio equipment, more have taken training from NRI than any other home study school. More than twice as many!

Not only that, but a national survey,* performed by an independent research organization, showed that the pros named NRI most often as a recommended school and as the first choice by far among those who had taken home study courses from any school. Why? Perhaps NRI's 60-year record with over a million students...the solid training and value built into every NRI course...and the designed-forlearning equipment originated by NRI provide the answer. But send for your free NRI catalog and decide for yourself.



Two Famous Educators... NRI and McGraw-Hill.

NRI is a part of McGraw-Hill, world's largest publishers of educational material. Together, they give you the kind of training that's geared for success...practical knowhow aimed at giving you a real shot at a better job or a business of your own. You learn at home at your convenience, with "bite-size" lessons that ease learning and speed comprehension. Kits designed to give you practical bench experience also become first-class professional instruments you'll use in your work.



25" Diagonal Color TV... Professional Instruments

As a part of NRI's Master Course in TV/Audio servicing, you build a big-screen solid state color TV with every

modern feature for great reception and performance. As you build it, you perform stage-by-stage experiments designed to give you actual bench experience while demonstrating the interaction of various stages of the circuitry. And your TV comes complete with console cabinet, an optional extra with other schools. Likewise, NRI's

instruments are a cut above the average, including a $3\frac{1}{2}$ digit precision digital multimeter, triggered sweep 5" oscilloscope, and integrated circuit TV pattern generator. They're top professional quality, designed to give you years of reliable service. You can pay hundreds of dollars more for a similar course and not get a nickel's worth extra in training and equipment.

Widest Choice of Courses and Careers.

NRI doesn't stop with just one course in TV/Audio servicing. You can pick from five different courses (including an advanced color course for practicing technicians) so you can fit your training to your needs and your budget. Or you can go into Computer Technology, learning on a real, digital computer you build vourself. Communications with famous Johnson transceiver. Aircraft or Marine Electronics. Mobile radio, and more.

Free Catalog... No Salesman Will Call.

Send the postage-paid card for our free color catalog showing details on all NFI electronics courses. Lesse n plans, equipment, and career opportunities are fully described. Check card for information on G.I. benefits. No obligation, no salesman will call. Mail today and see for yourself why the pros select NRI two to one!

If card is missing, write to:



NRI SCHOOLS

McGraw-Hill Continuing Education Center 3939 Wisconsin Avenue, Washington, D.C. 20016

^{*}Summary of survey results upon request.



- Complete range of replacement
- give you higher profit margins
- Quality your customers can depend on.

For the name of your local distributor call (516) 293-1500 Or write.

International Components Corporation

105 Maxess Road. Melville,

New York 11746 See us at NewCom booths #D20 & D22 May 5-8

Circle 5 on reader service card

new & timely (continued from page 6)

Dr. Lewis M. Hull honored by Radio Club of America

The Armstrong Medal for outstanding contributions to the radio art was awarded to Dr. Lewis Hull by the Radio Club of America, world's oldest radio club, at its 65th anniversary meeting and banquet November 15.

Dr. Hull pioneered in radio reception and in aircraft radio. Numerous firsts, such as single control for receivers. automatic volume control and the auto-



Dr. Lewis Hull

matic noise supressor, were developed under his direction. He was a leader in aircraft radio design and production, and in the early part of World War II practically every US combat plane was equipped with Dr. Hull's radios.

The Sarnoff Citation for significant contributions in electronic communication was given to Jack R. Poppele, former vice president of WOR and the Mutual Broadcasting System and later director of the Voice of America, Designer and builder of WOR, he and Dr. de Forest threw the switch that put it on the air in 1922. He then served as its Chief Engineer for 30 years. A Fellow and director of the Radio Club, he is also president of the Veteran Wireless Operators Association and of the de Forest Pioneers.

Dr. George Bailey, for years leader of the world's amateurs as president of the American Radio Relay League and the International Amateur Radio Union and later Executive Secretary of the IEEE, was made an Honorary Member of the Club. He is one of the seven members to hold that distinction.

The meeting was addressed by William M. Nicol, Director of Telecomnecessity of improved public safety munications of the British Home Office, London, England, who discussed the communication both nationally and internationally.

Besides the honors to Hull, Poppele and Bailey, 20 members of the Club were raised to the rank of Fellow. Among them were Norman Chalfin, author of a number of articles in this magazine, and Gerald F. J. Tyne, the historian of the vacuum tube, who described the making of early Audions for the readers of Radio-Electronics.

Ladies' electronic wrist watch tells time in two sentences

A new digital watch module, now in limited production at Hughes Aircraft Company's microelectronic products division, is called the first designed for ladies-size watches.

The solution of the size problem is unique, Instead of a four-digit display reading out the hour and minute, the new watch has a two-digit display, showing first the hour, then a second later, the minute.

As in earlier Hughes watch modules, the new model has a 768-kHz crystal oscillator, considered more accurate than the 32-kHz type used in most electronic watches. The integrated circuitry consists of CMOS (complementary metal oxide semiconductor) chips, and contains the equivalent of more than 1,500 transistors.

No Hughes watches will appear on the market. Hughes sells the modules to watch manufacturers, and the two-digit ladies' watches may soon be expected to appear under several of the better well-known brands.



TWO "POINTS IN TIME" ARE SHOWN in this interesting photo. The small wrist watch first shows the hour (above). The lower part of the picture, presumably photographed about a second later, indicates the minute. R-E

GENERAL ELECTRIC INTRODUCES THE 4-MINUTE HALF HOUR

GE's Latest In-Line Deflection and Convergence System hailed by TV technicians.

General Electric's latest in-line system makes it possible to converge a color set in three to four minutes, as opposed to the standard time of ten to 30 minutes. It was enthusiastically received at state conventions, where TV technicians and shop owners called it an important advancement in serviceability.



"Saves 30 minutes in convergence, compared to standard Delta convergence."
Dick Regner, RRR TV, Pearland, Texas



"G.E.'s...convergence system is great. They should have called it the 'time saver'." Sidney J. Sabel, Sabel's T.V. Service, Houston. Texas

"Easy to converge, little return to readjust controls."
Charles Miller, Miller's TV Service, Virginia Beach, Va.

Time saving. Very flexible. More control." G. F. Hill, Bay Area TV & Communication. Seabrook, Texas

Beats the heck out of other systems!"
E. B. Swanson, E. B. Swanson Company, Crosby, Texas

Another feature that met with enthusiastic approval was the fact that a technician requires no additional training to converge the set for a sharp, clear picture. A simple control location guide is included inside the set.

... simple convergence is extremely important. Will make training to technicians very easy."

Gary Gray, Master TV & Appliance Co., Roanoke, Va.

ʻIt's a serviceman's dream. Easy. Simple The way to go!'

Ira Evans, Evans TV, Freeport, Texas

"Fantastic! Great! I wish everyone weald go to it.

David Christian, Whitehill Elec., Kannapolis, N.C.

"Very simple. Easy to do without previous instructions.

Earl Asher, Asher TV, Denton, Texas



"Greatest improvement in convergence in 15 years. Bill Nichols, Radio & TV Service, Irc Petersburg, Va.

This latest in-line deflection and convergence system is in all GE 13" and 17" (diagonal) YA solid state chassis sets.

We're making it our business to make your business easier.

GENERAL (ELECTRIC

TV Receiver Products Dept., Portsmouth, Va.



CUT WIRE & CABLE INSTALLATION COSTS


. without cutting into insulation!

SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!





HEAT WIRE

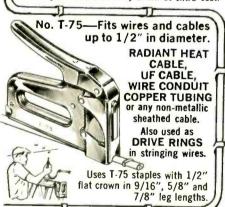

Arrow Automatic Staple Guns save 70% in time and effort on every type of wire or cable fastening job. Arrow staples are specially designed with divergent-pointed legs for easier driving and rosin-coated for greater holding power! All-steel construction and high-carbon hardened steel working parts are your assurance of maximum long-life service and trouble-free performance.

> Ask your Electrical Supply Dealer or write for further details.

ARROW FRSTENER COMPANY INC Saddle Brook, New Jersey 07663 Pioneers and Pacesetters For Almost A Half Century

Circle 7 on reader service card

equipment report

Hickok model 246 deluxe color bar generator



Circle 113 on reader service card

TEST EQUIPMENT IS GETTING MORE COMpact all the time. Unlike the circus, that says "bigger and better." they get "smaller and better." The use of IC's has been helpful in two ways, especially in the area of signal generators. The newest item in this line is the Hickok model 246 deluxe color bar generator. Only 8 by 3 inches, 6 inches deep, it has sixteen patterns instead of the five of older models.

For convergence work, there are three cross-hatch patterns; 15 by 21 bar, 7 by 11. and a single "crosshair" patternone vertical and one horizontal line, crossing in the center of the screen. For dots, the same counts, with the last being a single dot. Vertical line patterns have 21, 11 and one bar; the same for horizontal line patterns. These have 15, 7. and one in the middle. These singleline and dot patterns are most useful for finding that "center-dot" and adjusting the centering controls.

For any adjustment, alignment work or signal-tracing in the color section, the standard gated-rainbow 10-bar pattern can be used. The rainbow pattern without gating is also available. There's also a three-bar pattern, consisting of the R-Y, B-Y and G-Y bars, equally spaced.

For making grey-scale adjustments, a blank-raster pattern is provided. You name it, and there's a pattern in there that you need.

The rf-carrier output can be tuned to Channel 2, 3 or 4 with a simple screwdriver adjustment on the front panel. Output is balanced 300 ohm, with clips on a long lead. For signal-tracing and other testing, a composite video signal is also available. This may be modulated with any of the test-patterns. Amplitude of this is ± 2.0 volts p-p. The polarity and signal level can be adjusted by a slide control. The color level can also be adjusted from 0 to the standard 200%.

To make signal-tracing through the

color stages easier, two trigger output pulses can be used for a positive locking of the scope patterns. The horizontal pulse has a pulse-width of $10 \mu s$, the vertical pulse a width of 190 µs. Amplitude of the pulses is +10 volts. This can even be used as external sync with recurrent-sweep scopes, with good results.

If you like to use dots, but are getting old and dim-sighted (like me!) you can make the dots bigger. Just set the DOT ADJ. control on the front panel until the

dot is big enough to see.

The last item on the front panel is the gun-killer switches. These are very handy for making both purity and convergence adjustments. The leads, with insulationpiercing clips, are permanently connected and stowed in the handy compartment on the top of the case. The same compartment contains the power supply and line cord, RF output cable, and there's still room for alignment tools and other things.

That's about all of the dull statistics. The interesting thing about this type of instrument is its construction. IC design is very well suited to this kind of instrument. IC's generate very sharp, clean pulses, count up or down in frequency, and make special pulses of every conceivable shape. The model 246 uses a crystal at 378-kHz, and a frequency-divider IC counts down from this to develop the various patterns. A 3, 563795 MHz crystal, with a tolerance of 0.01%, is used to generate the signal for the rainbow display. So, all the patterns are rock-steady.

Most of the work in the model 246 Deluxe color generator is done by a very special MOS IC, developed by Hickok just for the purpose. It doesn't look too impressive; just an ordinary 16-pin DIP. Inside, however, is a complete outfit of all the digital logic circuits needed for these many functions. This has the equivalent of. 1,000 transistors! Two more stock linear IC's are used for generating the chroma signal and for the rf output amplifiers. Some plain old transistors fill out the list for such things as the dc regulator in the power supply. Incidentally, the dc power supply isn't even on the chassis; it's the black blob on the end of the line cord! This keeps any possible magnetic fields away from both generator and TV set. This has a dual-polarity output of +6.8 volts and -6.8 volts dc, tightly regulated.

Despite the many functions and parts used, this instrument is really "conservative." Its full power consumption is a tremendous ONE WATT!


410 to 1 you'll find the devices you need hore

Over 103,200 devices can be replaced by 250 RCA SK Series types. That's 410 to 1! Best ratio in the industry. Which means the odds are, SK is your best, fastest way to get what you need. With

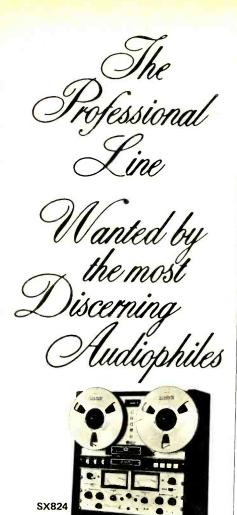minimum inventory.
And RCA provides the top quality you'd expect from a top manufacturer of OEM devices.
Same strict AQL standards, same strict Directorof Quality Assurance.
Get SK devices and your free 1975 SK
Series Replacement Guide from your local RCA distributor.







There is a distinct difference between tape equipment mass-produced by a consumer manufacturer and tape equipment built by a professional audio manufacturer. At Crown International this distinct difference involves five things: over-engineering, rugged construction, hand-crafting, exhaustive testing and conservative rating. After 26 years, Crown is the only remaining original U.S. tape equipment manufacturer still marketing professional quality to discerning audiophiles.

The Crown tape equipment line is designed for audio pros who make their living by recording, to whom an equipment failure at a taping session means money out the window. After four years, when many hi-fi models are traded in, Crown decks still produce recordings with truer fidelity than most new hi-fi decks. No wonder Crowns enjoy such high resale value.

At Crown, each active electronic component, each circuit module and each completed unit is tested from every angle. A tape deck undergoes over 100 hours cumulative testing. Finally, each unit is accompanied by its individual hand entered proof-of-performance report.

For free product data on Crown professional monaural, stereo and quadraphonic tape decks and players, write Crown, Box 1000, Elkhart, Indiana, 46514.



Made Only in America

Circle 9 on reader service card

letters

COMPUTER NEWSLETTER

A few of us in Denver are forming a support group of experimenters in microprocessors, their peripherals and programs. We are interested in providing a clearinghouse distribution service with particular emphasis on the Mark-8 Minicomputer and TV Typewriter. As many are aware, support from manufacturers to the individual experimenter is practically non-existent and comprehensive information exchange is difficult among individuals. We hope that a clearinghouse library service will help alleviate this situation.

The first major areas of interest are: Programs, Programming Aids, Circuits (Extensions and Modifications), Peripherals (TV Typewriter, Cassette Drives, Floppy Disk, etc.), BASIC Compiler Development, Suppliers of Parts and Literature, General Information. Others (as suggested).

We expect to produce a monthly newsletter containing abstracts of what is available and general information. Anyone with an interest in or a contribution/ suggestion for the clearinghouse should send a stamped self-addressed envelope to: The Digital Group Clearinghouse. P.O. Box 6528, Denver, CO 80209.

We hope this service will prove valuable and rewarding to all participants. THE DIGITAL GROUP **CLEARINGHOUSE** Denver, CO

STARLIGHT SCOPE

I really enjoyed the article on the Infrared Viewer in the August issue of Radio-Electronics. I have been building similar viewers since about 1971. I am glad to know that there are other people that are interested in the same things that I am

Fortunately I have been in situations where I could obtain more modern versions of infrared image converter tubes. The 6032 tube is an antique now, but it is available and at a reasonable price.

If you want to see in the dark, the only way to go is with image intensifier tubes that can amplify low light levels like starlight or moonlight. In my quest for better IR tubes, I discovered a company in Van Nuys, California that has surplus image intensifier tubes for sale. The tubes are larger than the 6032. They have 40-mm fiber-optic face plates on both ends of the tube and are about the size of a soft drink can. The fiber optics remove some of the optical distortion inherent in the older tubes with curved photocathode windows.

The image intensifier tubes were originally used in a night vision device

called an Owl Eye. They were used during the Viet Nam war for seeing in the dark, I have built two starlight scopes using these tubes and the results have been amazing. I thought that the IR viewers were good, but the starlight scopes are a thousand times better. Even on the darkest night, there is enough light for the tubes to amplify and make the scene being viewed look like daylight. Really amazing!

Anyway, I thought maybe some of your other readers might be interested in trying to build a viewer that uses starlight or moonlight instead of infrared. The company that has the tubes for sale is: Starlight Engineering, P.O. Box 7426, Van Nuys Main Post Office, Van Nuys, CA 91406

KEN LAWLER Glendale, CA

Thanks for the news, Ken; and while we're on the subject we've received a call from McNeal Electric Equipment Company, 4736 Olive, St. Louis, Mo. 63108. They state that they will supply a kit of parts, SS-8722 that contains 30 1/2-watt carbon resistors for the infrared viewer. It includes 24 100-megohm units; 5 22-megohm units and 1 100K unit. Total price is \$3.00 including postage. -Fditor

CB

Your attention is invited to a copy of the article from the October 1974 issue of the official publication of the International Associations Chiefs of Police. The Police Chief entitled "State Highway Patrol and CB'ers Work Together in Ohio." I am sure that your readers will find the article to be of interest.

While the Citizens Radio Service has many problems, there are millions of citizens who use it properly and regularly for good purposes. And also, the potential of Citizens Band emergency channel-9 is unlimited, especially as more and more local groups and police agencies monitor and respond to calls on channel-9.

After all the information about the bad aspects of Citizens band radio that have been publicized, it is only fair that the public and others such as Hams be informed of some of the good points. A lot is made over the actions of the CB'ers who violate the law, but (as with other things in our daily life) very little is said of the majority of law-abiding citizens who do things the way they are supposed to do.

Actually, even Hams could consider Citizens radio for their own use for contacts with their families, for contacts from their car in highway emergencies


(continued on page 18)

Weller controlled output soldering station

... has interchangeable brains in the form of a ferromagnetic sensor mounted in the tip that controls iron temperature through unique "closed-loop" circuit. Change tips...change temperatures. A Weller exclusive! It's that simple. 600, 700, or 800° F...your choice. Switching tips is always easy because Weller's exclusive triple-plated construction prevents oxidation and "freezing"... assures quick interchangeability. And nobody offers as many tip options. Over 50 combinations of configuration, reach, and temperature, one just right for optimum soldering action and maximum tip life on any job. UL-listed and OSHA-compliant, Weller's Model WTCP-L has its own built-in transformer...24 volt output for operator safety. Non-sinking holder supports and shields the comfort-grip, pencil iron when not in use. Grounded tip guards against static-discharge damage to sensitive workpiece circuitry. Base contains handy, tip-cleaning sponge and receptacle plus off/on switch and red indicator light. And non-burnable silicone power cord prevents annoying self-damage. Weller's WTCP-L Station has all the functional features you need for today's sophisticated soldering...at the most attractive price. No fancy extras that only add to cost. Also available as WTCP-2 for low-temperature service. See it...get it...at your local distributor. Ask, too, about DS-100 de-soldering units. Or request technical information Weller-Xcelite Electronics Division The Cooper Group

P O BOX 728 • APEX, NORTH CAROLINA 27502

Circle 10 on reader service card

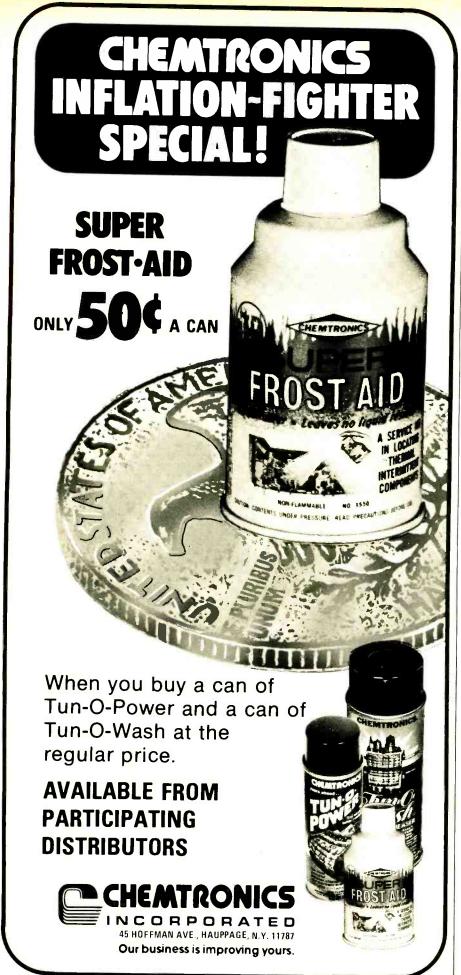

LETTERS

(continued from page 16)

and especially for monitoring at their home to provide a service to the general public. No matter how efficient ham radio is and how useful it is, the hams can't talk to the average citizen while the CB'er can.

The day is coming soon when every automobile will be equipped with a twoway radio at the factory. W. S. DAWSON

Portsmouth, VA

ELECTRONIC MUSIC

Interest in electronic music has grown and because of my wide experience in the medium-both theoretical and practical-I am starting a new journal entitled Analog Sounds. The new journal is based in the art of music and concerns the effect on the art of applied electronics. It will cover a range of subjects including discussions of method, procedure and practical techniques for making music.

Radio-Electronics has been a great stimulus to me in the development of my own creative work with the electronic medium. To help spread the word, I intend including with each issue of Analog Sounds an accumulative directory of relevant articles published in electronic magazines, including yours. This directory will take the form of a subject index with abstracts.

Analog Sounds is a quarterly journal depending solely on readers for support. Anyone interested in further information should contact me.

JACOB MEYEROWITZ Analog Sounds 145 West 55th Street Apt. 6-F New York, NY 10019


R-E

OLD SCOPE FOR COLOR TV?


I've got an old scope, in good working order, a 1957 kit model. Do you think it will do for color TV work? Don't know what it will do up around 4-5 MHz.-J.T., Commodore, Pa.

I'd say yes. Get a working color TV set, feed a color-bar pattern into it, and check the critical patterns, Compare these to the ones shown on the schematic. They don't have to be identical, but as long as you know what they look like, fine!

These critical patterns would be: Red, green and blue grids on picture tube; output of burst amplifier; output of 3.58-MHz oscillator, and output of bandpass amplifiers (through detector probe). If you can see a "bar" on the 3.58-MHz oscillator, you do not have to be able to see individual cycles. All you need to know is the p-p voltage. If you can get a good clean pattern at the video detector output, at horizontal frequency, it should do nicely.

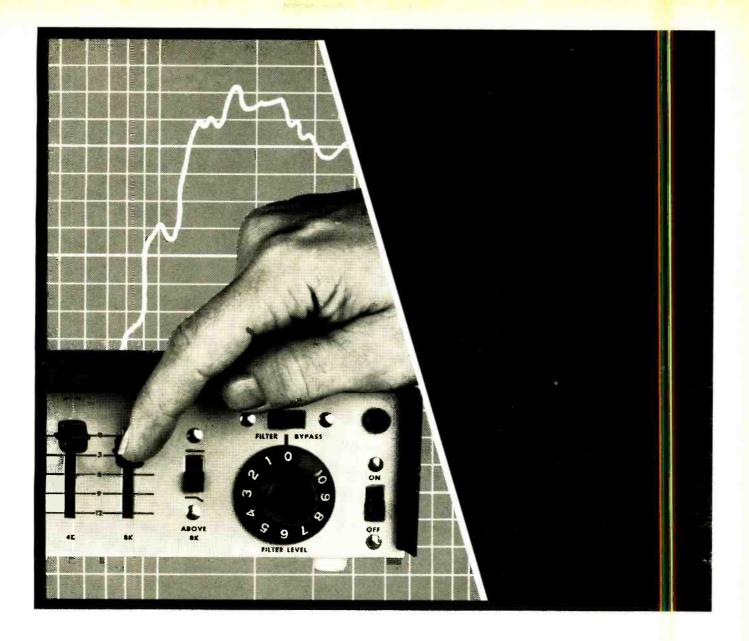

The Gain Mutiny.

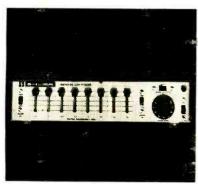

The gain limitation on most P.A. systems is often dictated by the ring threshold—that is, the point at which feedback sets in. Shure's M610 Feedback Controller suppresses these "ringleaders" before things have a charge to get out of hand. You can achieve significantly higher gain levels before feedback when you add the M610 to any existing system. Its versatile set of filters and roll-off switches smooths out the peaks and valleys in the system's frequency response, allowing you to shape the response to match the characteristics of any room. And, it will fit into a standard 19" audio equipment rack panel with its optional mounting kit. It might just be the essiest way ever for keeping feedback sources in line.

Shure Brothers Inc. 222 Hartrey Ave., Evanston, IL 60204 In Canada: A. C. Simmonds & Sons Limited



Manufacturers of high fidelity components, microphones, sound systems and related circuitry.



Anybody who's into electronics

certainly should be getting the everyday convenience and family security of automatic garage door operation...especially now, with Person Power's

great Electro Lift
opener...
made to fit
in the trunk
of your car,
designed for
easy handling
and simple
do-it-yourself
installation.
Available now at a
surprisingly low price from
your distributor.

P.S. Show off your opener to your friends and neighbors. You'll probably be able to pay for yours with what you make installing openers for them.

Perma Power


Chamberlain Manufacturing Corporation Perma Power Division

845 Larch Avenue, Elmhurst, Illinois 60126 Telephone (312) 279-3600

Circle 13 on reader service card

equipment reports

Telequipment D61 dual-trace scope

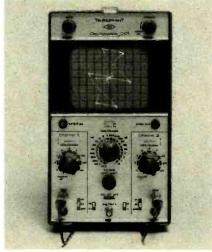

Circle 94 on reader service card

"TEKTRONIX" IS A MUCH-RESPECTED NAME in the field of "oscilloscopery," especially in the lab scopes and special units. So, when they put out another line of oscilloscopes, especially for electronics service technicians, these are apt to be pretty good. An example of this is the Telequipment line, originally from England. The model D61 is a good example of these new-generation test instruments. It's a compact, versatile instrument, with a response making it suitable for lab work, and special features for use in entertainment electronics servicing, particularly in color TV, stereo, quadriphonic, and so on.

This is a dual-trace, triggered sweep type, with identical vertical amplifiers having a bandwidth of up to 10 MHz, ac or dc. Risetime is 35 ns. You can do all of the standard tricks such as displaying two signals at once, from a single trigger source. You can also use both channels for making vectorscope patterns; you simply switch Channel 2 to act as the horizontal amplifier. The high bandwidth makes very good vectorscope patterns. As usual, I found this out the hard way. I was trying to make a flower by feeding the blue into the EXT. HORIZONTAL. Didn't work. So, I took a really drastic step; I read the instruction book. A flip of the switch and wham. Easy.

The triggered sweep can be used in NORMAL or AUTOMATIC modes, or externally triggered. A special "Tv" position uses a sync-separator to lock video waveforms firmly. It locks on the vertical sync

pulse for any setting of the TIME/DIV switch up to $100~\mu s/div$, and horizontal sync pulses from $50~\mu s/div$ on up to $0.5~\mu s/div$. (This switching is automatic.) Positive or negative pulses can be selected by the switch, for best lock.

The TIME/DIV (horizontal sweep speed) switch works from 500 ms/div up to 0.5 μs/div (That's one-half of a microsecond.) By pulling the TIMES-5 multiplier switch, the waveform is expanded 5 times for checking any part you need to see. This will give you sweep-speeds up to 100 ns/ div (A nanosecond is 1/1000 of a microsecond.) The trigger is free-running in the AUTO position. You do see a horizontal line on the screen to tell you that the thing's working. For those hard-tohold waveforms, external triggering can be used. For color TV, this is simple; just plug a plain test lead into the EXT TRIG jack, and place it near the deflection yoke cable. This will give you solid lock on anything. All you need is a minimum of 100 mV of pulse.

For either single- or dual-trace work, the trigger-selector switch will trigger the sweep on either the Channel 1 signal, the Channel 2 signal or on the external trigger pulse. For single-trace work, you move the Channel 2 trace off the screen (usually down) and set the trigger selector to Channel 1. This gives you the full height of the screen for p-p voltage readings, probably the most useful of any in TV work.

With modern construction, the matter of test-probe adaptability becomes very important. There are so many tight places that you've got to get into. The D61 uses the well-known "Tektronix probes." These are standard 10:1 low-capacitance type, compensated. There's a jack on the panel for instant checking of this calibration, and another for checking the volts/div calibration. The probe body isn't much bigger than a fountain pen; it has a very sharp pointed tip (result of actual experiment!)

Four special push-on tips are included. One is a plain, fixed hook tip, so that you can hang the light-weight probe to circuit points. The next is a spring-loaded retractable-hook type. This grips leads and connections firmly. The third is a special test-tip for any kind of IC's. It has a U-shaped cutout in the end, with another very sharp point centered in the U. With this, you can get the pattern on any pin of any IC without danger of shorting to adjacent pins. (With the dc position of the vertical amplifier switch,

(continued on page 22)

The New **January**Communications Frequency Counter



\$149⁵⁰

Mobile or Base Operation

THE NDC COMMUNICATIONS FREQUENCY COUNTER operates on 12 VDC or 115 VAC (with optional ac-dc converter). FIVE GIANT LED READ OUTS for easy day and night time clarity. Read out can be seen in bright sun light. FULLY SOLID STATE CONSTRUCTION on printed circuit boards that can withstand hard abuse and shocks. The counter contains a 10MHz TIME BASE for precision accuracy. The counter is easily connected via two SO-239 coax connectors.

FREQ RANGE: 1Hz- 99.999MHz

DISPLAY 5.6" LED

INPUT IMPEDANCE: 1 Meg ohm 40pf

SENSITIVITY: 1 volt in communications mode. With accessory probe 1 microvolt.

OTHER USES AND ACCESSORIES

In addition of being a communications counter, the counter can be used as a precision frequency counter for servicing or measuring unknown frequencys. Two optional accessories are available. Option probe NDC # 1174P converts the counter to a highly sensitive counter capable of reading any signal of one microvolt or more. In addition a 0-300 MHz prescaler is available which converts top counting range to 300 MHz.

ACCESSORY PRICES:

NDC test probe	\$39.95
NDC 300 MHz prescaler	\$49.95
	\$21.95

• GUARANTEE

The NDC COMMUNICATIONS FREQUENCY COUNTER is manufactured with premium parts, and is guaranteed unconditionally for 1 year against failure of parts or workmanship.

AVAILABLE FROM YOUR LOCAL DEALER OR FACTORY DIRECT

NATIONAL DIGITAL COMPUTER CO.

7502 MONTERY WAY, SCOTTSDALE, ARIZ, 85251 (602) 994-5110

Circle 14 on reader service card

(continued from page 20)

you can read logic highs and lows if you want to!)

Last but not least is a simple but very useful one; an insulating cylinder that will let you go right into an open BNC jack and read the signal. Due to the very small center connection of these jacks, this is very hard to do with an ordinary prod. The cables on the standard model are 4.5 feet long; another model is available with a 6-foot cable. The coax used is of a special type, very flexible and made for hard use.

The D61 is all solid state. The CRT is the only tube used. It is a flat-faced 8 x 10 cm type, with a P31 phosphor; a light green and very bright, due to the use of 3.5 kV accelerating voltage. The amplifier circuitry uses innumerable discrete transistors. FET inputs give the vertical amplifiers a very high sensitivity and high impedance.

The acid test of any scope, of course, is "How does it work on the bench?" The D61 passes with flying colors. I used it on quite a few sets, including one Hairy Monster with a difficult color-sync problem. Just to see if I could do it, I put the red-grid waveform on one trace, and the blue on the other, and then aligned the color stages. It worked (Using keyed rainbow source),

For the dual-trace mode, special baselines are provided on the graticule. These are dotted lines. The regular center baseline is a solid line. The vertical attenuators are calibrated from .01 to 5 volts/ cm. With the 10:1 low-cap probes, it gives you a useful range (single channel) from 100 mV/cm to 50 v/cm; since the graticule is 8 cm high, you can read waveforms with a maximum of 400

Controls are well-located and very easy to use. The vertical centering control, for each channel, is the center knob of a dual; the outer knob is the VOLTS/ DIV switch. The TIME/DIV switch's outer knob controls the sweep-speed, and its inner knob is the horizontal positioning for both channels. The switch, intensity and focus controls are above the crt. Once set up, you seldom have to touch these. The rest of the controls are grouped so that they can be very easily adjusted with one hand. The probes plug into jacks at the very bottom of the panel, out of the way.

The triggering of the D61 is very solid; even my pet test waveform, the flattopped comb from a keyed-rainbow color-bar generator, locks in firmly. This one has so many almost equal-amplitude peaks that it's tough to hold; the D61 grabbed it and held it!

With some of the things they're throwing at us now-IC's, modules, digital equipment, and so on and on, we are going to need good test equipment to handle them rapidly and accurately. The Teleguipment D61 fits this description very well. By the way, I was very pleasantly surprised when I compared the price of this instrument to others of similar spec's. One of the fringe benefits of this job is getting to work with a lot of fine test-equipment. I certainly got my jollies out of this one.

Castle "Master Subber" Mark V TV Signal Circuit **Analyst**



Circle 95 on reader service card

THE FASTEST AND EASIEST WAY TO FIND trouble in TV circuits is to feed in a normal test signal, then note the output. Normal output means that this stage is good. No output or abnormal output means that you've found the trouble. This is also the oldest way; we were using it with John F. Rider's "Servicing By Signal Tracing" back in the late 1930's! For any kind of signal testing in color or B/W TV, an instrument like (continued on page 24)

More for your money - \$199.00* - than any other Color Bar/Pattern Generator


Superpulse — Provides a big, fat square pulse for easy CRO tracing in the set, and a white window pattern for quick checks of gray-scale Bar Marker — Identifies tracking, smearing, and ringing right on the TV screen.

color bars, 3, 6, 9 - a "must" on overscanned sets.

IF Output — at 45.75 MHz for troubleshooting in mixer and IF stages. Excellent for servicing "modular" solidstate sets.

The RCA WR-515A offers time and moneysaving returns in fast diagnosis and adjustment in both home TV or commercial/industrial broadcast installations, including VTR's and video monitors. More details at any of the more than 1,000 RCA Distributors worldwide. Or, write: RCA Electronic Instrument Headquarters, 415 S. Fifth Street, Harrison, N.J. 07029.

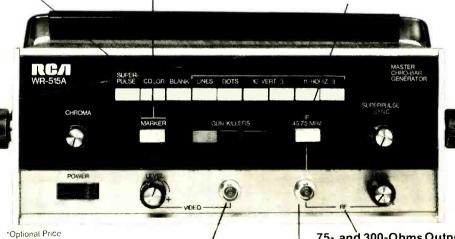Specialists demand the best tools of their trade.




2 volts. Video Output max. "+" and "-" at 75 ohms for commercial/industrial closed-circuit TV.

75- and 300-Ohms Output -at bothRFand IF. Snap-on BNC heads for fast impedance changes. RF works into MATV, CATV systems.

100% Digital ICs — Computer-type counters need no adjustments — ever! Patterns stay locked-in.

Electronic Instruments

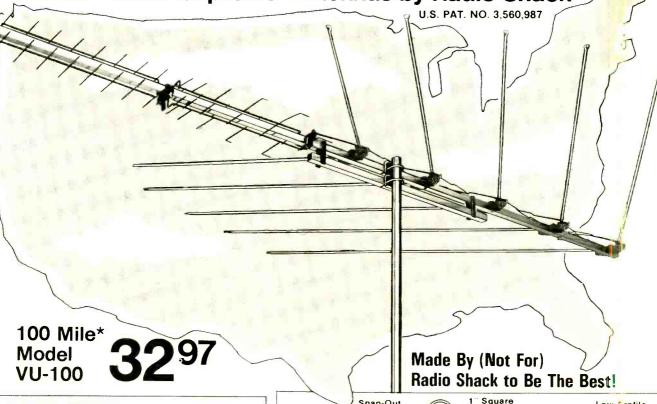

Snap-Out

Brackets

For Easy

Installation

igh-Impact Plastic

Insulators

Elements

Rigid

FREE New 1975 Radio Shack Catalog

OVER 2000 PRODUCTS EXCLUSIVES ON EVERY PAGE BEAUTIFUL FULL COLOR

Stereo • Quadraphonic • Phonographs TV Antennas • Radios • Citizens Band Kits • Recorders • Tape • Tools Auto Tune-Up • Electronic Parts Test Instruments • More!



164 pages of the finest in home and hobby electronics Respected brand names like Realistic, Micronta, Archer. Science Fair - and they re available only at Radio Shack stores and dealers nationwide! See what's really new in electronics by getting this catalog now

SEND FOR YOURS TODAY! FILL OUT COUPON BELOW

1975 Mail to Radio Shack, P Catalog Ft. Worth, Texas 76101	
Name	Apt. No
Street	
City	
StateZIP	

Radio Shack's 3-in-1 UHF/VHF/FM Color Supreme Antennas -

High Tensile

Aluminum

Boom with

Clamp

Secures

Antenna

To Mast

Multiple-Drive

System for

Best Reception

so good they're patented! You get unrivaled picture quality, superior FM even in rough signal locations. The "Sweep-Design" VHF elements enhance signal pickup and transfer. The special "Hi-Q" drive and parasitic systems capture more signals for the sharpest pictures on every UHF channel. And the gold bonded finish fights corrosion and rust to keep your antenna looking and working like new. U-bolt assembly maintains proper alignment. Pre-assembled for quick set-up - save of dealer

There's a Color Supreme to Meet Your Reception Needs — Near or Far

	Range in Miles*		Boom	No. of		
Model	VHF	UHF	FM	Length	Elements	Ony
VU-60	60	40	40	40"	12	12 97
VU-75	75	50	50	50"	14	17 97
VU-90	90	60	60	80"	23	26 37
VU-100	100	90	90	100"	32	32 37
VU-110	110	90	90	120"	34	42 97
VU-150	150	90	90	150"	35	5137

*Ranges based on reception over flat, open terrain

Radio Shack's the Place to Shop for TV Antennas --Everything in Installation, Hardware, Accessories



OVER 3000 STORES . 50 STATES . 7 COUNTRIES Retail prices may vary at individual stores

Circle 16 on reader service card

Low-Frofile

Cradle

Mounts on

Our Four

Lar pest Models


Lo's-Loss

Corrosion

Resistant

Te minals

24

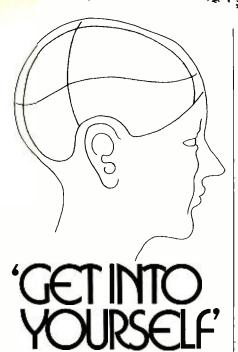

Discover your Alpha Brainwaves with this professional Biofeedback System.

Lowest Cost Brainwave Monitor

EICO introduces a price breakthrough in the fantastic new field of brainwave biofeedback...a completely safe, battery operated, biofeedback system that offers features and sensitivity comparable to professional models costing much more.

You Will Be Amazed At What You Hear

The BW-300 will detect your alpha brainwaves (which occur when you are totally relaxed) and produce a tone varying in frequency according to your mental state.

100% Solid State Circuitry

Reliable All Solid State IC Circuit Design features an active filter that isolates alpha brainwaves and a high-gain low-noise amplifier providing 5-microvolt sensitivity for easy alpha recognition. The BW-300 is supplied with stethescopic earphones, electrodes headband, contact cream and

FREE EICO CATALOG

For latest EICO Catalog on Test Instruments, Automotive and Hobby Electronics, Eicocraft Project kits, Burglar-Fire Alarm Systems and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

EICO-283 Malta Street, Brooklyn, N.Y. 11207

Leadership in creative electronics

instructions.



WIRED 59.95

EQUIPMENT REPORT

(continued from page 22)

Castle TV's "Master Subber Mark V" is invaluable.

The original Tuner Subbers were and are very useful. They will check out tuner and i.f. troubles. The Master Subber Mark V, will provide normal test signals for every signal-circuit in the set! It is a deluxe Tuner Subber, with 40-MHz i.f. output. This will check the tuner and i.f. stages. There's more: it also has not one but two video signal outputs, positive and negative going sync. So, you can match any type of detector circuitry. With a color program on the input, these signals also have the color informataion, so that this can be used for checking out bandpass amplifiers, demodulators, etc. (Want a fixed pattern instead of a TV station signal? Just feed rf output of your color-bar generator into input of Master Subber!) These video outputs can be up to 7 volts peak; so they will drive almost any video amplifier stage.

Check the sound stages? Sure. The unit has a 4.5-MHz sound i.f. output; this checks the sound i.f. and FM limiter stages. There is also an audio output, up to 500 mV, for direct testing of audio stages after the detector. This is also fed to a small built-in speaker in the Master Subber's cabinet; it has its own volume control, so that you can turn it off if you don't need it.

This instrument can be used to check antennas. By hooking it to the leadin, you can tell instantly whether you have a suitable signal-level. This can be done in two ways; one, listen to the TV sound from the built-in speaker. Two, watch the video-carrier level meter on the front panel. If you want to, you can calibrate the reading of this meter, at a certain

setting of the MASTER GAIN control, with a field-strength meter. If this is set to a certain reading at 1000 microvolts (standard level for most CATV systems), you can also check CATV and MATV systems. This is very useful in cases where that old question "Is it the set or the antenna?" arises. In strong-signal areas, where the set's on rabbit-ears, etc., you can check, just the same. The MASTER SUBBER has its own built-in monopole antenna which telescopes into the case.

All of these functions are built into a compact plastic case, no bigger than the original Tuner Subber. Power is supplied by two 9-volt alkaline batteries, or by a 120-Vac plug-in power supply; this automatically disconnects the internal batteries when used. A LED pilot light tells you when it's on.

One essential thing with an instrument like this is the correct output cables, so that it can be hooked to any type of set with no trouble. They are here. Four separate "Mastermatch-coupler" cables are included, some with "RCA Phono jack" terminations, both male and female, others with alligator clips (color coded), and so on. If greater length is needed, one can be plugged into another to reach hard to get-at places.


Dame Fortune makes it easy for me to test test equipment! This time, she provided me with an elderly Motorola B/W with indeterminate problems. Subbing the tuner didn't help. Subbing the video didn't help. I checked the sound. Something finally worked! The trouble eventually turned up in the contrast control on the video output stage! So, I got a chance to use all of the many functions of this versatile instrument at once, and it worked to perfection. All parts of any TV set, color or B/W, tube or solid state, or modular, can be checked quickly and accurately with "real TV" signals. Very useful indeed.

Leader LCG-395 universal color bar pattern generator

Circle 96 on reader service card

THE LATEST OFFERING FROM LEADER Electronics Corp. is a bar-dot generator with some interesting features. Built with IC's, this compact instrument provides the service technician with some unusual and quite handy patterns.

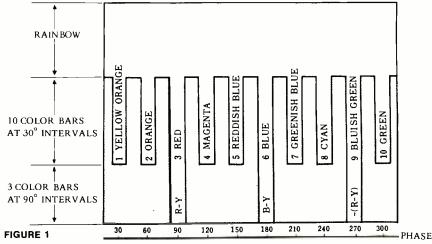The color-bar pattern (see Fig. 1) is basically the standard 10-bar keyed rainbow. However, the color-bar pattern is unusual in that it's divided into thirds. Across the top of the screen is (continued on page 30)



TeleMatic

PROFESSIONAL TEST RIG SYSTEM TRS 330

For SERVICING MOST OF TODAY'S TV

TUBE AND SOLID STATE

FACTORY Authorized \$30.90 Tube Allowance

SAVE HOURS WITH THIS PROFESSIONAL SYS-TEM. SIMPLEST TO USE. INCORPORATES STATIC CONVERGENCE. NO COMPLICATED AD-JUSTMENTS REQUIRED. YOU ARE PREPARED TO SERVICE MOST OF TODAY'S TUBE AND SOLID STATE TV'S WITH THE SYSTEM'S POPU-LAR ASSORTMENT OF ADAPTORS.

Free Subscription for Reference Material to thousands of TV Chasnis

leleMatic Com so-Dea



TeleMatic Sub-Tuners save hours of guesswork by rapidly pinpointing trouble in the antenna, UHF or VHF Tuners, or I.F. Stages. Powered by popular transistor batteries.

COMBO-DEAL STD 440

Send literature and name of my distributor.

Telematic 2245 Pitkin Ave., Brooklyn, N.Y. 11207

KT-730 VHF/SUB \$45.00 KTU-745 UHF/SUB 16.95 REGULAR PRICE \$61.95 SAVE (On deal) 12.00 SPECIAL ONLY \$49.95

NAME			
HAIVIE			-
ADDRESS			_
CITY	STATE	ZIP	



Circle 18 on reader service card

25

exciting **new** projects for '75



NEW Heathkit Color Organ

"Kaleidoscopic" light show you hang on a wall. 4 filters separate sound into 4 bands; each controls 35 brilliantly colored lights red for bass, blue for low midrange, green for upper midrange, amber for treble — 140 lights in all, pulsating in time to music of your hi-fi. Wide 25 db dynamic range; great for any type of music. Walnut-grain vinyl-clad case, 23" x 23" x 4½". On/off/sensitivity control.

Kit TD-100679.95*



NEW Portable Digital Multimeter

Professional performance at a budget price. 26 ranges resolve voltages to 100 µV, currents to 100 nA, measures AC & DC current up to 2 A, resistance from 100 to 1000K ohms. Big, bright 31/2-digit readout with automatic overrange & polarity indications. Built-in reference standards for easy field calibration. With rechargeable batteries & AC line cord.

Kit IM-2202179.95*



NEW DC-10MHz Oscilloscope

A great scope - a great value! Perfect for TV servicing. 10 mV vertical input sensitivity, time bases from 200 ms/cm to 200 ns/cm, internal or external digital triggering, two input channels. Mu-metal shielded tube with 8x10 cm graticule.

Kit 10-4530299.95*



NEW 40 kV Metered Probe

Ideal for high-voltage TV measurements—up to 40 kV with \pm 3% accuracy. On/off switch.

Kit IM-5210 Assembled SM-5210 ... 24.95*



NEW **Emergency Car Strobe Light**

Highly visible amber flash warns other drivers when your carstalls or breaks down. Non-marring magnetic base, 12' cord, plug fits cigarette lighter. For 12 VDC.

Kit GD-102629.95*



NEW Windshield Wiper Delay

Provides exactly the wiper speed you need for safe driving in any weather, from light mist to heavy rain. Works with most 12 VDC positive or negative ground cars.


Kit CH-106814.95'



NEW AM/FM Digital Clock Radio

Electronic digital clock with standby battery power to keep time (without display) during power interruptions, electronic "beep" alarm with adjustable volume, 5 μV FM sensitivity, quality sound. Less batteries.


Kit GR-1075129.95*

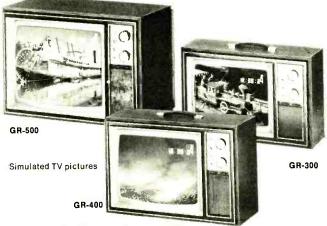

15. 17 & 19" (diagonal) Color TVs with On-Screen Digital Readout

Advanced Heath engineering and outstanding picture quality. All feature on-screen channel readout & optional plug-in clock modules. ture on-screen channel readout & optional plug-in clock modules. In-line picture tubes with slotted shadow masks provide exceptionally bright, sharp pictures. In the GR-400 and 500, black matrix tubes improve contrast. And here's something new—static toroid yoke & magnet assemblies never require convergence & fixed LC filters eliminate instrument IF alignment. GR-300 & 400 come with walnut veneer cabinets; cabinets for the GR-500 start at \$39.95.*

Kit GR-300 (15" diag.), with cabinet

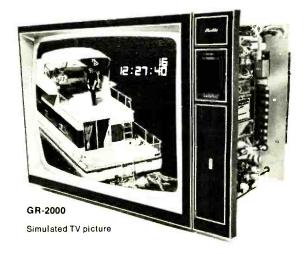

Highly Acclaimed GR-2000 Digital-Design Color TV

The set that brought TV into the digital age - and still one of the finest made. Tuning is totally digital solid-state & the channel number appears right on the big, 25" (diagonal) screen. The optional clock module also displays the time on the screen. For the ultimate in convenience, add the optional wireless remote control. Can be custom mounted; optional cabinets start at \$119.95*.

26

at traditional Heathkit savings

There are 350 more in the new FREE Heathkit catalog!


Who can build our kits? Anybody!


For over 27 years we've made superb electronic equipment that anyone can build—even with no prior knowledge of electronics or kit building. Famous Heathkit assembly manuals guide you step by step, showing you exactly what to do—even how to solder like a pro.

And we back every Heathkit purchase with people. Expert technical consultants at the factory and trained service personnel from coast to coast are ready to help every step of the way. Thousands of Heath customers will tell you—we won't let you fail!

When you're finished, you'll own one of the finest products available—kit or assembled. But don't take our word for it, independent reviewers consistently praise their quality.

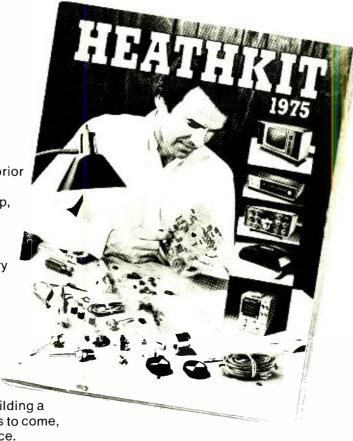You'll enjoy the satisfaction—and savings—of building a useful product with your own hands. And for years to come, you'll enjoy its unexcelled quality and performance. Build it yourself—with a little help from Heath.



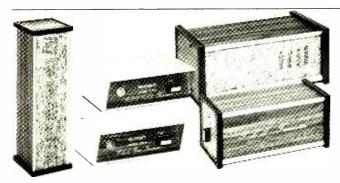

NEW Heathkit/Delta Home Security System

Everything you need for a complete home security system. Remote detectors connect to Central Processor through your home's electrical wiring. Inputs for ultrasonic intrusion detector, heat & smoke detectors plus "panic button" & remote on/off switch. Central Processor features built-in speaker; output for an external speaker. Sounds alarm during power failure.



Stereo & 4-Channel Components

Budget-priced systems with component-quality sound. Pick your own system—an AM/FM stereo receiver, \$139.95*; an AM/FM stereo receiver with 8-track player, \$179.95*; a 4-channel 8-track player, \$169.95* or a 4-channel AM/FM receiver with 8-track player, \$25.9.95*. Add speakers (just \$34.95* per pair) and our \$44.95 ceramic changes, and you get our 5% system discount. A whole stereo system (shown above) starts at just \$208.86*. See them in the new Heathkit Catalog.

Send for your free 1975 Heathkit Catalog today!

Your free 1975 Heathkit Catalog describes the world's largest selection of electronic kits. You'll find kits for every interest, every age, every budget. Choose from digital-design color TVs, stereo and 4-channel hi-fi components, fishing and boating electronics, model radio-control equipment, amateur radio kits, digital clocks, weather instruments, shortwave and digital clock radios, treasure finders, automotive tune-up tools, service instruments, and educational kits. See why you get more for your money when you build it yourself — send for your free copy today.

Heath Company Dept. 20-04 Benton Harbor, N	Aichigan 49022	Schlumberger
Name		
Address		
City	State	Zip
PRICES & SPECIFICATION MAIL ORDER PRICES; F.	NS SUBJECT TO CHANGE WITHOUT NOTICE.	C L-:i30

Circle 100 on reader service card



to dispute this Fact)

Never wears out or needs any Maintenance!



it gives you Maximum Power. with continuous PEAK PERFORMANCE

.. while reducing Maintenance and Operating Costs!

- The Allison OPTO-ELECTRIC System eliminates the Points and Condenser, replacing them with an OPTO-FLECTRONIC TRIGGER, using a Light-Emitting Diode and Phototransistor As there are NO moving parts in rubbing contact...Timing adjustments are PERMANENT. The only "TRUE" Electronic Ignition...that you can buy for under \$100
- Gives 40-Times more Timing Accuracy than ANY system using "Mechanical" Breaker-Points! UNLIMITED RPM! 'Electronically-Controlled' DWELL automatically supplies HIGHEST Performance at both Low and High speeds. Spa strength does not fall off at high RPM. POSITIVE SPARK helps eliminate "Misfire" for faster acceleration and improved Engine Performance! Smoother running (No timing fluctuation as with Magnetic Units). Easier Starting under any condition! Sparkplugs LAST 3 to 10-Times LONGER.

All SOLID-STATE Components. UNAFFECTED By Temperature.
Moisture, or Vibration! Highest grade materials Guarantee you solid, Dependable Performance.

Perfect Timing and Dwell never change.

Pays for Itself! Eliminates ignition Tune-Ups forever! "INFINITE LIFE"... Once installed... Never needs replacing.

 PERFECT TIMING INCREASES Engine Efficiency and Gas Mileage. SAVES Precious Fuel! Allison gives you MAXIMUM Engine Efficiency 100% of the time... and that's the name of the game for BETTER Gas Mileage and Economy.



QUICK AND EASY INSTALLATION

- # If you want the BEST, and SAVE! This is IT!
- OROER with CONFIDENCE.

Only \$4 Q 95 SATISFACTION GUARANTEED!

COMPLETE. 1-YEAR FACTORY WARRANTY. · As you can see, you're not taking any

- chances at all. Send your Order Today.
 State Make, Year, Engine Size. (Calif. Res. add Tax) ● (So New...it's Sold ONLY FROM FACTORY DIRECT).
- You may use your MASTER CHARGE or BANKAMERICARD. Send us (1) Your Number, (2) Interbank No., (3) Exp. Date. Before buying any other Type ignition system

Send Postcard for our FREE BROCHURE.

If you have already installed a C-D ignition system. Modernize and Increase its Efficiency. CONVERT YOUR "C-O" UNIT TO BREAKERLESS! Opto-Electric "TRIGGER UNIT"... Only '34.95



 Our BEST Salesmen are the owners and users of our ALLISON System!

ALLISON

AUTOMOTIVE COMPANY 1269- L, East EDNA PL., COVINA, CAL. 91722 **EQUIPMENT REPORT** (continued from page 24)

an unkeyed rainbow pattern. The center of the screen contains the standard 10-bar keyed rainbow, and the lower third of the screen is a spaced threebar pattern with R-Y, B-Y, and R-Y (Cyan or light green) color-bars. It sounds odd, but in use it can be very handy.



There is a white raster pattern for setting grey-scale and checking for hum bars in the video. Next comes another new pattern called a "window". It's a white rectangle in the middle of a black border and is used for checking the display pulses (sag, overshoot, ringing). After this, a "staircase" pattern which contains a black bar across the top third of the screen. The rest of the screen is made up of five equal-size vertical bars, of 20, 40, 60, 80 and 100% (white) modulation. This can be used for checking video response and contrast.

The convergence pattern (See Fig. 2) has some handy features. It's a

overscanned in either direction, etc. For the final touch, there is a small set of 6 dashes in the lower right corner. This is a "corner marker" which tells you whether the deflection yoke is hooked up with the right polarity. If this marker isn't in the lower right corner, something needs reversing.

A set of gun-killer leads, switches and clips are provided. All of the gunkiller and pattern-selector switches are generous-sized bushputtons. The RF output may be taken from either 300ohm balanced or 75-ohm unbalanced jacks. Output signal level is controlled by the RF adjustment, RF output can be set to Ch. 5 or Ch. 6 by a selector switch on the front panel. This switch also provides for the use of a 40-MHz video i.f. output for direct injection into the i.f. input, a useful feature for checking the tuner.

A 75-ohm video signal is also available at a front panel jack. Polarity and level (max. 10 mV) of this signal can be set by the VIDEO CONTROL. A trigger signal for signal tracing with a scope is also provided for on the front panel. This can be of either horizontal or vertical frequency, or a composite. This has an open-circuit voltage of about 3 V p-p.

The last control on the front panel is marked "Brightness". It does control the brightness of all patterns except for the staircase, which is fixed. It also acts as a "color" control for the color-bar pattern, with the normal range of 0-200% saturation.

The LCG-395 is a compact instrument, only 3" high by 8" wide, with a

SAFETY ZONE MARKERS CROSSHATCH DOTS VERTICAL CENTER SAFETY ZONE MARKERS HORIZONTAL -CENTER 80% 100% FIGURE 2 CENTER DOT CORNER MARKER

crosshatch with 10 horizontal and 7 vertical bars. This is only the beginning! Inside this is another pattern made up of dashed lines. There is a horizontal and vertical cross with a "center dot". Around the edges of the pattern is a "safety zone" dashed-line pattern. This shows you instantly whether the raster is centered, linear,

heavy bail-type handle that serves as a stand for bench use. Long standoffs are provided on the back, for storing the line cord or for use as legs if you want to use it in a vertical position. All controls on the panel are clearly marked, with lines going to the associated jack. All pushbuttons are big enough for easy use.

Why You Should Buy Telequipment

Telequipment products are designed to meet the needs of the cost-conscious buyer without sacrificing reliability or general utility.

The Telequipment line of Tektronix oscilloscopes combines low price with a number of features not usually found in other oscilloscopes of the same price range. Features such as calibrated sweep rate and vertical step attenuators, variable controls, triggered sweep, probe-calibrated outputs, illuminated graticule and TV-field or line triggering, make these instruments versatile and easy to use.

The 10 MHz, dual trace, D61 is exceptionally easy to operate and low priced at only \$545. Its stable triggering characteristics, front panel simplicity, and versatility make it an excellent choice for industrial and educational applications. X-y analysis vector capability and TV line or frame triggering also make it especially well suited for service shops.

The Telequipment line, in addition, includes the S51B, a single-trace, 3 MHz oscilloscope with either automatic or normal trigger modes—at \$325, the lowest priced oscilloscope offered by Tektronix—and is excellent for use in audio to medium frequency applications. In addition, there's the DM 64, a 10 MHz dual-channel, bistable storage oscilloscope for \$1195, and more...


... The D67 oscilloscope at \$1125 combines dual trace, the 25-MHz bandwidth at 10 mV/div, FET inputs, regulated power supplies, and all solid-state circuits with delayed-sweep capability—a combination of features seldom found in a low-priced oscilloscope. The D66 offers all of these features except delayed sweep at an even lower price, \$875. Both feature a SUM mode with normal/invert capability that improves display of small signals in the presence of common mode noise. The easy-to-operate CT71 curve tracer enhances the line providing a dynamic semiconductor measurement capability by displaying characteristic curves of transistors, FETS, and diodes

Available at only \$895, it is well suited for industrial application and student labs.

For more information about Telequipment instruments, contact your local Tektronix Field Office, or write Tektronix, Inc., Beaverton, Oregon 97077. In Europe, write Tektronix Limited,

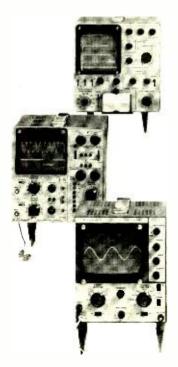P.O. Box 36, St. Peter Port, Guernsey, Channel Islands. In Canada, write Tektronix Canada Ltd., Quebec, Canada.













Circle 20 on reader service card

Circle 30 on reader service card for demonstration

31

Another advance in tube technology from RCA

RCA, the leading manufacturer of receiving tubes, offers you advanced types to satisfy the needs of the replacement market. We can do this because RCA has unique design capability that comes only with years of tube design and manufacturing experience. This means that when you install RCAmade tubes, you're selling quality tubes with the newest and best innovations in design and performance.

A dynamic approach to receiving tube technology, geared to the rigorous demands of the replacement market, RCA's exclusive, new 6MJ6/6LQ6/6JE6C brings added reliability to horizontal deflection cir-

cuits, the most critical in your customer's set. Manufactured exclusively by RCA, this new rugged horizontal output tube with the integral envelope-top-cap assembly, which totally eliminates loose top-cap problems, represents another significant advance in tube technology from RCA.

You can be certain that RCA will continue to lead the way in the receiving tube business. After all, your tube business is our tube business and we expect to share this high volume business with you for a long time to come.

See your RCA distributor for all of your tube needs.



Rugged Features of the 6MJ6/6LQ6/6JE6C

- Integral-Envelope-Top-Cap Assembly
- Rigid Cage
- Stable grid alignment
- Excellent Heat Dissipation

RСЛ

RCA/Electronic Components/Harrison, N.J. 07029

20 easy-to-build COSMOS burglar alarms - part 1

These burglar alarm circuits are simple yet very effective. Many options exist for each circuit, so the final circuit you build is entirely your own choice.

by R. M. MARSTON

A BURGLAR ALARM IS THE MOST VALUable piece of equipment that the electronics buff can build for use in the home. It helps give the owner peace-of-mind when the house is empty, and gives a high degree of protection against theft of property or damage. It may even help protect the owner's life.

The requirements of the ideal burglar alarm system are stringent. The system must be immune to giving false alarms. It must be battery powered and consume negligible standby current. It must be capable of driving almost any type of alarm generator (bell, siren, etc.). Finally, the system must be versatile enough to meet the differing needs of individual owners. It should, for example, be capable of providing either self-latch or autoturn-off operation, and have provisions for incorporating 'panic' and other facilities.

In Part 1 of this series, we show how you can use modern COS/MOS (COmplementary-Symetry Metal-Oxide Silicon) digital integrated circuits to build tailor-made burglar alarms which meet all of the requirements outlined above. These alarms can be as simple or as complex as you want to make them. Later in the article we'll show how you can make your own 10-watt alarm-call generators to use in place of alarm bells or sirens, and we'll give advice on how to select alarm sensor installations to suit your own home.

Basic alarm circuits

The simplest and most widely used type of burglar alarm circuit consists of a number of switches or other sensor devices wired to doors, windows, etc., The output of these sensor devices are used to trigger an alarm bell via a self-latching relay. The sensor devices may be the normally-open (N.O) type of switches or reed-relays which activate the alarm when they are momentarily closed, or they may be normally-closed (N.C) type of switches or lengths of wire or foil which activate the alarm when they are momentarily opened or broken.

Figure 1 shows a practical burglar alarm circuit using a normally-open type of sensor. During normal operation, when switch S2 is in the STANDBY position and sensor switch S1 is open, the relay is de-energized. When S1 is momentarily closed, it connects the relay coil (RY1) directly across the supply lines, and the relay is energized. As the relay contacts RY1-2 close and activate the alarm generator, contacts RY1-1 close and short out sensor switch S1, thus latching the alarm generator on. Any number of normally open sensor switches can be wired in parallel with S1 and used to activate the alarm system from different parts of the house.

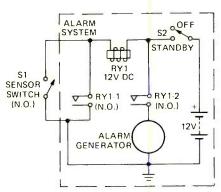


FIG. 1—BASIC BURGLAR ALARM CIRCUIT using normally-open sensor switches.

The advantages of the Fig. 1 circuit are that it is simple, virtually immune to giving false alarms, consumes zero standby current, and is capable of driving any type of alarm generator via relay contacts RY1-2. The disadvantages of the circuit are that it can be simply disabled by cutting the leads connecting S1 to the input of the alarm system, and the system lacks vers. tility.

An alternative basic type of burglar alarm circuit is in Project 1. This is a practical burglar alarm circuit using normally-closed sensor switches. During normal operation, when switch S2 is in the STANDBY position, the baseemitter junction of transistor Q1 is shorted out by sensor switch \$1 so Q1 is cut-off and the relay is de-energized. A standby current of 1-mA flows through resistor R1 under this condition. When sensor switch \$1 is momentarily opened, base current flows into Q1 via R1, driving the transistor into conduction and energizing the relay. When the relay is energized, contacts RY1-2 close and activate the alarm generator, and contacts RY1-1 close and short the relay directly

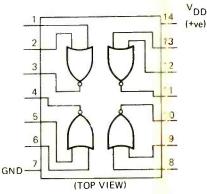


FIG. 2—PIN CONNECTION diagram of the CD4001AE quad 2-input NOR gate IC.

across the supply lines, thus latching the alarm generator on. Any number of n.c. sensor switches can be wired in series with S1 and used to activate the alarm from different parts of the house.


The major advantages of the Project 1 circuit are that it is simple, virtually immune to giving false alarms, can drive any type of alarm generator, and is difficult to disable-since it can be disabled only by shorting out the sensor switches or the leads connecting S1 to the input of the alarm system. The greatest disadvantage of the system is that it consumes an appreciable standby current (1-mA). A less serious disadvantage is that the basic circuit is lacking in versatility, although it should be noted that the design can be made to function simultaneously as both a make-to-operate and a breakto-operate alarm by simply wiring normally closed sensor switches in series with S1 and normally open sensor switches in parallel with relay contacts RY1-1.

Finally, Project 2 shows the practical circuit of a simple COS/MOS-aided relay burglar alarm that can be activated by both normally open and normally closed contact sensors. The COS/ MOS IC used in this circuit (and all the remaining circuits described in this article) is a CD4001AE quad 2-input NOR gate, manufactured by RCA. The basic circuit and pin connections of this IC are shown in Fig. 2. Each of the four gates of this IC feature a near-infinite input impedance, virtually zero standby current, and a low output impedance. In the Project 2 circuit, only one of the gates is used, and is connected as a simple inverter. All the unused inputs of the remaining three unused gates are tied to ground, as indicated in the diagram.


The circuit in Project 2 works as follows. During normal operation, when switch S3 is in the STANDBY position and sensor switch S1 is closed and sensor switch S2 is open, the input of gate A is held close to the positive voltage level via the voltage divider R1 and R2, so the output of the gate is at ground potential, and transistor Q1 is cut-off and the relay is de-energized. A standby current of only a microamp or so flows in the circuit under this condition (via R1-R2, and via the leakage resistance of Q1).

When sensor switch S1 is momentarily opened or sensor switch S2 is momentarily closed, the input of gate A is pulled to ground potential via R2 or S2, and the output of gate A immediately switches to the positive rail voltage and drives transistor Q1 into conduction and energizes the relay via resistor R3. When the relay is energized, contacts RY1-2 close and acti-


BASIC BURGLAR ALARM CIRCUIT

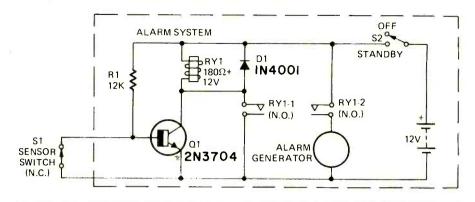

2. ALARM CIRCUIT USING COS/MOS LOGIC

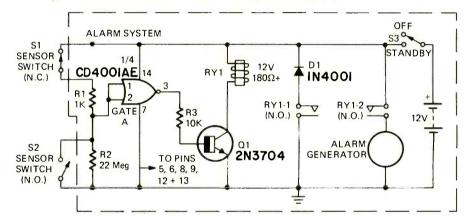

3 SIMPLE SELF-LATCHING BURGLAR ALARM

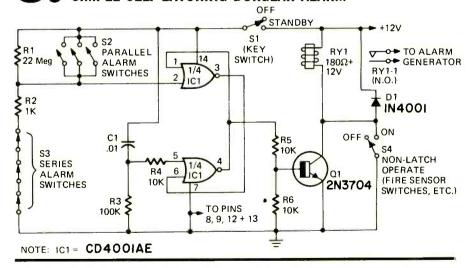


vate the alarm generator and contacts RY1-1 close and short the relay directly across the supply lines, thus latching the alarm generator on. Any number of n.c. sensor switches can be wired in series with S1, and any number of n.o. switches can be wired in parallel with S2.

The advantages of the Project 2 cir-


cuit are that it is reasonably simple, virtually immune to giving false alarms, is difficult to disable, can drive any type of alarm generator, and is very versatile. Its versatility comes from the fact that gate A can readily be used in a variety of modes, and forms only one quarter of the number of available gates in the CD4001AE COS/MOS

1975

AUTO-TURN-OFF BURGLAR ALARM

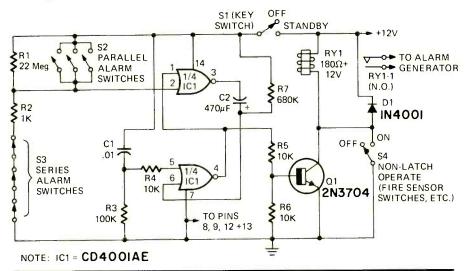

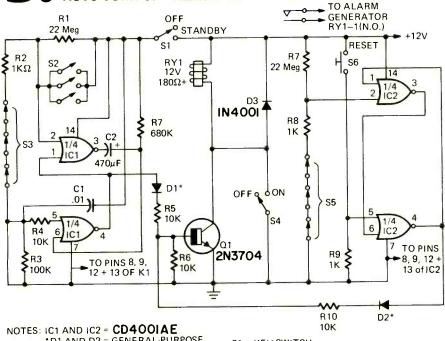AUTO-TURN-OFF ALARM WITH "PANIC" FACILITY



*D1 AND D2 = GENERAL-PURPOSE SILICON DIODES

S1 = KEY SWITCH

S2 = N.O. ALARM SWITCHES, IN PARALLEL S3 = N.C. ALARM SWITCHES, IN SERIES

S4 = N.O. FIRE-SENSOR SWITCHES

'PANIC' BUTTONS, IN SERIES

S6 = N.O. 'RESET' BUTTON FOR PANIC ALARM

package. The four available gates can readily be interconnected to act in a variety of gate, logic, time delay, and multivibrator modes, and can be used to give a variety of useful alarm facilities.

The Project 2 circuit has no significant disadvantages, and forms the basis of all the practical alarm projects described in the remaining parts of this article.

Practical COS/MOS alarm circuits

A practical alarm system may be of

either the self-latching type, which turns on as soon as it is activated and then remains on indefinitely, or it may be of the auto-turn-off type, which turns on as soon as it is activated but then turns off again automatically after a pre-set period. COS/MOS alarm systems of both these types are shown in Projects 3 and 4.


The self-latching operation of the Project 3 circuit is obtained by wiring two of the 2-input NOR gates of a CD4001AE IC so that they act as a simple bistable multivibrator. The action of this bistable is such that its output (taken from pin 4) goes low and self-latches when a positive voltage or pulse is applied to pin 5, and its output goes high and self-latches when a positive voltage or pulse is applied to pin 2. Power is applied to the bistable and to the alarm sensor switches (S2 and S3) via key-operated switch S1.

Assume, then, that alarm sensor S2 is open and \$3 is closed. Wher keyswitch S1 is first set to the STANDBY position, pin 2 is held low by the voltage divider R1 and R2, and a brief positive voltage pulse is fed to pin 5 from the supply line via C1 and R3-R4. Consequently, the output of the bistable automatically goes lcw as soon as S1 is closed. Under this condition, zero base drive is applied to transistor Q1, so Q1 is cut-off, the relay is de-energized and the alarm generator is off. The circuit draws a typical current of about 1-µA in this standby mode. Half of this current flows through the supply lines via R1 and R2, and the other half flows via the leakage resistance of transistor Q1.

The alarm can be activated by opening any one of series-connected sensor switches S3, or by closing any one of parallel-connected sensor switches S2. Under this condition, pin 2 of the bistable goes close to the positive supply voltage and the bistable changes mode and its output locks into the high state and switches the alarm generator on via transistor Q1 and the relay. The alarm then stays on indefinitely, and can be turned off only by opening key switch S1.

The auto-turn-off circuit of Project 4 is similar to that of Project 3, except that in this case the two gates of the IC are connected as a simple monostable multivibrator. The action of this monostable is such that its output goes to the low state when a positive voltage or pulse is applied to pin 5, but goes high for a pre-set period when a positive-going voltage transition is applied to pin 2. The value of this pre-set period is determined by the time constant of R7 and C2, and equals approximately four minutes (0.5 s. per μF of C2) with the C2 value shown. At the end of this period, the output of the monostable automatically switches back to the low state. Note that the monostable can be triggered only by a positive-going transition voltage applied to pin 2, and its action is not influenced by constant high or low voltages that may be applied to this pin.

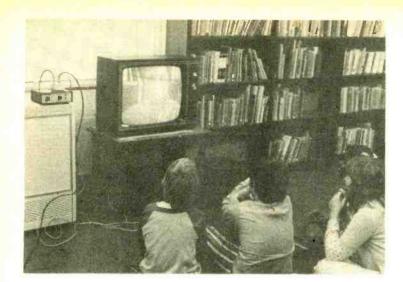Thus, the output of the monostable automatically goes low as soor as key switch S1 is set to the STANDEY posi-(continued on page 88)



Add GGTV to MATV

Adding closed circuit television to an MATV system is not difficult. Here's how to do it.

> by JAMES E. KLUGE TECHNICAL EDITOR WINEGARD COMPANY

IT'S EASY TO ALLOW FOR FUTURE EXpansion of, say, an apartment or condominium complex from 500 to 1,000 units. Judicious over-specification in the design of its MATV system can take care of most future expansion requirements. But the MATV designer who must plan a system capable of many more functions than mere distribution of off-the-air signals has a problem. Fortunately, he also has help —if he knows where to look.

Several manufacturing companies have taken a penetrating look at the potentials of MATV and CATV systems and have provided components to take advantage of those potentials. These components accept video and audio signals from almost any source, such as a TV camera, videotape or film chain, FM tuner, tape or record player and convert this input into a complete television signal. To accomplish this, the minimum components are an audio-video modulator and a sub-channel converter. A switcher can be added if multiple inputs are to be accepted.

Signal path

Let's follow a hypothetical signal from its origin through the system until it shows up on the TV screen. Winegard Company components are used for convenience, although others are available.

A low-cost TV camera can monitor, say, the swimming pool and adjacent area. If sound is desired, any standard microphone may be used. These video and audio signals are input to a Model IV-505 Audio-Video Modulator which combines them to produce a complete 6-MHz sub-channel television signal. This sub-channel lies in the range between 18 and 48 MHz to avoid interference with standard frequencies on the trunkline.

The IV-505 introduces this sub-

channel signal into the trunkline system via an institutional-type wall tap. When it reaches the head-end, the subchannel signal is picked off by a Model SVC-601 Converter/Strip Amplifier which converts it to the standard frequency of an unused vhf channel and reintroduces the signal into the trunkline system for distribution.

So, to check on whether little Susie Smith is at the pool, all her mother has to do is flip the TV tuner to, say, Channel 10.

There are two basic ways to handle multiple video inputs. the fiirst way is to use a separate set of components (IV-505, SVC-601) for each camera and microphone. This gives separate sub-channel conversion for separate vhf channel display. This is more expensive, both in terms of money spent on components and use of available vhf channels, but it does allow simultaneous coverage of different areas, such as pool and tennis courts.

Programming can be originated at any point within such a multiple dwelling complex, just as long as there is an institutional-type tap nearby. Obviously, such a set-up has dramatic potential for two-way communication within CATV systems, too.

The second way would be to use a pair of switchers (VS-401 Video Selector) for sequential coverage of up to four areas in a single sub-channel for single vhf channel display. Of course, if tenants can tolerate pictures without "live" sound, a single VS-401 could provide for sequential coverage of up to four areas, and background music could be fed directly into the IV-505 from another source such as a tape deck.

The beauty of the whole concept is that no additional trunkline is needed. The IV-505 feeds audio or video inputs right into the existing trunkline. So what was previously merely an MATV distribution system becomes a

closed circuit TV system on selected vhf channels.

Is it worth it

Why would anyone want to turn an existing MATV system into an inhouse closed circuit network? There are three sets of pressures on the MATV industry today. All three come from outside the industry, and they are just now beginning to be felt.


One pressure comes from the socalled "communications explosion," which is far from being over. Developments in the late 60's were only the initial shock wave, and the main blast is yet to come. During the last decade, the general public's relationship with the rest of the world has been drastically altered in unforeseeable ways. As a result, the demand for communication seems nearly insatiable. The more information we get, the more we want.

Another pressure is the growing acceptance of multiple unit housing, the very thing that has made the MATV industry as big as it is today. Vast numbers of Americans have suddenly realized that they can achieve the lifestyle they want for a lot less money than they figured. This relaization has sparked a widespread upheaval in housing patterns, as the construction industry is well aware.

There was a time when you had to have millions (and live near the country club) to enjoy luxuries like private swimming pools, tennis courts, golf courses and recreational areas, all on your grounds. Throw in garage parking, social centers, barber and beauty shops, plus a private security force to watch over all these, and it sounds like some millionaire's estate. Yet these conveniences, once the exclusive property of the very rich, today are enjoyed by a large number of middle-class Americans.

Promoters of these multiple-unit



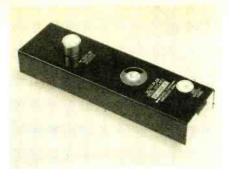

WINEGARD'S MODEL VS-401 video selector is designed to switch one of four video inputs to a single output.



WINEGARD'S MODEL SVC-601 converter strip amplifier mounts directly on the Ultra-Plex power panels.


housing complexes have offered an extravagant variety of inducements to prospective renters. What more can they offer in order to fill their apartments and keep them filled?

An obvious answer is the extended use of existing MATV systems for their tenants convenience. A couple of years ago, this might not have been practical, but a third development has made it economically feasible.

That third development is the cost of video cameras, which keeps edging lower and lower. Only a few years ago, you couldn't touch a decent TV camera for under a thousand dollars. Today, a camera with the same capabilities can be had for around \$100. This trend makes it practical for MATV system owners to provide their tenants with a wide variety of services through their TV receivers.

These services can include the monitoring of critical areas, such as entrances, swimming pool, restaurants and shops; entertainment, including replay of earlier programming at a more convenient time, as well as tapes on every conceivable subject drawn from extensive libraries developed for the purpose; and capsule information about the environment that the apartment dweller must cope with. Although it won't supplant regular news shows, such capsule information would contain such items as the weather, stock market news, traffic conditions and headline news stories, all recycled at a rapid rate.

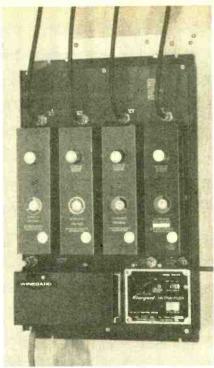This amounts to "in-house" origination, and it implies that the system



WINEGARD'S MODEL DSX-415 Ultra-Plex deluxe 4-strip power panel supplies power for the Ultra-Plex plug-in modules.

should have the capability for distributing the desired signals on channels not occupied by standard broadcast.

The equipment

Since the locally introduced signal has to "swim upstream" to get to the head end for distribution, it must not interfere with off-the-air signals coming "downstream." That's why the IV-505 translates the signal it receives from cameras, VTR's or audio equipment to one of three sub-channels between 18 and 48 MHz before introducing it into the trunkline.

Subchannel A covers 42 to 48 MHz and will convert to any vhf channel except 4 and 6. Subchannel C covers 30 to 36 MHz and converts to any vhf channel except 3, 4, 12 and 13. Subchannel E covers 18 to 23 MHz and converts to any vhf channel except 2, 5, 6, 10, 11, 12 and 13. None of these sub-channels will cause interference in the vhf range, particularly at the modulator's output of 58 dBmV on the +12 Vdc level.

The SVC-601 converter/strip amplifier that accepts the modulator's output and up-converts it to one of these vhf channel frequencies plugs right into the Ultra-Plex power panel at the head end. Once the sub-channel and vhf channel have been specified, the only further adjustment is in the age threshold control. It allows output levels to be set between 46 and 57 dBmV, to bring the output into alignment with other vhf channels in the distribution system.

The simple addition of a video selec-

tor (Model VS-401) makes available any one of four video inputs to the modulator, achieving great programming flexibility.

So, even though an Ultra-Plex MATV system may have been designed originally only for top-quality off-the-air signal distribution. It can be quickly expanded to add closed-circuit capabilities with these few modular components.

This kind of product isn't exclusive with Winegard, of course. Severa other manufacturers have similar components in their lines. What sets Winegard's apart is the way it can be integrated into the Ultra-Plex modular system inexpensively and at any future time.

At the time that Winegard introduced their Ultra-Plex line, the plug-in modules such as band separators and strip amplifiers seemed like the ogical way for the designer and instaler to get maximum results with minimum effort. It is generally recognized that it is better to separate charmels or bands and to process the signals separately before recombining them for distribution via the coax system. What Ultra-Plex did was to turn this expensive design approach into an Boonomical one, given the high cost of time and materials. And it opened the door for using every channel in the vhf range, with less chance of cross-modulation and more control over the signal level delivered to the individual receiver.

Each IV-505 modulator accepts any standard video output from cameras or video tape recorders, and audio from most dynamic microphones, AM-FM tuners, tape recorders and record players. Its output is crystal controlled (.005%) on one of three factory tuned subchannel frequencies. The choice of whf channel for the output determines which of the subchannels in the 18 to 48-MHz range must be used. Controls include an audio mode selector, video level control (75 to 100% modulation) and audio level control.

The SVC-601 converter/strip amplifier converts the modulator's output to a specified vhf channel frequency. Its age system provides constart output level of 0.7 volt (57 dBmV) with input level variance up to 14 dF. This output level is adjustable between 46 and 57 dBmV. It also accepts a plugin 15 dB booster for cases where high losses are incurred in returning subchannel signals to the head end

The converter/strip amplifier plugs in directly to the DSX-250 or DSX-415 Ultra-Plex power panels. The audiovideo modulator takes uhf type PL-259 video input connectors, Amphenol 70 Series audio input connectors and 75-ohm F type output connectors. R-E

Audio Signals You

Here's an audio problem that you may causing it. The problem is called audio picked-up, rectified and amplified by audio

by LEN FELDMAN

CONTRIBUTING HIGH-FIDELITY EDITOR

RECENTLY, A FRIEND OF MINE ASKED ME to appear on his weekly radio show in New York to discuss audio in general and events at the recently held New York Hi-Fi Show in particular. Since the show is taped in advance (as most talk shows these days are), I suggested that we do the taping at my laboratory and that my friend simply bring along two of his favorite microphones, since I had the necessary tape recording equipment with which to make a Dolbyized master tape of the interview. We had followed this practice on many previous occasions and were so confident of the results that, satisfied with the content of the interview, we never even bothered to play back the tape before my radio host left for his own studio to incorporate the interview into his hour-long musical show.

It was only after I heard the show on the air that I learned that my friend had to painstakingly re-do his "track", carefully fitting in and synchronizing his questions with my previously recorded answers. The extra work had taken him several hours and, much to his credit, even I could not detect the fact that his questions and my answers had been recorded days apart. Such are the miracles of modern tape recording. More recently, he gave me the original master tape and when I listened to it, I understood why he had to "fake" the session in that way. On his voice track (and ONLY on his voice track). there appeared almost continuously the garbled voice of my next door neighbor who is a dedicated radio amateur operator. While completely unintelligible, the raucous interference was no more than about 10-dB below the desired program material we had recorded. The youngster next door invited me to check out his equipment. Doing so revealed no illegal radiations and, in fact, his little station was a model of good radio amateur practice. All of which leads me to the subject called "audio rectification"-one of the most troublesome forms of interference common to a great many hi-fi audio systems. It manifests itself in the form of received radio signals when listening to your phonograph and has also been known to occur when using hearing aids, public address sound systems and even electronic organs. At a recent meeting of the audio sub-committee of the EIA (Electronic Industries Association), a proposed draft of a consumer products engineering bulletin was circulated which deals with this problem.

As the bulletin points out, because of the proliferation in the past few years of rf transmitting equipment (AM, FM, TV, radar, radio amateur, Citizens band, etc.), cases of audio rectification are becoming too frequent, and the cost of correction too high, to ignore this interference in the original design of audio equipment.

As defined by the EIA bulletin, audio rectification is rf energy from any sort of transmitter being received by an element in an audio amplifier. This rf energy is then rectified by the audio amplifier in any non-linear active element such as a vacuum tube, transistor or integrated circuit. The rectified signal is then amplified by the remainder of the audio amplifying circuits and appears as an unwanted signal at the speaker's output terminals.

FCC recognition of the problem

The Federal Communications Commission has been aware of this growing problem for some time, but so long as the source of rf energy (be it a transmitter or any other device which emits rf) is operating "within specs", the solution must be sought by the owners of the audio equipment. Some years ago, the FCC issued a brief bulletin which included two schematics showing possible additions that might be made to audio circuits to cut-down the audio rectification problem. The first

of these diagrams is reproduced in Fig. 1 and applies primarily to tube equipment.

This early bulletin suggests such modifications as bypassing the speaker output terminals to chassis ground with 0.01 µF disc capacitors, lowering of the input resistance (R1) to the first tube stage and bypassing that resistor with a small disc capacitor (about 500 pF), adding a series 75K resistor (R2) in series with the grid to form a sort of simple low-pass filter network. Additional suggestions in this bulletin applying to ac-dc equipment include the addition of a 0.001-µF disc capacitor from the heater line to the chassis and bypassing both sides of the 120volt ac power line with 0.01-μF disc capacitors.

Suggestions for transistorized audio equipment plagued with audio rectification problems are contained in the diagrams of Figs. 2-a and 2-b from the FCC bulletin. A 250-pF capacitor or a low pass filter "pi" section consisting of two 250-pF capacitors and a series rf choke (I'd suggest about 5 to 7 µH if the interference frequency is between 30 and 110-MHz, and about 1.5 µH if the frequency is between 80 and 200-MHz—Editor) is inserted in the base circuit of the first transistor stage. In the case of stereo equipment, the modification would have to be made in each channel.

Suggestions from the EIA

The Electronic Industries Association bulletin delves more deeply into the subject of audio rectification and methods used to alleviate the problem. As they point out, circuitry unprotected

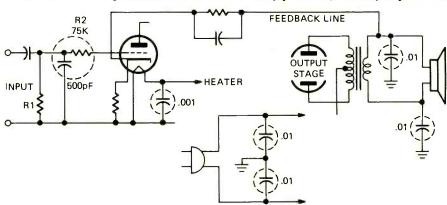


FIG. 1—FCC SUGGESTIONS of additional components to be added to tube amplifiers (circled components) to reduce interference from audio rectification of rf signals.

This timer produces an audible tick every second with the tenth tick emphasized. Construction A tick timer is a device which prois simple and it has many applications in photography

by FRANK H. TOOKER

NO MATTER WHAT OTHER TYPES OF timers a photography enthusiast may have in his darkroom, if he does any exposure manipulation of enlargements (dodging or printing-in), he needs a tick timer to get his best results.

duces an audible tick or click at precisely one-second intervals. It enables a darkroom worker to time the exposure intervals accurately without taking his eyes from what he is doing, thereby avoiding "spill-over" of the projected image into areas where it is undesired.

Do you like to go out on the streets with your camera and take pictures at night, as many of us do occasionally? If so, you know that night exposures can be a minute or more. Timing the exposures with a wrist watch and a small flashlight, while manipulating the camera shutter and at the same time keeping a wary eye open for the chance of an oncoming car with its bright headlights, can be almost too much at times. Take this accented tick timer along and let it do the exposure timing for you. It's battery operated and completely portable. Without fiddling with the wristwatch and flashlight to occupy and often frustrate you, you'll not only have a more enjoyable time, you'll probably end up with a batch of better pictures as well!

What's an accented tick timer?

The difficulty with the common tick

timer is identical to that of a dripping faucet — it's monotonus. Especially when you're working with a tricky exposure which requires concentration, it's easy to lose count, or to be in doubt as to whether the count is still accurate or not. And, of course, the longer the interval, the more likely it is that something like this will occur.

The timer described in the present article has been designed especially to overcome this difficulty. It provides accented ticks at regularly repeated intervals. Each 10th tick is made louder. So, if you've missed a tick, or think you have, your count can be corrected or assured at the conclusion of the 10-second interval. Furthermore, with an accented tick timer operating in the darkroom (if the count runs longer than 10 seconds (the usual case), it isn't necessary to count individual ticks until near the end of the count.

Suppose a particular exposure requires 35 seconds, for example. Keeping in mind that the louder ticks occur at 10-second intervals and the quieter ones at 1-second intervals, you simply begin the count and the exposure at the first louder tick. Count off the next 3 louder ticks (for the 30 seconds), then the next 5 quieter ticks for a total of 35 seconds.

How it works

The ticks of the electroric tick timer are current pulses made audible by a speaker. The unijunction transistor (UJT) is an excellent pulse generator. In fact, it's especially useful in this application because it synchronizes easily and because a UJT pulse-generator circuit is quite insensitive to variations in the powersupply potential. The accented tick timer operates from a 9-volt pattery, but even when the battery potential

PARTS LIST

All resistors 1/2 -watt 10% unless noted

R1-100,000 ohms, linear taper potentiometer

R2, R7-33,000 ohms

R3-100 ohms

R4, R8-300 ohms trimmer, linear taper

R5, R9-2,200 ohms

R6-100,000 ohms trimmer, linear taper

R10-220 ohms

C1, C4—10-μF, 12-volt electrolytic

C2-100-μF, 12-volt electrolytic

C3-0022-µF, 100-voit Mylar

Q1, Q3—2N2646 Unijunction Q2, Q4—2N697 silicon

B1-9-volt battery (see text)

S1—spst slide switch

ware and solder.

SPKR — 31/2-inch square intercom type speaker, 45-ohm V.C. (Quam 3AO7Z45) MISC-5 in. × 4 in. × 3 in. utility cabinet, screen wire for speaker grill, battery holder and connector, hard-


R6 100K 10/12V SPKR 100K CALIBRATE R10 ≸ ON-OFF .0022 220Ω 33K R2 Q2 33K 2N697 C 2N2646 2N697 2N2646 R3 100/12V R5 R9 **₹** R8 10/12V 300Ω 2N2646

FIG. 1—COMPLETE SCHEMATIC diagram. Circuit delivers a 1-Hz signal to the speaker with every tenth pulse accentuated.

Never Bargained For

have run across but weren't sure what was rectification. Its caused by rf signals being circuits. Here's an article on the causes and possible solutions.

from television and radio station interference is the main source of audio rectification. Interference can enter the affected unit by some portion of the equipment acting as an antenna and some other component acting as a detector. The form of interference may

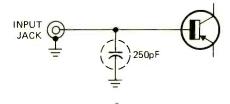

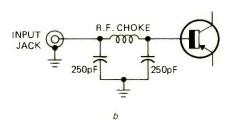


FIG. 2—SIMPLE BYPASS SCHEMES suggested by FCC for transistorized audio equipment.

range in frequency from as low as 50 kHz to as high as 1 GHz and may even include noise pulses from electric thermostats.

Determining the interference frequency

If interference is identified as audible voice or music over the speaker system. usually the offending AM station can be identified and its frequency thereby determined. If the interference is garbled and unintelligible (as was the case in our recording session) chances are it comes from a single-sideband (SSB) transmission—usually a local amateur radio operator. The frequency will usually be 3 MHz or higher. In the case of interference from FM transmissions, no actual sound will be heard but you may notice a decrease in volume of the desired program (records, tapes, etc.) whenever the interference takes place. Most FM transmissions (both amateur and commercial) are at a frequency above 30 MHz. Interference from a TV transmission is identifiable as a buzzing sound which changes its characteristics with time.

Isolating the problem

Most audio rectification occurs in

the audio detector or preamplifier section of a stereo component system or tape deck.

As a good first test, turn the master volume control down to its minimum position. If the interference is still present, the interference is occurring after the volume control, if not, it is being picked up ahead of the volume control.

RF interference ahead of the volume control

Some problem areas to consider are poor grounds, poor solder joints, electrolytic capacitors, long unshielded cables and the ac power lines themselves. Electrolytic capacitors that have been in use for several years may develop a high internal resistance. Paralleling a new capacitor across the suspected one is a good way to check this out. When multiple ground connections cannot be avoided in a system hook-up, interference due to resonance of loops formed by the shielded cables can be minimized by reducing contact resistance, shifting the position of the contact, or even changing lead lengths. Suspicious solder joints can often be the cause of audio rectification and should be carefully resoldered. Unshielded cables between components of a system or to extension speaker systems often act as excellent antennas for bringing the unwanted signal inside the chassis. Try replacing these with shielded cables.

If pickup is via the ac power lines, a line filter may solve the problem. One recommended circuit is shown in Fig. 3. Note that while 0.01-µf capacitors have been shown, these may or may not be safe for use across power lines, in terms of leakage current. Only components certified as being safe for use in power line wiring should be employed.

RF interference after the volume control

When the volume control is in its minimum position and the interference is still heard, some form of rf filter will be required in the audio amplifier itself. Shown in Fig. 4 is an example of the type of filter circuitry that has been proven effective in transistor audio circuitry. Values for the L, C and R components have been deliberately omitted because circuitry varies from product to product. The important

thing to remember is that these values should be selected so that there is no significant change in gain or frequency response. A small ferrite bead can often be substituted for L1 in the circuit of Fig. 4. Such beads, available in different inductance equivalent values, are simply threaded onto the bare wire leads of a component and act as finite inductances in the circuit. In the case

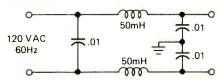


FIG. 3—POWERLINE RF FILTERING circuit suggested in new EIA bulletin on audio rectification.

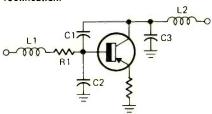


FIG. 4—SUGGESTED RF FILTERING CIR-CUITRY for use at input stage of audio equipment. Capacitors C1, C2, C3, series chokes L1 and L2 and series resistor R1 can be added separately or in combination.

of the diagram shown, the bead would be placed physically between the junction of C1-C2 and the base of the transistor shown.

All capacitors used in any of the circuits shown should be of the ceramic type, as these are better rf bypassing devices than paper types. Leads should be kept as short as possible and all ground connections should be soldered as close to the associated transistor stage as possible. It has been found that in areas of high rf energy, the inductor approach (used in a series connection) is more effective in blocking the transmission of such rf energy than is the shunt capacitor or series resistor approach.

Since interference may enter an amplifier via the output (especially in hifi amplifiers which invariably include a major feedback loop as part of the power amplifier design), speaker leads which are resonant to a particular frequency tend to aggravate the situation. For example, an 8-foot length of speaker cable will be resonant to incoming rf (continued on page 77)

SHORTER SEQUENCE LENGTHS					
STAGES	LENGTH	STAGES	LENGTH		
2	3	10	1023		
3	7	11	2047		
4	15	12	4095		
5	31	13	8191		
6	63	14	16,383		
7	127	15	32,767		
8	255	16	65,535		
9	511	17	131,071		

TABLE I-RANDOM SEQUENCE LENGTHS

					_	
				STATES FOR relength = 63)	1-6	
000000	(0)	011100	(28)	000111	(7)	001000 (8)
100000	(32)	101110	(46)	100011	(35)	100100 (36)
110000	(48)	010111	(23)	110001	(49)	110010 (50)
111000	(56)	101011	(43)	011000	(24)	011001 (25)
111100	(60):	110101	(53)	101100	(44)	001100 (12)
111110	(62)	011010	(26)	110110	(54)	100110 (38)
011111	(31)	001101	(13)	011011	(27)	010011 (19)
101111	(47)	000110	(6)	101101	(45)	101001 (41)
110111	(55)	000011	(3)	010110	(22)	010100 (20)
111011	(59)	100001	(33)	001011	(11)	101010 (42)
111101	(61)	010000	(16)	100101	(37)	010101 (21)
011110	(30)	101000	(40)	010010	(18)	001010 (10)
001111	(15)	110100	(52)	001001	(9)	000101 (5)
100111	(39)	111010	(58)	000100	(4)	000010 (2)
110011	(51)	011101	(29)	100010	(34)	000001 (1)
111001	(57)	001110	(14)	010001	(17)	(000000) ((0))

TABLE II—THE SEQUENTIAL STATES for the circuit n=6 in Fig. 1. The first (input) register stage is on the left, the last (output) on the right. Numbers in parentheses are the decimal equivalents of the binary words.

STAGES	SEQUENCE LENGTH	FEED EXCLUSIVE-NOR GATE FROM OUTPUTS		
17	131,071	14 and 17		
18	262,143	11 and 18		
20	1,048,575	17 and 20		
21	2,097,151	19 and 21		
22	4,194,303	21 and 22		
23	8,388,607	18 and 23		
24	16,766,977	19 and 24		
25	33,554,431	22 and 25		
26	67,074,001	21 and 26		
27	133,693,177	19 and 27		
28	268,435,455	25 and 28		
29	536,870,911	27 and 29		
30	1,073,215,489	23 and 30		
31	2,147,483,647	28 and 31		

TABLE III—HOW TO CONNECT FOR SEQUENCES UP TO 31

in a proper circuit to generate a *new* one or zero in unique response to the state the register is *now* in.

The logic for maximal length takes nothing but exclusive NOR gates and turns out to be unique. Any logical combination of outputs to drive the input will give us some sequence length. The problem with the majority of connections is that they only generate a very short (or maybe only a 1-bit!) sequence, and that the states going through the register do not have the random-looking properties that we need.

What we have to do is find the magic combination of logic and feedback that will generate the maximal length sequence for a given stage length. To do this takes a bunch of high-level math, but it has to be done only once. Circuits that will do that are shown in Fig. 1 for register lengths of 2 through 16.

Some more details

Let's actually build a real 63-bit sequence circuit. It's shown in Fig. 2. We use the first six stages of a 74164, one-half of a 7486 quad EXCLUSIVE-OR gate with the two sections cascaded to form an EXCLUSIVE-NOR, the usual 5-volt supply and decoupling, and a variable-speed clock made up from a MC1555 or 555 timer.

Every time the circuit is clocked, it advances one count and generates a pseudo-random sequence of 63 of its 64 possible states. The clock frequency determines how fast the states will change,

while the sequence time will be 1/63rd the clock frequency if you run the circuit continuously. We can use the serial bit stream or we can use the digital words that show up in parallel on the register outputs. Or, as we'll shortly see, these are easy to convert to analog "noise" or discrete, randomly varying analog levels.

The two cascaded EXCLUSIVE-OR circuits form an EXCLUSIVE-NOR or comparator. If both inputs are the same, a "1" is output. If the inputs are different, a "0" is output. Thus our feedback circuit looks at stage 5 and stage 6 to see what they were before the new clock arrives. The output of the EXCLUSIVE-NOR then sets up what stage 1 is to be after clocking, determined by whether the logic levels on stage 5 and 6 are the same or different.

For instance, in the 63-word sequence of Fig. 1 (n=6), if 5 and 6 are both 0's, a "1" gets entered into the first s age on the next clocking. What was in the first stage goes to the second; the second to the third, and so on. If 5 is a 1 and 6 is a 0, a "0" goes to stage 1 on the next clocking. The same thing happens if 5 is a 0 and 6 is a 1. Finally, if 4 and 6 are both 1's, a 1 is sent to the first stage on the next clocking.

In this manner, the entire pseudorandom sequence is built up. To see how beautifully it works, set up a table like that of Table II for some of the shorter sequences of Fig. 1—say the 5-word sequence of n-3.

All 63 states are shown in Table II. As you can see, any short-term group of bits in the middle jumps around in a very nearly random manner: If you count the number of sequential 1's and 0's you get and work up a distribution curve, it turns out to be a rather chunky approximation to a random probability curve. As we add more and more register stages, the curve smooths out, and the more stages, the better the randomness. For any circuit, the maximum number of sequential I's or 0's we can get has to be equal to or less than the register length. Opviously we get far more short bursts cut than long ones. If you go through all the statistical math, you find that you do have very nearly a truly random behavior on a short-term basis, only one that nicely repeats every time we ask it to. In fact, things turn out even better than random noise, since you get the andomness over one sequence length while "true" noise would theoretically take forever to be truly random. Longer sequences behave even better.

Available sequences

There are usually at least four possible maximal length sequences for any stage length. Circuits to get all jour are shown in Fig. 3. If we take the circuit we have and invert the input, we get an inverted sequence in which all he ones are zeros and vice versa. Or, instead of looking at what's going to happen next, we can look to see what already did happen and get a backwards sequence. Finally, we can both look backwards and invert to get a backwards sequence with interchanged ones and zeros. All four circuits have essentially the same random-



As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath Digital GR-2000 Solid State color TV** with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multimeter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-



5" OSCILLOSCOPE

clip coupon if card is missing.

MULTIMETER TRANSCEIVER & POWER SUPPLY tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or

SOLID-STATE 2-METER FM

NO OBLIGATION. NO SALESMAN WILL CALL

DIGITAL

APPROVED FOR VETERAN TRAINING

Get facts on new 2-year extension

TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905 Resident and Home-Study Schools 4000 So. Figueroa St., Los Angeles, Calif. 90037

4000 South Figueroa St., Los Angele Please send FREE Color Catalog an NO OBLIGATION. NO SALESMAN V	d Sample Lesson.
Color TV Servicing B & W TV and Radio Servicing Electronic Communications FCC License Course	 □ Electronics Technology □ Computer Electronics □ Basic Electronics □ Audio Electronics Servicing
NAME	AGE
ADDRESS	APT #
CITY	STATE
Please fill in Zip Code for fast servi	ce
 Check if interested in G.I. B 	Bill information.

SOLID-STATE

POCKET RADIO

SIGNAL GENERATOR ness properties. Which one you use depends on how you like to start the circuit and what output polarity you want. In electronic music, it's handy to use all four, for you can get a sequence, the sequence played backwards, or the sequence played on an inverted scale or on an inverted scale and backwards.

The disallowed state

One little detail we have to watch for is the unused state. If you ever get into the 111111 state with the normal circuit, it will stay there forever! The backwards version will also stick in 111111. while either inverted (complementary) sequence sticks in 000000. So, we must never allow this state to occur. It's easy to reset or preset our register or otherwise make sure we also start our sequence on a known valid portion of the sequence. By the way, this is true of almost all counters and sequential circuits in general. You have to investigate all the disallowed or "don't care" states to make sure none of them are self-perpetuating.

One other little detail is that we obviously must get an additional 1 or 0 (or one less zero or one) since our code

is always an odd number of bits long. This missing 1 or 0 will tend to skew the random distribution slightly and will tend to shift the bias on an analog conversion scheme slightly. This is easily avoided by compensating bias resistors, and the longer sequences have almost negligible skew and randomness bias.

Converting to analog

Figure 4 shows two different ways to convert the digits to numbers. In 4-a, we use an integrator or low-pass filter on the serial bit stream, and the output of the integrator is an analog voltage that varies in a random manner. The short-term output is noise that behaves just like white noise up to the filter's cutoff frequency or at least up to a good fraction of it. A cutoff frequency of 1/20 the clock frequency is recommended, particularly for longer sequences. A different possibility is shown in Fig. 4-b.

Here we directly D/A convert the parallel digital words to an analog signal. With this circuit, you get analog levels that jump to some new random value, once every clock cycle.

To find the time the sequence repeats,

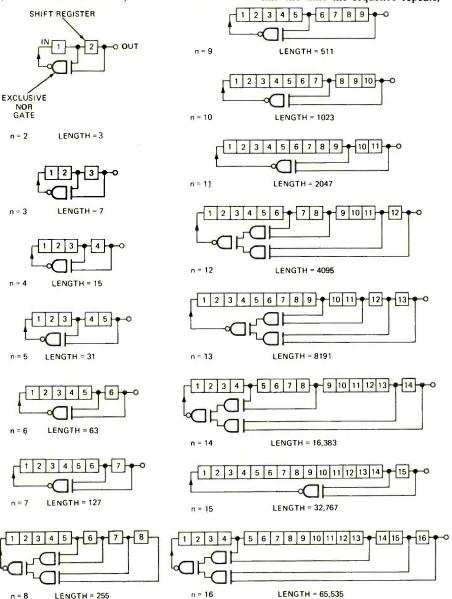


FIG. 1—PSEUDO-RANDOM CIRCUITS that produce sequences from 3 to 65,535 words.

just divide the clock frequency by the sequence, the repeat time will be 100,using a 100-kHz clock and a length 16 sequence, the repeat time will be 100,-000/65,535 or about 1.5 times per second. If you are using the 63-note sequence for electronic music at 3 notes per second, it repeats once every 21 seconds. A 127-note sequence would be good for 42 seconds, and so on. As an extreme example, if you used a 48-stage MECL shift register and a 100-MHz clock, it would take around 3 million seconds or over half a year to repeat. At lower clock frequencies, it would take decades or even centuries!

The serial conversion circuit of Fig. 4-a works best when the clock is at least 20 times the filter's cutoff frequency as determined by the capacitor values. Thus, for high-quality audio testing and requirements of this type, you use as long a register length and as fast a clock as you can.

Applications

Let's briefy turn to the things you can do with a pseudo-random sequence generator.

For audio testing and communications, you normally use a very fast clock and a sequence that repeats perhaps 30 times a second, so you can get a stable oscilloscope display. The filtering then gives you random signal variations that duplicate the effect of random combinations of voice or communications data or signal levels. Commercial instruments are available (Hewlett-Packard, among others) that do just this. The net result of the testing is that you simulate the real operating conditions in a realistic man-

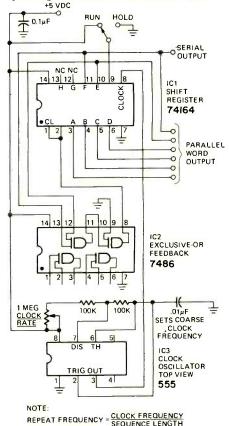


FIG. 2—THIS LENGTH-63 CIRCUIT uses 6 stages (n=6).



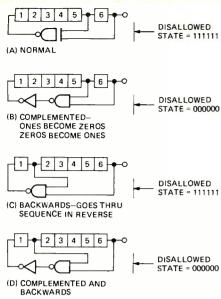


FIG. 3 - FOUR POSSIBLE SEQUENCES for any n can be made by rearranging the circuit.

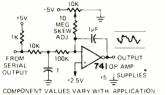

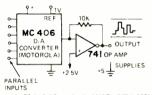COMPONENT VALUES VARY WITH APPLICATION
(A) USING SERIAL OUTPUT TO GET ANALOG PSEUDO NOISE



VALUES AND CONNECTIONS VARY WITH APPLICATION
(B) USING PARALLEL OUTPUTS TO GET RANDOM OUTPUT LEVELS

FIG. 4-ANALOG OUTPUT CIRCUITS.

ner but also in a way that lets you see the results as a stable display.

Electronic music uses are relatively obvious. By interchanging the outputs in a programmable manner, you can use one basic sequence generator to build a fantastic number of tunes and can obtain them frontwards, backwards, normal scale or inverted. Some of these combinations will be dull and others will be simply phase-shifted replicas of others, but the number of unique and interesting variations remaining are still a bunch. Figure 5 shows one possible electronic music composer. By adding random rhythm and pause combinations, you can end up with an essentially infinite number of variations. You can also use pseudorandom sequences to generate timbre waveforms for electronic music.

Secure computer communications encode the data to be transmitted onto a pseudo-random sequence that is locked to a replica at the far end. Usually, the sequence length is very long, days, months, even years. Cryptography and other security schemes are other applications of this type. As with any code, regardless of its complexity, it can be broken. The object of any code game is to make cracking the code so complex,

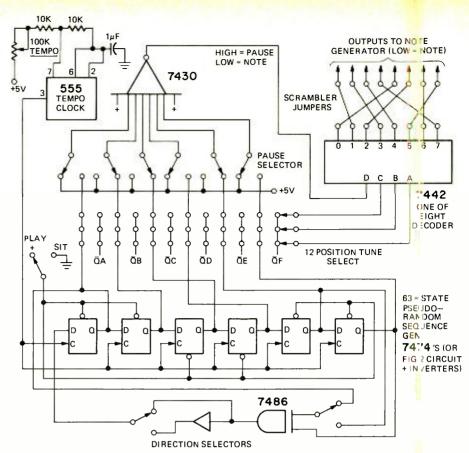


FIG. 5-POSSIBLE MUSIC COMPOSER.

make it take so long, or make it so expensive that the cost of cracking exceeds or at least severely diminishes the value of the information to be gained. So, as with all codes, the pseudo-random technique is a reasonably effective deterrent, not a fail-safe and foolproof route to security.

To encode or decode data, two EX-CLUSIVE-NOR gates are used, one at each end of our secure line. Remember that the output of an EXCLUSIVE-NOR is the same if the inputs are identical and different if they differ. So, if our pseudorandom generator happens to be in a "1" state, input data 1's stay ones and 0's stay zeros, e.g. they are transmitted with-out "error." On the other hand, if our pseudo-random generator happens to be in a "0" state, the 0's become 1's and 1's become 0's; we say the data is complemented. Since the line now consists of a random mixture of good and bad data, it appears to be garbage to anyone monitoring in the middle. At the other end, we simply add a new pseudo-random generator identical in length and sequence to the original; once again, it inverts when zero and passes when one; and all the data straightens back out again. Figure 6 shows the circuit.

Autocorrelation is a very complex subject, but it dramatically illustrates the power of pseudo-random sequences. Suppose we have a sequence length of 63 and that a 1 is +1 volt and 0 is -1 volt. If we multiply the code by itself on a bit-by-bit basis, we would get +63 volts out. On the other hand, if we multiply the code by a delayed replica of itself or a random string of ones and zeros, we will probably get a very low value,

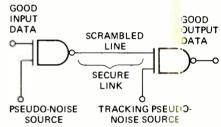


FIG. 6-A PSEUDO-RANDOM CODEFI or data scrambler for privacy or cryptography.

maybe +1 or -1 out. Thus when the code matches itself, you get a very strong output signal; otherwise you get very little. Only the Barker codes can give you perfect + and -1 sidelobe levels; the mismatch and noise level produced in a pseudo-random code is higher, but still has a very useful sidelobe level.

This tremendous build-up of signal buys you a signal-to-noise imprevement and the ability to extract a signal deeply buried in uncontrollable noise.

Longer sequences


The schematics for sequences longer than 16 get rather cumbersome to draw, so they are shown in table form in Table III. The lengths are shown up to 31 stages, which is a sequence length of 2,147,483,647. That should te long enough for just about anything. Note that this sequence can be built up with only four of the 74164 shift registers. Sequence 19 is omitted because it takes more than one exclusive OR sate to build it. There are likewise other possible maximally long or nearly maximal sequences for lengths 17, 21, 22, 23, 25, 27, 28, 29 and 31, but one should be enough for each length. R-E

49

INAKIT

4-Channel Storage
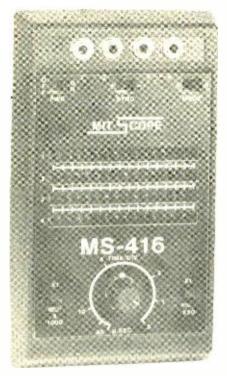
> Using LED indicators, this has full storage triggering. The LED matrix with 16



THE MS-416 has a time-base range of .5 μs to 200 ms that will cover most digital circuit needs.

WITH THE RAPID INCREASE IN INTEGRATED circuit technology, more and more electronic equipment is being designed around digital circuitry. These new circuits are full of complex timing sequences and elusive pulses. Elusive because the pulses occur one-time and one-time only.

There are many three- and four-channel oscilloscopes on the market which can handle complex timing relationships. But they are generally very expensive, cumbersome instruments and are usually found only in very well-equipped labs.


Another instrument sometimes used in testing digital circuitry is the logic probe. Many logic probes have built-in pulse catchers for those one-time pulses. However, they are inadequate for most circuit testing and nearly useless in complex timing situations.

As a result, a new instrument has been developed. It is called the MS-416, and it incorporates the best features of both the oscilloscope and the logic probe.

The MS-416 is an inexpensive, four channel, hand-held, digital logic oriented scope with full memory capability. The time-base range from .5 μ s to 200ms will cover most digital circuit needs. With four channels, extensive timing relationships can be easily observed. Signals are displayed on a 4 \times 16 LED matrix; 4 channels, with 16 LED's per channel.

In addition to the normal mode of operation, the MS-416 can be switched into storage operation at any time during

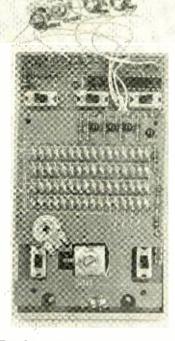The MS-416 is available in kit form for \$127.50, or assembled for \$189.50, from MITS, Inc., 6328 Linn, N.E., P.O. Box 8636, Albuquerque, NM 87108.



INTERIOR VIEW of the MS-416. Calibration of the unit is a simple one setting operation.

testing and will "remember" the information present on all four channels of its display. It will hold this information until it is switched back to normal operation or turned off. The storage mode also serves as an excellent pulse catcher for those elusive one-time pulses. The MS-416 will wait until the pulse occurs and then hold it in its memory as long as it is desired.

Together with positive- or negativeedge triggering, an auto-sweep mode for steady-state logic measurements and a Ni-Cad battery supply, the MS-416 becomes quite a versatile piece of equipment.

Circuit operation

The MS-416 consists basically of eight interconnecting circuits. The block diagram in Fig. 1 shows a power supply, a memory, a clock oscillator, a counter, a decoder, a mode select circuit, a sync circuit and a display.

The complete schematic of the MS-416 is shown in Fig. 2. The power supply will run on 117 Vac with an ac adapter. Using the adapter (a standard 9V unit), the supply is regulated by D1, a 5.1 V Zener diode. C1 provides filtering, and a separate filtering network (R6 and C2) is used for the clock oscillator IC-g. When the power switch S1 is in the OFF position, the adapter is used to charge the Ni-Cads through R1 and R2. To run on Ni-Cads, simply unplug the adapter, which shorts the A and C contacts of the ac jack, and switches the unit on, In battery operation, the supply is essentially unregulated to eliminate unnecessary current drain. It takes approximately 14 hours to charge the batteries, and with a full charge they will power the unit for about 1½ hours of continuous use.

The memory consists of a 64-bit RAM (Random Access Memory), Am31L01 (IC-a). The signal inputs are buffered through IC-b and the inverted signal is fed directly into the four word bit inputs of the RAM. Each word consists of 4 bits, one bit for each channel.

The 4 bit word is selected by the binary outputs of the counter (IC-c) connected to the four address inputs of the RAM. The RAM is addressed simultaneously with the 4×16 decoder (ICf). As the 16 words are addressed one at a time, the signal present at each of the 4 inputs is written into the memory and fed, inverted, to the RAM outputs. The chip-enable input of the RAM is pulsed high at the end of each 16 count, disabling the memory while the counter resets. This will cycle continuously as long as the unit is in the normal operation mode, and the mode select circuit holds the RAM in the Write mode. In the storage mode, the mode select circuit switches the read/write input of the RAM to Read after one full 16 count. The signals present on the RAM inputs will then be continuously displayed as long as the unit is in the store mode.

The clock oscillator uses four inverter gates of IC-g, along with two variable resistors (R4 and R5), and two capacitors (C3 and C4) to produce the variable frequency signal used for the timebase. Switch S4 selects either a 620-pF capacitor (C3) for the X1 range or a $.68\mu f$ capacitor (C4) for the X1000 range as part of the time constant for the oscillator, A 50-ohm trim pot R5 is used for calibration, and a 5K ohm linear taper pot is used to vary the time constant to select the initial sweep rate for the time-base, Switch S5 either sends the clock signal to IC-e in the X1 position or, in the X20 position, sends it through IC-j for a divide by 10 and IC-h for a divide by 2 before sending it to IC-e. Using S4, S5 and R4 you can produce a time-base from $0.5-\mu s$. to 200 ms. The final signal is fed through a NAND

Digital Scope


4-channel digital scope capability and automatic readout is a 4 X 16 LED's per channel.

by JAMES B. VICE

gate and an inverter gate to the counter. The counter is a 7493 4-bit binary counter (IC-c) operated in the ripplethrough configuration (series of flip flops), providing simultaneous divisions of 2, 4, 8 and 16 of the clock frequency on its four outputs. The outputs are fed to both the 4 \times 16 decoder and the RAM address inputs, keeping the two synchronized. The divide by 16 output, pin 11, is also fed to the clock inputs of the flip-flops (IC-d) in the sync and mode select circuits. As the 7493 counts up. the d output goes high on the 9 count and falls after the 16 count. This falling edge is used to toggle the flip-flops.

The decoder is an Am93L11 4-line to 16-line decoder/demultiplexer. As the counter feeds information into the decoder's four binary coded inputs, its outputs 0 through 15 are strobed low sequentially at the rate determined by the clock oscillator frequency. These outputs are fed through transistors to the display. The decoder is disabled at the end of each 16 count by the same signal that resets the counter.

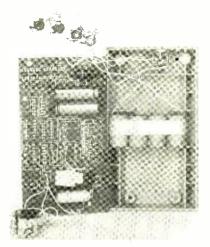The mode select circuit consists of switch S3 and one flip-flop of IC-d. In



INTERIOR VIEW of the MS-416. The main circuit board is swung away to show the underside of the main board and the batteries.

the normal mode of operation, the clear input of the flip-flop is held low by S3 to ground, keeping the flip-flop in the clear state. This prevents the clock input of the flip-flop, which is connected to the D output of the counter, from having any effect while in the normal mode. When S3 is switched to store, the clear input goes high so that when the signal on the counter D output falls after the 16 count, the flip-flop will toggle. The flip-flop is connected so that it latches. and it will stay latched until S3 is returned to the normal position. When the flip-flop latches, the Q output goes high, switching the RAM to the Read mode. Simultaneously, the Q output goes low and is used to block the signals on the input buffer (IC-b) and to block pulses from the sync circuit at pin 10 of IC-e. When S3 is switched back to normal the flip-flop immediately goes back to its clear state.

The sync circuit is both the most complex and the most important circuitry in the unit. It consists of a 9601 retriggerable one-shot (IC-k), four NAND gates of IC-e, two inverter gates of IC-g and one flip-flop of IC-d. The signal for the



INTERIOR VIEW of the MS-416. The display board is swung away to reveal the main printed circuit board.

sync is taken from the output of the channel one buffer (pin 3 IC-b). The sync signal is fed to S2 and one gate of IC-e which is connected as an inverter. The input to the one-shot is taken from S2. In this manner, switch S2 is used to select either the rising edge or alling edge of the input signal for synchronizing the MS-416.

The one-shot has an output pulse duration of approximately 160 ns. The Q output of the one-shot is fed into pin 5 of one NAND gate of IC-e where it is gated together with the Q output of one flip-flop of IC-d.

This gate is used to prevent any one-shot pulses from passing while the counter is counting up. The output of the NAND gate is again fed into one input of another NAND gate where it is gated together with the Q output of the mode select flip-flop. The output of this gate goes through an inverter gate of IC-g and to the clear input of the sync flip-flop. The clock input of the sync flip-flop is connected to the D output of the counter; therefore, when the signal on the counter falls after the 16 count, the flip-flop toggles.

This causes several things to happen at once. The O output of the flip-flop is connected to another NAND gate of IC-e, together with the clock signal, and then through another inverter to the counter. The NAND gate serves to block the clock pulses from reaching the counter while it is being reset. The Q autput of the flip-flop is used to resut the counter, disable the decoder and disable the RAM. It is also used to set conditions at pin 4 of IC-e to allow the next one-shot pulse to pass. When the next one-shot pulse occurs, it will pass through to clear the sync flip-flop, starting the entire sequence over again.

The display consists of 64 RL-50 LED's arranged in a 4 × 16 matrix; along with associated driving circuitry (Q1 through Q20 and resistors R8 through R15). Transistors Q17 to Q20

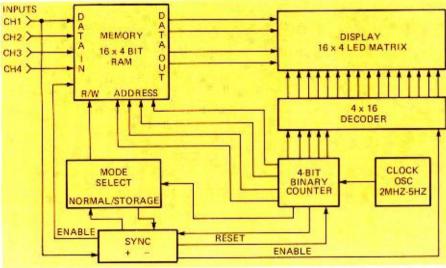


FIG. 1—MS-416 BLOCK DIAGRAM. The trigger circuits are synchronized to the channel-1 signal.

(CS4410's) are switched on and off with the information from the RAM outputs. Transistors Q1 to Q16 (EN2907's) are pulsed low at their bases one at a time by the decoder outputs, providing a path to ground for the LEDs. Each output word from the RAM consists of four bits, each bit corresponds to one channel, and each of the decoder outputs corresponds to one RAM address. The RAM address and the decoder output are changed at whatever rate is predetermined by the clock oscillator frequency. As an example; if the counter is at its 2nd count, the RAM will be at its 2nd address and Q2 will be turned on. If there is a positive signal on the RAM output to Q18 at this time, then LED D23 will light for however long the clock frequency determines.

There is also an auto-sweep circuit for measuring high or low steady-state conditions. Since the sync circuit requires a pulse to function, a steady-state condition has no effect and is never seen. Switch S6 allows the unit to measure these signals by switching the clock oscillator signal into the other A input of the one-shot. This allows the sync to be continuously triggered. When not in auto-sweep operation, S6 holds the input to the one-shot at $V_{\rm cc}$.

How's it's made

The MS-416 is built around two double sided PC boards with plated-through holes. As the unit is quite compact, the builder must be sure that all components are installed as close as possible to the boards and all excess component leads

and IC pins are cut off as short as possible without damaging the connection. The boards are assembled one at a time and then wired together after all the components have been installed on the component side of the boards. (There are five components mounted on the opposite side. These will be mentioned later).

The first step in construction is to install switches S1 to S5 on the main board. These are the only components on the boards that are not installed flat against the boards.

The next step is to install the integrated circuits. Orient them correctly according to the component layout, and be sure to push them down as flat against the board as possible.

At this point it is best to install the

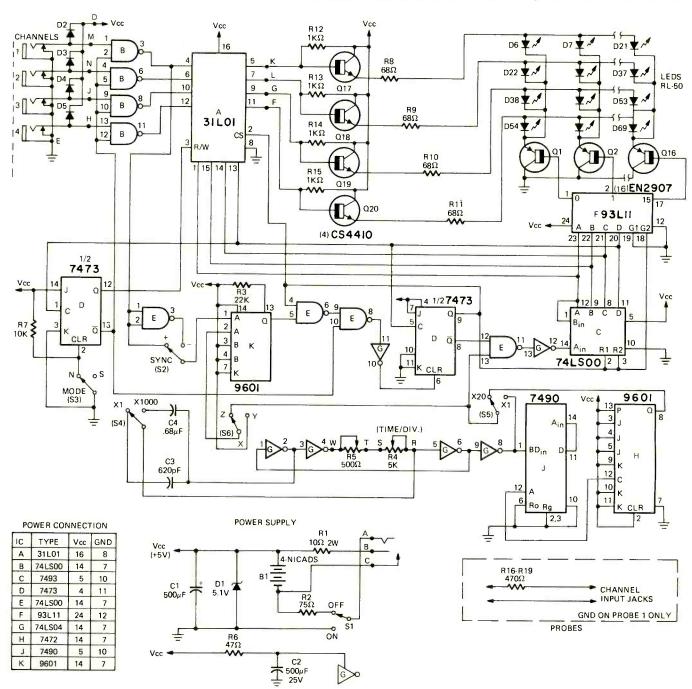


FIG. 2—COMPLETE SCHEMATIC DIAGRAM of the MS-416. Power can be supplied with an optional 117-Vac adapter.

components that go on the back side of the board (R1 and capacitors C1 through C4). Be sure that the polarity on C1 and C2 are correct.

Install Zener diode D1, and make sure polarity is right.

Resistors R2, R3, R6 and R7 are installed next and then transistors Q1 through Q16. Be sure the base-emitter-collector leads of the transistors are properly aligned. This finishes the main board for the time being.

Assemble the LED board in the following manner. Resistors R8 through R15 and transistors Q17 through Q20 are installed on the LED board in the same manner as those on the main board.

The next step requires the greatest care and takes the most amount of time. LED's D6 through D69 are installed. Be sure to align them in straight rows and columns. It is helpful when doing this to draw lines on the PC board with a ballpoint pen and follow these lines while installing the LED's.

The 500-ohm trim pot, R5, is now installed after bending its three leads downward. Insulate the body of the pot from any copper foil on the board by placing a small piece of tape placed directly underneath it. This finishes assembly on the LED board.

Wire the 5K potentiometer, R4, to the main board. Switch S6, located on the pot is also wired to its respective pads on the board. Insert these wires from the back of the board and solder them on the component side.

The two boards can now be wired together. The pads to be connected are marked the same on both boards to make wiring easier.

Finally, the case top and case bottom are assembled. The four input jacks and diodes D2 through D5, along with the

front panel fasten to the case top. It is best to wire the jacks before installing them in the case. The Ni-Cads and the ac jack are installed in the case bottom. Be sure battery polarity is correct. Wire the components in the top and bottom cases to the rest of the circuitry, and you are ready to calibrate the unit.

Calibration is easy

Calibrating the MS-416 is a simple, one-setting operation. In this method, a frequency meter or oscilloscope is needed; although instructions are included with the kit that show how you can set it up without special test equipment, but are less accurate.

For the most accurate calibration, switch S4 should be in the X1000 position and S5 in the X1 position. The TIME/DIV pot R4 should be set in its fully clockwise position. Connect your test instrument ground to the ground on the ac jack and your test probe to the switch terminal on R4 which connects with pad Z on the main board. Connect the unit to the ac adapter and turn the power switch to ON.

Adjust trim pot R5 until the clock oscillator frequency reads exactly 2kHz. Once this frequency is set, the unit requires no further calibration.

The unit can now be completely assembled using the hardware supplied with the kit, and the knob installed on R4. This is done by turning R4 fully clockwise and aligning the pointer on the knob with the $.5\mu$ s marking of the TIME/DIV scale on the front panel.

Using the MS-416

Although the inputs to the MS-416 are protected against overload, remember this is a digital logic oriented instrument; therefore, you should not measure sig-

nals which exceed digital logic voltage levels. In most digital logic, the maximum voltage for a logic "O" is 0.8 voit, the minimum voltage for a logic "1" is 2 volts. The maximum input voltage from the unit you are testing should not exceed 5.5 volts.

When measuring a signal, keep in mind that the sync operates from the channel one input and therefore this channel must be used if you are using less than all four channels. It is best to attach the probe with the ground lead to the channel one jack as a reminder. (Four probes are also supplied with the kit.)

The display of the MS-416 is interpreted in much the same manner as a conventional oscilloscope. The settings on R4 and switches S4 and S5 determine the TIME/DIVISION of the sweep, and each of the 16 LED's in each channel represent one division. Synchronizing from channel one, the signals are displayed showing the logic levels ("1"=LED on. "0"=LED off) and their respective timing relationship.

Turning the TIME/DIV knob fully counter-clockwise to AS (auto-sweep) illows the measurement of steady-state conditions by lighting the entire channel for a logic "1", or blanking the entire channel for a logic "0".

For storage operation simply witch the mode switch to "S" at any time, and the next sweep will store any information present.

If you wish to catch that elusive onetime pulse, simply place the unit in the proper conditions for usual storage operation, setting the mode switch to "S" before you place your probe on the test point you wish to measure. As soon as a pulse comes along it will be "caught" in the memory and held there as long for as

Portable record player introduces new ideas

A new portable two-speed record player operates without the need for the conventional on-off switch, and uses



a hither-to-unknown method of changing speeds. The player simply puts on the record and turns the spindle in a

clockwise direction to start the machine.

The new automatic speed changer operates around a "Magic Ring," a one-piece component made of Celcon (Celanese) plastic, which surrounds a spindle shaft centered within a shallow cupped base. This part acts as a weight sensor, and selects a speed of either 33½ or 45 rpm according to the weight of the record.

The center post of the "Magic Ring" is also the off-on switch. Turning it clockwise starts the machine. It is also the shaft of the volume control, and continuing to turn it brings up the volume.

Inventor and designer of the new-idea player is Art Tateishi, president of Seabreeze Products of Canada, a Toronto company which makes the unique player.

Industrial Research Institute honors zone-melting inventor

W. G. Pfann, who invented the zone melting technique for producing the high-purity metals that make modern transistors and integrated circuits possible, has been awarded the second Annual Achievement Award of the Industrial Research Institute.

The Bell Labs was given a sculpture symbolizing creativity in industrial research,

and was cited for "his vision and leacership in recognizing the requirements for ultrahigh purity materials. This foresight resulted in his research on zone melting and refining and crystal growth techniques.



W. G. PFANN, BELL LABS SCIENTISI, center, receives the award, a sculpturec work of art, entitled "Man and Technology.' from Dr. N. Bruce Hannay, I.R.I. president, right. The presentation address was given by Dr. William P. Slichter, at left in the photo.

Bell & Howell Schools announces two ways to learn new skills in electronics without ever going to class or giving up your job!

Pick the one

Here are two fascinating home-learning adventures that say, "Don't envy the man with skills in electronics... become one!"

If you had to drop everything and go off to school to learn new skills in electronics, there's a chance you might not do it. But Bell & Howell Schools' excellent home training has already proved to tens of thousands that you don't have to drop anything...except the idea that classrooms are the only place you can learn!

You can keep your job, your paycheck and your way of life while you're learning. Because these programs allow you to pick the training schedule that best fits in with your other activities. It's that convenient

I. AUDIO/ELECTRONICS

The first learn-at-home program including 4-channel technology. Explore this totally unique sound of the 70's as you experiment with testing equipment and build a sound center featuring Bell & Howell's superb quadraphonic equipment!

Learn about 4-channel sound—without a doubt the most impressive technical advancement in sound realism in years. A development by which separately-recorded channels literally wrap a room in sound.

And now, for the first time, you can also discover this latest achievement in audio electronics with a fascinating learn-at-home program that explores the whole area of audio technology including 4-channel sound reproduction. A program that could lead you in exciting new directions with professional skills and technical know-how.

You actually build and experiment with Bell & Howell's high-performance 4-channel audio center ...including amplifier and FM, FM-Stereo tuner.

Understanding today's audio technology requires practical experience with high caliber equipment. And with the Bell & Howell amplifier and tuner, you've got the technological tools you need to gain the knowledge and skills that could open up opportunities for



you in the audio field. Of course, we cannot offer assurance of income opportunities.

The sophisticated amplifier gives you the circuitry you need to conduct the comprehensive experiments necessary to master audio technology. Like signal tracing low level circuits, trouble-shooting high power amplifier stages, and checking the operation of tone control circuits.

You'll investigate the technology behind this amplifier's full logic, 4-channel decoder and learn how full logic decoding produces outstanding front to back separation.

The tuner you build has both superior performance specs and state-of-the-art features such as: all solid state, FET front end for superior sensitivity, crystal IF filters for wide bandwidth, and a superior stereo multiplex circuit for excellent stereo separation.

You cover the full range of electronic fundamentals.

But make no mistake. This learn-at-home program is not just about 4-channel sound. It covers the full range of electronic fundamentals leading to understanding audio technology. So when you finish, you'll have the occu-

technology. So when you finish, you'll have the occupational skills to become a full-service technician, with the ability to work on the full range of audio equipment such as tape recorders, cassette players, FM antennas, and commercial sound systems. Get complete information on this unique program by checking the appropriate box on the card—mail it today!

†Cabinets and speakers available at extra cost.



you want!



Simulated TV picture/test pattern.

II. HOME ENTERTAINMENT ELECTRONICS

Gain new skills in Home Entertainment Electronics in an unusual learn-at-home program that includes the new generation color TV you build yourself!

This is the first program of its kind to include the study of digital electronics. And what better or more exciting way to learn about it than to actually build and test a 25" diagonal color TV employing digital electronics?

You'll probe into the digital technology behind all electronic tuning and channel numbers that appear on the screen. An onscreen digital clock that shows the time to the second. You'll also gain a better understanding of the exceptional color clarity of the Black Matrix picture tube, as well as a working knowledge of "state-of-the-art" integrated circuitry and the 100% solid-state chassis.

As you build this remarkable, new generation color TV, you'll not only learn how advanced integrated circuitry works, but how to detect and troubleshoot problems in any area.

Sound good? Then mail the postage-paid card today for more details.

Whichever program you choose, you'll get to build and experiment with your own electronics laboratory.

"Hands on" working experience with the latest equipment is the key to Bell & Howell Schools' home training. That's why in both

programs we start you off with a set of equipment called the Lab Starter Kit, including a fully-assembled volt-ohm meter designed to help you experiment with and better understand basic electronic principles. So you don't just read about electronic principles, you actually make them work!

Next, in step-by-step fashion, you'll assemble Bell & Howell's exclusive



Electro-Lab* electronics training system. It includes a special design console that enables you to assemble test circuits. A digital multimeter for accurately measuring voltage, current and resistance. And a solid-state "triggered sweep" oscilloscope which will allow you to analyze the functioning of tiny integrated circuits. Putting these instruments together will give you experience in wiring, soldering and assembling. Then, further on, you'll use the lab equipment for experience in electronic testing, troubleshooting and circuit analyzing.

We try to give more personal attention than other learn-at-home programs.

Both of these programs are designed so that you can proceed through them smoothly, step by step. However, should you ever run into a rough spot, we'll be there to help. While many schools make you mail in your questions, we have a Toll-Free Phone-In Assistance Service for questions that can't wait. Bell & Howell



various times throughout the year. There you can talk shop with your instructors and fellow students and receive additional assistance.

Get details on one or both of Bell & Howell Schools home-learning adventures...

Mail the postage-paid card today for more information!

Taken for vocational purposes, these programs are approved by the state approval agency for Veterans' Benefits.

"Electro-Lab^R" is a registered trademark of the Bell & Howell Company.

748

If card is missing, write:

An Electronics Home Study School DEVRY INSTITUTE OF TECHNOLOGY



BELL & HOWELL SCHOOLS

4141 Belmont, Chicago, Illinois 60641



about curve tracers

This article tells what to look for when purchasing a curve tracer; how to test different solid-state devices, and how to interpret the resulting waveforms

by CHARLES GILMORE*

LAST MONTH WE COVERED THE FUNDAmentals of curve tracers and started discussing the testing of diodes.

This month we will complete testing and look into testing of bipolar and field-effect transistors.

The curve tracer can examine curves of the reverse-biased diode as well as the forward biased diode. When the diode is reverse biased, theoretically no current flows. However, as shown in Fig. 6, there is current flow once the reverse breakdown voltage of the diode is reached. When the unknown diode is being used as a replacement part in a circuit, the reverse breakdown voltage

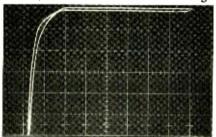


FIG. 6—THE REVERSE CHARACTERISTICS of the 1N4149 silicon small-signal diode. Settings are: cathode series limiting resistance, 10,000 ohms; horizontal sensitivity, 20 volts/cm; vertical sensitivity, 0.5 mA/cm. Note that some looping is caused by internal heating of the diode during sweep and by stray capacitances.

should be measured. Once the diode's reverse breakdown voltage has been determined, the circuit parameters will tell you if it can be used as a replacement part. Some diodes tend to show a fairly large reverse current before they reach reverse breakdown. This leakage current can make the diode an unsuitable replacement. Generally, with small signal diodes the leakage currents are so small that they are unnoticeable on most curve tracers.

The Zener diode is simply a diode whose reverse breakdown characteristics are known and controlled. Figure 7 shows the characteristics of a 1N750 Zener diode. Poor regulation in a Zener-regulated circuit can be caused by too high dynamic resistance when the Zener is conducting. The dynamic resistance of the Zener diode can be computed in

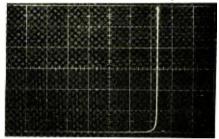


FIG. 7—THE REVERSE CHARACTERISTICS of the 1N709A silicon Zener diode. The diode is rated at 6.2 volts ± 5% at a Zener current of 25 mA. The curve tracer settings are: cathode series limiting resistance, 5000 ohms; horizontal sensitivity, 1 volt/cm; vertical sensitivity, 5 mA/cm. Note that the Zener curve passes through 6.4 volts at the horizontal line representing 25 mA.

exactly the same manner as the forward dynamic resistance of a diode. By referring to the manufacturer's data on the Zener diode, we can learn at what current the Zener voltage is specified and over what current ranges the dynamic impedance of the Zener is specified. When measurements are made "in circuit," the dynamic resistance of the diode is increased by the resistance of other circuit elements in series with the measurement.

The curve tracer is ideal for determining tunnel diode characteristics. As shown in Fig. 8, the characteristics of the tunnel diode are quite unique and you can readily identify the device by them. When using the tunnel diode, the limiting resistor may have to be adjusted to prevent oscillation. Tunnel diodes have a negative resistance region, where the current decreases as the voltage increases. Given the prop-

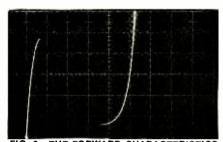


FIG. 8—THE FORWARD CHARACTERISTICS of a GE TD-716 tunnel diode. Settings are: anode series limiting resistance, 5000 ohms; horizontal sensitivity, 0.1 volt/cm; vertical sensitivity, 1 mA/cm. Note the area of trace between the peak current and the valley current is almost impossible to see. If this area of the display contains scrolls, read just the value of series limiting resistance and the sweep voltage to get a trace without scrolling.

er conditions, the negative resistance sustains oscillation.

When the display has been properly adjusted and there is no oscillation (identified by looping or scrolls on the trace), some of the frequently specified characteristics on a tunnel diode can be readily measured. These are: the peak voltage at the start of the tunneling region (V_p); the valley voltage at the end of the tunneling region (V_v); the peak current at the start of the tunneling region (I_p) ; and the valley current at the end of the current tunneling region (I_v). Once these parameters are known, the average value of negative resistance can be computed as $(V_v - V_p)$ divided by $(I_p -$ I_v). When tunnel diodes are displayed on the curve tracer, the region between the peak and valley voltages, that is, the region of negative resistance, is frequently quite dim.

The diac or trigger diode, that is frequently used in series with the gate of a Triac or SCR to fire the device, has the characteristic curve shown in

^{*}Design Engineer Heath Company, Benton Harbor, Mich.

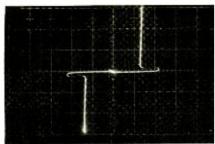


FIG. 9 — THE FORWARD AND REVERSE CHARACTERISTICS of a diac or trigger diode. A double exposure shows both forward and reverse curves in one photograph. Curve tracer settings for reverse measurements are the same as for the forward measurements except the polarity of measurement has been reversed. The curve tracer settings are: series limiting resistance, 5000 ohms; horizontal sensitivity, 20 volts/cm; vertical sensitivity 2.0 mA/cm. Note the match between the forward and reverse breakover voltages.

Fig. 9. Two curves are shown for the diac, a bi-directional device, as the diac has similar characteristics in the forward bias and reverse bias directions. The forward blocking voltage indicated on the display is that voltage where the horizontal line stops and a fine trace swings back to the high current point, showing low forward voltage drop. As the sweep voltage is decreased, the current through the diac is reduced until it finally stops abruptly. This point gives a measurement of the holding current.

2. The bipolar transistor — A large number of characteristics of npn and pnp transistors can be measured with a curve tracer. All measurements applicable to npn devices also apply to pnp devices. The only difference is in the initial set-up. To measure npn devices, the collector or sweep voltage must be positive, and often this is shown on the curve tracer as the npn position. The base or stepping generator must also be in the positive current or npn position. (Note that at this time we use a current generator, as a transistor is a current-operated device). Transistors can be easily damaged if the voltage output of the stepping generator is used.

If an unknown device is found and a curve tracer is used to checkout the characteristics of the device, including pnp or npn, the beam may be initially placed in the center of the curve tracer display. Very moderate levels of sweep voltage and step current are applied first, with a midrange setting of the steps per family control, in the npn direction and then in the pnp direction. One test will yield a family of curves, the other a straight line. The test yielding the family of curves identifies the device. Be sure to keep both the base current and the collector sweep voltage well within the reverse breakdown ratings of the transistor. If incorrect settings are used

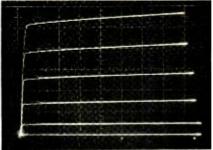


FIG. 10—A FAMILY OF SIX CURVES generated by a 2N3393 silicon npn general-purpose small-signal transistor. Settings are: step generator, 0.01 mA/step; collector series limiting resistance, 100 ohms; horizontal sensitivity, 2 volts/cm; vertical sensitivity, 1 mA/cm. At a collector voltage of 8 volts, the current change indicated by curves three and four is 1.3 mA. As this was caused by a step of 0.01 mA of base current, the beta of this device at this particular operatinig point is 1.3/0.01 = 130.

and the device is forced beyond the breakdown characteristics of its junctions, it could be damaged.

One transistor parameter we frequently measure is dc gain or beta, abbreviated h_{fo}. To a reasonable approximation, the beta of the transistor is the ratio of the collector current to the base current.

Each curve that the curve-tracer gives us represents the collector characteristics for a different base current. DC beta can be readily determined at various collector current and voltage levels. The curves in Fig. 10 show that the spacing between curves caused by the various base steps is not uniform, indicating the beta of the transistor is not uniform for large variations in collector current or voltage. Therefore, beta should be measured as the change in collector current from one step to another, caused by the change in base current from one step to another. Beta measured in this manner is often referred to as the ac beta or the h_{te} of the device. This is a better way to check a transistor because the test is made near the operating current and voltage for the device. However, this is not the high-frequency beta of the device, and does not represent the beta of the device at a few kilohertz

Once we know that a replacement transistor has enough beta, we must find out if its voltage breakdown characteristics allow it to operate successfully in the circuit. The characteristics in question are the collector to emitter voltage breakdown, V_{CB}, and the collector to base voltage breakdown, V_{CB}. The curves in Fig. 11 show the area of collector breakdown, defined as the area where the collector current becomes independent of the base current and begins to rise very sharply.

Voltage breakdown measurements must be made as rapidly as possible or

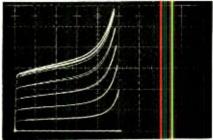


FIG. 11—A FAMILY OF CURVES for the 2N3393 showing collector breakdorn. Collector current becomes independent of the base current as the collector vol age exceeds the 30 to 40-volt region. Settings are: step generator, 0.01 mA/step; collector series limiting resistance, 200 ohrs; horizontal sensitivity, 10 volts/cm; vert cal sensitivity, 5 mA/cm.

excessive power dissipation in the transistor caused by the high collector currents and voltages used in the procedure may damage the device being tested.

To detect collector-to-base and base-to-emitter breakdowns, connect the base-collector or base-emitter terminals of the transistor to the curve tracer as though you were checking an ordinary two-terminal diods for reverse-breakdown characteristics. Do not connect the unused lead of the transistor.

When a transistor is used in relatively high-impedance circuits, the amount of leakage current may be important. This leakage current is often specified in two different forms: I_{CEO} , the collector-emitter current with the base open; and I_{CES} , the collector-emitter current with the base shorted.

To measure I_{CEO}, connect the collector and emitter leads to the curve tracer terminals and leave the base lead open. Then increase the sweep

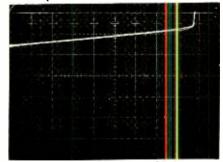



FIG. 12—A MEASUREMENT OF 100 on a 2N398A germanium pnp transister. Curve tracer settings are: collector serie i limiting resistance, 1000 ohms; horizontal sensitivity, 2 volts/cm; vertical sensitivity, 0.5 mA/cm. The step generator is not used, as the base lead is open. Germanium transistors generally have higher leakage currents than silicon. Leakage on this particular device is 800 mA with a collector-emitter veltage of 18 volts.

voltage far as possible, without exceeding breakdown, and measure the leakage current as shown in Fig. 12. If the leakage current is quite smill, you may have to use the magnifier on the curve tracer to see this current. Fre-

quently, it will not be measureable at all. If $I_{\rm CES}$ is to be determined, short the base lead to the emitter lead and make the measurement in the same way as for $I_{\rm CEO}$.

Transistors that are used in digital circuits have a few additional special characteristics, as they specify that the device may be used as a switch. When a transistor is used as a switch, the collector-to-emitter voltage when the transistor is saturated (that is, drawing its maximum collector current) is very important. For instance, if we wanted to use a transistor in a common-emitter circuit to drive the input of a series 7400 TTL gate, we would need a logic zero of at least 0.4 volt. This means that the collectoremitter voltage of less than 0.4 of a volt when sinking a maximum current of 1.6 mA from the input of the gate plus its own collector current.

To determine whether this transistor will properly drive its gates, use a curve tracer to measure $V_{\rm CE}$ (sat) or the collector-emitter saturation voltage. Figure 13-a shows the curves of an npn 2N2369 that is often used in such applications. Note that the saturation voltage increases as the collector current increases. Figure 13-b shows the same transistor, but here the base current is 100 times larger.

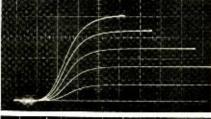

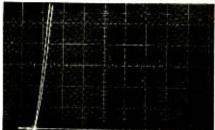


FIG. 13 — SATURATION VOLTAGE ON A 2N2369 switching transistor. a). The transistor is operated at moderate levels of base drive. Settings are: step generator, 0.02 mA/step; collector series limiting resistance, 50 ohms; horizontal sensitivity, 0.1 volts/cm; vertical sensitivity, 2 mA/cm. b). The transistor operates at high levels of the base drive, as might be found in a switching circuit. Settings are: step generator, 2 mA/step; collector series limiting resistance, 50 ohms. Horizontal sensitivity, 0.1 volt/cm; vertical sensitivity, 2 mA/cm.

In some critical applications, temperature has a great effect on transistor characteristics. One way to determine if a transistor will or will not cause problems in a circuit is to operate the transistor in a curve tracer, using collector voltages and currents that repre-

sent those of the anticipated application. Once a family of curves has been established, heat the transistor (a soldering iron, or even finger heat may be sufficient) and note any variations in these curves. With "looping", shown in Fig. 14, the characteristics of the transistor have actually changed

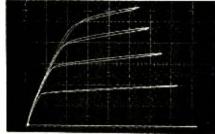


FIG. 14—THERMAL LOOPING CAUSED BY INTERNAL HEATING of the transistor. Transistor is a 2N3393, that has 200 mW dissipation. The curve tracer settings are: step generator, 0.1 mA/step; collector series limiting resistance, 100 ohms; horizontal sensitivity, 5 volts/cm; vertical sensitivity, 20 mA/cm. At the center of the display, the point where there is distinct thermal looping, represents a collector-emitter voltage of 20 volts at a current of 60 mA. This yields a power of 1.2 watts.

between the time the sweep makes the deflection from the left hand to the right hand side of the screen and its return.

In Fig. 15, we can see that with increasing collector voltages this effect can be carried to the limit, and

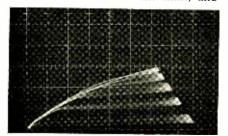


FIG. 15—THERMAL RUNAWAY CAUSED BY EXCESSIVE internal heating of the transistor. The entire characteristics of this transistor were changing as this photograph was being taken (one second exposure). The transistor was destroyed a short time later. Settings are: step generator, 0.1 mA/step; collector series limiting resistance, 50 ohms; horizontal sensitivity, 5 volts/cm; vertical sensitivity, 50 mA/cm.

the curves shown in Fig. 15 represent thermal runaway. At this stage, the transistor parameters are no longer under the control of the base current, but have completely succumbed to device heating. A transistor subjected to this test may be damaged quite rapidly, so work quickly.

When testing transistors on a curve tracer, setups should be made carefully, always starting with low initial voltages and currents, as semiconductor devices can be easily damaged. Curve tracers can produce large voltages and large currents, especially when compared to the limit parameters on small signal semiconductors.

You can destroy a transistor within the first few sweeps of an improperly set-up curve tracer.

Certain hazardous conditions exist when making measurements. Transistors can get very hot when their parameters are exceeded and severe burns can result from touching the cases of both power transistors and small-signal transistors that have been used beyond their limits.

Curve tracers can produce exceptionally high voltages to insure breakdown of most junctions; they also have fairly large current capabilities. The net result is power supplies that are potentially lethal. It is altogether too easy for a person to come in contact with leads on devices that are under test, especially those which have metal cans. Be sure to reduce the sweep voltage to zero before connecting or disconnecting the device from its test socket or leads.

When intermittent tests for transistor breakdown are desired, the A-B switch is an excellent way to rapidly control the curve tracer. To compare devices, a "standard" transistor can be left in one socket and the second socket used to interchange transistors that are being compared or sorted.

The user must remember when making in-circuit tests, that parameters may not be exactly as expected, due to other components in the circuit such as resistors and large capacitors. To make exact parameter measurements on a transistor, remove it from the circuit.

3. Field-effect transistors—Like the bipolar transistor, the field-effect transistor has two major categories of different polarity devices. Unlike the bipolar device, field-effect transistors are voltage operated devices. Initial set ups for measuring field-effect devices include changing the step generator from the current mode to the voltage mode. Today there are six major categories of field-effect devices. Their set ups are shown in the setup table (see May 75 issue). A special note should be made of enhancement-mode field-effect devices, as some curve tracers can not provide the combination of sweep polarity and step generator voltage polarity to properly display their characteristics. One method to overcome this, for example with the n-channel enhancement type, would be to use a positive collector sweep voltage and a negative step voltage. This step voltage must be offset by some positive voltage so the most negative step produces a zero gate to source voltage. One way to do this is to place a battery or an adjustable power supply in series with the gate (the base terminal) of the curve tracer.

(to be continued)

IN THE FEBRUARY 1975 AND MARCH 1975 issue of **Radio-Electronics**, we presented a general description of the TV Typewriter II, some foil patterns, the schematic of the main board and began a technical description.

This month the series will conclude with the construction details.

When the character counter reaches character slot 33, the 2⁵ and 2⁰ bits go to a one which in turn disable the "DOT CLOCK" until a new character line is started. Being in the 33rd character position also enables the video blanking circuit through IC12-c and IC5-b. Since the dot clock is stopped, the video generation ceases after the 33rd character until a new video line is started.

Now that we know how to get the data from the 2513 character generator data inputs to the screen, lets see how the incoming data is put into and accessed from memory. We must first have some means of inputting data to the TV typewriter which in most cases will be a standard keyboard/encoder with a seven-bit ASCII output. The input device must also provide some kind of a "data ready" line to tell the terminal when new data has been applied to the data input terminals. For a keyboard/encoder this is called a "keypressed strobe" line and gives us a pulse whenever a key has been depressed.

Although the seven data inputs are set up for positive logic, the "keypressed strobe" line may be either positive or negative going since NAND gate IC32-a has been provided as an optional inverter. When the "keyboard strobe" pulse reaches the "clock" input of IC9-a, it toggles forcing IC36-b, IC37-a, IC37-b, IC38-a, IC38-b, IC39-a and IC39-b to latch onto the new ASCII data provided at the data inputs, which is in turn fed to the data input terminal of the RAM memory but not loaded.

You must remember that the memory is constantly being readdressed and read and that the address of memory at the time of the "keypress strobe" is completely arbitrary and is most likely not the place where we want to store the character. Keep in mind also that we will want to input special control characters which will command the typewriter to perform a certain function but at the same time not write these control characters into memory.

The latched input character is fed to the function decode circuitry where it is determined whether or not a control function is being input. If it is, such as any input with bits 6 and 7 equal to zero or a rubout with all bits set to 1, the output of IC32 will go high forcing the output of IC11-b low

TV TYPEWRITER II

by ED COLLE

Build this new TV Typewriter. It has many new features including plug-on option boards



resetting IC9-a and preparing IC36-a to dump the input control character on the next load pulse for the "dot registers" IC23 and IC24 from IC25. Note the next time the "clock" input on IC36-a goes high it clears all of the data input latches IC36 through IC39. If on the other hand, the character is a printable character, IC32-b will stay low forcing IC11-b low thus eliminating IC9-a's clear command allowing the Q output to go to a one when toggled by the keyboard strobe. On the next "load pulse", IC16-b is clocked high. The high output of IC9-a and IC16-b are now AND'ed and prepare IC16-a to be switched on the next load pulse from IC25. When IC16-a toggles, its O output goes high setting up one of the two inputs to NAND gate IC15-b and it then waits for a "compare" command from AND gate IC3-d. The input from IC12-d is anded at the same gate just to eliminate false counts after the character counter has reached a count of 33.

The compare circuit will be discussed in detail later, but basically it determines and acknowledges when the memory is indexed to the position in which we want to store the character being processed. When the compare is confirmed, IC3-d goes high forcing IC3-b high, which forces IC15-b low. This makes IC10-a go high generating a write pulse for the memory, thus loading the character at the proper position. At the onset of

the next load pulse IC3-c goes high forcing IC11-b low which resets IC9-a and dumps the input latches, leaving the ASCII code for a blank of space stored. IC16-a and IC16-b both reset on the following load pulse.

Each input character requires 3 "load pulse" time or $4.5\mu s$ to load. Because of this requirement and the fact that only 9 load pulses per character can be guaranteed; 540 characters per second is the maximum input rate. The first 102 lines are slected twice per frame so the write speed on the 5% of each page will be doubled or 1800 characters per second.


The cursor and compare circuits are very interelated since the circuitry must know where the cursor is positioned on the screen and when the memory is indexed to match with the cursor location so the cursor will blink in the right location. Since the character we will be entering through the keyboard will be entered in the cursor's position, the cursor counter also provides the address of the character we want to load into memory. The memory location of the cursor or character to be loaded into memory is stored in a 10-bit counter made up of IC35, IC27-a, IC34 and IC27-b. IC35 holds the data for the first sixteen horizontal character locations on a line and IC27-b sets if the location is on lines 17 through 32. The number of one of the 16 vertical page lines is stored in IC34, and IC27-b holds the bit adcressing one of the two pages of memory.

IC41 and IC42 are two 4-bit comparators that tell us when the data on two sets of its inputs is identical. The required 9th-bit compare is provided by IC40-c and IC40-d. The comparators are cascaded to generate one output telling whether two independent 9-bit addresses are equal, the address being that of the cursor and the location presently indexed. It is not necessary to perform a compare on the tenth or page bit because we will never be writing to or blinking the cursor on the page that is not currently accessed. The comparator circuitry monitors the address of the cursor counter and the outputs of the character counter, IC21 and IC14, and the line counter, IC7, and generates a high "compare" output when there is a match.


The cursor itself is generated by turning on all 35 of the character dots when AND gate IC17-c sees both a "compare" match and inactive blanking. The several times per second blinking is generated by the timer IC8 operating as an astable oscillator.

The cursor is positioned by incrementing and decrementing the up/down cursor counters IC35, IC27-a and IC34, which have full wrap around in each location and automatically

61

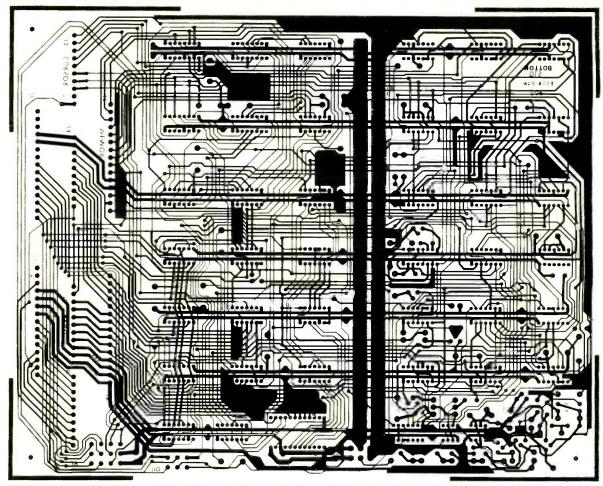

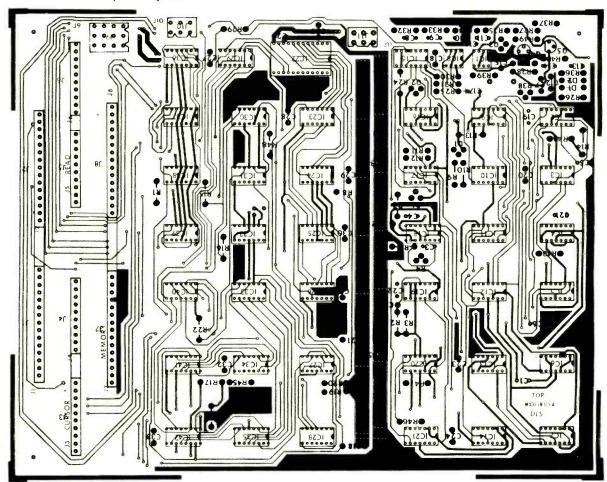MAIN CIRCUIT BOARD foil patterns shown half-size. Above is an X-Ray view of the double sided board. The component layout is shown below.




There are several cursor positioning functions provided. IC35 pin 5 and IC35 pin 4 move the cursor location one position forward and one location backward respectively. IC34 pin 5 and IC34 pin 4 move the cursor one location down and one location up respec-

(1) 10 13 IC1 2102 (10) 10 13 1C2 2102 (3) 10 IC3 2102 (2) 10 IC4 2102 (1) (7) 10 IC5 13 2102 (14) (6) 10 1C6 13 2102 1/10V 1/10V

SCHEMATIC DIAGRAM of the memory circuit is shown


tively. IC35 pin 14 generates a carriage return and IC34 pin 14 generates a return to line 1 which means together they generate a home-up. IC34 and IC35 are responsible for line feed. The interconnected gating allows combinations to be performed with only one control command.

The erase functions have been provided for as well and do not require the optional cursor control board. Erase from the cursor position to the end of the line is initiated by setting the preset input of IC9-b low, and erase from the cursor to the end of frame is initiated by setting the preset input of IC2-a low. If either of these two latches is set, it allows IC2-b to toggle at the onset of the next compare when the row counter reaches line nine. This generates a "memory load" command which loads a space or blank from the input latches into memory. IC2-b will

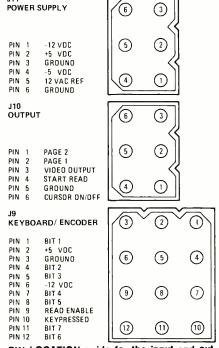

PIN LOCATION guide for the input and output jacks.

TO CIRCUITRY

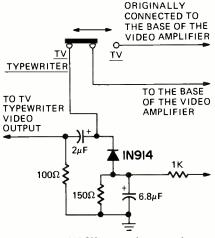

SWITCHING CIRCUIT permits normal operation of TV receiver or as TV Typewriter display.

reset on the first 33rd character indication from IC14 after latch IC2-b is set thus completing an erase to end of line (EOL). IC2-a will reset on the first blanking pulse from IC4-b after latch IC2-b is set, thus completing ar erase to end of frame (EOF). The resetting of either causes IC2-b to reset and return it to its initial state.

Assembly is not difficult

It cannot be emphasized enough that the best guarantee for initial and future trouble-free operation is to be extremely careful when putting the unit together.

The circuit board will be more rugged and reliable if the IC's are soldered in place on the board as shown in the photographs, but those with little experience in digital circuits, or electronic assembly might be wise to invest in some sockets; particularly for the memory IC's.

Install all of the integrated circuits, resistors, diodes, capacitors and then transistors before soldering anything. Note the components are to be mounted on the top side of the board, and the top side is marked "TOP". Double check everything to make absolutely sure all parts have been installed in their proper location and oriented correctly. Check carefully to be sure you haven't inadvertently oriented an integrated circuit incorrectly. This 13 easy to do and almost impossible to correct after soldering without ruining either the integrated circuit or the PC board, or both. When you are sure that everything has been installed correctly, then you may solder all of the component connections on the bottom of the board. All of the connections should be soldered regardless of whether cr not there are electrical connections to the pad. This helps insure that none of the integrated circuits or component leads get bent and inadvertently short out to near-by foil conductors.


Now is the time to carefully check the entire board to be sure that all connections where applicable have been soldered. Make sure also that there are no solder bridges, or improperly installed components.

Follow the same procedure for assembling the memory board as you did for the main circuit board. The memory integrated circuits are MOS devices which are very intolerent of static electricity so be sure to take appropriate precautions. Here again be sure to check over the board very carefully after assembly to be sure there are no mistakes.

Attach all of the wires to the connector plugs for the power supply, J11, output, J10, and keyboard, J9. Use the connector drawing to show the appropriate pin connection for each of the (continued on page 87)

63

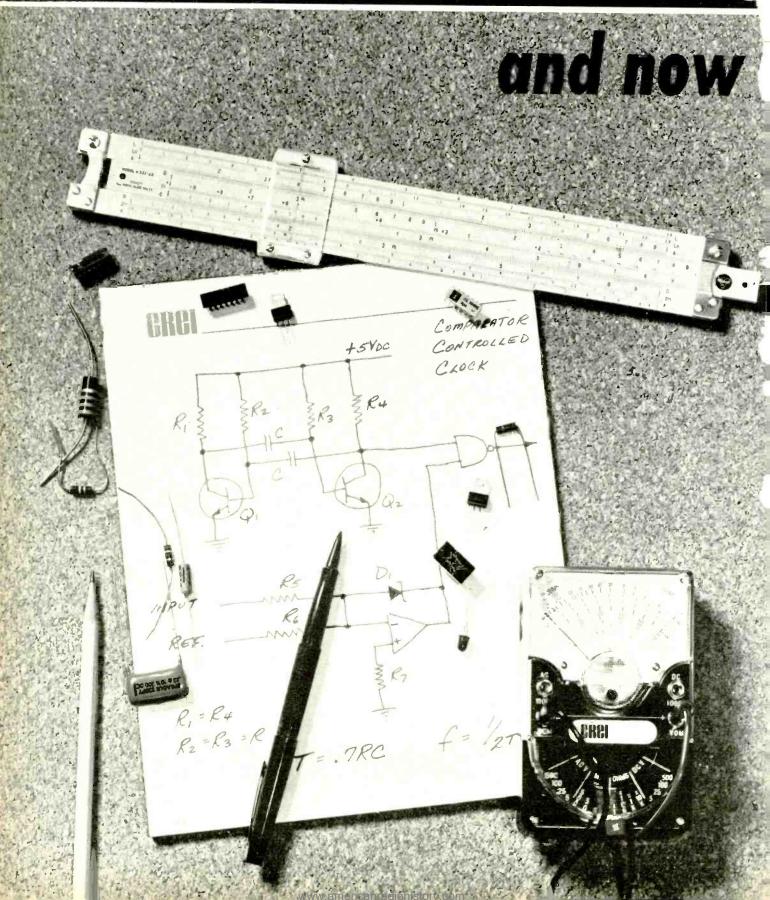CREI—the <u>only</u> home-study college-level training



program which gives you in electronic circuit design

only CREI offers you a complete college-level Electronic Design Laboratory to speed your learning

Electronic circuit design—source of all new development in the application of electronics to new products and services. Without this skill, we would be unable to monitor the heartbeat of men in space. Without it, the computer revolution would never have occurred. And we would have yet to see our first TV show. Yet, only CREI teaches electronic circuit design at home.

ELECTRONIC CIRCUIT DESIGN

A key skill which paces our nation's progress in countless fields—from pollution control to satellite tracking to modern medicine to exploring the ocean's depths. And beyond. A skill which you must have to move to the top in advanced electronics.

CREI programs open up new worlds of opportunity for you.

In addition to electronic circuit design, CREI provides you with a full advanced electronics education in any of thirteen fields of specialization you choose. Communications, computers, space operations, television, nuclear power, industrial electronics—to mention just a few of the career fields for which CREI training is qualifying. With such preparation, you will have the background for a career which can take you to the frontiers of the nation's most exciting new developments. And around the world.

This free book can change your life. Send for it.

If you are a high-school graduate (or equivalent) and have previous training or experience in electronics, then you are qualified to enroll in a CREI program to move you ahead in advanced electronics.



Send now for our full-color, eighty page book on careers in advanced electronics. In it, you will find full facts on the exciting kinds of work which CREI programs open up to you. And full facts on the comprehensive courses of instruction, the strong personal help, and the professional laboratory equipment which CREI makes available to you. All at a surprisingly low tuition cost.

And when you have it, talk with your employer about it.

Tell him you're considering enrolling with CREI. He'll undoubtedly be happy to know you are planning to increase your value to him. And he may offer to pay all or part of your tuition cost. Hundreds of employers and government agencies do. Large and small. Including some of the giants in electronics. If they are willing to pay for CREI training for their employees, you know it must be good.

Send for Advanced Electronics today. You'll be glad you did.



CREI Dept. E-1404F 3939 Wisconsin Avenue Washington, D.C. 20016

Type of Present Work

Rush me your FREE book describing my opportunities in advanced electronics. I am a high school graduate.

Address _______ State _____ ZIP ______

If you have previous training in electronics, check here

Employed by ______

Veterans and servicemen, check here for G. I. Bill information [

www.americanradiohistory.com

CREI

CAPITOL RADIO ENGINEERING INSTITUTE

WASHINGTON, D.C. 20016

RADIO-ELECTRONICS

Step-by-step TV Troubleshooters Guide

With the increasing number of manufacturers using integrated circuits in their television receivers, it's important for the service technician to know how these devices work.

by STAN PRENTISS

EVEN THOUGH SYLVANIA'S NEW GT-MATIC has a unique 31.5 kHz IC oscillator, other sections can develop an interesting problem or two. I was all set to do a narrative on Sylvania's well-engineered E03, E04, and E05 chassis (all pretty much the same except the E04 has electronic tuning) when the night before story time, my E05 popped its circuit breaker with the switch off. At least it popped first with the switch on then repeated continuously with the switch off. And, as any service technician familiar with semiconductors can tell you, this means only one possible thing—a

short! How fortunate that this receiver is completely guarded by a circuit breaker. On the other hand, what do you do with a dead set? Well, like Sherlock Holmes, you look for clues.

Trouble tips

Most of us are blessed with two eyes, and an ohmmeter is a common electronic tool. So let's not rush off and tear up the set. Go back and consider your basic symptom: that the circuit breaker trips no matter what position the off-on switch is in. This means that the fundamental

problem has to be in some circuit that isn't really controlled by the off-on switch—and that, of course, is the picture-tube filament transformer that's on all the time. Refer to the schematic diagram of the power supply in Fig. 1. With switch S502-b in the OFF position, R504 limits the picture-tube heater voltage to about 4.8 volts. With S502-b in the ON position (closed), heater voltage measures a full 6.3 Vac, plus +36 Vdc connected through R506 (150K) to reduce heater to cathode arcs.

With ac applied to the 120 V interlock,

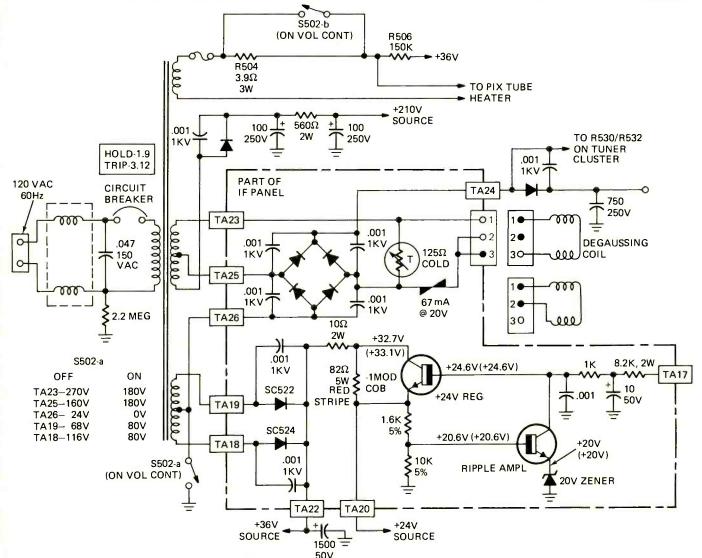


FIG.1—POWER SUPPLY schematic of Sylvania's EO3 and EO5 chassis.

FIG. 2—WAVEFORMS OF POWER SUPPLY shown in Fig. 1. Upper waveform is taken from TA-18, while lower waveform is at TA-25. The scope is set at 50V/div.

the power transformer hums a few seconds before the circuit-breaker pops. Does this indicate a bad transformer? Usually no—basically it's a sign that too much current is flowing and setting up vibrations in the transformer laminations. This is often caused by other circuit faults.

Trouble shooting

Unfortunately, a few initial ohmmeter checks at terminals TA18 through TA26 and a random front-to-back check of sev-

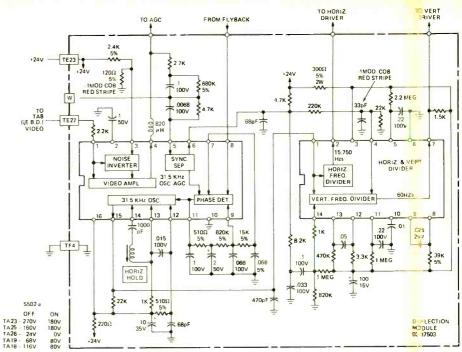


FIG. 3—IC300 and IC400 vertical and horizontal countdown IC's, block diagram and peripheral components.


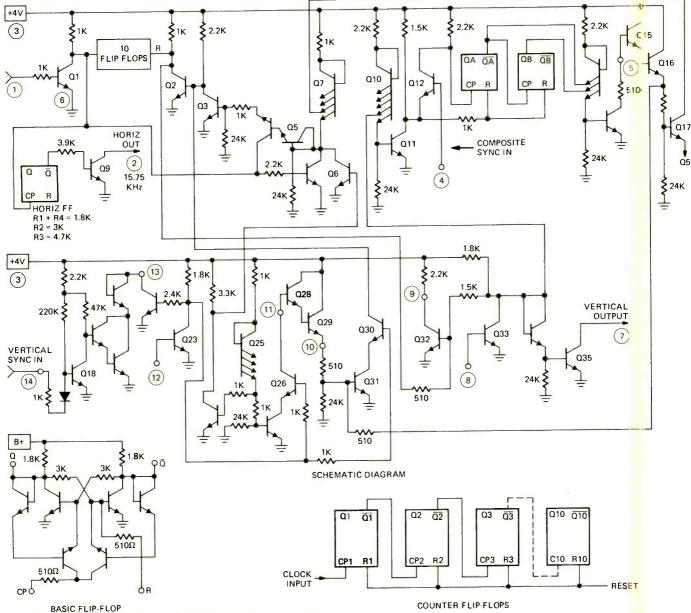


FIG. 5—IC300 HORIZONTAL AND VERTICAL countdown circuits.

69

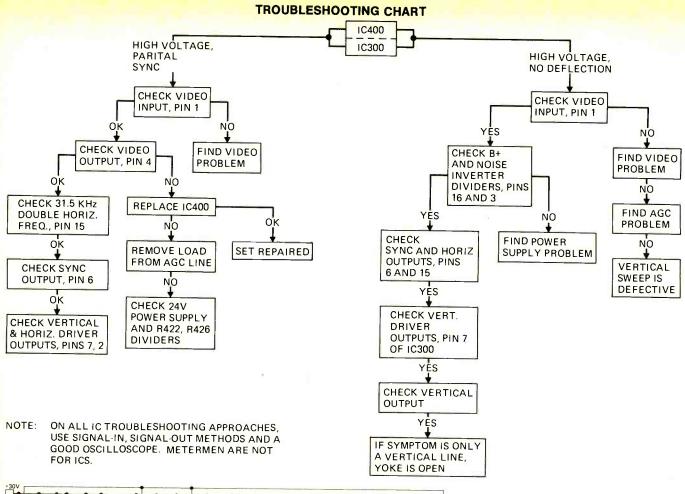

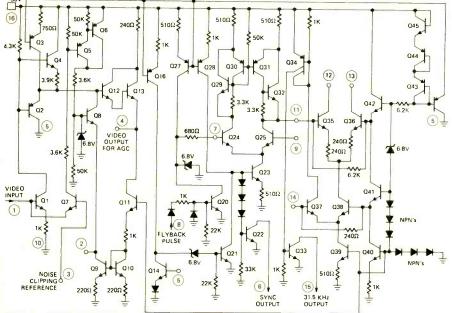


FIG. 4-IC400 SCHEMATIC DIAGRAM.

eral diodes revealed nothing. Disconnecting the picture-tube heater connections and applying power wasn't helpful either. With S502 on or off, the circuit-breaker still tripped. So, when all's said and done, you have one of two conditions-either the transformer is shorted, or there are problems somewhere across the 150K resistor that ties the +36 V source to the picture-tube heater. There is one sure way to find out, however, but you've got to be extremely careful. Specs on the circuit breaker says that it trips at 3.12 amps. Supposing that the transformer is all right. Put a 4 or 5 ampere fuse in place of the

circuit breaker and watch for smoke. With the set plugged in, wisps of telltale burning aren't long in coming.

In this case, smoke was quicker than the eye. It took a minute or two of probing before diode SC522, half of the fullwave rectifier for the 36 volt source, was discovered burned in two. Since ohmmeter checks revealed no low readings to ground at any of the power board's critical points, we can assume SC522 had developed leakage. Even though the centertap of the winding feeding it was open through S502-a, this diode (at least) was passing (continued on page 78)

R-E's Substitution guide for replacement transistors

PART XXV by ROBERT & ELIZABETH SCOTT

ARCH-Indicates the Archer brand of semiconductors sold only by Radio Shack and Allied Radio stores. Allied Radio Shack, 2725 W. 7th St., Ft. Worth, Texas 76107

DM-D. M. Semiconductor Co., P.O. Box 131, Melrose, Mass. 02176

G-E-General Electric Co., Tube Product Div., Owensboro, Ky. 42301

ICC-International Components, 10 Daniel Street, Farmingdale, N.Y. 11735

IR—International Rectifier, Semiconductor Div., 233 Kansas St., El Segundo, Calif. 90245

MAL—Mallory Distributor Products Co., 4760 Kentucky Ave., Indianapolis, Ind. 46241

MOT-Motorola Semiconductors, Box 2963, Phoenix, Ariz. 85036

-RCA Electronic Components, Harrison, N.J. 07029

-Sprague Products Co., 65 Marshall St., North Adams, Mass. 01247

SYL—Sylvania Electric Corp., 100 1st Ave., Waltham, Mass. 02154

WOR—Workman Electronic Products, Inc., Box 3828, Sarasota, Fla. 33578

ZEN—Zenith Sales Co., 5600 W. Jarvis Ave.,

Chicago, III. 60648

Radio-Electronics has done its utmost to insure that the listings in this directory are as accurate and reliable as possible; however, no responsibility is assumed by Radio-Electronics for its use. We have used the latest manufacturers material available to us and have asked each manufacturer covered in the listing to check its accuracy. Where we have been supplied with corrections, we have up-dated the listing to include them. The first part of this Guide appeared in March 1973.

	ARCH	DM	G-E	ICC	IR	MAL	MOT	RCA	SPR	SYL	WOR	#EN
2N5784 2N5785 2N5786 2N5787 2N5788	NA NA RS276-2025 NA NA	TS-3002 TS-3010 T-242 NA NA	NA GE-86 GE-28 NA NA	ICC-S3002 ICC-S3010 ICC-242 NA NA	NA NA NA NA	NA NA PTC 142 NA NA	HEP-S3002 HEP-S2010 HEP-242 NA NA	SK 3024 SK 3024 SK 3024 NA NA	RT-154 RT-154 RT-154 NA NA	NA NA ECG 186 ECG 5400 ECG 5401	WEP-WS3002 WEP-WS3003 WEP-242 NA NA	NA Z:N 207 NA NA NA
2N5789 2N5790 2N5804 2N5805 2N5806	NA NA NA NA	NA SR-1005 T-707 T-707 SR-1473	NA NA NA NA	NA ICC-R1005 ICC-707 ICC-707 ICC-R1473	NA NA NA NA	NA NA PTC 118 PTC 118 NA	NA HEP-R1005 HEP-707 HEP-R1473	NA NA NA NA SK 3509	NA NA NA NA	ECG 5402 ECG 5404 ECG 162 ECG 162 ECG 5543	NA NA WEP-707 WEP-707	NA NA ZIN 204 ZIN 204 INA
2N5807 2N5808 2N5809 2N5810 2N5811	NA NA NA RS276-2009 RS276-2021	SR-1475 NA NA T-53 T-51	NA NA NA GE-20 GE-67	ICC-R1475 NA NA ICC-53 ICC-51	NA NA NA NA	NA NA NA PTC 136 PTC 127	HEP-R1475 NA NA HEP-53 HEP-51	SK 3509 SK 3509 SK 3509 NA NA	NA NA NA RT-100 RT-101	ECG 5545 ECG 5546 ECG 5547 ECG 123A ECG 129	NA NA NA WEP-53 WEP-51	NA NA NA Z:N 102 Z:N 101
2N5812 2N5813 2N5814 2N5815 2N5816	RS276-2009 RS276-2021 RS276-2009 RS276-2021 RS276-2009	T-736 T-716 T-736 T-716 T-736	GE-63 GE-67 GE-20 GE-67 GE-20	ICC-736 ICC-716 ICC-736 ICC-716 ICC-736	NA NA NA NA	PTC 123 PTC 127 PTC 136 PTC 127 PTC 136	HEP-736 HEP-716 HEP-736 HEP-716 HEP-736	NA NA NA NA	RT-109 RT-115 RT-100 RT-115 RT-100	ECG 128 ECG 159 ECG 128 ECG 159 ECG 128	WEP-736 WEP-716 WEP-736 WEP-716 WEP-736	ZEN 120 ZEN 107 ZEN 120 ZEN 107 ZEN 120
2N5817 2N5818 2N5819 2N5820 2N5821	RS276-2021 RS276-2009 RS276-2021 RS276-2018 RS276-2025	T-716 T-736 T-716 T-243 T-242	GE-67 GE-63 GE-67 GE-63 GE-67	ICC-736 ICC-736 ICC-716 ICC-243 ICC-242	NA NA NA TR-25 TR-28	PTC 127 PTC 136 PTC 127 PTC 136 PTC 127	HEP-736 HEP-736 HEP-716 HEP-243 HEP-242	NA NA NA SK 3024 SK 3025	RT-100 RT-100 RT-115 RT-114 RT-115	ECG 128 ECG 128 ECG 159 ECG 128 ECG 129	WEP-736 WEP-736 WEP-716 WEP-243 WEP-242	ZEN 107 ZEN 120 ZEN 107 NA NA
2N5822 2N5823 2N2824 2N5825 2N5826	RS276-2018 RS276-2025 RS276-2013 RS276-2013 RS276-2013	T-243 T-242 T-729 T-729 T-728	GE-63 GE-67 GE-62 GE-62 GE-62	ICC-243 ICC-242 ICC-729 ICC-729 ICC-728	NA NA NA NA	PTC 136 PTC 127 PTC 121 PTC 121 PTC 121	HEP-243 HEP-242 HEP-729 HEP-729 HEP-728	NA NA NA NA	RT-114 RT-115 RT-109 RT-109 RT-109	ECG 128 ECG 129 ECG 123A ECG 123A ECG 123A	WEP-243 WEP-242 WEP-729 WEP-729 WEP-728	NA NA ZEN 115 ZEN 115 ZEN 114
2N5827 2N5828 2N5829 2N5830 2N5831	RS276-2013 RS276-2013 NA RS276-2008 RS276-2008	T-728 T-738 NA TS-0005 TS-0005	GE-62 GE-62 NA GE-20 NA	ICC-728 ICC-738 NA ICC-S0005 ICC-S0005	NA NA NA NA	PTC 121 PTC 123 NA NA NA	HEP-728 HEP-738 NA HEP-S0005 HEP-S0005	NA NA NA SK 3018 NA	RT-109 RT-109 NA RT-114 NA	ECG 123A ECG 123A NA ECG 123A NA	WEP-728 WEP-728 NA WEP-712 WEP-712	ZEN 114 ZEN 121 NA NA NA
2N5832 2N5833 2N5834 2N5838 2N5839	RS276-2008 RS276-2008 NA NA NA	TS-0005 TS-0005 TS-3031 T-707 T-707	NA NA NA NA	ICC-S0005 ICC-S0005 ICC-S3031 ICC-707 ICC-707	NA NA NA NA	NA NA NA PTC 118 PTC 118	HEP-S0005 HEP-S0005 HEP-S3031 HEP-707 HEP-707	NA NA NA NA	NA NA NA NA	ECG 194 ECG 194 ECG 189 ECG 162 ECG 162	WEP-712 WEP-712 WEP-WS3031 WEP-707 WEP-707	NA NA ZE № 204 ZE № 204
2N5840 2N5844 2N5845 2N5847 2N5848	NA NA NA NA	T-707 T-715 TS-0004 NA NA	NA NA GE-20 NA NA	ICC-707 ICC-715 ICC-S0004 ICC-S0006 ICC-S0007	NA NA NA NA	PTC 118 NA PTC 136 NA NA	HEP-707 HEP-715 HEP-S0004 HEP-S0006 HEP-S0007	NA NA NA NA	NA RT-115 RT-114 NA NA	ECG 162 ECG 159 NA ECG 194 NA	WEP-707 WEP-715 WEP-56 WEP-717 WEP-735	ZE 1 204 ZE 1 106 ZE 1 127
2N5851 2N5852 2N5853 2N5854 2N5855	NA NA NA NA	T-720 T-720 TS-5005 TS-5005 TS-3031	NA NA NA NA	ICC-720 ICC-720 ICC-S5005 ICC-S5005 ICC-S3031	NA NA NA NA	NA PTC 121 NA	HEP-720 HEP-720 HEP-S5005 HEP-S5005 HEP-S3031	NA NA NA NA	RT-105 RT-105 NA NA RT-115		WEP-720 WEP-720 WEP-WS5005 WEP-WG 5005 WEP-WS 3031	ZE 109 ZE 109 1A 1A 1A
2N5856 2N5857 2N5858 2N5859 2N5860	NA NA NA NA	TS-3020 TS-3031 T-714 TS-3002 TS-3002	NA NA NA NA	ICC-S3020 ICC-S3031 ICC-714 ICC-S0002 ICC-S0002	NA NA NA NA	PTC 141 PTC 144	HEP-S3020 HEP-S3031 HEP-714 HEP-S0002 HEP-S0002	NA NA NA NA	RT-114 RT-115 RT-144 RT-102 RT-102	ECG 188 ECG 189 ECG 190 ECG 192 ECG 192	WEP-WS3020 WEP-WS 3031 WEP-WS3021 WEP-735 WEP-735	TIA TIA TIA TIA
2N5861 2N5864 2N5865 2N5867 2N5868	NA NA NA NA	TS-3002 TS-3012 TS-3012 TS-5007 TS-5005	NA NA NA NA	ICC-S0002 ICC-S3012 ICC-S3012 ICC-S5007 ICC-S5005	NA NA NA NA	NA NA PTC 141 NA NA	HEP-S0002 HEP-S3012 HEP-S5007 HEP-S5005	NA NA NA NA	RT-102 NA NA RT-153 NA		WEP-735 NA NA WEP-WS 5007 WEP-WS 5005	LIA LIA ZELI 211 LIA
2N5869 2N5870 2N5871 2N5872 2N5873	NA NA NA NA	TS-5003 TS-5004 TS-5002 TS-5005 TS-5001	NA NA NA NA	ICC-S5003 ICC-S5004 ICC-S5002 ICC-S5005 ICC-S5001	NA NA NA NA	NA NA NA NA	HEP-S5003 HEP-S5004 HEP-S5002 HEP-S5005 HEP-S5001	NA NA NA NA	RT-152 NA NA NA NA	ECG 182 ECG 183 ECG 180	WEP-WS 5003 WEP-WS 5004 WEP-WS 5005 WEP-WS 5004	HA HA HA
2N5874 2N5875 2N5876 2N5877 2N5878	NA NA NA NA	TS-5004 T-248 T-248 T-247 T-247	NA NA NA NA	ICC-S5004 ICC-248 ICC-248 ICC-247 ICC-247	NA NA NA NA	NA NA NA NA	HEP-S5004 HEP-248 HEP-248 HEP-247 HEP-247	NA NA NA NA	NA RT-165 RT-165 RT-131 RT-131	ECG 219	WEP-WS5004 WEP-WS 7001 WEP-WS 7001 WEP-247 WEP-247	HA HA HA HA
2N5879 2N5880 2N5881 2N5882 2N5883	NA NA NA NA	T-248 T-248 T-247 T-704 TS-7001	NA NA NA NA	ICC-248 ICC-248 ICC-247 ICC-704 ICC-S7001	NA NA TR-21 TR-21 NA	NA NA NA NA	HEP-248 HEP-248 HEP-247 HEP-704 HEP-S7001	NA NA SK 3024 SK 3024 NA	RT-165 RT-165 RT-114 RT-114 RT-148	ECG 130 ECG 130 ECG 128 ECG 128 NA	WEP-WS 7001 WEP-WS 7001 WEP-247 WEP-704	RA RA RA

curve traver or lab-type transistor checker. NA=NOT AVAILABLE

ARCH

2N5884

DM

TS-7001

G-E

NA

ICC

ICC-S7001

IR

NA

MAL

NA

MOT

HEP-S7001

RCA

NA

SPR

SYL

WOR

ZEN

ECTRONI

山

Ò RADI

APRIL 1975

RE's Service Clinic

Servicing Electronic Organs

They are not as difficult as they look

by JACK DARR SERVICE EDITOR ELECTRONIC ORGANS AREN'T HARD TO repair. Any radio-TV shop can find and fix troubles, using only standard TV test equipment. Although they look complicated, they use only standard audio circuits; tone generators, wave-shaping networks, power amplifiers. (Actually, they don't look as complicated as the back view of one of the big stereo-theater consoles, with remote controls!) Tube and transistor electronic organs use the same basic circuits, with the usual differences.

Most organs use the master oscillator-frequency divider system. A tunable oscillator circuit, generally a Hartley, generates the highest frequency note. This is then fed to a series of frequency dividers. This is possible because of an inherent characteristic of music. Each note is exactly one-half of the frequency of the same note in the octave above it. Example: middle A is 440 Hz. The next higher A is 880 Hz and the next lower A is 220 Hz.

The first electronic organs used vacuum-tube circuits (and many, many tubes! 12AX7's all over the place!) Figure 1 shows a typical divider circuit using one-half of a 12-AX7. The master oscillator output is

22K
OUTPUT
TO KEYS
OUTPUT
TO KEYS
OUTPUT
COUPLING
CAPACITOR

TO NEXT
DIVIDER

1 12 AX7
FEEDBACK
COUPLING
CAPACITOR


PLATE
CAPACITOR
OR
470K

FIGURE 1

shaped into a rounded-corner sawtooth. The peaks of this are used to sync the divider stage. The time-constant is designed so that this stage delivers one output sawtooth for every two sync-pulses from the stage before it. So, it divides by two.

The transistor organs use a circuit that's a natural for frequency division. This is a bistable multivibrator, or flipflop. This circuit divides by two with the greatest of ease; the first syncpulse from the preceding stage makes

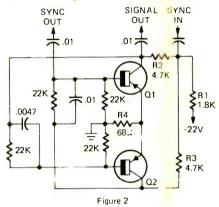it *flip*, then the next one makes it *flop*. To divide by two, we take the output from flop, and there you are. Figure 2 shows a typical flip-flop, as used in Magnavox transistor organs.



The basic signal in both electronic organs is the sawtooth. This gives the characteristic organ sound. The output of the tube divider is a sawtooth, and the flip-flop output is usually almost a square wave. This can easily be shaped into the desired sawtooth.

This is done in the voicing circuits. These are wave-shaping networks, some including amplifiers. Figure 3 shows some of the typical filters used. The low-pass circuit of Fig. 3-a is used to produce the Flute; the h gh-pass filter of Fig. 3-b is used for the violin

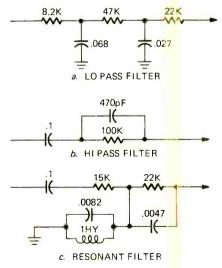


Figure 3

and viola tones, and the resonant filter of Fig. 3-c for such tones as hern and reed. From the output of the voicing unit, we go to an audio amplifier.

The keyboards of an organ aren't

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. If return postage is not included, we cannot process your question. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, N.Y. 10003.

MATHEMATICS ELECTRONICS

We are proud to announce two great new courses for the electronic industry.

These unusual courses are the result of many years of study and thought by the President of Indiana Home Study, who has personally lectured in the classroom to thousands of men, from all walks of life, on mathematics, and electrical and electronic engineering.

You will have to see the lessons to appreciate them!

NOW you can master mathematics and electronics and actually *enjoy* doing it!

WE ARE THIS SURE: you sign no contracts—you order your lessons on a money-back guarantee.

In plain language, if you aren't satisfied you don't pay, and there are no strings attached.

Write today for more information and your outline of courses.

You have nothing to lose, and everything to gain!

The INDIANA HOME STUDY INSTITUTE

DEPT. RE-475, P.O. BOX 1189 PANAMA CITY, FLA 32401

Circle 21 on reader service card

called keyboards; they're called manuals. In older models, the top one is the Swell manual and the lower one the Great manual. Some later units call the top one the Solo and the lower the Accompaniment. The different voices are controlled by tabs, and guess what they're called. Tabs! Incidentally, for the complete novice, when you start to check out an organ by playing it, be sure that at least one tab is in the ON position for each manual. In some organs, if they are all up or off, you may not hear anything when a key is pushed down. (The preceding data is included so that you'll have a better chance of knowing what the organist is talking about when she calls you for service! You gotta speak the language.)

To make a first check for trouble, turn the organ on. Check to see that one tab is down, for example, the flute or diapason on the top, and the horn on the lower manual (The tabs are in two groups of 5 or 6, one for each manual). Now, look under the organ; you'll see a foot-pedal. To us, it's a volume control, but they call it an expression pedal. The pedals control the bass, and look like a big wooden keyboard! Now, run up and down the keyboard and see if each note sounds, and how it sounds. You'll be able to tell, even if you're no more

musical than I am.

One common trouble is a defective frequency divider. The clue to this is when higher notes sound all right, for example the two high A's. However, the third A may sound the same (frequency) as the second! In most cases, the third note will have a burbling sound. Check the third divider, or whichever one is burbling. This type of trouble in tube organs is most often due to leaky capacitors or resistors which have changed value, thus upsetting the time-constants of the stage. When one note burbles, all of the same notes lower than it will burble too.

To check the voicing circuits, put each tab down, by itself, and run up and down the keyboard. Each one should have a definite effect on the sound. If you lose the sound completely when any tab is pushed down, check for a broken wire, open transistor in the bus amplifier, etc.

If you have any doubts as to whether any master oscillator isn't working, check it with a scope. In some organs, such as the Magnavox transistor organ, you can connect a jumper lead with a 100K resistor in series to the audio amplifier input. Touching this to the signal-output leads of any tone generator will produce this tone in the speaker, if it is working. You are by
(continued on page 76)

10MHz 5" scope with easier calibration and voltage measurement



Model 1465 \$428

Here are some B&K extra touches. Besides DC-to-10MHz bandwidth, triggered sweep, automatic sync, 16.6mV/cm vertical sensitivity, DC-coupled amplifier and front-panel Vectorscope capability, Model 1465 also has 5X magnification to increase sweep speed to 0.2usec/cm for complex waveform analysis. And Cali-Brain®, which collapses horizontal sweep to let you measure instantaneous peak-to-peak voltage easily while simultaneously displaying the full-scale voltage range. Now in stock at your local distributor or write Dynascan.



•

Circle 22 on reader service card

You'd probably expect a portable oscilloscope as rugged and reliable as this one to cost a lot.

You'd be wrong.

Introducing the B&K Model 1403 3" Solid-state oscilloscope. It's so compact, reliable, and inexpensive that it's the perfect scope for most onthe-line monitoring applications. Look at its specs: DC to 2MHz bandwidth at 20mV/cm. Recurrent sweep speeds from 10Hz to 100k Hz. New wide-angle CRT to reduce case depth to a minimum. Direct-deflection terminals for waveforms up to 150 MHz. Weighs only 8½ pounds. And has a smoked acrylic graticule for trace sharpness and easy reading. All the reliability and accuracy you need in a monitor scope—at a surprisingly low price.

Contact your distributor, or write Dynascan Corporation.

\$18900



Very good equipment at a very good price.

Dynascan Corporation. 1801 West Belle Plaine Avenue, Chicago, Illinois 60613

Circle 23 on reader service card

Introducing the expensive curve tracer that doesn't cost a lot.

The B&K Model 501A.

It's a lab-quality instrument that provides fast analysis of all semiconductors including J-FET's, MOS-FET's, signal and power bipolar transistors. SCR's, UJT's and diodes.

You can test transistors in circuit for GO/NO GO condition. Badly distorted curves will indicate the stage where a defective transistor or other faulty component exists.

The 501A is complete—with scope graticule and FP-3 probe for fast, one-handed in-circuit testing. It generates true current and voltage steps, with 3% accuracy, for measuring beta at all current levels.

And it has a sweep up to 100 volts and 100 milliamperes.

With the 501A, curves are displayed on an auxiliary scope screen. And you can hook it up to any scope—old or new.

All three controls can be set in quick-test positions to test and evaluate 90% of all solid-state devices without manufacturer's data sheets.

The 501A won't burn out either the semiconductors or itself.


With all these features, you'd think the 501A was an expensive curve tracer. But look at the price.

For complete technical data, call your B&K distributor. Or write Dynascan Corporation.

Very good equipment at a very good price.



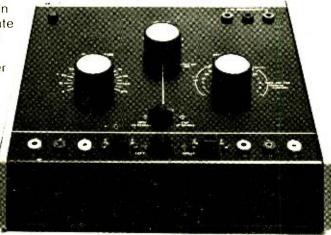Product of Dynascan Corporation 1801 West Belle Plaine Avenue, Chicago, Illinois 60613 \$163⁰⁰



change in the frequency.

frequencies.

passing the voicing circuits.

Electronic organs have a true vibrato effect. Although guitar amplifiers use the terms vibrato and tremolo interchangeably, in music they are not. (They do sound a lot alike, though!) Vibrato is a periodic variation in the frequency (pitch) of a note, and tremolo is a periodic variation in its volume. Organs get a true vibrato by feeding a slowly-varying dc voltage (about 6-8 Hz) to the base of the master oscillator. This causes a small

This is easy to check. Just hold any key down, and turn the vibrato switch on. You'll hear it. Some have a vibrato control; if you don't hear the vibrato, check to see that this isn't turned all the way off. The vibrato oscillator is just a very low-frequency multivibrator. You can identify it by the very large capacitors and resistors used for coupling. In fact, you can often check a vibrato oscillator with a dc voltmeter; the needle will vibrate visibly. A scope will usually show an almost straight line moving up and down.

All in all, after you get used to the things, they're not at all hard to service. You can do anything except tune


them. This is seldom needed, but when it is, a complicated strobe instrument is the only way. For normal repairs, just sit down at the keyboard and start looking for the Lost Chord. (I found it once, but I lost it again.) Just push the keys and find out what is working and what isn't! then look in the back to find out why. As the old saying goes, "Try it! You'll like it!" R-E

reader questions

ELECTROLYTIC BLOWS

The customer said there was a Bang, and this Truetone WEG-2297-A27 went out. When I turned it on, I got a weird raster, with a dark spot in the center. Opening it up, I found that a small electrolytic capacitor on the high-voltage sweep module had exploded. It's connected to the cathode of the 6GK6 horizontal output. I replaced it, and the new one exploded, too! I have no schematic on this set. What's causing this?—G.W., Waldron, AR.

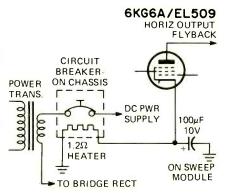Schematic on this one is in Sams 1216-3. This capacitor is apparently



used to bypass the horizontal output tube cathode. It returns to ground through a little heater in the *circuit breaker*. If this heater is open, the pulse voltage will blow this little capacitor; 100-µF, 10V. Check from pin 2 of the sweep module to ground for not more than 1.3 ohms.

SCOPE PROBLEM

In an old Supreme 546 scope, I get about 1/2 inch vertical deflection without input. Focus control has practically no effect. What does this?—E.S., New Ringgold, Pa.

Probably a resistor changed value in that long network from the negative high-voltage supply. Most likely one, that 470,000-ohm unit between the focus control and the focus pin on the 3AP1 base. (continued on page 94)



The FM-2400CH with its extended MHz. The range covers 25 to 1000 frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability: ± .0005% from +50° to +104°F.

Frequency stability. ± 10003 moin +30 to +104 ft. Frequency stability with built-in thermometer and temperature corrected charts: ± .00025% from +25° to +125° (.000125% special 450 MHz crystals available).

Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

Write for catalog!



Circle 28 on reader service card

AUDIO SIGNALS

(continued from page 39)


frequencies of about 30 MHz. The EIA bulletin, like the earlier FCC bulletin, suggests bypassing the output circuit to ground with ceramic capacitors. A properly stabilized audio amplifier can withstand fairly large values of capacitance across the speaker terminals without oscillating, and the low impedance of the output circuit precludes any loss in high-frequency response because of such capacitive bypassing. Nevertheless, if you have doubts about the relative stability of your amplifier under conditions of such capacitive loading, the best thing to do is to observe the output at the speaker terminals on an oscilloscope. Do this for several positions of the master volume control while musical program material is being played and watch for any evidence of high frequency "blips" superimposed on the low-frequency audio waveforms. Normally, the value of capacitance needed to eliminate rf interference at this point should be low enough so as not to cause oscillation, but it's a good idea to check this out before you discover that some super-audible high-frequency oscillation has burned out the tweeters in your speaker systems.

There is no single solution to the

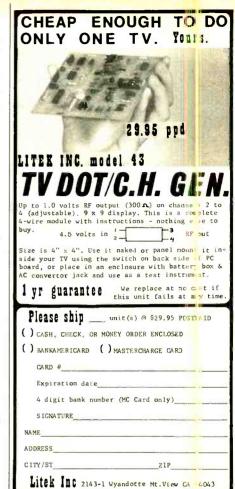problem of audio rectification in hi-fi component equipment, and we have suggested just a few things that may help. Undoubtedly, many readers have been plagued with these kinds of interferences and may have worked out unique solutions to specific problems. Perhaps those of you who have faced and solved the problems of interference would like to share your solutions with others. If so, please tell us how you solved the problems, preferably naming the equipment involved, and we'll devote more space to this subject in a future article. R-E



"Would you go for a malfunction in my electronic calculator"



Circle 29 on reader service card

You don't have to buy a new car to get an electronic ign<mark>it</mark>ion

West of the second of the seco



Let's face it. After 37 years, even a Phantom II can use a lift. That's why I put a Delta Mark Ten B Caracitive Discharge Ignition on my Phantom . . . to give he a spark I'd pit against any '75 model car. I went to Delta because they aren't Johnny-come-latelys. Delta's been making electronic ignition systems for over a decade.

Whatever kind of car you drive, you can give it the same great Delta performance I gave mine.

- Mark Ten B Capacitive Discharge Ignition Systems are manufactured by Delta Products, Inc., a comularly with a conscience, and with a proven record of reliatility both in product and in customer relations.
- The Mark Ten B really does save money by eliminating the need for 2 out of 3 tune-ups. Figure it out for yourself. The first tune-up or two saved pays for the unil, the rest is money in your pocket. No bunk!
- Because the Mark Ten B keeps your car in better tune, you actually can save on expensive gasoline.
- With a Mark Ten B, spark plugs stay clean and last longer . . . fouling is virtually eliminated.



Name				
Address				
City		_State	Zip	
	ELTA PROD	HOTO IN		

Mark Ten B. assembled Mark Ten B, kit

\$64.95 ppd \$49.95 ppd

Standard Mark Ten, assembled Deltakit(R) Circle 61 on reader service card

\$49.95 ppd \$34.95 ppd

TROUBLED BY TRIGGERED SCOPES?



The Hickok Model 512 Dual Trace Oscilloscope eliminates the set-up and precision problems you've had to accept using other triggered scopes.

It's easy to set up

- Simplified color-coded front panel controls.
- Beam finder quickly locates off-scale traces.
- Foolproof triggering to 15 MHz.

It gives you superior performance

- 10 MHz response flat within 3dB. Excellent pulse response.
- Unique automatic VITS sync separator.

Hickok industrial lab quality and construction

Glass epoxy PC boards used throughout. Regulated power supply.

Plus, our exclusive two-year warranty.

Ask to see the Hickok Model 512 or single trace Model 511 at your Hickok distributor or contact us for more information.

\$67500

complete with probes and accessories

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION THE HICKOK ELECTRICAL INSTRUMENT CO. 10514 Dupont Avenue • Cleveland, Ohio 44108 (216) 541-8060 • TWX: 810-421-8286

Circle 62 on reader service card

STEP-BY-STEP

(continued from page 70)

enough current to open the circuit breaker. In replacing SC522, I noted that its part No. had been changed to another diode from 13-17174-2 to 13-29165-2-45. The +36-volt bus supplies both the horizontal driver and the push-pull audio outputs.

Operationally, you'll find there is 2 Vp-pripple at the output cathode connections of the two diodes; but don't be alarmed, that's normal. Figure 2 shows the normal waveforms that should appear at TA18 and TA25, with the receiver plugged in and switched on. Each at 50V/div., the top waveform is TA18 and the bottom TA25—ac volts only. Then on Fig. 1, you'll see a list of the ac p-p inputs to the power rectifiers; \$502-a both on and off.

Sylvania's effective sync IC's

This article was supposed to be about some nifty circuits in the GT-Matic. These circuits contain IC's. You may not necessarily want to specialize in integrated circuits, but the day is coming, and soon, when a working knowledge of what they are and what they do can mean technical survival. In Fig 3, the video amplifier, noise inverter, 31.5-kHz oscillator, sync separator, and phase detector are all shown in the IC400 block diagram. The IC400 block diagram shows you "who and what," but it does not tell you "how" it works

Figure 4 shows the schematic diagram of the IC400 integrated circuit. Video enters pin 1 and the emitter of Q7 in negative phase. The video is inverted by Q1 and buffered by Q4 before it is applied to the base of Q12 (Q2 and Q3 are bias sources, with Q3 a base dc reference from point "S"). Without noise, the video signal is amplified by the Darlington configuration (Q12 and Q13) for a video agc output.

Video output is through pin 4 for age and is also returned through an RC bias network (Fig. 3) to the base of Q14 (Fig. 4), permitting only positive sync tips to forward bias this transistor, whose active load is Q16. Sync is inverted and amplified through a coupling Zener to Q21, where it is again inverted and applied both to the base of sync output Q22, and the base of current source Q23. Q28 is an active load. At the same time, a flyback comparison pulse is diodecoupled to the base of Q20 (pin 8), is inverted and appears at the base of Q24. Transistors Q24 and Q25 form a differential amplifier, which compares sync and flyback phase. Any difference voltage is fed to the base of Q35 as a correctional voltage. Transistors Q35, Q36, O37, O38, and O39 (the constant current generator) all form a stable 31.5 kHz oscillator. The load resistors connect to pins 12 and 13 (see fig. 3), and the L420 oscillator (horizontal hold) coil is connected between pins 13 and 14. Output is through multiple collector Q34, to Q33, and pin 15.

Count down IC300

A stable 31.5-kHz signal has been developed which is independent of stationgenerated sync and flyback phase comparison. It's now necessary to establish the precise 59.94-Hz field and 15,734-Hz line repetition rates that all television receivers must have for compatible vertical and horizontal deflection.

The 31.5 kHz output from IC 400 enters pin 1 of IC300 (Figs. 3 and 5), is amplified and inverted by transistor Q1, and routed both to the count down group of 10 flip flops (one of which is shown at the lower left corner of Fig. 5), and also to a single divide-by-two flip flop at the base of Q9. The IC400 31.5-kHz is now halved to 15,734 Hz and amplified by Q9 as the horizontal repetition rate drive pulse which, in turn, energizes the horizontal driver.

The chain of 10 flip flops are what digital logic people call a ripple counter since each stage drives another, and all succeeding stages operate at half the frequency of their driver or clocking stage. This means that 10 dividers will divide by 210 or 1024. However, all that's needed is a line count of 525 (262.5 lines for each field), and something additional for possible sync correction. So at the 9th flip flop, the count down from 31.5 kHz amounts to just about 60 Hz, and that's the frequency needed.

There are 10 flip flops in the chain instead of 9, however, so something must turn off the counter following the 9th flip flop. This is done by the gating circuits at the top right and center of Fig. 5. The vertical sync signal comes in at pin 14 and applied to the base of Q18. Also, composite sync is applied to pin 4 and the base of Q12. Without doing a complete timing diagram which would be surprisingly tedious, detected interlace pulses will operate the QA-QB flip flops so that Q15 thru Q17 will gate Q7. When this occurs the Q5, Q3, group resets the 10 flip flops at point R. This produces the sought-after 525 count that induces normal sync output at Q35 as Q32 turns on and Q33 turns off. The positive output pulse at Q33 also cuts off Q10, which causes Q11 to stop conducting and the QA-QB pair of flip flops in the 525 line reset counter are reset.

When no interlace signals are detected, the vertical sync input chain takes over, as well as Q25, Q26, Q28 etc. When reset fails to occur at 525 lines, coincident pulses arrive from Q23 (vertical sync input), Q29, and Q16 (the 525 counter): so that Q30 and Q31 become an AND gate. When this occurs, Q2 is cut-off and produces a reset signal at point R as the collector voltage of O2 rises toward the 4V source supply. At this point, the maximum count is 541, and the counter runs at such a rate until an interlace signal is again detected. Such gating is necessary where there are unusual noise or electrical interruptions, or where composite video originates from a source other than a broadcasting station that has no interlace sync. This could be a closed-circuit camera, some community cable systems, or other local varieties of signal origination which do not have broadcast quality transmitters. Counter flip flops at the bottom of Fig. 5 show how all 10 FF's of the count down chain are connected.

new products

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Reader Service Card inside the back cover.

IC MULTIMETER, PM2503, features voltage range protection up to 2 kV, automatic polarity with indication and linear scales for all ranges. Minimum 10 megohm input impedance provides virtually no-load measurements at 3% worst case accuracy. Circuitry allows linear scales to be used for all measurements except dB. Other features include: separate readings of dc and ac components of measured signals, pushbutton ac/dc



selection, single rotary switch for range selection and V-ohm on the same input sockets.

Has ac/dc current ranges of 1 μA to 1A, ac/dc voltage ranges of 100 mV to 1 kV and resistance ranges (also with linear scales) of 100 ohms to 10-megohms. Plastic housing is lined with layer of conductive material connected to meter's ground for protection against induced rf. Core construction of meter movement guards against stray magnetic fields. No zeroing or infinity adjustments are required; uses standard 9-volt batteries to supply 1000 working hours before replacement. \$169.00—comes complete with measuring leads and spare fuses incorporated inside.—Philips Test & Measurement Instruments, Inc., 400 Crossways Park Drive, Woodbury, NY 11797.

Circle 31 on reader service card

AUTOMATIC TURNTABLE, model 351 features industry's widest umbrella spindle that eliminates double record drop, record hangups or slanting of unbalanced records. Contains bi-directional viscous-damped cueing and counterbalanced pickup arm that operates on a horizontal and vertical gimbal bearing system. This system assures minimal friction in both vertical and horizontal planes. Slide-in cartridge adaptor facilitates cartridge change.

Other features include an anti-skate device for both spherical and elliptical stylus settings, gravity stylus pressure adjustment that contains no variable springs and a 4-

pole synchronous motor. Complete with uniplanar design wherein most moving parts have been placed on single horizontal plane. Tracking is ¼ gram. Unit comes equipped with a Shure M91E cartridge, ellip-



tical diamond stylus, walnut grain base and smoke-tinted hinged protective dustcover. Supplied with rotating manual spindle that eliminates record hole wear. When stub spindle is used, record plays once automatically, arm returns to rest position and turntable shuts off, \$160.00—Glenburn Corp. 787 Susquehanna Avenue, Franklin Lakes, NJ 07417.

Circle 32 on reader service card

RECORD CLEANER, *model AT6008*. Use on CD-4 discs as well as conventional 2-channel recordings and matrix 4-channel records. Comprised of velvet-surfaced cleaning unit



with handle, storage base, cleaning brush, special cleaning solution and solution applicator. Foam-backed velvet surface, together with the cleaning solution, loosens and collects dust and dirt from entire depth of record grooves. Special feature is the rotating handle which permits a fresh cleaning surface to be provided continually as the cleaner is moved across the record.

Cleaning solution is applied with special applicator to a reservoir atop the cleaner from which it is dispensed gradually to the velvet surface below; this feature avoids the

BENCH PERFORMANCE IN YOUR POCKET



The Hickok Model 239 color bar generator has an exclusive MOS LSI chip which provides 9 Rock Stable patterns and low battery drain.

- Simplified operation with 2 matrix slide switches.
- Crystal controlled chroma and timing oscillators.
- RF adjustable Channels 2-4.
- Powered by 2 standard 9v batteries.

Plus our unique 2-year warranty.

The Hickok Pocket Model 239 or our deluxe bench Model 246 are values you have to see to appreciate. See them at your Hickok distributor or contact us for more information.

\$115⁰⁰

HICKOK

the value innovator

INSTRUMENTATION & CONTROLS DIVISION THE HICKOK ELECTRICAL INSTRUMENT CO 10514 Dupont Avenue • Cleveland, Ohio 44108 (216) 541-8060 • TWX 810-421-£286

Circle 63 on reader service card

Circle 33 on reader service card

SOLID-TUBE, R-3DS3. Silicon solid-state plug-in rectifier tube replaces vacuum tube rectifier types 3DR3 and 3DS3. Emits no Xradiation, creates no heat and since it has



no filament, it makes an ideal substitute in cases where the filament or flyback transformer is faulty.-Electronic Devices, Inc., 21 Gray Oaks Avenue, Yonkers, NY 10710.

Circle 34 on reader service card

CASSETTE DECK, model CD-1669. ANRS-Automatic Noise Reduction System-reduces tape hiss to an inaudible level without af-



fecting the quality of the music. Accommodates tapes recorded with other noisereduction systems. Has automatic ANRS

Features include Super Cronios ferrite heads for longer life, two tape-select switches for bias and equalization, solenoid operated controls. Hysteresis synchronous motor drives the capstan and a dc motor drives the reels for accurate speed and decreased wow and flutter. Indicator lights show deck's function and peak-level indicator flashes a warning when over-recording takes place. Auto stop and auto play rewinds and restarts the deck automatically. There is independent input select switch for improved linearity. \$499.95—JVC America, Inc., 50-35 56th Road, Maspeth, NY 11378.

Circle 35 on reader service card


SMOKE ALARMS, SDA-2 & SDA-3 are for use in homes, apartments and businesses and are easily installed.

SDA-2 operates from standard electrical current. Has a built-in pilot light to indicate it is functioning. SDA-3 is powered by 12.6-

volt Duracell mercury-cadmium battery (304-116). Battery triggers smoke alarm when it approaches end of useful life thus calling attention to the need for a replacement battery. Each alarm is 61/2 in. in diameter and 3 in. thick. SDA-2 \$61.60; SDA-3 \$81.00.-Mallory Distributor Products Co., 4760 Kentucky Avenue, Indianapolis, IN 46241.

Circle 36 on reader service card

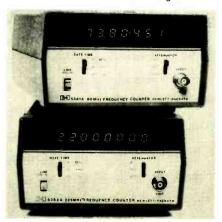ELECTRONIC COUNTERS, 5381A and 5382A. Lab-quality counter makes possible precise alignment of the crystal filters and high-Q i.f. strips found in costly stereo receivers, assuring they will operate in the home the way they did in the design lab. Similar satisfactions can be found from setting the SCA



trap precisely at 67 kHz. Sensitive inputs have protection against overload; in their wide-open settings, they will take 200 volts (peak ac + dc) without harm.

Both units operate on external precision time-base through a built-in rear connector

BONANZA

NEW

PRODUCTS

- (A128) 13 MINIATURE ELECTROLYTIC CONDENSERS \$1.00
 Axial & upright, popular values.
- (A150) 15 Hi-Fi KNOBS \$1.00 Every one superb! Purchased from Harmon Kardon, Fisher,
- (A127) 20 ASST. VOLUME CONTROLS \$ \$1.00
- Assorted ohmages, some with switches. (A158) 2 NORTRONICS

\$1.00

- TAPE HEADS
 One stero, one mono. (A153) CHASSIS MYSTERY \$1.19
 - Take a chance! Could be a tape recorder, radio, walkie talkie,
- (A156) 60 DISC CAPACITORS
 Asst. capacitances from to .1, most 600v, Z5U, \$1.00 most 600v, Z5U, NPO, N750, etc.
- (A147) 4 lb. GRAB BAG SPECIAL \$1.00 Full of exotic and exciting electronics parts.
- (A140) TAPE RECORDER (A140) IAPE RECURDER
 SPARE PARTS KIT
 Contains dozens of parts used in most tape recorders including: pilot lamp, capacitors, resistors, jacks, level meter, switches, volume controls, transistors, and MUCH MORE.
- ☐ (A155) TUBE BONANZA! \$1.00 0 asst. popular tubes, untested.



(A293) SEVEN SEGMENT LED'S \$1.00 14 pin DIP tested.

- (A223) 10 ASST. LED's \$1.00 Tested.
- (A178) 2 BATTERY MOTORS Misc. \$1.00

(A242) 3 LED's \$1.00 Yellow or green (specify).

☐ (A001) 5 RED LED's

☐ (A266) 2N3055 Si, NPN \$1.00 T0-3 case, audio, power, 115w, 100vbc, NFE 20-70.

(ALSS32) 10 ZENER DIODES

\$1.19 under ly forward 1w, 3-30v, un characteristic.



☐ (A253) 7 AMP POWER TRAN-**SISTOR** \$1.49 Si NPN. Similar to SK3054. 9v, 90w.

- (ALSS24) 25 ZENER DIODES \$1.19 400mw, 4-20v. Under 1v forward characteristic.
- ☐ (ALSS23) 25 POWER TRANSISTORS \$1.19
 Outstanding value! Asst. cases and types, up to 15w, RF to 2 mHz
- (A167) 10 MINIATURE POTENTIOMETERS \$
 For transistor applications.
- (A175) 70 1/2 w CARBON RESISTORS \$1.00 All Std. makes & EIA values. Some 5%.
- ☐ (A154) 150 CUT LEAD RESISTORS \$1.00 Carbon, all leads long enough for soldering.
- (A149) 20 POLYSTYRENE TOP GRADE CAPACITORS \$1.00
- Popular sizes (A159) 15 TRIMMER CAPACITORS \$1.00
- Includes duals and singles. ☐ (A132) 20 DUAL
- POTENTIOMETERS Asst. ohmages, originally for Hi-Fi stereo and TV.
- (A131) 13 ELECTROLYTIC \$1.00 CONDENSERS FP types, tubulars, some multiple sections.
- ☐ (A138) 10 SLIDE SWITCHES \$1 All types: DPDT, SPST, etc. \$1.00
- ☐ (A134) 8 ROTARY \$1.00 SWITCHES Some multiple gang.
- (A145) 50 TIE LUGS From 2 lugs up. \$1.00

MONEY BACK GUARANTEE Terms: Minimum order \$4.00. Include postage. Either full payment with order or 20% deposit, balance C.O.D.

WRITE FOR FREE VALUE PACKED CATALOG

BONUS FREE CAPACITOR KIT With Every \$5 Purchase SURPLUS TUBES All guaranteed for I full year.

ANY 3 FOR \$1.25

Acquired from U.S. Defense depots or removed from equipment (new and used). These are laboratory tested and guaranteed for one full year. Most are of such standard rankers as RCA, GE, etc.

3A3	6AQ5	6DE4	6X4
3AF4	6AQ7	6DR7	10EW7
3BN6	6AT6	6DW4	12AE7
3DG4	6AU6	6EA8	12AL5
3EJ7	6AV6	6EB8	12AL11
3KT6	6AV11	6EJ7	12AT7
3Q4	6AX4	6EM7	12AU7
4BC5	6AX5	6ER5	12AV6
4BN6	6AY3	6EY6	12BE6
4BU8	6AY11	6GF7	128H7
48Z7	6BA6	6GH8	1208
4CY5	6BG6	6GN8	17JZ8
4HA5	6BJ8	6GU7	18FW6
5V6	6BQ6	6K6	21KQ6
5Y3	6BZ6	6K11	25L6
6AC7	6CB6	6LB6	35EH5
6AF4	6CG7	6SN7	35Z5
6AG5	6CL6	6T8	36AM3
6AG7	6CM7	6V6	50A5
6AL5	6DA4	6W4	50L6
6AL7			

(A125) 4 TRANS-FORMÉRS \$1.00 Some power, filament, output, worth up to \$10 each.

(144) TRANSISTOR REPAIR KIT \$1.00 Various and sundry parts used to repair all transistorized

(A143) 20 RUBBER FEET \$1,00

- ☐ (A164) 4 ROLLS OF WIRE \$1.00 Approx. 25 ft. per roll, 20-28ga.
- (A148) 4 ROCKER SWITCHES \$1.00 Assorted. (A137) 10 INSTRUMENT
- KNOBS \$1.00
 Made for industry by Ratheon, etc. All high grade.

 (A141) 6 RCA JACK
 - STRIPS From 2-6 per strip. (A142) 50 PRECISION \$1.00
- RESISTORS \$1.00 All 1%, ½w and 1w, low and high ohmages.
- (A161) 50 CERAMIC AND MICA CONDENSERS
 Runs the gamut of sizes. \$1.00
- ☐ (A162) 25 CORNING GLASS RESISTORS
- Silicon inculated, most 10% tolerance, 2-7 watts.

 (A170) 4 RELAYS \$1.00
 Asst. types, 6-110v, some worth up to \$10.
- (A168) 12 TRANSISTORS \$1.00
 Asst. Not rejects, fully guar.
 (A171) 5 CRYSTALS \$1.00 (A171) 5 CRYSTALS Popular bands, asst. asst. holders.

☐ (A182) 2 TUNING \$1.00 Misc., miniature.

EDLIE ELECTRONICS, INC., 2700-L HEMPSTEAD TPKE., LEVITTOWN, N.Y. 11756

that works at levels from 250 mV to 25 V. 80-MHz model 5381A \$249.00; 225-MHz model 5382A \$450.00. High-stability temperaturecompensated oscillator adds \$100.00. Each weighs 4.75 lbs; power may be from 100 to 240 V; neither has battery option.-Hewlett-Packard Co., 1501 Page Mill Road, Palo Alto,

Circle 37 on reader service card

SOLDER/DESOLDER/RESOLDER DEVICE, Vented Tunnel Tip can be used with 90% of the soldering irons now being used in industry. Can solder, desolder and resolder all with the same tip. Features total solder flow control, total solder removal even in plated through holes, no need for additional desoldering aids, no more waste of precious



copper desoldering braid, minimum thermal risk to sensitive components and one hand operation. Production tool as well as printed circuit board salvage tool.

Unit is a hollow bored and vented soldering tip that operates by instant capillary action in two basic modes. Expulsion of accumulated solder within the unit may be performed by simple hand flicking motion. For 1/8 in., pencil iron 10T14-125T threaded tip; for 3/6 in., pencil iron 10T14-187P plug tip. Less than \$2.00.—Gunmaster Industries Corp,. 170 Old Country Road, Mineola, NY 11501.

Circle 38 on reader service card



Circle 65 on reader service card



FITS IN A BRIEFCASE

INTERESTED? Call Hal Wardein at (714) 279-6572, or write to us at 7170 Convoy Court, San Diego, California 92111. For local ordering information, dial TOLL-FREE 800-645-9200; in N.Y. State call collect (516) 294-0990.

From a Leader in Mini-Portable Oscilloscopes

AVAILABLE NOW FOR ONLY \$645

CORPORATION



Circle 66 on reader service card

Now...the most enjoyable do-it-yourself project of your life-a Schober Electronic Organ!

You'll never reap greater reward, more fun and proud accomplishment, more benefit for the whole family, than by assembling your own Schober Electronic Organ.

You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystal-clear instructions show you — whoever you are, whatever your skill (or lack of it) how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.

Five superb models with kit prices from \$575 to around \$2,300, each an authentic musical instrument actually superior to most you see in stores, easy for any musically minded acult to learn to play, yet completely satisfying 1:r the accomplished professional. And there are accessories you can add any time after your organ is finished - lifelike big auditorium reverbe ation. automatic rhythm, presets, chimes, and more

Join the thousands of Schober Organ billder-owners who live in every state of the Jnion. Often starting without technical or music skills, they have the time of their lives — first assem-bling, then learning to play the modern king of Instruments through our superlative instructions and playing courses.


Get the full story FREE by mailing the coupon

TODAY for the big Schober color catalo, with all the fascinating details!



The Schober (Organ Corp., Det. New York.	Dept. RE-137 N. Y. 10023
☐ Please send me Schober Organ Catalog. ☐ Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music.		rgan Catalog. or 12-inch L.P.
NAME		
ADDRESS		
CITY	STATE	ZIP

Circle 67 on reader service card

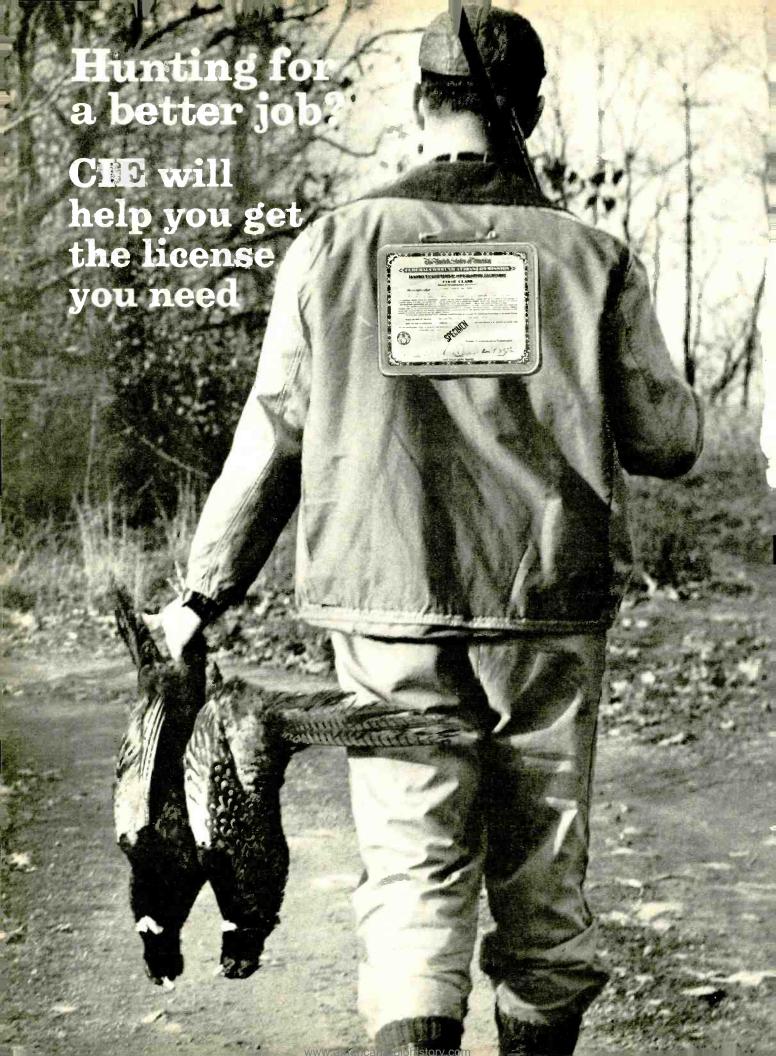

A Government FCC License can help you qualify for an exciting, rewarding career in ELECTRONICS, the Science of the Seventies. Read how you can prepare at home in your spare time to pass the FCC Licensing examination.

If you're out to bag a better job in Electronics, a Government FCC License can give you a shot at job opportunities with *real* futures.

According to the U.S. Office of Education Bulletin (4th Edition): "The demand for people with technical skills is growing twice as fast as for any other group, while jobs for the untrained are rapidly disappearing." There are new openings every year in many different industries for electronics specialists. And you don't need a college education to qualify.

But you do need knowledge . . . knowledge of electronics fundamentals. And one of the nationally accepted methods of measuring this knowledge . . . is the licensing program of the FCC (Federal Communications Commission).

Importance of an FCC License and CIE's Warranty of Success

If you want to work in commercial broadcasting . . . television or AM or FM broadcasting . . . as a broadcast engineer, federal law requires you to have a First Class Radiotelephone License. Or if you plan to operate or to maintain mobile two-way communications systems, microwave relay stations or radar and signaling devices, a Second Class FCC License is required.

But even if you aren't planning a career which involves radio transmission of any kind, an FCC "ticket" is valuable to have as Government certification of certain technical skills. It's a job credential recognized by some employers as evidence that you really know your stuff.

So why doesn't everyone who wants a good job in Electronics get an FCC License?

It's not that simple. To get an FCC License, you must pass a Government licensing exam.

A good way to prepare for your FCC License exam is to take one of the CIE career courses which include FCC License preparation. We are confident you can successfully earn your license, if you're willing to put forth an effort, because the vast majority of CIE students have. In fact, based on continuing surveys, close to 9 out of 10 CIE graduates have passed their FCC exams!

That's why we can offer this time-tested Warranty of Success: when you successfully complete any CIE career course which includes FCC License preparation, you will be able to pass the Government FCC Examination for the License for which the course prepared you or you will be entitled to a full refund of an amount equal to the cash price of tuition for CIE's Course No. 3, "First Class FCC License," in effect at the time you enrolled. This warranty is good from the date you enroll until the last date allowed for completion of your course.

CIE HAS CAREER COURSES THAT INCLUDE "HANDS ON" TRAINING

ELECTRONICS TECHNOLOGY with LABORATORY

Courses...takes beginner from fundamentals to skills required of technician or engineering assistant. Includes Experimental Electronics Laboratory for "hands on" training.

COLOR TV MAINTENANCE and REPAIR... several CIE courses combine electronics theory with the actual construction, testing and troubleshooting a big screen, stolid state color TV.

With CIE you learn at home

With CIE, you learn in your spare time at home ... or wherever else is convenient. No classroom time, ever. No one to make you go too fast ... or too slow. With C E's Auto-Programmed® Lessons you'll pick up facts, figures, and electronics theories you may have considered "complicated" ... even if you've had trouble studying before.

You can have attractive job opportunities

There have already been many exciting developments and breakthroughs in Electronics and some people might assume there will be no new frontiers... no new worlds to conquer. Not so.

Electronics is still growing. In nearly every one of the new and exciting fields of the Seventies you find electronics skills and knowledge in demand. Computers and data processing. Air traffic control. Medical technology. Pollution control. Broadcasting and communications. Once you have the solid technical background you need, you can practically choose the career field you want ... work for a big corporation, a small company or even go into business for yourself.

Yes, Electronics can be the door to a whole new world of career opportunities for you. And CIE training can be your key.

Send for FREE school catalog

Discover the opportunities open to people with electrorics training. Learn how CIE career courses can help you be ild new skills and knowledge and prepare you for a meaningful, rewarding career. We have courses for the beginner, for the hobbyist, for the electronics technician, and for the electronics engineer. Whether you are just starting out in Electronics or are a college-trained engineer in need of updating (or anywhere in between), CIE has a course designed for you.

Send today for our FREE school catalog and complete package of career information. For your convenience, we will try to have a representative call to assist in course selection. Mail reply card or coupon to CIE... or write: Cleveland Institute of Electronics, Inc., 1776 East 17th Street, Cleveland, Ohio 44114. Do it TODAY.

APPROVED UNDER G. I. BILL

All CIE career courses are approved for educational benefits under the G.I. Bill. If you are a Veteran or in service now, check box for G.I. Bill information.


CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114 Accredited Member National Home Study Council

Cleveland Institute of Electronics, Inc. 1776 East 17th Street, Cleveland, Ohio 44114		
Please send me your FREE school catalog and career information package today. I am especially interested in:		
☐ Electronics Tech ☐ FCC License Pre ☐ Color TV Mainte	paration 🗆 Ele	dustrial Electronics ectronics Engineering
Mobile Commun		· ·
Print Name		
Address		Apt.
City		
State	Zip	Age
Check box for G.I. Bill information.		
□ Veteran	On Active Dut	ty RE-53

FUNCTION GENERATOR KIT

Introductory Offer

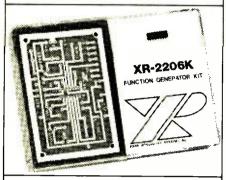

The Function Generator Kit features sine, triangle and square wave; THD 0.5% typ.; AM/FM capability.

XR-2206KA

Includes monolithic function generator IC, PC board, and assembly instruction manual.

\$19.95

XR-2206KB

Same as XR-2206KA above and includes external components for PC board.

\$29.95

MONOLITHIC IC'S

TIMERS		
XR-555CP	Monolithic Timer	\$1.10
XR-320P	Precision Timer	1.55
XR-556CP	Dual-555 Timer	1.85
XR-2556CP	Dual Timing Circuit	3.20
XR-2240CP	Programmable Counter/	
	Timer	4.80
PHASE LO	CKED LOOPS	
XR-210	FSK Demodulator	5.20
XR-215	High Frequency PLL	6.60
XR-567CP	Tone Decoder (mini DIP	1.95
XR-567CT	Tone Decoder (TO-5)	1.70
STEREO D	ECODERS	
XR-1310P	PLL Stereo Decoder	3.20
XR-1310EP	PLL Stereo Decoder	3.20
XR-1800P	PLL Stereo Decoder	3.20
WAVEFOR	M GENERATORS	
XR-205	Waveform Generator	8.40
XR-2206CP	Monolithic Function	
	Generator	5.50
XR-2207CP	Voltage-Controlled	
	Oscillator	3.85
OTHER EX	AR IC'S	
XR-1468CN	Dual ±15V Tracking	
	Regulator	3.85
XR-1488N	Quad Line Driver	5.80
XR-1489AN	Quad Line Receiver	4.80
XR-2208CP	Operational Multiplier	5.20

Satisfaction Guaranteed, \$5.00 Min. Order-1st Class Mail No Charge/ California Residents Add 6% Sales Tax

IAMES

P.O. BOX 822, BELMONT, CA. 94002 PHONE ORDERS - (415) 592-8097

Circle 69 on reader service card

TV TYPEWRITER II

(continued from page 63)

plugs and note that each of the connectors is indexed to allow them to be plugged in only one way. J10 and J11. however, are physically the same type of connector so use a felt tipped pen to mark one of the two sets to prevent yourself from inserting one of the plugs into the wrong jack. Try to keep all of the wires in the connector harnesses as short as possible and be sure the ground and +5v wires between the power supply and the main board are 18 gauge or heavier.

The power supply must be capable of supplying 5 Vdc, 2A at 5% regulation or better; -12 Vdc, 200 mA; and -5 Vdc, 15 mA. You can either build your own from scratch or purchase one from the source supplying the TV typewriter kits. You must make absolutely sure all of the power leads are wired correctly to the connector; otherwise you can cause a lot of damage when the power is applied.

Now its time to get out the television or monitor you plan to use. Although the actual modifications necessary will vary from set to set, the modifications shown will probably be satisfactory for most small screen transistor portables. The TV typewriter's output must be connected to the input of the television's video amplifier, which is located between the last video i.f. stage and the video output circuit. When you break the circuit right at the input to the video amplifier, you will probably have to provide a dc bias circuit for the stage since in most cases it is supplied by the now disconnected video i.f. amplifier. The circuit in Fig. 2 is for the Motorola 9TS-469 Q set used with the prototype. A switch and BNC connector were provided to allow either TV typewriter or normal television viewing.

A dc restoration circuit was also added to keep the screen intensity from changing as a function of the density of dots displayed.

Check the power supply to be sure the voltages are OK and that wiring to the connector is correct. Go back now to the main PC board and wire in the correct keyboard jumper. If your keyboard has a positive "keypress strobe" pulse, wire terminal 3 to terminal 1, and if it has a negative "keypress strobe" pulse, wire terminal 3 to terminal 2. These pads are just adjacent IC32 and are numbered on the top side of the board. If the keyboard has a 1 microsecond or less strobe pulse, either of the two positions will work properly.

Plug the "memory" board onto the main board using the set of connectors marked "memory." Be sure the top

SUPER BUYS!

FAMOUS MAKE, NEW . 80% OI	JOBBER-BOXED TUBES FF LIST
183 5 for \$5.00 1192 5 for \$3.95 24V2 5 for \$3.95 3A3 5 for \$5.05 3A12 5 for \$4.85 3HA5 5 for \$4.85 3HA5 5 for \$4.80 4B26 5 for \$4.70 5GH8 5 for \$4.70 5GH8 5 for \$4.70 5GH8 5 for \$5.05 6AY3 5 for \$5.05 6AY3 5 for \$5.05 6CG3 5 for \$4.70 6CG8 5 for \$4.75 6CG9 5 for \$4.75 6CG9 5 for \$4.75 6CH7 5 for \$4.75 6CH7 5 for \$4.80 6CH7 5 for \$4.95 6CH7 5 for \$4.50 6CH7 5 for \$4.75 6CH7 5 f	6HA5 5 for \$4.80 6HB7 5 for \$4.80 6HB7 5 for \$4.85 6HV5 5 for \$4.85 6HV5 5 for \$11.80 6JC6 5 for \$11.15 6JS6 5 for \$11.15 6JS6 5 for \$9.30 6JB8 5 for \$6.15 6KE8 5 for \$6.15 6KE8 5 for \$1.25 6KM6 5 for \$1.25 6KN6 5 for \$1.25 6KN6 5 for \$1.25 6LB6 5 for \$1.25 6LB
20-2.5 Amp. 1000 PIV (100-2.5 Amp. 1000 PIV (RCA DAMPER DIODES 12 4-6500 PIV FOCUS RECT. 5-13.5 KV FOCUS RECT. 25—1N34A—CRYSTAL E HEP 9001-DUAL DIODES	IR) \$3.00 (IR) \$11.95 10818 Ea \$1.50 \$2.00 \$3.00 DIODES \$2.00 CARDED 10 for \$2.98
AUDIO PHONO EQUIP. 10 RCA PHONO PLUGS . 5 Asst'd STEREO CART. BSR-SC5MD-EV5540D-Cart SONOTONE 8-T—Cart. (I BSR TC8S—Cart	
COLOR FLYBACKS MAGNAVOX 361461-2L RCA—136640 RCA—137545	
COLOR YOKES MAGNAVOX 361340 MAGNAVOX 361380-4 EQUIV. DY 95AC-Y109 (L SILVERTONE 80-56-4G JAP YOKE 70%—(21" CRT)	\$3.95 \$6.95 \$1.95 \$5.95 \$4.50 \$5.50
BLACK & WHITE YOKES THORDARDSON—Y-105 (I THORDARDSON—Y-130 Z	:
ANTENNA EQUIPMENT 2-Set Coupler 4-Set Coupler 6-ANT. CLOTHESPINS	Each ONLY \$1.49 Each ONLY \$1.89 \$1.00
ZENITH VOLTAGE TRIPLER—212- VOLTAGE TRIPLER—212- CONV. DIODE PAK—212	109Ea. \$4.95 136\$4.95 -722 for \$1.00
CONTROLS RESISTORS 50 Asst'd MALLORY CONT 50 Assorted W.W. Res 100 Assorted Carbon Res	ROLS \$2.59
CONDENSERS CANS 200-80-Mfd. 350V	
CEND FOR FRI	0474100

SEND FOR FREE CATALOG

TUBES UP TO 80% OFF MINIMUM ORDER \$15.00

SEND CHECK OR M.O.

TV TECH SPECIALS

P.O. BOX 603 KINGS PARK, L.I., NEW YORK 11754 PHONE 516-269-0805

Circle 70 on reader service card

side of the memory board faces in toward the main PC board. It must not be plugged on the other way.

Connect the power supply, keyboard and television to the main board and after making a final check for errors, apply power. If you haven't made any mistakes and have a little luck, the unit will work first off. The only adjustments are the oscillator frequency adjustment pot, R38, the left margin control, R4 and the horizontal character size control, R6. The phaselocked oscillator should lock in over most of the range of the control R38, but may vary from unit to unit. An out of lock condition will be indicated by a slight vertical roll and a litterey character presentation. The other two controls should be set to give the best

If the unit doesn't work, first check the power supply voltages to make sure they are OK and then use an oscilloscope to see whether or not there is a video output signal. If not, start checking from the phase-locked oscillator with your scope and try to locate the problem from there.

If you don't have any problems and everything seems to work correctly then go ahead and connect up the control switches. For maximum flexability the page-select switch, available at jack J10, should be a spdt center off switch; (continued on page 90)

WHAT SINGLE ELECTRONIC MACHINE CAN BE USED TO PERFORM/CONTROL ALL THE FOLLOWING TYPES OF SERVICES?

Send morse code

Control repeater stations

Operate as a calculator

Receive/send/buffer data between a wide variety of communication devices



Monitor instruments
Control machines
Sort/compile data
Test other devices
Play games

The SCELBI-8H MINI-COMPUTER can!

If you want to be really "state of the art" you should find out about the extraordinary flexible SCELBI-8H MINI-COMPUTER. This is a true digital mini-computer at a LOW price you may find hard to believe! It is all solid state and conservatively designed to provide years of service. It is a fully programmable machine.

We have a complete line of peripheral units availabe to use with the SCELBI-8H. Such is an interface that turns an oscilloscope into a complete alpha-numeric display system, low cost keyboard and TTY interfaces, and an interface that turns a low cost audio tape cassette unil into a "Mag-Tape" storage system.

In addition to the hardware we have a large selection of programs ready to "load and go." Programs such as Editors, Assemblers, Calculator packages, I/O routines for ASCII and Baudot machines and SCELBI interfaces, Data manipulating routines. Games, and more on the way!

Fully tested card sets for the SCELBI-8H start as low as \$399.00!* Complete computers (card set plus chassis kit) as low as \$529.00.* And for the real "do it yourself buffs" we now offer "unpopulated" p.c. card sets starting as low as \$109.00!* (*Domestic prices.)

Literature available by request:

SCELBI COMPUTER CONSULTING, INC.

1322 Rear—Boston Post Road, Milford, CT. 06460
Phone (203) 874-1573

Circle 72 on reader service card



WHAT'S AN "EBM"???

- # A new kind of electronics and electromechanical "encyclopedia" containing over a half-million words and more than a thousand charts, tables and circuit diagrams.
- # An applications handbook: from integrated circuits and electronic displays to hardware and gears.
- # Å "practices" manual covering soldering, painting, plating, wiring, construction, assembly, etc.
- # A reference handbook of data, formulas and tables including calculator operations.
- # A "high density" $^{\mathrm{T}}$ doc publication, packed with the equivalent of more than one dozen "paperbacks".
- # A looseleaf bench manual in a <u>rugged</u> polyethylene binder,easily expanded and up-dated.
- # A foundation-stone of the growing $^T\!$ doc system of guaranteed electronics publications.



Circle 71 on reader service card



RADIO-ELECTRONICS

88

DELUXE DIGITAL COLOR CONVERGENCE GENERATOR

NOW AT A PRICE EVERYONE CAN AFFORD

ROCK SOLID PATTERNS ALL IC COUNTDOWN CIRCUITS QUARTZ CRYSTAL OSCILLATORS 2 FULL YEARS' WARRANTY



MODEL SG-200

\$7995 reg. \$99.95

10 Patterns: Full & Gated Rainbow, 4 Crosshatch, 4 Dot, Die Casted 1/8" Aluminum Case.



MODEL SG-150

\$5995 reg. \$74.95

10 Patterns: B&W Bars, White Field, 4 Crosshatch, 4 Dot.



MODEL SG-100

ONLY **\$47**95 reg. \$59.95

2 Patterns: 20 x 16 Crosshatch, 320 Dots, weight only 17 oz.

SPECIAL PRICE LIMITED TIME ONLY **FULL 15 DAYS MONEY BACK GUARANTEE**

ELENCO ELECTRONICS INC. 8744 W. North Ter., Niles, III. 60648

312-825-3797

MODEL SG-

- My check or money order enclosed. COD-Add \$2.50 mailing & handling.

NAME

ADDRESS

STATE

ŽIP

DISTRIBUTORS' INQUIRIES INVITED

Circle 74 on reader service card

COSMOS BURGLAR ALARMS

(continued from page 35)

tion. Under this condition, the relay is de-energized and the alarm generator is off. The circuit consumes a typical standby current of 1-µA. The alarm can be activated by opening any one of series-connected sensor switches S3 or by closing any one of parallelconnected sensor switches S2. Under this condition, a positive-going transition appears on pin 2 of the monostable and its output switches into the high mode for a pre-set period and drives transistor O1 into conduction, thus energizing the relay and turning the alarm generator on. At the end of this period, the output of the monostable goes low again, independent of the states of S2 and S3, and the alarm generator turns back off. The circuit can then be reset either by opening and then closing S1 or by setting all S2 and S3 switches back to their original positions.

Note in the Projects 3 and 4 circuits, that power is permanently applied to the Q1-RY1 components, even when S1 is in the off position. This enables the alarm to be activated in the nonlatching mode at all times via a normally open temperature-sensing switch such as a thermostat, so that these circuits can also function as a permanently alert fire alarm system. Any number of normally open switches can be wired in parallel with S4.

A weakness of the Projects 3 and 4 circuits is that they give the owner no protection against intruders who may break into the house in daylight hours when the main alarm system is switched off. Protection against this type of intrusion can be obtained by scattering a number of series-connected normally closed 'panic' buttons around the house, so that a permanently-alert self-latching alarm system can be activated at any time. This facility can readily be added to the Projects 3 and 4 circuits. Project 5 shows how it can be wired into the auto-turn-off system of Project 4.

In Project 5, part of IC2 is wired as a simple bistable multivibrator circuit that is permanently connected to the supply lines. The output of the bistable is connected to the base of transistor Q1, via diode D2 and resistor R10, so that Q1, the relay and alarm generator can be turned on via the bistable. Diode D1 is wired in series with R5 of the main alarm system so that the two sections of the circuit do not interact adversely. The output of the bistable is normally latched into the low state, so the relay and alarm generator are normally off. If any of series-connected panic buttons S5 are momentarily opened, the bistable im-

FREE ALARM **SYSTEM CATALOG**





mountain west alarm 4215 n. 16th st. phoenix, az. 85016 (602) 263-8831

Circle 75 on reader service card

RGS ELECTRONICS

008A MICROCOMPUTER KIT

8008 CPU, 1024 x 8 memory; memory is expandable. Kit includes manual with schematic, programming instructions and suggestions; all ICs and parts supplied except cabinet, fuses and hardware.

Includes p.c. boards

MANUAL ONLY, \$25.00 (No Discount on Manual)

008A-C AUDIO CASSETTE ADAPTER KIT Kit includes all ICs, p.c. board, power supply, schematic and instructions. Will interface most audio cassette recorders to the 008A Microcomputer. NOT intended to interface with

any other computer. 008A-K ASCII KEYBOARD INPUT KIT

Kit includes keys, p.c. board, ICs, power supply, schematic and instructions. This kit is intended to interface ONLY with the RGS Electronics 008A Microcomputer **TRANSISTORS**

NPN General purpose TO-92 \$.08;\$5.95/100 PNP General purpose TO-92 \$.08.\$5.95/100 Other transistors and JFETS available at our usual low prices; all are tested, good units. Specs available in our flyer.

RGS ELECTRONICS, 3650 Charles St. Ste K. Santa Clara, CA 95050 (408) 247-0158

We sell many ICs and components not listed in this ad, included most of the 7400 series; send a stamp for our free flyer.

TERMS OF SALE: All orders prepaid; we pay postage on all U.S. orders. Handling charge of \$1.00 on U.S. orders under \$10.00, foreign orders under \$25.00. California residents please include sales tax. Please include name, address, and zip code on all orders and flyer requests. *DISCOUNTS: 10% OFF ORDERS OVER \$25.00 - 20% OFF ORDERS OVER \$250.

PRICES SUBJECT TO CHANGE WITHOUT NOTICE. Circle 76 on reader service card

mediately changes state and its output locks into the high state and drives relay RY1 and the alarm generator on. Once the alarm generator has been turned on, it can be reset to the OFF state by closing RESET switch S6.

This panic facility can be added to the Project 3 circuit by simply wiring diode D1 in series with R5, and adding IC2 and its associated circuitry.

Other points to note about the Project 3 through Project 5 circuits are as follows:

1. The relay used in each circuit can be any 12-volt type with a coil resistance of 180 ohms or greater, and with one or more sets of n.o. contacts.

2. Timing capacitor C2 of the Projects 3 through 5 circuits must have a reasonably low leakage resistance, otherwise the alarms may fail to turn off at the end of their pre-set periods. The best way to find out if the capacitor is suitable is to simply put it in the circuit and check that it works OK under operating conditions.

3. The three circuits can drive any types of alarm generators (bells, sirens, electronic generators, etc.) via the relay contacts RY1-1. Note, however, that these alarm generators must be operated from their own power supplies, otherwise they may interfere with the electronic functioning of the actual systems. (continued next month)

For faster service

USE ZIP CODE

> on mail

ELECTRONICS, INC.

RCA	ZENITH	
MAA001A MAB003A MAD001 MAL001B MAN002	9-83 9-87 9-88 9-90	\$ 5.95
	9-48 9-57 9-70 9-82 9-89 9-91 9-103 150-214	\$ 7.95
MAC002A MAC002B MAE001B MAG001B MAH001A	9-27 9-27X 9-69 9-86 9-92 9-97	\$ 9.95

THE LEADER IN TUNER SERVICE NOW OFFERS **FAST 8 HOUR**

MODULE REPAIR

IF-SUBCH.-MODULES \$12.50

1 YEAR GUARANTEE!

(Prices include all parts; shipping add.)

For fastest service, send faulty unit to:

PTS ELECTRONICS

"Precision Juner Service"



P.O. Box 272, Bloomington, Ind. 47401 • Tel. 812-824-9331

Circle 77 on reader service card


CMOS MICROLA

- * LEARN HOW DIGITAL CIRCUITS WORK
- * VERIFY DESIGNS QUICKLY
- * IDEAL TEACHING AID

The CMOS Microlab makes it possible to quickly check, or understand a variety of digital circuits. Battery operation makes the Microlab super convenient. Use it anywhere. Indicator lamps are all LED types that are rugged and will never burn out. Included in the Microlab are four (4) flip-flops, four (4) dual input NOR gates, four (4) dual input NAND gates, two (2) four input NAND gate and an inverter. No external signal sources are needed in most cases. Connections are made with reliable, easy to use push-on type connectors on the jumper wires. The entire instrument is "goof-proof". No possible combination of connections, no matter how wrong, can damage the circuit.

The kit is housed in a 5 x 7 x 3 break resistant impact plastic case. Powered by four (4) standard "D" cells. (Not included in kit)
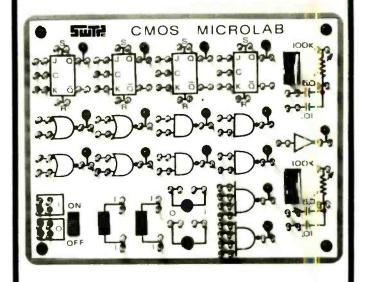
#CMOS Complete Microlab Klt......\$34.50 PPd






Southwest Technical Products Corp. 219 W. Rhapsody San Antonio, Texas 78216

THE NEW DIGITAL VOLKSMETER

World's lowest priced digital multimeter. Designed to be a more accurate replacement of delicate pointer-type meters.



LM-3

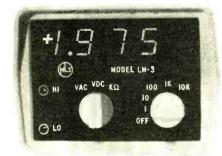

Features Include:

\$99.95

- Rugged ideal for field service use
- Auto polarity no more lead reversing or switching
- Three digits with 100% over-range and 1% accuracy on all functions
- 13 ranges: 4 vac, 4 vdc & 5 resistance
- 1 millivolt resolution with 500 volts and 20 megohms full scale
- Small Size: 1.9"H x 2.7"W x 3.9"D

Options Include:

- Rechargeable batteries with charger unit - \$15
- Leather case \$16
- High voltage probe \$30
- Current shunts \$6 each

Call our distributor, the G.S. Marshall Co., for more information.

For immediate delivery, fill in below and mail direct to NLS.

NON-LINEAR SYSTEMS, INC. BOX N, Del Mar CA 92014 PH (714) 755-1139 - TWX 910-322-1132

☐ Special offer of \$99.95 with your check and coupon. ☐ Single unit price of \$110 C.O.D. or valid purchase order.

One year guarantee.

Name		
Company		
Address		
OID.	Ch at a	7 to

California Residents Add 6% Sales Tax
Offer expires in 90 days
123 56789101112 * 23456789101112

Circle 79 on reader service card

TV TYPEWRITER II

(continued from page 87)

then when either of the two pages are selected, the cursor will always remain on the same page even when the end of frame is reached. In the center position, the cursor will alternately jump from one page to the other as the end of frame is reached. As with all of the other switch connections to follow, the inputs are all tied high with pull up resistors so all switching should be done by grounding the appropriate terminal.

The cursor on/off terminal, available on jack J10, if left unconnected will always cause the cursor to blink in the next character position to be typed. However, the blinking cursor may be turned off at any time by grounding the "CURSOR ON/OFF" pin on jack J10.

For maximum manual cursor control, the optional cursor control board should be used, however, the home-up (move cursor to upper left hand corner), erase to end of line (EOL) and erase to end of frame (EOF) are available at the pins to be used for the cursor control board. Temporarily grounding pin 10 of IC9-b will generate an erase of end of line, and temporarily grounding pin 4 of IC2-a will generate and erase to end of frame and grounding pin 12 of IC32-d will force a "home up."



Circle 81 on reader service card



12 REASONS YOUR CAR NEEDS TIGER CDI

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration and performance - Spark plugs last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - An Unconditional LIFETIME GUARANTEE Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State Ignition made.

SATISFACTION GUARANTEED or money back

TIGER 500 assembled \$53.95 TIGER SST assembled \$42.95 Post Paid in U.S.A.

Send check or money order with order to:

Tri-Star Corporation

P. O. Box 1727 B Grand Junction, Colorado 81501

DEALER INQUIRIES INVITED

Circle 80 on reader service card



Our 23rd year of service to the World's finest craftsmen and technicians.

A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.



Circle 82 on reader service card

next month

MAY 1975

■ Understanding Tape and Bias

Matching the bias to the tape and getting it right will improve the performance of any tape recorder. See why it works and how to do it.

■ Electronic Ignition — 1975

A study of several of the latest circuits and how they work.

■ Servicing MATV Systems

Finding a fault in an MATV system isn't alway's easy. But there are ways to speed the job. Let an expert show you how.

■ Using The Curve Tracer

Final installment shows how to test semiconductors with a curve tracer, and what the results mean.

■ New Power Supply Kits From Heath

Eight new power supplies, in kit form. Four with digital readouts, 4 with analog meters. See how they work and what you can use them for.

PLUS

Equipment Reports

Jack Darr's Service Clinic


Radio-Electronics Replacement
Semiconductor Guide

May issue goes on sale April 17, 1975

Put Professional Knowledge and a

COLLEGE DEGREE

in your Electronics Career through

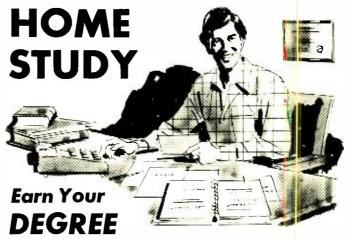

by correspondence, while continuing your present job. No commuting to class. Study at your own pace. Learn from complete and explicit lesson materials, with additional assistance from our home study instructors. Advance as fast as you wish, but take all the time you need to master each topic. Profit from, and enjoy, the advantages of independent study.

The Grantham correspondence degree program in electronics is comprehensive. It begins with basics, written in very simple language, and continues through the B.S.E.E. degree level. Throughout the entire program, heavy emphasis is placed on clear explanations written in great detail, progressing from the simple to the complex, in easy steps.

Our free bulletin gives complete details on the curriculum, the degrees awarded, the requirements for each degree, and how to enroll.

GRANTHAM SCHOOL OF ENGINEERING

2000 Stoner Ave., Los Angeles CA 50025

● Telephone (213) 477-1901 ●

Worldwide Career Training thru Home Study
Mail the coupon below for free bulletin.

Grantham Schoo 2000 Stoner Ave.,		
I have been in electronail me your free bul cerning your electron	letin which gi	ves details ::on-
Name		Age
Address		<u> </u>
City	State	Zip

INVENTORY DISCOUNT SALE

□ RCA COLOR BAR GENERATOR

- with basic patterns
- with AC and battery power supply

Reg. Price \$89.90

Our Price \$69.50



☐ CASTLE MEZZER Field Strength Meter

\$119.95 **Our Price** \$102.00



Model ESM-V

CASTLE TUNER SUBBER MARK IV Reg. Price \$45.95 Our Price \$36.50

☐ SOLDERING IRON 30 WATTS Pencil type _____\$1.95

LARGE DISCOUNTS ON **ALL TEST EQUIPMENT**

Free Catalog of Each Manufacturer

HICKOK BIJ

नामग

SENCORE

RCA

TUBES ICC/International Servicemaster

1B310 for \$11.00 1K310 for \$11.00	6EH710 for \$10.50 6EJ710 for \$10.00
1V210 for \$ 6.50 2AV210 for \$ 9.00	6JC610 for \$12.50
2AV210 for \$ 9.00 3A310 for \$11.00	6JE610 for \$25.00 6KD610 for \$25.00
3AT210 for \$11.00	8CG710 for \$ 8.50
6BK410 for \$20.00 6CG310 for \$11.00	17BF1110 for \$17.00
6CG710 for \$ 8.50	17JZ810 for \$10.00 23Z910 for \$13.00
6DW410 for \$10.00	33GY710 for \$18.00
GEA810 for \$11.00 ☐ GGH82 ☐	38HE710 for \$20.00

Complete line of RCA and Raytheon tubes also

İ	PARTS
ı	☐ Replacement Rods,
ı	4 Sections, Extending to 38"12 for \$9.00
ı	☐ Varco Cartridge; CN75, TN4Beach \$1.95
ı	☐ BSR Cartridge; SX1H, 5X5Heach \$1.75
ı	☐ Electrical Tape, ¾" x 66'10 rolls for \$4.99
ı	☐ Telematic CR 250 90° Color Booster5 for \$20.00
1	☐ Thordarson Y94, Y105, Y130each \$9.00
ł	25 ft. Speaker Cable
ı	RCA Plug to RCA Plug4 for \$3.90
ı	Speaker; 6x9, 10 oz., Cloth Rolleach \$4.95
1	☐ 6x8 Grilleeach \$.69
1	☐ AC Adapter; 6, 7, 5, 9V, 300maeach \$3.95

FREE CATALOG

Minimum order \$50.00. Send check or money order.
Add \$1.00 for shipping and insurance.

RADIO SUPPLY CO., INC. 558 Morris Ave., Bronx, N.Y. 10451 Tel: (212) 585-0330

new lit

All booklets, catalogs, charts, data sheets and other literature listed here with a Reader Service number are free. Use the Reader Service Card inside the back cover.

COMMUNICATIONS EQUIPMENT CATALOG. 30-page catalog has four sections: CB, marine, scanning monitor and business/ industry. Each section includes 2-way communications for Citizens radio service operations, scanning receivers for monitoring emergency broadcasts and other 2-way radios for business and marine use. Contains many illustrations, detailed specifications, a list of accessories and prices. -Pace Communications, 24049 South Frampton Avenue, Harbor City, CA 90710.

Circle 39 on reader service card

COMPONENTS CATALOG, 36-page catalog lists IC's, linear IC's, semi-conductors, hybrid audio amplifiers, keyboards, capacitor kits, transformers, panel meters, breadboarding devices, switches, connectors, adapters, power panels and strips and much more. Prices are listed as well as photographs. Order form is in middle of catalog. -K A Electronic Sales, 1220 Majesty Drive, Dallas, TX 75247.

Circle 40 on reader service card

ELECTRONIC INSTRUMENTS CATALOG. 36page catalog describes frequency counters, auto ranging counters, multimeters, portable volt-ohm meters, vtvms, oscilloscopes, solidstate oscilloscopes, subtitution boxes and accessories, function generator, TV alignment generators, audio and sine/square wave generators, high and low voltage supplies, reference and low voltage supplies, programmable chart recorders, record and modules, modules and accessories, lab stations, digital designers, plug-in circuit cards and ph meters. Many illustrations and prices.—**Heath Co.**, Benton Harbor, MI 49022.

Circle 100 on reader service card

TEST EQUIPMENT CATALOG 60-T. 16-page catalog contains full range of the company's products from general multi-purpose vom's through laboratory and special feature testers to general purpose portables, temperature testers and accessories. Features two new vom's-model 310, type 3 and model 615. Prices are given for all test equipment and accessories. Also contains a selection guide chart designed to help select a tester for specific requirements.-Triplett Corp., Dept. PR, Bluffton, OH 45817.

Circle 42 on reader service card

PRODUCT SELECTION GUIDE. 11-page catalog describes, illustrates and lists principal specifications for the company's current products. Prices are included. Contains 43/4digit multimeters, 10-MHz oscilloscope and modified static card readers with interface electronics along with other equipment.-Hickok Electrical Instrument Co., 10514 Dupont Avenue, Cleveland, OH 44108.

Circle 43 on reader service card



The Pencil Soldering Iron with Operating Light, 2 Heats and On/Off Switch

\$10.95

Aodel 540S Soldering Iron Length 81/2" Weight 2 oz.

- Light shows when it's on
- 2 heats-20w and 40wfor any job
- · Ironclad tips for longer life
- Cool, unbreakable polycarbonate handle
 - Burn-resistant neoprene cord
 - Converts to a desoldering iron with low cost attachment



- · Light shows when it's on
- Operates at 40w; idles at 20w for longer tip life
 - 8 tip sizes available to handle any job
- Cool, unbreakable polycarbonate handle
 - Burn-resistant neoprene cord
 - Exclusive new bracket insures alignment, prevents damage

New kits also available!

 Soldering Kits
 Desoldering Kits Soldering/Desoldering Kits

To locate your nearest distributor call toll-free 800-645-9200



Circle 85 on reader service card

new books

COLOR TV TROUBLE FACTBOOK, Second Edition, by the Editors of Electronic Technician/Dealer. TAB Books, Blue Ridge Summit, PA 17214, 348 pp. 8½ x 5¼ in. Hardcover \$8.95.

This book contains an indexed reference guide to color set troubles and recommended solutions. Manufacturers' service notes and production-change data are all numerically arranged by manufacturer and model. Service tips, troubleshooting data and special problem-solving aids for all the more popular U.S. and Canadian makes and models are included.

Of particular importance are the many model production changes not likely to be documented in manufacturers' manuals. This book contains a detailed accounting of such changes where they might logically affect set performance and where the service technician might replace a factory component with an unsuitable substitute.

The practicing TV service technician should be able to save many hours of troubleshooting time using this guide book. A complete cross-reference index is provided to put all the information at the reader's fingertip for easy and fast access. In all, over 600 specific items are included.

PHOTOFACT TELEVISION COURSE, Fourth Edition, by the Howard W. Sams Editorial Staff. Howard W. Sams & Co., Inc., 4300 West 62nd Street, Indianapolis, IN 46268. 208 pp. 10³/₄ x 8¹/₄ in. Softcover \$6.95 (in Canada \$8.35).

This book is a complete course in black-and-white television. Step-by-step and supported by numerous schematics, the text describes the functions of important circuits.

Television principles, operations and servicing procedures are covered in depth. Included is an extensive glossary of terms, questions and answers and exercises. If you are just entering the field of television servicing or engineering, this book should prove invaluable. Experienced television technicians will find it a useful, authoritative reference source.

TRANSISTOR SUBSTITUTION HANDBOOK NO. 14, by the Howard W. Sams Engineering Staff. Howard W. Sams & Co., Inc., 4300 West 62nd Street, Indianapolis, IN 46268. 152 pp. 10³/₄ x 8¹/₄ in. Softcover \$2.95 (in Canada \$3.75).

This latest edition contains easy-to-read large type. The transistors are arranged in numerical and alphabetical order. Types recommended by the manufacturers of general purpose replacement transistors are included at the end of each list of substitutes. Additional data on these general-purpose replacement types, the manufacturer, the polarity, the material and the recommended applications are also included.

This is a valuable source of information for anyone concerned with transistor replacement, industrial, commercial or home-entertainment devices.

TV BENCH SERVICING TECHNIQUES, by Art Margolis. TAB Books, Blue Ridge Summit, PA 17214. 227 pp. $8\frac{1}{2}$ x $5\frac{1}{4}$ in. Hardcover \$7.95; Softcover \$4.95.

The text explains the setup of a typical efficient shop, outlines shop repair methods and provides troubleshooting procedures for each section of color and black & white receivers.


Assuming only a basic knowledge of electronics on the part of the reader, the book examines the basic operation of tube-type, solid-state and modular receivers and tells how to cope with the fundamental inherent characteristics of each type—from a troubleshooting standpoint. Also included are detailed instructions for picture-tube tests and repairs and color setup adjustments, including purity, convergence and high voltage.

THE COMPLETE SHORT-WAVE LISTENER'S HANDBOOK, by Hank Bennett. TAB Books, Blue Ridge Summit, PA 17214. 288 pp. $8\frac{1}{2}$ x $5\frac{1}{4}$ in. Hardcover \$9.95; Softcover \$6.95.

For those persons searching for an extremely interesting and exciting hobby, this handbook will introduce them to short-wave listening. It is very easy to read and understand, even for those who know nothing about electronics or the art of tuning in distant stations.

This book is designed to acquaint the reader with the basics of the SWL hobby. It covers receivers, antennas, frequencies, radio-wave propagation, harmonics, Q codes, where to tune for various type signals, how to keep a log book and how to prepare and send reception reports. It contains a thorough guide to stations of the world by general continental area and frequency.

grabber grabber

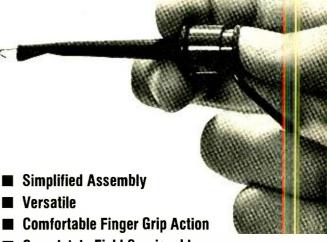


Model 3925 Mini Test Clip Shown Actual Size

■ Completely Field Serviceable


Molded of Tough Lexan*

Model :
Shown

This test clip with gold plated hook is excellent for rapid testing of components and Wire Wrapt pins. Clip is completely insulated to point of connection. Build any combination of test leads with wire up to .090 dia. Easy and comfortable to operate. Molded of rugged Lexan to resist melting when soldering. Write for literature and prices.

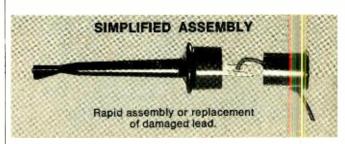

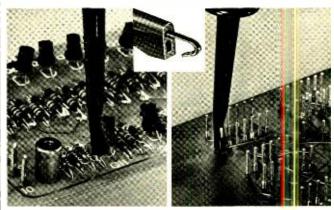MODEL 3925
hooks onto components or slips over square Wire-Wrap pins



Lexan is a General Electric trade-mark | †Registered trade-mark of Gardner-Denve Co AVAILABLE ONLY THROUGH ELECTRONIC PARTS DISTRIBLTORS

POMONA ELECTRONIC'S

A Division of ITT

1500 East Ninth St., Pomona, Calif 91766

Circle 86 on reader service card

Cut out this coupon and you may cut out a new career as a two-way radio technician.

Take advantage of the growth in electronic communications. Become a two-way radio technician. The need for qualified people has never been greater and opportunities are nationwide. Thousands have increased their knowledge of two-way radio through the 40-Lesson MTI home-study course.

Simply fill in this coupon and mail it to us. We'll send you information on how you can learn more about this specialized field, at home.

I am interested in cutting out a new career as a twoway radio technician. Please send full details of the MTI course.

Name______Address______City/State/Zip______

☐ I am a veteran or serviceman



MOTOROLA TRAINING INSTITUTE

103 College Hill Road, Summerdale, Pennsylvania 17093

Circle 87 on reader service card

ENJOY OLD RADIO-TV

A FLICK OF THE SWITCH your new 1930-1950 book



A FLICK OF THE SWITCH is your time trip through the golden days of radio broadcasting and into the dawn of television. Revisit "cathedral" radios, old Ham days and many more. Discover the rewards of collecting. Over 1,000 pictures make this book the 1930-1950 collector's reference. Order your copy of this 260-page book now! \$9.95 hard-cover, \$6.95 handbook.

Other valuable books are Vintage Radio (1887-1929) \$7.95 hard-cover, \$5.95 handbook; Radio Collector's Guide (1921-1932) \$4.95; 1927 Radio Encyclopedia \$12.95 hard-cover, \$9.95 soft-cover; 1926-1938 Radio Diagrams \$7.00. Also, we'll furnish any pre-1951 diagram for \$3.50.

Send today to Vintage Radio, Dep't R, Box 2045, Palos Verdes Peninsula, CA., 90274. Postage Paid. Cal. residents add 6% tax.

\$_	
\$	Vindogel Ad
 \$	
TOTAL	

Name ______Address_____

FREE Radio Age Guide with each order FREE

VINTAGE RADIO SERIES

CLINIC QUESTIONS

(continued from page 76)

DELAYED INSTANT-ON

The sound comes on instantly, in this RCA CTC-62. Owner says that the picture used to come on instantly, too. Now, it takes from 20 to 30 seconds to light up. Plays perfectly after it comes on. Only thing wrong is that it won't "Instant-On" any more. I'm lost.—G.C., Shreveport, La.

If the set works perfectly after it does light up, it's OK. In this chassis, the horizontal oscillator is left on, at reduced voltage, all the time. (See circuit in **Radio-Electronics** Dec. 1973, page 38.) The INSTANT-ON switch does not turn the dc voltage supply off, but it apparently "turns it down." The OFF-ON switch, in ON position, connects the ground side of the ac line to ground. The hot side stays connected at all times.

IN OFF position, the ground side of the ac line goes to ground through the degaussing coil and a thermistor, and a 2.7-ohm resistor. Since nothing is wrong but the Instant-On, this circuit must be open. Degaussing coil unplugged, etc.

INTERMITTENT FUSE-BLOWING

The 6146 tube plates get red hot and the fuse blows, in this high-powered RCA amplifier. It's used in a PA/communication system. No dead shorts, no shorted tubes. Any suggestions will be very welcome! It's intermittent!—W.J.M., Phoenix, Ariz.

Most likely cause for the kind of intermittent fuse-blowing you've got here would be intermittent failure of the bias supply for the 6146 output tubes. This is a fixed bias, coming from a tap on the power transformer secondary, through a diode restifier and filter, and probably through a variable resistor for adjustment. You could have an intermittent filter capacitor, a wire-short to ground, or something like that. Look for possible shorts where the bias lead crosses sharp metal edges; I had one of those not too long ago.

PALE PICTURE, POOR AGC

I've got a very pale picture, and odd agc action on this Truetone 2DC3916. No snow on the screen without antenna. I subbed the tuner; no help. I.f. tubes check OK. Voltages good. What's doing this?—M.D.O., Mena, Ark.

Pull the 8JV8 video output tube. Read the resistance from the control grid to ground. Reverse the ohmmeter prods. You should have a fairly low resistance; 150 ohms or so, one way and a high resistance, 3000 ohms or more, the other. If you read about 10 ohms one way and 30 ohms the other, the video detector diode is leaking. This is inside the last i.f. can, and it's not easy to get at. Use one of the small glass 1N60's; nothing else will fit.

HV REGULATION

I can't adjust the high voltage, on this Zenith, 6Z8C50 chassis. Here are the voltages I got around the 6HV5 high-voltage regulator. What do you think it is?—O.W., Hatfield, Ark.

I think your regulator isn't regulating! Note that grid voltage. You have +200 volts, and you ought to have +350. The cathode voltage is OK, at +390. So, the regulator grid is about 150 volts farther negative than it should be. This tube is cut off completely; it isn't conducting. Check some resistors, and possibly that VDR. One of them must be away off value.

SLOW FOCUS?

It takes about 5 minutes for this RCA CTC-15 to come into focus. This isn't normal, is it?—A.G., Oakland, N.J.

Nope. My CTC-15 comes on, focused, in 30 seconds. You have one of two possibilities; either the focus or the high voltage is a little slow warming up. Focus voltage must be a percentage (about 20%) of the high voltage at any given time. Read both focus voltage and the high voltage at turnon, and you'll know where to look.

OUND LAR

FREE \$1 BUY WITH EVERY 10 YOU ORDER Only applies to "\$1" Buys

FREE GIFT WITH EVERY ORDER

CANADIANS: Ordering is easy-we do the paperwork-try a smal order

RCA 110° FLYBACK TRANSFORMER

We scooped the Market. Latest type —
standard for all 110°

TV's (Blk. & Wht.).

RCA's design of large
Coil produces 18KV—
assuring adequate
width Irel. Schematic

WESTINGHOUSE ALL TRANSISTOR HOME/OFFICE **MESSAGE CENTER**

Built in speaker/

	SHANNON MYLAI	R RECORDING TAPE
31/4 ⁴ 5" 5"	225'	
	— 1200'	3" TAPE REEL09 31/4" TAPE REEL12 5" TAPE REEL29

width Incl. Schemation		Records up to 3 5" — 1800'	
for any TV. List price \$13.90 39	Control adjusts at	1.32 31/4" TAPE REEL	
Your price	BRAND NEW SOLD AS IS		1.99 5" TAPE REEL
	KLEPS "CLEVER" TEST PRODS	CUD LICUTE	MARKET SCOOP COLUMN
110° TV DEFLECTION YOKE 495 for all types TV's incl schematic "COMBINATION SPECIAL" 695	"Third-hand" test prods, reach into out of way places - Insulated - cannot	SUB-LIGHTS A safe decorative lighting system	CO-AX CABLE RG59U (Blick) 269
RCA 10° FLYBACK plus 110° DEFLECTION YOKE	slip - accommodates bare wire or banana plug—no soldering.	turns aquariums into underwater wonderlands.	IC4 and IC3 Integrated Circuit Used in Scott—Fisher etr.
90° FLYBACK TRANSFORMER 295	PRUF IO- QQc	Complete Sub-Light Kit contains 12 bulbs, Hanger assy., Suction cup,	15—ASSORTED IC'S For Experimenters
for all type TV's (Blk. & Wht.) 90° TV DEFLECTION YOKE 395	KLEPS 10— 139	Telescoping channel guide.	Silicon NPN HV TRANSISTOR
for all type TV's (Blk. & Wht.)	Boathook Clamp 4¾" long 149	Add. Sub-light available 6⁹⁸ Red, Blue, Clear	RCA—SK-3021—Hep-240 RCA—SK-3026—Hep-241
for all type TV's (Blk. & Wht.) 70° TV DEFLECTION YOKE for all type TV's (Blk. & Wht.)	Boathook Clamp 7" long 179	TRANSISTOR RADIO	Transister Specials—Your Chrice SK3006, SK3018, SK3020 100
for all type TV's (Blk. & Wht.) OLYMPIC & SHARP FLY-	flexible-forked Tongue 6" long 1 KLEPS 40 FLEXIBLE-PC 259	asst type good, bad, broken. 150	SK3122, SK3124 = a. Transistor Specials—Your Cioice 198
Stancor #HO-408— Thorderen #Ely220	Board Terminals 61/4" long 2 KLEPS I-ECONOMY Where for Light Work	TAPE RECORDER	SK3009, SK3024, SK3040
Thordarson #Fly339 90° COLOR YOKE For all	Kieps for Light Work	broken, as-is, potluck	cathode or Series connected 250
Color CRT's 795	Used in solid state application 100	200 ASST. ½ W RESISTORS Top Brands, Short Leads, 100	2-ELECTROLYTIC CONDENSERS Axial leads- 100
70 COLORE YOKE For all round color CRT's 895	VU I" PANEL METER 129	Excellent Selection 75—ASST 1/4 WATT RESISTORS 100	1000 Mfd — 25V
DELMONICO NÍVICO COLOR 795 FLYBACK Part # A20411-B	250—ASST SOLDERING LUGS 100 best types and sizes	stand, choice ohmages, some in 5% 100—ASST 1/2 WATT RESISTORS 100	most useful assortment #1 4 — TV ALIGNMENT 700LS 149
CADVEC TADZIAN TILNED	250—ASST WOOD SCREWS 100 finest popular selection	stand, choice chanages, some in 5% 170—ASST I WATT RESISTORS 100	For Color TV #2
SARKES TARZIAN TUNER	250—Asst Self Tapping SCREWS 100	stand, choice ohmages, some in 5% 100	TOOLS Most popular tyre
41mc	100—ASST 6/32 SCREWS 100—6/32 HEX NUTS 100	stand, choice changes, some in 5% 100 50—PRECISION RESISTORS 100	TV TWIN LEAD-IN 300 ohm 500'—\$7 100'—\$1.56. 50'
Latest Compact	100—ASST 8/32 SCREWS 100—8/32 HEX NUTS	asst. list-price \$50 less 98%	200 GREY SPEAKER WIFE 200 2 Cond. mini zip. 101 uses
Model good for all 41 mc TV's.	100—ASST 2/56 SCREWS 100 and 100—2/56 HEX NUTS	RESISTORS, 5, 10, 20 watt	WAHL-CORDLESS SOLDER IRON Complete with Auto 1095
BRAND NEW —	100-ASST 4/40 SCREWS 100	SPST, SPDT, DPDT, etc. 1 25—SYLVANIA HEAT SINKS 100	IRON Complete with Auto Charger - Fast Heating - Loc pact 1995 5—Audio Output TRANSFORM 100
	and 100—4/40 HEX NUTS 100—ASST 5/40 SCREWS and 100—5/40 HEX NUTS 100	For Transistors 20—ASSORTED TV COILS 100	Sub-min for Trans Radies 100
	500—ASSORTED RIVETS most useful selected sizes	I.F. VIDEO, sound radio, etc	456-kc for Transistor Radio
Best TUNER "SARKES TARZIAN"	300 ASSORTED WASHERS 100	200/300/100/100 MFD-25V	Top quality Special buy 12" UNIVERSAL SPEAKEII Top Quality Large Mas et
ever made — last word for stability, definition & smoothness of operation.	most useful selected sizes 100—ASST RUBBER BUMPERS 100	I—ELECTROLYTIC COND 100 MFD—300V 100 100 100 100 100 100 100 100 100	Top Quality Large Mag let 395
An opportunity—to improve and bring your TV Receiver up-to-date. 795	for cabinet bottoms—other uses 100—Asst RUBBER GROMMETS 100	20/20 MFD-450V	Top Quality Large Mag let 3
Complete with Tubes	best sizes 15—DIPPED MYLAR CAP. 100	2—ELECTROLYTIC Condensers 100/75 mfd-300 V, 70 mfd-25 V 100/75 mfd-300 V, 70 mfd-25 V 100 Mfd-25	Large Magnet—Special Buy 2 3" UNIVERSAL TWEETER 129
WESTINGHOUSE FM TUNER 399	15—01PPED MYLAR CAP. 100	2—ELECTROLYTIC Condensers 300 infd-200V, 100	1 oz Magnet
WESTINGHOUSE FM TUNER 100	15-DIPPED MYLAR CAP. 100	300/60 mfd-150V 4—ELECTROLYTIC COND 100	2½"x4" SPEAKER Special Buy 10 for \$5 EA. 69° 4"x6" "QUAM" 16 OHM SFK.
UHF TUNER—Transistor Type 395	0033-1000V 15-DIPPED MYLAR CAP. 100	ELECTROLYTIC CONDENSERS 100	Large magnet Special Bi Y 179
G.E. UHF TUNER-TRANSIS- 295	15—Molded Tubular Capacitors 100	200/200 mfd.—200V 100 100 100	UTAH 8"—HEAVY DUTY 0 OZ. 450 SPEAKER Ceramic Type—Ohm
ADMIRAL TY TUNER	15—DIPPED MYLER Condensers 100	ELECTROLYTIC CONDENSER 100	
Model #94C393-1 (2HA5-4LJ8) 795 Model #T94C441-3 (Transistor)	0039 400V	2—ELECTROLYTIC CONDENS- 100	Ceramic Type 8 Ohm 795
PHILCO TV TUNERS Model-76-13983-3 (5GJ7-3HQ5) 495	TACHOMETER 21/4" Sq. Panel Meter 1-VDC, full scale 33 Ohm 200	ERS 80/100/60 MFD—160V 100	3 SPEAKER—7 WAY SELECTOR 100
#7A 120-1 (4GS7-2HA7 Tubes)	I—CASSETTE type dynamic Mike 299	200/30/4—mfd—350V 3—ELECTROLYTIC COND 100	SWITCH Wall Mount STEREO MICROPHONES 650
G.E.—TV TUNER (2GK5-4L/8) 795 Model #EP 86x11	10-SETS PHONO PLUGS & 100	100 mfd.—100 V. 50 mfd.—75 V 100 mfd.—75 V 100	STEREO MICROPHONES FL 1979/01 Made in Holland SET 650 CONVERGENCE RECTIFIER—
PHILCO UHF/VHF TUNER 995		40 mfd—500V, 40 mfd—400V 100 5—AC LINE CORDS 100	For COLOR TV 4 Cell— Used in RCA—Philco, etc. 100
GE TV TUNER ET 86x196, (6GK5-6BL8)	8-MINI PILOT BULBS With 8" Leads-6.3V 30MA (5000 Hrs) 100 8-MINI PILOT BULBS With 12" 100	Approved 6' 100 4-50' HANKS Hook-Up Wire 100	Replace RCA part #120818 \$2.29
UNIVERSAL TV Antenna Back of 299 set mounting 5 section rods 299	Leads—6.3V, 150MA (5000 Hrs.) 1 32'—TEST PROD WIRE 100	assorted colors	COLOR POWER TRANS.
BLUE LATERAL Magnet Assy. Replacement for most color TV's 179	DELUXE QUALITY red & black 1 10—MINI ELECTROLYTIC Cond 100 For Transistor & miniature work 1	KNOB SPECIAL 100—Assorted RADIO KNOBS 100	Good for most sets 26R150 List Price—\$36.75
Universal type—good for most sets 249	— 101 11411111101 & 111111111111111111111	All standard types \$20 value	Model FT425 198
COLOR-TV RECTIFIER—Used in most color sets—6500 kv 3 for 195	With plug & volume control	POPULAR TYPES Mostly Selector & Fine Tuning 100	(Tests fuses, heaters, lamps, Etc.) ↓ VARCO Stereo Cartridge C ♥-72
2 COLOR-TV CRT SOCKETS Wired leads, for all color TV's 100	TUBES 100	20—Vertical Linearity KNOBS Long shank Front mount 100	With mounting bracket, f ipover 295 needle
Wired leads, for all TV's 100	10—ASST DIODE CRYSTALS 100 1N34, 1N48, 1N60, 1N64, etc. 100	assortment 20—Vertical Linearity KNOBS 100	RONETTE Stereo Cartridge 200 latest dual sapphire flippire type
RMS-9 ELEMENT COLOR	6-Top Brand Silicon RECT. 1000 PIV 1000 PIV	Side mount Standard sizes 25—Knurled Shaft KNOBS 100	Stereo Headphones Hi-Fi Quality Complete with Stereo p ug
Model HA-9 VHF/UHF 4—Polarized CHEATER CORD 100	5—PNP TRANSISTOR 100	Hard to get. Best selection 25—Clock & Radio KNOBS 100	DIO-STANDARD TRANSISTORS 100 NPN & PNP 2N404, 2N41, etc.
Grey	general purpose, TO-5 case 100	most popular types ANY 6 KITS FOR \$5	25' Shielded MIKE CABLE 189
BRIGHTNER	general purpose, TO-5 case 25—ASSORTED TRANSISTORS 100	Test Equip. Special Discount Prices	MERCURY COMPACT TUBE
90° COLOR TUBE BRIGHTNER 2—Colorburst Quartz-Crystal 189	big factory scoop—sold as-is		sized Speca Saver Full sized in performance 4995
For most color TV sets 3579.545 KC	Excellent for hobbyist 2—ELECTROLYTIC CON- 100	Bin Taldin	TELMATIC Tuner-Mate KT-730
Popular replacements for most COLOR TV 100	DENSERS Axial leads—500—25V KANDU—Printed Circuit Kit		Portable "Substi-Tuner"— Instant Tuner Check TELEMATIC Test Jig Model— 4250
UHF or VHF Matching Trans. Simple Fool-proof installation	Trace & Etch your own circuits—95 easy to use instructions	SENCORE	EJ-190—Master Rigs— Combo Rigs—Econo Rigs 4995
IMMEDIATE DELIVERY , Scientific light p	acking for safe delivery at minimum cost.	You offers will be returned in	Minimum 0 'der \$5.00
HANDY WAY TO ORDER Send check or my Please specify refund on shipping over		TAGE STAMPS MERCHANDISE (our	choice) with advantage <mark>to pu</mark> stomer

BROOKS RADIO & TV CORP., 487 Columbus Ave., New York, N.Y. 10024 TELEPHONIC 212-874 56:00

APRIL 1975

NEW! Build your own Circuits & Save with VeroBoard kits



Simple and easy to use - no etching or drilling. The BK-6 kit contains six assorted VEROBOARDS, two with 0.2x0.2 matrix and four with 0.156x0.1 matrix

\$8 95

The BK-P15 contains 15 assorted boards from a mini 1"x2½" to a maxi 3¾"x5". Eight boards have 0.1x0.1 matrix with 0.52 and 0.40 diameter holes and seven with 0.15x0.15 matrix. This kit contains a complete set of terminal pins

All kits include a spot face cutter and easy-to-follow instructions

VEROBOARDS are made of quality synthetic resin bonded paper laminate, copper clad on one side with a Build any circuit in three easy steps



2. Insert and solder components, 3. Use precision spot face "See Veroboards at IEEE Booths 1718-1720"

cutter supplied to remove

Kleps 10 - 20

Kleps 30

Kleps 40

Kleps 1

SEND CHECK OR MONEY ORDER N.Y. RESIDENTS ADD SALES TAX

Vero Electronics, Inc.

171 Bridge Road, Hauppauge, N.Y. 11787 Tel.: 516-234-0400 TWX: 510-227-8890

Circle 89 on reader service card



Clever Kleps

Test probes designed by your needs - Push to seize, push

Test probes designed by your needs — Push to seize, push to release (all Kleps spring loaded).

Kelps 10. Boathook clamp grips wires, lugs, terminals.

Accepts banana plug or bare wire lead. 434" long.

Kleps 20. Same, but 7" long.

Kleps 30. Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long.

Kleps 40. Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins.

Accepts banana plug or plain wire. 6\forall "long.

\$2.59

Kleps 1. Economy Kleps for light line work (not lab quality).

Meshing claws. 4\forall 2" long.

\$9.99

Pruf 10. Versatile test prod. Solder connection. Molded

Pruf 10. Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5½" long. All in red or black - specify. (Add 50¢ postage and handling).

Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

RYE INDUSTRIES INC.

128 Spencer Place, Mamaroneck, N.Y. 10543 In Canada: Rye Industries (Canada) Ltd.

Circle 90 on reader service card

BUILD A TICK TIMER

(continued from page 41)

over-tighten the mounting screws and make certain there are no sharp ends of the screen wire extending inwardly, to poke through the speaker cone. Locate the board assembly with its potentiometers toward the side of the cabinet, rather than toward the center, to make them easily accessible. Be sure there is sufficient clearance to prevent short-circuiting the potentiometer bodies to the metal cabinet, when the back/sides part is slipped into place.

Calibration

When the unit has been completely assembled, and checked for possible errors, turn switch S1 to OFF and install the battery. An ordinary transistor battery will suffice for casual operation of the timer, but if you contemplate using it often or for long periods, an alkaline battery such as the Mallory MN1604B, will give better service.

Set potentiometers R1 and R6 at maximum resistance in the circuit. Set potentiometer R4 at about mid-position, and potentiometer R8 at the grounded end of its rotation. Turn switch S1 to on, and after a brief pause, ticks should be heard from the speaker. There will be no accented ticks,

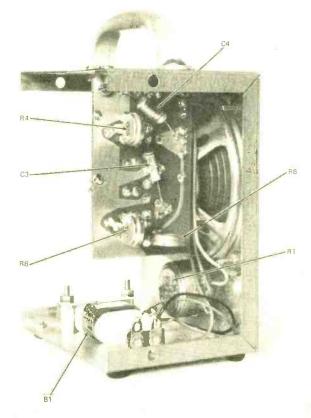


FIG. 3—COMPONENT LAYOUT from foll side of circuit board.

since this part of the setup has been momentarily disabled by the pre-setting of R8. Adjust potentiometer R1, the front-panel control, until the ticks occur at exactly one tick per second.

With R1 properly set, rotate R4 to the grounded end of its rotation and advance R8 to about mid-position. Now the 1-second ticks will not be heard. Adjust potentiometer R6, the 10-second rate control, to where a tick is heard from the speaker once every 12 to 13 seconds. The extra 2 to 3 seconds makes this generator run slowly enough to enable it to be synchronized with the pulses from the 1second generator.

With R6 adjusted as described, turn the timer off and solder capacitor C3 in place. Switch the timer on again, and

NOUSTRIES

advance potentiometer R4 to where the 1-second ticks are heard from the speaker. If you've been fortunate, every 10th tick will be louder. You may find, however, that every 9th or every 11th tick is being emphasized. If you're getting 9-second intervals, advance R6 slightly, to put a little more resistance in the circuit, and recheck performance. On the other hand, if you're getting 11-second intervals, R6 should be adjusted to put a little less resistance in the circuit. With R6 set as previously described, very little readjustment should be needed.

Adjust potentiometer R4 to where the 1-second ticks are heard distinctly but not too loudly. Then adjust R8 to where every 10th tick is obviously emphasized. Put the back/sides cover in place. The timer is now ready for use.


In using the instrument, it will be noted that the first louder tick, after the unit is switched on each time, is always later than normal. In my setup, the first emphasized tick occurs at 14 seconds. All lounder ticks after the first one will be at the required 10-second intervals.

OVERVOLTAGE RELAY

Vacuum-tube handbooks point out that 10% overvoltage cuts tube heater life in half. Cathode-ray tubes in oscilloscopes and TV receivers are expensive, often indispensable and—in some areas—replacements are not readily available. This overvoltage relay circuit was developed to protect voltage-sensitive devices by interrupting the power when the line voltage rises only a few volts above normal.

The $V_{\rm r}$ rating of Zener diode D2 is chosen by trial and is below the normal rms supply voltage by a little more than the dc operating voltage of RY1. Diodes D1 and D2 carry the coil current of RY1. D1 should have a PIV rating greater than the peak ac voltage (2.8 $E_{\rm rms}$ if $E_{\rm tm}$ is a sine wave). Electrolytic capacitor C1 is made large enough so RY1 does not chatter. The total resistance of R1 is chosen so $V_{\rm r}$ —the voltage across C1—approximates the rms voltage, not the peak voltage, R1-a is a pot or adjustable resistor for fine adjustment of the tripping voltage.

To energize the device protected by this overvoltage relay, close RY2's contacts manually or by pressing an optional momentary switch (S1) connected across the relay contacts. If the supply voltage is normal, RY2 will remain energized through the normally closed contacts of RY1. If the line voltage is too high, RY1 is energized so the RY2 contacts open to prevent power from flowing to the protected device.

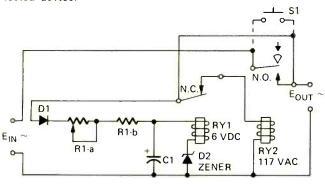

When adjusted for a 115-volt, 60-Hz normal supply; with RY1 rated at 6 volts dc and V_z selected as 100 volts, the overvoltage protector consistently shuts off at 120 volts without false triggering. The span between the normal and tripping voltages can probably be made smaller by selecting RY1 for a lower operating voltage.

R1 and C1 and the current ratings of D1 and D2 depend on the coil voltage and current of RY1. The greater the sensitivity of RY1, the lower the power wasted in the protector circuit. Diode D1 should have a PIV rating of 300 volts or more.—A.H. Taylor

Accuracy like a VTVM... Convenience like a VOM... NEW BATTERY-OPERATED FET SOLID-STATE VOLT-OHMMETER 116

Easy-to-build KIT

\$36.90 _{=116K}

Factory-Wired & Tested

\$49.49

Now you can get all the benefits of a VTVM (laboratory accuracy, stability and wide range) but with its drawbacks gone: no plugging into an AC outlet, no waiting for warm-up, no bulkiness. New Field Effect Transistor (FET) design makes possible low loading, instant-on battery-operation and small size. Excellent for both bench and field work.


Compare these valuable features:

• High impedance low loading: 11 megohms input or DC, 1 megohm on AC • 500-times more sensitive than a standard 20,000 ohms-per-volt VOM • Wide-range versatility: 4 P-P AC voltage ranges: 0-3.3, 33, 330, 1200V; 4 RMS AC voltage ranges: 0-1.2, 12, 120, 1200V; 4 DC voltage ranges: 0-1.2, 12, 120, 1200V; 4 Resistance ranges: 0-1K, 0-100K, 0-10 meg., 0-1000 meg.; 4DB ranges: —24 to +56DB.

4DB ranges: —24 to +56DB.
Sensitive easy-to-read 4½" 200 microamp meter. Zero center position available. Comprises FET transistor, 4 silicon transistors, 2 diodes. Meter and transistors protected against burnout. Etched panel for durability. High-impact bakelite case with handle useable as instrument stand. Kit has simplified step-by-step assembly instructions. Both kit and factory-wired versions shipped complete with batteries and test leads. 5½"H x 6¾"W x 2½"D. 3 lbs.



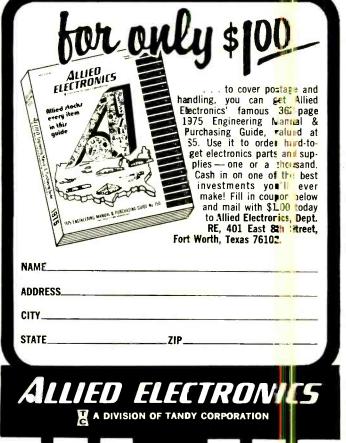ELECTRONIC MEASUREMEN S CORP. 625 Broadway, New York 10012



Quality Electronic Components

SPECIAL SAVINGS DISCOUNT ON LINEAR AND DIGITAL INTEGRATED CIRCUITS

Deduct 4% from the total of your I.C. proor if it exceeds \$25.00 based on single lat prices, 7% for \$50.00 or more, 10% for \$100.00 or more. Additional large quantity discounts offered

TTL & CMOS INTEGRATED CIRCUIT

111	. a cmos	INTEGRA	TED CIRC	UITS
7400N 25c	7445N 81c	7495N 90r	74193N . \$1.17	4027AE 67c
7401N 25c	7446N 81c	7496N 81c	74198N . \$2.75	
7402N 25c	7447N R1c	74107N 32c	74199N . \$2.75	
7403N 25c	7448N 90c	74121N 38c	4000AE 30c	4030AE 50c
7404N 25c	7450N 23c	74122N 45c	4001AE 30c	
7405N 25c	7451N 23c	74123N . \$1.08	4002AE 30c	
7406N 25c	7453N 23c	74141N 99c	4006AE . \$1.50	4035AE . \$1.42
7407N 25c	7454N 23c	74150N \$1.44	4007AE 30c	4040AE . \$1.67
7408N 25c	7459N 25c	74151N 90c	400BAE \$1,17	4041AE 92c
7409N 25c	7460N 23c	74153N 81c	4009AE 67c	4042AE . 84c
7410N 25c	7470N 36c	74154N. \$1.44	4010AE 67c	4043AE . 67c
7411N 25c	7472N 36c	74155N 81c	4011AE 30c	4044AE 67c
7413N 25c	7473N 32c	74156N 81c	4012AE 30c	4046Ae . \$2.51
7416N 25c	7474N 32c	74157N 72c	4013AE 53c	4049AE 58c
7417N 25c	7475N 54c	74158N, \$1.53		
7418N 25c	7476N 36c	74160N, \$1.26	4014AE . \$1.67	4050Ae 58c
7420N 25c	7480N 72c		4015AE . \$1,17	4051AE . \$1.50
7421N 25c		74161N. \$1.17	4016AE 63c	4052AE . \$1.50
7423N 72c	7483N 72c	74162N. \$1.26	4017AE . \$1.34	4053AE. \$1.50
7426N 2Sc		74163N . \$1.26	4018AE . \$1.67	4060Ae. \$1.67
7430N 25c		74164N. \$1.35	4019AE 58c	4066AE . \$1,00
7427N 25	7486N 32c 7489N \$4.47	74165N . \$2.45	4020AE . \$1.67	4071AE 30c
7437N 230	/489N \$4.4/	74166N . \$2.00	4021AE . \$1.50	4072AE 30c
7430N	7490N 50c	74175N. \$1.00	4022AE . \$1.25	4073AE 30c
74401 61.17	7491N 81c	74180N 81c	4023AE 30c	4075AE 30c
7441M \$1.17	7492N 50c	74181N. \$2.25	4024AE \$1.00	4081AE 30c
744 ZN 650	7493N 50c	74182N 90c	4025AE 30c	4082AE 30c
	7494N 81c	74192N . \$1.26	4026AE . \$1.67	

LINEAR INTEGRATED CIRCUITS

DODY MINIDIP TIMEK 82.50	5589 MINIDIP DUAL AMP /5.0c
565A DIP PLL\$3.38	567V MINIDIP DECODER \$3,38
741V MINIDIP OP AMP 50.0c	723A DIP VOLTAGE REG 82.5c
748V MINIDIP OP AMP 42.0c	747A DIP DUAL AMP 97.5c
L129 5 VOLT REG \$1.80	LM3900 DIP QUAD AMP 60.0c
L131 15 VOLT REG \$1.80	L130 12 VOLT REG \$1.80
	LM309K 5 VOLT REG \$1.75

MINIATURE ALUMINUM ELECTROLYTIC CAPACITORS - AXIAL LEAD TYPE

-40°C plus 85°C Tol	lerence -1	O plus 50% (greater ti	han 4.7 UFD) -10 plus 75% (4.7 Ur	Dor tess
1	10 100	1	10 100	1	10 100
1 UFD/50V 14c	12c 11c	33 UFD/16V 15c	12c 11c	330 UFD/16V 35c	25c 24c
2.2 UFD/50V 14c	12c 11c	33 UFD/25V 17c			
3.3 UFD/35V 14c					
4.7 UFD/35V 14c				470 UFD/25V 49c	
10 UFD/16V 14c	12c 11c	100 UFD 16V 19c	15c 14c	1000 UFD/16V 49c	39c 35c
		100 UFD/25V 24c			
22 UFD/16V 14c				2200 UFD/16V 75c	60c 55c
22 UF0/25V 15c	13c 12c	220 UFD/25V 35c	25c 24c		ı

1 AMP SILICON RECTIFIERS

1N4001 50 PIV 12/51 100/56 1000/548 1N4005 600 PIV 8/51 100/59 1000/570 1N4007 1000 PIV 6/51 100/511 1000/588 SUITCHING DIODE

MOLEX SOLDERCON IC TERMINALS

LED 7 SEGMENT DISPLAYS DATALIT-704 . . \$1.00 DATALIT-707 . . \$1.50

MACHINE SCREWS,	NUTS & LOCKWASHERS	REED REL	AYS
2-56 ¼ Screw . 90c/c 4-40 ¼ Screw . 96c/c	2-56 1/4 Screw . 98c/c 4-40 1/4 Screw . 96c/c	6 AMP SPST CONTAC	
6-32 ¼ Screw . 92c/c 8-32 3/8 Screw \$1.05/c 2-56 Hex Nut. \$1.45/c 4-40 Hex Nut. \$1.45/c 8-32 Hex Nut. \$1.50/c	6-32 1/2 Screw . 86c/c 8-32 5/8 Screw \$1.35/c 2 Lock Washer . 45c/c 4 Lock Washer . 45c/c 6 Lock Washer . 45c/c 8 Lock Washer . 45c/c	5V . \$2.00 6V . \$2.00 12V \$2.00 24V \$2.00	\$1.50 \$1.50 \$1.50 \$1.50

I.C. SOCKETS DISC CAPACITORS

	10	200	1000	1	10
100 pf/500V7c	5.5c	4.5c	3.6c	8 pin Solder . 27c	21 c
220 pf/500V 7c	5.5c	4.5c	3.6c	14 pin Solder. 29c	23c
470 pf/500V 7c	5.5c	4.5c	3.6c	16 pin Solder . 32c	25c
,001/500V7c	5.5c	4.5c	3.6c	18 pin Solder, 34c	26c
.0022/500V 7c	5.5c	4.5c	3.6c	24 pin Solder, 54c	42c
.0047/500V 7c	5.5c	4.5c	3.6c	1	10
.01/500V 10c	7.5c	6.3c	5.0c	8 pin W.W 38c	30c
.01/25V 5c	3.5c	3.0c	2.46		
.022/25V 6c	4.0c	3.5c	2.7c	14 pin W.W 50c	39c
.047/25V9c	6 Oc	5.3c	4.2c	16 pin W.W 54c	42c
.1/25V 12c	9.0c	7.5c	6.0c	18 pin W.W 88c	68c
				04 -'- 111 111 00	00

1/2 & 1/4 WATT CARBON COMP. RESISTORS

5 each of the 85 standard 10% values (2.2-22M) ½ W Resistors (425 pcs.) Sorted by value \$12/set 2.4 are \$11/set 5.9 are \$10/set. 5 each of the 70 standard 10% values (10.5-6M) ½ W Resistors (350 pcs.) Sorted by value \$12/set 2.4 are \$11/set 5.9 are \$10/set.

SILICON TRANSISTORS

	1.9	10.99	100		1-9	10-99	100
EN91B TO-106	21c	18.5c	16.5c	2N3645 TO-10S	20c	17.5c	16.0c
EN930 TO 106	21 c	18.5c	16.5c	2N3646 TO-106	22¢	19.0c	17.5c
EN222 TO-106	21c	18.5c	16.5c	2N3904 TO- 92	22c	19.0c	17.5c
EN2369A TO-106	21c	18.5c	16 5c	2N3906 TO- 92	22c	19.0c	17.5c
EN2907 10-106	21c	18.5c	16.5c	2N4124 TO- 92	22c	19.0c	17.5c
2N2712 TO- 98	18c	16.0c	14.5c	2N4126 TO- 92	22c	19.0€	17.5c
2N3391A . TO- 98	22c	19.0c	17.5c	2N4401 . TO- 92	22c	19.0c	17.5c
2N3392 TO- 98	22c	19.0c	17 5c	2N4403 . TO- 92	22c	19.0c	17.5c
2N3393 TO- 98	22c	19.0c	17.5c	2N5087 TO- 92	22c	19.0c	17.5c
2N3394 TO- 98	22c	19.0c	17.5c	2N5089 TO- 92	22c	19.0c	17.5c
2N3563 TO-106	20c	17.5c	17.5c	2N5129 TO-106	19c	17.0c	15.0c
2N3565 TO-106		17.5c	16.0c	2N5133 TO-106	19c	17.0c	15.0c
2N3638TO-105	20€	17.5c	16.0c	2N5134 TO-106	19c	17.0c	15.0c
2N3638A . TO-105	20c	17.5c	16.0c	2N5137 10-106	190	17.0c	15.0c
2N3640 . TO-106	22c	19.0c	16.0c	2N5138 TO-106	19c	17.0c	15.0c
2N3641 TO-105	20c	17.5c	17.5c	2N5139 TO-106	19c	17.0c	15.0c
2N3643 . TO-105	20c	17.5c	16.0c	2N3055 TO- 3	\$1.00	95.0c	85 Oc

FIELD EFFECT TRANSISTORS

MPF102 TO 92 44 .380 .350 2NS457 .. TO 92 .47 420 .375

NPN DARLINGTON TRANSISTOR Min. DC Current Gain of 5,000 at 10mA.

Send for Free Catalog or Mail Readers Service Card COD ORDERS ACCEPTED FOR SAME DAY SHIPMENT
CALL 218-681-6674

Orders Less than \$10.00 add 50c Service Charge—Others Postpoid "Only Quality Components Sold!"

DIGI-KEY CORPORATION

Thief River Falls, MN 56701 P.O. Box 126

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). \$1.40 per word . . . minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) 85c per . no minimum

FIRST WORD AND NAME set in bold caps at no extra charge. Additional bold face at 10c per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e. August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day. issue closes on preceding working day.

WANTED

QUICK cash . . . for electronic equipment, components, unused tubes. Send list now! BARRY, 512 Broadway, New York, NY 10012, 212 WAlker 5-7000

PLANS & KITS

EM synthesizer concept-features universal compatibility, modular construction. For complete information send SASE or 25c to: CFR ASSOCIATES, POB F, Newton, NH 03858

FREE catalog. Most unusual electronic kits available. Music accessories, surf, wind synthesizers, wind chimes, many others.

PAIA ELECTRONICS, Box B14359, Oklahoma City, OK 73114

CONVERT any television to sensitive, big-screen oscilloscope. Only minor changes required. No electronic experience neces-sary. Illustrated plans \$2.00. SANDERS, Dept. A-25, Box 92102, Houston, TX 77010

NEW organ kit builders manual \$3.00. Circuits, block diagrams, details on diode keyed IC divider and independent oscillator designs. Many new kits and models. Key-boards also for synthesizers. Manual cost refundable with purchase. **DEVTRONIX OR-GAN PRODUCTS**, Dept. B, 5872 Amapola Dr., San Jose, CA 95129

EDUCATION & INSTRUCTION

SHORTCUT to success: Highly effective, profitable short courses (75 courses). Study at home. Diploma awarded. Our 29th year! Free literature. CIEE-E, Box 20345, Jackson, MS 39209.

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. NEGEYE LABORATORIES, Box 547-RE, Pennsboro, WV 26415



TV tuner repairs—Complete course details 12 repair tricks. Many plans. Two lessons, all for \$2. Refundable, FRANK BOCEK, Box 3236 (Enterprise), Redding, CA 96001.

ELECTRONICS book discounts. Save! Free selected, reviewed list. T/DOC, Box 340, Centerville, VA 22020

LEARN design techniques. Electronics monthly newsletter. Digital, linear construc-tion projects, design theory and procedures. Sample copy \$1.00. VALLEY WEST, Box 2119-A, Sunnyvale, CA 94087

MANUALS for Govt. surplus radios, test sets, scopes, list 50c (coin). BOOKS, 7218 Roanne Drive, Washington, DC 20021

FOR SALE

ELECTRONIC parts! New! Solid state devices! Free flyer: **DARTEK ELECTRONICS**, 2460, Dartmouth, Nova Scotia B2W 4A5 U.S. inquiries.

ELECTRONIC Ignition: Capacitor, transistor, pointless. Auburn sparkplugs. Information 10c. ANDERSON ENGINEERING, Epsom, NH 03234

FREE catalog. IC's, Semi's. CORONET ELECTRONICS, 649A Notre Dame W., Montreal, Que., Canada, H3C-1H8 US Inquiries.



name	(please print)	
address		
city	state	zip code

Mail to: Radio-Electronics SUBSCRIPTION DEPT., BOULDER, COLO. C-MO)

4000AE 48 45
4001AE 48 40
4002AE 48 40
4002AE 58 5.85
4006AE 3.50 3.30
4007AE 48 42
4008AE 2.90 2.70
4009AE 87 86
4010AE 55 54
4011AE 48 45
4012AE 48 45
4013AE 95 85

0019AE 200 2 80 0020AE 270 2 80 0020AE 270 2 80 0020AE 48 48 48 0020AE 180 1.60 0020AE 180 1.60 0020AE 1.20 1.00 0020AE 1.20 1.00 0020AE 4.00 2.90 0030AE 1.00 90 0030AE 1.00 90 0030AE 2.80 2.60 0041AE 1.20 90 0040AE 2.80 2.60 00404AE 2.80 2.60 00404AE 2.80 2.60

4044AE 2.80 2.60 4047AE 3.10 3.00 4048AE 1.45 1.35 4049AE 1.10 .90 4051AE 3.35 2.90 4052AE 2.15 2.05 4053AE 2.90 2.80 4055AE 2.70 2.60 4056AE 3.45 3.41 4066AE 1.80 1.60 4069AE 8.0 70 4071AE 50 4.55 4076AE 2.70 2.50 4081AE 48 42 4510AE 2.90 2.80 4518AE 3.30 3.00 4901AE .48 .42

4030AE 1.00 4033AE 2.80 4040AE 2.80 4041AE 1.20 4042AE 2.80 4043AE 2.80 4047AE 3.10

WAVEFORM GENERATOR

XR205K KIT Only \$28.00

Here's a highly versatile lab instrument at a fraction of the cost of conventional unit. Kit includes two XR205 IC's, data & applications, PC board (etched & drilled, ready for assembly) and detailed instructions.

7409N 85
74100N 125
74108N 125
74110N 127
74111N 192
74111SN 1.51
74119N 1.80
7412N 1.81

74155N 1.08 74156N 1.18 74157N 1.18 74158N 1.44 74160N 1.50



LM 331N Vio = 6mV lie = 1000 nA lb= 2000 nA Noise = 1.5dB \$2.20

· 8 9

CALCULATORS

(Limited Qty.)

\$19.00

1024-BIT

N-Channel

RAM

2601-1 11.40 2601-21 11.40 2602B 8.00 2602-1B 8.00 2602-2B 8.00 MK4102P 11.40 7552-1CPE 8.00 7552-2CPE 8.00

IC SOCKETS

SOLDER - TIN

8 pin DIL .22 14 pin DIL .26 16 pin DIL .29 24 pin DIL .75 28 pin DIL 1.10 36 pin DIL 1.70 40 pin DIL 1.90

WIRE WRAP-GOLD
14 pin DIL 40
16 pin DIL 45
SOLDER - GOLD

MM

MM404H 12.00 MM405H 23.00 MM406H 6.50 MM407H 6.50 MM451H 11.40 MM454F 18.00

MM454F MM506H MM507H MM550H MM551H MM555H

.40

55

11.40 18.00 3.20 3.20 5.90 5.60 5.60

14 pin DIL 16 pin DIL

TEFLON 3 pin TO-5 4 pin TO-5 6 pin TO-5 8 pin TO-5 10 pin TO-5

PREMIUM QUALITY COMPONENTS

We've been buying and selling top quality components for nearly

ten years. Our annual volume exceeds \$3 million. We handle only original parts, from the world's

leading manufacturers and our customers include

some of the largest and most quality-conscious

companies. Now you can take advantage of our

component buying skills and power and select

from a broad range of advanced circuits.

Price

1.60 2.50 1.60 2.00 3.00 2.20 3.00 1.70

74161N 1.28 74162N 1.50 74163N 1.48 74164N 1.78 74166N 1.54 74170N 1.60 74173N 1.55 74170N 1.50 74171N 1.54 74177N 1.54 74177N 1.54 74171N 1.50 74181N 3.49 74182N 1.29 74188N 4.90 74181N 1.49 74181N 1.49 74192N 1.45 74192N 1.45 74193N 1.29 74194N 1.35 74195N 1.89 74194N 1.35 74195N 1.89 74195N



	DISPL	.AYS	
1	OPCOA	ı	
	SLA1	Red	2.2
	SLA11	Green	3.5
	SLA21	Yellow	3.51
_	SLA7	Red	1.6
	LITRO	NIX	
	DL80	Red	6.00
	DL81	Red	6.00
	DL 10	Red	6.00

SLA11	Gree	n	3.50
SLA21	Yello	w	3.50
SLA7	Red		1.60
LITRO	VIX		
DL80	Red		6.00
DL81	Red		6.00
DL 10	Red		6.00
DL10A	Red		4.00
DL 101	Red		4.90
DL57	Red		9.90
DL61	Red		12.00
DL33	Red		4.00
DL44	Red		6.00
DL 402	Red		4.00
DL701	Red		3.40
DL704	Red		2.25
DL 707	Red		2.35
DL747	Red		2.50
XCITO	N		
XAN72	Red		2.00
XAN52	Gree	n	2.00

FIRST

QUALITY

75107

75107BN 75108BN 75109N

75110N

75110N 75115N 75138N 75150N 75154N 75208N 75234N 75450N 75451N 75452N 75453N

7520 SER

SENSE AM

7520N 7521N 7522N 7523N 7524N 7525N

ONLY

o 688888888
EP 9125
9-DIGIT DISPLAY
\$7.90
- 1/8" character height


· compact, thin PC

OPTOISOLATORS

MONSANTO LITRONIX IL1 IL12 IL16 IL74 ILD74 1.75 ILQ74 3.40

9300 SERIES

74LS76 .92
74LS78 .92
74LS107 .92
74LS107 .92
74LS112 .92
74LS113 .92
74LS114 .92
74LS115 .23
74LS15 .23
74LS15 .23
74LS15 .23
74LS16 .27
74LS26 .36
74LS26 .36 **74LS** 9300PC 9301PC 9304PC 9306PC 9308PC 9309PC 9310PC 74LS00 74LS01 74LS02 74LS03 74LS04 74LS05 9310PC 1.50 9311PC 2.30 9312PC 1.20 9314PC 1.30 9316PC 1.50 9318PC 2.30 9321PC 1.30 9321PC 2.30 932PC 2.50 9324PC 2.50 9324PC 2.50 9334PC 2.50 934PC 5.00 934PC 5.00 934PC 5.00 934PC 4.10 934PC 1.75 9360PC 1.75 1.50 2.30 74LS08 74LS09 74LS10 74LS11 74LS15 74LS21 74LS22 74LS27 74LS32 74LS32 74LS51 74LS54 74LS54 74LS73 74LS73

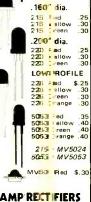

LEDS

.125° dia.

209 d 209 ellow 209 een

1-AMP RECTIFIERS

PHASE-LOIKED LOCAL

LM567CM M € dip 2.10

DECODED READ/WRITE RAM

7400N TTL

7444N 7445N 7447N 7448N 7448N 7450N 7451N 7453N 7453N 7460N 7462N 7466N 7470N 7471N 7472N 7473N 7474N 7478N 7478N 7478N 7478N 7478N 7478N 7482N 7482N 7482N

7484N 7485N

7485N 7486N 7489N 7490N 7491N 7492N 7493N 7494N

.70 1.15 .84 .71 1.29 .85

7400N 7401N 7402N 7403N 7404N 7405N 7406N 7407N

7408N 7409N 7409N 7411N 7411N 7412N 7414N 7415N 7416N 7416N 7420N 7421N 7422N 7425N 7425N 7425N 7426N 7427N 7428N 7430N 7440N
P1103 \$6.20

SCHOT	TKY	TTL		74S158N 2.40 74S160N 4.70
74S00N	.45	74S74N	1.30	74S161N 4.70
74S02N	.80	74S85N	6.10	74S174N 3.30
74S03N	.75	74S86N	2.70	74S175N 3.30
74S04N	.75	74S112N	2.20	74S181N10.20
74S08N	.80	74S113N	1.50	74S189N 5.10
74S10N	.75	74S132N	3.60	74S194N 3.30
74S11N	.65	74S133N	.90	74S 195N 3.30
74S20N	.80	74S138N	2.40	74S251N 2.40
74S30N	.80	74S139N	2.40	74S253N 2.40
74S32N	.80	74S140N	.90	74S257N 2.40
74S40N	.80	74S151N	2.40	74S258N 2.40
74S51N	.80	74S153N	2.40	74S260N .90
74S64N	.80	74S157N	2.40	74S280N 5.70

LOW POWER HIGH SPEED TTL TTI

74L00N .34	74H00N .34	74H53N	.36
74L02N .34	74H01N .34	74H54N	.36
74L03N .39	74H04N .38	74H55N	.36
74L04N .39	74H05N .37	74H60N	.36
74L10N .34	74H08N .40	74H61N	.36
74L20N .39	74H10N .36	74H62N	.36
74L42N 1.62	74H11N .36	74H71N	.80
74L51N .34	74H20N .36	74H72N	.74
74L73N .74	74H21N .36	74H73N	.90
74L74N .89	74H22N 36	74H74N	.87
74L90N 1.62	74H30N .36	74H76N	.90
74L93N 1.74	74H40N .36	74H101N	.80
74L95N 1.62	74H50N .36	74H102N	.80
	74H51N .36	74H103N	1.10
93L00 1.50	74H52N .36	74H106N	.95
93L01 1.60			
93L08 3.20			
93L09 1.80			
93L10 2.80	DIDOLA	D	
93L11 4.20	BIPOLA		P1
93L12 1.80	MEMOR	lY .	P1
93L14 1.70		• •	140
93L16 3.20	C3101	6.50	140
93L18 3.50	P3101	4.90	140
93L21 1.50	C3101A	7.30	140
93L22 1.80	P3101A	5.80	140
93L24 280	IM5501CDE	7.30	140
93L28 3.70	IM5501CPE	5.80	150
93L34 4.00	MM5560D	7.30	150
93L38 4.20	MM5560N	5.80	160
93L40 6.50	DM8599N	5.80	17
93L41 6.50	93403PC	5.80	C2
93L60 3.00			P2
93L66 2.70			C2

BIPOLAR

MEMO	• •
C3101	6.50
P3101	4.90
C3101A	7.30
P3101A	5.80
IM5501CDE	7.30
IM5501CPE	5.80
MM5560D	7.30
MM5560N	5.80
DM8599N	5.80
93403PC	5.80

COMPUTER INTERFACE

DM8820N	2.40
DM8820AN	6.90
DM8830N	2.40
DM8831N	5.20
DM8832N	6.00
N8T26B	4.40
9600PC	1.30
9601PC	1.20
9602PC	2.10
9614PC	2.30
9615PC	2.40
9616DC	5.00
9617PC	3.50
9620PC	4.00

A PORTABLE
4% DIGIT
MULTIMETER
FOR \$299.
A 10 MHZ
COUNTER OPTION FOR \$50

DIII CF GENERATOR Interdesign 1101: 0.1Hz-2MHz, 0-5V Output, var. width, line or battery operation. \$159.00

P1101A	6.90	C2102-2	8.00
P1101A1	8.50	P2102-2	6.00
1402AN	5.40	2505K	3.30
1403AH	8.00	2512K	5.50
1403AN	5.40	2521V	4.00
1404AH	8.00	2524V	3.90
1404AN	5.40	2525V	5.30
1405A	4.10	2533V	8.50
1506	4.00	3341PC	8.20
1507	4.00	MM5025N	20.00
1602	33.00	MM5026N	20,00
1702	33.00	MM5027N	20.00
C2102	8.00	MM5055N	5.50
P2102	6.00	MM5056N	5.50
C2102-1	8.00	MM5057N	5.50
P2102-1	6.00	MM5058N	5.50

TWO-PHASE MOS CLOCK

	MOS	-LSI	
P1101A	6.90	C2102-2	8.00
P1101A1	8.50	P2102-2	6.00
1402AN	5.40	2505K	3.30
1403AH	8.00	2512K	5.50
1403AN	5.40	2521V	4.00
1404AH	8.00	2524V	3.90
1404AN	5.40	2525V	5.30
1405A	4.10	2533V	8.50
1506	4.00	3341PC	8.20
1507	4.00	MM5025N	20.00
1602	33.00	MM5026N	20,00
1702	33.00	MM5027N	20.00
C2102	8.00	MM5055N	5.50
P2102	6.00	MM5056N	5.50
C2102-1	8.00	MM5057N	5.50
P2102-1	6.00	MM5058N	5.50

	MOS	-LSI	
P1101A	6.90	C2102-2	8.00
P1101A1	8.50	P2102-2	6.00
1402AN	5.40	2505K	3.30
1403AH	8.00	2512K	5.50
1403AN	5.40	2521V	4.00
1404AH	8.00	2524V	3.90
1404AN	5.40	2525V	5.30
1405A	4.10	2533V	8.50
1506	4.00	3341PC	8.20
1507	4.00	MM5025N	20.00
1602	33.00	MM5026N	20,00
1702	33.00	MM5027N	20.00
C2102	8.00	MM5055N	5.50
P2102	6.00	MM5056N	5.50
C2102-1	8.00	MM5057N	5.50
P2102-1	6.00	MM5058N	5.50

	MOS	-LSI	
P1101A	6.90	C2102-2	8.00
P1101A1	8.50	P2102-2	6.00
1402AN	5.40	2505K	3.30
1403AH	8.00	2512K	5.50
1403AN	5.40	2521V	4.00
1404AH	8.00	2524V	3.90
1404AN	5.40	2525V	5.30
1405A	4.10	2533V	8.50
1506	4.00	3341PC	8.20
1507	4.00	MM5025N	20.00
1602	33.00	MM5026N	20,00
1702	33.00	MM5027N	20.00
C2102	8.00	MM5055N	5.50
P2102	6.00	MM5056N	5.50
C2102-1	8.00	MM5057N	5.50
P2102-1	6.00	MM5058N	5.50

	MOJ.	LJI	
P1101A	6.90	C2102-2	8.00
P1101A1	8.50	P2102-2	6.00
1402AN	5.40	2505K	3.30
1403AH	8.00	2512K	5.50
1403AN	5.40	2521V	4.00
1404AH	8.00	2524V	3.90
1404AN	5.40	2525V	5.30
1405A	4.10	2533V	8.50
1506	4.00	3341PC	8.20
1507	4.00	MM5025N	20.00
1602	33.00	MM5026N	20,00
1702	33.00	MM5027N	20.00
C2102	8.00	MM5055N	5.50
P2102	6.00	MM5056N	5.50
C2102-1	8.00	MM5057N	5.50
P2102-1	6.00	MM5058N	5.50

AUDIO AMPS

6-27 6-18 5-30 4-20 3-16

5-20 6-24

2524V

Recirculating 512 Bit

Dynamic Shift Register

1-24: \$3.90 25 up: \$3.80

Туре

TBA641B11

TBA810AS

TBA820 TCA830 TCA940

TAA611B12 6-15 TAA621A12 6-27

LM352 LM354A

 $v w \Omega$

2.20 4 4.70 8 2.50 4 0.75 4 2.00 4 6.50 8

6-15 1.15 6-27 2.80 6-15 1.15 6-27 1.40 6-18 2.20

DRIVER MH0026CN

DEMODULATOR XR1310 \$3.90

FM STEREO

MINIMUM ORDER: \$10.00 Add \$1.00 to cover postage andline SEND CHECK OR MONEY ORDER (NO C.O.D.) TO:

California residents add 6% sales tax.

P.O. BOX 2208R, Culver City, CA 90230

INTER	FACE MODULES	
CY1010	Instr. Amp., Bipolar Input	29.00
CY1011A	Instr. Amp., Bipolar Input	49.00
CY1020	instr. Amp., FET input	34.00
CY1021	instr. Amp., FET Input	49.00
CY1021A	Instr. Amp., FET Input	59.00
CY2137	DAC, 10 Bit, Low Drift	39.00
CY2218	DAC, 12 Bit, 2 Quad Multiple in	g 149.00
CY2237	DAC, 12 Bit, Low Drift	69.00
CY2735	DAC, 4 Digit BCD, Low Com	79.00
CY3035	ADC, 8 Bit, Sect. Counting.	
	Low Cost	89.00
CY3635	ADC, 3 Digit BCD, Sect. Coulc,	
	Low Cost	119.00

LINEAR Ks

H-TOS N-DIP	M=MINI-DIP	D=CER-DIP	< =TO3
-------------	------------	-----------	------------------

	LM114H	3.00	LM311H	1.70	LM711CN	.90
-	LM300H	1.20	LM311D	1.90	LMF715 ICH	4.30
_	LM300N	1.20	LM311M	1.75	LM715 CD	4.60
2.60	LM301AH	.90	LM311N	2.00	LM7Z CH	.90
30	LM301AM	.80	LM312H	2.70	LMIZERN	.75
.20	LM301AN	1.10	LM318H	2.60	LMIZECH	5.00
.20	LM301M	.90	LM324N	1.90	LMIZECD	5.20
.25	LM301H	.90	LM331N	2.20	LM7.E.CH	1.40
.95	LM302D	3.50	LM339N	3.20	LM7ECD	3.50
3.10	LM302N	1.30	LM320 5K	2.90	LM7 ICN	1.30
1.10	LM302H	1.50	LM3205T	2.50	LM74 CH	.45
.70	LM304H	1.50	LM320-12K	2.90	LM74 3D	1.25
.50	LM305H	1.05	LM320-12T	2.50	LN:74 JM	.44
.25	LM305AH	1.05	LM340-05K	2.60	LN:74 CN	.70
.00	LM305N	1.00	LM340-06K	2.60	LN74COH	1.70
.00	LM306H	.95	LM340 08K	2.60	LM74 CN	.90
.00	LM307H	.75	LM340 12K	2 6 0	LMFEDD	2.50
	LM307M	.95	LM340 15K	2.60	LM74 CM	.55
RIES	LM307N	1.50	LM340 18K	2.60	LM74ICN	.55
APS	LM308H	1.20	LM340-24K	2.60	LMTTCH	2,15
nro	LM308AH	5.00	LM555CM	.90	LNITTOM	2.10
1.00	LM308D	2.00	LM556CN	1.30	LM 30- ISCN	.95
2.00	LM308M	1.20	LM709CH	.45	LM 30 MCN	1.50
.25	LM309H	1.75	LM709CN	.45	SG-15T T	2.20
.75	LM309K	1.95	LM710CH	.90	SG-15[N	2.20
00.5	LM310H	1.60	LM710CN	.90	LNEODK	7.50
.50	LM310M	1.80	LM711CH	90		

HYBRID Power AMPLIFIERS

SI-1010G 10W \$6.90 SI-1020G 20W 9.90 SI-1030G 30W 18.70 SI-1050G 50W 25.90

POWER

CACHENIA					
BU204	3A	1300V	\$4.14		
BU205	3A	1500V	4.95		
BU206	3A	1700V	5.94		
BU207	6A	1300V	5.85		
BU208	6A	1500V	6.93		
BU209	6A	1700V	8.64		

IC POWER REGULATORS

LM335K:	5V, 600mA	! 40
LM336K:	12V, 500mA	. 30
LM337K:	15V. 450mA	. 30

TRANSISTORS

		17411313	.01		
2N173	2.15	2N3445	5.00	2四世第57	1.60
2N512B	2.90	2N3563	. 15	温剂 8 9 7 1	1.00
2N677C	5.50	2N3565	.19	2114945	1.95
2N697	.25	2N3567	.19	2N4128	.50
2N711	.50	2N3569	.17	2N-1249	.18
2N918	.40	2N3642	.19	219-11-103	.30
2N1136	1.50	2N3643	.14	281341	1.35
2N1377	1.50	2N3645	.15	2N 1 47	1.60
2N1483	1.20	2N3657	9.00	2511048	2.00
2N1534	1.00	2N3684	1.25	3N 1095	1.30
2N1540	1.10	2N3702	.18	想物事 率16	.90
2N1544	.90	2N3707	.17	251158	1,10
2N1924	1.30	2N3711	.18	2541159	1.20
2N1934	9.40	2N3725	.36	2個4922	1.00
2N2102	.60	2N3731	2.00	2116136	1.18
2N2219	.30	2N3771	2.20	2M i 127	.16
2N2221	.25	2N3772	2.30	2HF 98	4.30
2N2484	.25	2N3773	3.40	2N6006	.27
2N2713	.15	2N3789	3.00	2M i 409	32.00
2N2906	.18	2N3819	.30	27111 ×53	5.40
2N2907	.20	2N3823	.70	270 i 457	.40
2N2926	.15	2N3866	1.10	2M i ≈58	.40
2N3053	.35	2N3905	.20	279年178	.55
2N3055	.95	2N3906	.25	进作证明27	.50
2N3202		2N3909	.80	2 NHE 628	.65
2N3227	1.80	2N3955	2.70	2NE 199	.85
2N3375	5.50	2N3955A	3.20	2NE 01	.85
2N3442	2.20			:: Mail: 03	.90

SPECIFICATION SHEETS: \$.25

DYNACO-A-R, transistors, repairs-boards & units, speaker service. Send for prices details. BEAR ELECTRONICS, 177-R Hi crest Road, Mt. Vernon, NY 10552 177-R Hill-

A NEW INVENTION

Adds resistance scales to your ohmmeter. Patent #3805151. If your ohmmeter now has, for example, Rx10 and Rx1K scales add Rx100 and Rx10K etc. Rx10 and Rx10K scales add Rx10O and Rx10K etc. Whatever the combination add scale or scales in a similar manner. Models offered for sale are recommended for 1½ or 3 volt ohmmeters and not for VTVM or FET meters. Designed to use 9E Bats. not included but test leads are.

Send \$12.75, N.Y. residence include sales tax, to: J.E.M. Mfg. 19 Phyllis Dr., Bethpage, N.Y. 11714

RADIO & TV tubes 36c each. One-year guarantee. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, CA 92105

COMPUTERS! You can build them large and fast or small and economical. Design procedure and construction manual \$3.00 cedure and construction manual \$3.00.
Free info. **DIGITRONICS CO.**, 667 East 1700 South, Orem, UT 84057

DIGITAL electronics! Complete schematics, parts lists, theories—Discrete Component Digital Clock, \$3.00. Increase technical competence, hobby skills—Complete course in Digital Electronics is highly effective, \$10.00. Free literature. **DYNASIGN**, Box 60R2, Wayland, MA 01778

LIQUID Cystal. 3½-digit wristwatch display. New, with instructions for building wristwatch. Final close-out. Less than original, factory wholesale price. \$5.50 each. Two for \$10. TRICOUNTY WINSLOW, Inc., Box 5885, Grand Central Station, New York, NY 10017

COMPLETE construction plans-Telephone: answering device, automatic dialer, "black boxes", call diverter, call limiter, conference bridge, central dial exchange, melodic ringing generator, recorder-actuator, remote control, schematics, speakerphone, Telelink burglar alarm, voice scrambler, \$3.00 each. **Electronic-B**iofeedback conditioner, horticulture stimulator, multifrequency encoder network (Speeds telephone dialing 500%!). \$5.00 each. One year subscription: Telephone electronics line (Tel) \$3.00. Super illustrated catalog of plans, many more, 50 cents. All of the construction plans above plus a years subscription to tel and catalog: 24.95. TELETRONICS COMPANY OF AMER-ICA, P.O. Drawer 3450, Hollywood, CA 90028

CATALOG

GOVERNMENT SURPLUS **ELECTRONIC EQUIPMENT**

For 1975

FREE UPON REQUEST! Write for Copy of Catalog WS-75 Now! Address: Attention Dept. RE

FAIR RADIO SALES 1016 E. EUREKA + Box 1105 + LIMA, OHIO + 45802

NEW Canadian Magazine, "Electronics Workshop", \$5.00 yearly, sample \$1.00. ETHCO, Box 741 "A", Montreal

SURPRISE! Build inexpensively, the most unusual test instruments, futuristic gadgets using numerical readouts! Catalogue free! GBS, Box 100B, Greenbank, WV 24944

QUALITY military and industrial surplus electronics. Send 25c for last 3 of our monthly picture flyers. It's different! U.S. only. STARTRONICS, Box 17127, Portland, OR 97217

SHOTGLASS. As seen in Esquire. Glasscone column speaker. \$129.50 each. F.O.B. moneyback guarantee. TACHYON, TM, Box 1012, Roselle, IL 60172

RECONDITIONED test equipment. \$0.50 for catalog. WALTER, 2697 Nickel, San Pablo, CA 94806

JAPANESE transistors, wholesale prices, free catalog. WEST PACIFIC ELECTRONICS, Box 25837, W. Los Angeles, CA 90025.

BUILD A "SPACE-AGE" TV CAMERA!! PHONE or WRITE for CATALOG. DIAL 402-987-3771 BOX 453-RE **ATV Research** DAKOTA CITY NEBR 687.

TV ping pong game. Plays through your set's antenna terminals; plans \$3.25. Four channel digital oscilloscope; plans \$4.50. ARS SYSTEMS, Box 1922A, Sunnyvale, CA 94088

POWER supplies. Regulated 5 volts, 1 amp. Tested, guaranteed, \$19.95. Free specs available. MULLERS, Rt. 4 Box 371, Auburn, ME 04210

CONVERT any transistorized TV tuner to a tuner substituter. Plans \$2.00. \$35.00 for completed and tested super substituter. RADIO TELEVISION TRAINING, Box 279, RE-35, Syracuse, NY 13206

COMPONENTS 8038CC, \$5.75. AY5-1013A UART \$13.95. AY5—1008 receiver \$7.95. Crystal time base kit, 5Vdc input, 60Hz TTL output, \$9.75 postpaid. Latest flyers, 10c stamp. TRI-TEK, 6522 N43 ave., Glendle A7 85001. dale, AZ 85301

LOGIC probe. LED readout indicates TTL DTL, CMOS logic levels. Hand held unit powered from logic supply. High impedance input. Guaranteed. \$8.95 postpaid. VALLEY WEST, Box 2119-S, Sunnyvale, CA 94087

INTEL 8008	TRANSISTO	D CDECIAL C	L 0 (1400 (D1005 0) 14105)
Eight Bit Microprocessing Chip	2N256 PNP CF TO	IR SPECIALS	C/MOS (DIODE CLAMPED)
(With Documentation) \$79.50	2N256 PNP GE TO 2N404 PNP GE TO	-54/	\$.50 74C 02 \$.55 CD 4022 \$2.10 \$1.00 74C 165 \$3.50 CD 4023 \$.53
MINIATURE TRIM POTS	2N3919 NPN Si TO MPSA13 NPN Si TO MPS3393 NPN Si)-3 RF	1.50 CD 4001 \$.53 CD 4024 \$2.15
5K, 10K, 25K, 50K, 100K	MPSAIS NPN SI IC)-923/: TO-92 4/9	\$1.00 CD 4002 \$.53 CD 4025 \$.50
\$.75 ea. 3/\$2.00	2N3767 NPN Si T	0-66	.70 CD 4006 \$3.60 CD 4026 \$5.00
	2N3767 NPN Si Ti 2N2222 NPN Si Ti	0-185/5	1.00 CD 4007 \$.60 CD 4027 \$1.20
MULTI-TURN TRIM POTS	2N3055 NPN Si T 2N3904 NPN Si TO	0-3	\$1.00 CD 4009 \$.80 CD 4028 \$2.75
Similar to Bourns 3010 style, 3," x 5," x 11,4"; 50, 100, 500, 2000, 5000, 10,000 ohms.	2N3904 NPN SI TO	1-924/3	\$1.00 CD 4010 \$.53 CD 4029 \$4.80 \$1.00 CD 4011 \$.53 CD 4030 \$.53 \$.50 CD 4012 \$.53 CD 4035 \$2.30
5000, 10,000 ohms.	2N5296 NPN Si T	0-220	5.50 CD 4012 \$.53 CD 4035 \$2.30
\$1.50 ea. \$3/\$4.00	2N6109 PNP Si TO	-220	5 .55 CD 4013 \$1.00 CD 4042 \$2.75
LIGHT ACTIVATED SCR'S	2N3866 NPN Si TO-5	SiRF POWER S	\$.75 CD 4015 \$3.35 CD 4046 \$3.75
TO-18, 200V 1A \$1.75	MJ2252 NPN Si T	0-66	\$.90 CD 4016 \$1.05 CD 4047 \$3.60 \$1.00 CD 4017 \$2.70 CD 4050 \$1.05
	2N3638 NPN Si To 2N2218A NPN Si	U-55/3	\$1.00 CD 4017 \$2.70 CD 4050 \$1.05 \$1.00 CD 4019 \$1.20 CD 4055 \$3.20
PRINTED CIRCUIT BOARD	CAPACITOR	S MAN	1 Ped or Vellow Full Wave Bridges
4½" x 6½" single sided epoxy	6V 30UF TANT	5/\$1 LED	-1, Red or Yellow Full Wave Bridges READOUT \$2.50 -3 READOUT \$1.75 -4 READOUT \$2.00 3 \$4.50 -7 \$1.00 600 1.35 1.75 6.00
board, 1/4" thick, unetched	20V 4.7UF TANT	5/\$1 MAN	1-3 READOUT \$1.75 PRV 2A 6A 25A
\$.50 ea. 5/\$2.20	6.8 UF 35V TANT	3/\$1 MAN	3 \$4.50 400 1.15 1.50 5.00
MC14435 AND MC1405L	10μf 12V ELEC	.5/\$1.00 MAN	-7 \$1.00 600 1.35 1.75 6.00
A two piece 3½ Digit A/D	1103 1024 bit RA	M \$4.75	
Converter System for panel	NEC 6003 2048 bi	t RAM\$9.50	HOLD COUNT, OUTPUT STROBE \$6.75
meters and dym's. \$39.95	l 1101 256 bit RAM	\$1.75	HOLD COUNT, OUTPUT STROBE \$6.75 5314 — CLOCK CHIP 6 DIGIT HOLD COUNT, OUTPUT STROBE\$6.75
	1702A UV PROM 8223-PROGRAMMA	\$24.00 BLF	5316 — ALARM CLOCK CHIP\$6.75
TIS 73 N FET\$.50 2N4891 UJT\$.50	ROM		2513 — 64x7x5
ER900 TRIGGER DIODES4/\$1.00	MM5203-2048 BiT		CHARACTER GEN\$9.95
2N6028 PROG. UJT\$.75	ERASABLE PROM	\$24.00	2516 64x6x8 STATIC
VERIPAX PC BOARD	Conductive Elast		SANKEN AUDIO POWER AMPS
This board is a 1/6" single sided paper epoxy board, 4½"x6½" (standard veripax), DRILLED and	profile calculator	keyboard. A	Si 1010 G 10 WATTS \$ 6.40
paper epoxy board, 4½"x6½"	1 Z-/4" × 31/4" × 1/2	" flex kev.	Si 1010 G 10 WATTS \$ 6.40 Si 1025 E 25 WATTS \$17.95 Si 1050 E 50 WATTS \$24.95
ETCHED which will hold up to	198K-6 keyboard i	K-⊢C buttons	Si 1050 E 50 WATTS\$24.95
ETCHED which will hold up to 21 single 14 pin IC's or 8, 16 or LSI DIP IC's with busses for	with off, on switch	h\$6.00	4 WATT IR LASER DIODE \$7.95
or LSi DIP IC's with busses for power supply connections. Is	CT5005 12 DIGIT		
also etched for 22 pin connec-	CALCULATOR CHIE	PS\$7.95	LINEAR CIRCUITS LM 309K 5V 1A REGULATOR\$1.50
tor. \$5.25	TTL IC SE	RIFS	309A VV HARBOLLANDR \$.58 301/748-Hi Per. Op. Amp \$.30 LM 320 — 5 or — 15 V REG \$ 1.75 LM 376 — V to 37V POS REG. \$.58 741A or 741C OP. AMP \$ 31
FLV 100 VISIBLE LED\$.50	74L00— .30	7476— .45	301/748-Hi Per. Op. Amp\$.30
ME-4 IR LED	7400— .17	7480— .61	LM 320 —5 or —15 V REG\$1.75
MT-2 PHOTO TRANS \$.60	7401— 17 7402— 17	7483— .99 7485—1.30	741A or 741C OP. AMP\$.31
GREEN GAP OSL-16 LED	/403— .1/	7486— .48	709C OPER. AMP\$.25
RED GAP OSL-3 LED \$.40 14 PIN DIP SOCKETS \$.40	7404— .21	7490— .71	709C OPER. AMP. \$ 25 340T-5, 12, 15, 18, 24V POS. REG. TO-220 \$1.75 101 OPER. AMP. HI PERFORM. \$.75
16 PIN DIP SOCKETS \$.50	7405— .21 7406— .37	7491—1.10 7492— .75	101 OPER. AMP. HI PERFORM\$.75
10 WATT ZENERS	/40/— .3/	749371	LM 308 Oper. Amp., Low Power \$1.05
3.9, 4.7 OR 5.6 V	7408— .23 7410— .17	7495— .85 7496— .85	747—DUAL 741. \$.75
3.9, 5.6, 6.8 OR 12 V\$.30 EA.	7411— .27	82201.50	LM 3900—QUAD OP. AMP \$.49
	741245	74107— .45	LM 324—QUAD 741\$2.20
Silicon Power Rectifiers	7416 37	74121— .55 74123— .91	747—DUAL 741 \$.75 537—PRECISION OP. AMP. \$.260 LM 3900—QUAD OP. AMP. \$.49 LM 324—QUAD 741 \$.20 560—PHASE LOCK LOOP \$.250 561—PHASE LOCK LOOP \$.250 565—PHASE LOCK LOOP \$.250 567—TONE DECODER \$.285 703—RF-IF AMP. \$.41
PRV 1A 3A 12A 50A	741737	74125— .65	565-PHASE LOCK LOOP\$2.50
100 .06 .14 .30 .80	/4201/	74126— .70 74150— .99	703_RF-IF AMP \$.41
200 .07 .20 .35 1.15	7427— .31	74151— .85	LM370-AGC SQUELCH AMP\$1.15
400 .09 .25 .50 1.40	7430— .17	74153—1.05 74154—1.49	555—2 μs — 2 HR. TIMER\$.88
600 .11 .30 .70 1.80 800 .15 .35 .90 2.20	7437— .41	74157—1.19	1458 DUAL OP AMP \$.60
800 .15 .35 .90 2.20 1000 .20 .45 1.10 2.60	7438— .35	74163—1.49 74164—1.79	LM 380-2W AUDIO AMP\$1.39
	/4401/	74164—1.79 74165—1.79	703—RF-1F AMP. \$41.15 1M370—AGC SQUELCH AMP. \$1.15 555—2 µS — 2 HR. TIMER \$88 1456 OP. AMP. \$95 1458 DUAL OP. AMP. \$60 LM 380—2W AUDIO AMP. \$1.39 LM 377—2W Stereo Audio AMP. \$2.50 LM 381—STEREO PREAMP \$1.69
REGULATED MODULAR	7442— .95	74173—1.55	IM 382—DUAL AUDIO PREAMP \$1.69
POWER SUPPLIES	7445—1.05	74175—1.80 74177—1.50	IM 311HIPER COMPARATOR 5 .95
+ -15VDC AT 100ma 115VAC INPUT \$24.95	7447—1.10	74181—3.50	LM 319—Dual Hi Speed Comp. \$1.15 LM 339—QUAD COMPARATOR\$1.45
5VDC AT 1A, 115VAC INPUT \$19.95	7448—1.10	74192—1.45	TRIACS SCR'S
12V .6A\$24.95	7450— .17 7472— .33	74193—1.30 74195— 89	PRV 1A 10A 25A 1.5A 6A 35A
	7473— .41	74195— .89 75324—1.75	100 .40 .70 1.30 .40 .50 1.20
IN 4148 14/\$1.00		75491—1.10	200 .70 1.10 1.75 .60 .70 1.60
Terms: FOB Cambridge, Mass. Send		CON	400 1.10 1.60 2.60 1.00 1.20 2.20
Check or Money Order, Include Postage, Minimum Order \$5.00.	8038C IC VOLTAGE	TOR \$4.95	600 1.70 2.30 3.00 3.00
. cotago. minimum order \$5.00.	I MOLLED GOOTLEA	φτ.σσ	Hamahira St. Cambridge Mass

SOMERVILLE, MASS. 02143 TEL. (617) 547-4005

Send 20c for our catalog featuring Transistors and Rectifiers; 145 Hampshire St., Cambridge, Mass

WE SHIP OVER 95% OF OUR ORDERS THE DAY WE RECEIVE THEM

INTERNATIONAL ELECTRONICS UNLIMITED

10% OFF

ON ORDERS OVER \$25.00

.)
TTL	AND THE	<u> </u>
Ea.	Ea.	Ea. 74141 \$ 1.23
7400 \$.19	7447 \$1.15	74145 1.15
7401 .19	7448 1.15	74150 1.09 74151 .89
7402 .19	7450 .24	74153 1.29
7403 .19 7404 .22	7451 .27 7453 .27	74154 1.59
7404 .22	7454 .39	74155 1.19
7406 .39	7460 .19	74156 1.29
7407 .39	7464 .39	74157 1.29 74161 1.39
7408 .25	7465 .39 7472 .36	74163 1.59
7409 .25 7410 .19	7473 .43	74164 1.89
7411 .29	7474 .43	74165 1.89
7413 .79	7475 .75	74166 1.65 74173 1.65
7415 .39	7476 .47 7483 1.11	74175 1.89
7416 .39 7417 .39	7483 1.11 7485 1.39	74176 1.65
7420 .19	7486 .44	74177 .99
7422 .29	7489 2.75	74180 1.09
7423 35 7425 39	7490 .76 7491 1.29	74181 3.65 74182 89
7425 .39 7426 .29	7492 .79	74184 2.69
7427 .35	7493 .79	74185 2.19
7430 .22	7494 .89	74190 1.59
7432 .29 7437 .45	7495 .89 7496 .89	74191 1.59 74192 1.49
7437 .45 7438 .39	74100 1.65	74193 1.39
7440 .19	74105 .49	74194 1.39
7441 1.09	74107 .49	74195 .99
7442 .99	74121 .57	74196 1.85
7443 .99 7444 1.10	74122 .53 74123 .99	74197 .99 74198 2.19
7445 1.10	74125 .69	74199 2.19
7446 1.15	74126 .79	74200 7.95
LOW POWE	R TTL	
74L00 .33	74L51 .33	74L90 1.69
74L02 .33	74L55 .33 74L71 .33	74L91 1.45 74L93 1.69
74L03 .33 74L04 .33	74L71 .33 74L72 .49	74L95 1.69
74L06 .33	74L73 .69	74L98 2.79
74L10 .33	74L74 .69	74L164 2.79
74L20 .33	74L78 .79 74L85 1.25	74L165 2.79
74L30 .33 74L42 1.69	74L85 1.25 74L86 .69	
HIGH SPEED		
74H00 .33	74H21 .33	74H55 .39
74H01 .33	74H22 .33	74H60 .39
74H04 .33	74H30 .33	74H61 .39 74H62 .39
74H08 .33 74H10 .33	74H40 .33 74H50 .33	74H72 .49
74H11 .33	74H52 .33	74H74 .59
74H20 .33	74H53 .39	74H76 .59
8000 SERIES	ΠL	
8091 .59	8214 1.69	8811 .69 8812 1.10
8092 .59 8095 1.39	8220 1.69 8230 2.59	8812 1.10
8121 .89	8520 1.29	8830 2.59
8123 1.59	8551 1.65	8831 2.59
8130 2.19	8552 2.49	8836 .49 8880 1.33
8200 2.59 8210 3.49	8554 2.49 8810 .79	0800 1.33
9000 SERIES	TIL	1
9000 3ERIES		9601 99

Data sheets supplied on request Add \$.50 ea. for items less than \$1.00

CMOS

	_				
74C00	.39	74C74 1.15		74C162	3.25
74C02	.55	74C76 1.70		74C163	3.25
74C04	.75	74C107 1.50		74C164	3.50
74C08	.75	74C151 2.90		74C173	2.90
74C10	.65	74C154 3.50		74C195	3.00
74C20	.65	74C157 2.19	1	80C95	1.50
74C42	2.15	74C160 3.25		80C97	1.50
74C73	1 5 5	74C161 3 25			

APRIL SPECIALS

5001	12 DIG 4 fun	ct fix dec	S2.95		1103	256 bit RAM	MOS	52.95
5002		exp btry pwr	4.95		5260	1024 bit RAM	1	2.95
5005	12 DIG 4 fun		6.95		5261	1024 bit RAM	1	2.95
5725		t chain & dec	2.25		5262	2048 bit RAM	1	7.95
5736	18 pin 6 DIG		4.45		2102	1024 bit statio	RAM	6.95
5738	8 DIG 5 fund		4.95		5203	UV Eras.		19.85
5739	9 DIG 4 fund		4.95		HP50827414	4 digit commo	on cathode	
5311	28 pin BCD 6		4.95		00027717		P11 bubb e	len: 2.75
		BCD 4 dig mux	4.95		MAN 7	Red 7 seg .270		.99
5312		BCD 6 dig mux	4.95		MAN 66	Red .6" space		3.50
5313			4.95		MAN 6	Red .6" solid		3.95
5314	24 pin 6 dig		5.95		MAN 1	Red 7 seg27		1.50
5316	40 pin alarm	4 dig	3.93		MAN 2	Red alpha nur		3.39
					WANZ	Red alpha nui	1132	3.35
74C00	\$.29	\$25/100 I	74L00	S .25	\$20/100	7454	\$.25	\$20/100
74C02	.49	40/100	74L02	.25	20/100	7460	.15	10/100
74C02	.59	50/100	74L03	.25	20/100	7490	.59	50/100
74010	.59	50/100	74L04	.25	20/100	7493	.59	50/100
	.59	50/100	74L04	.25	20/100	8836	.19	15/100
74C20			74L10	.25	20/100	380	1,19	00/100
74C73	1.15	100/100		.25	20/100	565	1.95	50/100
74C107	1.25	110/100	74L51		30/100	2N3933	TO-72	1.29
74C160	2.75	250/100	74L72	.35				
74C164	2.95	260/100	74L73	.49	40/100 I	40636	TO-3	1.55
80C97	1.25	110/100	74L74	.39	30/100			

MEMORIES w/data

1101	256 bit RAM MOS	\$1.75
1103	1024 bit RAM MOS	4.95
5203	2048 bit eras, PROM	24.95
5260	1024 bit RAM low power	3.95
7489	64 bit RAM TTL	2.75
8223	Programmable ROM	3.95

CALCULATOR & CLOCK CHIPS w/data

5001	12 DIG 4 funct fix dec	3.95
5002	Same as 5001 exc btry pwr	7.95
5005	12 DIG 4 funct w/mem	8.45
MM5725	8 DIG 4 funct chain & dec	2.79
MM5736	18 pin 6 DIG 4 funct	4.95
MM5738	8 DIG 5 funct K & Mem	7.95
MM5739	9 DIG 4 funct (btry sur)	6.95
MM 5311	28 pin BCD 6 dig mux	6.95
MM 5312	24 pin 1 pps BCD 4 dig mux	6.95
MM 5313	28 pin 1 pps BCD 6 dig mux	7.95
MM 5314	24 pin 6 dig mux	8.95
MM 5316	40 pm alarm 4 dig	8.95

LED & OPTO ISOLATORS

MV 10B	Red TO 18	S .25 ea
MV50	Axial leads	.20
MV5020	Jumbo Vis. Red (Red Dome)	.25
	Jumbo Vis. Red (Clear Dome)	.25
ME4	Infra red diff. dome	.60
MAN1	Red 7 seq270"	2.50
MAN2	Red alpha num .32"	4.95
MAN4	Red 7 seg. 190"	2.15
MAN5	Green 7 seg270"	2.95
MAN6	.6" high solid seg	4.95
MAN7	Red 7 seg270"	1.35
MAN8	Yellow 7 seg270"	3.95
MAN64	.4" high solid seg	3.50
MAN66	.6" high spaced seg	4.65
DL707	Red 7 seg3"	2.15
MCD2	Opto-iso diodes	1.09
MCT2	Opto-iso transistor	.69

DTI

930 S	17 937	S 17	949 S	.17
932	17 944	. 17	962	.17
936	17 946	17	963	.17

4000 SERIES -**RCA FOUIVALENT**

,					
CD4001	55	CD4013	1 20	CD4023	55
CD4009	85	CD4016	1.25	CD4025	55
CD4010	85	CD4017	2 95	CD4027	1 35
CD4011	55	CD4019	1 35	CD4030	95
CD4012	55	CD4022	2 75	CD4035	2 85

LINEAR **CIRCUITS**



Quad Op Amp
Quad Comparator
Pos Volt Reg
(5V-6V-8V-12V-15V-18VAGC/Squelch AMPL
AF-IF Strip detector
AM/FM/SSB Strip TO-22G TO-5 or DI' DIP DIP DIP DIP 1.15 .79 3.25 .59 2.69 1.29 1.25 370 372 373 376 380 380 380 555 560 565 566 709 710 723 739 741 747 748 1304 1304 1305 Pos. V Reg
2w Stereo amp
2w Audio Amp
6w Audio amp
Lo Noise Dual preamp
Lo Noise Dual preamp mDIP DIP DIP 1.69 .79 .99 2.75 2.75 2.65 2.95 .29 .39 .29 .69 Prec V Reg mDIP DIP Phase Locked Loop Phase Locked Loop Phase Locked Loop Function Gen Operational AMPL Hi Speed Volt Comp Dual Difference Compar Dual Difference Compar V Reg Dual Hi Perf Op Amp Comp Op AMP Dual 74 1 Op Amp Freg Adj 741 FM Mulpx Stereo Demod FM Mulpx Stereo Demod Dual Comp Op Amp Stereo multiplexer Dual LM 211 V Comp TV-FM Sound System FM Det-LMTR & Audio preamp .35 .79 .39 1.19 .82 .69 mDIP DIP DIP DIP 2.75 1.89 .69 LH2111 3065 3075 Audio preamp
Quad Amplifier
Core Mem Sense AMPL
Core Mem Sense Amp
9 DIG Led Cath Drvr DIP .79 .39 .79 .79 2.50 .39 .39 .79 .89 3900 7524 7534

SHIFT REGISTERS

Dual Perepheral Driver Dual Peripheral Driver (351) Dual Periph. Driver Quad Seq Driver for LED Hex Digit Driver

MM 5013 MM 5016 MM 5058	1024 bit accum, dynamic 500/512 bit dynamic 1024 bit static	mDIP mDIP DIP	\$1.95 1.75 3.95
MM 5058	1024 bit static	DIP	3.95
SL-5-4025	Dual 64 bit static	DIP	1.50

mDIP mDIP mDIP DIP



Shipment will be made via first class mail - postage paid in U.S., Canada and Mexico - within three days from receipt of order. Minimum order --\$5.00. California residents add sales tax.

INTERNATIONAL ELECTRONICS UNLIMITED MONTEREY, CA. 93940 USA P.O. BOX 1708 PHONE (408) 659-3171

CURTIS INDACHRON TIMER \$1.9 0-10,000 Hour Dial, Chemical Action. Works On 5V DC. 11/2	5
0-10,000 Hour Dial, Chemical Action. Works On 5V DC. 11/2 x 1/4" x 1/4", Adhesive Backed.	,,
74\$206 MEMORY IC—SCHOTTKY \$3.2 256 X 1 TTL Bipolar Ram Hi-Speed 3 Chip-Enable Lines. Full Data Furn	5
- SEVEN SEGMENT READOUTS -	
H-P 5082-7730 7-Segment LED Readout 3 Digit \$1.7 DL-707 The Universal LED Readout 1.9	5
MAN-1 By Monsanto 2.5	0
MAN-1A By Monsanto—Late Version 2.7	5
MAN-4 Monsanto 1.99 XMN-101 XCITON 8	5
DL-707 The Universal LED Readout 1.9	5
LEDR-8 8 Resistors in 16 Pin Dip—For All 7-Segments9! CA3081 7-Segment LED Drivers Comm. Emit. NPN9!	5
— LED'S —	,
MV-50 7 for \$1.00 MV-5020 5 for \$1.00 MV-2 Green 3 for \$1.00 NSL-100 Red 5 for \$1.00)
7/00 10%	
7400 7401 7402 7403 7404 7408 7410 \$ 10 7420 7430 7440 7450 7453 7454 7460 11 7441 7442 7445 7446 7447 7448 7483 90	5
7441 7442 7445 7446 7447 7448 7483	ŝ
747645 7412155 74156 1.31 7489 2.65 79123 95 74192 1.41	5
7413 .75 74107 .48 74154 1.5 7476 .45 .74121 .55 .74156 1.3 7489 2.65 .79123 .95 .74192 1.4 7495 .88 .74151 .95 .74193 1.3 7496 .88 .74153 1.25 .74195 1.25	5
741!	
00 02 03 04 10 20 30\$.32 0850 73, 7475 8660 90, 93, 95 1.50	2
7400 0 4400	
74C00 34 74C04, 74C10 65 74C76 1.60)
26.5 Shift Register	
8223 Rom-Programmable—32 8-Bit Words 4.75	
LM301 Hi-Perf On-Amn LM307 "Super 741" On Amn 35	1
LM301 Hi-Perf. Op-Amp, LM307 "Super 741" Op Amp. 33 LM709 Universal Op. Amp, LM741 "Standard" Op Amp. 35 Buy 10 of Any Group & Get a Big Asst. of Circuits10 for 3.00	
565 PLL, 566 Funct. Gen., 567 Tone DecoderEach 2.75	
555 Timer w/Specs & Applications	
LM308 Ultra Hi-Imped. Op-Amp 99	
LM309K SV 1A. Regulator 1.25 LM308 Ultra Hi-Imped. 0p-Amp 99 5314 Digital Clock Chip—With Data 6.99 5316 Digital Alarm Clock Chip—With Data 8.99 CA3047 Hi-Output 0p-Amp .50	
	-
ALL IC'S BY FIRST CLASS MAIL — NO EXTRA COST!	-
JTM ASSOCIATES P.O. BOX 843 MANCHESTER, MO. 63011	١
Circle 101 on reader service card	

Circle 101 on reader service card

DIGITAL/analog multimeters, logic probes-guaranteed lowest prices. Free catalog. ELECTRO INDUSTRIES, 4201 Irving Park, Chicago, IL 60641

FREE bargain catalog. LED's, transistors, IC's, PUT's, relays, xtals, unique microminiature components, misc. CHANEYS, miniature components, misc. Box 15431, Lakewood, CO 80215

NT TO USE WITH YOUR SCOPE MULTITRACER



\$19.95-CHECK OR MONEY ORDER PAY MORE?

BOX 14, LESCO ELECTRONICS, SKOKIE, ILL. 60076



INDIVIDUAL diagrams, servicing manuals, Radio-Television. Information. SUPREME PUBLICATIONS, 1760 Balsam, Highland Park, IL 60035

LED readouts—Wow! Jumbo 0.6" digit replaces Litronix DL-747, \$1.95—0.3", replaces places Litronix DL-747, \$1.95—0.3", replaces DL-707, DL-704, (specify type) \$1.50—kit of 150 discrete LED's builds 3½" 6-digit clock, \$25.00. Clocks described in Jan. '75 Radio-Electronics. Digital liquid crystal wrist-watch displays, \$3.95! All new, guaranteed. Bargain catalog, .50c DIAMONDBACK ENGINEERING, P.O. Box 194, Spring Valley, IL 61362

LOW-noise resistors—¼ W, 5% carbon film from 10 — 3.3 megohms for 3½c each. Fifty of one value for \$1.25. 1N4148 diodes for 6c. 75c postage. Free samples/specifications. COMPONENTS CENTER—RE, Box 13.4 Now York NY 10029 134, New York, NY 10038

MEMORY SYSTEM \$125.00

1024 core memory system, 1024 words memory 8, 9, or 10 bits/word. Random access, with all logic, register, timing, control, core select and sense functions in one package. New, with 60 page booklet includes schematics, Measures only 9x4x1 inches. Good start for

TONE GEN. BOARD

3 Octave tone gen. board from Magnus Organ. Unused, as is, with instructions & amp. \$9.95, two for \$18.00.

PIANO KEYBOARD \$9.95

For use with above organ or synthesizer, etc.

MULTI-USE XFMR \$8.95

Output 18 V @ 6 amp; 17 V @ 6 amps; 10 V @ 10 amp. Brand new, \$8.95 ea, 2 for \$15;

PHOTO-STROBE

Made for Instamatic but useful on any camera with instructions provided. Info also on trick uses, automotive strobe, slave strobe, automotive strobe. Psychadelic repetitive strobe, etc. Complete with charger & Nickel Cadmium batteries

\$9.00 or 3 for \$24.00

Please add shipping cost on above. FREE catalog

Meshna SURPLUS ELECTRONIC MATERIAL

P.O. BOX 62 E. LYNN MASS, 01904

Circle 103 on reader service card

AM FM STEREO MULT<u>IPLEX</u> CHASSIS



12"x5%"x4%"

AM/FM STEREO MUTIPLEX chassis, ready to go, requires 16 to 18 volta AC @ 2 amps. Ideal for custom installation.Each channel rated @ 15 watts. Has function switch, tuning control, volume control, balance, bass & treble controls. With pointer, but no escutchon.

STOCK NO.R5247 STOCK NO. R9858 \$26.50 ea.

2/50.00

Transformer for above, \$3.75 2/7.00

BURROUGHS PANAPLEX DISPLAY



BURROUGHS PANAPLEX II,12 digit display, BR13251 is a multidigitsegmented, thin panel display in a common envelope. Any or all digits may be used, along with right hand decimals.Characters are 0.25", and are ideal for clocks, counters, calculators etc. Compatible with DTL, TTL, CMOS. Display is neon glow discharge, and requires 160 VDC. We supply socket. 14 pages of data and applications.

STOCK NO.R5220

\$5.75 ea.

2/10.00

Include sufficient postage. Excess refunded. Send for new Catalog 13, just out, with many electronic bargains.



CODE on mai

For

faster

service

USE

ZIP

BILL GODBOUT ELECTRONICS BOX 2673, OAKLAND AIRPORT, CA 94614

LINEAR VARIETY PACK--ONE EA. OF THE FOLLOWING ICS: 555 TIMER, 741 OP AMP, 3900 QUAD OP AMP, 5558 DUAL OP AMP, SUR LETTS FIFT 723 REGULATOR, 309K 5V 1A REGULATOR, 339 70 WATT RMS

QUAD COMPARATOR. ALL OF THE ABOVE FOR

AMP TOP KIT-USE IT MONO FOR GUITAR OR PA, OR AS

BENCH A FAVOR FOR

\$10.95 +SHIPPING

\$3.95 A 35W/CHANNEL STEREO AMP. 8 OHM OUT, SHORT CIRCUIT PROTECTED, NOISE & HUM DOWN 80 DB AT 70W OUT. KIT COMES LESS CHASSIS AND HARDWARE, U.S. PPD FOR \$49.95

> DUAL TRACKING REGULATED SUPPLY-UNDER #1 TO MORE THAN #18V. PER-FECT FOR OP AMPS AND BREADBOARD-ING. FULLY PROTECTED AGAINST INPUT AND OUTPUT SHORTS, AS WELL AS THERMAL OVERLOAD. KIT DOES NOT INCLUDE LINE

SAVE CORD, HARDWARE, OR ON C-CHASSIS. DO YOUR MOS. TTI I INFARS. MORE KITS. READOUTS, RE-SISTORS, CAPACI-

TORS, TRANSISTORS, & MORE...DUR FLYER (SEND STAMP + ADDRESS) TELLS ALL

SEND FOR IT! BE SURPRISED. nclude 50d handling on orders under \$10.00

CALIFORNIA RESIDENTS ADD sales tax

LISTEN TO Spectacular

4-Channel Sound!

Latest High-Quality Quadraphonic Performance with the Vista SQ-3 Decoder

EXCLUSIVE CBS LICENSED CIRCUITY, SUPERB RESPONSE AND CHANNEL SEPARATION

FULL LOGIC, WAVE MATCHING AND VARIABLE BLEND

KIT SQ-3

ALL NECESSARY PARTS EXCEPT CASE AND +20V 75mA POWER SUPPLY

Shipped prepaid In USA \$2.00 additional for CANADA

TTL

NY State add Tax

CMOS

PHOTOLUME CORPORATION

118 East 28th STREET, New York, N.Y. 10016

Circle 104 on reader service card

7448 7450 7451

7453

7480

7485 7486 20% Discount for 100 pcs. Combined 7400's (Except Specials)

74164
74165
174166
174166
174166
174166
174166
174170
3.00
74173
1.85
74C164
3.74174
1.85
74C195
3.00
74175
1.85
74176
3.9
74177
1.85
3.9
74177
1.85
3.9
74177
1.85
3.9
74177
1.85
3.00
(Zener)
25
74181
3.75
1N456
6/\$
227
74182
1.00
1N456
6/\$
227
74182
2.30
1N485A
6/\$
2.25
74181
2.30
1N485A
6/\$
2.25
74187
1.50
1N1184
1.74
1.50
1N1184
1.15
1.39
74193
1.50
1N1184
1.15
1.75
74192
1.50
1N1184
1.15
1.75
74193
1.50
1N4001
1.75
1N4184
1.15
1N4004
1.15
1N4

1.70 1.80 6/\$1 .09 .10

2.50 74C107 2.50 74C151 2.50 74C154 1.75 74C163 3.00 74C164 1.75 74C173 1.85 74C195

CT 5001 CALCULATOR CHIP ea. 3.95

Close out sale while they last, w/data

8270 DIP 4-BIT SHIFT REGISTER

4-Bit Shift Register -- parallel and serial input and output; data entry is synchronized with clock pulse.

CARBON RESISTORS

Carbon Resistors '2-Watt 5%-full prime all values in stock.10 per value (min imum quantity). ten for \$.4

ea. only \$.89 10 for \$7.50
Brand new 20 turn precision trimmers. These are prime parts mostly individually packed in scaled envelopes. These values in stock:

50 OIM 1 K 5 K 25 K 5 K 10 K

POTTER BRUMFIELD

e KHP Relay 4 PDT 3A Contacts \$1.50 10/\$14.00 ea. \$1.75 10/\$15.7 VDC (650 coil) ea. \$1.5 VAC (10.5 MA coil) ea.

DIODE ARRAY

10 1N914 Silicon Signal Diodes in one

package 20 leads spaced .1"; no common connections. ea. \$.25 10 for \$2.25

IC SOCKETS

PBC Mounting 24 pin---\$.75 40 "--\$1.25

SEND FOR FREE FLYER!

C.O.D. PHONE ORDERS ACCEPTED--\$10 MINIMUN

parts surplus and tested; leads, gold or solder. Orders for 55 or more shipped prepaid; smaller orders add California residents add Sales Tax. shipped within 24 hours p. 0. Box 41727 Sacramento, Ca. 95841

Circle 105 on reader service card

MiniMicroMart

1101A	256 x 1		\$2.110
2202-3	1024 x 1	1500 ns	\$8.25
2102	1024 x 1	1000 ns	\$8.10
2102-2	1024 x 1	650 ns	\$9.15
2102-1	1024 x 1	500 ns	\$10.13
1103	1024	Dynamic	\$3.110

Less 10% - 8 or more, 15% - 32 or more. 20% - 100 or more

A.S.C.I.I. Computer Keyboard

Full 60 key ASCII Code Keyboard, plus space bar, two key roll over, debounced, with latest TTL and MOS encoder, a rare find, supply limited. \$40.00

Universal Asychronous Receiver/Transmitter **COM 2502 UART**

40 pin MOS ceramic. pin for pin with any standard version, and perfect for the UART TV type-writer add on. Feb. R-E, supply limited. \$9.95.

TV Typewriter II, Feb. R-E, all IC's w/memories, \$79.95.

Microprocessor Circuits

miciop		
8008 CPU-IC	\$120 value	\$47.50
	w/8-1101A's	\$60.95
	w/8-2102's	\$103.95
8080 CPU-IC	\$320 value	\$169.95
	w/8-1101A's	\$179.95
	w/8-2102's	\$209.95

Mini Computer Kits

BASIC 8008-8080 Mini Kits \$169-\$289, w/PC Boards, CPU, IC's, memory, write for details IC KITS FOR ALL POPULAR MINIS-Mark 8-Altair 8800-Scelbi.

NOTE: None of the above include power supply, resistors, caps connectors, etc.

Power Supply Kits

Components for any required supply

Send stamped, self addressed envelope for details on all of above and on many other items of interest.

Mini Micro Mart 1618 James Street

Syracuse, New York 13203 (315) 422-4467

Circle 106 on reader service card

APRIL SPECIALS

8008 Processor \$49.95 8080 Micro Processor \$249.95
1101 256 x 1 RAM 2.25 N8T97 HEX Inverter 2.95
2102 1024 RAM 7.95 1702 2048 EROM 29.95
5203 2048 EROM 19.958111 256 x 4 N Channel 11.95 4.00 CD4001 \$.55 25ea CD4002 .55 1.40 .60 .55 .55 1.50 1.40 2.75 1.25 1.50 Miniature Aluminum Electrolytic Capacitors MINIATURE Alluminum Electrotytic Capacitors

MFD-VOLTS 9 99100

47UFD/50V 14 12 11 474UFD/25V 19 15 .14

1UFD/16V 14 12 .11 100UFD/16V 19 .15 .14

1UFD/50V 15 .12 .11 100UFD/25V .24 .18 .17

2.2UFD/50V 14 .12 .11 220UFD/16V .24 .18 .17

3.3UFD/25V 14 .12 .11 220UFD/25V .24 .18 .17

4.7UFD/25V 14 .12 .11 220UFD/25V .35 .25 .24

10UFD/16V 14 .12 .11 470UFD/25V .49 .39 .35

10UFD/25V .14 .12 .11 470UFD/25V .49 .39 .35

10UFD/25V .14 .12 .11 1000UFD/16V .49 .39 .35

22UFD/16V 14 .12 .11 1000UFD/16V .75 .60 .55

22UFD/25V .15 .13 .12 2200UFD/16V .75 .60 .55

47UFD/16V 17 .14 .13 Axial or Radial Lead Type 1.50 2.50 .55 .55 1.25 4 45 70 65 65 1.15 3.25 3.25 1.50 2.90 3.50 2.90 3.00

50 VOLT CERAMIC DISC CAPACITORS .001 mf. 5c 3.5c 3c .033 mf. 6c 4c .0047 mf. 6c 4c 3.5c 7.047 mf. 6c 4c .01 mf. 5c 3.5c 3c 1.1 mf.12c .022 mf. 6c 4c 3.5c 100 pr 6c 4c 3.5c pr 6c

MPS-A05

5/\$1

TRANSISTORS

2N3905

4/\$1

2N918

25 2N2906A

4/\$1 2N3906

2N2219A

3/\$1 2N2907A

5/\$1 PN4249

4/\$1

2N2221A

4/\$1 2N3055

2N2369

5/\$1 2N3055

2N2369A

4/\$1 2N3725A

2/\$1 2N4409

5/\$1

2N2228A

5/\$1 2N3725A

2/\$1 2N5129

19

2N2369A

4/\$1 2N3903

4/\$1 C106B1-SCR-2/\$1

Cal. & CIK. Chips

CSkts

WALL or I.V. DIGITAL CLOCK

| Cal. & Clk. Chips | LC Skts | Short | Chips | C | Ch

Satisfaction Guaranteed. All Items 100% Tested \$5.00 Min. Order — 1st Class Mail — No Charge California Residents — Add 6% Sales Tax Wholesale Outlets — Write for Special Discounts Write for FREE 1975 Catalog — Data Sheets .25€ each

P.O. BOX 822, BELMONT, CA. 94002 PHONE ORDERS - (415) 592-8097

Circle 107 on reader service card

LINEAR

LM300H LM301H/N LM302H \$.69 .29 .69 .31 .69 .35 LM741H/N \$ LM747N LM748N LM1303N LM1304N LM1307N LM1310P LM1458N LM1496N LM1556V CA3013 CA3023 CA3023 CA3025 CA3039 CA3060 CA3065N CA3080 C .89 .35 1.05 1.25 1.19 LM305H/N LM307H/N LM308H/N 1.00 .79 3.95 .99 1.85 1.70 2.15 2.25 1.35 1.15 2.46 2.80 LM309K .95 1.69 1.19 1.50 1.85 1.95 1.95 1.89 1.05 2.05 1.00 1.25 3.00 -3.00 .79 2.46 2.80 .75 .85 1.60 .70 3.25 8.25 LM370N LM380N LM380N NE531T NE536T NE5550N NE5550N NE5601 NE5601 NE5662 NE5662 NE5667H/N 1.85 2.50 2.50 2.50 .65 1.75 5.75 .55 .75 .49 LM3905 LM7805 8038B LM9601 2.00 NE567H/N 2.00 .43 .29 .29 .29 .55 1.75 75451 LM703H/N LM709H/N 75452 75453 75491 LM710H/N LM711H/N LM723H/N LM733H/N .79 .89 75492 75494 75324N

1/4 W 5% CARBON COMP RES STORS 000 UP 5-25 30-95 100-495 500-995 .0275 .03

LM567F

1.50

M739N

LM565H

All Std. Values — 5 Ea. Nin. Add 5¢ per value if sorting is required

PROJECTS LEDS 8000 Series 8263 \$ 7.00 MV 10 5/1 8091-98 .55 8267 4.00 MV 500 6/1 8123 1.50 2513 11.00 MV 5024 5/1 8223 3.00 2518 7.00 MAN-1 1.95 8263 7.00 2519 4.00 MAN-3 .95 8267 4.00 2524 3.95 MAN-4 1.95 8281 .85 2525 7.00 MAN-7 1.50 8281 .85 2529 4.00 DL 33 1.95 8283 1.15 4024P 2.25 DL747 2.50 8883 1.35

1.75

prices

 $1-25/64 \times 2-11/64$

WE'RE NOT LION ... QUALITY COMPONENTS Hard-to-beat

BRIGAR

EACH

BRAND NEW MALLORY CGS

80 400

10000 1100 35 $1-25/64 \times 2-11/64$ 28000 100 350 1-25/64 x 2-11/64

\$1.00 . 90

100 CFM, Mfr. Howard Ind. Model # 1075-10-3369

Miniature Cooling Fan

3000 rpm.

10000

115 VAC, 60 cycle, 20 watt,

Size: 4" blade, 3" deep.

Complete with blade guard and mounted on a flat metal plate. Features low noise level, high vol ume of air. Great for cooling electronics and electrical equipment.

7000 units in stock BRIGAR SPECIAL \$4.95 each

INCANDESCENT LAMPS

GENERAL ELECTRIC # 387 LAMPS

28 volts, .04 amps. Bulb style - T 1-3/4, Base mid. flanged.

40,000 in stock, BRAND NEW BOXED



MAIL COUPON FOR

10 Alice Street, Binghamton, New York 13904

• Tel.: 607-723-3111

SEND CHECK OR MONEY ORDER

MIN. ORDER \$10.00

Address City State Include postage, excess refunded. ==

Circle 108 on reader service card

LATE MODEL MAGNUS ORGAN COMPONENTS



R5244 3 Octave (37 note) integrated circuit tone generator board.





R5246 Late model 3 octave keyboard.

R5245 Amplifier

We have acquired a limited quantity of MAGNUS ORGAN We have acquired a limited quantity of MAGNUS ORGAN components. The R5244 tone generator is made up of 19 ICs, and discrete components. The R5246keyboard is a 3 octave keyboard used with the R5244 board. The R5245 amplifier is the matching amplifier for use with the tone generator, and is rated at 13 watts. The amplifier is complete except for the power transformer, (rectifiers & filters included on amplifier board.) board.)

bases of circuits and data included	
STOCK NO.R5244 Tone generator board	17.95
STOCK NO.R5245 Matching 13 watt amplifier	9.95
STOCK NO. R5246 3 Octave keyboard	19.95
STOCK NO.R5249 Transformer for amplifier board	3.75
One each of above four items	49.00
NOTE: Kaubaard and and	40.00

NOTE: Keyboard not sold separately. Sold only with tone board.

Include sufficient postage; Excess refunded. Write for new catalog 13, just of the press & loaded.



BOX 1, LYNN, MASSACHUSETTS 01903 Phone (617) 388-4705

Circle 102 on reader service card

Japanese Transistors

SPRING CLEARANCE SALE!

OEM	SP	ECI	AL	S
O LIV	· ·	,	~-	•

	Japanes	c Hallolo	1013	O.		I O	/
2SA52 2SA101 2SA103 2SA221 2SA473	.60 .70 .70 .60 .85	2SB463 2SB471 2SB474 2SB481 2SB492	1.65 1.75 1.75 2.10 1.25	2SC605 2SC619 2SC620 2SC627 2SC644	1.00 .70 .80 1.75 .70	2SC1237 2SC1239 2SC1293 2SC1317 2SC1347	2.00 2.80 .85 .60
2SA495 2SA497 2SA505 2SA562 2SA607	.65 .55 .65 .70 2.25	2SB495 2SB605 2SB606 2SC15 2SC24	.95 2.00 2.00 .65 .65	2SC645 2SC681 2SC684 2SC687 2SC696	.85 2.50 2.10 2.50 2.35	2SC1377 2SC1383 2SC1393 2SC1409 2SC1410	6.75 .75 .60 2.75 2.75
2SA613 2SA643 2SA647 2SA673 2SA679	1.00 .85 2.75 .85 2.25	2SC32 2SC33 2SC41 2SC49 2SC56	65 65 4.00 80 95	2SC710 2SC711 2SC712 2SC713 2SC732	.70 .70 .70 .70 .70	2SC1450 2SC1454 2SD30 2SD45 2SD64	1.00 2.75 .95 2.00 .75
2SA682 2SA699 2SA699A 2SA705 2SA714	.95 1.30 2.00 .55 2.50	2SC143 2SC154 2SC162 2SC163 2SC185	3.50 3.75 3.75 4.50 1.00	2SC733 2SC735 2SC739 2SC756 2SC774	.70 .70 .70 1.50 1.75	2SD65 2SD68 2SD72 2SD88 2SD120	.75 .70 1.00 1.50 .85
2SA720 2SA733 2SB22 2SB54 2SB56	.70 .65 .65 .70	2SC202 2SC206 2SC240 2SC261 2SC291	1.00 1.00 1.10 .65 .65	2SC775 2SC778 2SC783 2SC784 2SC785	2.00 3.00 1.00 .70 1.00	2SD130 2SD141 2SD151 2SD170 2SD180	1.50 2.25 2.50 2.00 3.00
2SB77 2SB128 2SB135 2SB152 2SB172	.70 2.50 .95 4.50 .55	2SC320 2SC352 2SC353 2SC371 2SC372	.75 .75 .75 .70 .70	2SC792 2SC793 2SC828 2SC829 2SC833	3.00 2.50 .75 .75 .70	2SD 198 2SD201 2SD218 2SD235 2SD261	2.50 2.50 5.00 1.00 .80
2SB173 2SB175 2SB178 2SB186 2SB187	.55 1.00 .60	2SC380 2SC387 2SC394 2SC458 2SC460	.70 .70 .70 .70 .70	2SC838 2SC839 2SC930 2SC945 2SC1010	.70 .85 .65 .65	2SD291 2SD292 2SD300 2SD315 2SD318	.85 .85 2.50 .75 .95
2SB235 2SB303 2SB324 2SB337 2SB364	1.95 .65 1.00 2.10 .65	2SC478 2SC482 2SC491 2SC495 2SC497	.80 1.75 2.50 .70 1.60	2SC1012 2SC1013 2SC1014 2SC1018 2SC1030	.80 1.50 1.50 1.50 3.25	2SD341 2SD350 2SD352 2SD389 2SD390	.95 3.50 .80 .95

Power Units S	STUH SPECIA			METAL	EPOXY		METAL	EPOX
	are included		2N718 2N918	.27	.15	2N2222A	.35	.22
2N441 2N458A 2N538 2N1015	To-36 To-3 Mt-36 Mt-1	2/1.00 4/1.00 3/1.00	2N930 2N1420 2N1613	.55 .25 .25 .65	.25 .18 .15 .30	2N2369 2N2484 2N2904 2N2905	.18 .75 .50 .50	.13 .35 .20
2N1725	To-61	1 00 2/1.50	2N1711 2N2218	.65	.30	2N2905A 2N2906	.85	.35
2N2288 2N3054 2N3055	To-3 To-66 To-3	2/1.00 5/1.00 4/1.00	2N2219 2N2219A 2N2221	.50 .75 .25	.22 .30 .17	2N2907 2N3053 2N3251	.40 .20 .75	.16 .35
2N5002 2N5296/Tip31	To-59 To-220	3/2.00 7/1.00	2N2222	.23	.17	2N4036	.75	.35
	Mo	torola MK-2	O Power Tran	sistor Mo	unting Kit	.75		

Integrated (Circuits
UA703C	.40
CA3066	4.00
CA3068	6.50
MC1305	1.50
Replacement for 2 221-36, 221-37,	

World's Smallest Transistor! Now Available! Lin Case Size: .04 x .04 x .03 in. PNP 3	mited Time Only! 3:00 NPN 3:00
Transistor Grab Bag - Germanium and Silicon smal transistors. 95% yield.	sigs and power 30/1.00
Automotive Ignition Power IC Darlington 7 amp BVCEO 500v.	8.95

CITIZEN BAND A	PPLICATION
NPN Silicon 2	
RF Power Tr	ansistors
2SC781	3.25
2SC799	4.75
2SC1306	5.75
2SC1307	6.75
2SC517	4.75
MRF8004	3.00

	TRANSIST	RECTIF	IERS	
High Volta	ge TV Trans	istors		10
BU204	1300v	4.00	1N4001	.90
BU205	1500v	4.75	1N4002	1.00
BU206	1700v	5.80	1N4003	1.10
BU207	1300v	5.50	1N4004	1.20
BU208	1500v	6.75	1N4005	1.30
BU209	1700v	8.25	1N4006	1.40
2SC1170	1100v	4.00	1N4007	1.50
2SC1172B	1100v	4.50		
2SC1308	1100v	5.00	12' Line	Cords
2\$D380	1100v	6.00	2.25	ea

	î	
	EXTRA VALUES!	
	SCRs and Triacs, In-39, To-18	
	To-64. To-48	
	Sil glass rectifiers	5
	Germ. glass rect	5
	1N914 sil fast switch	3
	FET ONE AET NUMBER OF THE	
	FET 2N5457 N channel To-92 plastic	4
	NPN To-92 25v CEO HFE 25-100	
	100-300, and 300-500 @ 2MA	10
	C106Y	
	Hobbyist's 16 pin Digital	
	IC-Guaranteed	16
	709C Hi-Pert op amp	4
	IR-128 Heat Exchanger	
	IR Selenium Booster Rectifier	
	IR Selenium Bridge Rectifier	
	IR Silicon Replacement Rectifier	
1	iR Selenium 5 Pin Convergence	
ľ	Rectitier	
ı	IR Universal Selenium Focus Rectifier	
ı	Ohmite vitreous enameled Resistor	

2N6027 PUT 2N6028 PUT 2N1671 10/1.00 6/1.00

.50 1 00 50 .50 .35 40

To-5 To-18 D5E37 BRIDGES PRV 2 AMP PRV 2 AMP 1000

SILICON U	NJUNCT	IONS		CM	IOS
N2646 N2647 N6027 PUT N6028 PUT N1671 5E37	To-18 To-18 To-92 To-92 To-5 To-18	.65 .55 .75 1.00	SS4001AE SS4002AE SS4011AE SS4012AE SS4013AE SS4015AE SS4023AE	.55 .55 1.30	SS4025AE .55 SS4027AE 1.35 SS4028AE 2.80 SS4030AE .65 SS4049AE 1.35 SS4050AE 1.35
BRI	DGES		CHECK	OD M	ONEY ODDED

.95 1.10 400

NO CODS. INCLUDE 10% FOR POSTAGE AND HANDLING. MINIMUM ORDER 5.00

2SC564 2SC568 2SC582 2SC591 .70 1.25 .75 1.25 2SC1226 400mw-50w Zeners — Field Effect Transistors — Power Germanium Transistors 10-65 amp — Power Germanium Tetrodes from 15.00 — Write for complete list of prices!

.80 .95

.65 .70

.70 .70

2.50

2SC1051 2SC1061 2SC1096

2SC1098

2SC1166

2SC1173

2.50 1.65 1.20

2SC515 2SC535 2SC536 2SC537

2SC563

65

1.60 1.10

.65 .70

1.00 2.10

1 05

RADIO-ELECTRONICS

2SB365

2SB367 2SB370

2SB380

2SB405

2SB407

2SB415

ALL PARTS GUARANTEED AND TESTED ON PREMISES.
WRITE FOR FREE CATALOG AND LG. QUANTITY DISCOUNTS.

2SD437 2SD458

2SD1111 2SD1115

2SK19

2SK30

2SK40

IR Setenium 5 Piri Governa Rectifier IR Universal Setenium Focus Rectifier Ohmite vitreous enameted Resistor GE-X6 Cadmum suffice Photocell GE-6GD1 Dual Orode GE-6GX1 Qual Orode Circle 109 on reader service card

6.00 .80 3.50 3.75 2.25

1.25

New-Tone Electronics P.O. BOX 1738 BLOOMFIELD, N.J. 07003

FLASH! For every order of \$15.00 or more YOU RECEIVE A FREE DIVIDEND!!!!

INFLATION - FIGHTING DIVIDEND

> CHOOSE any item or group of items FREE that add up to 10% of your order Minimum order \$15.00

Poly Paks-1st with Lowest Prices! 1st with Quantity Discounts! 1st WITH DIVIDENDS!



"2001" BEEPIN' ALARM

10%

GIANT DIGIT CLOCK KIT

Only \$49.95

eke 10%

10%

"Alarmin" low price. Uses famous "MK" Beepin' clock chip. That's right, can you imagine a clock chip that's within itself. B-E-E-F LED MAN-6 or equal readouts from the B-E-E-F LED MAN-6 or equal readouts from the graph with black crackle tone. Giant "NO GIARE" red filtered panel. 10 minute SNOOZE ALARM.

3 push buttons and toggle control hours, minutes, alarms and AM-PM indications. EASY TO BUILD! FUN! Instruction booklet. With rubber mounting on cabinet. Power 115VAC. Size 7%4 x 7 x 2V₂". Wt. 2 lbs.



MITY DIGIT LED 'DCM'S'

Only

8.88
707 and 704, Opcoo's SLA-1 (the hast 4 hast
707 and 704, Opcoo's SLA-1 (the hast 4 hast
707 and 704, Opcoo's SLA-1 (the hast 4)
708 and 709 and with finances for an opcool of the state of t

JUMBO 0.6" MITY DIGIT DCM

JUMBO 0.6" MITY DIGII DUM
MAN-6. Same electrical specs as the MAN-1. Measures 1 x ½ x ½" encapsulated in red epoxy lens.
Outperforms all reflective bar types. MORE BRILLIANT! Made for distance and wide-angle viewing. Fits
into standard 1.4 pin DIP socket. Kit includes MAN-6,
right angle IC socket, edge connector, pc board, assorted resistors and capacitors, SN7475, SN7490,
Molex sockets and booklet.

19.95

Same as above except uses MAN-64, 0.4 ALL eadout, MAN-1 characteristics Only

555 TIMERS

2 for \$1 Sale good till May 15,1975 **XENON FLASH** STROBE \$1.95

TUBE

Sold elsewhere for several times our price. This tube is of extremely high intensity. This compact tube delivers a power strong burst of light when triggered, lever a power strong burst of light when triggered Requires 500 to 1000 electrode to law trigger with a comes with hookup, a character of the several results of the several result



MAN-5 as MAN-7 except green 1.49 MAN-8 as MAN-7 except yellow 1.49

"BLASTAWAY" ON 1N4000 RECTIFIER PRICES

Туре			Şa	le
☐ 1N4001	50	10	tor	350
☐ 1N4002	100	10	for	450
☐ 1N4003	200	10	for	550
□ 1N4004	400	10	for	656
☐ 1N4005	600	10	for	750
□ 1N4006	800	10	for	850
☐ 1N4007	1000	10	for	99

"PROFESSIONAL" 60 WATT AM-FM MUX TUNER AMP



The finest built 60 watt tuner amb we've had for years. We call it THE AUDIOPHILE BUY OF THE YEAR! It compares to Fisher and H H Scott quality. Crisp hi's. organ type quality for the lows. Fine linear response using a pair of 35 watt style matched power tab transistors for each channel. Built-in preamp for using magnetic cartridges, black and chrome-silver look molded panel with glass already attached to tuner. It's made to JUST SLIDE INTO CABINET! Push-button features for phono, am, fm, fm stereo, tape. Red 'FM and TAPE' show on glass. You can't see dial plate behind glass til you press any of the above push buttons, and then the scale illuminates. Two separate rocker switches for POWER ON-OFF and AFC Controls. Modern slide volume, balance, bass and treble controls. Modern slide volume, balance, bass and treble controls. Modern slide volume. Balance controls indicate the state of the stat

THE COMPUTER ON THE CHIF Only **579.95**

Usually called "Microprocessor" — it is a p Charmel Si gate MOS 8-bit Parallel Central Processor. A 479 U Central Processing Unit on a chip. Features compute instruction decoding and control. Capability to add ess 16K x 8 bits of memory (RAM, ROM, SR). Build a micro-computer system when interfacing with o her chips, such as 1101, 1103, 2102 (RAMS) etc. Vith spec sheets. 16-pin dip package. \$79.15 2102 1000-bit 'static" Ram for above . \$9.95

RAYTHEON-RCA

NATIONAL

16-BIT MICRO PROCESSOR BASIC SYSTEM 0 Only \$149.

The lowest-priced 16-bit system! Outperforms the 8008. The CPU (Central Processing Unit) includes 4-MM5750's, called RALU's, and one MM5751 CROM. RALU — called Register and Arithmetic Logic Unit — is a 4-bit control bus, and the CROM is a Control-and-Read-Only Memory. The four RALU's in parallel form a 16-bit unit. The RALU's are controlled by micro-instructions, stored in the CROM. With spec sheets.

"GIANT DIGIT" READOUTS □ \$4.50 each Mfgr Type Color
Opcos St.A-3 Green
Opcos St.A-3 Yellow
Imm' MaN-6* Red
Litronix 747 Red
Litronix 746** Red
All LED, 6ts standard 14-pin

NATIONAL NUMERICAL **DISPLAY PANEL** 2**72830**839

3 for \$15 Type NDP1252 cold cathode gas discharge. 7-segment/8-digit symbols minusoverflow and dot. Properly
multiplexed. Like Burroughs
Panaplex-Two. Color: ORANGE. Used in calculators,
equipment etc. Anode supply
voltage 190 vdc. We have
listed miniature hower supply for them. With schematic. 3 x 1½ x ½".

MANAGORIA

\$5.95

SIGNETICS LINEAR IC'S

GAS DISCHARGE DISPLAY POWER \$3.95

SUPPLIES

multiplexed. Like Burroughs
Panaplex-Two. Color: ORANGE. Used in calculators
guipment etc. Anode supply
voltage 190 vdc. We have
listed miniature hover supply for them. With schematic. 3 x 1½ x ½".

Same as the 9-digit Panaplex Two and the National unit, but 11 digits
with socket ... \$6.95

110 vac input, output. With

*State Voltages 5 turu 24 (D) = Duals; (Q) = Qua Type | Sale | M3001 | ... | ... | ... | ... | ..

Take 10 %

State 1st, 2nd, Choices of Case

CODE

! tyles

LM380

LM382

LM382

LM531

LM532

LM533

LM536

LM540

LM558

LM560

LM560

LM562

LM565 .88 .69 2.50 2.50 2.50 2.50

8 WATT

AUDIO AMP **STEREO** The factory "snipped" most of the cables to this compact 8 watt stereo unit with aluminum escut the on plate. It's easy to use because we have all the cables marked ready to use. With power supply. 115vic. 3 controls, LEFT and RIGHT VOLUME controls for two speakers for balancing and center TONE control. With knobs. 7 x 3½ x 3½. Hookup spec sheets.

\$3.98 0 2 for \$7 0 6 5 WATT AUDIO MPLIFIER BASIC 35 WATT AUDIO AMPLIFIER BASIC

For Class AB use, Basic includes: Sign 540, 30 transistor high power driver T 1C", with a pair of complimentary watt plastic transistors, i.e. 2N5296 and 2N6109 ppp. With schematics, printercuit and parts board layouts.

BUY 10 IC'S TAKE 15% - BUY 100 TAKE 25%

Inflation - Fighting

	•		-					0	- Indy
Type	Sale (Order by type nur	nher! Sp	ec sheets on requ	est "ON	LY" • Facto	ry Mark	ed	
☐ SN7400	\$.19	☐ SN7438	.49	☐ 5N7481	1.25	☐ SN74141	1.19	☐ SN7419	1.49
□ SN7401	.19	☐ 5N7440	.19	☐ SN7482	.99	☐ SN74145	1.19	☐ SN7419	
□ 5N7402	.24	☐ SN7441	1.00	☐ SN7483	1.19	☐ SN74148	2.95	□ SN7419	
SN7403	.19	☐ SN7442	1.00	☐ SN7486	.49	☐ 5N74150	1.19	☐ SN7419	
SN7404	.27	☐ 5N7443	1.00	SN7489	2.95	☐ 5N74151	.99	□ 5N7419"	
SN7405	.24	☐ SN7444	1.00	SN7490	1.81	☐ SN74153	1.39	□ 5N7419	2.4
SN7406	.79	SN7445	1.00	☐ SN7491	1.35	☐ SN74154	1.69	□ 5N7419	
□ SN7408	.27	SN7446	1.10	□ 5N7493	.99	SN74155	1.29	☐ \$N74201	7.50
SN7409	.27	SN7 447	1.10	☐ SN7495	.99	□ SN74156	1.45		
SN7410	.19	☐ SN7448	1.45	☐ SN7496	.99	☐ SN74157	1.45		
SN7411	.31	☐ SN7450	.27	☐ SN74100	1.55	☐ SN74158	1.45	1	0
SN7413	.89	☐ SN7451	.28	□ SN74104	1.25	□ SN74161	1.59	22	4
SN7414	2.25	☐ SN7453	.28	□ 5N74105	.95	☐ SN74163	1.75	1	2
☐ SN7415	.45	☐ SN7455	.28	☐ SN74106	.95	SN74164	2.85	11) 4	h
☐ SN7416 ☐ SN7417	.50	☐ SN7462	.39	☐ SN74107	.49	☐ SN74165	2.85	((0)	2
SN7417	.22	☐ SN7464	.39	☐ \$N74108	.95	☐ SN74166	1.85))	
SN7420	.29	☐ SN7465	.39	☐ SN74112	.95	☐ \$N74173	1.85	(4/
SN7422		☐ SN7471	.55	☐ SN74113	.95	☐ SN74174	2.25	1600 1	7731
5N7425	.32	☐ SN7472	.42	☐ SN74114	.95	☐SN74175	1.99	200	107
SN7426	.35	☐ SN7473	.52	☐ SN74121	.49	☐SN74176	1.25	1	
3147 420	.31	☐ SN7474	.39	□ SN74122	.55	☐ SN74177	1.25	Money-	ack

7-SEGMENT

OPCOA SLA-1 3 for \$6. REFLECTIVE \$2.50 Red LED READOUT



Terms: add postage Rated: net 30 Phone Orders: Wakefield, Mass. (617) 245 1829 Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED ☐ 20c CATALOG Fiber Optics, 'ICs', Semi's, Parts MINIMUM ORDER - \$4.00

POLY PAKS P.O. BOX 942R, LYNNFIELD, MASS. 0 1940

106

-Valu-Pak-**VOLTAGE REGULATORS TO-3**

1 AMP POSITIVE ma. 10 pak
LM 309k '5V \$1.25 \$10.00
7806 6V 1.50 13.00
7812 12V 1.95 17.50
7815 15V 1.95 17.50
7824 24V 2.25 20.00

CALCULATOR CHIP A1030

North American Rockwell Al030 4 function & percention-chip clock:8 digit floating or fixed DP:full memory and con-stant 42 pin staggered lead DIP (unbent).



w/data

74S206 SCHOTTKY BIPOLAR

74S206 Schottky Bipolar 256x1 Random Access Memory. ea. \$3.49 10 pak \$29.00

10 AMP FULL WAVE BRIDGE RECTIFIER

10 AMP Full Wave Bridge Rectifier 100 PRV Motorola MDA 762-2 ea. \$2.25 10 pak \$20.00



ea. \$1.75 OPTO ISOLATOR 10 pak \$6.95 Monsanto MCT 26 6 pin Dip

2N3055 NPN TRANSISTOR

2N3055 Transistor (power):PD-115W; VCE-60V; HFE-50; FT-30K; Case-TO-3 ea. \$1.15 10 for \$6.95

DIP RC NETWORKS

14 and 16 pin IC packages containing precision resistors and capacitors.

NO SCHEMATICS AVAILABLE Sample indicates most contain 10 to 15R and 1 or 2C. Assortment of 8,\$1.

All Merchandise is new unused surplus and is sold on a money back guarantee

Five dollar minimum order. Free first class postage on all orders. California Residents please add sales tax.

Send stamp for free catalog. Write to:

box AF Carmichael, Ca. 95608

Circle 111 on reader service card



Japanese ransistors

2SA12	\$.65	2SB439	\$1.05	000030	41.05
2SA15	.65	2SB463	1.75	2SC830	\$1.95
2SA101				2SC853	.95
2SA101	.80	2SB473	1.75	2SC859	.75
	.80	*2SB474	1.85	2SC875	1.65
2SA221	.65	2SB481	2.25	2SC876	1.50
2SA234	.80	*2SB492	1.35	2SC930	.75
2SA341	1.05	2SC281	.80	2SC933	1.55
2SA342	1.05	2SC 367	1.15	2SC936	6.75
2SA350	.80	2SC369	1.15	2SC937	7.50
2SA607	2.45	2SC371	.80	2SC945	.65
*2SA634	1.50	2SC372	.80	2SC959	1.95
2SA636	2.45	2SC373	.80	2SC960	2.25
2SA640	.70	2SC374	.80	2SC971	1.15
*2SA643	.95	2SC394	.80	2SC1000	.75
*2SA683	.85	*2SC458	.80	*2SC1030	3.50
*2SA699A	1.45	*2SC460	.80	2SC1060	1.80
2SB22	.75	2SC461	.80	2SC1061	1.80
2SB54	.80	2SC491	2.75	*2SC1096	1.35
2SB56	.80	2SC535	1.05	2SC1098	1.30
2SB73	.80	*2SC536	.75	2SC1116	5.50
2\$B75	.80	*2SC537	.75	*2SC1226A	1.35
2SB77	.80	2SC631	1.05	2SC1237	2.15
2SB156	1.05	2SC632A	1.15	2SC1317	.65
2SB171	.65	2SC633A	1.15	2SC1317	.80
2SB172	65	2SC634	1.15		
2SB173	.65	2SC644	.80	2SC1377 *2SC1383	7.50
2SB175	.65	2SC694	.70		.85
2SB178	1.15	*2SC710	.75	2SC1384	.85
2SB185	.70	*2SC711		2SD24	1.85
			.80	*2SD72	1.35
2SB186	.70	2SC727	1.15	2SD77	1.05
2SB187	.70	2SC732	.80	2SD141	2.45
2SB303	.75	2SC733	.80	2SD142	2.50
*2SB324	1.15	2SC734	.80	2SD178	2.05
*2SB337	2.25	2SC735	.80	2SD186	.80
2SB370	1.25	2SC799	5.45	2SD218	4.25
2SB400	.80	*2SC828	.80	2SD234	1.65
*2SB405	1.15	2SC828A	.85	2SD235	1.35
*2SB415	1.20	*2SC829	.85	*2SD261	.90

Kit TR24 \$23.44 Kit Contains 24 'Mark Transistors. You Save 20% ALL TRANSISTORS 100% TESTED ORDERS LESS THAN \$5.00 ADD 400; \$5.01 to \$10.00 ADD 500.—OTHERS POSTPAID. CALIF. RESIDENTS PLEASE ADD SALES TAX. Write for Free Catalog.—Over 500 Types Available SEND ORDER AND MAKE CHECK OR MONEY ORDER TO:



West Pacific Electronics P.O. BOX 25837

W. LOS ANGELES, CALIF. 90025

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

READER SERVICE CARD NO. PAGE Allied Electronics 97 19 Allison Automotive 30 AmperexCover III
7 Arrow Fastener14
22,23,24 B & K Division of Dynascan Corp.74, 75 Bell & Howell Schools54-57 ጸጸ Brooks Radio & TV Corp. 95 92 11 CIE, Cleveland Institute 68 of Electronics82-85 73 Continental Specialties Corp. 87 CREI, Division of the McGraw-Hill Continuing Education Center64-67 Crown International16 61 Delta Products Corp. 77 91 Edmund Scientific Co.108 17 EICO, Electronics Instrument, Inc. 24 Elenco Electronics 88 74 EMC, Electronics Measurement Corp. ,..... 97 85 Enterprise Development Corp. 92 69 Exar Fordham Radio Supply Co. 92 84 83 100 62,63 Instrument Co. Indiana Home Study 2.1 Institute 74 5 International Components Corp. 12 International Crystal 28 Mfg. Co. 76 29 Litek, Inc. 77 Mallory Distributor Co. 5 87 MTI, Motorola Training Institute 94 75 Mountain West 82 National Digital 14 National Technical Schools44-47 Non-Linear Systems, Inc. 90 NRI Training8-11 79 81 PAIA Electronics 90 13 Perma Power 20 86 Pomona Electronics 93 77 PTS Electronics 89 16 **RCA** Electronic Components Picture Tubes 32 15 Test Equipment 22 RCA Solid State Division 15 76 RGS Electronics 88 Rye Industries 96
Sams & Co. Howard W. 1E
Sansui Cover II
Scelbi Computer 90 2 Consulting, Inc. 87 67 Schober Organ 81 12 93 Shure Bros. 19 Simpson Electric Co.1A-1D

71	Technical Documentation 87
18	Telematic 25
65	Teletronics
	Company of America 81
20,30	Tektronix, Inc 31
80	Tri-Star 90
4	Tuner Service Corp 7
70	TV Tech Special 86
89	Vero Electronics 96
	Vintage Radio94
66	Vu Data 81
10	Weller-Xcelite
	Electronics Division 17
	MARKET CENTER
0.0	A
98	Ancrona Corp99
105	ATV Research
108	Brigar Electronics103
100	Command Productions 98
102	Delta Electronics102, 104
97	Digi-Key 98
	Fair Radio Sales100
	Bill Godbout Electronics102
99	International
40.00	Electronics Unlimited101
107	James Electronics103
101	J.E.M. Mfg100
101	JTM Associates 102 Lesco Electronics 102
103	Meshna Electronics,
105	John Jr102
106	Mini Micro Mart103
109	New-Tone Electronics 104
104	Photolume Corp103
110	Poly Paks105, 107
	Solid State Sales100
	Trumbull102
111	Valu Pak 106
112	West Pacific Electronics106

Radio-Electronics is published by Gernsback Publications, Inc. 200 Park Ave. S. New York, NY 10003 (212) 777-6400

President: M. Harvey Gernsback

Secretary: Bertina Baer

ADVERTISING SALES

EAST

Stanley Levitan, Sales Manager Radio-Electronics 200 Park Ave. South New York, NY 10003 (212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen The Ralph Bergen Co. 6319 N. Central Ave. Chicago, IL 60646 (312) 792-3646

PACIFIC COAST/Mountain States

Jay Eisenberg J.E. Publishers Representative Co., 8732 Sunset Blvd., 4th Floor, Los Angeles, CA 90069 (213) 659-3810

Sales Mart Building 1485 Bayshore Blvd., Box 140 San Francisco, CA 94124 (415) 467-0125

Southwest

Technical Products 89

ALL LED" MONSANTO READOUTS

Man.	MAN-3	M	AN. 6. MAN. 64
MONSANTO TYPE	CHAR. HT.	SALE	Quantity Discounts
☐ MAN-1	.27	\$3.50	3 for \$ 9.
MAN-2	.32*	4.95	3 for \$14.
MAN-3	.12	1.00	3 for \$ 2.50
MAN-6	.60	4.50	3 for \$12.
MAN-64	.4	3.50	3 for \$ 9.
☐ MAN-7	.27	1.50	3 for \$ 3.
*35 LED matr	ix	1	



20-Years of Business INTEGRITY

1.00 1.00 1.96

1.00 1.00 1.00 1.00

20-Years of Money-GUARANTEES 20-Years of Econom
LOWEST PRICES:

6-FUNCTION AC-DC \$24.50 CALCULATOR KIT! True credit bala

THE SIMPLEST! FINEST! SMALLEST!

Lightweight, pocket size

Extra large display 6 functions plus, minus,


times, percentage, constant • Constant multiplication Floating decimal and division
Chain and Mix calculations • AC adaptor jack

· Simplified Indexing · Mark up and Mark down

WRISTWATCH LIQUID CRYSTAL & DISPLAY



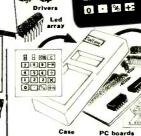digit, 7-segment 11/16 x 11/16 only 11/16 x 11/16 x 1/4". Includes readout, socket, 'slide-in-place chrome slide face plate'. Same display as found in \$200. units.



Daltone

ce c

7 8 9 =

4 5 6 ÷

123×

0 . % +=

Resisto

TITE

Drivers

and Mix calculations • AC adaptor jack

Designed specifically for Poly Paks under the Isltone
80 brand, IMAGINE 10nly 2½ x 1x 4½ x 1sides easily
into your vest pocket, brief case, or handbar, We
hunted everywhere to find a calculator kit the can
be small, do the many functions, with fine engire-ring
design and SIMPLE TO BUILD! WHY? Because it has
the fewest parts in a kit. Imagine the pc boar! only
has the chip, 4 resistors, two trunsistors, two driver
it's with the 9 digit readout. SIMPLE! You be! it is.
the entire kit is even packed in a multicolor attractivel ded greet includes: attractive black case with red
filter; Flex Key (type 20SK-66) 18 key keyboard that
measures only 2½ x 2" with 2 switches, one for ONOFF. one for K constant: MAIN pc board: readout
board: famous Cal Tech 5030 26-jin calculator
two 75491 is drivers; Hewlett Packard 9 digit array;
ac jack; 9 Volt battery connector resistors; two
transistors; back protective plate; necessary wire plugs;
easy instructions. (Less 9 volt standard battery and
AC adapter) FASIFET MIT TO Pall III AC adapter) EASIEST KIT TO BUILD

GIANT SALE ON LED'S

LIGHT EMITTING DIODE GAS INDICATORS

3-MV2, TO-18, dome, green, visible
一 3.MV2, green small dome. green diff. lite
3-MV3, micro-mini 'pin head' dome, TO-18, green lite
3-MV3, visible, 'coax pin pak', red, mini dome lens
5-MV10B, visible, red, clear dome lens TO-18
5-MV10C, visible, red, diffused, dome lens, 10-18
□ 8-MV50, axial leads, micro-mini dome, clear, red. TO-18
3-MV52, micro-mini, axial green lens, green lite
3-MV53, micro-mini, axial yellow lens, yellow lite
5-MV54, micro-mini, axial leads, red lens, red lite
5-MV5012, red small dome lens, red lite, TO-18
5-MV5013, sm. dome, 2 hi red dome, soft red diff. lite, TO-18
5-MV5020, jumbo clear dome, visible, red, TO-18
□ 5 MV5054, red jumbo dome lens, TO-18 red lite, upright
5-MV5080. TO-18, micro-mini red dome, red lite
5-MV5080, TO-18, micro-mini flat clear lens, red lite
1-MV5094, red bi-potar, solid state lamp V to 110-115VAC-DC
3-MV5222, green jumbo dome, green lite, panel snap-in
3-MV5282, micro-mini, green lens TO-18, green lite
3-MV5322, yellow jumbo dome, yellow lite, panel snap-in
2-MT2 photo translator light sensor TO-19

COUPLERS 2. MCT2, 1500V isolation photo transistor . . .

BASIC KIT #2 — same as Basic #1 except enderlator chip is National 8-digit MM5725.

S.8.95
BASIC KIT #3 — same as Basic #1 except culculator chip is National 6-digit MM5736 and 75492.

S.16.95 N G - 7 1 3 - 4 5 6 X 1 2 3 + CHIP

READ

OUTS

12 DIGIT BASIC #4 — Key parts include: CT 001 chip, 4-3 digit readouts, factory etched PC board, case, carrying case, 2-resistor networks, decimal sytch. Wild Rover Keyboard with ON-OFF switch dag ams. Sale \$19.95 □

8-DIGIT "TEXAS INSTRUMENT" BASIC KIT includes Texaskeyboard, 1KS149, standard 4-funzion. With T-I calculatior chip TMS-0, 128, pc. board, rase, lens. Microswitch (on-off). 9-digit array: includes diagram. \$46-95.

SEMI-KON Dollar Stretchers

1.5316 CLOCK CHIP, hobby
2.5005 MEMORY CALCULATOR CHIPS, 28-pin HOBBY
5.555 TIMERS, min DIP, hobby
10-741 OP AMPS, min DIP HOBBY
2 - 2N5296 33-WATT NPN PLASTIC TRANSISTORS, for NE-540
2 - 2N6109 40-WATT NPN PLASTIC TRANSISTORS, for NE-540
10-1N82 GERMANIUM UHF diode, clip-in type*
10-IN82 GERMANIUM UHF diode, clip-in type*
1-EPOXY 2-AMP SILICON BRIDGE RECT. 1000 V "comb. type"
10-MOS FETS, 3N187, 3N200, 3N128, TO-18, Fairchild*
15-SCRS & TRIACS up to 25 amps. 6-12-24 prv. studs too
2 - 2N3849, Texas, N channel, 6500 umho TO-18
2 - 2N3646 UNIJUNCTIONS, plastic transistors. Texas
50 - SILICON, glass rectifiers, computer, axial leads 2 — ZNZ948 UNIJUNCTIONS, plastic transistors, Texas
50 — SILICON, glass rectifiers, computer, axial leads
50 — GERMANIUM, glass rectifiers, signal, axial leads
6 — 1-AMP 1000 PlV, epoxy, submini, silicon rectifiers
50 — 1-W ZENERS, axial 4, 8, 9, 10, 12V rectifiers, et.
4 — ZN305S, HOBBY, 40W npn silicon transistors, TO-3
30 — 3-AMP RECTIFIERS, silicon, epoxy, assorted V. axial*

--- PHOTO TRANSISTOR, with darlington amp filter,
--- PHOTO TRANSISTORS, with darlington amp, 2N5777, GE.
--- PHOTO CELLS, Clairex, pancake, 30K-70 ohms.

2. Sylvania 18.000V Matchstik TV rectifier, 4" x ½ with leads
5 - ER990 TRIGGER DIODES for SCRs & Triacs
2 - FET'S 2N5457 N channel 5000 umbos. T0-92 plastic
10 - 1N914 fast switch diodes, silicon, 4 nanoseconds
2 - 6 AMP TRIAC 200 PRV. T0-5
50 - UTT MICRO MINI RECTIFIERS silicon porcelain to 1KV50 - WORLD'S SMALLEST RECT. & zeners. IW. assorted volts:
4 - 6000 PIV 50 mil epoxy rectifiers, axial leads!
10 - BERDIX 2S WATT "pellet" power transistors, silicon 10 - BENDIX 25 WATT 'pellet' power transistors, silicon'
3-DARLINGTON, powers, plastic, HFE up to 60K, 6W, 30V.
10 POWER TABS, plastic includes Darlinstons, HI AMP, HI V \$
1 - 2N5036 HI-PWR plastic trans 100 vece, 7 amp 86 watts.
4 - 2N5296 HOBBY, 36 watts, plastic powers, NPN
4 - 2N6109 HOBBY, 40 watts, plastic powers, NPN
5 - PLASTIC 35W powers, npn, silicon, hobby 2N6121
5 - PLASTIC 35W powers, npn, silicon, hobby 2N6121
2 - MOS FETS, DUAL GATE, N chan. 3N187, TO-18, RCA
2 - MOS FETS, DUAL GATE, N chan. 3N187, TO-18, RCA
2 - MOS FETS, DUAL GATE, N chan. 3N140, TO-18, RCA
2 - MOS FETS, DUAL GATE, N chan. 3N140, TO-18, RCA
2 - MOS FETS, DUAL GATE, N chan. 3N147, TO-18, RCA
2 - MOS FETS, DUAL GATE, N chan. 3N147, TO-18, RCA
2 - MOS FETS, DUAL GATE, N chan. 3N147, TO-18, RCA
3 - RCA 2N3600 NPN. UHF transistors, tv-fm, TO-18, 1000mc
2 - MPF-1000. Moroola MOS dual gate 'The Claw
2 - 2N5655 200 hfe. 250 vceo. power tab \$1.

RASICS

MAKE YOUR OWN

CALCULATORS WITH OUR LOW PRICED 6-8-12 DIGIT



Heavy-duty powerful hi-torque motor, ruggedly con-structed. Permanently lubristructed. Permanently lubricated type bearings. Thermalloy protected, Motor size: 3 x 3 x 2½/w. By Molon ZM04047. 115 vac 60 hz. 0.77 amps. With 6½ TORIN fan blade, 1500 rpm. For all types of ham & industrial equipment.



6 & 8 DIGIT MINI CALCULATOR BASICS

Hall S ALLS Assequers approx. 6 more price.

KIT NO. 5030 — 6 functions. Includes mind lase,
with lens, HP nine digit readouts with multiples of
oard main per board, that keybord of the
the too
oard main per board, that keybord of the
the too
oard main per board, or the too
oard main per board, or the too
oard main per board, or the
the too
oard main per board, or the
the too
oard main per board, or the
the too
oard main per board, or the
the too
oard main p



H

KEY

Buy Any 3 LANE" 1101 256 Bit RAM MOS 1103 1024 Bit RAM MOS 17489 64 Bit RAM MOS 8223 Pre-Programmable ROM Mm5220 1024 Bit RAM Mm5200 1024 Bit RAM Mm5203 Eraceuble PROM

NATIONAL. LM-340T VR's Buy 3 - Take 10 To Type Voits LM-340-057 Sv LM-340-067 Sv LM-340-087 8 v 1.75 LM-340-12712 v LM-340-18718 v LM-340-18718 v LM-340-24724 v

INDUSTRIAL SPEED CONTROL . \$4.95

A \$30 item from G.E. Model 533A (made for Xerox) that controls home, shop and industrial lighting too! A very elaborate circuit for controlling many electrical and electronic devices. Easily controls speeds o electric drills, brush type motors, etc. 115vac, rated at 1100 watts. With variable speed or dimming centrol in heavy-duty aluminum case. 3 x 23/4 x 2. With diagram and hookups.

I.C. & LED HOBBY-ONICS

UNTESTED GUARANTEED SATISFACTION

MM5311 6-digit 28-Pin MM5312 4-digit 24-Pin MM5313 6-digit 28-Pin MM5314 6-digit 24-Pin MM5316 4-digit 40-Pin, alarm MM5316-A no alarm CT7001 4-6-digits Alarm & Calendar BEEPER" AND "DATER" CLOCK ON THE CHIPS

CLOCK CHIPS ON A "DIP"

WITH DATA SHEETS

CLOCK ON THE CHIPS
Imagine a chip (MK50250)
"Beepin" and audible alarm!
All chers are external. It is also features internal brightness control. The CT7001 requires external triggering of alarm, date of the month and direct drive to LED readouts. Both require minum current drain and voltages, for either 4 to 6 LED readouts. 12 or 24 hours. AM and PM.

CT7001 Alarm and Date . . . \$9.95

Sanken Watts Sale
SI-1010G 10 \$ 8.88
SI-1020G 20 \$ 4.95
SANKEN HYBRID
14.95 SANKEN HYBRID
14.95 SANKEN HYBRID
14.95 SANKEN HYBRID
14.95 SANKEN HYBRID
14.95 SANKEN HYB



"C" MOS IC'S

\$4.95 6-VOLT TICAD Includes 4 'A' cell nicad batteries hooked up to give you 6-volts for all trpes of energy uses. The best batteries made. Rechargeable.

AC ADAPTERS & CHARGERS

110 vac input; out ut for 5. 6, 7.5 and 12 volt calculators @ 200 mil. For nicads too! Your choice

Jerms: add postage Rated: net 100 Phone Orders: Wakefield, Mass. (617, 15-382 Retail: 16-18 Del Carmine St., Wakefiel: Mass. (off Water Street) C.O.D.'S MAY BE PHONED 20c CATALOG on Fiber Optics, 'iCs', Semi's, Parts MINIMUM ORDER — \$4.00

POLY PAKS

LIVE IN THE WORLD OF TOMORROW...TODAY!

And our FREE 180 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4.500 finds for fun. study or profit . . . for every member of the family.



A BETTER LIFE STARTS HERE

3-CHANNEL COLOR ORGAN KIT




Stock No. 41,831 EH

\$18.95 Ppd.

AN ALPHA MONITOR FOR \$34.95?

Yes, because you built it! Use your ability to tune in your brainwaves, an aid to relaxation, concentration. Kit incls, everything you need (except 9v trans. batt.) to own a portable self-cont. BIOFEEDBACK unit for a pittance; steth, earphones, electrode headband, solid-state circuitry; 5 microvolt sensitivity, more! Compl. assembly instructions & op. manual. With basic electronics knowledge, you can do it!

No. 61.069 EH (KIT) \$34.95 Ppd.

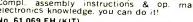

No. 61,069 EH (KIT) No. 71,809 EH (FULLY ASSEMBLED)

\$34.95 Ppd. \$55.00 Ppd.

AM RADIO FITS IN/ON YOUR EAR!

Wear it inconspicuously everywhere, Wear it inconspicuously everywhere, Listen as you work (lawn, yard, office), watch (game, beach) or wait. Instant music, news. sports. No gimmick, our 6/10 oz. Technological wonder has integrated circuit, 11 transistors, patented ferrite antenna/tuner/volume dial. Uses normal silver oxide hearing aid batt. (incl) for approx. 100 hrs. New batt to slip in avail. at drug stores (about lengthy wires, bulky cases, or power-packs!

stores (about 50c).

Stock No. 42,275 EH

\$14.95 Ppd.

WHICH ARE YOUR CRITICAL DAYS?

Can Bio-rhythm tell you? We're not sure, but we're told that vast mood shifts are caused by your body's Internal Time Clock whose rhythms can be charted ahead to possibly warn you of "critical" days. Some are great, some blah. Maybe it's your physical, emotional & intellectual rhythms converging at the right or wrong time. Compute your cycles with our Bio-rhythm kit and judge for yourself. Incls Charting kit, metal Dialgraft Calc. instrs.

Stock No. 71,949 1 YR. PERSONALIZED REPORT — BY COMPUTER Stock No. 19,200 (Send Birthdate)

\$11.50 Ppd. \$15.95 Ppd.

ı

RUN A WORKING STEAM ROLLER!

Authentic English hand-crafted model Authentic English hand-crafted model made of heavy-gauge metal, powered by steam so you can run it forward, backward, regulate speed, pull other models, lock roller and run engine independently. Just set steering or use the 12" extension steering rod and drive it yourself! The fun even can power the mighty whistle. To run, fill the safe vaporizing spirit lamp w/wood alcohol (not incl).

No. 71.934 EH (4 lb.: 101/x672")

\$25.00 Ped

No. 71,934 EH (4 lb.: 101/ax6x7")

\$35.00 Ppd.



TEST YOUR DEGREE OF ESP!

Which light comes on when you push the button — Star, Square, Triangle or Circle? If you've got ESP you or your subject will guess right, significantly. Solid state ESP Tester has guaranteed random circuit for accuracy — you can't beat the ability, telepathy experiments. Portable. Reg. 4 "D" batt.

No. 72 090 EH (6\(\frac{1}{2}\)\(\frac{2}{3}\)\(\frac{2}{3}\)\(\frac{2}{3}\)\(\frac{2}{3}\)\(\frac{2}{3}\)\(\frac{2}{3}\)\(\frac{2}{3}\)

\$29.95 Ppd.

No. 72,090 EH (61/4x33/4x2")

EXTRA PADS TO RECORD 250 EXPERIMENTS Stock No. 72,092 EH

\$3.50 Pnd.



LOW COST 7X INFRA-RED VIEWER

New, great buy for Infra-red crime detection surveillance, security system alignment, I. R. detection, laser checking, nite wildlife study, any work requiring I. R. detection and conversion to visible spectrum. Self contained scope w/everything but I.R. light source works in any I.R. lit area: 6V or 12V power. 6032 I.R. converter tube, f/4.5 objective lens, adjustable triplet eyepiece. shockproof housing. See bright in dark! Under 4 lb., comparable to others at \$350. No. 1648 EH (11x14¼x3") \$225.00 Ppd. DELUXE—WITH I.R. LIGHT SOURCE No. 1659 EH \$275.00 Ppd.

NEW! KIRLIAN PHOTOGRAPHY KIT!

Experiment in the fascinating new field of "Kirlian electrophotography"—images obtained on film without camera or lens by direct recording of electric charge transmitted by animate & inanimate objects. Each "aura" differs—animate aura said to change corresponding to physical lated from power source; instructions.

No. 71,938 EH

No. 71,938 EH \$49.95 Ppd. "HIGH VOLTAGE PHOTOGRAPHY" by H. S. Dakin No. 9129 EH (60-PG.) PPBK BK.) \$5.00 Ppd. DELUXE KIRLIAN PHOTOGRAPHY SET NO. 72,053 EH



. . . . 3" ASTRONOMICAL REFLECTING TELESCOPE

See stars, moon, planets close-up! 30 to 90X. Famous Mt. Palomar Type. Aluminized & overcoated 3" diameter f/10 primary mirror, ventilated cell. Fork type equatorial mount. Durable PVC tube. Includes 1" F.L. 30X Ramsden, Barlow lens to triple power, 3X finder telescopes, hardwood tripod.

No. 85 240 FM.

\$399.00 Ppd.

No. 85,240 EH DELUXE 3" REFLECTOR TELESCOPE #80,162 EH\$79.95 Ppd. 41/4" REFLECTOR (45X to 135X) #85,105 EH\$149.50 FOB 41/4" REFLECTOR W/CLOCK DRIVE #85,107 EH \$189.50 FOB 6" REFLECTOR (48X to 360X) #85,187 EH \$249.50 FOB 6" REFLECTOR W/CLOCK DRIVE #85,086 EH ... \$285.00 FOB



MAIL COUPON

180 PAGES . MORE THAN 4500 UNUSUAL BARGAINS

Completely new 1975 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenius scientific tools. 1000's of comproperts

ious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.
300 Edscorp Building, Barrington, N.J. 08007

Please rush Free Giant Catalog "EH".

Name		
Address		
City	State	Zip

•		1
	- 45	
	7-36	
	-	ı

COMPLETE AND MAIL WITH CHECK, M. O. OR CHARGE NO. EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

	How Many	Stock No.	Description	Price Each	Total
→ PLEASE SEND GIANT FREE CATALOG "EH"					
Charge my BankAmerican	d *			77	
Charge my Master Charge Interbank No.	* Add Hand	dling Chg.: \$	1.00, Orders Under \$5.00, 50¢, (Orders Over \$5.00	
My Card No. Is			l enclose 🗌 check 🔲 money o	rder for TOTAL \$	
			Signature		
Card Expiration Date 30-DAY MONEY-BACK GUA	RANTEE.	Name			
You must be satisfied o any purchase in 30 days refund, *\$15.00 m	for full	Address City		Zij	·

Circle 91 on reader service card


...and who has the broadest line of industrial and power replacement components in the business?

Amperex Distributors, that's who!

- ...Broadest line? Broadest line!
- ...In stock? In stock!

...Name some —

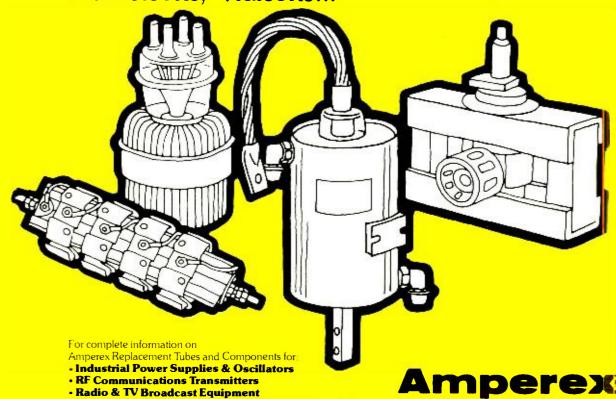RF Power Tubes, RF Power Transistors,
Industrial Magnetrons, Rectifier Tubes,
Transmitting Tubes, Industrial Receiving Tubes,
Photomultipliers, Silicon Rectifier Stacks,
Ignitrons, Trigger Tubes, SCR's, Industrial CRT's,
Radiation Counter Tubes, X-Ray Tubes,
Plumbicons,* Vidicons...



*Registered trademark of NV Philips of the Netherlands

contact Bob Norris. Distributor Sales Operation.

· Scientific Instruments...

Telephone: 516-931-6210

· Microwave Ovens & Commercial Radar Equipment

Amperex Electronic Corporation, Hicksville, New York 11802.


A NORTH AMERICAN PHILIPS COMPANY



The Tuner People

Pioneers of TV Tuner Overhauling Originators of Complete TV Tuner Service

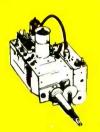Castle offers the following services to solve ALL your television tuner problems.



Universal Replacements from \$8.95

These universal replacement tuners are all equipped with memory fine tuning and uhf position with plug input for uhf tuner. They come complete with hardware and component kit to adapt for use in thousands of popular TV

	SHAFT		LF.		
HEATERS	Min.*	Max.*	Snd.	PRICE	
Parallel 6.3v	13/4′′	3′′	41.25	8.95	
Series 600mA	13/4"	3′′	41.25	9.50	
Series 450mA	13/4"	3′′	41.25	9.50	
Parallel 6.3v	21/2"	12"	41.25	10.45	
Series 600mA	21/2"	12"	41.25	11.00	
Series 450mA	21/2"	12''	41.25	11.00	
	Parallel 6.3v Series 600mA Series 450mA Parallel 6.3v Series 600mA	HEATERS Min.* Parallel 6.3v 1¾" Series 600mA 1¾" Series 450mA 1¾" Parallel 6.3v 2½" Series 600mA 2½"	MEATERS Min.* Mox.* Parallel 6.3v 1¾" 3" Series 600mA 1¾" 3" Series 450mA 1¾" 3" Parallel 6.3v 2½" 12" Series 600mA 2½" 12"	MEATERS Min.* Mox.* Snd. Parallel 6.3v 134" 3" 41.25 Series 600mA 134" 3" 41.25 Series 450mA 134" 3" 41.25 Parallel 6.3v 2½" 12" 41.25 Series 600mA 2½" 12" 41.25	





Castle Replacements

\$15.95

Castle custom replacements made to fit in place of original tuner. Purchase outright . . . no exchange needed. Write for current list of Castle replacements, or request the part number you require (use number on ORIGINAL TUNER ONLY; do not use service literature numbers). Available for many of the popular models of following manufacturers: Admiral, Curtis Mathes, Emerson, GE, Heathkit, Magnavox, Motorola, Muntz, Philco, RCA, Sears, Sylvania, Westinghouse, Zenith and many private labels.



Overhaul Service

This is the service pioneered by Castle! We are now in our third decade of serving the TV Service Industry



Service on all makes and models, vhf or uhf, including transistor and color tuners ... one price \$9.95 Overhaul includes parts, except tubes and transistors.



Castle overhaul service is as near as your post office




Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

Dismantle tandem uhf and vhf tuners and send in defective unit only. Remove all accessories



Custom Exchange Service

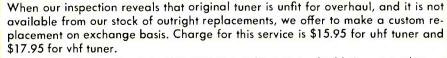



If custom replacement cannot be made we will custom rebuild the original tuner at the exchange replacement price.



All replacements are new or rebuilt. All prices are f.o.b. our plant. Add shipping and handling of \$1.25 on all prepaid orders. We will ship C.O.D.



CASTLE TV TUNER SERVICE, INC.

5715 N. Western Ave., Chicago, III. 60645 • Ph. 312-561-6354







