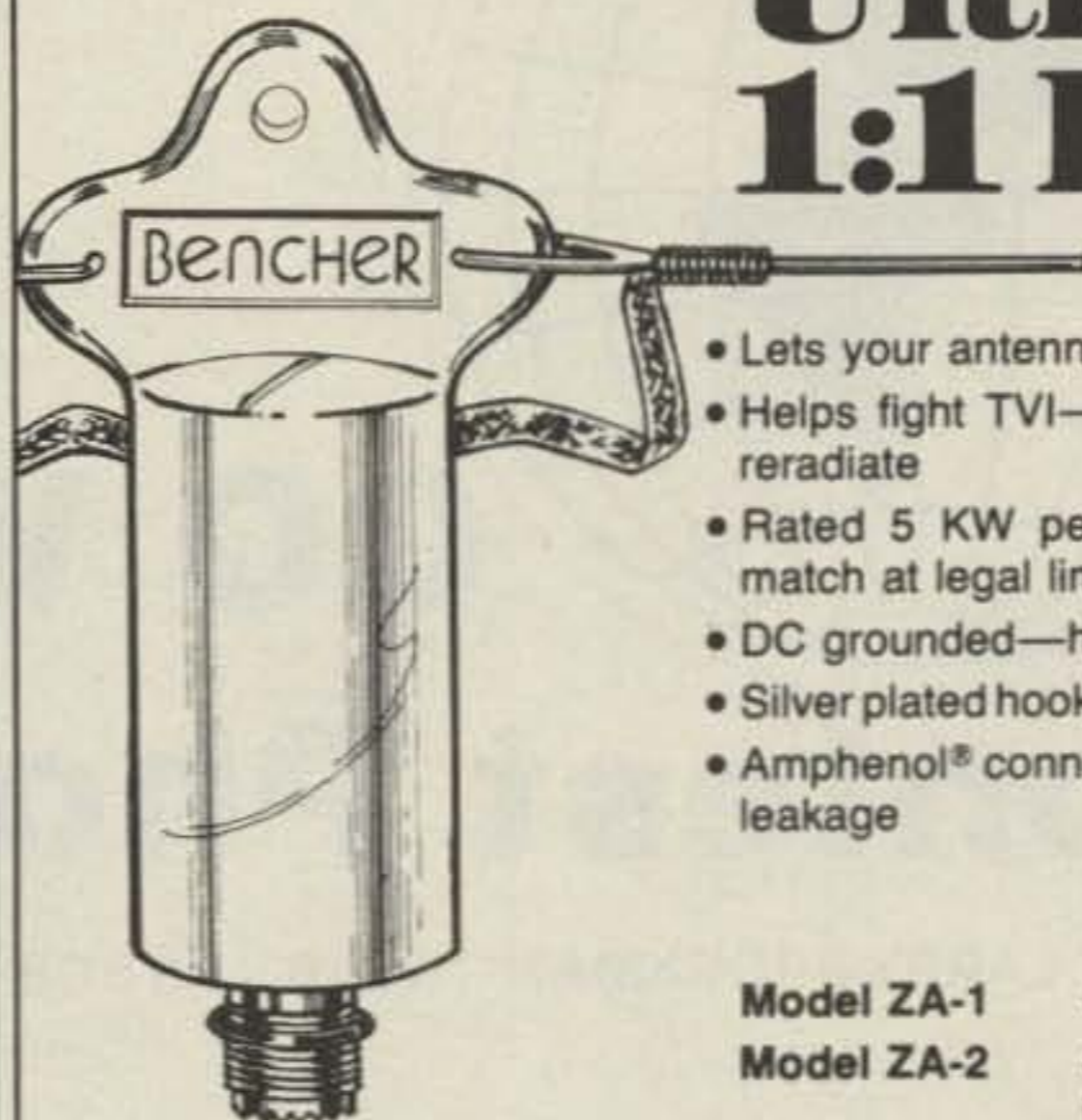


the Ultimate 1:1 BALUN



- Lets your antenna radiate—not your coax
- Helps fight TVI—no ferrite core to saturate or reradiate
- Rated 5 KW peak—accepts substantial mismatch at legal limit
- DC grounded—helps protect against lightning
- Silver plated hook-up braid; Custom molded case
- Amphenol® connector; Rubber ring to stop water leakage

Model ZA-1	3.5-30 mHz	\$15.95
Model ZA-2	optimized 14-30 mHz includes hardware for 2" boom	\$17.95

Available at selected dealers, add \$2.00 postage and handling in U.S.A.
WRITE FOR LITERATURE

BENCHER, INC.
333 West Lake Street, Dept. D
Chicago, Illinois 60606 (312) 263-1808

CIRCLE 60 ON READER SERVICE CARD

NEW MFJ ALL BAND XCVR PRESELECTOR

Copy weak, barely readable signals. Reject images, out-of-band signals. 1.8 to 54 MHz. Up to 20 db gain. Automatic bypass. PTT. 20 db attenuator. Use 2 ant., 2 rigs.



Copy weak, barely readable signals.
Automatic XCVR bypass.

\$99⁹⁵

NEW MFJ-1040 transceiver/receiver preselector lets you copy weak, barely readable signals.

Rejects out-of-band signals, images.

Strong signal ability reduces cross mod, overloading. Excellent signal-to-noise ratio.

Continuous 1.8 to 54 MHz: all HF amateur, shortwave bands. Up to 20 db gain. Gain control. Dual gate MOSFET, bipolar transistors for low noise, high gain, strong signal ability.

Push button switches for 20 db attenuator, ON/OFF BYPASS, 2 antennas, 2 receivers.

Dual coax and phono jacks for antennas, receivers. RF sensing relay automatically bypasses preselector when transmitting up to 350 watts input. Delay control. Jack for push-to-talk.

LED. 9-18 VDC or 110 VAC. 8x2x6 inches.

MFJ-1045, \$69.95. Same as MFJ-1040, less attenuator, xcvr auto bypass, delay control, PTT.

Use 1 ant., 1 rcvr. 5x2x6 in. 9 V bat., 9-18 VDC or 110 VAC with optional AC adapter, \$7.95.

Order from MFJ and try it — no obligation. If not delighted, return it within 30 days for refund (less shipping). One year limited warranty by MFJ.

Order today. Call toll free 800-647-1800. Charge VISA, MC or mail check, money order for \$99.95 for MFJ-1040 or \$69.95 for MFJ-1045 plus \$4.00 shipping and handling.

Don't wait any longer to pull out weak, rare DX.

CALL TOLL FREE ... 800-647-1800

Call 601-323-5869 for technical information, order/repair status. Also call 601-323-5869 outside continental USA and in Mississippi.

MFJ ENTERPRISES, INC.
BOX 494, MISSISSIPPI STATE, MS 39762

CIRCLE 19 ON READER SERVICE CARD


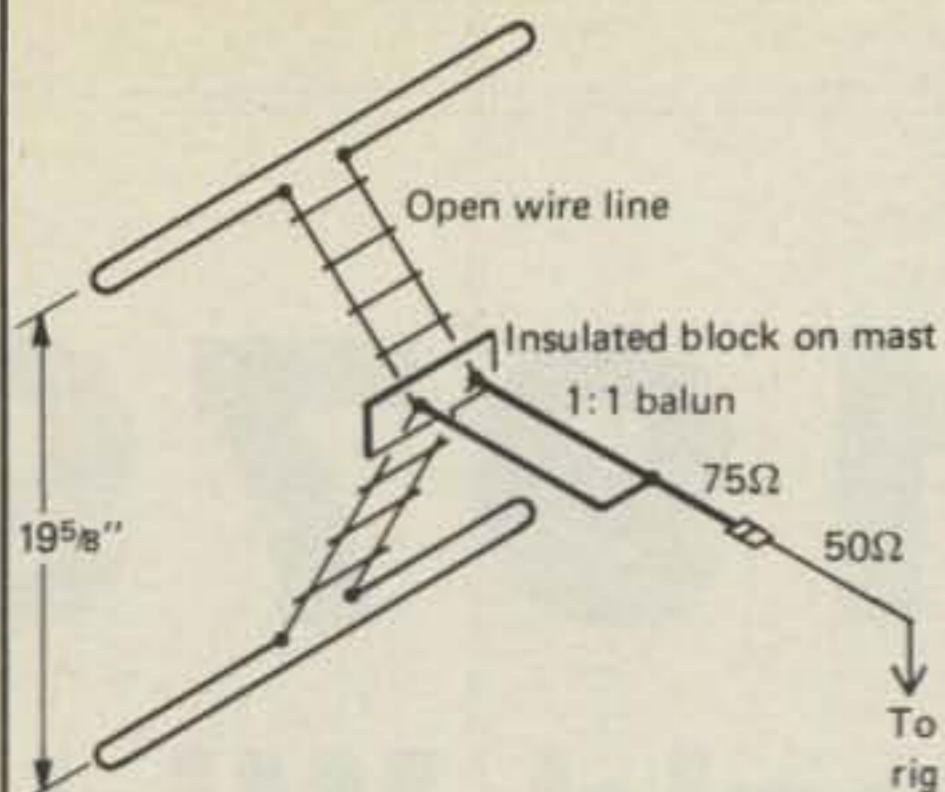


Fig. 2—A feed system for a two-stacked array.

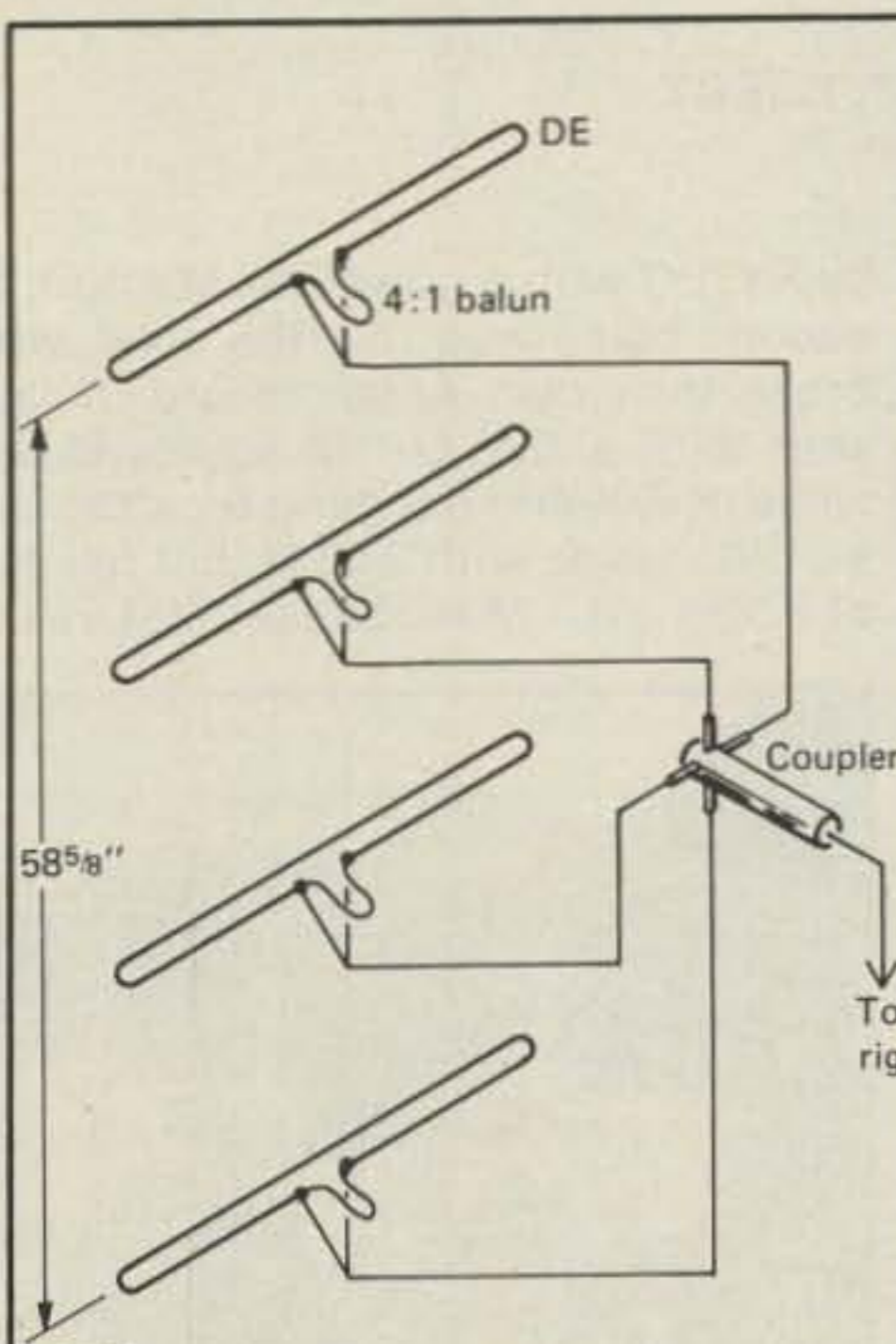

NOTE:
All branches are of equal length (any odd multiple of $\lambda/4$)

Fig. 3—Feeding a four-stacked array.

feedpoint. To match 50 ohm downlead, a 75 ohm section with a 1:1 balun is used as a transformer. Type N fittings are mandatory. Don't use "UHF" types. And if a long coax run is unavoidable, use the newer type having a #18 or even #14 center conductor.

Four-bay arrays should use 4 equal lengths of coax with 4:1 $\lambda/2$ loop baluns. These ideally should terminate into a 4-port transformer-coupler (commercially available from KLM Electronics), with a 50 ohm run to the shack.

The overall dimensions of even a 4-bay array are quite reasonable, and many hours of good DXing will reward the u.h.f. amateur who constructs this "Ultra Yagi."

Say You Saw It In CQ

September, 1980 • CQ • 45