

# EDN®

ELECTRONICS DESIGN NETWORK

JUNE **21**  
Issue 12/2012  
[www.edn.com](http://www.edn.com)



Welcome to the new  
EDN.com Pg 10

Baker's Best Pg 18

Fluid power: the  
hidden giant Pg 24

Design Ideas Pg 44

Supply Chain Pg 50

Aluminum box foils Frank-  
enstein's monster Pg 54

## WIRELESS-SENSOR NETWORKS' OPERATING POWER ARRIVES VIA THIN AIR

Page 36

A closer look at  
LSI's MegaRAID SAS  
9260CV-4i controller  
Page 20

The analog view:  
examining TI's audio  
capacitive-touch  
booster-pack  
demo board  
Page 27




**NEW  
PRODUCTS  
ADDED DAILY**

**DIGIKEY.COM/NEW**
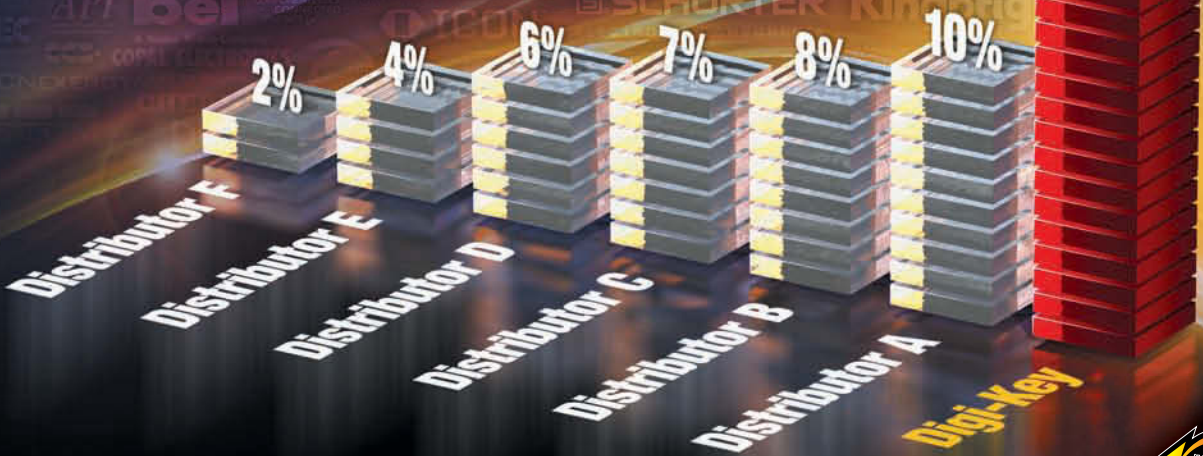
# BEST of CLASS!

Which single distributor comes to mind as being 'best of class' for broadest overall product selection?

SOURCE: 2011 DESIGN ENGINEER AND SUPPLIER INTERFACE STUDY, HEARST BUSINESS MEDIA ELECTRONICS GROUP



1.800.344.4539  
**DIGIKEY.COM**

2 MILLION PARTS ONLINE | 500+ INDUSTRY-LEADING SUPPLIERS | NEW PRODUCTS ADDED DAILY

Digi-Key is an authorized distributor for all supplier partners. New products added daily. © 2012 Digi-Key Corporation, 701 Brooks Ave. South, Thief River Falls, MN 56701, USA





- Distributed
- Factorized
- Power Management
- Innovation
- Integration
- Performance
- Speed
- Efficiency
- Density

# More **Flexibility**

Vicor gives power system architects the flexibility to choose from modular, plug-and-play components, ranging from bricks to semiconductor-centric solutions with seamless integration across all power distribution architectures. From the wall plug to the point of load.

Don't let inflexible power products slow you down. Choose from limitless power options to speed your competitive advantage.

**Flexibility. Density. Efficiency.**  
Trust your product performance to Vicor

- Support
- Expertise
- Productivity
- Reliability
- Qualified

**VICHIP**  
High Performance Power Modules

**PICOR**  
Semiconductor Power Solutions


**BRICK**  
Flexible Module Power

**VICOR**  
The Power Behind Performance

[vicorpower.com/rp/flexibility/edn](http://vicorpower.com/rp/flexibility/edn)

**TIP 1** For an inductor with the absolute maximum Q, pick one of these air core “Springs”. They have flat tops for easy mounting and exceptional current ratings.

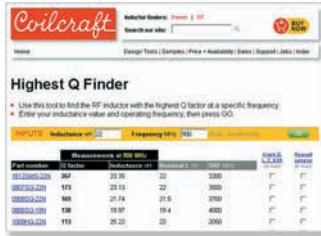**TIP 2** If you prefer conventional chip inductors, you’ll get the highest Q with our new ceramic body 0402HP and 0603HP families. These tiny wirewound coils handle up to 2 times more current than the nearest competitor.



*This new web tool finds inductors with the highest Q at your operating frequency*

**TIP 3** Need to find coils with the best Q at your L and frequency? Our **Highest Q Finder** web tool tells you in just seconds. Click again to plot the L, Q, Z and ESR of up to 4 parts simultaneously.


**TIP 4** When it's time to build your prototypes, be sure to ask us for evaluation samples. They're always free and we can get them to you overnight. To get started, visit [www.coilcraft.com/Q](http://www.coilcraft.com/Q)
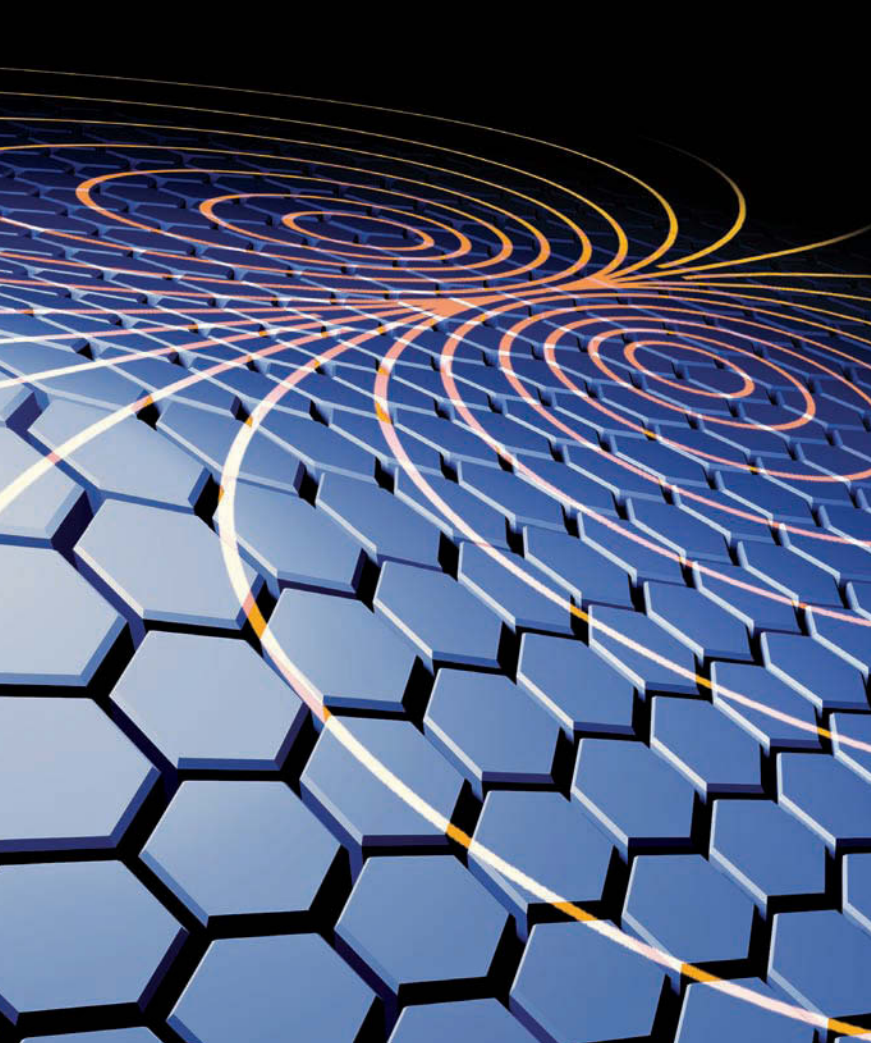
# Here are some high Q tips



[WWW.COILCRAFT.COM](http://WWW.COILCRAFT.COM)





# EDN contents

6.21.12



## Wireless-sensor networks' operating power arrives via thin air

**36** Transmitting usable energy through the air to power wireless-sensor-network nodes may sound like a pipe dream, but several companies are proving that it can work.

*by Dan Strassberg,  
Contributing Technical Editor*


## The analog view: examining TI's audio capacitive-touch booster-pack demo board

**27** A look at the analog architecture provides insight into the design choices Texas Instruments made for its audio capacitive-touch booster-pack demo board.

*by Steve Taranovich,  
Senior Technical Editor*

COVER IMAGE: SHUTTERSTOCK IMAGES / GIULIA-FINI-GULOTTA

## DESIGN IDEAS

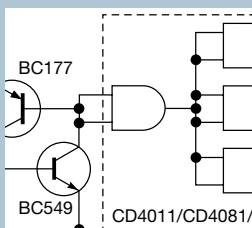

44 Complementary-pair dc/dc converter simultaneously doubles, inverts supply voltage

46 Adjust power-efficient LED switch to any light intensity

47 Obtain a gain of 450 from one vacuum tube

48 Probing system lets you test digital ICs

► Submit your own Design Idea to [edndesignideas@ubm.com](mailto:edndesignideas@ubm.com).

# Welcome to the mobile age of data monitoring and control.



Scan the QR code or visit <http://goo.gl/nELPY> to see a 34972A product tour video



The Agilent 34972A Data Acquisition Switch Unit takes our best-selling Agilent 34970A to the next level with built-in LAN and USB connectivity. You can even control everything remotely via mobile Web interface (phone or tablet). So you can collect and understand more data, more quickly.

34972A	34970A
BenchLink data logger software SCPI programming	
3-slot LXI unit with built-in 6½ digit DMM	
USB and LAN	GPIO and RS-232
Graphical web interface	N/A
\$1,845*	\$1,597*

\* Prices are in USD and are subject to change

**Agilent and our  
Distributor Network**  
Right Instrument.  
Right Expertise.  
Delivered Right Now.



866-436-0887  
[www.metrictest.com/agilent](http://www.metrictest.com/agilent)

**FREE mobile app and wireless  
connectivity measurement tips**  
[www.metrictest.com/agilent/daq.jsp](http://www.metrictest.com/agilent/daq.jsp)

© 2012 Agilent Technologies, Inc.

Anticipate — Accelerate — Achieve



**Agilent Technologies**



- 12 3-D heterogeneous FPGA targets line-card applications
- 14 Wireless rechargers cut the cord to devices
- 14 72W LED driver targets use in outdoor lighting
- 16 MEMS-based tennis racquet enhances playing experience
- 16 Monolithic component integrates isolation plus ADC for ac-line-voltage monitoring
- 17 LED drivers go modular to eliminate external components
- 17 Sub-\$1000 oscilloscopes offer powerful capabilities

## DEPARTMENTS & COLUMNS



52



54

- 8 **EDN online:** Join the conversation; Content; Engineering Community
- 10 **EDN.comment:** Welcome to the new EDN.com
- 18 **Baker's Best:** EMI problems? Part five: Check out amps with EMIRR specs
- 20 **Teardown:** A closer look at LSI's MegaRAID SAS 9260CV-4i controller
- 24 **Mechatronics in Design:** Fluid power: the hidden giant
- 50 **Supply Chain:** Cost analysis: Reshoring is viable; Smartphones, media tablets propel mobile-memory chip market
- 52 **Product Roundup:** Memory and Storage
- 54 **Tales from the Cube:** Aluminum box foils Frankenstein's monster

EDN® (ISSN# 0012-7515) is published semimonthly by UBM Electronics, 600 Community Drive, Manhasset, NY 11030-3825. Periodicals postage paid at Manhasset, NY, and at additional mailing offices. SUBSCRIPTIONS—Free to qualified subscribers as defined on the subscription card. Rates for nonqualified subscriptions, including all issues: US, \$150 one year; \$250 two years; \$300 three years. Except for special issues where price changes are indicated, single copies are available for \$10 US and \$15 foreign. For telephone inquiries regarding subscriptions, call 847-559-7597. E-mail: edn@meda.com. CHANGE OF ADDRESS—Notices should be sent promptly to EDN, PO Box 3609, Northbrook, IL 60065-3257. Please provide old mailing label as well as new address. Allow two months for change. NOTICE—Every precaution is taken to ensure accuracy of content; however, the publishers cannot accept responsibility for the correctness of the information supplied or advertised or for any opinion expressed herein. POSTMASTER—Send address changes to EDN, PO Box 3609, Northbrook, IL 60065-3257. CANADA POST: Publications Mail Agreement 40612608. Return undeliverable Canadian addresses to APC, PO Box 503, RPO West BVR CRE, Rich Hill, ON L4B 4R6. Copyright 2012 by UBM. All rights reserved. Reproduction in whole or part without written permission is prohibited. Volume 57, Number 12 (Printed in USA).

# Benchmark MOSFETs

## DC-DC Buck Converter and POL Applications

**SO-8**

Part	V	nC	mΩ
IRF8788PBF	30	44	2.8
IRF8714PBF (Ctrl)	30	8.1	8.7
IRF7862PBF (Sync)	30	30	3.7

**PQFN (5x6)**

Part	V	nC	mΩ
IRFH5303	30	15	4.2
IRFH5304	30	16	4.5
IRFH5306	30	7.8	8.1
IRFH5301	30	37	1.9
IRFH5302	30	4.8	2.1
IRFH5302D	30	26	2.5

**PQFN (3x3)**

Part	V	nC	mΩ
IRFHM831	30	7.3	7.8
IRFHM830	30	15	3.8
IRFHM830D	30	13	4.3

**PQFN (2x2)**

Part	V	nC	mΩ
IRFHS8342	30	4.2	16
IRFHS8242	25	4.3	13

**Your FIRST CHOICE for Performance**

For more information call 1.800.981.8699  
or visit [www.irf.com](http://www.irf.com)

International  
**IR Rectifier**  
THE POWER MANAGEMENT LEADER




## JOIN THE CONVERSATION

Comments, thoughts, and opinions shared by *EDN's* community



In response to “USB 3.0 bringing SuperSpeed connectivity to mobile devices,” a technical article by **Vikas Dhurka and Steven Chen of Cypress Semiconductor**, <http://bit.ly/JZqmc9>, **William K** comments:

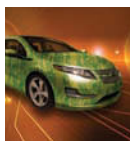*“I see USB3 as a marketing gimmick that will not deliver as promised because the hardware will never be adequate for that data rate. It is just one more effort to make current systems obsolete in order to sell new systems. We simply don't need it.”*



In response to **Rick DeMeis's** May 10 cover story, “**Teardown reveals Chevy Volt's electronic secrets,**” <http://bit.ly/JFt9KQ>, **Adam Perry** comments:

*“How would such a vehicle detect whether it was inside or outside? What about variables like parking garages and carports wherein it would be perfectly acceptable to have a gasoline engine running? And why would it matter?”*

*Based on the description in the article, wherein they ‘left some systems on,’ it sounds to me like they left the car both on and doing something (heating or cooling, or perhaps just powering some lighting).*

*I'll bet dollars to donuts that the car's manual (which is not necessarily optional reading material on such a machine) has numerous stern warnings about not leaving the car on inside of an enclosed space due to the possibility of the engine starting.*

*Meanwhile, it's plainly preferable to have this functionality as it is so that it's possible to (say) wait to pick someone up in a parking garage—and—have heat at the same time, regardless of the battery's state of charge.”*

**EDN invites all of its readers to constructively and creatively comment on our content. You'll find the opportunity to do so at the bottom of each article and blog post.**



## CONTENT

Can't-miss content on EDN.com

### GaN-ON-GaN BREAKTHROUGH LED BOOSTS MR16 PERFORMANCE

A young start-up has developed the technology to grow GaN crystals on its native GaN substrate so that the crystals grow with fewer imperfections and can accommodate higher power densities. The company claims the LED emits five to 10 times more light from the same crystal area.

<http://bit.ly/LPMIwd>



### OSCIUM'S LOGISCOPE: NOT QUITE THE SECOND COMING OF STAR WARS, BUT STILL A NEW TESTING HOPE

Oscium not-so-humbly claims that its product line represents “the future of test equipment.”

Although he has some doubts on pricing, see why one engineer can't argue with its prognostication.

<http://bit.ly/KnmYvK>




## ENGINEERING COMMUNITY

Opportunities to get involved and show your smarts
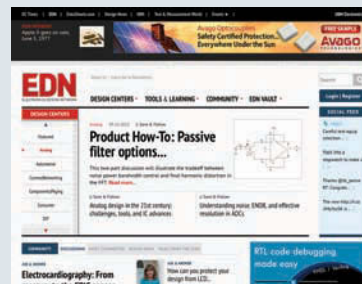
### A NETWORK FOR THE ENGINEERING COMMUNITY

We've redesigned EDN.com to better represent the community of engineers and electronics specialists it comprises. Fill out your EDN.com profile today and gain access to our full network of resources, including the ability to follow like-minded users of EDN.com, save content and tools to your personal library, and follow discussions. [www.EDN.com](http://www.EDN.com)





**BRAND DIRECTOR**

Patrick Mannion  
1-631-543-0445;  
patrick.mannion@ubm.com

**EXECUTIVE EDITOR**

Rich Pell  
*Consumer*  
1-516-474-9568  
rich.pell@ubm.com

**MANAGING EDITOR**

Amy Norcross  
*Contributed technical articles*  
1-781-869-7971;  
amy.norcross@ubm.com

**MANAGING EDITOR, ONLINE**

Suzanne Deffree  
*Electronic Business, Distribution*  
1-631-266-3433;  
suzanne.deffree@ubm.com

**SENIOR TECHNICAL EDITOR**

Margery Conner  
*Design Ideas, Power Sources,  
Components, Green Engineering*  
1-805-461-8242;  
margery.conner@ubm.com

**SENIOR TECHNICAL EDITOR**

Steve Taranovich  
*Analog, Systems Design*  
1-631-413-1834;  
steve.taranovich@ubm.com

**DESIGN IDEAS  
CONTRIBUTING EDITOR**

Glen Chenier  
edndesignideas@ubm.com

**SENIOR ASSOCIATE EDITOR**

Frances T Granville  
1-781-869-7969;  
frances.granville@ubm.com

**ASSOCIATE EDITOR**

Jessica MacNeil  
1-781-869-7983;  
jessica.macneil@ubm.com

**COLUMNISTS**

Howard Johnson, PhD, Signal Consulting  
Bonnie Baker, Texas Instruments  
Pallab Chatterjee, SiliconMap  
Kevin C Craig, PhD, Marquette University

**CONTRIBUTING TECHNICAL EDITORS**

Dan Strassberg  
strassbergedn@att.net  
Brian Bailey  
brian\_bailey@acm.org  
Robert Cravotta,  
robert.cravotta@embeddedinsights.com

**VICE PRESIDENT/DESIGN DIRECTOR**

Gene Fedele

**CREATIVE DIRECTOR**

David Nicastro

**ART DIRECTOR**

Giulia Fini-Gulotta

**PRODUCTION**

Adeline Cannone, Production Manager  
Laura Alvino, Production Artist  
Yoshihide Hohokabe, Production Artist  
Diane Malone, Production Artist

**EDN EUROPE**

Graham Prophet  
Editor, Reed Publishing  
gprophet@reedbusiness.fr

**EDN ASIA**

Huang Hua  
Operations General Manager  
huang.hua@ednasia.com  
Grace Wu  
Associate Publisher  
grace.wu@ednasia.com  
Vivek Nanda  
Executive Editor  
vnanda@globalsources.com

**EDN CHINA**

Huang Hua  
Operations General Manager  
huang.hua@ednchina.com  
Grace Wu  
Associate Publisher  
grace.wu@ednasia.com  
Jeff Lu, Executive Editor  
jeff.lu@ednchina.com

**EDN JAPAN**

Masaya Ishida, Publisher  
mishida@mx.itmedia.co.jp  
Makoto Nishisaka, Editor  
mnishisa@mx.itmedia.co.jp

**UBM ELECTRONICS  
MANAGEMENT TEAM**

Paul Miller,  
Chief Executive Officer, UBM Technology  
Kathy Astromoff,  
Chief Executive Officer, UBM Electronics  
Brent Pearson  
Chief Information Officer  
David Blaza  
Senior Vice President  
Karen Field  
Senior Vice President, Content  
Jean-Marie Enjuto  
Vice President, Finance  
Barbara Couchois  
Vice President,  
Partner Services and Operations  
Felicia Hamerman,  
Vice President, Marketing  
Amandeep Sandhu,  
Director of Audience Engagement  
and Analytics




For a complete list of editorial contacts,  
see <http://ubmelectronics.com/editorial-contacts>

# MAXIMUM SELECTION OF PCB PINS & RECEPTACLES



## OVER 800 STYLES AND OPTIONS IN STOCK

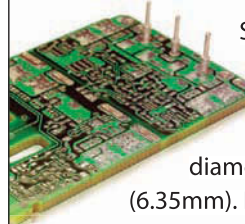

Suitable for applications subject to high amounts of vibration and shock, Mill-Max pins and receptacles are available in diameters from .008" (.20mm) to .250" (6.35mm). Receptacles feature a 4 or 6 finger beryllium copper or beryllium nickel contact to ensure integrity of connection for use in the harshest environments.

**Don't see what you need? Rapid prototyping and custom designs are our specialty.**

# MILL-MAX®

[www.mill-max.com/EDN621](http://www.mill-max.com/EDN621)



Follow us  
**MillMaxMfg**




Like us  
**Mill-Max Mfg. Corp.**



BY PATRICK MANNION, BRAND DIRECTOR
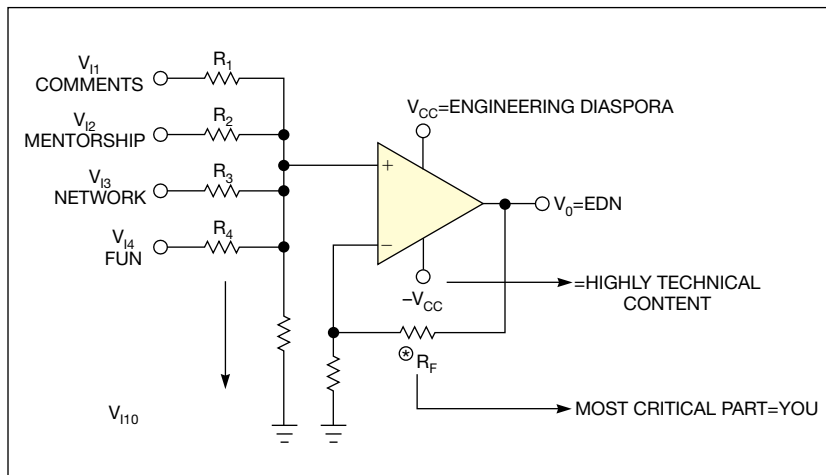
## Welcome to the new EDN.com

**W**elcome to the new EDN.com: the Electronics Design Network for electronics engineers, innovators, and creators who want to get from concept to reality as quickly as possible, and just maybe take time out to have a little fun in the process. For many of you, the name Electronics Design Network may raise an eyebrow, and well it should. The print publication was launched originally in 1956 as *Electrical Design News*. The name later morphed into simply *EDN*, an information resource for engineers, by engineers. The word “network,” however, goes to the heart of what the redesigned site is all about: empowering designers in your effort to make a difference by connecting you with the information, peers, resources, tools, companies, services, and people you need to get your ideas realized and out the door.



This sounds like a lot, and it is. That said, over the years *EDN* has remained true to its promise to provide solid technical information and insight for the working engineer, but information can take you only so far. We’ve seen on our site increased interaction and discussions that were for the most part hidden from view. With the new site, we’ve taken your voices, insights, and opinions and put them front and center. But that’s just the beginning.

*EDN* has made the shift from a site with information you *consume* to a community platform for information, resources, and connections you can *use*. From the ground up, the site has been designed to make it just that: more useful for you. Improvements include a cleaner and more navigable look and feel, as well as added features that are a nod to the most practical and interesting aspects of social media, but in a safe environment tailored for engineers’ specific needs.

Other enhancements include Profile pages: Use yours to let the world know who you are, your technical expertise, and how you like to pass your time. You can also start here to upload your own content to *EDN*, see who you’re following, keep track of your *EDN* library, and view your comments and articles. And that’s just for now. Look soon for points you’ve accrued as you’ve used the site. You can use these points to show your domain expertise, or you might want to cash them in for attendance at technical conferences such as DesignCon, Design West, and Design East, or spend them at the *EDN* Store.

## The Electronics Design Network [is] for electronics engineers, innovators, and creators.

We’ve also added a tools section, more design centers, simpler comment functionality, and the ability to follow your favorite threads. Forums are now central to our offering, and we’ve opened the floodgates to your own open-mic blogs. Let us know if you want to get something off your chest; we now have the platform that will allow you to do so.

I could spend pages talking about what we’ve done to the site, but instead, I drew up a quick sketch that may save a lot of time (see **figure**).

In the end it boils down to being all about you. We hope you like the new *EDN.com* and can find ways to make it work for you. If there are things you’d like to see added, let us know. If there are elements you’d like to see tweaked or removed, let us know that, too. The site is a living entity that depends upon you to make it live. Six months from now, it could look different and have different elements. And that’s good, because what changes will be based on your feedback. So let ’er rip! **EDN**

Contact me at [patrick.mannion@ubm.com](mailto:patrick.mannion@ubm.com), or comment directly on the new *EDN.com* at <http://bit.ly/KdZXHA>.

# Touch The Future

The Aeroflex S-Series is the future and the future is **touch**. The future is fast and complex and needs an instrument platform to meet your evolving needs. The S-Series has evolved to make complex measurements fast with the simplicity of our unique totally touch measurement interface.

The S-Series is uniquely scalable with multiple instruments 'Aerolocked' together within a standard 19" format. Build your measurements from our S-Series range of signal generators, signal analyzers and function modules and control them using Aeroflex automation framework.

The **SGA** sets the standard for switching speed and noise. **That's fast.**

The **SGD** leads the way with the bandwidth required for the latest wireless standards including 802.11ac, LTE-A and beyond. With coherent signal generation over multiple sources for MIMO. **That's smart.**

The **SVA** is the widest band and fastest signal analyzer in its class. **Now that's fast and smart.**

**Touch the future with the fast and smart Aeroflex S-Series!**



See Aeroflex performance in action.

See how we did it - view our video at: [www.aeroflex.com/touchedn0612](http://www.aeroflex.com/touchedn0612)

**AEROFLEX**  
A passion for performance.

[www.aeroflex.com](http://www.aeroflex.com)

# pulse

INNOVATIONS & INNOVATORS

## 3-D heterogeneous FPGA targets line-card applications

Xilinx Inc has begun initial shipments of the Virtex-7 H580T FPGA, a single-chip solution for addressing key Nx100G and 400G line-card applications and functions. The 3-D heterogeneous FPGA uses the company's stacked silicon interconnect technology and is built on TSMC's 28-nm process. The all-programmable Virtex-7 H580T FPGA features up to 16 28-Gbps and 72 13.1-Gbps transceivers. Xilinx claims other monolithic FPGAs are able to integrate only a quarter of the number of 28-Gbps channels.

The heterogeneous implementation of Virtex-7 HT devices also enables Xilinx to make independent technology choices for the core FPGA and 28-Gbps transceiver die, which avoids burdening the FPGA with high-leakage transistors that waste system power and bring no benefit to computation tasks. Having 28-Gbps transceivers on silicon separate from the core FPGA fabric further allows for good noise isolation, enabling solid overall signal integrity and system margin, as well as improved productivity for design closure and faster

time to market, according to the company.

Effectively upgrading networks to handle exponential growth in data usage requires power and port-density improvements in optical modules while reducing cost per bit. Driven by the migration to CFP2 and, in the future, CFP4 optical modules, Virtex-7 HT devices are designed to enable that integration capability for communication equipment vendors designing Nx100G and 400G line cards.

"Competing ASSP-based solutions will comprise five devices, will remain unavailable for more than a year, will consume at least 40% additional power, and will cost 50% more," says Mark Gustlin, system architect for wired communications at Xilinx.


The upcoming Virtex-7 H870T device is also 400GE ready and will be able to support future 400GE modules that require 16x25-Gbps interfaces. —by **Nicolas Mokhoff**

▷ **Xilinx Inc**, [www.xilinx.com](http://www.xilinx.com).

### TALKBACK

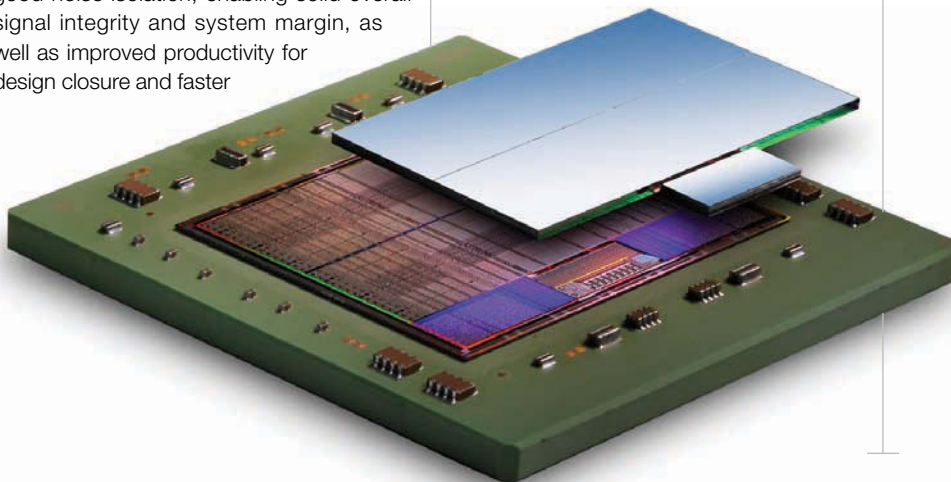**"I have been working in the LCD field for 23 years. The lack of standards on connectors and pin definitions has been a sore point with me also. We could never use the same circuit twice because the customer needed a slightly different display."**

—Commenter GregD52, in response to an entry in *EDN's* PowerSource blog, at <http://bit.ly/K9Wwq3>. Add your comments.



The Virtex-7 H580T uses the company's stacked silicon interconnect technology in the 3-D heterogeneous FPGA, which is built on TSMC's 28-nm process.

# Rarely Asked Questions

Strange stories from the call logs of Analog Devices

## Transformers: They're Not All Boat Anchors

**Q.** What is the most undervalued analog component?

**A.** Probably the transformer. From college, many engineers remember transformers as the large components in power supplies which contain a lot of iron and copper and which are heavy enough to do serious damage if dropped on one's foot.

This is certainly true of the large low-frequency (50- or 60-Hz) power transformers which are sometimes disparagingly called "boat anchors" (the transformers in power stations would do catastrophic damage if dropped on a battleship), but today a wide variety of inexpensive transformers may be as small as an aspirin tablet.

Even though their input supply may be the 50-/60-Hz mains, switching power supplies work at much higher frequencies. They can use much smaller, lighter, and cheaper transformers than traditional supplies of the same power rating, so even the transformers in power supplies are lighter today. Analog Devices manufactures controllers for such switching supplies, but they are not the subject of this RAQ.

For innumerable ac analog applications, a transformer is the most appropriate component. This was widely known sixty to eighty years ago when amplifiers often used transformers for interstage coupling, and as phase splitters between single-ended and push-pull circuits. About forty or fifty years ago, however, transistors—and shortly afterwards integrated circuits—started to use dc interstage coupling, so the use of signal transformers was largely forgotten.

In many applications these dc-coupled techniques are indeed the optimum solution,



but where ac signals must cross an isolation barrier (where there may be a large potential difference between the signal circuitry in different parts of the system, for example) or where there is severe ground noise, the use of a transformer may simultaneously simplify the design and improve performance. It is normal for transformers to have absolute maximum interwinding voltage values of hundreds or even thousands of volts. In addition, the primary-secondary capacitance is rarely more than a few pF and may be even less for a screened transformer.

Where an ac signal must be sent an appreciable distance in the presence of ground noise, a transformer may well have considerably better ac common-mode rejection (CMR) than a differential amplifier; and where a differential ac amplifier is being fed with a single-ended signal, a transformer will probably be the best possible phase splitter.

And then there are current transformers for ac current measurements....



**Contributing Writer**  
James Bryant has been a European Applications Manager with Analog Devices since 1982. He holds a degree in Physics and Philosophy from the University of Leeds. He is also C.Eng., Eur. Eng., MIEE, and an FBIS. In addition to his passion for engineering, James is a radio ham and holds the call sign G4CLF.

**Have a question involving a perplexing or unusual analog problem? Submit your question to:**  
[www.analog.com/askjames](http://www.analog.com/askjames)

For Analog Devices' Technical Support, Call 800-AnalogD

**To Learn More About AC Signal Processing**  
<http://dn.hotims.com/41003-100>

SPONSORED BY



<sup>1</sup> For example see <http://www.meppi.com/Products/Transformers/Pages/GSU.aspx>

## Wireless rechargers cut the cord to devices

Wireless inductive battery rechargers have cut the cable to many devices, such as electric toothbrushes, but until recently they still required a proprietary recharge station because there were no standards in place. However, now that the Wireless Power Consortium has more than 100 members for its Qi standard, analysts predict that the time is ripe for a global wireless-charging market, which is expected to exceed 100 million units annually by 2015, according to IMS Research.

Japan's Docomo has been test-marketing Qi-compatible recharge stations in public places to support its deployment of power-hungry LTE smartphones, and even auto-

mobile makers are getting onboard, with Dodge promising a Qi-compatible smartphone recharger built into its console. These and other commercial Qi-compatible rollouts are promised over the next three years.

For OEMs that want to quickly enter the Qi-compatible wireless-recharging-station market, Freescale Semiconductor has crafted three reference designs enabling users to wirelessly recharge any tablet, smartphone, or other mobile device. The company offers reference designs for smartphones that can supply as much as 5W; for tablets that supply as much as 30W; and for power tools, kitchen appliances, medical devices, and



Wireless rechargers cut the last cord to tablets merely by lying them on a specially wired surface.

laptop computers that can supply more than 100W in wireless-recharge power, according to Ron Lowman, industrial- and multimarket-marketing manager at Freescale.

Freescale recently began a partnership with Fulton Innovation, which has more than 186 granted patents and 496 pending in the wireless-recharge area. By including the latest

innovations in Freescale's reference designs, OEMs can achieve efficiencies of more than 80%, support multiple coils so that devices do not need perfect placement, and take advantage of safety features that keep foreign objects from heating up.

—by R Colin Johnson

► **Freescale Semiconductor**, [www.freescale.com](http://www.freescale.com).

## 72W LED driver targets use in outdoor lighting

The 72W, constant-voltage PDA072B-24VG LED driver from Pihong powers area, wash, and architectural lighting in harsh environments. The device has a Class 2 output of 24V dc at 3A and complies with Energy Star specifications for solid-state-lighting luminaires. With separate driver ICs to power several luminaires from one

source, the PDA072B works in both damp and dry environments. The fully potted, water-resistant device has an ingress-protection rating of 65 and operates in temperatures of -40 to +60°C. It also features power-factor corrections greater than 0.9 and bears safety-approval markings from UL and CE.

The power supply's mini-

mum average efficiency is 84% for 120V-ac input and 88% for 277V-ac input. The device has a measured lifespan of 50,000 hours at maximum load and offers overvoltage, overcurrent, short-circuit, and open-circuit protection.

The PDA072B-24VG carries a standard five-year warranty, measures 241x43x30.5 mm, and weighs 750g. Prices for

the unit start at \$87.84 (one).

—by Fran Granville

► **Pihong**, [www.pihong.com](http://www.pihong.com).



The 72W, constant-voltage PDA072B-24VG LED driver from Pihong powers area, wash, and architectural lighting in harsh environments. The device has a Class 2 output of 24V dc at 3A and complies with Energy Star specifications for solid-state-lighting luminaires.

### DILBERT By Scott Adams



# Purity & Precision Speed & Ease Rohde & Schwarz FSW

The most advanced signal and spectrum analyzer for aerospace and defense applications.

The highest bandwidth, lowest phase noise, clearest user interface and a host of convenient new tools — all on the largest touchscreen available. The R&S®FSW is the perfect analyzer for testing all types of radar signals in aerospace and defense. Execute the most complex measurements with ease. See things that were previously undetectable. Go where no one has been before. The R&S®FSW. Compatible with today's technology. Built for tomorrow.

- ▮ Analyze oscillators and synthesizers with a phase noise of  $-137$  dBc (1 Hz)
- ▮ Measure frequency-hopping and chirp signals with a bandwidth of up to 160 MHz
- ▮ Find spurious signals five times faster
- ▮ Measure pulses, spurious and modulation at the same time with MultiView
- ▮ See more and obtain faster results on the large touchscreen

The R&S®FSW. Create the future.

[www.rohde-schwarz.com/ad/fsw](http://www.rohde-schwarz.com/ad/fsw)



## MEMS-based tennis racquet enhances playing experience

**M**ovea SA, a manufacturer of motion-sensing and gesture-recognition technology, has teamed with tennis-equipment manufacturer Babolat to develop a motion-sensing-enabled rac-

quet to analyze game play and improve performances. The companies demonstrated the first Babolat Play & Connect racquet prototype at the 2012 French Open tennis tournament in Paris.



The MEMS-enabled Play & Connect racquet aims to inform players about their skills, improve their game, and share the information on social networks.

Motion-sensing technologies are enabling a new generation of sports equipment and sportswear that can monitor, analyze, and improve the performance of sports enthusiasts and athletes. The microelectromechanical-system-technology-enabled racquet can gather and analyze game data and provide information that previously required manual measurement. It uses Movea's SmartMotion data-fusion technology to measure specific elements of a player's technique.

According to the companies, the Play & Connect racquet has three key objectives: to inform,

to improve, and to share. It aims to inform by enabling measurement and analysis of game play for elements, such as stroke qualification, ball spin, power during play, and service speed. It enables improvement by allowing players and instructors to set goals and follow progress on a daily, weekly, or monthly basis. It enables sharing by letting players post their game-play data on their social networks to encourage themselves; challenge their friends; and seek tips and advice from friends, instructors, and amateur and professional players.

—by Anne-Françoise Pele

► **Movea SA,**

[www.movea.com](http://www.movea.com).

► **Babolat,**

[www.babolat.com](http://www.babolat.com).

## Monolithic component integrates isolation plus ADC for ac-line-voltage monitoring

Monitoring ac lines is an important requirement for systems such as smart residential and commercial power, solar-power inverters, and uninterruptible power supplies. This monitoring involves challenges, however. The line voltages are higher than electronic circuits should directly handle, a problem you can easily solve using a resistor network. Such monitoring also involves serious system- and user-safety issues, requiring advanced techniques to achieve the mandatory galvanic isolation. To solve the isolation issue and address the data-acquisition function, the Si890x trio from Silicon Laboratories Inc incorporates capacitive-based digital isolation along with a 10-bit ADC. The small, low-profile devices come in a standard IC package.

The ICs, with 2.5- and 5-kV isolation rating, meet applicable safety standards, including IEC 60950-1, 61010-1, and 60601-1, and have UL, CSA, and VDE certifications. Targeting 120 and 220V-ac mains, the devices have a 1200V working voltage, providing an isolation barrier that allows more than 60 years of operation, using standard test and data-extrapolation techniques.

The Si890x devices provide a three-channel analog multiplexer feeding an isolated ADC, thus allowing the device to monitor as many as three differential channels—typically, current and voltage, plus a spare channel. The ADC reference can be either the IC's

supply rail or a separate user-supplied reference. The ADC offers a maximum of  $\pm 1$ -LSB integral and differential nonlinearity and a maximum of  $\pm 2$ -LSB offset and full-scale errors, along with a PGA (programmable-gain amplifier) with a gain of 0.5 or one. You can set the ADC to convert on demand or in burst mode. The devices also provide transient immunity of more than 35 kV/ $\mu$ sec and electric- and magnetic-field immunity of more than 300V/m and more than 1000A/m, respectively. The ICs operate from an input-side supply of 2.7 to 3.6V and an output-side supply of 2.7 to 5.5V; the isolated devices require separate supplies for each side.

The three members of the family differ in only their bus-interface digital I/O. Users can choose among the Si8900, with a 234k-sample/sec UART interface with automatic baud-rate selection algorithm; the Si8901, with a 240k-sample/sec I<sup>2</sup>C interface; and the Si8902, with a 2.5M-sample/sec SPI. The pinout for all three versions is identical except for the bus-interface pin assignments, so changing from one interface and IC to another requires minimal PCB rerouting.

The Si890x evaluation kit is a complete PCB with all three versions, along with a microcontroller, I/O connections, and a protective enclosure. The versions are available in a 16-pin wide-body SOIC package and sell for \$1.65 (10,000). —by Bill Schweber

► **Silicon Laboratories,** [www.silabs.com/pr/isolation](http://www.silabs.com/pr/isolation).



# PICO

## LED drivers go modular to eliminate external components

Texas Instruments' most recent introduction in the LED power-management space comprises two fully integrated LED-driver micromodules. TI claims the 450-mA TPS92550 and TPS92551 dc/dc buck modules are the industry's first to incorporate all of the required power and passive circuitry into a single IC-like package to deliver up to 23W of power to the LED array. These modules eliminate most external components as well as the complex layout decisions common in LED-driver designs by integrating the power management and control circuitry, the power inductor, and a handful of other passive components into a single 7-pin 10.16x9.85x4.57-mm package.

The TPS92550 is a high-power floating-buck LED driver with an input-voltage range of 4.5 to 36V. It requires no external current-sensing elements or loop-compensation network. The integrated power switch enables high output power up to 14W with 450-mA LED current. The TPS92551 can power up to 23W with an input-voltage range of 4.5 to 60V. High-speed dimming control input through the 0 to 5.5V  $V_{DIM}$  signal allows precision and high-resolution brightness control for



Together with TI's Webench LED Architect, LED-light designers can design a power-management circuit with a minimum number of components to drive a string of up to 18 LEDs at up to 96% power efficiency.

applications that require fine brightness adjustment.

Together with TI's Webench LED Architect, LED-light designers can design a power-management circuit with a minimum number of components to drive a string of up to 18 LEDs at up to 96% power efficiency. The 14W TPS92550 is \$5, and the 23W TPS92551 is \$5.50 (1,000).

—by Margery Conner

►Texas Instruments, www.ti.com.

## Sub-\$1000 oscilloscopes offer powerful capabilities

Agilent Technologies has introduced the 1000B series of two-channel oscilloscopes, with bandwidths of 50, 70, 100, or 150 MHz. The devices feature color LCDs with as many



The 1000B series of two-channel oscilloscopes offers bandwidths of 50, 70, 100, or 150 MHz and features color LCDs with as many as 16,000 points of memory per channel.

as 16,000 points of memory per channel and a 1G-sample/sec channel rate. The devices display 23 automatic measurements, including those it makes with a built-in frequency counter, and a standard go/no-go mask-testing capability. A sequence mode allows users to record and replay as many as 1000 occurrences of a trigger. The user interface and front-panel labels are available in 11 languages, and the devices include USB connections. A free educator kit helps teachers and professors teach essential oscilloscope skills.

Prices for the 50-, 70-, 100-, and 150-MHz versions are \$790, \$990, \$1190, and \$1589, respectively. —by Janine Love

►Agilent Technologies, www.agilent.com/find/1000BSeries.

[www.edn.com]

**DC-DC Converters**  
**2V to 10,000 VDC Output**

- Over 2500 Std. DC-DC Converters
- Surface Mount
- From 2V to 10,000 VDC Output
- 1-300 Watt Modules
- Isolated/Regulated/Programmable Models Available
- Military Upgrades Available
- Custom Models, Consult Factory

Delivery-Stock to one week for sample quantities

1509001:2000  
ANAB  
AS 9100 REV B

for **FREE** PICO Catalog  
Call toll free 800-431-1064  
in NY call 914-738-1400  
Fax 914-738-8225

**PICO Electronics, Inc.**  
143 Sparks Ave. Pelham, N.Y. 10803  
E Mail: info@picoelectronics.com  
www.picoelectronics.com



BY BONNIE BAKER



# EMI problems? Part five: Check out amps with EMIRR specs

As technology progresses, electromagnetic interference becomes more of a threat to the proper performance of circuits, due to the fact that electronic applications are moving to wireless communication or portable platforms. With this concept in mind, consider that most interfering EMI signals eventually convert into the PCB trace as conducted EMI.

As you strive to design robust EMI circuits, you'll find that analog sensor circuits tend to be great EMI receptors because sensor circuits often produce low-level signals and have many high-impedance analog ports. These circuits also use denser component spacing, which provides more opportunities for systems to acquire and conduct noise into the traces. Operational amplifiers can be prime targets in this EMI scenario (Reference 1).

A standard op amp has low-impedance positive-power, negative-power, and output pins and two high-impedance input pins (Figure 1a). Although all of these pins can sustain an EMI hit, the input pins are the most vulnerable.

The characteristics of the inverting and noninverting pins of a voltage-feedback amplifier are essentially equivalent. However, you can easily test the

EMI ruggedness of an amplifier at the noninverting input (Figure 1b), as the following equation shows:

$$\Delta V_{OS} = \left( \frac{V_{RFPEAK}^2}{100 \text{ mV p-p}} \right) \times 10^{-\left( \frac{EMIRR_{IN+} \text{ (dB)}}{20} \right)}$$

where  $V_{RFPEAK}$  is the peak amplitude of applied RF voltage,  $V_{OS}$  is the dc offset voltage of the amplifier, EMIRR is the EMI rejection ratio, and 100 mV p-p is the positive EMIRR to an input signal of 100 mV p-p.

You can compare amplifiers' EMI immunity with the EMIRR metric. Figure 2, available online at [www.edn.com/4374916](http://www.edn.com/4374916), shows the EMIRR positive input response of TI's OPA333 CMOS op amp. The figure indicates that the device can reject frequency signals greater than the device's bandwidth of 300 kHz.

An IC's internal EMI filter provides three distinct benefits over an external RC filter. First, it allows users to test the performance of the amplifier containing an integrated filter to ensure its EMIRR over a wide frequency range (references 2 and 3). Passive filter components suffer from nonidealities in parasitic capacitances and inductances, which limits the filter's ability to suppress noise at high frequencies. In contrast, IC processes closely match electrical characteristics of the on-chip passive components. Finally, the IC, with the internal filter, also offers reduced parts count, cost, and board area.

To reduce a circuit's EMI susceptibility, a board designer should pay attention to good layout practices by keeping traces short, using surface-mount components, and using a PCB with a dedicated ground plane for the signal returns. Keep the ground plane as complete as possible and keep the digital signals away from the analog-signal paths. Additionally, place RF-bypass capacitors on all of the IC's power-supply pins, position these capacitors close to the device pins, and make sure their impedances are as close to 0Ω as possible at the potential EMI frequencies. EDN

Bonnie Baker is a senior applications engineer at Texas Instruments and author of *A Baker's Dozen: Real Analog Solutions for Digital Designers*.

Go to [www.edn.com/4374916](http://www.edn.com/4374916) for links to the references used in this column.

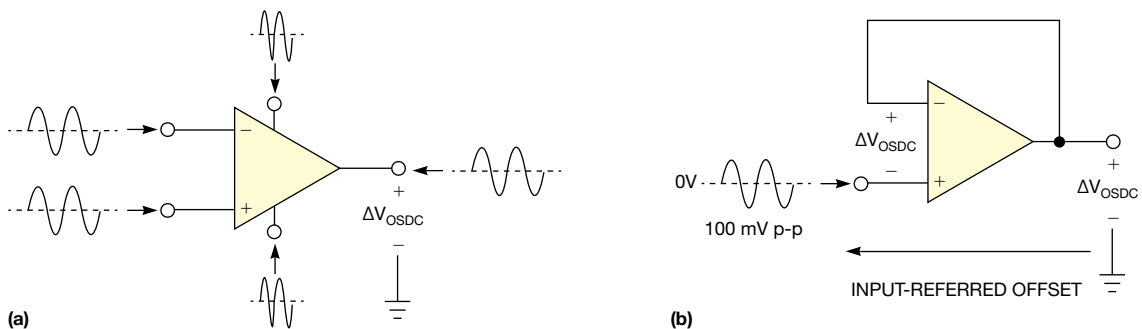


Figure 1 A standard op amp has low-impedance positive-power, negative-power, and output pins and two high-impedance input pins (a). You can easily test the EMI ruggedness of an amplifier at the noninverting input (b).

# FIVE YEARS OUT.

**AUTOMOTIVE:** More intelligence, more sensors, more sustainable and, of course, more electronics. Are you Five Years Out? Then you're probably working with us.

**ANALOG**  
Five Years Out

## WANT MORE?

- + Go to [www.edn.com/learning/teardowns](http://www.edn.com/learning/teardowns) for more Teardowns.
- + EDN partner UBM TechInsights publishes even more teardowns here: [www.ubmtechinsights.com/teardowns](http://www.ubmtechinsights.com/teardowns).

## A closer look at LSI's MegaRAID SAS 9260CV-4i controller

Hardware RAID (redundant array of independent disks) controllers have been around for quite some time, growing in popularity with the rise in use of ATA hard drives. A crowded market, featuring products from companies such as Intel, Adaptec, HP, and Promise, requires manufacturers of these types of cards to produce devices that will stand out against the rigorous testing and benchmarks set by users. In the relatively short history of RAID controllers, a changing of the guard took place when SAS and SATA replaced parallel SCSI and PATA as the serial interfaces of choice. LSI's MegaRAID SAS 9260CV-4i controller takes advantage of both the SAS and SATA interfaces to operate stably and offer high performance, the two biggest demands of its market.

The MegaRAID controller features the proprietary 800-MHz LSISAS2108 ROC (RAID-on-Chip), 512-MByte DDR2 cache memory, and a x8 PCI Express 2.0 host bus interface. Its strongest feature, however, is CacheVault technology, which uses NAND flash memory powered by a supercapacitor to protect data stored in the MegaRAID controller cache. CacheVault technology claims to have a "greener" approach to cache protection, eliminating the need for the lithium-ion battery that traditional PCI-based RAID controllers require to protect DRAM cache memory.

In this controller, data is automatically written to the cache via the NAND flash when a power failure occurs, while the charged supercapacitor keeps cur-

rent continuous during operation. Once power returns, the DRAM is recovered from the NAND flash, and the system experiences no loss of data. Based on CacheVault alone, you could see the appeal of MegaRAID controllers to IT workers everywhere.


The MegaRAID 9260CV-4i controller consists of three boards: a main board, which features the I/O of the controller; a daughterboard that houses the DDR2 SDRAM array; and the CacheVault power-module board, which is the heart of the CacheVault technology that distinguishes the MegaRAID controller from its competitors.

The primary components of the CacheVault power-module board are AGIGA Tech supercapacitors and a



Cypress Semiconductor CY8C29466 programmable SOC. The Cypress SOC acts as a smart controller, while the four large capacitors are used in conjunction with this SOC to supply power in case of power failure. Cached information in the volatile SDRAM will be transferred to NAND flash before power is completely drained.

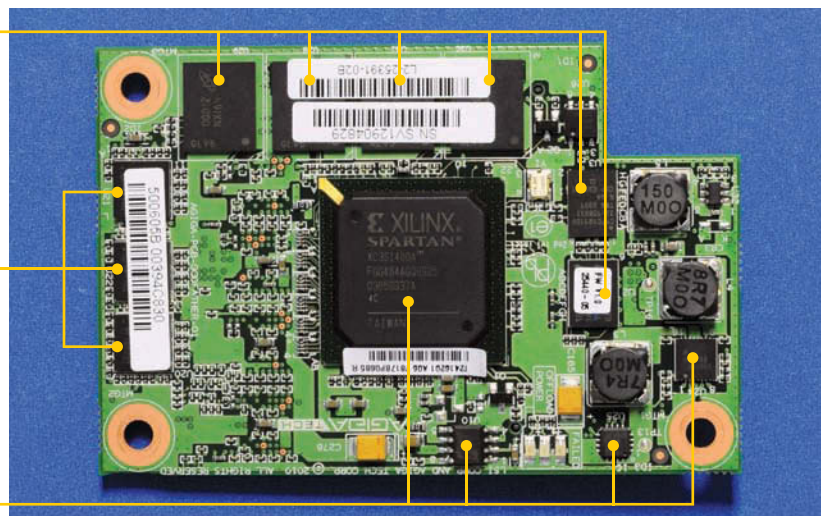The daughterboard consists of numerous design wins from large-scale companies such as NXP, Analog Devices, Cypress, and ST Microelectronics. The notable devices on the front side of the board include Xilinx's XC3S1400A Spartan-3A FPGA and four 4-Gbit NAND flash devices provided by Micron Technology.





Find it at  
[mathworks.com/accelerate](http://mathworks.com/accelerate)  
datasheet  
video example  
trial request

# GENERATE HDL CODE AUTOMATICALLY

from


# MATLAB and Simulink



**HDL CODER™** automatically converts Simulink models and MATLAB algorithms directly into Verilog and VHDL code for FPGAs or ASIC designs. The code is bit-true, cycle-accurate and synthesizable.
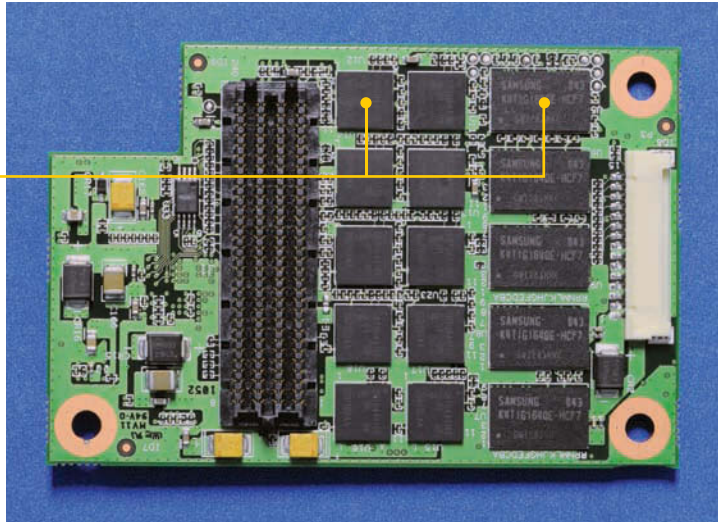
## TEAR DOWN


The back side of the daughter-board features five Samsung 128-MByte DDR2 SDRAM components (K4T1G164QE) and 10 NXP CBTU4411EE DDR2 SDRAM multiplexers that operate with the aforementioned Samsung SDRAM.



The third board on the RAID controller, the main board, consists of socket wins for Texas Instruments, providing the Hex-Schmitt-trigger inverter (SN74LVC14APW), and NXP, providing the I<sup>2</sup>C switch and the I<sup>2</sup>C-bus LED driver. The major IC on this board is LSI's LSISAS2108 SAS ROC, which drives the prime functionality of the RAID controller.



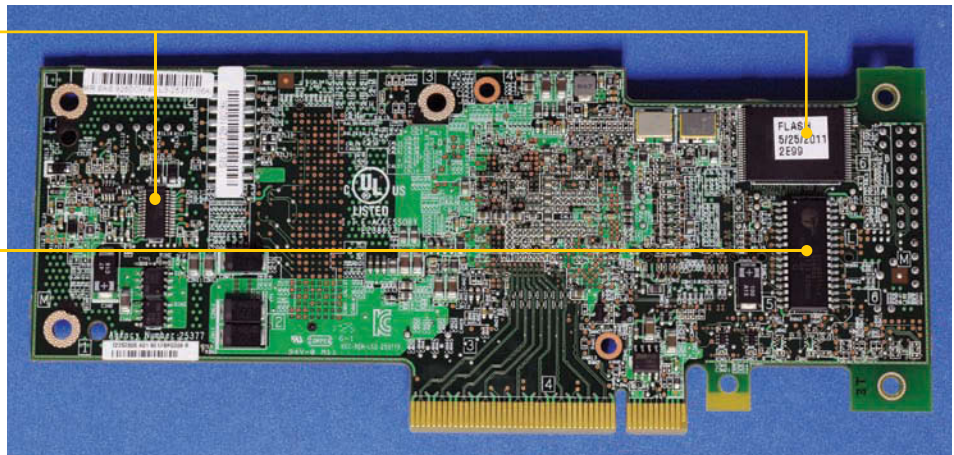The back of the main board features NOR flash from Intel, a Maxim buck controller, and a Cypress CY14B256LA nvSRAM.






## Now Enhanced & Interactive

EXPERT CONTENT | DESIGN CENTERS | TOOLS & LEARNING | COMMUNITY

You turn to us for the resources, ideas, & solutions you trust.  
Now get even more with the new **EDN.com**.
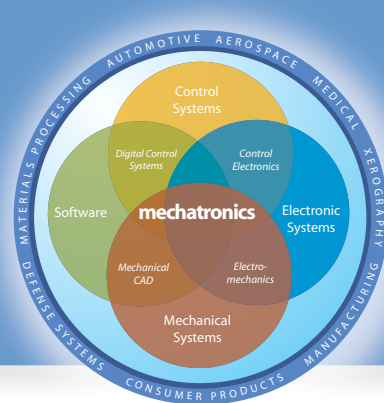
# MECHATRONICS IN DESIGN

FRESH IDEAS ON INTEGRATING MECHANICAL SYSTEMS, ELECTRONICS, CONTROL SYSTEMS, AND SOFTWARE IN DESIGN



## Fluid power: the hidden giant

Dynamic application of fluid power requires a systems approach.

By Kevin C Craig, PhD

**F**luid-power systems: almost as fast as a speeding bullet, definitely more powerful than a locomotive, and possibly able to leap tall buildings in a single bound. They should sport a Superman logo. This pervasive, hidden technology employs a simple principle that leads people to think that implementation of fluid power is just a select-assemble-and-run task. Nothing could be further from the truth.

At the end of the 19th century, in response to the need to more effectively transmit power from one point to another, hydraulic systems replaced traditional mechanical systems. Developers during the Industrial Revolution emphasized fluid power, but most applications were steady in nature and required only static considerations for design. At the beginning of the 20th century, hydraulic-control-system development experienced a major setback, and decades of stagnation followed, with the phenomenal growth of electrical power. The stagnation ended as World War II drove the need for power transmission requiring high effort and fast response, which only hydraulic systems could provide because of their superior power density over electrical devices. Over the next 40 years, industry was the steward of technology for the fluid-power world. A resurgence of interest in fluid-power-control systems is occurring at universities, and industry/university collaboration is growing.

Unfortunately, some people consider fluid power a specialist subject. Hydraulic-control systems are essential, however, in applications requiring large forces or torques, with a fast response and high accuracy. They have a better power-to-weight ratio than electrically actuated systems, which are limited by magnetic saturation, and they excel in environmentally difficult applications. In addition, the hydraulic medium is mechanically stiffer than the electromagnetic medium. Self-lubrication and inherent heat transfer are also advantages. Fluid-power applications are numerous. They include vehicle steering, braking, and suspension systems; industrial-mechanical manipulators and robots; and actuators for aircraft and marine vessels. They are all multidisciplinary systems and require a systems approach to design and implement. The required engineering background includes fluid mechanics, electromechanics, system dynamics, computer-control systems, and electronics—in other words, a mechatronics background.

Power conversions occur throughout a basic hydraulic-control system (Figure 1). A variable-speed-motor-driven pump pressurizes the hydraulic fluid. A relief valve and an accumulator (not shown) regulate and stabilize the pressure of the fluid. A servovalve, driven by an electric valve actuator, provides a controlled supply of fluid into the actuator, which is either a piston-cylinder device or a hydraulic motor, controlling both flow rate and pressure. Low-pressure fluid from the servovalve is filtered and returned to the reservoir. A feedback digital-control system completes the system.

Today, the competitive advantage of fluid power is greatest in mobile applications, such as mobile heavy equipment, human-assistance devices, mobile human-scale equipment, and hydraulic hybrid passenger vehicles. In these applications, fluid power can be a compact, efficient, and effective source of energy transmission. The opportunities are great for mechatronics engineers in this re-emerging field. **EDN**

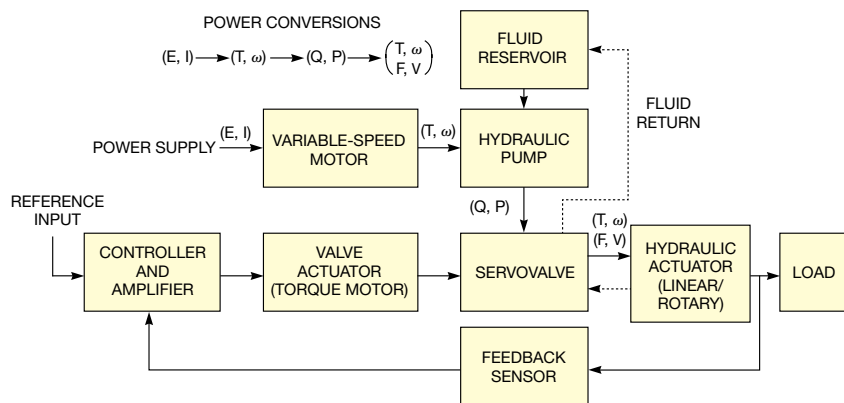


Figure 1 Power conversions occur throughout a basic hydraulic-control system.






**ams** 
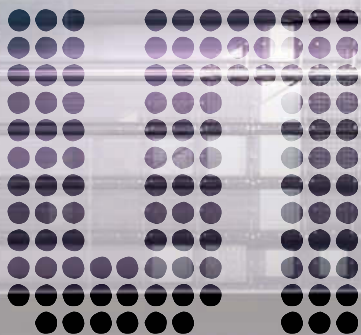
# analog makes sense.

austriamicrosystems and TAOS  
are moving forward as ams




**ams provides innovative  
analog solutions to  
the most challenging  
applications in sensors and  
sensor interfaces, power  
management and wireless.**



**Snap Dragon Only At MPD**  
**[www.batteryholders.com](http://www.batteryholders.com)**

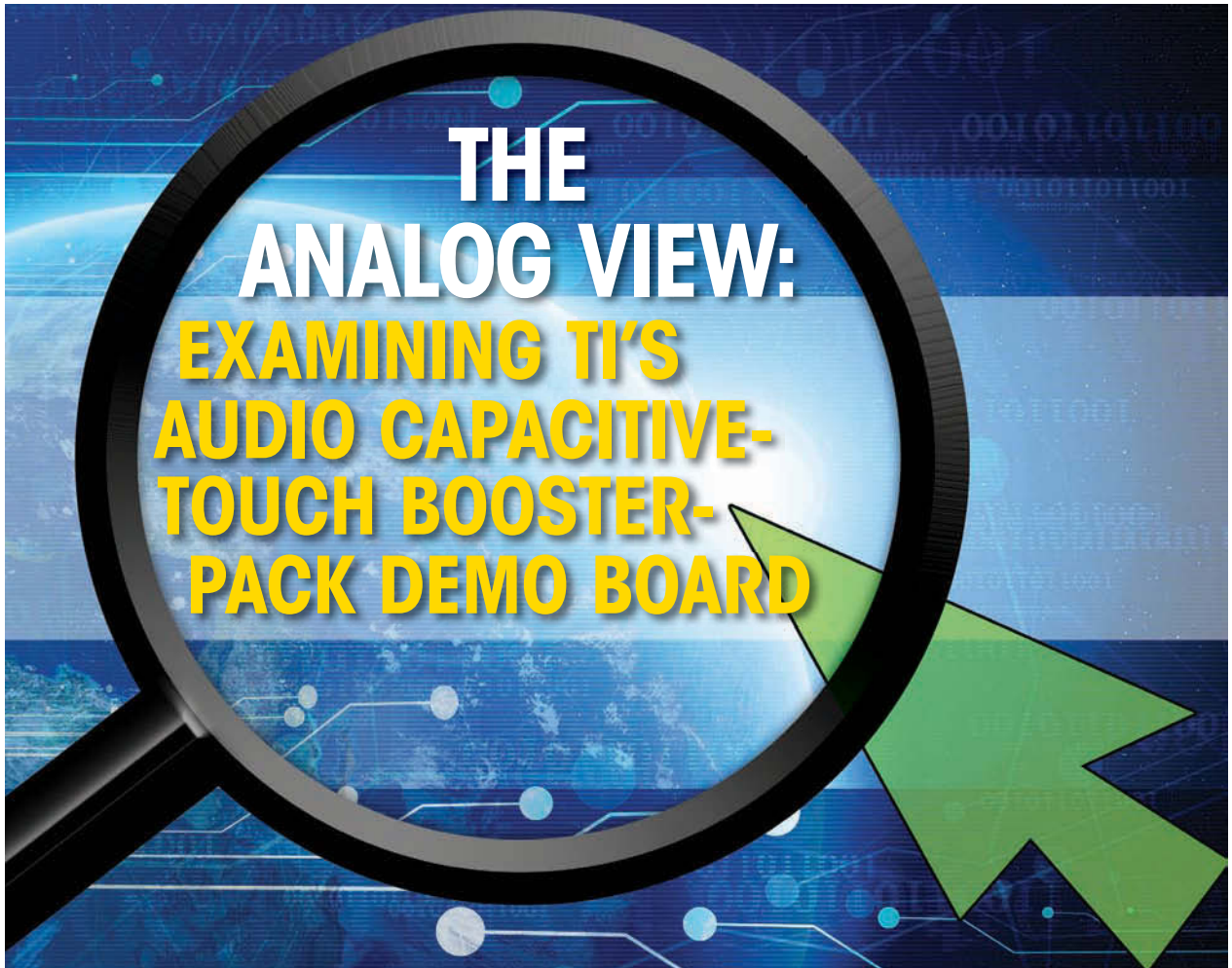**Patent pending    [sales@batteryholders.com](mailto:sales@batteryholders.com)    631-249-0001**



## A LOOK AT THE ANALOG ARCHITECTURE PROVIDES INSIGHT INTO THE DESIGN CHOICES TEXAS INSTRUMENTS MADE FOR ITS AUDIO CAPACITIVE-TOUCH BOOSTER-PACK DEMO BOARD.

BY STEVE TARANOVICH • SENIOR TECHNICAL EDITOR

Suppliers put a great deal of effort into making their demo boards show off the best performance possible for their products. They thoroughly test layouts, and designers implement many iterations to squeeze out the last microvolt of noise, the extra fraction of a decibel of dynamic range, or some other important performance parameter of the ICs or functions the manufacturer wants to highlight. Texas Instruments' audio capacitive-touch booster-pack demo board employs a DSP and a microcontroller (**Reference 1**). The microcontroller provides analog assistance to

simplify and enhance design, and the DSP provides higher-level assistance to what essentially becomes an MP3 player.

Designers need first to understand the capacitive-touch mechanism (**Figure 1**). A finger disrupts the electric field, which sees the finger as a conductive foreign object, thus changing the capacitance. A ground plane beneath the touchpad helps shield the structure from other electronics in the design, such as microcontrollers, DSPs, and clocks. The MSP430 microcontroller constantly monitors and tracks slowly changing environmental effects, such as temperature and humidity, which can affect operation.

# Benefits of the R&S®RTO Oscilloscope's Digital Trigger Application Note

**The trigger is a key element of an oscilloscope. It captures specific signal events for detailed analysis and provides a stable view on repeating waveforms.**

**Since its invention in the 1940s the oscilloscope trigger has experienced continuous enhancements. The fully digital trigger of the R&S®RTO digital oscilloscopes sets an innovation milestone that brings significant advantages for the oscilloscope user in terms of measurement accuracy, acquisition density and functionality.**

**This application note introduces the working principles of a conventional trigger system and explains the advantages of the real-time-capable digital trigger of the RTO oscilloscopes.**

## 1 Principle of a Conventional Trigger System

### 1.1 Relevance of a Trigger for an Oscilloscope

The trigger of an oscilloscope has basically two main applications:

#### 1. Ensuring a stable display

The invention of the trigger was a breakthrough for oscilloscopes as a debug tool for electrical and electronic design [1]. Triggering ensures a stable display of waveforms for continuous monitoring of repetitive signals.

#### 2. Display of specific signal characteristics

The trigger can react to dedicated events. This is useful for isolating and displaying specific signal characteristics such as logic levels that are not reached ("Runt"), signal disturbances caused by crosstalk (e.g. "Glitch"), slow edges ("Rise time") or invalid timing between channels ("Data2Clk").

The number of trigger events and the flexibility of the trigger setup have been continuously enhanced over the years.

The accuracy of a trigger system as well as its flexibility determines how well the measurement signal can be displayed and analyzed.

### 1.2 Implementation of a Conventional Trigger System

Today most oscilloscopes are digital, meaning that the measurement signal is sampled and stored as a continuous series of digital values. However, the trigger, which is responsible for the detection of a signal event, is still an analog circuit that processes the original measurement signal. Figure 1 provides a simplified block diagram of a digital oscilloscope.

The input amplifier is used to condition the signal under test to match its amplitude to the operation range of the A/D converter and the display of the oscilloscope, respectively. The conditioned signal from the amplifier output is distributed in parallel to the A/D converter and the trigger system. In one path, the A/D converter samples the measurement signal and the digitized sample values are written to the acquisition memory. In the other path, the trigger system compares the signal to valid trigger events (e.g. crossing of a trigger threshold with the "Edge" trigger).

When a valid trigger condition occurs, the recording of the A/D converter samples will be finalized, and the acquired waveform further processed and displayed. Figure 2 shows an example of an acquired and displayed waveform. The digitized sample points from the A/D conversion are marked on the signal with circles. For this example the trigger event "Edge" with positive slope is applied. The crossing of the trigger level by the measurement signal results in a valid trigger event.



### 1.3 Impairment of an Analog Trigger

For an accurate display of the signal on the oscilloscope grid, the timing of the trigger point needs to be determined precisely. If the trigger time evaluation is inaccurate the displayed waveform does not intersect the trigger point (cross point of trigger level and trigger position) in the diagram. An example is given in Figure 3.

An inaccurate trigger position can be caused by the following:

1. Inaccurate measurement of trigger edge  
In the trigger system the measurement signal is compared to a trigger threshold via a comparator. The timing of the edge at the output of the comparator needs to be measured very precisely. For this purpose a time-to-digital converter (TDC) is applied. Inaccuracy of the TDC results in an offset of an individual displayed waveform to the trigger point. The random component of TDC error causes this offset to change on each trigger event, which results in trigger jitter.

2. Systematic error sources in the two paths for the measurement signal

The measurement signal is processed via two different paths – the acquisition path with the A/D converter, and the trigger path (Figure 1). Both paths contain different linear and non-linear distortions that cause a systematic mismatch between the displayed signal and the determined trigger

point. In the worst case, the trigger might not react to valid trigger events though they are visible on the display, or the trigger reacts to trigger events that cannot really be captured and displayed by the acquisition path.

3. Noise sources in the two paths for the measurement signal

The two paths to the A/D converter and to the analog trigger system include amplifiers with different noise sources. This results in delays and amplitude variances that appear as trigger position offsets (trigger jitter) on the oscilloscope screen. The trigger jitter is displayed on the right-hand side of Figure 4 as the width and height of the superimposed signal traces. On the left-hand side of Figure 4 the trigger jitter appears as a random vertical and horizontal offset with respect to the ideal trigger point. In the following chapter, the implementation of a digitally implemented trigger system is introduced.

#### More information...

...online at  
[www.scope-of-the-art.com/ad/bb/edn](http://www.scope-of-the-art.com/ad/bb/edn)

There you will find further interesting application notes, brochures and films about the oscilloscopes from Rohde & Schwarz.

Just go online and immerse yourself in our scope world.

To measure the sensor's capacitance, the MSP430 counts the number of relaxation-oscillator cycles within a fixed gate period (Figure 2), comparing the fixed-timing domain of the reference and the variable-timing domain of the finger's capacitance. You can implement the relaxation oscillator with a comparator or, in the case of the MSP430, using a pin-oscillator feature, in which the frequency of the oscillation is a function of the resistance and the capacitance of the circuit. The capacitance is the intended variable and increases with a touch. In the time domain, the rise and fall times increase. Conversely, in the frequency domain, the frequency decreases. With an increase in capacitance, the number of relaxation-oscillator cycles decreases within the fixed gate time.

### AT A GLANCE

- ▶ TI's audio capacitive-touch booster-pack demo board employs a DSP and a microcontroller.
- ▶ The high integration in the microcontroller allows the luxury of a relatively straightforward capacitive sensor input.
- ▶ The microcontroller provides analog assistance to simplify and enhance the design; the DSP provides the higher-level assistance to what essentially becomes an MP3 player.

The relaxation oscillator feeds into a Schmitt-trigger circuit that generates a square packet and then counts the pulses. Texas Instruments offers a free

capacitive-touch library, which enables buttons, sliders, wheels, and proximity sensors on all MSP430 microcontrollers, eliminating the need for developers to create complex touch-sensing algorithms (Reference 2).

Figure 3 shows a bus-connection diagram of all elements in the audio capacitive-touch booster pack.

Both USB ports provide 5V, but the booster pack requires 3.6V to source the 1.3, 1.8, and 3.3V power rails; the 13V for OLED backlight; and the 3.6V for the MSP430. The ACTBP USB connector feeds a 5 to 3.6V dc/dc converter to provide 3.6V from the 5V USB port. The device uses the TPS62260 synchronous-step-down converter, which touts efficiency greater than 90% with a 15- $\mu$ A quiescent current. It provides as much as 600-mA output current from one lithium-ion cell. The device's high switching frequency allows the use of small inductors and capacitors to achieve a small product that comes in a TSOT-23-5 or a 2x2-mm TXFN package (Figure 4a).

The MSP430 launchpad connector provides power to the launchpad and the booster pack. The launchpad provides 3.6V for the main power-supply voltage from the 5V USB port. The 1A, 3.3V TPS79633 low-dropout, low-power, fixed linear regulator has a power-supply rejection ratio of 49 dB at 100 kHz and noise of 40  $\mu$ V rms. It comes in an SOT-223-6 package. The TPS79633 powers most analog ICs,

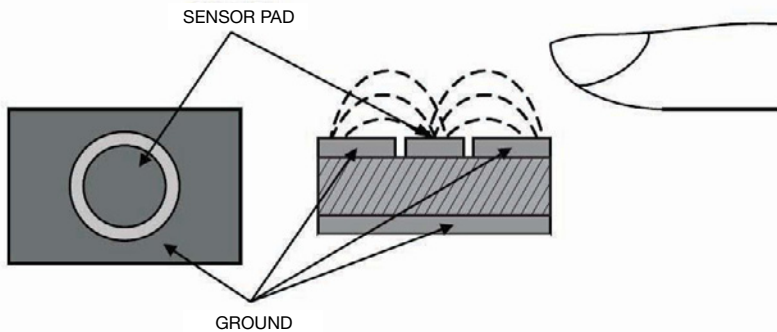


Figure 1 An opened capacitor structure acts as a single-touch sensitive capacitor sensor in capacitive-touch systems.


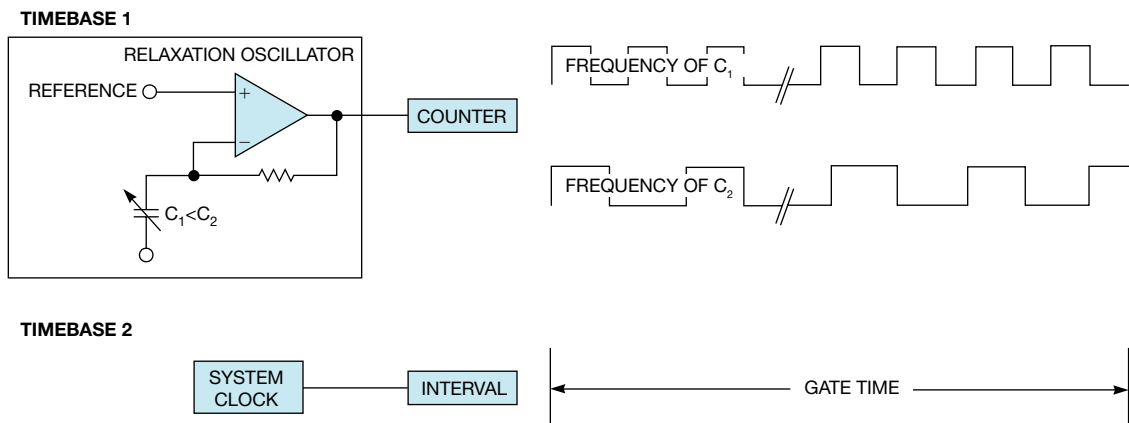


Figure 2 This design uses relaxation oscillation to sense capacitance.  $C_2$  represents the large capacitance of a finger close to the sensor.

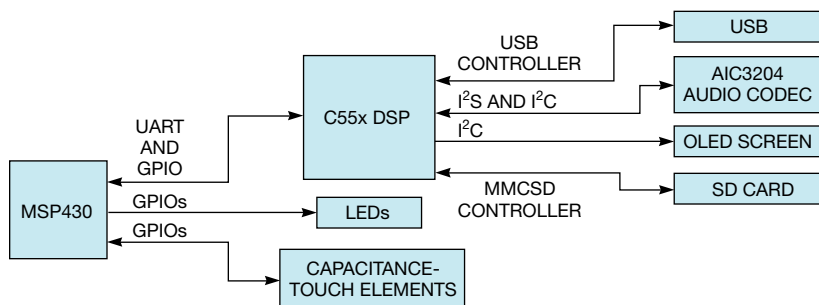

**Figure 3** The audio capacitive-touch booster pack bus-connection block diagram shows a connection to an MSP430 microcontroller launchpad board. All pertinent bus structures in the design are shown.

such as the AIC3204 codec, and the TS3A225E audio switch (**Figure 4b** and **Reference 3**).

Other available power supplies for the MSP430 include the TPS79501 (**Figure 4c** and **Reference 4**) and the TPS77801 (**Figure 4d**). The TPS79501 500-mA low-dropout, low-power linear voltage regulator features a power-supply rejection ratio of 50 dB at 10 kHz in a small-outline SOT223-6 package. This device is stable with a small 1- $\mu$ F ceramic capacitor on the output. The low noise and fast response time make the TPS79501 a good choice for the 1.8V supply.

The TPS77801 low-dropout regulator, in an 8-pin SOIC package, is designed to have a fast transient response and be stable with a 10- $\mu$ F, low-equivalent-series-resistance capacitor. The device converts the 3.3 to 1.3V supply for the DSP (running at up to 100 MHz) digital core voltage and other core supplies in the DSP. The quiescent current is independent of output loading, making the TPS77801 a good choice for a low-power system.

### AUDIO CHOICES

The booster pack has a headset jack for stereo-headset output and headset-microphone input. To support the various types of headsets, the TS3A225E autonomous audio switch with headset-type detection connects the headset jack and the stereo audio codec.


The designers of the demo board chose this codec because of its low power and because it allowed them to reuse software from other demo boards. Software reuse is a great time saver. The

layout was also used on some other reference designs, so the hardware reuse saved time and allowed for the board to be introduced to designers as quickly as possible. This flexible, low-power, low-voltage stereo audio codec has programmable inputs and outputs, a low-power analog-bypass mode, power-tune features, fixed predefined and programmable microphone bias, parameterizable

signal-processing blocks, an integrated programmable phase-locked loop, integrated low-dropout regulators, and flexible digital interfaces. Its high level of integration also makes this codec a space saver (**Figure 5**).

The TS3A225E autonomous audio switch with headset-type detection detects the presence of an analog microphone and switches a system's analog-microphone pin between connectors in an audio stereo jack (**Figure 6**). Some connector manufacturers allow you to swap the microphone connection in a stereo connector with the ground connection. When the IC detects a certain configuration, the device automatically connects the microphone line to the appropriate pin. The device also reports the presence of an analog microphone on an audio stereo jack and takes up little space on the PCB.


The demo board also includes four analog I<sup>2</sup>C devices, which the C5535 DSP controls—an audio codec, an OLED (organic light-emitting-diode) display, the power supply's core power monitor, and the headset detector and



# EDN

VOICE OF THE ENGINEER

# Customize Your Reprints!

Reprints can be used in:

- Trade Show Handouts
- Media Kits
- Point-of-Purchase Displays
- Direct Mail Campaigns

## REPRINTS • EPRINTS • POSTERS • PLAQUES

**Create** a powerful statement for your product, service or company through professionally designed marketing materials utilizing editorial content from *EDN*.

**Contact Wright's Media** to discuss how we can customize these materials to enhance your current marketing campaign.

U.S. copyright laws protect against unauthorized use of published content.

**Call today**  
**877-652-5295**  
*and allow our reprint coordinator to assist you with some proven marketing ideas.*

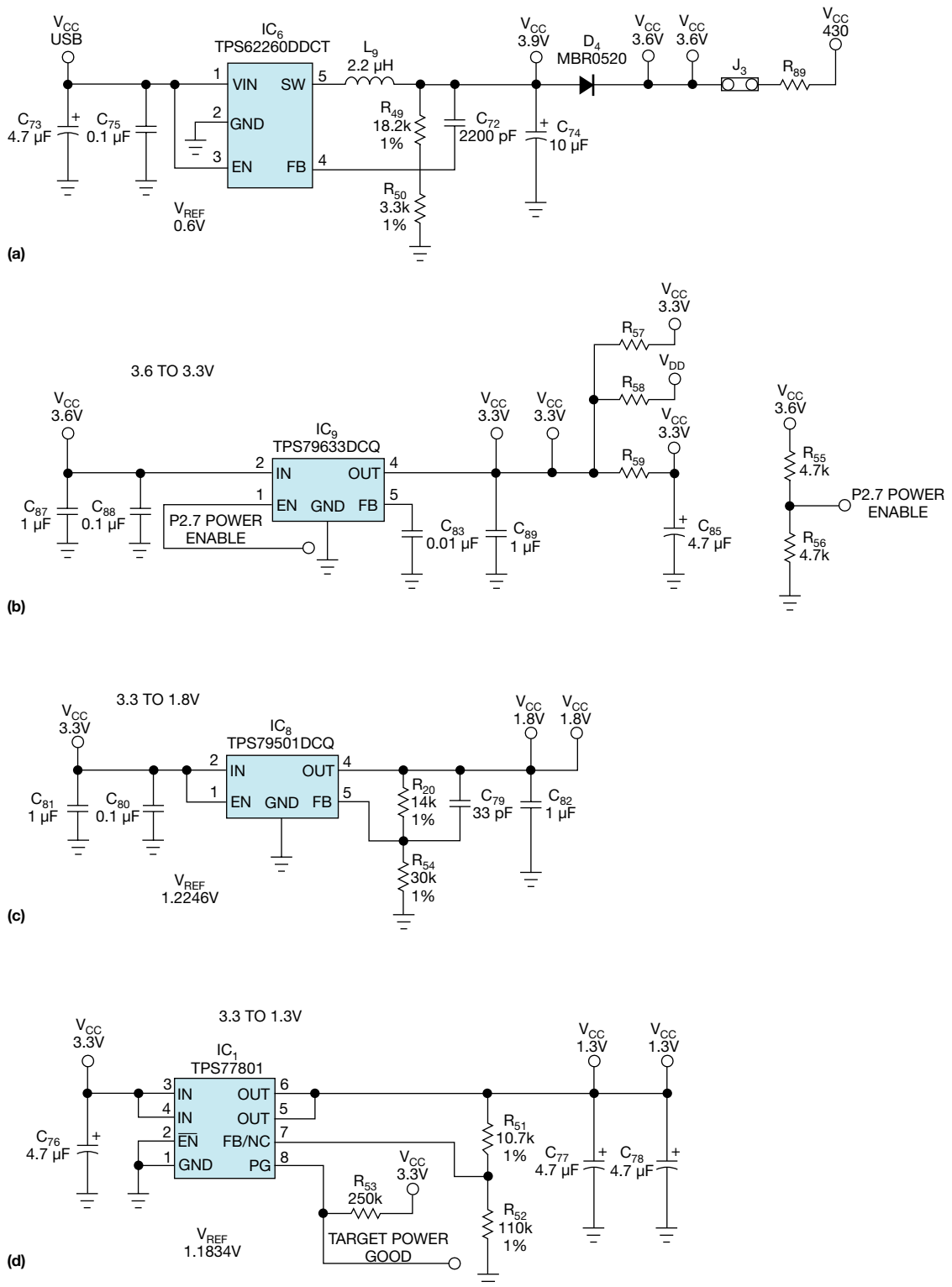


Figure 4 The TPS62260 provides USB input to 3.6V (a). The TPS79633 powers most analog ICs, such as the AIC3204 codec, and the TS3A225E audio switch (b). The TPS79501 provides 3.3 to 1.8V (c). The TPS77801 provides 3.3 to 1.3V (d).



# DesignNews



## CONTINUING EDUCATION CENTER

# Get current, without the hassle.

With Digi-Key's Continuing Education Center, catch up to 180 days of free, interactive courses engineered by Design News, starting January 2012. Build your engineering know how. Take one or all. It's your choice.

Tracks include: Microcontrollers Basic, Microcontrollers Advanced, MEMS Sensor Technology, Lighting, Embedded Internet and Cloud, Wireless, and Power.

**REGISTER AT**  
**[DesignNews.com/dkcec](http://DesignNews.com/dkcec)**

**FOLLOW US**


@DigiKeyCEC




Digi-Key Continuing Education Center



**UBM**  
Electronics

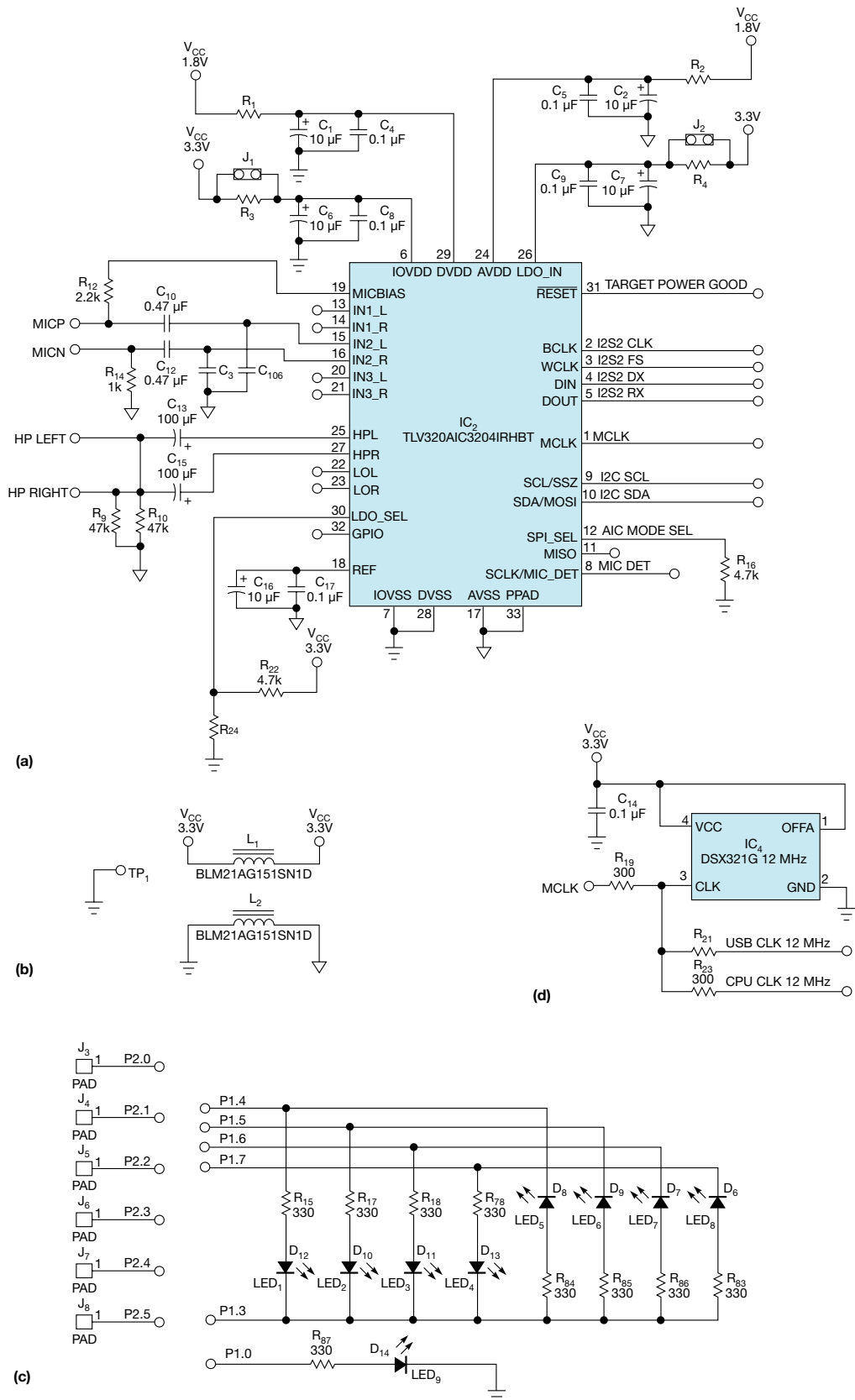

**Figure 5** To support the various types of headsets, the TS3A225E autonomous audio switch with headset-type detection connects the headset jack and the stereo audio codec (a), the BLM21AG151SN1D inductors (b), the capacitive-touch sensor (c), and the 12-MHz DSX321G clock (d).

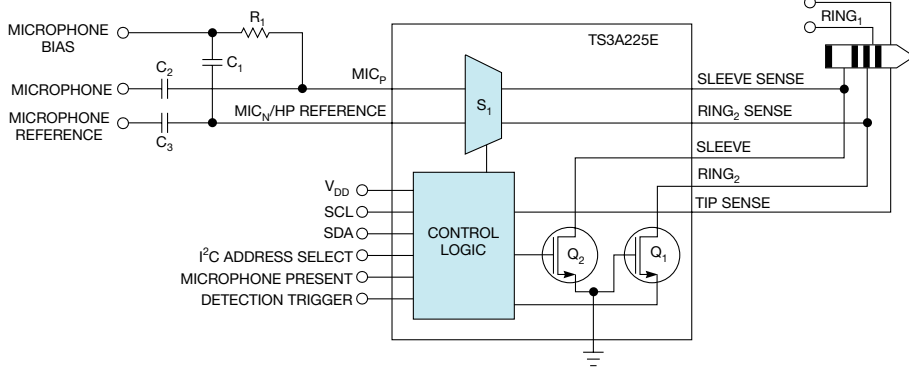

**Figure 6** The TS3A225E autonomous audio switch with headset-type detection detects the presence of an analog microphone and switches a system's analog-microphone pin between connectors in an audio stereo jack.

switch. The MSP430 sends UART commands to the DSP to configure the I<sup>2</sup>C devices—writing characters to the OLED display, for example. The INA219 provides the DSP's core power usage to maintain efficient power management.

Using the INA219, you can characterize the CMOS DSP's power consumption on the application board when application code is running. You can then tailor the application code, code structure, and operating frequency for minimum power consumption. The zero-drift, bidirectional INA219 current/power monitor reports current, voltage, and power through the I<sup>2</sup>C bus and comes in an SOT-23-8 package.**EDN**




## REFERENCES

- 1 Maxfield, Clive, "TI announces audio capacitive touch BoosterPack for ultra-low-power MSP430 MCUs," *EE Times*, March 27, 2012, <http://bit.ly/Jp1s3w>.
- 2 "Capacitive Touch Library, Programmer's Guide SLAA490," Texas Instruments, April 2011, <http://bit.ly/KTXKiw>.
- 3 "TPS79633 Ultralow-Noise, High-PSRR, Fast, RF, 1A Low-Dropout Linear Regulators," Texas Instruments, September 2002, <http://bit.ly/Kq8mtQ>.
- 4 "TPS79501 Ultralow-Noise, High-PSRR, Fast, RF, 500-mA Low-Dropout Linear Regulators," Texas Instruments, August 2010, <http://bit.ly/MVVWM7>.

You can reach Senior Technical Editor **Steve Taranovich** at 1-632-413-1834 and [steve.taranovich@ubm.com](mailto:steve.taranovich@ubm.com).



# Be As Small As You Can Be

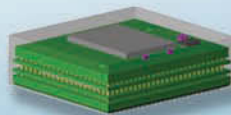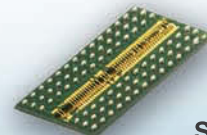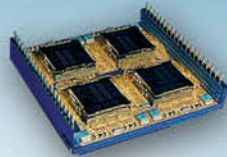

Optical-Die Packaging  
System in Package  
Multi-Chip Module  
3D Packaging  
Flip Chip

## 3D & Advanced Packaging Cost Effective at Any Quantity

You don't need cell-phone production volumes to miniaturize & cost reduce your next design using the latest packaging technologies.

## Quick-Turn, On-Shore Capabilities

Reduce your concept-to-production cycle time with our multi-discipline design teams and vertically-integrated manufacturing.

Stacked Die  
Chip on Board  
Hybrid Assembly  
Package in Package  
Package on Package

**Interconnect Systems, Inc.**


Designed and Manufactured in the U.S.A.  
[www.isipkg.com](http://www.isipkg.com) 805.482.2870 [info@isipkg.com](mailto:info@isipkg.com)

# WIRELESS-SENSOR NETWORKS' OPERATING POWER ARRIVES VIA THIN AIR

BY DAN STRASSBERG • CONTRIBUTING TECHNICAL EDITOR

**F**or several good reasons, wireless-sensor networks and the technologies that underlie them have become important topics to many EEs who work in system design. Although engineers who design systems for process or manufacturing control are familiar with distributed data acquisition and control, the architecture of systems with distributed intelligence—a common characteristic of these networks—is another topic that now appears at center stage. Wireless data communication is yet another key topic, but so are self-organizing system design, network topologies, RF design, ruggedized system design, micropower design, energy harvesting, wireless delivery of power, energy storage, and data security in wireless systems. Moreover, although wireless-sensor networks have been around in significant numbers for perhaps a decade, their structure continues to evolve, causing almost daily growth in the number and diversity of technologies with which their designers must become adept.

IMAGE SHUTTERSTOCK

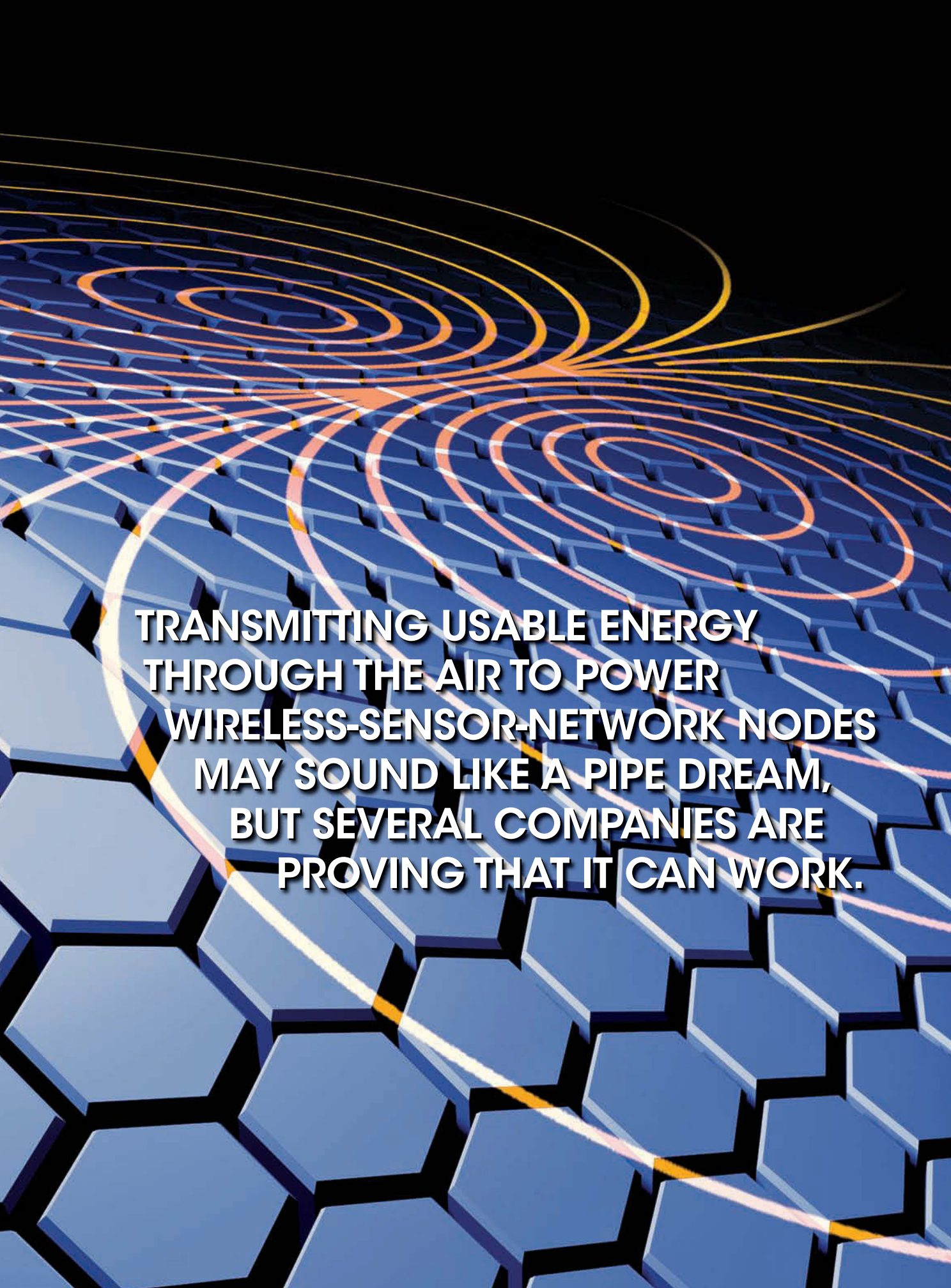

**TRANSMITTING USABLE ENERGY  
THROUGH THE AIR TO POWER  
WIRELESS-SENSOR-NETWORK NODES  
MAY SOUND LIKE A PIPE DREAM,  
BUT SEVERAL COMPANIES ARE  
PROVING THAT IT CAN WORK.**

Although these networks' architects can choose among a plethora of wireless-networking-protocol standards, in which low power consumption is a key requirement, they appear to favor ZigBee, an extension of the IEEE 802.15.4 standard. Compared with alternative protocols, such as Wi-Fi, ZigBee, with a fastest data rate of only 250 kbps, is no speed demon. However, the speed seems to suffice for many industrial applications in which a priority is low power.

Wireless-sensor networks have long relied on batteries to power sensors deployed throughout large process and manufacturing facilities. At first, designers regarded the deployment of wireless sensors in relatively inaccessible locations in these facilities as a great boon. Such arrangements eliminated the need to route signal wiring through difficult-to-reach areas and often presented hazards to not only the installers but also the signal cables.

It then became obvious that the necessary labor for replacing sensor batteries could become a major ongoing cost in keeping these networks on the air. If a network incorporates, for example, 365 sensors—one for each day of the year, each with a signal conditioner that uses one battery—and the average battery life is one year, the plant manager must budget for the time to replace the battery in one sensor per day, every day

## AT A GLANCE

Traditionally, energy harvesting in wireless-sensor-network nodes captures packets of energy from environmental sources. These energy packets accumulate in a reservoir (a battery or a capacitor) until it contains enough energy for the node to acquire and send data to a system's central database.

It is now feasible to send energy continuously to the nodes as RF. In such architectures, the system's wireless-communication protocol limits the speed of data interchange between the remote nodes and the central database.

The popular ZigBee protocol handles data transfer at speeds as high as 250 kbps, sacrificing speed to gain energy efficiency.

Ultracapacitors (also called EDLCs) offer many advantages; a key benefit is their nearly infinite charge/discharge cycle life. Their successful application requires familiarity with their unusual characteristics, however.


edly, perhaps because a battery required replacement earlier than scheduled or a wire broke after it flexed one time too many.

Such concerns gave rise to the idea of energy harvesting—powering wireless sensors by converting, storing, and using small amounts of energy from such ambient sources as light, heat, and vibration. This promising new technology has drawn great interest, especially among academics, and is now starting to produce commercially worthwhile results.
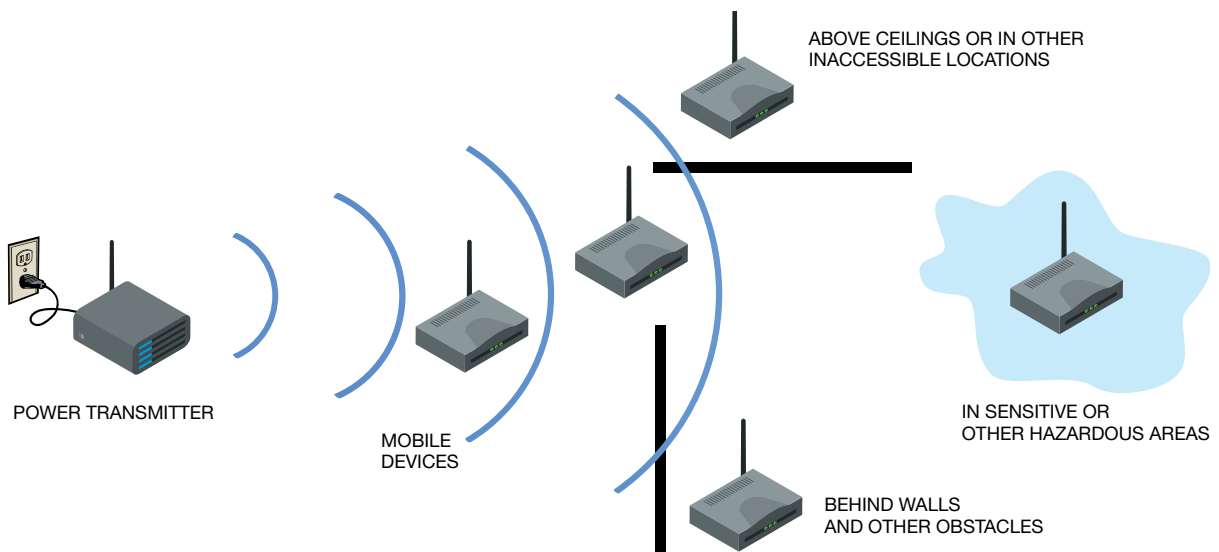
## THE REAL OBJECTIVE

Somewhere in this scenario, some system designers, who perhaps had become fascinated with the “green” revolution, may have lost sight of the real objective. It's nice to minimize the amount of energy supplied to the network to power it, but, in most networks, that power is already low. A more important objective is often to minimize maintenance and its associated costs. A good way to reduce maintenance is to eliminate both remote power wiring—with its susceptibility to damage in rugged environments—and batteries—with their limited cycle life (the number of charge/discharge cycles they can typically withstand before their energy-storage capacity significantly diminishes). If the objective is reducing maintenance, further reducing network

of the year, including weekends and holidays. Also, it is nearly impossible to budget for the events that can occur when a system element fails unexpect-



A wireless power-distribution system can provide coverage for an entire facility in a manner similar to that of a lighting system or a wireless-communication system (courtesy Powercast).



# Give your customers faster test results and see how quickly they value your designs.


## Faster product designs, faster test results from the leading test and measurement supplier.

ADI offers the broadest portfolio of ICs for any test and measurement application. Advantages such as higher sampling rates and shorter settling times enable faster test results—while integrated functions and tested reference circuits shorten your design time. See why leading OEMs trust ADI to meet their performance and supply chain needs. Explore products and design resources at [analog.com/FasterTest](http://analog.com/FasterTest).

### Recent Test and Measurement IC Innovations

- ADF41020: 18 GHz microwave PLL**  
 Industry's highest frequency PLL eliminates frequency doubling; includes PFD, charge pump, and dividers.
- ADA4940-1/ADA4940-2: ADC drivers**  
 Ultralow power consumption, low distortion, low noise, fully differential amps; ideal for driving 16-bit ADCs.
- ADuM1280: Dual channel digital isolator**  
 Optocoupler alternative provides increased performance, higher reliability, lower power in a smaller package.
- AD5780: System-ready 18-bit,  $\pm 1$  LSB INL, DAC**  
 Ultralow noise, integrated precision reference amp; speeds designs, reduces board space by 60%.
- ADL5565: Differential RF/IF amplifier**  
 Industry-best distortion levels; perfect for driving high performance 12- to 16-bit ADCs.
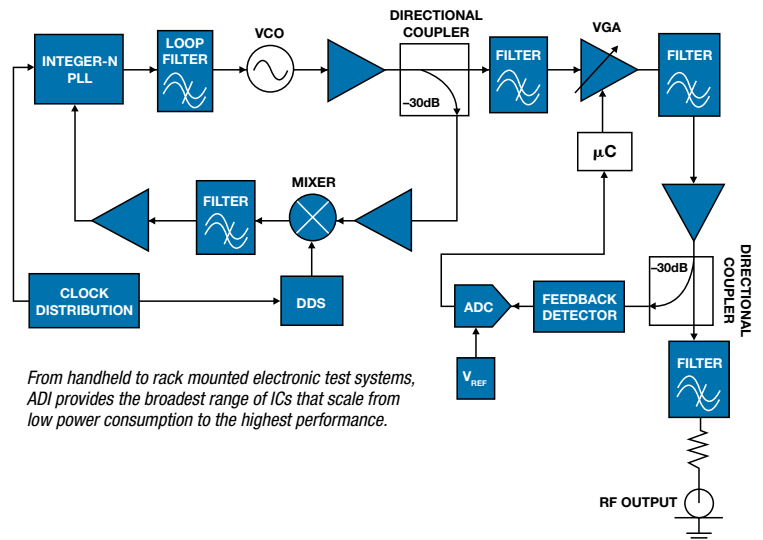
### Frequency Translation Loop Signal Chain



From handheld to rack mounted electronic test systems, ADI provides the broadest range of ICs that scale from low power consumption to the highest performance.



**Circuits from the Lab™**  
 Reference Circuits  
 Engineered. Tested.  
 Ready to Integrate.

**ENGINEER ZONE**  
 The online support community for engineers.

power consumption can begin to appear like an unattainable goal, whereas the idea of continually supplying energy to the sensors—wirelessly through RF fields—may start to sound surprisingly intriguing.

At the core of most energy-harvesting schemes is the idea that, much of the time, available ambient-energy sources can provide packets, or boluses, of energy only at unpredictable intervals and can't continuously energize typical wireless

sensors and their associated signal conditioners, ADCs, and transmitter/receivers. Therefore, energy-harvesting approaches usually accumulate these energy packets when they can and query the sensors for information on a schedule that does not exceed the average power the ambient-energy sources can supply.

Often, EDLCs (electrochemical dual-layer capacitors), often called supercapacitors or ultracapacitors, form the reser-

## EDLCs' HIGH C: PERFECT PITCH FOR APPS THAT NEED LOW MAINTENANCE, LONG LIFE

Marketers describe ultracapacitors, EDLCs (electrochemical dual-layer capacitors), as true capacitors in an effort to distinguish them from rechargeable batteries. You can buy EDLCs in several surface-mountable package styles, as well as in cylindrical and rectangular packages with axial or radial leads, so it's easy to think that EDLCs' performance must resemble that of true capacitors (Figure A). However, many characteristics distinguish EDLCs from true capacitors—even from electrolytic capacitors, which, before the advent of EDLCs, provided the highest capacitance of any form of capacitor.

Controversy even surrounds the meaning of the letter E in EDLC. Some say that the E stands for electrochemical, pointing to EDLCs' use of a liquid electrolyte. Others say that the E stands for electric, pointing out that, even though the electrolyte becomes polarized when you apply a dc voltage to an EDLC's terminals, energy storage within the device—unlike that in an electrolytic capacitor—involves no chemical reactions.

Today, EDLCs with capacitance of tens of farads commonly appear in many applications. Devices with capacitance of more than 100F already exist, and EDLCs' maximum capacitance is likely to continue increasing as engineers devise new applications that require larger energy reservoirs, such as consumer, automotive, and "green" systems.

EDLCs may appear outwardly simple. Most have only

two terminals, which may not even be polarized the way electrolytic capacitors' terminals are. However, you cannot successfully apply them without first familiarizing yourself with their many unusual characteristics. Even if you believe that you can skip the self-education step, you'd be wise to allot some time in your project schedule for a learning experience.

From freshman physics, you probably remember the formula for a capacitor's capacitance:  $C = \epsilon A/d$ , where  $C$  is the capacitance,  $\epsilon$  is the dielectric constant of the insulating material between the capacitor's plates,  $A$  is the area of the plates, and  $d$  is the distance between them. EDLCs achieve their high capacitance values by reducing  $d$  by as many as three orders of magnitude and maximizing  $A$  through the use of rough-surfaced electrodes. The device manufacturer's challenge is to reliably achieve stable, high values of capacitance plus stable, low ESR (equivalent series resistance) to deliver high stability in other parameters and to produce parts in large unit volumes under tight cost constraints.

An unexpected phenomenon in EDLCs is a result of the fact that actions within the device do not take place instantaneously. For example, if you impress an ac voltage across its terminals and measure a device's capacitance, you may discover that the capacitance depends on the ac voltage's frequency. A 20F device operating at, say, 5 Hz is likely to exhibit a capacitance of less than 10% of that value at 1 kHz. Suppose you want to use the capacitive reactance,  $X_C$ , to limit the ac current in a simple circuit to which you want to apply sinusoidal ac excitation. As you increase the excitation frequency, the current decreases because capacitive reactance is inversely proportional to capacitance. This effect may require you to redesign the circuit or choose a higher-value capacitor. You would also likely find that, over time at temperatures above the rated range, the capacitance decreases and the ESR increases.

Unlike a rechargeable battery, which has a typical cycle life of hundreds of charge/discharge cycles—after which its ability to store a charge drops significantly—an EDLC may suffer no permanent catastrophic damage after hundreds of thousands or even millions of charge/discharge cycles. Nevertheless, its capacitance



Figure A AVX supplies EDLCs in a variety of cases, including these 28×17-mm units. The case thickness depends on the energy a device can store. You can calculate the stored energy using the formula  $W = 0.5 \times C \times V^2$ , where  $W$  is the stored energy in joules,  $C$  is the capacitance in farads, and  $V$  is the working voltage in volts. Clockwise from left, the values are 0.429, 1.584, and 0.756J.



voir in which the harvested energy accumulates until the system calls for information from the sensor (see sidebar “EDLCs’ high C: perfect pitch for apps that need low maintenance, long life”). However, this approach may not always meet system needs. For example, emergencies can arise in which unforeseen conditions necessitate acquiring sensor data to make quick decisions about and enable immediate response to situations that endanger lives or property. In such cases, accumulated

after, say, 100,000 cycles may be only 90%, and its ESR may be as much as 125% of what it was after the first cycle. Moreover, these changes are likely to increase if you operate the device at elevated ambient temperatures beyond its ratings.

EDLCs have a generally well-deserved reputation for high leakage, or self-discharge current. In many cases, however, you can find ways around the shortcoming. For example, whenever the primary power source—usually, the ac line—is operating normally, uninterruptible power supplies that use EDLCs commonly keep the devices in a trickle-charge mode. This mode provides just enough current to satisfy the leakage requirement.

EDLCs can be expensive components, and most batteries store more energy than do EDLCs of the same size. Why, then, would you want to use EDLCs—especially in a wireless-sensor network? A key answer lies in their virtually unlimited cycle life. When you use them alone or in combination with primary—that is, nonrechargeable—or rechargeable batteries, EDLCs can eliminate or at least greatly reduce the need for maintenance of somewhat-inaccessible network nodes. Such maintenance represents a major operating cost. EDLCs are also an important part of those wireless-sensor networks that accept the penalty of higher node power to achieve faster response to emergency conditions in the system or the equipment they monitor.

With the aid of EDLCs, you can substantially increase the cycle life of rechargeable batteries. If you parallel an EDLC that guarantees low ESR with a battery that periodically delivers high-current pulses—a common operating condition in energy-harvesting applications—the battery’s cycle life is likely to increase by a factor of 4-to-1. Thanks to their low ESR, EDLCs deliver most of the pulse current, thereby limiting the battery’s contribution and limiting thermal cycling due to internal heating of the battery.

Typically, you can purchase prism-shaped EDLCs with low-profile designs and voltage ratings of 4.5 to 15V for approximately \$4.50 to \$7.50 each. At volumes of many millions of pieces, the unit prices are correspondingly lower.



National Instruments offers a comprehensive line of hardware products for wireless-sensor networks. The line includes the small, rugged, real-time NI9792 embedded controller (left), with prices starting at \$1647; the 16-bit, four-channel WSN-3202 high-level analog-input node (center), with prices starting at \$399; and the 24-bit, four-channel WSN-3212 thermocouple-input node (right), with prices starting at \$499. The WSN-3202 and WSN-3212 each include four digital I/O channels. The WSN-3202 also includes a 12V, 20-mA dc source, which can supply sensor power.

energy in the reservoir may prove inadequate for meeting a sensor’s peak-power demands. This situation can occur at any time but is most likely to occur when a sensor returns to the air after technicians have removed it from service for calibration, maintenance, or system reconfiguration.

## TRANSMITTING HARVESTABLE RF

Powercast’s approaches differ somewhat from more familiar energy-harvesting approaches. Instead of harvesting ambient energy, Powercast can wirelessly provide energy to the sensors in the form of RF at frequencies in the ISM (industrial/scientific/medical) bands, such as 915 MHz and 2.4 GHz. In the United States, you don’t need a broadcast license to use these bands at power levels that the Federal Communications Commission prescribes. The frequencies and power levels are low enough that the FCC classifies the energy as nonionizing radiation. This classification means that, employing the best information available to them, the US Environmental Protection Agency and the FCC have declared that the signals do not constitute a hazard to human health. As with any health-related information in the 21st century, however, plenty of material on the Internet disputes the EPA and FCC claims.

Among Powercast’s alternative approaches is one that harvests energy from the signals of radio- and television-broadcast stations and cellular base stations. Unless your system is near the transmitting antenna of such a station, the RF signals may be too weak to avoid the need to use an energy reservoir and periodically query the sensors for updated data. Further, although most radio and TV stations seldom go off the air, you can’t assume that a neighboring broadcast transmitter will always be operating or that a neighboring cellular base




Working with IC-supplier Microchip Technologies, Powercast has produced several evaluation/development kits for its wireless RF energy-harvesting approach, including the P2110-Eval-01 kit. The kit has (top row from left) a 915-MHz, 3W power/data transmitter; two 1-dBi omnidirectional antennas; two 6-dBi directional antennas; a Microchip PICtail/PICtail-Plus daughtercard; and a Microchip PICkit-3 programmer/debugger. It also includes two Powerharvester-receiver evaluation boards (middle row); two wireless-sensor boards (bottom row, left); and a Microchip 16-bit development board (bottom row, right).

station will be handling a message volume sufficient to fulfill your system's energy needs.

If the ambient-RF power is inadequate, however, you can use any 1-MHz to 6-GHz transmitter that produces a sufficiently powerful signal to create the necessary RF field. A properly tuned Powercast Powerharvester receiver can then capture the signal and derive dc power from it at a voltage your system can use. Using a 3W ISM-band transmitter and simple antennas, the RF-power transmissions' range is 40 to 45 feet.

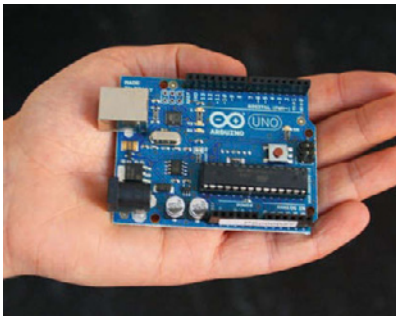Powercast recently announced an RF-based chip set, which is available through its global-distributor network. In concert with the company's licensable reference design for embedded



Design engineers use the Arduino open-source electronics-prototyping platform for quick trials of the practicality of ideas. The family includes several wireless-modem cards, such as this one, featuring a user-friendly interface in modifiable onboard firmware.

low-power, wireless-charging, and wireless-power applications, the chip set simplifies and reduces the cost of embedding the manufacturer's core RF energy-harvesting technology in such rechargeable-battery-based and non-battery devices as wireless-sensor-network nodes, enabling them to perpetually receive their operating power from RF energy. Powercast estimates that the reference design's bill-of-material cost, including the chip set, will be less than \$2 per unit (large volumes).

### MOVING ENERGY

WiTricity has 10 US patents on its technology and has filed approximately 100 additional applications. The technology differs substantially from Powercast's but is nevertheless RF-based, albeit at 140 kHz, 6.8 MHz, and other frequencies that are lower than the ISM-band frequencies that Powercast uses. WiTricity isn't now actively pursuing the wireless-sensor-network market; it believes it has much bigger fish to fry in consumer and automotive applications. Still, these networks should be able to make good use of the company's technology, which employs a little-known phenomenon: the ability to build efficient air-core transformers even though appreciable distances separate the primary and secondary coils—in WiTricity's case this distance is as much as 8 feet.

To achieve good efficiency at significant distances, you must excite the primary winding at its resonant frequency—usually in the RF range

and determined by the winding's leakage inductance and distributed capacitance. Moreover, the coils' self-resonance must exhibit high Q (quality factor), a measure of the ratio of peak energy stored to energy dissipated per cycle, and you must closely match the windings' resonant frequencies.

At a distance of 8 feet between the primary and the secondary, the efficiency of power transfer is almost 40%, according to the company. Unlike higher-frequency wireless-energy-transfer schemes, which carry energy in both electric and magnetic fields, WiTricity's energy transfer depends almost entirely on the magnetic field. The technology achieves best results if the excitation signal is sinusoidal, but the system suffers only a slight reduction in efficiency if the excitation waveform is square or trapezoidal.

The bugaboo, however, is shorted turns. Suppose that the transformer's primary and secondary coils center one



With the Solarcraft solar-energy harvester, you can deploy multiple solar-powered National Instruments wireless-measurement nodes to form a wireless-mesh network that communicates measurement data back to a network gateway for processing and analysis. Prices for the solar-energy harvester begin at \$604.



The Perpetuum vibration-energy harvester can power wireless-sensor networks built from National Instruments' wireless-sensor-network components. NI refers customers who are interested in vibration-energy harvesting directly to Perpetuum for technical assistance and for application-specific energy-harvesting subsystems.

above the other in parallel horizontal planes. When you apply an excitation voltage to the primary coil, a toroidal, or donut-shaped, RF-magnetic field with a vertical axis surrounds the two coils. If you mount the coils on metal plates, you must slit each plate along a coil radius so that no low-resistance current path—that is, no shorted turn—surrounds the toroidal field's axis. If you were to create such a path, a large current would circulate in it and would counteract the field from the coils, thereby reducing nearly to zero the efficiency of the coil-to-coil power transfer. The circulating current could also cause dangerous heating of the metal plates.

A similar shorted-turn problem potentially exists with a more common power-transfer approach: ac-line-frequency inductive coupling, such as is used to charge electric-toothbrush batteries. In that case, however, the primary and secondary coils are in close proximity, and the coil supports are made of nonconductive plastic. Unlike the metal plates in the earlier example, there are no legitimate concerns about their structural integrity. **EDN**

#### ACKNOWLEDGMENT

*I much appreciate the assistance of industry sources who helped me to research this article. In particular, I wish to thank Harry Ostaffe, vice president of marketing and sales at Powercast Corp, and Bharat Rawal, manager of BestCap technology at AVX Corp.*

#### REFERENCES

- 1 Akyildiz, IF; W Su; Y Sankarasubramaniam; and E Cayirci, "Wireless sensor networks: a survey," Georgia Institute of Technology, 2002, <http://bit.ly/JC5DzD>.
- 2 Conner, Margery, "Advances in energy-storage technology power wireless devices," *EDN*, Feb 3, 2011, <http://bit.ly/fK800u>.
- 3 Gummesson, Jeremy; Shane S Clark; Kevin Fu; and Deepak Ganesan, "On the Limits of Effective Hybrid Micro-Energy Harvesting on Mobile CRFID Sensors," University of Massachusetts—Amherst, <http://bit.ly/JJnKgu>.
- 4 Ostaffe, Harry, "Wireless power energizes wireless sensor networks," *Powercast*, March 19, 2009, <http://bit.ly/ic5zk5>.
- 5 "Boostcap ultracapacitors," Maxwell Technologies, 2009, <http://bit.ly/KTwke7>.
- 6 Seah, Winston KG; Zhi Ang Eu; and Hwee-Pink Tan, "Wireless Sensor Networks Powered by Ambient Energy Harvesting (WSN-HEAP)—Survey and Challenges," Institute for Infocomm Research, 2009, <http://bit.ly/JhVfqI>.

You can reach  
Contributing  
Technical Editor  
**Dan Strassberg**  
at [StrassbergEDN@att.net](mailto:StrassbergEDN@att.net).




[[www.edn.com](http://www.edn.com)]

# PICO

**SURFACE MOUNT**  
(and thru-hole)  
**Transformers**  
& **Inductors**

**Size**  
**does**  
**matter!**

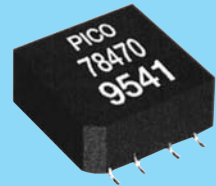

from  
low-  
profile

**.19"ht.**

- **Audio Transformers**
- **Pulse Transformers**
- **DC-DC Converter Transformers**
- **MultiPlex Data Bus Transformers**
- **Power & EMI Inductors**

See Pico's full Catalog immediately  
[www.picoelectronics.com](http://www.picoelectronics.com)

or send direct for free PICO Catalog

Call Toll Free 800 431-1064

Fax 914-738-8225

E Mail: [info@picoelectronics.com](mailto:info@picoelectronics.com)

**PICO** Electronics, Inc.

143 Sparks Ave. Pelham, N.Y. 10803-1837



*Delivery - Stock to one week*

## Complementary-pair dc/dc converter simultaneously doubles, inverts supply voltage

Ajoy Raman, Bangalore, India

The circuit in this Design Idea uses an intrinsic property of collector voltages in one-transformer push-pull dc/dc converters: They have a swing of twice the supply voltage. When you implement these circuits with an NPN device, the collector swings from 0V to twice the supply-rail voltage. When you use PNP devices, the collector voltage swings from  $V_{CC}$  to an equal amplitude but negative  $V_{CC}$  (Reference 1). In this circuit, a complementary pair of transistors, simultaneously imple-

menting a voltage doubler and a negative-voltage source, drives the two windings of the transformer.

One of the windings of transformer  $T_1$  connects to ground, driven by PNP transistor  $Q_1$  from  $V_{CC}$  (Figure 1). The other winding of  $T_1$  connects to  $V_{CC}$ , and NPN transistor  $Q_3$  drives the lower end to ground.  $Q_2$  and  $Q_4$  drive  $Q_1$  and  $Q_3$ , respectively. The collectors of  $Q_3$  and  $Q_1$  through resistors  $R_4$  and  $R_3$  provide cross-coupled drives to  $Q_2$  and  $Q_4$ .  $R_1$  and  $R_2$  form the collector loads for  $Q_2$

### DIs Inside

46 Adjust power-efficient LED switch to any light intensity

47 Obtain a gain of 450 from one vacuum tube

48 Probing system lets you test digital ICs

► To see and comment on all of EDN's Design Ideas, visit [www.edn.com/designideas](http://www.edn.com/designideas).

and  $Q_4$ .  $D_1$  and  $D_4$  prevent the reverse breakdown of  $Q_1$  and  $Q_3$ . The drive configuration and the transformer's winding polarity provide regenerative feedback and self-oscillation so that the transformer alternates between positive and negative saturation, inducing voltages to drive transistors  $Q_1$  and  $Q_3$  alternately on and off.

A square wave with an amplitude twice  $V_{CC}$  is generated at the collector of  $Q_1$ , which swings nominally from  $V_{CC}$  to the equal but negative output voltage. Simultaneously, a square wave with an amplitude twice the supply-rail voltage is generated at the collector of  $Q_3$ , which swings nominally from 0V to twice the supply-rail voltage.

$D_2$  and  $C_2$  provide half-wave rectification and filtering of the  $Q_1$  collector waveform generating the negative voltage output. Half-wave rectification and filtering of the  $Q_3$  collector waveform using  $D_3$  and  $C_3$  generate the doubler's output.

$T_1$  is 200 turns of bifilar AWG 37 enameled wire


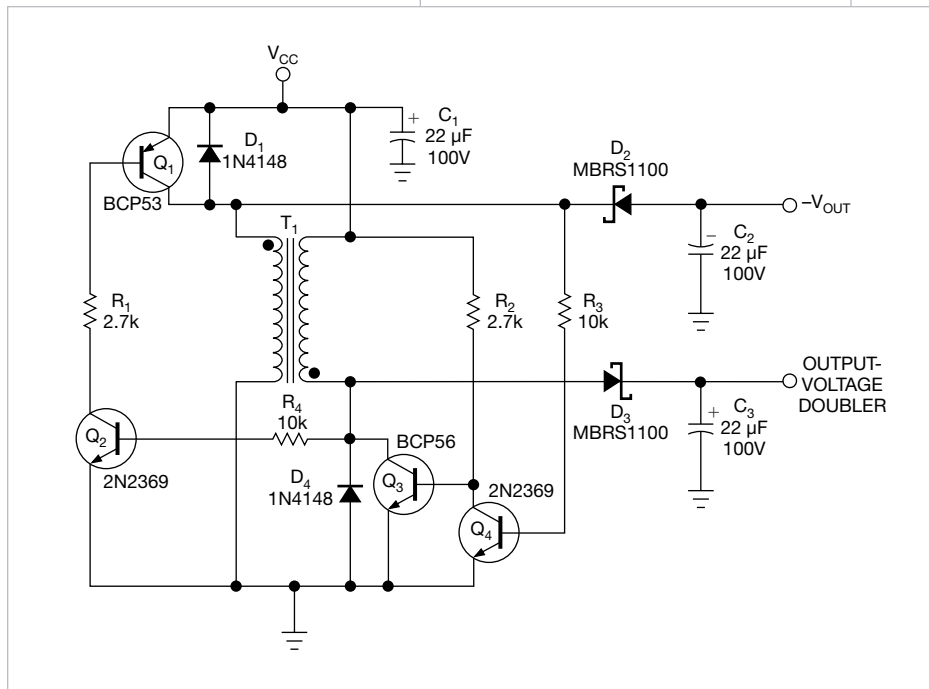


Figure 1 Cross-coupled regeneration drives switching transistors  $Q_1$  and  $Q_3$  and the windings of the transformer. The resulting voltage swings at their collectors are rectified to twice the positive and the negative power-supply rails.
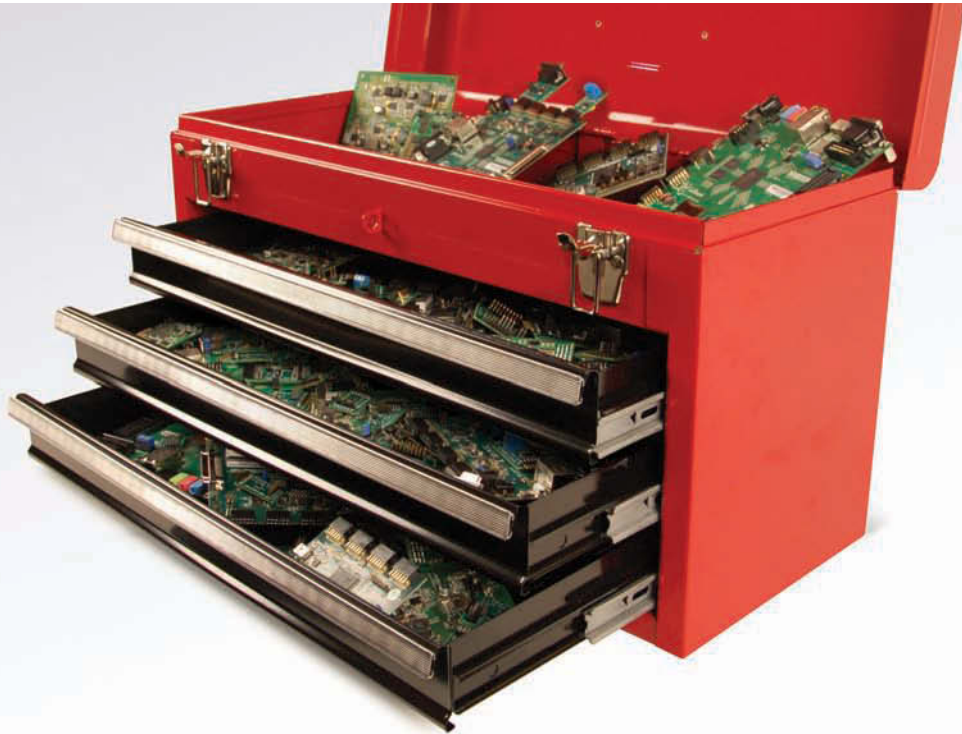
# Plug-and-Play FPGA Design Tools

*Quickly add power, signal chain, and other functions to your design*



**Hardware prototyping doesn't have to be hard.** With Maxim's new design tools, you can quickly add analog and mixed-signal functions to your FPGA reference platform without having to solder a single pin. Snap on peripherals using a Pmod™ port. Or plug in a module to power it all. With the right tools, everything is easier.

## Tools for FPGA Design

- 15 Pmod-compatible peripheral modules are available-buy individually, or buy the full collection for \$89.95
  - Bitstream allows use in any port without HDL recoding for plug-and-play ease
  - Sample C code is included to give you a head start on customization
- Compact power modules provide all the rails you need to power your FPGA design

Get the tools you need today.

[www.maxim-ic.com/FPGA-Design](http://www.maxim-ic.com/FPGA-Design)

**MAXIM**  
INNOVATION DELIVERED®



[www.maxim-ic.com/shop](http://www.maxim-ic.com/shop) [www.em.avnet.com/maxim](http://www.em.avnet.com/maxim) [www.digikey.com/maxim](http://www.digikey.com/maxim) [www.mouser.com/maximic](http://www.mouser.com/maximic)

© 2012 Maxim Integrated Products, Inc. All rights reserved. Innovation Delivered, Maxim, and the Maxim logo are trademarks or registered trademarks of Maxim Integrated Products, Inc., in the United States and other jurisdictions throughout the world. Pmod is a trademark of Digilent, Inc. All other company names may be trade names or trademarks of their respective owners.

**TABLE 1** EXPERIMENTAL RESULTS

Input voltage (V)	Input current (mA)	Frequency (kHz)	Voltage doubler (V)	Current doubler (mA)	Negative voltage (V)	Negative current (mA)	Input power (W)	Output power (W)	Efficiency (%)
5	253	2.1	7.68	81.7	-3.41	-72.5	1.27	0.87	69
9.97	360	4.05	17.33	115.5	-8.65	-86.5	3.59	2.75	76.6
15	420	6.02	27.2	136	-13.58	-90.5	6.3	4.93	78.2
19.4	400	7.37	34.9	145.4	-18.33	-61.1	7.76	6.19	79.8
25	340	10.47	48.5	97	-23.8	-79.3	8.5	6.59	77.5
30	410	12.07	56.5	113	-27.6	-92	12.3	8.92	72.5

wound 1-to-1 on a ferrite toroid core (references 2 and 3). Table 1 shows the experimental results with the voltage doubler and negative-voltage-generation circuit operating over an input voltage of 5 to 30V, demonstrating operation over a wide input volt-

age range and providing power at both outputs simultaneously at moderate efficiency. **EDN**

### REFERENCES

1 Raman, Ajoy, "Voltage doubler uses inherent features of push-pull dc/dc


converter," *EDN*, Aug 16, 2007, pg 72, <http://bit.ly/GTlveF>.

2 "T503125," Ceramic Magnetics Inc, <http://bit.ly/L3FzeW>.

3 MN60 manganese-zinc material specs, Ceramic Magnetics Inc, <http://bit.ly/KoyO4Y>.

## Adjust power-efficient LED switch to any light intensity

Raju Baddi, Tata Institute of Fundamental Research, Pune, India


 You can use an LED as a photoelectric sensor. A previous Design Idea shows that such a switch is highly power-efficient, consuming almost no power (Reference 1). However, you cannot adjust that configuration to switch at the desired light intensity. You can adjust the circuit in this Design Idea to any threshold level of light intensity necessary to maintain the on state of the photoelectric switch while retaining almost the same power efficiency of the original circuit (Figure 1).

Illuminating the reverse-biased green LED with ambient light causes the small current that flows through the LED to form the base current of the BC549 NPN transistor, which is amplified and passed on to the base of the BC177 PNP transistor. A magnified version of this current flows through the emitter of the BC177. The voltage drop across the emitter resistor depends on its value and the current flowing through it, which in turn determines the voltage drop across the CE terminals of the BC549.

By adjusting the value of the series emitter resistor you can set a voltage

corresponding to logic zero of a CMOS gate for any desired intensity of light falling on the green LED. This intensity depends heavily on the response of the green LED and the current gains of the

two transistors, so you select the resistor value by shorting out combinations of the series string of resistors and use the 10-M $\Omega$  potentiometer as a fine adjustment. Once you find a suitable value,

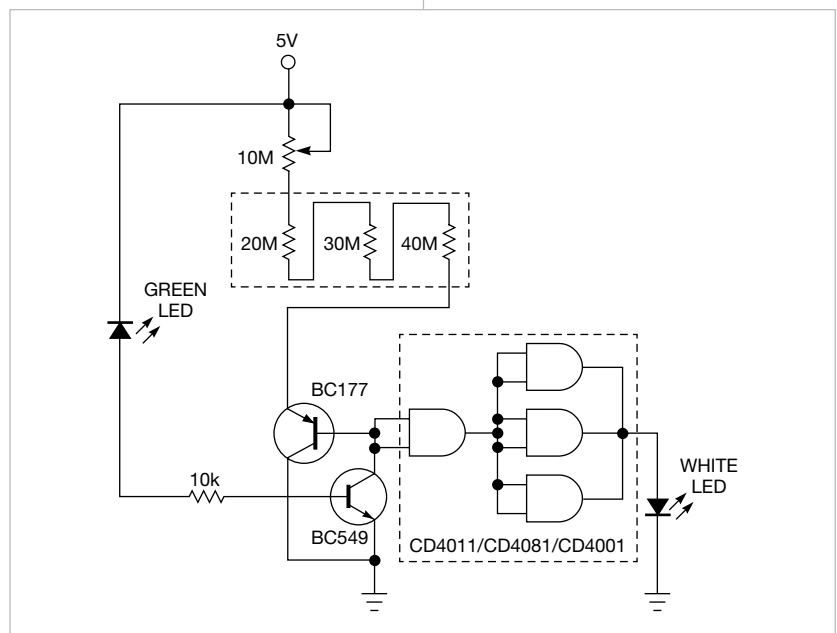

**Figure 1** The photocurrent through the green LED amplifies to CMOS-logic levels to turn on the white LED when ambient light falls.

you can remove the unused resistors from your circuit.

When the ambient light intensity falls below this level, both the base current of the BC549 and the current through the emitter series resistors decrease. This decrease raises the input voltage at the CD4011 logic gate higher than the CMOS switching threshold. The typical gate sourcing current at a 3V output is approximately

3 to 4 mA per gate; running three gates in parallel delivers approximately 10 mA to the white LED. You can use inverting or noninverting gates for the same result. The circuit still retains its power efficiency because the required series-resistor values normally exceed 10 M $\Omega$ .

You can check a green LED's suitability for use as a photodiode by measuring the voltage drop across the LED

with a 200-mV digital multimeter. If the LED is suitable as a photoelectric sensor, you will see a voltage of 0.3 to 1 mV across it, and this voltage changes with the intensity of light falling on the LED. **EDN**

## REFERENCE

■ Baddi, Raju R, "Use LEDs as photodiodes," *EDN*, Nov 18, 2010, pg 45, <http://bit.ly/HaLItFu>.

## Obtain a gain of 450 from one vacuum tube


Lyle Russell Williams, St Charles, MO

➔ A direct-conversion radio receiver required an audio gain of 450 from a pentode vacuum tube. A pentode has a high transconductance—that is, the ratio of the change in plate current to the change of the control grid voltage that caused it. To get high gain, however, it needs a high load impedance. RF applications with pentodes often used LC-tuned circuits in their plate loads in which the impedance at resonance and, therefore, the gain is high. It is typically impossible to implement a high load impedance using an untuned circuit because of the dc requirements of the tube.


### RF APPLICATIONS WITH PENTODES OFTEN USED LC-TUNED CIRCUITS IN THEIR PLATE LOADS.

For instance, a 6AU6 pentode vacuum tube needs a quiescent plate current of approximately 5 mA (**Figure 1**). If the quiescent dc plate voltage is to be 60V, the load resistance must be no more than 12 k $\Omega$ . The 0.5-M $\Omega$  plate resistance of the tube and the 1-M $\Omega$  load of the next stage are negligible with respect to the 12-k $\Omega$  load. With a transconductance of 3900 siemens, those requirements demand an audio gain of 45. You can easily achieve this gain with a triode tube.

To get a high load impedance with an untuned plate circuit, you can use a transistor current source for the tube (**Figure 2**). The transistor has no gain but functions as an active load for the tube and supplies the 5-mA plate current. You adjust the 500 $\Omega$  potentiometer to obtain 60V dc at the plate. The gain of the circuit is approximately 450. This gain implies a 150-k $\Omega$  load impedance that the transistor supplies in parallel with the plate resistance and the resistance of the next stage. Alternatively, you can use two triode tube circuits in series, each having a gain of 21. **EDN**

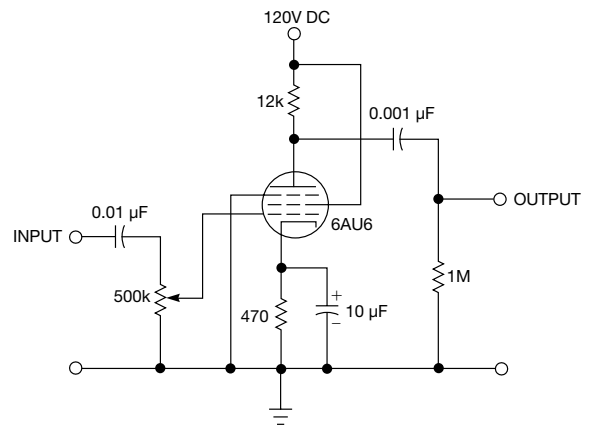

**Figure 1** A 6AU6 pentode vacuum tube needs a quiescent plate current of approximately 5 mA.

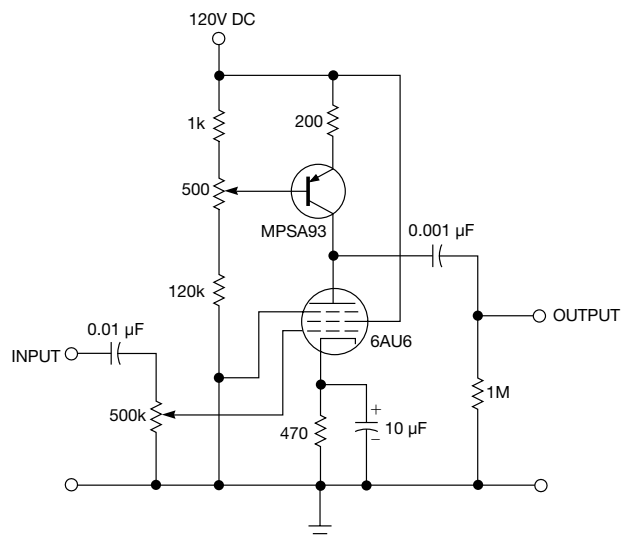

**Figure 2** To get a high load impedance with an untuned plate circuit, you can use a transistor current source for the tube.

# Probing system lets you test digital ICs

Raju Baddi, Tata Institute of Fundamental Research, Pune, India

This Design Idea describes a simple yet powerful handheld probe that you can use as both a logic probe and a pulse generator either individually or simultaneously. This feature makes the probe useful for testing DIP digital ICs, such as gates, flip-flops, and counters, using a socketed fixture with three-post jumpers to connect each pin to logic high or logic low or to 5V or ground. Three pushbutton switches, two dual-color LEDs, and two probe tips are built

into a plastic cylinder, such as an empty 20g-or-larger glue-stick tube. The generator's probe tip hooks to fit onto the test fixture's jumper pins and mounts onto a spring, such as those in retractable ball-point pens, for flexibility, and it allows the logic-probe tip to move to the output under test. Two of the pushbutton switches set the generator's quiescent state for a high output or a low output. The third switch briefly single-pulses the output to the opposite state. If the switch

is pressed for longer than 2 seconds, the output produces a pulse train.

IC<sub>1A</sub>, an NE556, is a 2-sec monostable circuit, which triggers a 1-msec-pulse-generator circuit employing gate G<sub>1</sub>, resistor R<sub>1</sub>, and capacitor C<sub>1</sub> (Figure 1a). G<sub>4</sub> buffers the circuit. The output of the monostable circuit also passes through G<sub>2</sub> and G<sub>3</sub> to mask the output of the astable component, IC<sub>1B</sub>, an NE556 that provides the pulse train. To prevent any spurious pulse from reaching output Probe A when switch S<sub>1</sub> is not depressed, keep IC<sub>1B</sub> deactivated by applying a low voltage to its reset Pin 4 through transistor Q<sub>1</sub>, whose biasing a 0.68-μF capacitor further guards.

When you press switch S<sub>1</sub> for a short

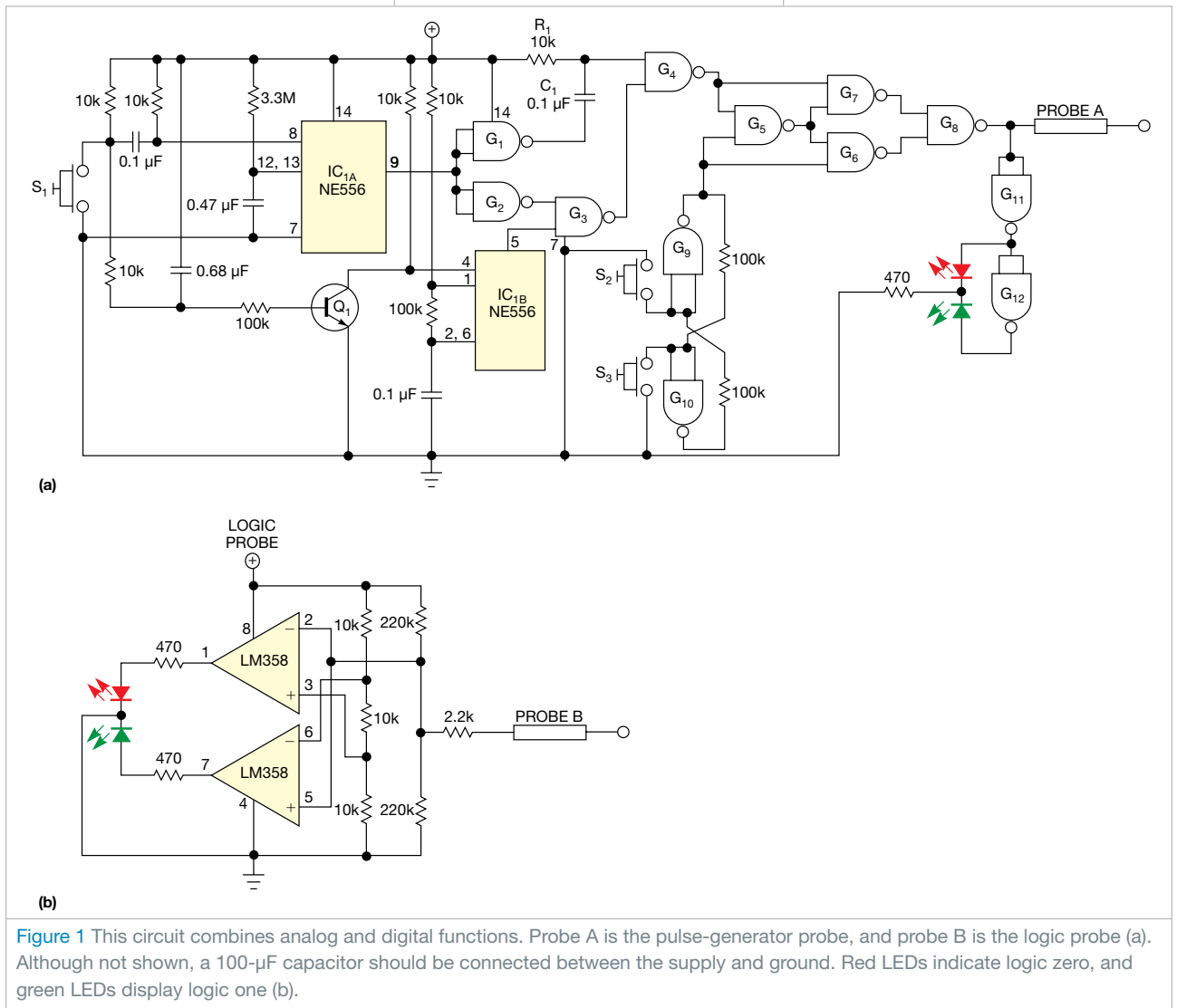


Figure 1 This circuit combines analog and digital functions. Probe A is the pulse-generator probe, and probe B is the logic probe (a). Although not shown, a 100-μF capacitor should be connected between the supply and ground. Red LEDs indicate logic zero, and green LEDs display logic one (b).



time, IC<sub>1A</sub> fires and produces a high output for approximately 2 sec. The 1-msec pulse from G<sub>1</sub>, R<sub>1</sub>, C<sub>1</sub>, and G<sub>4</sub> reaches the pulse Probe A through the XOR function comprising G<sub>5</sub> through G<sub>8</sub>, and

the output of the astable IC<sub>1B</sub> is masked at G<sub>3</sub> from reaching the XOR. If you depress switch S<sub>1</sub> for longer than 2 sec, the monostable IC<sub>1A</sub> times out. This action un masks G<sub>3</sub> and allows the 70-Hz

oscillation from IC<sub>1B</sub> to reach the XOR.

G<sub>9</sub> and G<sub>10</sub> form a bistable circuit, which “remembers” the most recently pressed S<sub>2</sub> or S<sub>3</sub> switch and controls the inverting and noninverting operation of the XOR function. G<sub>11</sub> and G<sub>12</sub> together drive the dual-color LED to indicate the pulse generator’s polarity. Red indicates that Probe A’s output is mainly logic zero, with the single 1-msec pulse a logic high. Green indicates the opposite.

The LM358 acts as a window-detector logic probe (Figure 1b). With the values in the figure, the red LED lights at Probe B voltages of less than 35% of the supply voltage, and the green LED lights at voltages greater than 65% of the supply voltage. Neither LED lights between these voltages. You may wish to adjust the resistor network to reduce the lower threshold to include the transistor-transistor-logic zero of less than 0.8V.

If you use CD4011 quad NAND gates, you can externally power the probe at 4.5 to 15V. Using a CD4093 Schmitt-trigger quad NAND for G<sub>1</sub> through G<sub>4</sub> ensures no spurious oscillations as a result of the slow voltage rise at timing capacitor C<sub>1</sub>. If your design requires a higher-current generator drive, you can add a pair of NPN and PNP boost transistors to the output.

Figure 2 shows a jig for testing the digital ICs. You configure the 16-pin DIP socket for the device under test with an array of triple-post headers and push-on jumpers. You can connect any pin directly or through a resistor to power or ground to configure power or logic levels. The resistors can be any suitable value; approximately 2 kΩ is appropriate. To set a TTL low, the pin must connect directly to ground. To inject a signal, hook the flexible spring-mounted generator, Probe A (Figure 3), onto the appropriate input post and then move logic Probe B to the corresponding output post or pin. To see a suggested perf-board layout, go to [www.edn.com/4374947](http://www.edn.com/4374947).EDN

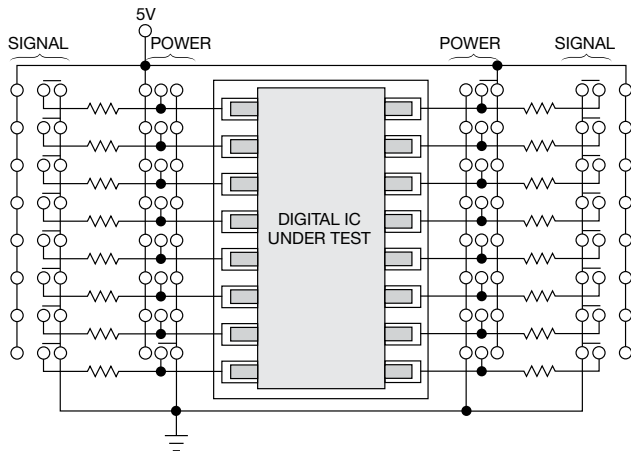


Figure 2 Program this test jig with header posts and jumpers for the IC under test.

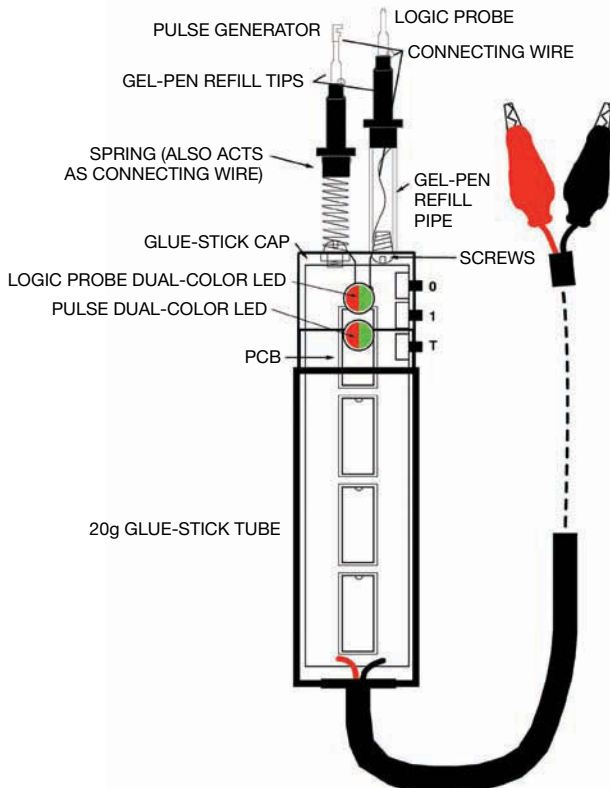


Figure 3 To inject a signal, hook the flexible spring-mounted generator, Probe A, onto the appropriate input post and then move logic Probe B to the corresponding output post or pin.

## REFERENCES

- 1 Baddi, Raju, “Logic probe uses six transistors,” *EDN*, Dec 15, 2010, pg 46, <http://bit.ly/n24oau>.
- 2 Rentyuk, Vladimir, “Logic probe uses two comparators,” *EDN*, Aug 25, 2011, pg 54, <http://bit.ly/wtuKgi>.

# supplychain

LINKING DESIGN AND RESOURCES

## Cost analysis: Reshoring is viable

A recent report on manufacturing-site selection contains both good and bad news for the United States. According to The Hackett Group's "Reshoring Global Manufacturing: Myths and Realities," the cost gap between manufacturing in China and production in the United States is narrowing. By 2013, says the report, the total landed cost of manufacturing in China will be only 16% lower than that of the United States. This margin, analysts believe, represents the "tipping point" where manufacturers consider reshoring as a viable option.


In contrast, the study also finds that companies are pursuing sites in other developing nations as a low-cost alternative to China. China has been a handy scapegoat in the debate about US jobs moving offshore. According to The Hackett Group, jobs will remain offshore, just not in China.

Countries including India, Thailand, Vietnam, and Brazil continue to successfully grow their share of global manufacturing as they become more cost-effective locations for manufacturing. "The cost increases in China are impossible ... to ignore," says Michel Janssen, chief research officer at The Hackett Group. "As Chinese wage rates rise, companies are

looking to maintain their competitive edge by either bringing that production closer to developed markets, moving it to lower-wage countries, or increasing productivity in China."

From one perspective, the question now is, Will these nations become as vilified



 The cost gap between manufacturing in China and production in the United States is narrowing.

as China? They are, after all, landing jobs that 20 years ago would have existed in the United States. The answer may depend on whether the United States accepts the fact that these jobs are never coming back: "Few of the low-skill Chinese manufacturing jobs will ever return to advanced economies; most will simply move to other low-cost countries," the report concludes.

A number of other factors have contributed toward the vilification of China, including the theft of IP, human-rights abuses, unfair trading practices, and low-quality merchandise. From a purely practical

perspective, however, costs in the United States and China aren't that different.

Reshoring is expected to become more viable with each passing year, as the total landed cost gap of manufacturing offshore shrinks. The Hackett Group's research found that the cost gap between the United States and China has shrunk by nearly 50% over the past eight years and is expected to be minimal by 2013. Rising labor costs in China, as well as rising fuel prices globally, which affect shipping costs, are driving this trend.

Total landed manufacturing cost continues to be the leading factor in companies' site selection. The key components of this cost are raw-material and component costs, manufacturing costs, transportation and logistics, inventory carrying costs, and taxes and duties. According to The Hackett Group, the cost differential between other developing nations and the United States is as much as 20%. As long as the majority of manufacturers—85%, according to the study—measure cost as the main driver in site selection, manufacturing is likely to remain offshore.

—by **Barbara Jorgensen**,  
**EBN Community Editor**

*This story was originally posted by EBN: <http://bit.ly/Nkenb4>.*

## SMARTPHONES, MEDIA TABLETS PROPEL MOBILE-MEMORY CHIP MARKET

OUTLOOK

**New smartphones and tablets will act as key catalysts for continued healthy growth of the mobile-memory semiconductor space in the next few years, with revenue growing a modest but healthy 6% this year, according to IHS iSuppli. Revenue for mobile memory is projected to reach \$14.9 billion this year, up from \$14.1 billion in 2011. The mobile-memory forecast includes the flash-memory segments of NAND and NOR, the NAND subsegment of eMMC (embedded multi-media card), and the mobile DRAM sector.**

A 9% increase is anticipated in 2013 for mobile memory as more smartphone and tablet products requiring higher memory densities enter the marketplace, with revenue climbing to \$16.2 billion. By 2015, mobile-memory revenue will peak at \$17.9 billion.

"The mobile space has been the engine for overall memory growth in the last few years, and it continues to shape and define the success of suppliers," says Michael Yang, senior principal analyst for memory and storage at IHS. "Given the ongoing passion of consumers for mobile devices ... the outlook for mobile memory remains exceedingly optimistic."

—by **Amy Norcross**

# Support Across The Board.™

## From Design to Delivery™



### Now, you can have it all.™

Faster and easier than ever before. Our commitment to customer service is backed by an extensive product offering combined with our supply chain and design chain services – which can swiftly be tailored to meet your exact needs. We have dedicated employees who have the experience to provide the highest level of customer service with accuracy and efficiency. All of our technical experts are factory certified on the latest technologies, providing you the expertise to move projects forward with speed and confidence.

Avnet offers the best of both worlds: extensive product and supply chain knowledge, and specialized technical skill which translates into faster time to market – and the peace of mind that comes from working with the industry's best. **Avnet is ranked Best-In-Class\* for well-informed sales reps, knowledgeable application engineers and our design engineering services – proof that we consistently deliver:**

- > Industry recognized product expertise
- > Specialized technical skills

#### Ready. Set. Go to Market.™

Visit the Avnet Design Resource Center™ at:  
[www.em.avnet.com/drc](http://www.em.avnet.com/drc)



*Accelerating Your Success™*




\*As rated by Hearst Electronics Group: The Engineer & Supplier Interface Study, 2009.  
©Avnet, Inc. 2011. All rights reserved. AVNET is a registered trademark of Avnet, Inc.

1 800 332 8638  
[www.avnetexpress.com](http://www.avnetexpress.com)

Follow us on Twitter!  
[www.twitter.com/avnetdesignwire](http://www.twitter.com/avnetdesignwire) 

## MEMORY AND STORAGE

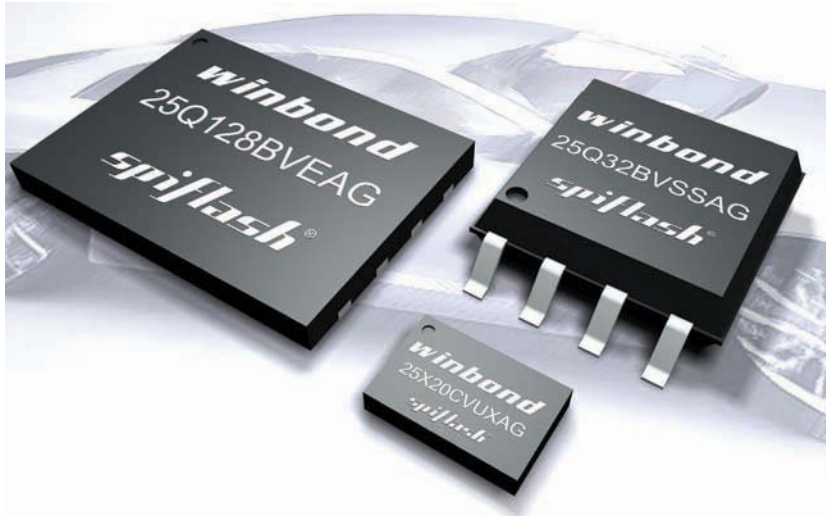


### Winbond SpiFlash features 2- to 128-Mbit densities

↘ The SpiFlash family of serial-flash memory devices includes the 90-nm automotive-grade 2 and industrial-grade plus, which operate at  $-40$  to  $+105^{\circ}\text{C}$ , and the automotive-grade 3 and industrial grade, which operate at  $-40$  to  $+85^{\circ}\text{C}$ . The devices come in 2- to 128-Mbit densities and target use in automotive audio telematics, navigation and GPS systems, media centers, digital displays, cameras, data recorders, and safety-monitoring devices. The prices for the W25X/25Q SpiFlash devices range from 25 cents for 2-Mbit densities to \$2.12 for 128-Mbit densities for full automotive-grade-2, AEC-Q100-qualified units with PPAP charge control (100,000). **Winbond Electronics Corp**, [www.winbond.com](http://www.winbond.com)
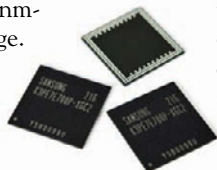
### Samsung LPDDR2 memory uses 20-nm-class technology

↘ Using 20-nm-class technology, the 4-Gbit LPDDR2 memory targets mobile devices, such as large-screen tablets and smartphones. The device allows vendors to deliver 2-Gbyte products with a thickness of 0.8 mm, which stack four 4-Gbit LPDDR2 chips in one LPDDR2 package. The 2-Gbyte package can process data at speeds as high as 1066 Mbps using the same amount of power as that of a 30-nm-class, 2-Gbyte package.

**Samsung**,  
[www.samsung.com](http://www.samsung.com)



### Ramtron FM25e64 FRAM improves POS products

↘ The FM25e64 FRAM operates on 1.5 or 1.8V power rails; offers 20- $\mu\text{A}$  active-current operation; and requires 20  $\mu\text{sec}$  to start up, write data, and shut down. Targeting security applications, such as point-of-sale terminals and utility-metering products, the device securely erases data during a breach or power cycle and wipes out confidential transactions in as little as 10  $\mu\text{sec}$ . The



FM31T378 companion processor comes with a real-time clock and other common peripherals. The FM25e64 is available from DigiKey, Mouser, and other distributors for 95 cents (10,000).

**Ramtron International Corp**,  
[www.ramtron.com](http://www.ramtron.com)

### Intel SSD 330 series has affordable prices

↘ The 330 series of SATA 6-Gbps solid-state drives comes in capacities of 60, 120, and 180 Gbytes. It contains the vendor's 25-nm multilevel-cell NAND memory, and the SATA interface provides read speeds as fast as 500 Mbytes/sec, sequential-write speeds as fast as 450 Mbytes/sec, random-read performance as fast as 22,500 I/O operations/sec, and write speeds as high as 33,000 I/O operations/sec. It comes in a 2.5-in./9.5-mm form factor and sells for \$89, \$149, and \$234 for the 60-, 120-, and 180-Gbyte capacities, respectively.



**Intel Corp**, [www.intel.com](http://www.intel.com)

### Microchip SuperFlash Kit 1 enables serial-flash-memory evaluation

↘ The AC243005-1 SuperFlash Kit 1 memory-development kit enables designers to evaluate the vendor's SPI and SQI serial-flash-memory devices. It includes three serial-flash PICtail Plus daughterboards with the SST25VF016B, SST25VF064C, and SST26VF032 flash devices, respectively. The boards interface with the Explorer 16 development board and work with the MPLab X IDE to enable quick creation of code and to shorten development time. Example code and software drivers



are available for download from <http://www.microchip.com/get/9RX5>. The SuperFlash Kit 1 sells for \$30.

**Microchip Technology Inc,**  
[www.microchip.com](http://www.microchip.com)

## WD's Scorpio Blue stores 2 million songs or 1.6 million photos

➔ The Scorpio Blue hard drive for mobile computers touts a shock tolerance of 400g and a capacity of 500 or 320 Gbytes. The 5400-rpm drive has an average nominal latency of 5.5 msec and SATA or PATA interfaces. Buffer-to-host transfer rates for the SATA interface are a maximum of 3 Gbps. The drive is compatible with standard 9.5-mm slots, making it a storage option for



use in notebook computers and Ultrabook computers requiring a 7-mm drive height. The vendor claims that the unit can store as many as 2 million songs or 1.6 million photos. The

500- and 320-Gbyte versions sell for \$99.99 and \$79.99, respectively.

**Western Digital Corp,** [www.wdc.com](http://www.wdc.com)

## Toshiba Exceria memory cards provide transfer rates as fast as 95 Mbytes/sec

➔ The Exceria SDXC and SDHC memory cards tout capacities of 8, 16, and 32 Gbytes. All devices have power-supply voltages of 2.7 to 3.6V. Type 1 devices have maximum read and write speeds of 95 and 90 Mbytes/sec, respectively; Type 2 devices have maximum read and write speeds of 95 and 60 Mbytes/sec, respectively; and Type HD versions have maximum read and write speeds of 90 and 30 Mbytes/sec, respectively.

**Toshiba America Electronic Components,** [www.toshiba.com/taec](http://www.toshiba.com/taec)



## Alliance Memory enters SDRAM market with SC4 family

➔ The 64-Mbit AS4C4M16S, 128-Mbit AS4C8M16S, and 256-Mbit AS4C16M16S CMOS synchronous DRAMs find use in communications, medical, and consumer products requiring high memory bandwidth. Internally configured as four banks of 1M, 2M, or 4M words by 16 bits with a synchronous interface, the units operate from one 3.3V power supply and are lead- and halogen-free. They come in 44-pin, 400-mil, plastic TSOP II packages and offer access time from the clock as low as 4.5 nsec at a 5-nsec cycle and clock rates of 143 to 200 MHz. The burst lengths are one, two, four, eight, or full-page, with a burst-termination option. Clock rates for the 64-, 128-, and 256-Mbit devices are 166 or 143; 166 or 143; and 200, 166, or 143 MHz, respectively. Prices are 80 cents, \$1.30, and \$1.60, respectively.

**Alliance Memory Inc,**  
[www.alliancememory.com](http://www.alliancememory.com)



## EDN ADVERTISER INDEX

Company	Page
Aeroflex	11
Agilent Technologies	6, C-3
Analog Devices	13, 39
Arrow Electronics	19
ams	25
Avnet	51
Coilcraft	4
Digi-Key Corp	C-1, C-2
Hapro Inc	53
Interconnect Systems Inc	35
International Rectifier	7
Linear Technology	C-4
MathWorks	21
Maxim Integrated Products	45
Memory Protection Devices	26
Mill-Max Manufacturing	9
Pico Electronics Inc	17, 43
Rohde & Schwarz	15, 28-29
Sealevel Systems Inc	53
UBM EDN	23, 31, 33
Vicor Corp	3

EDN provides this index as an additional service. The publisher assumes no liability for errors or omissions.

# EDN product mart

This advertising is for new and current products.

**HAMEG®**  
Instruments  
A Rohde & Schwarz Company

**\$2,115**

**200kHz LCR-Bridge HM8118**

- ☑ Basic Accuracy 0.05%
- ☑ Measurement Functions L, C, R, |Z|, X, |Y|, G, B, D, Q, Θ, Δ, M, N
- ☑ Test Frequencies 20Hz...200kHz
- ☑ Up to 12 Measurements per Second
- ☑ Parallel and Series Mode

**HAPRO Electronics**  
Tel: +1-516-794-4080 · [www.hameg.us](http://www.hameg.us)

## High Speed 4-Port USB 2.0 Hub with Battery Charging Downstream Port




Sealevel's HUB4PH is a powered USB 2.0 4-port hub with Port 1 configured as a Charging Downstream Port (CDP) and

the remaining 3 ports configured as Standard Downstream Ports (SDP).



[sealevel.com/edn/hubs](http://sealevel.com/edn/hubs)
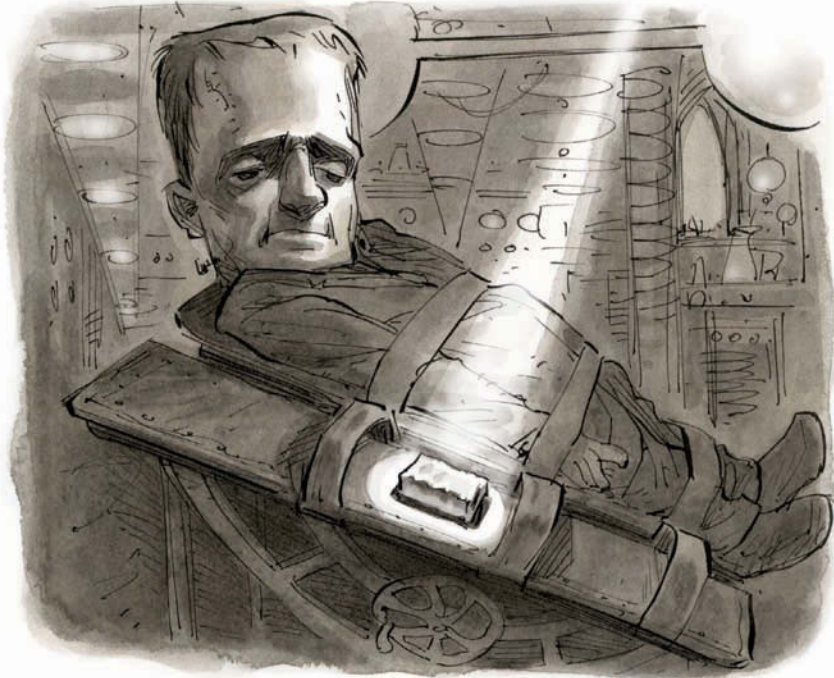
## Aluminum box foils Frankenstein's monster



In the early 1970s as a fresh Perdue graduate, I took a job at a local factory. It was one of several manufacturing facilities of a large company. Except for one resident engineer, all design and engineering flowed down to us from the home office. Our plant produced thick-film hybrid circuits: a ceramic baseplate with conductors screen-printed on it, then screen-printed resistors, and, finally, discrete components soldered in place. A few parts needed resistors with close tolerances; we intentionally printed those parts with resistance lower than desired, then sand-blasted the resistors to the correct value. A final dip in epoxy produced the rectangular, multilead parts you have likely seen in old radios and other devices.

The company took an order for a part that had tight phase-angle tolerances. We needed to adjust three resistors to achieve precise phase angles with the capacitors soldered to the plate; this fix was a so-called functional adjust. This product was worth a great deal of money to the company, and we needed to get it right. In due course, the engineers arrived with a truckful of oscillators, digital phase meters, comparators, controllers, and all manner of other support gear to do the critical adjustments. It was interconnected with GPIB cables,

and we were renting it by the month.

The learning curve on this part was slow and painful. We had to run the sandblasters at the lowest possible speed so that we did not overshoot the phase angle. We had low output and a high failure rate at final testing. Our resident engineer was spending a great deal of time trying to get everything working right, but it was obvious that he and the other higher-ups were worried.

I was on third shift to keep the production equipment, including the all-important functional adjust, running

through the night. Although I was just a technician, I was the de facto shift supervisor, as well.

Functional adjust had me pulling my hair, too. One night, when fixing yet another problem with it, I went through the entire setup. It struck me that the biggest problem was that, by the time the phase comparator saw the proper phase angle, it could not quickly enough signal through GPIB to cut off the sandblaster. To my amazement I discovered that the manufacturer had specified all of the phase-angle tolerances at one frequency, meaning that we could perform the phase-angle adjustment by trimming to a precise time lag between the input and the output. We had all been admonished to leave the setup alone to the extent possible; after all, it was the fruit of many months of work by many engineers.

I took advantage of my third-shift situation to secretly build a box with comparators and one-shots taking the place of the ohmmeter circuits we used for more mundane resistor adjustment. When it was ready, I set up the 2×5×7-in. aluminum box next to Frankenstein's monster from the home office. I ran off about 10 parts and felt vindicated when final test showed a much tighter scatter in values, plus it ran about four times faster than the monster.

When the day crew arrived, I told our lone engineer what I had done, showed him the setup, and handed him the parts I had adjusted earlier. As I left for home, I saw him practically running to final test, giddy with the prospect of knocking me down a few pegs for insubordination and no doubt directing the heat for our poor output in my direction.

Instead, he ran tests on my box for a couple of days, and my setup was soon running in parallel with Frankenstein's to increase our output. Within a week or two, Frankenstein's monster was sitting idle, and my box was going full-tilt. Production was up, and rejects were down. We later unceremoniously packed up the rented gear and returned it to the rental company. **EDN**

*Richard Oliver is an engineer working on the 4.2m Discovery Channel Telescope at Lowell Observatory (Flagstaff, AZ).*

# Power your most demanding setups with ease.



## No matter your application, accelerate with Agilent.

Whether it's automotive ECU, military communications, base station power amplifiers or general purpose test, maximize manufacturing throughput and R&D productivity. With seven new high-power modules from 300 to 500 W, Agilent helps you execute a wide range of high-power setups with the performance to measure milliamps accurately, too.

### Agilent N6700 Modular Power System

- 4 mainframes—manufacturing or R&D
- 34 modules from 20 to 500 W
- 4 performance levels—basic to precision



To view application videos scan QR code



or visit <http://goo.gl/sgwbK>

© Agilent Technologies, Inc. 2012. \*While supplies last. Terms and conditions apply.

Get a **FREE 8 GB USB drive** loaded with power product resources\*  
[www.agilent.com/find/N6700Power](http://www.agilent.com/find/N6700Power)


u.s. 1-800-829-4444 canada: 1-877-894-4414

Anticipate — Accelerate — Achieve



Agilent Technologies

# DDRx–We Have You Powered

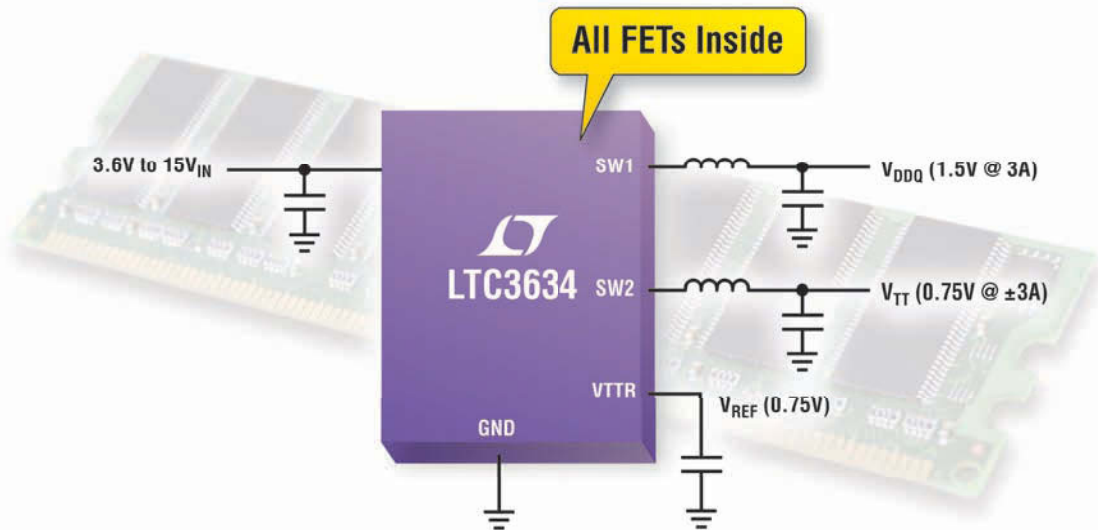

## Monolithic & Controller Solutions Provide Minimal Power Loss & Compact Footprints

The LTC<sup>®</sup>3634 is just one of our growing family of synchronous step-down regulators providing power supply and bus termination rails for double data rate (DDR 1, 2, 3 & 4) SDRAM controllers. The family features 90%+ power conversion efficiencies, minimizing power loss and simplifying thermal design. Operating input voltages can be as high as 38V, enabling operation from 5V, 12V and 24V system rails and various battery-powered systems. The  $V_{TT}$  regulated output voltage is equal to  $\frac{1}{2} V_{DDQIN}$ . An on-chip buffer is capable of driving up to 10mA, providing a low noise reference output  $V_{TTR} = \frac{1}{2} V_{DDQIN}$ .

### ▼ DDR Power Solutions

Part Number	$V_{IN}$ Range (V)	$I_{OUT}$	$V_{TTR}$ Current (mA)	Min $V_{TT}$ (V)
LTC3413	2.25 to 5.5	±3A	-	1.1
LTC3617	2.25 to 5.5	±6A	±10	0.5
LTC3618	2.25 to 5.5	$V_{TT} \pm 3A$ & $V_{DD} + 3A$ or $V_{TT} \pm 6A$	±10	0.5
LTC3634	3.6 to 15	$V_{TT} \pm 3A$ & $V_{DD} + 3A$ or $V_{TT} \pm 6A$	±10	0.5
LTC3876	4.5 to 38	$2 \times \pm 20A^*$	±50	0.5

\*Depends on external MOSFETs.

### ▼ Info & Free Samples

[www.linear.com/products/regulators](http://www.linear.com/products/regulators)

1-800-4-LINEAR



<http://video.linear.com/p4483>

LT, LT, LTC, LTM, Linear Technology and the Linear logo are registered trademarks of Linear Technology Corporation. All other trademarks are the property of their respective owners.

