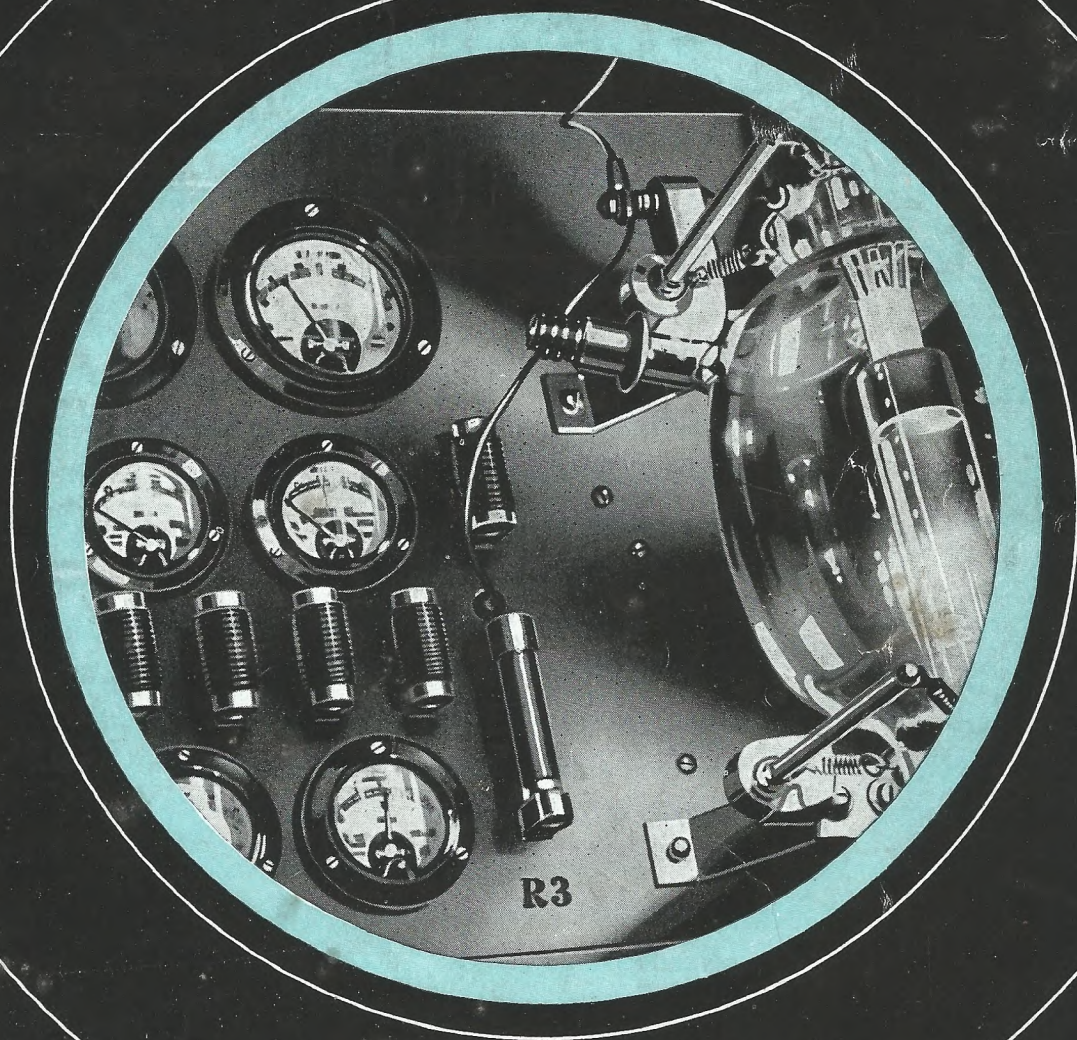


Wireless World

RADIO • ELECTRONICS • ELECTRO-ACOUSTICS



DEC. 1942

1/3

RESISTANCE-CAPACITY AF OSCILLATOR

Vol. XLVIII No. 12



THE DEMAND for Frequentite, which possesses outstanding properties of Low Loss and High Mechanical Strength, continues to increase rapidly—and to be met. Production capacity has been stepped up over a period of years by extensions to plant, the


employment of specialised new equipment, and progressive improvements in manufacturing technique. Bulk supplies of the most intricate designs can be delivered promptly, and all manufacturers are invited to write for Catalogue No. SP.10.

STEATITE & PORCELAIN PRODUCTS LTD.

Head Office: STOURPORT-ON-SEVERN, WORCS.

Telephone: Stourport 111. Telegrams: Steatite, Stourport.

Pollard

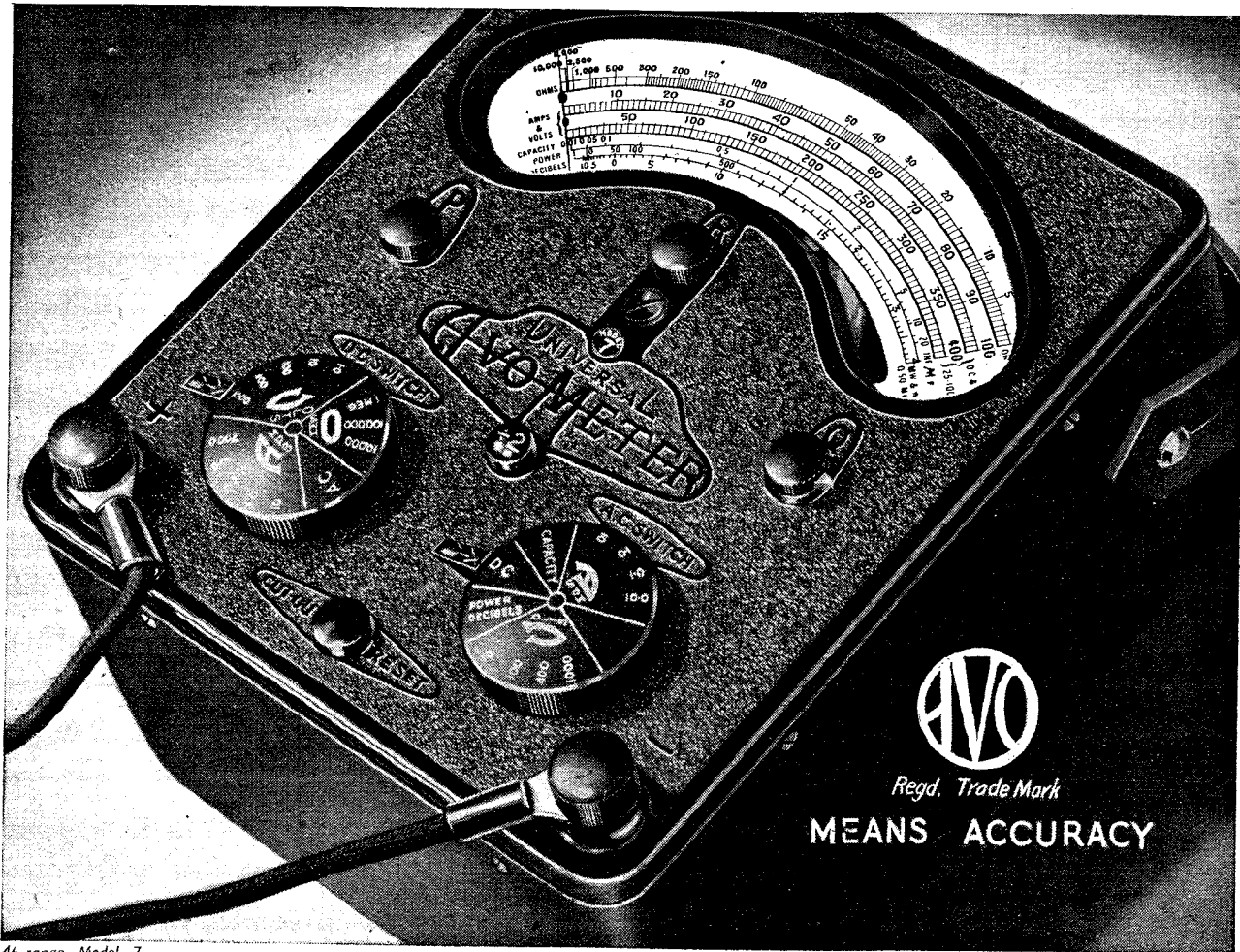

46-range Model 7
Universal AvoMeter

The Model 7 Universal AvoMeter (illustrated) is a compact combination electrical measuring instrument of B.S. 1st Grade accuracy. Its 46 ranges cover A.C. and D.C. amperes and volts, resistance, capacity, audio-frequency power output and decibels. No external shunts or series resistances. Protected by automatic cut-out against damage through overload.

Some delay in delivery of Trade Orders is inevitable, but we shall continue to do our best to fulfil your requirements as promptly as possible.

Sole Proprietors and Manufacturers:

AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD., Winder House, Douglas Street, London, S.W.1

Telephone: VICToria 3404/7

The world-wide use of "AVO" Instruments is striking testimony to their outstanding versatility, precision and reliability. In every sphere of electrical test work—laboratory, shop or out on a job—they are appreciated for their dependable accuracy, which is often used as a standard by which other instruments are judged. There is an "AVO" Instrument for every essential electrical test.

Useful Christmas Gift Suggestions

ELECTRIC IRONS, BEST QUALITY, HEAVILY PLATED, WITH LEAD AND CONNECTOR, 200/250 volts A.C./D.C., 32/6, including tax.

ELECTRIC KETTLES, IMMERSION HEATER TYPE, WITH LEAD AND CONNECTOR (VITREOUS ENAMEL FINISH), 230/250 volts A.C./D.C., 39/6, including tax.

ELECTRIC TOASTERS, NICKEL-PLATED, WITH LEAD AND ADAPTOR, 30/9, including tax.

SMALL ELECTRIC BREAKFAST COOKER WITH DUAL BOILER, SWITCH, IMITATION VITREOUS ENAMEL FINISH, SUPPLIED WITH LEAD, 200/250 volts A.C./D.C., £2/2/-, including tax.

"UTILITY" ELECTRIC FIRE (750-watt low consumption), SUPPLIED IN ATTRACTIVE CRACKLE FINISH WITH LEAD, 200/250 volts, £1/2/6, including tax.


DE LUXE 1 kW. ELECTRIC FIRE, VERY ATTRACTIVE DESIGN, ENAMEL FINISH IN PASTEL SHADES, SUPPLIED WITH LEAD, 27/6, including tax.

ELECTRIC SOLDERING IRONS, 60-WATT, WITH FLEX, 200/250 volts A.C./D.C., CHROME-PLATED, BEST QUALITY, 12/6, tax free.

LOUDSPEAKER TRANSFORMERS Limited Quantity Available. HEAVY DUTY PENTODE, 7/- each. MIDGET PENTODE, 5/- each.

Please Note.—All orders C.O.D. or Cash with order, carriage paid. We cannot hold ourselves responsible for goods damaged or lost in transit.

SPECIAL OFFER! MODEL AEROPLANE KITS

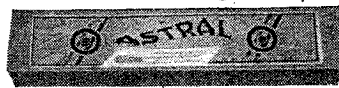

**Flying Models AUTHENTIC AIRCRAFT
3 SIZES, LATEST TYPE BOMBERS, FIGHTERS, Etc.**

16" WING SPAN .. 1/9
24" " " .. 8/6
30" " " .. 12/6
TAX FREE

Supplied complete with diagram, glue, dope, wood frame, etc., etc. All you need is a razor blade, pair of scissors and nimble fingers.

**A FASCINATING AND INSTRUCTIVE HOBBY.
AN IDEAL XMAS GIFT**
State Model required. This, however, cannot be guaranteed.

ROLA P.M. LOUDSPEAKERS:
With Transformer Without Transformer
6in. 19/6 14/9
8in. 24/9 18/9
ONLY A FEW LEFT

SPECIAL LINE
PRE-WAR STOCK OF HAND-MADE WROUGHT IRON ELECTRIC FIRES (Callers Only).

CHROME-PLATED ELECTRIC BELLS, WITH TRANSFORMER, A.C. 200/250 Volts, SUPPLIED WITH INSTRUCTIONS FOR FITTING, 15/6, tax free.

WORTH DOUBLE
(Do away with that old "Le 'clanche" cell or dry battery and fit a reliable door bell.)

REPLACEMENTS. — IMMERSION HEATER ELEMENTS FOR ELECTRIC KETTLES, FIT MOST MAKES. (State voltage.) 22/6 each.

FIRE BARS WITH ELEMENT, FLAT TYPE. 200/250 volt : 750 W., 3/9 each ; 1 kW. 4/9 each.

ROUND TYPE BAR WITH SPIRAL, 200/250 volt : 750 W., 3/9 each.

THERMOSTATICALLY CONTROLLED ELECTRIC GEYSERS, 1½ Gallon, WITH ALL FITTINGS, 200/250 volt A.C. AS NEW, FROM STOCK OF A FAMOUS MANUFACTURER. £6/19/- each.

If you need hot water in a hurry an electric geyser is indispensable. It is very economical, too.

H. H. LINTON & CO. LTD. 2, Highgate High Street, N.6. Mountview 9431

MALLORY

P. R. MALLORY & CO. Inc.

PRECISION RADIO PRODUCTS

IT is in the interests of the cause for which the Allies are fighting that we cannot continue to supply you with Mallory precision radio products unless you possess the necessary Import Licences and Priorities. Mallory activities extend far beyond the manufacture of radio parts and our plant is busily engaged on work of National importance. Much of your service equipment is Mallory equipped and when conditions permit you can rest assured that we shall once again be ready to supply you with:—

- MALLORY VIBRATORS AND VIBRAPACKS.
- MALLORY SEALED STRATOSPHERE VIBRATORS.
- MALLORY WAVE CHANGE AND CIRCUIT SWITCHES.
- MALLORY F.P. ELECTROLYTIC CONDENSERS.
- MALLORY TUBULAR AND PAPER CONDENSERS.
- MALLORY GRID BIAS CELLS, PLUGS, JACKS AND OTHER PRECISION RADIO PARTS.

★ Register your name with our Representative now. He will forward you information on our products as soon as they become available.

**P. R. MALLORY & CO. INC.
INDIANAPOLIS, INDIANA, U.S.A.**

Represented exclusively in Gt. Britain by

FRANK HEAVER LTD., Kingsley Rd., Bideford, N. Devon, Eng.

— VALVES —

AMERICAN AND INTERNATIONAL OCTALS. Most types available as per last month's advert.

B.V.A. VALVES. Mullard numbers generally quoted, but we may send B.V.A. equivalents. Prices quoted are current B.V.A., plus purchase tax.

BATTERY TYPES. VP2, 11/-; SP2, 11/-; PM12M, 11/-; FC2A, 12/10; TDD2A, 9/2; PM22A, 11/-; PM22D, 11/-; QP22B, 15/3; PM2A, 7/4; PM202, 12/4; PM2, 7/4; PM2DX, 5/6; PM2BA, 12/10; PM2HL, 5/6; Mazda Specials HL23, 5/6; Pen 25, 11/-.

A.C. MAINS TYPES. TH4A, 14/-; FC4, 14/-; ACTP, 14/-; TDD4, 9/2; VP4B, 12/10; VP4, 12/10; 354V, 9/2; PM24A, 18/3; FW4500, 18/3; Mazda Octals SP41, 12/10; VP41, 12/10; HL41, 9/3; HL41DD, 11/7; TH41, 14/-; Pen 45, 12/10; UUG, 11/-; Mullard E Types, ECH3, 14/-; EK2, 14/-; EFS, 12/10; EFG, 12/10; EBC3, 11/7; EL2, 14/-; EL32, 14/-; AZ1, 11/-; EL3, 12/10; EBL1, 15/3;

UNIVERSAL AC/DC TYPES. FC13, 14/-; SP13, 12/10; HL13, 11/7; VP13C, 12/10; SP13C, 12/10; TDD13C, 11/7; Pen 36C, 12/10; 13VPA, 12/10; 13SPA, 12/10; 2D13A, 9/2; 2D13C, 9/2; Mazda Octals, TH233, 14/-; VP133, 12/10; HL133DD, 9/7;

AMERICAN TYPES. 6A7, 14/-; 6A8, 14/-; 6K8, 14/-; 6K7, 12/10; 6U7, 12/10; 6F5, 9/2; 6Q7, 11/7; 6F6, 12/10; 25A6, 12/10; 80, 14/6; 5Y3, 14/6; 6V6, 12/10; 25Z6, 11/-.

RECTIFIERS. Non-B.V.A. Replacement Types, all at 14/6 each. Replacements for American 80, 5Y3, 5Z4. Marconi Ossram U50, U10, U12, MU12; Mullard IW2, IW3, IW4, DW2, DW3; Cosor 422BU, 506BU; Brimar R1, R2, R3; Phillips 1821, etc.

SPECIAL NOTE.—The valves listed above represent only a small proportion of our stocks. Please mention any other types you are requiring and we will send them if in stock.

To save time, order valves C.O.D.

— SPARES —

See last month's advert. The following are also available:

MIKE CABLES. Twin conductors, fully screened and tough rubber-covered overall, 3/- per yard.


SERVULOS Switch Cleaner, at 5/- per ½-pint tin.

CELLULOSE CEMENT for valve bases, speaker cones, etc., at 5/- per ½-pint tin.

P.M. SPEAKERS. Rola dustproof type, 4in. with transformer, at £1/1/6; without transformer, at 17/6; 5in. with transformer, at £1/3/6; 10in. with transformer, at £1/17/6.

TERMS: Cash with order or C.O.D. We prefer C.O.D. orders, but such orders cannot be sent to H.M. Barracks.

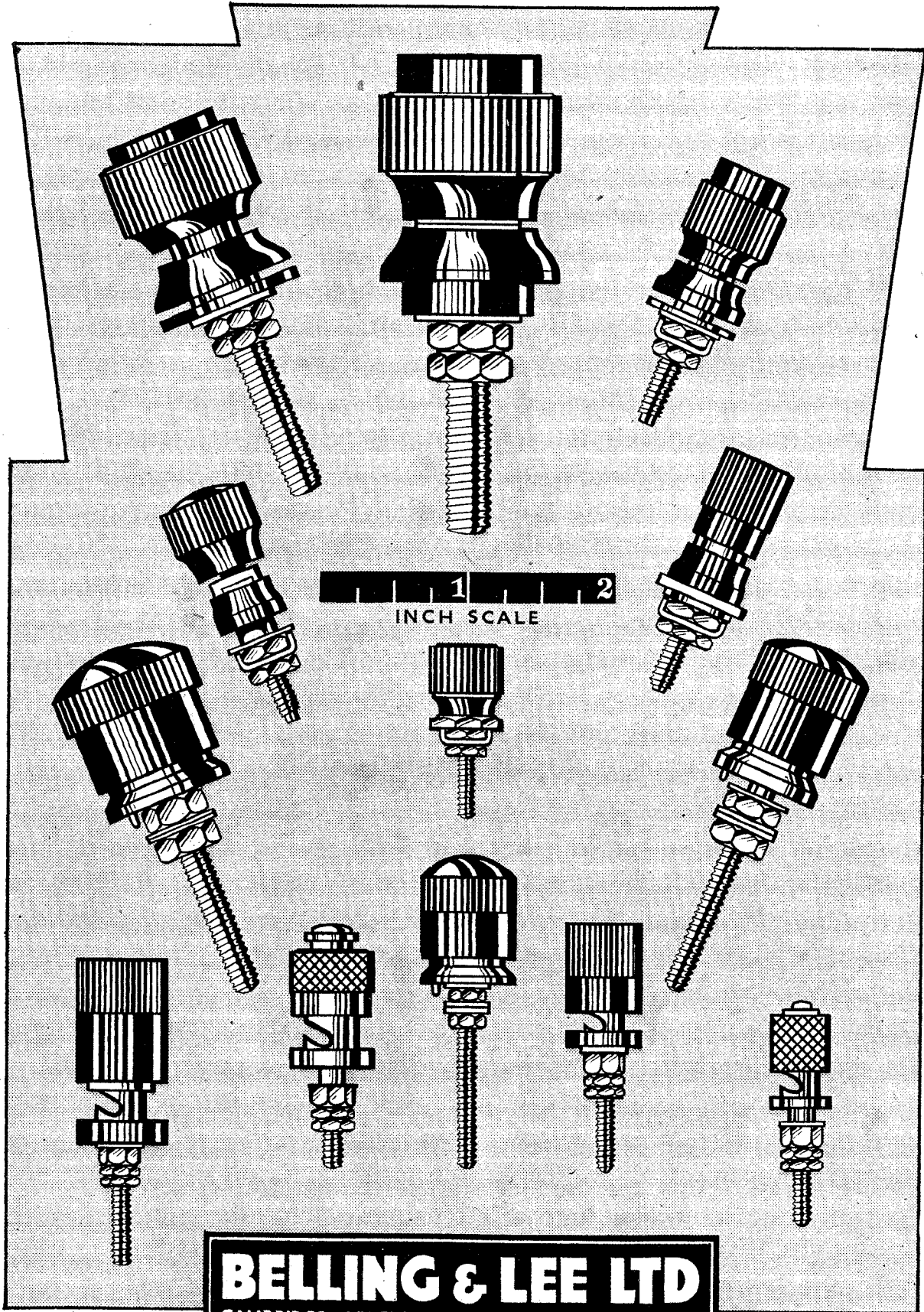J. BULL & SONS, Radio House, Melthorne Drive, Ruislip, Middx.



BELLING & LEE LTD
CAMBRIDGE ARTERIAL ROAD, ENFIELD, MIDDX

WEBB'S *Radio*

SPECIALITY:—

**MORSE EQUIPMENT
for Class-room and
individual practice:—**

Schools Type Oscillator (A.C. Mains) operates Loud Speaker or up to 50 pairs phones. Adjustable Note **£7 10 0**

Junior Oscillator (A.C. Mains) for three pairs phones **£2 5 0**

Battery-operated Audio Oscillator, Type B1, works on 2 volts only	27/6
Streamline Metal Key, U.S.A. pattern	6/6
G.P.O. Bar Type Practice Key	8/6
G.P.O. Bar Type Keys, first grade finish (2 contacts)	17/6
G.P.O. Bar Type Keys, first grade finish (3 contacts)	22/6
G.P.O. Bar Type Heavy Duty Operating Key (3 contacts)	28/6

COMPONENTS from stock:—

Push Back Insulated Flex (single)	doz. yds.	1/-
Screened Braided Wire (finest quality)	per yd.	9d.
Resistance Cord for A.C./D.C. Receivers (100 ohms per ft.)	per ft.	2/-
Potentiometers and volume controls—all usual values from stock at		4/6
Midget type Centralab at...		5/6
Collapsible Microphone Stands		42/-
4 1/2 in. Permanent Magnet "Rola" Loud Speakers		18/9
Goodman 8 in. Permanent Magnet		15/-
Output Transformers for above, tapped triode and pentode		5/6
A.C. Battery Chargers, output 2, 6 and 12 volts, 1 amp.		45/-

CERAMIC TUNING CONDENSERS

.00016	4/6
.0002	5/-
.0001	4/6

ALL EDDYSTONE
Components available,
but service requisitions must take
priority.

★ Additional charge of 1/- for postage and packing on orders below 10/-

WEBB'S RADIO

14 Soho Street, Oxford Street, London, W.1

Telephone: GERRARD 2089

Open 9 a.m. to 4 p.m. Sats., 9 a.m. to 12 noon

**KEYSTONE
OF POWER**

MASTERADIO VIBRATOR PACKS

Wherever Portable Power—sturdy, reliable, efficient—is required for Transmitters, Receivers, Amplifiers, etc., this Supply Unit is the most obvious choice.


Masteradio LTD GRAMS: MASTIOLA
PHONE: WATFORD 9885/9890
VIBRANT WORKS, WATFORD, HERTS.

Greenwood

TENAPLAS
EXTRUDED PLASTICS
REGISTERED TRADE MARK


We are pioneers in the manufacture of extruded plastics and our specialised knowledge is entirely at your service. If you believe extruded plastics will improve your products we shall be pleased to advise you.

TENAPLAS LTD.,
Head Office: 7 PARK LANE, LONDON, W.1




With all the Ocean for a Road

. . . . a ship ploughs its way to port. Often contact with the world seems all but lost through fog or gale. But thanks to radio, contact is *never* lost. Each ship, great or small, can receive whatever warnings, whatever orders, whatever news or encouragement its guardians afloat and ashore may send forth. Dubilier are proud to know that they are helping this great work, helping in the equipment which is bringing the ships home.

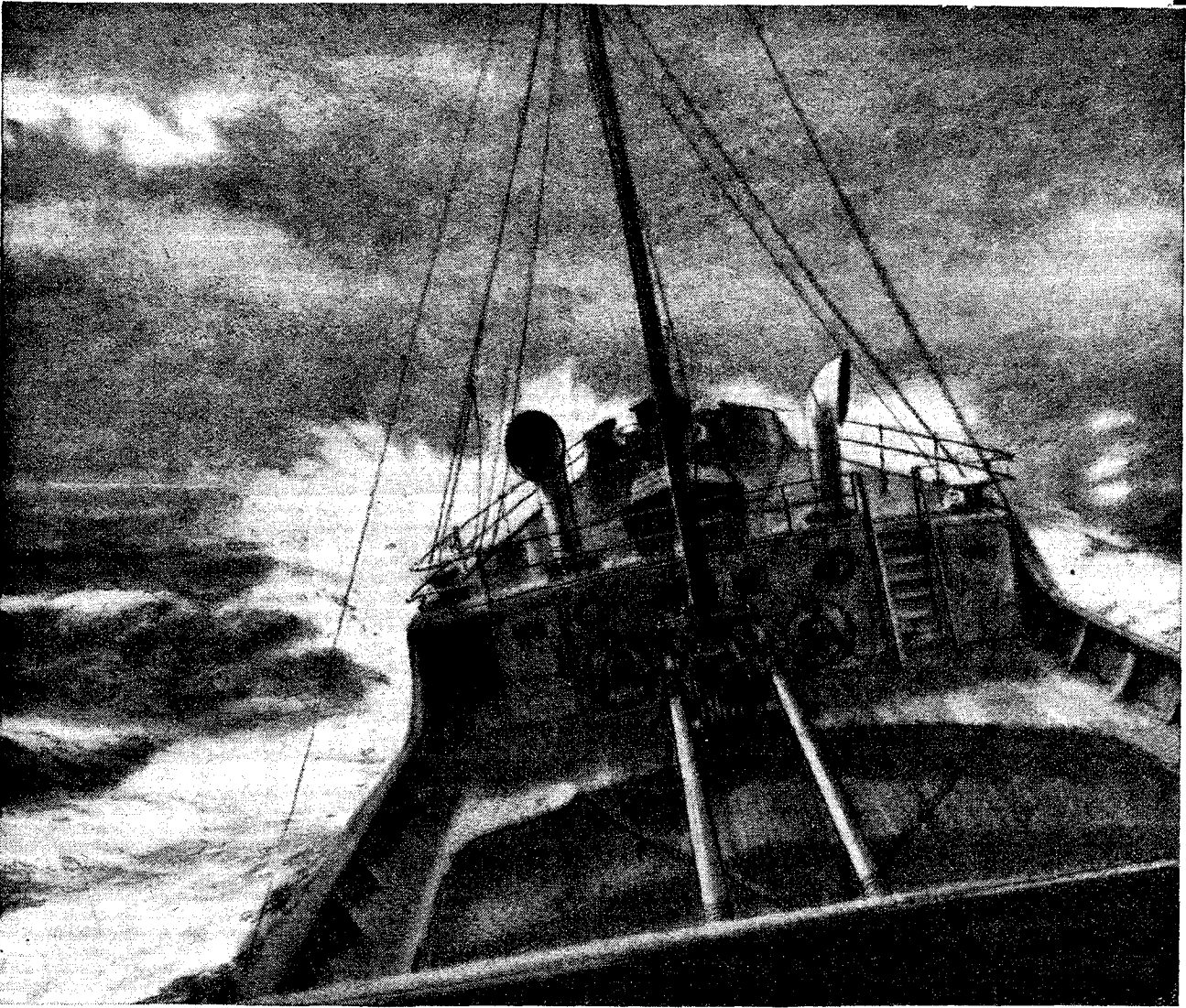

DUBILIER
CONDENSER CO. (1925) LTD.



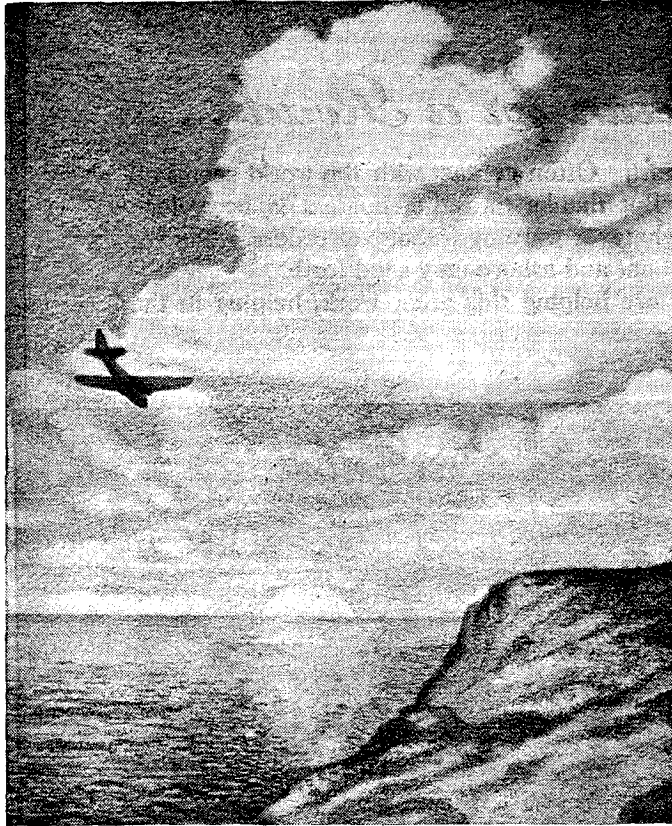


New horizons

The time will come when Goodmans' Loud-speakers will bring you news of a 'brave new world' in which we can accept your orders again and devote our energies and the accumulated experience of war years to giving you apparatus that will open up new horizons in the search for perfect sound reproduction.

GOODMANS
INDUSTRIES LIMITED

Lancelot Road, Wembley, Middx.

WHARFEDALE
GOLDEN CHASSIS

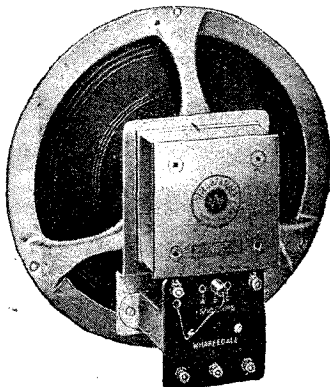


As supplied to the B.B.C.

Speech Coil 2-3 ohms :
Flux Density 10,000 lines,
7-8 watts • 10" Chassis

Although we are making more than ever of this excellent Loud Speaker the output is absorbed by the B.B.C. and other Priority users.

PRICE 70/-
(Less Transformer)


RESPONSE CURVE

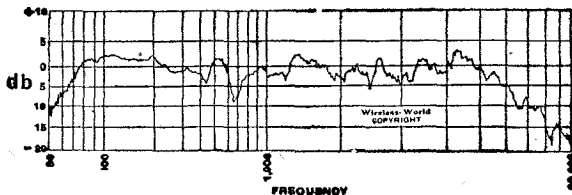

WHARFEDALE WIRELESS WORKS
SOLE PROPRIETOR : D. E. BRIGGS
HUTCHINSON LANE, BRIGHOUSE, YORKS.
PHONE : BRIGHOUSE 50. GRAMS : "WHARFDEL."



Transformers to
TROPICAL
specification

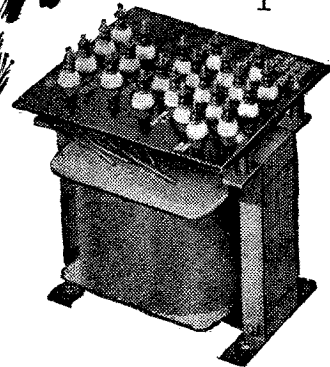

from
10 VA-10 kVA

Every precaution, including vacuum impregnation, special materials and exceptional care in manufacture, is taken to ensure that Woden Transformers made to tropical specification will give reliable service under the most arduous conditions.

WODEN Transformer Co.
THORNLEY STREET · WOLVERHAMPTON
TEL: WOLVERHAMPTON 22829

MAKERS OF TRANSFORMERS, POWER PACKS, & SPECIAL RECEIVING & TRANSMITTING APPARATUS

MINISTRY



OF SUPPLY

NON-FERROUS METALS ARE URGENTLY NEEDED

Upon them largely depend the accuracy, deadliness and efficiency of Britain's instruments of war. Practically all of them have to be imported across thousands of miles of dangerous seas, making heavy demands on shipping space.

Make a clean sweep of your unwanted COPPER, ZINC, LEAD, PEWTER, WHITE METAL BRASS AND BRONZE, ALUMINIUM SCRAP

The need for vast and increasing quantities of these metals must be met by a national search for everything made from them which is broken or serving no useful purpose.

WHAT TO SEARCH FOR

Here is a list of some of the important non-ferrous metal articles, parts and equipment likely to be found on your premises. Use it as a guide to your search for everything you can spare.

COPPER—cable, electrical parts and fittings, sheathing, tube, turnings, wire.

ZINC—sheet, cuttings.

LEAD—covered cable, pipe, sheet, solder.

WHITE METAL—anti-friction metal, plumbers jointings, solder waste.

BRASS—pipe, sheet, tube, turnings.

BRONZE—bearings, bushes, cocks, couplings, crown wheels, junction boxes, unions, valves.

ALUMINIUM SCRAP (and its alloys)—pipe, sheet, castings, tube, turnings.

HOW TO DISPOSE OF IT

- 1 Sell your non-ferrous scrap to a Merchant.
- 2 Or hand it in to a Local Authority Depot.
- 3 **SPECIAL COLLECTIONS** of amounts over **ONE TON** may be obtained by getting in touch with the nearest Demolition and Recovery Officer. If you don't know his name, write to The Ministry of Works & Planning, Lambeth Bridge House, London, S.E.1.

NOTE: Under the provisions of the Scrap Metal (No. 2) Order, 1942, if you are in possession of more than 3 tons of Scrap Metal, it is now an offence not to disclose the fact to The Ministry of Works & Planning, Lambeth Bridge House, London, S.E.1.

WANTED! INDUSTRIAL SALVAGE STEWARDS

Salvage is of such great and increasing importance that it should be made the personal responsibility of one particular individual in the various departments of every organisation. Appoint your own Industrial Salvage Stewards. Put them in sole charge of an intensive drive for

STILL MORE PAPER, RUBBER, RAGS, BONES, KITCHEN WASTE—AND METAL

◆ LINAGLOW LIMITED ◆

WATCH OUR ADVERTISEMENTS EVERY MONTH—IT WILL PAY YOU

We have secured the entire stocks of a famous manufacturer and offer these at from 33-45% below normal prices.

TUBULAR PAPER CONDENSERS, 500V., D.C. WORKING. .5 mfd., 16/- doz.; .25 mfd., 8/- doz.; .01, .02, .03, .001, .002, .003, .005 mfd., 6/- doz.; .0001, .0002, .0003, .0005 mfd., 4/- doz., etc., etc., or Parcel of 50 for £1/7/6. Equal Assortment. Minimum orders, 1 doz., any type.

FIXED CARBON RESISTORS. Wire Ends—Assorted and Useful Values. 1/- watt, 24/-; 1/2-watt, 30/-; 1-watt, 36/-; 2-watt, 55/-; 3-watt, 84/- per 100. Minimum orders 50 assorted. Assorted Parcel for £3. Contains 25 1/2-watt, 50 1/4-watt, 50 1-watt, 25 2-watt, 10 3-watt.

FIXED WIRE WOUND RESISTORS. Wire Ends.—Assorted and Useful Values. 4-watt, 110/-; 6-watt, 118/-; 8-watt, 135/-; 10-watt (800 ohm only), 150/- per 100. Minimum orders 50 Assorted.

HEAVY DUTY WIRE WOUND RESISTORS. Copper Ends. 8-watt, 100/25,000 ohm, 2/6 each; 12-watt, 900/40,000 ohm, 3/- each; 15-watt, 200/175,000 ohm, 3/6 each; 20-watt, 6,000, 7,000 and 8,000 only, 4/- each; 25-watt, 250/75,000 ohm, 5/6 each; 50-watt, 435/100,000 ohm, 7/- each.


TAPPED WIRE WOUND RESISTANCES. Special Offer. 25-watt, 375 ohm, tapped 125 and 250, 6/6 each; 50-watt, 840 ohm, tapped 600, 680 and 760, 8/- each.

ALUMINIUM CAN CONDENSERS. .01 500 v. D.C. 18/- doz.

Special Offer!

5-v. ALL-WAVE SUPERHET CHASSIS. Complete with VALVES and M.C. SPEAKER. **LATEST MODEL.**

DE LUXE

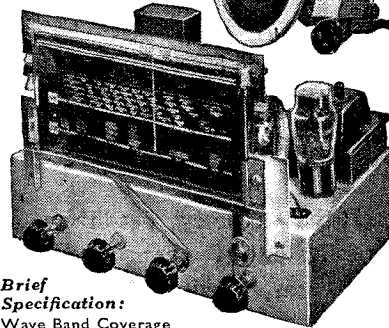

Brief

Specification:

Wave Band Coverage 18 m. to 2,000 metres, 5 watts output. Large 6" Glass Dial. Separate tone and volume controls. Extremely good selectivity and sensitivity. Really "Hot" on Short Waves. Heavy gauge steel Chassis.

£14.15.0

(Including Purchase Tax.)

Don't miss this opportunity. These prices cannot be repeated. All goods are brand new. Guaranteed best quality. Close Tolerance.

VOLUME AND TONE CONTROLS, with and without switch—suitable for all well-known makes of radio. 6 Assorted and useful Values for £1/7/6.

ELECTROLYTIC CONDENSERS. Tubular Paper. 25 x 12, 2/- each; 25 x 25, 2/6 each. Limited Quantity only.

SILVER MICA CONDENSERS. Flat Wire End—Assorted and Useful Values. 17/6 per 100 (not more than 5 alike).

I.F. AND AERIAL TRIMMERS. 12 Assorted and Useful Values for 2/6.

SUNDRIES

ELECTRIC APPLIANCE LEADS, 6ft. Long. With Connector one end for kettle, iron, radio, toaster, etc., Light adaptor or 2-pin plug other end, 5/9 each; Iron Connectors, 1/6 each; 2-Pin 5 amp. plugs, 12/- doz.; Insulating Tape (best qual. American), 3/- per lb.; MILLERS FALLS Radio Mechanic's Screw-drivers, 2/11 each.

CLEAR BULBS. 2.5, 15/9 per 100; 3.5, 20/9 per 100. Inc. Tax. Limited quantities only.

We cannot hold ourselves responsible for goods damaged or lost in transit.

NOTE.—All Orders C.O.D. or Cash with Order, carriage paid.

3, HAMPSTEAD LANE, LONDON, N.6. Phone: Mountview 9432.



NOBODY WANTS TO HANDLE IT!

It's one of those jobs bristling with difficulties, a job that it needs considerable courage to tackle at all. Never mind if the drawing has come back so often that it's wearing thin, let us see it—and if it can be stamped or pressed, we'll find a way of doing it. We make all sorts of small stampings and pressings to customer's specifications—and we specialise in the overcoming of tough propositions.

F. Dowler & Sons
ASTON BIRMINGHAM


CELESTION

CELESTION-AMPHENOL

valveholders are preferred by radio engineers because of their Strength, Efficiency, Uniform Contact and exceptional Insulation.

All standard British and American types are available.

AMPHENOL

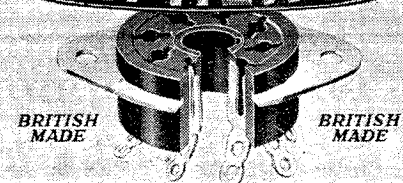


BRITISH MADE

BRITISH MADE

CELESTION LTD.

(Engineers)
KINGSTON-UPON-THAMES, SURREY.

Telephone: KINGston 5656-7-8.

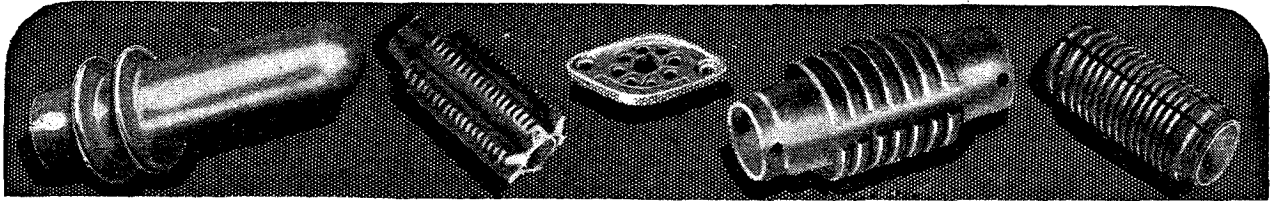

*Clear as a
Crystal*

**AND HERE IS
THE REASON..**

... the answer has been found in Bullers Low Loss Ceramics to the problem of Dielectric Loss in High Frequency circuits.


Years of laboratory research and development have brought these materials to a high degree of efficiency. To-day, they are in constant use for transmission and reception and play a vital part in maintaining communications under all conditions.

Made in Three Principal Materials.

FREQUELEX—An Insulating material of Low Dielectric Loss. For Coil Formers, Aerial Insulators, Valve Holders, etc.

PERMALEX—A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

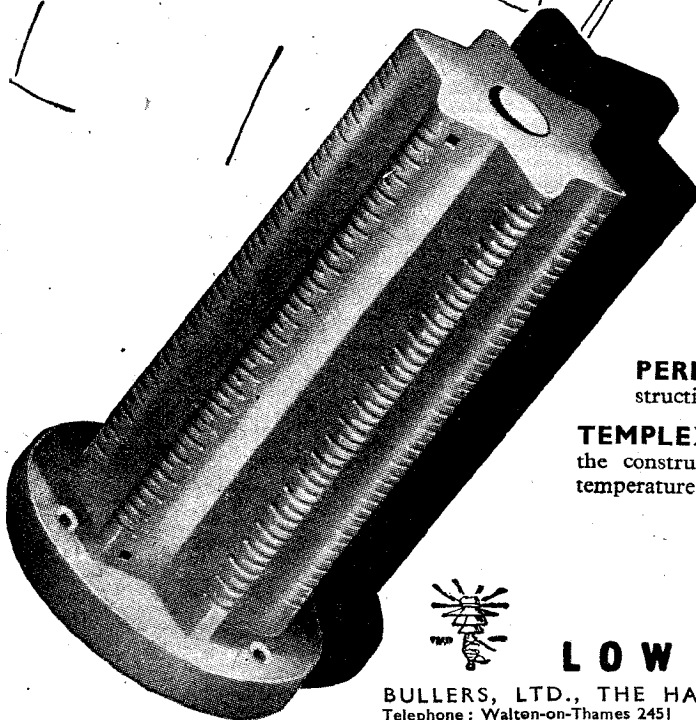
TEMPLEX—A condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.




Bullers


LOW LOSS CERAMICS

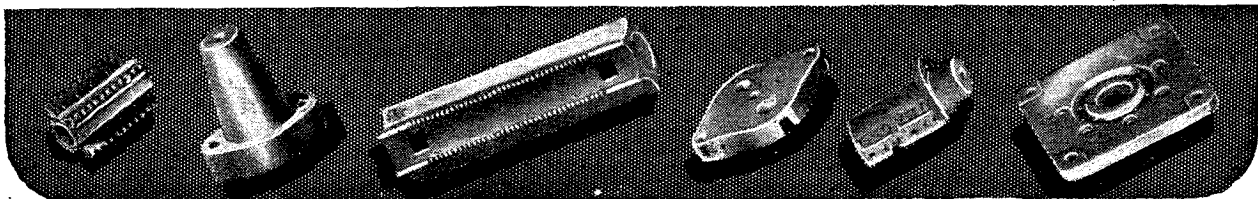BULLERS, LTD., THE HALL, OATLANDS DRIVE, WEYBRIDGE, SURREY
Telephone: Walton-on-Thames 2451
Manchester Office: 195 Deansgate, Manchester



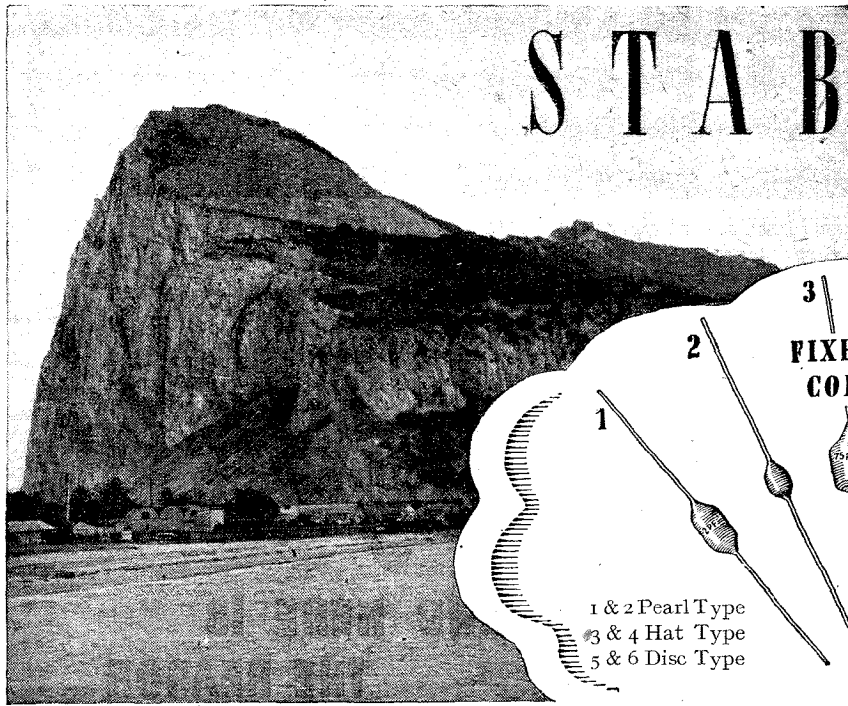

STABILITY

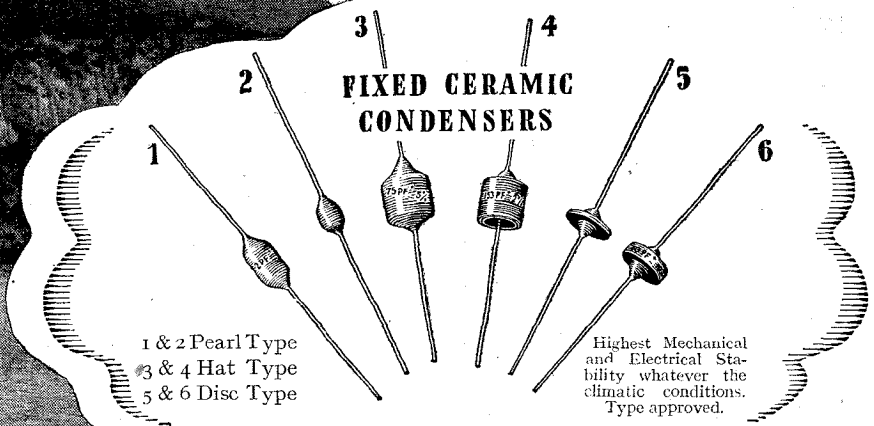

1 & 2 Pearl Type
3 & 4 Hat Type
5 & 6 Disc Type

Highest Mechanical and Electrical Stability whatever the climatic conditions. Type approved.



UNITED INSULATOR CO. LTD.


12-20 LAYSTALL STREET, LONDON, E.C.1

Phone: TERminus 7393

Grams: Calanel, Phone. London

The Pioneers of low-loss Ceramics

CERAMIC GOODS AND INSULATORS

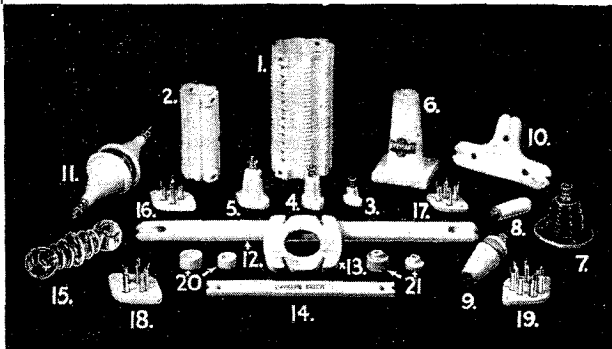

Our range of Ceramic goods and Insulators is most extensive. The selection available is not just confined to the 21 different lines illustrated above.

The latest addition to our range is the Raymart High Frequency Coil Former. This has a multitude of uses, in particular we would mention the making up of Aerial Coupling Units or Tapped Tank Coils.

Enquiries which are not from Government Departments and Traders should be accompanied by a stamped addressed reply envelope.

RAYMART

CRAFT A CREED

48, HOLLOWAY HEAD, BIRMINGHAM, 1

Cables: Raymart, Birmingham.

Telephone: Midland 3254.

DAGENITE

AND

PERTRIX

— the dependable


BATTERIES



FOR
RADIO, CARS
MOTOR CYCLES
COMMERCIAL
VEHICLES
ETC.

Sales Concessionaires:
HOLSUN BATTERIES LIMITED

137 Victoria Street, London, S.W.1

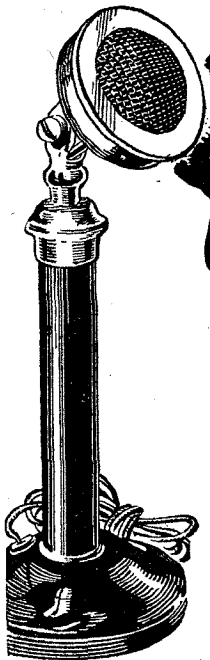

Piezo-Crystal Hand-Table MICROPHONE

for


Crystal-clear broadcasts

In factories, canteens, at public meetings, dances, etc., this Piezo-Crystal Microphone is unsurpassed for quality of speech and music. Fitted with the well-known Rothermel D104 microphone insert, the frequency response is remarkably uniform throughout the musical scale and the characteristic is practically level from 25 to 10,000 c.p.s. No energising current or transformer is required, therefore installation and operation are exceptionally easy. Equally convenient for hand or table use. All metal lacquer and chromium finish with adjustable mouthpiece. Price **£4-2-6**

Good Quality Components by PHILIPS

PHILIPS HIGH QUALITY SUPER SENSITIVE PERMANENT MAGNET SPEAKERS

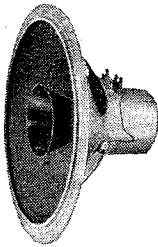These brand new speakers are fitted with concentrically mounted Hi-note Diffusers. 8½ in. cone. Complete with Pentode Transformer. Price **32/6**



PHILIPS HIGH VOLTAGE TRANSFORMERS


They are robust in construction; weight approx. 13 lb. Dimensions: 5½ × 5½ × 4½ in. Specification: 350-0-350 v., 70 m.a. Four tapplings giving 4 v. 3 amps., 6.3 v. 4 amps., 4 v. 0.65 amp. and 4,000 v. at 3 m.a. Input 100/250. Free wiring diagram. Carriage forward. Price **32/6**

PHILIPS WET ELECTROLYTIC CONDENSERS. Can Type

32 mfd., 450v. working ... each **10/3**
35 mfd., 350v. working ... each **9/6**
8 mfd., 320v. working ... each **6/6**

PHILIPS TRIMMER CONDENSERS

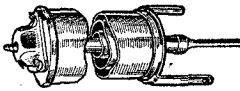Non-drift air dielectric, 60 mmfds, suitable for S.W. work. Price **1/3**



PHILIPS DOUBLE WET ELECTROLYTIC CONDENSERS

15 mfd. at 275v., and 50 mfd. at 320v. ... each **12/6**

PHILIPS WIRE WOUND POTMETERS


450 ohms and 10,000 ohms ... each **6/6**

PHILIPS CARBON POTMETERS

700,000 ohms, with 2-pole M and B Switch 100,000 ohms, less switch ... **4/6** ... **3/6**


PHILIPS SMOOTHING CHOKES

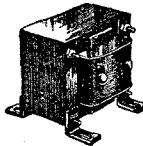Brand new, well-built chokes, 80 ohms D.C. resistance 400/120 m.a. Core size: 2in. × 1½ in. × 1in. ... each **5/6**
Also 400 ohms D.C. resistance 60 m.a. Core size: 1½in. × 1in. × ¾in. ... each **3/6**



PHILIPS CONCENTRIC SPIRAL VANE VARIABLE CONDENSERS

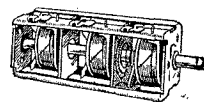
3-Gang 0.0005 mfd. without trimmers. As used in Philips well-known Push-Button receivers. Price **4/6**



ALSO

PUSH-BUTTON CONDENSERS

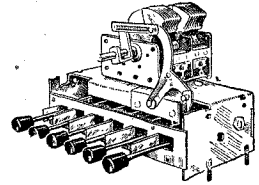
A chance for Experimenters! 0.0005 mfd. 2-gang, 6 push-button Superhet Condensers. Mechanical cam lever type (not trimmer type), easily adjustable, to receive any six stations desired. Excellent workmanship. A product of General Instrument Corp., U.S.A. A real bargain. Price **10/6**



LOUDSPEAKERS

ROLA PERMANENT MAGNET

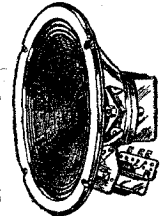New, 10in. M.C. with transformer for power, super power and pentode output ... **39/6**
Rola P.M. 5in. without transformer **25/-**



CELESTION

5in. P.M. moving coil, pentode output. New ... **25/6**


TELEPHONE HAND-PIECE

Combined Transmitter and Receiver, as illustrated. All in good working order. Price **7/6**




CELESTION AMPHENOL VALVE HOLDERS

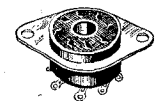The best quality obtainable
8-pin International Octal
Price **1/3** each.




OAK SWITCHES

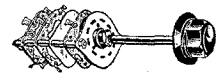2½in. spindle. Complete with knob:
4-way, 2-bank with connecting block ... **4/6**
4-way, 2-bank ... **3/9**



G.P.O. MORSE KEY AND BUZZER UNIT

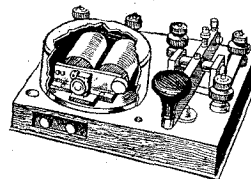

We have only a small number of these instruments left. Made for professional use. All parts of heavy solid brass mounted on mahogany base. The Key is fitted with platinum contacts. An excellent opportunity for those requiring a robust unit which will give years of service. Price **40/-**

BAIRD T26 TELEVISION RECEIVERS

Brand new. See November issue for full details. Price **£35.10.0**

MULLARD EA50 DIODES

60 mm. × 12 mm. overall. 6.3v. heater at 15 amp. Each **10/6**


For details of other numerous offers, see our Economy Column on page 15, November issue.

YES
When sending your orders you must
ADD POSTAGE

LONDON CENTRAL RADIO STORES

23, LISLE ST. GERrard 2969 LONDON, W.C.2

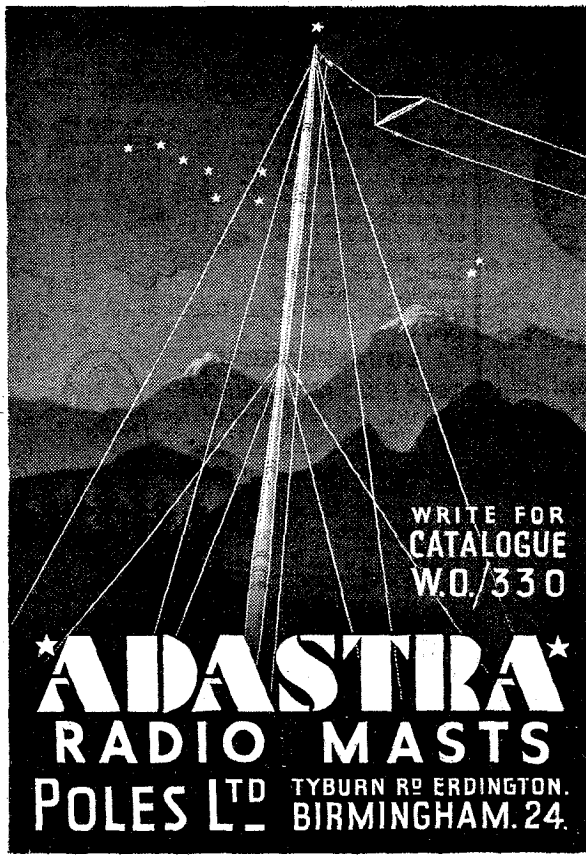NO
We are sorry, but we cannot accept
C.O.D. ORDERS




WRITE FOR
CATALOGUE
W.O./330

ADASTRA
RADIO MASTS
POLES LTD TYBURN RD ERDINGTON,
BIRMINGHAM. 24.

Enquiries should be accompanied by Government Priority Reference



ELECTRIC SOLDERING IRONS

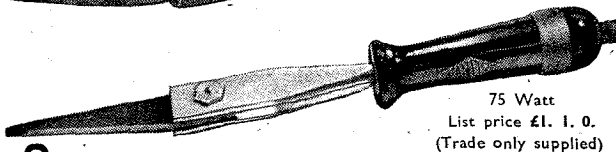

Stanelco Electric Soldering Irons have been designed for industrial purposes. Heating elements and copper bits can easily be fitted when replacements are necessary. The 150 watt type is fitted with a general purpose bit and the 75 watt type is available with either long, short, or hammer bit. Each iron, fitted with 5½ feet of 3-core flexible cable, is available for 100/110, 200/220, 230/250 voltages.

When ordering, the voltage and type of bit required should be specified.

RESIN CORED SOLDER, SOLDER WIRE, Etc.

Stanelco Products

PROPRIETORS: STANDARD TELEPHONES AND CABLES LIMITED
FERNDOWN, NORTHWOOD HILLS, NORTHWOOD, MIDDLESEX
Telephone: PINNER 4885

Electronic Engineering Services, Ltd.

24 STANLEY ROAD HEATON MOOR
STOCKPORT
TELEPHONE HEATONMOOR 3107

SOLE DISTRIBUTORS OF
AMERICAN EQUIPMENT

MADE BY

RADIO ENGINEERING LABORATORIES
S.W. TRANSMITTERS, A.M. & F.M.
LORAIN COUNTY RADIO CORPORATION
AUTOMATIC TRANSMITTER-RECEIVERS
BRUSH DEVELOPMENT COMPANY
PIEZO-ELECTRIC DEVICES
MICROTUBE LABORATORIES
MIDGET TUBES
ACME ELECTRIC & MANUFACTURING CO.
SPECIFICATION TRANSFORMERS

THROUGH OUR AMERICAN ORGANISATION, WE ARE
OFTEN ABLE TO LOCATE SOURCES OF SUPPLY FOR SPECIAL
COMPONENTS UNOBTAINABLE IN THIS COUNTRY.
SEND US YOUR ENQUIRIES.

ROLA

LOUD SPEAKERS

THE WORLD'S FINEST REPRODUCERS

TRANSFORMER LAMINATIONS

Core Widths $\frac{3}{8}$ " to 1½" (E's and I's.)



EIGHT STOCK SIZES

A Comprehensive Bulletin together with details of Associated Covers and Clamps with design data will be sent to manufacturers on request.

BRITISH ROLA LIMITED

MINERVA ROAD · PARK ROYAL · N.W.10 · WILLODEN 4322

SYMBOLS OF PRECISION

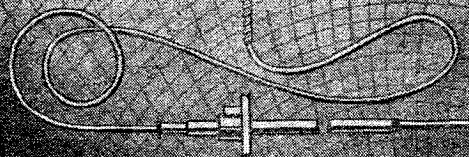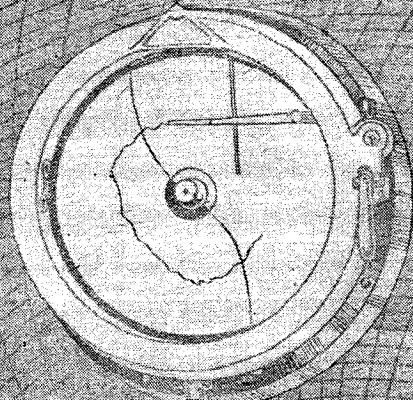

MAZDA

RADIO
VALVES

Mazda Radio Valves are manufactured in Gl. Britain for the British Thomson-Houston Co. Ltd., London & Rugby, and distributed by

THE EDISON SWAN ELECTRIC CO. LTD  155 CHARING CROSS RD., LONDON, W.C.2

For full particulars write to Technical Service Department

CO-AX CABLES

FOR HIGH FREQUENCIES

Unequaled

In performance * range of characteristics *

AIR-Insulated and flexible

CO-AX Valve Connectors
Very low and constant capacity.

TELEQUIPMENT CO.
16, THE HIGHWAY, BEACONSFIELD, BUCKS.

THREE USEFUL BOOKS

RADIO DESIGNER'S HANDBOOK

Edited by Langford Smith.. Fully illustrated with diagrams.

Useful to all Radio Engineers, experimenters and service mechanics.

Price 10/6. Post free 11/1

* * *

RADIO LABORATORY HANDBOOK

by M. G. Scroggie. Fully illustrated. Useful to all radio electricians.

Price 12/6. Post free 12/10

* * *

WIRELESS SERVICING MANUAL

by W. T. Cocking (of the *Wireless World*). Fully illustrated with diagrams.

Price 7/6. Post free 7/10

* * *

Order and send remittance to :


SHERRATT & HUGHES,
Booksellers
34, CROSS STREET, MANCHESTER

TUNGSRAM VALVES

Our production of Radio Valves is both large and continuous. So, too, is the demand for them for urgent purposes. Some are available for domestic use, but the range is necessarily limited. You may be assured of our willing help whenever possible.

Announcement of

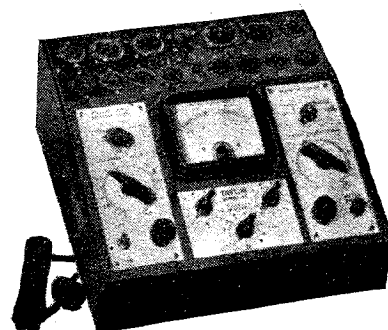BRITISH TUNGSRAM RADIO WORKS LTD., WEST ROAD, TOTTENHAM, N.17



TAYLOR

MUTUAL CONDUCTANCE

VALVE TESTER

MODEL 45

A robust, compact and accurate test instrument essential to all radio manufacturers, servicemen and dealers.

Operates on A.C. 200/250 volts, 40/100 cycles.

PRICE

£15.15.0

Portable Model 45P, with compartment for tools, £17/6/6.

Taylor Valve Testers are supplied with a book of instructions, including wiring diagram, a valve chart covering over 1,000 types of valves, and a grid connecting lead.

Further details on request.

BRITISH MADE AND GUARANTEED 6 MONTHS

SPECIFICATION

Mutual Conductance. Accurate and quick measurements are available for practically all British, American and Continental valves, from 0.25 to 24 mA/V.

Valveholders. 17 holders cover all modern types and include Loktal, Octal, Mazda Octal and side contact types.

Tests. Additional tests are available for Filament Continuity, Electrode Shorts, Cathode Leakage and Rectifier and Diode Emission.

Each section of full wave Rectifiers,* Double Diodes, Frequency Changers, etc., are tested independently. Anode and Screen Volts are adjustable to suit the valve under test, and a choice of 17 Filament Volts are available.

Meter. The meter has separate scales for Mutual Conductance, Cathode Leakage, and also a coloured scale for Replace, ? , Good.

TAYLOR

ELECTRICAL INSTRUMENTS LTD.
419-422, Montrose Avenue, Slough, Bucks.
Telephone : SLOUGH 21381

COIL WINDING MACHINES

TAPING MACHINES

WIRE COVERING MACHINES

ARMATURE AND STATOR

COIL WINDERS

NEVILLE'S

Contractors to
the Admiralty and
other Government Departments




NEVILLE'S (LIVERPOOL) LIMITED

SIMMONDS TOWER · GREAT WEST ROAD · LONDON

Please address all enquiries to Western Office:
City House, St. Stephen Street, Bristol, 1.

A DIVISION OF THE SIMMONDS GROUP

From night club  to night shift

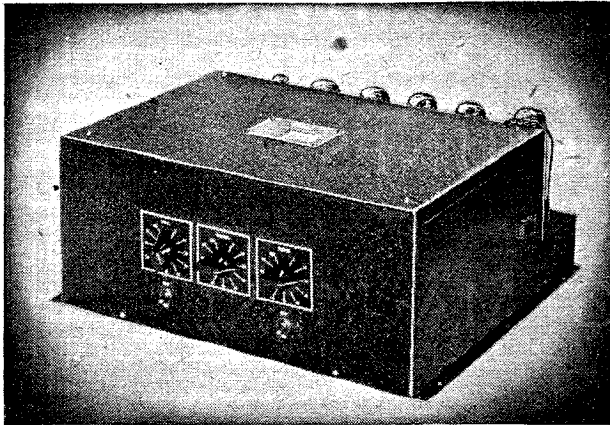

they all trust **TRIX** Quality SOUND Equipment

Night clubs then and night shifts now have one thing in common—their trust in Trix Sound Equipment. From the Trix range there is equipment to serve widely divergent needs with equal reliability.

Amplifier (illustrated), Model T.633. Undistorted output 30 watts. Suitable for audiences of up to several thousand people.

TRIX ELECTRICAL CO. LTD.
65, Bolsover St., London, W.1.

Phon.: EUS 5471/2. Grams: Trizadio, Wcso, London. AVAILABLE FOR PRIORITY WORK

M.R. SUPPLIES

invite your urgent attention to the following offers in first-class RADIO and ELECTRICAL MATERIAL. Immediate delivery from present stock. All prices strictly nett cash.

MEASURING INSTRUMENTS. Remarkable opportunity for high-grade Milliammeters and Ammeters by Weston, Ferranti, Elliott, etc. (We cannot undertake to select particular maker). Housing 2 1/2 in. square black bakelite, dial 1 1/2 in. diameter, flush panel requiring 2 1/2 in. mounting hole, back terminals. **MOVING COIL MILLIAMMETERS**, deflection 0/50 m.a., 32/6. Deflection 0/150 m.a., 32/6. **THERMO-COUPLE AMMETERS**, for any frequency and D.C., 0/2.5 amp., 0/3.5 amp. (two models), either 39/6. These meters are secondhand ex Govt., in new condition and all laboratory tested, and guaranteed accurate.

SLIDING RHEOSTATS, by prominent London makers. Fitted overhead spiral drive with knob control, 6 ohms 6 amps., 42/-. Also same type, 0.4 ohm 25 amps., same price. Various other ratings on view. Also our own well-known model without spiral drive, all 100-watt capacity, in following range: 10 ohms 3 amps., 50 ohms 1.5 amp., 100 ohms 1 amp., 200 ohms 0.7 amp. and 400 ohms 0.5 amp., fully enclosed, any one 21/-. **HEADPHONES**, by Ericsson, complete with headgear, 2,000 ohms. Brand new maker-boxed, 25/- pair. Also a few secondhand, perfect, 12/6 pair.

SMALL GEARED MOTORS, constant speed induction, for recording instruments, process timing, etc., 200/250v. A.C. final speed variable from 1 to 6 r.p.m., low torque only. In metal housing 4 1/2 in. dia., with flex and plug, 32/6 each, last few.

INDUSTRIAL LOUDSPEAKERS, by G.E.C. Opportunity: ex stock. Junior model only now available. Housed in 9 in. grey enamelled metal drum with front and rear grille and mounting bracket, fitted transformer for multi-matching. Handling up to 5 watts and suitable also for extension speaker for any receiver, 45/- (1/6 packing and post).

ROTHERMEL-BRUSH PIEZO-CRYSTAL MICROPHONES, well-housed with knuckle-joint for angle adjustment. Response level to 8,000 c/s. Output level—60 db. Fitted 6 ft. screened lead, 72/6. **FLOOR STANDS** to suit, collapsible type, folding to 2ft. and extending to 5ft. 6 in., 37/6.

STEP-DOWN TRANSFORMERS for chargers, models, 1v. lighting, etc., primary 200/250v. (tapped) and sec. tapped 7. 11. and 15v. at 1.5 amp., 14/6.

MERCURY SWITCHES, S.P.C.O., tube 2in. long, with bead-insulated leads, capacity 6 amps., 4/9.

RELAYS, new compact model with powerful electro-magnetic action, operating from 4 to 12v. D.C. and breaking 6 amps., 8/6. Also London, operating from 12v. D.C. or 50v. A.C., 10 amp. break, 2-point silver contact switch, in steel housing, 35/-. **ELECTRIC SOLDERING IRONS** (S.T.C.). We only offer the best industrial types. All voltages in stock. 100/110, 200/220 and 230/250v., 75 watt with 4in. pointed bit, 21/-. Also same make with massive flat bit, 150 watts, 230/250v., 32/6.

RESIN-CORED SOLDER, highest tin content. 40 per cent. tin, on 1 lb. reels, 4/6 per reel.

SHADOW TUNING INDICATORS (Philco). Suitable for any set or for adapting to many other uses, meter, relay, polarity indicator, etc., resistance of wire-wound coil, 1,000 ohms, complete with clip for bulb, 1/8.

G.P.O. MICROPHONES, mounted, with diaphragm, 2/11. **CYLDON** .0005 variable **CONDENSERS**, 3/3. **G.E.C. INTERVAL TRANSFORMERS**, Hilux model, ratio 3/1, 5/-.

The following items are offered to CALLERS ONLY.

G.E.C. PROJECTOR P.A. SPEAKERS, with 8-watt P.M. Projector Unit and 42in. Metal Horn, complete, 49. Opportunity from stock.

ALL-STEEL TOOL or AMPLIFIER RACKS. Height 30in. with three strong trays, each 16 by 15in., sprayed black, 27/6.

D.C. CHARGING PANELS, with resistances, high-grade meters, etc., in fine new condition, best makes, various prices—please inspect.

Please include sufficient for packing and postage—any excess will be refunded.

M. R. SUPPLIES, 68, New Oxford St., London, W.C.1
(Phone: MUSeum 2958)

B.I. RADIO MATERIALS

We have had a long experience in the manufacture of all kinds of Cables and Wires, Static Condensers, Insulators and Iron Work, Telephone Cords and Copper Earthing Rods, for Radio use.



U.K. Regd. Trade Mark.

BRITISH INSULATED CABLES LTD.
CABLE MAKERS AND ELECTRICAL ENGINEERS
Head Office:
PRESCOT, LANCS. Tel. No. PRESCOT 6571

HIVAC
THE SCIENTIFIC VALVE
BRITISH MADE

Specialists in **MIDGET VALVES**

HIVAC LIMITED
Greenhill Crescent,
Harrow on the Hill, Middx.
Telephone: Harrow 0895.

COSMOCORD CRYSTAL PICK-UP SERIES III

It is regretted that production is severely curtailed and only very limited supplies are available through existing channels.

Sole Selling Agents :

SALE, TILNEY & Co. LTD.
3, LLOYD'S AVENUE, LONDON, E.C.3
Phone : ROYal 4811


SERVICE ON COSMOCORD CRYSTAL PICK-UPS IS MAINTAINED AS HITHERTO

Owing to lack of replacement parts and shortage of labour it is regretted that service on all other products and apparatus must be discontinued.

THINGS TO COME— HIGH FIDELITY REPRODUCTION

Are you interested? If so, will you kindly forward your name and address to

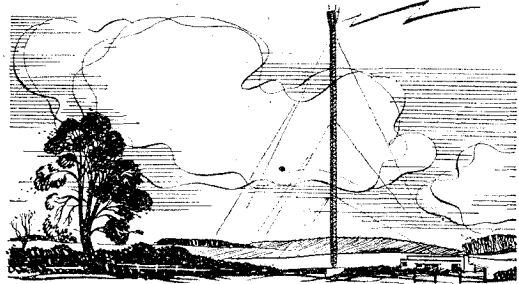COSMOCORD LTD.
SERVICE DEPT.
700, GREAT CAMBRIDGE ROAD,
ENFIELD, MIDDLESEX



Things to come



IN 1939 we were able to claim to be the largest U.K. suppliers of fixed condenser replacements, with unequalled range and variety of products.

In nineteen when radio and other electrical services return to their right use for the benefit of mankind and when the pace of technical improvement will be greatly accelerated, we shall be immediately ready to resume our cordial co-operation with the distributing trade in meeting the great public demand.

TRADE **HUNTS** MARK

*The
Home of Condensers*

Established 1901

Advt. of A. H. HUNT, Ltd., London, S.W.18



Battle of Wits

IT takes experience and a good head to ride the production problems of today. By good fortune the emergency is bringing into the saddle brains and ability equal to the task.

Certainly the Simmonds Organization—youthful, unconventional, dynamic—irresistibly attracts brilliant men and women, but the proof of the pudding lies in the many parts played by the products of the Simmonds Organization in widely diverse fields of essential production. There each day they are successfully introducing new methods to quicken the national pace.

SIMMONDS

THE SIMMONDS "WAS" NUT
SIMMONDS-CORSEY CONTROLS
SIMMONDS CONTENTS GAUGES
FOR AIRCRAFT.
SIMMONDS POSITION INDICATORS
SIMMONDS ELECTRIC TEMPERATURE
AND PRESSURE GAUGES
SIMMONDS AIRCRAFT FLOORING



SPIRE "WAS" NUTS
FRAM OIL & ENGINE CLEANER
SIMMONDS INDUSTRIAL AND
MARINE CONTENTS GAUGES
SIMMONDS JOINTING COMPOUND
SIMMONDS CRYSTAL UNITS
SIMMONDS-GOUDIME
NAVIGATIONAL INSTRUMENTS

SIMMONDS AEROCESSORIES LTD

A COMPANY OF THE SIMMONDS GROUP
LONDON · MELBOURNE · PARIS · NEW YORK.

P.I.T.

ALL ENQUIRIES TO GREAT WEST ROAD, LONDON.

Wireless World

Radio • Electronics • Electro-Acoustics

32nd YEAR OF PUBLICATION

DECEMBER 1942

Proprietors :
ILIFFE & SONS LTD.

Managing Editor :
HUGH S. POOCK,
M.I.E.E.

Editor :
H. F. SMITH.

Editorial, Advertising
and Publishing Offices :
DORSET HOUSE,
STAMFORD STREET,
LONDON, S.E.1.

Telephone:
Waterloo 3333 (35 lines).

Telegrams:
"Ethaworld, Sedist, London."

△

**PUBLISHED
MONTHLY**

Price: 1/3

(Publication date 20th
of preceding month)

Subscription Rate
Home and Abroad
17/- per annum.

EDITORIAL	277
DESIGNING A RESISTANCE-CAPACITY OSCIL- LATOR. By R. C. Whitehead	278
TRAINING SIGNAL INSTRUCTORS	283
LAMINATION DESIGN. By N. Partridge, Ph.D., B.Sc. (Eng.), M.I.E.E. ..	286
LETTERS TO THE EDITOR	290
PHYSICAL FOUNDATIONS OF RADIO.—IV: Com- posite Cathodes, Photosensitive Surfaces, Cold Emission. By Martin Johnson, D.Sc.	291
INSTRUMENTS.—VIII: Multivibrators. By W. H. Cazaly	294
RECENT INVENTIONS	298
RANDOM RADIATIONS. By "Diallist"	299
"WIRELESS WORLD" BRAINS TRUST	300
WORLD OF WIRELESS	302
NEWS IN ENGLISH FROM ABROAD	303

Branch Offices :

COVENTRY:

8-10, Corporation Street.
Telephone: Coventry 5210.
Telegrams: "Autocar, Coventry."

BIRMINGHAM:

Guildhall Buildings,
Navigation Street, 2.

Telephone:
Midland 2971 (5 lines).

Telegrams:
"Autopress, Birmingham."

MANCHESTER:

260, Deansgate, 3.

Telephone:
Blackfriars 4412 (4 lines).

Telegrams:
"Iliffe, Manchester."

GLASGOW:

26B, Renfield Street, C.2.

Telephone: Central 4857.
Telegrams: "Iliffe, Glasgow."

△


*As many of the circuits and
apparatus described in these
pages are covered by patents,
readers are advised before
making use of them, to satisfy
themselves that they would
not be infringing patents.*

Exclusive features

of the
'STRATOSIL'
series of
**SEALED
VIBRATORS**
for use at all altitudes


- 1 All steel construction—even to the rivets—ensuring uniform expansion under extremes of temperature.
- 2 Reed driving coil—wound on a bakelite moulded bobbin to meet all climatic conditions.
- 3 Metal can, sponge rubber lined—Acoustically and electrically shielding the vibrator.
- 4 Driving contact of non-tarnishable precious metal—ensuring starting under the lightest of pressures and voltages.
- 5 Contacts ground almost to optical limits.
- 6 Stack assembly. Mica and steel only are used.
- 7 International Octal base sealed by the WEARITE STRATOSIL process.

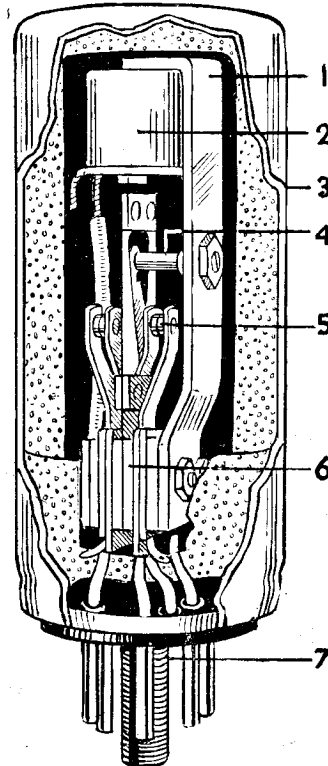Embodying "Oak Manufacturing Co.'s"
patent's 450470, etc.



WRIGHT & WEAIRE LTD.

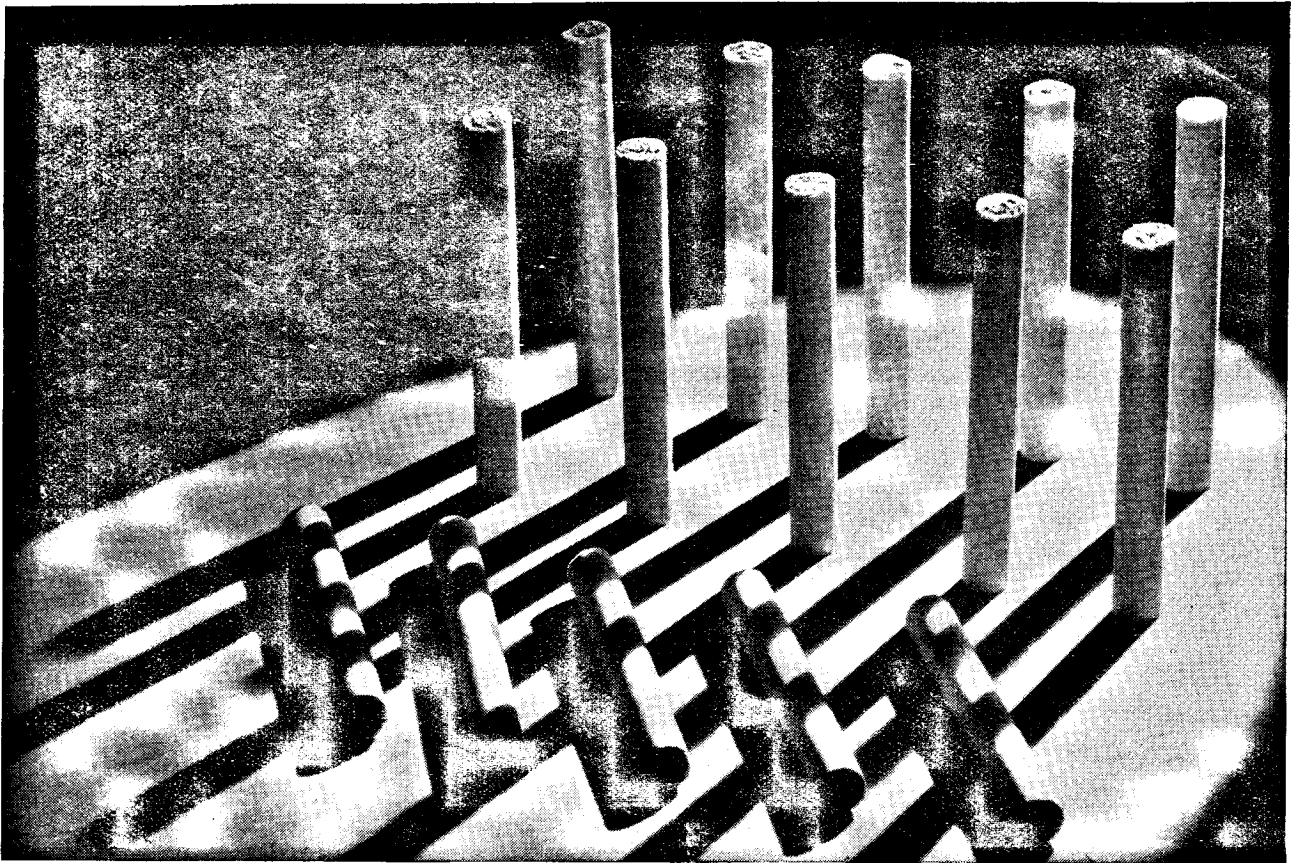HIGH ROAD, TOTTENHAM, N.17. Telephones: TOTtenham 3847-8-9



Valves and Cigarettes

In the processing of tobacco before it is made into cigarettes, it was found necessary to maintain a close control of the room temperature.

An essential requirement of the controlling equipment was that it should be entirely automatic in action. Continuity in the process was also of vital importance, and provision had therefore to be made to guard against a temporary break-down in the power supply.

Mullard Valves made it possible to design an

electrical controlling device which maintained the temperature within the necessary close limits, despite large fluctuations in the supply voltage and a change-over from the A.C. supply mains to an auxiliary source of D.C. supply.

This is typical of the specialised problems of control which arise in almost every industry; and the fact that the thermionic valve so often provides the solution is because Mullard have the right valve for the purpose.

MULLARD
THE MASTER VALVE

A Valve for Every Purpose

DOMESTIC · COMMERCIAL · INDUSTRIAL · SCIENTIFIC · MEDICAL · EXPERIMENTAL

THE MULLARD WIRELESS SERVICE COMPANY LIMITED, CENTURY HOUSE, SHAFESBURY AVENUE, LONDON, W.C.2. (45)

Wireless World

Radio • Electronics • Electro-Acoustics

Vol. XLVIII. No. 12

DECEMBER 1942

Price 1s. 3d.

Classification of Frequencies

Need for a Universal System

PRESENT-DAY trends towards the use of higher and higher frequencies accentuate the need for some system of classification that is explicit and precise and at the same time sufficiently simple and easily memorised to be used by all wireless technicians in their daily work. Such expressions as "very high frequencies" and "ultra-high frequencies" are at best ambiguous and clumsy, and have almost lost what little meaning they ever had. No useful purpose is served by what a correspondent recently described as a hectic search for more "hypers" and "supers."

So far as the nomenclature of wavebands is concerned, it seems hard to improve on the system agreed upon in 1937 by the International Radio Communications Conference (C.C.I.R.). It was advocated by Dr. Smith-Rose, Chairman of the I.E.E. Wireless Section, writing in *Wireless Engineer*, and is given below.

Although some of the metric units employed are not in common use, particularly in this country, the C.C.I.R. system does in most cases divide up the wavebands at those natural boundaries where changes in methods of propagation or transmission and reception technique are known to occur. The table has the additional advantage that it may be extended downwards to embrace the infra-red and visual parts of the spectrum. But most technicians now think, talk and write in terms of frequency, and so any wavelength classification,

however good in itself, fails to satisfy their needs completely. The frequency equivalents of the C.C.I.R. wavebands are not particularly difficult to memorise, though they cannot fairly be described as mnemonic.

For working in terms of frequency, a useful system of nomenclature is that first suggested by B. C. Fleming-Williams in *Wireless Engineer* for May, 1942. The system, which embraces both audio and radio frequencies, is quite simple. Each band is given a number; that number may be found by expressing a frequency (in cycles per second) as a number between 1 and 10 multiplied by a power of ten. The band number is given by that power of ten. For example, medium frequencies between 10^5 c/s and 10^6 c/s are in Band 5. The complete table of "power of ten" band numbers follows:—

Band No.	Frequency band	Approx. equivalents in present system
0	1-10 c/s.	
1	10-100 c/s.	Bass register
2	100-1,000 c/s.	Middle register
3	1,000-10,000 c/s.	Top or treble register
4	10-100 kc/s	Long-wave band.
5	100-1,000 kc/s.	Medium-wave band.
6	1-10 Mc/s.	Short-wave band.
7	10-100 Mc/s.	VHF
8	100-1,000 Mc/s.	UHF
9	1,000-10,000 Mc/s.	Micro-wave or cm.-wave band.
10	10,000-100,000 Mc/s.	Millimetre-wave band.

It will be seen that the "power of ten" system, like that devised by the C.C.I.R., gives no convenient and easily memorised correspondence between frequency bands and wavebands. That is perhaps no great objection if one ordinarily thinks in terms of frequency. But in dealing with such things as aerials and wave-guides it is often necessary to work in wavelengths.

At first sight it seems almost impossible to devise a universally acceptable classification applying both to frequencies and wavelengths, but it would be well worth while devoting some thought to the task.

Designation of waves in terms of wavelengths	Wavelength in metres	Designation of waves in frequencies	Frequency in kilocycles per sec.
Myriametre	Above 10,000	Very low	Below 30
Kilometre	10,000-1,000	Low	30-300
Hectometre	1,000-100	Intermediate	300-3,000
Dekametre	100-10	High	3,000-30,000
Metre	10-1	Very high	30,000-300,000
Decimetre	1-0.1	Ultra-high	300,000-3,000,000
Centimetre	0.1-0.01	Super-high	3,000,000-30,000,000

RESISTANCE-CAPACITY OSCILLATOR

Covering Frequencies from 40 to 13,000 c/s in Four Ranges

WHEN an oscillator is required to have a frequency range which will cover the whole of the audio-frequency spectrum, the beat-frequency principle is usually employed. Simple types of BF oscillator are, however, liable to suffer from a number of troubles, and these prompted the writer to design a resistance-capacity oscillator.

The RC oscillator operates on the following principle. If a suitable chain comprising maintaining amplifier and

By

R. C. WHITEHEAD

two effects cancelling out at the operating frequency only. Some suitable basic circuits are shown in Figs. 1, 2 and 3. For various reasons the 180-degree phase shifter was chosen as being the most suitable in the present instance.

To determine how the frequency

C or R change is 10 to 1, the variation of frequency will be 1 to 10, and not 1 to $\sqrt{10}$ as occurs when C or L is varied in an LC oscillator. This frequency variation characteristic necessitates the use of components having very stable circuit values in order to maintain good frequency stability.

The AF spectrum cannot be covered efficiently on one frequency range. It must be decided whether to vary the resistance in steps and the capacity continuously, or vice versa. High

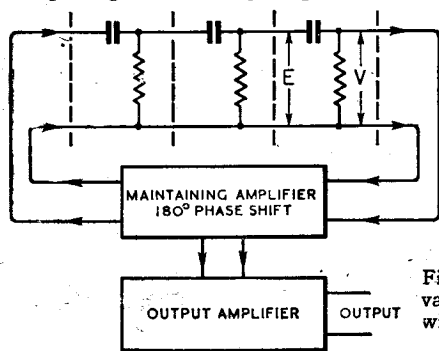


Fig. 1. Phase advancing oscillator with three-section phase shifter.

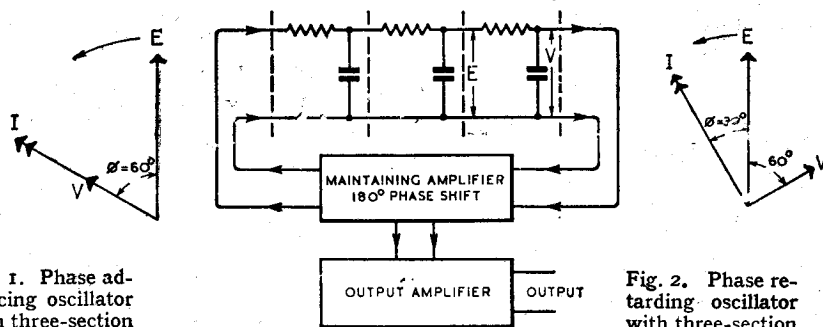


Fig. 2. Phase retarding oscillator with three-section phase shifter.

phase shifter be connected with the output fed back to the input, then if the gain of the amplifier exceeds the loss of the phase shifter oscillation will occur at a frequency which produces zero phase shift for the complete chain.

An RC-coupled amplifier with an odd number of stages produces a phase shift of 180 degrees, so to make it into an oscillator combinations of resistances and reactances (normally condensers) capable of producing a phase shift of 180 degrees are required. An RC-coupled amplifier with an even number of stages produces zero phase shift, so to make this oscillate, combinations are required which will produce a phase shift of zero or 360 degrees.

One cannot quite produce a phase shift of 90 degrees with a single RC combination, so that to produce 180 degrees phase shift, at least three such combinations are required. To produce a phase shift of zero or 360 degrees one may use either a minimum of five such combinations (or sections as it is convenient to call them from now on), or a phase-retarding section and a phase-advancing section, the

varies with change in capacity or resistance, let us note that the total of phase shifts in any RC oscillator is fixed at zero for all frequencies of operation. Since in any section of the phase shifter, the phase angle ϕ between the input voltage and the current $= \arctan (X/R) = \arctan (1/2\pi fCR)$ this value must also be fixed. Therefore, if either C or R is varied, f the oscillation frequency will vary in inverse proportion. Then if R is fixed and C varied the reactance of C will always be the same at the frequency of oscillation. If the total

quality multiple gang variable resistances are not easily obtainable. Rubbing contact variable resistances are not as reliable as variable condensers. These reasons favour the selection of the first alternative, so a ganged variable condenser is employed, and fixed resistances are selected by means of a Yaxley type switch.

It is generally known that all oscillators produce harmonics, and in an LC oscillator the tuned circuit is made as efficient as possible in order to attenuate them. In the RC oscillator there is no tuned circuit, but the phase shifter can be arranged to produce a similar effect.

Fig. 4 shows the variation of attenuation with frequency for single phase-advancing sections (a), and phase-retarding sections (b). The curves show that the former circuit will attenuate the harmonics less than the fundamental, whilst the latter circuit will attenuate the harmonics more than the fundamental. This led to the adoption of the phase-retarding circuit.

This circuit has been called a phase-retarding circuit because the output voltage from any phase shifting section

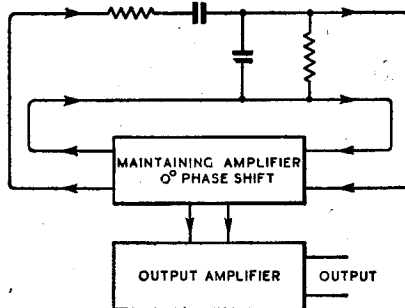


Fig. 3. Phase "advance-retard" oscillator.

in Fig. 2 or Fig. 4(b) lags behind its input voltage. However, in a circuit containing only resistance and capacity, the current must lead the input voltage, but because the voltage across a condenser lags behind the current by 90 degrees, the output voltage in a phase-retarding section lags behind the input voltage. This is made clear by the vector in Fig. 2.

It will be seen that the current lead on the input voltage must be the complement of the required voltage lag in the phase-shifter section. Table I gives a comparison between three-, four- and five-section 180-degree retarding shifters as regards attenuation, etc. The greater the number of sections used to produce a given phase shift the lower will be the attenuation and the required value of CR.

The CR values should be kept as low as possible, because when generating the lower audio frequencies, if one uses a variable condenser having a maximum capacity of the order of 0.0005 mfd., the value of R will run into several megohms. There is a danger that R may have a value comparable with unavoidable leakage resistances. Also the final section of the phase shifter must be shunted by the input impedance of the maintaining amplifier, which must not be

TABLE I
180-DEGREE PHASE-RETARDING SHIFTER

No. of Sections in Phase Shifter	3	4	5
Required voltage lag per section (degrees) ..	60	45	36
Required current lead per section (degrees) ..	30	45	54
Attenuation E/V per section2	1.4	1.25
Total phase shifter attenuation	8	4	3.1
Required CR product	0.28/f	0.16/f	0.12/f
Required phase shifter resistance in megohms when C=0.00055 μ F.	513/f	295/f	218/f

Some of the complications of the phase shifter are beyond the scope of this article. To illustrate basic principles, only basic equations are used. For this reason and for reasons stated in the text, these figures should be taken as general indications only. This applies especially to the figures for attenuation.

The first is that the final section is shunted by the input impedance of the maintaining amplifier, and the lower the frequency range the more troublesome this shunting effect becomes.

The second reason is that there exists across the resistance elements some stray capacity, and when this capacity is an appreciable fraction of the capacity of the condenser (i.e., when the condenser is near its minimum capacity setting) the attenuation increases. This complication constitutes a major controlling factor in the design. To reduce this effect fixed

circuit on all ranges. It is therefore necessary to employ three or four ranges to cover the AF spectrum.

A three-range phase shifter will conveniently cover 40 to 10,000 c/s, and a four-range phase-shifter 40 to 13,000 c/s. Suitable component values are given in Table 2. Not only does the four-range phase-shifter cover a wider frequency band, but it improves the waveform and frequency stability and the voltage output varies less with frequency.


To reduce the attenuation at the minimum capacity settings of the condenser when operating on the lowest frequency range, a fifth section is added to the phase shifter on this range. Its capacity and resistance values are fixed and are represented by C₉ and R₁₇. The resistance should be adjusted to give a constant voltage output over the lowest frequency range. The addition of this section reduces the maximum frequency on this range, without affecting materially the minimum frequency. Additional circuits of this type cannot be used on the other ranges without modification to the switching. The use of the fixed section is a refinement which can be omitted if desired when using the four-range model.

The very high resistances and reactances used in the phase shifter necessitate the use of special precautions in construction. All condensers must have very high insulation dielectrics and must be protected against dust, etc. The trimmers fitted to the ganged condenser must be removed, because their capacity values are not sufficiently stable. No paste or liquid flux should be used when soldering up the range switch. It is desirable to have a blank position on the switch between the lowest frequency range and the adjacent range. The metal framework of the switch must be earthed. The "group board" method of construction should not be used in the phase shifter because of stray leakages and capacities. The resistances should be

condensers are connected across the variable condensers to raise the minimum capacities. These have the effect of lowering the frequency coverages on all ranges.

The third reason is that there exists across the condensers some unavoidable leakage conductance, and

Fig. 4. Variation of attenuation E/v with frequency for single 45 degree phase advancing section (a), and retarding section (b). The vectors apply to the fundamental frequency only—in this case 100 c/s. CR = 0.0016.

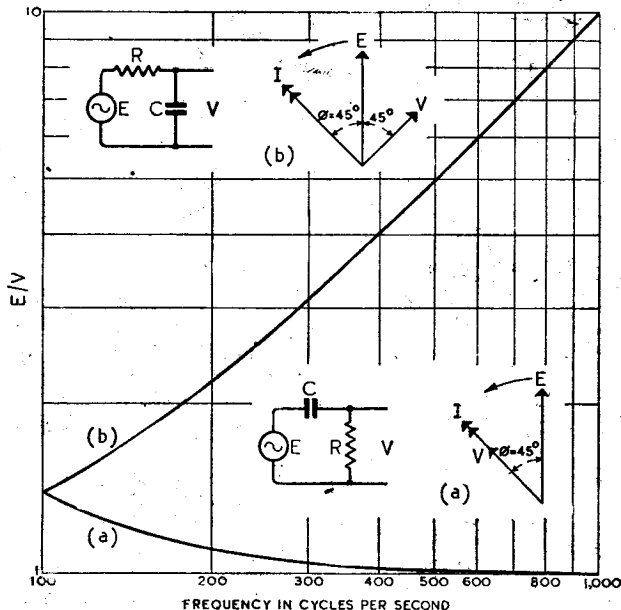

allowed seriously to affect the phase-shifter characteristics.

A four-section phase shifter is used because this provides a fair compromise between efficiency and complication. It is desirable that the phase shifter should introduce the same attenuation at all frequencies. Unfortunately a simple circuit does not do so for three reasons.

when this becomes comparable with the conductance of the resistance elements of the phase shifter (i.e., when operating on the lowest frequency range) the attenuation again increases. These conditions limit the frequency coverage ratio on the lower frequency ranges to a low value. To avoid switching complications, the fixed capacity shunt condensers are left in

Designing a Resistance-Capacity Oscillator—wired up with stout wire directly to the switch tags, and stand-off porcelain insulators used where necessary. The switching can be arranged so that the phase shifter has a switch section either at the input end or at the output end. If the arrangement shown be used, then leakages in the first switch section are unimportant. With this arrangement R₁ changes the effective value of R₂, so that the final frequency calibration should not be undertaken until all the resistances have been selected to give the correct frequencies on all ranges.

When adjusting the resistances in the phase shifter to secure the required frequencies it is not necessary to make all of the resistances absolutely identical on one range. This would necessitate the use of several standard values to make up one non-standard value. Fine adjustments of frequency can be made by adjusting one resistance only.

Maintaining Amplifier

The following is a brief specification of the maintaining amplifier:—

(a) Its input resistance including the first grid leak must be high compared with 11 megohms. (The highest resistance used in the phase shifter.)

(b) Its input capacity must be either very small or it must be very constant under all conditions.

(c) It must introduce a phase shift of 180 degrees approximately. Whilst it is permissible for the phase shift to deviate slightly from 180 degrees with frequency, it must remain constant with age, warming up, etc.

(d) It must be designed for an input signal of approximately 3.5 volts RMS and must introduce negligible harmonic distortion up to the point where connection is taken off to the output amplifier. Distortion introduced after this point is not so

**TABLE II
THREE-RANGE PHASE SHIFTER**

Range	Section				Min. Freq.	Max. Freq.
	1st R ₁ , 2 & 3	2nd R ₅ , 6 & 7	3rd R ₉ , 10 & 11	4th R ₁₃ , 14 & 15		
1	11	11	11	11	40	200
2	2	2	2.5	2.5	180	1,500
3	0.2	0.2	0.2	0.2	1,400	10,000

R₁₇ = 0.4 and C₉ = 0.002 μF. Fixed capacity shunt condensers C₅, C₆, C₇ and C₈ = 50 μμF.

FOUR-RANGE PHASE SHIFTER

Range	Section				Min. Freq.	Max. Freq.
	1st R ₁ , 2, 3 & 4	2nd R ₅ , 6, 7 & 8	3rd R ₉ , 10, 11 & 12	4th R ₁₃ , 14, 15 & 16		
1	10	10	10	10	40	150
2	2	3	3	3	140	600
3	0.2	0.5	1.0	1.0	600	3,000
4	Nil	0.1	0.2	0.25	3,000	13,000

R₁₇ = 0.5 and C₉ = 0.001 μF. Fixed capacity shunt condensers C₅, C₆, C₇ and C₈ = 100 μμF.

All resistance values are in megohms. All resistances may be of 1/4-watt rating.

important but should be kept low.

These points will now be dealt with in order:—

(a) The grid leak of a small valve should not normally exceed 2 megohms, except when automatic bias is used, when it may be somewhat higher than this. To raise the total effective input resistance, a resistance R₁₉ is connected in the cathode circuit of V₁. This causes considerable nega-

tive feedback, with the result that the voltage across the grid-leak and grid-cathode space is much smaller than that between grid and earth. This raises the effective input resistance at the cost of a reduction in stage gain. V₁ should have a top-cap grid connection. A push-pull connection to the output amplifier may be taken from the cathode and a tapping on the anode load of V₁.

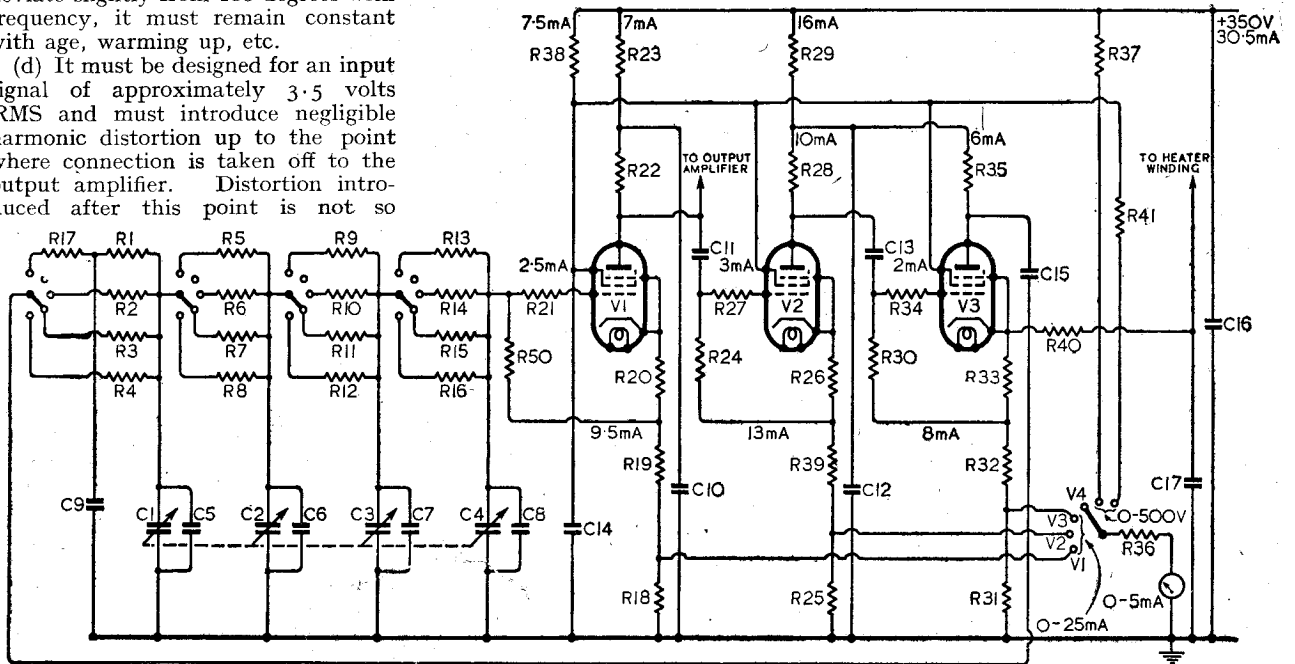


Fig. 5. Circuit diagram of phase shifter and maintaining amplifier. Component values are given in a separate list.

(b) The input capacity is reduced by the action taken to raise the input resistance. The input capacity may be kept to a minimum by making V1 either a cathode follower or a screened pentode. (See "The Cathode Follower," *Wireless World*, July, 1941.)

(c) The CR combinations in the maintaining amplifier should be such as to cause negligible phase shift.

LIST OF COMPONENTS
Resistances

R. No.	Ohms	Watts
18	10*	1/4
19	4,000	1/2
20	250	1/4
21	1,000	1/4
22	20,000	2
23	2,000	1/4
24	2,000,000	1/4
25	10*	1/4
26	250	1/4
27	1,000	1/4
28	20,000	2
29	5,000	1
30	2,000,000	1/4
31	10*	1/4
32	5,000	1
33	200	1/4
34	1,000	1/4
35	25,000	2
36 + res. of meter	40*	1/4
37	100,000*	2
38	10,000	2
39	500	1/4
40	1,000,000	1/4
41	100,000*	2
42	250,000	1/4
43	4.44*	1/4
44	1,000	1
45	320	1/4
46	1,000	1/4
47	5,000	3
48	490*	1/4
49	50,000	1/4
50	5,000,000	1/4

* Indicates plus-or minus 1 per cent.

Condensers

C. No.	Capacity (μF)	Volts (Working)	Type
1, 2, 3 and 4	0.0005 max.	—	Variable air
10	32	350	Electrolytic
11	0.02	350	Mica
12	16	350	Electrolytic
13	0.01	350	Mica
14	8	350	Paper
15	0.01	350	Mica
16	24	400	Electrolytic
17	0.05	350	Paper
18	32	350	Electrolytic
19	16	350	Paper
20	0.02	350	Mica

For R1 to R17 and C5 to C9 see Table 2. Valves.—V1, V2 and V3, Type TSP4; V4, Type 41 MP.

Then, if their values change slightly, the effect on the frequency stability will be very slight. For operation at a minimum frequency of f c/s no effective CR product should be below $1/f$. To introduce a phase shift of 180 deg. an odd number of phase-reversing stages is necessary. A single phase-reversing stage, either with or without a cathode follower, could not be used—except at high audio frequencies—because of insufficient gain. It became necessary to use three valves. In an earlier model a cathode follower, an "in-phase amplifier" (see *Wireless World*, February, 1942), and an ordinary stage were used. Finally, a straightforward three-pentode circuit was decided upon.

In cases where there is no phase-shift measuring equipment available, the following test will provide a relative indication of phase shift. Disconnect C9 temporarily. Measure the maximum and minimum frequencies produced on all ranges. Then, if the phase shift in the maintaining amplifier is 180 deg. at all frequencies, the frequency coverage ratios will be approximately equal. If phase advancing occurs at the lower frequency end of a range (due to a low CR product in a coupling circuit), it reduces the frequency coverage ratio. If phase retarding occurs at the lower frequency end of a range (due to a low CR product in a decoupling circuit), the ratio is increased. If phase retarding occurs at the high frequency end of a range (due to a high product of load resistance and stray capacity), the ratio is reduced. Do not forget to reconnect C9.

(d) The negative feedback provided in the first stage is also useful in keeping distortion in V1 at a low level. The resistances R26 and R39 in the cathode circuit of V2 reduce distortion in this stage. Although some distortion is permissible here, grid current in V2 should be avoided, because it will produce distortion at the anode of V1, the point at which connection is made to the output amplifier. For this reason V2 should be given a higher bias than V1. The value of R39 should be determined by experiment. If the amplified "motorboats," then the gain is too low and R39 should be reduced. However, it should be adjusted to the highest value that will produce reliable oscillation at all frequencies. When making this adjustment, the variable condenser should be set to minimum capacity and the oscillator tested on the two lowest frequency ranges. Oscillation should commence readily when the controls are set to the posi-

tions mentioned and the oscillator is switched on from cold. These settings are the least favourable for oscillation. If for test purposes a variable resistance is used for R39, it should be noted that the instrument is more willing to continue an oscillation than to initiate one. The resistances R32 and R33 reduce distortion in the third stage. The sum of R32 and R33 should not be so high as to produce excessive heater-cathode potential. The V3 bias resistance R33 has very little effect upon the normal operation of the oscillator, because this stage is biased mainly by grid current passing through the grid-leak R30. However,

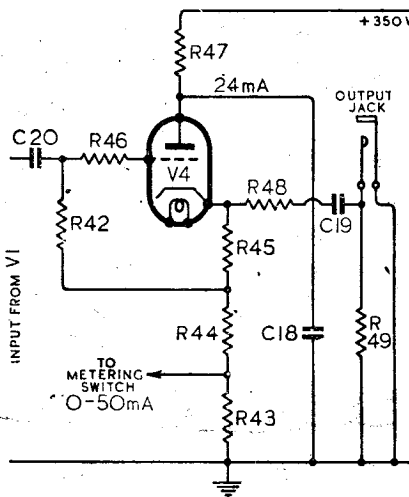


Fig. 6. Output cathode follower stage—with component values listed, the output impedance is 600 ohms.

should oscillation fail, then the anode current of V3 would rise to a high value in the absence of the minimum bias provided by R33.

The output waveform is such that when it is inspected on a small cathode-ray tube it appears as a sine wave at all frequencies. In order to reduce the heater-cathode potentials the heater winding of the transformer is connected via a simple CR filter to the cathode of V3.

A metering circuit is incorporated by means of which the cathode currents and HT and screen voltages may be determined. The switch should not be left in the position for measuring screen voltage, because this has an effect upon the frequency generated. Alternatively, a press button may be connected in series with this lead to the switch.

This should be designed to suit individual requirements. The maximum input available is approximately 18 volts RMS. The impedance input should be high and constant. This

War Office Communications

Keeping in Touch

Designing a Resistance-Capacity Oscillator—rules out the use of an ordinary triode voltage amplifier. There must be no transformer or gain control between the maintaining amplifier and the separator. The output amplifier may be connected either to the anode or the cathode of V_1 , for either a high or a low voltage output.

The first valve consists of a separator, and must be located on the same chassis as the maintaining amplifier and preferably close to V_1 . The separator should consist of either a screened pentode, preferably of the small transmitter type, or a cathode follower. In the former case a parallel-fed transformer may be used if a low output impedance is required.

Variation of output level by variable cathode negative feedback in the separator stage is inadmissible because of the change in input impedance. A "volume range compressor" is preferable.

For the majority of purposes a separator stage will provide sufficient output without further amplification.

In case a design for an output cathode follower is required, Fig. 6 shows the type used by the writer.

APPENDIX

Attenuation E/V per section of the phase shifter, for a phase retarding circuit

$$\frac{R + jX}{X} = 1 + j \cot \phi$$

where ϕ = current lead.

Gain of pentode stage with anode load

$$R_i \text{ and cathode load } R_c = \frac{R_i}{\frac{1}{G} + R_c} = R_i/R_c$$

approximately when $1/G$ is small compared with R_c .

(G is the mutual conductance in amperes per volt, e.g. $G = 0.005$ for a TSP₄ valve having a mutual conductance of 5 mA/volt.)

Multiplying the effective input resistance of the maintaining amplifier

$$M = R_{19}G + 1 \text{ or } R_{19} = \frac{M - 1}{G}$$

where M = multiplying factor.

Effect of fixed parallel condenser on the frequency coverage ratio N on any range where a fixed phase shifter is not used.

$$Cp = \frac{Cv_{max} - Cv_{min}}{N - 1} - (Cv_{min} + Cs)$$

$$\text{or } N = \frac{Cv_{max} + Cp + Cs}{Cv_{min} + Cp + Cs}$$

where Cp = capacity of shunt condenser, Cs = stray capacity

and Cv_{max} and Cv_{min} = capacities of variable condenser at maximum and minimum capacity settings respectively. If frequency coverage ratio on each range = N , total frequency coverage ratio = N_T and number of ranges = R


$$N_T = N^R \quad N = N_T^{\frac{1}{R}} \quad \text{and } R = N_T^{\frac{1}{N}}$$

This takes no account of the reduced frequency coverage on any range where a fixed phase shifting section is used.

THE War Office Signals Office, which is situated deep underground, not far from Whitehall, may fairly be described as the nerve centre of all the British Armies. Through it pass all telegraphic communications between the War Office and the various military units at home or abroad. It is the responsibility of the Royal Corps of Signals to maintain this vital service and to ensure speedy communication with any part of the world where British troops are to be

Wireless Room of the Office, in which the receivers are installed.

For overseas communication there is a 7½-kW short-wave wireless telegraph station, the transmitting and receiving units of which are situated in the country. The transmitter is keyed by high-speed Wheatstone gear in the War Office Signals Office, where the recording and printing apparatus, actuated by signals from the remote receiving station, is also installed. By means of this station, communication

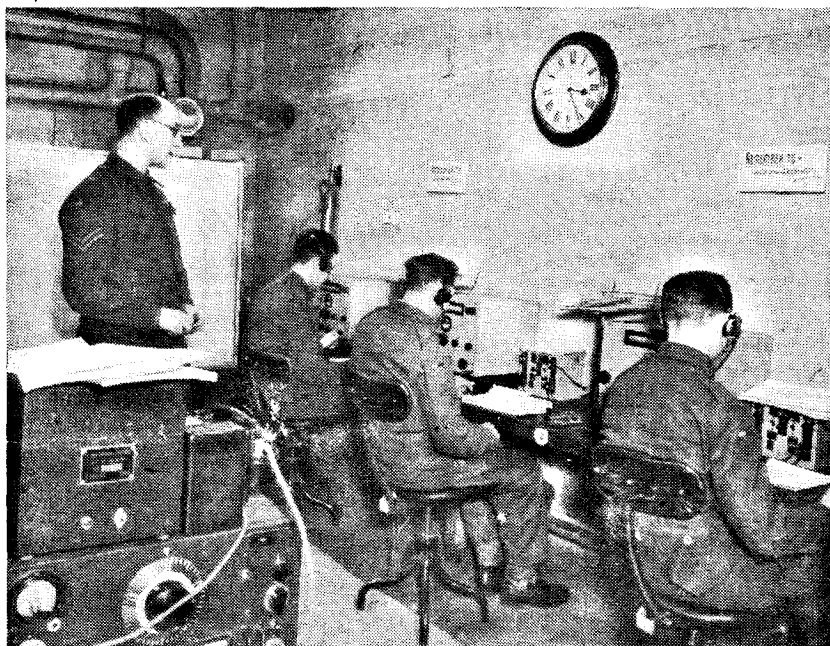

DEEP UNDERGROUND, not far from Whitehall, is the War Office Signals Office, through which communication is maintained with British troops in all parts of the world. It is operated by the Royal Corps of Signals. This *Wireless World* photograph shows a corner of the Home Wireless Room.

found. Many of the messages handed in for despatch are passed on over wire or wireless circuits actually operated by R. Signals, while others are routed by the Office through civil cable or wireless links.

Inland Communications

Naturally, most of the messages to the various Home Commands are normally passed by landline, and in the Office is a large battery of teleprinters, which, incidentally, are mainly operated by A.T.S. girls, who wear the R. Signals badge. For use in emergencies, or in the event of line breakdown, there is a network of hand-keyed wireless transmitting stations which are dispersed at a distance and remotely controlled from the Home

is maintained with our Forces in the Middle East through a corresponding station in Egypt.

Mention of an underground Signals Office may conjure up a picture of extemporised equipment operated under dismal and comfortless conditions. Actually nothing could be farther from the truth. Except for the khaki uniforms, one might imagine oneself in a very busy and smoothly running civilian telegraph station with the most modern equipment. Thanks to air conditioning and fluorescent lighting, the Chief Signalmaster and his staff carry out their vital task of handling some 30,000 messages a week in surroundings that many engaged in communications above ground might envy.

Training

SIGNAL INSTRUCTORS

Interesting Facts About the School of Signals

THE ever-increasing use of wireless in the Army creates a growing demand for signal instructors. This demand is being met by men who have passed through the School of Signals established in the North of England. The School is not concerned with the initial training of signals personnel, which is undertaken by the various Signal Training Centres, but with the training of officers and N.C.O.'s of all arms of the Service who will return to their units as instructors.

The school is divided into two wings, one for Royal Signals and the other for Regimental Signals, for which widely different technical standards are required.

Nine different training courses are conducted in the Royal Signals Wing, for each of which there is a different entrance examination. Only two of these courses are for officers; one being the Advanced Wireless Course and the other the Advanced Lines Course.

Some of the officers entered for the Advanced Wireless Course are selected from Officer Cadet Training Units, whilst others are released from their respective units of R. Signals. Before being accepted for the course they must have a sound knowledge of plane trigonometry; a basic knowledge of two-dimensional vectors; an elementary knowledge of statics and dynamics (such as is required for the School Certificate) and be able to employ the calculus to differentiate any simple expression including products and quotients. Here is a sample question from a recent qualifying examination paper:—"Draw a vector diagram to illustrate the current-voltage relationships in this circuit." (See Fig. 1.)

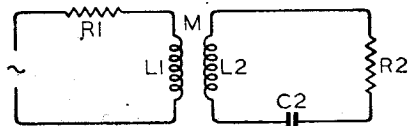


Fig. 1. Prospective officer students of the School of Signals have to draw a vector diagram to illustrate the current-voltage relationships in this circuit.

Another question in a recent qualifying examination relates to a circuit diagram containing "three gross

To give a true picture of the organisation of the Royal Corps of Signals and the chain of communications it maintains throughout the widely dispersed war zones would be impossible in a single article. But, as a result of a recent visit by a member of the "Wireless World" staff to the School of Signals we are able to give some interesting facts about one important, although little known, side of R. Signals organisation.

errors" which had to be indicated by the officer students.

The course, which occupies 11 weeks, deals at considerable length with general circuit theory. During the 96 hours spent on this subject the students deal with AF and RF amplifiers, modulation and demodulation, AF, RF and UHF oscillators, filters (including T, Pi and M derived sections), FM, UHF technique, electron optics; television, diversity reception and DF. The students are given every opportunity of putting into practice the theoretical instruction received and for this purpose there is an experimental laboratory.

A great deal of time is spent on test equipment, such as signal generators (including FM types), oscilloscopes and AF generators. As would be expected, the circuit details of Army transmitters and receivers are studied intensively. A typical, though obsolescent, set still employed in considerable quantities in the Army is the No. 11, which is a transmitter-receiver, mainly used in trucks, which derives its power from a 12-volt accumulator which heats the filaments and supplies HT through a rotary converter. A novel feature of the design is that it incorporates a valve test socket on the panel to facilitate maintenance.

The fundamentals of high-speed telegraphic equipment such as is used in fixed point-to-point stations is also covered by the syllabus for

the officers' Advanced Wireless Course. The instructional centre is equipped with a complete transmitter and receiver so that the students go through the complete operation from the perforator to the automatic printer. Although not in regular use an undulator is maintained as a reserve or monitor.

It is noteworthy that a visit to a B.B.C. transmitting station is included in the course. The reason for this is that R. Signals personnel may be called upon to take over and if possible restore to working order a broadcasting station in occupied territory. This actually happened in Abyssinia.

For R. Signals personnel to enter for any one of the seven N.C.O. courses they have to pass a qualifying examination which varies according to the grade or category in which they aspire to act as instructors. One of a set of ten questions for the qualifying examination for the seven-week N.C.O.'s Wireless and Line Course is

"simplify $\frac{x^4 - y^4}{(x^2 + y^2)(x - y)}$." Another

question in the paper relates to a network of five resistances (see Fig. 2) and asks, "What is the resistance of the network shown between A and B?" These questions will suffice to give some idea of the standard required to enter the school for this course. An approximate allotment of the 245 hours available for the course is: elementary mathematics and electricity, 51 hours; wireless theory, 77 hours; wireless schemes, (the modern term for exercises in the field) 32 hours; line instruments, miscellaneous subjects and examinations, 55 hours; fault-finding, 18 hours and


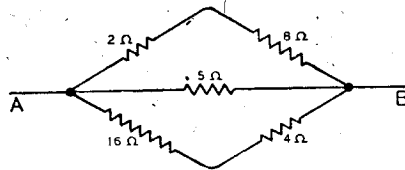


Fig. 2. The resistance between A and B has to be calculated by N.C.O. students during the qualifying examination for the Wireless and Line Course.

12 hours of students' lectures. This latter allotment is very important, for it must be remembered that these N.C.O.'s hope to pass out as instructors.

Training Signal Instructors—

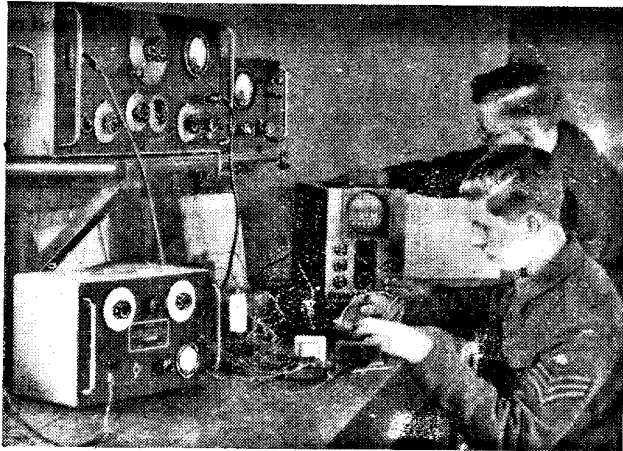For the Advanced Wireless Course for Operators the entrance examination is more exacting, and the course, which covers 6 weeks, is correspondingly more advanced. There is also an Advanced Wireless Course for Workshop Trades, i.e., instrument mechanics and electricians, which occupies ten weeks and deals mainly with the



It must be remembered that a Foreman of Signals has to be a really competent fault finder in the field, where he works with a minimum of test gear, and he must be able to effect and supervise repairs. It is essential, therefore, that he should have a very thorough grounding in general circuit theory and be conversant with the apparatus met with in the field, in order that he can make the best use of the testing and repair facilities at his disposal. As in all other courses, the student is taught how to impart to others the knowledge he gains, and for this

Students in the Laboratory. Each bench position has a set of test apparatus as shown, together with two multi-range meters.

maintenance of apparatus, and a seven-week course for Foremen Mechanics.

It is not possible to deal adequately with each of the N.C.O. courses in a short article, and we will, therefore, confine ourselves to what are perhaps the most interesting, and certainly the most exacting—those for Foremen of Signals. There are two—the Basic, which runs for 18 weeks, and the Continuation, which occupies 13 weeks. The qualifying examination for entry to the Basic Course is in two parts—mathematics and electricity. It will be seen from the following sample questions that a fairly high standard

is required: "Evaluate $\int_{3\pi/4}^{\pi/4} \sec^2 \theta \cdot d\theta$ ";

"Explain the principles used in the superheterodyne wireless receiver. What is second channel interference and why does it occur?"; "Explain the terms 'carrier wave,' 'modulated wave' and 'side-bands' applied to R/T, taking as an example an R/T transmitter tuned to 3,000 kc/s and emitting a tuning note of 1,000 cycles per second. Assuming the frequency band for speech to be 300 to 2,000 c/s, what is the smallest frequency separation that can be allowed between two R/T stations so that they may work without mutual interference?"

The syllabus for the Basic Course of over 700 hours allows nearly 250 hours for wireless theory and practice, 87 for mathematics, 70 for workshop practice and the remaining time for electricity, magnetism and line communication.

purpose the students deliver lectures which are criticised by their fellow students.

A few of the students who pass through the Foremen of Signals Basic Course are selected for the 13-week Continuation Course, the title of which is self explanatory. So far as wireless is concerned this course covers transmitting apparatus of relatively high power, aerials, the propagation of electro-magnetic waves, CR equipment, Service sets and high-speed morse equipment.

One of the later and more interesting transmitters on which Foremen of Signals receive instructions during the Continuation Course is the No. 33,

which, operated from AC mains or from its own petrol-driven alternator, has an output of 60 watts on 'phone and 250 watts on CW. It has an input of 1.2 kVA and is used mainly in three-ton lorries.

To give Foremen of Signals an opportunity of handling high-powered transmitting apparatus such as might be met with at a captured telegraph or broadcasting station, an obsolete 5-kW transmitter is used for training purposes. A visit to a B.B.C. station is also included. This is, incidentally, the only course for N.C.O.'s which includes instruction in the principles of FM.


A considerable part of the students' time is spent in the experimental laboratories, where they have to undertake a number of experiments with standard test apparatus, such as would be found in rear areas. Experimenting during spare time is encouraged.

It must be remembered that the job of a Foreman of Signals who has undergone the Continuation Course will be to instruct men normally working in rear areas where the more complicated transmitting, receiving, and test equipment is to be found. He will, of course, also be largely responsible for the maintenance of this and all other signalling equipment in his unit.

It may be of interest to note that in the Signals Wing there are to be seen men from the equivalent branches of the armies of our allies, including American, Belgian, Polish, and Czechoslovakian.

It should be added, that in addition to those already mentioned there are short courses for senior officers (lieut. colonels and majors) and company commanders in the Signals Wing; these comprise a general brush-up in technical and tactical subjects.

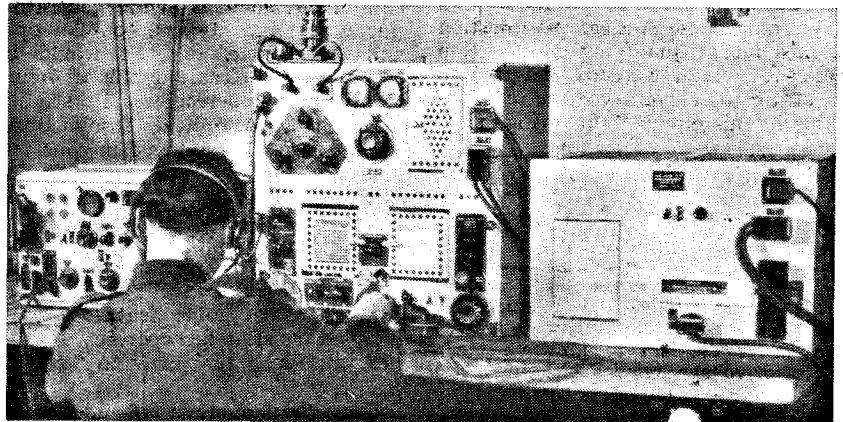Although the Regimental Wing of the school also comes under the command of the Commandant it is very



A semi-mobile medium-power transmitter (No. 33), for telegraphy or telephony, which operates from 230 volts AC. The receiver (R107), is on the left, and the power unit on the right.

much a separate entity from the Signals Wing and is staffed by officers and N.C.O.'s of various regiments. The three distinct sections to the Wing are concerned, respectively, with the training of signals instructors for the Infantry, Royal Artillery and Reconnaissance regiments.

In the Regimental Wing the courses, which occupy eight weeks, differ from those in the Signals Wing in that they include very little theory, the main reason being that the students will not be called upon to give theoretical instruction when they return to their Corps or Division. The qualifying examinations for admission to the courses for officers and N.C.O.'s are very much simpler than those for entry to the Signals Wing. To qualify, an N.C.O. must have an aptitude for imparting knowledge to others, be conversant with the apparatus used in the section of the Army to which he is attached and be a qualified signaller. It should, perhaps, be pointed out that, whereas in R. Signals the term "signalman" is used, in all other arms of the Service "signaller" is employed.

In the Infantry section the course is roughly divided into two four-week periods. The first is confined to instruction and the second to working on schemes as a platoon in which the officers and men combine.

Considerable stress is laid on the use of wireless, for although these students have to be conversant with line work there is seldom opportunity for the use of line communication in the field. Communication procedure, which, incidentally, has recently undergone radical changes, is, of course, an important part of their training. Essential fault finding and maintenance is undertaken in the field by regimental signals personnel but the training is not highly technical as no major fault is rectified in the field. In all the courses in the Regimental Wing theoretical instruction is confined to block schematics.

Different types of transmitters, receivers and transceivers (the official term for apparatus in which some of the components are common to both transmitter and receiver) are used by the three sections. The Infantry (including rifle battalions, airborne troops and machine gunners) mainly use pack transceivers. Of the three or four types in production the most common is the No. 18 which was described in our September issue. A lighter and more compact set—the No. 28—has been produced. This is of the "all-dry" type and is carried in a canvas case little larger than a haversack. Like its predecessor it has a tubular sectional aerial, the socket for which rotates through 90 deg. to allow the

aerial to be vertical when the infantryman is lying down.

A later type of pack set is the No. 38 which is intended for the use of officers and is for 'phone only. It is quite



This small infantry pack set (No. 38) employs a throat microphone and is so arranged that it does not interfere with the wearer's fighting efficiency.

small being capable of being worn on the chest next to the respirator. The batteries are carried in a separate case. This set has a three-section 8ft. aerial which, when not in use, is carried in a canvas sling. An interesting feature of this set, the range of which is, for reasons of secrecy, very limited, is the use of laryngaphones so that there is no obstruction to the use of the voice for normal purposes and to leave the hands free.

Students in the section which trains anti-tank and anti-aircraft personnel are trained to the "driver operator" standard in morse, which is twelve words a minute, as they will have to instruct both signallers (10 w.p.m.) and driver operators. Throughout their training in receiving morse they are continually reminded of the prevalence of interference in W/T. For many of their receiving periods they are given an R4 signal with R3 interference superposed. It should be pointed out that the signal strength scale, which used to be graded R1-R9 is now R1-R5.

It may be of interest to give a few brief details of some of the sets more widely used by the men in this section.

The No. 19 transmitter-receiver, which derives its power from an accumulator through a rotary convertor, has some interesting refinements to simplify operation. One of these is push-button tuning to facilitate the process of "netting"—which is the term used for grouping stations into a network. Another refinement makes it possible accurately to tune the transmitter without radiating.

Remote control is provided on the No. 21 transmitter-receiver, which is of the transportable type, so that the set can be erected in an advantageous position for radiation whilst the operator is under cover as much as 120 yards away. Working on 'phone, CW and MCW in the 19-31 and 4.2-7.5 Mc/s bands, the No. 21 is largely used by field artillery. This set, which derives its HT from an accumulator through a vibrator, succeeds the No. 11, mentioned earlier.

Like the infantry and airborne troops, the reconnaissance and motor battalions, or mobile infantry, depend mainly on wireless for communication and their course of instruction therefore stresses this side of the students' training. Tactical training is, of course, of vital importance to reconnaissance troops, and for this reason a large part of the time is devoted to schemes under service conditions. Because of their reliance on their own resources these men are, of course, trained in practical fault-finding.

Most of the maintenance of the training equipment at the school is undertaken on the spot. This is no mean task, for there are some 400 or 500 sets in constant use, and something like a thousand batteries are handled in the charging room.

Although not concerned directly with the training of personnel a branch of the School which is of considerable importance is the Publications Section. All manuals and instruction booklets relating to signals apparatus and procedure are prepared by, or pass through the hands of, the staff. The close co-operation between our own Forces and those of our American Allies has called for a revision of the rules of procedure, and incidentally of the phonetic alphabet.

It is interesting to note that the instructors for both wings of the school are drawn from officers who have passed through the courses. When other Signal Schools, such as those in the Middle East and India, are established the signal instructors are picked from officers who have attended the school, the activities of which have been described.

LAMINATION DESIGN

Influence of Shape on the Cost and Weight of Transformers and Chokes

By

N. PARTRIDGE,
Ph.D., B.Sc. (Eng.), M.I.E.E.

LAMINATIONS manufactured for use in the construction of mains transformers and smoothing chokes have a very definite and specific function to perform. One might reasonably expect, therefore, to find a wide range of sizes all having the same general proportions. But nothing of this sort occurs in real life. Large windows, little windows, tall lean patterns and stocky varieties are (or were) obtainable for the asking.

Two questions at once present themselves. Does the shape matter very much and, if so, why produce anything but the best shape? The former question is capable of logical treatment and will be dealt with in some detail. The latter touches upon the perversity of human nature and is probably unanswerable.

The merit of a lamination can be assessed in a number of ways depending upon the particular purpose for which it is required. In the case of components for radio equipment cost and weight are the principal criteria. The present investigation will therefore be twofold. First, we will discover how the shape of the lamination influences the cost of the materials necessary to produce a component of given performance, and secondly, we will see how the weight of the component is affected thereby.

Mains Transformers

Fig. 1 shows a lamination of typical proportions together with a sectional plan and a side elevation of the complete transformer. As a tentative approach to our problem, consider a square core section ($y = 1$) and examine the effect of varying the height (x). By assigning various values to x it will be possible to calculate the relative costs and weights per watt output for each of the resulting transformers.

The upper portions of Tables 1 and 2 show how this may be done. Column 1 of Table 1 gives the values assigned to x . The second column shows the volume of the space occupied by the winding. This is the area of the window multiplied by the length of the mean turn (see Fig. 1 (b)). For equal performances, the temperature rise must be the same for each transformer, and to take account of this the effective cooling surface of

The fixing of the proportions of a lamination is in reality the first step in transformer design. The author shows the important influence it has upon the economy of the resultant component.

the bobbin must be known. The cheeks of the bobbin dissipate a negligible proportion of the heat and therefore the effective cooling surface of the winding is obtained by multiplying the height of the bobbin ($x - 1$) by the length of that portion of the periphery of the winding which is exposed to the air (see Fig. 1 (b) and (c)).* The results are set down in column 3.

At constant current density, the temperature rise depends upon the available area of cooling surface per unit of volume. This is discovered by dividing the surface by the volume, the result of which is shown in column

*This treatment is not exact but can be accepted as a first approximation.

4. The ratio of surface to volume is seen to be independent of x , since both the volume and the surface of the bobbin are directly proportional to its height, and therefore constant current density will result in equal temperature rises throughout.

Columns 6, 7 and 8 are similar to columns 2, 3 and 4 but relate to the iron core. The effective cooling surface of the iron is that part formed by the edges of the laminations. The conduction of heat across the stack from one lamination to another is relatively small. This time the ratio of surface to volume (column 8) varies with x . It follows that at constant flux density the temperature rise will also vary with x . But the generation of heat within the iron varies approximately as the square of the flux density. Hence to ensure a constant temperature rise throughout, the flux densities must be adjusted in proportion to the square roots of the figures in column 8. These square root values are given in column 9.

The relative outputs for the series of transformers can now be deduced. If both current and flux densities were constant, the output would be proportional to the length of the bobbin ($x - 1$). But to allow for the adjustments to the current and/or flux densities, ($x - 1$) must be multiplied by the figures in columns 5 and 9.

In this particular instance column 5 is constant throughout and can be ignored. Column 10 is therefore derived by multiplying ($x - 1$) by the figures in column 9.

Now pass to Table 2. The relative weights of the windings, complete with bobbin, insulation, etc., are obtained by multiplying the volume of the winding space

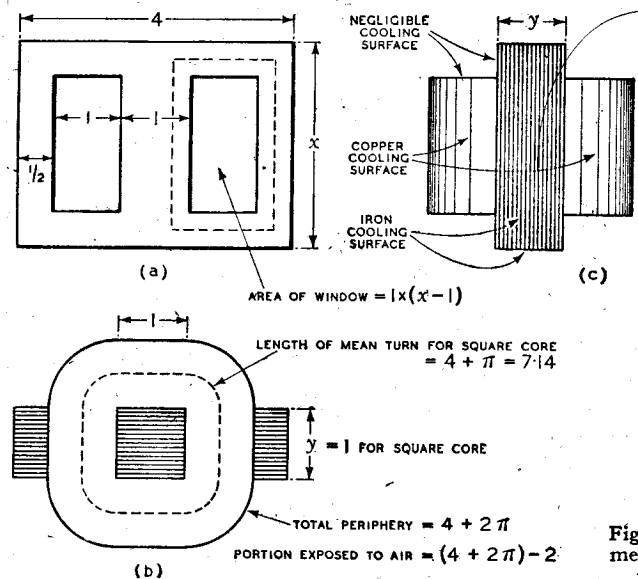


Fig. 1. Relevant dimensions of a typical mains transformer

(column 2, Table 1) by the weight per cu. in. of an average winding. The total weight of a complete winding will, of course, depend upon the size of the transformer to which it belongs. But

and thereafter rises slightly. For practical purposes the minimum values can be regarded as having been attained when the height of the lamination is comparable with its

by multiplying y by the figures in columns 5 and 9 (Table 1). But column 9 is constant throughout and can therefore be ignored.

Again it will be seen that both the cost and the weight per watt output are reduced by increasing y . However, the stack thickness employed in practice is determined very largely by manufacturing expediency. A square section bobbin is the easiest to wind and is therefore frequently used. Next to this, stacks up to $1\frac{1}{2}$ times the width of the centre limb are satisfactory from the winding point of view, but greater stacks become very difficult to handle. Table 2 indicates that for a given lamination a $1\frac{1}{2}$ stack produces approximately 40 per cent. more total output than a square section. Also the former achieves a small but useful advantage in both the cost and weight per watt output.

Lastly, the width of the centre limb of the lamination has to be determined. (In view of the high flux densities normally employed in transformers, it can be accepted without discussion that the outer limbs shall be precisely one-half the width of the centre limb.) The task is complicated by the fact that the stack cannot be definitely fixed on account of the practical considerations mentioned above. But it is evident from Table 2 that, for a general-purpose lamination to be used in anything from a 1 to a $1\frac{1}{2}$ stack, the limb width should be designed for optimum results in the former case. When the stack is increased the cost and weight per watt automatically improve.

Proceeding on this basis, the height of the lamination has been fixed as being equal to its width, and the stack as being equal to the width of the centre limb. To show that there was no undisclosed subtlety in the selection of 4 as the main dimension in Fig. 1, and to increase the reader's familiarity with the geometry of iron-cored com-

TABLE I

Height x	Copper				Iron				Relative Output
	Volume V_c	Surface S_c	$\frac{S_c}{V_c}$	$\sqrt{\frac{S_c}{V_c}}$	Volume V_f	Surface S_f	$\frac{S_f}{V_f}$	$\sqrt{\frac{S_f}{V_f}}$	
2	7.1	8.3	1.16	1.08	6	12	2.0	1.41	1.41
3	14.3	16.6	1.16	1.08	8	14	1.75	1.32	2.62
4	21.4	24.8	1.16	1.08	10	16	1.6	1.26	3.80
5	28.6	33.1	1.16	1.08	12	18	1.5	1.22	4.9
6	35.7	41.3	1.16	1.08	14	20	1.43	1.19	5.97
Stack y									
0.75	19.9	24.8	1.25	1.12	7.5	12	1.6	1.26	0.84
1.0	21.4	24.8	1.16	1.08	10	16	1.6	1.26	1.08
1.25	22.9	24.8	1.08	1.04	12.5	20	1.6	1.26	1.30
1.5	24.4	24.8	1.02	1.01	15	24	1.6	1.26	1.52
1.75	25.9	24.8	0.96	0.98	17.5	28	1.6	1.26	1.70
(1)	(2)	(3)	(4)	(5)	(6)	(7)	(8)	(9)	(10)

the weight per cu. in. is appreciably constant over a wide range of sizes for a given type of construction. The figure used for the present purpose is 0.083 lbs. per cu. in. and was obtained from manufacturing experience. Similarly, the relative weights of the cores are discovered by multiplying the core volumes by the weight per cu. in. of core, which is 0.26 lbs. The relative total weights are obviously the sums of columns 2 and 3, and the relative weights per watt output are calculated by dividing column 4 of Table 2 by column 10 of Table 1.

The relative costs per watt output are worked out in columns 6, 7, 8 and 9. There is one important point to note. The cost of laminations depends upon the gross area and is not altered by the sizes of the window holes. This is because the same amounts of material and labour are expended in their production whatever the size of the window. Hence the price per cu. in. of actual iron will be high when the window is large and low when the window is small. But the price per cu. in. of gross volume i.e., including window space, will be constant. The cost per cu. in. of winding has been taken as 3.02d., and that per cu. in. of gross stack as 3.32d.* As with the weights per cu. in., these costs per cu. in. remain appreciably constant over a wide range of sizes.

Table 2 shows that the weight per watt output continues to improve as x increases, while the cost per watt reaches a minimum value when $x = 4$

*These manufacturing costs are fictitious. The final results depend only upon the ratio of the winding and core costs. This ratio is correct and therefore the deductions remain valid.

width. There seems little point in making x slightly shorter than the width, or, for that matter, slightly taller. But several advantages accrue from making the lamination precisely square. In particular, the same end plates, the same chassis space and the same fixing holes, will serve for mounting the bobbin either vertically or horizontally. Hence we deduce that transformer laminations for general use might, with a substantial measure of reason, be made square in shape.

Having fixed the value of x at 4 (= width) we can proceed to study the effect of varying the stack (y). The calculations are exactly as before and are set out in the lower portions of Tables 1 and 2. At constant current and flux densities the output would be directly proportional to y . The relative outputs for constant temperature rise are therefore derived


TABLE II

Height x	Relative Weights				Relative Costs			
	Copper	Iron	Total	Per watt	Copper	Iron	Total	Per watt
2	0.59	1.56	2.15	1.52	21.5	26.6	48.1	34.0
3	1.19	2.08	3.27	1.25	43.2	40.0	83.2	31.8
4	1.78	2.60	4.38	1.15	64.6	53.2	117.8	31.0
5	2.37	3.12	5.49	1.12	86.4	66.4	152.8	31.2
6	2.96	3.64	6.60	1.10	107.6	79.8	187.4	31.3
Stack y								
0.75	1.65	1.95	3.60	4.29	61.0	39.8	100.8	120
1.0	1.78	2.60	4.38	4.07	64.8	53.2	118.0	109.4
1.25	1.90	3.25	5.15	3.96	69.2	66.4	135.6	104.2
1.5	2.03	3.90	5.93	3.91	73.8	79.8	153.6	101.4
1.75	2.15	4.55	6.70	3.95	78.2	93.0	171.2	101.0
(1)	(2)	(3)	(4)	(5)	(6)	(7)	(8)	(9)

Lamination Design—

ponents, let us now consider a lamination 5 × 5. This is illustrated in Fig. 2 where the width of the centre limb has been called z.

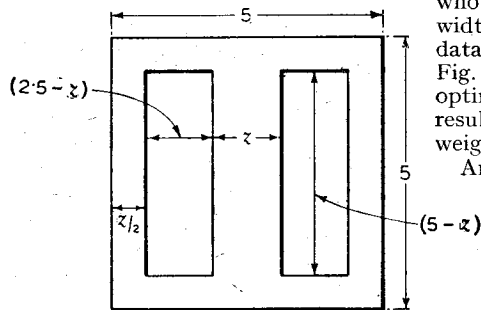Construct two tables similar to Tables 1 and 2 but having z, instead of x or y, in the first column. Assign values to z such as 0.25, 0.5, 0.75... 2.25.



FOR SQUARE STACK:—

$$\text{VOLUME OF WINDING} = (2.5 - z)(5 - z)[4z + \pi(2.5 - z)]$$

$$\text{COOLING SURFACE OF WINDING} = (5 - z)[2z + 2\pi(2.5 - z)]$$

$$\text{NET VOLUME OF IRON} = z^2(15 - 2z)$$

$$\text{GROSS VOLUME OF STACK} = 25z$$

$$\text{COOLING SURFACE OF IRON} = 20z$$

$$\text{OUTPUT AT CONSTANT DENSITY} \propto z^2(5 - z)(2.5 - z)$$

Fig. 2. Formulæ for surfaces and volumes in relation to the core width for a 5 × 5 lamination.

The figures to be entered in the various columns can now be calculated. To avoid misunderstanding, the required formulæ are noted in Fig. 2. It will be found that both the current and the flux densities have to be adjusted for constant temperature rise.

If the costs and weights per watt output obtained as described above be plotted against z, a definite minimum point will be found in each case. By giving this point the arbitrary value 100, the other points can be expressed as percentages of the minimum. This has been done in the lower part of Fig. 3 which at once reveals the information we want. When z is 1.2 the transformer has the lowest weight per watt output but the cost is about 15 per cent. higher than it need be. For minimum cost, z should be 1.6 at which point the weight becomes 15 per cent. up. The most significant spot of all occurs at the intersection of the two curves when z = 1.4. This marks the most satisfactory compromise between cost and weight, each being between 3 and 4 per cent. above the lowest possible value.

As a matter of interest it may be noted that the minimum cost per watt output does not occur when the cost of the winding is equal to the cost of the core. This fact is contrary to the teaching of several standard text-

books dealing with the design of AC equipment.

The optimum proportions for general purpose transformer laminations as deduced above are shown in Fig. 8. These proportions hold good for the range of outputs from say 30 to 600 watts.

To satisfy the curiosity of those who want to know the optimum limb width for a 1½ stack, the necessary data is shown in the upper part of Fig. 3. It will be observed that the optimum lamination for a square core results in low cost but rather high weight when used in a 1½ stack.

And now a few words of warning addressed to those idealists to whom reference to cost might seem irrelevant. The reference to low cost as employed in the foregoing discussion has no connection with things "cheap and nasty." The finished transformer, be it designed for minimum cost or minimum weight, will employ the same quality materials and will enjoy the same quality workmanship. It will, in fact, have the same performance and reliability. But the low weight transformer will be very wasteful of materials

and labour. Fig. 3 shows that a low weight calls for a relatively thin limb and therefore a large window. Thus we start off by creating a large piece of scrap metal — wasted labour and wasted material. Next we have to buy additional wire to fill the larger window and to spend extra time winding it on to the bobbin — more wasted labour and wasted material. As a matter of fact, the large bobbin with its greater number of turns per volt, will tend towards poorer regulation. Hence there is an excellent case for taking cost fully into account unless weight is an overriding consideration. Furthermore, cost takes on a new significance as an

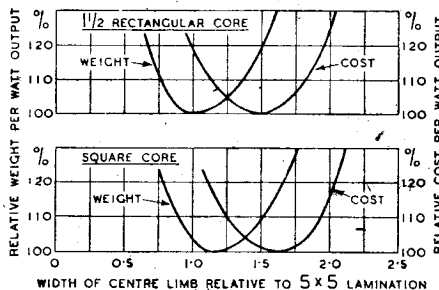


Fig. 3. The width of the limbs has a critical effect upon the weight and the cost of a transformer of given performance.

index of labour and materials instead of being merely money paid out.

Smoothing Chokes

Three major parameters are needed for the electrical specification of a smoothing choke:— the inductance (L), the DC resistance (R), and the DC to be carried by the winding.

It is clearly advantageous to have a high value of L together with a low value of R. Thus the ratio L/R should be a maximum. Fortunately, the conditions making for this desirable state of affairs are the same for a non-gapped choke carrying AC alone as for a choke carrying DC and having the optimum air gap in the magnetic circuit. Hence the consideration of DC can be omitted from the present discussion.

Let N be the number of turns on the bobbin, A_F and A_C the cross-sectional area of the iron and the area of the window respectively, l_F and l_C the lengths of the mean flux path and the mean turn. Then, working in terms of the initial permeability:—

$$L \propto \frac{N^2 A_F}{l_F} \text{ and } R \propto \frac{N^2 l_C}{A_C}$$

$$\text{Therefore } \frac{L}{R} \propto \frac{A_F A_C}{l_F l_C} = C \cdot \frac{A_F A_C}{l_F l_C}$$

where C is the appropriate constant.

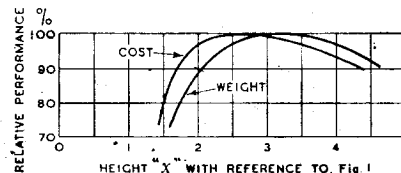


Fig. 4. In the case of a smoothing choke an optimum value exists for the height of the lamination.

Increase the size of this imaginary choke so that all lengths become k times longer without upsetting the geometrical proportions. The new volume, weight and cost will each increase directly as k³. The new value of L/R is:—

$$\frac{L'}{R'} = C \cdot \frac{k^2 A_F \cdot k^2 A_C}{k l_F \cdot k l_C} = k^2 \cdot C \cdot \frac{A_F A_C}{l_F l_C}$$

It follows that in a series of chokes of different sizes but having the same geometrical proportions, L/R varies directly as k² which is itself directly proportional to $\sqrt[3]{(\text{Volume})^2}$, $\sqrt[3]{(\text{Weight})^2}$ and $\sqrt[3]{(\text{Cost})^2}$. This theorem is going to be very useful a little later.

Now consider a choke of typical proportions. Fig. 1 will serve for this purpose from which it can be seen that:

$$\frac{L}{R} \propto \frac{A_F A_C}{l_F l_C} \propto \frac{(1 \times y) [1 \times (x - 1)]}{[3 + 2(x - \frac{1}{2})](2 + 2y + \pi)}$$

If the stack be fixed, i.e. y made constant, the effect upon L/R of varying the height (x) can readily be

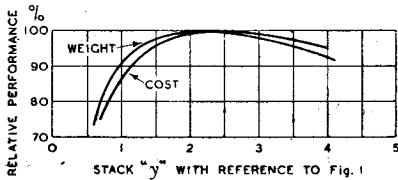


Fig. 5. A choke also has an optimum stack. Practical difficulties prevent it being employed in practice.

deduced. Simplifying the above expression and deleting unnecessary constants we find:—

$$\frac{L}{R} \propto \frac{x - 1}{x + 1}$$

Assign specific values to x and calculate the resultant values of L/R , the weight and the cost.* Our introductory theorem showed that a series of chokes each having the best value of x would produce values of L/R in proportion to $\sqrt[3]{(\text{Weight})^2}$ and/or $\sqrt[3]{(\text{Cost})^2}$. Hence to compare our calculated values for L/R with those given by chokes of optimum design we need only to divide by $\sqrt[3]{(\text{Weight})^2}$ for an equal weight comparison or by $\sqrt[3]{(\text{Cost})^2}$ for an equal cost comparison.

The result of doing this is shown in Fig. 4. A critical ratio exists between the width and the height of the lamination for optimum performance. In the particular instance where the former is 4, as in Fig. 1, the latter should be 2.8.

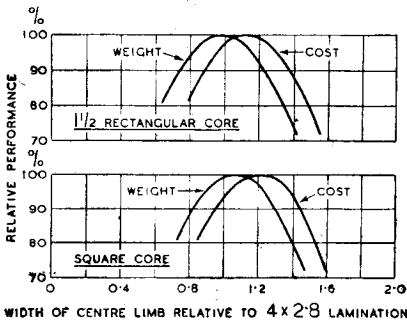


Fig. 6. These curves enable the best widths for the limbs to be determined in the case of a smoothing choke.

In expression (1) above, fix the height (x) at 2.8 and consider the effect of varying the stack (y). It is thus found that:—

$$\frac{L}{R} \propto \frac{y}{2.57 + y}$$

Assign specific values to y and divide the resultant values of L/R

*On account of the better space factor given by chokes and of the smaller average wire gauge, the average bobbin weight per cu. in. is increased to 0.114 lb. and the cost to 3.8d.

by the corresponding values of $\sqrt[3]{(\text{Weight})^2}$ and $\sqrt[3]{(\text{Cost})^2}$. These results are shown in Fig. 5. Again a critical value exists. But for the reasons already discussed only stacks between 1 and 1½ times the width of the centre limb need be regarded as practical. The latter will clearly possess advantages over the former.

To determine the optimum width of the centre limb, fix the height at 2.8, the stack at 1, and call the width of the centre limb z . Assuming the outer limbs to be one-half the width of the centre limb, it can readily be deduced from Fig. 1 that:—

$$\frac{L}{R} \propto \frac{z^2(2-z)(2.8-z)}{(9.6-z)(0.86z+6.28)}$$

$$V_C = (2-z)(2.8-z)(0.86z+6.28)$$

$$(\text{net}) V_F = 4z^2 + 2(2.8-z)z^2$$

Assign specific values to z and proceed exactly as before. The resultant curves are shown in the lower part of Fig. 6 from which the optimum width for the centre limb is seen to be 1.12.

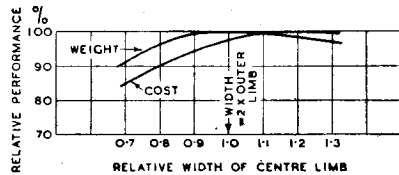


Fig. 7. Showing the effect of varying the centre limb while keeping the outer limbs at a constant width of 0.5.

The above formulae can readily be modified to suit a 1½ stack. Repeating the process on this basis gives the curves in the upper part of Fig. 6. It will be noted that the stack makes very much less difference to the optimum limb width than in the case of mains transformers (see Fig. 3).

Lastly, we have to refute the current superstition that an advantage is gained by making the centre limb less than twice the width of the outer limbs. The argument seems to be as follows: For a given stack of laminations the average value of A_F will be little altered by reducing the centre limb. But more turns can be added as a result, and L varies as N^2 in addition to which these turns, being on the inside, will add little to R . This argument may be plausible but it ignores the most cogent factors. Taking all relevant facts into account the truth is as shown in Fig. 7. If one must meddle with the width of the centre limb it should be made wider and *not* narrower! For many reasons it is altogether undesirable to depart from a 2 to 1 ratio for the widths of the centre and outer limbs.

Unfortunately, we started to design the present choke lamination by assuming "typical proportions" for the very first calculation. The result

must therefore be regarded as a first approximation and the whole process repeated substituting this approximation in place of the original guess. The only effect of the repetition is to increase the optimum height to 3 instead of 2.8 relative to a width of 4.

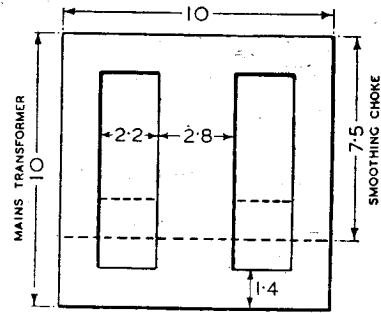


Fig. 8. Showing the optimum proportions deduced in the article. The relative widths of the limbs are the same for both transformers and chokes. But a choke requires to be shorter than a transformer.

The final result is shown in Fig. 8. It is perhaps surprising to see how closely the choke and transformer designs agree in spite of the totally different method of attack. It would appear that a compromise could be reached such that one stamping would serve both purposes without appreciable loss of efficiency in either application.

The foregoing applies specifically to mains transformers and smoothing chokes employing silicon steel. Audio-frequency transformers and components using nickel iron have to be tackled on a different basis, there being nothing to suggest that the optimum proportions will approach those deduced above.

"Unique in Technical Literature"

DURING his inaugural address as Chairman of the Wireless Section of the I.E.E., Dr. R. L. Smith-Rose referred to "the comprehensive series of abstracts and references published monthly in *Wireless Engineer*." He said that these abstracts, which have been prepared by the Radio Research Board for the past fourteen years, "are unique in wireless technical literature and are greatly appreciated by radio engineers and research workers in all parts of the world."

This section of our sister journal occupies 27 pages in the November issue, which also includes original articles on reducing the band-width in frequency-modulated receivers, harmonic distortion in audio-frequency transformers, and the "tracking" of tuning circuits. *Wireless Engineer* is published on the first of the month and is obtainable to order through newagents, or direct from our Publishers at Dorset House, Stamford Street, London, S.E.1, at 2s. 8d. (including postage).

Letters to the Editor

Reproduced Music: Transmitter Volume Compression

Player-Piano v. Gramophone

"CATHODE RAY" is quite correct in saying (in your November issue) that the sound of a note on a piano is exactly the same whether it is played by the finger of an expert pianist or by an inanimate object dropped from a suitable height. What he has forgotten, however, is that piano music consists of a sequence of chords or groups of notes, whose individual intensities may differ widely. It is these contrasts which give "expression" to music played by a good pianist, and make it sound better than the same music played at the same speed by a bad pianist.

The player-piano is quite incapable of reproducing these differences in intensity of notes sounding together, and so it destroys the most important part of the music.

The gramophone, on the other hand, although it fails at the extreme frequencies, and has considerable background noise, and may completely upset the transient at the beginning of each note, reproduces practically all the "expression" put into the music by the performer.

Considering the two as musical instruments, therefore, the gramophone wins, in that it sounds like a rather unusual piano played well, while the player-piano sounds like a good piano "played" extremely badly.

Cambridge. R. W. HAIGH.

I WAS surprised and distressed to find anyone of such wide culture as "Cathode Ray" reviving, on p. 271 of your November issue, an appalling statement which I always hoped had been secretly buried in an unhonoured grave: that "pianist's touch" is bunk. At its first appearance (under the auspices, not of Sir James Jeans, but of an American worker), it was, if I remember rightly, definitely *proved*; and I recollect rejecting it on the spot as one of those occasional scientific "facts" which, spurned instinctively by the wise in spite of "proof," are recognised a little later as fiction arising from incomplete knowledge. Such, for instance, was the rigorous mathematical proof, which some of your readers may remember, that wireless communication between Europe and America was fundamentally impossible. I feel convinced that when more is known about "touch" on a piano it will be found to involve some factor, or factors, which were unknown (or unremembered) at the time

of that proof; just as the unknown (or unremembered) ionsphere justified Marconi's instinctive and wise rejection of the transatlantic fallacy.

As a matter of fact, I see that the invaluable "Abstracts and References" in your sister journal *Wireless Engineer*, while quoting Weyl's paper in Abstract 1856 of 1936, already seem to question its finality by remarking, "but compare Ferrari, Abstract 1061 of 1936," where I find that apparently opposing results were obtained in Italy. But, in any case, the essential wrongness of the statement is unwittingly brought out by "Cathode Ray" when he uses it to indicate that a player-piano can give results indistinguishable from those given by a first-rate pianist. Now, it is a fact that an expert player-pianist can get much more out of his machine than an inexpert, by various little tricks of technique; but, even so, it is only to himself as he sits playing, that, for some subjective reason, the result sounds equal to a Cyril Smith performance—to a passive listener the difference is only too painfully plain. Hence the well-known fact that no one wants to listen to a player-piano and everyone wants to play it.

D'ORSAY BELL.

Chesham Bois.

Post-war Broadcasting

I SHOULD like to put forward a plea for controlled volume compression in post-war broadcasting. The chief arguments in favour of it are:—

1. The range of intensities met with in most musical broadcasts is too wide for the average living room.
2. Most receivers nowadays have diode detectors; it is well known that when the modulation depth expressed as a fraction exceeds the ratio of AC load to DC load harmonic distortion is produced; this sets an upper limit to the depth of modulation for high fidelity.
3. The present system of control by the engineer monitoring the broadcast is unsatisfactory due to its necessarily inexact nature.

With regard to the first argument there are certain exceptions, notably in the case of high-fidelity reproduction, where extraneous noise is negligible and high sound levels can be tolerated. This could adequately be met by controlled volume expansion at the receiver.

The second consideration is of importance to those interested in high

fidelity. Owing to the exigencies of wartime service, the maximum depth of modulation employed by the B.B.C. has been considerably increased, and the inevitable result has been deterioration in quality; this has been particularly noticeable in some recent broadcasts of cathedral services, where the normal absence of overtones in the voices renders harmonic distortion more than usually prominent and unpleasant.

The third point hardly requires elaboration; it stands to reason, for instance, that the present system of monitoring cannot deal satisfactorily with transients; an excellent example of its inadequacy was provided in the recording of the Coronation Service (direct from B.B.C. by transmission line) of the anthem "Zadok, the Priest"; the first climax, at the entry of the full chorus, was obliterated by the control engineer's excess of zeal.

This plea is also to be addressed to gramophone record manufacturers, though, perhaps, for somewhat different reasons.

Some time ago I had the opportunity of hearing a large number of records on an electric gramophone which had a total harmonic distortion of less than 1 per cent. at 1,000 c/s, as measured on a Marconi-Ekco Distortion Factor Meter, and a correspondingly good frequency response; this enabled considerably more discrimination than usual to be applied, and the correlation between high quality and low level of recording was astonishingly complete.


Rugby. A. H. KING.

YOUR leading article in the October issue raises, in good time, the future of broadcasting. One would hesitate on many grounds to welcome the competition due to pure commercialism, but there are many who would welcome more competition in ideas than seems obtainable by the present system. One suggestion I should like to put forward for consideration is that a certain proportion of broadcast time should be sold to advertisers for the benefit of the hospitals. The public at large would be making a contribution, through licences, whilst the profits of the advertisers would come from their sales to a wide public.

If this idea stimulates thought and discussion in relation to the problems of providing a better broadcasting system, some good will come of it.

"HOPEFUL."

Manufacture of piece-parts

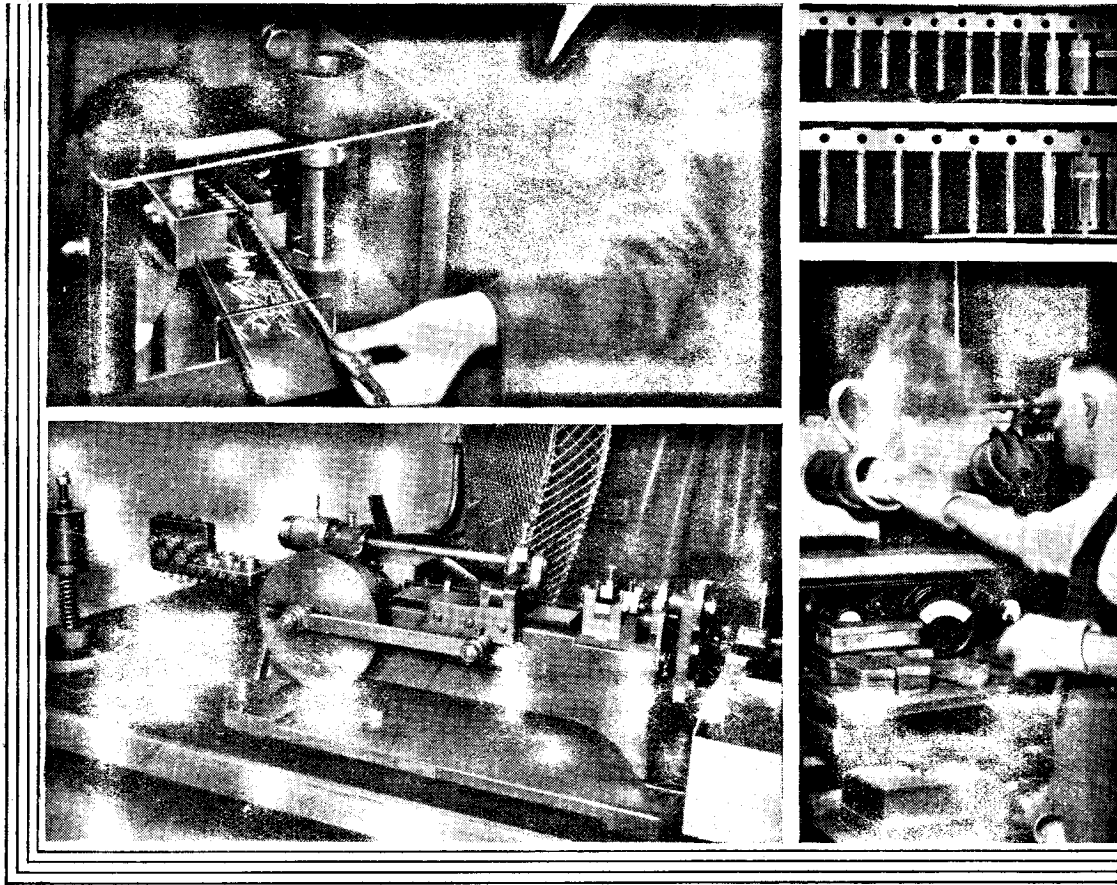

MASS production piece-part manufacture and processing are now an essential part of valve making: millions of these items are needed annually.

Our illustration is designed to show some of these manufacturing processes, while the two illustrations (top right) give an idea of the number of operations required on base pins.

BRIMAR
 (BVA)
VALVES

STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.



ACHIEVEMENT

“ Since the first Philips lamp was made, just over half a century ago, the House of Philips has played an ever-increasing part in peace and war in harnessing electricity more effectively and efficiently in the service of the nation.”

PHILIPS



LAMPS • DISCHARGE LIGHTING • RADIO RECEIVERS TRANSMITTERS • VALVES & THERMIONIC DEVICES • MEDICAL & INDUSTRIAL X-RAY & ELECTRO-MEDICAL EQUIPMENT • ARC WELDING EQUIPMENT & ELECTRODES • LIGHT ALLOY RESISTANCE WELDING PLANT • MAGNETIC OIL FILTERS • MAGNETS • SOUND AMPLIFYING INSTALLATIONS

PHYSICAL FOUNDATIONS OF RADIO

IV.—Composite Cathodes, Photosensitive Surfaces, Cold Emission

By

MARTIN JOHNSON, D.Sc.

IN the last article we emphasised the controlling influence of the work-function over the emission of electrons from a hot cathode, the expression $e^{-\phi/kT}$ in the Richardson equation indicating that for a bright filament at 2,000 degrees a reduction of ϕ from the $4\frac{1}{2}$ electron-volts of pure tungsten to 2 would increase emission about a million-fold. Pure metals refractory enough to stand up to heating all possess work-functions in the neighbourhood of 4, 5, or 6 volts, so that not much is to be hoped for in simple materials. Instead, the dull-emitters required to supply copious anode currents for a low consumption of heating power in small radio valves are often chemical compounds painted or otherwise coated onto a base metal filament or onto the outside of a tiny cylinder which surrounds the actual heating element. Whether thus directly or indirectly heated, the emitting surface is at a much lower stage of incandescence than when the electrons were from the "conduction levels" of the tungsten.

The use of these cooler emitters raises three questions of interest. First, what chemical elements and compounds have work-functions marking them out as suitable emitters. Secondly, why is the reduction of work-function more effective for a very thin coating than if the new material were to replace completely the old refractory material. For instance an alkali film upon nickel or tungsten may be a better emitter than the bulk alkali alone, and not merely better than the nickel or tungsten. Thirdly, there is the practical question of how the coating is to be made and stabilised for long life of a valve.

Alkalis and the "Adsorbed Grid."

On correlating thermionic and chemical properties, it will be found that the alkali metals (sodium, potassium, caesium, etc.) and the alkaline earths (strontium, barium, etc.) have lower work-functions than other elements. The cause involves their crystal structure and atomic size as well as their ease of ionisation or loss of an electron from the individual atomic structure. The crude idea of manufacturing cathodes out of any of these elements is not helpful; among other reasons some have extremely low melting

temperature. Their better use as coating a more refractory base such as tungsten depends upon the phenomena of "adsorption," i.e. the adherence of a foreign layer to an underlying surface, the layer clinging with a strength greatly in excess of its attachment to its own kind. For example, an alkali might melt at a low temperature, its atoms easily separating from their own kind, whereas far more drastic heat treatment might be needed to evaporate it from some other metal on which it was "adsorbed." The prefix "ad-" in contrast to absorbed denotes that the attraction is that of a single layer of atoms to a surface, rather than the swallowing up of even a small bulk of the one material in the other.

Imagine the electrical effects of such a thin adsorbed layer of an alkali such as caesium upon tungsten. The layer is electropositive to the underlying material, having an atomic field which facilitates migration of electrons. The layer must not necessarily be regarded as having lost electrons, though in some cases where an alkali vapour is squirted at a hot metal it does rebound in the ionised state as positively charged remnants of atoms whose electrons have been captured by the target metal. But the nature

diagrams to represent how conditions vary from the interior of a cathode to the interelectrode space and then to the anode, and the effects of the "adsorbed positive layer as grid" may be shown similarly. (Fig. 1.)

Thin Potential Barriers.—When discussing in an earlier article the escape of electrons from one equipotential to another inside the metal, we made use of the behaviour associated with their "wave-like" properties. A completely "particle-like" electron would not find the barrier of (b) in Fig. 1 any less of an obstruction than the barrier of (a) to passage from left to right, if the initial height of the step were the same: in each case it would have to acquire kinetic energy equal to the step in order to escape. But the "wave" character of the electron confers a finite probability of a non-zero wave amplitude on the far side of the barrier; this amplitude falls rapidly as the thickness of the barrier increases, and only remains of importance for two or three hundred millionths of a centimetre. The sudden change over the thickness of an adsorbed layer provides one or more very thin walls in any complex potential barrier and the penetration of these plays a large part in emission from coated surfaces.

The "effective" work function is one way of representing the increased facility of electron escape, though it must be remembered that the emission

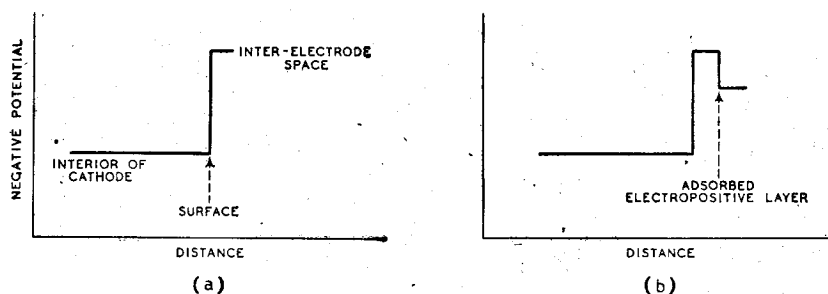


Fig. 1. Potential (a) at "clean" and (b) at "coated" cathodes. The variation of potential will actually be more complex, but has been simplified here to bring out the main feature of difference.

of the field set up by the layer is much as if we could imagine the grid of a valve to be positively charged and moved up to within a ten millionth of a centimetre of the cathode.

We have already utilised potential

constant "A" in Richardson's equation may also be modified. Observed values of ϕ , compared with 4.54 volts for tungsten and 5.03 for nickel, may be inserted in the equation we used and the increased emission in thou-

Physical Foundations of Radio—sand- or million-fold computed. For barium we have 2.11 volts, caesium 1.81, while for tungsten covered with caesium 1.36 and covered with barium as low as 1.2. Variations depend on whether the layer involves only adsorbed metal or has oxygen in the "sandwich." The latter makes a more complex potential diagram of peaks and valleys, and apart from its electrochemical effects serves to bind the coating against evaporation by introducing a new chemical term into the forces of adsorption.

These composite cathodes could not stand the high temperatures of the bright emitter; but they have no need to. There is both numerator and denominator on the exponential term of our Richardson equation, and if a tungsten emitter yields 8 milliamps anode current for a watt heating at 2,600 degrees, the same with a thorium layer on it may yield 40 at only 1,800 degrees and with barium coating 100 at 1,100 degrees.

"Activating" a Composite Cathode.

—These surface layers which are so essential for full emission may arrive by external deposition or by diffusion from an impurity dissolved in the cathode itself. As example of the less refractory and more highly emitting but less easily replenishable layers, a mixture of barium and strontium carbonates is sprayed or painted on to a cathode; the whole is heat-treated until the carbonates break up into

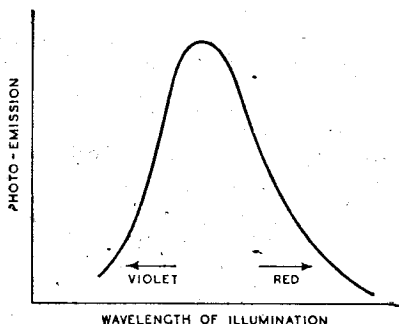


Fig. 2. Selective response of alkali photo-cell. The curve is usually unsymmetrical, and its peak may be in the green, red, or infra-red, according to how the adsorbed surface layers have been treated.

oxides and give off gas, then at another carefully calculated temperature the oxygen atoms arrange themselves into their sandwich with the two or more metals. It is clear that the subtle cookery will be ruined by any subsequent trace of vapour, and such valves need rigorous "degassing" before sealing, if their life is not to be extremely short.

To obtain one's layer from inside

instead of outside, offers more chance of repairing loss of emission without remaking the valve: thoriated cathodes are worth study as example of this other mode of forming the surface. Early in the development of the tungsten lamp industry, it was found that at incandescence the filament tended to recrystallise into long hair-like crystals, which on AC would "rattle" and lead to rapid "burn-out." To prevent this, about 1 per cent. of thorium oxide was added in manufacture. The work-function of thorium itself is about 3.4 compared with tungsten 4.5, but tungsten coated with thorium shows 2.4, offering enormous increase of emission. To form or activate the thoriated tungsten simply means therefore to spread some of the dissolved impurity over the surface in the correct chemical state. "Flashing" the wire at a preliminary temperature of 2,800 degrees reduces some of the thorium oxide to metallic thorium, and is followed by a longer "activation" at a rather lower temperature which allows a trace to diffuse up to the surface but not to evaporate therefrom. A trace of dissolved carbon assists the reduction of the oxide, and there are other little-understood tricks based upon the physicist's experience that "to fetch out an impurity, send another one in" is sometimes good advice.

Photo-Cathodes.—Hitherto we have only considered thermionics, or the emission of a metal's electrons from a pure or a coated surface by heating. But television and other specialised developments of electronics also require the emission from cathodes which are not heated but are exposed to light or other radiation to which they are sensitive. If we recall that energy had to be supplied to the "gas of free electrons" within a metal in order to evaporate some portion of it into a vacuous space for collection on an anode, it is reasonable to look for other modes of supplying that energy than mere heating of the interior of the whole metal.

A beam of "light," visible or ultra-violet or infra-red, carries electromagnetic energy just as a beam of the much longer wavelengths generated by a valve oscillator and its resonating circuit. The vibration of the electric vector in the radiation communicates energy to the electrons in the metal surface which is absorbing it, and if the frequency is suitable some electrons will escape under this stimulus.

In such a science of "photoelectricity," barriers and work functions are discussed in the same way as in "thermionics," but there is no counterpart of the Richardson equation as the emission is not temperature-

controlled. In fact any variation of photo-emission with heating is apt to mean merely that a composite surface is getting altered in structure, and most laws of photoelectricity assume the cathode remains cold.

The energy with which the electron emerges is also quite different from that of thermions, and depends upon the frequency of the light employed. The practical uses of photoelectric emission mostly depend on the property that the anode current or number of electrons emitted is conveniently proportional to the light intensity. Alkali adsorbed layers, however, are as important in photoelectricity as in

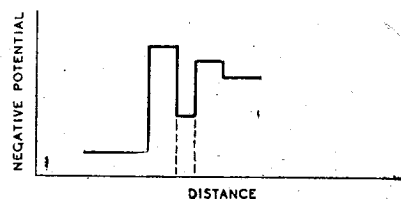


Fig. 3. Idealised shape of possible potential barrier at caesium-silver-oxide photo-cathode.


thermionics, and quite low melting materials can be used as the cathode is not heated. The commoner pure metals are not sensitive to light of lower frequency than ultra-violet, but potassium and the other alkalis do respond to visible light. They also show selectivity, and yield a larger emission over a preferential range of wavelength (Fig. 2) even while the intensity of light remains constant.

It is probable that this selectivity would not occur with a perfectly pure surface: even when this is prepared by driving atomised metal electrolytically through the sealed walls of the photo-cell it is almost impossible to avoid traces of foreign vapour if only from the glass, and the "alkali" is usually a "sandwich." The form of the response curve (Fig. 2) depends on the exact ingredients and seems to smooth out disconcertingly if extreme purity is for once achieved. A favourite sandwich is a layer of caesium only one atom thick separated from a base of silver by an electro-negative layer of oxide or hydride. The "activation" sometimes involves flashing a gas discharge in the cell.

The exact form of the most profitable potential barrier has been disputed; it probably includes a valley between two summits somewhat as we have expressed in Fig. 3. Fowler, who has done much to make these processes intelligible, suggested that the selectivity depends on the "valley" allowing formation of stationary electron waves analogous to the stationary electromagnetic waves in a UHF

resonator. It is a possible way of accounting for the characteristic property of these alkali sandwiches of showing selective response to illumination of a particular frequency. By ingenious treating of these layers, chemically or thermally or by ionic bombardment in a gas discharge, the peak of the curve of Fig. 2 can be raised or lowered and also shifted sideways until the sensitivity is in the visible or ultra-violet or infra-red region, and the resulting "photo-cell" adapted to television, industrial control devices, gadgets such as burglar alarms, or cinematography.

"Field" Emission.—We have considered emission stimulated by heating a cathode or by illuminating it, but these are not the only ways in which the metal's electrons can be extracted for use in a valve. If a very high anode potential is applied extremely close to the metal surface, the "clean" barrier previously discussed can be reduced to atomic thinness; the sloping line already illustrated in a previous account of the ordinary potential graph becomes so steep that the top of the barrier is a razor-edge. (Fig. 4.) Hence, as in the thinning by adsorbed layers, a finite leak through becomes possible. In this case, however, the emission depends on field and not on temperature. These "field" currents from a cold cathode become important at 10^7 volts per cm., but grids for many kilovolts at interelectrode distances of a small fraction of a millimetre are obviously not easy to design. We

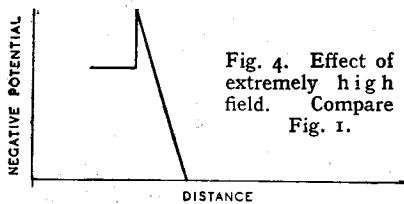

mention only the X-ray tubes designed by the Philips workers in Holland and the Westinghouse workers in U.S.A. to utilise this phenomena. In one of these, a discharging condenser controlled momentary fields of enormous strength, and the "cold" emission reached 2,000 amps. at 100,000 volts for 10^{-8} second. Obviously, space charge difficulties confine such currents to brief transients, but they were valuable for instantaneous X-ray photography.

Secondary Emission.—In addition to field emission and photo-emission, electrons can be ejected from a cold cathode by bombarding it with another beam of electrons from outside. It is a matter of exchange of momentum

between impinging electrons and the first few atomic layers near the target's surface. Reaction with the target atoms causes some of their associated electrons which are in a semi-free state to acquire sufficient backward momentum for ejection right out of the surface. Under favourable conditions each impinging or "primary" electron ejects several such "secondaries." This is used in certain "electron multipliers" which amplify without a thermionic current at all, a photoelectric stream ejecting multiple secondaries at each of several successive anodes. Secondaries also play a large part, of course, in the dynatron characteristic of an oscillating triode. But in many valve applications secondary emission is a nuisance, and the early history of the pentode shows the designer's ingenuity in circumventing its effects.

Thin Film Field Emission.—We mention finally a curious group of effects which may in the future, we think, play a large part in valve practice. Strictly it comes under "cold" and "field" emission, but it is also in a sense a "secondary" emission, and so combines our two last cases. It occurs with the thin and stable oxide film which covers aluminium and some other metals. When bombarded with a primary beam of electrons or with the positive ions from a trace of gas, there is emitted from the aluminium an enormous rush of electrons. The ratio of secondary to primary may reach thousands, so it is clearly not the usual "secondary" exchange of momentum, and suggests a high local field. The best known experiments are those of Malter, whose name is often given to this kind of emission. The enormous local field is probably derived from adjacent layers of opposite charge in the oxide: the "anode volts" are on an "electrode" which is simply the neighbouring atom grossly distorted. Maintenance of the field is probably by adsorption of positive ions from gas traces or by the residual charge left when the first secondaries depart. The emission is therefore subject to uncontrollable time lags, and will need closer study before it can be reliably utilised. That is no excuse for despising it as a mere laboratory freak to amuse the physicist: thirty years ago, O. W. Richardson with no interest whatever in communication engineering, made possible all modern radio by his purely scientific curiosity about why electrons should ever escape from metals. It is such disciplined curiosity which provides the foundation on which the technician is later to build.



**VARIABLE CONDENSERS
—DRIVES—
AUTOMATIC TUNERS**

WE are designing and building even better equipment with our enlarged and extended facilities and these improvements will be available for your use when the present struggle is over.

For the time being domestic receiver design and production has ceased but your radio receiver manufacturers will be ready to equip their sets with General Instrument variable condensers, automatic tuners and other G.I. devices as soon as conditions permit.

Always remember General Instruments
**VARIABLE CONDENSERS—DRIVES
—AUTOMATIC TUNERS**

Register your name with our Representative now. He will forward you information on our products as soon as they become available.

**THE GENERAL INSTRUMENT
CORPORATION
ELIZABETH, N.J., U.S.A.**

Exclusively Represented by
Frank Heaver Ltd. Kingsley Road,
Bideford, N. Devon



**COME LOVELY
FLOWERS**

And so be that from the darkness of the present hour will emerge a brighter day, on the brain and brawn of modern industry, will be utilised in furthering peacetime products and pursuits. While serving the Government to-day we are broadening both creative and manufacturing possibilities for a happier world to-morrow. Astatic engineers are available to work in co-operation with electronic engineers in the development of new wartime equipment, especially as it may have to do with pickup and transmission of sound. Astatic crystal microphones, pickups, crtridges and recording devices will be available again for your use when those brighter days are here.

Register your name with our Representative for your future benefit.



**THE ASTATIC CORPORATION
YOUNGSTOWN, OHIO, U.S.A.
TORONTO, CANADA.**

Exclusively Represented by
Frank Heaver Ltd. Kingsley Road,
Bideford, N. Devon

INSTRUMENTS : *Test and Measuring Gear and Its Uses*

By W. H. CAZALY

VIII.—Multivibrators

THE multivibrator is a device that generates alternating potentials of non-sine-wave form. The value of such a wave-form lies in the fact that it can be analysed into a large number of harmonics of the fundamental frequency, and these harmonics can be selected by tuned circuits. Thus, the multivibrator may be regarded as a kind of generator at the output of which there are simultaneously present many frequencies, each an exact multiple of the fundamental. For example, if the fundamental is 100 kc/s, or 0.1 Mc/s, there may be available for use at the output as many as 500 frequencies, starting with 0.1 Mc/s and going up, at intervals of 0.1 Mc/s—i.e., 0.2, 0.3, 0.4, 0.5 Mc/s, etc.—to as high as 50 Mc/s. Whether they become usable at these high frequencies depends on the design and power of the multivibrator. At the other end of the frequency gamut, it is possible to arrange a multivibrator circuit to oscillate at a frequency as low as 1 c/s.

Further, it is possible to lock the fundamental frequency of a multivibrator readily to that of some high-precision generator, so that the multivibrator fundamental and all the harmonics each have precision of frequency of as high an order as that of the primary controlling frequency. One obvious use of such a controlled multivibrator lies in the quick and accurate calibration of receivers, especially when many of them are being so dealt with. The multivibrator is set going at, say, 100 kc/s, or 0.1 Mc/s, and its output fed to the input terminal of the receiver under test. Then by tuning the receiver over the range required to be calibrated—say 6 to 8 Mc/s—signals will be found at every 0.1 Mc/s interval, and these points will give a fairly accurate calibration scale. When once set up, the multivibrator does not have to be touched or retuned; all the required frequencies for calibration present are simultaneously in its output, and each has the same accuracy as that of the primary controlling or triggering frequency.

The multivibrator is a comparatively simple device to construct and may be either battery or mains driven.

It consists essentially of two resistance-capacitance coupled amplifiers arranged in a mutual feed-back circuit as shown to the right of the dotted line in Fig. 1, which is a practical circuit as it stands. Such an arrangement—quite apart from the crystal oscillator on the left of the dotted line, which is the accessory triggering source—will oscillate on its own in the manner peculiar to this type of circuit; it is, in fact, a form of "relaxation" oscillator.

Frequency Control

The action of the multivibrator has been the subject of close study, and the sequence of events over a complete cycle of oscillation was described, with the aid of oscillograms in an article by Dr. Edward Hughes in the last issue. In view of this recent exposition we will not devote space here to the basic principles of operation, but pass on to the modifications of the multivibrator necessary for test purposes.

Left entirely to itself, the multivibrator circuit does not perform its reversals at a very constant frequency, since at the moments of equilibrium, any random voltage, however tiny,

wave-forms shown in Fig. 2 will indicate the outlines of the effect of applying a controlling voltage to a grid.

An uncontrolled wave-form is shown in Fig. 2 (b). On this line, at point A, the potential of the grid is not very far from the "zero" or change-over value—i.e., the value of negative potential at which anode current just begins to flow. It can be easily jolted, as it were, towards the zero line by an injected voltage in the right phase, which is at point A in Fig. 2 (a). If it is large enough, this controlling voltage can cause the change-over to take place a little earlier than it would do naturally if solely dependent on the circuit constants of the multivibrator alone.

Once the change-over is started, the grid and anode potentials very soon move well away from the zero line and so can remain unaffected by the comparatively small controlling voltages. This brings out the interesting and valuable fact that a natural multivibrator frequency can be controlled by a voltage of sine-wave form at a much higher frequency—in practice, as much as ten times the frequency. The net effect as shown on an oscilloscope is a wavy line of the shape shown

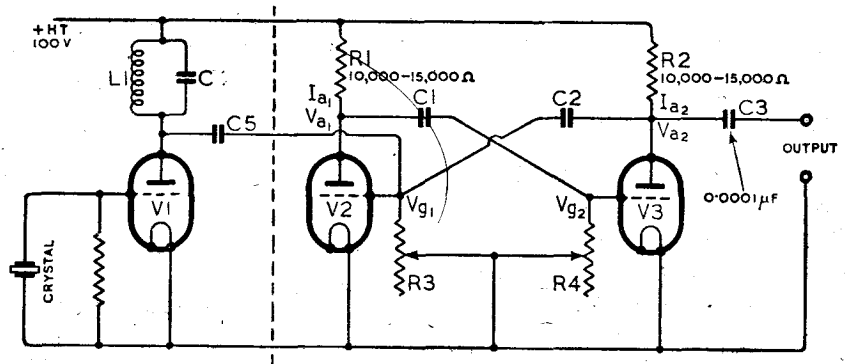


Fig. 1. The multivibrator circuit is shown to the right of the dotted line after C5. The values of C1, C2, R3 and R4 depend on the frequency required, and are calculated from formulæ given in the text.

can set off the change-over of conditions a little before or after it would occur naturally. This leads on to the use of a controlling or triggering voltage that may be injected from an external generator of high precision as regards frequency. A glance at the

in Fig. 2 (d). This wave-form is obviously composed of a very large number of harmonics as well as the fundamental. Whether these harmonic voltages are of sufficient amplitude to be usable depends partly on the power in AC form developed by the

multivibrator, partly on the order of harmonic, and partly on the overall range of frequencies included by the fundamental and its harmonics.

In a usual type of battery-driven vibrator used for RF work at what are conventionally taken to be the "short waves," up to the 100th harmonic of a 200 kc/s fundamental

of whistles that have been counted. For example, let it be supposed that a receiver covers 18 whistles in moving from some one multivibrator harmonic to exactly double the frequency at which the receiver was first tuned. Then it will end up on the 2×18 th or 36th harmonic. With this as a reference point, other harmonics can be

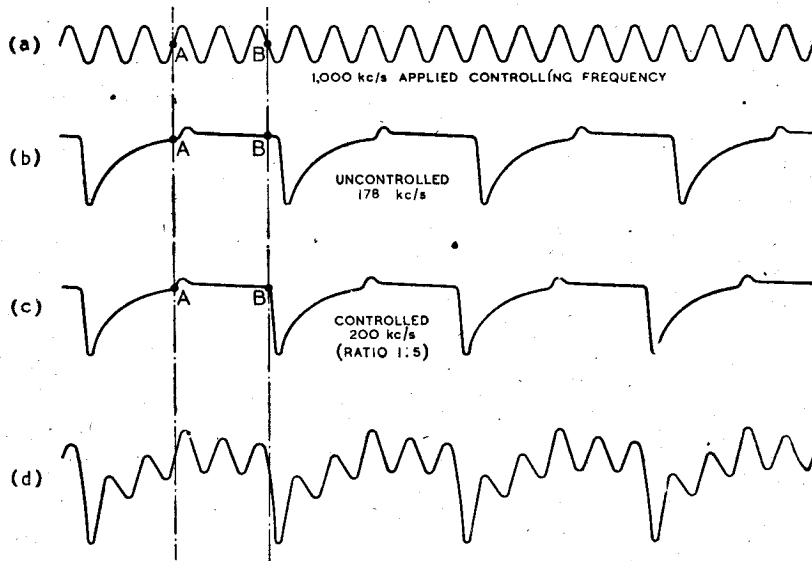


Fig. 2. Diagram showing the action of a triggering sine-wave potential in controlling the frequency of a multivibrator. (a) is the controlling sine-wave voltage. (b) is the uncontrolled multivibrator grid potential. (c) is the grid potential when controlled—without the sine-wave fluctuations superimposed. (d) is the resultant that would appear on the screen of a cathode-ray oscilloscope.

is normally found of practical utility. Beyond that, not only are the harmonics weak, but they are so closely adjacent that it is difficult to distinguish between them.

In this connection, it will be useful to note how the particular harmonic in use can be ascertained when working amongst the high ranges. If it is desired, for example, to ascertain whether one is working on, say, the 34th or the 35th harmonic, the procedure is to tune a CW receiver exactly to any harmonic of that order (using, for instance, the zero-beat-method), and then change the receiver tuning to exactly double the frequency. If this cannot be done with the receiver scale alone, a simple temporary oscillator can be set up to beat with the multivibrator harmonic and the 2nd harmonic of the oscillator used to indicate twice the frequency. While tuning the receiver through to this 2nd oscillator harmonic, the whistle obtained as the *multivibrator* harmonics are passed are counted. Then, when the receiver tuning is halted dead on the oscillator 2nd harmonic (which gives the last whistle) it will then be tuned to the multivibrator harmonic given by $2 \times N$, where N is the number

distinguished by counting whistles up and down the tuning range. Further, if the fundamental is known, the precise frequency involved at any harmonic can be calculated. Thus, if the multivibrator fundamental is 200 kc/s, the 36th harmonic would occur at a frequency of 200×36 kc/s, or 7.2 Mc/s.

It will have been noticed in Fig. 2 that it is necessary, if locking is to take place, for a not excessive difference in phase between the controlling and the multivibrator frequencies to be present. When widely asynchronous either locking does not take place, or it may do so at some undesired ratio between the controlling and natural frequencies. Hence, it is necessary that the multivibrator should be designed so that its natural uncontrolled frequency is *approximately* some desired ratio in respect to the controlling frequency chosen.

Frequency Calculations

The natural frequency of a multivibrator is determined mainly by the time-constants of the coupling condensers and grid resistances— C_1 , C_2 , R_3 , and R_4 , in Fig. 1—and when

RAYTHEON

WORLD'S LARGEST EXCLUSIVE TUBE MANUFACTURER

NEW Electronic developments have created new valve designs. We at Raytheon are indeed fortunate to be placed in the advantageous position of engineering these new intricate designs. Our research engineers have developed special valves to meet the newest of today's electronic developments. We are meeting the demand for valves used in special applications. . . . Raytheon has always been proud of the ability of its engineers to meet any emergency demand for unorthodox valve designs. To-day our pride has been more than justified by the electronic problems they have solved and the quality of the product they are fabricating. When the present conflict is over RAYTHEON engineers will be in possession of priceless electronic experience to build advanced valve designs for better transmission and reception. Register your name with our Representative now for your future benefit.

RAYTHEON
PRODUCTION CORPORATION
 NEWTON, MASS., U.S.A

* * *
 Exclusively Represented by
Frank Heaver Ltd Kingsley Road,
 Bideford, N. Devon.

CROWE

RADIO COMPONENTS

ESCUTCHEONS
 TUNING CONTROLS
 DIALS—REMOTE CONTROLS
 POINTERS, ETC

FOR BOTH HOME AND COMMUNICATION EQUIPMENT

The Crowe organisation, now a part of the Arsenal of Democracy, will have available enlarged facilities after the war.

The Crowe plant will again be devoted to the supply of smartly designed and executed dials, dial scales, escutcheons, pointers and the like for radio receiver manufacturers all over the World.

Crowe also manufactures precision tuning devices for Communication Receivers.

Register your name now with our British Representative for details as soon as available of Crowe Products.

CROWE NAME PLATE & MANUFACTURING CO.

3701 RAVENSWOOD AVENUE
 CHICAGO, ILL., U.S.A.

Exclusively Represented in Great Britain by
Frank Heaver Ltd. Kingsley Road,
 Bideford, N. Devon.

Instruments—

some particular multivibrator fundamental is desired, it can be derived approximately from the formula

$$f = \frac{1}{(R_3 C_1) + (R_4 C_2)}$$

where R_3 and R_4 are in megohms, C_1 and C_2 are in microfarads, and f is in cycles per sec. If it is assumed that the time constants are to be equal (so that $(R_3 C_1) = (R_4 C_2)$) the values of the capacitances and resistances can be found as a first rough design approximation from

$$R = \frac{1}{2fC} \text{ and } C = \frac{1}{2fR}$$

These are only approximations to give an idea of the order of resistance or capacitance required, and in making up a multivibrator, it is usual to make the grid resistances variable, the two being ganged on the one controlling shaft. They can then be adjusted in use until locking takes place.

The upper limit of oscillation frequency is set by the amplification obtainable with resistance-capacitance coupling and hence is not very high—only of the order of 200 kc/s or so. If the high-order harmonics are to be preserved at reasonable strength, the whole circuit must be designed as for RF amplification with low losses.

The multivibrator can also be used for the production of audio frequencies and may be triggered by some stable and accurate AF generator such as a magnetostriction bar or electrically driven tuning fork; the main difficulties then arise in designing sharply tuned AF filters for the selection of the desired harmonics in the output, which is not so easy at AF as it is at RF. It is usual to employ tuned bridges for the purpose, or else to start with a comparatively high controlling AF


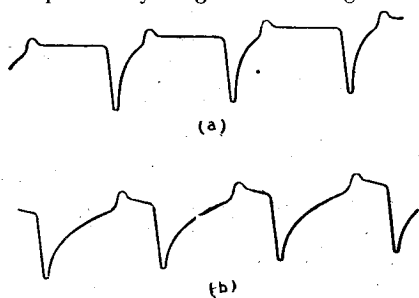


Fig. 3. Diagram showing the effects of differing time-constants on the grid potential wave-form.

(say 10 kc/s) and use a series of vibrators to obtain lower frequencies in multiples of ten. Usually the time constants are made equal in the two amplifiers. If they are unequal, the effect is to make a difference between the duration of the positive and negative part-cycles of grid or anode poten-

tial, as shown in Fig. 3. In the upper wave-form (a), the negative part-cycle is of shorter duration than the positive. This indicates that the time constant of the condenser and resistance connected to the grid at which the potential is being observed is larger than that of the other. If the potential were observed at the other grid, it would be found to have the shape shown in the lower wave-form (b).

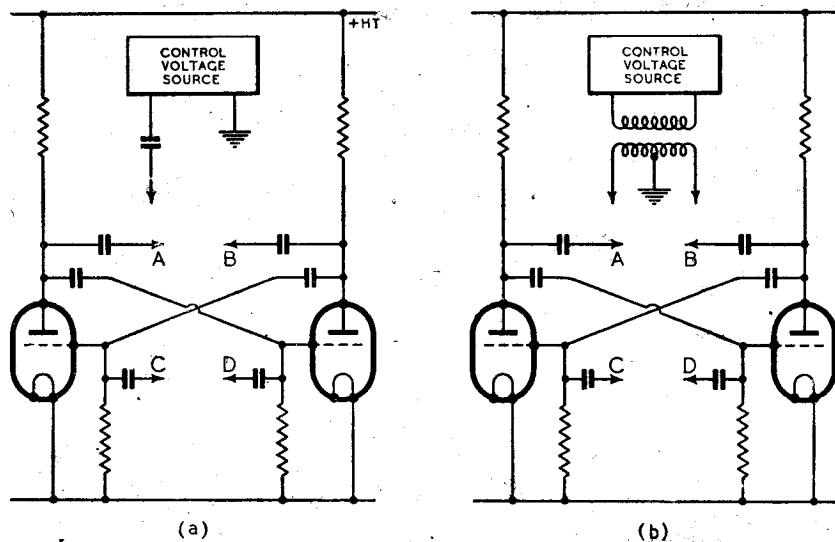

CIRCUIT	CONTROL APPLIED	RATIOS CONDUCTIVE TO OSCILLATION
(a)	A, B, C OR D ONLY	ODD OR EVEN
(a)	A & B SIMULTANEOUSLY OR C & D SIMULTANEOUSLY	EVEN
(b)	A & B IN "PUSH-PULL" OR C & D IN "PUSH-PULL"	ODD

The ratios of the controlling to the natural frequency at which locking tends to take place are determined by factors that are not so much abstruse as rather laborious to study. They will become clearer if several extended representations are made, to show the phase relationships between the natural and controlling frequencies at grids and anodes. In the first place, the ratios obtainable can only be integers, or complete numbers. In the second place, this fact limits the range of frequencies at which a multivibrator can be set up for locking with a given controlling frequency. For example, if the controlling frequency is 1,000 kc/s (a crystal oscillator, for instance), possible ratios are only 5, 8 and 10. At a lower ratio than 5 the multivibrator frequency would be too high to be easily set up; at the higher ratios, only 5, 8, and 10 are exactly divisible into 1,000. Hence, in such a multivibrator, locking could take place only when the fundamental

was 200, 125, and 100 kc/s. Which of these possible ratios was selected would depend partly on the relative magnitudes of the controlling and natural potentials, and partly on where the controlling voltage was injected—whether at grid or anode, singly or at both.

The effect of increasing the controlling voltage is to make the multivibrator jump from one locking fre-

Fig. 4. Table showing the ratios between the controlling and multivibrator fundamental frequencies to be expected with a few common circuit arrangements.

quency to the next lower, with increasing uncertainty and instability as the divergence between the natural and the controlling frequencies increases. The effect of the point of application of the controlling frequency is perhaps set out in the simplest practical form of a table referring to Fig. 4, so that whether the output of the controlling generator is applied to one grid or one anode, or to two grids or two anodes depends on whether odd or even ratios are desired.

The multivibrator lends itself to an

The subjects already dealt with in this series of articles on instruments are:

- I. Standard Signal Generators and Test Oscillators (March, 1942).
- II. Output Meters and Attenuators (April, 1942).
- III. Valve Voltmeters (June, 1942).
- IV. Testers and Bridges for Inductance and Capacitance (July, 1942).
- V. Beat Frequency Oscillators (August, 1942).
- VI. Electrolytic Condensers: Inductance and Capacitance at Radio Frequencies (October, 1942).
- VII. Valve Testers (November, 1942).

increasing number of practical uses. It has been mentioned earlier as a source of precision signals in a laboratory or workshop for calibration or frequency determination purposes. It is also employed in various types of electronic switching circuit. One of its most interesting uses lies in very high accuracy primary or sub-standard wave- or frequency-meters in which the general arrangement is to control a series of multivibrators by a single extremely high-precision crystal oscillator. The generating of frequencies starts with this temperature-controlled crystal, which is placed in an oven regulated by a gas-discharge valve circuit and a bridge that is unbalanced by changes of temperature. The output of this crystal oscillator is fed, through buffer amplifiers, partly to an output terminal and partly to a multivibrator working at a fundamental 1/10th of the crystal frequency (which is usually 1 Mc/s). The output of this multivibrator is fed partly to an output terminal and partly to another multivibrator which is working at a fundamental of 1/10th that of the first vibrator. This goes on, in a chain of multivibrators, until one at a frequency of 100 c/s ends the gamut of frequencies covered. The output of the 1,000 c/s stage is amplified sufficiently to work an electric clock, the time shown by which to a small fraction of a second may be checked by star transit observations with astronomical instruments or against time signals from some standard transmission. With such costly and elaborate apparatus, an accuracy better than one part in many millions is obtainable with a constancy extending over many months. In fact, frequency can be known to a much higher accuracy than either the velocity of transmission or wavelength.

The Wireless Industry

SIMMONDS AEROCESSORIES, LTD. have been granted the registered trade mark of "Simmonds" for their self-locking nuts.

The latest illustrated list of service components issued by Norman Rose (Electrical), Ltd., 80, St. Mary's Road, London, W.5, includes many additions such as line cord replacement resistances, HF chokes and spindle extension couplings for volume controls. Copies are free to dealers on application.

We have received a copy of "Increased War Production," a comprehensive catalogue of the meters, tools, etc., made by Runbaken Electrical Products, 71-73, Oxford Road, Manchester, 1.

Through an error in repeating old copy, the advertisement of Vortexion, Ltd., in our November issue gave details of an earlier 50-watt amplifier chassis. This has been superseded by an improved version priced at £18 10s. plus 25 per cent. war increase, as announced in the October issue.

"Instruments," Part VI.—A Correction

THE section dealing with the principle of the "Q" meter and starting on line 28 of the first column of page 236 should read:

"Let the applied voltage be V_1 , and the voltage across the coil L be V_2 . When measured by the valve voltmeter, V_2 will be found much greater than V_1 —in fact, it will be $Q \times V_1$.

$V_1 = IR$
and $V_2 = I\omega L$ Where I is the current through the tuned circuit.

$$\therefore \frac{V_2}{V_1} = \frac{I\omega L}{IR} = \frac{\omega L}{R} = Q$$

"If now . . . etc."

Two other points, the balancing resistance mentioned in column 3, page 232, is, of course, R_3 or R_4 and not R_2 ; and in the circuit of Fig. 5 the live lead of the valve voltmeter should be joined to the junction of R and the circuit LC.



"Try to get China," said OO,
"Let's see what this old set will do."

But sad to relate
The strain was too great
For it blew up! Oh, what a to-do.

See that **FLUXITE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for 30 years in Government works and by leading engineers and manufacturers. Of Ironmongers—in tins, 8d., 1/4 and 2/8.


Ask to see the **FLUXITE SMALL-SPACE SOLDERING SET**—compact but substantial—complete with full instructions, 7/6.

Write for Book on the art of "soft" soldering and for Leaflet on **CASE-HARDENING STEEL** and **TEMPERING TOOLS** with **FLUXITE**. Price 1d. each.

TO CYCLISTS! Your wheels will NOT keep round and true unless the spokes are tied with fine wire at the crossings AND SOLDERED. This makes a much stronger wheel. It's simple—with **FLUXITE**—but IMPORTANT

THE FLUXITE GUN
puts Fluxite where you want it by a simple pressure. Price 1/6, or filled 2/6.

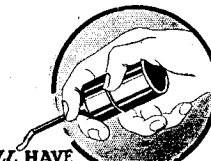FLUXITE LTD.
(Dept. W.W.),
BERMONDSEY STREET, S.E.1.



ALL MECHANICS WILL HAVE
FLUXITE
IT SIMPLIFIES ALL SOLDERING

BOOKS ON WIRELESS

issued in conjunction with "Wireless World"

	Net Price	By Post
"FOUNDATIONS OF WIRELESS," by A. L. M. Sowerby, M.Sc. Third Edition revised by M. G. Scroggie, B.Sc., A.M.I.E.E.	6/-	6/4
"RADIO LABORATORY HANDBOOK," by M. G. Scroggie, B.Sc., A.M.I.E.E. Second Edition Revised and Enlarged	12/6	12/11
"WIRELESS SERVICING MANUAL," by W. T. Cocking, A.M.I.E.E. Sixth Edition Revised and Enlarged	7/6	7/10
"HANDBOOK OF TECHNICAL INSTRUCTION FOR WIRELESS TELEGRAPHISTS," by H. M. Dowsett, M.I.E.E., F.Inst.P., M.Inst.R.E., and L. E. Q. Walker, A.R.C.S. Seventh Edition	27/6	28/3
"WIRELESS DIRECTION FINDING," by R. Keen, B.Eng. Hons. Sheffield, A.M.I.E.E. Third Edition	27/6	28/3
"RADIO DATA CHARTS," by R. T. Beatty, M.A., B.E., D.Sc. Second Edition Revised	6/-	6/3
"TELEVISION RECEIVING EQUIPMENT," by W. T. Cocking, A.M.I.E.E.	8/6	9/-
"RADIO INTERFERENCE SUPPRESSION," by Gordon W. Ingram, B.Sc.	5/-	5/4
"LEARNING MORSE." Tenth Edition. 285th thousand	6d.	7½d.
"INTRODUCTION TO VALVES," by F. E. Henderson, A.M.I.E.E.	4/6	4/9

Obtainable from Leading Booksellers or by post from

ILIFFE & SONS LTD., Dorset House, Stamford Street, London, S.E.1


RECENT INVENTIONS

A Selection of the More Interesting Radio Developments

LIGHT INTENSIFIER

THE picture to be intensified is first focused upon a photo-electric cathode C, and the resulting stream of electrons is then projected on to a secondary-emission target T at the opposite end of the tube. From here an augmented stream, comprising both primary and secondary electrons is reflected back on to a fluorescent viewing screen S.

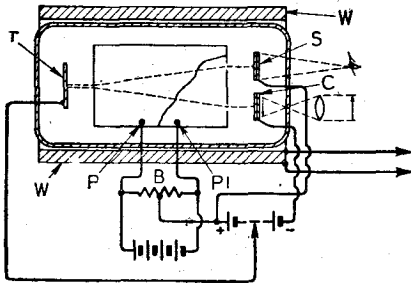
The magnetic field from an external coil W guides the stream in a path which is substantially parallel with the axis of



Light intensification by secondary emission.

the tube at both ends, until the stream passes between two plates P, P₁, which are biased, as shown at B, so as to deflect the stream along the dotted-line path. The deviation from the straight-line path is, of course, reversed by the electrostatic field as the electrons take the return journey towards the viewing screen S. The target carries a fixed biasing potential which is positive with respect to C but negative with respect to S.

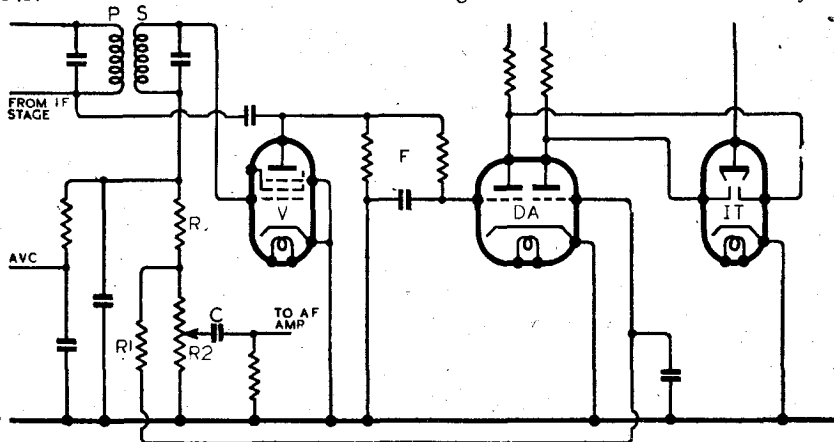Marconi's Wireless Telegraph Co., Ltd. (Assignees of A. Rose). Convention date (U.S.A.) August 31st, 1939. No. 543710.



Detector for frequency and amplitude modulation.

FREQUENCY-RESPONSIVE CIRCUITS

THE phase-relation between the primary and secondary voltages of a coupling transformer is used to operate a visual tuning indicator of the cathode

ray type. As shown in the figure the primary winding P of the transformer is connected to the anode, and the secondary winding to the control grid of a valve V.

The primary produces an output voltage having an amplitude which is determined by the difference between the signal or carrier-frequency and the frequency to which the IF transformer is tuned; this is applied through a filter circuit F to one of the grids of a duplex amplifier DA.


The secondary produces a rectified voltage which is fed through resistances R, R₁ to the other grid of the duplex amplifier DA; this voltage will be of a substantially constant value if the AVC control is flat. By suitably adjusting the resistances, the output from the duplex amplifier can be balanced at the carrier frequency, so as to give a corresponding indication at the visual tuning indicator tube IT. The AC component of the AVC voltage is fed to the AF amplifier through a tapping from the resistance R₂ and a condenser C.

A similar circuit arrangement can also be used to detect frequency modulated signals, or to discriminate selectively be-

tween two amplitude-modulated signals. Marconi's Wireless Telegraph Co., Ltd. Assignees of W. R. Koch. Convention date (U.S.A.) November 30th, 1939. No. 545577.

FLUORESCENT SCREENS

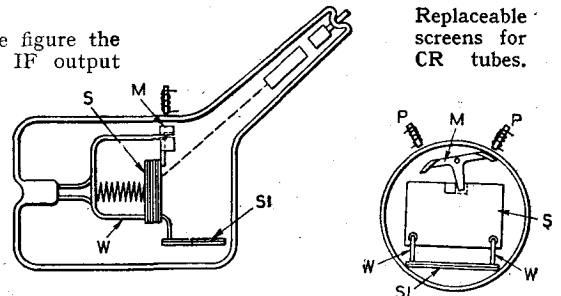A CATHODE-RAY tube is fitted with a number of "spare" fluorescent screens so that when one burns out or deteriorates, it is replaced by another, thus prolonging the life of the tube. As shown, a pack of thin metal sheets S, coated with fluorescent material, is strung through a pair of lower supporting wires W inside the tube, and is pressed forward by a spring against an upper



Replaceable screens for CR tubes.

three-armed support M. The top of each sheet is recessed, the recesses being alternately staggered, so that when the armature M is swung from one side to the other by a pair of external magnets P the old screen is pushed forward into the discarded position S₁ and a fresh one is presented for use.

J. L. Baird. Application date, 7th September, 1940. No. 544,413.

AUTOMATIC CALENDAR FOR SHORT-WAVE RECEPTION

AN adjustable chart for indicating the most favourable conditions for short-wave reception at any given time consists of three circular discs arranged so that they can be relatively rotated about a common centre. One disc is marked with the hours of the day, and also with the names of the principal short-wave transmitters spaced according to their geographical longitude. A second disc is marked with a scale of wavelengths. The third disc is formed with cut-out slots shaped in accordance with the seasonal variations of the ionosphere throughout the year.

The discs are set by hand to a given time in order to show which stations can best be heard; or conversely they can be set to show the best time to hear a selected station. The calibrations are valid for a five-year cycle, corresponding to periods of maximum and minimum "sunspot" activity.

N. A. M. McKie. Application date April 22nd., 1941. No. 544533.

The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.

RANDOM RADIATIONS

By "DIALLIST"

Ducks and D-Xers

THESE notes are being written in Scotland. One thing about life in the Army is that, though you may have long periods in which you may stay put in one place or another, you do, as time marches on, eventually see a good deal of this country of ours. Ever since I arrived at my present northerly station, the rain has pelted down in torrents. That, I fear, appears to be normal for the locality. It is reputed that the village wiseacres say that when you can see the surrounding hills you know it is going to rain, and that when you can't see them you know it is raining! It seems to me to be an ideal place for ducks and medium-wave wireless D-Xers. The heavy, wet soil must make for earth connections of surprising excellence, and the long hours of darkness in autumn and winter should ensure some fine opportunities for long-distance work on the medium waves.

Better Batteries

A DAY or two ago my electric torch glowed only a dimmish red when I switched on, and I realised that it was high time to see about a new battery for it. How long had the old one been in use? I couldn't think for the moment, and then it occurred to me that I'd bought it in Somerset last December. Eleven months' use is pretty good. The cells are of the large type (2½ in. x 1½ in.), but a dozen years or so ago even big cells would have run down in eleven months if they'd stood on the shelf and had no use at all. The advances made in this country in the design and manufacture of dry cells have been striking, as those wireless folk who use battery sets should appreciate. Not so long ago a standard-capacity HTB of 100 volts usually cost a good guinea, and soon threw up the sponge if its load was more than 5 or 6 milliamps. Its shelf life, too, wasn't as a rule much over 3-4 months. Now, even in wartime, batteries cost far less. They stand up to bigger loads, and they can remain on the shelf for long periods without serious deterioration. A good step forward.

But, With a Big B

But may I give one warning about dry batteries of both the flashlamp and HT kinds? You may find some of indifferent make which have either


been too long in the shop that offers them or were not too good to begin with. Only the day before this was written, I went forth to get the 3-volt refill battery that my torch needed. Seeing some of the right type in a shop window, I went in and asked for one. The man behind the counter handed it over, but, before calling it a deal, I asked to see what the voltmeter had to say about it. The voltmeter could say nothing better than about 2.3 volts; and so, although I was assured fervently that this was "normal for wartime batteries," I prefer to try my luck elsewhere. A low reading like this from a presumably unused battery is a sure indication that it won't give much service. A few doors away I found one that read a bit over the 3 volts (as it should), thus giving concrete proof of the inaccuracy of shopkeeper No. 1's statement. The moral is that you should always see the battery's voltage read before parting with your money. Not that a full voltage reading under practically no load is any real indication that a battery is in good condition. It isn't; but a low-voltage reading from a new battery shows definitely that there is something very much amiss with it.

One Man's Meat

Some years ago I made a set for high-quality reproduction of Regional and National programmes from the local station, some fifteen miles away as the wireless wave waggles. It was rather an elaborate affair, containing eight or ten valves, and one of its features was that it had separate AF and output circuits yoked to separate loudspeakers, for the low and the high audio frequencies. Each of the two AF circuits had its own volume control. I got the idea from a big American set, and it worked very well indeed. You didn't get more bass by cutting the "top"; you turned up the VC responsible for the lower audio frequencies. The other VC made speech and music more or less brilliant at will. By working the two controls together you could produce what appealed to your ear as the ideal balance. Each VC was given a graduated dial, and I asked every musical friend who came to visit me to adjust the pair until he considered reproduction to be as nearly perfect as possible. I kept a record of the dial readings, and it is interesting to

New!!

VORTEXION 50 WATT AMPLIFIER CHASSIS

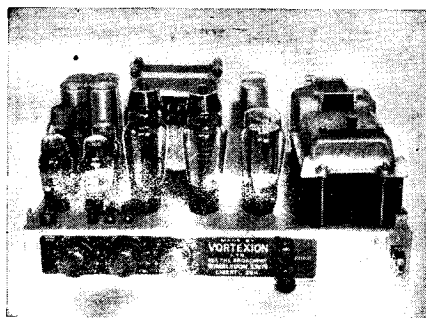

The new Vortexion 50 watt amplifier is the result of over seven years' development with valves of the 6L6 type. Every part of the circuit has been carefully developed, with the result that 50 watts is obtained after the output transformer at approximately 4% total distortion. Some idea of the efficiency of the output valves can be obtained from the fact that they draw only 60 ma. per pair no load, and 160 ma. full load anode current. Separate rectifiers are employed for anode and screen and a Westinghouse for bias.

The response curve is straight from 200 to 15,000 cycles. In the standard model the low frequency response has been purposely reduced to save damage to the speakers with which it may be used, due to excessive movement of the speech coil. Non-standard models should not be obtained unless used with special speakers loaded to three or four watts each.

A tone control is fitted, and the large eight-section output transformer is available in three types: 2-8-15-30 ohms; 4-15-30-60 ohms or 15-60-125-250 ohms. These output lines can be matched using all sections of windings and will deliver the full response to the loud speakers with extremely low overall harmonic distortion.

PRICE (with 807 etc. type valves) £18.10.0

Plus 25% War Increase

MANY HUNDREDS ALREADY IN USE

Supplied only against Government Contracts

VORTEXION LTD.

257, The Broadway, Wimbledon, S.W.19

Phone: Liberty 2814

Random Radiations—

note that no two people agreed exactly in their settings. From this one deduces that it would be impossible to make a high-fidelity receiver that would satisfy the requirements of every musical ear: some kind of tone control, which is, I suppose, really a distortion-producing device, must be provided in order that each listener or group of listeners may be able to arrive at the most pleasing balance of upper and lower audio frequencies. It's a queer business altogether, this matter of the individual human ear.

Preventing Breakdowns

APPARATUS of all kinds in the Services must, of course, always be kept right up to the knocker, so that the possibility of a breakdown is brought to the irreducible minimum. There is a complete system of examination and tests of every accessible part, and this thorough vetting is done at definite intervals of time. I wonder whether, when peace returns, wireless fans who have had a training in almost any branch of the Services won't work out something on

the same lines for their own broadcast, short-wave or communication receivers. It would save a vast deal of trouble-hunting if we took methodical steps to prevent breakdowns by drawing up tables of tests to be made, say, once a week. It would help, too, if we kept records of the service life, current readings and so on of all the valves in our sets, taking the latter, perhaps, once a week. Thus any valve that was on the downgrade would plainly be shown up, and we wouldn't have far to look when it finally threw up the sponge.

Wireless World Brains Trust**G.P.O. Control ◊ Is S-W Radiation Harmful?**

Question No. 6.—In this country the control of all wireless matters is vested in the Post Office. Would it not be better for this function to be in the hands of an independent body, like the Federal Communications Commission in U.S.A.?

RONALD W. HAMILTON.

P. P. ECKERSLEY, M.I.E.E., formerly Chief Engineer of the B.B.C., replies:—

THE distinction between the Post Office in this country and the Federal Communications Commission in America is, so far as I know, that the Post Office is executive while the Federal Communications Commission is advisory. Both bodies have, of course, the responsibility of taking a detached view of radio problems and giving advice or taking actions which are in the public interest.

There are two ways of examining the relative merits of different public bodies; one by looking into their constitutions, the other by examining the results of their activities. Frequently the constitution of a body is not so rigid as to compel the people who run it to act in the way intended by that constitution.

The constitution of the Post Office would allow it to take a detached view of its problems if it were not for the fact that its policy is to make no mistakes and lots of money. Some people say that the Post Office should be constituted as a "business concern." The chief faults it commits, however, are brought about by its sound business outlook.

I am at the disadvantage of not knowing the exact legal constitution of the Federal Communications Commission. I know enough of it to say that it is constituted to advise legislators as to what actions should or should not be taken concerning public communications, and that it exists to take

the detached point of view, regarding the public interest as paramount. I have heard interested American business men become almost lyrical in their condemnation of its activities. Thus, clearly, it has not taken the point of view of the big vested interests. Fairly detached critics, however, have said that while the commission is conscientious, it is timid, and while wholly trustworthy, it can be trusted to be both inexperienced and conservative.

It is fairly clear that the modern world demands public control of public services, such as communication, but that the difficulty, because of the legacy of the past, is to constitute such bodies so that they can, in fact, be independent of any interest save that which they serve, and can yet be expert and enthusiastic. The difficulty with the Post Office is that it is answerable in too large a measure to Parliament on questions of financial profit, and that Parliament acts like a majority shareholder with no knowledge of the business. The conditions of service are not such as to attract people who think that informed enthusiasm deserves bigger rewards than are paid to civil servants. All honour, then, to those brilliant people in the Post Office who accept the conditions; there could be more of such people if the pay were more attractive.

One might summarise the answer to the question by saying that it is not only the form of organisation of public bodies which is important; it is more important to know how public bodies interpret or are allowed to interpret their duties. One might get an ideal organisation and staff it with numskulls, or a bad constitution served by a brilliant personnel. It is doubtful which would be worse. Then again, one must look deeper into the political structure of the country which asks the public bodies to serve them.

Are the bodies asked to serve the public, or only a section of the public?

Thus the question is obliquely answered, in the best Brains Trust manner, by saying that there seems no good reason for substituting the Post Office by something more American, but that there might be some advantage in freeing the Post Office from a profit-making control and yet making its conditions of service more attractive.

[Other subsidiary issues arise. Should the P.M.G. be ultimately responsible (in normal times) for the B.B.C.'s artistic and cultural activities? Is it right that the G.P.O. should control those with whom it might be more or less in commercial competition? Question No. 6 is still open for discussion.—ED.]

Question No. 7.—It has been observed that the incidence of headaches and tiredness among the technical staff at a certain high-power short-wave station is much above normal.

Is there any foundation for the belief that this is due to the high field-strength in the proximity of the transmitter? And have any other physiological effects due to high-intensity RF radiations been observed?

G. W. SMILES.

This question has been passed to Dr. P. P. DALTON, M.R.C.S., L.R.C.P., who, in addition to being qualified to answer it from the medical point of view, has also studied radio technique in its applications to medicine, and is a Fellow of the Brit. I.R.E. Dr. Dalton writes:—

IT has long been known to medical experts in high-frequency therapy that many susceptible individuals suffer unduly from electro-magnetic radiation. Given a certain minimal exciting power these effects appear to be related more to the frequency than

to the power of the transmitter. Exposure to wavelengths of less than about 15 metres produces undesirable effects.

Schliephake, of Jena, states that in working a 400-watt transmitter at a wavelength of 3 m. marked sensations occurred at once, whilst with a 1,500-watt transmitter working close at hand on a 15 m. wavelength no trouble occurred until some hours had passed.



The most marked symptoms noted have been undue fatigue and headaches, irritability and depression extending outside the working day, insomnia and nightmare, lack of confidence in fellow workers, and a "drawing" sensation in the forehead and scalp. It would appear desirable that such ultra-high-frequency transmitters should be screened with an earthed cage of metal. The expense might soon be covered by the increase in the quality of the work done by the station staff.

Medical research, which has led to the development of the modern short-wave radiotherapy, was first initiated when it was noted that workers in the neighbourhood of HF transmitters, who had in the past suffered from neuritic pains such as sciatica, felt a recurrence of these pains when exposed to the HF field.

These facts are all, of course, confirmatory of the existence of a *specific effect* of short-waves—which is strenuously denied by most medical research workers in this country but accepted by those on the Continent and in America. Such specific effects were demonstrated by the writer on frog nerve-muscle preparations in papers read at the first International Congress of Short Waves in Physics, Biology and Medicine held in Vienna in 1937 and are used in medicine by treatment with low-intensity short-wave apparatus.

Other physiological effects which are known to occur through the use of short waves of high or low intensities are markedly a sedative effect on the nerve endings, leading to relief of pain, great increase in the circulation of the blood caused partly by heat and partly by a dilatation of the capillaries, selective killing of bacteria by means of exposure to varying wavelengths, increase in the rate of bloodclotting, local increases in the number of white blood cells and various changes in the blood chemistry. There are definite effects on the vegetative nervous system and the internally secreting glands of the body. The writer has observed, but not yet published, remarkable improvement in diabetes following extremely low-intensity irradiation of the pituitary region.

COMMUNICATIONS DEPEND...

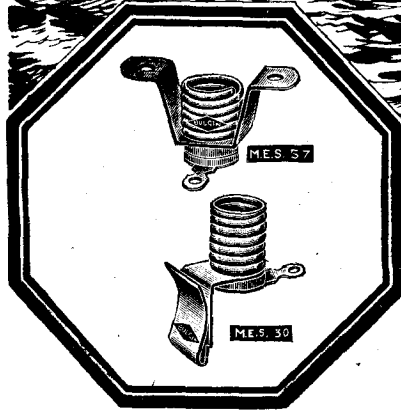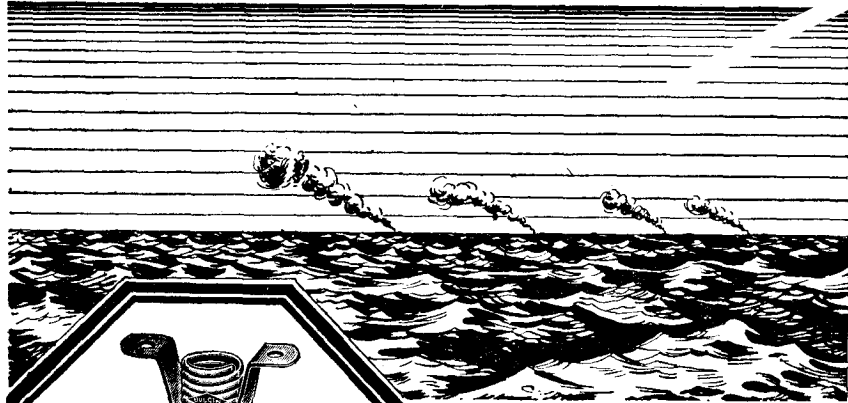

ON SMALL PARTS....

IN countless instances quite intricate pieces of apparatus are wholly dependent on the proved reputation and reliability of their component parts.

All products from the House of Bulgin are pre-eminent for superior design and workmanship and every article bearing our Trade Mark has to pass exacting and exhaustive tests during the course of its production.

We ask the kind indulgence of the Trade on delivery until peaceful conditions return.

The Choice of Critics

BULGIN FOR LAMP HOLDERS

The largest and most extensive range in the World. All kinds of lamp-caps are accommodated, including M.E.S. and E.S., to B.S.S.98, and M.B.C. (the new miniature bayonet cap, single-contact). In the large range there is a full choice of fixing-brackets, -strips, and -clips both 'live' and 'dead.' The screw types are made in rolled, drawn-and-embossed, spring-grip, etc. A lampholder for every use.

"The Choice of Critics"

BULGIN

REGISTERED • TRADE • MARK

A. F. BULGIN & CO. LTD., BY-PASS RD., BARKING, ESSEX.
TEL.: RIPPLEWAY 3474 (4 lines).

THE WORLD OF WIRELESS

U.S. INTERNATIONAL STATIONS

FOR some months the policy of operating United States international short-wave stations in wartime has been under consideration. It was at first proposed that the Government should take over the operation of the existing stations but this plan has given place to one of Government "partnership" with existing operating companies.

The proposed scheme provides for the erection of twenty-two new short-wave stations, the power of which will vary from 50 to 100 kW. It is also proposed that the frequencies required for the new stations should be taken from those allocated to other than international broadcasting services.

The Government, through the Board of War Communications, will pay for the erection and operation of the new stations which will be licensed to existing or new operators. It is proposed to offer the transmitters for sale after the war to the companies operating them. Programmes of all short-wave transmitters will continue to be controlled by private operators but with the Government holding a "watching brief."


Commenting on the plan, our American contemporary *Broadcasting* writes: "It seems a pity that so simple a plan should have taken so long to evolve. It will probably take at least six months to get the projected 22 new short-wave transmitters on the air. Meanwhile, the Axis powers, with their own and their seized stations, numbering at least 100, are scattering their propaganda far and wide to the corners of the earth."

R.A.F. WIRELESS MAINTENANCE

TO facilitate the maintenance of the wireless equipment of bomber aircraft at the numerous airfields, mobile wireless testing vans are now being used by R.A.F. Bomber Command. In addition to being used for general maintenance of W/T and R/T airborne equipment, they are also employed for frequency checking of aircraft apparatus.

The van illustrated is equipped with an aircraft-type W/T and R/T transmitting and receiving set to permit of two-way working with aircraft on the ground. A petrol engine generator is included in the equip-

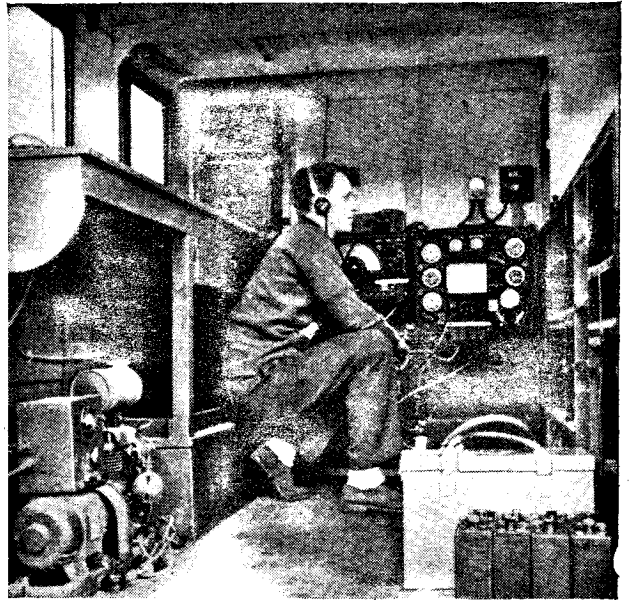Mobile wireless maintenance van used by R.A.F. Bomber Command. The spaces on the right are for housing test gear and spares.



ment so that accumulator charging and servicing can be undertaken when other facilities are not available. To enable the wireless mechanic to reach inaccessible parts of an aircraft, a catwalk is provided on the roof of the vehicle.

EMPIRE COMMUNICATIONS

TO deal with the many Empire communication problems arising out of the war a Commonwealth Telegraph Conference is shortly to be held in Australia. Government representatives from Canada, New Zealand, the Union of South Africa, India, Southern Rhodesia, Australia and the United Kingdom will be taking part. The United Kingdom representative will be Sir Campbell Stuart, chairman of the Imperial Communications Advisory Committee in London, who will also be chairman of the conference. He has left for Canberra accompanied by Colonel Zambra, who is secretary to the Imperial Communications Advisory Committee.

It is understood that, as the conference is being called for Government representation only, Cable and Wireless has not been invited to take a seat at the conference table.

It is also learned on enquiry that the General Post Office will not be represented.

AMERICAN VALVES

AT the time of writing the promised release of the American Lease-Lend valves for replacements in "silent" sets announced last month has not materialised.

It is understood that some difficulty is being experienced in formulating a scheme of distribution to ensure that the valves supplied are for replacements in domestic receivers at present out of commission.

WEATHER AND U-S-W

SOME interesting facts regarding the influence of weather on the propagation of ultra-short waves emerge from a study of the records of signal strength variations in the Post Office radio telephone link between Guernsey and England from 1937 to 1939.

The path between stations was about 85 miles in length over sea, of which 36 miles was outside the optical range; the wavelengths employed were 5 and 8 metres. Continuous records taken by the Post Office were analysed by Dr. R. L. Smith Rose and Miss A. C. Strickland, M.Sc., to show correlation between signal strength and atmospheric conditions. The results are given in a paper recently read before the I.E.E.

It is clearly established that weather has an influence on the variations signal intensity. During periods high barometric pressure, often accompanied by temperature inversions, signal strength was at a maximum, but there was much fading of the slow type. Low-pressure conditions with very little temperature inversion gave the steadiest signals though of rather low level. Snowy and foggy weather also gave a steady signal even when the atmospheric pressure was high.

The authors conclude: "It seems clear that the main agencies causing variations in signal intensities on these wavelengths are the variations in refractive index of the air in the lower atmosphere, due notably to changes in moisture content, and in addition the presence or absence of temperature inversion layers from which the waves can be reflected at heights of from a few hundred to a few thousand feet."

The World of Wireless—

of the programmes for India's many rural listeners, "whose work and habits are ruled more by the movements of the sun than by the hands of the clock."

New Indian Station

WHEN in 1937 the Government of India, at the request of the Government of the North-Western Frontier Province, took over the 0.25-kW broadcasting station erected by Marconi's at Peshawar five years earlier, there were but a few villages equipped with communal receivers. The situation has changed sufficiently to warrant the erection of a new 10-kW transmitter, which is now working on a wavelength of 476.9 metres. The station has a 350ft. mast radiator aerial.

Dr. Leonard Klatzow

WE record with regret the death at the early age of thirty-five of Dr. Leonard Klatzow, who since 1934 had been engaged on research work at Electric and Musical Industries. A native of South Africa, he came to this country as a Rhodes Scholar in 1930 and obtained his Ph.D. degree three years later. His work on the Emitron television camera from the photo-electric angle was largely responsible for the success of the transmissions from the London television station. A colleague wrote in *Nature*: "His work, largely unpublished, did not receive the wide recognition it deserved, but there is no doubt that a career of increasing distinction was opening before him."

GOODS FOR EXPORT

The fact that goods made of raw materials in short supply owing to war conditions are advertised in this journal should not be taken as an indication that they are necessarily available for export

United States High-power Transmitter

It is learned from Washington that the United States Government has purchased a new 500-kW short-wave broadcasting transmitter.

School Broadcasting

A TOTAL of 10,429 schools in England and Wales have registered as listening schools with the Central Council for School Broadcasting. This is the highest number recorded at the beginning of a school year, being 469 more than the number registered at the beginning of the previous year, which was itself over 2,400 higher than the figure for any other year.

"Spoils of War"

MENTION is made in the official story of the conquest of Italian East Africa that signal material captured at Addis Ababa was valued at £250,000. This figure, of course, does not include the wireless station, which had been very little damaged and was rapidly repaired by Royal Signals personnel and put to use for propaganda purposes.

I.E.E. Meetings

A DISCUSSION on "The Electronic Control of Industrial and Power Plants" will be opened by S. G. King at the informal meeting of the Institution of Electrical Engineers arranged for Monday, November 23rd, at 5.30. Dr. G. E. Donovan, M.Sc., B.Ch., M.B., will deliver a paper on "The Electrical Amplifying Stethoscope and Phono-Electro Cardioscope," and give a demonstration of the apparatus at the Wireless Section meeting on Wednesday, December 2nd, at 5.30.

Scottish Radio Club

A CLUB conducted on parallel lines to the Radio Industries Club in London has now been formed in Glasgow. The membership of the new Radio Industries Club of Scotland is drawn from all fields of wireless activity, and is already nearing the hundred mark. A. S. Black, Scottish manager of the G.E.C., is chairman; James Robertson, who played a prominent part in forming the club, is vice-chairman; while the secretary is Elliot Macintosh, Principal of the Wireless College. His address is 3, Park Gardens, Clifton Street, Glasgow.

The Ever-growing Need

PROTECTION against the dangers of electrical short-circuit is one of the advantages claimed for the new petrol containers made of specially treated cardboard. This new application of paper stresses the ever-growing need of economy in its use, and of salvaging every scrap of waste paper.



KURZ-KASCH RADIO KNOBS—DIALS INSTRUMENT KNOBS

Modern plastics are materially helping to bring the war to a successful conclusion, and Kurz-Kasch with its extensive plant and equipment is assisting in that direction.

Apart from those good-looking and well-designed knobs which form equipment of test instruments and receivers, we are moulding other very important items for the combined Services.

Kurz-Kasch Inc. look forward to serving you again as soon as circumstances permit.

Register your name with our Representative now. He will forward you information on our products as soon as they become available.

KURZ-KASCH INC.

Moulders of Plastics,

DAYTON, OHIO, U.S.A.


* * *

Exclusively Represented by

Frank Heaver Ltd. Kingsley Road, Bideford, N. Devon.

CODE COURSES

For Beginners and Operators

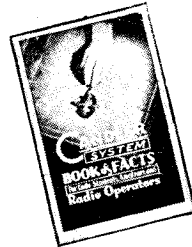

The Candler System of Code training is just what one needs for entering or advancing in Army, Navy, Air Force, Amateur Radio work, or the Commercial side of telegraphy.

JUNIOR AND ADVANCED COURSES

on Cash or Monthly Payment terms.

There's no royal road to learning—but there IS a quick, sure way to genuine CODE skill. Thousands of Candler Trained Operators have proved the value of this truly remarkable system of Morse Code instruction.

J. Clarricoats, Sec., Radio Society of Great Britain—says: "I regard the Candler System as being the most important system of its kind and already large numbers of Members of the Radio Society of Great Britain have intimated to me that they are studying the course of instruction with a view to preparing themselves for service in one branch or another of H.M. Forces."

In the "BOOK OF FACTS," which will be sent FREE on request, you will see that full information is given concerning the subjects covered by Morse Code Courses for beginners and also for operators.

COUPON

Please send me a free Copy of Candler "Book of Facts."

NAME

ADDRESS

Post Coupon in 1d. unsealed envelope to London Manager

CANDLER SYSTEM CO. (Room 55W), 121, Kingsway, London, W.C.2

Candler System Co., Denver, Colorado, U.S.A. 1242

F.W.S.CO.

TRADE MARK
SINCE 1910

I.F. TRANSFORMERS of all types

AERIAL & OSCILLATOR COILS TRIMMER & PADDER CONDENSERS

"SILVERCAP" CONDENSERS COIL FORMS, etc.

Our factory has been expanded considerably, our knowledge is increasing daily and our added experience and facilities will be available for you as soon as conditions permit.

We are making many intricate parts for the U.S. Army, Navy, Air and Signal Corps, and we are happy to assist in the great effort to bring this struggle to a successful conclusion.

Sickles I.F. transformers, coils, trimmers and other radio parts will be ready for you again in due course.

Register your name with our Representative now. He will forward you information on our products as soon as they become available.

THE F. W. SICKLES CO. CHICOPEE, MASS., U.S.A.

Exclusively Represented by


Frank Heaver Ltd. Kingsley Road, Bideford, N. Devon

AUDIO AMPLIFIERS

and SUB-ASSEMBLIES

One of our range of Standard Amplifiers available for work of National Importance

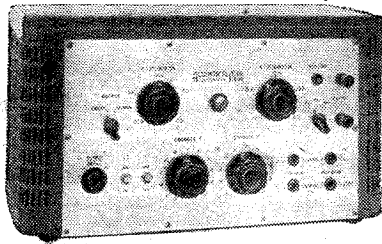Standard Amplifiers • Special Amplifiers for Industrial Applications • Transformers and Coil Winding • Sheet Metal Work and Stampings • Switch Assemblies • Microphones, etc.



ACOUSTICAL
MANUFACTURING COMPANY LTD
HUNTINGDON
TEL: 361

SALFORD METAL RECTIFIERS

FOR ALL RADIO, TELECOMMUNICATION AND POWER PURPOSES

RECTIFIERS BUILT TO INDIVIDUAL REQUIREMENTS

MANY THOUSANDS IN USE

SALFORD ELECTRICAL INSTRUMENTS LTD.,
PEEL WORKS, SILK STREET, SALFORD, 3
Proprietors: The General Electric Co., Ltd., of England.

MELTON METALLURGICAL LABORATORIES LTD

LIQUID SILVER

for metallising CERAMIC, MICA, QUARTZ or GLASS

Low melting-point SOLDER from 70°C. or to specification. Non-corrosive Liquid FLUX for all electrical or Radio purposes.

Pre-War Deliveries. Overseas enquiries invited.

IPSWICH ROAD, TRADING ESTATE, SLOUGH, BUCKS. Phone: Slough 20992

RADIO SERVICE SUPPLIES

MAINS TRANSFORMERS. Chassis Mounting.
Primaries 200/230/250 v.
Type "A." 300-0-300 100 ma. 4 v. 2 amp. 4 v. 5 amp. CT. 22/6
Type "C." 300-0-300 100 ma. 5 v. 2 amp. 6.3 v. 5 amp. CT. 22/6
Type "H." 325-0-325 100 ma. 4 v. 2 amp. 4 v. 5 amp. CT. 23/6
Other types, details on request.
(Postage on 1 transformer, 9d.)

SPEAKER TRANSFORMERS. Standard Multi-ratio (including PP.) 7/-

SPEAKERS. Eight-inch PM Speakers, Rola, Celestion, R. & A., etc., 4-watt types, with pentode transformers 23/6

GONDENSERS. All types stocked, paper and mica. Electrolytics, card case and can types.

VOLUME CONTROLS. TONE CONTROLS. RESISTORS. TAPPED DROPPERS.

WIRE-WOUND RESISTORS, 5-watt, 1/9; 10-watt, 2/3

SUNDRIES. Solder, best resin-cored, half-pounds, 2/-; Insulating Tape, 4 ozs., 9d.; Sleeving, 2/6 dozen yards; Push-Back Wire, 12 yards, 1/6; Valve Holders, Fuses, Pilot Lamps, etc.
Postage extra. Send stamp for full lists.
Orders over £3, carriage paid.

Please mail your orders; no trade counter facilities

RADIO INSTRUMENT SERVICE CO.
116 LITTLEHEATH ROAD, BEXLEYHEATH, KENT

WARD ROTARY CONVERTERS

Petrol Electric Generating Plants, H.T. Generators, D.C. Motors, Frequency Changers, etc., up to 25 K.V.A.

CHAS. F. WARD 37 WHITE POST LANE
Phone: Amherst 1393. HACKNEY WICK, E.9

SAVE TO SPEND Why! not!

SEE OUR POST-WAR DELIVERY SCHEME "W.W." MAY p. 20

The Courts, Silverdale, London, S.E.26.

Phone: SYD. 6666. VOIGT PATENTS LTD

KESSLERS (London) LTD

for TURNING and MACHINING OF PLASTIC MATERIAL SIGNAL LAMP CAPS SWITCH KNOBS AND HANDLES

Albion House, 201-3, Church St., London, N.16
Tel.: Clissold 6247



INVENTORS

The world-wide Simmonds Organisation has established new methods and new products in many industries with great success. Simmonds Development Corporation seeks new ideas and inventions of brilliance and ingenuity to be developed by the technical resources and marketing knowledge of the Simmonds Group.

The SIMMONDS GROUP

LONDON
MELBOURNE
PARIS
NEW YORK
LOS ANGELES

SIMMONDS DEVELOPMENT CORPORATION LTD · BUSH HOUSE · W.C.2

Printed in England for the Publishers, LIFFE AND SONS LTD., Dorset House, Stamford Street, London, S.E.1, by THE CORNWALL PRESS LTD., Paris Garden, Stamford Street, London, S.E.1. "The Wireless World" can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch, Ltd. INDIA: A. H. Wheeler & Co. CANADA: Imperial News Co.; Gordon & Gotch, Ltd. SOUTH AFRICA: Central News Agency, Ltd.; Wm. Dawson & Sons (S.A.), Ltd. UNITED STATES: The International News Co.



Sorry U.S.A.—
after Victory we'll be with you

It sounds like "coals to Newcastle"—but U.S.A., the home of cored solder, found it worth while to import British made Ersin Multicore—the A.I.D. approved solder wire with three cores of non-corrosive Ersin flux, although Ersin Multicore, after paying freight and duty, cost American manufacturers fifty per cent. more than American made solders.

Why? With the correct, rapid soldering technique, H.R. or "dry" joints are impossible with Ersin Multicore, and production is speeded up.

Present conditions do not permit the export of Multicore to U.S.A., but after Victory, U.S.A. manufacturers will once again be able to use "the finest cored solder in the world."



ERSIN

MULTICORE

THE SOLDER WIRE WITH 3 CORES OF NON-CORROSIVE ERSIN FLUX

MULTICORE SOLDERS LIMITED, BUSH HOUSE, W.C.2. Phone Temp. Bar 5583/4

★ PRE-EMINENT IN PEACE



★ INDISPENSABLE IN WAR

ADVERTISEMENT OF THE TELEGRAPH CONDENSER CO., LTD.

G.P.5261