

# Wireless World

RADIO AND ELECTRONICS



SEPT. 1946

1/6

Vol. LII, No. 9

IN THIS  
ISSUE:

V.H.F. COMMUNICATION SYSTEM




# RUBBER-TO-METAL BONDING

The Problem of Insulating delicate instrument panels from vibration and shock by means of Flexilant Mountings
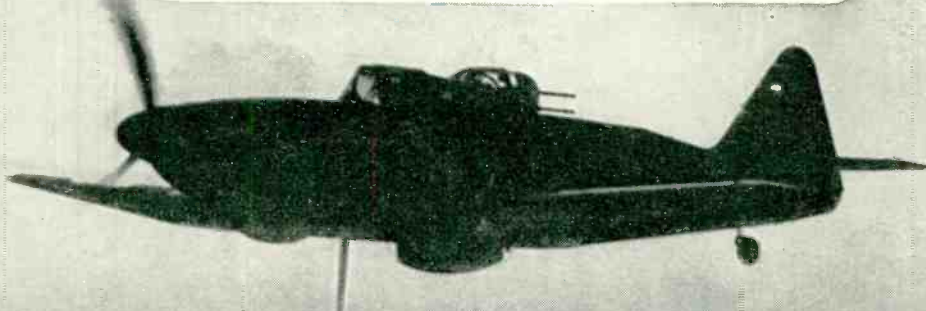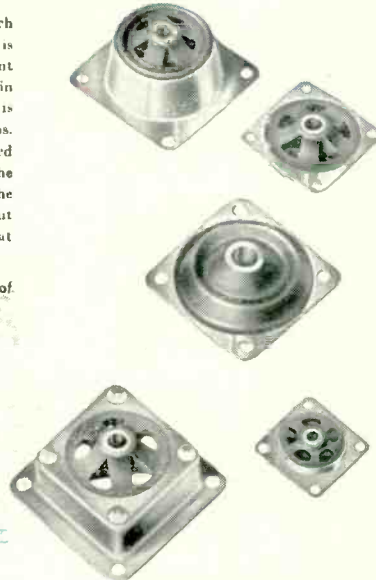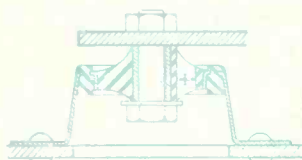
## "FLEXILANT" Mountings: Examples from the SERIES.

The "Flexilant" Mounting of which several varieties are illustrated here is so accurately made that its displacement under load can be calculated to within .010" of requirements. The series is designed to carry loads of from 1 to 45 lbs. per mounting and these may be arranged with bolt axis at 90° to position, or the complete mounting may be inverted. The mountings can be supplied with or without holder and they can be arranged so that two utilize the same bolt.

We should appreciate the opportunity of helping with your vibration problems.



**RUBBER BONDERS Ltd.**  
*Engineers in Rubber bonded to metal*

**FLEXILANT WORKS · WATLING STREET · DUNSTABLE, BEDS.**  
TELEPHONE: DUNSTABLE 803

TELEGRAMS: FLEXILANT, DUNSTABLE

A Short Review of FLEXILANT Products is available on enquiry . . .



R.B.12




Regd. Trade Mark

PRECISION

TESTING INSTRUMENTS

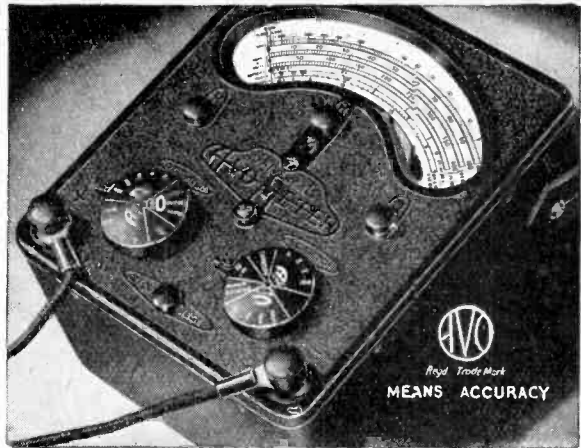**H**IGH accuracy, simplicity, exceptional versatility and proven reliability have won for "AVO" Instruments a world-wide reputation for supremacy wherever rapid precision test work is demanded. There is an "AVO" Instrument for every essential electrical test.



The MODEL 7 50-Range Universal

**AVOMETER**

Electrical Measuring Instrument

A self-contained, precision moving-coil instrument, conforming to B.S. 1st Grade accuracy requirements. Has 50 ranges, providing for measuring A.C. & D.C. volts, A.C. & D.C. amperes, resistance, capacity, audio-frequency power output and decibels. Direct readings. No external shunts or series resistances. Provided with automatic compensation for errors arising from variations in temperature, and is protected by an automatic cut-out against damage through overload.

Sole Proprietors and Manufacturers

**THE AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO. LTD.**, Winder House Douglas Street, London, S.W.1. 'Phone: VICToria 3404/8



*34 different*

**"SOMERFORD"  
POWER TRANSFORMERS**

Now in full peace-time production, Gardners are still combining the skill of their engineers and operatives with the best of materials to give the Radio and Electronic Industry the finest range of Power Transformers. Now numbering 34, they are all different as regards their secondary outputs and tappings. No difference though in their fine Quality, Dependability, and first-class Workmanship—these remain, as always, their constant factors. There is a Gardners Power Transformer to suit the job you have in hand or the one you are planning.

Write to-day for full data and specifications. If you have a problem regarding Transformers, please consult us—our experience, developed over many years, is at your disposal.


Gardners "SOMERFORD" Power Transformers are available also through our accredited Stockist Wholesalers, a list of whom will gladly be sent on request.

**GARDNERS  
TRANSFORMERS & CHOKES**

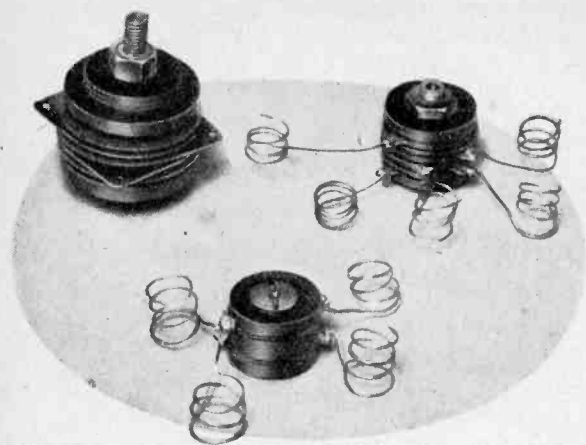Gardners Radio Ltd., Somerford, Christchurch, Hants. Tel.: Christchurch 1025







## METAL RECTIFIERS for electrical measuring instruments

The addition of a Westinghouse Metal Rectifier enables a D.C. instrument to be adapted to read alternating current quantities and, at the same time, retain all the advantages of the D.C. moving-coil movement.


Rectifiers are available for instruments requiring an input of up to 500 millivolts at currents of from 100 microamperes up to 500 milliamperes and full details are given in descriptive pamphlet No. M.R.3, a copy of which may be obtained from Dept. W.W.

Made in England by



**BRAKE & SIGNAL CO. LTD.,**  
82, YORK WAY, KING'S CROSS, LONDON, N.1.

# PERTRIX REDRESSED FOR PEACE

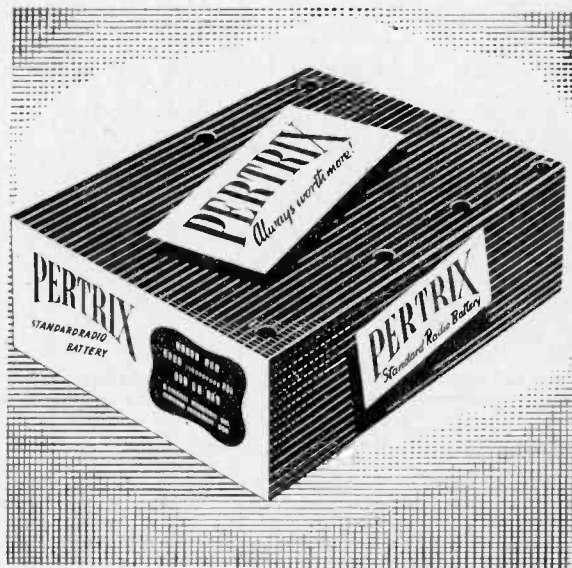

**P**ERTRIX BATTERIES have emerged from the testing ground of war as more reliable, more efficient than ever before. You will soon see them in the smart new post-war pack shown above. It denotes the finest battery for radio use yet made.



**HOLSUN BATTERIES LIMITED**

137 Victoria Street, London, S.W.1.

P.I.A.

## MICA *Capacitors*

**THE STANDARD OF TECHNICAL EXCELLENCE,  
QUALITY AND RELIABILITY**

Dubilier Capacitors fully justify the confidence placed in them by leading designers and production engineers.

The Moulded Mica and Metallised Mica Capacitors are small, light and dependable in arduous service and they have excellent electrical characteristics.

The 635 is the smallest Moulded Mica Capacitor manufactured, and the 680 is particularly suitable for Television or other apparatus where higher voltages pertain.

The Protected Metallised Mica Capacitors are manufactured by a specially developed process and they provide inexpensively a high degree of stability.

**MAKERS OF THE WORLD'S FINEST CAPACITORS**

D.5

# DUBILIER

CONDENSER CO. (1925) LTD.

DUBILIER CONDENSER CO. (1925) LTD., DUCON WORKS, VICTORIA ROAD, NORTH ACTON, W.3


Phone: ACOB 2241.

Grams: Hivoltcon, Phone, London.

Cables: Hivoltcon, London.

Marconi International Code.

# NTR CATE PARTS

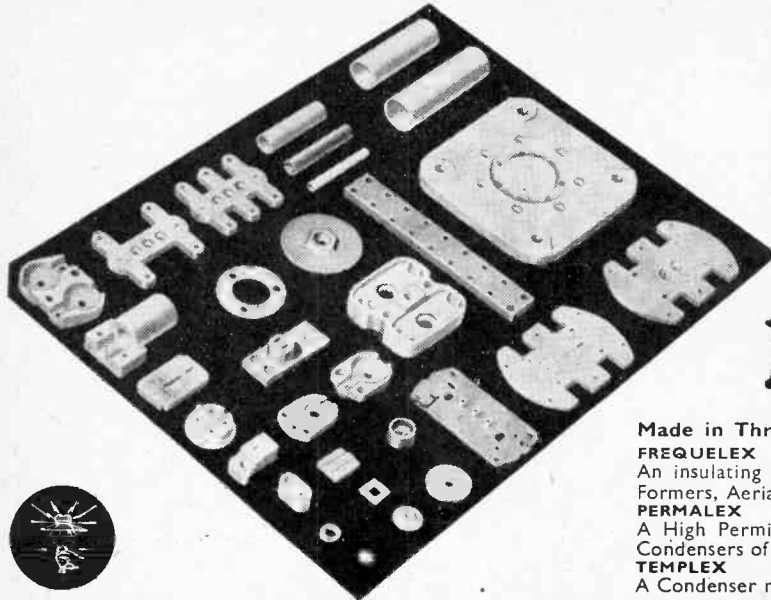

but not too  
intricate  
for

## Bullers

Made in Three Principal Materials

**FREQUELEX**

An insulating material of Low Di-electric Loss, for Coil Formers, Aerial Insulators, Valve Holders, etc.

**PERMALEX**

A High Permittivity Material. For the construction of Condensers of the smallest possible dimensions.

**TEMPLEX**

A Condenser material of medium permittivity. For the construction of Condensers having a constant capacity at all temperatures.




**BULLERS LOW LOSS CERAMICS**

**BULLERS LTD.**, 6, Laurence Pountney Hill, London, E.C.4  
Telegrams: "Bullers, Cannon, London"

Phone: Mansion House 9971 (3 lines)

RT. 10.

*No Hint  
of Doubt*

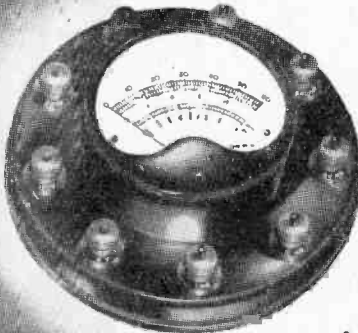

...with Sifam precision—  
The ideal D.C. Radio Service Tester. Long scale 3 3/4" Moving coil instrument mounted on a black bakelite base. The circular design allows terminals to be well spaced, positive contact being obtained without switching. Ten ranges and a resistance scale as follows:—  
100 mV, 2, 6, 120, 300 Volts, D.C. 1, 6, 600 mA, 6 Amperes D.C. 50,000 Ohms, 2,000 Ohms at mid scale reading.


PRICE :  
£6. 0. 0 TYPE RT. 10.

with  
**SIFAM**

21  
YEARS  
SPECIALISED  
EXPERIENCE

ELECTRICAL  
INSTRUMENT  
CO., LTD.,  
TORQUAY

## THE P.A.10 PORTABLE AMPLIFIER

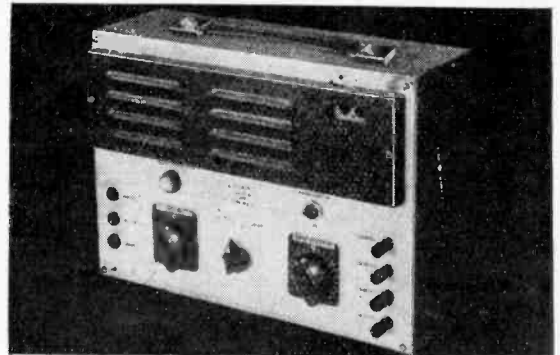

**BSR**

A portable 10 watts A.C. operated Amplifier, with inputs for one crystal or moving coil microphone and one pickup. Output impedance 2.5, 7.5 and 15 ohms. Ideal for Hotel paging systems, Dance Bands, etc.

All B.S.R. Amplifiers are built to a scientific standard, by pioneers in the art of Sound Reproduction.

**BIRMINGHAM SOUND REPRODUCERS LTD.**  
CLAREMONT WORKS, OLD HILL, STAFFS. TEL: CRADLEY HEATH 6212-3  
LONDON OFFICE: 115 GOWER STREET, W.C.1 TEL EUSTON 7515  
M-W.67


# TCC

# CAPACITORS

PAPER  
ELECTROLYTIC  
MICA

SILVERED MICA  
CERAMIC

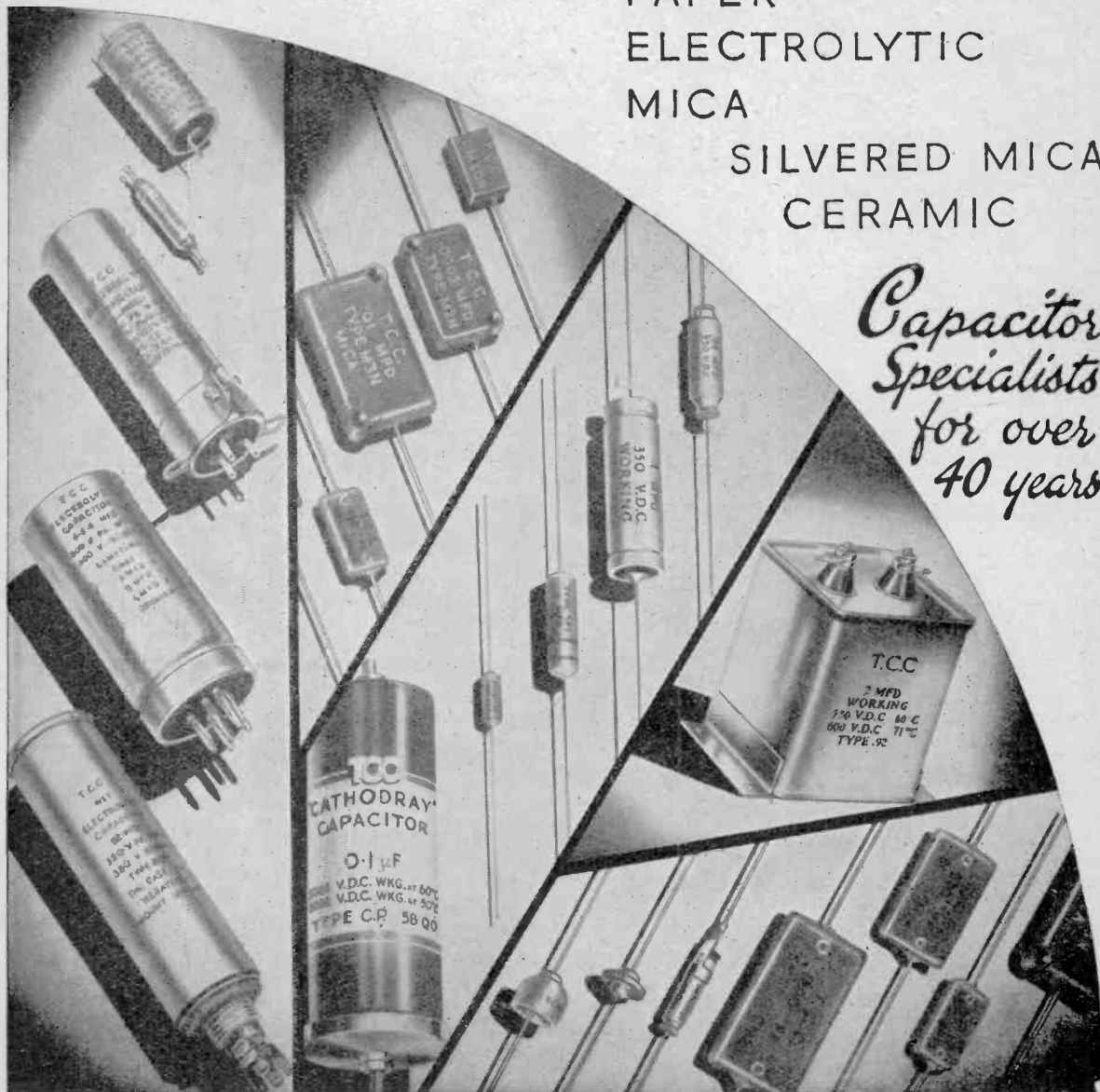*Capacitor  
Specialists  
for over  
40 years*



**THE TELEGRAPH CONDENSER CO., LTD.**

**RADIO DIVISION**

**NORTH ACTON · LONDON · W.3**


**Telephone. ACORN 0061**

# HY-MEG

*for modern impregnation*

**GIVES STABILITY  
IN INSULATION**

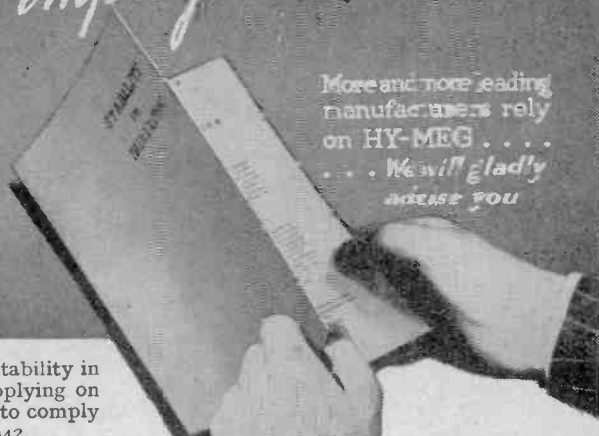More and more leading  
Manufacturers rely  
on HY-MEG . . . .  
We will gladly  
advise you



★ A copy of the recently printed Brochure "Stability in Insulation" will gladly be sent to those applying on Business Heading or Card and enclosing 2d. to comply with the Control of Paper (No. 48) Order, 1942.

**LEWIS BERGER & SONS LTD. (Established 1760) 35 BERKELEY SQUARE, LONDON, W.1**  
Telephone: MAYfair 9171

MANUFACTURERS OF INSULATING VARNISHES AND ENAMELS

# CELESTION


## LOUDSPEAKERS

Chassis Diameters range from  
2½" to 18"

Power Handling Capacities range from  
25 Watt to 40 Watt.

Celestion Limited  
Kingston-upon-Thames  
Telephone: KINgston 5656-7-8

**EARTH FREE**  
*& Silent as the Stars*

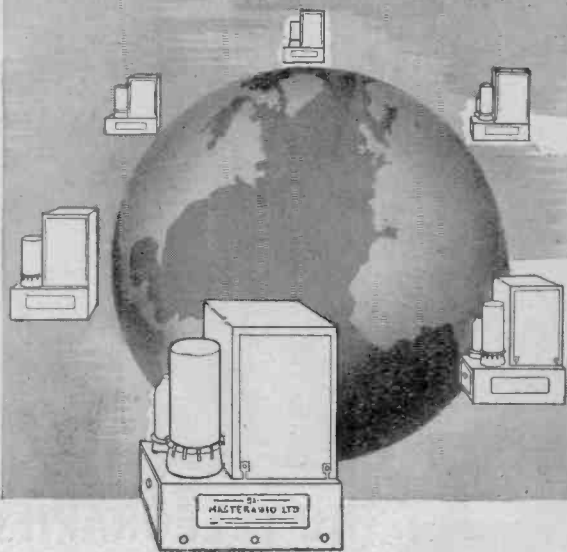

**Masteradio**  
VIBRATORPACKS

PROMPT DELIVERY NOW ASSURED

MASTERADIO LTD. VIBRANT WORKS. WATFORD. HERTS




# METALLISED CERAMICS





for

## Hermetic Seals and Soldered Assemblies

### FREQUENTITE BUSHES


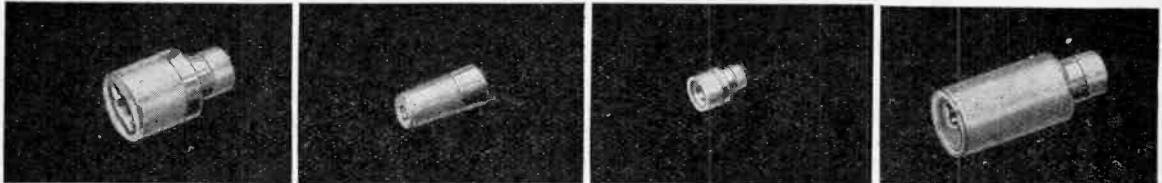


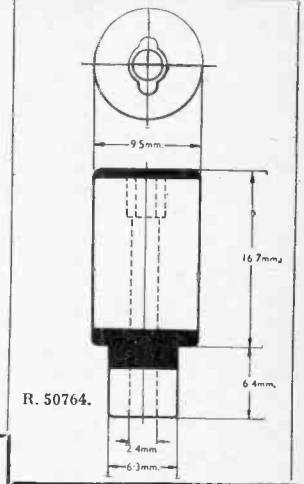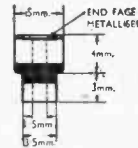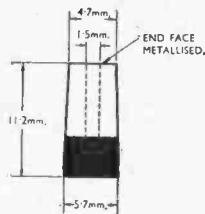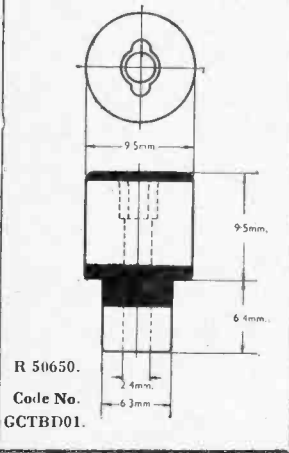Photographs (above) actual size.  
Drawings not to scale.



Code nos. are those used in I.S.C.Tech.C.  
Specification No. R.C.L./330.11.

### PORCELAIN BUSHES

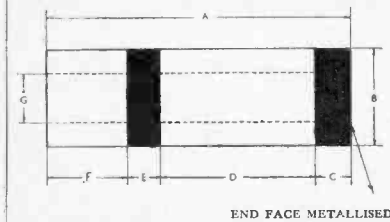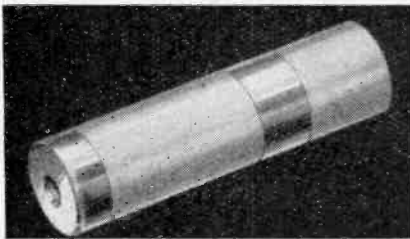

TYPE	CODE	A mms.	B mms.	C mms.	D mms.	E mms.	F mms.	G mms.
R. 50734	GCTBC01	20.3	7.6	3.8	6.4	4.6	5.5	3.0
R. 50768	GCTBC02	20.3	12.7	3.8	6.4	4.6	5.5	5.1
R. 50769	GCTBC03	20.3	15.2	3.8	6.4	4.6	5.5	6.4
R. 50770	GCTBC04	38.1	10.2	5.1	15.7	6.4	10.9	4.1
Q. 2092	GCTBC05	55.9	12.7	6.4	25.4	8.9	15.2	5.1
Q. 1982	GCTBC06	78.7	15.2	6.4	38.1	8.9	25.3	5.1

For full information and prices please write to:

# STEATITE & PORCELAIN PRODUCTS LTD.

STOURPORT-ON-SEVERN, WORCS. T'phone: Stourport III. T'grams: Steatain, Stourport.



ARE YOU USING THE  
SLEEVING BEST SUITED  
TO THE JOB



"Best suited" means an insulating sleeving that meets every Service or general requirement. The DELAFLEX range includes non-fraying Woven Fibre Glass and Tropical Grade ROLLED SILK in a complete range of colours and in sizes from 0.5 mm. to 35 mm. Thus, a recommendation from De La Rue Insulation Limited is unbiassed . . . you get the sleeving best suited to your needs, not only from the standpoint of efficiency, but of economy as well. Fullest details, samples and prices gladly sent on request.


# Delaflex

*Insulating Sleeving*

DE LA RUE INSULATION LTD  
84 REGENT STREET • LONDON • W.1  
TELEPHONE : REGENT 2901



FROM AUG. 1  
OUR LONDON  
ADDRESS IS

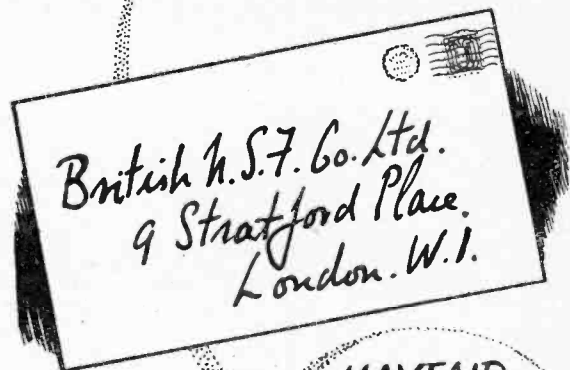

MAYFAIR  
4234


### N.S.F.—OAK SWITCHES

N.S.F. Paper Capacitors, Silvered Mica Capacitors,  
Wire-wound Resistors and Volume Controls.  
Details on request. GA



Manufacturers  
of  
LOUDSPEAKERS  
•  
LAMINATIONS  
•  
SCREENS  
in  
RADIOMETAL  
•  
PERMALLOY  
•  
SILICONALLOYS

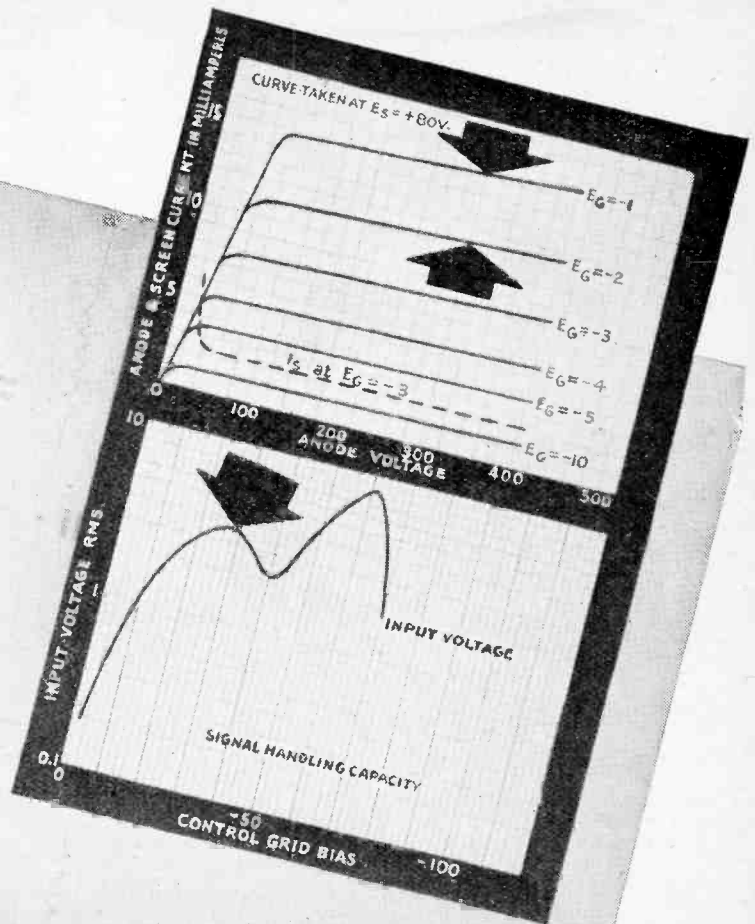ELECTRICAL SOUND & TELEVISION PATENTS LTD.  
12, Pembroke Street, London, N.1. Terminus 4355  
2/4, Manor Way, Boreham Wood, Herts. Elstree 2133



## POINTERS FOR DESIGNERS

### THE KTW61

A screened tetrode with suppressor plates and with variable-mu characteristics, the OSRAM KTW61 is specially suitable for use as an R.F. or I.F. amplifier in superhet receivers. Its outstanding features include:—

- High order of mutual conductance (2.9 mA/Volt) combined with low leakage capacitance (0.0025  $\mu\mu F$ ), which facilitates high stage gain.
- Negligible distortion with the maximum signal likely to be encountered in practice. Conditions of use — as an I.F. amplifier with screen dropping resistance, and in conjunction with OSRAM frequency changer X61M.
- Marked improvement in signal to noise ratio, particularly on the short waves, when used as an R.F. amplifier with fixed screen voltage.

A detailed technical data sheet is available on request.

**Osram**  
PHOTO CELLS

**G.E.C.**  
CATHODE RAY TUBES

**Osram**  
VALVES



Over prickly pear  
or paddy field or  
pasture-across all the  
trackless wastes of  
the world, you know  
where you are with

# MARCONI

MARCONI'S WIRELESS TELEGRAPH CO. LTD.  
THE MARCONI INTERNATIONAL MARINE  
COMMUNICATION CO. LTD. MARCONI HOUSE,  
CHELMSFORD, ESSEX.



## Here are a few Specialities

- MINIATURE WIRE WOUND RESISTORS
- INSTRUMENT STUD SWITCHES
- VARIABLE ATTENUATORS

From  
the House



PAINTON & COMPANY LTD • KINGSTHORPE • NORTHAMPTON

### M.R. SUPPLIES Ltd.

offer the following brand new and reliable Radio and Electrical Material. Prompt despatch. All prices net.

**SIGNAL GENERATORS.** We confidently recommend the new BPL Instrument and have already supplied many of the large firms' laboratories. Operation 200/250 v. A.C. Frequencies:—100/250, 250/500, 500/1,000 Kc/s. 1.6/4.5, 4.5/12, 12/30 Mc/s. Accuracy 1 per cent. 1 volt in 10 ohms. All ranges modulated to depth of 30 per cent. by internal 400 c. oscillator (off switch provided). 6in. illuminated scale. 400 c. brought out separately. Double screening, £21 nett (desp. 2/6). Ex stock.

**MEGGERs.** The "Wee-Megger" by Evershed again in stock. Pressure 500 volts. Range 0/20 megohms and inf. Supplied with pocket and log books, £9 10s.

**ROTHERMEL PIEZO-CRYSTAL PICK-UPS,** new low prices:—Senior, in black bakelite, 5/6. Also 8.8, with channel steel arm, 5/4-. ROTHERMEL Sapphire Gramophone Needles, permanent, fine reproduction, 12/6. STROBOSCOPES (card-board) showing 78, 79 and 80 r.p.m. on 50 c. viewing, 1/-.

**METAL RECTIFIERS** by STC (Selenium). All for charging up to 12 volts at 1.5 amp., 12/6; 3 amp., 32/6; 6 amp., 39/6; 10 amp., 49/6. These are all full-wave, bridge connected. Suitable TRANSFORMERS, all with tapped primary, 200/250 v. Sec.—7, 11 and 15 v. at 2 amps., 20/- Sec.—8 and 14 v. at 3 amps., 32/6. Sec.—5, 12 and 17 v. at 6 amps., 49/6 (desp. 2/-). These can be sold separately.

**MILLIAMMETERS** by Taylor. High-grade moving coil, 2 1/2 in. flush mtg. Deflection 0/500 milliamms (can be deshunted for lower reading), 29/6.

**VARIABLE RESISTANCES.** Cressall wire-wound p/meters (or rheostats), 10 ohms, 1 amp., with knob, 5/6. SLIDING RESISTANCES, fully enclosed, 100 watt range:—4 ohms 5 amps, 10 ohms 3 amps, 50 ohms, 1.4 amps., 100 ohms 1 amp., 200 ohms 0.7 amp. or 400 ohms 0.5 amp., any one, 27/6. Also 6 ohms 10 amps (600 watts) 59/6 (desp. 3/-).

**INSTRUMENT KNOBS,** 1 1/2 in. with 2 in. skirt, brass bushed with 1/2 in. bore, with 2 set screws, 1/3 each, 11/9 dozen.

**POINTER KNOBS,** brass-bushed, 1/2 in., 8d. each, 6/6 doz.

**LOUDSPEAKERS.** We only offer the superior types. Vitavox High-fidelity P.M. models, with high-flux Alconal magnets, 12in. dia-cast chassis, 15 ohms coils, the K12/10 (10 watt), £7. K12/20 (20 watt), £11 (desp. either 5/-). The new Gramplan 7 watt, 9in. P.M. Speaker with either 2 or 15 ohms coil, 38/- (desp. 1/6). The ideal unit for horn-loading. PROJECTOR SPEAKERS, large range in stock for immediate delivery:—Vitavox 10 watt P.M. Unit (15 ohms) with 2 1/2 in. all-metal round Horn, £10 10s. (desp. 7/6). With 30in. all-metal square Horn, £8 17s. 6d. (desp. 5/-). Units only:—Vitavox 10 watt, £6. G.E.C. 12 watt (with line transf.), £7 10s. Reslo and Gramplan 10 watt, £7 5s.

**HAND MICROPHONES,** ex-Govt., new. Superior carbon type with press-switch, 5 1/2 in. lead and plug, 9/6.

#### FOR CALLERS ONLY

Large range of G.E.C., Gramplan and Vortexion POWER AMPLIFIERS, A.C. and Mobile (12 v.), with or without radio stage. 15 watts to 50 watts, prices £12 to £37 10s. WAVEMETERS, ex-Govt. Class D Mk II, new, great bargain. £5 17s. 6d. Useful range of ROTARY TRANSFORMERS.

Please include sufficient for despatch where not stated

M.R. SUPPLIES Ltd., 68, New Oxford Street, London, W.C.1

Telephone: MUSeum 2958



# WEBB'S

are pleased to introduce the

## EDDYSTONE

"504"

### COMMUNICATION RECEIVER

The new British made "504" Receiver embodying refinements and technique resulting from close contact with war-time research.

Unique unit construction gives great mechanical rigidity. Precision type tuning mechanism, free from back-lash, effective scale length of tuning dial is 36 inches per band. For A.C. operation, 40 to 60 cycles, 110 and 200/240 volts.

We are registering orders for delivery August and September. Supplies will be in strict rotation and early booking is desirable.

Write for details of our registration arrangements, also brochure giving full technical data on the "504."



Some salient features:—

- Nine valves.
- Two R.F. and two I.F. stages.
- Crystal Filter.
- Noise Limiter.
- B.F.O.
- Five switched bands.
- Continuous coverage 30,000 to 600 Kc/s.
- Sensitivity better than 2 microvolts.
- "S" meter.

Specimen Receivers are on show at 14, Soho Street, London, W.1, and our Midlands Depot at 41, Carrs Lane, Birmingham, 4.

PRICE: £48:10s.

(PLUS PURCHASE TAX, £10:8:6)

#### DURALUMIN TUBE

For receiving and transmitting aerials. In 8' 6" lengths covering five and ten metre radiators and reflectors. Outside diameter 3/8".

Per 8' 6" length..... 4s. 6d.

NOTE: CALLERS ONLY FOR THIS TUBE!

#### STAND OFF INSULATORS

For mounting aerial elements, etc. Eddystone "Beehive" type 916, height 2 3/8" 1s. 6d.

Webb's "Heavy Duty," height 6" with clip for 3/8" tube, very strong, long insulation path. 6s. 6d.

#### AERIAL INSULATORS

Pyrex "Strain" type, 3 1/2" long ..... 9d.

Pyrex Heavy Duty, 6" long ..... 6s. 3d.

Pyrex "Shackle" or Egg Insulators for aerial or guy wires ..... 1s. 3d.

#### AERIAL RELAYS

Stocks now available of new double-pole Aerial Changeover Relay. Approximate size 3" x 2 3/8" x 1 3/8" high, low-loss construction. Contacts take 4 amps R.F. Coil operation 4 to 6 volts A.C. .... £2.17s. 6d.

#### CO-AXIAL CABLE

0.54" diameter Polythene insulation, copper braided with green P.V.C. outer covering. Impedance 80 ohms. Per yard ..... 1s. 6d.

(Minimum length supplied is 18 yards.)

#### EDDYSTONE

New Illustrated Eddystone Component Catalogue now available, Post Free for 2 1/2d. stamp.

# Webb's

14 SOHO ST., LONDON, W.1. Phone: Gerrard 2089

# RADIO

Write, phone or call—

Our shop hours are 9 a.m. to 5 p.m. (Saturdays, 9 a.m. to 1 p.m.)



**SIT BACK  
AND RELAX...  
RECEPTION WILL BE  
FAULTLESS  
IF YOU'RE USING**

**Exide**  
L.T. ACCUMULATORS  
**AND**  
**Drydex**  
H.T. BATTERIES

*The perfect pair for  
battery Radio sets*

THE CHLORIDE ELECTRICAL STORAGE CO. LTD.  
CLIFTON JUNCTION · NR. MANCHESTER


EDX2 D

## Portable Electric Fans

S.E.M. design and manufacture electric fans up to 5 h.p. capacity and have had special experience in fans for searchlight and valve cooling and for ship ventilation.

Typical of the range is the compact and portable fan unit designed for ship ventilation. This "centrifugal" unit, with fan mounted on the same shaft as the motor, is capable of displacing 500 cu. ft. of air per minute at 6 inches water gauge pressure.

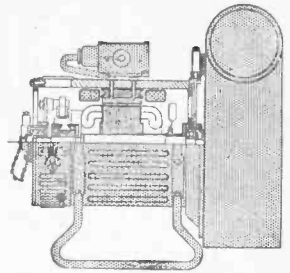In common with all S.E.M. machines, this fan is manufactured to the highest standards of mechanical detail and passes rigid inspection tests.




*S.E.M. Portable Electric Fan for Ship Ventilation*

### SMALL ELECTRIC MOTORS LTD.

have specialized for over 30 years in making electrical machinery and switchgear up to 10kW capacity. They are experienced in the design and manufacture of ventilating fans and blowers, motors, generators, aircraft and motor generators, high-frequency alternators, switchgear, starters and regulators.

*A subsidiary of Broadcast Relay Service Ltd.*

**BECKENHAM · KENT**

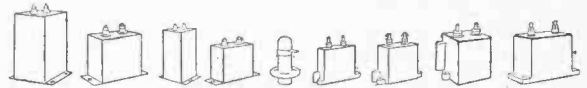


## Wego CAPACITORS

★ **CALCULATED TO ANSWER  
THE MOST EXACTING DEMANDS**


★ **FOR ALL RADIO  
AND ELECTRONIC PURPOSES**

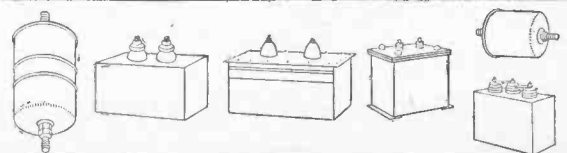**WEGO CONDENSER COMPANY LIMITED**  
ÉIDÉFORD AVE · PERIVALE · GREENFORD · MIDDX · Tel. PERIVALE 4277



# U.I.C.

# Silvered Mica & Ceramic CAPACITORS

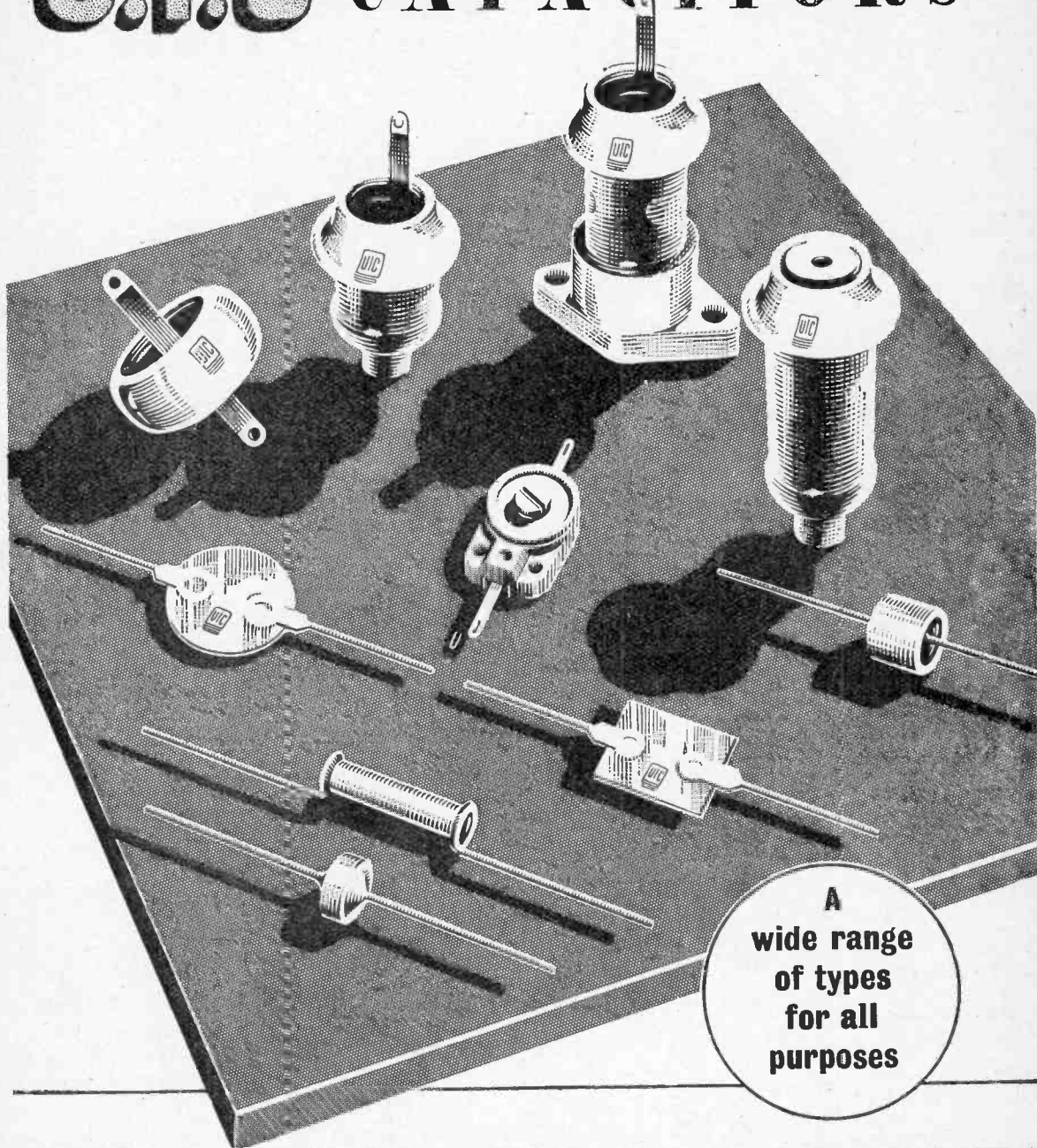

**A  
wide range  
of types  
for all  
purposes**


**UNITED INSULATOR CO. LTD., OAKCROFT ROAD., TOLWORTH, SURBITON, SURREY**

Telephone : Elmbridge 5241 (6 lines)

Telegrams : Calanel, Surbiton

*Unsurpassed In Ceramics*

ANNOUNCING

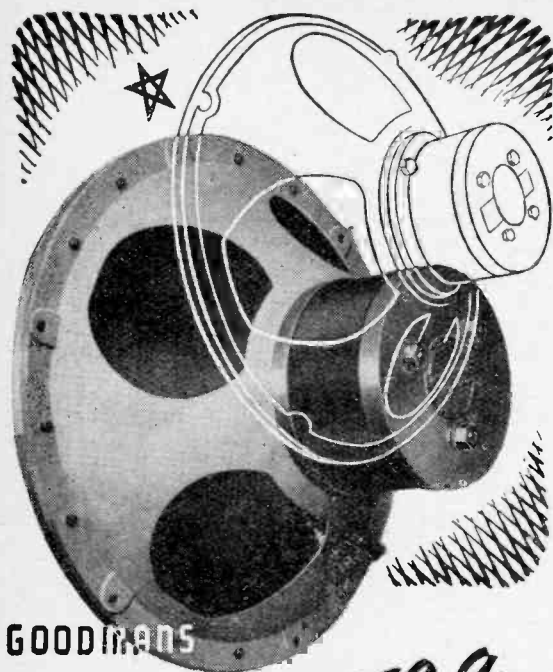

GOODMANS

Announce a  
**15 in**

LOUDSPEAKER

The illustration shows the comparative sizes of a Goodmans 15 in. and 12 in. Loudspeaker. You already know the performance of the famous 12 in. Now consider the technical data of the new 15 in. model.

Overall Diam. 15 in.—  
Overall Depth 8 in.  
Fundamental Reso-  
nance—55 c.p.s.  
Voice Coil Diam—2 in.  
Voice Coil Imped.—4  
ohms at 400 c.p.s.  
Flux Density—14,500  
gauss.  
Max. Power Capacity—  
25 W. peak A.C.  
Net Weight—26lb. 8oz.

With an excellent re-  
sponse up to 6,000 c.p.s.,  
and an unusually high  
power handling capacity,  
this instrument sets a new  
standard in Loudspeakers  
for the Dance Hall, Rink,  
Cinema and Heavy Duty  
P.A. installations.

PRICE £18.10s. *subject*)

The **GOODMANS** T10/1501/3-5  
*Loudspeaker*

GOODMANS INDUSTRIES LTD., LANCELOT RD., WEMBLEY, MIDDX.  
Telephone: Wembley 4001 (8 lines).



NOW IN PRODUCTION

- ★ Artistically designed — scientifically developed.
- ★ Light in weight—small in size.
- ★ Constant Velocity type, response from 30 C.P.S. to 12,000 C.P.S. without objectionable resonances.
- ★ Weight of pick-up on to record 30 grams, armature and needle weight .090 grams.
- ★ When used on high fidelity reproducing equipment the realism is amazing.

MADE BY  
**A. R. SUGDEN & CO. (ENGINEERS) LTD.**  
BRIGHOUSE YORKSHIRE

**R.F. ELECTRONIC VOLTMETER**

By **RADIO-AID LIMITED**  
29 MARKET ST., WATFORD, HERTS.

TYPE B. Full scale deflection 1 volt R.M.S., four ranges to 250 volts.  
Standard Probe impedance 6 Mc/s in parallel with 3 pf thermal drift compensated.



TYPE B £42-12-0

Sole London Agents  
**WEBB'S RADIO, 14, SOHO STREET, W.1.**





*prefers*

**B.I.**  
*Callender's*

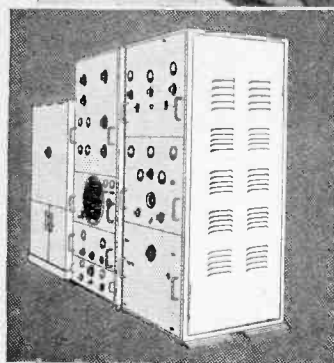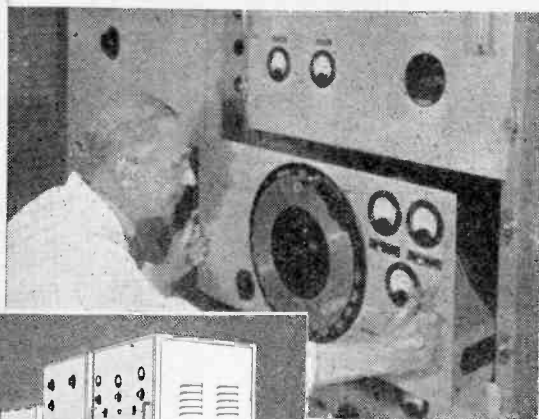**PRODUCTS**

Our products for the Radio Industry range from the tallest steel radio towers to 0.001  $\mu$ F capacitors. If you're not interested in monsters or midgets we make a lot of other things besides, including every type of cable and wire used in radio work. You get the benefit of 60 odd years' research and manufacturing experience when you specify B.I. Callender's.

**BRITISH INSULATED CALLENDER'S CABLES LIMITED**  
NORFOLK HOUSE, NORFOLK STREET, LONDON W.C.2



**REDIFON**

**G.12T**

**Transmitter**

**102 to 1200 Kilocycles**

**T**HE Redifon G.12T transmitter covers the very wide frequency range of from 102 to 1,200 k/cs, divided into four overlapping bands with continuous tuning throughout.

This transmitter is suitable for long-range aircraft beacons and communications, for shipping control and services, and general telegraphic transmissions over distances extending to upwards of 1,000 miles. The power is 2,000 watts on C.W. or 450 watts telephony or M.C.W.

Many of these transmitters have been used on arduous service involving continuous operation at full load, with only one 3-hour break for maintenance each three months. This is typical of their overall reliability.

The extremely compact design of the Redifon G.12T makes it suitable for mobile use, particularly in areas undergoing reconstruction. The three bays take up a floor space of only 8 feet 8 inches by 2 feet 4 inches and the overall height is 5 feet 5 inches.

This transmitter is available for almost *immediate delivery*. Further particulars can be supplied on request.

**REDIFFUSION LTD.**

*Designers and Manufacturers of Radio Communication and Industrial Electronic Equipment.*

Subsidiary of Broadcast Relay Service Limited,


**CARLTON HOUSE, REGENT STREET, S.W.1**

**BERRY'S (SHORT WAVE) LTD.**

*have been appointed Distributors of*

**'Labgear'**

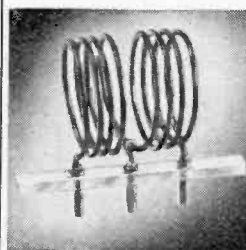**HIGH CLASS COMPONENTS FOR EXPERIMENTAL AND AMATEUR TRANSMITTING AND SHORT WAVE WORK.**



- Single section and Split stator Transmitting Condensers.
- Plug-in Inductances with fixed coupling link.
- Neutralising Condensers.
- Transmitting Chokes.
- Crystal Calibrators.
- Cathode Ray Viewing Units.

**"Q-MAX" SLOW MOTION DIAL for Individual Calibration—**

9—1 slow motion drive. Dial engraved five blank scales and one 0-180, with escutcheon, glass and black fluted knob. **15/6**  
(Post 9d. extra)

**"Q-MAX" CHASSIS CUTTER**

This cutter ends your tiresome drilling and scraping.

For 1½ in. holes (octal base). (Post 9d. extra) **10/6**

**BERRY'S**  
**(SHORT WAVE) LTD.**

**25, HIGH HOLBORN, LONDON, W.C.1**

(Phone: HOLborn 6231)

(Opp. Chancery Lane)

**Varley**  
TRADE MARK.  
**SLIDER RESISTANCES**



A resistance of exceptionally robust construction, wound on high quality vitreous enamelled tubes. Nickel-copper alloy wire is used for the resistance. An ideal product for use in:—

**LABORATORIES  
TEST EQUIPMENT  
BATTERY CHARGING  
SPEED CONTROL, etc.**


**OLIVER PELL CONTROL LTD**

**CAMBRIDGE ROW · WOOLWICH · S.E.18**

**TELEPHONE: WOOLWICH: 1422**
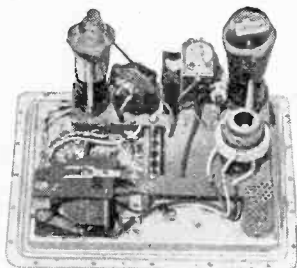
# LINAGLOW LIMITED

To meet the demand for various parts of the well-known **R.A.F. PORTABLE DINGHY RADIO TRANSMITTER**, which cost approximately £39 to manufacture, we are this month offering the Transmitter in the following sections and components :—



### TOP PANEL

Comprising: Valves 6J7 and 6V6.—Crystal, 500 kc/s. accuracy .025%—Variable Condenser with Neon Radiation Indicator—Litz Wound Coils (Iron Dust Core)—Transformer—H.F. Choke—Various Condensers and Resistors, etc.

PRICE **22/6**

Postage and packing 1/6

### CRYSTAL

500 Kc/s. Accuracy .025%. Mounted in bakelite holder with two pin ( $\frac{3}{8}$ " spaced) fitting

PRICE **10/6**


Post paid

### WOODEN BOXES

Cost 30/- to manufacture. Ideal for Tool Box or for storage of spare parts. Made of  $\frac{7}{16}$ " plywood with hinged lid. Divided into two sections 12" and 4" wide. Internal dimensions  $16\frac{1}{2}$ " x 12" x  $9\frac{1}{2}$ " deep.

PRICE **5/6**

Postage 1/1

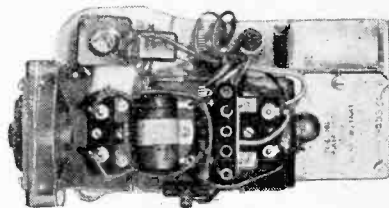

### POWER PACK

Comprising: Hand Generator with handle (300 volts 60 mA. H.T. and 6 volts 2 amp. L.T.)—Voltage Regulator—Smoothing Unit—Relays—Electrolytic Condenser, etc.

PRICE **22/6**

Postage and packing 1/6

LINAGLOW LIMITED, Dept. M.O.70, 34, OSNABURGH ST., EUSTON RD., LONDON, N.W.1 (Nr. Gt. Portland Street Station) Telephone No. EUSTON 8406 (5 lines).

## Don't play blind man's buff

Quick identification of cables and components saves labour, time and error. Lasso Identification Tapes provide neat, legible markers that are quickly applied at any point. They also make neat, permanent name tabs for marking furniture, containers, plastics and tools. Lasso Tapes are supplied in 10 yard rolls, printed with your own inscriptions at intervals spaced to suit diameters and other measurements. Inscriptions cannot be erased. Lasso Tapes are self-adhesive, resistant to water, oil, petrol and solvents, and are tested for tensile strength, durability and electrical resistance. An interesting booklet is free on request.

LASSOVIC · LASSOTHENE · LASSOBAND · LASSOFIBRE  
LASSOTHYL · LASSOPHANE · LASSOLASTIC

# LASSO PRODUCTS

TRADE MARK


Pressure Sensitive Tapes

FOR SEALING, LABELLING AND IDENTIFICATION

Herts Pharmaceuticals Ltd., Welwyn Garden City, Herts Tel.: Welwyn Garden 3333 (6 lines) (C4)

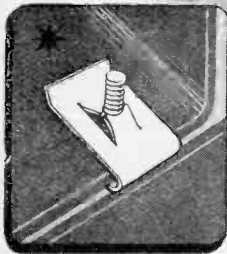
# READY...AYE READY!

What a fine fumbling job it is, messing around with dozens of tiny nuts and washers and bolts, picking up the nut, holding the bolt with one hand while the other fiddles round the back to get the nut on the thread. And drops it! You know! Spire solves the problem. Spire U nuts slip into position over the bolt holes—no washers needed with a Spire fixing, of course. So both hands are free to put in the screws and once they're in, they're in for good. Sounds easy and it is easy!


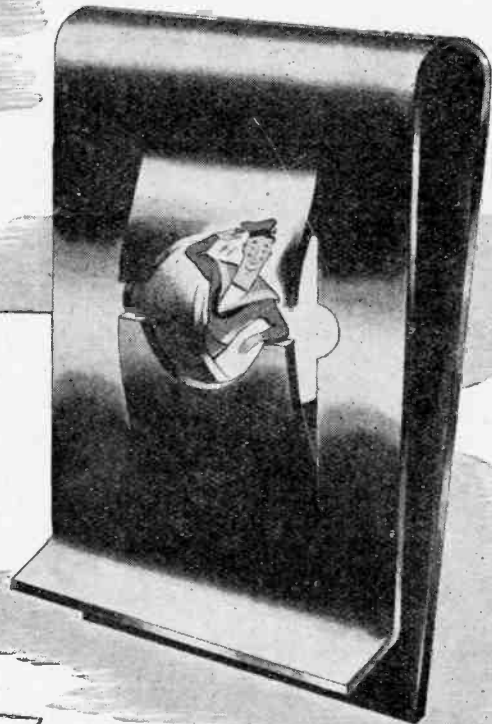
### THAT'S Fixed THAT!

Here's a little chap in action Reference No. NU 531. Its uses are legion. Wherever there is blind assembly work, wherever your operatives are fumbling with nuts and washers the NU 531 will save time and cost and a lot of bad temper. Clip it into position and it stays "put" until you are ready to drive home the screw. No washer needed of course.



# Spire

(Regd.)

\* A BETTER Way of Fixing

Simmonds Aerocessories Limited • Great West Road • London • A Company of the Simmonds Group



# Wireless World

Radio and Electronics

36th YEAR OF PUBLICATION

## SEPTEMBER 1946

Proprietors:  
ILIFFE & SONS LTD.

Managing Editor:  
HUGH S. POCOCK,  
M.I.E.E.

Editor:  
H. F. SMITH

Editorial, Advertising  
and Publishing Offices:

DORSET HOUSE,  
STAMFORD STREET,  
LONDON, S.E.1.

Telephone:  
Waterloo 3333 (50 lines).

Telegrams:  
"Ethaworld, Sedist, London."



**PUBLISHED  
MONTHLY**

Price : 1/6

(Publication date 26th  
of preceding month)

Subscription Rate:  
Home and Abroad  
20/- per annum.

MONTHLY COMMENTARY .. .. .	281
ARMY NO. 10 SET .. .. .	282
RADAR IN NATURE By Thomas Roddam .. .. .	286
ELECTROMAGNETIC FRAME SCANNING By W. T. Cocking .. .. .	289
SHORT-WAVE FORECASTING (Concluded) By T. W. Bennington .. .. .	292
WORLD OF WIRELESS CONVENTIONS AND VIEWPOINTS By "Cathode Ray" .. .. .	299
DESIGN DATA (7) Video Amplifier H.F. Response..	301
AIDS TO TRAINING By M. G. Scroggie .. .. .	303
AMERICAN SERVICE VALVE EQUIVALENTS ..	305
RADIO AUSTRALIS .. .. .	306
RANDOM RADIATIONS By "Diallist" .. .. .	308
SHORT-WAVE CONDITIONS .. .. .	309
LETTERS TO THE EDITOR .. .. .	311
RECENT INVENTIONS .. .. .	314

Branch Offices :  
COVENTRY :  
8-10, Corporation Street.  
Telephone : Coventry 5210.  
Telegrams :  
"Autocar, Coventry."

BIRMINGHAM :  
King Edward House,  
New Street.  
Telephone :  
Midland 7191 (7 lines).  
Telegrams :  
"Autopress, Birmingham."

MANCHESTER :  
260, Deansgate, 3.  
Telephone :  
Blackfriars 4412 (4 lines).  
Telegrams :  
"Iliffe, Manchester."

GLASGOW :  
26B, Renfield Street, C.2.  
Telephone : Central 4857.  
Telegrams : "Iliffe, Glasgow."




*As many of the circuits and apparatus described in these pages are covered by patents, readers are advised, before making use of them, to satisfy themselves that they would not be infringing patents.*


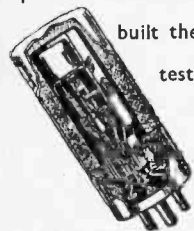
## ... but **WEARITE** Stratosil Sealed VIBRATORS OPERATE EFFICIENTLY UNDER ALL CLIMATIC CONDITIONS

Come rain, come shine, or any other climatic condition, Wearite 'Stratosil Sealed' Vibrators will continue to operate without trouble. Why? Oh! We designed and built them with just that end in view, and after tests, specified the following as essentials ...




- All steel construction — even the rivets — uniform expansion under temperature extremes ensured.
- Vibrator acoustically and electrically shielded by Metal Can, sponge rubber lined.
- Precious metal driving contacts — non-tarnishable — ensure starting under the lightest pressures and voltages.
- Contacts ground almost to optical limits.
- Stack assembly — mica and steel only used.
- Base sealed by the WEARITE Stratosil process.
- Always keep going ...

## STRATOSIL Sealed VIBRATORS

SEND TODAY FOR FURTHER DETAILS, AND REMEMBER, WE ALSO MAKE SOME OF THE BEST TRANSFORMERS, COILS AND SWITCHES.

**WRIGHT and WEAIRE LIMITED**  
HIGH ROAD · TOTTENHAM · LONDON · N.17 · TELEPHONE: TOTTENHAM 3847-9

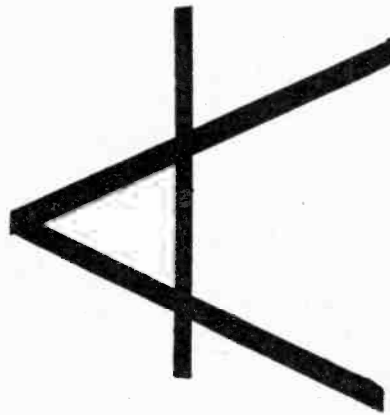*This*  
*mathematical*  
*symbol means*  
**'not less**  
**than'**



*This*  
*well-known*  
*emblem*  
*means*  
**'not less than**  
**the best'**

**PHILIPS**

**LAMPS · RADIO · X-RAY · COMMUNICATIONS EQUIPMENT  
 AND ALLIED ELECTRICAL PRODUCTS**

PHILIPS LAMPS LIMITED · CENTURY HOUSE · SHAFTESBURY AVENUE · LONDON · W.C.2

(1251)

# Wireless World

Radio and Electronics

Vol. LII. No. 9

SEPTEMBER, 1946

Price 1s. 6d.

## Monthly Commentary

### *Illicit Transmission*

IT had to come. Although we do not know, at the time of closing for press, how complete the ban on the sale of ex-Government transmitters will be, it is clear that gear with enormous potentialities for doing harm should not be sold indiscriminately to all comers, as it has been during the past few months. True, complete suppression of sale to the public will not put an end to the clandestine transmitter, but it will at least remove an almost irresistible temptation from the path of the irresponsible kind of person who is likely to cause the maximum of interference to legitimate services.

The position at present seems to be that, by agreement between the Government departments concerned, the sale of transmitters, at any rate of certain classes, is to be discontinued, except under conditions which reduce the risk of the sets falling into undesirable hands. No doubt methods will ultimately be devised whereby those qualified to make legitimate use of the sets will be able to obtain them. In the meantime, it seems likely that a certain amount of hardship will be suffered. It is a pity that the inevitable results of indiscriminate sale were not foreseen, and proper steps taken from the first to dispose of the sets to those who could make good use of them, or at least of their components. In particular, we can see no reason why the offer of the Radio Society of Great Britain to purchase sets on behalf of its members, made some considerable time ago, should have been flatly declined.

### *Guarantees*

MUTUAL goodwill between producer and consumer is surely something to be striven for. If that can be accepted as axiomatic, it is to be regretted that, in framing the new standardized form of broadcast receiver guarantee,

the British Radio Equipment Manufacturers' Association has lost an opportunity to remove a common cause of friction between seller and customer. We refer to the clause which states that the labour costs incurred in replacing a faulty component may, at the manufacturer's discretion, be charged to the customer.

Not unnaturally, the owner of a receiver feels aggrieved if he is charged an appreciable sum for the replacement of a component that is admittedly defective through faulty workmanship or materials. His ruffled feelings are not soothed by the fact that the replacement component itself has been given to him without cost. He argues, with some force, that the replacement was made necessary by an admitted error of judgment or negligence on the part of the manufacturer; why should he have to pay?

We have little doubt that the offending clause will in most cases be interpreted liberally, but that is hardly enough. The question of maintenance service is likely to assume particular importance during the early period of television development. The revised form of guarantee applies to television sets, and it is highly desirable that the growth of the new art should not be hampered by unsavoury squabbles over repair charges. The whole matter should be put upon a firm and equitable basis.

### *F.M. versus A.M.*

THE issue between F.M. and A.M. is one that cannot be determined in the laboratory, but only by widespread field test. Consequently, the results of the B.B.C. frequency modulation trials, described by H. L. Kirke (head of the research department) in the current *B.B.C. Quarterly* will be read with particular interest. The general conclusion is very much in favour of F.M. as a means of distributing high-quality noise-free broadcasting.

# ARMY No. 10 SET

## Some Details of the U.H.F. Equipment

**S**IGNALLING Equipment No. 10 which forms part of the Army Wireless Set No. 10, was described under the title "Pulse Width Modulation" in

waveguides and coaxial cables. The principles of waveguide engineering and their uses in connection with coaxial cables have been dealt with in the issues of

*Wireless World* for September and October, 1944. Resonant cavities are used in U.H.F. equipment for tuning purposes in much the same way as the more familiar tuned circuits are employed at lower frequencies.

These cavities are described below in relation to this particular equipment, but it is as well to give some general remarks at this point. The same principles apply to them as to waveguides and it is assumed that reference has been made to the earlier *Wireless World* articles. A resonant cavity is merely a waveguide of a certain length, usually a multiple or sub-multiple of a wavelength, closed at each end. Where such a cavity is, say, one wavelength long and energy of the appropriate frequency is fed into it, this energy will build up until quite large amplitudes are obtained. It will then be seen that if a cavity is equipped with a movable piston at one end it fulfils much the same purpose as the more familiar tuned circuit consisting of coils

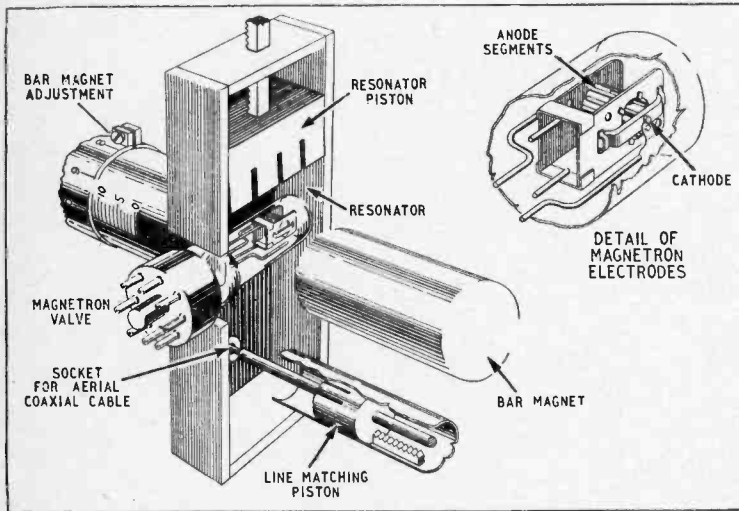


Fig. 1. This cut-away drawing shows the interior of the resonator used with the magnetron in the sender. The construction of the magnetron itself is indicated in the inset-sketch.


the June issue of *Wireless World*.

It was explained how eight audio-frequency channels were made to modulate in width a series of rectangular pulses in the pulser or sending section of the equipment and how the separator recovered the audio channels from the received width-modulated pulses.

The width-modulated pulses produced by the pulser are used to modulate a magnetron U.H.F. sender working at a frequency of about 4,500 Mc/s. The receiver is of the super-heterodyne type and the pulses in its output are passed to the separator section of the Signalling Equipment No. 10.

It is the purpose of the present article to conclude the account of the 10 set with a description of the U.H.F. sender, receiver and aerial system.

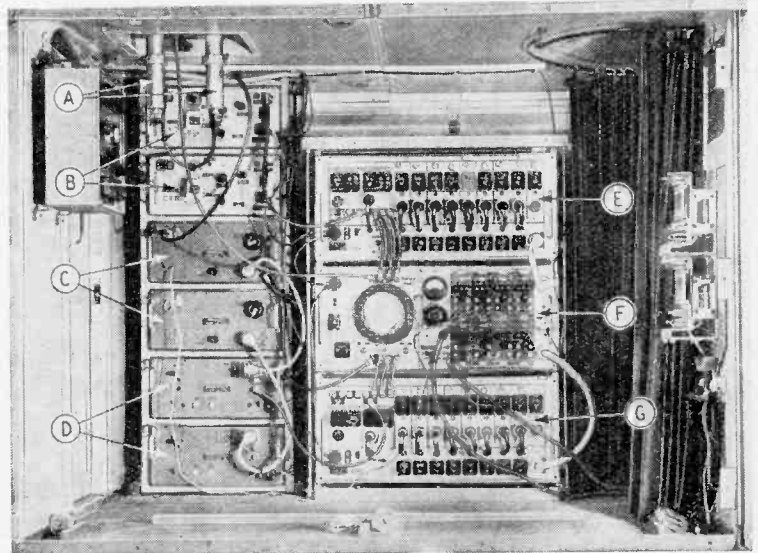It is usual in U.H.F. equipment to conduct the energy from one unit to another by means of



An interior view of the trailer of the No. 10 station. The various units are: A, waveguide matching sections; B, duplicate sender units; C, duplicate receivers; D, duplicate power supply units. The Signalling Equipment No. 10 consists of the pulser E, the monitor F, and the separator G.



and capacitors at lower frequencies. Arrangements for feeding in



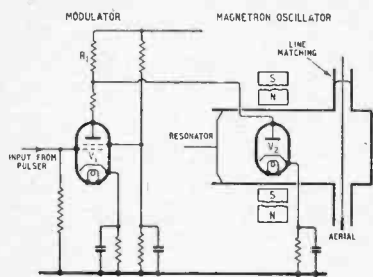


Fig. 2. Circuit diagram of the sender including the modulator valve which is fed with the pulses produced in the pulser unit.

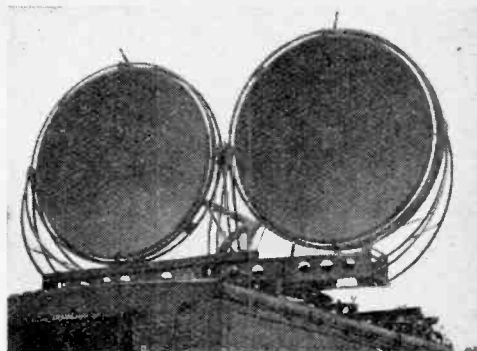

The aerial system is mounted on the roof of the trailer

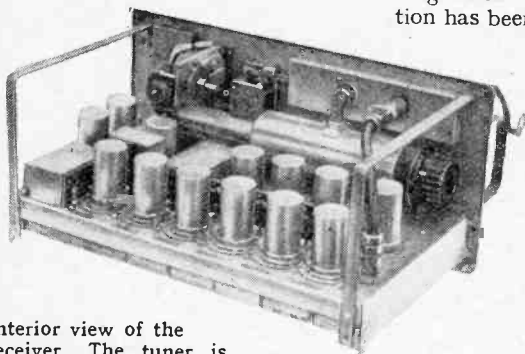and abstracting energy from a resonant cavity are similar to



Interior view of the receiver. The tuner is just visible close to the panel

those used for the waveguides treated in the earlier articles. The tuning cavities are of rectangular cross-section and are designed for electromagnetic waves of  $H_{01}$  mode. It will be remembered that for  $H_{01}$  waves longitudinal loops of magnetic lines of force are formed and electric lines of force stretch from one side of the enclosure to the other. In a resonant cavity, the loops build up to form standing waves, the amplitude reached de-

pending on the power dissipated in the material of which the cavity is made and the load to which it is coupled.

The waveguides used in this equipment are of circular cross-section and propagate  $H_{10}$  waves. Longitudinal loops of magnetic lines of force are formed in this case also and the transfer of energy along the waveguide may be considered as due to the loops of magnetic lines of force moving down the waveguide.

A frequency of about 4,500 Mc/s is generated by a split-anode magnetron valve. The use of the magnetron valve in this connection has been described elsewhere, but it is of interest to note the construction of the electrodes which is shown in the inset of Fig. 1. The anode segments are arranged in cylindrical formation, the cathode lying along the axis. The magnetic field required to give the necessary spiral motion to the electrons is supplied by two cylindrical bar magnets and the magnetron

mounting allows the valve to be rotated to a certain extent to bring the axis of the cylindrical anode parallel with the field. One of the magnets has a micrometer adjustment which enables the strength of the magnetic field to be varied, to suit the particular type of valve employed.

Energy is extracted from the magnetron by arranging that it lies in a rectangular cavity. This cavity is tuned to resonance at the frequency of the oscillator by an adjustable piston. The central conductor of a coaxial line crosses the cavity at a distance approximately one-quarter wavelength from the end and this picks up energy which is conveyed by the coaxial line to the aerial system. The impedance of the coaxial line is matched by an adjustable pis-

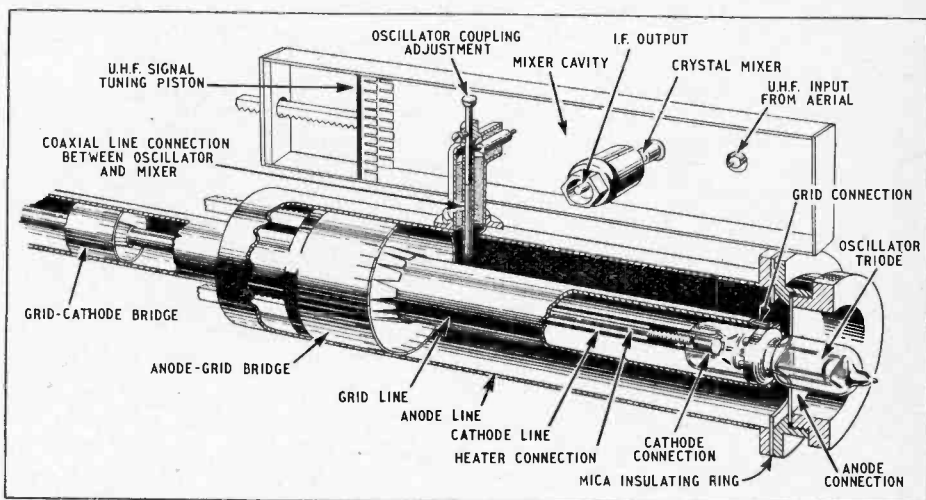



Fig. 3. Construction of oscillator and mixer used in the receiver is shown here. The oscillator is a triode and the third harmonic of its output is fed to the crystal mixer.

**Army No. 10 Set**—  
ton in a cavity into which the  
centre conductor extends on the

a mixer cavity or resonator, from  
a coaxial cable, the centre con-  
ductor projecting into the cavity

quency is tuned by a resonat-  
ing cavity instead of the more  
familiar coil and capacitor. It is

**Fig. 4. Circuit of the receiver.** The mixer is followed by a wide-band I.F. amplifier with diode detector and a V.F. stage. The output pulses are fed to the separator.

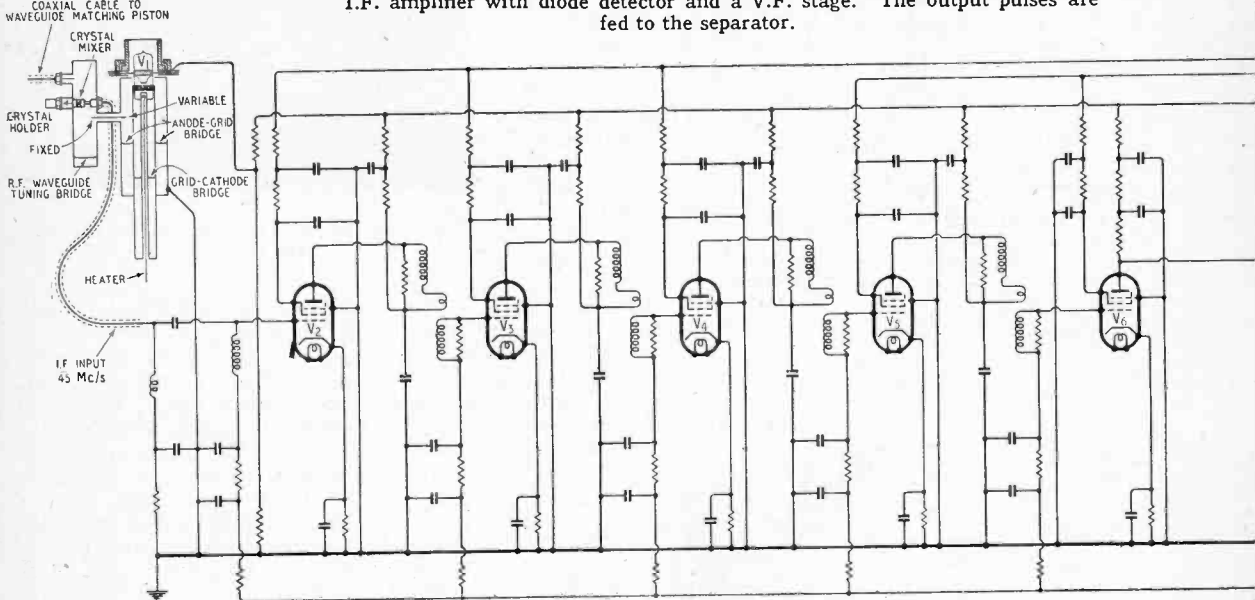

side of the resonator opposite the  
point where the coaxial line  
enters.

The manner in which the mag-  
netron is modulated may be un-  
derstood from the circuit of the  
sender shown in Fig. 2.  $V_2$  rep-  
resents the oscillator and  $V_1$  the  
modulator. With no input from  
the Signalling Equipment No. 10,  
 $V_1$  is so biased that it draws cur-  
rent. The magnetron H.T.  
supply is taken from a voltage-  
dropping resistance  $R_1$  common  
to both valves and when  $V_1$  is  
taking current, the anode poten-  
tial of  $V_2$  is too low for that valve  
to oscillate. The arrival of a nega-  
tive pulse from the Signalling  
Equipment No. 10 at the grid of  
 $V_1$ , however, stops that valve  
from drawing anode current and  
the consequent rise in the anode  
voltage of  $V_2$ , about 300V, is suf-  
ficient to start the magnetron  
oscillating.


The output of the Signalling  
Equipment No. 10 consists of a  
series of negative-going pulses and  
thus the output from the sender  
consists of corresponding pulses of  
U.H.F. energy.

At the receiver (Fig. 3), the  
input from the aerial is fed into

about  $\frac{1}{4}$  wavelength from one end.  
Energy from a local oscillator  
is similarly fed into the cavity at  
the other end. A crystal detector  
mounted across the cavity, i.e.,  
parallel to the direction of the  
electric field, rectifies the oscil-  
lator and signal frequencies, thus  
producing a difference frequency  
(i.e., signal frequency minus oscil-

also interesting to notice that the  
principle of heterodyning applies  
also at these frequencies although  
the arrangements required to  
carry it out are somewhat differ-  
ent.

The local oscillator uses a  
miniature-type triode valve oscil-  
lating at about 1,485 Mc/s. The  
third harmonic of this frequency  
is used to mix with the signal fre-  
quency. The arrangement of the  
oscillator itself is very similar to  
that of the familiar triode oscil-  
lator tuned by a Lecher-wire  
system, the difference in this  
case being that the wires are re-  
placed by concentric cylinders. Such  
an arrangement constitutes a system

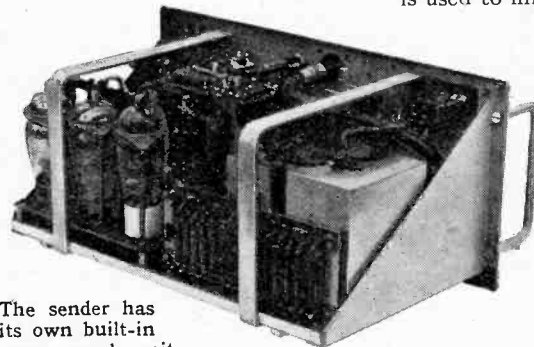

The sender has  
its own built-in  
power supply unit.


lator frequency) of about 45 Mc/s  
which is amplified by an I.F.  
amplifier. It will be seen that  
there is nothing fundamentally  
different between this circuit and  
that of an ordinary superhetero-  
dyne receiver. The signal fre-

quency of about 45 Mc/s which is amplified by an I.F. amplifier. It will be seen that there is nothing fundamentally different between this circuit and that of an ordinary superheterodyne receiver. The signal fre-

and the grid-cathode lines to cause the circuit to oscillate is provided by internal capacitance in the valve. The coupling between the mixer cavity and the cavity between the anode and grid lines is by means of a concentric feeder,

citance diode  $V_8$  acts as detector and this is followed by an amplifier  $V_9$  and a cathode-follower stage  $V_{10}$ , the latter giving a low impedance output required to match the input of the Signalling Equipment No. 10. This output

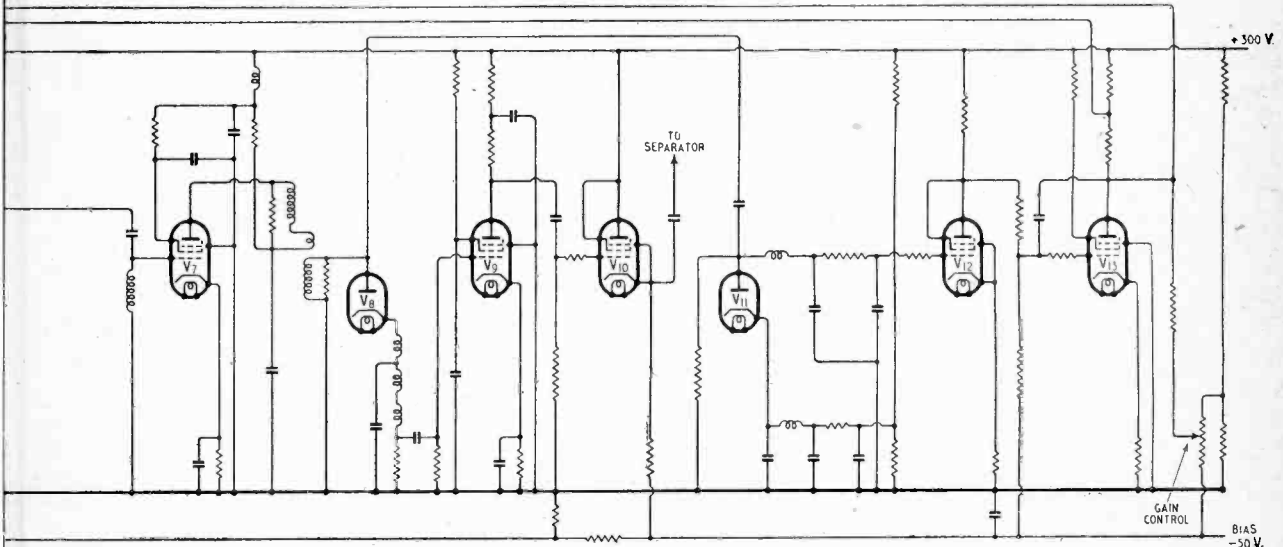ble waveguide connects the mirror to a waveguide matching section just below the trailer roof and a coaxial cable connects the matching section to the sender or receiver. The waveguide enters the centre of the mirror at the rear



the centre conductor extending into the mixer and oscillator cavi-

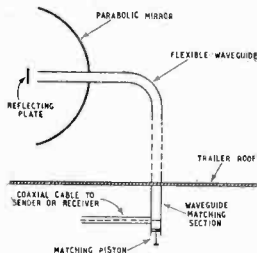


Fig. 5. This sketch shows the arrangement of the aerial system. A paraboloid is energized by a waveguide having a reflector plate opposite to its open end.

ties at each end. The oscillator coupling adjustment shown in Fig. 3, by varying the extent to which the centre conductor can protrude into the oscillator cavity, varies the amount of coupling between the oscillator and the mixer cavity.

The I.F. amplifier ( $V_2$ - $V_7$  in Fig. 4) is of conventional design and similar to the television amplifiers met with in commercial television receivers. A low-capacitance

consists of a series of positive-going pulses. Automatic gain control is provided by the diode  $V_{11}$ , which rectifies part of the output of the I.F. amplifier, followed by the D.C. amplifiers  $V_{12}$  and  $V_{13}$ . The control is applied direct to the screens of the

and carries a circular reflecting plate in front of its open end. This reflecting plate lies in the focal plane of the mirror. Inside the trailer the waveguide terminates in a matching section. This consists of a rigid tube connected at one end to the flexible guide and closed at the other by a movable matching piston. The centre line of a coaxial cable crosses the tube in front of the piston which can be adjusted to give the correct impedance match.

This article is published by permission of the Director General of Scientific Research (Defence).

WIRELESS TELEGRAPHISTS' HANDBOOK

THE eighth edition of the "Handbook of Technical Instruction for Wireless Telegraphists," by H. M. Dowsett and L. E. Q. Walker, which first appeared in 1913, was recently published from the offices of *Wireless World*. In addition to providing a complete theoretical course for the P.M.G. certificate for sea-going wireless operators, the Handbook, which costs 30s, gives practical details on the installation and maintenance of marine radio equipment. It contains 668 pp. and includes 618 illustrations and diagrams.

OUR COVER

This month's cover illustration shows the parabolic reflectors for the Army's No. 10 set, mounted on the roof of the trailer. The half-wave dipoles, located off the centre of the paraboloid, are for monitoring purposes

first three I.F. valves from the anode of  $V_{13}$ .

The aerial system which is illustrated diagrammatically in Fig. 5, comprises two parabolic mirrors, one for the receiver and one for the sender. These aeri- als are mounted on the roof of a trailer, the remainder of the equipment being inside. The connection between each aerial and its sender or receiver is in two stages. A flexi-

# RADAR IN NATURE

## Pulse Technique at Supersonic Frequencies

THE original plan of this article was that it should give a general description of an acoustic system analogous to radar, for the benefit of any *Wireless World* readers who might care to construct a model radar system. Only in such a way can the home constructor work in the radar field, for the power required for radar working is quite prohibitive even if many other practical difficulties did not exist. Unfortunately, the writer has had no opportunity of making such an acoustic model and was still nervous lest he should be asked for more details, when a most interesting paper<sup>1</sup> appeared on the acoustic equipment of bats which suggested a broader treatment.

Immediately, it must be explained that there is no suggestion that readers should become bat-fanciers: such a suggestion would probably cause a deputation of readers' wives, led by Mrs. Free Grid, to storm my attic in Pimlico. Equally, however, there is no suggestion that the younger readers should not take twilight walks along secluded lanes to study the habits of bats.


The interesting thing about bats to the radio engineer is their habit of flying about at full speed in dim lights. In fact, they can fly perfectly safely in total darkness. This apparent recklessness, however, does not lead them into constant collisions with the many obstructions which might harm them: even telegraph wires do not seem to constitute a hazard. To explain this behaviour it was suggested in 1920 by Professor Hartridge that bats were fitted with what would now be called a sonar system. Quite recently it has been shown that this is in

By THOMAS RODDAM

fact the case, and that bats are equipped with a very efficient system for blind flying. This equipment is sometimes unserviceable, and a particular form of unserviceability occurs when the bat has a cold in the head, a disorder common in all animals kept in captivity, such as members of the Government Scientific Service. If a bat is deafened by plugging its ears it also loses the use of its blind flying system.

In flight a bat may, according to Hartridge (*loc. cit.*), produce any of four different kinds of sound:

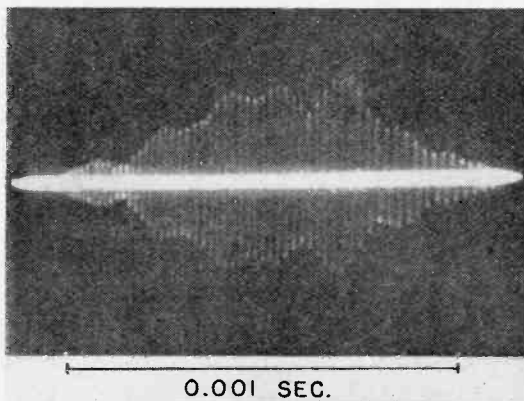- (1) A buzz of about 12-60c/s;
- (2) A tone of about 7,000c/s and lasting for about a quarter of a second. This is probably used



Oscillogram of supersonic cry of a bat taken by Dr. D. R. Griffin of Harvard University. The horizontal sweep motion is from left to right.

as a communication channel to enable messages to be sent to other bats.

- (3) A supersonic tone usually about 40-50c/s, but sometimes as low as 30kc/s or as high as 70kc/s. Pulses of this tone, each lasting about 1,1,000th second, are produced and normally twenty or thirty pulses per second are emitted. At rest the rate falls to 5-10 pulses per second, while when

there is an obstacle immediately ahead the rate rises to sixty pulses per second.

- (4) A click, which is probably a single pulse of the supersonic tone.

The mechanism which produces these various sounds is outside the scope of this article: it is discussed in the paper referred to above. A further discussion of the click appears in a later paper<sup>2</sup> and a letter<sup>3</sup>. Details of the various theories will not be given here, as the evidence does not seem to be sufficient to enable any really final conclusions to be drawn. There is also some conflict of opinion about just how the sound is radiated. Hartridge considers that it is emitted from the nose of the bat, while Griffin is convinced that the mouth is used. It would perhaps be un-

kind to suggest that there is some difference between Harvard bats and London bats in this matter. Many bats have snouts so shaped that fairly good beaming of the supersonic tone would be obtained, thus giving a useful power gain in the direction of dangerous obstacles. In addition, as the bat uses its ears for reception and direction finding, beaming of the signal reduces the level of the direct sound and thus prevents the echo being masked by a strong transmitted pulse. There is almost certainly some additional protection provided which desensitizes the hearing while the pulse is being emitted. The receiving system is also directive; a large flap extends from the side of the bat's head behind each ear, providing considerably increased sensitivity in a forward direction.

It is interesting to note that the sonar system used by bats is just

<sup>1</sup> *Nature* Vol. 156, p. 490 (1945). (This paper has a list of 14 references which can profitably be consulted.)

<sup>2</sup> *Nature* Vol. 158 p. 46.

<sup>3</sup> *Nature* Vol. 158 p. 135.

good enough for the job. In a description of the flight of bats towards a large lighted window<sup>4</sup>, it is stated that on nearing the window the bats went into steep turns, stalled turns or half-rolls. An interesting avoiding technique adopted consisted of folding the starboard wing, which gave an unbalanced and reduced lift, swinging the bat on to its back and allowing the nose to drop. The wing was then opened again and the bat dropped in a vertical dive with its belly towards the window and pulled out about four feet lower down. This manoeuvre was carried out within a foot of the window, avoiding action having begun about two feet from the obstruction. Assuming a speed of 25 feet/second and a reaction time of 1/10th second, the decision to turn must have been taken at a range of about four feet.

The pulse length is sufficiently short for a minimum range of about one foot, which corresponds to a total delay time of 2 milliseconds. Any muting during transmission will probably increase the minimum range, but clearly the performance is quite adequate for ordinary flying.

So much for this natural form of "supersonic radar" as it is observed by the zoologists. Let us now consider the "design data."

The reader will remember that in an ordinary radar system a short train of radio waves is produced. This train of waves travels off into space with a velocity of  $3 \times 10^{10}$  cm/sec, is reflected by the target and the echo is picked up by the receiver. If the time between the transmitted pulse and the received echo is 10 microseconds, the target is clearly at a distance of 1,500 metres. Sound waves in air have a velocity of 34,250 cm/sec. at a room temperature of 20°C. (At other temperatures the velocity is  $33,170 + 54t$  cm/sec.) The ratio of sound velocity in air to radio velocity in free space is therefore about  $1.1 \times 10^6$ . As far as timing goes, therefore, a one-

inch range with sound waves is roughly equivalent to 16 miles range with radio waves. For making a model radar system using supersonics the standard international map series with a scale of  $1:10^6$  can be used to replace the actual area of a radar system.

It is not very convenient to scale all the other dimensions of a radar system in the same way, and it is usual to base supersonic systems on the attenuation charac-

teristic of supersonic waves in air. In Fig. 1 the range for a fall in intensity of 10db is plotted against frequency. It will be seen that with a frequency of 100kc/s the range is four metres. A perfect reflector at this range would, therefore, produce an echo 20db down. At the lower frequency of 50kc/s used by bats the corresponding range is greater, about 12 metres on this 20db criterion.

The actual transmitted field strength is about 10-50 dynes/cm<sup>2</sup>, but there does not seem to be much information on the minimum size of object which can be detected. It seems that useful information could be obtained by jamming experiments, in which the room was filled with noise distributed throughout the 30-70kc/s band. With a noise field exceeding the pulse strength which the bat expects, the bat should find it impossible to detect objects in time to avoid them.

A frequency of 100kc/s corresponds to a wavelength of 3.3

millimetres: with an aperture of the "aerial" of 2 centimetres a beam about 10° wide will be obtained. A model-maker can easily obtain an aperture of this size in one dimension by using a flat quartz plate (X-cut) in longitudinal vibration.

The pulse length is fixed by the carrier frequency. At least ten wavelengths should constitute a pulse train, and in general about 30 should be used. This means that a pulse train of 3 to 10 centimetres, with duration 0.1 to 0.3 milliseconds is desirable. The resolution in range which is obtainable is thus of the order of 5 to 15 centimetres and the band-width required in the receiver is from 3 to 10kc/s. For ease in model making, it may be noted that this band-width is that of a conventional receiver: if a broadcast receiver with a long-wave band is used the carrier frequency can be increased to 150kc/s, and the only modification required will be the provision of a modified detector circuit for pulse working.

The pulse repetition rate is fixed by the maximum range: a pulse must not be transmitted until the echo of the previous pulse from the most distant target has been received. If the range is chosen as 3 metres, a repetition rate of 50 pulses per second can be used. It will be found very convenient to choose either 50 pulses per second, or some other rate simply related to the mains frequency, as this reduces the need for smoothing the supplies to the various circuits;  $33 \frac{1}{3}$  pulses per second or  $65 \frac{2}{3}$  pulses per second can be used, for example. As we saw above, bats at rest transmit about 5 to 10 pulses per second and in flight up to 60 pulses per second. Thus at rest the bat is using a long range warning system, presumably to detect approaching enemies up to 15-30 metres away. In flight the bat is interested in much shorter ranges with more frequent measurement in order to avoid obstacles. It is interesting to note how closely the blind flying system of the bat ap-

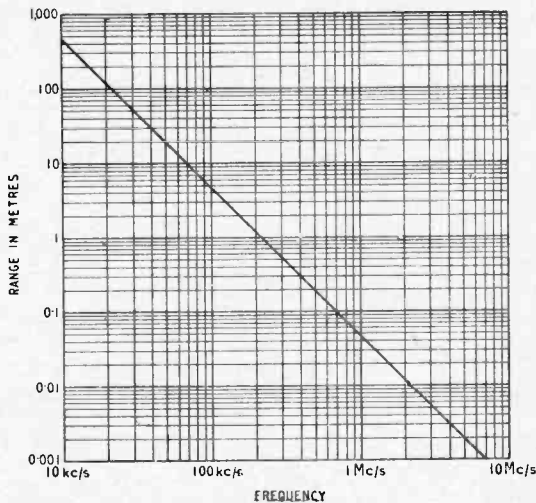


Fig. 1. Range of supersonic waves in air for a 10db fall in intensity. (Courtesy: Nature)

teristic of supersonic waves in air. In Fig. 1 the range for a fall in intensity of 10db is plotted against frequency. It will be seen that with a frequency of 100kc/s the range is four metres. A perfect reflector at this range would, therefore, produce an echo 20db down. At the lower frequency of 50kc/s used by bats the corresponding range is greater, about 12 metres on this 20db criterion.

The actual transmitted field strength is about 10-50 dynes/cm<sup>2</sup>, but there does not seem to be much information on the minimum size of object which can be detected. It seems that useful information could be obtained by jamming experiments, in which the room was filled with noise distributed throughout the 30-70kc/s band. With a noise field exceeding the pulse strength which the bat expects, the bat should find it impossible to detect objects in time to avoid them.

A frequency of 100kc/s corresponds to a wavelength of 3.3

<sup>4</sup> Nature Vol. 156 p. 693 (1945).



**Radar in Nature—**

proaches the system designed purely on the basis of the discussion above. Only the pulse length differs substantially, and this limitation does not affect flying, for the bat does not want to know anything about an obstacle which is too close to be avoided. The minimum range requirements are less stringent than with an A.I. system, in which the object is to come as nearly as possible into collision with the target.

A model radar system using supersonic waves in air was used for demonstration at the 1946 exhibition of the Physical Society. In this demonstration the signal frequency used appeared to be about 12kc/s, corresponding to a wavelength of about 3 cm. With the size of horn used the beam is rather wide. The resolving power in range appeared to be about 30 cm, which would mean pulses containing about ten cycles and lasting for about a millisecond. The peak power used in this demonstration is not known, but there is little difficulty in getting several hundred watts from a pair of push-pull KT8 valves. Powers of this order can most conveniently be used to drive magnetostriction radiators. It is thought that a much more successful demonstration would be produced by using higher frequencies as then the range limitation due to attenuation would prevent permanent echoes from the walls of the work-room, and the ranges could be laid out on a map to give a fair degree of verisimilitude.

It is equally possible to make a supersonic system working in water. Radar training devices have been produced on this basis, and "Asdic" is another well-known application. The velocity of propagation in water is 1,475 metres/second, so that the radar/Asdic scale ratio is 4 miles/1 inch. The range quoted for Asdic systems is 2,500 yards so that the pulse repetition rate for general search purposes can only be about one pulse every three seconds. The frequency used is not known, although references to "pinging" and attenuation considerations suggest that it is probably between 5kc/s and 10kc/s. This means that the wavelength in water will be about 14-28 centi-

metres, which would permit a range resolution of a few metres. For short range tracking repetition rates of more than one pulse in 3 seconds are probably used, as in this time the relative movements of two ships may be as much as 100 feet. Readers may be interested to know that even "Window" had an underwater equivalent. Just as metal foil strips provided artificial radar echoes, so "Pillenwerfer" produced artificial Asdic echoes. These devices were balls filled with chemicals which, like the familiar fruit salts, produced streams of bubbles. A stream of bubbles in water provides an impedance discontinuity which reflects the supersonic waves and thus provides an artificial echo.

These notes on the application of supersonic waves to range and distance measurement cannot, unfortunately, be completed by a description of a practical system which has been used for this purpose. They do, however, indicate to the keen experimenter a new field which he can explore without excessive apparatus costs. The signal frequency arrived at on

purely theoretical grounds is convenient in that a long-wave receiver can be used with very little modification. The cathode-ray oscillograph will probably already be available. The writer does not know whether an ordinary "tweeter" will give an adequate output at such high frequencies, but if so the only apparatus to be constructed is an unsymmetrical multivibrator keying a self-oscillator. From this stage the addition of a rotating head to link the supersonic beam to a P.P.I. and construction of models of all the main radar systems offers a very interesting field for home study: a field, moreover, which does not involve the possession of a transmitting licence. Extensions to the study of polar diagrams using scale models can also be made using the same equipment. One word of warning must be added. Multivibrators can be very unpleasant neighbours if they are lashed up to produce very square pulses. A neat layout, with some screening, and capacitances added to round the pulses will prevent the circuit acting as a general-purpose jammer.

## INDUSTRIAL ELECTRONICS

### B.T.-H. Exhibition

RECENT developments in industrial electronics was the theme of an exhibition by the British Thomson-Houston Co. held last month at Rugby, and the application of thyratrons to industrial control was a major part of the display. As an example of the control now possible with such valves, a pentode-type thyatron can control currents up to 33 A, the thyatron itself being controlled by a photo-electric cell with no intermediate amplification.

Voltage regulation is one of the most interesting applications of the thyatron. A pair of such valves, with one hard valve, is usually employed and regulations up to 0.25 per cent are obtainable. The alternator output is rectified and the D.C. is amplified by a hard valve, the output of which controls the grid bias of a pair of thyratrons. These are fed with A.C. in push-pull on both anode and grids, but the grid voltage is 90° out of phase with the anode. The striking voltages are controlled by the D.C. bias and the thyatron output thus depends on the bias. It is used for the field supply and hence controls the alternator output. Similar

principles are used in speed regulators, the control voltage being frequently derived from a tachometer.

Electronic timing circuits, ensuring that the amount of heat applied to the work is under exact control, are employed in the B.T.-H. radio heating equipment.

The Ignitron is a valve which effectively disposes of the idea still held by many that valve currents are small. Some Ignitrons pass peak currents of 10,000 A. They are steel-jacketed, and often water-cooled, with a mercury-pool type cathode and they are used for the control of A.C. power and for the conversion of A.C. to D.C. In this latter application six valves fed from a six-phase supply can provide an output of 900 A.

Magnetrons and klystrons form the major development at the other end of the scale—in centimetre-wave engineering. In conjunction with waveguide technique they have made modern radar possible and in the B.T.-H. marine radar equipment the aerial system is simply a slotted waveguide. Radiation takes place from slots across the wall of the guide and a beam angle of 1.5° is obtained. The display is in the form of a plan position indicator.

# ELECTROMAGNETIC FRAME SCANNING

## Time-base Amplifier

By W. T. COCKING,  
M.I.E.E.

THE characteristics of television line-scan amplifiers were recently dealt with\* and it might be thought that the frame-scan amplifier would differ only in minor matters brought about by the lower operating frequency. While it is true that the differences all arise through this difference of frequency, they are very far from being minor ones. In fact, they are so great that line-amplifier theory is of very little help and it is better to start quite afresh than to attempt to modify it.

The ampere-turns needed in the deflecting coil are approximately the same as in the case of the line scan, for although the frame deflection required is only 80 per cent. of the line, the deflecting coils themselves are necessarily shorter for the frame than for the line. The two effects roughly cancel. It is, therefore, reasonable to take as a first approximation a current of 0.6A p-p in a coil of 200 turns with an inductance of 3 mH. The actual coil can have any number of turns, but the product of turns and current will remain constant at 120 A-turns and the inductance will be, approximately, proportional to the square of the turns. Thus, if we use 2,800 turns, the current will become  $120/2,800 = 0.0428A = 42.8$  mA, and the inductance will be about  $3 \times (2,800/200)^2 = 588$  mH = 0.588 H, or say, 0.6 H.

The resistance, too, will vary as the square of the number of turns because, as the winding space is roughly constant, it is necessary to use finer wire when the turns are increased. Thus, if the 200-turn coil has a resistance of  $6.4\Omega$ , the coil of 2,800 turns will have a resistance of about 1,250  $\Omega$ .

The current through the coil is required to rise linearly with time for the 19 msec. devoted to the frame scan in the present transmissions and fly-back in 1 msec. If the current is 0.6A

in a 3 mH coil, the back e.m.f. on the scan is  $Ldi/dt = 3 \times 10^{-3} \times 0.6/0.019 = 0.095$  volt; the drop across the resistance is 0 to  $0.6 \times 6.4 = 3.84$  volts. With a 0.6 H coil and 43 mA, the figures become 1.35 volt and 0 to 53.8 volts, respectively. In both cases the inductive back e.m.f. is negligible in comparison with the drop across the resistance.

If the fly-back were linear the inductive back e.m.f. would be 19 times as great as on the scan. It will not be linear, however, and so will be greater still. Referring to Fig. 1, the conditions on the fly-back are as if the deflector coil, itself of inductance  $L_L$  and resistance  $R_L$ , were shunted by

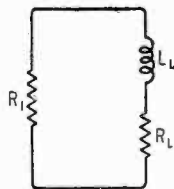


Fig. 1.

a resistance  $R_1$ , and the maximum current  $i_0$  were allowed to die away.

The current at any instant is then  $i = i_0 \Sigma^{-t/T}$  where  $T = LL / (R_L + R_1)$ . The total voltage across the deflector coil terminals is  $R_1 = i_0 R_1 \Sigma^{-t/T}$ . This is a maximum when  $t = 0$ , that is, at the start of the fly-back, and is simply  $i_0 R_1$ .

The fly-back is 99 per cent. complete when  $i = 0.01i_0$  and then  $t/T = 4.5$ . Therefore,  $R_1 = 4,500L_L - R_L$  in henrys and ohms. This is the minimum value of  $R_1$  permissible if the fly-back is to be 99 per cent complete in the nominal fly-back period.

For the 3 mH coil, we have  $R_1 = 4,500 \times 0.003 - 6.4 = 7.1\Omega$  and for the 0.6 H coil  $R_1 = 4,500 \times 0.6 - 1,250 = 1,450\Omega$ . These are minimum values of resistance for the required fly-back time, and with them the maximum back e.m.f. for the smaller coil is 4.26 volts and for the larger 62.3 volts.

It will thus be clear that the maximum voltage across even a high-inductance deflector coil is not sufficient to cause serious insulation difficulties. In the case of the line scan, the back e.m.f. reaches 1,000–2,000 volts, and a high-inductance coil is ruled out by the impossibility of providing adequate insulation. No such difficulty arises in the frame scan and a choice between the two must be made on other grounds.

The use of low-inductance deflector coils is desirable for two reasons; they reduce interaction between the line and frame deflection circuits and they are easier to wind. However, a transformer is necessary and its construction demands a large quantity of fine gauge wire which is not easy to obtain at the moment.

The usual transformer circuit

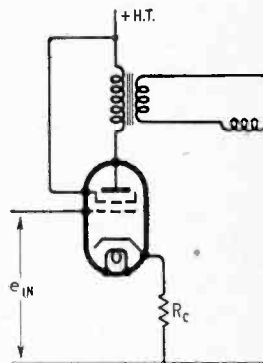


Fig. 2.

is shown in Fig. 2 and has the equivalent of Fig. 3 (a). This can be further reduced to Fig. 3 (b) in which  $R_1$  represents the total shunt damping of valve and transformer-core losses,  $r_p$  is the transformer-primary winding resistance and  $L_p$  the primary-inductance.  $R$  is the sum of the deflector coil resistance  $R_L$  and the secondary winding resistance  $r_s$  multiplied by the square of the transformer ratio ( $n$ ), and  $L = n^2L_L + 2L_p(1 - k)$  where  $k = M/\sqrt{L_pL_s}$  = coupling co-efficient. The circuit capacitances,

\*Electromagnetic Deflection, by W. T. Cocking, *Wireless World*, July, 1946.

so important in the line-scan case, can here be ignored. It is to be noted that  $k$  is taken as unity except where its difference from a nearly equal quantity is involved; the approximation  $2(1-k)$  instead of  $(1-k^2)/k^2$  is then used.

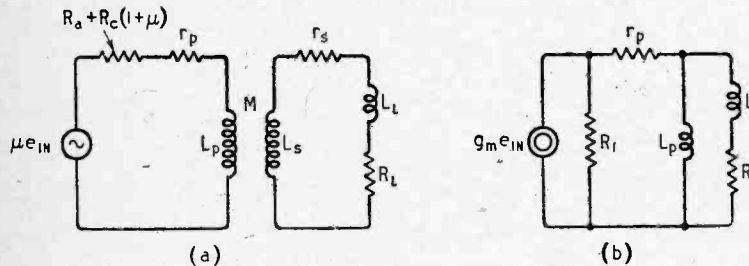


Fig. 3.

Taking a 3-mH deflector coil, if the transformer ratio is arbitrarily made 14:1, the primary current required becomes 43mA and, ignoring the leakage inductance for the moment,  $L$  becomes 0.6H. These are the same values as for the high inductance coil without a transformer. Ignoring  $r_p$ , temporarily,  $R = 1,250\Omega$ . Our aim is now to form a preliminary estimate of the primary inductance needed.

It is not difficult to show that during the scan the deflector-coil current is proportional to  $1 - \Sigma^{-1}R/(L + L_p)$  if the valve is linear. If 2 per cent distortion at the end of the scan is permissible, then at this time  $tR/(L + L_p) = 0.02$ . As  $t$  is 19 msec., we have  $L + L_p = 0.95R$  in henrys and ohms. With  $R = 1,250\Omega$ ,  $L + L_p = 1,185H$ .

This is a very large inductance and cannot be obtained in any reasonable size with negligible winding resistances;  $r_p$  is unlikely to be less than  $1k\Omega$  and  $r_p n^2$  about the same. The value of  $R$  will thus be around  $2.25k\Omega$  instead of  $1.25k\Omega$  and  $L_p$  will have to be further increased to 2,130H.

Taking into account the fact that the valve will need 30-40mA mean anode current, which flows through the transformer primary, the primary winding is likely to need some 20,000-40,000 turns with an iron core similar to that of a small mains transformer.

The leakage inductance then

becomes very important. Even if many interleaved primary and secondary sections are used it is unlikely that  $k$  can be made greater than 0.998. Taking this figure and with  $L_p = 2,000H$ , the leakage inductance is  $2 \times 2,000(1 - 0.998) = 8H$ . The

true value of  $L$  is thus 8.6H and the leakage inductance pulls more weight than the deflector coil.

Using the formula given earlier, the minimum shunt resistance for an adequate fly-back time is  $4,500 \times 8.6 - 2,250 = 36,500\Omega$ . Of this  $r_p$  will account for at least  $1,000\Omega$ , so that  $R_1$  of Fig. 3 (b) would be not less than  $35,500\Omega$ . As the current is 43mA, the peak voltage across the transformer primary is  $35,500 \times 0.043 = 1,530$  volts.

The voltage on the transformer, and valve, is thus of the same order as in the case of line-scanning and very high insulation is needed. This is particularly difficult in view of the large number of interleaved primary and secondary sections needed to secure tight coupling.

As an example of the fantastic voltages which can be reached, in theory at least, suppose that the coupling is 0.99—a value which is quite likely to be obtained if the primary and secondary are not interleaved. Then the leakage inductance is 40H, so  $L = 40.6H$ ;  $R_1 = 4,500 \times 40.6 - 2,250 = 180,000\Omega$ , and the peak voltage is  $180,000 \times 0.043 = 7,750$  volts.

Such a voltage is not likely to be reached in practice, because iron losses in the core and the valve A.C. resistance would prevent  $R_1$  from being made high enough. The practical effect of inadequate coupling would thus be to slow down the fly-back.

The question now arises as to what can be done to ease matters, for the requirements laid down lead to an impracticable design. The fly-back time can be increased slightly, and this will result in slight curvature of the scan at the top of the picture. In a small degree this is not important, but it must be kept small and then the situation is eased only slightly.

The second thing is to permit increased curvature towards the end of the scan, which will cramp the picture towards the bottom. Quite a bit can be done to correct for this by the natural curvature of the valve characteristic, so that much more distortion can be allowed than would otherwise be permissible.

Before proceeding further with a consideration of transformer coupling, however, it is as well to investigate the alternative of a high-inductance deflector coil with a resistance-capacitance feed. Choke-capacitance feed is ruled out because the choke would have to be of as large an inductance as a transformer. The circuit is shown in Fig. 4, and its equivalent in Fig. 5, in which  $R$  represents  $R_1$  in parallel with the output resistance of the valve  $[= R_a + R_c(1 + \mu)]$ .

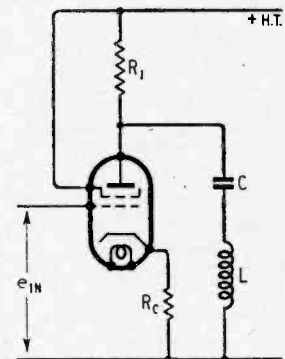


Fig. 4.

On the fly-back  $C$  has a negligible effect, and the circuit is essentially the same as that of Fig. 1 with  $R$  written for  $R_1$ . We found earlier for this that with  $L_L = 0.6H$ ,  $R_L = 1.25k\Omega$  and a current of 43mA, the value of  $R$  should not be less than  $1.45k\Omega$  for a fly-back time of 1 msec. This can easily be achieved with a pentode valve.

On the scan the deflection current is proportional to  $1 - e^{-t/T}$  where  $T = C(R + R_L)$ . For 2 per cent distortion at 19 msec.  $t/T = 0.02$ ; therefore,  $C(R + R_L) = 50t = 0.95$  in farads and ohms. If  $R = 2k\Omega$  and  $R_L = 1.25k\Omega$ ,  $C = 0.95/3,250 = 0.000292F = 292\mu F$ . This is inconveniently large, for in a 500-volt rating the component would be both

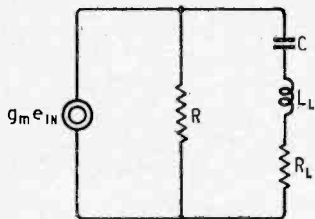


Fig. 5.

expensive and bulky. The working voltage on the valve will, of course, be well below 500V, but this rating is desirable to allow for the voltage rise when switching on.

By permitting more distortion the capacitance can be reduced just as in the case of transformer coupling. Thus, if 6 per cent distortion is allowed it can be brought down to  $100\mu F$ . It can be further reduced by increasing  $R$ , for it is the product  $C(R + R_L)$  which is important, not the individual values.

As  $R$  consists of the coupling resistance  $R_1$  in shunt with the output resistance of the valve, and as the only limitation to the maximum value of  $R_1$  is set by the loss of anode voltage in it, it is clearly desirable to make the valve resistance as high as possible. The use of a pentode valve is thus indicated in preference to a triode, which would be permissible on the score of fly-back time. With a pentode and any reasonable value of  $R_1$ , the output resistance of the valve is high enough to be ignored, and to all intents and purposes  $R = R_1$ .

The limit to  $R_1$  is set by the minimum permissible anode voltage of the valve, and with a positive-going saw-tooth input this occurs at the end of the scan when the anode current is a maximum. Ignoring the inductive back e.m.f., and assuming that the change of voltage across  $C$  is negligibly small during the scan, the change of

anode voltage  $\Delta E_a$  on the scan is  $\Delta i R_L$ , where  $\Delta i$  is the peak-to-peak coil current. In this instance it is  $0.043 \times 1,250 = 53.8$ , or say 54 volts.

The saw-tooth anode current is 
$$\Delta i_a = \Delta E_a \frac{R_1 R_L}{R_1 + R_L} = \Delta i (1 + R_L/R_1)$$
 so that in effect  $R_1$  robs the coil of current and the valve must provide a greater output. It is again advantageous to make  $R_1$  as large as possible compared with  $R_L$ .

If we call the mean anode voltage  $E_a$  and the current  $i_a$ , the minimum anode potential is  $E_a - \Delta E_a/2$  and with a pentode this should not be less than about 100 volts in most cases. With some valves it can be a little lower, but this is a reasonably safe figure. Therefore, the mean anode voltage must not be less than  $E_a = 100 + \Delta E_a/2 = 127$  volts in our example.

Now this voltage is also  $E_{HT} - i_a R_1$ , so that it is necessary to determine  $i_a$ . There is a minimum permissible anode current  $i_{min} = i_a - \Delta i_a/2$  which is necessary for reasonable linearity. This varies with different valves, but one is not far out in taking it around 15mA.

These factors are expressed in Eqns. (1) to (5) in the Appendix, and lead to Eqns. (6) and (7) for the values of  $R_1$  and  $i_a$ . If we have  $E_{HT} = 350V$ ,  $E_{amin} = 100V$ ,  $i_{amin} = 15mA$ ,  $\Delta i = 43mA$ ,  $R_L = 1.25k\Omega$ , we find  $R_1 = 5.35k\Omega$  and  $i_a = 41.5mA$ . Then  $R_L + R_1 = 6.6k\Omega$  and  $C = 144\mu F$ .

In the foregoing it has been assumed that the valve characteristic is linear. In practice, it will not be unless an uneconomically large valve is used. If the input saw-tooth wave is positive-going on the scan the curvature at the start of the scan is in the right direction to compensate for the curvature introduced by  $C$ . Valve curvature towards the end of the scan, however, can be in the opposite direction, and so may accentuate the non-linearity of the scan. This can be avoided by the use of an adequate H.T. voltage, but even then the curvature at this point may not be sufficient to correct the circuit distortion.

From all this it is clear that it

is necessary to make use of valve curvature in order to obtain an economical time-base. An attempt to design for linearity in each part by itself, while the ideal, is much too expensive for normal purposes. Adequate valve linearity demands a heavy anode current and a large amount of negative feedback. Adequate linearity in the coupling to the deflector coil demands either an impracticable transformer or an uneconomically large capacitance.

By letting the defects of one piece of apparatus offset those of another, a much more economical design is obtainable. Of course it is too much to expect exact compensation, but the distortion can be greatly reduced without difficulty, and a reasonable amount of negative feedback can be employed to clear up the residue.


It is of the first importance to note that for such compensation it is essential for the output valve to be fed with a positive-going saw-tooth wave. This is necessary in any case on the line scan for other reasons, but there is no obvious objection to the use of a negative-going input on the frame scan. However, with a negative-going input the valve distortion is in the same direction as the circuit distortion and the two accentuate each other. Only with a positive-going input are the valve and circuit distortions in opposition.

The estimation of the effect of valve and circuit together will be considered in detail in a further article.

APPENDIX

Units (mA, V,  $k\Omega$ )

- Let
- $i_a$  = mean anode current.
- $\Delta i_a$  = peak-to-peak saw-tooth anode current.
- $\Delta i$  = peak-to-peak saw-tooth coil current.
- $i_{amin}$  = minimum permissible instantaneous anode current.
- $E_a$  = mean anode voltage.
- $\Delta E_a$  = peak-to-peak saw-tooth anode voltage.
- $E_{amin}$  = minimum permissible instantaneous anode voltage.
- $E_{HT}$  = voltage of H.T. supply.
- Then  $\Delta i_a = \Delta i (1 + R_L/R_1)$  (1)
- $\Delta E_a = \Delta i R_L$  (2)
- $E_a = E_{amin} + \Delta E_a/2$  (3)
- $E_{HT} = E_a + i_a R_1$  (4)
- $i_a = i_{amin} + \Delta i_a/2$  (5)
- and  $R_1 = \frac{E_{HT} - E_{amin} - \Delta i R_L}{i_a - i_{amin} + \Delta i/2}$  (6)
- $i_a = i_{amin} + (1 + R_L/R_1) \Delta i/2$  (7)

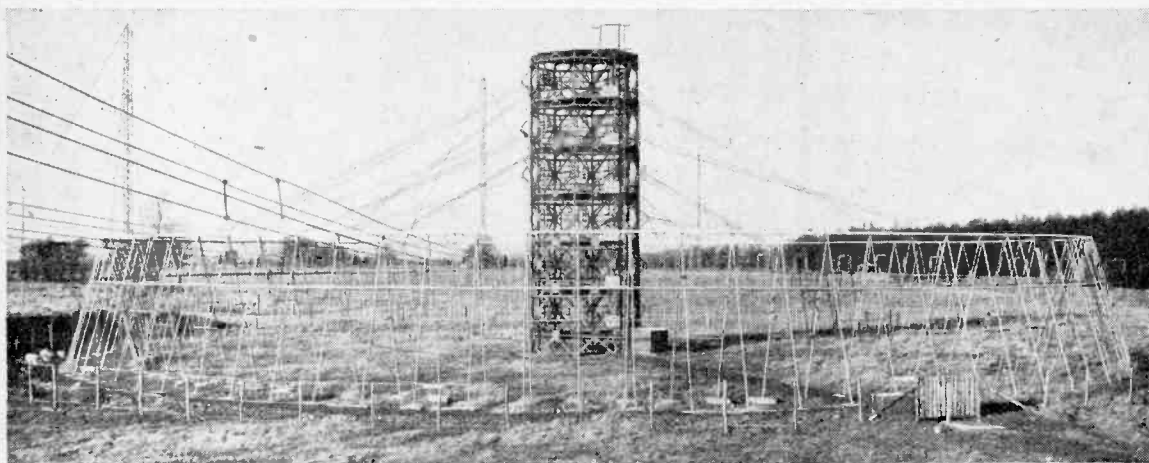

# SHORT-WAVE FORECASTING

## Using Ionosphere Charts for Choosing Frequencies

(Concluded from page 250, August issue)

By **T. W. BENNINGTON**  
(Engineering Division, B.B.C.)

**TABLE I**

Distance Factors by which F layer 2,500-mile contours or E layer 1,000-mile contours must be multiplied to obtain M.U.F. for shorter distances.

Distance : miles	Factor		
	For F <sub>1</sub> layer	For E layer	For F <sub>1</sub> layer
0	0.35	0.22	—
250	0.36	0.39	—
500	0.42	0.64	—
750	0.52	0.85	—
1,000	0.64	1.00	—
1,250	0.74	1.10	—
1,500	0.83	1.14	—
1,750	0.90	—	1.15
2,000	0.95	—	1.14
2,250	0.98	—	—
2,500	1.00	—	—

**C**HARTS prepared in the way described last month may be used to find the predicted average M.U.F.—and from this the Optimum Working Frequency, or O.W.F.—for a transmission path of any distance, in any part of the world, for every hour of day for the month for which they are valid.

If the transmission path is exactly 2,500 miles long, then the M.U.F. will be read off *directly* from the chart at the point at the centre of the path. If the path is less than 2,500 miles long then, as has been explained, the M.U.F. will be less than that indicated on the chart. It is only necessary in this case to read off the M.U.F. at the centre of the path and multiply it by a factor which is the ratio of the M.U.F. for 2,500 miles to that for the given distance. A set of such "Distance Factors" for various distances is given in the second column of Table I.

When the transmission path is *more* than 2,500 miles long the transmission will be by multiple hops, but the M.U.F. can still be read off *directly* from the chart. Experience has shown that beyond 2,500 miles the M.U.F. does not at first decrease, as might have been expected owing to the sudden decrease in the length of each hop,

and transmission cannot be considered as a simple extension of one-hop transmission to multiple hops. In multi-hop transmission there is considerable scattering at each reflection at ionosphere and earth, resulting in energy travelling by a multiplicity of paths, and, because of this and other effects, it is not possible to con-

Putting ionosphere theory into practice. Our title picture above shows the aerial switching tower and feeder terminating ring at the B.B.C.'s short-wave station at Skelton, near Carlisle, by means of which transmissions are fed to the previously selected aerial arrays. The output from six transmitters is handled by this tower and it is possible to connect each one to six arrays. With its twelve 100-kW transmitters Skelton is the world's largest short-wave broadcasting centre.

sider the conditions at certain separate ionospheric points as if transmission were by a "single ray" of radio energy. It has been found in practice, however, that if ionospheric conditions are considered at two points 1,250 miles (the distance of "half a hop") from each end of the path, good results are obtained. If the frequency used is such as will be reflected at both of these "control points," then the wave will, in general, be propagated by the ionosphere over the whole path.

**Finding the Working Frequency.**—The full procedure for the determination of the M.U.F.s and other relevant quantities for any transmission path is thus as follows: Using a Mercator map of the same size and co-ordinates as those used for the contour charts the location of the transmitting and receiving points is first marked off, and the great circle path between them is drawn in. If the path is 2,500 miles or less in length, the centre of the path is then marked off, whilst, if it is of greater distance than this, the two control points 1,250 miles from each end of the path are similarly indicated. By reference to the map of Fig. 3 (last month's issue) it is next ascertained in which zone the separate control



points lie. If, as in the case of paths 2,500 miles or less in length, there is only one control point, or if where there are two they both lie in the same zone, it is only necessary to make use of one contour chart, but if the control points lie in different zones, then the contour charts appropriate to both zones must be consulted.

We will deal with multi-hop circuits first. Using the appropriate chart, this is placed over the Mercator map so that the equators on each coincide, and the transparency is slid over the map until its 00 hours meridian coincides with the meridian on the map corresponding to the standard time in which it is desired to work. For instance, if it is desired to work in terms of G.M.T. we start operations with the 00 hours meridian coincident with the 0° longitude meridian on the map. Fig. 4 will help to make this clear. The 2,500-mile M.U.F. at each control point is then read off, and by sliding the transparent contour charts along so that each hour in turn coincides with the Greenwich meridian, this is done for every hour of the day, the M.U.F.s indicated being entered upon a Work Sheet like that shown in Table II, which is for a multi hop path with control points in two zones.

Having done this it is only necessary to strike out the *higher* of the two M.U.F.s appearing on the work sheet to be left with a

value which is the M.U.F. for the whole path.

It must be remembered that the contour charts are compiled from critical frequency measurements which are the *average* of those obtained on every day of the month, so that what the contours show is the average predicted 2,500-mile M.U.F. for the month. On some days the M.U.F. is likely to be considerably above this value and on others considerably below it. It is likely

like that of the B.B.C. where the aim is to provide regular service on every day, we cannot afford to work on a frequency which is likely to fail for a considerable portion of the total time. We must work somewhat below the average M.U.F., though it is always advisable to work as near it as possible, because of the fact that as we reduce the frequency ionospheric absorption increases, and with a given power radiated the field intensity at the receiv-

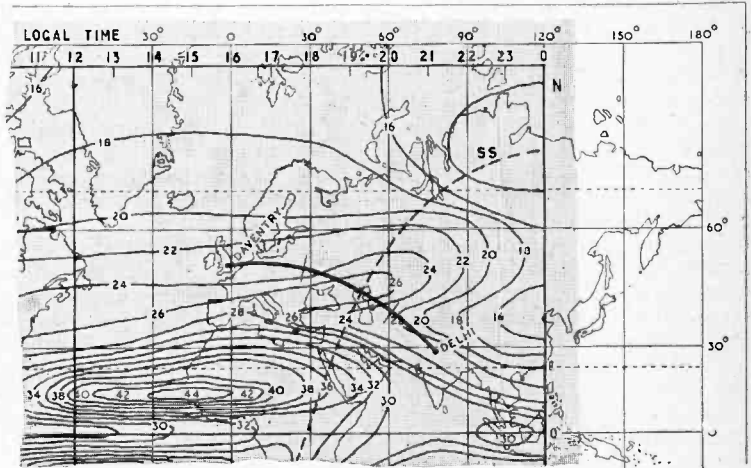


Fig. 4. Showing the method by which the M.U.F. is read off for every hour of day. The transparency is shown over the Great Circle path to Delhi at 16 hours G.M.T.

to be somewhat below it, in fact, on about half the days of the month, and in operating a service

ing end will tend to decrease.

The extent of the departure of day-to-day critical frequencies from the average for the month, both up and down, is known, and it has been found that, except during ionosphere disturbances, they do not often vary by more than about 15 per cent. So if we work on a frequency 15 per cent below the M.U.F. for the path we ought to be able to maintain regular service on all days except those on which ionosphere storms are in progress. The next step on the work sheet is therefore to find a figure 15 per cent below the M.U.F. for the path, and this is called the Optimum Working Frequency. Those whose interest lies in the exploitation of a particular frequency band rather than in the operation of a regular service would find that they can often work on frequencies well above the Optimum Working

TABLE II: PREDICTED WORKING FREQUENCY WORK SHEET  
 TO INDIA ..... d = 4,220 MILES ..... MAY, 1946  
 DELHI ..... FREQUENCIES IN MEGACYCLES

G.M.T.		00	02	04	06	08	10	12	14	16	18	20	22
FIRST CONTROL POINT I CHART	F <sub>1</sub> , F <sub>2</sub> 2,500 M.U.F.	14.4	14.0	17.4	20.5	22.3	23.0	25.2	25.6	23.8	25.8	22.0	15.8
FIRST CONTROL POINT E CHART	F <sub>1</sub> , F <sub>2</sub> 2,500 M.U.F.	15.8	20.0	22.2	25.5	27.0	27.7	29.0	26.2	23.3	19.6	20.2	17.4
K =		14.4	14.0	17.4	20.5	22.3	23.0	23.2	23.6	23.3	19.6	20.2	15.8
F <sub>1</sub> , F <sub>2</sub> M.U.F. FOR PATH													
F <sub>1</sub> , F <sub>2</sub> O.W.F.	-15%	12.5	11.9	14.8	17.5	19.0	19.6	19.8	20.0	19.8	16.7	17.2	13.5
E 1,000 M.U.F.													
K =													
E, F <sub>1</sub> M.U.F. FOR PATH													
M.U.F. FOR PATH		14.4	14.0	17.4	20.5	22.3	23.0	23.2	23.6	23.3	19.6	20.2	15.8
O.W.F. FOR PATH		12.5	11.9	14.8	17.5	19.0	19.6	19.8	20.0	19.8	16.7	17.2	13.5

K = DISTANCE FACTOR

Frequency or even well above the M.U.F. They would, in fact, often obtain best results by working on such frequencies, but that is a different matter from the operation of a regular broadcasting service, where no immediate reports from the receiving end are available.

**Circuit Curves.**—It is now advantageous to plot the data from the Work Sheet in the form of curves, as is done in Fig. 5. We are now in a position to choose our actual working frequencies for every time of day and these will depend upon the allocations made for the particular services in which we are interested; i.e., the highest frequency band, not above the O.W.F. at the various times of day, which we may have available. Fig. 5 shows (in horizontal full lines) the actual working frequencies inserted into the curves in terms of the broadcast bands, while the vertical lines connecting them indicate the times when a frequency shift is necessary. Of course, it does not follow that one would necessarily change frequency at all the times indicated, particularly in a broadcast service, in which continuity of transmission on a single frequency for as long as possible is a desirable feature. Nevertheless, such curves show at a glance the frequencies which should be used at any time of day, and, in general, the transmission schedules will be compiled in conformity with them. Thus, having available, some three months in advance, curves like this for every circuit over which it is desired to transmit, one is able to plan the transmitting schedules with some facility.

**Single Hop Circuits.**—Now let us return to the case of the single-hop circuit; i.e., one of 2,500 miles or less in length, such as we meet in the B.B.C. European services. As has been said, the 2,500-mile M.U.F. is read off at the centre point of the path. This is then multiplied by the Distance Factor from the second column of Table I appropriate to the length of the circuit and the result is the M.U.F. for the path. The O.W.F. is obtained in the same way as for multi-hop paths, and this completes the operation for most circuits and times of day.

There is however, a further complication in certain cases. Because the  $F_1$  and E layers are lower than the  $F_2$ , they are capable, at certain times of day when their ionisation is highest and yet lower than that of the  $F_2$ , of controlling the transmission at certain distances. What this means is that at these times the M.U.F. for certain distances is determined by the critical frequency of the lower layer and not by that of the  $F_2$ , and any frequency which penetrates the E (or  $F_1$ ) at the particular angles necessary to cover these distances will also penetrate the  $F_2$ . Thus the E layer can, during the summer day, act as the controlling layer for distances out to about 1,400 miles, whilst the  $F_1$  layer can do the same thing up to about 2,000 miles.

It will be noticed that on the chart of Fig. 2 there are plotted (in dotted lines) contours of E layer M.U.F. for a distance of 1,000 miles. These are calculated from the measured values of E layer critical frequency obtained from the observatories, these being multiplied by the E M.U.F. factor for 1,000 miles, and contours drawn in a manner similar to that already described for the F M.U.F. contours. It may be

noted about the E layer that, unlike the F, it is always more or less symmetrical (in its ionisation) about local noon, and that the highest values of ionisation always exist over the sub-solar point. Thus the contours move north and south as the seasons progress in accordance with the relative movement of earth and sun. It may also be of interest that the E layer is always at the same height and so the M.U.F. factors for any distance remain constant for all times of day and seasons, and that it is only, in any case, of any significance in short-wave communication during daylight.

In order to take account of these effects it is necessary during the daylight hours and for distances up to 2,000 miles, to read off the E layer 1,000-mile M.U.F. as well as the 2,500-mile  $F_2$  M.U.F. When the former is multiplied by the E layer distance factor appropriate to the distance (Table I) the result is the E layer M.U.F. for that distance. This is entered on the Work Sheet, and whenever it exceeds the F layer M.U.F. for the path it is the controlling M.U.F. Fig. 6 shows a curve for a distance of approximately 1,100 miles during June, and the

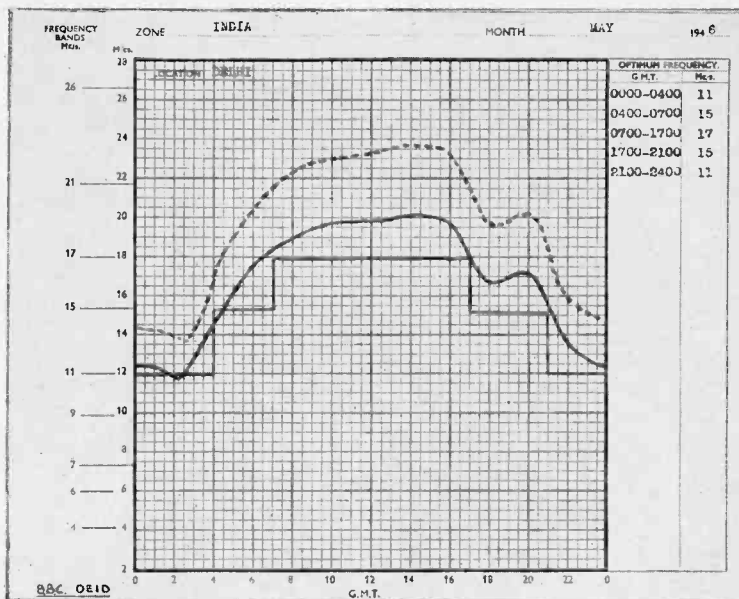


Fig. 5. Curves of frequencies for a specific route. Dotted line shows M.U.F. for path, while the full lines refer to O.W.F.; broadcasting bands are shown.

hump in the centre of the day shows the effect of the E. It is seen that because of this effect higher frequencies may be used

E layer; i.e., if the M.U.F. so found for the  $F_1$  is higher than that for the  $F_2$  then the former is the controlling M.U.F., and as

where this low limiting frequency may exceed the O.W.F. for several hours a day; i.e., the circuit may become unworkable. The low limit frequency, however, unlike the high limit, does not depend on the ionosphere alone, but varies also with the power radiated, the noise level at the receiver, the type of service and other factors. The technique has, however, been so developed that this low limiting frequency may also be calculated with the aid of contour charts, and inserted into the circuit curves, but the principles underlying this operation are too complex to deal with here.

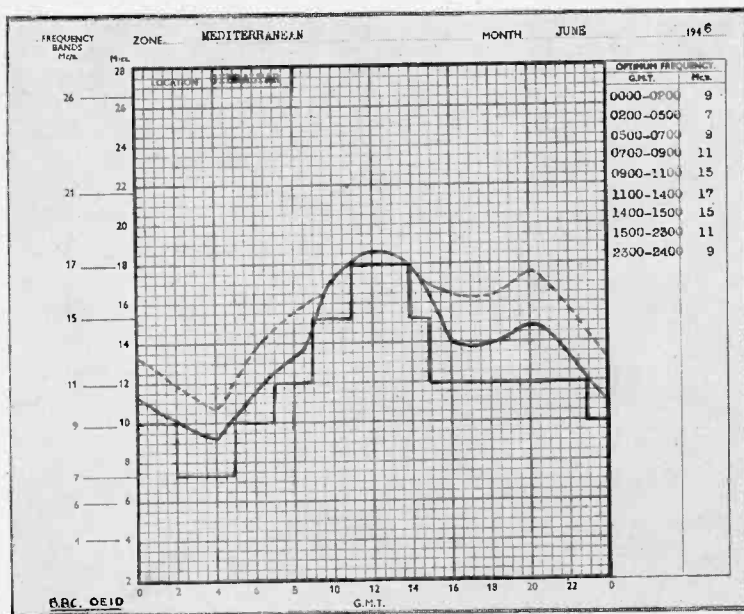


Fig. 6. Frequency curves for a relatively short route.

for this distance at that time of day than would otherwise have been possible. Incidentally it has been found that the E layer ionisation varies so little from day to day that it is not necessary to take any account of the departure of the M.U.F. from the average for the month; i.e., one may with reasonable safety work right up to the M.U.F. for the path on all days of the month.

For distances between 1,400 and 2,000 miles it is the  $F_1$  layer which sometimes controls the M.U.F. and since the  $F_1$  ionisation, although somewhat higher than that of the E, follows that of the E layer in the nature of its variations, it has been found convenient to avoid plotting the  $F_1$  M.U.F. contours on the charts, but rather to obtain the M.U.F. from the contours of E M.U.F. For the distances 1,400-2,000 miles (the only cases where it applies) it is therefore only necessary to multiply the E layer 1,000-mile M.U.F. by the  $F_1$  distance factor (Table I) in order to obtain the  $F_1$  M.U.F. for the path. This is applied in the same way as was described for the

such is plotted into the curve.

This, then, is the modern technique in which, by the use of world-wide M.U.F. contour charts, the scientific data is put to use in practical engineering. There are two other features which may be mentioned — though not discussed in detail. The first is that, particularly during the months of May, June, July and August, the M.U.F. for single-hop transmission may sometimes be higher than those found because of the presence of sporadic E. This, however, is not predictable. It appears and disappears at random and during most months of the year is not present often enough to be of significance. During the months just mentioned, however, it is much more prevalent; so much so that it does become a tangible factor in transmission over 1-hop circuits.

The second point is that, although it is a good principle always to work as near to the O.W.F. as possible, it is useful also to know the lowest frequency on which it is possible to obtain communication. Particularly is this so on long multi-hop circuits

## AMATEURS' EXAMINATION

IN view of the number of applications for amateur transmitting licences it has been decided by the City and Guilds of London Institute to hold an additional Radio Amateurs' Examination this year on November 15th from 7-10 p.m.

It will be held at a number of centres throughout the country, and intending candidates are asked to apply to their local technical colleges. The Institute's examination fee is 10s, in addition to which a small accommodation charge may be made by the examination centres. The closing date for applications is October 8th.

It is intended that in future the examination will be held annually in May.

Prospective candidates will be interested in the following questions set at the first examination, when 145 of the 182 entrants passed.

1. A 100-ohm resistor and a 300-ohm resistor are joined in parallel and connected to a battery of e.m.f. 7.5 volts and negligible internal resistance—

(a) What is the total current taken from the battery?

(b) What power is dissipated in the 100-ohm resistor?

2. What do you understand by the term "resonance"? If an inductance of 100  $\mu$ H is connected in parallel with a capacitance of 100  $\mu$ F, what is the resonant frequency of the circuit?

3. Draw a diagram of a self-oscillating valve circuit and explain simply its method of functioning.

4. Why are quartz crystals frequently used in radio transmitters? Describe, with diagram, a typical crystal-controlled oscillator.

5. Explain why "standing waves" are undesirable in a feeder system connecting a transmitter to an aerial. How would you detect their presence and minimize them?

6. Describe an "artificial aerial." How can an "artificial aerial" be used to measure the power output of a transmitter?

7. In what ways may a low-power transmitter interfere with radio and television reception? What precautions should be taken to minimize such interference?

8. What are the conditions laid down by the Postmaster-General for the frequency measurement and control of amateur transmissions?

# World of Wireless

## SERVICING EXAMINATION

**A**RRANGEMENTS have now been made for the first of the joint servicing examinations to be held since the merger of the examinations previously held by the Radio Trade's Examination Board and the City and Guilds of London Institute. It will be on May 17th.

It will be known as the Radio Servicing Certificate Examination, the practical tests for which will be conducted under the auspices of the Radio Trade's Examination Board whilst the written examination will be conducted by the City and Guilds.

Applications to sit for the examination should be made to the Secretary, R.T.E.B., 9, Bedford Square, London, W.C.1.

## PORTABLE LICENCES

**T**HE Postmaster-General has announced that he will now issue permits for licensed amateurs to operate portable transmitters for an additional fee of 10s.

This permit will allow a transmitter to be operated within a radius of 10 miles of the permanent address of the licensed amateur or, alternatively, within a similar radius of a given point if different from the operator's address.

As in the past, amateurs will suffix their call sign with "/P." The maximum permissible power is 25 watts on all present bands, with the exception of 1.8-2.0 Mc/s on which 10 watts is the limit. Applications should be made to the Engineer-in-Chief, Radio Branch, W5/5, G.P.O., London, E.C.1.

## FACSIMILE

**T**HERE has been a tremendous growth in the interest in facsimile transmission and reception in the U.S.A., especially among newspaper proprietors. Apparatus has been installed in some 100 public buildings in New York and a small four-column facsimile newspaper, called *Air Express*, is being produced twice a day.

The apparatus, which has been installed by Finch Telecommunications, Inc., is similar to that illustrated on this page. At a recent demonstration a four-page paper, each page measuring  $8\frac{1}{2} \times 11$  in., took eight minutes to produce—that is, at a speed of approximately 44 sq in a minute. This means that it takes one minute to reproduce 550 words of 8pt type—the size in which this paragraph is set.

The transmissions were radiated

by the recently completed F.M.-facsimile station, WGHF, New York, operating on 99.7 Mc/s.

Another New York demonstration, arranged by Radio Inventions, Inc., a research organization sponsored by some 20 newspapers and broadcasting stations, showed a facsimile attachment which can be connected to an ordinary F.M. receiver. During the demonstration printed



The Finch facsimile receiving unit which reproduces pages a little larger than those of *Wireless World* at the rate of thirty an hour.

pages measuring  $9\frac{1}{2} \times 12$  in were reproduced, complete with illustrations, at a rate of 16 an hour.

The F.M. station used for this transmission was WBAM, New York, working on 96.5 Mc/s.

## SLOW MORSE PRACTICE

**R**EADERS who, from time to time, have asked for details of slow morse transmissions for practice reception, will be glad to hear that the Radio Society of Great Britain has now organized a regular service of transmissions.

The stations participating in the service and the frequencies (kc/s) on which they operate are: G2CPF (Yorks), 1,892; G2BJY (Staffs), 1,930; G3JK (Notts), 1,865; G3LP (Glos), 1,865; G5UM (Herts), 1,900; G6GD (Ches), 1,885; GW3GL (N. Wales), 1,965.

The operating schedule (B.S.T.), which has been arranged by D. Rock, G8PR, "Sandhurst," Vicarage Road, Amblecote, Stourbridge, Worcs, to whom further offers of help from licensed amateurs should be sent, is:—

Sundays, 0900, G3LP, G3JK.  
1030, G5UM.  
1130, GW3GL.

Mondays, 2130, G2CPF, G2BJY, G6GD.  
Wednesdays, 2130, G2CPF, G3LP, G6GD, GW3GL.  
Saturdays, 2130, G2BJY, G6GD.

## MEASURING INTERFERENCE

**W**E referred in our June issue to the fact that the G.P.O. was adapting a number of Army interception receivers, Type R206, for the measurement of radio interference and that these would be made available to manufacturers of electrical equipment through the British Standards Institution.

The B.S.I. has notified us that a limited number of these modified receivers will be available early next year and will cost about £350 each. Manufacturers who are in a position to undertake the modification will be able to purchase sets at £250.

Applications for sets should be addressed to the Director, B.S.I., 28, Victoria Street, London, S.W.1, quoting reference OC/1/3.

## FULLY AUTOMATIC RADIOPHONES

**A**CCORDING to a correspondent, the Bell Telephone Laboratories, U.S.A., have recently patented a V.H.F. radio-telephone communication system in which the operation of dialling calls the distant station and, at the same time, causes the transmitting aerial to orient itself in the desired direction. The system is particularly adapted to inter-communication between a small group of islands or in other circumstances where metallic links would be uneconomic.

## DECCA CHAIN

**T**HE first chain of Decca Navigator Stations, cited in the South of England, was officially declared operational by the Admiralty and Ministry of Transport on July 18th, following a test period of transmission. The Master Station is at Buntingford, Herts, the "Red" slave station at Stokeholy Cross, near Norwich, and the "Green" slave station at East Hoathley, near Lewes, Sussex. A third slave (Purple) will be at Wormleighton, Warwickshire.

## HIGH-POWERED P.A.

**P**HILIPS have introduced a high-power A.F. amplifier with a maximum output of 1,000 watts; the characteristic is flat within better than 1db from 50 to 10,000 c/s; total harmonic content at 1,000 c/s is 1 per cent. The "Philowatt," as it is called, is designed for very large P.A. installations or relay networks serving up to 6,000 subscribers. Automatic monitoring allows unattended operation of the amplifier. When no audio signal has been present in the output stage for 3 minutes, a test impulse is automatically applied to the input. If

this impulse fails to reach the output, an alarm signal is sounded, or, alternatively, a stand-by amplifier may be switched on.

### TELECOMMUNICATIONS RESEARCH

THE formation of a new company to promote telecommunications research in this country is announced by British Insulated Callender's Cables and the Automatic Telephone and Electric Co. (A.T.M.), the sponsoring companies.

Laboratories are being established at Taplow Court, near Maidenhead, which will be under the direction of Air Vice-Marshal O. G. Lywood, C.B., C.B.E., managing director. He recently retired from the R.A.F. after 33 years' service in the Signals Branch.

The chairman of the new company is P. V. Hunter, C.B.E., director and engineer-in-chief of B.I.-Callenders. Dr. T. Walmsley, C.B.E., formerly of the G.P.O., is a director and chief engineer. The other members of the Board are: Dr. J. L. Miller, chief engineer (equipment and telecommunications), B.I.-Callenders; A. F. Bennett, director and manager, A.T.M., and A. J. Leyland, director and chief engineer, A.T.M.

### PERSONALITIES

**Sir John Lennard-Jones**, K.B.E., D.Sc., F.R.S., who has been Director General of Scientific Research (Defence) in the Ministry of Supply, is returning to his post at Cambridge University, but will continue as Chief Scientific Adviser to the Ministry.

**Sir Clifford Paterson**, O.B.E., F.R.S., D.Sc., director of the G.E.C. Research Laboratories, has been elected a vice-president of the Royal Society of Arts.



**DR. T. WALMSLEY, C.B.E., Ph.D., B.Sc.**, director and chief engineer of the new telecommunications research organization announced above. He was staff-engineer in charge of the G.P.O. Wireless Broadcasting Branch until 1940, when he was seconded to the M.A.P.

**Air Vice-Marshal R. S. Aitken**, C.B., C.B.E., has been appointed to the Board of Radio and Television Trust, Ltd., as a full-time director. He was appointed chief signals officer, R.A.F. Fighter Command, in 1940, and the following year became Air Officer Commanding 60th Signals Radar Group.

**S. L. Capell**, vice-president and general manager of the Philco Corporation of Canada, has been elected president of the Radio Manufacturers' Association of Canada.

**Prof. G. W. O. Howe**, D.Sc., Technical Editor of our sister journal *Wireless Engineer*, is retiring from the James Watt Chair of Electrical Engineering at Glasgow University at the end of the present session. Old students and friends of Prof. Howe are invited to contribute to a presentation to be made to him, contributions for which should be sent to Dr. A. J. Small, Electrical Engineering Department, The University, Glasgow, W.2.

**R. G. Clark**, who until recently was head of the Research and Development Department of Philips Lamps, which he joined in 1928, has been appointed manager of the Engineering Departments of Ferguson Radio Corp., Ltd., Enfield, Middx. Mr. Clark was a member of the B.R.E.M.A. sub-committee responsible for the industry's Plan for European Broadcasting.

**J. M. Flemming**, who has been appointed chief development engineer of the Micanite and Insulators Co., was secretary of the U.K. Radio Materials Mission to the U.S. in 1944.

**H. MacDougall** has been appointed secretary of the Electronic Manufacturers' Association, the offices of which will temporarily remain at Vernon House, Sicilian Avenue, Bloomsbury Square, London, W.C.1. In the Association's rules the term electronic apparatus is defined as including "all apparatus depending for its functioning in whole or in part on the emission of a stream of electrons, including apparatus incorporating thermionic valves."

**A. Parsons**, until recently of the Overseas and Engineering Information Department, B.B.C., has rejoined the Radio Department of the Municipal College, Portsmouth.

**J. W. Ridgeway**, manager of the Radio Division of Edison Swan Electric Co., has been re-elected for his fifth term of office as chairman of the British Radio Valve Manufacturers' Association (B.V.A.). He has also been appointed vice-chairman of the Radio Industry Council. The new B.V.A. vice-chairman is **G. A. Marriott**, who preceded Mr. Ridgeway as chairman. He is a director of the Marconi-Osram Valve Company and manager of the Osram Valve Sales Department.

**G. R. Scott Farnie**, GW5FI, has been appointed to handle the section of E.M.I. which is to cater for the particular needs of the radio amateur.

**C. W. Goyder**, C.B.E., has relinquished his appointment as chief engineer of All-India Radio and is returning to this country. He went to India in 1936 as the first chief engineer (broadcasting) to be appointed by the Government to develop a broadcasting system in British India. This now

comprises 22 medium- and short-wave transmitters at nine broadcasting centres, with an engineering staff of some 300. Mr. Goyder, who was created a C.B.E. in the New Year Honours, will be remembered by many readers as the amateur who, in 1924, with his station G2SZ at Mill Hill School, was the first British amateur to obtain two-way communication between England and New Zealand.



**C. W. GOYDER, C.B.E.**, until recently chief engineer, All-India Radio.

### IN BRIEF

**Television Interference.**—Amateurs operating in the 14.1 to 14.3 Mc/s band have been warned by the R.S.G.B. that interference may be caused to television receivers if due care is not taken to suppress the third harmonic.

**No Radio Imports Yet.**—As in the case of the taken imports permitted from the U.S.A. and Canada, radio apparatus (except H.T. batteries) is not in the list of goods now allowed into this country from Belgium.

**Overseas Receiver Wanted.**—The superintendent of a leper colony in Africa asks for suggestions as to where a short-wave (10-50 m) broadcast receiver to operate entirely from a 6-volt accumulator can be obtained.

**Dry batteries** of not more than 6 volts are now exempt from Purchase Tax.

**Coming of Age.**—We offer our congratulations to the *R.S.G.B. Bulletin* which, with the publication of the July issue, attained its majority.

**B.R.E.M.A. Secretary.**—The British Radio Equipment Manufacturers' Association announces the appointment of **S. E. Allchurch**, O.B.E., as secretary.

**Singapore.**—Reception reports of transmissions from the Singapore broadcasting stations are welcomed by the Department of Broadcasting, Cathay Buildings, Singapore, Federated Malay States. Transmissions on 4.78 Mc/s are radiated from 1130-1630 B.S.T. and on 7.22 Mc/s from 0530-0730. A third transmitter works on 9.54 Mc/s.

**Radio SEAC**, the 100-kW station of the South-East Asia Command, which is now broadcasting in the 19-, 25- and 49-metre bands, welcomes reception reports, which should be sent to Radio



## World of Wireless—

Unit, S.E.A.C., 191, Turret Road, Colombo, Ceylon. The latest schedule gives transmission times (G.M.T.) as 0000-0245, 25.49 m; 0315-1145, 19.84 m; 1215-1700, 49.42 m.

**Amateurs' Examination Course.**—A course covering the syllabus of the City and Guilds Radio Amateurs' Examination has been arranged by the Brentford Evening Institute for the 1946-47 session. The fees for the course, which commences on September 23rd, are: students over 16 years of age 5s, under 16, 2s 6d. A prospectus is obtainable from the Chiswick Polytechnic, Bath Road, Bedford Park, London, W.4.

**F.M. Goes Ahead in U.S.**—According to our Washington, D.C., contemporary, *Broadcasting*, the number of constructional permits for F.M. stations granted by the F.C.C. totalled 102 at the middle of July. It is also stated that the number of applicants to whom formal permission has been granted to operate F.M. stations, although they have not yet received permission to erect stations, totals 349. In addition, some 380 applications are pending.

**Television Slow-down.**—As a result of a request made by the American Television Broadcasters' Association the Federal Communications Commission has deferred for six months—until January 1st, 1947—the introduction of the rule requiring television stations to broadcast a minimum of 2 hrs on any one day and not less than 28 hrs of programme service a week. A further indication of the television slow-down is provided by the withdrawal of some 80 applications for the erection of television transmitters.

**I.E.E. Council.**—The following members of the I.E.E. Radio Section have been elected to serve on the I.E.E. Council for the ensuing year:—V. Z. de Ferranti, M.C., president; Prof. E. B. Moullin, M.A., Sc.D., vice-president; and Dr. F. C. Williams, O.B.E., an ordinary member.

**I.E.E. Radio Section.**—The vacancies which will occur on the Radio Section Committee on September 30th have now been filled. Prof. Willis Jackson, D.Sc., D.Phil., recently appointed head of the Electrical Engineering Department of the Imperial College of Science, has been elected chairman; R. T. B. Wynn, assistant controller, B.B.C. Engineering Division, vice-chairman; and Dr. R. F. T. Jarvis, G.P.O. Research Station, B. N. MacLarty, O.B.E., B.B.C., Dr. E. C. S. Megaw, M.B.E., Admiralty Signal Establishment, Dr. R. L. Smith-Rose, N.P.L., and G. M. Wright, Marconi's, as ordinary members.

**Glasgow Exhibition.**—Enquiries regarding the exhibition of engineering components relating to electrical, scientific and marine instruments, to be held in the Kelvin Hall, Glasgow, from November 15th to 27th, should be addressed to D. M. Slorach, the honorary director, at 19, Ladysmith Avenue, Sheffield, 7.

**Southampton's Enterprise.**—An attendance of nearly 400 was recorded at the recent course of lectures and demonstrations on telecommunications and electronic navigation at the School

of Radiotelegraphy, University College, Southampton.

**Licence Figures** for the three months ended June 30th show an increase of 279,000. The total is 10,671,000.

## INDUSTRIAL NEWS

**Television School.**—Since the opening of the Television School by Pye, Ltd., last February, some 200 students have been trained. Those wishing to take the ten-day course should apply for particulars to the Service Manager, Pye, Ltd., Cambridge.

**Equipment** for high-quality reproduction of radio and gramophone is to be the main interest of the H. A. Hartley Co., 132, Hammersmith Road, London, W.6. A new loudspeaker with 9-inch diaphragm and Ticonal magnet is already available at £8 5s, and other items in preparation include radio tuner units, amplifiers and a pick-up.

**Rola Speaker** repairs will in future be undertaken by a newly formed company—Speaker Services, 50, Malden Road, Cheam, Surrey (tel.: FAIRlands 9531). The managing director, W. T. Maynard, has been works director of British Rola for 15 years.

**Philco Patents.**—Some 600 patents relating to radio, television and electric gramophones have been licensed by the Philco Corporation to the Radio Corporation of America. The corresponding patent rights in Great Britain are licensed to Airmec, Ltd., manufacturers of Philco sets, a subsidiary of Radio and Television Trust.

**Morgans at War** is the title of an excellently produced book telling the story of the Morgan Crucible Company's achievements at their Battersea, London, S.W.11, factory. Isotope charts show that, among other increases in production, the company's wartime output of resistors was seven times that of its pre-war figure.

**Frank Murphy of London, Ltd.**, incorporated in May, 1944, as a private company for the production of wood-



VINCENT Z. de FERRANTI, M.C. chairman and managing director of Ferranti Ltd., the new president of the Institution of Electrical Engineers. His father, the late Dr. S. Z. de Ferranti, was president in 1910 and 1911.

ware, was converted to a public company on June 6th, and the balance of the authorized capital, approximately £6,000, is now the subject of a public issue. A further public issue of shares will shortly be made to establish a factory to produce receivers which it is planned to retail at between £10 and £12, including purchase tax.

**R.S. Amplifiers** have moved to a new factory in Reynolds Road, Acton Lane, London, W.4. Tel.: CHISwick 1011.

## CLUBS

**Chatham.**—Meetings of the Medway Amateur Transmitters' Society are held every Monday at 7.30 at the Co-operative Employees' Welfare Club, 207, Luton Road, Chatham. The Club's transmitter will soon be operating, using the call G2FJA. Sec., S. J. Coombe, "Stanvic," Longhill Road, Chatham.

**Coventry.**—Members of the Coventry Amateur Radio Society are to visit the B.B.C. station at Daventry on September 14th. A revival of the pre-war transmitting and receiving contest in competition with the Midland Amateur Radio Society is planned for October. The new secretary is J. W. Swinerton, G2YS, 118, Moor Street, Coventry.

**Holloway.**—The Grafton Radio Society meets three times a week, on Monday, Thursday and Friday, at 7.30 at the Grafton L.C.C. School, Eburne Road, Holloway, London, N.7. Details of the current syllabus are obtainable from the Secretary, W. H. C. Jennings, 82, Craven Park Road, London, N.15.

**Oswestry.**—As a result of a meeting held on July 31st the Oswestry and District Radio Society has been formed. Details are obtainable from A. D. Narraway, "Lamorna," Pant, Nr. Oswestry, Salop.

**Reading.**—At a recent meeting of the Reading and District Radio Club, G6CU, formerly of Cocos Island, spoke of his activities on the island. The club, which has been in existence for just over two years, has a membership of 75 and meets at the Palmer Hall, West Street, Reading, at 6.30 on the last Saturday in the month and again fourteen days later. Hon. Secretary, P. J. Nash, 9, Holybrook Road, Reading.

**Romford.**—Meetings of the Romford and District Amateur Radio Society will in future be held in the Mawney Road Schools, Romford, each Monday at 8. Secretary, R. C. E. Beardow, G3FT, 3, Geneva Gardens, Whalebone Lane North, Chadwell Heath, Essex.

**South Shields.**—Meetings of the South Shields Amateur Radio Club are held every Friday at 7.0 in St. Paul's School Room, Westoe. Secretary, W. Dennell, 12, South Frederick Street, South Shields.

**Wolverhampton.**—Meetings of the Wolverhampton Amateur Radio Society will in future be held at 7.30 on the first Monday in each month in the canteen of Messrs. Baynell, Merridale Street, Wolverhampton. W. O. Sturmeay, G8KL, of 3, Broome Road, Wolverhampton, is the secretary.

# CONVENTIONS AND VIEWPOINTS

Where Readers and Writers Have to Take Care

I WONDER how many thousands of *Wireless World* readers had to do their bit towards winning the war by trying to stay awake while listening by the hour to this sort of thing—" . . . negative square wave cuts off  $V_{99}$ , charging  $C_{270}$  positive and making current flow through  $R_{1001}$  and  $R_{1002}$  in parallel, biasing  $V_{1000}$  positive. . . etc., etc." Does that bring it back at all? No? Then at least you must often have tried to follow some printed explanation of circuit action. In doing so did you ever feel in your inner heart that when a condenser was said to be charged it was really being discharged? Or that "positive" should have been "negative," or "parallel" should have been "series"? If you have never been confused in ways like this you must either be very clever or (forgive me) very inattentive; and just to make sure, will you please answer the following simple questions:

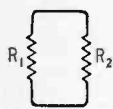


FIG. 1



FIG. 3

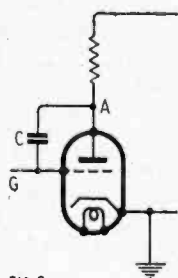


FIG. 2

In Fig. 1, are  $R_1$  and  $R_2$  in series or in parallel? When G in Fig. 2 is made positive, does it charge C or discharge it? If it charges C does it do so positively or negatively? An arrow alongside the resistor in Fig. 3, to show the direction of the voltage drop, should point downwards—true or false? In the "valve equivalent circuit" (Fig. 4) does the signal current  $i_a$  flow in the same direction as the signal voltage  $\mu v_g$  or in the opposite direction?

If you have given the right answers to all these I bow to your omniscience. The last question

By "CATHODE RAY"

was hotly debated for several months by Prof. G. W. O. Howe, D.Sc., M.I.E.E., K. R. Sturley, Ph.D., B.Sc., A.M.I.E.E., D. A. Bell, M.A., B.Sc., and D. H. Parnum, B.Sc., A.R.C.S., Ph.D., among others, in at least three different technical journals; while the easiest-looking of the lot (Fig. 3) was the subject of controversy in the inconceivably learned pages of *Wireless Engineer*. So perhaps I am not insulting readers by hinting at the possibility of their being confused, even in such elementary matters.

In fact, failure to crack off ready answers to these questions is no ground for shame or despondency. Quite the reverse. Whether or not it is true that there are two sides to every question, there are certainly two sides to these. There are so many sides to the Fig. 4 problem that it might almost be described as a polygon.

For there are quite a number of crossroads in electrical science where Nature does not give an indisputable lead, so the direction has to be settled by convention or general agreement. And where there is no general agreement, how is one to know which is right and which is wrong?

The direction of electric current is a good example. When the need first arose for specifying it, nobody had much of a clue to what an electric current was or how to tell which way it was flowing. So it was agreed to make a guess and say that in the external circuit of a cell the current flowed from copper to zinc. When electrons were discovered, this looked like a bad guess, because it was found that they flowed in the opposite direction to the supposed current. So long as only wire circuits were involved, it didn't matter a great deal. Electrons were only a theory, anyway. But when vacuum valves came into use, electrons could no longer be treated as a collective pheno-

menon in which direction was a mere matter of convention. They became real and individual. So a lot of people have reversed the original guess and now say current flows from "negative" to "positive" (two more conventional terms). The maximum confusion thereby exists. The revisionists contend that obviously everyone ought to change over, instead of clinging to what is now known to be wrong. To which the conservatives answer that an electric current *can* flow in the conventional direction, and does so in soft valves and electrolytes.

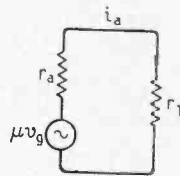


FIG. 4

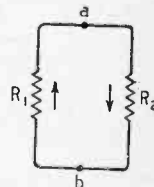


FIG. 5

So until an international authority succeeds in persuading everyone to do one thing or the other (and international authorities don't seem to be having much luck at this kind of thing just now) confusion can only be avoided if people take the trouble to say which convention they personally are using.

Fig. 3, for all its apparent simplicity, is a little more subtle. It was discussed on page 442 of the September 1945 *Wireless Engineer*, and has nothing to do with the current flow convention, being a question of e.m.f. and potential difference (p.d.). To me the answer seems to be bound up with the Fig. 1 question. Two circuit elements connected as shown there are in series and in parallel. Which is the more appropriate way to regard them depends mainly on what is not shown—the e.m.f. or e.m.f.s. If the source of e.m.f. is external, connected between the points a and b in Fig. 5, then with respect to this source  $R_1$  and  $R_2$  are in parallel. Any currents flowing must be downwards in both or upwards in both, and

### Conventions and Viewpoints—

arrows indicating their directions will also mark the direction of the e.m.f. driving them.

But suppose the sole source of e.m.f. is in  $R_1$  ( $R_1$  might be the resistance of a battery supplying the e.m.f.). Its direction, and that of the resulting current, is indicated by the upward arrow alongside.  $R_2$  is in series, and although the arrow beside it is pointing downwards it correctly indicates the direction of current, which is the same as in  $R_1$ , i.e., clockwise. But what about the voltage drop across  $R_2$ —the p.d.? Where should its arrow point?

The e.m.f. in  $R_1$  causes a p.d. between the points  $a$  and  $b$ , which according to the pre-electronic convention would be marked + and - respectively. It is impossible with any convention to have two different p.d.s between the same two points, so according to one school of thought it seems natural to make the p.d. arrow alongside  $R_2$  point upwards. To them it indicates the voltage drop across the resistance, which opposes the e.m.f.; just as when you push a heavy box across the floor by pressing against it your hand feels an equal pressure in the opposite direction. Others hold that voltage arrows ought to show the direction of the electric field every time. Again, either of two opposite customs can be intelligently adopted, but until everybody agrees to adopt the same there is the risk of confusion, not to say acrimony.

The uncertainty about charging and discharging in circuits such as Fig. 2 is one of those that arises when it is a matter of opinion whether to count voltages and currents that have to do with the feeding of valves, or to ignore them and reckon only the "signal" voltages and currents. When the voltage across the condenser never reverses, I think it is clearest to call it charging when that voltage increases, and discharging when it decreases. According to this,  $G$  going negative in Fig. 2 charges  $C$ , and *vice versa*. As for the polarity of charge, it all depends which side of the condenser is temporarily understood to be at zero potential. While  $G$  is going negative,  $A$  is going positive.

Sticking rigidly to this rule when the condenser voltage is periodically reversed by the signal may lead to very cumbersome explanations. Then it may be better to ignore incidental "base-

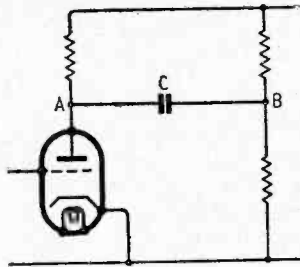


FIG. 6

line" potentials. For instance, in Fig. 6 suppose the effect of a recurring signal at the input to the valve is to make  $A$  alternately positive and negative with respect to  $B$ . A detailed description of this by the first method would involve one in a discharge and a charge in opposite polarity at each stroke of the signal. It is easier to forget the fixed positive potential of  $B$  and call each positive movement of  $A$  a charge, and *vice versa*.

The same question crops up in specifying potential changes.  $A$  in Fig. 2 is always positive, if it is understood that earth is zero. But one would generally say that making  $G$  positive drives  $A$  negative. The initial potential of  $A$  is understood for the time being to be zero. At least, it is understood by the more experienced, but I am sure it must be terribly muddling to the novice who has only learned the printed rules and not the unspoken traditions. Even the experienced would sometimes like to be told whether "negative" means really negative (with respect to earth) or just less positive. I find it helpful to call a signal "negative-going" rather than "negative" if one wants to indicate its direction rather than its relationship to earth.

There is another aspect of this relative potential business that I am sure learners must often find confusing, just because it may never occur to their instructors to point it out. They are told, for example, that a positive voltage is applied to  $a$  in Fig. 7.  $C$  is charged by it; so as  $a$  is its

positive terminal,  $b$  must be its negative terminal. But when  $R$  is considered,  $b$  is not negative; it is positive. Then are both terminals of  $C$  positive? Easy enough, you say. But if you are teaching somebody else, do make quite sure he is following the leaps and jumps of your potential "zero."

No, I am *not* going to answer Fig. 4. If you want some of the answers, you can turn up the following and sort it out for yourselves:

*Wireless World*: May 1945, p. 140; July 1945, p. 209; Aug. 1945, p. 252.

*Wireless Engineer*: June 1945, p. 261; Aug. 1945, p. 390; Nov. 1945, p. 532.

*Electronic Engineering*: Feb. 1946, p. 56.

All I will add is to drag in the series-parallel question by mentioning that Fig. 4, showing valve internal resistance and load resistance in series, is only the better-known of two alternative valve equivalent circuits. The other shows  $r_a$  and  $r_l$  in parallel with one another and with the e.m.f. Both equivalents work.

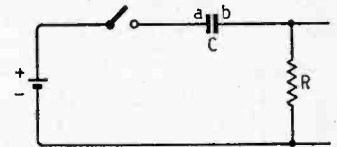


FIG. 7

Moral: Whether you are the explainer or the explainee, make quite sure that in matters of viewpoint or convention you are both on the same ground at the same time. Polarity, direction, positive and negative, charge and discharge, even series and parallel, are relative things; and if you don't take care about them the ambiguity bug will get you.

### MARINE NAVIGATION PRIZE

THE Royal Society of Arts is again offering a prize of £50 under the Thomas Gray Memorial Trust for "an invention, publication, diagram, etc., which . . . is considered to be an advancement in the science or practice of navigation proposed or invented between January 1st, 1941, and December 31st, 1946." Further details are obtainable from the Secretary, Royal Society of Arts, John Adam Street, London, W.C.2. Last year's prize was awarded to W. J. O'Brien for the Decca Navigator.

★ THE TREND OF MODERN ELECTRONICS ★

THE PINT VALVE

HALF-PINT GLASS

IN THE



**BRIMAR**


**BVA**

**VALVES**

*Bantam Range*

STANDARD TELEPHONES AND CABLES LIMITED, FOOTSCRAY, SIDCUP, KENT.

# Standard Cases for DELIVERY NOW

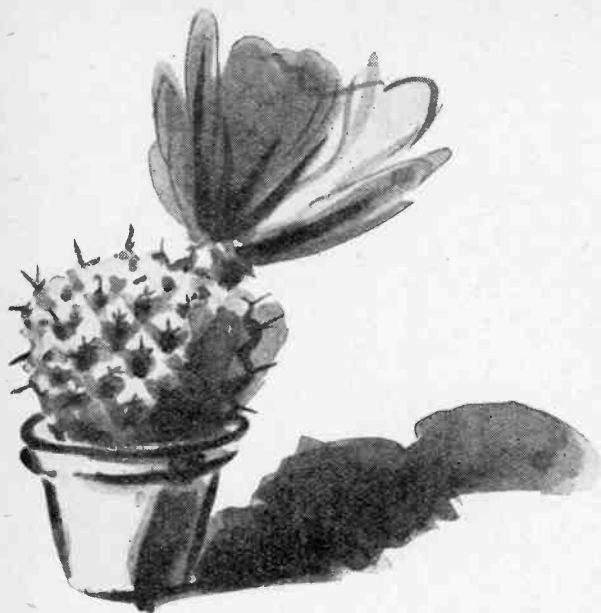

There's a moral in the  
ECHINOCACTUS NAPINUS CHILE . . .


. . . a moral in so far that if you don't know anything about cacti and start messing about with them you are liable to get stung rather badly.

Now apply the same thought to Transformers; some people want a few Transformers and think the order is not large enough to bother us with (nonsense of course, as you know, but some people do think that) so they knock a few up themselves from odds and ends that are lying about.

Of course, the so called Transformers are just not quite perfect and don't just do the job they should. The same thought applies also to very cheap quality Transformers which some people buy and attempt to use.

The moral is when buying Transformers - go to an expert and get the right article - it may cost you a little more but, in the long run, you are saving money.

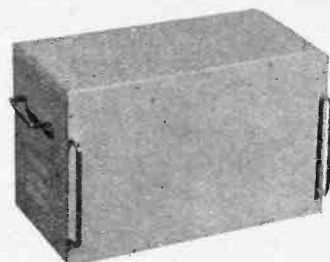PARMEKO of LEICESTER.  
Makers of Transformers.



Superbly finished model of highest quality heavy gauge sheet steel, strongly welded and complete with internal metal chassis. Finished in light grey, brown, yellow, red or black.

Type 1053A	15½" w. × 8" d. × 9" h.	£4 15 0
Type 1053B	17½" w. × 9" d. × 10½" h.	£6 15 0
Type 1053C	24" w. × 12" d. × 15" h.	£8 17 6

## IMHOF'S

112-116 NEW OXFORD ST. LONDON, W.C.1. Dept.

THERE ARE TRIX  
AMPLIFIERS FROM  
5-500 WATTS . . .

*Critical*  
users

Trust  
**TRIX**

*Quality SOUND Equipment*

THE TRIX ELECTRICAL CO. LTD.  
15 MAPLE PLACE - TOTTENHAM COURT ROAD,  
LONDON, W.1.  
MUSEUM 5817 *Branches at Colchester, TRUXADIO-WESDO-LONDON*



## Design Data (7)

# VIDEO AMPLIFIER H.F. RESPONSE

## 1.—Shunt-Corrector

**S**IMPLE resistance coupling is of little use when the high-frequency response of an amplifier extends into the megacycle region because of the shunting effect of the valve and circuit capacitances. In order to obtain a useful amplification from each stage, therefore, inductance is associated with the circuit in such a way that it tends to compensate the unwanted effects of the capacitance.

Of the many possible circuits the shunt-corrector, of which the circuit is shown in Fig. 1, is one of the most widely used. It has the great merit of combining good performance with simplicity. The procedure for determining the optimum circuit values is given below and followed by some examples.

### Assumptions

That the anode A.C. resistance of the valve is very large compared with  $R$ , and that the resistance of  $L$  is very small compared with its reactance at high frequencies, and small compared with  $R$  at low frequencies.

### Conditions

The formulae are derived for the condition of the flattest frequency response, curves A, and for critical damping, curves B.

### Procedure

Given the drop in response (db) required at a maximum frequency  $f$ , and the total circuit capacitance  $C$ , to find the other circuit values:—

(a) for the flattest frequency response

1. Determine  $fCR$  from curve A, Fig. 2.
2.  $R = (fCR)/fC$
3.  $A = g_m R$
4.  $L = 0.414CR^2$
5.  $C_1 = 0.352 C$

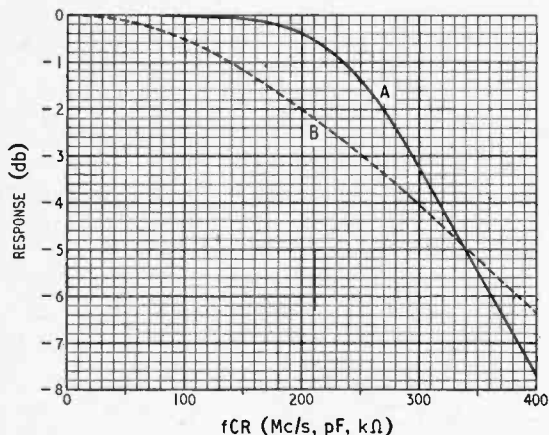


Fig. 2.

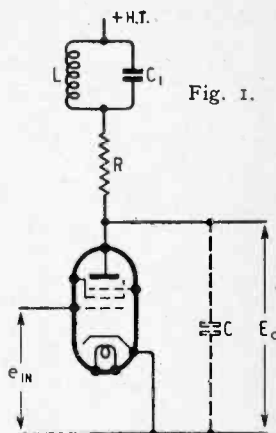


Fig. 1.

(b) for critical damping

1. Determine  $fCR$  from curve B, Fig. 2.
2.  $R = (fCR)/fC$
3.  $A = g_m R$
4.  $L = 0.296 CR^2$
5.  $C_1 = 0.125 C$

Alternatively, given the response required at a

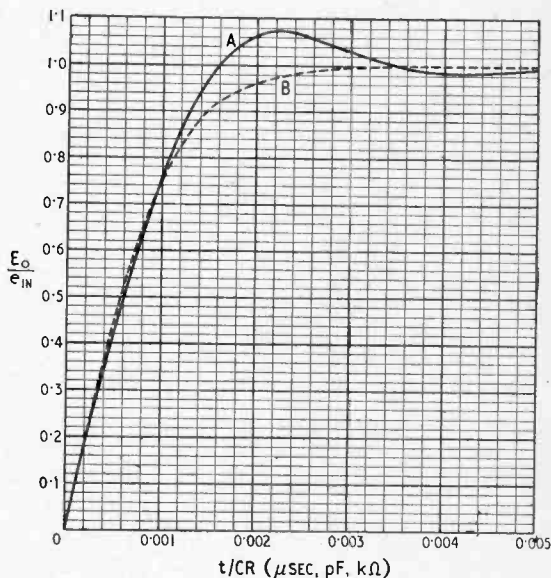


Fig. 3.

given time  $t$  after the onset of a pulse:—

(c) for the flattest frequency response

1. Determine  $t/CR$  from curve A, Fig. 3.
  2.  $R = (t/C)/(t/CR)$
- then proceed as in (a) 3, 4 and 5.

(d) for critical damping

1. Determine  $t/CR$  from curve B, Fig. 3.
  2.  $R = (t/C)/(t/CR)$
- then proceed as in (b) 3, 4 and 5.

## Design Data—

## Symbols

- $E_o$  = output voltage  
 $e_{in}$  = input voltage  
 $A = E_o/e_{in}$  = amplification  
 $g_m$  = mutual conductance of valve  
 $R$  = coupling resistance  
 $L$  = correction inductance  
 $C$  = total stray capacitance  
 $C_1$  = capacitance across  $L$   
 $f$  = maximum frequency required  
 $t$  = time

## Units

mA/V; k $\Omega$ ;  $\mu$ H; pF; Mc/s,  $\mu$ sec.

## Examples

Referring to Fig. 1,  $C$  represents the sum of the stray circuit capacitances and is the starting point of design. Its value must be measured or estimated and, in practice, it is rarely less than 25 pF, and may be 40—50 pF. The capacitance  $C_1$  bears a definite optimum relation to  $C$ ; in its smaller values the self-capacitance of  $L$  can provide it without an additional component.

The circuit relations are given for the alternative conditions of the flattest frequency response and for critical damping. The former leads to rather higher amplification but for pulse excitation there is some overshoot. The latter is free from overshoot.

As an example of the procedure, suppose that a response of -1 db at 3 Mc/s is required when the total capacitance is 40 pF and that the condition of flattest response is satisfactory. From curve A of Fig. 2  $fCR = 232$ , and hence  $R = 232/(40 \times 3) = 1.93$  k $\Omega$ . If the valve has  $g_m = 6$  mA/V,  $A = 11.6$ . Then  $L = 0.414 \times 40 \times 3.74 = 62$   $\mu$ H; and  $C_1 = 0.352 \times 40 = 14$  pF.

It will be noticed that  $R$ , and hence  $A$ , is inversely proportional to  $C$ , so that in the interests of maximum amplification it is important to keep the circuit capacitance as small as possible.

The transient response is indicated by Fig. 3, curve A showing  $E_o/e_{in}$  as a function of  $t/CR$ . This curve indicates the way in which the output voltage varies with time for an input step voltage, that is, a voltage which changes instantaneously from one value to the other.

It will be observed that the output oscillates slightly about its final value before settling down. This can be avoided by a different choice of circuit values, but only at the expense of amplification. For television purposes when only a single V.F. stage is usual this small degree of overshoot is usually permissible.

For oscilloscope amplifiers and for multi-stage television amplifiers it is often necessary to avoid overshoot. With critical damping different relations exist between the components and a different set of design equations is given. Curves B in Figs. 2 and 3 then apply.

As an example, taking the same values as before, but working from curve B of Fig. 2, we find  $fCR = 140$ , so  $R = 140/(3 \times 40) = 1.165$  k $\Omega$ . Then  $A = 7$ ;  $L = 0.296 \times 40 \times 1.36 = 16.1$   $\mu$ H; and  $C_1 = 5$  pF. There is thus a considerable loss of amplification as compared with the condition of flattest frequency response.

To illustrate the pulse performance of this last condition we have  $CR = 40 \times 1.165 = 46.5$ . We want to know how many microseconds after the application of a pulse the output reaches 90 per cent of its final value. Curve B of Fig. 3 gives this information;  $t/CR$  for  $E_o/e_{in} = 0.9$  is 0.00145, so that  $t = 0.00145 \times 46.5 = 0.0675$   $\mu$ sec.

For the example with the flattest frequency response we use curve A and find  $t/CR = 0.0013$ , while  $CR$  is

$40 \times 1.93 = 77.3$ , so that  $t = 0.0013 \times 77.3 = 0.101$   $\mu$ sec.


As another example, suppose that overshoot cannot be tolerated and that it is required that the pulse response be 90 per cent complete in 0.1  $\mu$ sec. Let the stray capacitance be 30 pF and the valve have a mutual conductance of 6 mA/V, what circuit values are needed?

From Fig. 3, curve B,  $t/CR = 0.00145$ , hence  $R = \frac{0.1}{0.00145} = 2.3$  k $\Omega$ ;  $A = 6 \times 2.3 = 13.8$ ;  $L = 0.296 \times 30 \times 5.3 = 47$   $\mu$ H;  $C_1 = 0.125 \times 30 = 3.75$  pF. If the condition of flattest response had been permissible, we should have used curve A and obtained  $t/CR = 0.0013$ , giving  $R = \frac{0.1}{0.0013} = 2.56$  k $\Omega$ ;  $A = 6 \times 2.56 = 15.4$ ;  $L = 0.414 \times 30 \times 6.6 = 82$   $\mu$ H;  $C_1 = 0.352 \times 30 = 10.55$  pF.
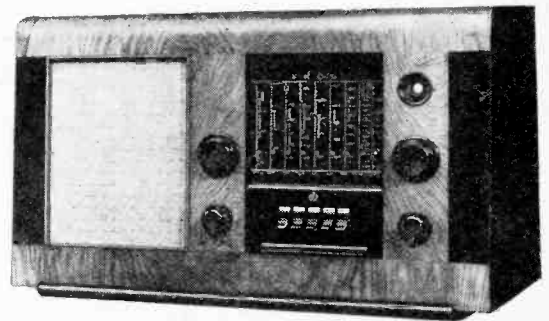
## NEW BROADCAST RECEIVERS

**B**ANDSPREAD tuning for television sound and the 13, 16, 19, 25, 31, 41 and 49 metre bands is provided in the Ekco Model A28 by a system of permeability tuning which is claimed to obviate microphony on the short waves. Station selector switches for three medium-wave and two long-wave programmes are additional to normal slow-motion drive tuning. The four-valve plus rectifier superhet circuit employs a pentode output valve with negative feedback and there is a "magic eye" tuning indicator. The price is £29 8s (purchase tax £6 6s 5d). In the Ekco Model A23 a similar circuit is employed with five station selection buttons, and television sound as well as short, medium and long wave ranges. The price of this receiver is £21 (purchase tax £4 10s 4d). The makers are E. K. Cole, Ltd., Southend-on-Sea.

The Model A4653, produced by Allander Industries, Milngavie, Glasgow, is a superhet (four valves plus rectifier) and is available in two forms: (1) for the home market; (2) for export. The home model uses British valves and has wavebands of 17-50, 185-565 and 820-2,300 metres, while the export model uses international octal, covers 185-565,




Bandspread tuning on seven short-wave bands and the television sound channels is provided in the Ekco Model A28.

33-100 and 12-37.8 metres, and is fitted with tropicalized components. The price of the home market receiver (Model A4653/1) is £15 15s, plus tax £3 7s 9d.

Three new domestic receivers are now in production by Masteradio, Ltd., 193, Rickmansworth Road, Watford. The Model D10 is a small table model for A.C./D.C. mains, housed in a moulded plastic cabinet with a choice of three colours. It covers short, medium and long waves and the price is £14 3s 6d, plus tax £3 3s. A similar chassis in a walnut cabinet (Model D10W) costs £15 4s 6d. A larger table model for A.C. mains in an acoustically designed two-colour plastic cabinet (Model D11) is priced at £18 7s 6d, plus tax £3 19s 4d. In each case the basic circuit is a four-valve superhet, plus rectifier.
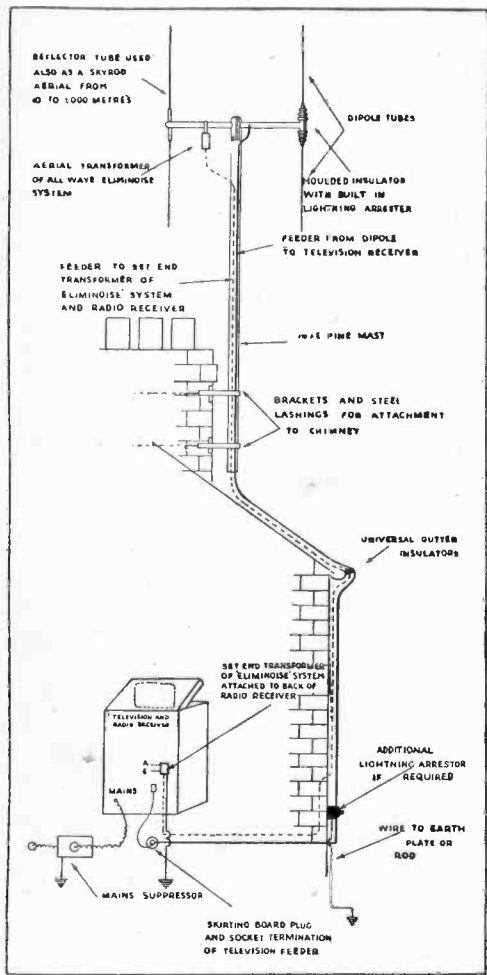
# BELLING-LEE QUIZ (No. 3)

A selection of answers to questions we are continually being asked by letter and telephone



Minimum length roft. depending on peculiarities of the site.

**Q.13.** Would a metal mast adversely affect the picture?

**A.13.** In practice no, provided it is earthed. The presence of a conductor in this position between the dipole and reflector is taken into account in the design and suitably allowed for. The disadvantage is a mechanical one. A metal pole of the above mentioned dimensions is necessarily heavy, costly and difficult to handle on sloping roofs, etc.

**Q.14.** Can a television aerial be used for broadcast reception?

**A.14.** Yes, in districts where there is little or no interference, many people have got into the bad habit of doing without an aerial and have never heard their sets at their best because they have always had to operate with the volume control unnecessarily full. When installing a television receiver a television aerial is almost essential, so when it is being erected an insulated lead should be taken\*3 from the metal cross arm to the broadcast receiver. This lead need not be disconnected when receiving television—it exercises a negligible effect.

**Q.15.** Can a television aerial be used as an anti-interference aerial?

**A.15.** Yes. A kit\*\* comprising transformers and cable is available, provision being made to secure the aerial transformer to the\*3 cross bar of the television aerial, the rest of the system being carried out as an ordinary anti-interference installation.

**Q.16.** Must a dipole and reflector always point directly at the television transmitting station?

**A.16.** Generally yes, but an installation department or any people doing a large number of installations know that it is often advantageous to rotate the television aerial slightly one way or the other due to distortion of the polar diagram caused by local conditions at the receiver end. The rotation of the receiver aerial is also often used to improve the "signal to noise" ratio where there is local interference. See next question 1, repeated.

**Q.1.** (Repeated from Quiz No. 1). What are the advantages obtained when using a reflector with a dipole?

**A.1.** (a) It is necessary in areas of weak field strength to increase the signal input to the receiver.

(b) The directional properties can be utilised as a means of minimising interference, particularly so, if the aerial can be installed in such a position that the location of the source of interference is placed behind the reflector in relation to the transmitter.

(c) By rotating the aerial, ghost image can be reduced or eliminated.

**Q.17.** What type of plug and socket is recommended for use with L.336 balanced feeder?

**A.17.** The L.303\*\* range for skirting board terminations and wander plugs for the receiver. The L.303 range are flat pin plugs complying with BSS.613 and are available for flush mounting and proud mounting and in Brown and Cream (Cream in short supply).

**Q.11.** Are masts supplied with Belling-Lee\*1 aerials?

**A.11.** Normally yes, but at the present time the bulk purchase of suitable wooden masts is almost impossible. That is why we ask customers to supply their own. It is generally possible to obtain a single one locally.

**Q.12.** What kind of pole is required?

**A.12.** We specify turned pine 2½ in. in diameter by approximately 16ft. in length. In practice any stout mast will do but the 2½ in. diameter is important, as this has to fit pole clamps and a pole cap\*1

\*1 L.502/L Dipole, reflector and cross arm, chimney lashings (less mast), £5 5 0

Supplied also without reflector and/or chimney lashings from £2 3 6

\*2 Belling-Lee Patent No. 526587.

\*3 Belling-Lee Patent Nos. 520628, 519883.

\*4 L.392/100 ... .. £7 10 0  
L.392/120 ... .. £8 6 0  
Including 2 transformers. Suffix No. denotes length of L.1221 Feeder Cable.

\*5 L.303/F 3-way socket flush mounting ... 3/- each  
L.303/P 3-way plug flush mounting ... 1/4½ each  
L.303/S 3-way socket surface mounting ... 2/9 each  
Cream approx. 25% dearer

**BELLING & LEE LTD**  
CAMBRIDGE ARTERIAL ROAD, ENFIELD, MIDD

TO BE CONTINUED .



1093

# ERIE


## *Electronic Components*

The engineering resources which produced hundreds of millions of Erie components for war-time needs are now at your service. May we advise you, quote you, or send you samples?

**ERIE RESISTOR LTD.**  
 CARLISLE ROAD, THE HYDE,  
 LONDON, N.W.9.

Telephone : Colindale 8011

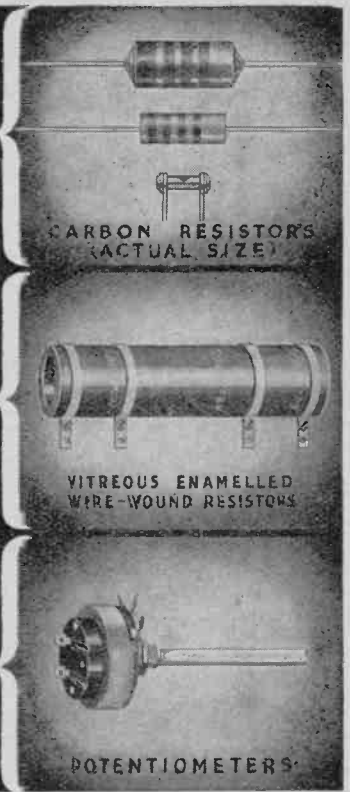FACTORIES : London, England  
 Toronto, Canada • Erie, Pa., U.S.A.



# Musical Radio

## The POLYPHONIC RADIOGRAM

A combined quality Instrument without cabinet "dialect," incorporating the phase inverter speaker, and seven valve three band tandem coupled variable selectivity super-het with paraphase **£67.10.0** triode output. *Plus Purchase Tax.*

## Sound Sales Ltd.

WEST STREET, FARNHAM, SURREY.

FARNHAM 6461-2-3.

Agents. LONDON : Messrs. Wallace Heaton, Ltd., 127, New Bond St., W.1  
 KENT : Messrs. Potter Bros., 49, High Street, Tenterden.  
 S. WALES : Messrs. Sound Ltd., 46, Charles Street, Cardiff.

SURREY : West End Radio, West Street, Farnham.  
 LANCOS : Liverpool Sound Studios, 83a Bold Street, Liverpool, 1.  
 CHANNEL ISLANDS : Sound Services, 16 Charing Cross, St. Helier, Jersey.

# AIDS TO TRAINING


## "Synthetic" Methods in the R.A.F.

By

M. G. SCROGGIE,

B.Sc., A.M.I.E.E.

**D**URING the war enormous numbers of people, most of whom possessed no previous knowledge of radio, had to be trained in the operation and maintenance of ever more complex equipment, in the shortest possible time. At the start, blackboard and chalk, and sometimes (but not always) a sample of the equipment to be taught, were the only training apparatus available. Anything else had for the most part to be extemporized from salvage by the instructors themselves, who were already fairly well loaded with teaching. Nevertheless, a mere selection of the aids developed for use in the R.A.F. Group concerned with radio training was sufficient to make up a large and interesting exhibition held recently at Cranwell.

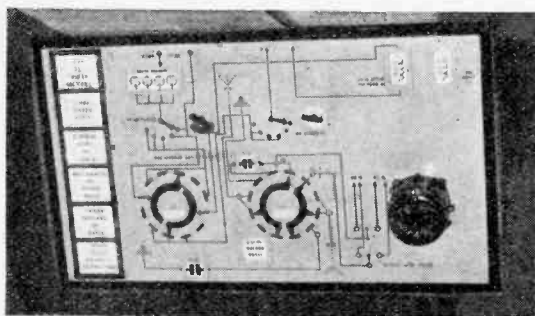

The exhibits represented great changes in methods of teaching. They were of two main categories: those designed to make the teaching more palatable and digestible, such for example as a mechanical model of wave motion; and synthetic devices such as the Harwell Box, into which radio signals and engine noises are fed, in order to simulate the surroundings of wireless operators in flight without having to provide aircraft.

Blackboard and chalk, even in the hands of the most capable lecturer, leave much to be desired. For some of the instruction they are being supplanted by cathode-ray tubes large enough to be seen

by a whole class, or alternatively a number of small tubes mounted on the classroom desks and wired in parallel. A good example is the trainer for AI Mark X (American SCR-720). It consists of a boldly drawn circuit diagram the size of a blackboard, a working set of the equipment, and an outsize in oscilloscopes with two 12-in cathode-ray tubes. By means of push-button switches the instructor can connect either of the tubes to any important point in the equipment, and at the same time as the waveform appears on the tube an indicator lamp marks the corresponding point on the circuit diagram. Similar apparatus is used for a number of other circuits.

Illuminated panels are used to demonstrate the functions of an aircraft aerial switch.

This scheme has many advantages. It saves the instructor's time in drawing diagrams, and is more legible (generally!). It is more convincing to the trainee, who sees an actual oscillogram coming from an actual set. The effects on waveform of operating the controls can be demonstrated. It adds usefully to familiarity with oscilloscopes. Direct correlation of the gear itself, its circuit diagram, and its oscilloscope pictures, is far more effective than blackboard sketches which have to be related elsewhere to the thing itself.

During the war radio and radar equipments were too numerous and transitory for such refined

methods to be used universally, but in peacetime these difficulties should lessen.

Although the policy in R.A.F. instruction is towards study of the equipment itself rather than theoretical blackboard sketches, the external or even the internal appearance of a set seldom goes far towards enabling a trainee to grasp how it works. It is helpful therefore to demonstrate some of the more involved processes by means of aids that are part-model and part-diagram. For instance, the Type J aerial switch in the aircraft radio T1154/R1155 is connected to a diagram in which illuminated panels show the circuit changes as the switch is operated.

Another modern trend is to give the trainee opportunities for repeating demonstrations himself until they are thoroughly absorbed. The push-button devices already mentioned can be used for this. Another self-teaching aid is the Quiz Board, down one side of which are a number of questions, and down the other, in random order, are the answers. Question and answer can be selected by push-buttons; and if the trainee ventures the right answer he is rewarded by a green light. Any other answer results in a red light and (to rub it in) a blast from a horn.

A very important qualification in radio is being able to deduce the nature of a fault quickly from the symptoms. If this can be done without the aid of any instruments, so much the better. Devices for associating the fault with the symptoms include an R1155 receiver in which by means of a selector switch any valve heater could be open-circuited to simulate a faulty valve. Another, for teaching the use of the oscilloscope in tracing radar faults, is similar to the "live" circuit diagrams already described, except that, instead of being provided with push-buttons for selecting waveforms, the key points in the working equipment were brought




### Aids to Training—

out through screws to the appropriate points on the circuit diagram. The instructor organizes a fault behind the board; and the trainee, armed with an oscilloscope, has to check the test points and deduce the fault.

The properties of centimetre-wave equipment were demon-

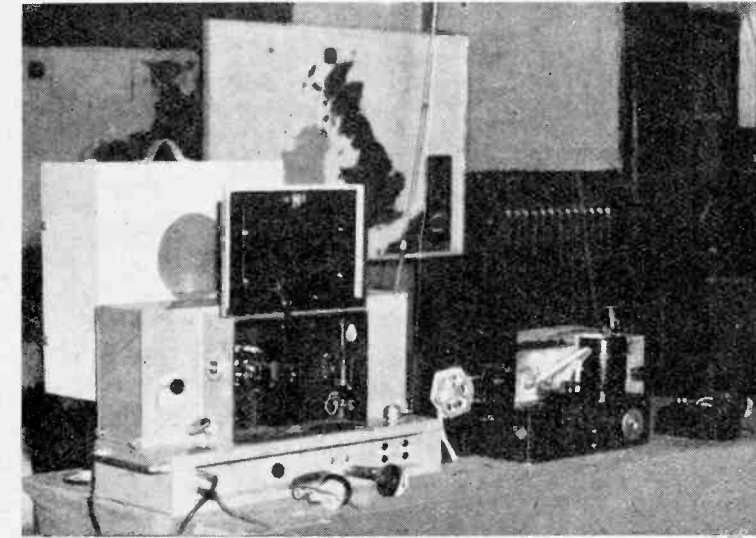strated by assemblies in which the output from a magnetron could be passed into waveguides fitted with all the gadgets known to modern electro-magnetic plumbing. The paths taken and the relative field strengths were indicated by neon lamps and explored in space by means of a vacuum-enclosed dipole and thermo-junction with indicating meter.



A morse transcription unit used to enable pupils to assess accurately their proficiency in sending. The tape from the undulator is passed through a transcriber, the speed of which can be varied.

strated by assemblies in which the output from a magnetron could be passed into waveguides fitted with all the gadgets known to modern electro-magnetic plumbing. The paths taken and the relative field strengths were indicated by neon lamps and explored in space by means of a vacuum-enclosed dipole and thermo-junction with indicating meter.

Centimetre waves are used not only to demonstrate their own techniques but also for scale-down study of aerial polar diagrams. The output of a klystron can be coupled to any one of a number of model aerial systems, rotating at about 6 r.p.m. Radiation is picked up by a receiver a short distance away, and the amplified output displayed as the length of a radial line on a C.R.T., rotating in synchronism with the model aerial. The polar diagram of the aerial is thus continuously painted on the tube.

A synthetic trainer of true

scientific elegance is Type 54, for simulating flight conditions with H2S radar. H2S, it will be remembered, is the centimetric radar with a rotating scanner mounted on the underside of a bomber, showing on a plan position indicator a picture of the terrain beneath within a controllable radius. The scaling-down neces-

sary to enable echo pictures to be obtained from an indoor model of the country is effected by replacing radio waves travelling at 300,000,000 metres per second by supersonic sound waves travelling in water at about 1,500 metres per second. One mile can therefore be represented by about 8 millimetres in the model, which consists of a sheet of glass forming the bottom of a tank of water a few feet square. The glass is left smooth to represent water and sandblasted to represent land, with towns built of grains of corundum. The scanner of the H2S set is replaced by a quartz crystal mounted over the glass model at a distance representing to scale the height of the bomber. By means of its mounting the crystal can be moved about to simulate the flight of the imaginary aircraft; if necessary, under the control of a Link Trainer. These movements are traced on a glass map forming the lid of the tank.

The crystal is rotated at the scanning speed and pulsed at the normal pulse frequency, setting up a beam of sound waves in the water at 14.5 Mc/s, which is the H2S intermediate frequency. Echoes impinging on the crystal generate piezo-electric voltages which are passed straight to the I.F. amplifier, from which point the normal H2S equipment is used; and the P.P.I. traces simulate effectively those that would appear in a flight over real country. The trainee radar operator is able to practice bombing runs, and as a check on the accuracy of his work the position on which the bomb would have fallen is indicated on the map.

### STABILIZED POWER UNITS

A SERIES of voltage-stabilized supply units is being produced by S. Szymanski and O. Dzierzynski, 95, Strodes Crescent, Staines, Middlesex. The units are electronically controlled and are notable for the large number of independent supplies available from each instrument. As an example, the Model 3S/46 gives three adjustable and stabilized H.T. supplies: 250-700 V, 200-50 mA; 120-350 V, 200-80 mA; 40-120 V, 70-25 mA—all stabilized to within 2 per cent. In addition there are A.C. auxiliary circuit supplies of 2, 4, and 6 V, 2 amps; 1, 4 and 5 V, 3 amps and 300 V centre tapped, 80 mA. Two grid bias supplies of 0-45 V D.C. with common positive and negligible ripple content and a 3,000 V D.C., 5 mA supply for C.R. tubes complete the picture.

The three stabilized voltages have + and - insulated from the chassis and can be connected in series.

### POLYTHENE AT V.H.F.

AN interesting letter by J. G. Powles and W. G. Oakes appears in *Nature* for June 22nd, 1946, regarding the behaviour of polythene at high frequencies. As might be expected, the power factor increases with frequency for the lower radio frequencies, rising from  $0.9 \times 10^{-4}$  at 100 kc/s to about  $2.6 \times 10^{-4}$  at 1,000 Mc/s (30 cm wavelength). At higher frequencies, however, the rise is not continued; there is a flat maximum around 1,500 Mc/s and thereafter the power factor falls. At 10,000 Mc/s (3 cm) it is down to some  $2.2 \times 10^{-4}$  and the curve falls quite rapidly at higher frequencies.

The reason for this rather unexpected state of affairs does not seem to be fully understood.

# AMERICAN SERVICE VALVE EQUIVALENTS

## CORRESPONDING CIVIL TYPES

WE published in the August, 1945, issue a list of British Service valve equivalents, and since then many readers have written asking if we can identify various American types. No claim to completeness is made for the following list, but we have found that it answers all the enquiries we have so far received and we think that it will be useful as it stands.

The short list of "JAN" serials at the end of the main list gives the few types in which the "JAN" number differs from the normal civil number.

To avoid confusion with R.A.F. types, some of which also bear "VT" numbers, two appendices are given. Appendix A indicates those valves which are not immediately distinguished by their British or American bases, and Appendix B gives types which have different "VT" numbers in the British and American Services.

Suffixes A, B, C, D to a "VT" serial generally distinguish between M, G, GT or GT/G, though not necessarily respectively.

Service Number	Civil Type	Service Number	Civil Type	Service Number	Civil Type	Service Number	Civil Type
VT24	864	VT104	12SQ7	VT184	VR90/30	VT229	6SL7GT
VT25	10	VT105	6SC7	VT185	3D6/1299	VT231	6SN7GT
VT27	30	VT107	6V6	VT188	7E6	VT233	6SR7
VT28	24A	VT109	2051	VT189	7F7	VT234	HY114B
VT29	27	VT111	5BP4/	VT190	7H7	VT235	615
VT30	01A		1802-P4	VT191	316A	VT236	836
VT31	31	VT112	6AC7/	VT192	7A4	VT237	957
VT33	33		1852	VT193	7C7	VT238	956
VT35	35/51	VT114	5T4	VT194	7J7	VT241	7E5/
VT36	36	VT115	6L6	VT197A	5Y3GT		1201A
VT37	37	VT116	6SJ7	VT198A	6G6G	VT243	7C4/
VT40	40	VT117	6SK7	VT199	6SR7		1203A
VT44	32	VT118	832	VT200	VR105/30	VT244	5U4G
VT46	866	VT119	2X2/879	VT201	25L6	VT245	2050
VT47	47	VT120	954	VT202	9002	VT247	6AG7
VT48	41	VT121	955	VT203	9003	VT250	EF50
VT49	39/44	VT124	1A5GT	VT205	6ST7	VT255	705A/8021
VT50	50	VT125	1C5GT/G	VT206A	5V4G	VT259	829
VT52	45	VT126	6X5	VT207	12A17GT	VT260	VR75/30
VT55	865.	VT131	12SK7	VT209	12SG7	VT264	3Q4
VT56	56	VT132	12K8	VT210	1S4	VT266	866Jr.
VT57	57	VT133	12SR7	VT211	6S87	VT268	12SC7
VT58	58	VT134	12A6	VT212	958	VT269	717A
VT59	59	VT135	12J5GT	VT213A	6L5G	VT286	832A
VT62	801	VT136	1625	VT214	12H6	VT287	815
VT63	46	VT137	1626	VT215	6E5	VT288	12SH7
VT64	800	VT138	1629	VT216	816	VT299	12SL7GT
VT65	6C5	VT139	VR150/30	VT221	3Q5GT/G		
VT66	6F6	VT145	5Z3	VT222	884	JAN-	
VT68	6B7	VT146	1N5GT	VT223	1H5GT	3B-22	EL1C
VT69	6D6	VT147	1A7GT	VT224	2C3A/	JAN-	
VT70	6F7	VT148	1D8GT		RK34	38142	45 Special
VT73	843	VT150	6SA7	VT225	307A	JAN-	
VT74	5Z4	VT151 B	6A8GT	VT226	3EP1/	UH50	834
VT75	75	VT152	6K6GT		1806-P1	JAN-	
VT76	76	VT153	12C8	VT228	8012	VT25A	10 Special
VT77	77	VT154	RK47/814				
VT78	78	VT161	12SA7				
VT80	80	VT162	12SJ7				
VT83	83	VT163	6C8G				
VT84	84/6Z4	VT164	1619				
VT86	6K7	VT165	1624				
VT87	6L7	VT167	6K8				
VT88	6R7	VT168A	6Y6G				
VT89	89	VT169	12C8				
VT90	6H6	VT170	1E5GT				
VT91	6J7	VT171	1R5				
VT92	6Q7	VT172	1S5				
VT93	6B8	VT173	1T4				
VT94	6J5	VT174	3S4				
VT95	2A3	VT175	1613				
VT96	6N7	VT176	6A B7/				
VT97	5W4		1853				
VT98	6G5/6U5	VT177	1LH4				
VT99	6F8G	VT178	1L0C	6J7G ..	VT91A	VT74	
VT100	807	VT179	1LN5	RK34 ..	VT224	VT61	
VT101	837	VT182	3B7/1291	807 ..	VT100	VT60	
VT103	6SQT	VT183	1R4/1294	832 ..	VT118	VT88	

### APPENDIX A

Service Number	Civil Type	
	U.S.A.	British
VT52 ..	45	EL32
VT75 ..	75	KT66

### APPENDIX B

Civil Type	Service Number	
	U.S.A.	British
6J7G ..	VT91A	VT74
RK34 ..	VT224	VT61
807 ..	VT100	VT60
832 ..	VT118	VT88

# PREMIER RADIO Co.

MORRIS & CO. (RADIO) LTD.

All Post Orders to  
167 Lower Clapton Rd., London, E.5.

'Phone: Amherst 4723

Callers to  
169 Fleet Street, London, E.C.4.

'Phone: Central 2833

Our New List will be ready the 10th September. Price 2½d., post paid.

**RADIOGRAM CABINETS.** Dignified appearance and good workmanship. Size 34½ in. high, 19 in. deep, 36 in. wide. Send for illustration. Cabinet only, £26. With Electric Motor and Pick-up, £32/16/-. With Record Changer, £42/16/-.

**CANADIAN R.103 CAR RADIOS** (SPECIAL OFFER). A high grade receiver in metal case with adjustable rod aerial and spare set of valves and vibrator. Operates on 6 v. battery. Has a modern 7 valve superhet circuit, including R.F. stage and B.F.O. Self-contained speaker. Covers 19-300 metres in 3 bands. Size 20 in. x 10 in. x 8 in. The ideal radio for boat, car or caravan. Price £23/10/-.

Adaptor to operate above on A/C mains, £5.

**ROTARY TRANSFORMERS.** Size only 7 in. by 4½ in. diameter. With 6 v. input; output 200 v. 50 m/a. With 12 v. input; output 400 v. 80 m/a. Price 20/-.

**ROTARY TRANSFORMERS.** With 12 v. input; output 600 v. 250 m/a. With 6 v. input; output 280 v. 250 m/a. Price £3.

**D.C. to A.C. ROTARY CONVERTERS.** Input 24 v. Output 230 v. 200 watts. Or with 12 v. input, output 100 v. 80 watts. £7.

**PLAYING DESKS.**—Consist of an Electrical Gramophone Motor with automatic stop, and speed regulator, a quality magnetic Pick-up mounted on a strong metal frame. Price complete, £6/17/6; without Pick-up, £5/10/-.

**MIDGET RADIO KITS.**—Complete with drilled chassis, valves and loudspeaker, only cabinet required, medium and long wave T.R.F. Size 10 in. x 6 in. x 6 in., 4 valves, inc. rect., tone control. AC/DC operation, 200/250 v. Circuit and constructional details supplied. Price, including tax, £6/17/6. Cabinet, if required, 25/- extra.

**FIRST GRADE OIL FILLED PAPER CONDENSERS,** with miniature stand-off insulators and fixing clips, 2 mfd. 1,000 v.w., 2/6 or 20/- per dozen; 2 mfd. 600 v.w., 1/3 each or 10/- per dozen; 1 mfd. 600 v.w., 1/- each, 8/- per dozen. Super Quality Oil Filled Tubulars. Insulation as good as Mica. 1 mfd. 500 v.w., .02 mfd. 750 v.w., .5 mfd. per dozen.

**SERVICEMAN'S KIT.**—Consists of 50 resistances, 50 condensers. All useful values, 20/- only.

**B.P.L. SIGNAL GENERATOR,** 100 Kc/s to 30 mc/s in six bands, 1 per cent. calibration, 1 volt into 10 ohms. 30 per cent. modulation by 400 cycle osc., mains driven, £21.

# RADIO AUSTRALIS

## Wireless in the Commonwealth : Openings for British Goods

From a Correspondent

AUSTRALIAN radio is slowly but surely taking its post-war shape. First efforts of manufacturers to catch up with a receiver demand starved over the war years have as yet not been completely successful. Various bottlenecks in production such as the shortage of parts, i.e., loud-speakers, variable condensers and electrolytic condensers, added to industrial hold-ups, have tended to slow things up. Nevertheless, a good range of broadcast, dual wave and kit sets is gradually becoming available.

It may not be generally known that Australian manufacturers have been able, behind a very high tariff wall, to found a very large business, and at this date an imported receiver is a rarity. Australian broadcast receivers are first-class articles. Largely of American design and mostly with an American valve kit, they give first-class results.

Customs duties leave a very small field for the British manufacturer. There is, however, scope for some lines of S.W. components. The writer had occasion recently to approach the "sole" agents in Australia for two well-known brands of English S.W. components which sold well in the pre-war days. One firm had no stock at all, the other almost none.

**Broadcasting.** — No concrete plans have as yet been formulated for the future of F.M., television or facsimile. The present A.M. service is a combination of national (Government-owned) and commercial stations. Powers range to 10 kW in the case of national stations and 2 kW in the case of commercial stations. The commercial stations are entirely dependent on income from advertising.

There is a good deal of dissatisfaction among the commercial stations on the questions of power

and frequency; on these they claim parity with the national service. There are still some 900 ungranted applications for commercial station licences. When a licence is issued a chorus of protest arises from the have-nots, and the usual vigorous protests were made when a licence was recently granted to the Queensland Labour Party. The administration of all radio is firmly in the hands of the Postmaster General, who in effect makes the regulations and interprets them too. Certain quarters are now asking that the whole of radio administration be taken from Ministerial control and placed in the hands of a Federal Communications Commission.

At the present time the Federal Parliament is being advised on broadcasting matters by a standing committee of both sides of the House who take evidence at the request of Parliament. They have issued ten reports which deal with such matters as station licences, sex broadcasts and salaries for staff of the Australian Broadcasting Commission who are responsible for the national programmes.

This committee has recently taken evidence on the desirability of setting up F.M. and television services, but no report has been issued to date. Broadcasting circles are hardly satisfied with the slow-moving methods of this committee, claiming that technical progress is being impeded.

**Amateurs.**—The re-licensing of amateurs has been going on steadily since January, some 1,500 licences having been issued. The new amateur requirements have been set out in a new set of regulations issued by the P.M.G.'s Department in a booklet called "Handbook for the Guidance of Experimental Wireless Stations." Principal changes from pre-war licences is the grading of operators' licences "A" and "B," and the provision of two classes of

stations, "A" class with a final plate input of 100 watts, and "B" class with a similar input of 50 watts. Frequencies available until recently have been 28-29, 50-54, 166-170 and 1,345-1,425 Mc/s, but the bands 14.1-14.3 and 7.15-7.2 Mc/s have just been allotted.

**Aviation.** — Radio facilities, greatly expanded during the war, have now been established on a firm footing. A complete string of Aeradio stations has been established, with D.F., navigational and communication facilities on the main airways. These are likely to be further expanded and improved as the Government has established its own Airlines Commission and is shortly to enter the Interstate Airways business in competition with private airlines.

**Communications.**—It is proposed that legislation will shortly be brought before Parliament to enable the Government to take over the communications facilities of Amalgamated Wireless, Ltd. This step is said to be in accordance with Empire policy. This action will be somewhat peculiar, in that the Government already controls 51 per cent of the £1,000,000 capital. The Government is still negotiating with the management on the matter of compensation. Amalgamated Wireless will presumably concentrate on its industrial activities, which are already large.

M.S.U.

Another contribution from Australia, in the form of a letter from a reader, is printed below.

### British Test Equipment

IT was with considerable interest that I read your article in the February number on the Physical Society's Exhibition. This, together with numerous letters which have appeared in your pages from time to time concerning British radio equipment for the overseas market, has prompted me to make this approach to you.

As a physicist in the Australian Munitions Supply Laboratories, having the supervision of the General Physics Laboratory, including an expanding electronics group,

I am required to select the equipment necessary for the work. I regret that very rarely have I been able to recommend the purchase of British test instruments, the majority of the orders being placed in the U.S.A. The manufacturers of American test equipment evidently consider it worth while to make known their products to the world. By turning to a readily available trade index one can usually find dozens of manufacturers of a given type of instrument, and from so large a choice it is rare if a suitable standard instrument cannot be chosen. They advertise their instruments in the trade and professional publications with a wealth of technical data, thus enabling the reader to determine their suitability for his particular requirement. As an example of this one need only peruse the pages of *Electronics*, or the *Proceedings of the Institute of Radio Engineers*, to be able to choose instruments for almost any requirements in the field of electronics. Further, one need only send a request for data to most of the manufacturers in U.S.A. to receive very expeditiously volumes of valuable performance data, characteristics and all necessary purchasing information.

If one wishes to buy British the story is a very different one. It is a matter of some difficulty to find the names of even two or three manufacturers of a required instrument. Often no British instrument can be located. No British publication carries advertisements in any way comparable with those in *Electronics* either in range of products or technical information supplied. When the name of a possible manufacturer has been obtained, a request for information has generally produced the minimum data neces-

sary to comply with the request. Thus on the score of publicity alone the chance of an order going to Great Britain is small.

Then, of course, there is the great drawback of non-standardization of components and valves, particularly valves. There is an obvious objection to holding in stock a spare set of valves for each test instrument. This is unnecessary with the majority of American test instruments, for when a valve becomes faulty a standard one is drawn from the ordinary valve stock. This objection also applies to the use of British types of valve in constructional work. The idea of designing equipment to use British valves is rarely worth considering.

We did have hopes in Australia that Great Britain would attempt to attract orders from the Dominions in the immediate post-war period. We realize that Great Britain is working under difficulties incomparably greater than those encountered by the American manufacturers. We would prefer to buy British equipment. Unfortunately, it would appear that even if Britain desires a market here, the race for orders is already lost. In our own case plans for the next year have already been made and we still don't know what Britain can offer us in the way of equipment, even less are we aware that British instruments are comparable with the American competitors.

In conclusion, may I state that I have recently requested information from the four British manufacturers whose address I have been able to obtain concerning the performance and availability of their products. I await the replies with interest. A. W. PYBUS, M.Sc.

Ascot Vale, Victoria,  
Australia.

BOOKS RECEIVED

**Radio-Communications.**—By W. T. Perkins and R. W. Barton. The authors have used the question and answer technique in producing this book which is intended for those intending to take the City and Guilds of London Institute examination in radio-communications. The thirteen chapters deal, *inter alia*, with components, valves, receivers, A.M. and F.M. transmitters, power supplies, aeriols, ship-shore radio, landlines, measuring instruments and interference. The final chapter outlines some 22 experiments and the book concludes with a section giving tables and data. 312+viii pp., with 184 diagrams. George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2. Price 12s 6d.

**Soul of Lodestone.**—By Alfred Still. The author traces the story of magnetism through the ages from Greek


mythology to the present time. The book includes an extensive bibliography and numerous quotations from authoritative works on the subject. 233+x pp. Murray Hill Books, Inc., 232, Madison Avenue, New York, 16, U.S.A. Price \$2.50.

**Varnished Cloths for Electrical Insulation.**—By H. W. Chatfield, Ph.D., B.Sc.(Hons.), and J. H. Wredde. The results of the authors' investigations into the use of various fabrics and methods of impregnation in providing high-class insulating cloths are given in this book. The authors have brought together in one volume the results of the researches carried out by the manufacturers of textiles, varnishes and electrical equipment. 255+xiv pp, with some 75 illustrations and diagrams. J. & A. Churchill, Ltd., 104, Gloucester Place, London, W.1. Price 21s.

NEW!



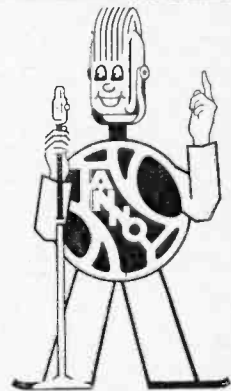Tannoy are introducing many new features in their post-war range of products, and highly specialised equipment is now available. Illustrated is the latest pattern Tannoy Ribbon Velocity Microphone. Write for full details of the extensive range of Tannoy Sound Equipment.



**TANNOY**  
*The Sound People*

"TANNOY" is the registered trade mark of equipments manufactured by **GUY R. FOUNTAIN LTD.**  
"THE SOUND PEOPLE"  
WEST NORWOOD, S.E.27. Gipsy Hill 1131  
and at Manchester, Belfast, Newcastle, Birmingham  
Bristol, Edinburgh, Glasgow, etc., etc.  
The largest organisation in Great Britain  
specialising SOLELY in Sound Equipment.

# RANDOM RADIATIONS

## Shock Tactics

ALL who went through the radar course at Watchet during the war (as hundreds of *Wireless World* readers probably did) will remember "Nobby," to say nothing of his awful little dog, Percy, who went through life with the ineradicable conviction that table legs and lamp-posts were one and the same thing. Nobby was in charge of the lab., where he spent his time in guiding students in their practical investigations of the forbidding array of complex circuits that go to make up a radar set. If the circuit on which you were engaged wasn't working properly, you sought Nobby's fatherly aid. No matter how high the voltages involved, it was a point of honour with Nobby never to switch off before going in up to the elbows amongst the maze of wires. Of course, he must have been more or less shock-proof, you say. Far from it; he got just what was coming to him in the way of shocks and his reaction in the shape of skyward leaps and naughty words were much the same as yours and mine. His fingers were covered with burns due to encounters with unexpected "hot spots"; but switching off he regarded as something pusillanimous, something definitely not done by the best people. Once when he was rather shakily recovering after "buying" 500 volts on my particular bit of apparatus I ventured to remonstrate with him, telling him that he really ought to make a point of switching off. "Wastes too much time," he said! I'd like to meet this hero again—provided he didn't bring Percy.

□ □ □

## Positive and Negative

REALLY it's about time that in schools and other places where they teach they scrapped the old erroneous idea of a "positive current" and adopted in its stead the conception of a current as a flow of electrons. I cannot see any point in retaining a view which is utterly wrong, especially as it makes things far more difficult for the student when he comes to electro-magnetism and its applications and to electronics. One objection often advanced to the change-over from wrong to right is that so many of the ancient rules and aids to memory would have to be dropped or changed. Many of them could actually be scrapped and a very good thing too! No need to bother about idiotic imaginary men swim-

## By "DIALLIST"

ming in currents, or to wonder whether its the right or the left hand whose thumb, forefinger and second finger must be arranged in odd ways if you remember the one fundamental rule that the magnetic field round a conductor carrying a stream of electrons towards you has a clockwise direction. Matters such as the polarity of electro-magnets and the direction of induced currents then present little difficulty. The Army gave a good lead during the war. We found it infinitely easier and quicker to teach the elements of electricity if we started off right away with the conception of an electron current. There could be no better time than the present for making the change everywhere; school textbooks are largely out of print and there is a golden opportunity of correcting the ancient error in the new ones that will presently be appearing.

□ □ □

## A Workshop Warning

IN my own den I have just fitted up one of the new 40-watt fluorescent tube lights and I find its white "daylight" a real joy to work by at night. If you're thinking of doing the same, here is a tip that you may find of value. For all their usefulness, these lamps, with the severely "commercial" holders and reflectors that are the only fittings now available are *not* beautiful. You will probably feel that, much as you would like to have the fluorescent tube when you are working, an ordinary lamp and shade would be preferable when a friend comes in for a chat. Easily managed, and here's how it's done. To a joist in the ceiling fix a good strong batten lampholder. Into two other joists, suitably spaced, screw two large brass cup hooks. Attach two lengths of brass chain to the holder of your fluorescent lamp and provide it with a suitable length of good flex, fitted with a bayonet connector. In the 40-watt model the choke and the condensers are built into the holder. To bring the lamp into use, hang it up by the chains and insert the adaptor into the batten holder and there you are. Have in reserve an ordinary pendant lamp and shade with a bayonet adaptor at the end of its flex. Then to take down one kind of light and put the other in its place is a matter of a couple of minutes. One word of warning about fluorescent tubes. Do

not install one in your workshop if this contains any fast-running power-driven machines such as a lathe or a drill. The tubes have a 50-cycle flicker which is imperceptible in the ordinary way. But it may "strobe" a fast-turning pinion, wheel or chuck so that it appears to be motionless and—well, need I say more?

□ □ □

## Pilot Lamps

ONE of the very weak spots of present-day receivers is the pilot lamp, or perhaps I should say the pilot lamps, for many sets contain two or more of them used as dial illuminators. The life of these lamps is apt to be so short that they are a continual worry to service-men—and to set designers. After studying an oscillogram kindly sent to me some time ago by a reader I'm surprised that any lamp with a metal filament ever survives the switching-on process more than a few times. As you know, the resistance of a cold metal filament is very low. This oscillogram shows current leaping to ten times its working figure immediately after being switched on and taking an appreciable fraction of a second to drop to normal. What we seem to need for pilot lamps is some kind of protective device, to be connected in series with them, containing an element which has a high resistance when cold and becomes a better and better conductor as it warms up.

□ □ □

## Up-the-pole-arization

A KIND correspondent has sent me a cutting from a lay paper containing an article in which the reader is promised knowledge without tears of everything that matters about F.M. In excited anticipation of finding a crystal-clear exposition of a subject so hedged about with difficulties for the wet-nose listener I plunged into the article. Are you by any chance a little shaky about the basic difference between A.M. and F.M.? Well, here is what it has to tell you. The simplest explanation, says the writer, is that, whereas A.M. sends out waves which go up and down, F.M. sends out waves which go from side to side! I deduce, my dear Watson, that the gifted writer had been in conversation with someone who knew his onions and that that someone had passed from the respective merits of A.M. and F.M. to those of horizontal and vertical polarization. It



could, though, be argued that A.M. as we know it is an "up and down" business, since all broadcast transmissions are vertically polarized, whilst F.M. in this country is a "side to side" affair in that the B.B.C.'s experimental transmissions using this system are horizontally polarized.

### BOOK REVIEW

**Alternating Current Measurements at Audio and Radio Frequencies** (2nd Edition). By David Owen, B.A., D.Sc., F.Inst.P. Pp 120 + vii, with 80 diagrams. Methuen and Co., Ltd., 36, Essex Street, London, W.C.2. Price 5s.

THIS revised edition of a book that first appeared in 1937 still serves a most useful purpose by providing information, in concise form and at a moderate price, on a selection of the best methods of measuring inductance (self and mutual), capacitance, A.C. resistance, voltage, current, and frequency. The author has succeeded in covering theory and principles adequately while being thoroughly practical.

The first chapter recapitulates as much A.C. theory as is necessary to a clear understanding of bridge and resonance methods, and there is also a chapter on conditions of accuracy in bridge methods. The remaining five chapters deal with specific methods. In these, theory is applied in comparing their respective merits, and practical points are illustrated by examples. The order of accuracy is everywhere indicated. Methods for mutual inductance, so often neglected even in large texts, are included in considerable variety,

and at greater length even than methods for capacitance. The quantities involved and the mode of operation and of working out results are clearly and concisely set out. In this an important contribution is made by the diagrams, which, although not of the highest standard of draughtsmanship, deserve praise for their clarity.

As the book is one of a series intended to supply readers with "a compact statement of the modern position" in their subjects, however, it is a pity that revision was not carried further, as at this date there is a slightly archaic flavour, especially in the chapter devoted to R.F. measurements, comprising one-third of the volume. For example, the statement that "at high frequencies bridge methods are in general no longer suitable" can hardly be squared with the modern position, in which bridges are commercially available up to at least 60 Mc/s. The wavemeter circuit diagram (Fig. 55) with terminals for a coupling coil in series with the calibrated oscillatory circuit, and a variable condenser across phones and H.T., among other strange features, suggests the early 1920s. The present generation, too, is so used to thinking of coils as synonymous with inductors that the expression "inductive coils" may seem tautological; and the use of the word "coil" for a non-reactive component may confuse some.

With this one qualification, the book can be highly recommended, especially to students who want something clear and more concise than the large textbooks.

M. G. S.

## SHORT-WAVE CONDITIONS

*Expectations for September*

By T. W. BENNINGTON

(Engineering Division, B.B.C.)

DURING July the average maximum usable frequencies for this latitude were almost the same as during June, both day and night. The midnight M.U.F. was, in fact, little lower than that for noon, and frequencies as high as 17 Mc/s could have been regularly used till long after midnight on most routes. As was expected, the daytime M.U.F. was relatively low, and communication on exceptionally high frequencies by way of the regular layers was therefore very infrequent, especially to countries in the Northern Hemisphere. This situation should soon change consider-

ably, as is indicated in the forecast given below.


Sporadic E was, however, very prevalent during the month and a considerable amount of communication on very high frequencies by way of this medium was possible out to medium distances, as had been forecast in this column.

Several ionosphere storms occurred and some were of a more severe nature and caused more interruption to communications than is often the case in July. The worst one appeared to be associated with an exceptionally large sunspot which crossed the sun's central meridian on July 26th. The most disturbed periods were 3rd-4th (slight), 18th-20th (severe on 19th) and 25th-28th (very severe 26th and 27th). Incidentally a "very great" magnetic

# M. WILSON LTD

## SUPERHETERODYNE 3-WAVEBAND COIL UNIT

16-47, 200-540, 800-2,000 m.

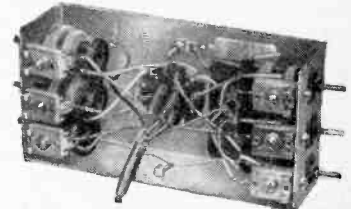

Midjet Iron-cored, high Q, very selective Litz-wound coils mounted in 18 s.w.g. aluminium screen with all necessary paddlers and trimmers. LF-400 Kcs. Completely wired up to switch with colour-coded connections, ready to fit into receiver chassis. 39/6 Aerial tested.

### AMPLIFIER CHASSIS

#### 4-VALVES (Inc. Rectifier), 4-WATTS

Assembled on 16 s.w.g. aluminium chassis fitted with separate Tone Control, Volume Control with on/off switch, sockets for microphone, gramophone and extension speaker. Hum free, good quality reproduction. A.C. only. Input 200/250 v. Size overall, 8x6 1/2 x 7 1/2 in. Ready to play. Price, 10 Gns. including valves and 8 in. P.M. speaker

#### 4-VALVES, 6-WATTS

With EX-4 output. Specification as above, including valves and 8 in. P.M. speaker 12 Gns. Theoretical and practical Blue Prints of the above available separately. 3/6 per set.

### TO AMATEUR RADIO ENTHUSIASTS

We can supply Blue Prints and complete lists of parts boxed, to build any type of receiver from a simple Crystal Set to an Advanced Frequency Modulation Receiver.

Details will be sent upon receipt of your particular requirements.

### OUR POLICY

QUALITY is given priority in our effort to produce Radio Receivers better than most. Careful design, English craftsmanship, first-class components and rigid inspection combine to give you something really good.

**MIDGET 2-GANG CONDENSERS.** .00035 mfd. Ceramic insulation, 12/6.

**MIDGET IRON-CORED PERMEABILITY TUNED COILS** 460 Kcs. Wavebands cover the following standard ranges: 16-47, 200-550, 800-2,000 m., A, H.F. Osc. 3/- each coil.

**SMALL IRON-CORED PERMEABILITY TUNED I.F. TRANSFORMERS.** Screened 400 Kcs., 15/6.

**VARIABLE CONDENSERS.** 25 pf. ceramic plate midjet single—can be ganged, 4/6; .0015 ceramic plate 2-gang, small, 12/6; .0005 ceramic insulation, 2-gang, small, 12/6; .00015 standard, 2-gang, 8.5V. 12/6. Reaction condensers, .0003 mica dielectric, 3/-.

**TRIMMERS.** 3/30 ceramic base air spaced, n.w. 2/-; 40 pf. 8.5V. pre-set neutralising cond. 2/-; T.C.C. 4 a., 6.3 v. 4 a., 5 v. 2 a., 175 ma., £2 12s. 6d.; 10-0-200, 230, 240 v. primary, L.F. chokes, 20 hp., 500 or 1,000 ohms. 100 mA., interleaved with mounting feet, 21/-.

#### TO OVERSEAS TRADERS

Wholesale and retail enquiries are invited.

Orders can be executed for B.A.O.K., C.M.F., and S.E.A.C. customers.

**307, HIGH HOLBORN.**  
LONDON, W.C.1, Phone: HOLborn 4631

**Short-wave Conditions**— storm also occurred on the 27th, and on this day the interruption to communications was on a world-wide scale.

Several "Dellinger" fadeouts, also apparently associated with the large sunspot, occurred during daylight hours on 21st, 23rd, 24th and 25th.

**Forecast.** — In September the seasonal effect in the Northern Hemisphere is such as to produce an increase in F-layer daytime ionization, and, as there is also at the present time the rapid increase in sunspot activity to enhance this effect, a very considerable increase in the daytime working frequencies to most parts of the world is ex-

pected to occur during September of this year. The night-time frequencies for long-distance transmission will, however, decrease somewhat as compared with August.

Amateur transmitters working the 28 Mc/s band may expect very many more opportunities for DX contacts, especially with distant countries in the Northern Hemisphere, than they have had of late, provided that they work the band at the right time of day.

Sporadic E is likely to decrease considerably in the frequency of its occurrence during the month, and medium-distance transmission on high frequencies by way of this medium should be much less frequent than of late, though it may

occasionally occur. It is not expected that the normal E layer will often control transmission for any distance in these latitudes during September.

Below are given, in terms of the broadcast bands, the working frequencies which should be regularly usable during September for four long-distance circuits running in different directions from this country. In addition a figure in brackets is given, which indicates the highest frequency likely to be usable for about 25 per cent of the time during the month for communication by way of the regular layers:—

<b>Montreal :</b>	0000	11 Mc/s	(18 Mc/s)
	0200	9 "	(14 " )
	0800	11 "	(18 " )
	1000	15 "	(22 " )
	1100	17 "	(26 " )
	1300	21 "	(31 " )
	2000	17 "	(26 " )
	2200	15 "	(22 " )
<b>Buenos Aires :</b>	0000	11 Mc/s	(17 Mc/s)
	0400	9 "	(15 " )
	0900	15 "	or (23 " )
		17 "	
	1100	21 "	(30 " )
	1400	26 "	(34 " )
	1800	21 "	(30 " )
	2100	17 "	or (23 " )
	2300	15 "	(19 " )
<b>Cape Town :</b>	0000	11 Mc/s	(17 Mc/s)
	0600	17 "	(24 " )
	0700	21 "	(31 " )
	1100	26 "	(35 " )
	1600	21 "	(31 " )
	1900	17 "	(24 " )
	2100	15 "	(21 " )
	2300	11 "	(19 " )
<b>Chungking :</b>	0000	9 Mc/s	(15 Mc/s)
	0200	11 "	(17 " )
	0500	15 "	or (24 " )
		17 "	
	0800	21 "	(29 " )
	1400	17 "	(26 " )
	1600	15 "	(21 " )
	1800	11 "	(17 " )
	2200	9 "	(15 " )



## POCKET RADIO

WITH the general release of "sub-miniature" valves, developed by the Raytheon Manufacturing Company for the proximity fuse, the Belmont Radio Corporation of Chicago has produced this pocket receiver. It is a five-valve superhet, the case for which measures 3in wide, 1/2in thick and 6 1/4in high and weighs only 10 oz with batteries. Some idea of the compactness of the construc-

tion will be gained from the photograph of the interior.

The five valves, each of which measures 1 1/2in long and is oval in cross section—0.4 x 0.3in—weigh about half an ounce. The H.T. voltage required for these miniature valves is only 22 1/2.

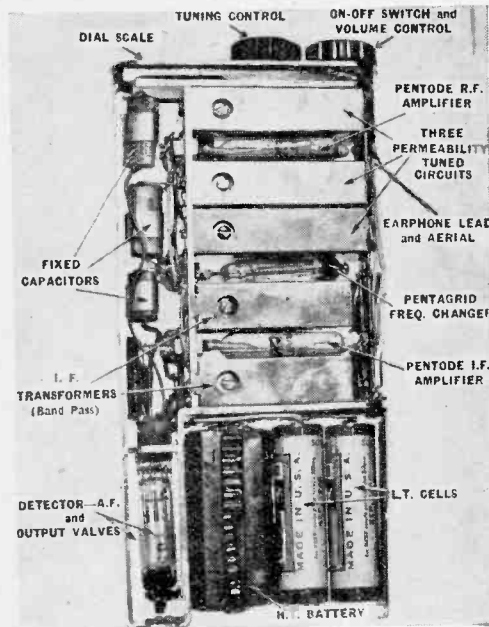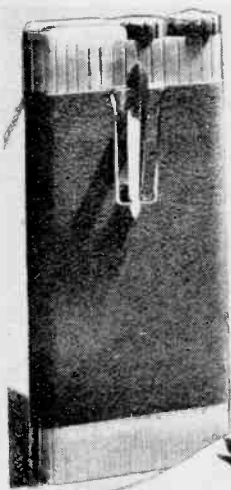A miniature earpiece is used with the Belmont Pocket Receiver which has been photographed . .



. . with a fountain pen for the purpose of comparison. The annotated view of the chassis shows the disposition of the main components.

Ionosphere storminess is quite likely to be particularly prevalent during September, and periods of poor short-wave communication must be expected. Although one cannot be at all certain, it would appear that such disturbances are more likely to happen within the periods 1st-3rd, 10th-13th, 19th-21st and 28th-30th than on the other days of the month.

**Footnote.** — Readers of this column may be interested to know of a prediction of the sun's activity during the next several years, recently published by M. Waldmeier, of Zurich Observatory. According to this the coming maximum is expected to be higher than the last and to occur in the latter part of 1947. Thereafter the sun's activity should gradually decrease till about 1954, the whole cycle thus occupying less than ten years. Usable radio frequencies are, of course, high at the maximum and low at the minimum.

**LETTERS TO THE EDITOR****Internal-fitting Earphones ♦ Pulse Modulation ♦ Impregnated Winding****Hearing-Aid 'Phones**

WITH reference to the letter from A. P. R. Mackie in your July issue, may I point out that the earpiece described by me in *Wireless World* of June is intended to work as an air conductor, and it has been shown that it has a smaller bone conductor component than an ordinary Post Office telephone receiver? It does not compete in efficiency with the latest miniature crystal earpieces, but while these are inclined to have an upper frequency response, the shell earpiece, as I have called it, can very easily have its response tailored, and if required it will give a very level response over a wide range, or it can even be made to accentuate the bass by varying the masses and springs (rubber pads) and the damping. The mathematics are very complicated, but theory confirms practice in this matter. In fact, far more amplitude can be delivered by the shell than is allowed by the mechanical restrictions to be found in the small diaphragm associated with a miniature electromagnetic receiver.

I think I am not laying myself open to contradiction if I state that the shell earpiece is considerably more efficient than any bone conductor that has been produced; also that it has all the practical advantages of a bone conductor receiver without the necessity of a head band; but I agree with Mr. Mackie that a number of sizes of receivers will have to be in stock against only a number of anatomical fittings, but this is a point where the manufacturers will have to make provision and good service should obviate the difficulty.

C. M. R. BALBI.  
Durban, Natal.

**"Miller" Integrator?**

I HAVE noted with interest M. G. Scroggie's suggestion, in your June issue, that the Miller Integrator should be re-named "Blumlein."

The problem of correctly attributing many of the wartime electronic developments is clearly going to present many difficulties, although few of the circuits are of such broad significance as the so-called "Miller" integrator.

I agree with Mr. Scroggie that the present name is inappropriate but, although not wishing to detract in any way from the many achievements of the late A. D. Blumlein, would enquire how Mr. Scroggie's suggestion can be reconciled with British Patent 575,250, recently issued to Messrs. A. C. Cossor and J. W. Whitley (with whom, incidentally, I am in no way connected).

R. J. F. HOWARD.

Walton, Staffs.


**Pulse Terminology**

IN your issue of April, 1946, "Cathode Ray," in an article entitled "Pulse Modulation," gives useful information on various aspects of a transmission system which has very great possibilities. However I think that the choice of certain descriptive terms is not exactly happy. May I suggest the following definitions.

(1) When the time of occurrence of one or both edges of the pulses of one class in a train of pulses of the same class (the pulses having constant amplitude) vary in accordance with a modulating intelligence, the pulse train is said to be "Time Modulated." The general term "Time Modulation" should be applied to all such transmissions.

(2) When a train of pulses of one class (the pulses having constant amplitude and duration, and in the unmodulated condition one of the pulses periodically occurring during successive equal time periods) is time modulated in accordance with a modulating intelligence within limits such that one pulse of said class always occurs during each of the successive equal time periods, the pulse train is said to be "Phase Time Modulated."

(3) When a train of pulses of

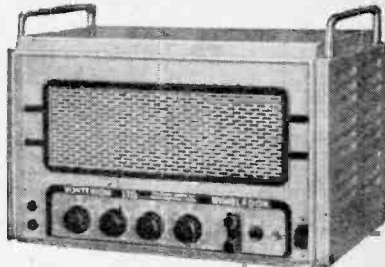**VORTEXION  
"SUPER FIFTY WATT"  
AMPLIFIER**

30 cps. to 15,000 cps. within  $\frac{1}{2}$  db. under 2% distortion at 40 watts and 1% at 15 watts, including noise and distortion of pre-amplifier and microphone transformer. Electronic mixing for microphone and gramophone of either high or low impedance, with top and bass controls. Output for 15-240 ohms, with generous voice coil feedback to minimise speaker distortion. New style easy access steel case gives recessed controls, making transport safe and easy. Exceedingly well ventilated for long life. Amplifier complete in steel case, as illustrated, with built-in 15 ohms mu-metal shielded microphone transformer, tropical finish. Price 29½ gns.

**C.P. 20A 15 Watt AMPLIFIER** for 12-volt battery and a.c. mains operation. This improved version of the old C.P.20 has switch change-over from a.c. to d.c. and "stand-by" positions, and only consumes 5½ amperes from 12-volt battery. Fitted mu-metal shielded microphone transformer for 15-ohm microphone, and provision for crystal and moving iron pick-up with tone control for bass and top and outputs for 7.5 and 15 ohms. Complete in steel case, with valves. £22.10.0.

**A.C.20 AMPLIFIER**.—This well-known model has been retained and has a response 30—15,000 cps., mixing arranged for crystal pick-up and microphone, large output transformer for 4—7.5 and 15 ohms to deliver 15 watt at less than 5 per cent. total harmonic distortion to the speakers. Price £15 15 0  
Case for above model, Price £3 0 0.

**RECORD REPRODUCER**.—This is a development of the A.C.20 amplifier with special attention to low noise level, good response (30—18,000 cps.) and low harmonic distortion (1 per cent. at 10 watts). Suitable for any type of pick-up with switch for record compensation, double negative feedback circuit to minimise distortion generated by speaker. Has fitted plug to supply 6.3 v. 3 amp. L.F. and 300 v. 30 M.A. H.T. to a mixer or feeder unit. Price £18 0 0  
Case for above model, Price £3 0 0.

We very much regret that owing to increased costs we are reluctantly compelled to advance the above prices by 10% on orders placed as from July, 1st.

**Dealers and Export Agents** should write for special terms to:—

**VORTEXION LTD.**

257-261, THE BROADWAY,  
WIMBLEDON, LONDON, S.W.19

Telephones: Liberty 2814 and 6242/3.  
Telegrams: "VORTEXION, WIMBLE., LONDON."

### Letters to the Editor—

one class (the pulses having constant amplitude and duration, and in the unmodulated condition,  $n$  of said pulses, where  $n$  is a number equal to or greater than unity, periodically occur during successive equal time periods) is time modulated in accordance with a modulating intelligence in such a manner that, over a succession of the successive equal time periods, the number of pulses of said class occurring during one or more of said time periods varies within the limits  $n$  plus and or minus  $n/r$ , where  $r$  is preferably greater than unity; the pulse train is said to be "Frequency Time Modulated."

(4) When the durations of the pulses of one class (in a train of pulses of the same class, the pulses having constant amplitude) vary in accordance with a modulating intelligence, the pulse train is said to be "Duration Time Modulated." The terms "Width" or "Height" are to be deprecated in this connection. The word "Duration" has been used in this sense for a number of years by earlier workers.<sup>1</sup>

These three systems of time modulation can each be characteristic of the phase, frequency or amplitude of the modulating intelligence. Thus Duration Time Modulation can be characteristic of the phase of a signal, the phase in turn being characteristic of the amplitude.

"Cathode Ray" is in error in saying that Frequency Time Modulation has not been used. In actual fact this is the most widely used system,<sup>2</sup> being in daily use for photo-radio transmission over world-wide circuits. At the receiving station a train of time modulated pulses of constant amplitude and duration has a time modulation which is characteristic of the variable frequency of a signal, this variable frequency being characteristic of the contrast of the picture being transmitted.

Two practical examples of time modulation may be of interest. When riding in a train running

alongside a row of equally spaced fence posts, the apparent spacing of the posts can be modulated by turning the head quickly in the direction of travel, giving the effect of closer spacing, while turning the head quickly in the opposite direction gives the effect of wider spacing.

Again, when travelling in a train, and when passing a station name board at such a speed that it cannot be read in the normal manner, sometimes it is possible to read the name if the head is turned quickly in the opposite direction to that in which the train is travelling.

"Cathode Ray" is wrong in saying that a road sweeper would have missed his vocation if he indulged in some form of frequency modulation in his disposal of refuse.

I remember that in the days of unsurfaced roads, in a small country town, it used to be the practice to sweep the mud into small heaps of fairly constant size but spaced according to the amount of mud, this varying on different parts of the road. After a suitable interval for draining away surplus water, a horse-drawn cart travelled at walking pace alongside the mud heaps, two men walked alongside and without stopping the horse shovelled up the small heaps of mud into the passing cart. The shovelling energy, over equal periods of time, varied in accordance with the frequency of the heaps.

W. A. BEATTY.

London, W.13.

*The author of "Pulse Modulation replies as follows:—*

I AM grateful to W. A. Beatty for the information that pulse frequency modulation is widely used.

With regard to the terms for different kinds of pulse modulation, he proposes to add one—"Time Modulation"—to cover the three types that I called "Pulse Phase Modulation," "Pulse Frequency Modulation" and "Pulse Length Modulation." If such a term is wanted, I hardly think anyone will quarrel with the choice of the word "time" for the purpose. I can't quite see, however, why it is necessary to drag in the same word in all three sub-types too; surely "phase," "frequency"

and "duration," in this connection, imply time? The word "pulse," which I used instead, really is necessary, to distinguish them from C.W. systems. W. A. Beatty's substitution of "time" for "pulse" seems to me a change very much for the worse. But I entirely approve "duration" instead of "length," and perhaps weakly used the latter because "Pulse Duration Modulation" seemed rather a mouthful. These things always become abbreviated to letters, however, and "P.D.M." is not only technically more precise but less liable to be confused with a well-known French railway company than "P.L.M."

I would have liked Mr. Beatty, or anyone else to comment on my one original suggestion—"wave pulses." There is a crying need for such a term, because as far as I know there just isn't one at all at present to refer to groups of R.F. waves. They are commonly called "pulses," which is obviously wrong and very liable to confuse.

I didn't intend to suggest that the frequency-modulating road sweeper wouldn't be excellent at the job, but that he ought to be in a more intellectual one!

Readers who may practice time modulation in railway compartments should, I suggest, take care that their gestures are not misinterpreted. "CATHODE RAY."

### "Tropicalizing"

THE treatment applied to radio components to render them suitable for tropical use is a problem faced by many of your readers during the war, and is of importance in Britain's export drive. In components such as transformers and chokes, it is essentially the problem of preventing the corrosion of metal parts and guarding against mould growth in windings, etc. This latter is frequently dealt with by processes of vacuum impregnation with suitable varnishes, the essential purpose of which is to prevent the ingress of moisture. It is recognized that such a method is not always successful, and I think that some of my observations during my work in the high vacuum field may throw some light on the mechanism of such failures.

Reference to my letter in

<sup>1</sup> "Proposals for Television and Broadcasting Transmission Systems," W. A. Beatty, *Journal Brit. I.R.E.*, March-April, 1945. Bibliography gives a number of references to time modulation.

<sup>2</sup> "Facsimile by Sub-Carrier Frequency Modulation," R. E. Matthes and J. N. Whitaker, *R.C.A. Review*, October, 1939.

*Nature*, dated 5th Jan., 1946, supporting the experimental work of Dr. Reekie, (*Nature*, 156. 367 (1945)), shows that very fine channels of the order of  $10^{-3}$ mm, and under, will admit water in preference to air, owing to the high pressure due to the surface tension of water. Thus it might be that imperfections in the impregnation would admit either water or air, or both. It seems significant that the better the impregnating process, the more likely it is to leave the finer leaks which admit water only. This moisture is not likely to be expelled by the heat generated in the coil during service.

The answer, therefore, seems to be either to seal the component hermetically, or to adopt an open construction. For tropical use the former is the only solution; while for temperate climates the latter might be cheaper and better, as any moisture entering the coils would automatically evaporate owing to the warmth generated during service.

At the very high pressures developed by surface tension and osmosis the question of vacuum becomes meaningless when dealing with the risk of very small channels of the order indicated. It might be worth while inviting the observations of your readers, who may perhaps be able to throw even more light on this subject.

Reading. O. P. SCARFF.

#### MANUFACTURERS' LITERATURE


Bulletin No. 42, issued by Aero Research, Duxford, Cambridge, describes the part played by Ardus cement in the construction of the Mark IV land mine detector. It also gives some particulars of Ardus 120 for bonding metals and other non-porous materials to wood, laminated sheet, etc.

Data sheets for "Midgetron" valves for hearing aids and portable receivers have been received from Park Royal Scientific Instruments, 52, Minerva Road, London, N.W.10.

Specifications of a constant-voltage high-tension supply unit (Model 101-A) and a high-voltage test set (Model 301-A) are given in illustrated leaflets issued by All Power Transformers, 8a, Gladstone Road, Wimbledon, S.W.19.

Technical details of the "Lectrona" permanent magnet loudspeaker and output transformers are given in a leaflet issued by Edstone, Ltd., 41, Spencer Street, London, S.W.1. The 8-inch diaphragm is provided with a dustproof centring device.

## *Bulgin Components in*

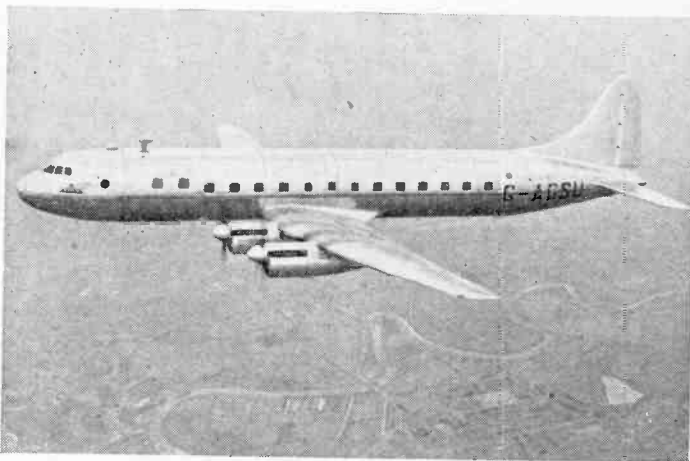

## *Britain's Greatest Air Liner*

The Avro Tudor II is making aviation history. Huge in size, with a wingspan of 120 feet and a length of 105 feet, the Tudor II is the commercial air liner of the future, bringing the capitals of the world within easy reach of Britain. Precision-built to the last detail, this flying giant incorporates every modern accessory, including components by BULGIN. Switches and signal lamps by these famous makers play their part as they did in the mighty bombers of the R.A.F. That battle record and the skill and research of twenty-five years are behind every component that bears the BULGIN name.

★ *Bulgin Toggle Switches available in over 200 standard types from light to heavy duty.*


★ *Bulgin Signal Lamps in 36 types from miniature to wide vision-angle panel mountings for button-neons or M.E.S. bulbs.*

# BULGIN

*A name Famous in Radio  
for over 1,000 Components*

A. F. BULGIN & CO. LTD · BYE PASS ROAD · BARKING · ESSEX

Telephone: RIPPleway 3474 (5 lines)

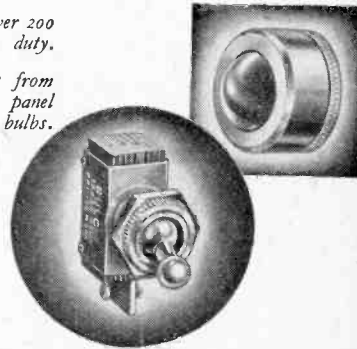



# RECENT INVENTIONS

## CAVITY RESONATORS

**A** BI-METALLIC plate or strip, which flexes under the action of heat, is arranged to alter the shape, and therefore the tuning, of a hollow resonator. The device may be used to offset any frequency drift, due to ambient changes of temperature, or to the heat generated under working conditions.

The tuning of a resonator mounted inside a sealed electron-discharge tube, for velocity modulation, can be adjusted within limits by deliberately applying heat from an external battery to the bi-metallic control element.


*The M-O Valve Co., Ltd.; N. L. Harris; and J. W. Ryde. Application date, April 22nd, 1940. No. 574934.*

## RADAR PRESENTATION


**R**ELATES to equipment for assisting a fighter pilot to detect and close in on an enemy craft, at night, or under conditions of bad visibility.

Exploring pulses are radiated, and the echo signals are presented against the time base of a cathode-ray tube to indicate the distance of the enemy craft, in known manner.

The incoming echoes are picked up by four separate aerials, which are respectively selective to directions above and below, and to the right and left of the axis of the pursuit plane. For part of the duration of each echo pulse, the combined input from all four aerials is applied additively to produce a distance-indication along the time base of the C.R. tube. During the remainder of each echo pulse, the directive effect of each aerial is brought

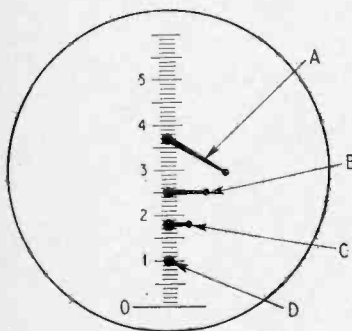

(a)

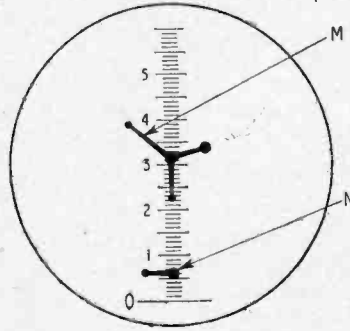

(b)

Target indications in airborne radar

into play, the voltage difference between the up and down aerials being applied across one pair of deflecting plates, and the difference between right and left aerials being applied to the other pair of plates. The trace thus produced on the fluorescent screen will then show the relative position of the hostile craft, as well as its distance.

In diagram (a) the indication A shows the presence of a craft nearly four miles away, to the right, and

## A Selection of the More Interesting Radio Developments

slightly below the pursuit machine. B, C and D show subsequent indications as the fighter banks to the right, and closes on its target. In diagram (b) the trace M represents a flight of three enemy machines, about three miles away. One lies straight ahead, and a little below, whilst the other two are above, one to the right, and one to the left. The indication N shows a friendly escort, nearly a mile away, flying on a level with, and to the left of the pursuit plane.

*Standard Telephones and Cables, Ltd. (assignees of E. Labin). Convention date (U.S.A.), March 13th, 1941. No. 574676.*

## GRAMOPHONE REPRODUCTION


**W**HEN recording sound, it is usual to contract or reduce the amplitude of loud passages, and to increase that of quiet passages, the correct balance being restored in reproduction by applying a suitable expansion control to the gramophone amplifier. Although one setting of the expansion control is usually sufficient to play the whole of any given record, different records may require different settings. In this respect, however, all records fall within one or other of a few distinct groups.

the appropriate degree of expansion control to the amplifier.


*The British Thomson-Houston Co., Ltd., and A. P. Castellain. Application dates, August 24th, 1943, and January 13th, 1944. No. 574557.*
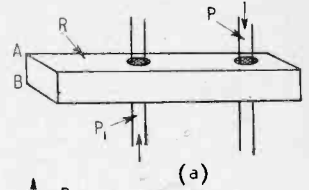
## GENERATING MICROWAVES

**A**N electron stream is passed twice through a hollow resonator R, diagram (a), first at P and then at P<sub>1</sub>,



(a)

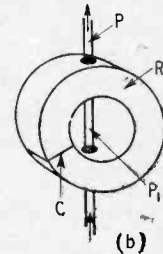

(b)

Cavity resonance generator

in the direction of the arrows. Any lack of uniformity in the stream as it enters will be sufficient to impulse the resonator, thus velocity-modulating or "bunching" the outgoing stream, which then provides inductive feedback as it re-enters at P<sub>1</sub>.

The intensity of the internal electric field varies sinusoidally from zero at both the closed ends to a maximum at the centre of the resonator, so that the degree of feedback is determined by the position of the low-potential entry at P relative to the high-potential entry at P<sub>1</sub>. The output is drawn off by a small loop (not shown) inside the resonator.

By bending the resonator into a ring, as shown in diagram (b), with the two closed ends abutting at C, the same effect is secured without having to divert the electron stream. Alternatively, the resonator may have the shape of the letter J, so that the stream can pass straight through electrodes at the upper end of the short limb and at the lower end of the long limb.

*Patelhold Patentverwertungs- und Electroholding A.G. Convention date (Switzerland), September 1st, 1942. No. 573193.*

The British abstracts published here are prepared with the permission of the Controller of H.M. Stationery Office, from specifications obtainable at the Patent Office, 25, Southampton Buildings, London, W.C.2, price 1/- each.

The latest  
circuits  
demand the  
best valves —  
Marconi of  
course!



**MARCONI VALVES**  
The REAL Thing

THE MARCONIPHONE COMPANY LIMITED HAYES, MIDDLESEX

## OUR NEW BARGAIN LIST

This New List gives details of many selected New Lines which we have just purchased from Government departments. All are perfect and clean components and apparatus (we refuse to buy rejects, scrap or dump material). Our purchases include the following:—

**SMOOTHING CHOKES.** YAXLEY TYPE SWITCHES, 2-pole, 6 positions. **AUDIO TRANSFORMERS** Mu Metal cores. **ROTARY CONVERTERS** 12v. output 300v. 70 ma.; also some 400v. 60 ma. **SELENIUM L.T. RECTIFIERS**, several types. **MICROPHONES**, 4 types, including Hand Microphones. **DIALS**, H.R.O. type. **MORSE KEYS**, etc., etc.

*If you are interested in any of the above, or would like a copy of our New Bargain List "W," please send us a stamped addressed envelope.*

### HERE ARE TWO MORE EXCELLENT BARGAINS

#### CANADIAN TRANSCEIVER No. 58

An 8-valve Superhet and Transmitter complete with power supply, 3 aerials, 2 pairs of headphones, 2 crystal differential microphones, and full instructions. A **WONDERFUL BARGAIN.** Brand new in maker's cases. Cost £100. **OUR PRICE is 13 Gns.**

#### R.A.F. 1154 TRANSMITTERS

Complete with valves, but require a power pack. Covers the 'Ham' bands. These transmitters are secondhand but are in good condition. Excellent value. **OUR PRICE is 6 Gns.**

**READY SHORTLY.** A New Range of 'RAYMART' Super Transmitting and Neutralising Condensers.

Don't forget to send us a stamped addressed envelope for our New Bargain List "W."

**RADIOMART**  
C. S. (GRAM) LTD.

**48 HOLLOWAY HEAD, BIRMINGHAM, 1**

# R & A

*Suppliers of Loud Speakers  
to Britain's foremost  
Radio Manufacturers.*

REPRODUCERS & AMPLIFIERS LTD.  
WOLVERHAMPTON. ENGLAND.

*Miniature or Midget*

ACTUAL SIZE      ACTUAL SIZE

50%      24%

10 7/8"      10 7/8"


XY 1-4A      XY 0-75A

**NEW TYPES FOR**  
MIDGET RECEIVERS  
HEARING AIDS  
METEOROLOGICAL  
INSTRUMENTS  
ETC.

**HIVAC**  
THE SCIENTIFIC  
VALVE  
BRITISH MADE

**HIVAC LIMITED** Greenhill Crescent. Phone HARROW  
Harrow on the Hill. Middx. O 0895

## "Cyldon" Transmitting Capacitors

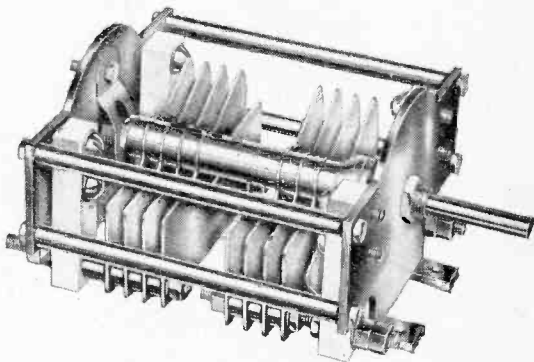

TYPE TRMSS

Max. Capacity	List Price
30 + 30 pF	£1 : 7 : 6 each
60 + 60 "	£1 : 10 : 0 "
80 + 80 "	£1 : 12 : 0 "
100 + 100 "	£1 : 17 : 6 "

**SYDNEY S. BIRD & SONS, LTD.**

Cambridge Arterial Road, Enfield, Middlesex

'Phone: ENField 2071-2.

Telegrams: "Capacity, Enfield."

Rate 6/- for 2 lines or less and 3/- for every additional line or part thereof, average lines 5-6 words. Box Numbers 2 words plus 1/- Press Day 1946 issue, first post Monday, September 9th. No responsibility accepted for errors.

## WARNING

Readers are warned that Government surplus components which may be offered for sale through our columns carry no manufacturer's guarantee. Many of these components will have been designed for special purposes making them unsuitable for civilian use, or may have deteriorated as a result of the conditions under which they have been stored. We cannot undertake to deal with any complaints regarding any such components purchased.

### NEW RECEIVERS AND AMPLIFIERS

**A**R 88s and other types of communication receivers, enquiries invited.—Alert Radio Co., 27 Temple Fortune Mansions, N.W.11, Speedwell 4352. [5755]

**14** watt amplifiers for mike or gramo operation, low intermodulation distortion, 25gns; transformers (bakelite impregnation, special stallo), from £12/6; castings, turning, duraluminium cases and decks to customers' specification.—R.R. Development Laboratories (consulting engineers), Barnard Road, Bradford. [5801]

**F**IDELITY with sensitivity, genuine offer to build 4v T.R.F. ac/dc semi-midget receiver, Litz M. & L. coils, first-class results with improved and tested circuit, diagram and instructions to genuine enquiries 4/6 refunded on kit purchase, complete kit incl. drilled chassis, screws, etc., only £3/15, 6½ in L.S. and trans. with 4 specified valves, £5/12/6.—T. R. S., 35, Meadvale Rd., E. Croydon. [5554]

**K**ITS, kits, 2 waveband, all mains 4 valve, tube line-up, 6K7, 6J7, 25Z6, 25L6, polished aluminium chassis, really first grade components, station named dial, delivered complete to last nut, full wiring instructions; price £7/8, c.w.o. or c.o.d.—Isherwoods, 81, Plungington Rd., Preston, Lancs. Tel. 3348 Preston. Radio repairs est. 1936.

**T**ELERADIO offer following kits: 4-2 wave t.r.f., Mullard E valves, £4; 5v 2-wave t.r.f. battery £3, 3v 4-watt ac/dc amplifier, £2/10; 5v Midget superhet, either long, medium or short wave, £6/10; blueprints with list of parts and instructions, 2/6 (superhet 5/-), all less valves, speaker and cabinet; send 2/6 stamp for further particulars and comprehensive list of components.—Telradio, 157, Fore St., London, N.18. Tot. 3386. [5674]


**B**RIERLEY "Ribbon" and "Armature" pick-ups. Please write your name and address in block letters and include 3/6 for booklet containing illustrations, responsive curves, technical details, delivery and prices. These booklets explain aspects of pick-up design, developments, including the "Boating element" design, leading to the use of ¼ and ½ oz downward pressures; the importance of adequate and constant point pressure and its practical achievement; correct point shape; the relation of pick-up weight, point pressure and vertical motion, etc., etc.—J. H. Brerley, Ltd., 46, Titebarn St., Liverpool, 2. [5701]

**19** 60watt U.D.O. class A rack mounted amplifiers; 6 intermediate voltage amplifiers for use with the above, all aluminium panels, complete with 3in 0.150ma flush-mounted meters in each anode circuit, all complete with valves: 1 3-phase 400v motor generator, 5.5kw (750v) dc output, for supplying h.t. for above amplifiers; also 1 3-phase 400v motor generator, 500v, 2.5 amp dc output, suitable for radio relay station or amateur transmitters.—Further details or inspection at J. S. Ramsbottom & Co., Ltd., radio and electrical engineers, Bow St., Keighley. Tel. 3774

**E**XCEPTIONALLY high fidelity amplifiers. Incorporating the new cathode follower output circuit and flexible bass and treble tone control, now available for home constructors; to music lovers these amplifiers set a new high standard of reproduction; 7watt and 3watt amplifiers and radio tuner unit; full drawings and point-to-point wiring diagrams 2/6 each, 5/- the set of three; separate components or complete kits of parts for all units available, including ready drilled chassis. Send stamp for details and price lists. All types of components available c.o.d.—Send your requirements (post only) to Charles Amplifiers, 14, Lupetons Gardens, Kington, Middlesex.

**R**ECEIVERS, AMPLIFIERS—SECOND-HAND EDDYSTONE 358 communications, new condition; best offer accepted.—Box 1104

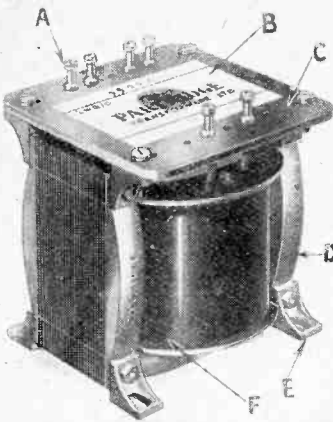**N**ATIONAL H.R.O. Senior with ac power supply and full set of nine coils in case. all in new condition; £55.—Harris, Strouds, Bradford, Berks. [5703]



## PARTRIDGE Precision Built TRANSFORMERS

famous for their high electrical performance also incorporate the following external features:—

- A** Silver plated turret terminals giving a low potential drop and carrying up to 15 amps. Adequate room on each for easy soldering of several external circuit wires.
- B** Permanent indelible marking of terminals by means of a transfer.
- C** Laminated plastic panel of the highest electrical grade.
- D** Firm clamping of the laminations by means of scientifically designed pressure die-castings with a large margin of strength.
- E** Fixing feet interlocking with the clamps so as to provide horizontal or vertical mounting.
- F** Bobbin with flanges of optimum shape for the protection of windings and location of the outleads.

It should be noted that accurate fixing centres and overall dimensions are ensured by close manufacturing tolerances.

Partridge transformers can be wound to suit individual requirements, Precision Built from standardised parts.

Telephone:



Abbey 2244

## PARTRIDGE TRANSFORMERS LTD

76-8, PETTY FRANCE, LONDON, S.W.1

**H**ALLICRAFTER S-20-R, as new; £30 or near offer.—43, Nightingale Rd., Carshalton, Surrey. [5676]

**P**YE television receiver, complete unit without case but with aerial and suppressor; offers.—Box 1092. [5721]

**H**ALLICRAFTER Skychief, new valves, EF50 preselector; offers.—Write, 1, Hurstcourt Rd., Sutton, Surrey. [5769]

**A**C.S. HATHO, 44, Widmore Rd., Bromley, Kent, offer small selection com. sets, radio receivers and amplifiers; list free.

**G**E.C. 6-volt receiver, 12-550M, 4 ranges, 2 watts output, £20; quantity s.w. components.—Isley, Waterworks, Andover, Hants.

**S**ALE.—National H.R.O. receiver with crystal gate, practically unused, complete with speaker, 6v power pack, coil range 0.05-30 meg.; reasonable offer.—Box 683. [5640]

**R**A.F. 1155a, modified, with power pack, 8 spkr., 'phones, £28; 8-valve commercial relay rec., covers 150kc to 21mc, £18.—Gosning, 23, Nottingham Place, W.1. [5864]

**H**R.D. and power pack coils, Eddystone 358x, McMurdo silver, Cossor double-beam oscillograph, 343 Cossor oscillator, Av0.7, Av0.40, 807 valves; amateur giving up.—Box 1091. [5719]

**R**.C.A. A.R.88 communications receiver, as brand new 14 valves, 550K/cs to 33 M/cs, 2 complete spare sets valves; free delivery by road anywhere in England.—Offers over £25 to Box 967. [5690]

**A**RMSTRONG 9-valve 4-waveband chassis, push-pull output, separate power pack with super quality output transformer feeding the PX4's into Vitavox 12in speaker, superb quality; £21 the lot.—Box 1537. [5799]

**Q**UANTITY radiogram kit, partly assembled, all cert. new, complete, valves, circuit, W.V., q. 8w, amp, 3-wave superhet with pre-amp, tun. ind., massive power pack, also el. gr. motor, Baker's 12in 3-cone eng. spkr.; £40 or offer, must sell.—Box 936. [5682]

**A**MATEUR wishes to dispose of all his equipment, including signal gen. meters, transformers, valves, two communication receivers by Hallicrafter, also 1155B converted and with power unit 20 and 4-watt amplifiers, 12in and 18in speakers, etc.—Irish, 144, Adelaide Rd., London, N.W.3. [5722]

**18**-VALVE Scott radiogram, 230 volts A.C., remote tuning, mixed record changer, 4 to 2,200 metres unbroken, variable selectivity, contrast expansion, bass and treble controls, recording channels, magnificent modern cabinet, perfect condition; £175.—Crampin, Watham, Lincolnshire. Tel. 2265. [5653]

**R**1155 R.A.F. receivers as described in *Wireless World* last month, excellent condition, £15; can be supplied modified for civilian use, receivers already purchased expertly modified to your requirements, and amplifier/power packs supplied.—R.T.S., Ltd., 8, Gladstone Rd., Wimbledon, S.W.19. Tel. Lib. 3303. [5659]

**4**-WATT Hi-Fi ac gramo amplifier in steel case, £6; Rola 8in P.M., unused, suit above; 8in energised with X-10, former unused, £1; superhet kit, hand coil, 2-gang condenser, dial, 2 i.f.t., new, £3; Klaxon worm reduction motor, adaptable for recorder, £3; magnetic cutter 600Ω, 30/-; offers considered.—Ellis, 55, Chalkhill Rd., Wembley, Mdx. [5711]

**TEST EQUIPMENT**  
**C**OSSOR Model 343 ganging oscillator; £35.

**C**OSSOR Model 3589 impedance bridge; £18.

**M**ULLARD oscilloscope Model 3152/65; £50.

**A**UTOMATIC coil winding, Douglas wave winder, complete with motor and gears; £75.—Box 1090. [5718]

**F**.D. COSGROVE, radio and electrical equipment engineers, are now producing various types of radio and test equipment; details free on request.—185, Langley Rd., Slough, Bucks. [5369]

**O**SCILLOSCOPE.—Constructor offers drawings and full instructions to build your own oscilloscope; all details of circuit, components values and lay-out. 3/6-2.00. Malzeard Rd., Luton. [5569]

**C**OSSOR 339 oscilloscope, £25; Linaglow sig. generator, £14; radio wave valve tester, £15; Ferranti testmeter, £7; 0-259 microammeter, £2; 0-5 milliammeter, £2, 0-100 milliammeter, £2; all as new.—BM/TPR, London. [5686]

**S**TABILISED power supply unit, comprising three independent outputs up 1,000v, 250 ma dc, 300v 5ma, different ac low voltages, bias voltages up 40v, etc., in black crinkle finished ventilated steel case, available in limited quantities.—Box 1308.—£768

**V**OMETERS.—Model No. 7, £19/10; Universal Avominors, £8/10; dc Avominors, £4/4; B.P.L. signal generators, £21; c.w.o.; immediate delivery; bridges, valve testers, quick delivery; please state requirements.—Young, Radio Service, Southwick, Sussex.

**LASKY'S RADIO**  
**EVERYTHING FOR THE HOME SET**  
**CONSTRUCTOR, AMATEUR RADIO**  
**EXPERIMENTER, TRANSMITTER AND**  
**SERVICEMAN.**

**COILS.**—Long- and Medium-wave, with reaction and circuit, 8/6 per pair. Long-, medium- and short-wave superhet coils, 2s. and osc. with circuit, 10/6 per pair. Wierle "F" coils, P.A.I., P.O.I., P.H.F.I., P.O.Z., P.O.S., P.A.S., P.A.T., etc., 3/- each. Wierle Midget, I.F. Transformers, 4/6 Kc/s, 10/6 each; 21/- pair. Weymouth all-wave coil pack, with all switches, padders, trimmers, with superhet circuit, 38/6 complete.

465 Kc/s I.F. Transformers, 15/- per pair. All-wave coil pack, complete with switch, padders, trimmers, gang condenser, dial and drive, circuit, 50/6.

**YAKLEY TYPE SWITCHES.**—4-pole, 2-way, 2/9. 2-bank, 4-pole, 11-way, 3/11. 4-bank, 2-pole, 6-way, 2/9. Single-bank Midget, 3-pole, 2-way, 2/6. Single-bank Midget.

**CONDENSERS, ELECTROLYTIC.**—500 v.v. Midget cans, 8 mfd., 3/-; 10 mfd., 4/6. 8 x 8 mfd., 5/6. 4 mfd., 4/0 v.v., 3/4. 4 mfd., 400 v.v., 3/9. 1 mfd., 8,000 v.v., tubular, 10/6 each.

**P.M. MOVING-COIL SPEAKERS.**—8in. Plessey, with O/trans., 27/6. 8in. R. & A., with O/trans., 32/6. 6in. Celestion, 23/6; 2 1/2in. Celestion, 27/-; Goodmans, 3 1/2in., 29/6; 6in. R.A., 23/6.

**VITAVOX.** 12in., K12/10, 15 ohms, 26 19s. 6d. RADIO VALVES.—We carry a very large stock of all types. American: metal and glass, G.T., G. U.X., etc. English: Mullard, Mazda, Tungstram, Cossor, Britmar, etc. All at B.O.T. prices. Send us your requirements.

**TERMINALS.**—4 B.A. brass, 5/- per doz. 4 B.A. chrome insulation, 7/6 per doz.

**VIBRATORS.**—6-volt, 4-pin, 12/6; 12-volt, 4-pin, 15/-.

Send id. for our Current List. All Goods sold covered by our Guarantee. Money refunded if dissatisfied.

**OUR AIM: SATISFACTION AND VALUE.**  
**TERMS: CASH WITH ORDER, PRO-FORMA or**  
**C.O.D. (No C.O.D. under £1 0s. 0d.)**

**LASKY'S RADIO**  
**370, Harrow Road, Paddington, W.9**  
 (Opp. Paddington Hospital). Phone: Cunningham 1979

**FOR sale.** Weston Analyzer 772 (20,000 o.p.v.). Yankee valve voltohmmeter. Avo's, etc.; no fancy prices.—BCM/METERS, London, W.C.1. (5651)

**COMPREHENSIVE** Mullard Universal test equipment as used by makers for all American and English types to latest 14v. includes 525 punched bakelite cards with data, quick push-button control, self contained for all possible radio tests; nearest offer 265.—Woodcroft, Merdon Ave., Chandlersford, Hants.

**FOR sale,** thermionic voltmeter Moullin patt. D, Wheatstone bridge Gambrell, millivoltmeter Unipivot, Cambridge & Paul, and various multipliers for same; micro-ammeter, 0-15, Onwood; electrometer, Dolazalek; galvanometer, mirror; also a number of other electrical instruments; all these instruments are in very good condition; view by appointment after 7 p.m.—Wilson, 22, Ashcombe Ave., Surbiton, Surrey. [5789]

**DYNAMOS, MOTORS, ETC.**  
**M.G. set,** input 1/4hp 230volts, single phase, 50 cycles, 1,440revs, output 10volts 8amps dc; £10 or nearest offer.—Box 1364.

**BATTERY** chargers for home and export. B 4 models 2-6.12v, 1, 2 or 4amp dc, any mains voltage; generous trade terms. Write for catalogue. Tel. Hoddesdon 2659.—The Banner Electric Co., Ltd., Hoddesdon, Herts.

**ROTARY** converters, E.D.C. 180 watts, R 110v dc to 230v ac, £14; Crypto 300 watts, 220v dc to 230v ac, £17; Crompton 1,500 watts, 250v dc to 110v ac, £25; several others.—Harris, Strouds, Bradfield, Berks.

**TUNER** unit, 16-50, 200-550, 800-2000. 3 valves, dial, etc. £6/10; ac/dc or ac out put units, ac/dc, 2 valves, £2/10; ditto, 4 valves, 8 watts, £3/15; power units, ac/dc, Barreter rectifier, £2/10 chassis to take 3 units, 6/-; speakers, 8in., 27/6; 6in., 24/-; sheet aluminium, 16g., 2/6 sq ft, cut to size; chassis made to order.—R. T., 64, St. Leonards Rd., S.W.14. [5796]

**NEW LOUSPEAKERS**  
**£5 18/6.**—New Baker Super Quality 12in Auditorium permanent magnet speaker with triple cone, manufactured by Bakers Selhurst Radio, the pioneer manufacturers of moving coil speakers since 1925, wide frequency range, even response, ideal for quality reproduction, fitted with magnet, having exceptionally high flux density in the air gap.

When suitable for public address equipment, when quality reproduction is first consideration; send 2d. stamp for leaflet giving details of new acoustic chamber designed to extend loud speaker frequency range.

£2/19/6.—New Baker super power cinema permanent magnet speaker with 18in triple cone of new design, giving wide frequency response free from objectionable resonances; speech is clear and natural and music is reproduced with exceptional realism; fine engineering job, extremely sensitive; ideal for public address equipment when power handling capacity, plus realistic reproduction, is required; prompt delivery per pass train.—Bakers Selhurst Radio, 75, Sussex Rd., S. Croydon (Croydon 4226).

**LOUDSPEAKERS, SECOND-HAND**  
**12** in Goodmans, £3/10; K12/20 Vitavox, £5/10.—R. K. Wilson, Alnwick. [5772]

**MAGNAVOX** 66, 2,000Ω, rectifier; offers.—113, Hazel Rd., Huyton, Liverpool. [5715]

**VOIGHT** light twin, with rectifier; offers.—Pearson Coupe Green, Houghton, Preston.

**GRAMOPHONE AND SOUND EQUIPMENT**  
**THE** CDP recording machine, £25 complete; please write for details.—Bourne Instruments, Bourne, Lincs. Tel. 224. [5759]

**PRESTO**, Junior, portable disc recorder, new condition, microphone, blanks, etc.; £35.—"Strathdee," Studley Rd., Torquay [5738]

**COILS** for "W.W." tone control and filter circuits (Brierley & Hartley spec.), high fidelity, mic. line and output transformers; s.a.e. full list.—R. Clark, 30, Langland Cres., Stanmore, Middx. Wor. 5321. [5685]

**EXPERT** non-metallic needles.—We have over twenty-five years' experience in the selection, grading and special treating of Thorn needles; for use in pick-ups; type A thick, type B thin, 3/- per 10, including purchase tax; sharpener, 7/4; guaranteed harmless to the record.


**EXPERT GRAMOPHONE & RADIO, Ltd.** Ingerthorpe, Great North Rd., London, N.2.

**PROFESSIONAL** recording equipment, MSS recording machine, 20watt amplifier, complete, £100, new, from stock; blank discs, etc.; full range Sound Sales equipment available.

Garrard transcription motors and plating desks.—Liverpool Sound Studios, 83a, Bold St., Liverpool. [5342]

**HIGH** grade amplifiers of special design for recording, modulation of transmitters, musical instruments, P.A. shortly available. push button operated automatic disc recording machines.—Recordomat Co., Ltd., 19, Exmouth Market, E.C.1. Terminus 7802-3.

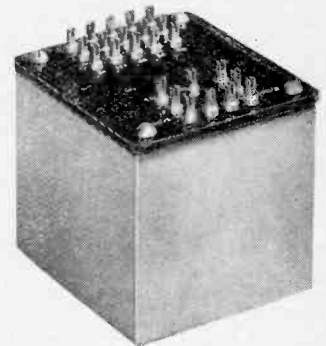**'ASTRONIC'**  
**HERMETICALLY SEALED**  
**TRANSFORMERS**



- Direct fixing to component structure —no strain on container to cause distortion or leaks.
- No unsightly fixing lugs external to container.
- Male or female threads, for upright or inverted mounting at will.

**ASSOCIATED**  
**ELECTRONIC ENGINEERS Ltd.**  
 DALSTON GDNS. · STANMORE · MIDDX  
 Wordsworth 4474-5-6.

e.h.W.S

**YOU**  
**can become**  
**a first-class**  
**RADIO**  
**ENGINEER**

We are specialists in Home-Study Tuition in Radio, Television and Mathematics. Post coupon now for free booklet and learn how you can qualify for well-paid employment or profitable spare-time work.

**T. & C. RADIO COLLEGE**  
**North Road, Parkstone, Dorset**

(Post in unsealed envelope, id. stamp)

Please send me free details of your Home-Study Mathematics and Radio courses.

NAME .....

ADDRESS .....

W.W.51.

The **"PYROBIT"**  
**SOLDERING IRON**

Brit. Patent No. 560,80

for Precision  
**Instrument Work**

Can be operated like a pencil.



With only 45 watts a Bit Temperature of over 300°C is obtained.

for all Voltages from 6—250 volts

**THE**  
**ACRU ELECTRIC TOOL MFG. Co. Ltd.,**  
**123, HYDE ROAD, ARDWICK,**  
 Phone: ARDWICK 428 4 MANCHESTER, 12



**STANDARD** Telephones 4021 moving-coil mike, with table stand, condition perfect; best offer over £30.—Box 987. [5695]

**ADAPT** your silent projector for sound, complete 16mm and 9.5mm precision made sound heads now available for the following projectors: Pathe 200B, Bolex G, Bolex D, Kodascope C, easily attached in a few minutes; 9.5mm model £21, 16mm model £22/10, including P.E.C. exciter, lamp and full instructions; enquiries for other makes invited.

**COMPACT** 15-20-watt amplifier for use with above, £12/17/6, complete with case, ready for use; all sizes of speakers supplied; terms, c.w.o.—A. E. C. Gine, 9. Larbeck Av., Blackpool, Lancs. 5725

**VALVES**

**HUTCHESON RADIO** Cottingham Rd., Hull.

**VALVES**, thousands available, list prices; speakers, Rola 8in. 24/-, Celestion 6in 27/-; volume controls, 3/9, with switch 5/-; electrolytics, 8mfd 450v 4/6, 8x16x16mfd 450v 12/6; resistors, 1/4w 6d., 1w 1/-, 2w 1/6; spanners, King Dick, ring and adjustable. **SEND** list for requirements; guaranteed service; terms, c.w.o., pro forma c.o.d. 5804

4 807 valves, new condition; offers.—Hattie, 76 High St., Johnstone, Renfrewshire.

**OFFERS** wanted for quantity of American Acorn valves, types 954, 955, 956, all unused.—Box 1107. [5751]

1 T4, 955, 9003, 25/- each; 807's, 20/- each, or offers; 6N7's, offers; all new, boxed and guaranteed.—Box 1110. [5752]

1 R5, 1T4, 1R5, 3S4, 25/- each; EP50, 12/10; RL16, 20/-, all unused; 6A3, 10/-.

P625A, 5/-.—Box 1094. [5654A]

**ALL** types of valves supplied, list prices, enquiries invited; voltage regulators, 150/50; gas gap protectors 991.—Alert Radio Co., 27, Temple Fortune Mans., N.W.11 Speedwell 4352.

**COMPONENTS—SECOND-HAND, SURPLUS VALUE!** Matt has it.

**SPECIAL** offers, all new goods.

**VOLUME** controls (Centralab), less switch, 2/6; with switch, 3/6.

**RESISTORS**, 1/2 watt, assorted values, 4/- doz; 0.3 mains droppers, 3/9 ea.

**CAR** radio suppressors; 16/- per doz.

**ROTHERMEL** pick-ups (crystal) de luxe; £2/16/3.

**LINE** cord, 0.3 amp (60 ohms per ft), 2-way 1/- yd, 3-way 2/- yd.

**GLASS** accumulators, 2 volt 45 amp; 10/6.

**SPEAKERS**, Celestion 1/trans, 2 1/2, 3 1/2, 5, 6 1/2, 8, 10in, all t.m. in stock.

**MATT RADIO SERVICE** (Kingston 4881), 15, Richmond Rd., Kingston-on-Thames, Sy.

**SOUTHERN RADIO'S** wireless bargains.

**LATEST** radio publications:

"Radio Valve Manual," equivalent and alternative American and British types with all data 3/6; "Radio Circuits," fully illustrated, receivers, power packs, etc., 2/-;

"Amplifiers," fully descriptive circuits, 2/-;

"Radio Coil and Transformer Manual," 2/-;

"Short Wave Handbook," 2/-; "Manual of Direct Disc Recording," 2/-; "Test Gear Construction Manual," 1/6; "Radio Pocket Book," formulas, tables, colour code, etc., 1/-;

"How to Build Radio Constructors," 1/-;

"Radio Reference Handbook," cloth bound, comprehensive and up-to-date, covering all branches of radio, 12/6; "American Service Manuals," Sparton-Emerson, Crosley-Belmont (Parts 1 and 2), Stewart-Warner-Fada, Emerson, 12/6 per volume; "Radio Resistor Chart," colour codes at a flick, 1/- each; "Bulgin Radio Service Manual," 2/6; "Radio Constructors Manual," 3/-; postage extra.

**YAXLEY** type 2-way rotary switches, 5/6; tubular condensers, 0.1+0.1+0.1 (cans), 2/6; Resistances, brand new wire ended, 1/4, 1/2 and 1 watt, assorted values, 30/- per 100; 1/2 watt only, assorted values, 20/- per 100; 1/2 watt only, 22/6 per 100.

**SOUTHERN RADIO SUPPLY Co.**, 46, Lisle St., London, W.C. Gerrard 6653. [5803]

**UNIVERSAL ELECTRONIC PRODUCTS** (GBOU), 36, Marblebone High St., London, W.1. Tel. WE 4058.

**WE** stock a comprehensive range of the type of components essential to the needs of the amateur transmitter and experimenter, including meters, transformers, waxolin, polystyrene, aerial equipment, Denon and Ramvart products, etc. **Send s.a.e. for lists.**

**OUR** works, under the personal supervision of GBOU, are equipped to undertake the construction of all types of radio and electronic equipment, from an extension spindle or small chassis to a complete 500watt transmitter.

**We** are practical people and amateur enthusiasts are always welcome—call in next time you are in town. [5852]

**ELECTRADIX**

**Headphones—Telephones, etc.**

**HEADPHONES.** Single low resistance phone for circuit testing or house telephone, 60 ohms, bakelite case and cap, best British make, with headband and cord, 8/6.

**High resistance double headphones**, as new, with headband and cord, type S.G.B. light weight, sensitive to crystal, 22/6, delivery from stock.



**HAND COMBINATION** Telephone, Phone and Mike; ebonite body with switch for speech on bell circuit, 6ft. 4-way cord, as new, 15/- (as illustrated).

**SWITCHES.** Dewar panel switches 8-pole, new flush fitting, 5/- each. 8-way ex-R.A.F. switch box, 3/6. 6-way, 3/- G.P.O. Lab. switches D.P.



reversing, for model control motors, etc., 7/6. R.I. 7-stud multi-contact on ebonite panel, teak box base 4 1/2in. x 4 1/2in., 7/6. Linked 5 amp. tumbler, 2/6. Yaxley type 3-pole 3-way, 3/6.

**RELAYS.** Below are some of the types we have available; see your enquiries, we have large stocks all in new condition for immediate delivery. New Siemens Relays, 500 + 1,000 ohms, 2 makes, 10/-; 2 makes I.S.P.C.O., 12/6; 3 makes I break, 12/6. 500-500 ohms S.P.C.O., 10/-; 2000 ohms I break I.S.P.C.O. slugged, 12/6; 10,000 ohms S.P.C.O., 21/-.

Send for Special Leaflet. Relay Contact Assembly, thermal action, 12/6. Siemens High-speed Relays in heavy brass case, £3/5/-.

Telephone type No. 6. 2-coil polarised, S.P.C.O., 6-volts 25 ma., 325 ohms, 8/6. No. 1A, S.P. on-off, 2 volts 40 ma., 5/-.

Relay movements, 1,000 ohms, less blade and contact, 2/6. Moving-coil relays by Weston, Elliott and Sullivan.

**METER MOVEMENTS.** Moving-coil large movement, 7 1/2 ma. full scale, 1st grade type, with pointer, few only at 21/- each.

**Hand MAGNETO GENERATORS.** Output approx. 70 v., 25 ma, A.C. permanent steel magnet, wound armature, driven by gearing in handle, suitable for A.C. experiments, bell circuits, shocking coils, etc., 10/- each, pst'g. 1/-.

**DYNAMOS.** D.C. car type circular body for charging 6 volt 10 amps, £4, 12 volt 10 amps, £4 10/-, 24 volts 10 amps, £10, 30 volts 5 amps, £7/10/-, 80 volts 12 amps, £10.

**AUTOPULSE PUMPS,** 12 volt Petrol Pumps, in new condition, 35/-.

**FANS.** D.C. Table Fans 110 and 220 volt, 10/12in. blade and guard, 45/-; Oscillator type, 12in. blade and guard, 55/-.

A.C. 10in. Table Fans, 65/-.

Fan Motors only, 110 and 220 volt bulkhead size, 35/-.

**BELLS.** Large Tangent ironclad bells, 6in. gong, 230/250 volts, A.C., new condition, 42/-.

Circular A.C. Bells, 5/8 volts, 3 1/2in. diam., bakelite base 2 1/2in. diam. metal gong, 6/6.

House bells, bakelite base, with 2 1/2in. gong, 6/9.

Bell Transformers 230/3-5-8 volts, 7/6.

**BZZERS.** Test buzzers, double contact blades for distant signals or converting for vibrators, robust construction, 8/6.

Morse practice buzzers, tunable type in metal case, 7/6, or bakelite case, 3/6.

Tiny Townsend high note vavemeter buzzers, platinum contacts, 10/-.

**G.P.O.** Connection strips of solder dials, telephone type moulded mounting 60-way, 3/6 each.

**MAGNETS.** AC/DC mains magnets, 2-pole 220 volts, 7/6 each. The wonder midget Magnet, alni perm. steel disc, weight only 1/2 oz., 3/4in. dia. 3/4in. thick with 3/16in. centre hole, 3/6 each. Large selection of horseshoe Magnets in stock. Send for leaflet "W."

**ELECTRADIX RADIOS**

214, QUEENSTOWN ROAD LONDON, S.W.8

Telephone: MA CAulway 2159

**FOR** sale, H.R.O., M.F. and L.F. coils.—Box 1106.

**RADIO CLEARANCE** Ltd., 27, Tottenham Court Rd., W.1, Museum 9138.

**MAINS** Trans 300-0-300, 110ma, 5v 2a, 6v 3a, 22/6; Electrolytics, 2mf 250v, 1/9; 4mf 350v, 2/-; 4mf 500v, 2/11; 8mf 500v, 3/3; 16mf 500v, 4/-; 32mf 250v, 3/6; 20mf 150v, 2/9; 20mf 50v, 2/-; 40mf 50v, 2/6; 200mf 12v, 2/-; 250mf 25v, 2/-; 500mf 12v, 2/6; Mansbridge Condensers, 1mf 350v, 9d.; 2mf 400v, 1/6; 4mf 450v, 4/-; 0.5mf 400v, 6d.; mica, 0.0001-0.0005, 4d.; 0.002-0.007, 5d.; 0.01, 6d.; 0.01-2,200v Test, 9d.

**SILVER** Mica, 50-5000pf, 6d.; Tubulars, 0.01, 0.02, 0.05, 6d.; 0.1, 350v, 7d.; 0.1, 500v, 9d.; 0.25, 500v, 9d.; 0.5, 350v, 1/-; Resistors, 1/4w 3d., 1/2w, 4d.; 1w 6d., 2w 10d., 3w 1/3, all values.

**ALIGNED INSTRUMENTS SERVICES.** 25, Park Grove Rd., Leytonstone, E.11. Tel. Leytonstone 5601.

**ALL-WAVE** superhet kit, 16.47, 200-550, 800-2,000 metres, a.v.c. high "q" i.f.a. ext. i.s. and p.u. sockets, 8in spkr., uses model 20 coil pack, fully aligned and tested, ac model, £12, ac/dc, £12/10.

**MODEL** 20 coil pack, aligned and tested, only 5 connections, 39/6; i.f. trans. 465Kcs, high "q," aligned and tested for gain, 17/6 pair; model 20 tuning heart, fully assembled, with 3 valves, £6/15/10; handsome tuning scale, glass, etc., and s/motion drive for above, 12/6; amplifier kits, really well-designed, ac models, 6watt, £7, 12watt, £11; ac/dc, 5watt, £7, 15watt, £12; tuning units, 3-band s/het type, assembled cpte. with valves, ac or ac/dc, £6/17/6; TRF type, two med. wave stations only, high fidelity design ac or ac/dc, £6; other kits available, send id. for lists, circuit, and tech. data for any above, 2/6; post trade only at present, send c.w.o. if possible—saves clerical work, orders over £5 post free, no c.o.d. under £2.

**TELEVISION.**—New Corsor 44 C.R.T. 6 1/2in white screen, electrostatic, very sensitive, data supplied; £6-66, Crombie Rd., Sidcup.

**HENRY'S RADIO & ELEC. COMPONENTS,** 5, Harrow Rd., Edgware Rd., London, W.2. Pad 2194, 11ours: 9.30-6 o'clock Mon-Sat., Thurs. 1 o'clock.

T.C.C. and B.I., 8mfd, 500v wkg, 3/-; 8x 8mfd, 500v wkg, 4/-; metal rectifiers, input 200-600v, output 300ma, 30/-; 4mfd, 1,000v wkg., 7/6 each; oil-filled 1mfd, 1,000v wkg., 3/-; oil-filled 2-gang 0.0005 standard condenser with trimmers, 12/6; 4-gang 0.0005 standard condenser, 10/-; Amphenol valveholders, 4-, 5- and 7-pin, English and Mazda Octal, Int. Octal 4- and 5-pin U.X., 9d each, 7/6 doz.

T.R.F. M and L wave with reaction, 8/6 pr. with circuit coils; T.R.F. med wave coil, 5/- pr. with circuit; i.f. transformers, standard 465k/cs, iron cored, 15/- pr.; standard 110 k/cs, small cans, air-spaced trimmers, 12/6.

**RADIOGRAPHIC** Ltd. (B.R.S. 12040), of Glasgow, are forging ahead in getting supplies of vital interest to all radio enthusiasts; keep in constant touch for the latest news of still greater supplies.

**TRANSMITTERS,** transceivers, valves (RX and TX), and all components.

**RADIOGRAPHIC** Ltd. 66, Osborne St., Glasgow, C.5. [5516]

**ALUMINIUM** panels, 18in x 12in, 4/-; 18in A x 8in, 2/6; 18in x 6in, 2/-; 18 gauge, 18in x 8in, 14g, 3/6; post 4d. extra per sheet; aluminium foil, 18in x 8in, 1/3, post pd.; metal speaker grille, 6 1/2in x 7 1/2in, 2/6 post pd.—Fenwick, Dept. P, Gt. Brickkiln St., Wolverh'p'n.

**BUILD** a "super" set "Dorset" all-dry battery 4-valve 3-wave superhet circuit. **USES** latest 1.4 volt Mullard valves; short, medium and long waves; no accumulator; wonderful tone and volume; price 5/-; theoretical circuit only with price list, 2/6d.

"DORSET" 5-valve 3-wave ac superhet circuit, price 5/-; theoretical circuit only with price list, 2/6d.


**ABSOLUTELY** the finest sets of drawings and instructions ever produced for the home constructor; six pages of full size drawings, point to point wiring instructions and parts list; we supply 3 wave coil pack, group board and chassis specially designed for the above two sets.

**ALSO** "Wizard" 4-valve TRF medium wave with conversion for long wave ac/dc circuit, 5/-; "Dorset" amplifier 6-8 watt ac/dc circuit, 5/-.—Weldona Radio Accessories, Ltd., Swanage. [5803]

**RELAYS.**—Unrepeatable offer of best priced type A, 500 ohm, 1 co., 1 3/4 ea.; B, 200, slugged, 1 co., 1 b, 3/- ea.; C, 200 ohm, slug, 1 co., 1 m., 3/- ea.; D, dble. wdg., 500 and 1,000 ohm, 2 m., 2/6 ea.; E, 500 and 1,000 ohm, 1 co., 2 m., 4/- ea.; F, 500 and 1,000 ohm, 3 m., 1 b., 4/- ea.; G, thermal delay, 100 ohm, 1 co., 2/- ea.; H, 10,000 ohm, 1 adj. coil, 6/- ea.; a.a.e. for leaflet; no c.o.d.—BM/RXBF, W.C.1.

# DALY

## ELECTROLYTICS

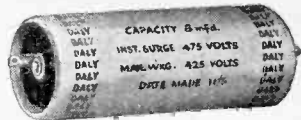

Tube-size 2 1/2" x 1"



Can-size 1 1/2" x 1 1/2"



Block-size 4 1/2" x 1 1/2"

The DALY range covers all requirements

Note—All Condensers bear the date made

### DALY (CONDENSERS) LTD

Condenser Specialists for over 20 years  
West Lodge Works, The Green, Ealing, W5  
Phone—Ealing 4841



## FOR THE RADIO SERVICE MAN, DEALER AND OWNER

The man who enrolls for an I.C.S. Radio Course learns radio thoroughly, completely, practically. When he earns his diploma, he will KNOW radio. We are not content merely to teach the principles of radio, we want to show our students how to apply that training in practical, every-day, radio service work. We train them to be successful!

Special terms for members of H.M. Forces and discharged disabled members of H.M. Armed Forces

**INTERNATIONAL CORRESPONDENCE SCHOOLS**


Dept. 38, International Buildings,  
Kingsway, London, W.C.2

Please explain fully about your Instruction in the subject marked X.

Complete Radio Engineering  
Radio Service Engineering  
Elementary Radio Television

And the following Radio examinations:  
British Institution of Radio Engineers  
P.M.G. Certificate for Wireless Operators  
City and Guilds Telecommunications  
Wireless Operator & Wireless Mechanic, R.A.F.

Name.....Age.....  
Address.....

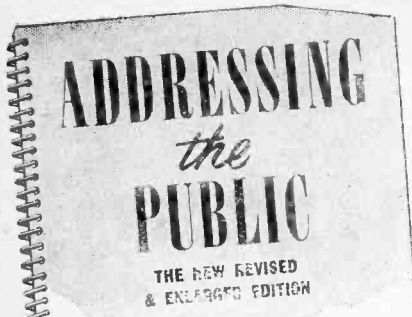

## the fundamentals of PUBLIC ADDRESS TECHNIQUE FOR RADIO ENGINEERS

Devoted exclusively to public address, this handbook deals with the technical and practical problems confronting the public address engineer. Contents include:—Specifications — Distortion — Frequency Response — Gain, etc. — Loudspeaker Location — Feedback — Echo — Time Delay — Masking — Reflection — Wind Effect, etc. — Loudspeaker Matching — Phasing — Impedances — 120v. Line etc. — Microphone Lines — Mixing, etc. Pickup Correction — Filtering, etc. — Operating — Speech Boosting — Background Music, etc. — Appendix Tables, etc.

**PRICE 3/6**  
**POST FREE**



MANUFACTURING CO. LTD., HUNTINGDON TEL. 361

## RADIO CORNER

(Proprietor, T. R. WILLIAMS)

138 GRAY'S INN RD., LONDON, W.C.1

Terminus 7937

**MAIL ORDER.** Delivery by return. THE BANNER CHARGER. Type 1/1, 1 amp, ideal for Motorists, a really first-class job. Input 240 v A.C. Output 2, 6 or 12 v D.C., at £3. Designed for the motorist who likes to keep his batteries in tip-top condition.

**RADIO VALVE MANUAL**, giving American and British Valve Equivalents and Data. Price 3/6.  
**Radio Constructors Manual.** Price 3/-.  
**Radio Tuner Unit Manual.** Price 2/6.  
**Engineers and Electricians Handbook.** Price 1/-.  
**Cathode Ray Oscilloscope Manual.** Price 2/-.  
**Radio Reference Book.** Price 12/6.

**American Radio Valves.** Types as under at controlled prices. 45Z5GT, 5Y3G, 1A5GT, 1C5GT, 1Q5GT, 1T5GT, 80G, 35Z5, at 11/- each. 6J5GT, 12J5GT, 1H5GT, 12S5FGT, at 9/2 each. 6Q7GT, 12Q7GT, 12SQ7GT, 75G, at 11/7 each. 12SK7GT, 6K7GT, 6K6GT, 6V6GT, 42G, 43G, at 12/10 each. 6A7G, 6A8GT, 6K8GT, at 14/- each. Postage paid. Other types as they become available for distribution.

### AMERICAN RADIO SERVICE MANUALS

- Volume 1. Spartan Emerson.
- II. Crosley Belmont. Part I.
- III. Crosley Belmont. Part II.
- V. Emerson. Part II.
- VI. Stewart Warren. FADA.

At 12/6 per Volume, or complete set of six manuals £3 12s. 6d. These Manuals cover the complete range of American Radio Receivers as given and are invaluable and contain all the technical data necessary.

Terms. Cash with Order only. We regret that we are unable to send goods C.O.D.

**COULPHONE RADIO**, Station Rd., New Longton, Nr. Preston.—The returns of Post Mail Order Service. New goods only C.O.D. or cash with order. Orders over 5/ post free. Note prices.

**EDDYSTONE Model 504** communications receiver. Rotational deliveries now commenced.

**ALL** Tungram and B.V.A. valves; list prices. **LINE Cord** 3 amp, 60Ω per foot, 2-way 1/6 yd., 3-way 1/9 yd.; mains droppers, Feet, 2 sliders, 2 amp 4/3, 3 amp 4/6.

**GOODMANS T2/1205/15** 12in P.M. quality speakers, £6/15; Goodmans T10/1501/35 15in P.M. super quality speakers to handle, 25 watts, weight 28 1/2 lb, £18/10.

**1946 AIRMASTER** 5v superhet chassis with 8in M.E. speaker, all ready to switch on; 13/30, 30/60, 200/550, 800/2,000 metres, high-class job; £16/10; carr. paid pass train. **WEYMOUTH** 3-waveband coil packs, completely wired and tested, for 465 kcs, 38/6; matched pairs, iron-cored I.F. trans., 14/6. **TUNING** condensers, Midget 2 gang, 0.0005 mfd, with 2 speed reduction drive and rubber mountings, 16/6.

**MAINS** transformers, - highest quality, primaries tapped, 200/250 volts, 300/0/300, 60 m.a. 4v 3a, 4v 2a or 6.3v 2a, 5v 2a, 17/6; 350/0/350 100 m.a., 4v 6a, 4v 2.5a or 6.3v 3a, 5v 2a, 24/-; bobbins 15/6; 450/0/450 200 m.a., 4v 8a, 4v 4a, 4v 4a or 6.3v 4a, 6.3v 4a, 5v 3a, 42/6; or 6.3v 6a, 4v 2a, 4v 2a, 5v 3a, 45/6.

**EDDYSTONE** short-wave components. **TUNING** units; model A3, R.F. stage, 16/50, 200/550, 800/2,000, completely assembled and aligned with 3-gang condenser, drive scale and escutcheon, £5/15; model B3 as above, but with I.F. stage and D.D. stage, £8/15. Everything from a grid clip to a Vortexion 50-watt amplifier; send 2/6d. stamp for new 12-page catalogue.

**COILS**, high gain t.r.f. combined metal long wave, 2 1/2in long, a really first-class job; aerial and hf, 7/- pair, post paid, suitable switch, 2/3; trimmers, 9d; 2-colour station scale, 1/3;—Aneloy Radio, 36, Ilindmans Rd., E. Dulwich, London, S.E.22. £5379

**B & H. RADIO** offer all sizes of electrolytics, 2- and 3-core line cord, transformers, chokes, volume controls, etc., transformers, etc., made to specification; quality amplifier components and designs; trade only; send for list.—Huntley St., Dartington. £5195

**B**EAUTIFULLY moulded solid oak radio-gram cabinet for sale, size 29in x 18in x 48in high, provision for twin turntables, £15. **Vitavox K1210** loudspeaker on oak pedestal baffle, area 25in x 30in x 1in thick, £15. **Rothermel De Luxe** pick-up and Simpson's turntable, £5. Seen in Surrey.—Box 1034.

**AVO** 7s, new, £19/10; Avo valve tester, A single English panel, £10; Vortexion CP 20, new vib. and valves, £14; B.T.H. Minor P.U., £1; Philips P.U. type 2922, needle hole, new atk., £1/4; 3 1/2 watt amp. with bass boost for gram, £4/4.—Pearce, 56, Gt. Percy St., London, W.C.1. Ter. 4528.

**SANGAMO** Synchronous Motors, self-starting, exceptionally good torque; rotor speed 200rpm, 200-250v ac, 50c, consumption 2 1/2 watts. Size 2 1/4 x 2, geared 1 rev 60 min, can be reset to zero by friction drive from front or back; shaft 3/8 x 1/10, to run clockwise; ideal movements for making electric clocks, time switches, etc.; nickel-plated finish; price 22/6 each; 12 to 1 dial trains to fit above spindle, per set 2/6. **SANGAMO** Synchronous Motors (as above) geared 1 rev 60 sec, ideal movements for making electric dark room clocks, time switches, etc., nickel-plated finish; price 22/6 each.

**CHAMBERLAIN & Hookham** Synchronous Motors (enclosed type), self-starting exceptionally good torque, rotor speed 200rpm, 200-250v ac, 50c, consumption 33 watts, size 2 1/4 x 2, geared 1 rev 60 min, can be reset to zero by friction drive from front or back; shaft 3/8 x 1/10, to run clockwise; ideal movements for making electric clocks, time switches, etc., nickel-plated finish; price 25/- each; 12 to 1 dial trains to fit above spindle, per set 2/6.

**CASH** with order post paid on all above goods. **TO** callers only. A comprehensive stock of scientific instruments, meters, gears, relays, etc. **H. FRANKS**, Scientific Stores, 58, New Oxford St., W.C.1. Tel. Mus. 9594. £5805

**TRANSFORMERS** for every purpose, highest grade workmanship, competitive prices, immediate delivery; microphone, intervalve and P.P. driver trans., O.P. trans. 1 to 60 watts; chokes, all sizes, fluorescent light chokes; mains trans to 2kva auto-trans, 1kva to 2kva (200-250v, 115v and 24v at max. current); test gear trans for bridges, oscilloscopes, valve testers, etc.; list 1d.—Radio Services, Field St. Works, Blackpool. Tel. 1250. £5602

**ELECTROLYTICS.** 8mfid 500v can, 2/10; 1mfid 200v can, 2/-; tubulars, 0.01mfid 1,000v, 1/9; 0.02mfid 750v, 1/3; 1mfid 450v, 1/-; 75 mfd 12v, 1/11; trimmers, airspice 5-50pf, 2/9; Philips 3-30pf, 1/-; line cord, 0.3 amp 190ohms yard, 2-way 1/4, 3-way 1/7; mains droppers, 0.2amp, 1.000ohm 4/-; 0.3amp 800ohm, 4/3; short-wave folding aerials, 5/-, s.a.e. for list.—U.E.I. Corp., 32, St. Gabriel's Rd., London, W.4. (5742)

**RECONDITIONED meters,** moving coil, any range, 5ma to 25ma. 2in 23/-, 2½in 28/6; new moving coil flush meters, 2½in, 100 microamps 66/-, 1ma 42/-, 5ma 38/6; 3, 10 or 150 volts 38/6, 300 volts 42/-; new M.I. meters, 1, 3 or 10 amps dc, 13/6; West-inghouse meter rectifiers, 5ma, 7/6; vacuum mercury switches, 20 amp, 5/-; c.w.o. post free.—R. Massey, 58, Wakefield Ave., Hull.

**METAL rectifiers,** charger kits, microphones, metal rectifier, 12v 2amp, with transformer and ballast bulb for 2v to 12v charger, rheostat or ammeter required, 37/6, post 10/-; ditto, with 3amp rectifier, 46/6, post 1/-; metal rectifier 2v 0.5amp, with transformer, makes ideal trickle charger for 2v cell, 13/6, post 7d; transformer, metal rectifier, ballast bulb for one cell to 20 cell, 1amp charger no rheostat and ammeter needed, ideal for small radio store, £5/5; ditto for 2 amps, £7/5; will handle up to 80 radio cells per week; dc lux transformer and rectifier, 12v 5amp, with lamp for 6v, £4/10; ditto, 4 amp, £3/6; ditto, 3.5amp, 23; ammeters, 0-6amp, 15/- extra on above.

**METAL rectifiers:** 12v 0.75amp, 7/6; 12v 1.5 amp, 10/6, post 6d; 12v 2.5amp, 15/6; 12v 3amp, 21/-; 12v 4amp, 27/6; also rectifiers in stock for conversion of valve type chargers to metal rectification, all types; no surplus goods stocked; H.T. rectifiers, small space, selenium, 250v 60ma, 11/9; 110v 100ma, 11/6; 120v 30ma, eliminator, 11/9; 10v, eliminator, 11/9; heavy duty type transformer, rectifier, two condensers for 120v 25ma output, 32/6; with 2v trickle charging, 39/6, post 10d.

**INSTRUMENT rectifiers,** M.B.S.I., 1 milliamper, 18/6; 5 milliamper for Avo. Avominer, 18/6; 8 mfls 450v and 500v tubular electrolytics, all best makes, not surplus, 3/6 ea; Rothermel "Bullet" crystal microphones for stand mounting, £3/5; Lustraphone m/c mikes, £4/4.—Champion, 43, Uplands Way, London, N.21. Tel. Lab 4457. (57556)

**COTTON covered** copper wire, ¼lb reels, 1s, 2s, 22, 24g, 1 lead 1/6; 1/2 lb, 1/9; 3/8, 1/3; 2/-; 3/4g, 2/3; enamelled ditto, same prices, including 36g, 2/3; 38, 40g, 2/6; 43, 44g available; silk covered ditto, 2oz reels, 24, 26, 28g, 1/6; 30, 32, 34, 36g, 1/9; 40, 42g, 2/-; 44, 45g, 1oz 2/-; 22g d.s.c., ¼lb 2/6; 16g d.s.c., 1lb 5/-; 18g d.s.c., 1lb 7/-; laminated bakelite panels, ¼in thick, 6inx4in, 1/3; 6inx6in, 1/9; 8inx8in, 2/5; 10inx6in, 2/9; 10inx8in, 3/6; 12inx8in, 4/-; ditto, ¼in thick, same sizes, 10d, 12, 1/6, 1/10, 2/4, 2/8; polished ebonite panels, ¼in thick, sizes as above, 1/9, 2/9, 3/6, 4/6, 6/-, 7/-, respectively; R.A. screws, gross useful sizes, 2/6; ditto nuts, 2/6 gr; assorted gross screws and nuts, 2/6; brass washers, 1/6 gr; fibre washers, 1/6 gr; assorted soldering tags, 2/- gr; assorted small eyelets and rivets, 1/5 gr; finest quality straws and single push-back wires, 12 yds 2/3; resin cored solder, 1lb 3/6; heavy insulated aerial wire, 50ft 1/6, 75ft 2/3, 100ft 3/-; lead-in tubes, 4in 9d, 6in 1/-, 9in 1/4; all postage extra; trade supplied.—Post Radio Supplies, 33, Bourne Gdns., London, E.4. (5631)

**THE Simplex Four,** still the best, complete constructional details; Midget AC/DC (total cost of construction £9), theoretical and full scale layout diagrams, with instructions, per copy, 4/6; Midget polished wood cabinets, 35/-; Midget m. wave t.r.f. coils, high gain, 5/-; milled paper condensers, high v wks, small size, 4mfid 1,000v, 7/6; 8mfid 1,000v, 12/6; 8mfid 600v, 7/-; 10mfid 600v, 7/-; midget electrolytic 16x16mfid 350v, 7/-; 16mfid 200v, 3/-; 16mfid 350v, 3/6; all wave coil pack, wired, tested, 5 leads to receiver, boxed with AC/DC circuit, 38/6; Midget ivorine coloured Jials, s.m.l. wave, 4x3½, 2/6; slow motion string drum drive, 3/-; epicycloid drive, 5/3; square plane drive assembly, complete with station named dial, 4½x3¼, m.l. wave, pointer, glass, oxidised escutcheon and mounting brackets, 11/6; full vision ditto drive assembly, size of dial 7x3¼, s.m.l. wave, 11/6; miniature rotary switches, 4p 3w, 4/-; 2p 6w, 2/6; d.p.d.t., 3/-; chokes midget 50ma, 6/-; standard 80ma, 8/6; heavv. 150ma, 12/6; Midget Simplex chassis, fully drilled with four valve holes, etc., 11x4¼x2in, 6/6; monthly comprehensive lists, 2/6d. stamp with enquiries, postage all orders.

**O. GREENLOCK, Ltd.,** 34, Bancroft Rd., Cambridge Heath Rd., London, E.1. Ste 1334.

# LONDON CENTRAL RADIO STORES

**ELECTRIC DRILLS**  
**KILSWAY** jin. special duty Drill, model 141, low speed, high torque. A.C./D.C. 220 v. 3 amps. Up to 60 cycles. Speed 200 r.p.m. .... **£16.10.0**

**CHICAGO PNEUMATIC TOOL CO. 1" DRILL**  
 Model A, size 985, A.C./D.C., 200/230 v. 4.25 amps. Speed 300 r.p.m. .... **£21.10.0**

**SIGNALLING TORCHES**  
 Ex. Admiralty. 3-cell (type 17). Coloured lenses (red, green and amber) easily unscrewed for use as ordinary torch. Powerful beam. Strong metal case. Highly plated 2in. reflector, jin. lens with 3.5 v. bulb and spare bulb. Less batteries **12/6**



**SAFETY CAP LAMP**  
 Bakelite moulded case. Diameter 3in., fitted with double filament 2.5 v. 1 amp. and 7.5 amp. gas-filled bulb, with 2-way switch. Complete with 10 a. hour accumulator in metal case, with webbing head-band and waist strap. Uses alkaline electrolyte solution. .... **£3.3.0**

**FOR FULL TECHNICAL DATA**  
 See Editorial Article July Issue  
**EX.-R.A.F. Type R1155**  
**COMMUNICATION RECEIVERS**  
 Comparatively new. These receivers are made to the stringent specification of the Air Ministry and are fitted with a large-scale dial calibrated from 7.5 mcs to 1,500 kc/s. Complete with 10 valves, including magic eye. Fitted in a strong metal cabinet. They require only a power pack to be ready for immediate operation. .... **£15**

**EX-ARMY No. 58 Mk. 1**  
**Self-contained 8-v. Short-wave TRANS-RECEIVER**

- 5-valve Superhet Receiver, 3 v. Transmitter.
- A.V.C.
- Frequency range: 6 mcs to 9 mcs (50 to 33.3 metres).
- Working range: 5 miles with 12ft. rod aerial.
- Panel Test Meter for check on batteries and various parts of circuit.
- Chassis suspended in case by rubber shock mounts.
- Three aerials in carrier (12ft. rod, 8ft. Gins. Telescopic, 25ft. wire).

**BARGAIN OFFER (less Vibrator) £7**  
 As above but COMPLETE with set of 8 spare valves, spare Vibrator and Fuses, 2 Accumulators, 2 Differential type noise-cancelling Mikes, 2 prs. Headphones, 6,000 ohms, Connecting Cables, and

**VIBRATOR POWER UNIT £15**

8-v. V.H.F. Receivers. 100-125 mcs. Type 7I. Complete with valves ..... **£4.5.0**  
 TRANSMITTER for above. Complete with 7 valves ..... **£3.10.0**  
 3-v. R.F. AMPLIFIERS V.H.F. 100-125 mcs. Type 24. Complete with valves **35/-**  
**EX-ARMY BATTERY 3 VALVE MINE DETECTOR AMPLIFIER PANELS,** size 6in. x 6in. (less Valves). Uses the latest type Baseless Midget Valves. Ideal for use as pre-amp tone unit, etc. Components include 9 tubular condensers, resistors, 3 Ceramic Valve Holders, Midget Transformer, Volume Control and a heavy duty 12-hour ..... **15/-**

You are invited to call and see the stocks of R.A.F. gear we have for sale. It will pay you!

**N.B.** We do not issue lists and cannot deal with correspondence on the goods we offer.

**Closed Thurs. 1 p.m. Open all day Sat.**  
**23, LISLE STREET**  
**LONDON GERard 2969 W.C.2.**

**G. A. RYALL,** 65, Nightingale Lane, London, S.W.12. Mail order only, at present, no C.O.D. under £1 please. Postages extra. U.S.A. make 0.1mf 500v tubular metal cased wire end condensers, 5/- doz. 0.5mf 3 2/-, or 6/6 doz. Resistances, carbon type, best make, ½ watt sizes, 47, 100, 220, 270, 500, 1,000, 2,200, 5,000, 15,500, 50,000, 1.5meg, 2meg, 3/- doz. Best makes 2-watt carbon resistors, 6,800, 36,000, 43,000, 140,000, 150,000, 220,000, 470,000, 820,000, 4/- doz. Good assortment 15 sizes of ¼w, ½w, 1w resistances, at 1/6 doz. and 1,800 wire wound 1/6 doz, 2,200 1/- doz. Vitreous 30ohm and 470ohm, 1/6 doz. Vitreous 4,700ohm 20w with clips, 2/- each. Panels with screened 0.1mf and 12 ½w resistances and condensers, 2/3 each. Set five 30m trimmers on metal base, 1/- Pairs of 10in, Ed. Octal plugs with metal caps 3 1/-, with solder tags 2 1/-; chassis mounting valve holders to suit plugs, 3 1/- Valve holders, U.S.A. 4, 5, 6-pin and British 7-pin and International Octal, all 4/- doz. Miniature 4-pin plugs, sockets, metal caps, 4/6 doz complete. Relays, 150ohm 2v 15ma, 2p, M & B. 1p CO high class ceramic insulation, British make, unused, 5/- each. Volume controls less switches, best makes, ¼meg bakelite cased, ¼meg metal cased, 1meg bakelite cased, short spindles, all 1/6 each; 1meg with 2½in spindle, 2/- Switches, Yaxley type single bank 1p 2-way, 2/5; 10-way, 2/6. Double bank 2p 5-way 2/6; single bank, 2p 2-way, 2/3; three bank 4-way 2p with riddle scrap, etc. 3/9. Rubber ends for wiring completion one inch lengths, with ¼in bore, 250 for 5/- Goods advertised in Aug. issue still available. buzzers, control boxes, meters, power mikes, double phone and mike transformers, Mansbridge 1mf, 2mf, 4mf anchor tags, input strips, screened wire, push back wire, mike and phone sets, etc., all perfect goods. (5841)


**FOR 2/6 you can obtain a set of six large drawings showing construction of under chassis wiring of the "Weymouth" high fidelity receiver; a free circuit is enclosed with every coil pack; this coil pack costs only 38/6; iron cored Litz wound, i.f. colour coded, made for the above, 15/- per pair; immediate delivery.—Castle Radio, 101, Poverest Rd., Orpington, Kent. (5798)**

**MISCELLANEOUS**  
**18 B.I. R.F.E. Jnls.** 30 "W.W.s." '43-46, 30/-;—50, Rowland St., Rochdale. (5688)  
**TIME Recorders**—Write for particulars.—Gleehill-Brook "Time Recorders, Ltd., 84, Empire Works, Huddersfield. (6241)  
**FOR sale,** "Wireless World," Nov. 1939, to Dec., 1935, 6 vols., bound; 6 gns.—109, Collingwood House, Dolphin Sq., S.W.1. (5744)  
**GENTLEMAN** requires competent personal tuition; reasonable fee expected and paid; keen, friendly; London, N.W.—Box 1879.  
**ALUMINIUM** chassis, panels, cabinets, sheet. A finished in colour crackle; s.a.e. lists.—Amateur Radio Service G6HF, Canning St., Burnley. (5715)

**IDEAS mean money!**—If you have an idea we can help you to make the most of it; write at once for full information on the technical, legal and financial services we offer to inventors.—Technico-Legal Services Bureau, 55, Romney St., Westminster, S.W.1. (4948)  
**TELEPHONE** manufacturers and wholesalers.—Telephone hand-sets for intercommunication; complete telephone units for shops, factories and mines; carbon insets, switch keys, jack plugs and chokes; all new material; expert enquiries invited.—Jack Davis, 30, Percy St., London, W.1. Mus. 7960.  
**WANTED, EXCHANGE, ETC.**

**WTD., "W.W."** June 29, July 6, 13, 20, 1939.—Box 1087. (5710)  
**SET** of Monodial coils.—Roberts, 242, May Lane, Birmingham, 14. (5757)  
**WTD.** Hartley-Turner P.M. de luxe speaker.—Clowes, Pesham, Pershore, Wores.  
**WANTED,** R.C.A. or Bell and Howell amplifier—98, North Lane, Coventry. (5687)  
**WANTED,** dr. radiogram, preferably auto, in first-class condition.—Box 1033.  
**URGENTLY** required, February 1946 issue "Wireless World."—Details to Box 1105.  
**GOODMAN'S** infinite baffle speaker.—R. Bidgood, 7, Cranbourne Rd., Manchester, 21.  
**WANTED,** Voigt 1s. units, horns, reflector speakers, any condition.—Lowther Mfg. Co., Bromley, Kent. (5625)  
**WANTED,** H.M.V. hypersensitive pick-up with transformer; state price.—D. Westwood, c/o Napier, Dumfries. (5677)  
**WE** offer cash for good modern communication and all-wave receivers.—A.C.S. Radio, 44, Widmore Rd., Bromley, Kent.  
**WANTED,** several Hivac A15 all-purpose valves, new or second-hand, in good condition.—5, Chorley Rd., Standish, Lancs. (5743)  
**WANTED,** rotary converter, 12 to 36v D.C. input, 200 to 250v, 230w A.C. output with smoothing.—D. Blackford, Tudor House, Calne, Wilts. (5739)

## G.L. TRANSFORMERS

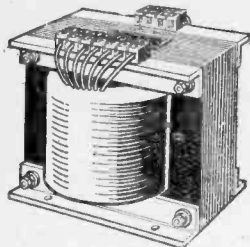

The illustration shows a new design of particular interest to the radio man. Power transformers and audio units are available in twenty varied specifications.

Write for leaflet "CT/7."

### AMPLIFIERS

A.18 Gramo. only, 10 watt .....	£10 7 0
A.23 with HG mike stage, 20 watt ...	£16 4 0
A.36 De luxe, 35 watt .....	£23 16 0

All factory assembled with cases.

2½d. stamp should accompany requests for literature.

## RADIO INSTRUMENT CO.



Radio Products  
294, BROADWAY,  
BEXLEYHEATH, KENT  
Bexleyheath 3021

## The NEW HARTLEY-TURNER SPEAKER

is now ready. It has a far better performance than the pre-war models—wider, smoother response, and greater sensitivity. Every speaker tested personally by H. A. Hartley on music in addition to the usual tests.

Price £8.5.0 without transformer.

Please send for descriptive leaflet.

**H. A. HARTLEY Co. Ltd.**  
132, Hammersmith Rd., London, W.6

## THE NORTHERN POLYTECHNIC, HOLLOWAY ROAD, N.7.

Principal: T. J. DRAKELEY, D.Sc. Ph.D.,  
F.R.I.C., F.I.R.I.

Department of Radio and Musical  
Instrument Technology.

Head of Department:  
S. A. Hurren, M.C., M.Brit.I.R.E.

## Full-time Day Courses in RADIO TECHNOLOGY

in preparation for all  
recognised qualifications in this subject.  
Practical laboratory and workshop experi-  
ence provided.

Prospectus free on application to Secretary  
New Term begins September 23rd

W.T.D. for export to the East, hundreds of wireless sets, ac. dc.—Quilliam Products, 16, Waldegrave Park, Twickenham, Mdx.

RADIO service data sheets, all makes, old and new; also portable P.A. equipment, horn speakers.—B.M.NEN, London, W.C.1.

URGENTLY wanted, cable flex P.V.C. and millimetre wire, all descriptions purchased for cash, any quantity.—Alec Davis, 8, Percy St., W.1.

SERVICE sheets, American and English, any date, wanted, unlimited number; any offer considered.—113, Bignor St., High town, Manchester, 8.

WANTED, Pye 815 television receiver, either working order or set requiring servicing considered.—Price, etc. to R. Street, Roselea, Carlton Rd., Ryde, I.O.W. [5714

WANTED, 24-28v D.C. motor-generator, output 1,200-1,500v, 200-300 mA, also Voigt or Hartley-Turner speaker unit.—Leach, 51, Manchester St., Cleethorpes, Tel. 61997. [5654

W.T.D., solid radiogram cabinet, R.G.D. or similar preferred, also good television; can exchange typewriter, 18ct gold watch, chain, dress suit, service sheets, etc.—Write "Radio,"

6, Charlwood St., Pimlico, S.W.1. [512

FEEDER unit, superhet, variable selectivity, RF stage all ways wanted, new or second-hand, immaterial; also large radiogram cabinet front, uncut, new or second-hand.—Box 1472

WE buy for cash, new, used, radio, electrical equipment all types; especially wanted, radios, radiograms, test equipment, motors, chargers, recording gear, etc.—If you want to sell at the maximum price, call, write or phone to University Radio, Ltd., 22, Lisie St., Leicester Square, W.C.2. Ger. 4447.

### REPAIRS AND SERVICE

MAINS transformer rewound and constructed to any specification; prompt delivery.—Brown, 3, Bede Burn Rd., Jarrow, [3460

ACCURATE radio rewinds, mains transformers, fields, op. transformers, etc.—Southern Trade Services, 297-299, High St. Croydon. [5158

LOUDSPEAKER repairs, British, American, any make; moderate prices.—Sinclair Speakers, 12, Pembroke St., London, N.1. Terminus 4355. [5308

REWINDS and conversions to mains and output transformers, fields, etc. from 4/6. PP equipment a speciality.—W. L. Rewinds, 4, Brecknock Rd., N.7. Tel. Arnold 3390 [5185

ELECTRICAL measuring instruments skillfully repaired and recalibrated, immediate delivery.—Electrical Instrument Repair Service, 329, Kilburn Lane, London, W.9.

"SERVICE with a Smile."—Repairers of all types of British and American receivers; coil rewinds; American valves, spares, line cord.—F.R.I., Ltd., 22, Howland St., W.1. Museum 5675. [575

STURDY rewinds, mains transformers, chokes and fields; we give prompt delivery and guarantee satisfaction; 14 years' experience; prices on request.—Sturdy Electric Co. Ltd., Dipton, Newcastle-on-Tyne. [4316

TELEVISION and radio receiver serviced by certified engineers; Murphy and Pye specialists; amplifiers rebuilt or repaired; sound repairs for 15 years.—T. E. Fevver, F.I.P.R.E., 50, Vine St., Uxbridge. [5266

REPAIRS to moving coil speaker, cones, coils fitted, field rewound or altered; speaker transformers, clock coils rewound, guaranteed satisfaction, prompt service. (11)

L.S. REPAIR SERVICE, 49, Trinity Rd., Upper Tooting, London, S.W.17. [4819

ALL makes and kinds of electrical and radio instruments repaired by skilled technicians A.I.D. approved; over 60,000 instruments repaired for R.A.F.; all work quoted by return without charge.—C. Gertler, Dept. D, 29-31 Cowcross St., E.C.1. Cle. 6783. [4829


REWINDS, mains transformers, speaker field coil-chokes, high-grade workmanship, 7-day delivery; new transformers constructed to customers' specification, singly or in quantities.—Metropolitan Radio Service Co., 1071, Finchley Rd., N.W.11. Speedwell 3000. [3219

LOUDSPEAKER repairs, any make, reasonable prices, prompt delivery, to the trade and quality fans; 25 years' combined experience with Rola, Magnavox, Combians, Celestion.—Sound Service Radio, 80, Richmond Rd., Kingston-on-Thames, Kin. 8008. [4977

24-HOUR service, 6 months' guarantee, any transformer rewinding, mains outputs and i.f.s., etc., all types of new transf., etc., supplied to specification; business heading or service card for trade prices.—Majestic Wind- ing Co., 180, Windham Rd., Bournemouth.

REWINDS, mains transformers, layer wound was impregnated, O/P transformers, chokes, fields, clock coils, pick-ups, fractional hp motors, competitive prices; prompt delivery; guaranteed work.—W. Groves, Manufacturing Electrical Engineer, 154, Ick- nield Port Rd., Birmingham, 16. [4547

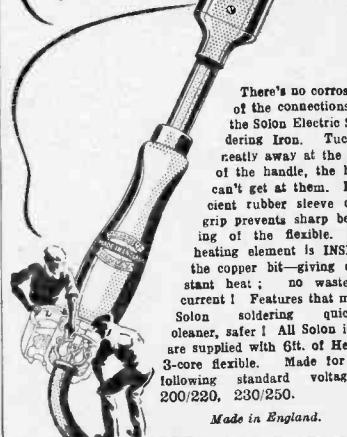Connections  
housed at  
end of handle  
—away from  
the heat!



There's no corrosion of the connections in the Solon Electric Soldering Iron. Tucked neatly away at the end of the handle, the heat can't get at them. Efficient rubber sleeve cord grip prevents sharp bending of the flexible. The heating element is INSIDE the copper bit—giving constant heat; no waste of current! Features that make Solon soldering quicker, cleaner, safer! All Solon irons are supplied with 6ft. of Henley 3-core flexible. Made for the following standard voltages—200/220, 230/250.

Made in England.

Illustration shows standard 240 watt model. Other types and sizes for various specialised jobs.

## SOLO

Electric  
SOLDERING IRON FOR INDUSTRIAL USE

W. T. HENLEY'S TELEGRAPH WORKS CO. LTD  
Engineering Dept., 51-53, Hatton Garden, London, E.C.1.

## The Scratch Filter for the COIL PICKUP

Costs £2/2/-.

Purchase Tax 9/4d.

WILKINS & WRIGHT, LTD.,  
Utility Works, Holyhead Road,  
Birmingham, 21.

## TRANSFORMERS & COILS TO SPECIFICATION.

MANUFACTURED OR REWOUND.

STANLEY CATTELL LTD  
9-11, East Street, TORQUAY, Devon

Phone: Torquay 2162.


### REWINDS

Armatures, Fields, Transformers, Pick-ups, Vacuum Cleaners, Gram. Motors, Speakers Refitted New Cones & Speech Coils.

All Guaranteed and promptly executed Valves, B.V.A. and American, good stocks. Send stamped addressed envelope for list of Radio Spares, and C.O.D. Service.

A.D.S. Co. ASTON, BIRMINGHAM, 6

## THIS Does these

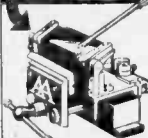


ACCURATELY and QUICKLY  
Chassis, Brackets, Shrouds, Conden-  
sors and Transformer clips—Steel or  
Aluminium. Five sizes—12" to 36".

Full particulars from:

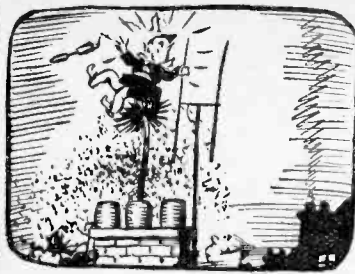A. A. TOOLS, (W),  
197, WHITEACRE ROAD,  
ASHTON-UNDER-LYNE





### THE "FLUXITE QUINS" AT WORK

"We'll finish this job before tea,  
Thanks to FLUXITE and solder and ME!"

Lift me up 'just a spot  
Just a bit, not a lot . . .

NOT TEN FEET! HEY, STOP IT!" bawled EE.

See that FLUXITE is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 30 years in Government works and by leading engineers and manufacturers. Of all Ironmongers—in tins, 8d., 1/4 & 2/8.

Ask to see the FLUXITE  
POCKET BLOW LAMP,  
price 2/6.

TO CYCLISTS! Your wheels will  
NOT keep round and true unless the  
spokes are tied with fine wire at the crossings  
AND SOLDERED. This makes a  
much stronger wheel. It's simple—with  
FLUXITE—but IMPORTANT.

The FLUXITE GUN puts FLUXITE  
where you want it by  
a simple pressure.  
Price 1/6, or filled,  
2/6.

ALL MECHANICS WILL HAVE

# FLUXITE

IT SIMPLIFIES ALL SOLDERING

Write for Book on the ART OF "SOFT"  
SOLDERING and for Leaflets on CASE-  
HARDENING STEEL and TEMPERING  
TOOLS with FLUXITE. Price 1d. each.

FLUXITE LTD.

(Dept. W.W.), Bermondsey Street, S.E.1

**DEGALLIER'S, Ltd.**—"Service with a guarantee." You cannot get your receiver serviced, let American specialists with proper test gear do the job: first-class workmanship only; we specialise in Air-King, Belmont, Challenger, Emerson, Ferguson, Garod, Halli-crafter, Hammerlund, McMurdo, Midwest, Majestic, Pilot, Scott, etc., also any British set; send s.a.s. with all enquiries.  
**DEGALLIER'S, Ltd.**, 9, Westbourne Court, London, W.2. [5276]

**R**EWINDING mains, field coils, outputs, etc., best work, quick service; alterations to specification; transformers made for instruments, amplifiers, etc.; television; hi transformers a speciality; terms c.o.d.; send trade card for special trade prices.—North-West Electrical Co. (W.W.), 36, Rosslyn Hill, London, N.W.3. [5775]

**T**RANSFORMER rewinds, trans. replacement coils, machine layer wound on bakelite former, interleaved, impregnated and clearly marked; rewinds £1, standard windings to 70 watts, coils 15/6; extra secondaries and larger types pro rata; new transformers or chokes to specification singly or in quantity; trade list on application; delivery by return of post most types; state model and iron size when ordering coils, pick-up coils, O.P. trans., field coils, etc., rewound or replaced; fully guaranteed.—Radio Services, Field St. Works, Blackpool. R.T.R.A. Service members, Ph. 1250. [5603]

**BUSINESSES FOR SALE OR WANTED**  
**R**DIO, electrical repairs, busy area, well equipped premises, takings £80 p.w., expert staff employed; £6,300 incl. valuable stock, freehold and car.—John Swait, Ltd., 34, Malb., Ealing 2866. [5785]

**R**DIO and electrical, Kent Coast town, rent £70, and corner shop, 4 workshops, 4 roomed flat, s.c. turnover £9,656, net profit £1,932, audited accounts; £2,500; s.a.v.—Lansley, 53, Friar St., Reading. [5790]

**N**OW is the time to dispose of your business to best advantage; negotiations strictly confidential; advice free; no obligation.—Jassoy & Harris, 479, Green Lanes, London, N.13. (Palmer's Green 4123). [5558]

**R**DIO, electrical, cycles.—Hackney large d.l. shop in busy market; freehold premises, 12 rooms; 7 radio agencies; good business, suit multiple; £5,000 s.a.v.—Jassoy & Hayes, Business Valuators, 479, Green Lanes, N.13. (Pal. 4123). [5648]

**O**WING to health reasons, radio and sound equipment manufacturer wishes to sell complete manufacturing rights; Board of Trade licence, several thousands pounds' worth of orders on hand, nationally organised sales dept., complete equipment, including modern spraying plant, drilling machines, benches, 8hp van, etc.; offers over £3,000; stock at valuation.—Box 1421. [5782]

**SITUATIONS VACANT**  
**N**ORTHERN Polytechnic, Holloway, N.7.

**R**DIO laboratory steward (male) required immediately in the Department of Radio and Musical Instrument Technology. Candidates should have a thorough knowledge of radio communications, technical electricity and civilian radio servicing, preferably with industrial experience; salary £190 to £250 per annum, plus a cost-of-living bonus, at present £78 per annum.—Applications should be made in writing to the Secretary, Northern Polytechnic, Holloway, N.7, giving full details of age, qualifications and experience. [5767]

**C**ROWN AGENTS FOR THE COLONIES.

**COLONIAL** Government appointments. APPLICATIONS from qualified candidates are invited for the following post:

**BROADCAST OFFICER** required by the Gold Coast Government, Broadcasting Department, for one year of 13 to 24 months with possible permanency. Salary according to age and war service in the scale £450 rising to £720 a year. On a salary of £450 a total allowance of £48 is payable and for married men separation allowance between £84 and £204 according to number of dependants. Outfit allowance £60. Free passages and quarters. Candidates should be of good education and have had a thorough training in the theory and operation of wireless broadcast transmitters and in studio technique. They should understand thoroughly the system of distributing radio programmes by wire and have a thorough knowledge of modern super heterodyne shortwave receivers. A knowledge of gramophone disc recording is desirable. APPLY at once by letter, stating age, whether married or single, and full particulars of qualifications and experience to the Crown Agents for the Colonies, 4, Millbank, London, S.W.1, quoting M/N 13418. [5832]

**J**UNIOR draughtsman required for company engaged in light current electrical measuring equipment, Hertfordshire.—Box 1470. [5788]

# GALPINS

GOVERNMENT SURPLUS ELECTRICAL STORES

408 High St., Lewisham, London, S.E.13

Telephone: Lee Green 0309. Near Lewisham Esplanade

**TERMS: CASH WITH ORDER, NO C.O.D.**

**EX-G.P.O. MAGNETO GENERATORS**, hand-driven approx. output 75 volts 20 m/amps A.C. useful to the experimenter, small pattern 7/6 each.  
**ROTARY CONVERTERS**, condition as new. 24 volts D.C. input at 2½ amps 75 volts A.C. 1 phase output 55/- each post 2/6.

**TRANSMITTER RACKS, EX-G.P.O.**, size 5½ ft. × 19in. × 3in., a very useful rack for building your own Transmitter Power Pack etc., Price 20/- each carr. forward.

Useful Panels as fitted to the above Racks comprising of Smoothing Chokes, Mod. Transformers, Condensers marked in decibels and various other components useful to the Amateur, all components as new 20/- each, carriage 2/6.

**HAND COMBINATION TELEPHONES**, late Pattern, receiver and Transmitter, ebonite body. 10/6 each post 0d., condition as new; Pedestal Type Telephones 15/- each, Breast Microphones, small ebonite pattern 7/6 each, single earphones with headband, low resistance, condition as new, 6/- each.

**TRANSFORMERS BY WELL-KNOWN MAKERS**, input 200/250 volts 50 cy. 1 phase output 1,500 volts at 3 Kilowatts twice. £12 10s. each. Voltage Regulation Transformer oil type 200/250 volts 50 cy. 1 phase, 7 kW. £15 each, new condition.

**RECTIFIERS (SELENIUM)** 24 volts 6 amps output 55/- each. 150 volts 300 m/amps output, 25/- each. New and unused.

**BALLAST LAMPS (GOOD MAKERS)**, new 125 volt 30 watts E.S. fitting, 6/- per dozen.

**METERS ALL BY WELL-KNOWN MAKERS**, edge type 1st grade moving coil 2½in. 0 to 3 amps, 35/-; 0 to 2 amps, 35/- . Both the above read 2 m/a without shunt. Ditto, 0 to 1 volt 1,000 Ohm. per volt 1 m/a 45/- . Another ¾ Decibel Meter reading zero—10—3 F.S.D. 50 microamps 85/- each. Another 2½in. round face meter 0 to 2½ and 100 volts A.C. fitted rectifier 55/- each. All fully guaranteed and condition as new.

**LARGE POWER UNITS BY WELL-KNOWN MAKERS**, input 100 to 260 volts 1 ph., 50 cycles output 24 volts 11 amps and 130 volts 600 m/amps, smoothed all fitted in metal cabinet size 5½in. × 10½in. × 12½in. fitted cutout, fuses, relay and switches, new condition, £12 10s. each carriage forward.

**VOLTAGE CHANGER TRANSFORMERS**. Auto-wound, fully guaranteed, immediate delivery. 350 watts, 55/-; 500 watts, 70/-; 1,000 watts, £5 15s.; 2,000 watts, £8 15s. All tapped 0, 110, 200, 230 and 240 volts.

**MAINS TRANSFORMERS**, all by well-known makers and fully guaranteed, input 200/250 volts, 50 cy. 1 phase; output 2,000/0,200/0 volts at 250 m/amps with 2 L.T. tappings, 75/- . Ditto, 475/0/475 volts at m/amps, with 3 L.T. tappings, 4v. and 6v., price £2.6. Ditto, 80, 100, 120, 140, 200, 240 volts at 3,000 watts. £12 10s. Ditto, 6, 16 volts at 14/00 amps output, £15. Transformer cores, suitable for winding 2,000 watts, 27/6; 100 watts, 7/6 each.

**EX-R.A.F. 10-VALVE CHASSIS** (sold for components only). Consisting of: 2, 150 ohm Mult. Contact Relays, 9 British type Octal Base Valve Holders, 30 Tubular Condensers, ranging from 10 P.F. to 1 M.F. 25/30 Resistances ¼, ½, 1 and 2 watts, all mounted on chassis, size 12in. × 8in. × 2in. Components all in good condition. "A real bargain" at 12/6 each, postage 1/6.

**EX-GOV'T. ROTARY CONVERTERS**, input 12 to 18 volts D.C. at 3½ amps. output 450 volts 60 m/amps fitted with automatic switching and smoothing 32/6 each. 2/6 carriage.

**ELECTRIC LIGHT CHECK METERS**, guaranteed electrically, 200/250 volts 50 cy., 1 phase, input 5 amp type, 12/6, 10 amp type, 15/- each. Carriage 1/-.

**D.C. MOTORS**, approx. ¼ h.p. series wound, all guaranteed electrically for 110 or 250 volts mains Price 15/- each. Carriage 1/-.

**HIGH-GRADE SWITCHBOARD TYPE AMP. METERS**, 5in. dial for A.C. or D.C. calibrated 50 cycles, 0 to 30 amps, 32/6 each. Ampermeters moving coil, 3in. dial 0 to 10 amps, 20/- each.

**LARGE TYPE RECTIFIERS**, 12 volts 4 amps, 15/-; 12 volts 6/8 amps, 55/-; 6 volts 1 amp. 12/6; 50 volts at 2 amps, 42/6. All fully guaranteed.

**MAINS TRANSFORMERS**, to suit the above 12 volt rectifiers, with tapped output of 6, 12 and 24 volts at 6 to 8 amps, 40/- . Carriage 2/-.



**SEND YOUR "WANTS" TO VALLANCE'S**

TEST EQUIPMENT. DELIVERY FROM STOCK.

Avo Model 40, £17 10s.; Taylor 85A, 20,000 ohms/volt, A.C./D.C. Taylor 90A, 40 ranges, A.C./D.C., 1,000 ohms/volt. Universal, Avo Minor, 22 ranges, £8 10s.; Taylor 90A, 1,000 ohms/volt, A.C. and D.C., 40 ranges, £15 15s.; E.I.C. Universal, 1,000 ohms/volt, A.C./D.C., £8 10s.; Walsell, Model 845, 2,000 ohms/volt, with low ohms range, £14 6s. 8d.; Taylor, 120A Junior A.C./D.C., 21 range, 1,000 ohms/volt, £8 10s.; Hunts, C. and R. Bridge, 0.00001 mfd.-50 mfd., power factor 50%, 50 ohms to 5 meg., insulation test, £18 18s.; Taylor, C. and R. Bridge, 110A, capacity measurements up to 120 mfd., resistance 120 ohms-12 meg., power factor measurements on all capacity ranges, £14 14s. Mullard C. and R. Bridge, 10 m.m.-10 mfd. and 10 ohms-10 meg. power factor. 15 gns. B.P.L. Signal Generators.—Frequency ranges, 100-250, 250-650, 650-1,600 kc/s; 1.6-4.5, 4.5-12, 12-30 mc/s; accuracy of calibration, 1%; internal modulation, 400 cycles; 6-step multiplier and attenuator, £21. A.C. mains 200/250 volts or 105-115 volts, 50/60 cycles.

Transmitting Valves.—RK34, Twin Triode 300r, 10 watts anode dissipation, 6.3 v. 0.9 amp, £1 10s.; RK25, Pentode, 500 v, 10 watts anode dissipation, 6.3 v. 0.9 amp, £2; 807, Beam Power Tetrode, 750 v. 30 watts anode dissipation, 6.3 v. 0.9 amp., £1 10s. 5d.; 866, Rectifier (mercury vapour) 10,000 v. inverse peak 1,000 m.a., half wave 2.5 v. 5 amp, £1 7s. 6d.; D441, direct equivalent to American T240, 7.5 v. 2.5 amp, 15 m.a., 40 watts anode dissipation, £2 15s.; 615 (metal) Beam Power Tetrode, 500 v. 21 watts anode dissipation, 6.3 v. 0.9 amp, 18/3. 83 type Rectifier, 15/3.

TRANSMITTERS  
Crystal Controlled Transmitters.—C.W. 25 watts, £30 10s. 30 watt-phone and C.W., £40. 50 watt-phone and C.W., £50. Delivery, approximately 6 weeks, against orders placed now.

Also large stocks of bias and by-pass Condensers by best makers; Mains Transformers with standard inputs and outputs, or with special windings to your specification; Output Transformers, small or heavy duty types; Speakers PM or ME, Coils, Coll. assemblies—in fact, everything you want for transmitter, receiver, amplifier, or experimental work.

Immediate attention to all orders and enquiries. Goods sent C.O.D. or against C.W.O. whichever best suits you. When sending C.W.O. please include sufficient for packing and postage.

**VALLANCE'S**

144 BRIGGATE, LEEDS, I.

**A.C.S. RADIO**

FOR COMMUNICATION RECEIVERS, AMATEUR TRANSMITTING GEAR, ALL TELEVISION AND RADIO EQUIPMENT AND COMPONENTS.

Preliminary LIST NOW READY, but with new stocks constantly being added we suggest enquiry or definite items if not listed.

44, WIDMORE ROAD, BROMLEY, KENT

**"VIBRO-ARC" Engraving Pen**

10/-



For rapid engraving any metal—hard or soft. Operates from 4-6v. Battery or A.C. Transformer giving 6-10 amps.

**HOLBOROW,**  
46, BOURNBRODGE, Yorks.



**W. BRYAN SAVAGE LTD.**

Expert assistance in the solution of problems relating to

- TRANSFORMERS, CHOKES
- AMPLIFIERS
- POWER UNITS

and Specialised Equipment embodying

**ELECTRONIC CONTROL**

WESTMORELAND RD., N.W.9  
COLINDALE 7131

SENIOR draughtsman required for company engaged in light current electrical measuring equipment, Hertfordshire.—Box 1469 [5787]  
LARGE electrical firm in London area require two experienced radio set designers, 5 years' experience essential.—Box 1769. [5837]

LAMINATION toolmakers wanted experience required; good rates.—P.S. & T.P. Ltd., 3, 4, Manor Way, Boreham Wood, Herts.  
RADIO service engineer, extensive pre-war practical experience.—Apply Norman's Cycle Stores, 236, High St., Brentford, Mdx.  
ENGINEER wanted for loud speaker production, must have experience.—Sinclair Speakers, 3, 4, Manor Way, Boreham Wood, Herts. [5607]

PHILIPS have a vacancy in their receiver design laboratory for a qualified engineer, capable of responsible work on television development.

CANDIDATES must possess theoretical qualifications to degree standard, and have had at least 3 years' experience on television practice. SALARY will be commensurate with ability & experience.—Application should be made by letter only, marked SD.215, & addressed: The Secretary, Mitcham Works, Mitcham, Surrey.

URGENTLY required, radio service engineer.—Particulars of experience, age, together with references, to Morlings, Ltd., 18, New Market, Beccles. [5761]

RADIO engineer required to take charge of new service department, commercial experience essential.—Taylor Radio, 324 Ravens Lane, Pinner, Middlesex. [5733]

DEVELOPMENT engineer required for domestic radio receiver design, pre-war experience essential.—Invicta Radio, Ltd., 79a, Parkhurst Rd., Holloway, N.7. [5792]

SERVICE engineer wanted by sound equipment manufacturers, central London, good prospects for keen man well qualified.—Write with details. Box 1747. [5830]

MEASURING instrument mechanic for repair work, Midlands, must be first-class craftsman; opportunity partnership if desired.—write in confidence for interview.—Box 920. [5830]

EXPERIENCED radio service mechanic for E. Wiltshire; some experimental work; first-class prospects for enthusiast; ex-Service preferred.—Adams, The Croft, Wilton, Salisbury.

MANUFACTURERS seek services of free lance technical journalist with knowledge of radio and electronics.—Write Box L5607, A.K. Advg., 212a Shaftesbury Ave., W.C.2.

SOUND equipment engineers required for testing analysis and fault-finding on production tests of high-grade amplifiers, good prospects, central London; write with details of experience.—Box 1749. [5831]

PRODUCTION engineer required by well-known London firm of condenser manufacturers; good salary and scope for right man; must have radio (preferably component) manufacturing experience.—Box 1892. [5897]

DESIGNER-DRAUGHTSMAN required for work on test equipment and measuring instruments.—Write, giving full particulars of experience and salary required, to Taylor Electrical Instruments, Ltd., Slough, Bucks.

TECHNICAL assistant (junior) required with working knowledge of radio valve applications; interesting and progressive job in technical/commercial department of large organisation.—Full particulars to Box 1258.

RADIO service engineer required by manufacturer, to reside in Colchester and cover surrounding area, commercial repair experience essential and some television knowledge desirable; salary £6 plus bonus, expenses and car allowance.—Box 1419. [5779]

FOREMAN for loudspeaker manufacturers, North London area; excellent opportunity and prospects for first-class man with speaker experience; able to control and co-operate.—Write, giving full details, age, experience and wages required, to Box 1088. [5716]

SALES order and correspondence clerk required to take charge of sales office of radio component manufacturers, London, some technical knowledge would be an advantage; state in confidence, education, experience in full, age and salary required.—Box AC11576, Samson Clark, 57-61, Mortimer St., W.1. [5812]

ELECTRICAL development engineers with experience of development for production of all classes of radio equipment are required by a well-established firm; remuneration exist for applicants having the necessary experience and qualifications.—Reply, giving full details, to Box 1366. [5777]

THE MIDDLESEX HOSPITAL MEDICAL SCHOOL, LONDON, W.1.—Technician required by department of Physiology for construction and maintenance of electronic apparatus, including high-gain amplifiers and cathode ray oscillographs, used for research and diagnostic purposes, experience in wireless, radar or related branches of physics essential; initial salary £6 p.w.; duties commencing 1st October, 1946. Applications to the Secretary of the Medical School. [5791]

**THESE ARE IN STOCK**

THE PRACTICAL WIRELESS ENCYCLOPEDIA, by F. J. Camm. 10s. 6d. Postage 6d.  
THE WIRELESS WORLD VALVE DATA, 2s. Postage 2d.  
FOUNDATIONS OF WIRELESS, by M. G. Scroggie, 7s. 6d. Postage 4d.  
RADIO ENGINEERING, by F. E. Terman, 30s. Postage 7d.  
RADIO UPKEEP AND REPAIRS, by A. T. Wittes, 7s. 6d. Postage 4d.  
FREQUENCY MODULATION, by K. R. Sturley, 2s. 6d. Postage 2d.  
RADIO HANDBOOK SUPPLEMENT, 2s. 6d. Postage 3d.  
COMMUNICATION ENGINEERING, by W. L. Everitt, 27s. 6d. Postage 7d.  
RADIO TECHNOLOGY, by B. F. Weller, 21s. Postage 6d.  
THE TECHNIQUE OF RADIO DESIGN, by E. E. Zepler, 21s. Postage 6d.  
HIGH FREQUENCY THERMIONIC TUBES, by A. F. Harvey, 18s. Postage 5d.  
SHORT WAVE WIRELESS COMMUNICATION, by Ladner & Stoner, 35s. Postage 6d.  
WE HAVE THE FINEST STOCK OF BRITISH AND AMERICAN RADIO BOOKS, WRITE OR CALL FOR COMPLETE LIST.  
**THE MODERN BOOK COMPANY**  
(Dept. W.15), 19-23, PRAED STREET, LONDON, W.2.

**PUBLICATIONS FOR SERVICEMEN**

AMERICAN MIDGETS HANDBOOK .. 2/3  
VALVE EQUIVALENTS CHARTS with quick ref. index .. 1/7  
ESSENTIAL VALVE DATA giving base data and diagrams of all valves listed in our valve equivalents charts .. 2/7  
RUNNING A RADIO REPAIR BUSINESS, with notes on starting, and including lists of valves and essential stock .. 7/3  
V.E.S., Radio House, Ruistip, Middx.

**Aladdin RADIO CORES**  
for all purposes  
GREENFORD, MIDDx. WAXLOW 2300

**NEW DUAL TESTSCOPE**

Ideal for high and low voltage testing; 1/30. 100/850 A.C. and D.C.  
Allowance made on old models  
Send for interesting leaflet (R.14) on Electrical and Radio Testing, from all Dealers or direct.

**RUNBAKEN-MANCHESTER**

**VOIGT PATENTS LTD.**  
WE APOLOGISE to those who have been waiting months for replies. Our post-war plans have been frustrated so far. Sorry!  
Be WISE and PATIENT

**MIDLAND INSTRUMENT CO.**

Immediate delivery of:  
Model 7 Avometers, £19 10 0. Universal Avominors, £8 10 0. D.C. Avominors, £4 4 0. Also limited quota of Model 40 Avometers, Avo Valve Testers, Avo Test Bridges, Avo Oscillators, Evershed and Vignoles Leve-Meggers, high and low resistance Ohmmeters, also Leve-Meggers Instrument Wires, resistance wires, and many other interesting Radio and Electronic items. Lists 2d. & a.s.o.  
18, Harborne Park Road, Birmingham, 17.  
Tel.: HARborne 1808 or 2664.

**INLAND C.O.D. TO- Millions of RADIO ENTHUSIASTS Anywhere.**

Amount to be collected

POUNDS	SILLINGS	PENCE	£	S.	d.

Above well-known labels are covers of securely packed parcels containing your orders chosen from 10,000 Popular and Rare Radio Valves, exact types or suitable Replacements: AOHLD, AOP, AC2HLL, ACpen, AC2pen, AC2penDD, AC5pen, AC5penDD, AC6pen, AC6penM, AC6P, AC6V, AC6V2, AC6V4, APFA, APFA4, APFB, APV4, AZ1, AZ31, B30, CL, C1C, C1C, C31C, C31, D63, DA30, DCP, DDB, DD1, DD20, DD620, DD14, DDT, DG2, DH63, DL, DL63, DN41, DQ24, DW2, DW4/350, DW4/500, EA60, EB34, EBC3, EBC33, EB11, ECC31, ECH36, ECR30, EFG, EFB, EFL2, EFB9, EFP50, EL2, EL3, EL5, EL11, EL12, EL33, EL5, EL50, EM, E2, F2, F22, F24, F4, F4, FC13, FC13C, FW4/500, GTIC, GU50, H30, H63, H141D, H210, HA2, HD24, HL41, HL2, HL13, H141D, HL21DD, HL23, HL23DD, HL41DD, HL133DD, HL1320, HL/DD/1320, IV4/350, KT2, KT24, KT32, KT61, KT69, KT66, KTV61, KTW63, KT263, LP2, M14, M141, M1411, M1415, M141D, M141B, M14, MPPen, MS4B, MSP4, MSPen, MSPenB, MU14, OM4, P2, P41, P21A, P650, PA20, PM24, PM24H, PM22D, PP3/250, PP5/400, PX4, PX25, Pen383, Pen4DD, Pen453DD, Pen4VA, Pen25, Pen45, Pen45DD, Pen46, Pen41, Pen428, PenA3, Pen14, PenDD4/20, QP221, QP22, QP23, R4, S4VB, SF2, SP13, SP13C, S14, SP48, SP41, TDD13C, TDD2A, TDD4, TH2, TH21C, TH233, TH2921, TH30C, TH4B, TH41, TP22, TP25, TP26, TP2620, T60, TX4, TX41, U5, U10, U14, U16, U18, U21, U31, U50, U52, U403, U4920, UR1C, UR3C, U15, U16, U17, V414, VMP40, VMS45, V12, V14, V1A, VP14, VP13A, VP23, VP41, VP138, VPT4, W21, W42, XH, X80, XP, X22, X24, X41, X61M, X63, X65, Y63, Z21, Z22, O1A, 1A4, 1A5, 1A6, 1A7, 1B4, 1C5, 1C7, 1I5, 1I6, 1D7, 1E7, 1P4, 1P5, 1P6, 1F7, 1G6, 1H4, 1H5, 1H6, 1J6, 1J6S, 1R5, 1R5, 1T4, 1T5, 2A7, 2B7, 2D13C, 2B14, 2F, 2H4, 3V4, 5Y3, 5Z3, 5Z4, 6A4, 6A7, 6A8, 6A9G, 617, 618, 6C5, 6C8, 6C8, 6D5, 6D6, 6D7, 6F5, 6F6, 616, 6J5, 6J7, 6J8, 6K6, 6K7, 6K8, 6L5, 6L6, 6L7, 6N7, 6P5, 6Q7, 6R7, 6S7, 6S7, 6S7, 6T7, 6U5/6G5, 6U7, 6V6, 6X5, 6Y5, 6Z5, 6Z5, 7A7, 7B5, 7B6, 7B7, 7B8, 7C5, 7D3, 7D5, 7Y4, 8D2, 9D2, 10, 10D1, 11I5, 12A, 12A5, 12B7, 12L5, 12L5, 12Q7, 12B47, 12S15, 12SK74, 12SQ7, 12ZF5, 13SP4, 14, 15, 15D1, 18, 19, 20, 20D2, 22, 24, 25A6, 25Z4, 25Z6, 26, 27, 29, 31, 32, 33, 34, 35, 35Z4, 35Z5, 37, 38, 408UA, 41MP, 41MTA, 41MTL, 41MTB, 41RTH, 42, 42M1Ppen, 41MPT, 42PTB, 43, 46, 48, 90, 53, 55, 57, 59, 71A, 74, 75, 76, 77, 79, 80, 81, 82, 85, 85, 89, 99, 164V, 210DDT, 220P, 220TH, 301, 302, 303, 304, 354V, 605BU, 954, 955, 956, 1921, 2151, 9001, 9002, 9003, 9004, 9005.

All above at List Prices. Order C.O.D. Also enquire for types not listed here.  
**COMPONENTS:** Full range of tested quality in stock.  
**BOOKS:** Comprehensive Radio Literature available.  
**METERS:** Latest models of Instruments, Test Gear and Equipment.  
**SHORTWAVE:** Stock of RAY-MART Products.  
**SPECIALS:** R.A.F. R1155A Communication Receivers. As described on pages 212-216 in July issue "Wireless World".  
 Army Transmitter Receiv. No. 58 M.K.I.  
 New Car Radio Sets.  
**LISTS:** Complete set on application (stamp).  
**EXPORT:** Speedy despatch, safe packing, full insurance.  
**DEMOLISHED and Forces:** Special attention.  
**STOP PRESS:** Those readers who wish to be incorporated in our 1946/47 mailing scheme should send us a postcard with name and address in block capitals.  
**J. BULL & SONS (W.W.)**  
 246, HIGH STREET, HARLESDEN, N.W.10

**MATRICULATION**  
*brings Success & Security*

Whatever your age, you can now study for the all-important Matriculation Examination at home on "NO PASS—NO FEE" terms. "MATRIC" is the accepted passport to all careers, and opens up opportunities which would otherwise be completely closed to you. Ensure the success and security of you and yours through post war difficulties by writing for our valuable "Guide to Matriculation" immediately—FREE

**B.T.I. (Dept. 114)**  
 356, Oxford Street, London, W.1.

**R**ADIO valve and cathode ray tubes.—Person with experience in the assembly of experimental electrode structures required, some experience in tool making an advantage. location 50 miles London.—Apply, stating experience, age and salary required, to Box 1420.

**E**STABLISHED dealer West London district specializing Murphy, H.M.V., Pye, requires service engineer, experienced radio, television, installations, etc., permanent and progressive post; write, stating age, experience, wages required, to Box 1587.

**A**PPPLICATIONS are invited for the position of television engineer, capable of creating and taking charge of department, good up-to-date knowledge of design and development and first-class qualification essential; good salary to the right man; factory 30 miles London on S. Rly.—Write Box 1670.

**R**ADIO engineer.—Large radio firm in London area requires an engineer to act as deputy to the head of its radio design section; the engineer concerned should have theoretical and practical experience of radio set design, preferably for the Services.—Write to Box 1817.

**D**RAUGHTSMEN and traders required for S. London, with experience in prod. of working drawings from data supplied by designers; (1) mech. draughting; (2) elect.; preferably with exp. on radio comm. equipment; workshop experience preferred.—Apply in writing, with full details, to R.T.E., Ltd., 45, Nightingale Lane, S.W.12. [5538]

**D**RAUGHTSMAN required for the preparation of detailed drawings of electro-acoustic apparatus; experience of similar equipment though desirable, not essential, but the applicant must have a good knowledge of factory procedure; written applications only; state experience and salary required to: Vitavox, Ltd., Westmoreland Rd., N.W.9.

**D**RAUGHTSMEN and mechanical designers required by firm engaged in the production of a wide range of equipment for all classes of radio communications, radar, electronic applications to industry, domestic radio and television receivers; excellent prospects and good remuneration for suitable applicants.—Applications should give full details of experience, age, etc., to Box 1365. [5776]

**J**UNIOR executive to take charge of life test dept., radio valve factory at Sunderland, under B.Sc., or H.N.C. standard with knowledge of electronics essential, experience in valve industry desirable.—Full particulars of education, experience and salary in first instance to Personnel Dept., Cosmos Mfg. Co., Ltd., Brimsdown, Enfield. [5807]

**V**ACANCIES exist for draughtsmen and mechanical designers with experience in the development of production of radio communications equipment and broadcast television receivers; designers should have experience in the development of small mechanisms.—Reply, giving details of experience, qualifications, age and salary required to Personnel Manager, G.E.C. Radio and Television Works, Spon St., Coventry. [5860]

**B**.B.C. invites applications from men (British) for three posts in Television Section, Research Dept., based firstly near Oxford, but at times to work London and elsewhere. For (a) and (b) recognized engineering qualifications, i.e., university degree or equivalent are essential, and for (c) technical qualifications at least to Higher National Certificate. Training in communication engineering essential.  
 (a) SENIOR engineer, grade max. £800 p.a. Must be thoroughly conversant with television technique, including practical experience. General knowledge optics and photographic technique an advantage. Organizing ability, energy and initiative desirable. Duties comprise research in problems relating to development of television, both general principles and detail.  
 (b) ENGINEER, grade max. £600 p.a. Knowledge of television technique, with practical experience an advantage. Duties include television research and development, with particular reference to circuits and equipment comprising a television channel. Normally works under supervision but ample scope for initiative.  
 (c) ASSISTANT engineer, grade max. £400 p.a. Must be keenly interested, though practical experience television technique not essential. Work includes all aspects of television research. Ample scope for initiative, but normally works under supervision.  
 COMMENCING salary dependent on age, qualifications and experience. Annual increments up to grade maximum, subject favourable reports. Cost of living bonus (£44/4 p.a.) and family allowances paid in addition to salary. Appointment to unestablished staff; entry to permanent staff for later consideration. Applications to Engineering Establishment Officer, Broadcasting House, London, W.1, with details of age and experience, not later than 9th September, 1946. [5813]

# ARMSTRONG

## Model EXP53

### ALL-WAVE 7-STAGE RADIOGRAM CHASSIS

This new radiogram chassis incorporates wave-band expansion on all bands, e.g., the 16-50 m. band covers just over 20 inches on the large glass scale. Volume and tone controls work on both Radio and Gram. 4½ watts R.C. coupled output. Supplied complete with full size loudspeaker. This chassis has a lively performance, good quality reproduction, and represents excellent value. For 200-250 v. A.C. Mains.

Price, with speaker **£13 plus tax.**

## Model EXP83

### ALL-WAVE 8-VALVE SUPERHET CHASSIS

incorporating wave band expansion. Large glass scale treble boost control. Gram. switching. High quality push-pull output gives 10 watts audio. For 100-250 v. A.C. mains.

Price **14 gns. plus tax**

## Model EXP43

### ALL-WAVE SUPERHET FEEDER UNIT

incorporating wave band expansion manual I.F. gain control, etc.

Price **11 gns. plus tax.**

## Model EXP63

### ALL-WAVE 6-VALVE SUPERHET CHASSIS

incorporating wave band expansion. Gram. switching. R.C. coupled output. For 100-250 v. A.C. or D.C. mains.

Price **12 gns. plus tax.**

## Model AMP14

### HIGH GRADE AMPLIFIER

in well finished metal instrument case. Two inputs, bass compensating circuit, treble boost control. 14 watts push-pull output preceded by 4 triodes.

Price **15 gns.**

Demonstration Sets are now available for interested callers to hear and illustrated technical specifications are now ready.

**ARMSTRONG WIRELESS & CO. LTD**  
 WALTERS ROAD, HOLLOWAY, LONDON, N.7  
 'Phone: NoRth 3213

## L-R-S IN STOCK!

### AVOMINOR TEST METERS

A.C./D.C. Universal ..... £8 10 0  
 D.C. .... £4 4 0

Regd. Post 10d.

### CYLDON ELECTRIC DOOR CHIMES

Beautifully made. Far more pleasant than buzzer or bell. Front door push operates double chimes, back door only single. Universal model for battery, or mains with bell transformer (extra). Postage 10d. £2 9 6

### STUART Centrifugal Electric PUMPS

for machine tool cooling, garden fountains and all pumping purposes. Three sizes.

List of Chimes 1d.

ANY OF THE ABOVE SUPPLIED ON EASY TERMS  
**The LONDON RADIO SUPPLY CO.**  
 (Est. 1925) BALCOMBE, SUSSEX

**ILLUSTRATED CATALOGUE**



**NOW AVAILABLE**

Please send 2/6 stamp for post free copy.

Our staff includes: G3AD A. N. Simmonds, G8ZD E. P. Appleby, SPIHH/SP2HH M. Kasia.

**TELE-RADIO (1943) LTD.**

177, Edgware Road, London, W.2.  
Telephone: PADdington 6116.

**ENGINEERING OPPORTUNITIES**



This unique handbook shows the easy way to secure A.M.I.Mech.E., A.M.Brit.I.R.E., A.M.I.E.E., City and Guilds, etc.

**WE GUARANTEE—“NO PASS—NO FEE.”**

Details are given of over 150 Diploma courses in all branches of Civil, Mech., Elec., Motor, Aero, Radio, Television and Production Engineering, Tracing, Building, Govt. Employment, R.A.F. Maths., Matriculation, etc.

Think of the future and send for your copy at once—FREE.

B.I.E.T., 387, SHAKESPEARE HOUSE, 17, STRATFORD PLACE, LONDON, W.1

**QUARTZ CRYSTAL UNITS**

FOR AMATEURS  
For your  
TRANSMITTER

HIGHER ACCURACY  
COMPETITIVE PRICES

Delivery FROM STOCK

For your  
FREQUENCY STANDARD

SALFORD ELECTRICAL INSTRUMENTS LTD.  
PEEL WORKS, SALFORD J  
Proprietors: THE GENERAL ELECTRIC Co. Ltd., of England

**R**ADIO service engineer, male or female; opportunity for first grade craftsman or craftswoman to join progressive old-established private concern with good prospects, permanency, superannuation, etc., must be efficient, methodical, quick and tidy worker. Only those capable of fault-clearing in modern home radio need apply; opportunity to train in public address installation and maintenance if so desired; write, giving full particulars, age, experience, salary required; fare paid for interview.—Holder Bros., Ltd., 118, High St., Scunthorpe, Lincs. [5774]

**T**ELEVISION and radio engineers required in the near future, experience essential in one or more of the following research and design fields: Wide-band receivers, scanning and C.R.O. tube circuits, frequency modulation, recording systems, etc.; applicants must have had actual design experience, a degree and mathematical ability are advantageous; write, giving age, particulars of training, experience and salary required, etc.; salary range £400-£800; five-day week.—R.F. Equipment, Ltd., Langley Park, Nr. Slough, Bucks. 15802

**SITUATIONS WANTED**

**E**X-RADAR mech. (Sgt.), 5 years R.A.F. 3 years prev. military and P.A., seeks progressive post; South.—Box 1089. [5717]

**E**X-SGT. R.E.M.E., tele-com. mechanic (4 years), released July, 10 years' pre-war Exp. of radio, seeks good permanent position.—Box 1669. [5815]

**E**X-SIGNALS Major, public school, university, 6 years' technical officer, pre-war radio research, seeks position of responsibility.—Box 1548. [5808]

**C**.Q.M.S. (foreman of Signals), 26, single, C. & G. qualifications, on release leave, seeks position with facilities for further study and experience.—Box 1745. [5834]

**E**X-P.O. radio mechanic, 35, 4 years' experience radio and U.H.F. transmitters and receivers, construction and maintenance, desires position; B.I.E.T. (A.M. Brit. I.R.E.) student.—Box 1767. [5840]

**R**EPRESENTATIVE desires post, radio, electrical manufacturer, sales or technical; covered Midlands, S.W. Lancashire, Cheshire, N. Wales; first class technical knowledge; car owner.—Box 1471. [5786]

**E**NGINEER, 31, A.M. Brit. I.R.E., C. & G., 15 years' telecommunications, including television, development, production, inspection in administrative capacity, desires change; present salary £470.—Box 1518. [5797]

**R**ADIO engineer, 31, 11 years Government radio lab, and industrial experience, desires responsible post, technical or representative, calling for good education, personality, initiative and knowledge.—Box 1093. [5720]

**E**X-R.E.M.E. S/Sgt., 4 years Army (37), experience radio since 1926, C. & G. II, C. & G. servicing, 15 months i/c workshop in tropics, excellent knowledge construction and repair all types test equipment, British, U.S.A. civilian receivers, P.A. amplifiers, under rigorous tropical conditions, good knowledge sheet metal work and lathe work, desires responsible, progressive position, radio service, or with manufacturer for export.—Box 1487. [5797]

**PATENT AGENTS**

**A**. E. HILL, chartered patent agent, 27, Chancery Lane, London, W.C.2. [4368]

**AGENCIES**

**C**OMPANY with strong selling organisation in Spain and Portugal is desirous of representing substantial British manufacturer of radios and accessories.—Box 1489.

**R**ADIO manufacturers specialising in high quality radio chassis, amplifiers, and transformers, cordially invite applications for agencies from bona fide radio dealers; export enquiries are specially welcome.—Box 7993.

**AGENCIES WANTED**

**A**GENCIES required for goods likely to be of interest to wireless manufacturers, vacuum cleaner manufacturers and the general electrical trade.

**I**F your product is of good quality we are in a position to introduce it to all the leading electrical manufacturing concerns in the country.—Write full particulars in first place to: Box 1100. [5736]

**TUITION**

**R**ADAR—RADAR—RADAR.  
THE British National Radio School, first in the field in this new science (see W.W. for April), now offers a three months' practical course in radio physics and general laboratory practice. Correspondence courses for C. & G., Brit. I.R.E., and I.E.E. Examinations. Our "Four Year" Plan for the ambitious Radio Officer may be had on application to The Studies Director, B.N.R.S., 66, Addiscombe Rd., Croydon. [5484]

**RADIO SPARES**

MAINS TRANSFORMERS. Primaries 200/250 volts		
Secondaries 350-0-350 volts.		
TYPE C.	100 ma. 4 v. 5 a., 4 v. 3 a.	34/6
TYPE D.	100 ma. 6.3 v. 5 a., 5 v. 3 a.	34/6
TYPE E.	120 ma. L.T.s as Type C.	37/6
TYPE F.	120 ma. L.T.s as Type D.	37/6
TYPE H.	200 ma. Three L.T.s of 4 v. 6 a. x 4 v. 3 a.	47/6
Rectifier		
TYPE I.	200 ma. Three L.T.s of 6.3 v. 6 a. x 5 v. 3 a. Rectifier	47/6
Secondaries 500-0-500.		
TYPE J.	200 ma. Three L.T.s of 6.3 v. 6 a. x 5 v. 3 a. Rectifier	52-
TYPE K.	200 ma. Three L.T.s of 4 v. 6 a. x 4 v. 3 a. Rectifier	52-
TYPE L.	250 ma. Three L.T.s of 6.3 v. 6 a. x 5 v. 3 a. Rectifier	56-
TYPE M.	250 ma. Three L.T.s of 4 v. 6 a. x 4 v. 3 a. Rectifier	56-
Secondaries 400-0-400.		
TYPE R.	120 ma. 4 v. 5 a., 4 v. 3 a.	40-
TYPE S.	120 ma. 6.3 v. 5 a., 5 v. 3 a.	40-
Please note Types H to M have 2 of the L.T.s centre tapped. Owing to dimensions and weight of these types, kindly add 2/6 for carriage and packing.		
<b>HEAVY DUTY MULTI-RADIO OUTPUT TRANSFORMER.</b> 120 ma. 15 watts, tapplings for 6L6s in push pull, 6X4s in push-pull, low impedance triode, low impedance pentode, high impedance triode, 27/6; complete instructions with each unit.		
<b>SMOOTHING CHOKES.</b> 20 henrys 100 or 120 ma., 12/6. 20 henrys 150 ma., 15/6; 30, 35 or 40 henrys 200 ma. or 250 ma., 21/6.		
WOULD FRIENDS PLEASE NOTE THAT OWING TO DEMAND FOR OUR TRANSFORMERS AND CHOKES WE HAVE CEASED TO STOCK OTHER RADIO COMPONENTS		
H. W. FIELD & SON, Colchester Road, HAROLD PARK, ESSEX Telephone: INGRebourne 2842.		

**RADIOGRAPHIC**

The Mail Order Specialists

**HAVE GOT THE STUFF**

Transmitting valves, Crystals (RX & TX) and U.S.A. Valves, Walki-Talki, H.V. Transformers.

Condensers, Q.C.C. Raymatt Stockists, chassis work.

★ Radio Metal Work Specialists.

**RADIOGRAPHIC LIMITED**

66 OSBORNE ST. GLASGOW


**AMBASSADOR**



**SPECIFICATION**

20 Watt A.C. Amplifier with built-in Super-bet Receiver covering 200-550 Metres. Specially recommended for Schools, Factories, Hospitals, etc. Full specification on request.

INDUSTRIAL RADIO AMPLIFIER

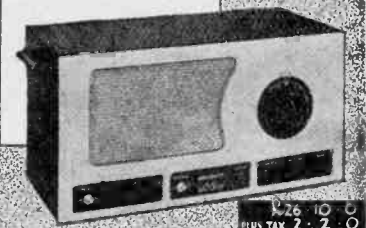

**R. N. FITTON, LTD.**

HUTCHINSON LANE, BRIGHOUSE. Tel.: 283

Scottish Distributors:

BRITISH ELECTRICAL & MFG. CO. LTD.  
133 West Campbell St., GLASGOW. Tel.: Cen. 3286

## WARD ROTARY CONVERTERS

For Radio, Neon Signs, Television, Fluorescent Lighting, X-ray, Cinema Equipment and innumerable other applications


We also manufacture:—

Petrol Electric Generating Plants, H.T. Generators, D.C. Motors, Frequency Changers, etc., up to 25 K.V.A.

**CHAS. F. WARD**

37, WHITE POST LANE, HACKNEY WICK, E.9  
Phone: Amherst 1393

## LONDEX for RELAYS

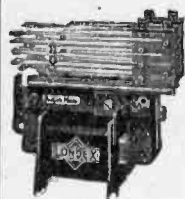

for A.C. and D.C.  
2 VA Coil consumption from 2 to 600 volts and tested to 2000 volts, Aerial Changeover Relays, Mercury Relays, Measuring Relays and Time Delay Relays.

Multiple contact Relay LF.

Ask for leaflet 205/WW

## LONDEX LTD

MANUFACTURERS OF RELAYS  
AWBLEY 207-ANERLEY ROAD-LONDON-S.E.20

## COVENTRY RADIO

COMPONENT SPECIALISTS SINCE 1925

Now Ready. **21<sup>ST</sup>** Birthday

LIST OF COMPONENTS

Price 3d. Post paid.

Prompt Service, Complete Satisfaction.

## COVENTRY RADIO

191, DUNSTABLE RD., LUTON, BEDS.

RADIO training.—P.M.G. exams. and I.E.E. Diploma; prospectus free.—Technical College, Hull. [0611]  
A NEW course now available deals with practical radio servicing and introduces new and hitherto unpublished methods; unsuitable for beginners; send for free details to: BCM/CIRCUIT, London, W.C.1. [5735]

## TECHNICAL TRAINING

ENGINEERING careers and qualifications. BOTH Government and industry have announced and emphasised that young men with technical knowledge and qualifications must receive every chance to rise to the highest positions within their capacity, in post-war engineering and allied industry, write to-day for "The Engineer's Guide to Success"—200 courses free—which shows you how you can become A.M.I.E.E., A.M.I.A.E., A.M.I.Mech.E., A.F.R.Ae.S., etc., and covers all branches in radio, automobile, mechanical, electrical, production, aeronautical, etc.

THE Technological Institute of Great Britain, 82, Temple Bar House, London, E.C.4. [4918]  
P.M.G. radio theory exams, model answers to 12 papers (analysed); 7/6.—Liddiat, Alveston, Bristol. [5735]

A.M.I.E.E., City and Guilds, etc., on "No pass—no fee" terms; over 90% successes. For full details of modern courses in all branches of electrical technology send for our 112-page handbook, free, post-free.—B.I.E.T. (Dept. 388A), 17, Stratford Place, W.1. [3838]  
RADIO Engineering, Television and Wireless Telegraphy, comprehensive postal courses of instruction—Apply British School of Telegraphy, Ltd., 179, Clapham Rd., London, S.W.9 (Estd. 1906). Also instruction at school in wireless for H.M. Merchant Navy and R.A.F. [9249]

ENGINEERING Opportunities.—Free 112-page guide to training for A.M.I.Mech.E., A.M.I.E.E., and all branches of engineering and building; full of advice for expert or novice; write for free copy and make your peacetime future secure.—B.I.E.T. (Dept. 387B), 17 Stratford Place, London, W.1. [3837]

THE Tuitionary Board of the Institute of Practical Radio Engineers have available home study courses covering elementary, theoretical, mathematical, practical and laboratory tuition in radio and television engineering; the text is suitable coaching matter for I.P.R.E., Service-Entry and progressive exams. Tuitionary fees—at pre-war rates are moderate.—The Syllabus of Instructional Text may be obtained post free from Secretary, 20, Fairfield Rd., Crouch End, N.8.

PATENTS The proprietor of British patent No. 537177, entitled "Electro-acoustic means for producing sound effects," offers same for licence or otherwise to ensure practical working in Great Britain.—Enquiries to Singer, Ehlert, Stern & Carlberg, Steger Building, Chicago 4, Illinois, U.S.A. [5809]

## Beethoven RADIO

BEETHOVEN ELECTRIC EQUIPMENT LTD.  
BEETHOVEN WORKS, CHASE RD., LONDON N.W.10

## POST-WAR TELEVISION

The advance in Radio Technique offers unlimited opportunities of high pay and secure posts for those Radio Engineers who have had the foresight to become technically qualified. How you can do this quickly and easily in your spare time is fully explained in our unique handbook.

Full details are given of A.M.I.E.E., A.M.Brit.I.R.E., City & Guilds Exams., and particulars of up-to-date courses in Wireless Engineering, Radio Servicing, Short Waves, Television Mathematics, etc. etc.

We Guarantee "NO PASS—NO FEE"

Prepare for to-morrow's opportunities and post-war competition by sending for your copy of this very informative 112-page guide NOW—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 388)

17, Stratford Place, London, W. 1

## MORSE CODE TRAINING



There are Candler Morse Code Courses for BEGINNERS AND OPERATORS.

Send for this Free "BOOK OF FACTS"

It gives full details concerning all Courses.

THE CANDLER SYSTEM CO., (Room 55W), 121 Kingsway, London, W.C.2  
Candler System Co., Denver, Colorado U.S.A.

## HILL & CHURCHILL LTD

BOOKSELLERS

## SWANAGE DORSET

ENGLISH & AMERICAN BOOKS IN STOCK ON

RADIO AND TELECOMMUNICATION

CATALOGUE ON APPLICATION

# Superspeed

SPECIAL

## CORED SOLDER

A.I.D. APPROVED

**H. J. ENTHOVEN & SONS LTD.**  
230 THORNTON ROAD, WEST CROYDON, SURREY  
THORNTON Heath 2462

## ERG'S HAVE THE URGE TO GO ABROAD

SPEAKING EXPORTLY...



ERG Resistors have an exceptional electrical specification and performance, with mechanical strength.

High-grade Vitreous Enamels used on our Tropical Resistors give long life, and definitely assist in the trouble-free manufacture and performance of Radio Receivers, Television and Test Equipment.

ERG Resistors are processed up to the highest Service Standards at a competitive Price.

ERG INDUSTRIAL CORPORATION LTD.  
SALES OFFICE: 10 PORTMAN SQUARE, LONDON, W.1  
TELE.: WELBECK 3892





# A World-wide Reputation!

IN 1908 Mr. S. G. Brown invented the rightly famous S. G. BROWN Type "A" Headphone. This type is still acclaimed as the finest and most sensitive headphone procurable.



Type "A"

Radio Amateurs desiring maximum reception results over all wavebands, coupled with quality reproduction and highest possible efficiency, should ask their dealers for a pair of S. G. Brown Type "A" Headphones.

**TYPE "A"**  
Adjustable Reed Movement  
57/6


For a less expensive pair of headphones, which will also give excellent results, ask for the S. G. Brown Type "F" Featherweight. Price 23/-.

Phone :  
ACOrn  
5021

## S.G. Brown, Ltd.

VICTORIA ROAD, NORTH ACTON, LONDON, W.3

# —Wharfedale—

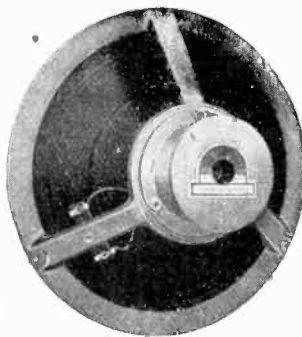

**NEW GOLDEN 10 inch LOUDSPEAKER**

During the last six years hundreds of Wharfedale Golden Units have been supplied, and are still being supplied, to the B.B.C. and G.P.O. It was selected by reason of

Speech Coil 3 or 15 ohms.  
Impedance. **PRICE 75/-**

its level response. The new model is fitted with precision die-cast chassis, improved spider, and Alcomax II Magnet increasing the flux density from 10,000 to 12,500. The price is only increased by 5/-.

Made and Guaranteed by

**WHARFEDALE WIRELESS WORKS**

NEW ADDRESS

**BRADFORD ROAD, IDLE, BRADFORD.**

Phone: Idle 461.

Grams: "Wharfedale, Idle, Bradford."

Even a double load doesn't shorten the life of a

## Welwyn Resistor



"No property of the resistance presented any apparent alteration." Such is the independent report after testing a Welwyn Vitreous Resistor for 670 hours at continuous double load. (Normal load gives working temperature of 450°C.) Sizes:—1 w. to 300 w.

New Trade catalogue available.

**WELWYN ELECTRICAL LABS. LTD**  
Welwyn Garden City, Herts. Pho: Wel. Gar. 3814

# CLIX

Radio & Television Components

- Manufacturers of
- Plugs and Sockets
  - Panel Mounting Sockets
  - Coil Pins and Valve Pins
  - Chassis Mounting Strips
  - Panels
  - Terminals and Connectors
  - Tag Strips
  - Cartridge Fuses
  - Valveholders
  - Cathode Ray Tube Holders
  - Valve Bases

**BRITISH MECHANICAL PRODUCTIONS LTD.**

21 BRUTON STREET, BERKELEY SQUARE, W.1

Grams: Trolinx, Wesdo, London

Phone: Mayfair 5543

**WALTER CONDENSERS**  
ARE MADE FOR



## WALTER INSTRUMENTS LTD.

**GARTH RD., LOWER MORDEN, SURREY**  
DERWENT 4421. Grams: WALINST, MORDEN, SURREY

G. R. O. 70



# 5 mmf/ft

NEW LOW LEVELS in capacity and attenuation of CO-AX Cables mean new possibilities in electronic equipment design both for the war effort and for the post-war electronic age.

**BASICALLY BETTER AIR-SPACED**

## CO-AX LOW LOSS CABLES

**TRANSRADIO LTD. 16 THE HIGHWAY-BEACONSFIELD-4-BUCKS**





# STABILITY

*and accuracy*

Of unflinching interest to visitors to the Royal Observatory is the historical plate let into the outer wall, carrying the gages which give the master measurement of the British Yard.

**T**HE familiar buildings of the Royal Observatory house a proud and stable tradition of British scientific accuracy . . . "Greenwich Time" is never questioned.

Where stability, accuracy of capacitance are essential requirements, Hunts Silvered Mica Capacitors can be relied upon. They also possess the advantages of initial low cost

and also economical application, the lightweight construction allowing them to be used without fixing holes or special mountings.


A range from 10 to 10,000 pF is available in a variety of types and sizes — full details upon request.

**HUNTS**  
**CAPACITORS**

TRADE MARK,

**PROTECTED**  
**SILVERED MICA**

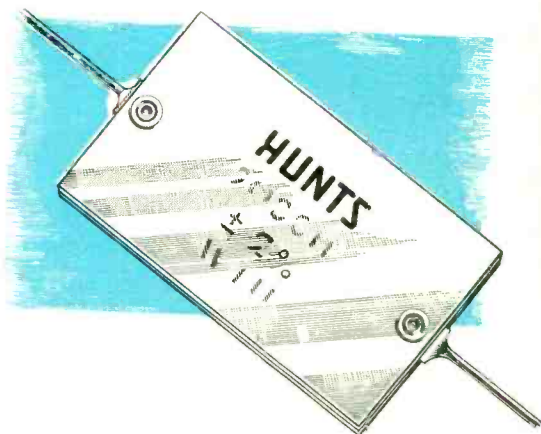A. H. HUNT LTD. LONDON, S.W.18  
Established 1901





**SAFETY  
IN  
QUALITY**

The cost of solder for a joint is so little and a sound joint means so much. Whether you make 10,000 sets or repair 1—be safe—use the finest cored solder in the world. Ersin Multicore—the only 3 core solder. Our job is to send you details—please ask for them.

**MULTICORE SOLDERS LTD., MELLIER HOUSE, ALBEMARLE STREET, LONDON, W.1**