

ELECTRONICS & Wireless World

FEBRUARY 1984

85p



**GPIB-to-BBC
Micro interface**

Morse on a ZX 81

**Improvising
with Forth**

Current following




Australia	A\$	3.00
Denmark	DKr	34.50
Germany	DM	7.00
Greece	Dr	220.00
Holland	DFL	8.50
Italy	L	3800
Norway	Nkr	29.20
Singapore	M\$	5.50
Spain	Pts	340.00
Switzerland	SFr	7.00
U.S.A.	\$	3.75

EP8000

EPROM EMULATOR PROGRAMMER

**NEW
PRODUCT**

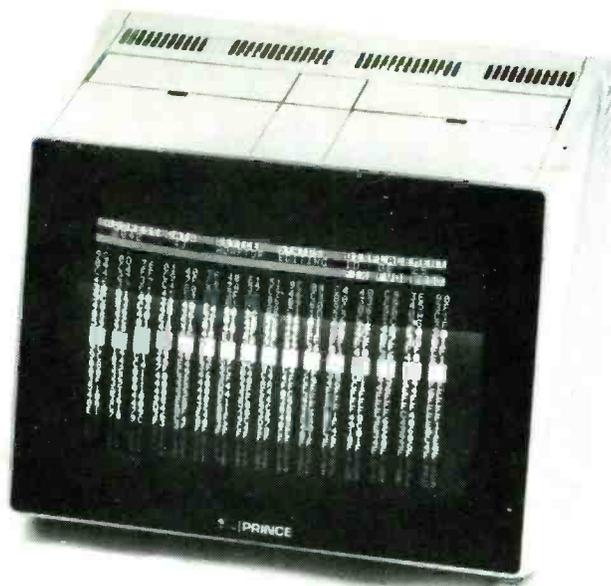

The new microprocessor controlled EP8000 Emulator Programmer will program and emulate all EPROMs up to 8k x 8 sizes, and can be extended to program other devices such as 16k x 8 EPROMs, Bipolar PROMs, single chip microprocessors with external modules. Personality cards and hardware changes are not required as the machine configures itself for the different devices. The EP4000 with 4k x 8 static RAM is still available with EPROM programming and emulation capacity up to 4k x 8 sizes.

● EP8000 8k x 8 Emulator Programmer – £695 + £12 delivery ● BSC8 Buffered emulation cable – £49 ● SA27128 Programming adaptor – £69 ● SA25128 Programming adaptor – £69 ● EP4000 4k x 8 Emulator Programmer – £545 + £12 de-

FEATURES

- Software personality programming/emulation of all EPROMs up to 8k x 8 bytes including 2704, 2708, 2716(3), 2508, 2758A, 2758B, 2516, 2716, 2532, 2732, 2732A, 68732-0, 68732-1, 68766, 68764, 2564, 2764. Programs 25128, 27128 with adaptors.
- No personality cards/characterisers required.
- Use as stand alone programmer, slave programmer, or EPROM development system.
- Checks for misplaced and reversed insertion, and shorts on data lines.
- Memory mapped video output allows full use of powerful editing facilities.
- Built-in LED display for field use.
- Powerful editing facilities include: Block/Byte move, insert, delete, match, highlight, etc.
- Comprehensive input/output – RS232C serial port, parallel port, cassette, printer O/P, DMA.
- Extra 1k x 8 scratchpad RAM for block moving.

livery ● BSC4 Buffered emulation cable – £39 ● BP4 (TEXAS) Bipolar PROM Module – £190 ● Prinz video monitor – £99 ● UV141 EPROM Eraser with timer – £78 ● GP100A 80 column printer – £225 ● GR1 Centronics interface – £65

VAT should be added to all prices

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513


Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN

WW-001 FOR FURTHER DETAILS

ELECTRONICS & Wireless world

FEBRUARY 1984

VOL 90 NO 1577

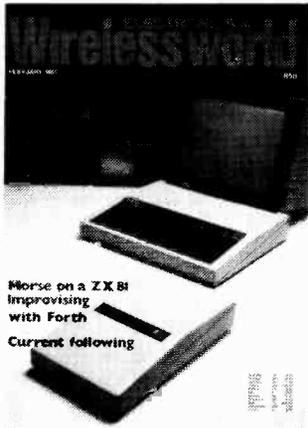

Morse on a ZX81
Improvising
with Forth
Current following

Acorn's GPIB/BBC interface
— above — is described by its
originator on page 24.
Photo by courtesy of Acorn
Computers and Optimus
Graphic Design.

NEXT MONTH

Differential temperature
integrator developed at the
O.U. provides weekly average
temperature differences
between each of three house
zones and outside, as a
measure of insulation quality.

Voltage multiplying converter
provides 120 volt supply from a
9 volt battery.

Adaptable typewriter interface
connects computer parallel
output to a daisy wheel printer.
Pascal is used to show how a
printing routine is constructed.

Improving colour television
decoding continues with David
Read's decoder circuit.

Current issue price 85p, back issues (if
available) £1.06, at Retail and Trade
Counter, Units 1 & 2, Bankside Industrial
Centre, Hopton Street, London SE1.
Available on microfilm; please contact
editor.

By post, current issue £1.30, back issues
(if available) £1.40, order and payments
to EEP General Sales Dept, Quadrant
House, The Quadrant, Sutton, Surrey
SM2 5AS. Tel: 01-661 8668.

Editorial & Advertising offices: Quad-
rant House, The Quadrant, Sutton,
Surrey SM2 5AS.

Telephones: Editorial 01-661 3614.
Advertising 01-661 3130. See leader
page. **Telex:** 892084 BISPRS G.

Subscription rates: 1 year £15 UK and
£19 outside UK.

Student rates: 1 year £10 UK, and
£12.70 outside UK.

Distribution: Quadrant House, The
Quadrant, Sutton, Surrey SM2 5AS.
Telephone: 01-661 3248.

Subscriptions: Oakfield House,
Perrymount Road, Haywards Heath,
Sussex RH16 3DH. Telephone: 0444
459188. Please notify a change of
address.

USA: \$49.40 surface mail, \$102.60 air.
Business Press International (USA).
Subscriptions Office, 205 E. 42nd Street,
NY 10017.

USA mailing agents: Expeditors of the
Printed Word Ltd, 527 Madison Avenue,
Suite 1217, New York, NY 10022. 2nd
class postage paid at New York.

© Business Press International Ltd 1984
ISSN 0043 6062.

21 **FREEDOM — OR LICENCE?**

22 **COMMUNICATIONS COMMENTARY**
Drive by data 10.1MHz and s.s.b Cable and m.d.s.

24 **IEEE488 INTERFACE FOR THE BBC MICROCOMPUTER**
by A. G. Ray

27 **MICROPROCESSOR PROGRAMMING SIMPLIFIED**
by G. A. M. Labib

30 **EDISON'S ELECTRIC INDICATOR**
by D. Thackeray

32 **CIRCUIT IDEAS**
Fractional division Keyboard encoder Rotation sensor

36 **MICROCOMPUTER ORGAN INTERFACE — FORTH IMPROVISATION**
by R. Easson

40 **CURRENT FOLLOWERS**
by F. J. Lidgley

44 **LETTERS TO THE EDITOR**
Bus standards Energy saver Current dumping Jamming

52 **ACTIVE FILTER CALCULATIONS**
by J. L. Linsley Hood

55 **MORE ACTIVE FILTER CALCULATIONS**
by K. Kraus

57 **ELLIPTIC FILTER DESIGN USING TI59**
by K. Kraus

58 **COMPENSATED ACTIVE SUMMER**
by A. M. Soliman

60 **NEWS OF THE MONTH**
IT and Alvey Cruise reliability Micro User show

64 **IMPROVING COLOUR TELEVISION DECODING — TUBE LIMITATIONS**
by D. C. A. Read

69 **INDUCTANCE MEASUREMENT**
by D. R. Fownes

70 **MORSE ON A ZX81**
by D. Ibrahim

74 **NEW PRODUCTS**
Image processor Chroma-cad Bespoke firm wave Computer

RECORD DECKS 240 volt AC. Post £2				
Make	Model	Drive	Cartridge	Price
BSR	P170	Rim	Ceramic	£22
GARRARD	6200	Rim	Ceramic	£24
GARRARD	SP25	Rim	Magnetic	£36
GOLDRING	G102	Belt	Magnetic	£30

AUTOCHANGERS 240 VOLT			
BSR	Budget	Rim	Ceramic
BSR	Deluxe	Rim	Ceramic
BSR	Deluxe	Rim	Magnetic

THE "INSTANT" BULK TAPE ERASER £11.50 Post 95p
 Suitable for cassettes and all sizes of tape reeFs. AC mains 200/250V. Hand held size with switch and lead (120 volt to order). Will also demagnetise small tools.
Tape Head Demagnetiser only £5.



ALUMINIUM CHASSIS. 2 1/2in. deep 6x4 £1.75; 8x6 £2.20; 10x7 £2.75; 12x8 £3.20; 14x9 £3.60; 16x10 £3.80; 12x3 £2.20; 14x3 £2.50; 13x9 £2.80.
ALUMINIUM PANELS. 6x4 55p; 8x6 90p; 14x3 90p; 10x7 £1.15; 12x8 £1.30; 12x5 90p; 16x6 £1.30; 14x9 £1.75; 12x12 £1.80; 16x10 £2.10.
ALUMINIUM BOXES. 4x4x1 1/2 £1.20. 4x2 1/2x2 £1.20. 3x2x1 £1.20. 6x4x2 £1.90. 7x5x3 £2.90. 8x6x3 £3. 10x7x3 £3.60. 12x5x3 £3.60. 12x8x3 £4.30.
POTENTIOMETERS 5k/2meg. LOG or LIN. L/S 50p. DP 90p. Stereo L/S £1.10. DP £1.30. Edge Pot 5L SP 45p.

MINI-MULTI TESTER
 De luxe pocket size precision moving coil instrument. Impedance + Capacity - 4000 o.p.v. Battery included. 11 instant ranges measure: DC volts 5.25, 250, 500. AC volts 10, 50, 500, 1000. DC amps 0-250µA, 0-250mA. Resistance 0 to 60K ohms. **£7.50** Post 50p

De Luxe Range Doubler MULTI-METER **£19.50**
 50,000 o.p.v. 7x5x2in. 50 Micro Amp 43 Ranges, 1,000V, AC-DC, 20 MEG 10 amp DC Post £1

PANEL METERS 50µA, 100µA, 500µA, 1mA, 5mA, 50mA, 100mA, 500mA, 1 amp, 2 amp, 25 volt, VU 2 1/4x2 1/4. Stereo VU 3 1/4x1 1/8x1in. **£5.** p.p. 50p

RCS SOUND TO LIGHT CONTROL BOX
 Complete ready to use with cabinet size 9x3x5in. 3 channel, 1000 watt each. For home hi-fi disco OR KIT OF PARTS **£19.50** Post £1

BATTERY ELIMINATOR Mains to 9 volt D.C. 400MA. Smoothed, stabilised, safety cutout, 5x3 1/4x2 1/2in. **£5.** Post £1.

FAMOUS LOUDSPEAKERS						
MAKE	MODEL	SIZE	WATTS	OHMS	PRICE	POST
GOODMANS	HIFAX	7 1/2x4 1/4	100	4/8/16	£30	£2
GOODMANS	WOOFER	8in	25	4/8	£7.50	£1
GOODMANS	HB WOOFER	8in	60	8	£12.50	£1
WHARFEDALE	WOOFER	8in	30	8	£9.50	£2
CELESTION	DISCO/GROUP	10in	50	8/16	£19	£2
GOODMANS	HPG/GROUP	12in	120	8/15	£29.50	£2
GOODMANS	HPD/DISCO	12in	120	8/15	£29.50	£2
GOODMANS	HP/BASS	15in	250	8	£72	£3
GOODMANS	HPO/BASS	18in	230	8	£84	£4

RCS STEREO PRE-AMP KIT. All parts to build this pre-amp. Inputs for high, medium or low imp per channel, with volume control and PC Board. Can be ganged to make multi-way stereo mixers **£3.50** Post 65p

MAINS TRANSFORMERS		
		Post
250 0-250V 80mA, 6.3V 3.5A, 6.3V 1A		£7.00 £2
350 0-350V 250mA, 6.3V 6A CT		£14.00 £2
220V 25ma 6V 1amp £3.00	220V 45ma 6V 2 Amp	£4.00 £1
250V 60mA, 6V 2A		£4.75 £1

GENERAL PURPOSE LOW VOLTAGE			
Tapped outputs available		Price	Post
2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V		£6.00	£2
5-8 10-16V 1/2 amp.	£2.50	£1	
6V 1/2 amp.	£2.00	£1	
6-0.6V 1/2 amp.	£3.50	£1	
9V 400mA.	£1.50	£1	
9V 3 amp.	£5.00	£1	
9-0.9V 50ma	£1.50	£1	
9-0.9V 1 amp	£3.50	£1	
10-0.10V, 2 amps	£4.00	£1	
10-30 40V, 2 amps	£5.50	£1	
12V 100ma	£1.50	£1	
12V 750 ma	£2.50	£1	
12V 3 amps	£4.50	£1	
12-0-12V 2 amps	£5.50	£1	

300mF 12V 15p; 25V 20p; 50V 30p. 1200mF 76V 80p. 1000mF 12V 20p; 25V 35p; 50V 50p; 100V 120p. 2000mF 30V 42p; 40V 60p; 100V £1.40; 1500mF 100V £1.20. 2250mF 50V 70p. 3000mF 50V 65p; 4700mF 40V £1. 63V £1.80.

CAPACITORS WIRE END High Voltage
 .001, .002, .003, .005, .01, .02, .03, .05 mfd 400V 10p.
 .1MF 400V 14p. 600V 15p. 1000V 25p.
 .22MF 350V 12p. 600V 20p. 1000V 30p. 1750V 50p.
 .47MF 150V 10p. 400V 25p. 630V 30p.

HIGH VOLTAGE ELECTROLYTICS			
2/500V	45p	32+32+16/350V	90p
8/450V	45p	100+100/275V	50p
16/350V	45p	150+200/275V	50p
32/500V	95p	32+32+32/450V	95p
50/450V	95p	50+50+50/350V	95p
125/500V	£2	8+8/500V	£1

BAKER AMPLIFIERS BRITISH MADE
PA150 Watt MICROPHONE VOCAL AMPLIFIER £129
 4 channel mixing, 8 inputs, dual impedance, 50K-500 ohm, volume, treble, bass. Presence controls on each channel. Master volume control, echo send return socket. Slave sockets. Post £3.
150 Watt MIXER AMPLIFIER 4 Inputs £99
 Discotheque, Vocal, Public Address. Speaker outlets for 4, 8 or 16 ohms. Four inputs, 20 mv, 50K ohm. Individual volume controls "Four channel" mixing. Slave output. 16" x 8" x 5 1/2". Wt - 14lb. Master volume control. British made. 12 months' guarantee. 240V AC. 120V to order. All transistor and solid state. Post £2.
100 Volt Line Model, 150 watt £114. MONO SLAVE, 150 watt £80. Baker Stereo Slave 150 + 150 watt 300 watt Mono £125. Post £4.

BAKER MOBILE PA AMPLIFIER. All transistor, 60 watt RMS, 12v DC & 240V AC, 4 inputs 50k. Aux + 2 mics + 1 phono. Output 4-8-16 ohm + 100 volt line. £89 p.p. £2

BAKER PORTABLE DISCO 150 watt. Twin console + amplifier + mike and headphones + twin speakers £300. 300 watt £399. Carr. £30. Console + decks + pre-amp £95. Carr. £12.

PA CABINET SPEAKERS, Complete. 8 ohm 60 watt 17x15x9in. £27. Post £4. 4 or 8 or 16 ohm 75 watt 23x15x11in. £52. 90 watt 32x15x11in. £71. 150 watt £80. Carr. £10. Black vinyl covered with handles.

FAMOUS BAKER LOUDSPEAKERS						
MODEL	INCHES	OHMS	WATTS	TYPE	PRICE	POST
MAJOR	12	4-8-16	30	HI-FI	£16	£2
SUPERB	12	8-16	30	HI-FI	£26	£2
AUDITORIUM	12	8-16	45	HI-FI	£24	£2
AUDITORIUM	15	8-16	60	Woofers	£37	£2
GROUP 45	12	4-8-16	45	PA	£16	£2
OG 75	12	4-8-16	75	PA	£20	£2
GROUP 100	12	8-16	100	PA	£26	£2
DISCO 100	12	8-16	100	Disco	£26	£2
GROUP 100	15	8-16	100	PA	£35	£2
DISCO 100	15	8-16	100	Disco	£35	£2


SPEAKER COVERING MATERIALS. Samples Large S.A.E. B.A.F. LOUDSPEAKER CABINET WAFFLING 18in wide 35p ft

MOTOROLA PIEZO ELECTRIC HORN TWEETER, 3 3/8in. square **£5** 100 watts. No crossover required. 4-8-16 ohm, 7 1/8x3 1/8in. **£10**
HORN BOXES, complete 200 watt **£30.** 300 watt **£35.** Size 16x6x6in, post £4.

CROSSOVERS. TWO-WAY 3000 c/s 30 watt **£3.** 100W **£4.** 3-way 950 cps/3000 cps. 40 watt rating. **£4.** 60 watt **£6.** 100W **£8.**
LOUDSPEAKER BARGAINS. Please enquire, many others in stock.
 4 ohm, 5in, 7x4in, **£2.50;** 6 1/2in, 8x5in, **£3;** 8in, **£3.50;** 6 1/2in 20W **£7.50.**
 8 ohm, 2 1/2in, 3in, **£2;** 5x3in, 6x4in, 7x4in, 5in, **£2.50;** 3in, 10W **£4**
 8x5in, **£3;** 8in, **£4.50;** 10in, **£5;** 12in, **£6.** 8in 25W **£6.50** 60W **£12.50**
 15 ohm, 2 1/4in, 3 1/2in, 5x3in, 6x4in, **£2.50** 6 1/2in 10W **£5.** 8in **£4.** 10in **£7.**
 25 ohm, 3in, **£2;** 5x3in, 6x4in, 7x4in, **£2.50.** 120 ohm, 3 1/4in dia. **£1.**
 EMI 13 1/2x8in. Bass & Tweeter 4 or 8 ohm 10 watt **£8** pp £1.

RADIO COMPONENT SPECIALISTS

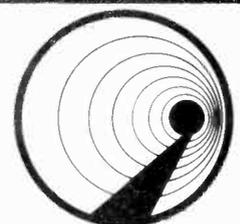Books and Components Lists 32p stamps. (Minimum post/packing charge 65p.) Access or Barclaycard Visa. Tel: 01-684 1665 for SAME DAY DESPATCH. Cash prices include VAT. WW-7



INSIGHT VISION SYSTEMS LIMITED
 Unit 1, Merebrook, Hanley Road, Malvern, Worcs WR13 6NP, England
 Tel (0684) 310001
 Telex 334480 INSIGT G

DESIGNERS AND MANUFACTURERS OF HIGH QUALITY CCTV CAMERAS & SYSTEMS



This self-contained black and white camera has been developed for use in situations where space is at a premium but the need for high quality is of paramount importance. Features include:

- LOW POWER CONSUMPTION
- UNPROCESSED VIDEO OUT TO EE LENS
- EXTERNAL LOCK
- AUTOMATIC VIDEO BLACK LEVEL
- INBUILT IRIS DRIVE SERVO
- HIGH RESOLUTION, LOW NOISE PICTURE
- MOTORIZED VIDICON RACKING
- 10 TO 32 VOLT DC OPERATION
- PLUG ON BATTERY AND REMOTE CONTROL MODULES
- EDGE ENHANCEMENT CORRECTION

We believe this is the smallest self-contained black and white TV camera available.
 Contact Andrew Smith on (0684) 310001

WW - 044 FOR FURTHER DETAILS

PPM5 20-PIN DUAL IN-LINE HYBRID

- Vcc 8.5V-35V at 3mA
- Only signal level and meter tolerance presets required
- Applications Note and full specifications on request
- +9dB IBA flasher with Mother Board 3



SURREY ELECTRONICS LTD.
 The Forge, Lucks Green Cranleigh, Surrey, GU6 7BG
 Tel: 0483 275997

APOLLO 68000 SYSTEM

Powerful 68000 runs at 10MHz without wait states. 16KB EPROM and 4KB fast static RAM, expandable. 24 line programmable parallel I/O port. RS232 programmable serial port. Comprehensive monitor in 2764 Eproms. Optional plug-in Eprom programmer card. Cross Assemblers for Z80 based microcomputers. Code can be developed, downline loaded to 68000, debugged, and then written into Eprom.


- ★ 10 MHz 68000 CPU Board £295+VAT
- ★ EPROM PROGRAMMER card £95+VAT
- ★ CROSS ASSEMBLER for Z80 hosts from £55+VAT

APOLLO SOFTWARE. Tel: (0635) 201150
 The Alley, Cold Ash, Newbury, Berkshire RG16 9NN

WW - 035 FOR FURTHER DETAILS

TELESCOPIC MASTS

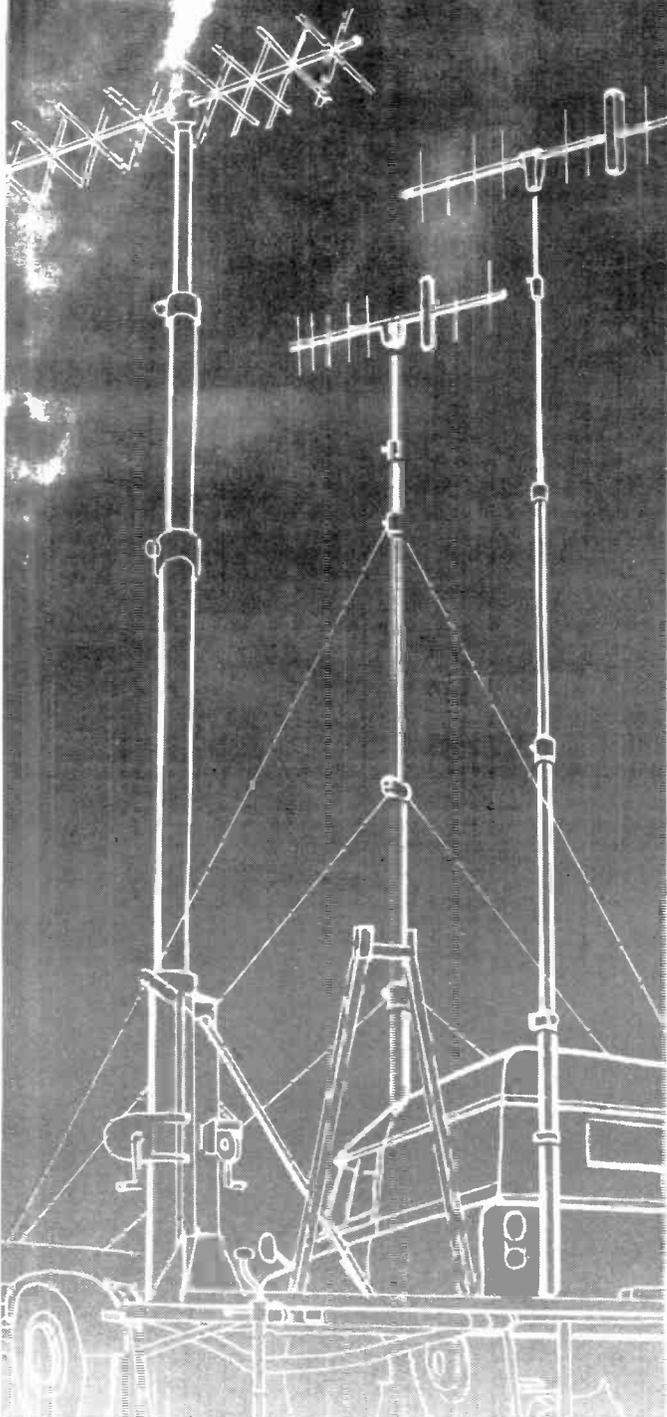
Pneumatically operated telescopic masts.
25 Standard models, ranging from 5 metres
to 30 metres.



Hilomast Ltd

THE STREET HEYBRIDGE — MALDON
ESSEX CM9 7NB ENGLAND
Tel. MALDON (0621) 5E430
Telex No. 995355

WW - 031 FOR FURTHER DETAILS

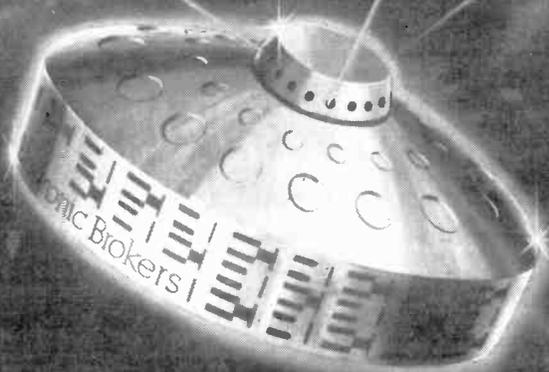

THE SOURCE OF ALL GOOD USED TEST EQUIPMENT

ANALYSERS

Hewlett Packard	
334A Distortion Analyser	£1200.00
3581A Wave Analyser	£1800.00
3582A Dual-Channel Spectrum Analyser	
0.02Hz-25.5KHz	£6650.00
5004A Signature Analyser	£550.00
Marconi	
TF2330A Wave Analyser	£950.00
Tektronix	
AA501 opt 01. Distortion 10Hz — 100KHz to Less than 0.0025%	£1450.00
DAS 9103 opt 01 02. Logic Analyser	£11,000.00
DF1 Display Formatter For 7D01	£850.00
308 Portable 6 Channel 20MHz Data Analyser	£2100.00
492 (opt 01, 08) Spectrum Analyser 50KHz-21GHz	£13000.00
492P (opt 01, 2, 3) Programmable Version of 492	£20000.00
7L12 Spectrum Analyser 100KHz-1.8GHz	£8000.00
7L13 Spectrum Analyser 1KHz-1.8GHz	£7500.00
7L18 Spectrum Analyser 1.5GHz-60GHz	£7500.00
TR503 Tracking Generator (for 492/496 series)	£3250.00
5L4N Spectrum Analyser 20Hz-100KHz	£2350.00
7D01 16 Channel 100MHz Sample Rate	£2450.00
7D02/01 Logic Analyser	£3950.00

OSCILLOSCOPES

Hewlett Packard	
1332A High Quality CRT Display 9.6 x 11.9cm	£1250.00
1740A 100MHz Dual Trace	£1500.00
1744A 100MHz Variable Persistence Storage	£3000.00
1809A 100MHz 4 Channel Plug in	£2000.00
1821A Timebase Plug in	£1000.00
Phillips	
PM3232 Dual Beam 10MHz	£495.00
PM3244 50MHz 4 channel	POA
Tektronix	
305 Portable battery scope/DMM, DT 5MHz	£975.00
335 Dual Trace 35MHz Small portable with delay T Base	£1300.00
200C Trolley for 400 Series	£120.00
465 100MHz Portable	£1500.00
466 100MHz Storage	£3750.00
7313 100MHz Storage Mainframe	£2225.00
5441 50MHz Variable Persistence Storage Mainframe	£1600.00
7603 100MHz Mainframe	£1950.00
7623 100MHz Storage	£2500.00
7704A Scope DC-200MHz Mainframe	£2850.00
7613 Storage Scope Mainframe DC-100MHz	£3250.00
7844 Dual Beam 400MHz Mainframe	£7750.00
7854 Waveform Processing Scope DC-400MHz	£9000.00
7904 opt 02, 03 500MHz	£5350.00

SIGNAL SOURCES

E H Labs	
132A Pulse Gen	£1200.00
139B Pulse Gen	£950.00
Hewlett Packard	
204C Oscillator	£200.00
204D Oscillator	£240.00
214A Pulse Gen	£950.00
11720A Pulse Modulator	£1950.00
612A Sig Gen	£1500.00

8004A Pulse Gen	£450.00
8011A-01 Pulse Gen	£895.00
8013B Pulse Gen	£750.00
8640A Sig Gen	£2750.00

Marconi	
TF2008 Sig Gen	£3000.00
TF2015 Sig Gen	£1350.00
TF2015/1 Sig Gen	£1350.00
TF2169 Pulse Modulator	£200.00
TF2120 Waveform Gen	£850.00

Wavetek	
148 Funct Gen	£650.00

TEKTRONIX PLUG INS

We stock a complete range of Plug Ins
for use with 7000 and 5000 series
Mainframes.

TEKTRONIX TM500 SERIES

We stock a very wide range of these
versatile modular equipments

MISCELLANEOUS

Avo	
Model 8 Multimeters	£80.00
VCM 163 Value Characteristic Meter	£495.00
7 Electricians Multimeter	£85.00
Bruel & Kjaer	
2209 Sound Level Meter	£850.00
1613 Filter	£400.00
Datalabs	
DL901 Transient Recorder	£750.00
DL905 Transient Recorder	£995.00
Fluke	
515A Portable Calibrator	£1750.00
845 AB Null Detector	£610.00
931B Diff V Meter	£1000.00
2020A-3-6 Printer	£500.00
5205A Precision Power Amplifier	£3500.00
8921A DMM	£695.00
Hewlett Packard	
467A Amplifier	£725.00
415E VSWR Meter	£950.00
3556A Psophometer	£850.00
3552A Trans Test Set	£1,500.00
4815A Vector Impedance Meter	£3850.00
Marconi	
TF1313A LCR Bridge	£775.00
TF2603 RF Millivoltmeter	£750.00
TF2604 Electronic Voltmeter	£350.00
TF2700 LCR Bridge	£295.00
Recal	
9514 Counter/Timer IEEE	£850.00
Tektronix	
106 Square Wave Generator 1nS risetime 10Hz-1MHz without accessories	£175.00
191 Constant Amplitude Generator	£250.00
832 Data Comms Tester	£925.00
833 Data Comms Tester	£1350.00
2701 Step Attenuator 50Ω 0.79dB in 1dB steps DC to 2GHz	£295.00

SPECIAL OFFER

TEKTRONIX. A complete
Measurement System.
TM506 c/w FG501, PG501,
PS501-1, DM501, SC501,
DC503. 1 YEAR WARRANTY.
£2000 THE LOT


Please note: Prices shown do not include VAT or carriage.

**Electronic Brokers Ltd., 61/65 Kings Cross Road,
London WC1X 9LN. Tel: 01-278 3461. Telex 298694**




WW - 202 FOR FURTHER DETAILS

AMPLIFIERS

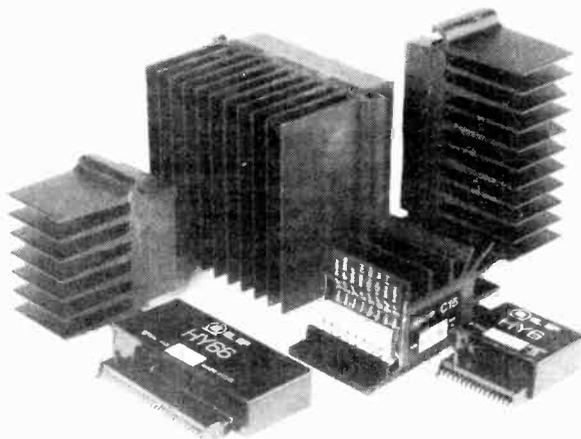

Over the last few years we have received feedback via the general public and industry that our products are from Taiwan, Singapore, Japan, etc... ILP are one of the few 'All British' electronics Companies manufacturing their own products in the United Kingdom. We have proved that we can compete in the world market during the past 12 years and currently export in excess of 60% of our production to over twenty different countries - including USA, Australia and Hong Kong. At the same time we are able to invest in research and development for the future, assuring security for the personnel, directly and indirectly, employed within the UK. We feel very proud of all this and hope you can reap some of our success.

I.L.Potts - Chairman

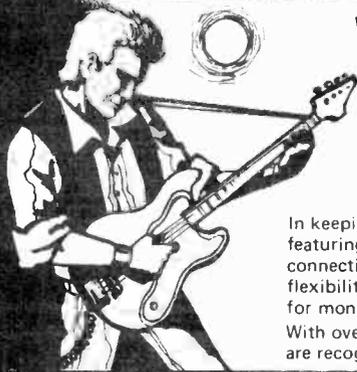

WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
HY30	15	4.8	0.015%	<0.006%	± 18	76 x 68 x 40	240	£8.40
HY60	30	4.8	0.015%	<0.006%	± 25	76 x 68 x 40	240	£9.55
HY60/60	30 + 30	4.8	0.015%	<0.006%	± 25	120 x 78 x 40	420	£18.69
HY124	60	4	0.01%	<0.006%	± 26	120 x 78 x 40	410	£20.75
HY128	60	8	0.01%	<0.006%	± 35	120 x 78 x 40	410	£20.75
HY244	120	4	0.01%	<0.006%	± 35	120 x 78 x 50	520	£25.47
HY248	120	8	0.01%	<0.006%	± 50	120 x 78 x 50	520	£25.47
HY364	180	4	0.01%	<0.006%	± 45	120 x 78 x 100	1030	£38.41
HY368	180	8	0.01%	<0.006%	± 60	120 x 78 x 100	1030	£38.41

Protection: Full load line. Slew Rate: 15V/ μ s. Risettime: 5 μ s. S/N ratio: 100dB. Frequency response (-3dB) 15Hz - 50KHz. Input sensitivity: 500mV rms. Input Impedance: 100K Ω . Damping factor: 100Hz >400.

PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY6	Mono pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY66	Stereo pre amp	Mic/Mag. Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY73	Guitar pre amp	Two Guitar (Bass Lead) and Mic + separate Volume Bass Treble + Mix	20mA	£15.36
HY78	Stereo pre amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT)

POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93
PSU 41X	1 or 2 HY60, 1 x HY60/60, 1 x HY124	£13.83
PSU 42X	1 x HY128	£15.90
PSU 43X	1 x MOS128	£16.70
PSU 51X	2 x HY128, 1 x HY244	£17.07

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance Ω	DISTORTION		Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
			T.H.D. Typ at 1KHz	I.M.D. 60Hz/7KHz 4:1				
MOS 128	60	4.8	<0.005%	<0.006%	± 45	120 x 78 x 40	420	£18.11
MOS 248	120	4.8	<0.005%	<0.006%	± 55	120 x 78 x 80	840	£31.89
MOS 364	180	4	<0.005%	<0.006%	± 55	120 x 78 x 110	1030	£45.53

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).
Slew rate: 20V/ μ s. Rise time: 3 μ s. S/N ratio: 100dB.
Frequency response (-3dB) 15Hz - 100KHz. Input sensitivity: 500mV rms.
Input impedance: 100K Ω . Damping factor: 100Hz >400.

'NEW to ILP' In Car Entertainments

C15

Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use.

£9.14 (inc. VAT)

Robust construction.

Mounts anywhere in car.

Automatic switch on.

Output power maximum 22w peak into 4 Ω .

Frequency response (-3dB) 15Hz to 30KHz. T.H.D. 0.1% at 10w 1KHz.

S/N ratio (DIN AUDIO): 80dB. Load Impedance 3 Ω .

Input Sensitivity and impedance (selectable) 700mV rms into 15K Ω 3V rms into 8 Ω .

Size 95 x 48 x 50mm. Weight 256 gms.

C1515

Stereo version of C15.

£17.19 (inc. VAT)

Size 95 x 40 x 80. Weight 410 gms.

ILP Electronics Ltd.

Graham Bell House, Roper Close
Canterbury CT2 7EP, Kent, England
Telephone: (0227) 54778. Telex: 965780

WW - 046 FOR FURTHER DETAILS

Keep those
Contacts **CLEAN**

BY USING A

DIACROM SPATULA



Manufactured in France
British Patents applied for

No other cleaner has all these advantages:—

1. Only 100% pure, natural diamond grains are utilised.
 2. Blades are treated with hard chrome to reinforce the setting of the diamond grains, to obviate loosening or breakaway during use. This process also prevents clogging of the diamonded surface by residues resulting from use.
 3. All diamonded blades are rectified to ensure an absolutely smooth surface by eliminating diamond grains which may rise above the surface. This eliminates all excessive scratching during use.
 4. All diamond grains are rigidly calibrated to ensure a perfectly uniform grain size of either 200, 300 or 400.
 5. The chrome gives a very weak co-efficient of friction and the rigidity of the nylon handle is calculated to permit proper utilisation and yet pliant enough to avoid undue pressures on highly delicate relays.
- Grain size 200, thickness 55/100 mm., both faces diamonded. For quick cleaning of industrial relays and switching equipment, etc.
 - Grain size 300, thickness 55/100mm., both faces diamonded. For smaller equipments, like telephone relays, computer relays, etc.
 - Grain size 400, thickness 25/100 mm., one face diamonded. For sensitive relays and tin-contacts. Two close contacts facing each other can be individually cleaned, because only one face of the spatula is abrasive.

Sole Distributors for the United Kingdom

SPECIAL PRODUCTS (DISTRIBUTORS) LTD

81 Piccadilly, London W1V 0HL. Phone: 01-629 9556

As supplied to the M.O.D., U.K.A.E.A., C.E.G.B. British Rail and other Public Authorities; also major industrial and electronic users throughout the United Kingdom.

UK and Export Agents: DIACROM, 17 Hancock Nunn House, London, NW3

WW - 033 FOR FURTHER DETAILS



Orange aid!

No! It's not a floating drinks dispenser, it's the Neptune hand-held radio case. Neptune is brilliant orange, it floats, it's waterproof and could save your life if your ICOM hand-held fell in the drink. Neptune cases are easily retrieved from:

Thanet Electronics Ltd.

143 Reculver Road Herne Bay Kent.

Tel: (02273) 63859/63850.

Sole U.K. Importers of ICOM equipment.

WW - 028 FOR FURTHER DETAILS

WIRELESS WORLD FEBRUARY 1984

DEC SALE

a selection from our
huge stocks. All items
reconditioned unless
otherwise stated.

WINTER '83/'84
CATALOGUE
NOW OUT

Send for your Free copy now.

DISK DRIVES

RK07ED 28MB NEW.....	£2,500
RK07PD 28MB NEW.....	£2,500
RL01A 5MB.....	£995
RM03AD 67MB NEW.....	£6,250
RM80 124MB.....	£9,500
RPO6AB 176MB.....	£7,500

UNIBUS OPTIONS

AR11 A/D Conv.....	£650
DB11A Bus Repeater.....	£250
DD11A/B Backplanes.....	£125
DD11CK Backplane.....	£275
DL11E Serial I/O.....	£395
DMC11AL I/P Link.....	£975
DMC11AR Network Link.....	£895
DMC11DA EIA Link.....	£575
DMC11MD I/Modem Link.....	£875
DMF32 Multiplexor.....	£2,750
DR11C Gen. Pur. I/O.....	£350
DR11K Digital I/O.....	£425
DR11W DMA I/F.....	£850
OU11DA Synch. I/F.....	£195
DZ11D 20mA MUX.....	£995
FP11C Floating Point.....	£2,750
FP11E Floating Point.....	£1,800
KE11B Ex. Arith.....	£595
KE44A CIS.....	£995
KG11A CRC Option.....	£350
KJ11A Stack Limit.....	£75

KK11A Cache Memory.....	£1,500
KMC11A Aux. Proc.....	£695
KT11C Memory Mgt.....	£750
KT11D Memory Mgt.....	£425
KW11L RT Clock.....	£75
KW11P Prog. Clock.....	£345
XY11 Plotter I/F.....	£275

PDP11 SYSTEMS

Just a few from the many configurations available.

PDP11/34A 256KB

2 x RK07 Disk Drives
H960 Cabinet
VT100 Console

£11,500

PDP11/40 32KW Core

2 x RK05 Disk Drives
H960 Cabinet
LA36 Console

£4,750

11/23AB Processor
128KB MDS Memory
DLV11J 4-line Interface
2 x RL01 Disk Drives
VT100 Console
Cabinet £7500

PRINTERS AND VDUS


ANDERSON JACOBSON

AJ832 30cps Daisy Wheel Printer with Keyboard, Stand and RS232 Interface.....	£750
AJ860 RD Desktop Matrix Printer 120 cps, RS232 Interface.....	£595

1620 KSR Daisy Wheel Printer EIA I/F.....	£795
1640 KSR Daisy Wheel Printer EIA I/F.....	£1,350
1650 Daisy Wheel Printer EIA I/F.....	£1,275

DATA PRODUCTS

B300 Band Printer.....	£2,750
M200 Matrix Printer with Stand.....	£1,875
2230 300 Lpm Drum Printer, U/L case, NEW.....	£2,500
2470 1200 Lpm Drum Printer NEW.....	£5,500

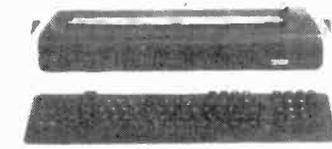

DEC

LA34 30 cps DECwriter IV from.....	£425
LA35 30 cps RD DECwriter II with stand, 20mA I/F.....	£250
EIA I/F.....	£275
LA36 30 cps <SR DECwriter II with stand, 20mA I/F.....	£295
EIA I/F.....	£325
LA180PD 180 cps Matrix Printer with stand, parallel I/F.....	£495

DIABLO

1345A RD Daisy Wheel Printer with stand, parallel I/F.....	£1,100
1355HS RD Daisy Wheel Printer, parallel I/F.....	£850

HAZELTINE

1410 VDU Terminal.....	£295
1420 VDU Terminal.....	£325
1500 VDU Terminal.....	£325
1510 VDU Terminal.....	£395
8020E Executive 80 VDU.....	£675
ESPRIT VDU Terminal.....	£395

QUME

S5/SS Daisy Wheel Terminal.....£625

RUTISHAUSEN

Sheet feeder for Diablo Daisy Wheel Printer.....£375

TEXAS

745 Portable 30 cps terminal with integral acoustic coupler.....£850

ADD 15% VAT TO ALL PRICES

Carrriage and Packing extra

Electronic Brokers Ltd., 61/65 Kings Cross Road, London WC1X 9LN. Tel: 01-278 3461. Telex 298694




Electronic Brokers

WW - 203 FOR FURTHER DETAILS

RADIOCODE CLOCKS SOLVE PROBLEMS

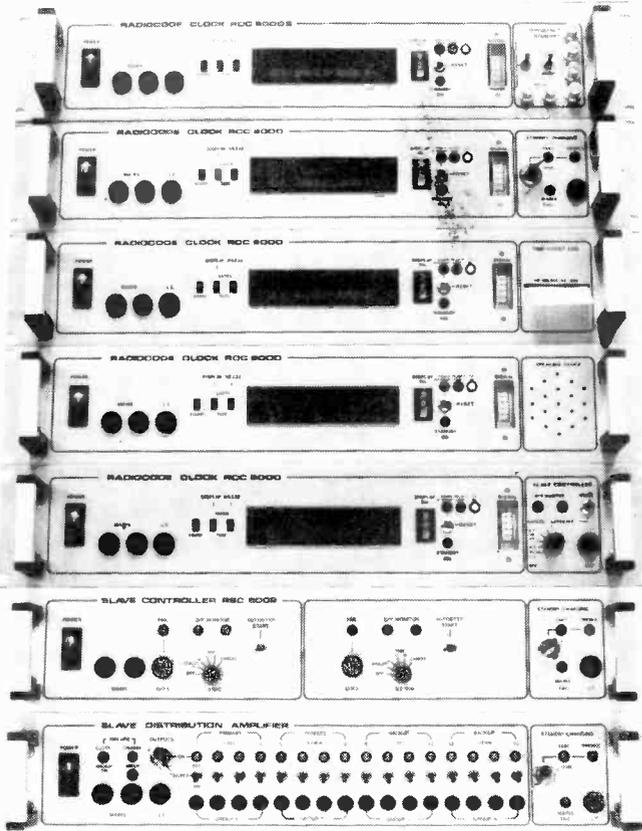ATOMIC TIME, FREQUENCY AND SYNCHRONISATION EQUIPMENT



NEW PHASE-MODULATION SYSTEMS

Until recently, atomic time and date information was only available on v.l.f. transmissions using amplitude modulation. The RCC 8000AM series of equipment uses these transmissions to offer high noise immunity and high accuracy, particularly at very long range.

The new RCC 8000PM series of equipment uses, for the first time, phase modulated transmissions with massive radiated powers of up to 2 Mega-Watts to offer long range, excellent noise immunity and no scheduled maintenance periods.

NEW PRODUCTS

The AM and PM series of Radiocode Clock equipment has been further expanded to include seven new models (from top) **8000S** – combined clock, frequency standard and optional stopclock. **Internal standby power supply** – with dual rate constant current charger. **Time-event log** – prints hours, minutes, seconds, milliseconds and day of year, on receipt of a log pulse. **Speaking clock** – time announcement or audio recording. **Slave controller** – total control of single-standard master/slave systems ie one pulse/sec. **Dual standard slave controller** – total control of two different and independent slave systems, ie. one pulse/sec and one pulse/half min. **Slave distribution amplifier** – maximum flexibility for the largest master/slave installations requiring dual standard operation, multiple circuits and complete master/slave backup.

NEW OPTIONS

A continuously expanding range of fully integrated software and hardware is available for both series of Radiocode Clock equipment. Standard options now include:

- IRIG B precision serial o/p
- RS232/V24 1mS resolution
- General purpose parallel o/p
- FSK record/replay system
- Keypad entry of alarm times
- Keypad entry of time/date
- Time code generators
- Intelligent slave systems
- Standard frequency outputs
- Stopclock operation
- Calibrated systems for increased accuracy

Radiocode Clocks Ltd*

Unit 19, Parkengue, Kernick Road Industrial Estate
Penryn, Falmouth, Cornwall. Tel: Falmouth (0326) 76007
(*A Circuit Services Associate Co.)

WW – 037 FOR FURTHER DETAILS

HOME CONTROL CENTRE

This kit enables you to control up to 16 different appliances by means of coded pulses in the mains wiring which may be decoded by special receivers anywhere in the house. The transmitter may be controlled manually or by the computer interface enabling your favourite micro to make your coffee in the morning, switch lights anywhere in the house, or your electric blanket in your bedroom. Just think of the possibilities – and no wiring!

The Kit comprises a transmitter with pre-drilled box and two receivers. **XK112 £42.00**

XK111 (additional receivers) **£10**

REMOTE CONTROL KITS

FOR A DETAILED BUKLET ON REMOTE CONTROL send 30p + 6" x 9" S.A.E.

These kits have been designed to enable infra-red remote control to be incorporated into virtually any application from switching car locks or alarms to controlling Hi-Fi or TV. The exact application will determine the interface circuitry (not supplied) between the receiver and the device to be controlled. In many cases this could be a relay or triac. General instructions and applications are supplied with the kits. The kits are coded and provide a high degree of noise immunity and security.

MK18 Transmitter Kit For use with MK11/MK12 Receivers and MK9/10/13 keyboards. Requires PP3 battery. Size 8x2x1.3cms. Range approximately 60ft. **£6.80**

MK11 Receiver Kit Mains powered Provides 10 latched plus 3 analogue outputs. Ideal for controlling audio amplifiers, TV or lighting circuits where control of lamp brightness is required. **£13.50**

MK12 Transmitter Keyboard **£4.35**

MK13 DC Controlled Stereo Amplifier Kit (control of stereo amplifier is required, the MK19 may be used, providing for remote control of base, treble and volume (or balance). This kit also includes a one of 10 decoder with LEDs for remote selection of programme or channel. May be connected between the pre-amp and power amp sections of almost any audio amplifier! **£10.70**

MK12 Receiver Kit **£13.50**

MK9 4-way Transmitter Keyboard **£1.90**

MK10 16-way Transmitter Keyboard **£5.40**

MK15 Dual Latched Solid State Relay **£4.50**

SEND SAE 9"x6" for FREE YELLOW CATALOGUE

XK114 OPTIONAL RELAY KIT

Kit includes one relay, PCB to accommodate up to four relays, terminal blocks, etc., to fit inside CT6000 box. Provides up to four 3amp 240V changeover contacts. Additional relays £1.65 each.

MICROPROCESSOR CONTROLLED MULTI-PURPOSE TIMER

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a seven-day cycle, eg. to control your central heating (including different switching times for weekends), just connect it to your system programme and set and forget it: the clock will do the rest!

Add 65p postage & packing + 15% VAT to total Overseas Customers.
Add £2.50 (Europe), £6.00 (elsewhere) for p&p.
Send S.A.E. for further STOCK DETAILS
Goods by return subject to availability
9am to 5pm (Mon to Fri)
OPEN 10am to 4pm (Sat)

COMPUTER SHOWROOM
TOP HARDWARE, LATEST SOFTWARE
PERIPHERALS, ACCESSORIES AND MUCH, MUCH MORE!

FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to

TK ELECTRONICS
11-13 Boston Road London W7 3SJ

TEL: 01-567 8910 ORDERS
01-578 9794 ENQUIRIES
01-578 2842 TECHNICAL AFTER 3PM

WW – 029 FOR FURTHER DETAILS

E.M.S. POWER SYSTEMS



Solve all your Power Problems by contacting E.M.S.

E.M.S. specialise in systems to eliminate your power problems.

Products range from 35VA switched square wave Power Packs to 1KVA fully uninterruptible sine wave systems.

E.M.S. also manufacture chargers which range up to 60 amps.

For further details please contact:

E.M.S. Manufacturing Limited
Chairborough Road
High Wycombe
Bucks
Tel: (0494) 448484


WW – 024 FOR FURTHER DETAILS

Essex Tiny Basic System

The Essex Tiny Basic Computer is an ideal choice for data acquisition and process control systems. Its crystal controlled timer and interrupts provide accurate timing and fast response to critical events, while the watchdog timer ensures reliable operation. Programs can be entered and tested from an RS232 terminal, then be copied into EPROM. Alternatively, instant ROM modules may be used both during development and for program storage.

£185

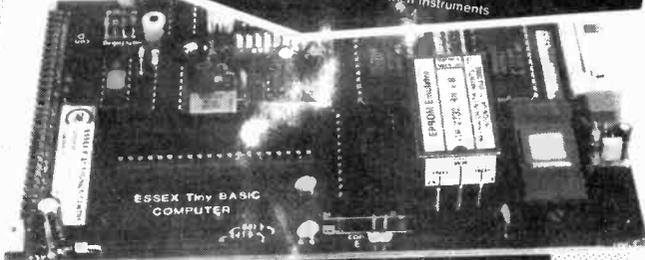
INSTANT ROM is the trademark of Greenwich Instruments



Essex Buffer Timer

A convenient method of buffering the I/O lines of the Essex Tiny BASIC Computer provides 24 inputs, 16 outputs and four hardware timers.


£78

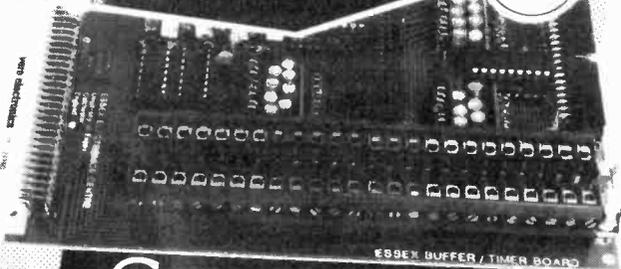

Essex Opto-Isolator

Connects to the Essex Tiny BASIC System bus to provide an additional 12 opto-isolated inputs and 12 opto-isolated outputs per card for safe connection to external equipment, isolation voltage = 1500 volts.

£150

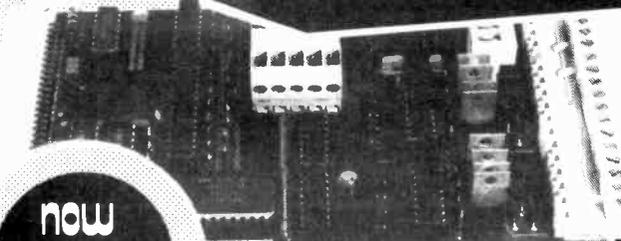

now available...

Essex Backplane

A four slot backplane with printer and terminal connectors to accept these cards. £35

'Alex'

A powerful software utilities package that provides the user with an enhanced editor and all the tools needed to program efficiently in assembly language.

* Text Editor * Assembler
* Disassembler * Debug Monitor
Supplied as a 4K EPROM with comprehensive manual. £65

all prices exclude V.A.T.
* substantial quantity discounts available
* carriage within U.K. £2

Essex Electronics Centre

Wivenhoe Park, Colchester, Essex CO4 3SQ
Telephone: Colchester (0206) 865089

WW - 053 FOR FURTHER DETAILS

Electronic Brokers Test Equipment DISTRIBUTORS



For detailed specifications of our complete range send for our new catalogue.

PHILIPS



Philips PM 2517X Handheld DMM £172

Multi-function, 4 digit autoranging with manual override. True RMS to 10Amp. Battery operation. Optional accessories extend measurement capabilities.

Philips PM 3207 15MHz Oscilloscope £325

Tough light-weight portable for field service work with big screen. Dual trace, TV triggering, X-Y operation, add and invert.




Philips PM 5107 Function Generator £295

Designed for audio and educational applications. Low distortion LF generator 10Hz to 100kHz, sine and square waveforms. TTL output.

Philips PM5503 Pattern Generator

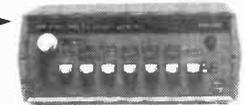£139 Small, light-weight for TV servicing. Five different test patterns for colour and monochrome. Tone for audio checking. Video output.



Philips PM 6667/01 Frequency Counter £290

High resolution 7 digit computing counter from 10Hz to 120MHz. Auto ranging on all waveforms. PM 6668/01 (£425) performs to 1GHz.

FLUKE

New Fluke 70 series Analog/Digital Handheld Meters All meters have 3 year warranty, all feature measurement functions of volts, ohms, amps and diode test.

JF 73 £65 DC accuracy 0.7% Autoranging

JF 75 £75 DC accuracy 0.5% Auto/manual ranging

JF 77 £95 DC accuracy 0.3% Touch hold function
Multi purpose holster





HAMEG



Hameg HM 103 10MHz Oscilloscope £158 Single trace, suitable for field service or home constructor. Two year warranty applies to this and all Hameg instruments.

Hameg HM 203-4 20MHz Oscilloscope £264

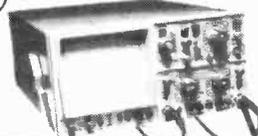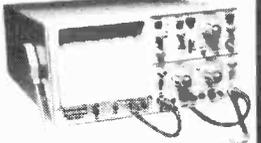Dual trace for general purpose applications in industry and education. X-Y operation, TV triggering, add/invert and component tester.



Hameg HM 204 20MHz Oscilloscope £365 High performance instrument with sweep delay. Versatile triggering to 50MHz, variable hold off control, Z modulation and internal illuminated graticule.

ICE

I.C.E. Microtest 80 Multimeter £19
Compact meter in robust case. 40 ranges of measurement with high sensitivity and accuracy. Large range of inexpensive accessories.



ADD 15% VAT TO ALL PRICES Carriage and Packing extra


**Electronic Brokers Ltd., 61/65 Kings Cross Road,
London WC1X 9LN. Tel: 01-8331166. Telex 298694**

Electronic Brokers

WW - 076 FOR FURTHER DETAILS

ambit INTERNATIONAL

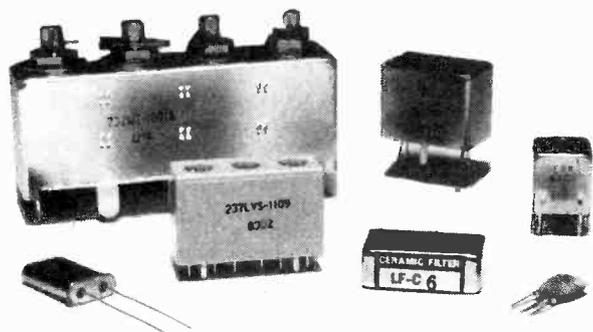PRACTICALLY ALL THE WIRELESS PARTS YOU'LL EVER NEED, GATHERED TOGETHER IN ONE CATALOGUE...




Coils, crystals, filters

TOKO coils, filters chokes. UNI crystals, filters, NTK and Murata ceramic filters. Probably the broadest stock ranges of these types of component in the world, and a full service from AMBIT INDUSTRIAL MARKETING to support the OEM with custom requirements.

Semiconductors for radio communications

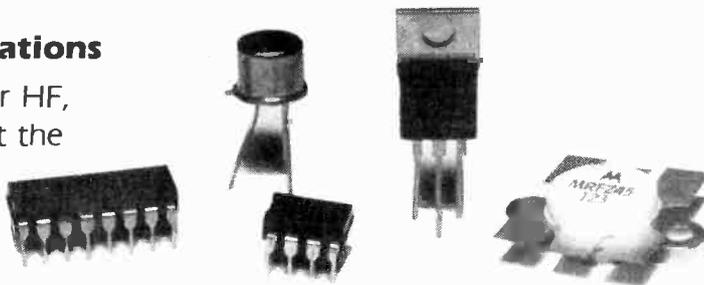ICs, Varicaps, FETS, MOSFETS, RF Power for HF, VHF, UHF. A broad selection that will meet the majority of requirements in receiver and transmitter designs




High Performance Coax Relays, switches etc.

PC and connector relays engineered to the highest standards, plus a broad range of electro-mechanical support including push, toggle, and keyboard switches, rotary switches, plugs sockets etc.

Test Gear and Tools

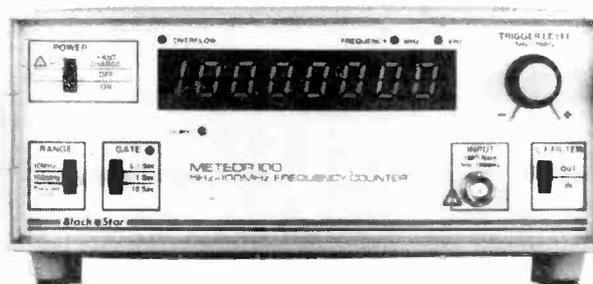New Black Star Frequency counters, Weller and Antex soldering tools, plus a wide selection of all types of equipment and tools for home and work.



Communications Technology

for the enthusiast
(and professional)


200 North Service Road, Brentwood, Essex CM14 4SG
Tel: Consumer (0277) 230909. Industrial (0277) 231616
Telex: 995194 AMBIT G.
Data: (0277) 232628 REWTEL» (300 baud duplex)

★ **REGIONAL SALES COUNTERS**
Solent Component Supplies, 53 Burrfields Road,
Portsmouth
Broxlea, Park Lane, Broxbourne, Herts

★ **SPRING CATALOGUE**
Parts, Project Packs, Test Gear
Info and 3 x £1 discount vouchers!
ORDER NOW for FEB Shipment — 80p

**ambit
INTERNATIONAL**
COMPONENTS CATALOGUE 80p

SATELLITE RECEIVING EQUIPMENT

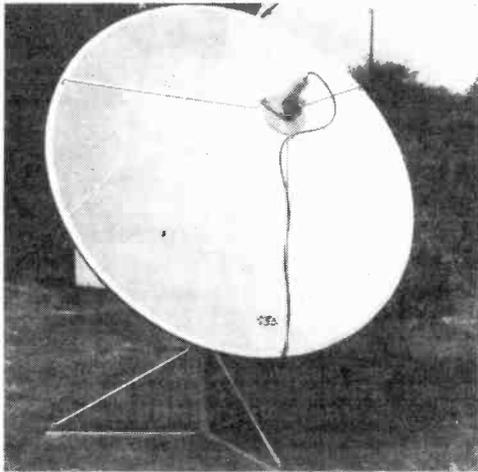


1.9M, 2.5M and 5M Harrison Dishes. Sat-Tec R5000 4GHz Receivers. Avcom COM-2B 4GHz Receivers. California Amplifier 4GHz LNAs. Chaparral Horns. Harrison Feed Horns. Demonstrations by appointment only.

For further details contact: Harrison Electronics, 22 Milton Road, Westcliff-on-Sea, Essex SS0 7JX. Telephone: Southend (0702) 332338.

WW - 018 FOR FURTHER DETAILS

NEW

Get started in Fibre Optics

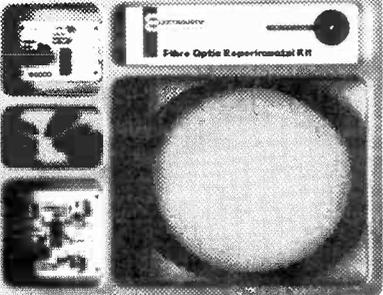

... with our new fibre optic experimental kit.

Features include:

- 0-10Mbit/s (NRZ) guaranteed to 15m with Polymer Cable. (Can be extended by using a glass fibre).
- TTL Compatible.
- No tools required to terminate cable.
- Fully tested modules.
- Complete with transmitter, receiver connectors and 5m of Polymer Cable.
- Also a full range of components for glass systems available.

Electroustic Ltd.
Hayward House, Northchapel, West Sussex, GU28 9HL
Tel: (042 878) 611/2. Telex: 858966

WW - 054 FOR FURTHER DETAILS

MIDWICH

COMPUTER COMPANY LIMITED

RICKINGHALL HOUSE, HINDERCLAY ROAD, RICKINGHALL, SUFFOLK IP22 1HH TEL DISS (0379) 898751

BBC Microcomputers

Model B	348 26
Model B +Disc Int	433 21

NB Credit cards are not accepted in payment for BBC Microcomputers

BBC Micro Econet

Full range of products available. Installation service available

BBC Compatible Disc Drives

Cased drives, finished to match the BBC Micro are supplied complete with connecting cables, manual and utilities disc.

All single cased drives may be expanded to dual configuration by the addition of the appropriate uncased mechanism

Disc capacity	Single	Dual	Uncased
100K 40T	175 00	315 00	140 00
200K 40T D S	225 00	420 00	195 00
400K 40/80T D S	285 00	525 00	240 00

Trade/quantity discounts are available

BBC3 Disc Interface 84 95
Please send for our BBC Micro price list. Full range of accessories available

Memories

2114L-20	D1 0.92
4116-15	D2 1.05
4116-20	D2 0.98
4118-15	D1 3.75
4164-15	D2 4.33
4164-20	D2 3.95
4416-20	D2 6.60
4564-15	5.25
5516-25	7.73
6116-3	D1 3.72
6116-LP3	D2 4.67
2532-45	D2 3.50
2708-45	D2 3.25
2716-35	D1 4.50
2716-45	D1 3.50
2716-3	D1 4.50
2732-35	D1 4.58
2732-45	D1 3.75
2764-30	D1 3.92
2764-250NS TI	3.92
2764-250NS BBC	5.95
2564-30	D2 6.00
27128-30	D2 24.50

Buffers

81LS95	0.95
81LS96	0.95
81LS97	0.95
81LS98	0.95
8T26A (6880AP)	0.78
8T28A (6889)	0.78
8T35 (6885)	0.78
8T37A (6887)	0.78
8T98 (6888)	0.78

Data Convertors

ZN435	D1 3.70
UPD7002	D1 4.65
ZN425E-8	D1 3.13
ZN426E-8	D1 1.67
ZN427E-8	D1 5.75
ZN428E-8	D1 4.38
ZN429E-8	D1 1.33
ZN432CJ-10	D1 25.98
ZN432E-10	D1 10.88
ZN433CJ-10	D1 20.98
ZN440	D1 47.43
ZN447	D1 6.70
ZN448	D1 5.75
ZN449	D1 2.35
ZN441	D1 40.32

Crystals

A111B 1MHz	4.22
A112A 1.008MHz	3.42
A113A 1.8432MHz	2.88
A116A 2.4576MHz	1.00
A169A 3.6864MHz	1.55
A120B 4MHz	0.85
A132A 6MHz	0.72
A140A 8MHz	1.00
A173A 9.8304MHz	1.40
A182A 19.6608MHz	2.07

UHF Modulators

UM1111 6MHz	2.17
UM1233 8MHz	3.25

Floppy Disc Controllers

8271P	53 33
FD1771P	D5 21 25
FD1791	D6 17 00
FD1793	D6 17 00
FD1795	D6 24 35
FD1797	D6 24 35
WD1691	D2 12 00
WD2143 01	D2 7 90

8080 Family

8085A	D4 3.07
8212	D4 1.50
8216	1.37
8224	1.92
8228	3.25
8251A	D5 2.50
8253	3.33
8255A	D5 2.50

Prices: all prices exclude V.A.T. and carriage. Please add these to your order.

All prices correct at time of going to press.



6500 Family

6502	D3 4.40
6502A	D3 4.67
6520	D1 2.67
6520A	D1 2.80
6522	D5 3.47
6522A	D5 4.40
6532	D2 5.33
6532A	D2 5.87

Linear & Interface Devices

6402	6.00
AY3-1015	D2 2.92
AY3-1270	6.56
AY3-8910	D6 4.48
AY5-3600	D2 7.37
DP8304	D1 1.92
L203	0.80
LF398	3.17
LM301AN	0.24
LM308AN	0.73
LM308N	0.84
LM311N	0.47
LM319	2.23
LM324N	0.32
LM339N	0.37
LM348N	0.53
LM358N	0.28
LM393N	0.34
LM725CN	1.33
LM741CP	0.18
LM747CP	0.48
LM748CP	0.22
MC1413P	D1 0.66
MC1416	D1 0.66
MC1458CP	0.25
MC1495L	7.13
MC1496P	0.65
MC1723P	0.32
MC3242A	5.25
MC3302P	0.40
MC3340P	1.97
MC3357P	1.56
MC3423PL	0.67
MC3441AP	D1 2.40
MC3446AP	D1 2.40
MC3447P	D1 3.32
MC3448AP	D1 3.32
MC3470P	5.23
MC3480P	D5 6.47
MC3487P	D1 1.50
MC14411	D1 8.52
MC14412	11.87
NE555P	0.19
NE556CP	0.45
RC3-2513L	D1 7.92
RC3-2513U	D1 7.92
SN75107BN	0.58
SN75110AN	0.68
SN75150P	0.72
SN75154N	0.87
SN75159N	1.19
SN75160AN	2.15
SN75161AN	2.35
SN75162AN	3.31
SN75172NG	1.64
SN75173N	1.21
SN75174	1.64
SN75175	1.21
SN75182	0.62
SN75183	0.62
SN75188	0.44
SN75189	0.44
SN75451BP	0.24
SN75452BP	0.24
SN75453BP	0.24

SN75454BP

SN75454BP	0.24
SN75458N	1.08
SN75491AN	0.46
SN75492AN	0.61
TL010CP	0.38
TL061CLP	0.28
TL062CP	0.47
TL064CN	0.89
TL066CP	0.28
TL071CP	0.47
TL074CN	0.91
TL081CP	0.24
TL082CP	0.41
TL084CN	0.85
TL091CP	0.41
TL092CP	0.60
TL094CN	1.37
TL487CP	0.55
TL489CP	0.55
TL494CN	1.96
TL496CP	0.30
TL507CP	1.02
ZN450E	5.25
ZN451E	6.38
ZN451KIT	25.65

DIL Sockets

Pin	Tin	Gold W/W
8	0.10	0.24 0.58
14	0.12	0.28 0.77
16	0.13	0.32 0.86
18	0.16	0.32 1.08
20	0.17	0.41 1.23
22	0.17	0.48 1.31
24	0.20	0.63 1.44
28	0.23	0.57 1.59
40	0.33	0.99 1.96

ZIF Sockets

24 Pin	5.80
28 Pin	6.35
40 Pin	8.45

Data sheets are available on items marked D

Prices are as follows
D1 0.75 D5 2.50
D2 1.00 D6 3.00
D3 1.25 D7 4.00
D4 2.00

A full range of the following products is carried in stock and is listed in our FREE catalogue

- ★ 74LS Series TTL
- ★ 4000 Series CMOS
- ★ TL Bipolar Memories
- ★ 9900 Series Micros
- ★ Crystals
- ★ IDC Card Edge & D-Type Connectors
- ★ Dip Jumpers
- ★ Monochrome & Colour Monitors (NIC & KAGA)
- ★ Eprom Programmers & Erasers
- ★ Custom Cable Assemblies

SPECIAL OFFER: SPECTRUM 32K UPGRADE KIT £24.95

Carriage Orders up to £199 are sent by 1st class post and £200+ by Securacor. 0-£1000 50-£100-£199 1 25-£200+ 5.00 by Securacor

Prices quoted (+ carriage charges) are exclusive of VAT and are subject to change without notice

Quantity Discounts are available on many products, please nng for details

Official Orders are welcome from Education Establishments, Government Bodies and Public Companies

Credit Accounts are available to others subject to status. Payment is due strictly net by the 15th of the month

Credit Cards are accepted (Access and Visa) for telephone and postal orders and NO SURCHARGE is made

Out of stock items will follow automatically, at our discretion, or a refund will be given if requested



SPECIAL TELEPHONE NUMBER FOR FAST, IMMEDIATE SERVICE, TELEPHONE YOUR ORDER TO: DISS (0379) 898751

For FREE CATALOGUE post to Midwich Computer Company Limited, Rickinghall House, Hinderclay Road, Rickinghall, Suffolk IP22 1HH

Name _____
Address _____
Telephone _____

WW - 026 FOR FURTHER DETAILS

JOIN UP WITH LITESOLD

Professional Soldering Equipment at Special Mail-Order Prices.

EC50 Mains Electronic Iron. £26.19




Features spike-free, solid state

proportional electronic temperature control inside the handle. Adjustable 280° to 400°C. Burn-proof 3-wire mains lead. Fitted 3.2mm Long-Life bit. 1.6, 2.4 and 4.7mm available. 240v a.c.

SK18 Soldering Kit. £15.24

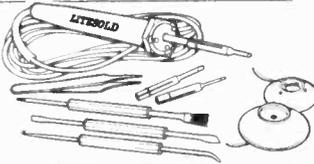Build or repair any electronic project. LC18 240v 18w iron with 3.2, 2.4, and 1.6mm bits. Pack of 18 swg flux-cored 60/40 solder. Tweezers. 3 soldering aids. Reel of De-Solder braid. In PVC presentation wallet.



ADAMIN Miniature Iron. £5.97




Possibly smallest mains iron in the world. Ideal for fine work. Slim

nylon handle with finger grip. Interchangeable bits available 1.2, 1.6, 2.4, 3.4 and 4.7mm. Fitted with 2.4mm. 240v 12w (12v available). Presentation wallet.


'L' Series Lightweight Irons. 12w £6.23.

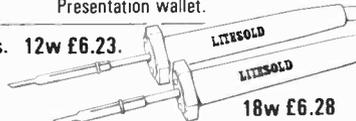High efficiency irons for all electronic hobby work. Non-roll handles with finger guards. Stainless steel element shafts. Screw-connected elements. Slip-on bits available from 1.6 to 4.7mm. LA12



model, 12w, 2.4mm bit. LC 18 Model, 18w, 3.2mm bit. 240v Std - 12v available. Presentation wallet.

Soldering Iron Stands. £5.11

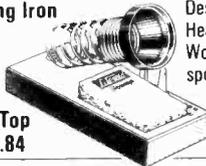

Designed specially for LITESOLD irons. Heavy, solid-plastic base with non-slip pads. Won't tip over, holds iron safely. With wiping sponge and location for spare (hot) bits.

No 5 stand for EC50 iron No 4 stand for ADAMIN miniature Iron No 3 stand for LA12 and LC18 Irons All same price

Spring/Top only. £1.84

Replacement Bits

For all above irons. Non-stick designs, machined from special copper alloy, with Inconel retaining rings. Two types - Chromium plated with copper face (for economy and ease of use) and Iron plated with

Pre-tinned face (Long Life). State tip size, iron and type.

	Copper	L/I
EC50	-	£1.58
Adamin 12 and LA12	92p	£1.56
LC18	£1.01	£1.70

BRADEWICK De-Solder Braid.



£1.05 per Reel

For simple, safe and effective de-soldering of all types of joint, using a standard soldering iron. Handy colour-coded packs of 1.5 metres in 3 widths: Yellow - 1.5mm, Green - 2mm, Blue - 3mm.

De-Solder Pumps. £6.19

High Quality version of increasingly popular type of tool. Precision made anodised aluminium body, plunger guard and high-seal piston. Easy



thumb operation. Automatic solder ejection. Conductive PTFE nozzle - no static problems.

Miniature Tool Sets



Top quality Japanese metric hardened and tempered tools. Swivel-top chrome plated brass handles.

Fitted plastic cases. 113 set - 6 miniature screwdrivers 0.9 to 3.5mm £2.70
227 set 5 socket spanners 3 to 5mm £2.80
305 set 2 crosspoint and 3 hex wrenches 1.5 to 2.5mm £2.70
228 set 20 piece combination:
5 open, 5 skt spanners, 2 crosspoint, 3 hex and 3 plain drivers, scriber, handle/holder £4.83

Microcutters. £3.21 Light weight hardened and precision ground. Flush cutting. Screw joint, return spring, cushion-grip handles. Safety wire-retaining clip.



Soldering Aids.



Set of 3 £3.63
Scraper/Knife, Hook/Probe, Brush/Fork. 3 useful double-ended aids to soldering/desoldering/assembly. In plastic wallet.

Solder. £0.90

Top grade resin flux cored 60/40 wire, 18 swg, in handy plastic dispenser. Approximately 3 metres (26gm).



ADAMIN Electric Stylus. £15.04

Writes like a ballpoint in Gold, Silver, Copper or 6 colours, on card, plastics, leather etc. Personalise wallets, bags, albums, books, electronic equipment, models... Operates at 4.5v from its own plug/transformer - totally safe. Supplied with coloured foils.




Prices include p&p and VAT. Send order with Cheque/P.O. Ring for Access/Visa sales, or ask for order forms.

LIGHT SOLDERING DEVELOPMENTS LTD. DEPT. W
97-99 GLOUCESTER ROAD, CROYDON CR0 2DN. 01 689-0574

WW - 030 FOR FURTHER DETAILS

TDS900

FORTH COMPUTER

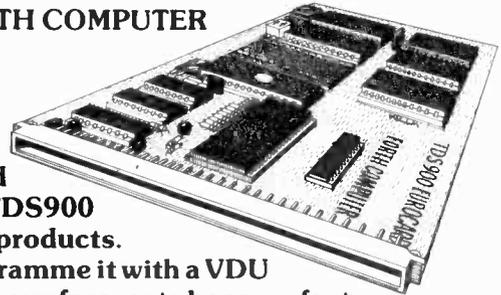

Build the TDS900 into products. Programme it with a VDU and your forecasts become fact.

Software costs are significant in all industrial applications of microprocessors. They cannot be amortised over the large quantities associated with personal computers and electronic games. This C-MOS embedded computer card aims at resolving this problem by including FORTH high level language programming and developmental facilities. The software can be written quickly and made to work correctly at lowest possible expense. Using a high level programming language rather than assembler gives a fast reaction time to market opportunities. Production products use the same board as employed in the prototypes.

No microprocessor development system is needed since the card contains a screen editor working with simple visual display units (VDUs). It also has the compiler for the FORTH source code. Debugging is inherent in the FORTH language and once the code is working, this can be output to a PROM programmer.

Use of C-MOS throughout has brought the power consumption down to 28mA, making the TDS900 especially suitable for portable and battery-driven applications.




Triangle Digital Services Limited

100a Wood Street, Walthamstow, London E17 3HX Tel: 01-520 0442

Visitors to our laboratories at are - welcome by appointment

WW - 032 FOR FURTHER DETAILS

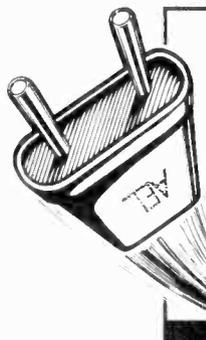

AEL AT SPEED

TO BE CRYSTAL CLEAR

Tel. 029-34-5353 Telex 87116 Aero G
MOD approved CAA approved

WW - 048 FOR FURTHER DETAILS

ELECTRONIC VALVES WANTED

All Types Receiving, Transmitting, Industrial

CV136 - CV138 - CV329 - CV345 - CV2209
- PL508 - PL509 - PL519 - PCL805 - PY500A

Phone/write to:
PYPE HAYES RADIO LTD.
606 Kingsbury Road
Birmingham B24 9PJ
021-373 4942

WW - 045 FOR FURTHER DETAILS

An in-depth series in understanding today's world of electronics.

From Texas Instruments.

SPECIAL OFFER
Order three books and get
any one of the
"Understanding" series
FREE.

The Understanding Electronics Series was specially developed and written to give you an in-depth knowledge of this world.

Each book is comprehensive, yet easy to understand. As informative for the electronics buff as for someone who's simply interested in what's going on today.

Together the library will give you the most complete range of titles available. Take advantage of our special offer and choose the book, or books you want from the titles below. You'll find whole new worlds of advanced technology unfolding before you.

1. Understanding Electronic Control of Energy Systems.

1st edition. Ref. LCB 6642. Covers motor, generator, power distribution, heating, air conditioning, internal combustion engine, solar and nuclear systems. Softbound 272 pages. £4.50.

2. Understanding Electronic Security Systems.

1st edition. Ref. LCB 720L. A complete guide covering the basics of hard wired, photosensitive, infrared, ultrasonic and microwave systems and their use in different applications. Softbound 128 pages. £2.95.

3. Understanding Solid State Electronics.

3rd edition. Ref. LCC 336L. The principles of solid state theory. It explains electrical movement, with intermediate tuition on the applications of solid state devices. Softbound 282 pages. £4.50.

4. Understanding Digital Electronics.

1st edition. Ref. LCB 331L. Describes digital electronics in easy-to-follow stages. It covers the main families of digital integrated circuits and data processing systems. Softbound 260 pages. £4.50.

5. Understanding Microprocessors.

1st edition. Ref. LCB 4023. An in-depth look at the magic of the solid state chip. What they are, what they do. Applications of 8-bit and 16-bit microprocessors, and design from idea to hardware. Softbound 288 pages. £4.50.

6. Understanding Computer Science.

1st edition. Ref. LCB 547L. This book tells you in everyday English how today's computer has been developed, what goes on inside it, and how you tell it what to do. Softbound 278 pages. £4.50.

7. Understanding Communications Systems.

1st edition. Ref. LCB 452L. An overview of all types of electronic communications systems. Softbound 282 pages. £4.50.

8. Understanding Calculator Maths.

1st edition. Ref. LCB 332L. Brings together the basic information - formulae, facts, and mathematical tools - you need to "unlock" the real power of the hand-held calculator. Softbound 230 pages. £4.50.

9. Understanding Optronics.

1st edition. Ref. LCB 5472. Optronics is the application of light and electronics to perform a wide range of useful tasks. From car headlights to missile guidance systems. Softbound 270 pages. £4.50.

10. Understanding Automotive Electronics.

1st edition. Ref. LCB 577L. Learn how electronics is being applied to automobiles. How the basic mechanical, electrical and electronic functions and the new microprocessors and microcomputers are being applied in innovative ways for vehicle drive train control, motion control and instrumentation. Softbound 288 pages. £4.50.

11. Understanding Telephone Electronics.

1st edition. Ref. LCB 714L. The powerful, positive thrust of electronics is making the telephone an even more important communication link. Conventional telephone fundamentals, analog and digital electronics, principles, newer digital techniques and hardware implementation are covered in this book. Softbound 288 pages. £4.50.

12. Understanding Electronic Control of Automation Systems.

1st edition. Ref. LCB 664L. This book is about automation - explains in simple language the subject of electronic control of automation systems, and to help the reader understand the terms, principles, techniques and effort used to automate processes. Softbound 280 pages. £4.50.

How to order

Fill in the coupon below or if someone else has already used it, simply:

1. List reference numbers and quantities required.
 2. Calculate total order value. Add £1.50 for postage and packing.
 3. Send the list, plus your cheque payable to Texas Instruments Ltd, PO Box 50, Market Harborough, Leicestershire.
- Allow 30 days for delivery.

WW - 038 FOR FURTHER DETAILS

To: Texas Instruments Limited, PO Box 50, Market Harborough, Leics

Please send me the following publications:

REFERENCE NO	QTY	REFERENCE NO	QTY
1		7	
2		8	
3		9	
4		10	
5		11	
6		12	

Free title choice: Understanding _____

I enclose a cheque for £ _____

Name _____

Company (if any) _____


Address _____

Please send me details of TI's range of Technical Books (please tick)

Registered office: Texas Instruments Ltd, Manton Lane, Bedford MK41 7PA
Registered number: 574102 England. WW2

TEXAS INSTRUMENTS 

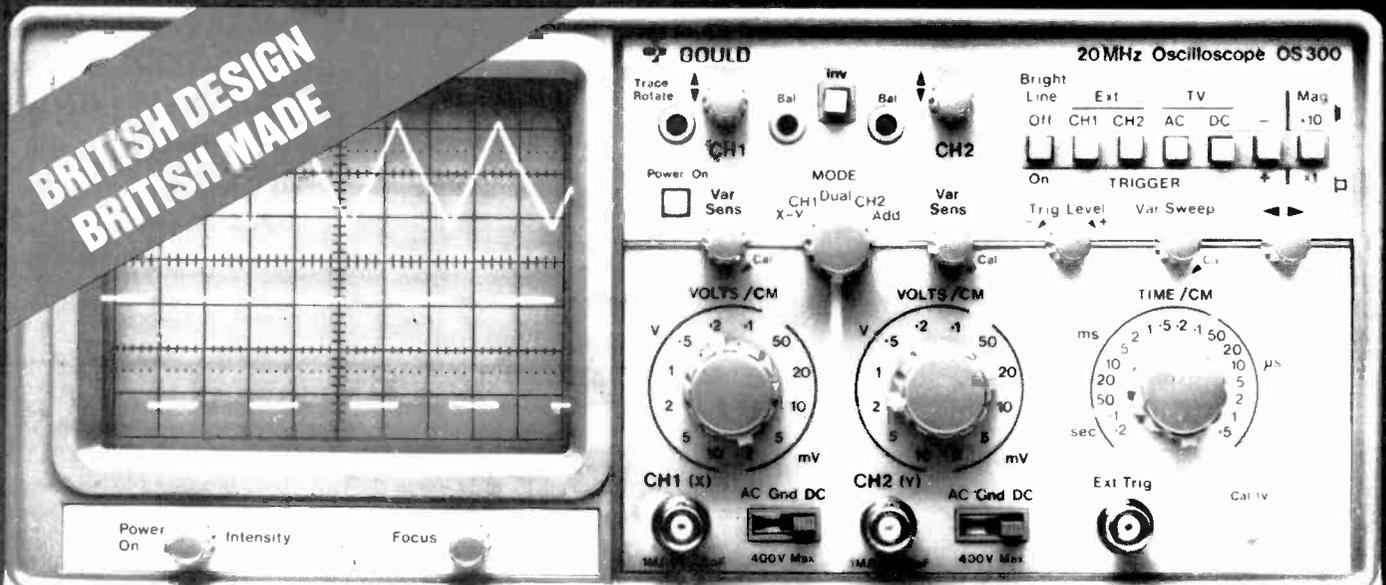GOULD OSCILLOSCOPES SET A HIGHER STANDARD



The Gould OS300 Dual Trace 20MHz Scope

A tough, professional instrument you can trust - at a price you can afford! ★ Max. sensitivity 2mV/cm. ★ Stepped and continuously variable attenuator and timebase controls. ★ D.C. coupled triggering and "active" T.V. sync separator. ★ 'Add' and 'Invert' for differential measurements. ★ X-Y facility.

Built to do more - safely, reliably and for longer. Ask for our 8-page data sheet for full details and applications information.


GOULD
Electronics

Design & Test Systems Division
Gould Instruments Limited
Roebuck Road, Hainault, Ilford, Essex IG6 3UE
Telephone: 01-500 1000 Telex 263785

WW - 010 FOR FURTHER DETAILS

BBC Micro Computer System OFFICIAL DEALER

Please phone for availability

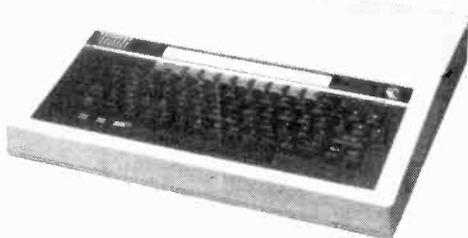

Software from ACORNSOFT/
PROGRAM POWER/GEMINI in
stock

BBC Model B £348
B + Econet £389
B + DFS £409
B + DFS + Econet £450
Carr £7
Model A to B Upgrade
Kit £75
Installation £15

LANGUAGE ROMs
BCPL Rom + Disc + Manual £87
PASCAL-T Rom £44

WORD PROCESSOR ROMs
VIEW 16k Rom £52
WORDWISE 8k Rom £32
Carr £1.50

FLOPPY DISC INTERFACE £95 & £15 installation

BBC COMPATIBLE DISC DRIVES

All drives are supplied with necessary cables
Single Drive without PSU: 100k £150; 200k £215; 400k
£225

Single Drive without PSU: 400k £240
Dual Drive with PSU: 2x100k £335; 2x200k £440*; 2x400k
£490

* These drives are switchable 40/80 drives.

40/80 Switch Module for 1x400k and 2x400k Drive £32

DISKETTES

40 track SS £15; 80 track SSDD £24

80 track DSDD £26

BBC FLOPPICLENE DRIVE HEAD

Cleaning kit with 50 disposable discs £14.50

Phone or send for our BBC leaflet

CASSETTE RECORDER

SANYO DR101 Data Recorder £34 + £2.50 car-
riage
BBC Tape Recorder £28.50 + £2.50 carriage
Cassette Lead £3 + £1 carriage
HOBBIT Floppy Tale £135 + £2.50 carriage
HOBBIT Zero Memory Option £25 + £1 car-
riage
Computer Grade C12 cassette 50p each. £4.50
for 10 £1 carriage

MONITORS


MICROVITIC 1431 14" RGB Std Res £215
MICROVITEC 1451 14" RGB Med Res £320
MICROVITEC 1441 14" RGB Hi Res £440
MICROVITEC 2031 20" RGB Std Res £287
KAGA VISION 12" RGB Std Res £230
KAGA VISION III 12" RGB Hi Res £385
KAGA 12" GREEN Hi Res £106
SANYO DM8112CX 12" Green Hi Res £99
All leads included. Carriage £7

TORCH Z-80 PACK

Your B.B.C. computer can be converted into a business machine at a cost slightly higher than an 800k disc drive. The Torch pack with twin disc drive and a Z80A processor card greatly enhances the data storing and processing capability of the computer. (NOTE: In BBC mode the disc pack functions as a normal BBC drive.) Z80A card comes with 64k of RAM and a CP/M compatible operating system. The system is supplied complete with a BBC owner's user guide, a Systems/Demo disc, a PERFECT software package and COMANEX, a business management game. The PERFECT software package comprises of a DATABASE, CALC, WORDPROCESSOR and SPELLER commercially valued at over £1,000. The complete package for only £730. Installation £20. Carr. £8.

PRINTERS & PLOTTERS

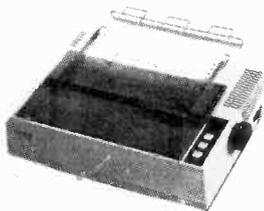EPSON FX80 £350
EPSON RX80 FT £270
EPSON FX-100 £555
NECPC80 23BE-N £310
SEIKOSHA GP 100A £170
SEIKOSHA GP 250X £199
SEIKOSHA GP 700A Colour £375
JUKI 6100 Daisy Wheel £365
MCP 40 Col Printer/Plotter £129
GRAPHICS Plotter £270
Carriage £7



ACCESSORIES

Parallel Printer Lead £10 + £1 carriage
Serial Printer Lead £8 + £1 carriage
Epson Serial Interface 2K £60 + £1 carriage
Epson Serial Interface £50 + £1 carriage
NEC Serial Interface £42 + £1.50 carriage
Epson Paper Roll Holder £17 + £1.50 car-
riage
FX80 Tractor Attachment £37 + £1.50 car-
riage
Paper Fanfold 2000 sheets £13.50 + £2.50
carriage

'TIME-WARP'

REAL-TIME-CLOCK/CALENDAR

A low cost unit that opens up the total range of Real-Time applications. With its full battery backup, possibilities include an Electronic Diary, automatic document dating, precise timing and control in scientific applications, recreational use in games, etc - its uses are endless and are simply limited by one's imagination. Simply plugs into the user port - no specialist installation required - No ROMS. Supplied with extensive applications software. £29.

BBC EPROM PROGRAMMER

A fully self-contained Eprom Programmer with its own power supply, able to program 2516, 2716/32/32A/64/128 single rail Eproms.
★ Personality selection is simplified by a single rotary switch.
★ Programming voltage selector switch is provided with a safe position.
★ Warning indicator to show programming in progress.
★ Programmer can read, blank check, program and verify at any address/addresses on the EPROM.
★ Simple menu driven software supplied on cassette (transferable to disc).
★ Full editor with ASCII disassembler.
Programmer complete with cables, software and operating instructions: £79.50 + £2 p. & p.

PRODUCTION PROGRAMMER: P8000

P8000 provides reliable gang programming of up to 8 EPROMS simultaneously with device sizes up to 16k x 8 bytes. Devices supported range from 2704 to 27128 in single and three rail versions. Simple menu driven operation ensures easy eprom selection and reliable programming in minimum programming times. £695 + £6 carriage.

BOOKS (no VAT; p&p £1/book)

Assembly Lang Prog. for BBC £8.95
Assembly Lang programming on BBC
Micro by Ferguson and Shaw £7.95
Basic Prog. for BBC £5.95
BBC An Expert Guide £6.95
Easy Programming on BBC £5.95
Further Programming on BBC £5.95
Introducing BBC Micro £5.95
Programming the BBC £6.50
30 Hour Basic £5.95
35 Educational Programs £6.95
BBC Sound & Graphics £7.95
Creating Adventure Programs £6.95
Discovering Machine Code £6.95
Structured Programming £6.50
The Friendly Computer Book BBC £4.50
Beyond Basic BBC £7.25

Large number of other titles stocked

EPROM ERASERS

UV1T Eraser with a built-in timer and mains indicator. Built-in safety interlock to avoid accidental exposure to the harmful UV rays. It can handle up to 5 eproms at a time with an average erasing time of about 20 mins. £59 + £2 p&p.
UV1 as above but without the timer £47 + £2 p&p.
UV140 up to 14 Eproms £61.
UV141 as above but with timer £79.

★ SPECIAL OFFER ★

2532	£3.50	27128-3	£15
2732	£3.50	4164-2	£4.50
2764-25	£5		

RH LIGHTPEN

The Acorn-approved superior design, with a programmable 'push tip' switch, status indicator LED and an interface box. Supplied complete with manual, full software and basic demo programs. Colour graphics programs will be available separately. £39.50.

SMARTMOUTH

The 'infinite vocabulary' self-contained speech synthesiser unit. Uses only 5-10 bytes per word - no ROMs required - simply plugs into the user port. (Has Aux. Audio output skt.). Supplied with Demo/Development programs and simple software instructions, £37 + £2 p. & p.

NEW COMPREHENSIVE CATALOGUE AVAIL-
ABLE - PLEASE SEND FOR PRICE LIST

CONNECTOR SYSTEMS

I.D. CONNECTORS

(Speedblock Type)			
No of ways	Header Plug	Recep- tacle	Edge Conn.
10	90p	85p	120p
20	145p	125p	195p
26	175p	150p	240p
34	200p	160p	320p
40	220p	190p	340p
50	235p	200p	390p

D CONNECTORS

No. of ways			
9 15 25 37			
MALE			
Solder	80p	105p	160p 250p
Angled	150p	210p	250p 365p
FEMALE			
Solder	105p	160p	200p 335p
Angled	165p	215p	290p 440p
Hoods	90p	85p	90p 100p
IDC 15-way plug	340p	Socket	400p
IDC 25-way plug	385p	Socket	450p

TEXT TOOL ZIF

SOCKETS 24-pin £5.75
28-pin £8.00 40-pin £9.75

DIL SWITCHES

4-way 70p 8-way 90p
6-way 85p 10-way 140p

JUMPER LEADS

24" Ribbon Cable with Headers			
1 end	14 pin	16 pin	24 pin 40 pin
2 ends	145p	165p	240p 350p
	210p	230p	345p 540p
24" Ribbon Cable with Sockets			
1 end	20-pin	26-pin	34-pin 40-pin
2 ends	160p	200p	280p 300p
	290p	370p	480p 525p

Ribbon Cable with D Conn.
25-way Male 500p Female 550p

RS 232 JUMPERS

(25-way D)
24" Single end Male £5.60
24" Single end Female £5.25
24" Female-Female £10.00
24" Male-Male £9.50
24" Male-Female £9.50

DIL HEADERS

Solder Type IDC Type
14pin 40p 100p
16pin 50p 110p
24pin 100p 150p
40pin 200p 225p

AMPHENOL CONNECTORS

36-way plug Centronics Parallel
Solder £5.25 IDC £4.95
36-way socket Centronics Parallel
Solder £5.50 IDC £5.20
24-way plug IEEE Solder £5
IDC £4.75
24-way socket IEEE Solder £5

RIBBON CABLE

(Grey/meter)
10-way 40p
16-way 60p
20-way 85p
26-way 120p
34-way 160p
40-way 180p
50-way 200p
64-way 280p

EURO CONNECTORS

DIN 41617	Plug	Skt.
21-way	160p	165p
31-way	170p	170p
DIN 41612		
2 x 32-way St. Pin	220p	275p
2 x 32-way Ang. Pin	275p	320p
3 x 32-way St. Pin	260p	300p
3 x 32-way Ang. Pin	375p	350p


TEST CLIPS

14-pin 275p 40-pin £6 16-pin £3

EDGE CONNECTORS

2x12-way (Vic)	0.1" 0.156"
2x18-way	350p
2x22-way	190p
2x23-way	175p
2x25-way	225p
2x28-way	190p
1x43-way	260p
2x43-way	365p
1x77-way	600p
S100 Conn	600p

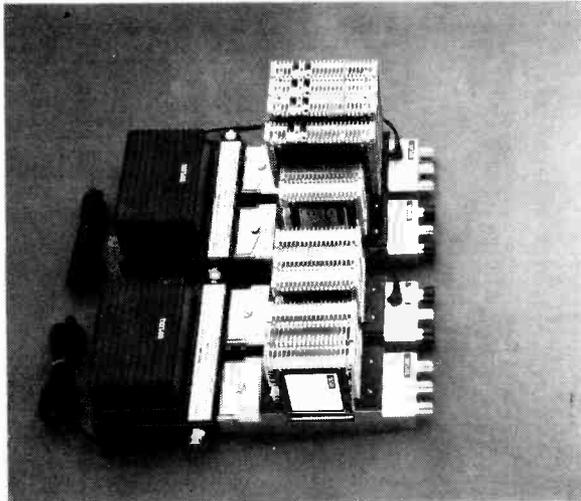CABLE T.V. HEAD END AND REPEATER AMPLIFIERS



CHANNEL CONVERTERS

TCUU UHF-UHF Single channel converter. Gain adjustable +2dB - 16dB. Maximum output +26dBmV. Crystal controlled oscillator. Power requirement 14V 25mA. (Quote Channels required).
TCUV As TCUU except UHF to VHF converter. (Quote Channels required).
TCVU As TCUU except VHF to UHF converter. (Quote Channels required).

SINGLE CHANNEL AUTOMATIC GAIN CONTROL AMPLIFIERS

TAG4863 Gain 48dB, maximum output 63dBmV. Regulator + or - 8dB. Power requirement 14V 210mA.
TAG4063 Gain 40dB, maximum output 64dBmV. Regulator + or - 16dB. Power requirement 14V 210mA.

SINGLE CHANNEL AMPLIFIERS

TSS4663 Gain 28-46dB adjustable. Maximum output 63dBmV. Power requirement 14V 170mA.
TSS3062 Gain 12-30dB adjustable. Maximum output 62dBmV. Power requirement 14V 26mA.

DRIVER AMPLIFIERS

TS1030FM FM driver amplifier. 10dB Gain. Maximum output 30dBmV. Power requirement 14V 10mA.
TS1030B3 Band III driver amplifier. 10dB gain. Maximum output 30dBmV. Power requirement 14V 10mA.
TS1030UHF UHF driver amplifier. 10dB gain. Maximum output 30dBmV. Power requirement 14V 10mA.
TS1040S Single channel UHF driver amplifier 10dB gain. Maximum output 40dBmV. Power requirement 14V 10mA. (Quote channel required).

DISTRIBUTION AMPLIFIERS

TE2042 Domestic distribution amplifier. 1 input, 1 output. Gain 20dB. Maximum output 42dBmV.
TE1638 Domestic distribution amplifier. 1 input, 2 outputs. Gain 16dB. Maximum output: 2 at 38dBmV.
TS2046 40-860MHz. Gain 20dB UHF, 18dB VHF. Maximum output 46dBmV.
TS2846 40-860MHz. Gain 28dB UHF, 22dB VHF. Maximum output 46dBmV.
TS2845 Separate UHF/UHF inputs. Gain 28dB UHF, 22dB VHF. Maximum output 46dBmV.
TS2054 40-860MHz. Gain 20dB UHF, 18dB VHF. Maximum output 54dBmV.
TS2060 40-860MHz. Gain 20dB UHF, 18dB VHF. Maximum output 60dBmV.
TS5565 Gain 55dB UHF, 55dB VHF, 42dB FM. Maximum output 65dBmV.

REPEATER AMPLIFIERS

TSC3600 Repeater. Gain 16-36dB UHF, 10-30dB VHF. Maximum output 60dBmV.
TSC3665 Repeater. Gain 16-36dB UHF, 10-30dB VHF. Maximum output 60dBmV.
TSC3060 Repeater. Gain 10-30dB VHF. Maximum output 60dBmV.

QUALITY AT LOW COST

TAYLOR BROS (OLDHAM) LTD

LEE STREET, OLDHAM - TEL. 061-652 3221 - TELEX 613911

WW - 054 FOR FURTHER DETAILS

Happy Memories

Part type	1 off	25-99	100 up
4116 200ns.....	1.25	1.15	1.10
4164 200ns.....	4.95	4.40	4.20
6116/2016.....	3.85	3.45	3.30
6116 150ns Low power.....	5.25	4.70	4.50
2716 450ns 5 volt.....	3.15	2.85	2.70
2716 450ns three rail.....	5.75	5.00	4.65
2732 450ns Intel type.....	3.85	3.45	3.30
2532 450ns Texas type.....	3.85	3.45	3.30
2764 250ns.....	Call	Call	Call
27128 300ns.....	Call	Call	Call

Z80A-CPU£2.99 Z80A-P10.....£2.99 Z80A-CTC.....£2.99
 6522 PIA.....£3.70 7805 reg.....£0.50 7812 reg.....£0.50

Low-profile IC sockets: Pins: 8 14 16 18 20 22 24 28 40
 Pence 12 13 14 16 18 22 24 27 38

Soft-sectored floppy discs per 10 in plastic library case:
 5 inch SSDD £17.00 5 inch SSDD £19.25 5 inch DSDD £21.00
 5 inch SSQD £23.95 5 inch DSQD £26.35

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or phone for list.

Please add 50p post & packing to orders under £15 and VAT to total
 Access & Visa welcome. 24-hr phone service on (054 422) 618
 Government & Educational orders welcome, £15 minimum
 Trade accounts operated, phone or write for details

HAPPY MEMORIES (WW)
 Gladestry, Kington
 Herefordshire HR5 3NY
 Tel: (054 422) 618 or 628

METAL FILM RESISTORS

1% Tolerance

High quality, British made (4)
 values, only 3p each. VAT, p&p
 inclusive.

SPECIAL OFFER
 5 of each 445 resistors
£12.60

SPECIAL 'POP' PACK
 50 pcs: 100R, 1K, 4K7, 10K, 47K, 100K,
 1M, 25 pcs: 330R, 470R, 1K5, 2K2, 3K3,
 22K. Total 500 pcs. £11.50.

Extra special 1 of each kit £22

ORION SCIENTIFIC LTD - 16 Orange Street - London WC2H 7ED

WW - 012 FOR FURTHER DETAILS

IN VIEW OF THE EXTREMELY RAPID CHANGE TAKING
 PLACE IN THE ELECTRONICS INDUSTRY, LARGE QUANTI-
 TIES OF COMPONENTS BECOME REDUNDANT. WE ARE
 CASH PURCHASERS OF SUCH MATERIALS AND WOULD
 APPRECIATE A TELEPHONE CALL OR A LIST IF AVAILABLE.
 WE PAY TOP PRICES AND COLLECT.

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, N. Finchley, London, N.12. 5 mins. from Tally Ho corner

Telephone 445 2713/0749

WW - 036 FOR FURTHER DETAILS

VISIT OR
PHONE
OPEN 6 DAYS
A WEEK
ALL STOCK
ON DISPLAY

HENRY'S AUDIO ELECTRONICS

Electronics
Specialists

Quantity
Enquiries
Invited

COMPUTERS • COMMUNICATIONS • TEST EQUIPMENT • COMPONENTS



THERMAL • MATRIX • LINE PRINTER
150 to 180 LPM • Full 96 CH ASCII • 40 CPL • 280 Opts P/L • Auto-underline • 50 Graphic Symbols • Back Space • Self Test • VU/HOR TABS • 7 x 10 Matrix • 4.4" Wide Paper • Bidirectional • 220/240V AC • Size Approx. 9.8 x 2.8 x 7.2 • SUITABLE FOR: TANDY • BBC • DRIC • NASCOM • GEMINI • ACORN • NEW BRAIN • DRAGON • etc. etc. (Your enquiries invited)
Complete with 3 rolls paper.
£99.95 inc. V.A.T. (UK C/P £1 05)
List price approx. £187 with paper



ALL MODELS 3 1/2
DIGIT UNLESS
STATED

DIGITAL MULTIMETERS

Free carry case (rotary controls)
* Carry case £2.95 (side buttons)
HAND HELD
K025C 13 range 0.2A DC 2 meg ohm £23.50
K030C 16 range 10A DC 2 meg ohm £26.95
K030C 26 range 1A AC/DC 20 meg ohm £29.50
K055C 28 range 10A AC/DC 20 meg ohm £33.50
METEX 3000 30 range 10A AC/DC 20 meg ohm £33.24
6010+ 28 range 10A AC/DC 20 meg ohm £34.40
7030+ As 6010 but 0.1% basic £41.30
K0615 16 range 10A DC 2 meg plus Hfe tester £39.95
DM2350 21 range 10A AC/DC 20 meg ohm miniature hand held auto range with case £49.95
Beckman T100 34 range 10A AC/DC 20 meg ohm £56.35
Beckman T110 As T100 plus Cont test etc £67.85
Sifam 2200B 21 range 2A AC/DC 20 meg ohm **SPECIAL OFFER** £29.95



SK6330 24 range P-B autorange 10A AC/DC buzzer with case £90.85
Metrix (ITT)
MX522 21 range 10A AC/DC £77.00
MX562 24 range 10A AC/DC Plus continuity buzzer £109.25
MX563 30 range true RMS Plus many features £178.25
MX575 4% Digit true RMS £201.25
BENCH MODELS
TM356+ 27 range LCO 10A AC/DC 20 meg £97.75
TM355+ 29 range LCO 10A AC/DC 20 meg £86.25
TM351+ 29 range LCO 10A AC/DC 20 meg £120.75
* Optional carry case £6.84
2001 28 range LCO 10A AC/DC plus 5 range cap Meter with case £108.00
TM451 4% digit LCO every facility (0.02%) £171.00
1503a 4% digit LCO every facility (0.05%) £171.00
1503Ha 0.03% basic version of above £189.00
1504 True RMS version £201.25
Sifam 2500 24 range LCO 2A AC/DC 20 meg **SPECIAL OFFER** £79.95

SANYO DM2112 HIGH RESOLUTION MONITOR

12" green display. Composite video. 1280 characters. Over 15 MHz B/W. 240V AC 34 w. 16" x 11 1/4" x 12 1/16". Alphabetic and Graphic display.
Usually £89.95 - £99.95 Price **£69.95** incl VAT (UK C/P & ins £2.05)



SAVE £20 TO £30

PROFESSIONAL SERIES COMPUTERS IN STOCK
GEMINI • GALAXY • NASCOM • 80 Bus multiboards.
Complete and part systems to suit your needs. Frames, boards, power supplies, keyboards, disc systems, etc. FOR THE PROFESSIONAL USER - SEND FOR DETAILS

DELUXE 69 KEY ASCII KEYBOARD
General purpose steel plate, output, redelible, +5 and -12 volt, neg. strobe pulse. 4 user definable keys. Shift and control keys. etc.
£42.95 incl VAT (UK C/P £85p)
ALSD Type 756A £51 Type 771 £66 incl VAT

3 NEW SOFTWARE PRODUCTS
MOIS (C) INTELLIGENT DIS ASSEMBLER For all CP/M based machines £57.50 incl VAT
DISKPEM (C) Version 3. Lost cost word processor. For Gemini and others (please enquire) provides pseudo high resolution graphics. £17.25 incl VAT
PLUS range of overlays available for Diskpen. Send for details of all above.
(C) Copyright Cubegate Ltd 1983. All rights reserved)

I.T.T. 2020 CABINET
Complete PROFS SIGNAL Case beautifully constructed with cut out for one CHERRY keyboard plus ample room to house a COMPLETE SYSTEM and power supply. Complete with fittings. (Case top detachable). Unit is silver-grey in colour. Robust construction. Sloping front with side ventilation. Ideal for NASCOM, ACORN, TANGERINE or your own system. Size 18" x 15" x 4" (front slopes)
£27.50 incl VAT (UK C/P £25.00)

COMPUTER POWER SUPPLY
Switched mode, stabilised, self protecting, S/C protected, etc. 220/240 V AC - 5V 3.3A - 12V 2.4A 40% cycle. -5V 0.5A - 12V 0.5A. Suitable Apple replacement
£57.50 incl VAT (UK C/P £1.50)

PRESTEL ADAPTOR 3 card set with data etc (P/S +/- 12V and -5V) £69.95 incl VAT
CHERRY ADD-ON KEYPAD 16 button pad, non encoded £5.95

TOROIDAL TRANSFORMER
100 watts isolation 230/240 V AC plus 0-8 0V 4A 15-0 15V 0.645A 30V 0.16A. Size approx 4 1/2" dia. x 1 1/2"
£7.95 (UK C/P 75p)

MODEM CARD
BT approved ready assembled unit with data and accessories £39.95 incl VAT

SELECTION OF SPECIAL OFFERS - QUANTITIES AVAILABLE FROM HENRY'S

POCKET RADIATION DETECTORS
Dosimeter for Gamma and X-Rays. 0-5r
£6.95 Quantities available

CENTAUR FANS
CU7983 115V 50/60HZ 12/13W Impedance protected (use 2 in series for 230V) 4" x 4" x 1 1/2"
Two for £10.00 (UK C/P 70p)
220/240V 'as new' £5.50 each (UK C/P 50p)

CASSETTE MECHANISMS
Fitted counter, motor, record and erase heads, solenoid, etc. Brand new available 6V DC or 12V DC (state which)
£5.95 (UK C/P 65p)

ASTEC UHF MODULATORS
UM1233 cased for computers, etc. £3.50 (UK C/P 40p)

TOROIDAL POWER SUPPLY
12V and 5V 1 amp max stabilised. 6 1/2" x 2 1/2" x 1 1/2"
£5.95 (UK C/P 65p)

TRANSISTOR TESTER
Direct reading PNP-NPN, etc. TCI £21.95 (UK C/P 65p)
DIGITAL THERMOMETER
TH301 LCO 50 C to -75.0 with thermocouple £68.43

ALSO STOCKED - LARGE RANGES All semiconductors, valves, relays and other components. Plus millions of Res. Caps, presets, pots, etc. for bulk and export users.

ULTRASONIC TRANSDUCERS with cables. 40 KHZ £2.95 per pair (UK C/P 40p)
MULLARD MODULES (UK C/P 65p per 1.3) LP1171 IF and LP1179 AM/FM Tuner £5.00 pr £5.75 LP1186 Varicap Tuner £5.00 LP1157 AM Tuner £2.50

FREQUENCY COUNTERS
PFM200A 200 MHz hand held pocket 8 digit LED with batteries £77.60
MET100 8 digit LED bench 2 ranges 100 MHz with AC Adaptors £102.35
MET600 8 digit LED bench 3 ranges 600 MHz with AC Adaptors £132.25
MET1000 8 digit LED 3 ranges 1 GHz with AC Adaptors £182.95
TF400M 8 digit LCD 40 MHz with batteries £126.50
TF200M 8 digit LCD 200 MHz with batteries £166.75
* Optional carry case £6.84 AC Adaptor £4.95
Probe kits x1 £7.95, x10 £9.45, x1 -x10 £10.50
Prescalers - Extended range of most counters
TP600 600 MHz £43.00
TP1000 1 GHz with AC Adaptors £74.00

ELECTRONIC INSULATION TESTER
YF501 500V/0-100m with carry case £68.00
Large range stocked. Ask for leaflet

SIGNAL GENERATORS (UK C/P £1 00)
FUNCTION: All sine/square/triangle/TTL etc.
TG101 0.02HZ-200KHZ £113.85
TG102 0.2HZ-2 MHz £166.75
PULSE
PG105 Various facilities 5 Hz-5 MHz £97.75
AUDIO: Multiband Sine/Square
LAG27 10 Hz to 1 MHz £90.85
A £202A 20 Hz to 200 KHz (list £94.50) £83.50
LAG 120A 10 Hz-1 MHz Low Distortion £159.85
RF
SG402 100 KHz to 30 MHz (list £79.50) £69.50
LSG17 100 KHz to 150 MHz (450 MHz HARM) £79.35

OSCILLOSCOPES
Full specification any model on request. SAE by post
'HM' Series HAMEG: 'SC' THANDAR: 'CS' TRIO: '3' CROTECH: 'V' HITACHI SINGLE TRACE UK C/P £3.00
3030 15 MHz 5mV. 95mm tube plus component tester £177.10
SC110A Miniature 10 MHz battery portable. Post free Nicads £12.50 AC adaptor £6.69
HM103 15MHz 2mV. 6 x 7 display plus component tester C/P £3.00
DUAL TRACE (UK C/P £4.00)
HM203/4 Dual 20 MHz plus component tester £303.60
CS1562A Dual 10 MHz (List £321.00) £269.50
31321B Dual 20 MHz - component tester £325.45
CS1566A Dual 20 MHz All facilities (List £401.35) £349.50

MULTIMETERS (UK C/P 65p)
HM1028B 20K/V 10A DC 22 range & cont buzzer £13.50
C7081 50 K/V Range Doubler 10A DC Total 36 Ranges **SPECIAL OFFER** £12.50
TMX500 23 ranges 30K/V 12A DC plus cont. buzzer £23.95
NH50R 20K/V 22 range pocket £10.95
830A 26 range 30K/V 10A AC/DC overload protection, etc. £23.95
360TR 23 range 100 K/V Large scale 10A AC/DC plus Hfe £39.95
AT100 10A AC/DC 31 range 100 K/V deluxe £33.50
AT1020 18 range 20K/V. Deluxe plus Hfe tester £18.95
YH560TR 19 range 20K/V plus Hfe tester £15.95
Metrix Professional multimeters in stock 3 models from £74.75

HM204 Dual 20 MHz plus component tester sweep delay £419.75
HM705 Dual 70 MHz sweep delay £676.00
V212 Dual 20 MHz £399.25
V222 Dual 20 MHz plus extra facilities £391.00
V422 Dual 40 MHz portable £586.50
V203F Dual Trace 20 MHz sweep delay £408.25
V353F Dual 35 MHz Sweep delay £569.25
V134 Dual Trace 10 MHz storage £1092.50
All HITACHI, CROTECH & TRIO MODELS AVAILABLE
OPTIONAL PROBE KITS • With probes
X1 £7.95 X10 £9.45 X1 - X10 £10.50 X100 £12.95

VARIABLE POWER SUPPLIES (UK C/P £1 00)
PP241 0/12/24V 0/1A £35.00
PP243 3 amp version £59.95
230N 0/30V 1A Twin meter £99.50

AC CLAMPMETER
ST300 0/300A 0/600 V AC. 0/1 Kohm 9 ranges With carry case (UK C/P 65p) £28.50

LOGIC PROBES
LP10 10 MHz £26.95
DLP50 50 MHz with carry case and accessories £49.95

HIGH VOLTAGE METERS
Direct reading 0/40 KV 20K/V £23.00 (UK C/P 65p)
Also 0/30, 0/45KV version £39.95

Cubegate Ltd **RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL** Official orders welcome. (Subject to confirmation)


HENRY'S 404-406 Edgware Road, London, W2 1ED
Computers 01-402 6822 • Equipment 01-724 0323 • Components 01-723 1008
AUDIO ELECTRONICS 301 Edgware Road, London, W2 1BN
01-724 3564 (All post to 301 Edgware Road, London, W2 1BN)

ORDER BY PHONE OR BY POST OR CALL IN AND SEE FOR YOURSELF
Please state type required. Send large S.A.E. (20p UK). Test Equipment Computers Audio Communications Components Schools, Colleges, Companies Export Free on Written Request
Official orders welcome. (Subject to confirmation)
Order by Post with CHEQUES/ACCESS/VISA or you can telephone your order.

TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

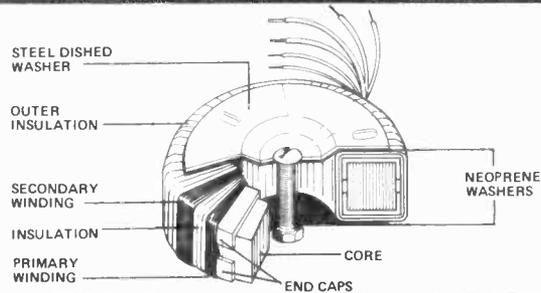Our large standard range is complemented by our **SPECIAL DESIGN** section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.



15 VA 62 x 34mm Regulation 19%		50 VA 80 x 35mm Regulation 13%		120 VA 90 x 40mm Regulation 11%		225 VA 110 x 45mm Regulation 7%		500 VA 140 x 60mm Regulation 4%	
SERIES	SECONDARY	2x010	6+6 4.16	4x010	6+6 10.00	6x012	12+12 9.38	8x016	25+25 10.00
No.	Volts	2x011	9+9 2.77	4x011	9+9 6.66	6x011	18+18 6.25	8x017	30+30 8.33
	Current	2x012	12+12 2.08	4x012	12+12 5.00	6x015	22+22 5.11	8x026	40+40 6.25
0x010	6+6 1.25	2x013	15+15 1.66	4x013	15+15 4.00	6x016	25+25 4.50	8x025	45+45 5.55
0x011	9+9 0.83	2x014	18+18 1.38	4x014	18+18 3.33	6x017	30+30 3.75	8x033	50+50 5.00
0x012	12+12 0.63	2x015	22+22 1.13	4x015	22+22 2.72	6x018	35+35 3.21	8x042	55+55 4.54
0x013	15+15 0.50	2x016	25+25 1.00	4x016	25+25 2.40	6x026	40+40 2.81	8x028	110 4.54
0x014	18+18 0.42	2x017	30+30 0.83	4x017	30+30 2.00	6x025	45+45 2.50	8x029	220 2.27
0x015	22+22 0.34	2x018	110 0.45	4x018	35+35 1.71	6x033	50+50 2.25	8x030	240 2.08
0x016	25+25 0.30	2x029	220 0.22	4x028	110 1.09	6x028	110 2.04		
0x017	30+30 0.25	2x030	240 0.20	4x029	220 0.54	6x029	220 1.02		
				4x030	240 0.50	6x030	240 0.93		
(encased in ABS plastic)		80 VA 90 x 30mm Regulation 12%		160 VA 110 x 40mm Regulation 8%		300 VA 110 x 50mm Regulation 6%		625 VA 140 x 75mm Regulation 4%	
30 VA 70 x 30mm Regulation 18%	0.45Kg	3x010	6+6 6.64	5x011	9+9 8.89	7x013	15+15 10.00	9x017	30+30 10.41
1x010	6+6 2.50	3x011	9+9 4.44	5x012	12+12 6.66	7x014	18+18 8.33	9x018	35+35 8.92
1x011	9+9 1.66	3x012	12+12 3.33	5x013	15+15 5.33	7x015	22+22 6.82	9x026	40+40 7.81
1x012	12+12 1.25	3x013	15+15 2.66	5x014	18+18 4.44	7x016	25+25 6.00	9x025	45+45 6.94
1x013	15+15 1.00	3x014	18+18 2.22	5x015	22+22 3.63	7x017	30+30 5.00	9x033	50+50 6.25
1x014	18+18 0.83	3x015	22+22 1.81	5x016	25+25 3.20	7x018	35+35 4.28	9x042	55+55 5.68
1x015	22+22 0.68	3x016	25+25 1.60	5x017	30+30 2.66	7x026	40+40 3.75	9x028	110 5.68
1x016	25+25 0.60	3x017	30+30 1.33	5x018	35+35 2.28	7x025	45+45 3.33	9x029	220 2.84
1x017	30+30 0.50	3x028	110 0.72	5x026	40+40 2.00	7x033	50+50 3.00	9x030	240 2.60
		3x029	220 0.36	5x028	110 1.45	7x028	110 2.72		
		3x030	240 0.33	5x029	220 0.72	7x029	220 1.36		
				5x030	240 0.66	7x030	240 1.25		

Why a Toroid?

- * Smaller size & weight to meet modern 'slimline' requirements.
- * Low electrically induced noise demanded by compact equipment.
- * High efficiency enabling conservative rating whilst maintaining size advantages.
- * Lower operating temperature.

Why ILP?

- * Ex-stock delivery for small quantities.
- * Gold service available. 21 days manufacture for urgent deliveries.
- * 5 year no quibble guarantee.
- * Realistic delivery for volume orders.
- * No price penalty for call off orders.

Prices including P&P and VAT

VA Size	£	VA Size	£
15 0	7.43	160 5	12.90
30 1	8.08	225 6	16.30
50 2	10.10	300 7	18.55
80 3	10.81	500 8	25.73
120 4	11.73	625 9	31.63

Mail Order - Please make your crossed cheques or postal orders payable to ILP Electronics Ltd.

Trade - We will open your credit account immediately upon receipt of your first order.

Post to: ILP Electronics Ltd., Dept. 3
Graham Bell House, Roper Close,
Canterbury, Kent. CT2 7EP
Tel: (0227) 54778 Telex: 965780


For 110V primary insert "0" in place of "X" in type number.
For 220V primary (Europe) insert "1" in place of "X" in type number.
For 240V primary (UK) insert "2" in place of "X" in type number.
IMPORTANT: Regulation - All voltages quoted are FULL LOAD.
Please add regulation figure to secondary voltage to obtain off load voltage.



ELECTRONICS LTD.

WW - 047 FOR FURTHER DETAILS

Audio Jackfields?

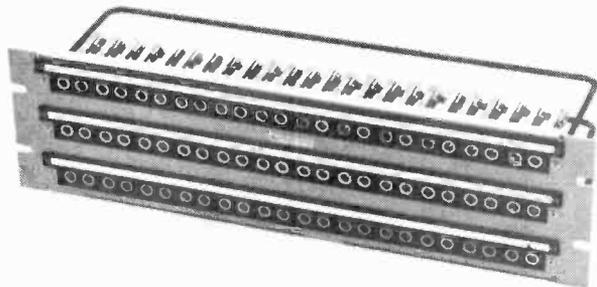

Over 100 listed
in our Catalogue.




Write or call
for your
free copy.

FUTURE FILM DEVELOPMENTS

114 Wardour Street, London W1V 3LP Telephone: 01-434 3344.
Telex: 21624 ALOFFD G Cables: Allotrope-London W1.

WW - 040 FOR FURTHER DETAILS

ROBOTICS!!

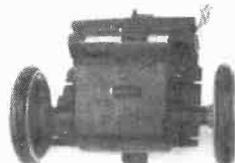

MOTORIZED GEARBOX

These units are as used in a computerized tank, and offer the experimenter in robotics an opportunity to buy the electromechanical parts required in building remote-controlled vehicles. The unit has 2 x 3V motors, linked by a magnetic clutch, thus enabling turning of the vehicle, and a gearbox contained within the black ABS housing, reducing the final drive speed to approx. 50 rpm. Data is supplied with the unit showing various options on driving the motors, etc. £5.95. Suitable wheels also available: 3" dia. plastic with black tyre, drilled to push-fit on spindle, 2 for £1.30 (limited qty.), 3" dia. aluminium disc 3mm thick, drilled to push-fit on spindle, 2 for 68p.

5mm RED LED SCOOP!

Full spec brand new devices at a low, low price!! 25 £1.95; 100 £6; 250 £13.50; 1000 £39.50.

COMPONENT PANELS

Z904 Panel 240x165mm with 6x4099, 723 all in sockets, 14x8A 200V triacs, 45 small signal transistors, 14 R/C networks, 30x1N4001, sub-min relay, Rs, Cs, etc. £4.95
Z905 Finned black ally heatsink 125x198x23mm with 4x2N3055 and 4x0R25 5W Rs. Only £2.50



ALL PRICES INCLUDE VAT; JUST ADD 60p P&P

GREENWELD
443G Millbrook Road, Southampton SO1 0HX

WW - 016 FOR FURTHER DETAILS

★ THE 1984 GREENWELD CATALOGUE ★

Now in the course of production, the 1984 GREENWELD catalogue will be published in January. It's Bigger, Brighter, Better, more components than ever before. With each copy there's discount vouchers, Bargain List, Wholesale Discount List, Bulk Buyers List, Order Form and Reply Paid Envelope. All for just £1. Order now for early delivery!

COMPUTER GAMES

Z901. Can you follow the flashing light/pulsating tone sequence of this famous game? Supplied as a fully working PCB with speaker (no case) plus full instructions. Only £4.95
Z902. Probably the most popular electronic game on the market - based on the old-fashioned pencil and paper battleship game, this computerized version has brought it bang up-to-date! We supply a ready built PCB containing 76477 sound effect chip, TMS1000 microprocessor chip, Rs, Cs etc. Offered for its components value only (board may be cracked or chipped), it's only £1.95. Instructions and circuit, 30p.

BULK BUYERS - LOOK!

OUR LATEST LIST IS NOW READY - SEND FOR YOUR COPY NOW. LOW PRICES ON SEMIS AND PASSIVES

SEATBELT ALARM

Originally for sale at £8.95, these well-made units 70x50x25mm provide both audible and visual alarms. Uses 2 ICs, PB2720 transducer, etc. Available ready built, with circuit and instructions for just £4.95. Also available as a kit, PCB + all components, box, wire, etc. together with instructions. Only £3.95.

SHOP SALE

4th-11th FEB.
CLEARANCE BARGAINS

LOGIC ANALYSERS

TA2080

8 channels, 20MHz, timing and state. 252 byte data and reference memories. 23 bit triggering with trigger delay by events and/or clocks. Compare and search facilities. Composite video output. Microprocessor disassembly (Z80, 6800 and 6502) and RS232 option.

TA2160


16 channels, 20MHz, timing and state. 252 word data and reference memories. Can be configured as two independent or linked 8 channel analysers with separate clocks and independently set parameters. 34 bit triggering on two levels with trigger delay by events and/or clocks. Powerful compare and search facilities. RS232 interface, composite video output. Microprocessor disassembler options for Z80, 8085, 6809 and 6502.

Both analysers can display data either as any 8 channels in timing diagram format, with cursor, window and expansion facilities, or in state format with cursor, memory compare and word search features. All inputs are high impedance and variable threshold.

Optional accessories include the TA232P serial data (RS232) pod and TP55 video printer.

For further information contact:-

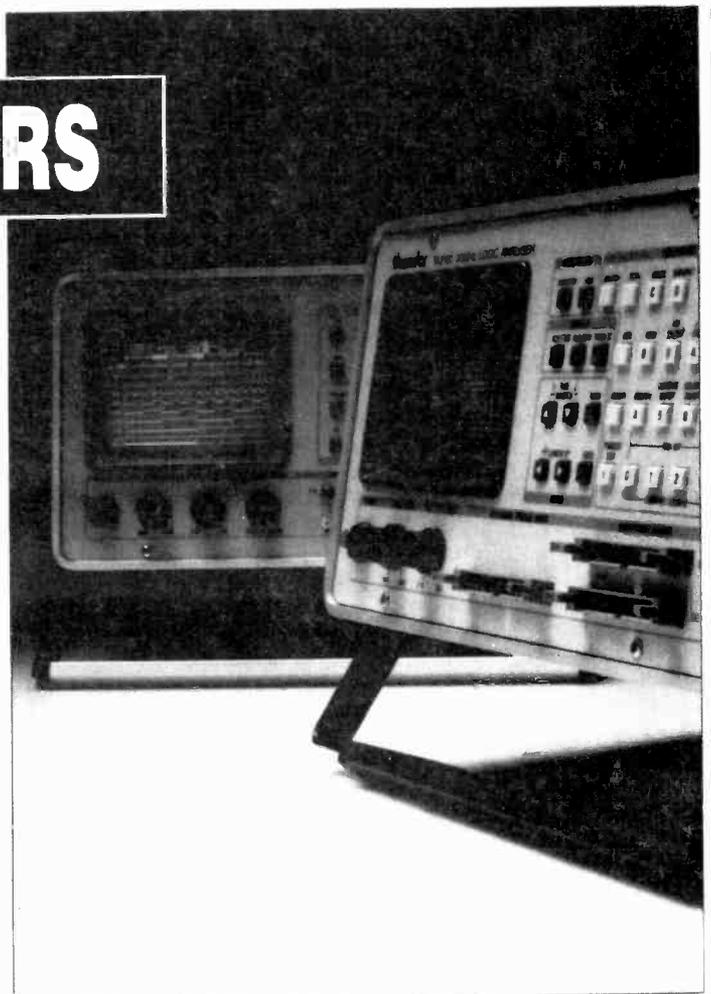Thandar Electronics Ltd, London Road, St Ives,
Huntingdon, Cambridgeshire PE17 4HJ
Telephone: (0480) 64646. Telex: 32250.



 **thandar**
ELECTRONICS LIMITED

WW - 019 FOR FURTHER DETAILS


Now, really reason with IC's

With the new LM2A logic monitor from GSC, you can see just what's going on in an integrated circuit for only £103.*

The LM2A's sixteen LED indicators show the static and dynamic logic states of all the pins on 14 or 16-pin IC packages, and GSC's unique Proto Clip provides rapid, reliable contact with the circuit.


You can use the LM2A with different logic families, too. A front-panel switch lets you select TTL or C-MOS, and a variable threshold control covers any voltage from +1V to +9V for other logic levels. It's small and light enough to hold in the hand, and operation is simplicity itself.

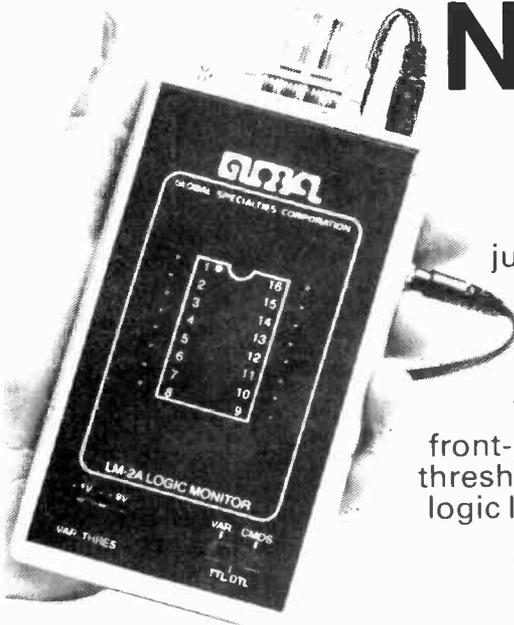Take the logical course of action - fill in the coupon now.



* Price excluding P&P and 15% VAT

GLOBAL SPECIALTIES CORPORATION

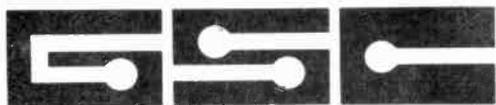

G.S.C. (UK) Limited, Dept. 7L
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Telephone: Saffron Walden (0799) 21682.
Telex: 817477.

G.S.C. (UK) Ltd., Dept. 7L, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ

Model LM2A	LOGIC MONITOR	Unit price inc. P & P 15% VAT £121.90	Qty Req.
------------	---------------	---------------------------------------	----------

Name _____
Address _____

I enclose cheque/P.O. for £ _____ or debit by Barclaycard/Access/
American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION - The G.S.C. 24 hour, 5 day a week service
Telephone (0799) 21682 and give us your Barclaycard, Access, American
Express number and your order will be in the post immediately.

For FREE catalogue tick box

WW - 007 FOR FURTHER DETAILS

COMMUNIQUE

HIGH PERFORMANCE COMMUNICATIONS EQUIPMENT

At a price you can afford

We can offer you a range of U.K. Home Office Type Approved UHF, VHF and Low Band communications equipment. Our range has been designed and built to very high standards using the latest technology to give years of trouble-free use.

DO YOU NEED:

- ★ Competitive Prices?
- ★ Long Term Hire?
- ★ Short Term Hire?
- ★ Outright Purchase or Leasing?
- ★ Ex-Stock Delivery?
- ★ Excellent Technical Back-up?
- ★ Experienced Service Agents?
- ★ Nationwide Service Coverage?

WE CAN HELP YOU!

All export enquiries welcome

For further details, please contact us at:

Communique
Communications House
Purley Avenue
London NW2 1SB
Tel: 01-450 9755
Telex: 298765 UNIQUE G




VISIT COMMUNIQUE AT COMMS' 84
AT THE N.E.C. 15-19 MAY 1984
STAND No 5H8

WWW - 025 FOR FURTHER DETAILS

Accurate Digital Multimeters at Exceptional Prices

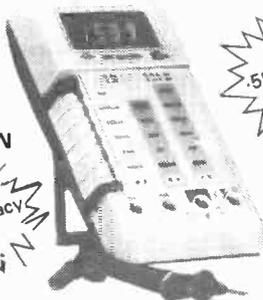28 RANGES
EACH WITH
FULL
OVERLOAD
PROTECTION



6010
5% Accuracy
£29.95

7030
1% Accuracy
£35.95

OTHER features: Auto polarity, auto zero, battery low indicator, ABS plastic case with tilt stand, battery and test leads included, optional carrying case.



6010 & 7030 MODELS SPECIFICATION

- 10 amp AC/DC
- Battery: single 9V drycell Life: 200 hrs
- Dimensions: 170 x 89 x 38mm
- Weight: 400g inc. battery
- Mode Select: Push Button
- AC DC Current: 200µA to 10A
- AC Voltage: 200mV to 750V
- DC Voltage: 200mV to 1000V
- Resistance: 200Ω to 20MΩ
- Input Impedance: 10MΩ
- Display: 3 1/2 Digit 13mm LCD
- D/load Protection: All ranges



NEW
HM102 BZ
£13.00

ANALOGUE HM102BZ WITH CONTINUITY Buzzer and BATTERY SCALE

- * DC Voltage: 0-25, 1, 2.5, 10, 25, 100, 250, 1000 volts 20,000 ohms/volt.
- * AC Voltage: 0-10, 25, 100, 250, 1000 volts 10,000 ohms/volt.
- * Decibels: -20 to +22dB
- * DC Current: 0-50, 500µA, 0-5, 50, 50mA 10A.
- * Ohmmeter: 0-6 Megohms in 4 ranges. 30 ohms Centre Scale.
- * Power Supply: One 1.5V size 'A' battery (incl)
- * Size & Weight: 135 x 91 x 39mm, 280gr.

ARMON ELECTRONICS LTD.

Cottrell House, 53-63 Wembley Hill Road
Wembley, Middlesex HA9 8BH, England
Telephone: 01-902 4321 (3 lines). TELEX No. 923985

Quantity discount for trade on application
Add 15% to your order for V.A.T. P&P is free of charge
Payment by cheque with order



WWW - 025 FOR FURTHER DETAILS

PANASONIC 12" MONITORS

£95

- monochrome green screen
- high quality and reliability
- genuine 80 character and high resolution display

RING NOW ON OUR HOTLINE

0865 726639

WWW - 022 FOR FURTHER DETAILS

Crystals HC6U Ex. Equip. 5,000 mc/s, 7,000 mc/s, 8,000 I.M.C. mc/s, 9,000 mc/s. Also Glass Crystal 100 Kc/s, to fit B7G base. All at £2 p&p paid.

Telephones - Type 706 good condition £5 p&p paid.

Small 230V fans, 4 in. x 2 1/2 in. 2,500 r.p.m. £4.50 p&p paid.

Pye Pocketfone PF1, battery charger, 12 way with meter £10 p&p paid.

Ex-Gov. 27ft telescopic aerial close to 5ft. Good condition, complete with all base & fittings £45 p&p paid. Callers welcome £25.

Pye Pocketfone Nightcall for PF1/TX/RX. New boxed £17.

Whip aerial Ex-Gov. 4ft collapsible £1.

Ni-Cad batteries for Pye PF1 RX. 5 for £2 p&p paid. Min. order 5.

PF1 TX batteries £2 each p&p paid.

All these batteries are ex-eq. but good condition.

AVO multiminor test meter. Tested. £20. Ex eq. p&p paid.

AVO 7X. Tested. Ex. eq. £40 p&p paid.

Opening times: Monday-Friday 8.30am-5pm, Saturday 8.30am-12noon

Please allow 14 days for delivery.

A. H. THACKER & SONS LTD
HIGH STREET, CHESLYN HAY, NEAR WALSALL, STAFFS

WWW - 027 FOR FURTHER DETAILS




FOR FULL DETAILS
PLEASE CONSULT THE
CRICKLEWOOD
CATALOGUE
NOW ONLY 60p + SAE. FREE
TO SCHOOLS, COLLEGES ETC.

CRICKLEWOOD
ELECTRONICS LTD
40 CRICKLEWOOD BROADWAY
LONDON NW2 3ET
01-452 0161/01-450 0995 Tlx: 914977

This list contains only a fraction of
CRICKLEWOOD'S stock. Please add
60p p & p & 15% VAT to all orders.
Official orders from schools, colleges,
Govt. Depts. etc. welcome.

RESISTORS	Siemens	7491	44p	74LS161	50p	4072	19p	1 Amp TO220	57p	40412	90p	BC338	15p	BFY50	23p	ZTX500	14p	Samp type	SL480	2.99	Single sided
OHM FILM	Axial (wires each end)	7432	44p	74LS162	50p	4073	19p	90S 500	57p	40413	90p	BC340	15p	BFY51	23p	ZTX501	14p	Square with hole	SL490	2.99	100 x 160 2.10
8% HI STAB	V	7433	44p	74LS163	50p	4074	19p	912T	57p	40414	90p	BC411	15p	BFY52	23p	ZTX502	14p	PW01 (100 95p)	SN76003	2.95	100 x 220 2.50
LOW NOISE	47	63	8p	74LS164	50p	4075	19p	915T	57p	40415	90p	BC412	15p	BFY53	31p	ZTX503	17p	PW02 (200 95p)	SN76013	2.95	203 x 114 2.40
100T	47	100	9p	74LS165	50p	4076	19p	924T	57p	40416	90p	BC413	15p	BFY54	31p	ZTX504	17p	K04 4000 3.25	SN76023	2.95	500 x 220 5.00
10M	47	350	7p	74LS166	50p	4077	19p			40417	90p	BC414	15p	BFY55	40p	ZTX510	24p	PW06 (6001.39)	SN76033	2.95	Double Sided
1/4W E24	2p	100	9p	74LS167	50p	4078	19p			40418	90p	BC415	15p	BFY56	40p	ZTX520	24p		TA7204	1.99	105 x 160 2.20
1/4W E24	2p	100	9p	74LS168	50p	4079	19p			40419	90p	BC416	15p	BFY57	40p	ZTX530	24p		TA7205	1.99	100 x 200 2.80
1/4W E24	2p	100	9p	74LS169	50p	4080	19p			40420	90p	BC417	15p	BFY58	40p	ZTX540	24p		TA7222	1.75	203 x 114 2.90
1/4W E24	2p	100	9p	74LS170	50p	4081	19p			40421	90p	BC418	15p	BFY59	40p	ZTX550	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS171	50p	4082	19p			40422	90p	BC419	15p	BFY60	40p	ZTX560	24p		TA7207	2.00	Developer for above lds not used
1/4W E24	2p	100	9p	74LS172	50p	4083	19p			40423	90p	BC420	15p	BFY61	40p	ZTX570	24p		TA7208	2.00	500ml
1/4W E24	2p	100	9p	74LS173	50p	4084	19p			40424	90p	BC421	15p	BFY62	40p	ZTX580	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS174	50p	4085	19p			40425	90p	BC422	15p	BFY63	40p	ZTX590	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS175	50p	4086	19p			40426	90p	BC423	15p	BFY64	40p	ZTX600	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS176	50p	4087	19p			40427	90p	BC424	15p	BFY65	40p	ZTX610	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS177	50p	4088	19p			40428	90p	BC425	15p	BFY66	40p	ZTX620	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS178	50p	4089	19p			40429	90p	BC426	15p	BFY67	40p	ZTX630	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS179	50p	4090	19p			40430	90p	BC427	15p	BFY68	40p	ZTX640	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS180	50p	4091	19p			40431	90p	BC428	15p	BFY69	40p	ZTX650	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS181	50p	4092	19p			40432	90p	BC429	15p	BFY70	40p	ZTX660	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS182	50p	4093	19p			40433	90p	BC430	15p	BFY71	40p	ZTX670	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS183	50p	4094	19p			40434	90p	BC431	15p	BFY72	40p	ZTX680	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS184	50p	4095	19p			40435	90p	BC432	15p	BFY73	40p	ZTX690	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS185	50p	4096	19p			40436	90p	BC433	15p	BFY74	40p	ZTX700	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS186	50p	4097	19p			40437	90p	BC434	15p	BFY75	40p	ZTX710	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS187	50p	4098	19p			40438	90p	BC435	15p	BFY76	40p	ZTX720	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS188	50p	4099	19p			40439	90p	BC436	15p	BFY77	40p	ZTX730	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS189	50p	4100	19p			40440	90p	BC437	15p	BFY78	40p	ZTX740	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS190	50p	4101	19p			40441	90p	BC438	15p	BFY79	40p	ZTX750	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS191	50p	4102	19p			40442	90p	BC439	15p	BFY80	40p	ZTX760	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS192	50p	4103	19p			40443	90p	BC440	15p	BFY81	40p	ZTX770	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS193	50p	4104	19p			40444	90p	BC441	15p	BFY82	40p	ZTX780	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS194	50p	4105	19p			40445	90p	BC442	15p	BFY83	40p	ZTX790	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS195	50p	4106	19p			40446	90p	BC443	15p	BFY84	40p	ZTX800	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS196	50p	4107	19p			40447	90p	BC444	15p	BFY85	40p	ZTX810	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS197	50p	4108	19p			40448	90p	BC445	15p	BFY86	40p	ZTX820	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS198	50p	4109	19p			40449	90p	BC446	15p	BFY87	40p	ZTX830	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS199	50p	4110	19p			40450	90p	BC447	15p	BFY88	40p	ZTX840	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS200	50p	4111	19p			40451	90p	BC448	15p	BFY89	40p	ZTX850	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS201	50p	4112	19p			40452	90p	BC449	15p	BFY90	40p	ZTX860	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS202	50p	4113	19p			40453	90p	BC450	15p	BFY91	40p	ZTX870	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS203	50p	4114	19p			40454	90p	BC451	15p	BFY92	40p	ZTX880	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS204	50p	4115	19p			40455	90p	BC452	15p	BFY93	40p	ZTX890	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS205	50p	4116	19p			40456	90p	BC453	15p	BFY94	40p	ZTX900	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS206	50p	4117	19p			40457	90p	BC454	15p	BFY95	40p	ZTX910	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS207	50p	4118	19p			40458	90p	BC455	15p	BFY96	40p	ZTX920	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS208	50p	4119	19p			40459	90p	BC456	15p	BFY97	40p	ZTX930	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS209	50p	4120	19p			40460	90p	BC457	15p	BFY98	40p	ZTX940	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS210	50p	4121	19p			40461	90p	BC458	15p	BFY99	40p	ZTX950	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS211	50p	4122	19p			40462	90p	BC459	15p	BFY00	40p	ZTX960	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS212	50p	4123	19p			40463	90p	BC460	15p	BFY01	40p	ZTX970	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS213	50p	4124	19p			40464	90p	BC461	15p	BFY02	40p	ZTX980	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS214	50p	4125	19p			40465	90p	BC462	15p	BFY03	40p	ZTX990	24p		TA7227	5.82	233 x 220 5.90
1/4W E24	2p	100	9p	74LS215	50p	4126	19p			40466	90p	BC463	15p	BFY04	40p	ZTX000	24p		TA7227	5.82	233 x 220 5.90
1/4W E24</																					

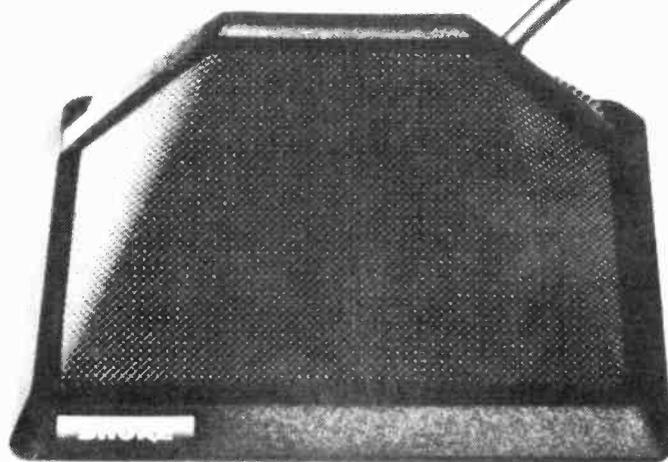THE WORLD'S FIRST AND ONLY AUTOMATIC MICROPHONE SYSTEM— FROM SHURE.



31.8H x 88.9W x 76.2D (mm)

Whenever someone has something to say in public, it's often the microphone system that makes or breaks their speech.

Clicks. Pops. Crackles. Background noises and missed syllables. Just a handful of the hazards that can turn a speaker's finest hour into a fiasco.

Which is why we'd like to introduce you to something completely new—the Shure AMS. Microphone, mixer and advanced logic technology, combined in a totally dedicated system.

In short—a sound revolution.

At the heart of the AMS are angle-sensitive microphones. Speak into any one of them within its own 120° 'window of acceptance' and it turns on; change the surrounding audio conditions

and it compensates. Quickly. Quietly. Automatically.

The rear panel of every AMS mixer features logic terminals that not only give unprecedented flexibility but also eliminate many of the usual adjustments and controls.

As a result no other unit sets up as quickly; handles as easily. And for larger gatherings, AMS mixers combine simply to effectively control over 200 mics.

The new Shure Automatic Microphone System. It makes speeches not mistakes.

IT'S SO SMART IT CAN 'MAKE' SPEECHES

For more information, write to:

HW International, Dept WW, 3-5 Eden Grove, London N7 8EQ.
Tel: 01-607 2717

WW - 005 FOR FURTHER DETAILS

SHURE

You simply can't make it
any clearer.

Editor

PHILIP DARRINGTON
01-661 3128

Deputy Editor

GEOFFREY SHORTER, B.Sc.
01-661 8639

Technical Editor

MARTIN ECCLES
01-661 8638

Projects Editor

RICHARD LAMBLEY
01-661 3039

News Editor

DAVID SCOBIE
01-661 8632

Drawing Office Manager

ROGER GOODMAN
01-661 8690

Technical Illustrator

BETTY PALMER

Advertisement Manager

BOB NIBBS, A.C.I.I.
01-661 3130

BARBARA MILLER
01-661 8640

ASHLEY WALLIS
01-661 8641

Northern Sales

HARRY AIKEN
061-872 8861

Midland Sales

BASIL McGOWAN
021-356 4838

Classified Manager

BRIAN DURRANT
01-661 3106

IAN FAUX
01-661 3033

Production

BRIAN BANNISTER
(Make-up and copy)
01-661 8648

Publishing Director

DAVID MONTGOMERY
01-661 3241

Freedom – or licence?

To speak of culture is to brand oneself a poseur, a pretending aesthete, an unwordly, impractical bore. "When I hear anyone speak of Culture", Goering is said to have remarked, "I reach for my revolver". His other activities make it seem unlikely that he was impelled to deliver this thought by considerations of market potential, but nevertheless it seems to be in tune with the outlook of producers of software for the millions of stored-programme video display devices that nightly hypnotise a large part of the population.

In an ideal world, the 'freeing' of television programmes from the autocracy of established broadcasting organizations would be a step in the right direction. Why, it may be asked, should the viewing public be constrained by the views of three or four broadcasting authorities, when it can use a video recorder/player to display any one of thousands of programmes, and even make its own?

The world is, however, far from ideal. Freedom is always to be sought assiduously, but when it turns to licence, controls may be required as a regulator.

Engineering applied to domestic 'information systems' has an enormous capability – to inform, to entertain, to instruct and educate – the application of just one form, the v.c.r., being limited only by man's small imagination. People's breadth of view and understanding of others' problems and aspirations could be vastly enhanced by a proper choice of software. Freedom from the shackles of broadcast television as it currently exists

could open wide the accumulated knowledge and wisdom of the world.

And what do we find? A wealth of material, certainly. But into which category of mental stimulation should one place an instructional film on ventilating the frontal lobe of the brain by means of a Black and Decker, or some such? Or, indeed, anyone of the cosy little stories designed to encourage the more flamboyant tendencies in the human psyche? The proliferation of such atavistic products of diseased minds is one, regrettable, result of 'freedom'.

The promise of dozens of extra channels of broadcast television by satellite and cable does not do much to encourage hope for the future, either, if the American scene is taken as an example.

Demoralising as it may be, it seems true to say that alternative viewing – that not originated by BBC or IBA – comes nowhere near exploiting the promise of the word 'freedom'. The IBA has to keep market forces well in mind, more so than the BBC, but there are overriding constraints on both organizations of public decency and overall quality. BBC and IBA have unparalleled reputations in both engineering and programme making. With the awful example of video tapes before us, it hardly seems sensible to allow optical, satellite or cable television to flout the laws governing broadcast television simply because they employ different media to carry the signal or because satellite is not, strictly speaking, broadcast. The dissemination of any kind of information to the public should not be solely a money-making venture.

COMMUNICATIONS

Hearing and seeing

Engineers would find it easier to optimize high-fidelity sound systems and high-definition television if only they knew more about human hearing and seeing. It has, for instance, been said of the human auditory system that "The ear presents some of the most disputed problems of human physiology. Regarded purely technically the ear is of comparatively simple construction, so that one might hold the view that an accurate examination would immediately expose the purpose and function of each individual constituent part. Exactly the opposite is the case, and all theories are still full of contradictions."

In particular, the ability of many people to distinguish very small differences in pitch and the ability to locate the direction of sound from extremely small time differentials cannot be explained by the conventional theories. Similarly, the human visual system can detect vernier misalignments with an extraordinary accuracy that cannot be accounted for by simple optical or anatomical considerations — the so-called hyperacuity.

A controversial new theory of hearing has been advanced by Hugo Zuccarelli (*New Scientist*, November 10, 1983) who claims to have developed an electronic recording system that produces spatial effects in a monaural channel. He argues that the ear does not simply and passively receive sound. It also generates a sound wave that interacts with external sound to produce an acoustic hologram or interference pattern. As evidence in support of his theory he notes that several people have succeeded in recording continuous sound at about 1-2kHz emitted in the ears of individuals. Just as each piece of an optical hologram produced by coherent light contains the information for a solid image, so, he argues, the acoustic hologram developed in each ear provides full directional information. No details of his recording system have so far been released.

The question of whether conventional "stereo" is really necessary was raised also by Yoshimutsu Hirata in the October 1983 issue of *Wireless World* (pages 60-63) where he showed how ambience can be added to the mono sound transmitted by a.m. radio and television stations. Ever since the pioneer work by Alan Blumlein, engineers have been struggling to reproduce spatial effects without really being sure how the ear/brain system really works!

Current work on digital sound and vision seeks to overcome fidelity problems by transmission at very high data rates, even though human sensors are relatively slow acting devices. Sony, however, have managed to pack four digital stereo audio channels into a 6MHz channel for use with multichannel cable tv systems, basically using the Compact Disc format. Four hi-fi stereo channels, with 8 bits of synchronization and 4 service bits form a 168-bit word

with a sampling rate of 44.1kHz and a data rate of about 7.4 Mbit/s.

Millimetric rain scatter

The effects of rain-scatter at frequencies between about 10 to 20GHz are well documented. Scatter signals can, for example, result in much interference to terrestrial microwave systems from the high-power up-link satellite communications terminals. Heavy rain can also be used by amateur 10GHz-band enthusiasts to provide extended range contacts from locations shielded by hills. But millimetric signals, although scattered by rain drops, are themselves severely attenuated by rain, with the result that rain-scatter effects tend to be far less evident.

A Japanese rain-scatter experiment in the millimetric range (34.8GHz) has been described by Jun Awaka, Kenji Makamura and Hideyuri Inomata in *IEEE Trans. Ant. & Prop.*, vol. AP31 no. 5, September 1983. Using 10-watt c.w. transmitter power with 10-metre dish aerials roughly 45km apart, it was shown that for a small percentage of time relatively strong signals could be received as a result of rain scattering. However for this to happen there has to be an isolated region of heavy rainfall at the scatter point but with no rain over most of the path. During the field test such conditions were infrequent.

Drive by data

Many schemes for providing traffic and vehicle-navigation information have been proposed but have floundered because of cost or lack of radio frequencies or both. However a new "Autoscout" system, developed by Siemens and Volkswagen, is currently undergoing road tests in Wolfsburg, Federal Germany. An on-board microprocessor control unit, plus magnetic field sensor, provides a form of inertial navigation, displaying both direction and bearing of the keyed-in destination on an l.c. display. However, information on local routes, detours etc are provided from beacon units mounted on traffic lights. Cost is kept low and spectrum problems overcome by the use of low-cost infra-red beacon transmitters. These continuously emit data on the main roads in the area. The vehicle control unit selects only data applicable to the destination the driver has keyed into his unit. It is claimed that Autoscout could even direct drivers to a specific building, garage or parking space.

If the idea catches on, quantity production could bring vehicle unit costs down to that of a good car radio, with correspondingly low costs for equipping traffic lights with infra-red beacons, it is claimed.

The Merriman Report appears to have

removed any incentive for mobile two-way radio to switch to pilot-carrier s.s.b. in 5kHz channels. Yet J.P. McGeehan and A. J. Bateman of Bath University remain convinced that their system of feed-forward signal regeneration could overcome the severe multipath propagation effects shown up in the field trials a few years ago. They consider that the potential advantages of mobile s.s.b. on frequencies up to 1GHz should continue to be investigated. Their f.f.s.r. circuitry could be integrated on a single chip, using current large-scale integration techniques, as simple add-on circuitry to pilot s.s.b. systems.

Exit Radio Officers?

For some time, Inmarsat, the organization set up to provide satellite communication with the world's shipping, has believed that emergency position-indicating radio beacons carried on ships, lifeboats and fitted on buoys designed to float free from sinking ships, will form an integral part of a future global maritime distress and safety system. In the 1990s Morse radiotelegraphy will be replaced, Inmarsat believe, by a combination of satellite and terrestrial telephone and data communications. All countries are expected to make mandatory the carrying of low-power distress beacons. Ships equipped with satellite communication systems are already permitted in some countries to use their facilities in harbours and territorial waters, forbidden on h.f. and m.f.

Shuttle success

The in-flight 144MHz transmissions by Dr Owen Garriott, W5LFL, during a number of orbits of the Columbia space shuttle during the STS-9 mission certainly attracted world-wide publicity for the hobby. Even if the technical value of the experiment, using a low-power handheld transceiver, was questionable, it did mean that many more amateurs became interested in the calculation of orbital data, tracking and mixed polarization, etc. It also underlined how much terrestrial v.h.f. ranges are restricted by the curvature of the earth and local obstructions, with signals receivable during 8-minute windows from the 250km high spacecraft. Unlike for the Oscar satellites, standard 144MHz transceivers were all that was needed.

Dr Garriott also came up on a number of unscheduled occasions despite experiencing difficulties with his lightweight headset in high ambient noise. He recorded most incoming signals on tape, but succeeded in two-way contacts with a number of amateur stations including that of King Hussein, JY1.

Impressive also was the role of the

COMMENTARY

national societies, including RSGB, in providing their members with up-to-date information on the flight. Far less impressive, and of serious concern, was the amount of unnecessary interference, some deliberate, some caused by sheer bad operating.

AMATEUR RADIO

Grenada and Spratly

Similar publicity, but in more contentious circumstances, surrounded the activities of KA20RK/J37, an amateur station operated by Americans on Grenada during the invasion of the island by American and East Caribbean forces.

The US State Department waived limitations on third-party traffic and many of the transmissions from this only radio link with Grenada were used on tv and radio stations. The American government stated that it was "well pleased" with the role played by radio amateurs in keeping open this news channel, and providing information as to the safety of the American medical students and their families.

But from this side of the Atlantic the situation could be seen quite differently, opening up the risk of putting the whole question of reciprocal licensing and the licensing of foreign nationals into jeopardy. It is one thing to provide emergency communications during a natural disaster such as an earthquake or hurricane, but the events on Grenada can hardly be regarded in this light. It differs also from the use made of amateur radio in 1982 in the Falkland Islands on behalf of the government responsible for the issue of the licences!

The sensitivity of the Third World countries to anything remotely resembling "covert" amateur activities is well established but often overlooked by Americans and Europeans. The disaster, resulting in the loss of two lives, that overtook the 1983 German DX-pedition to the Spratly Islands (*WW*, July 1983, page 23) when the *Siddhartha* was sunk by Vietnamese gunfire had overtones that were not widely reported at the time.

According to a lengthy report headed "Hide and seek spy" in *The Strait Times* of Singapore, one of the German survivors, Baldur Drobnya, was an official of the West German "Office for the Protection of the Constitution", a secret counter-intelligence organization. Although there is no reason to doubt that he was on holiday at the time, it led inevitably to suggestions that the expedition might not have been so innocent as it appeared and that, in any

case, any expedition to these disputed islands unwisely courted disaster.

Those resident in the Far East point out that, to an extent not appreciated in the West, national security is there a highly sensitive issue. Any suggestion of amateur transmitters being involved in political or covert activities makes the position of licensed amateurs, particularly if not nationals of the country concerned, much more difficult. They urge that when planning such expeditions the greatest care should be taken not to bring upon the hobby such unfortunate publicity and unnecessary loss of life.

10.1MHz and s.s.b.

Last September I reported the mounting problems of international "planning" of the use of the amateur bands and questioned the extent to which the International Amateur Radio Union is justified in assuming a "regulatory role" without becoming more accountable to the wishes of a clear majority of radio amateurs. An example of IARU pressure on national societies had arisen in respect of the then use of s.s.b. by South Africans in the 10.1MHz band.

Dave Perry, ZS1SG, bandplanner for S.A.R.L., has written to point out that although the society approved s.s.b. operation on the band in 1982 this was changed at the 1983 a.g.m. and members are now advised to adhere to the IARU recommendations.

Nevertheless, he points out, many South African amateurs remain concerned about the validity of IARU's reasoning and initial assessment. SARL are to raise this subject at the 1984 IARU Region 1 conference.

South Africa is the only country in Region 1 south of the Mediterranean area with appreciable activity. The distances involved means that 10.1MHz is not being used for telegraphy during daytime, since the relatively small number of c.w. enthusiasts are usually not interested in working stations in their own country. Yet the band would be excellent for internal working on s.s.b., especially for mobile operation over distances up to 2000km.

SARL now finds it difficult to justify to its members the IARU's ban. In Europe circumstances are very different yet even those of us who are c.w. enthusiasts suspect that complete banning of s.s.b. on 10.1MHz, at all times of the day and night, is difficult to justify on a world-wide basis.

Cable and MDS

American amateurs continue to complain about the interference problems caused by signal leakage into and out of multichannel cable tv systems that often distribute some

programmes in the 144MHz band or within or close to other amateur frequencies. The cable people, on the other hand, claim that there is no problem with correctly-installed well-maintained systems and tend to put at least some of the blame on to the significant number of viewers (including amateur radio enthusiasts) who run 300-ohm twin cable close to the coaxial cables in order to receive subscription channels without payment. Even where the tv programmes are encrypted or scrambled this is often of an unsophisticated type that enables those with technical knowledge to descramble the signals. The "pirate" coupling wires, it is claimed, are one of the main causes of leakage problems, with signals radiated from the twin wire.

Rather similar disputes have arisen from those increasingly used multichannel microwave distribution systems (MDS) in which the high-power omnidirectional microwave transmitters at about 2.15 GHz are used to send programmes, often initially carried over distribution satellites, to homes. In some locations MDS has considerable economic advantages over cable.

The MDS operators are convinced that many of their subscription channels are being pirated and in a recent lawsuit named 40 radio amateurs as being among some 3000 "pirate" viewers, on the evidence that they had 2GHz aerials on their roofs. The cases have now been dropped after most of the amateurs named had signed as affidavit that they had not used the aerials to receive Home Box Office subscription channels, and pointing out that the MDS frequencies are close to the 2.3 to 2.45GHz amateur band. But it is clear that the bad feeling between American radio amateurs and the cable and MDS operators has not yet ended.

I understand that interest is being shown in the UK in microwave distribution systems although these do not have any of the interactive facilities advocated in the Cable and Broadcasting Bill.

In brief

The 23-cm beacon, GB3WX, that incorporates weather telemetry, is now back in service . . . A number of earth-moon-earth tests are being organized on the 2.3GHz band where it is possible that some moon-bounced signals could be heard on dishes of only 4ft diameter. . . . The Bury Radio Society has a Ham Feast at Mosses Community Centre, Cecil Street, Bury, Lancs on February 5 . . . RSGB National VHF convention is at Sandown Park Racecourse, Esher, Surrey on March 24. . . . RSGB National Amateur Radio Exhibition is at the National Exhibition Centre, Birmingham on April 28-29.

PAT HAWKER, G3VA

IEEE488 interface for the BBC Microcomputer

The BBC Microcomputer lacked a GPIB (IEEE488) interface – until Intelligent Interfaces designed this one for Acorn.

Many features of the BBC Microcomputer make it eminently suitable for use in the research and development laboratories of educational and industrial establishments. These include its fast structured Basic interpreter, high resolution colour graphics and a number of input/output interfaces for connecting peripheral equipment. However, it did lack an IEEE488 interface, an omission now rectified by Acorn Computers. This article includes a short introduction to the IEEE488 standard* and describes the hardware and software design of the interface.

The IEEE488 (GPIB) interface has been adopted by major instrument manufacturers throughout the world as a means of connecting instruments such as digital voltmeters and spectrum analysers to one another and to a controlling computer to form automatic test equipment systems. A number of computer and peripheral equipment manufacturers have used the interface to connect computers to disc units, graphics plotters and so on.

The IEEE488 standard specifies a system for exchanging digital data in bit-parallel, byte-serial form at up to 1Mbytes between a number of devices in a local area. The interface makes use of two types of messages: interface messages used to manage the interface (commands) and device-dependent messages (data).

Up to 15 devices, including the controlling computer, can be connected using IEEE488 standard cable assemblies. These have a plug and socket at each end permitting star or linear interconnection of devices. The connectors are provided with two securing screws which allow them to be stacked on the socket of each device. The standard permits individual cable lengths of up to 4m and a total cable length in a system of 2m per device or 20m, whichever is the shorter. The cable consists of eight data lines, three handshake lines and five control and management lines. The three handshake lines are used

by Andrew G. Ray

to transfer data between devices; the slowest device determines the rate at which this occurs.

Each device in an IEEE488 system must have a unique address. Some devices have only one address (a primary address) whilst others have extended addressing (both primary and secondary addresses). Secondary addresses are often used to select different functions within the same device: for example an analogue-to-digital converter with a number of inputs may have the input selected by the secondary address.

A device can have the ability to send data (act as a talker), receive data (act as a listener) or do both (act as a talker-listener), or manage the system (act as a controller). Only one device in a system can act as system controller. This is the device which has the control function when the system is initialized.

In my experience, the use of even a fairly simple IEEE488 system transforms research and development work. Apart from the obvious advantage of speed, performing a test automatically has other advantages:

- repeatability, as the test is defined by the program running on the controlling computer
- fast analysis, as the computer can rapidly compare the results of different tests
- faster development, as the results of a test are almost instantly available.

The third advantage means that decisions in the course of development are based on facts rather than speculation and enable further tests to be planned in an informed fashion.

Complex IEEE488 systems, working at high data transfer rates, usually employ a minicomputer as controller. However, most systems consist of one or two instruments connected to a microcomputer and this offers an extremely cost-effective automatic test system.

The overall objectives in the design of the Acorn interface were to allow it to act

as system controller and operate as controller, controller-talker and controller-listener with the ability to pass control to another device on the bus and request it back. Additionally, the interface was required to be easily used from any language running on the computer or a second processor.

Hardware

Two approaches to the hardware design were considered: the use of peripheral interface adaptors (p.i.a.) with t.t.l. open collector drivers and terminating resistors; or else the use of an l.s.i. general-purpose interface bus adaptor (g.p.i.a.) with IEEE488 bus transceivers.

The first requires all interface functions, such as source and acceptor handshakes, to be implemented in software. This imposes an unacceptable burden upon the processor and significantly reduces total system performance. In the second approach the g.p.i.a. implements most interface functions, interrupting the processor only when action is required.

The 6502 microprocessor of the BBC Microcomputer has many tasks and makes extensive use of interrupts, and so the second approach was chosen. As the controller function was to be implemented, this restricted the choice of l.s.i. GPIB adaptors. It soon became apparent that the Texas Instruments TMS9914A was the most suitable in that it was the most easily interfaced to the 6502 microprocessor and, together with the Texas SN75160A and SN75162A octal GPIB transceivers, resulted in a compact circuit board layout.

Connection to the 1MHz bus of the computer is via a 34-way ribbon cable. A 34-way header provides a feed-through connection to further 1MHz bus peripherals. Resistor packs provide optional 2.2k Ω pull-up and 2.2k Ω pull-down terminations for the 1MHz bus. All 1MHz bus lines are buffered. A clean NPGFC select signal is produced by an RS flip-flop formed by three gates on IC₆. Address decoding is performed by gates of IC₅, 6, 7. The read and write registers of IC₁ are located in page &FC between &FC20 and &FC27. Two gates of IC₉ are used to produce a chip-enable signal, qualified by

* The 488 general-purpose interface bus standard, which is identical with IEC625-1 apart from connectors, was described by P. R. Ellefson in 'IEEE bus standard' *Wireless World* June/July 1980 pages 75-8.

the buffered 1MHzE signal. This ensures the correct timing relationship between the processor and the TMS9914A. Note that both register select and data lines of IC₁ are designated using the Texas Instruments convention. This is opposite to that used for 6502-based systems, such as the BBC Microcomputer.

The crystal and IC₈ generate a 5MHz clock for IC₁. Trigger output from IC₁ is available at PL₃; however, this is not fitted in the standard interface. Link 1 determines whether the interface is system controller and link 2 determines whether the outputs of IC₂ are open-collector or three-state.

Software

To enable ease of use with any high level language and permit parameters to be passed as variables, the IEEE488 software was designed to appear to the BBC Microcomputer operating system as an additional filing system. The IEEEFS is selected by *IEEE, in the same way as other filing systems.

Communication between a language and the interface is via two channels. The first is the command channel used for transmitting IEEEFS commands and receiving information on the state of the interface. The second is the data channel used for reading and writing data to other 488 devices. IEEE commands are sent to the IEEEFS by PRINT# via the command channel. Data is sent to and received from other devices by PRINT# and INPUT# via the data channel. These channels must be OPENED before use.

The table lists the commands available. Full simple English syntax produces easily readable programs. However, the use of upper and lower case together with minimum abbreviations eg L. for LISTEN, makes rapid entry of programs possible. The experienced user of IEEE488 systems will appreciate the functions of most commands but the following facilities are worthy of note.

The state of the interface is available through the STATUS command which returns a 32-bit status word. For example, this can indicate whether the computer is controller in charge, or if another device is requesting service, whether a source handshake or timeout error has occurred, etc.

Although it is not part of the standard, an optional timeout after 2.5 seconds is provided to avoid waiting interminably for a device which never responds.

Data can be sent and received as strings of up to 255 characters or, through the use of the READ and WRITE BINARY commands, as longer sequences of binary-coded data.

The standard does not specify a particular delimiting character for strings. The END OF STRING command enables the default delimiter of linefeed to be redefined as either one or two characters.

The TRANSFER command permits the computer to carry out some other task while a talker sends data to a listener or listeners on the bus. The end of this sequence is indicated in the status word.

IEEE commands together with their minimum abbreviations

BBC DEVICE NO	B.
CLEAR	C.
DEVICE CLEAR	D.
END OF STRING	E.
EXECUTE	E.
GO TO LOCAL	G.
LISTEN	L.
LOCAL LOCKOUT	LO.
PARALLEL POLL DISABLE	PARALLEL POLL D.
PARALLEL POLL ENABLE	PARALLEL POLL E.
PARALLEL POLL REQUEST	P.
PARALLEL POLL UNCONFIGURE	PARALLEL POLL U.
READ BINARY	R.
REMOTE DISABLE	REMOTE D.
REMOTE ENABLE	REM.
REQUEST CONTROL	REQ.
SELECTED DEVICE CLEAR	SEL.
SERIAL POLL	SE.
STATUS	S.
TAKE CONTROL	TAK.
TALK	T.
TIMEOUT OFF	TIMEOUT OFF
TIMEOUT ON	TI.
TRANSFER	TR.
TRIGGER	TRI.
UNLISTEN	UNL.
UNTALK	U.
WRITE BINARY	W.

Commands are available that allow both serial and parallel polls to be conducted. All addressed and universal commands specified in the IEEE488 standard can be sent, e.g. GO TO LOCAL, LOCAL LOCKOUT etc.

The TAKE CONTROL and REQUEST CONTROL commands enable control to be passed to another device and requested back.

Example

The following example program in BBC Basic might be used for obtaining the frequency response of an amplifier. An input signal is provided by a programmable signal generator and the output signal is measured with a digital voltmeter.

In the example, lines 10 and 20 select the disc filing system and open a file for storing the results of the test. Lines 30, 40 and 50 select the IEEEFS and open the command and data channels.

Line 60 is used to specify the primary address of the computer. This can be any primary address not used by an instrument in the system.

Line 70 returns the IEEE488 system to a known state; line 80 enables the remote operation of the devices in the system; and lines 90 and 100 pass the primary addresses of the signal generator and digital voltmeter to the IEEEFS.

Line 120 commands the signal generator to listen and line 130 sets its signal amplitude and frequency. Line 140 commands

```

10 *DISC
20 result%=OPENOUT("RESULTS")
30 *IEEE
40 cmd%=OPENIN("COMMAND")
50 data%=OPENIN("DATA")
60 PRINT#cmd%,"BBC DEVICE NUMBER",1
70 PRINT#cmd%,"CLEAR"
80 PRINT#cmd%,"REMOTE ENABLE"
90 siggen%=OPENIN("7")
100 dvm%=OPENIN("3")
110 FOR frequency%=1000 TO 10000 STEP 100
120 PRINT#cmd%,"LISTEN",siggen%,"EXECUTE"
130 PRINT#data%,"0.1V,"+STR$(frequency%)+ "Hz"
140 PRINT#cmd%,"UNLISTEN"
150 PRINT#cmd%,"TALK",dvm%
160 INPUT#data%,reading$
170 PRINT#cmd%,"UNTALK"
180 response=20*LOG(VAL(reading$)/(0.1*0.7071))
190 *DISC
200 PRINT#result%,frequency%,response
210 *IEEE
220 NEXTfrequency%
230 CLOSE#dvm%
240 CLOSE#siggen
250 *DISC
260 CLOSE#result%

```

Microprocessor programming simplified

A new technique for transferring a program directly to machine-code language avoids the necessity of writing the program out in high-level or assembly language

To write a new program it is often necessary or desirable to set up the sequences in the form of a flowchart. This may then be translated into a computer language, be it high-level, assembly or machine-code depending on the facilities available to the user. In all cases the process of translation can be tedious and time consuming. In order to speed up the process, a simple method is presented here to enable flowchart steps to be entered directly into the system by defining a number of key functions with symbols. It is no longer necessary to key in assembly mnemonics or even remember their exact abbreviations. The symbol sequences can be added to the flow chart and then keyed in.

The proposed symbolic forms of the instruction set are presented in Table 1. Although this particular set is for the Intel 8085 processor, it may be adapted quite easily for use on other processors. The blocks at the left of each instruction represent the keys used, in their correct order.

by Gemal A. M. Labib


It can be seen that the number of key-strokes for each instruction is less than that required with the usual assemblers. There are few symbols and they are easy to remember. For example, the arrow keys, →, ←, are used for data transfer between registers, register pairs and memory as well as for jumps and return instructions. Similarly, the + and - signs are used for increment, decrement, add and subtract, as well as positive and negative condition flags. Although not shown in the table, every statement must end with a comma terminator.

The symbolic assignments of the keys are shown in Table 2. In order to minimize the number of keys required, two or three functions are assigned to most keys. Eight hexadecimal numeric keys are used as control keys for editing and program execution. The other keys are used to enter some instruction mnemonics and logic operators. 16 further keys are used for the other symbols shown in Table 1. The function of the eight control keys are as follows:

Stmnt start positions the cursor at the start of the current statement.

Clear deletes the statement at the cursor position.

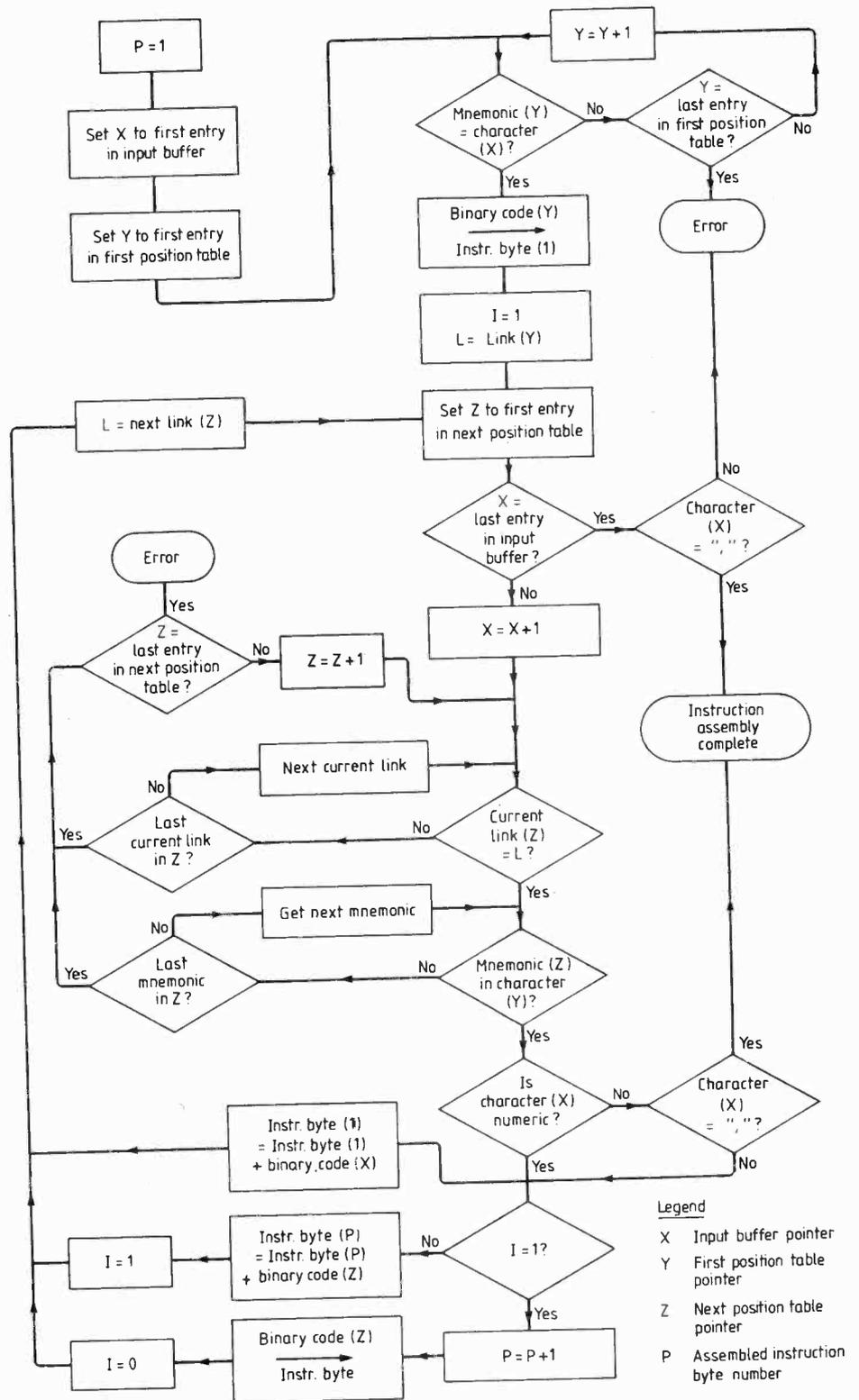Flowchart of the software that implements Tables 3 and 4.



- Legend**
- X Input buffer pointer
 - Y First position table pointer
 - Z Next position table pointer
 - P Assembled instruction byte number

Forward and backward position the cursor at the next or previous statement.

Delete and **insert** operate on individual keystrokes at the current cursor position.

Single step allows statements to be translated into machine-code and to be executed one at a time. Following the execution of a statement, control is returned to the operating system so that register and memory contents may be checked.

Run causes program statements to be transferred to a secondary buffer. They are translated into machine code as a whole, and the program executed.

A few notes may help to avoid syntax errors and simplify key entry. 1. Instructions dealing with register pairs should begin with the (rp) operand. 2. No statement should begin with a numerical operand or the Immediate marker. 3. The source and destination register, register pairs or memory operands may be reversed

Table 3: First position

Mnemonic	Binary coded hexadecimal	Next entry link
A	38	1
B	00	1
C	08	1
D	10	1
E	18	1
H	20	1
L	28	1
M	30	2
A	07	3
B	00	3
C	01	3
D	02	3
E	03	3
H	04	3
L	05	3
M	06	4
BC	00	5
DE	10	5
HL	20	5
SP	30	6
PSW	30	18
L	28	14
M	30	14
A	38	14
B	00	14
C	08	14
D	10	14
E	18	14
H	20	14

if the appropriate arrow symbol is included. 4. All instruction statements must be terminated by a comma.

The driving software that handles the machine-code translation operation of the entered statement is detailed in two tables. The data contained in the tables is specific to the 8085 processor but by following certain rules the software can be applied to a variety of processors.

Table 3, the first position table, contains three fields for each entry: the mnemonic field contains the ASCII codes for the symbols that may appear at the start of each statement; the binary code field contains the corresponding binary combination that will be transferred to the first byte of the assembled machine-code instruction; the next-entry link specifies the group of entries in Table 4 which are related to each symbol in Table 3. Table 4,

Table 1. Symbol sequences needed to produce the full instruction set. Variables r and rp represent registers or register pairs; d8 and d16 are single or double-byte constants.

Symbolic statement	8085 instruction mnemonic	Symbolic statement	8085 instruction mnemonic
$r_1 \leftarrow r_2$	MOV r1, r2	\leftarrow	RET
$r_2 \rightarrow r_1$		\leftarrow C	RC
M \leftarrow r	MOV M, r	\leftarrow nC	RNC
r \rightarrow M		\leftarrow Z	RZ
r \leftarrow M	MOV r, M	\leftarrow nZ	RNZ
M \rightarrow r		\leftarrow +	RP
r \leftarrow I 0-F 0-F	MVI r, d8	\leftarrow -	RM
M \leftarrow I 0-F 0-F	MVI M, d8	\leftarrow even	RPE
rp \leftarrow I 0-F 0-F 0-F 0-F	LXI rp, d16	\leftarrow odd	RPO
rp \leftarrow A	STAX rp	r +	INR r
rp \rightarrow A	LDAX rp	r -	DCR r
A \rightarrow 0-F 0-F 0-F 0-F	STA adr	M +	INR M
A \leftarrow 0-F 0-F 0-F 0-F	LDA adr	M -	DCR M
HL \rightarrow 0-F 0-F 0-F 0-F	SHLD adr	rp +	INX rp
HL \leftarrow 0-F 0-F 0-F 0-F	LHLD adr	rp -	DCX rp
HL \leftarrow \rightarrow DE	XCHG	+ r	ADD r
DE \leftarrow \rightarrow HL		+ r C	ADC r
\rightarrow 0-F 0-F 0-F 0-F	JMP adr	+ M	ADD M
\leftarrow C 0-F 0-F 0-F 0-F	JC adr	+ M C	ADC M
\rightarrow nC 0-F 0-F 0-F 0-F	JNC adr	+ I 0-F 0-F	ADI d8
\rightarrow Z 0-F 0-F 0-F 0-F	JZ adr	+ I 0-F 0-F C	ACI d8
\rightarrow nZ 0-F 0-F 0-F 0-F	JNZ adr	rp + HL	DAD rp
\rightarrow + 0-F 0-F 0-F 0-F	JP adr	HL + rp	
\rightarrow - 0-F 0-F 0-F 0-F	JM adr	- r	SUB r
\rightarrow even 0-F 0-F 0-F 0-F	JPE adr	- r b	SBB r
\rightarrow odd 0-F 0-F 0-F 0-F	JPO adr	- M	SUB M
HL \rightarrow PC	PCHL	- M b	SBB M
PC \leftarrow HL		- I 0-F 0-F	SUI d8
		- I 0-F 0-F b	SBI d8

Table 2: Key assignments

Original Key label	Assigned Label	Original Key label	Assigned label
0	CALL/NOP	K1	A/RST0/PUSH
1	HLT/ROT	K2	B/RST1/POP
2	DAA/COMP	K3	C/RST2/Left
3	CMA/OR	K4	D/RST3/ \rightarrow
4	STC/EXOR	K5	E/RST4/ \leftarrow
5	CMC/AND	K6	H/RST5/Right
6	IN/RST	K7	L/RST6/C
7	OUT/INT	K8	M/RST7/nc
8	Stmnt Start	K9	HL/+
9	Clear	K10	BC/-
A	Delete	K11	DE/Z
B	Insert	K12	PC/nz
C	Forward	K13	PSW/even
D	Backward	K14	SP/odd
E	Single Step	K15	Stack Top/b/Immed.
F	RUN	K16	

Table 1. Symbol sequences needed to produce the full instruction set. Variables r and rp represent registers or register pairs; d8 and d16 are single or double-byte constants.

Symbolic statement	8085 instruction mnemonic	Symbolic statement	8085 instruction mnemonic
^ r	ANA r	INT E	EI
⊕ r	XRA r	INT D	DI
V r	ORA r	INT M E	SIM
COMP r	CMP r	INT M D	RIM
^ M	ANA M	NOP	NOP
⊕ M	XRA M	HLT	HLT
V M	ORA M	ROT L	RLC
COMP M	CMP M	ROT R	RRC
^ I 0-F 0-F	ANI d8	ROT L C	RAL
⊕ I 0-F 0-F	XRI d8	ROT R C	RAR
V I 0-F 0-F	ORI d8	DAA	DAA
COMP I 0-F 0-F	CPI d8	CMA	CMA
rp PUSH	PUSH rp	HL	STC
rp POP	POP rp	CMC	CMC
HL ← → STK TOP	XTHL rp	CALL 0-F 0-F 0-F 0-F	CALL adr
STK TOP ← → HL		CALL C 0-F 0-F 0-F 0-F	CC adr
HL → SP		CALL 0-F 0-F 0-F 0-F	CNC adr
SP ← HL		CALL 2 0-F 0-F 0-F 0-F	CZ adr
RST RST ₀	RST 0	CALL nZ 0-F 0-F 0-F 0-F	CNZ adr
RST RST ₁	RST 1	CALL + 0-F 0-F 0-F 0-F	CP adr
RST RST ₂	RST 2	CALL - 0-F 0-F 0-F 0-F	CM adr
RST RST ₃	RST 3	CALL even 0-F 0-F 0-F 0-F	CPE adr
RST RST ₄	RST 4	CALL odd 0-F 0-F 0-F 0-F	CPO adr
RST RST ₅	RST 5		
RST RST ₆	RST 6		
RST RST ₇	RST 7		
√ 0-F 0-F	IN d8	^ AND	
OUT 0-F 0-F	OUT d8	⊕ EXOR	
		V OR	

lowing rules should be adhered to:

1. The first position table: a. If symbol used at the start of a statement represents different instruction groups, it will have multiple entries in the table with the appropriate binary codes. These can be distinguished by having different next-entry links; b. Symbols that use the same key should always use the same ASCII code; c. Each entry will require three bytes of memory.
2. The next-entry table: a. All symbol sequences must be linked with and terminate with the comma entry; b. As for 1b above; c. Symbols with several different binary codes must not have the same current entry link; d. Each current entry link must have a corresponding next entry link; e. The minimum memory space required for each instruction is four bytes, expandable in segments of two bytes; f. Mnemonics having the same current entry and next entry links may be grouped together so that both fields are stored once only for the

Table 4: Next position

Mnemonic	Binary coded hex.	Current entry	Next entry
←	40	1,2	7,8
B	00	7,8	32,32
C	01		
D	02		
E	03		
H	04		
L	05		
A	07	7,8	32,32
M	06	7	32
0-F	00-F0	12,16	13,17
0-F	00-0F	13,17	16,32
B	00	9,10	32,32
C	08		
D	10		
E	18		
H	20		
L	28		
A	38	9,10	32,32
M	30	9	32
→	40	3,4	9,10
←	01	5,6	11,11
I	00	11,15	12,16
←	06	14	15
PUSH	C5	5,18	32,32
POP	C1	5,18	32,32
-	-	32	0

whole group. This will reduce the size of the table.

The tables printed here demonstrate the MOV, MVI, LXI, Push and Pop groups. By following the sequence of the flow chart any instruction within these groups may be assembled. For example, the instruction MOV AB; by reference to the 8085 instruction set it is found to have the hexadecimal code of 78. The Key depressions A, forward arrow, B, comma, used in conjunction with the links give the numbers 38, 40 and 00 which when combined give 78.

WV

the next position table, contains four fields for each entry: the mnemonic field is similar to that in Table 3, except that the position for the symbol is after the first position; the binary code field contains the corresponding binary combination that will be added to the contents of the first byte of the assembled machine-code instruction as long as the related symbol is not numeric (otherwise the binary code will be transferred to the second or third byte of the assembled instruction or added to that byte's contents depending on whether it is the first or second hexadecimal digit in the byte) the current entry link and next-entry link determine whether the symbol is a part of a symbolic sequence which will produce a valid instruction code.

The flow chart shows how the lists are used by the driving software, and how the translation is accomplished. It can be seen that there are a number of error traps so that it is impossible to terminate a statement with anything other than a comma; to key in more than eight symbols (including the comma) in any one statement; or to use any non-valid symbol combinations. The software described in the flowchart occupies about 280 bytes of memory. Features may be added such as the ability to display the next instruction address; and display the next statement number during program entry; to have a user-defined starting address; and to save programs on tape or disc in their symbolic format for further editing or modification.

When setting up the tables, the fol-

Edison's electrical indicator

Last November, on the Centenary of Edison's patent of the thermionic diode, James Franklin argued that Edison had no idea of the significance of his invention and that therefore this could not be taken as the birth of electronics. Here Desmond Thackeray of Surrey University replies


by Desmond Thackeray, Ph.D.

The interest *Wireless World* has in the realms of electronics brings with it the responsibility for acknowledging inventions (and their inventors) of significance. A use for one electronic invention of great importance, the thermionic diode, was patented by Thomas Edison¹ some 20 years before J. A. Fleming thought to use it as a wireless detector. In these two decades, and even before 1883 when my story starts, there was a great deal of investigation into the physics of rather gassy vacuum tubes and the emission from heated and cold surfaces. This work came to fruition in a number of useful inventions, such as the Braun cathode-ray oscillograph tube² of 1897, the Wehnelt oxide-coated cathode³ of 1904 and the Cooper-Hewitt mercury pool rectifier⁴ of 1903.

Fleming himself reported^{5,6} in 1890 and 1896 that unidirectional current flowed through an Edison thermionic diode when its filament was heated by an alternating current (though these are not his own words). What Fleming had observed was the process of rectification; but apparently it had little significance to him at the time. One must remember that alternating power supplies were very much a novelty, and rejected by Edison himself.

So, naturally, Edison's American patent no. 307,031 filed November 15, 1883, for

an "Electrical Indicator" did *not* cover the application of his thermionic diode to the conversion of the despised alternating current into his well-regarded direct current. And he did not claim novelty for the diode itself, seemingly regarding it as simply an electric lamp, the use of which as an electrical indicator, and for controlling generators, he wished to cover. Edison must have observed that the emission from his hot carbon lamp filaments only appeared when the filaments *were* visibly hot, and then increased super-proportionately as the filament current was raised. By connecting the filament to his power lines "changes in the candle-power of the lamp (filament), and consequently in the electromotive force of the source of supply, are made apparent". His diagram

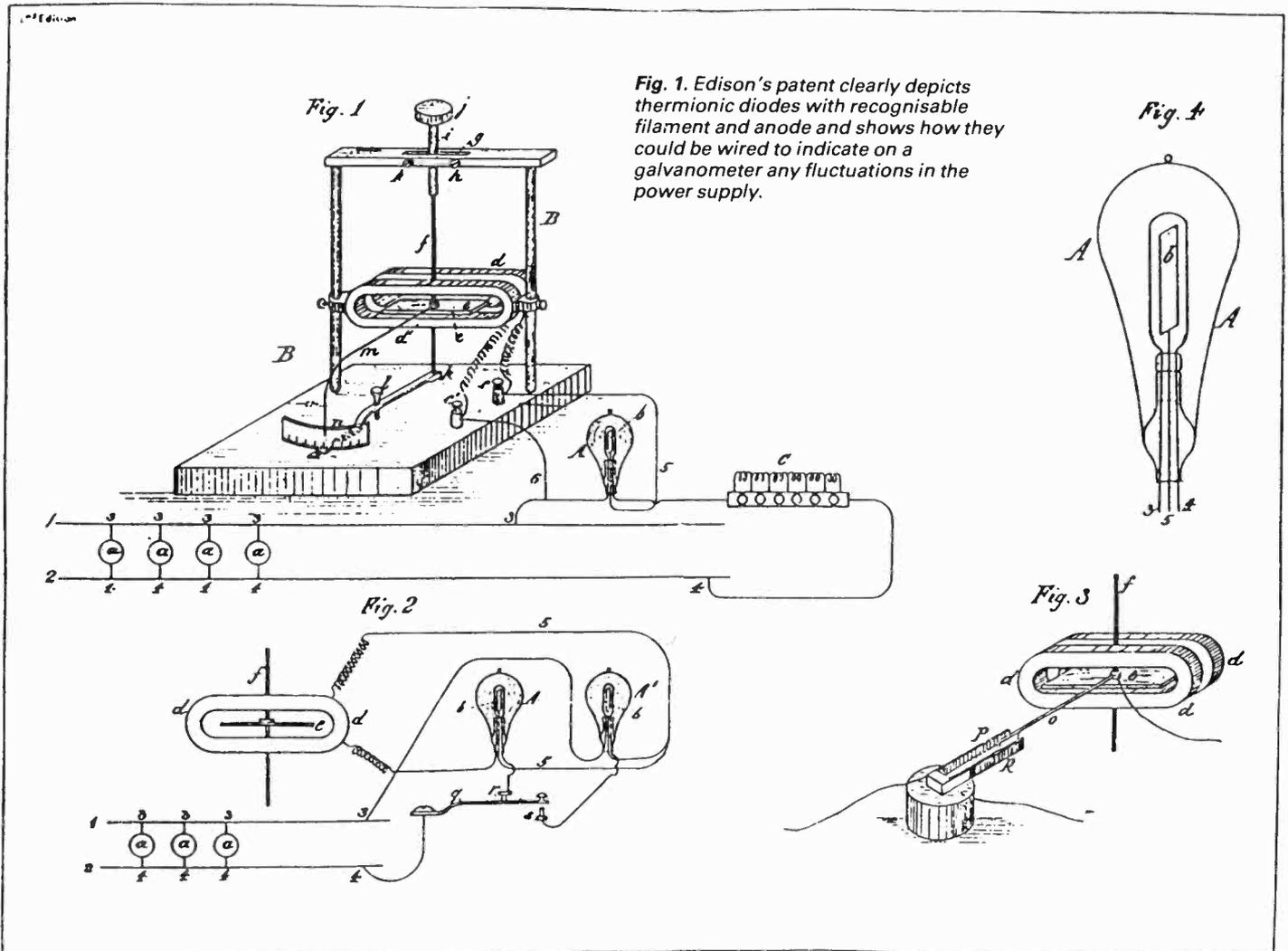

(Fig. 1) shows a galvanometer in the plate (anode) circuit to display the changes in filament emission current. The arrangement no doubt exhibited a very high sensitivity to small changes in power line voltage. It seems therefore a completely practicable application of the thermionic diode in any situation where a plant engineer *actually required* a more sensitive indicator than say a conventional voltmeter with offset zero. But we cannot be sure that there was such a need.

Edison continues the quoted sentence "or . . . instead . . . are made to affect circuit controlling apparatus, automatic regulators or other electrical apparatus. . . ." Here he is envisaging the galvanometer as a relay; and later in the patent he specifies how this may be interfaced to the generator control via "a mechanism such as shown⁷ in my patent no. 287,524". Whether or not this latter mechanism worked successfully hardly matters, because Edison could have used here any "sure-fire" interface, such as a reversible motor driving a field rheostat. Clearly, what Edison had invented in 1883 was not only a sensitive incremental electronic voltmeter, but also a complete electronic servo-controller of the discontinuous (or bang-bang) kind. Again we might wonder whether a control system of such high sensitivity (loop gain?) was actually needed, and would be used. There could also have been stability problems to solve. Writing in the magazine *Scientific American* in March 1969, George Shiers⁸ draws attention to the historic importance of what he calls "this first patent in electronics"; but he does add the rider that it "was of no commercial value". I think that this is rather a brief dismissal of the topic, arising because Shiers' article is really concerned with the string of thermionic developments that were eventually to contribute to early wireless.

Even in wireless, generator regulation must have had some value; but the modest d.c. stability required so long ago could probably have been met adequately with simpler techniques, compound winding of the generator, or the buzzing relay once ubiquitous in automobile battery charging; and so Edison's invention lay idle. It seems to have been the exigencies of World War I, requiring sensitive valved receivers intolerant of such interference sources as buzzing relays, that prompted H. M. Stoller⁹ to use a thermionic diode (called a Kenotron by the General Electric Company of America) to stabilise the output of an aircraft generator supplying thermionic tubes.

Gerald Tyne, in his *magnum opus* "Saga of the Vacuum Tube"¹⁰, devoted more than a page to the TB1 Kenotron (Fig. 2) and said that "approximately 4,500 of these were delivered to the Signal Corps." Then if one turns to the contemporary account¹¹ by Van der Bijl in the "Thermionic Vacuum Tube", there is a circuit diagram of a regulator (as devised by Stoller) and some regulation curves.

"Edison triumphs at last" we might say? Sadly, not so; there is one little flaw here. The circuit shows that the plate current of the diode (20 to 130mA) actually flows

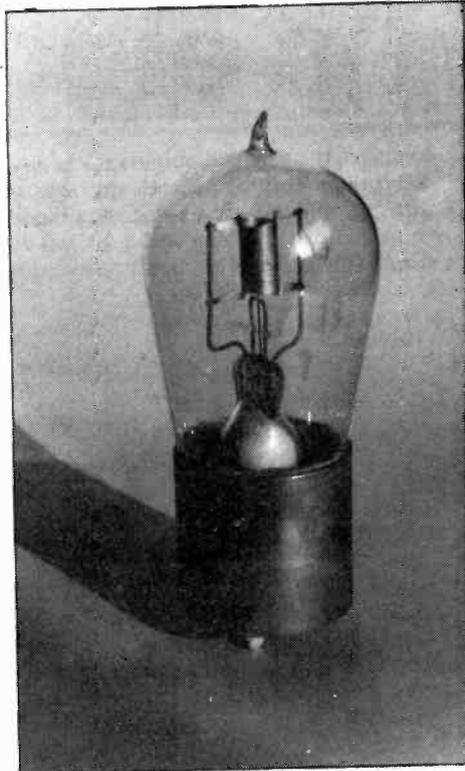


Fig. 2. Early regulator diode, the TB1, as used in American aircraft equipment during the first World War.



Fig. 3. One of the modern successors to the TB1, the GE10, though not equivalent in ratings, has a straight tungsten filament rather than the hairpin or carbon loop filament of the Edison tube.

through the differential field winding of the generator itself, so providing continuous regulation without steps. This was a simplification seemingly not envisaged by Edison in his original patent, though the wording "in any suitable manner" was obviously intended to pave the way for alternatives and afterthoughts.

The British version of the Edison patent ran¹² to a second edition in 1922; and Stoller was into hardware again¹³ in 1929 with a more sophisticated regulator which added three triodes and a saturable reactor to the diode. This time he was regulating an alternating voltage, for the Edison invention (unlike other methods) would work just as well for regulating an alternating supply as it would when controlling a d.c. generator. Considering how bitterly Edison himself had once opposed alternating supplies, it seems ironic that this work of Stoller should have applied Edison's invention in just that field. Benson quotes¹⁴ a number of later usages, during the next 20 years or so; but it is doubtful whether the users gave much credit to the patent Edison filed on November 15, 1883.

So, should we have been toasting Thomas Edison on November 15, 1983, for the first electronics patent ever? I think that we should. The Germans set us an example by honouring 100 years of the Edison effect itself, in organising a conference on electron tubes May 18-20, 1983, in the Garmisch-Partenkirchen congress centre. In its way, this helped to compensate for much neglect of Edison's invention, which preceded such currently important thermionic devices as the cathode-ray tube of Braun, the X-ray tube of Coolidge, and the fluorescent lamp. WWW

References

1. T. A. Edison, Electrical Indicator US Patent 307031 of October 21, 1884, filed November 15, 1883
2. F. Braun, *Ann. der Physik*, 1897, vol. 60, pp. 552-9.
3. A. Wehnelt, German Patent 157845 of January 15, 1904.
4. P. Cooper-Hewitt, *Electrician*, vol. 50, January 16, 1903, pp. 509-11.
5. J. A. Fleming, 1890, *Proc. Roy. Soc.* 47, p. 120.
6. J. A. Fleming, 1896, *Phil. Mag.* 42, p. 99 and *Proc. Phys. Soc.* 14, pp. 238-9.
7. T. A. Edison, Regulator for Dynamo-Electric Machines, US Patent 287524 of October 30, 1883, filed December 8, 1882.
8. G. Shiers, The first electron tube, *Scientific American*, March 1969, pp. 104-10.
9. E. B. Craft & E. H. Colpitts, Radio telephony, *Jour. A.I.E.E.*, 1919, vol. 38, pp. 305-35.
10. Gerald F. J. Tyne, *Saga of the Vacuum Tube*, Sams 1977, pp. 147-8.
11. H. J. van der Bijl, *Thermionic Vacuum Tube*, McGraw-Hill, 1920, pp. 142-4.
12. T. J. Handford, British Patent 2988 of February 8, 1884.
13. H. M. Stoller & J. R. Power, Precision regulator for alternating voltage, *Electrical Engg.*, 1929, vol. 48, pp. 110-3.
14. F. A. Benson, *Voltage Stabilised Supplies*, Macdonald, 1957, pp. 254-61.

Keyboard encoder

Besides being cheap, this keyboard encoder has roll-over protection, letters-only shift lock and can produce 128 ASCII characters and 128 control codes. It is not necessary to unlock the shift key to type single lower-case characters — an led status indicator prevents ambiguity. When function key S_5 is locked, shift lock is released so that bit seven may be active with shifted or unshifted characters or control codes, providing an eight-bit set of codes.

Circuit IC_2 is a 16-line decoder for key-

Keyboard connections

Row	ASCII column							
	7	6	5	4	3	2	1	0
0	P			@				SP
1	Q	A						
2	R	B			2			
3	S	C			3			
4	T	D			4			
5	U	E			5			
6	V	F			6			
7	W	G			7			
8	X	H			8			
9	Y	I			9			BS TAB
10	Z	J			10			LF
11	(K			11			ESC
12)	L			12			
13		M			13			
14		N			14			
15	DEL	O			15			

output goes high, IC_{2a} forces the DDR line high and clears the uart data-ready output.

If the program retrieved from cassette is as follows

```

NOP
NOP
.
.
NOP
LXI H, 000016
MVI M, byte 1
INX H
MVI M, byte 2
INX H
MVI M, byte 3
.
.
INX H
MVI M, byte n
HLT
NOP
.
.
NOP
    
```

the processor stores the operating system programs contained in bytes 1 to n starting at memory location 0000. After the program is loaded, the switch is set to the normal position and the reset button pressed to execute the loaded program.


G. A. M. Labib
Heliopolis
Cairo

board scanning and IC_3 is a priority encoder for sensing. Input sequence of IC_3 is the reverse of the priority sequence to provide positive logic at the three data outputs. Each of the 16 decoder outputs is connected to three character switches to provide four least-significant ASCII bits. Switches one to three provide shift-lock, shift and control functions respectively and further optional switches four and five provide control lock and determine the

state of bit 7 for special functions. Shift operates differently on letters and numbers by gating which controls bit 6.

Minimal screen flicker and program interruption will occur when the decoder is driven by vertical sync. from the v.d.u. I used a 7493 instead of developing software.

E. Goodchild
Rotorua
New Zealand

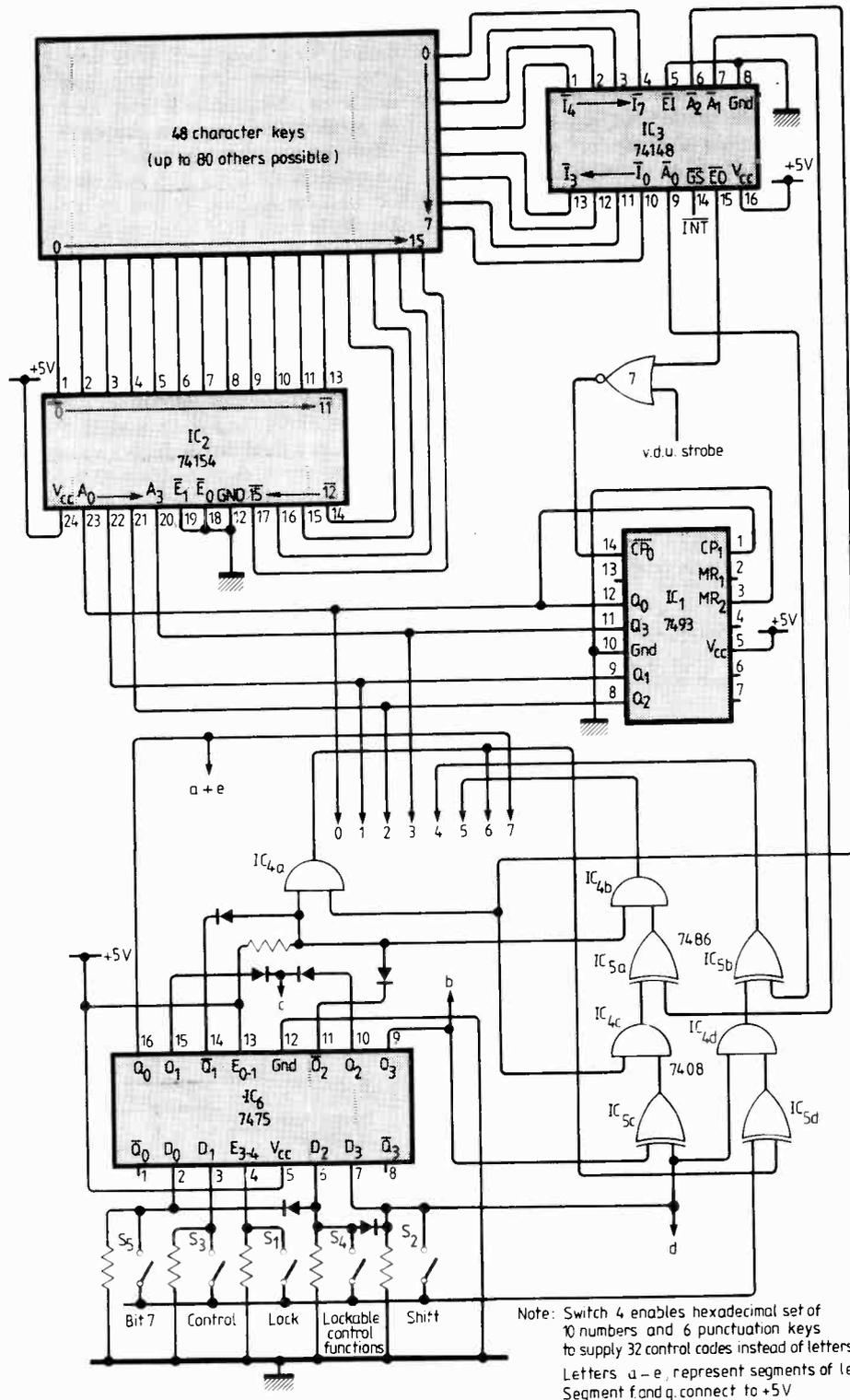

CIRCUIT IDEAS

High-resolution point display

This circuit was developed to display up to 512 points logged to 9-bit resolution on a tv point-digitizing system. Only 2K bytes of memory are used since it is not necessary to reserve a memory location for each possible coordinate on the screen.

Video memory consists of just two MK4801AN, 70ns byte-wide devices. During data loading, video memory is connected to data and address buses of the digitizing system (in this case Z80-based) at the points indicated on the diagram through software-controlled three-state buffers; outputs of these buffers are high-impedance while the display is in use. The memories are divided into four pages of 512 bytes designated X₀, X₁, Y₀ and Y₁.

Data outputs of X memory are connected to one side of an eight-bit comparator, the other side of which is fed by the lower eight bits of a nine-bit counter. This counter is clocked by an 8MHz crystal oscillator gated by a modified line-sync. pulse* which also resets the counter. Similarly Y-memory data output is compared with an eight-bit counter clocked by line-sync. pulses and cleared by a field-sync. pulse. The state of the line-sync. pulse from the TDA2571A sync. separator is latched on field-sync. pulses by the field-identifying bistable i.c. to determine which of the two

*Line sync. pulses from the TDA2571A have a 46% duty cycle and are satisfactory for field identification but must be modified for oscillator gating and counter reset.

fields of the 2:1 interlaced picture is currently being displayed. Output from the bistable i.c. (l.s.b. Y) is connected to A₉ of the Y memory and is used to select either page Y₀ or Y₁. The X counter's most-significant bit (m.s.b. X) is connected to A₉ of the X memory and selects either page X₀ or X₁.

Active-low comparator outputs feed a NOR gate, the output of which is injected into the video signal to produce a positive bright-up pulse when X and Y comparisons are true. This pulse is also used to clock a 9-bit video memory counter, connected to address lines A_{0,8} of the video memory, which selects the next set of coordinates for comparison. After field 1, i.e. after one complete picture has been displayed, this counter is reset. Four bytes of memory are required for each point displayed and the two bytes not holding coordinates are filled with null characters, i.e. 01₁₆ for X₀, Y₀, Y₁ and FF₁₆ for X₁. During line and field blanking the comparators are disabled so coordinates represented by these bytes have no effect. Blanking pulses are regenerated from sync. pulses but this is not shown on the diagram.

Coordinates must be stored in the video memory in time-sequential order with field zero before field one and low-value Y coordinates in a field before higher values and the same for X coordinates within a line. Bytes stored in video memory are not true coordinates but related to them.

X coordinate <255 - store X coordinate

directly in X₀ and put FF₁₆ in corresponding X₁ location.

X coordinate >255, <511 - store X coordinate - 256 in X₁ and put 01₁₆ in corresponding X₀ location.

Even Y coordinate - store Y coordinate/2 in Y₀ and put 01₁₆ in corresponding Y₁ location.

Odd Y coordinate - store (Y coordinate - 1)/2 in Y₁ and put 01₁₆ in corresponding Y₀ location.


Values of X and Y lower than say 10 will occur during the blanking period and will not be compared or displayed. Possible hexadecimal addresses for the four pages of video memory connected to the processor buses would be


X₀ 1000-11FF
X₁ 1200-13FF
Y₀ 1400-15FF
Y₁ 1600-17FF

Examples of five points loaded into video memory are shown in this table

Coordinates (Y,X)		Y0	Y1	X0	X1
40	40	20	01	40	FF
160	258	80	01	01	02
160	262	80	01	01	06
41	60	01	20	60	FF
301	286	01	150	01	30

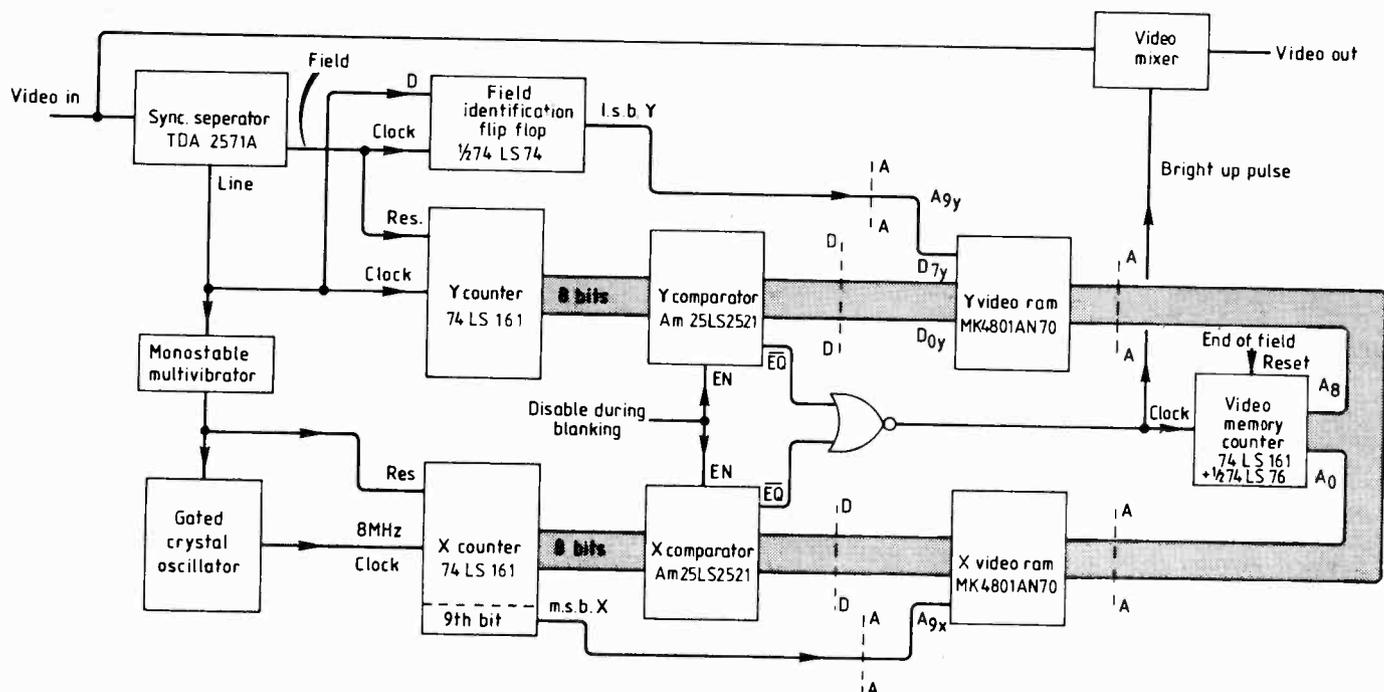J. M. Graham
Dunstaffnage Marine Research
Laboratory
Oban
Argyll



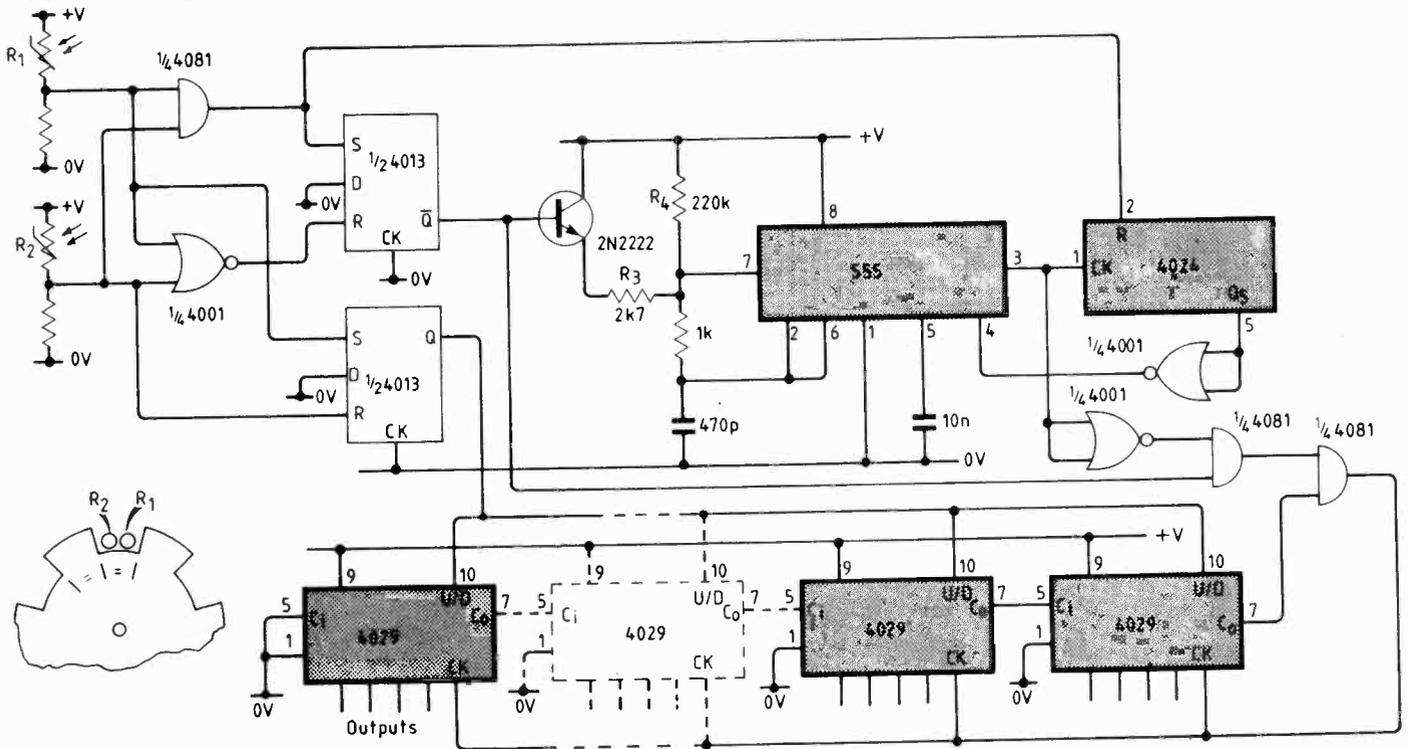

Non-linear rotation sensor

Useful when both coarse and fine adjustments have to be made using the same rotary control, this circuit provides between one and 16 pulses for each slot passing the sensors, depending on the disc's rotary speed. These pulses increment or decrement counters depending on the direction of rotation of the disc. Any number of counters may be used, whether binary or b.c.d. Resistor R_4 is chosen to suit the disc and R_3 is to set the 555 timer to the highest frequency possible.

D. F. Cook
Cleveland
Yorkshire

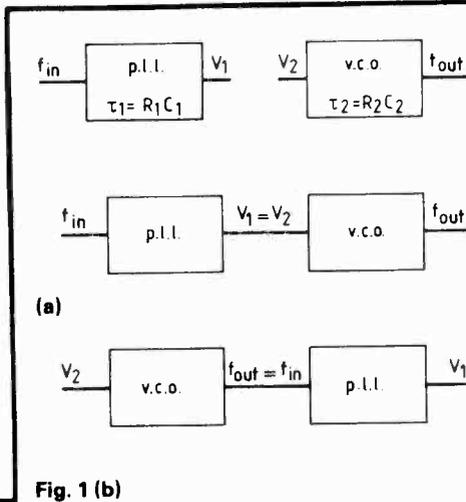


Fig. 1 (b)

Simple divide-by-fraction circuit

A stable p.l.l. with a frequency range of 0.01Hz to 100kHz may be obtained using the XR-2207 v.c.o. and an XR-2208 operational multiplier. These i.c.s are used in two ways - to design a divide-by-fraction circuit shown schematically in Fig. 1(a) and a low-noise amplifier as shown in Fig. 1(b). In both cases the mathematical treatment is the same and can be derived using Fig. 1(a). Since

$$f_{in} = V_1 / V_{cc} R_1 C_1$$

and

$$f_{out} = V_2 / V_{cc} R_2 C_2$$

it follows that

$$f_{out} = \frac{R_1 C_1}{R_2 C_2} f_{in} = \frac{R_1}{R_2} f_{in}$$

for $C_1 = C_2$. Also, the system functions as a simple divide-by-fraction circuit in which the fraction frequency is set by the ratio of $R_1 : R_2$.

The same holds for Fig. 1(b). Under the assumption $f_{out} = f_{in}$,

$$V_1 = R_1 V_2 / R_2$$

i.e. the circuit may be used as a low-noise amplifier. A practical circuit is shown in Fig. 2. Values of R_1 and C_1 can be calculated according to the lock and capture range as usual.

Kamil Kraus
Rokycany
Czechoslovakia

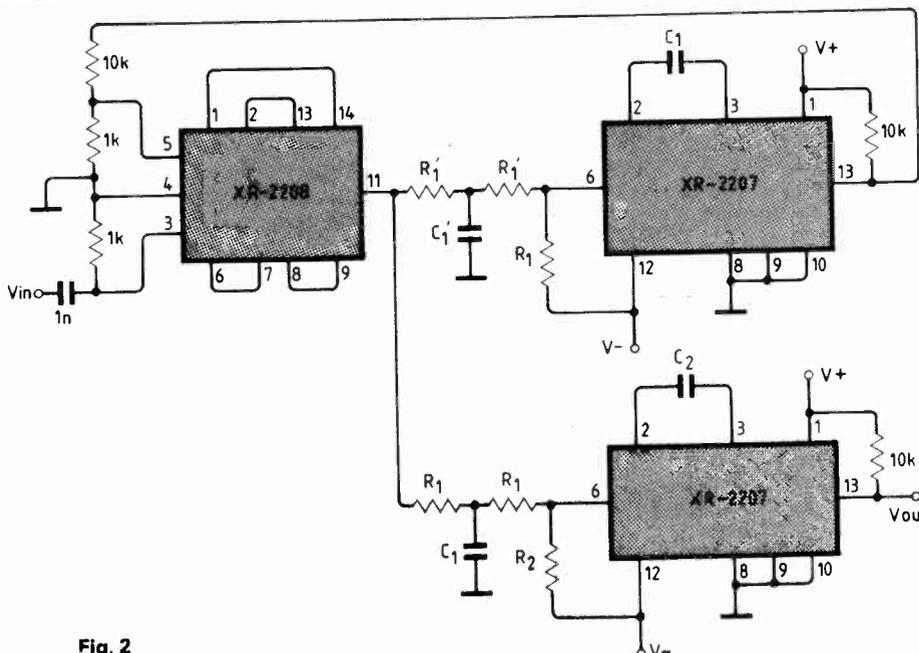


Fig. 2

Microcomputer organ interface — improvisation by Forth

Complete details of a vocabulary that will provide polyphonic improvisations when used with the Nascom 2 organ interface described in the June and July 1983 issues

The Forth application to provide simple polyphonic extemporizations from a given theme was described in outline in last July's issue. Full details of this are now given, including the entire vocabulary (List 3) and a glossary.

The first steps were to find Forth and to put it in a convenient place in ram. This was done by assembling 8080 FIG-Forth release 1.1 (a public domain listing) under the Nascom Zeap editor assembler. Having removed most of the comments, a month of spare-time typing yielded a 40K edit buffer which took about 15 minutes to assemble. The origin was placed at 1500₁₆, leaving space below Forth for the essential parts of the organ interface plus a substantial scratchpad area for additional console fields. A Forth-compiled editor from the Forth Installation Manual was added, together with simulation of virtual memory, to suit a Nascom 2 with 64K of ram but without discs.

Forth uses postfix or reversed Polish notation, e.g. `HEX 2 A + .` when entered returns the answer `C .` Code groups are separated by spaces. Each group is interpreted as a word (a command, variable or constant) or, if it is not in the vocabulary, a number if possible. Thus `FFFF` is meaningless in standard Forth unless operation is in a suitable number base such as hexadecimal, which as above is achieved by the word `HEX`. In this simple example the two code groups after `HEX` are interpreted as numbers and are transferred to the stack. The `+` pops them into the `HL` and `DE` register pairs respectively, adds them and pushes the answers back onto the stack. The `.` (pronounced 'dot' although 'print' might be more appropriate) displays the answers and leaves the stack empty.

At first sight, a screen of Forth code such as List 2 might be incomprehensible whilst having a startled appearance because of the sprinkling of exclamation marks, but the mysteries soon fall away. `!` is pronounced 'store' and it is a word which does just that, e.g. `9400 TUN !`

by R. D. Easson

stores the value 9400 (in whatever number base has been set, being 16 throughout this article) in the variable `TUN`, which was created with initial value 7400 by loading 0 of List 2. The complementary word is `@`, pronounced 'fetch'. `C!` and `C@` are the equivalents for single-byte numbers, although these are kept on the stack as two-byte numbers, one byte being zero. Double-precision (four-byte) numbers are also provided for but are not used in this article. The letter `U` as in `U.` or `U<` indicates unsigned, so that positive 16-bit numbers can go up to `FFFF`. (Any number base can be used. If `HEX B250` is entered and operation then changes to base 36 (by `DECIMAL 36 BASE !`) the number is returned by `. as Z80`).

Forth has two stacks. The principal one is referred to as the parameter or computation stack, or just as the stack. The other one is called the return stack, used mainly as a temporary parking area for numbers which would otherwise get in the way on the parameter stack.

`DUP`, `SWAP`, `OVER`, `DROP` and `ROT` (pronounced rote, short for rotate) and their four-byte equivalents rearrange the stack. `ROT`, for example, brings the third (two-byte) item to the top. `DUP` duplicates the top item; `OVER` duplicates the second item and pushes it on top; `SWAP` swaps the two top items; and `DROP` drops one item.

Conditional tests such as `=` take two parameters from the stack, replacing them with the true (1) or false (0) result, which is in turn destroyed when the test result is used.

An example of a definite loop occurs in List 2, line 1, as far as 'loop'. This also illustrates one use of the return stack. The 'limit' for the first loop (10H) and its 'index' (initially 0) are put to the return stack when the loop is executed. The

Forth word `I` copies the top item on the return stack to the parameter stack, thus allowing the index to be used as a parameter in the loop itself, as in the same example from List 2.

Examples of indefinite (conditional) loops occur in List 2 lines 14 and 15 and in List 3 Screen 6 lines 2 and 3. Forth does not have a 'goto' instruction so that its users are forced to structure their programs and not to be quite so lazy as they might otherwise be.

Perhaps Forth is best known for its so-called self-compiling ability, meaning not that it compiles itself but that it is compiled by Forth. In many applications, such as the one described in this article, this need mean no more to the user than that Forth words may be strung together to form new words, as is done throughout List 2 and List 3. For example, line 7 of List 2 comprises the 'colon definition' of `I.PDPS`. When this is loaded, `I.PDPS` is compiled as a new word in the Forth dictionary. `I.PDPS` can then be used, which causes the words in its definition to be executed, i.e. the value of variable `TUN` is fetched, incremented, the result stored at 1430H, and similarly for `IMP`. `I.PDPS` will disappear after a cold start unless the appropriate Forth start-up parameters are changed. In this way a program can be developed on screens, which may be held in virtual memory or in ram, until a satisfactory version is obtained. This can then be loaded from cold and kept in the protected dictionary. It is not necessary to use the editing screens: the vocabularies of Lists 2 and 3 could be compiled directly.

For the application of Forth described in this article it is not necessary to delve into it more deeply, but `ORCF` from List 1 is taken as an example of a Forth word. Lines 8140 to 8155 comprise the 'head' and lines 8160 to 8240 form the 'body'. The code pointer distinguishes between the different kinds of word (machine code, colon definition, constant or variable). If `ORCF` were written in Forth rather than

1545	8000	ORC	1545H	
1545	8005	ENT		
1545 0A	8010	NEXT	A (BC)	
1546 1F51	8015	DEFS	1E51H	
3397 00	8020	DUMP	DEFB 0	
3398 0010	8025	DEFS	1DH	
33E5 85	8030	DEFS	85H	; UUCF1
33E6 55554346	8035	DEFM	/UUCF/	
338A E1	8040	DEFB	"1+80H	
33E8 9033	8045	DEFM	DUMP-7	; Vocabulary-link to DUMP
33B0 EF33	8050	UUCF1	DEFW *+2	; Code pointer
33EF C5	8055		PUSH EC	; Save Forth IF
33C0 2A3014	8060		LD HL (1430H)	; Ready FDP
33C3 8A00	8065		LD E 0DH	; MSE of CFF to B
33C5 4E	8070		LD C C	; LSB of CFF to C
33C6 79	8075		LD A C	; & to A
33C7 06FF	8080		SUB ZFF	; Finish if
33C9 2806	8085		JR Z 08H	; end of frame
33C8 23	8090		INC HL	; Inc FDP
33C0 7E	8095		LD A (HL)	; Data to
33C0 02	8100		LD (BC) A	; console field
33CE 23	8105		INC HL	; Inc FDP
33CF 1BF4	8110		JR -0AH	; Go back for more
33D1 C1	8115		POP EC	; Return Forth IF
33D2 23	8120		INC HL	; Inc FDP
33D3 223014	8125		LD (1430H) HL	; Park FDP
33D6 C34515	8130		JP NEXT	; Goto Forth Interpreter
33D9 00	8135		DEFB 0	
33DA 84	8140		DEFB 84H	; ORCF
33DB 4F5243	8145		DEFM /ORC/	
33DE C6	8150		DEFB "F+80H	
33DF 8533	8155		DEFM UUCF1-B	; Voc-link to UUCF1
33E1 E333	8160	ORCF	DEFW *+2	; Code pointer
33E3 09	8165		EXX ; Save IP	
33E4 0610	8170		LD B' 10H	; Set byte count
33E6 E1	8175		POP HL	; Top stack item to HL'
33E7 09	8180		EXX ;	; (2nd CF source & dest.)
33E8 E1	8185		POP HL	; Next stack item to HL
33E9 09	8190		EXX ;	; (1st CF source)
33EA 7E	8195		LD A (HL')	; Load byte from 2nd CF
33EE 09	8200		EXX	
33EC E6	8205		OR (HL)	; Combine two CF bytes
33ED 23	8210		INC HL	; Inc CFF
33EE 09	8215		EXX	
33EF 77	8220		LD (HL') A	; Combined byte to 2nd CF
33F0 23	8225		INC HL	; Inc CFF'
33F1 10F7	8230		DJNZ -7	; Loop until done
33F3 09	8235		EXX ;	; Return IP
33F4 C34515	8240		JP NEXT	; Goto Forth Interpreter
33F7 85	8245		DEFB 85H	; CC4/3
33F8 4343342F	8250		DEFM >CC4/>	
33FC B3	8255		DEFB "3+80H	
33FD D633	8260		DEFM ORCF-7	; Voc-link to ORCF
33FF 0134	8265	CF43	DEFW *+2	; Code pointer
3401 00	8270		NOP	
3402 211814	8275		LD HL 1418H	; Ready FU pointer
3405 09	8280		EXX ; Save IP	
3406 0618	8285		LD B' 18H	; Set byte count
3408 2A3214	8290		LD HL (1432H)	; Ready output FDP (FO)
340E 110014	8295		LD DE' 1400H	; Ready FO pointer (E' is
	8300 ;		also register number)	
340E 1A	8305		LD A (DE')	; Load FO byte
340F 09	8310		EXX	
3410 96	8315		SUB (HL)	; Sub FU byte from FO one

List 1. Four Forth words in machine code provide fast communication between the Forth stack and the interface console and data fields. Two further words hasten semitone transposition.

3411 2807	8320	JR Z 9H		; Hop if there's no change
3413 7E	8325	LD A (HL)		; Ready FU byte
3414 09	8330	EXX		
3415 73	8335	LD (HL') E'		; Regno. to data field
3416 23	8340	INC HL'		; Inc FDP (FO)
3417 77	8345	LD (HL') A		; Reg status to data field
3418 23	8350	INC HL'		; Inc FDP (FO)
3419 09	8355	EXX		
341A 23	8360	INC HL		; Inc FU pointer
341B 09	8365	EXX		
341C 13	8370	INC DE'		; Inc FO pointer
341D 10EF	8375	DJNZ -15		; Loop until done
341E 7FFF	8380	LD A E'FF		; Ready frame byte
3421 77	8385	LD (HL') A		; Frame byte to data fld.
3422 23	8390	INC HL'		; Inc FDP (FO) to T posn.
3423 223214	8395	LD (1432H) HL'		; Park FDP (FO)
3424 09	8400	EXX ;		; Return IP
3427 00	8405	NOP		
3428 C34515	8410	JP NEXT		; Goto Forth Interpreter
342B 83	8415	DEFB 83H		; CF
342C 4346	8420	DEFM /CF/		
342E BE	8425	DEFB "3+80H		
342F F733	8430	DEFM CP43-8		; Voc-link to CC4/3
3431 3334	8435	DEFW *+2		; Code pointer
3433 09	8440	EXX ;		; Save IP
3434 01	8445	POP DE'		; Destination from stack
3435 E1	8450	POP HL'		; Source from stack
3436 011000	8455	LD BC' 0018H		; Set byte count
3439 E080	8460	LDIR ;		; Do CF transfer
343B 09	8465	EXX ;		; Return IP
343C C34515	8470	JP NEXT		; Goto Interpreter
343F 85	8475	DEFB 85H		; 2/MOD
3440 321404	8480	DEFM 2/MOD		
3441 04	8485	DEFB "D+80H		
3445 2E24	8490	DEFM CF-4		; Voc link to CF
3447 4034	8495	DEFW *+2		; Code pointer
3449 11	8500	POP HL		; Get data from stack
344A 0A00	8505	SK1 ;		; Shift (divide by 2)
344C 54	8510	LD D H		; Save quotient
344D 50	8515	LD E L		
344E 310000	8520	LD HL 0		
3451 3033	8525	JR NC 5		; Push carry flag
3453 210100	8530	LD HL 1		; to stack
3456 E0	8535	PUSH HL		
3457 05	8540	PUSH DE		; Quotient to stack
3458 C34515	8545	JP NEXT		; Goto Interpreter
345E 8A	8550	DEFB 8AH		; 2*M
3460 302A	8555	DEFM 2*/		
3461 00	8560	DEFB "M+80H		
3462 0E34	8565	DEFM MOD2-8		; Voc-link to 2/MOD
3463 6334	8570	DEFW *+2		; Code pointer
3464 E1	8575	POP HL		; Get data from stack
346A 0025	8580	SLA L		; Shift (mult. by 2)
346F 3004	8585	JR NC 6		; Add carry if
346B 110001	8590	LD DE 0100H		; present and
346E 19	8595	ADD HL DE		; push answer
346F E5	8600	PUSH HL		; to stack
346D C34515	8605	JP NEXT		; Goto Interpreter

machine code it would have a different code pointer (the address of a machine code routine called 'do colon') followed by a series of two-byte numbers called the parameter field, being the code pointer addresses of the words which would form the body of the definition. When such a word is executed, each code pointer ultimately leads to a machine code routine, which might be many levels below it.

'Starting Forth' by Leo Brodie (Prentiss Hall, 1981) provides a more detailed introduction to Forth.

Forth as 'composer'

Following the installation of Forth, the next thing was an interesting test to see whether Forth and the organ interface software would co-exist. Fortunately they did. Four Forth words were then written to enable Forth to work in the interface data fields (in data format) and console fields. These were written in machine code (List 1) rather than Forth partly to achieve faster operation (a challenge to someone to prove that Forth is faster?) but mainly because the elements of three of them already existed, the extra one being ORCF.

The next objective was to achieve the simplest kind of improvisation, a parallel doubling of the theme at any chosen interval (and, as it happened, at any desired pitch for each part). Thus far,

therefore, a sledgehammer to crack a walnut, but of course with further development in mind.

It took two weeks of spare time from the coexistence test to reach this objective, the additional nine-word vocabulary for which is shown in List 2, which also illustrates two console fields. T.OUT later became the two words TOR2 and OWT, but the other eight words all survive (albeit with some changes) in the current vocabulary (List 3) which was completed five weeks later. Certain weaknesses were identified in the vocabulary of List 2:

-use of hexadecimal addresses rather

- than variables and constants (this becomes tedious if more than a few such numbers are required)
- lack of clear functional allocation of console fields
- badly structured multiple function of T.OUT
- eccentric way of leaving the WHILE loop, with the bogus conditional in ?AA inefficient use of /MOD and 2 for the nine-bit divide and multiply by two required for semitone transposition. (The substitution of 2/MOD and 2*M also on List 1 speeded things up by a factor of three.)

```

1 LIST
2 SCR # 1
3 0 HEX 7400 VAR TUN 8400 VAR IMP
4 1 I.CF 10 0 DD 0 0D03 1 + C' LOOP 7 0 DD FF 0D01 I + C'
5 2 LOOP 80 0D00 C' 0D00 1400 CF> 0D00 141B CF> 0D00 0D18 CF> ;
6 3 TU 0 0 10 DO 141F I + C' 2* + DUF FF > SWAP 141F I
7 4 + C' -1 + LOOP DROP ;
8 5 TD 0 10 0 DD 0D20 I + C' 2 /MOD ROT + 0D20 I + C'
9 6 IF 80 ELSE 0 THEN LOOP DROP ;
10 7 I.PDS TUN @ 1+ 1430 I IMP @ 1+ 1432 I ;
11 8 DODE 1430 @ DUF @ 1432 @ DUF ROT SWAP I
12 9 2+ 1432 I 2+ 1430 I ;
13 10 U.CFS UUCF1 0D00 141B CF> 0D00 0D18 CF> ;
14 11 T.OUT TD TU TU TU 0C20 1 20 ORCF CC4/3 141B 1400 CF> ;
15 12 ?AA 1430 @ 2- @ AAAA = IF . Improvisation completed "
16 13 QUIT THEN I ;
17 14 ORGANUM I.CF I.PDS BEGIN DODE ?AA WHILE
18 15 U.CFS T.OUT REPEAT ;
19 OR

```

```

1400 80 FF FF FF FF FF FF FF
1408 00 00 00 00 00 00 00 00
1410 00 00 00 00 00 00 00 00
1418 80 FF FF FF FF FF FF FF
1420 00 00 00 00 00 00 00 00
1428 00 00 00 00 00 00 00 00

```

List 2. Nine-word vocabulary provides improvisation as parallel "organum" in two parts. Two of the console fields as set by I.CF are also shown.

```

1 LIST
SCR # 1
0 HEX 8400 VAR TUN 8900 VAR IMP 1 VAR FI 1 VAR FO 1 VAR F1
1 1 VAR F2 1 VAR F3 1 VAR F4 1 VAR T1 1 VAR T2 1 VAR T3 1 VAR T4
2 1 VAR BOF2 1 VAR BOF3 1 VAR TA 9900 VAR IMP2 9100 VAR IMP3
3 0000 CON F1 0D18 CON F2 1418 CON FU 1400 CON FO 0 VAR BOFMO
4 1438 CON F1 1450 CON F2 1468 CON F3 1480 CON F4 1498 CON OF1
5 14E0 CON OF2 14CB CON OF3 14E0 CON OF4 0 VAR FOFU 0 VAR POFD
6 2 VAR FOFHA 2 VAR FOFHB
7
8 : U.CFI FI @ 1430 ! UUCFI 1430 @ FI ! ;
9 : I.CF 10 0 0 0 FI 8 + I + C! LOOP 8 0 DO FF FI I + C!
10 LOOP 8 0 DO FI LOOP 80 FI C! FD CF FU CF> FO CF>
11 FI CF> F2 CF> F3 CF> F4 CF> OF1 CF> OF2 CF> OF3 CF> OF4 CF> ;
12 : TU 0 0 10 DO FU 7 + I + C@ 2*M + DUF FF > SWAP FU 7 + I
13 + C! -1 + LOOP DROP ;
14 : TD 0 10 0 DO FO 8 + I + C@ 2/MDD ROT + FO 8 + I + C!
15 IF 80 ELSE 0 THEN LOOP DROP ;
OK
2 LIST
SCR # 2
0
1 : TDR 0 6 0 DO FD C + I + C@ 2/MDD ROT + FD C + I + C!
2 IF 80 ELSE 0 THEN LOOP DROP ;
3 : TRDHE POFHE @ 0 = 0 IF POFHE @ 0 DO TDR LOOP THEN ;
4 : CS 6 0 DO OF1 12 + I + @ 0 = 0 IF I I LEAVE THEN LOOP ;
5 : CSCB CS OF1 12 + @ 0 = 0 IF DUP OF1 12 + @ SWAP OF2 C +
6 @ = IF OF2 FD CF> TRDHE FD OF2 CF> THEN I THEN DROP ;
7 : TUA 0 0 6 DO FU 8 + I + C@ 2*M + DUF FF > SWAP FU 8 + I
8 + C! -1 + LOOP DROP ;
9 : THUA OF2 FU CF> TUA TUA FU OF2 CF> ;
10 : THDA OF2 FD CF> TDR TDR FD OF2 CF> ;
11 : TRUHA POFHA @ 0 = 0 IF POFHA @ 0 DO TUA LOOP THEN ;
12 : CSCA CS OF1 12 + @ 0 = 0 IF DUP THDA OF1 12 + @ SWAP
13 OF2 C + @ = 0 IF OF2 FU CF> TRUHA FU OF2 CF> THEN THUA
14 I THEN DROP ;
15 : AMS CSCB CSCA ;
OK
3 LIST
SCR # 3
0
1 : TRU POFU @ 0 = 0 IF POFU @ 0 DO TU LOOP THEN ;
2 : TRD POFD @ 0 = 0 IF POFD @ 0 DO TD LOOP THEN ;
3 : TOR2 TRD TRU FD 8 + FU 8 + ORCF ;
4 : TOR3 TRD TRU FD 8 + FU 8 + ORCF FI 8 + FU 8 + ORCF ;
5 : TUB F 0 DO FD 7 + I + C@ FD 8 + I + C! LOOP 0 FU 17 + C! ;
6 : TR1-2 6 0 DO TUR LOOP TU ;
7 : TR2-1 6 0 DO TDR LOOP TD ;
8 : TR2 P 4 0 DO TUR LOOP TU TU TU TU ;
9 : TRIPS 5 0 DO TUN @ J+ LOOP FI P1 ! P2 ! P3 ! P4 !
10 IMP @ 1 ! FO ! ;
11 : CPUVD FO @ 1432 ! CPUV 1432 @ FO ! ;
12 : DODE FI @ DUF @ FO @ DUF P@T SWAP ! 2+ PO ! T2 @ TA ! ;
13 : OWT CPUVD FU FO CF> ;
14 : U.CFS U.CFI FI FO CF> FI FO CF> ;
OK
4 TRIAD
SCR # 4
0 : PAA FI @ 2 - @ AAAA = 0 = ;
1 : KWIT "Improvisation completed" QUIT ;
2 : ORGANUM POFD POFU ! I.CF I.PDFS BEGIN DODE ?AA WHILE
3 U.CFS DUF 3 = IF TOR3 ELSE TOR2 THEN OWT REPEAT DROP KWIT ;
4 : D1R T1 C@ T1 1+ C@ T1 C! T1 1+ C! ;
5 : D2R T2 C@ T2 1+ C@ T2 C! T2 1+ C! ;
6 : D3R T3 C@ T3 1+ C@ T3 C! T3 1+ C! ;
7 : DUF F1 @ DUF @ T1 ! D1R T1 @ DUF BOF2 @ 10 * + T2 ! BOF3 @
8 10 * + T3 ! 2+ DUF DUF P1 ! P2 ! P3 ! ;
9 : STUF I.CF POFD ! POFU ! BOF3 ! BOF2 ! I.PDFS DUF ;
10 : ODD1 FO @ DUF D1R T1 @ D1R SWAP ! 2+ PO ! T1 @ TA ! ;
11 : ODD2 FO @ DUF D2R T2 @ D2R SWAP ! 2+ PO ! T2 @ TA ! ;
12 : ODD3 FO @ DUF D3R T3 @ D3R SWAP ! 2+ PO ! T3 @ TA ! ;
13 : UDF1 F1 FI CF> P1 @ PI ! U.CFI FI F1 CF> FI OF1 CF>
14 FI @ P1 ! ;
15
SCR # 7
0 : UDOF2 POFU @ POFD @ < IF FO ELSE FU THEN OF2 CF> ;
1 : UDF2 F2 FI CF> P2 @ PI ! U.CFI FI @ P2 ! FI FU CF> FI F2 CF>
2 TR1-2 FU FD CF> TRU TRU UDOF2 ;

```

List 3. Larger vocabulary provides organum and canon ("melisma") and variation with accompaniment ("motet"). AMS harmonizes two of the parts.


```

3 : UDF3 F3 FI CF> P3 @ PI ! U.CFI FI F3 CF>
4 FI FU CF> TR1-2 TR2-P FU OF3 CF> PI @ P3 ! ;
5 : TORCF AMS FU CF> 8 + FU 8 + ORCF ;
6 : TORCF3 OF1 OF2 TORCF OF3 8 + FU 8 + ORCF ;
7 : UDEF UDF1 UDF2 OF1 OF2 TORCF ;
8 : DIFT2 T2 @ TA @ -1 - T2 ! ;
9 : DOT1 P1 @ DUP @ T1 ! D1R 2+ P1 ! ;
10 : DIFT1 T1 @ TA @ -1 - T1 ! ;
11 : DOT2 P2 @ DUP @ T2 ! D2R 2+ DUF FI ! P2 ! ;
12 : DIFT3 T3 @ TA @ -1 - T3 ! ;
13 : DOT3 P3 @ DUP @ T3 ! D3R 2+ P3 ! ;
14 : WRAA AAAA FO @ ! ;
15 : T2* T2 @ 2* T2 ! ;
SCR # 8
0 : UDOF2 T1 @ T2 @ = IF DOD1 UDEF DOT1 DOT2 ELSE T1 @ T2 @
1 U< IF DOD1 UDF1 OF2 OF1 TORCF DIFT2 DOT1 ELSE DOD2
2 UDF2 OF1 OF2 TORCF DIFT1 DOT2 THEN THEN OWT ;
3 : ZCLOOP BEGIN UDRD2 ?AA WHILE REPEAT WRAA ;
4 : ZCANON STUF ZCLOOP KWIT ;
5 : UDF2M F2 FI CF> P2 @ PI ! U.CFI FI F2 CF> PI @ P2 !
6 FI OF2 CF> ;
7 : UDRD.M T1 @ T2 @ 2DUP = IF DOD1 UDF1 UDF2M DOT1 DOT2 ZDRDP
8 ELSE U< IF DOD1 UDF1 DIFT2 DOT1 ELSE DOD2 UDF2M DIFT1 DOT2
9 THEN THEN FI FU CF> OWT ;
10 : MLOOP BEGIN UDRD.M ?AA WHILE REPEAT WRAA ;
11 : MELISMA STUF MLOOP KWIT ;
12 : UDRD3 T1 @ T2 @ U< IF T1 @ T3 @ U<
13 IF DOD1 UDF1 TORCF3 DIFT2 DIFT3 DOT1 ELSE T1 @ T3 @ =
14 IF DOD1 UDF1 UDF3 TORCF3 DIFT2 DOT1 DOT3
15 ELSE DOD3 UDF3 TORCF3 DIFT1 DIFT2 DOT3 THEN THEN -->
fig
OK
9 LIST
SCR # 9
0 ELSE T2 @ T3 @ U< IF T1 @ T2 @ =
1 IF DOD1 UDF1 UDF2 TORCF3 DIFT3 DOT1 DOT2
2 ELSE DOD2 UDF2 TORCF3 DIFT1 DIFT3 DOT2 THEN
3 ELSE T1 @ T2 @ = IF T2 @ T3 @ =
4 IF DOD1 UDF1 UDF2 UDF3 TORCF3 DOT1 DOT2 DOT3
5 ELSE DOD3 UDF3 TORCF3 DIFT1 DIFT2 DOT3 THEN
6 ELSE T2 @ T3 @ = IF DOD2 UDF2 UDF3 TORCF3 DIFT1 DOT2 DOT3
7 ELSE DOD3 UDF3 TORCF3 DIFT1 DIFT2 DOT3 THEN
8 THEN THEN THEN OWT ;
9
10 : 3CLOOP BEGIN UDRD3 ?AA WHILE REPEAT WRAA ;
11 : 3CANON STUF 3CLOOP KWIT ;
12 : UDF2P F2 FI CF> P2 @ PI ! U.CFI FI F2 CF>
13 FI FU CF> TR1-2 TR2-P FU OF2 CF> PI @ P2 ! ;
14
15
OK
10 LIST
SCR # 10
0 : UDEFPP UDF1 UDF2P OF1 OF2 TORCF ;
1 : UDRD2P T1 @ T2 @ = IF DOD1 UDEFPP DOT1 DOT2 T2* ELSE T1 @
2 T2 @ U< IF DOD1 UDF1 OF2 OF1 TORCF DIFT2 DOT1 ELSE DOD2 UDF2P
3 OF1 OF2 TORCF DIFT1 DOT2 T2* THEN THEN OWT ;
4 : 2PCLOOP BEGIN UDRD2P ?AA WHILE REPEAT WRAA ;
5 : DU2' P1 @ DUP @ T1 ! D1R T1 @ BOF3 @ 10 * + T2 !
6 2+ DUF P1 ! P2 ! ;
7 : MOTET BOFMO ! STUF 2PCLOOP IMP2 @ 1+ PO ! TUN @ 1+ P1 ! DU2'
8 MLOOP IMP @ 1+ P1 ! IMP2 @ 3 + P2 ! P1 @ DUP @ T1 ! D1R
9 T1 @ BOFMO @ 10 * + T2 ! 2+ P1 ! IMP3 @ 1+ PO ! ZCLOOP KWIT ;
10
11
12
13
14
15
OK

```

The operation of TU and TD (and, later on, TR1-2 etc) may be understood from the particular wiring sequence (chosen by chance before even translate mode has been planned) for the 128 connections to the keying registers. The three divisions of the organ for which the interface was designed are designated M1 (Manual 1 or Hauptwerk), M2 (Manual 2 or Rugpositiv) and Pedal, with 49 notes on each manual and 30 on the pedal, allocated as in Fig. 1. The odd feature of this arrangement is that a carry from the top (most-significant bit) of one register appears at the bottom of the register below it in the numerical sequence.

List 2 serves as an introduction to the larger vocabulary of List 3, in which the earlier weaknesses are corrected although Forth experts could no doubt find many more. In the shorter vocabulary, the only word which the user need know about is ORGANUM, which unlike the List 3 version does not take any parameters from the stack, so that it is necessary to edit and reload the Forth source code if different transpositions are required. In the List 3,

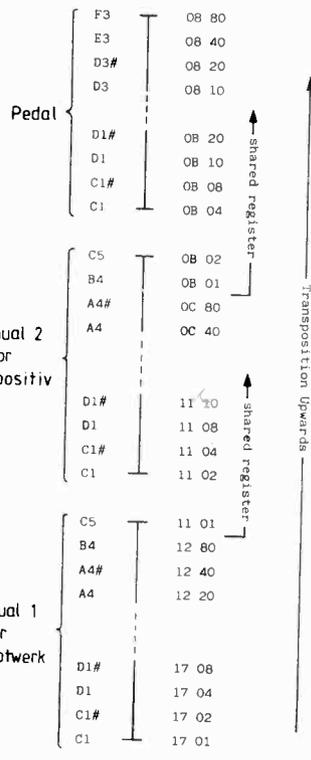

vocabulary five words are available to the user: ORGANUM, 2 CANON, MELISMA, 3CANON and MOTET, executed as described in the glossary. (Apologies for the fanciful use, or misuse, of some of these terms).

It is assumed for the harmonization rule that the improvisation is a strict duo or trio, that is, with a single line of notes on each of two or three divisions of the instrument.

An incidental point is that some of the words can be used degenerately (e.g. 0 0 0 MELISMA) to strip out the redundant information which can be caused by L in translate mode. The difference is not usually significant: a saving of perhaps 20% of memory.

I am indebted to Ernest Hart for

Fig 1. Allocation of the 16 keying registers. By accident rather than design, the register numbers count in the opposite sense to the bit numbers. Registers also overlap between divisions of the organ. Register and bit-number registers 0-7 are used for stops and thumb-pistons.

drawing my attention to the theme of Tallis' canon, arranged with remarkable forethought about 400 years ago to give the improvisation vocabulary something to get its teeth into. The theme comprises four phases of eight notes, each having the same value. The phrases are

G G F# G G A A B
 G C C B B A A G
 D C A B B A A G
 D E F# G B A A G

To get consistent results the theme

needs to be in strict time, which can of course be achieved by the use of translate mode. If the notes are crotchets the first of each pair of repeated notes can be treated as a dotted quaver followed by a semiquaver rest. The possibilities appear endless – for example, by changing TUN and IMP one can produce an intricate three-part canon form from a melisma of a melisma of the original theme.

An improvement needed before the vocabulary is developed any further is to

provide buffers in the console fields, between the three divisions of the organ, to avoid the ambiguities which can occur at the extremes due to the shared registers (Fig. 1). The structure of the two-part words could also be improved to provide any of the three permutations, and more could be done to provide variation of speed between parts, rather than just having T2* in UDRD2P. Beyond that, some rules for the movement in pitch of one part in relation to another might be useful. WWW

Glossary

Variables					
TUN	start of input (theme) data field.	TRU	transpose FU up POFU semitones.	UDBP	update both parts when both change together in two-part canon, then TORCF.
IMP, IMP2, IMP3	start of output (extemporization) data fields.	TRD	transpose FD down POFD semitones.	DIFT1	difference T1. Update T1 by TA to correspond with changes in parts 2 and 3.
PI	temporary pointer in input data field.	TOR2	TRD then TRU; OR FU and FD; leave result on FU.	DIFT2, DIFT3	complementary to DIFT1.
P1, P2, P3	pointers in input data field for the first, second and third parts.	TOR3	TRD then TRU; OR FU and FD; OR result with FI and leave it on FU.	DOT1	do T1. Fetch the new value of T1 from input data field and update P1.
T1, T2, T3	durations for the three parts, taken from the input data field and corrected for the movement of each part.	TU8	transpose FU up eight semitones.	DOT2, DOT3	complementary to DOT1, but DOT2 also sets PI temporarily to stop the improvisation when P2 reaches the end of the input data field.
BOF2, BOF3	beat offsets for the second and third parts in semiquavers (units of 16 frames).	TD8	transpose FD down eight semitones.	WRAA	write AA AA as final duration in output data field.
TA	duration actual (relating to the output data field, to which the individual parts are referenced).	TR1-2	transpose from M1 (Manual 1) to M2 (Manual 2).	T2*	multiply T2 by two to make the pedal part play at half speed (see 2PCLOOP).
POFU, POFD	pitch offsets (up and down) for Manual 2 part, in semitones.	TR2-1	transpose from M2 to M1.		
POFHB, POFHA	pitch offsets for harmonization rule, in semitones.	TR2-P	transpose from M2 to Pedal.		
Constants define start addresses but their names are used for the fields themselves		I.PDPS	initiate pointers.		
FI, FD, FU, FO	input, transpose down, transpose up and output console fields (FU is also used as the most recent field for CPU/O. For this use, FO and FU are equivalent to console fields 1 and 2 in read mode).	CPU/O	transpose PO to and from scratchpad for CC4/3.	Two-part canon	
F1, F2, F3, OF1, OF2, OF3	input and output console fields for each part.	DODE	do delay. Transfer duration from input to output data field.	UDRD2	update registers and durations for two parts. Write information to one frame of output data field for either part, or both, as appropriate.
Vocabulary		OWT	write to output data field. CPU/O and transfer FU to FO, ready for next FU.	2CLOOP	two-part canon loop. UDRD2 until end of input data field is reached by PI (= P2, see DOT2).
Words written in machine code		U.CFS	update FI and transfer it to FD and FU.	2CANON	write output data field as two-part canon; from IMP. Execute as BOF2 0 POFU POFD 2CANON. (Either POFU or POFD may be used, the other being zero, e.g. 20 0 7 0 2CANON will transpose the M2 part up by seven semitones).
UUCF1	Update input console field FI (take pointer from scratchpad).	?AA	query AA. Check whether the end of the input data field has been reached, usually by P2.	Melisma	
ORCF	OR two console fields as specified by two stack parameters, leaving result on one of them (as specified by the second parameter).	KWIT	write "improvisation completed" to VDU, then QUIT.	UDP2M	update F2, P2 and OF2, without the transposition to M2.
CC4/3	compare FU with FO and read keying information to output data field (takes pointer from scratchpad).	ORGANUM	write output data field as parallel organum in n parts, from IMP. Execute as n POFU POFD ORGANUM (n = 2 or 3).	UDRD.M	update registers and durations for one frame of output data field as a single line from two input parts separated by BOF2.
CF>	Transfer console fields as specified by two stack parameters.	D1R	reverse bytes of T1 to put i.s.b. first.	MLOOP	melisma loop. UDRD.M until the end of input data field is reached by PI (= P2, see DOT2).
2/MOD	nine-bit divide by two (using Shift Right Logical).	D2R, D3R	complementary to D1R.	MELISMA	write output data field as variation on the theme, from IMP. Execute as BOF2 0 0 0 MELISMA.
2*M	nine-bit multiply by two (using Shift Left Arithmetic).	DUI	store initial values of duration variables T1, T2 and T3 with beat offsets (BOF2, BOF3) for the second and third parts; update pointers.	Three-part canon	
Words written in and compiled by Forth		STUP	start-up (takes four variable values from stack).	UDRD3	update registers and durations for three parts. Write information to one frame of output data field for any part, any two parts, or all three, as appropriate.
In some cases the explanation of a word is preceded by the pronunciation of its name.		DOD1	do duration 1. Write duration for first part to output data field and update TA.	3CLOOP	three-part canon loop. UDRD3 until end of input data field is reached by PI (= P2, see DOT2).
U.CFI	transfer PI to and from scratchpad for UUCF1.	DOD2, DOD3	complementary to DOD1.	3CANON	write output data field as three-part canon, from IMP. Execute as BOF2 BOF3 POFU POFD 3CANON. (Either POFU or POFD may be used, the other being zero).
I.CF	initiate console fields.	UDP1	update console fields and pointer associated with first part (F1, OF1 and P1).		
TU	transpose FU up one semitone (note – bit numbers increase but register numbers decrease with increase in pitch).	UDOF2	update OF2. Take FD as OF2 if POFU is less than POFD, otherwise take FU.		
TD	transpose FD down one semitone.	UDP2	update F2 and P2, then transpose the second part to M2 and by POFU or POFD, then update OF2.		
(see subheading Harmonization between M2 and M1 for screen 2 including AMS).		UDP3	update F3, then transpose the third part to Pedal, then update OF3 and P3.		
		TORCF	AMS, then transfer and OR two console fields (e.g. OF1 and OF2 for two-part canon) leaving result on FU.		
		TORCF3	similar to TORCF, but then adding the third part for three-part canon.		

continued on page 43

Current followers

Adaptable universal op-amp can be used in any of four basic configurations

The conventional operational amplifier such as the 741 type is a very high voltage-gain stage, the single-ended output voltage being proportional to the difference voltage between the two input terminals. This basic amplifier is easily configured into two gain stages, a trans-resistance stage and a voltage-gain stage, as shown in Fig. 1.

It is not so simple to configure the conventional operational amplifier to produce a current gain stage with well-defined current transfer ratio, low input impedance and high output impedance; nor a transconductance amplifier with well-defined transfer ratio, high input impedance and high output impedance.

There have been a number of proposals to develop a universal operational amplifier which has a differential input and a differential output. Such a circuit has the distinct advantage that it may be configured into any of the four basic amplifier stages without the complex multiple-pair resistor-matching requirements that typify many current and transconductance amplifier circuits using conventional operational amplifiers.

Current-follower characteristics

A current follower is a circuit with extremely low (ideally zero) input impedance and an extremely high (ideally infinite) output impedance. The net performance when used with a signal source is to produce a current drive to a load equal in value to the short circuit current obtainable from the input signal source, as shown schematically in Fig. 2 (a). In contrast, Fig. 2 (b) shows the better known voltage follower. Comparing the two shows that the current follower is the antithesis of the voltage follower.

Practically, it is simple to configure the standard operational amplifier as a voltage follower, it being merely a special case of the voltage amplifier shown in Fig. 1. However, realisation of a current follower is not so straightforward. Nordholt* has shown that a current follower may be constructed using a balanced current source and sink with two series-connected Zener diodes strapped across the supply pins — Figure 3 (a) shows a schematic of the circuit. The result is that the amplifier is effectively biased with floating d.c. supplies and the circuit behaves as a conventional operational amplifier, with the exception that it has a differential output as well as input. This basic building block can be configured into almost any type of

* Nordholt, E. H. Extending Op-Amp Capabilities by using a Current-Source Power Supply. *IEEE Trans. Circuits and Systems*, vol. CAS-29, no. 6, June 1982.

by F. J. Lidgley
Ph.D., B.Sc., M.I.E.E.

amplifier, as shown by Nordholt. In this article, attention is restricted to using this differential-input, differential-output operational amplifier as a current follower, as shown in Fig. 3 (b).

Practical current follower

Taking the circuit of Fig. 3 as a basis, I built the current follower shown in Fig. 4 for evaluation purposes. It is not suited for direct implementation as an integrated circuit, but it is feasible to produce a similar performance from a circuit which could be manufactured relatively easily as a single-chip device.

The section of the circuit associated with OA₁, Tr₁, D₁ and R₁ produces a constant-current source of about 20mA. Similarly the circuitry associated with OA₂, Tr₂, D₂ and R₂ produces a constant current sink of about -20mA. The potentiometer in the current source bias network provides trimming of the source to enable the output offset to be reduced to zero. The load current is limited by the maximum output available from the operational amplifier; for example, if OA₃ is a 741, then the limit is approximately ± 10mA.

Dr Lidgley is Principal Lecturer in electronics, Department of Engineering, Oxford Polytechnic

Analysis of the current follower

An incremental equivalent circuit of the current follower is shown in Fig. 5, the operational amplifier being modelled by the input impedance of R_i (typically 1MΩ), output impedance of R_o (typically 100Ω) and dependant generator A.V_i in the output circuit, where A is

$$A = \frac{A_0}{(1 + jf/f_p)}$$

A₀ is typically 10⁵ or so and f_p is the internal compensation pole, typically at 10Hz, giving the amplifier unconditional stability when used with any value of resistive feedback. The amplifier's bias network is assumed to be ideal, giving a full differential input/output performance.

From the diagram the input current i_{IN} is

$$i_{IN} = i_{OUT} + i_i = i_{OUT} + v_{IN}/R_i \quad (1)$$

Solving Kirchoff's voltage law gives the input voltage


$$v_{IN} = -A.v_{IN} + i_{OUT}(R_o + R_L) \quad (2)$$


Combining equations (1) and (2) to eliminate v_{IN}, the current transfer ratio is obtained,

$$i_{OUT}/i_{IN} = \frac{1}{1 + (R_o + R_L)/R_i(A + 1)} \quad (3)$$

Generally R_i(A + 1) >> (R_o + R_L) and so

$$i_{OUT}/i_{IN} \approx 1 \quad (4)$$

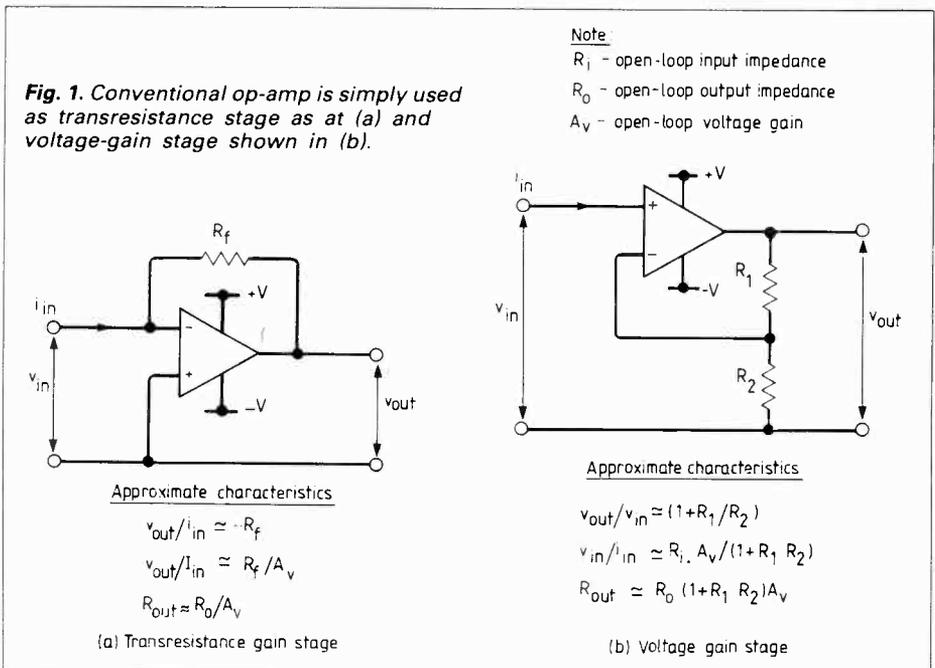

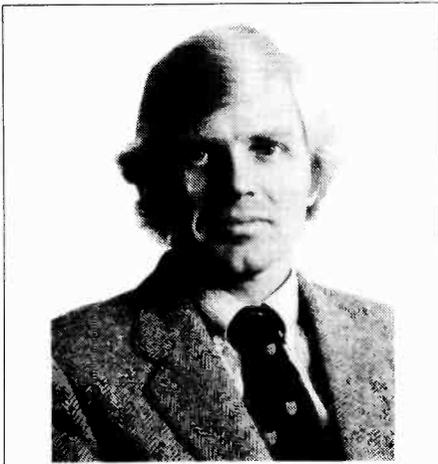


John Lidgley is Principal Lecturer in Electronics in the Department of Engineering at Oxford Polytechnic. He completed his Ph.D. in microwave electronics at Surrey University in 1973. After a period of four years teaching electronics at the University of Newcastle, Australia, he returned to England to take up his present post. His interests include design of microwave oscillators and the design and applications of operational amplifiers. He is also actively engaged in industrial electronics consultancy at the Polytechnic.


Using the binomial expansion, equation (3) gives

$$i_{OUT}/i_{IN} \approx (1 - E) \quad (4)$$

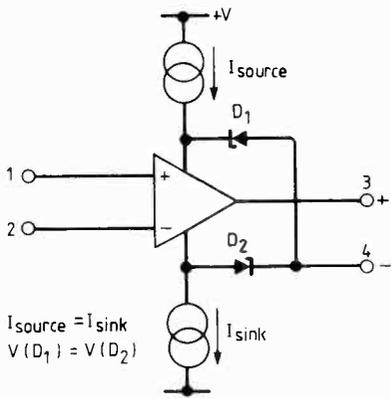where $E = (R_o + R_L)/A(A + 1)R_1$ is the error in the current follower from the




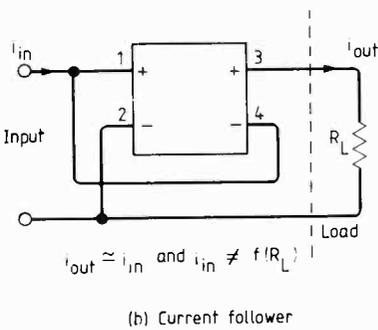(a) Conventional op-amp with floating supplies




(b) Current follower

Fig. 3. Op-amp using floating power lines and giving effective differential output. Current follower arrangement shown at (b).

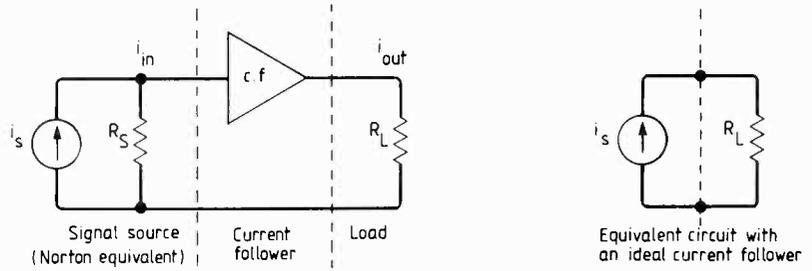

(a) Current follower stage

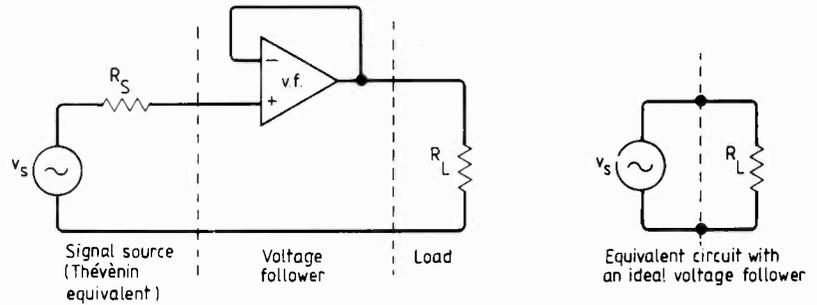

(b) Voltage follower stage

Fig. 2. Current follower at (a) produces current into R_L equal to current available into short circuit from i_s . Voltage follower at (b) ideally provides voltage across R_L equal to open-circuit voltage from source.

ideal. To assess the accuracy of the current follower E can be evaluated for particular values of the circuit components. For example, taking the typical values stated earlier for the operational amplifier gives the d.c. value of E as

$$E = 10^{-8} (1 + 0.01 R_L)$$

$$E = 1.01 \times 10^{-7} \text{ for } R_L = 10\text{k}\Omega$$

The accuracy of the circuit is clearly excellent at low frequencies; however, the

performance degrades at the higher frequencies where the product of $(A + 1)R_1$ reduces due to the high-frequency roll-off in the operational amplifier gain A .

Whilst equation (3) above is correct for the ratio of output current to input current the input current i_{IN} will not be equal to the Norton equivalent signal source current, i_s , unless the input conductance is infinite.

Referring to the circuit of Fig. 2 (a), the

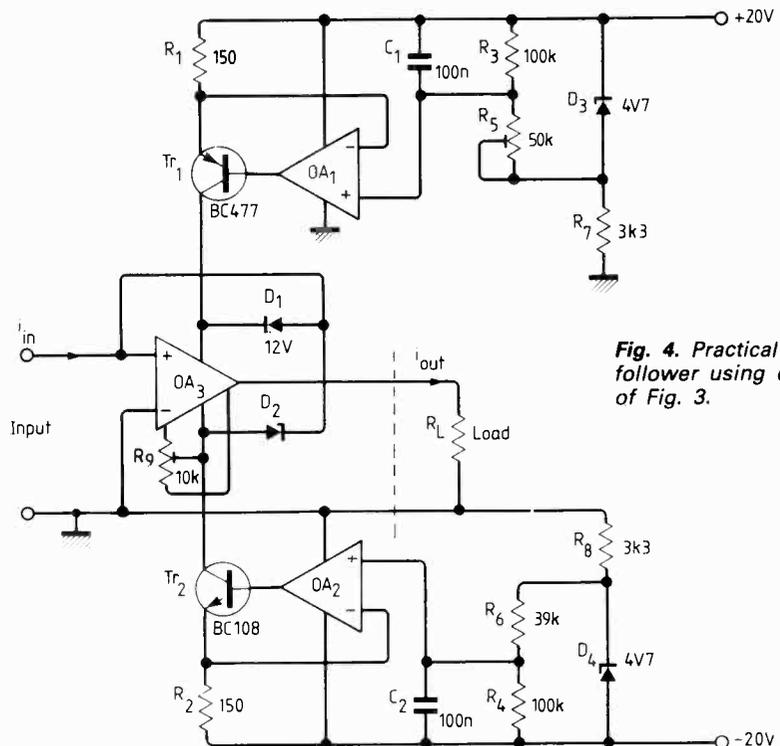


Fig. 4. Practical current follower using op-amps of Fig. 3.

Note: OA1, 2, 3 - 741; OA3 offset pot is trimmed to zero the output when the input is short-circuited and R_5 is used to zero the output when the input is open-circuited

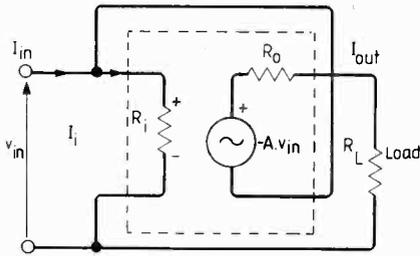


Fig. 5. Incremental model of current follower of Fig. 4.

significant parameter for assessment of the current follower is the ratio i_{OUT}/i_S . Now

$$i_{OUT}/i_S = (i_{OUT}/i_{IN}) \cdot (i_{IN}/i_S) \quad (5)$$

and clearly one also needs to evaluate the second term i_{IN}/i_S . From Fig. 2 (a)

$$i_{IN}/i_S = R_S/(R_S + Z_{IN})$$

where $Z_{IN} = v_{IN}/i_{IN}$.

From equations (1) and (3), the input impedance Z_{IN} is given by

$$1/Z_{IN} = 1/R_i + (A + 1)/R_o + R_L \quad (6)$$

$$\therefore Z_{IN} \sim (R_o + R_L)/(A + 1) \quad (7)$$

as the second term of the r.h.s. of equation (6) is dominant. Taking (4), (5) and (7) gives

$$i_{OUT}/i_S \sim R_S/R_S + (R_o + R_L)/(A + 1) \quad (8)$$

Equation (8) shows that if the operational amplifier gain A is high then the follower will behave almost ideally, i.e. $i_{OUT}/i_S = 1$. But, if the operational amplifier is a utility device with dominant-pole compensation, then by combining equations (3) and (8) the complete current transfer function is obtained

$$i_{OUT}/i_S = \frac{(1 + jf/f_z)^2}{(1 + K_1/(A_0 + 1))(1 + K_2/(A_0 + 1))(1 + jf/f_{p1})(1 + jf/f_{p2})} \quad (9)$$

where $f_z = f_p(A_0 + 1)$ is voltage gain-bandwidth product of the operational amplifier (GB), $K_1 = (R_o + R_L)/R_S$, $K_2 = (R_o + R_L)/R_i$,

$$f_{p1} = \frac{(A_0 + 1 + K_1)}{(1 + K_1)} \cdot f_p;$$

$$\text{and } f_{p2} = \frac{(A_0 + 1 + K_2)}{(1 + K_2)} \cdot f_p.$$

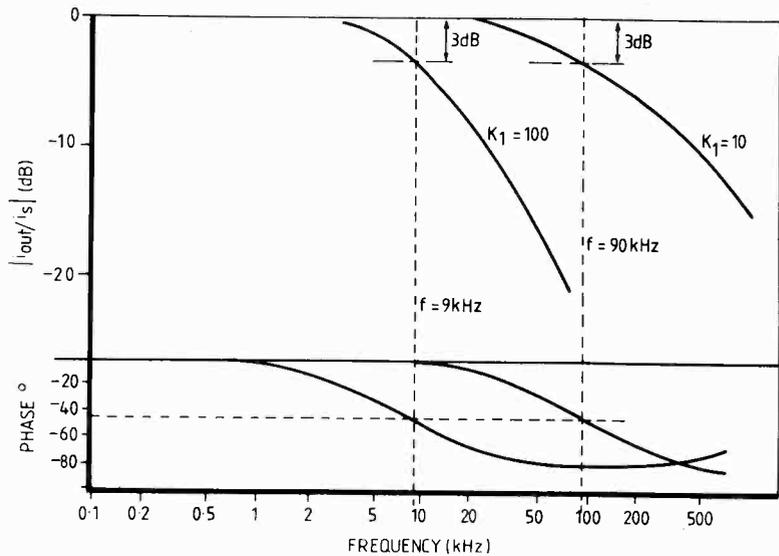


Fig. 6. Frequency response of current follower shown in Fig. 4.

It is likely that R_i , the input impedance of the operational amplifier, will be significantly higher than $(R_o + R_L)$ and so K_2 tends to zero and equation (9) reduces to

$$i_{OUT}/i_S \approx \frac{(1 + jf/GB)}{(1 + K_1/(A_0 + 1))(1 + jf/(GB/K_1))} \quad (10)$$

and for $K_1 \ll A_0$ this expression reduces still further to

$$i_{OUT}/i_S \approx 1/(1 + jf/GB/K_1) \quad (11)$$

giving a -3dB frequency of $f = GB/K_1$.

close agreement with the theoretical value predicted from equation (11).


Proposed general-purpose 'follower' amplifier

Using current followers and voltage followers as basic building blocks it is feasible to develop an extremely useful quad operational amplifier, the proposed circuit containing two voltage followers and two current followers. With this general-purpose integrated circuit it can be configured very easily into any of the four basic amplifier types.


Figure 7 shows the circuit diagrams for a current gain stage, a voltage gain stage, a transconductance and a transresistance stage based on the proposed follower i.c. As an example, examine the first shown, which is a current amplifier. The input into the first current follower provides a low input impedance and drives the input current through resistor R_1 , converting the input into a voltage drive. The second drive of the amplifier is a voltage follower which transfers the voltage $i_{IN} \cdot R_1$ to a low-impedance voltage source driving into R_2 . As the third stage is a current follower with

Figure 6 shows a plot of the current transfer function for the circuit of Fig. 4 using two different values of K_1 . The performance of the follower is good, with measured upper -3dB frequencies in


Fig. 7. An i.c. with two current and two voltage followers would enable any of these circuits to be easily obtained.

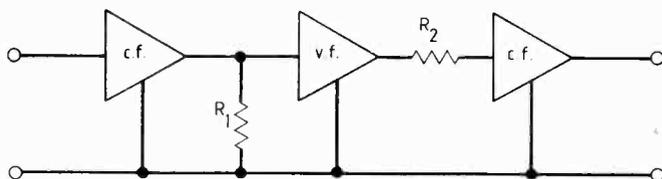


(a) Current amplifier $A_i = R_1/R_2$

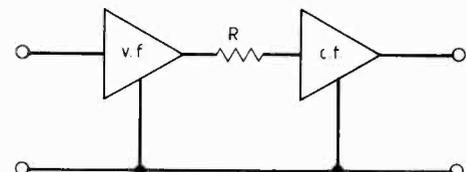

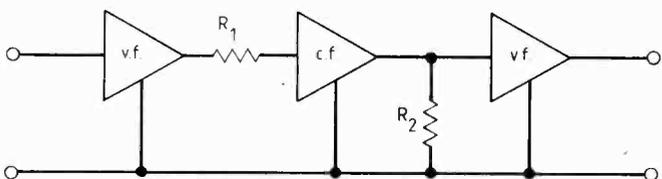(c) Transconductance amplifier $G_T = 1/R$



(b) Voltage amplifier $A_v = R_1/R_2$

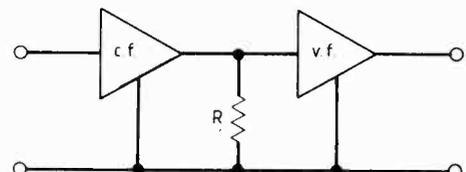

(d) Transresistance amplifier $R_T = R$

low input impedance, the input current drive to this third and final stage is $i_{IN} \cdot R_1/R_2$, which is equal to the output current feeding the load R_L with

$$i_{OUT} = R_1/R_2 \cdot i_{IN}$$

and clearly the current gain is

$$A_i = R_1/R_2$$

Using this same approach it is relatively easy to verify the remaining three basic amplifier circuits shown in Fig. 7.

This proposal for a general-purpose 'follower' operational amplifier is extremely

simple to configure into any type of analogue amplifier. Feedback is localized to each follower, there being no output to input feedback.

As a result, any phase lag from input through to output is insignificant in terms of controlling the stability of each of the amplifiers. The frequency response will depend somewhat on the values of voltage and current-defining resistors, but no instability is likely to be encountered if each of the followers is internally compensated, and a broad bandwidth is possible with careful choice of resistor values. It is interesting to note that none of the resis-

tors are used as feedback components but as voltage-to-current and current-to-voltage converters.

It is feasible for a single i.c. to be constructed with two voltage followers and two current followers on the chip, thus providing a general purpose quad operational amplifier. With such an i.c. any of the circuits of Fig. 7 can then be constructed, the only additional components required being a maximum of two fixed resistors.

Thanks to R. D. Coombes and C. Toumazou for the experimental evaluation of the follower. WW

Microcomputer organ interface

Glossary continued

Two-part accompaniment

UDP2P similar to UDP2, but the second part is transposed to Pedal.

UDBPP similar to UDBP but with one part in Pedal.

UDRD2P similar to UDRD2 but one part (Pedal) moves at half the speed of the other.

2PCLOOP two-part accompaniment loop. UDRD2P until end of input data field is reached.

Motet

DU2I store initial values of duration variables T1 and T2 for motet, after accompaniment has been written.

MOTET write output data field as "motet" in three parts, from IMP3. Firstly write the two-part accompaniment, from IMP2, then write Melisma from IMP, then combine the two with offset BOFMO, from IMP3. $IMP3 < IMP2$ so that the accompaniment might be overwritten.

Execute as BOF2 BOF3 POFU POFD BOFMO MOTET (BOF2 is for the accompaniment, BOF3 for the melisma).

Harmonization between M2 and M1 (see Fig. 1 and associated text on register allocation. CSCB and CSCA are not symmetrical because of the one-bit offset between corresponding notes in M1 and M2, e.g. HC3 is 1401 and RB2 is OEO1. In these names above (and below) essentially mean "assume the M2 part is above (or below) the M1 one". Hence the curious name for THDA, which transposes the M2 part down (temporarily) to see whether it was above the M1 part).

TDB transpose down below. Transpose the M2 part of FD down one semitone.

TRDHB transpose down harmonization below. TDB by POFHB semitones.

CS check semitones. Find which byte if any in the M1 part of OF1 is non-zero.

CSCB correct semitone clash below. Compare the active byte (if any) in the M1 part of OF1 with the corresponding one in the M2 part of OF2. TRDHB if the

M2 part was a semitone below the M1 one (i.e. if the bytes were equal).

TUA transpose up above. Transpose the M2 part of FU up one semitone.

THUA transpose harmonization up above. TUA OF2 twice. (See CSCA).

THDA transpose harmonization down above. TDB OF2 twice.

TRUHA transpose up harmonization above. TUA by POFHA semitones.

CSCA correct semitone clash above. Compare the active byte (if any) in the M1 part of OF1 with the corresponding one in the M2 part of OF2. TRUHA if the M2 part was a semitone above the M1 one (THDA makes such bytes equal, THUA restores the offset).

AMS augment minor seconds. CSCB then CSCA. (If POFHA = POFHB = 2, minor seconds between the M1 and M2 parts are augmented, i.e. turned into minor thirds).

IEEE488 interface

the signal generator to cease listening.

Line 150 commands the digital voltmeter to talk and line 160 obtains a voltage reading from the digital voltmeter as a string of ASCII characters. Line 170 commands the digital voltmeter to stop talking.

Line 180 converts the amplifier output voltage reading as an ASCII string to the amplifier's response in dB. Line 190 selects the disc filing system and line 200 prints the results to disc.

Line 210 reselects the IEEEFS for

further measurements; lines 230 and 240 cancels the reference to the digital voltmeter and signal generator; and lines 250 and 260 close the results file on the disc.

For assembler programmers, all the IEEE commands are available through a single operating system OSWORD call which makes use of a command code in the parameter block.

For users who wish to simulate a simple talker-listener device, i.e. one not possessing the control function, the option select link must be changed to the not-system-

controller position and the TMS9914A programmed directly. The excellent Texas Instruments TMS9914A General-Purpose Interface Bus (GPIB) Controller Data Manual contains all the information required to do this.

Every effort was made in the design of the interface and the writing of the User Guide to facilitate the use of IEEE488 instruments by the occasional user of the BBC Microcomputer and it is hoped that this article gives some idea of the potential of this powerful combination. WW

Literature received

An eight-page catalogue from Lascar Electronics describes the company's range of digital panel meters, which include l.e.d. and l.c.d. voltmeters with 3½ and 4½ digits and a choice of six- or eight-digit counter-timers. Lascar Electronics Ltd, Module House, Whiteparish, Salisbury. WW 401

Maplin Electronics' 1984 catalogue runs to over 500 pages. For the first time it includes construction kits and educational courses by Heathkit, whose products Map-

lin now distribute. The catalogue is available from branches of Maplin or W. H. Smith for £1.33, or by post for £1.65 from Maplin Electronic Supplies Ltd, PO Box 3, Rayleigh, Essex SS6 8LR. WW 402

The 1984 edition of *Hobby Herald*, BICC-Vero's catalogue of products for the hobbyist, lists several new items among which are some insulation-displacement connectors for use with ribbon cable and a range of British Telecom-style pluggable telephone connectors. *Hobby Herald* costs 50p from BICC-Vero Electronics Ltd, Indust-

rial Estate, Chandlers Ford, Hampshire SO5 3ZR. Tel. 02415-62829. WW 403

More than 2½ million components are held in stock by Comway who have recently issued the 11th edition of their catalogue. It not only lists the available components but also has some useful specification and dimensional details. Along with semiconductor devices and microprocessor development systems is a range of connectors, switches and other hardware, Comway Ltd, Market Street, Bracknell, Berks RG12 1QP. WW 404

LETTERS

BUS STANDARDS

I was pleased to see the article on the IEEE 696 (S1000) Standard in the December issue. I congratulate the author on an interesting and informative article. In passing, the author mentioned several other IEEE standards activities: 796, 896 and the Euro-STD bus; unfortunately, some of the information presented was out of date. I would like WW readers to be informed of the current status of these activities:

The Euro-STD bus evolved into the STE bus because the working group could not reconcile the signal specification of the STD bus with their goals of processor independence and longevity of the standard. The IEEE standards board approved the PAR (project authorization request) number P1000 to the working group in February, 1983. The P1000 specification now provides 20 address bits, 8 data bits, and a simple, but processor independent, asynchronous handshake. P1000 recommends single Eurocards and uses the IEC603-2 (DIN41612) connector. It is intended primarily for use in cost-sensitive applications which still require the modularity afforded by a bus. The P1000 draft is due to be voted out of the working group for public comment in January 1984. Information on the current status of the P1000 standard may be obtained from the European secretary: Timothy Elsmore, GMT Computer Systems, Newport House, 22 Hartfield Road, London SW19 3TD. I should point out that although the original Euro-STD bus is not now an IEEE effort, it is still the basis of several commercial products. GMT Computer Systems manufacture and market boards to the original Euro-STD bus specification.

The P796 (Intel's Multibus) specification (incorrectly called A796 in the article) was approved by the IEEE standards board along with the P696 specification in December 1982. Copies of both the 696 and 796 standards may be obtained from: IEEE Service Center, Attention CP Dept, 445 Hoes Lane, Piscataway, New Jersey 08854, USA.

The VME bus has been the subject of IEEE standardization efforts since January 1983. The IEEE standards board issued the PAR number P1014 for the 'versatile backplane bus' (VME) in September 1983. The P1014 working group are currently re-writing the VME specification in the IEEE standards format, and expect to complete their work in early 1984. Information and current status of the P1014 activity may be obtained from the Chairman: Wayne Fischer, 82 Shereen Place, Campbell, California 95008, USA.

The IEEE P896 work has progressed much further than is suggested in the article. Indeed, the work has now been completed and a proposed specification is available. The P896 working group voted to release their completed draft for public comment in September 1983. P896 is a very high performance backplane bus providing a 32-bit highway governed by a fully asynchronous and technology independent protocol. Although P896 has a decentralized arbitration scheme, multiple bus locking features, and an independent serial highway, making it ideal for fault-tolerant systems, it is primarily intended for high-performance general-purpose multiprocessor systems. P896 provides its complete signal-set on a single IEC603-2 (DIN41612) connector, and is intended for use on double and triple Eurocards up to 280mm deep. The UK IEE hosted a colloquium on the P896 specification in London on November

29 to provide UK industry with advance information on this potentially far-reaching standard.* Information on the P896 draft specification may be obtained from Andrew Wilson, Computing and Control Division, IEE, Savoy Place, London WC2R 0BL.

UK involvement with the IEEE bus activities is co-ordinated by the IEE Working Party on Backplane Buses at the IEE address given above. Other work on microprocessor standards is carried out in the BSI Committee ECL/OIS-1. I should like to point out to *Wireless World* readers that participation in (particularly the IEEE and IEE) standardization activities, is open to anyone who has the time and energy, as well as the technical knowledge, to contribute to these standards.

Paul L. Borrill
IEEE Microprocessor Standards Committee

* Reported in News January issue, page 45. Please read IEE for IEEE in line 10 of that item. — dep. ed.

BEHIND THE MICRO

From my experience when buying a micro a year ago, it seems that you make no mention of the biggest single difficulty confronting someone trying to choose a suitable machine. I do not expect you to overcome this difficulty, but it would have been wise if you had printed the very prominent warning "Many manufacturers' specifications are barely true and are carefully designed to mislead".

I wanted a machine for mathematical work, and was looking for something which you would describe as being in the basic price range of £2,000 to £3,000, i.e. a complete price of perhaps £10,000. I will give you two examples of misleading specifications. One manufacturer claimed to supply Fortran, but it did not emerge until late in the discussions that this was a very cut down subset of Fortran, lacking some essentials such as double precision variables. Another manufacturer said that Fortran was available on his micro, but it emerged that it was necessary to compile the source code on a bigger machine of his, and then transfer the object code to the micro. One manufacturer never mentioned this snag in any of his literature; the other one only mentioned it in very small print on a part of the sheet where you would not expect to find such information. A specialist dealer who stocked one of the machines was completely unable to understand (and still less to answer) technical questions in the area of languages.

In short, to get reliable information on which to base a rational choice is exceedingly difficult. J. G. D. Pratt
West Horsley
Leatherhead

AURAL COGNITION

I owe many thanks to D. Wattson (Letters, September 1983) for the extraordinary precision with which he has stated the problem of aural interfacing between a cognitive biological unit (the brain and/or whatever else) and a multinoise environment.

It gave me the idea that if the buffering stated therein cannot be implemented with hardware, nature most probably resorts to software. The idea may appear original, but it is not mine. It appeared initially in the WW editorial of January 1982, viz. that nature interfaces with

humans through programming. In the case of aural cognition, I think, nature makes use of variable microprogramming techniques, that obviously, like instruments, we are destined to utilize but are not yet able to understand.

Some experimental hints along these lines. A person (or animal) may be microprogrammed to fall asleep in a sound-polluted environment. Subsequent silence will set the flags of software interrupt, overflow will occur, forcing awakening. A second example: People exist that hear voices. Maybe flow of the microprogramming instructions energizes the interface (the ear) by an output, which bounces and returns to the unit, masqueraded as input. In this respect the program generates virtual inputs that do not manifest elsewhere in the world.

I began setting up experiments along similar lines. And I have had another idea: Declare the computer a severe mentally-handicapped configuration. Then program (microprogram will be the final objective) it toward cognitive research; e.g. the computer having memorized via transducers the sounds "a" and "b" to search in real time a stream of words and let all phonemes other than "ab" pass through unmemorized, but to operate software interrupt when there is "ab" or seems to be. It will not be easy.

G. Xenoulis
Toronto
Ontario

THE PERSUADERS

Your editorial in the October issue whilst putting forward a valid point of view was nevertheless somewhat confused.

Truth is absolute and can be neither accentuated nor minimized. Morality is a function of truth and therefore has no degree nor shades of grey, less than moral is immoral and morality is what we should be concerned about.

The society in which we live is immoral, as are all societies because they deny all human beings that most fundamental of human rights, the truth.

Education must be defined as teaching the truth and the methods by which truth can be comprehended.

Therefore it is evident that we do not educate our young, rather we indoctrinate them with the dogmas of our current society, paying little regard as to the relevance of our teachings to the truth.

The minds of children are naturally dedicated to the process of determining the truth but the continual brainwashing together with the instilling of irrational fear stimulates a child's emotions and inhibits logical thinking.

This is no more apparent than when following puberty the teenager exhibits a somewhat confused pattern of behaviour.

To achieve a moral society we must assert our dedication to the truth, to logic and discipline our emotions to the role of slave, not master.

By believing in illogical dogmas whether religious, political or whatever, we abdicate our responsibilities to the human race.

Norman Webster
Leyland
Lancashire

FOWBERRY ENERGY SAVER

It is good to see engineers turning their skills to

the saving of natural resources, so I was pleased to read of Mr MacHarg's device which is saving energy in Fowberry Tower*. I too have been devoting some time to this subject, so I hope he will not object to me offering some comments.

I do not feel that the question of thermal lag and temperature overshoot is the fundamental one. After all the system, overshoots and all, is set up to give the desired average temperature, usually about 80°C, and the water temperature cycles by a few degrees about this. The temperature of the gas side of the heat-exchanger may briefly overshoot further, but the associated stored energy is small.

It seems to me that the main achievement of the Fowberry energy saver, as illustrated in Fig. 1, is to reduce the boiler temperature as demand falls. This must be a valuable objective. The 80°C set-point is appropriate for full output, either in extreme weather or when a rapid increase in temperature is required. Under normal steady conditions in the most common mild, damp weather, the heat demand is much less than this. To avoid guarantee claims, heating installers err on the side of over-capacity, and as fuel costs increase house occupiers improve their heat conservation. The result is a lot of powerful boilers running at a fraction of their full output. On a day when the outside temperature was 7°C my gas boiler was running with a duty cycle of 20%. Its own constant loss at 80°C is 7.5%, so over 37.5% of the input was going straight up the flue!

The efficiency, especially at part load, will be improved if the boiler temperature is reduced. A simple-minded calculation on my above example, assuming flue losses proportional to the temperature difference between the boiler and the combustion air, suggests that the boiler could be run at 32°C if the house is at 20°C, giving 20% of the fixed losses. Even if this is over-optimistic, and if boiler temperature has to be kept up to avoid corrosive condensation, the potential for saving is considerable.

I too considered using thermostat off-time as a measure of heat demand. The problem is that it is an awkward function of heat demand so an open-loop strategy which does not use a fairly accurate model will give far from optimal results. Hence in Fig. 1 only a 10°C reduction in boiler temperature has been achieved at most. What is needed is a variable which will respond to changes in boiler temperature, so that a closed-loop strategy may be employed.

The philosophy I have arrived at is to compare radiator flow and return temperatures. Assuming thermostatic valves on all radiators, the return temperature is 10-20°C below flow temperature with valves fully open, falling quite sharply towards room temperature as they commence to control. The economiser cuts off the boiler if this differential exceeds a limit of around 30°C and brings it back on when the differential falls to about 5°C, the pump staying on constantly. The result is a limit-cycling controller which adapts boiler temperature to hold the differential at an average of 17.5°C with the highest-set thermostat wide open. There is an override when hot-water heating is demanded, since this is best served by a short interval at 80°C.

I have tested this scheme briefly using my

* Diode D₅ should be reversed in the circuit on page 27 (December). The 78L12 i.c. regulates a 12-volt rail and not 5V as shown. Mr MacHarg tells us that capacitors C₃, C₆ and C₇ must be low-leakage types.

ZX81 as the controller, and it certainly reduces average boiler temperature on a mild day to around 40-50°C. Heating time from cold and response to sudden valve-opening are unimpaired, the boiler temperature going straight to 80°C until the disturbance is corrected.


Because the ZX81 obliterates Radio 3 and crashes a little too frequently I am now building an analogue version (two i.c.s) for a long-term trial, to see whether the potential 50% loss reduction is achieved.

The possible improved performance over the Fowberry device is achieved at the cost of some convenience, since temperature sensors have to be fitted in the appropriate part of the system. It is only applicable where radiator thermostats are fitted. Systems with a single room thermostat inherently adapt the average boiler temperature to demand, but the lack of temperature control in the other rooms causes overheating, discomfort, or both.

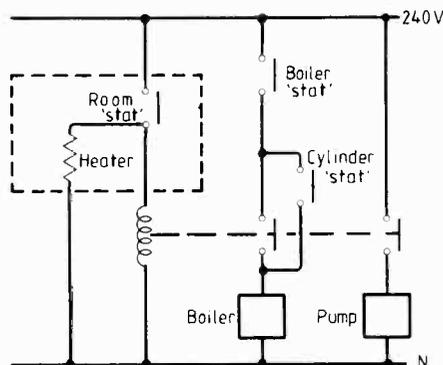C. Hargis
Bristol

The pulsing boiler controller described in Mr MacHarg's article (December issue) possesses some disadvantages. If one increases the thermostat setting during a period of pulses of reducing width it must be irritating to have to wait whilst the controller decides that the boiler should run for longer bursts. The "short cycling" that a pulsing controller of this type produces is not desirable - supply dips - boiler condensation - wear and tear on the boiler starting gear - thermal expansion stresses etc.

An alternative that I have had in use for some



years uses one relay and is arranged to fire the boiler if the boiler thermostat and the room thermostat or the cylinder thermostat call for heat. Judicious selection of a boiler start-up time delay which "grades" with the room thermostat heater time lag will ensure that "short cycling" of the boiler will not occur.

In normal operation the boiler thermostat will only switch off when no room heating is required ie in warm weather. Boiler control is usually carried out by the room thermostat relay.

J. R. Ball
Timperley
Cheshire

The author replies

Everything introduced by man into his domain provides disadvantages (not the least the sheer expense of convenience), and the problem is always to reduce untoward priorities which are in effect resonances: integration is made easier by increasing frequency which tends to avert

catastrophe by reducing big swings into little roundabouts. Firstly, I ask Mr Ball, how often he should wish to adjust his thermostat if it is carrying out adequately the function for which it was designed? If it possesses an off-position, turning it off for a few seconds would simulate high demand with immediate response from the energy saver: judging from his letter, his system is in dire need of some "optimization" because if his room thermostat only controls his boiler directly he must be wasting a lot of energy.

It is unclear what Mr Ball means by supply dips, but if he is referring to the supply of heat then the opposite is the case because by supplying a little and often greater constancy is achieved whereas with his own system which introduces a boiler delay temperature troughs are inevitable: the human body dislikes these and quite gladly turns up the temperature to overcome them, neglecting the slight but constant over-temperature which is thus provided wastefully between them if not actually enjoying it. Boiler condensation is a permanent potential hazard from the products of combustion, the degree to which the hazard is realised being largely determined by the time allowed for the boiler to cool down: timer-controllers and time-switches, including the human variety, are far greater culprits in this respect. He has a point over wear and tear on the starter gear, but even the cost of repeated replacement should be well offset by the saving of energy in all but the smallest installations. Thermal expansion stresses obviously would be increased in frequency but it is difficult to see how they would not be reduced in severity at the same time, both effects being desirable and good engineering.

A much more important point, brought to my notice by a well-known firm of burner manufacturers, is that it might be undesirable to use the energy saver with larger burners for which a pre-firing purge is provided: this blows clean and probably cold air through the boiler for periods of from 10 to 30 seconds before each ignition and obviously cools the boiler fractionally, and greater frequency of purging increasing the energy wastage up the flue. It is suggested that the energy saver may make the heart of an excellent and inexpensive "optimizer" when used with efficient thermostats, more particularly to control a central heating pump or other distribution means when a boiler serves a dual purpose including the heating of domestic hot water for which purpose it must run at a constant temperature. Those wishing to use one in this mode during the winter may care to devise a switching means so that its attentions may be channelled in the appropriate direction for the season, or, as he with the vested interest is bound to suggest with tongue in cheek, why not improve the operation of all thermostats by applying an energy saver to each and every item which is thermostatically controlled?

Following exhortations from the said burner manufacturers, further development has been carried out with the specific aim of producing improved "optimizer" characteristics which are an extension of the original thinking, the accent being upon greater versatility and thus only indirectly upon greater general energy saving. The possibility of supplying thick-film microcircuits is being investigated, obviating much assembly and testing time for those who may wish to set up in business assembling and selling the device at their own rate, but all this takes time and testing.

LETTERS

As the designers and manufacturers of a very successful energy saving product for gas boilers we were compelled to write to you after reading the design for the Fowberry Energy Saver.

Our energy-saving product is called the Gas-aver which has a patent application pending on the design. The unit principally inserts a fixed delay into the boiler off-period of about four minutes and has proved to give reductions of between 20 and 30% gas consumption in average domestic situations. We spent a lot of time experimenting with variable delays and quite complex self-regulating versions of our product but in the end our simple and cheap design (£40) has proved to be entirely adequate. The benefits of the more complex schemes were very small when the increased cost of the product was considered. The Fowberry design is complex and therefore more likely to fail in service, a factor which is very important when dealing with low cost consumer goods.

Mr MacHarg quite rightly points out that boiler-cycling, or 'hunting' as it is often called, wastes fuel but a number of his points are not accurate and the solution proposed, we feel, is probably only relevant to his own system which has the consideration of secondary heat input, something few of us have, let alone 80 tons of timber!

The initial argument concerns the thermal inertia of boilers. A lot of modern boilers use very low water content heat exchangers which have very little thermal mass and extremely good rates of exchange. These boilers suffer from the fact that there is little lag in heating the water back to the desired temperature setting and in fact tend to cycle more than boilers with cast exchangers which have greater thermal mass, and therefore lag.

The 'holiday cottage' effect only occurs, in our experience, when the boiler is undersized for the heating installation. In practice we find that boilers are often oversized which as any heating engineer will tell you is by far the best way. This oversizing allows for additional radiators and also compensates for crude heating requirement calculations. Both our own measurements and users reports show that our design has never caused a noticeable change in room temperature or comfort levels.

One of the losses caused by cycling is the gas wasted during ignition. Since the boiler doesn't light immediately some gas goes straight up the chimney followed by the familiar 'whoosh' sound. The Fowberry design actually causes the boiler to pulse during the On period and this must waste some considerable amounts of gas in itself! The pulsing action will also confuse some boilers such as the Potterton Netaheat, which has its own relay-based timer arrangement for the ignition sequence, a process which takes approximately 45 seconds.

The Fowberry design also has some basic omissions. The first omission is a bypass switch which is necessary for boiler maintenance and also in case of unit failure. The second omission is the facility to work with 24V control systems. Glow-Worm boilers, which have been nearly 50% of our installations, all use 24V systems, and a number of new designs are using 24V with integral transformers within the boiler.

Should Mr MacHarg feel that we have been unjust in our comments then we add that we will gladly challenge his design in a domestic situation under controlled conditions.

David V. Goadby
Pixel-Plus Ltd
Nailstone
Warwickshire

I was alarmed to see the suggestion that sheets


of polythene should be nailed over ceiling joints and insulation. While this may cause no problems in a large and well ventilated house, there is a very real danger of condensation occurring within the loft insulation of a small, well sealed modern house. The problem arises because the combination of a near airtight structure and a high occupancy (in terms of persons per cubic metre) frequently leads to high temperatures and high levels of water vapour in the house. This water vapour will, to a greater or lesser extent depending on the particular construction, penetrate through the ceiling and into the insulation. While the base of the insulation will be close to the internal temperature of the house, the top will be close to the much lower loft air temperature, and condensation of the percolating water vapour in the upper, colder sections of the insulation is very probable. Sporadic, short lived outbreaks of condensation can usually be tolerated if there is an airflow over the insulation allowing fairly rapid drying out, but if Mr MacHarg's suggestion were implemented, ventilation would be eliminated and the condensed water would remain for long periods and help to promote an outbreak of dry rot.

The heat saving adduced by Mr MacHarg for his polythene sheets is truly minimal if adequate insulation is installed: the penalties could be very severe. The advice to readers is quite unequivocal - don't do it.

Nicholas Pillans
Thames Polytechnic School of Architecture
Dartford
Kent

555 MARK/SPACE CONTROL

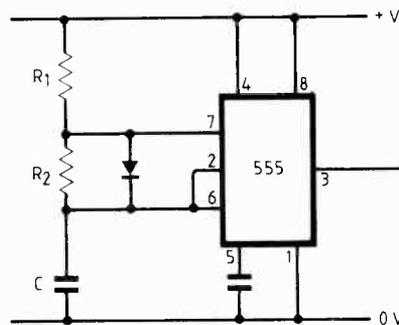The "555 mark/space control circuit" of Filanovsky and Piskarev (Circuit Ideas, September, p.68) can be simplified to:



C charges through R_1 and the diode, and discharges through R_2 . The diode gives a constant offset during the charge time of $\approx 0.6V$, effectively reducing $V+$ by this amount and so slightly increasing the charge time (by a predictable amount). Discharge time is unaffected.

Replacing R_1 and R_2 with variable resistors will produce an independent control of on and off times.

John Bonell
Leicester Forest East

CURRENT DUMPING REVIEW

About the September and October articles:

1. The distorting dumper V_{be} is there modelled by a voltage generator. Then the circuit becomes linear, allowing the effect on output of

this generator to be studied by itself. As mentioned, current despatched by it through Z_1 of Fig. 11 (all references are to the October article) meets an unpredictable emitter input impedance at Tr_2 . This is due to the presence of R_{12} as seen through the emitter, and it results in some loss of current through the 180Ω shunt path. Thus Tr_2 current gain enters the balance condition through the new factor λ , to yield

$$\lambda \cdot \frac{Z_4}{Z_1} = \frac{Z_3}{Z_2} + \frac{1}{gZ_p} \left[1 - k + \frac{Z_3}{Z_0} \right] \quad (9)$$

The meaning of the symbols is explained. The third term is called the gain term, because it depends on the parameter g of the driver amplifier. Mr Baxandall (Letters, December issue) supports the view that this term is much too small to figure, given the tolerance errors likely to be present in the other terms.

He also insists on ignoring λ , and proposes to stick to $Z_4/Z_1 = Z_3/Z_2$. Then, with 5% components, each side of his equation may depart 10% from its designed value due to tolerance errors. This unbalance is measured by defining a quantity e such that when his left hand side is multiplied by $(1-e)$ it again becomes equal to the right hand side. His e may rise in size to 0.2 or so. The reasoning would hold for (9) if λ was absent.

But λ is present, and nothing has been found against it. As explained, it may descend to 0.65 if Tr_2 has its minimum gain. Baxandall has set $Z_4/Z_1 = Z_3/Z_2$, and if the 5% errors possible in these components conspire with this value of λ then the left hand side of (9) above falls to 0.53 of its right hand side. (Now $e = -1$.) Nearly 100% increase in the value of Z_4 is required to rectify matters! It is R_{12} which is causing the new factor λ and its uncontrollable variations. It must go.

Nonsense, replies Baxandall. The design is splendidly uncritical, and takes such things in its stride. But surely we are trying to find the correct value for Z_4 ? Is a 100% error of no interest? Actually the article already mentions apparatus to evaluate this suggestion. As just shown, ignoring λ instead of disposing of it has pushed up the maximum value of e by a factor of five. Equation 13 shows that crossover distortion promptly multiplies by five. Uncritical? Distortion follows e in direct proportion. It has been overlooked that an amplifier is a slave to its feedback loop, and any signal delivered to its input thereby is faithfully reproduced at the output. Accurate balance of (9) is essential, and R_{12} must be removed to kill the uncontrollable λ .

2. From the first patents onwards current dumping has been explained as a method for nulling the distortion caused by the variable dumper V_{be} . As this varies during the signal cycle it produces no effect at the output terminal. The easiest picture is perhaps the bridge model of Fig. 8, where the essence of the technique is revealed as setting the bridge balance equation off balance by a small but precise amount: the gain term in (9) above. Mr Baxandall supports the view that this term is too small to figure. Worse, there is a reason of principle why it must be ignored. It is real and constant, while the other two terms of (9) are imaginary and proportional to frequency. The gain term must be neglected, and the equation balanced without it. This throws out any current dumping, as the term has always been understood, and establishes the deafening thesis that the Quad 405 current dumping amplifier (as it is named) is not using the current dumping techniques.

CONNECTION PATTERN TESTER

FAST EPROM PROGRAMMER

£395
+ VAT



DATAMAN I.C.T.

£1
PER
POINT
approx.

FOR CABLES LOOMS, BARE PCBs, ETC.

(Picture shows 1,144 Point tester, measuring 10.5 x 11.75 x 1.5 inches) If an array has N connection nodes, then (N-1) + (N-2) + (N-3) ... + 1 tests are required to discover its connection pattern. An old-fashioned method would be to use a buzzer, with a probe in each hand to complete the circuit, and check each node with the remainder. The formula simplifies to N(N-1)/2 which means that 653,796 tests are required to check a PCB with 1,144 component pads. DATAMAN's ICT performs in the same way — but finishes the task in seconds. The results can be compared with a previously learned pattern or formed into a standard ASCII file (a list of what-is-connected-with-what) and transmitted to a printer, terminal or computer in serial (RS232) or parallel (CENTRONICS) format. ICT uses CUSTOM LSI designed by DATAMAN. A tester of the size and format you need can be BUILT-TO-ORDER. DATAMAN can also provide a COMPLETE SOLUTION with fixtures, beds-of-nails, N.C. drilling from your artworks etc.

BUS EXERCISER/DIAGNOSTIC AID




£295
+ VAT

Plugs into microprocessor socket, reads and writes to system ROM, RAM and I/O. Prints memory contents in HEX, ASCII or ASSEMBLER MNEMONICS. Prints MEMORY MAP of addressing space. Performs CHECKSUMS. TESTS RAM, prints addresses and bits which default. Tests data lines for SHORTS to rails, other data or address lines. Tells engineer of address/data faults impossible to find with other tools. Easy to program, retains sequences for testing up to fifteen different products in permanent memory. Microdoctor is supplied in Z80, 6500, 6800 and 8085 format with appropriate disassembler (say which you want).

MICRODOCTOR £295.00
Conversion card & ROM (Changes configuration and disassembler e.g. Z80 to 6500 say which) £35.00
Clip-over PROBE (only needed if uP is soldered-in) £35.00
10 Rolls Thermal Paper £9.00

FAST EPROM PROGRAMMER

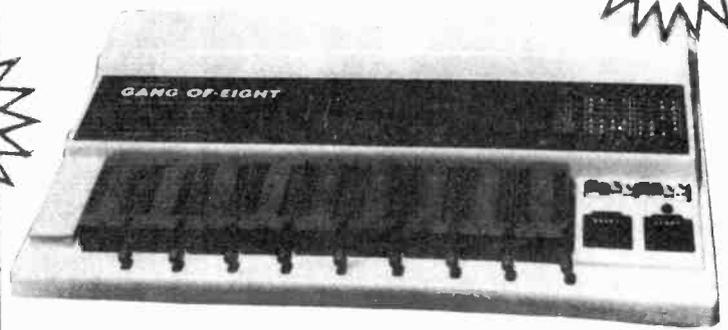

NINE TEXTTOOL ZIPDIP SOCKETS
LCD ALPHA DISPLAY
PROGRAMS ALL SINGLE RAIL EPROMS TO 27256
80% CUT IN PROGRAMMING TIME USING MANUFACTURERS' SUGGESTED ALGORITHMS (e.g. 2764 takes 1.25 mins not 7 mins typical)
SWITCH-SELECT OF EPROM TYPE (NO MODULES)


Z80 TEACHING AID

£99
+ VAT

MENTA GIVES REAL INSIGHT

TV DISPLAY of program, register and stack. Outstanding editing, debugging, single-step, set breakpoint etc. Very useful on-line ASSEMBLER — also DISASSEMBLER to serial output. Cassette interface. 24 I/O ports. Good for ROBOTICS. Designed for British schools-council to teach micro-control — appears in GCE syllabus. MENTA complete with power-supply, leads, manual etc. £99.00
Module for Course in Microprocessor control: Teachers' Guide £2.50
Pupil Reader £3.00
Universal I/O Module £21.00
Analogue to Digital Module £18.00
Digital to Analogue Module £14.00
D.C. Motor & control Module £12.00
Switched Input Module Analogue/Digital £10.00
Complete set of all above including MENTA £160.00

EPROM PROGRAMMER/EMULATOR

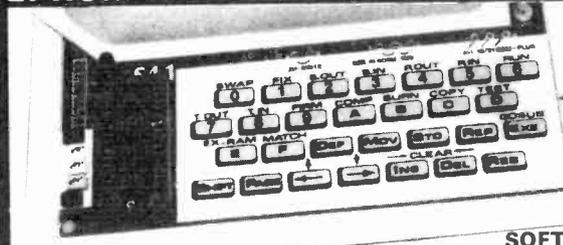

£169
+ VAT

SOFTY programs
2716, 2732 and 2532 EPROMS
Will copy any EPROM to any other — same type or different. Uses TV for display of HEX MEMORY MAP with many code inserting, deleting, shifting and editing features. Has standard serial and parallel I/O routines for communication with computers and printers — and cassette interface. Also popular as in-circuit ROM emulator for product development.

2764/128 ADAPTOR for SOFTY
With 28 pin Zero-Force Textool socket.
Rotary switch selects bank to be programmed £25.00

EPSON thandar NEC H/H TIGER

WE HAVE COMPUTERS, LOGIC ANALYSERS, PRINTERS, SOFTWARE IN STOCK INCLUDING QX10, HX20, TA2080 £ call us for a good deal.

THANDAR TA2080 — DATAMAN ADDS RS232 OUTPUT AND DISASSEMBLERS

12K of retrofit ROM and interface board allows printing complete D or R store in STATE or TIMING diagrams — also DISASSEMBLES in Z80, 6502 or 6800 MNEMONICS on-screen or to printer. You fit or we fit — no fitting charge but you pay carriage. £295

OLIVETTI TYPEWRITER INTERFACES

For ET121 and ET221 machines which permit the typewriter to be used as a DAISY WHEEL PRINTER for computers implementing the RS232, IEEE 488 (PET) or CENTRONICS PARALLEL busses, almost all computers in fact. Great for word processing and letter-writing! Same price, fitting free if requested (you pay carriage on typewriter if we fit) £195

ULTRA-VIOLET EPROM ERASERS from

..... £39

DATAMAN PRODUCTS ARE USED IN INDUSTRY AND EDUCATION ALL OVER THE WORLD. GET FREE LIT PACK PHONE NOW OR ANYTIME (24 HR answering)

NO RIP-OFF GUARANTEE
MONEY BACK WITHOUT QUESTION IF PRODUCT RETURNED WITHIN 14 DAYS (less p & p)
ALL GOODS HAVE 12 MONTHS WARRANTY, PARTS AND LABOUR

**LOMBARD HOUSE,
CORNWALL ROAD,
DORCHESTER, DORSET DT1 1RX.
Telephone: Dorchester (0305) 68066
Telex 418442 DATAMAN**

Prepaid orders normally shipped by return
Prices include first-class recorded post in UK
Securicor, Red Star, etc. at extra cost
VAT should be added at current rates

Carriage Free on Orders in excess of £50.00
Add £2.50 if less.

Some may wish at this stage to change the established meaning of current dumping, so the same thesis is restated without using these words, in the form it had in the article: The bridge network in the Quad 405 has no power to cause nulling of the distorting dumper V_{be} . There is no escape from this: balancing (9) above without the third term cancels the coefficient of V in the feedback voltage C found in constraint (4) in Fig. 12. Thus no fraction of dumper V_{be} is fed back to the driver, contrary to what is required in Fig. 8.

As an example it was shown that once the gain term was abandoned, the amplifier could easily be converted into a traditional type of identical performance. Mr Baxandall observes that this is not a practical proposal, as the alternative is not stable at r.f. The error is admitted. But it only affects the example. The deafening thesis is unaffected, and the grounds for it untouched. Indeed, collecting and strengthening some of Mr Baxandall's remarks, his comments fuse with that thesis to yield the following key paragraph.

Admit that the Quad 405 is quite incapable of using the current dumping technique. Its feedback circuits have no power to null the dumper distortion, even if all components have zero tolerance error. Instead, its operation is to be explained in the following quite different manner. Firstly, drop the usual bias arrangements on the output transistors, thus disposing of adjustments and thermal problems. Then use a powerful driver amplifier together with massive negative feedback to remove the distortion so generated. But note that every powerful amplifier has a capacitor within it to ensure Nyquist stability. Observe that C in Fig. 11 is just that capacitor. Indeed if the driver triple is thought of as a single transistor then C is in just the classical position. Admit that C will cause a drop in the gain of the driver when it is handling the h.f. components introduced by the quasi-rectangular V_{be} , thus allowing measurable crossover distortion to reappear. So add L to modify the feedback at h.f. provided by the capacitor C . Remove R_{12} and ignore tolerance errors. Then use bridge technique ($Z_4/Z_1 = Z_3/Z_2$) to cancel the V_{be} let through by C . However, this V goes on to distort the output volts E in the usual way. It is left to the usual negative feedback from E to reduce this (constraint 4 now shows feedback is given by $hC = pE$ nearly.) No V is fed back. And certainly not the appropriate small fraction of it required to arrange cancellation of V in E . (This is current dumping.)

If sound, this key paragraph would require adjustments all round. Except for the stability errors admitted here, the two articles stand. Previous explanation of this amplifier is regarded as erroneous. L does nothing directly to cancel the effect of V on output. What it does is to cancel the crippling effect C would otherwise have on driver gain when it is handling the higher a.f. components of V . This restores the usual negative feedback at those frequencies. The inventive step is the addition of L . And UK patent 2278/74 with US patent 3,970,953 must be examined to discover how much is still relevant to this remarkable amplifier. But focus on the circuit itself, and introduce tolerance errors. With R_{12} removed e can rise in size to 0.2 only, and the correction provided by L to cancel the V let through by C is between 4/5 and 6/5 of that required. Distortion is indeed divided by five or more. (Two or more with R_{12} included as at present.) This good effect is clearly not enough to outweigh dropping the usual bias arrange-

ments, and the amplifier must be expected to have higher crossover distortion than with bias but no L . These are worst-case figures and cannot simply be tested on a single specimen.

3. After theory, practice. Baxandall now observes that this discussion has lost meaning, because we have fallen below the distortion levels caused anyway by wiring pickup and the like. Figures would be needed in support. And if provided they furnish a point against the superior claims of this amplifier. Are the figures in line 1 of Table 1 that good compared to other amplifiers? (As Mr Baxandall observes, the arrangements discussed in lines 2 and 3 are unstable and thus must be withdrawn from the discussion.)

M. McLoughlin
Haberdashers' Aske's School
Elstree

Michael McLoughlin's analysis of current dumping contains some interesting observations, but clashes strongly with our earlier analysis (June, July 1978) and a later more complete paper of ours in the Journal of the Audio Engineering Society*. We shall address three relevant points in the debate.

Mr McLoughlin argues (part 1, page 41) that a feedforward explanation does not exclude other explanations, and suggests that Peter Baxandall's letter does not support feedforward. We disagree strongly. In negative feedback two or more signal paths to the output are not necessary. It may appear that there is only one, but that is because current dumping has intertwined the feedforward and feedback paths. It does not really matter how one "derives" current dumping, a feedback explanation alone is insufficient. We struggled many hours over these concepts, and are quite sure that no feedback taken *simply* from the load can achieve what current dumping does. Thus we are forced to include the concept of feedforward in the description of any circuit that is capable of complete cancellation of distortion in principle, although a *simple* feedforward scheme may not be evident in a particular realization of the concept.

A second point concerns the practicability of current dumping, using components of standard tolerance so that the bridge is not quite balanced. Table 1 of part 2 is quite misleading. It implies that a resistive bridge is better than a reactive one, and that a "traditional amplifier" is better than both. We wish Mr McLoughlin had tried out each of these options experimentally, for unless the theory is done fairly the comparison is not meaningful. Examination of our AES paper shows some comparisons, using a model experimental circuit, which contradict Table 1. When the bridge is unbalanced, there are error pulses, but they are very brief (microseconds) and do not give rise to a large harmonic distortion. On the other hand an unbalanced resistive bridge (ignoring for the moment the infinite implied gain-bandwidth of the amplifier A) results in roughly a square-wave error with substantial harmonic distortion. In a traditional amplifier the necessary finite gain-bandwidth (for stability and other reasons) generally gives greater error pulses than current dumping.

To make the process clearer, consider a current dumping amplifier that has a reasonably

balanced bridge. The distortion error pulses will be small but not negligible. How shall we compare it to normal feedback? Can we short Z_4 , the inductor? This increases the distortion greatly, by about the inverse of the relative bridge balance accuracy. In addition, the circuit stability usually suffers, because the inductor tends to feed back a stabilizing signal representing the derivative of the load current. It may be argued that, when Z_4 is shorted, Z_3 (the resistor) should also be removed to be more representative of a normal class B amplifier. This helps a great deal, actually, but does not approach the low distortion of the original slightly unbalanced current dumping circuit. In addition, removal of Z_3 significantly destabilizes many practical realizations, necessitating in some cases a reduction of the gain-bandwidth of A, resulting in a greater error. In any event, although there may be theoretical situations where a 10% bridge unbalance is worse than a "similar" traditional amplifier, we do not know of any practical cases where this would be true. Contrary to Mr McLoughlin's assertion, Z_2 or its equivalent cannot be removed in a traditional amplifier. It is necessary for feedback compensation in some form.

A third point is that Mr McLoughlin casts a doubt on our interpretation that eddy currents are at work in the inductor. We can assure him that the bridge was optimally balanced (by adjustment of Z_3) to produce our oscillograms in our AES article, the only circuit change being the type of inductor. Our Fig. 9 (b) and Fig. 10 contain distinctly different time constants, the latter being about twice as long as the former. With some effort the error residual could be calculated in each case, but to simply speculate on a few of the obvious time constants does not seem very fruitful to us.

In summary, we welcome many details of analysis and insight offered by Mr McLoughlin, but we disagree on some of the basic points. Not only is current dumping necessarily viewed as error feedforward, but its use in practice significantly improves the performance of audio power amplifiers. It should also be noted that there is nothing inherent in the "current dumping" concept which necessitates the "dumper" stage being class C (i.e. biased off). This clearly was a conscious design decision made by Quad to eliminate the need of quiescent current adjustment and it has been shown in experiments that the residual distortion is below audibility. In addition we believe that feedforward audio amplifiers by other manufacturers are clearly derived from the genius shown in the Quad 405.

L. Vanderkooy
S. P. Lipshitz
University of Waterloo
Waterloo
Ontario

The author replies

Nothing said about the Quad 405 in my articles appears to have been overturned. I made three incautious comparisons with other arrangements, and these had to be withdrawn on grounds of instability. Unfortunately these comparisons bulked large in the conclusions, which have now been rewritten to yield my letter above. Until it is clear whether they will prevail I prefer not to comment on anything other than the Quad 405. I agree that if $e = 0.2$ then a fivefold decrease in distortion is to be expected if a short on L is removed. Inverse of the relative bridge balance accuracy, as our friends suggest. This deals completely with their second point, as the other comparisons mentioned are

* John Vanderkooy and Stanley P. Lipshitz, "Feedforward Error Correction in Power Amplifiers," Journal of the Audio Engineering Society, vol. 28 1980, pp 1-16.

LETTERS

not related to the Quad 405. Their third point about the inductor is their own, and this damaging criticism of the Quad 405 would benefit by confirmation from a second authority.

This leaves their first point, that feedforward alone is the only correct explanation of current dumping. (See also the second sentence of their last paragraph above.) This assertion fully confirms my account of their views. But the italics indicate a great deal. Feedback, it seems, is not feedback unless it is taken *singly*, and from the load. Whereas feedforward apparently, may be *simple*, or a good deal more elastic. With this special language current dumping violates the feedback definition on both counts, and can only be feedforward.

But starting with Walker in the patents and continuing through Baxandall many authors have given perfectly correct explanations in terms of voltage fed back to the input from one or two points near the load. This use of the term feedback is entirely natural, even though it does violate the above curiously narrow definition. There is nothing wrong with this usage, and opposition to it should be dropped. Nothing is at stake: the equivalence of the two explanations (and three others!) was demonstrated in the Sept/Oct articles.

THUNDERSTRUCK

I must admit when I read Chirp's account 'Thunderstruck' in *WW* (Random Echoes, November) it was with some smug satisfaction, that it should happen to such an august company as IBM. Really it should be recognised that this is something which has arrived with microprocessors. The c.p.u. has only to skip one byte (or word) due to electrical interference and it will lose synchronism with the program it is executing. In general it will not regain synchronism of its own accord and the equipment it is supposed to be controlling will remain mute or continually 'doing something'.

These effects will not be evident in equipment which may do a '9-to-5' job, because the power-up reset each morning will keep everything in order, on the other hand those equipments which operate continuously can, for no explicable reason cease to function. This latter is in the category of 'press reset' and everything will be alright again.

On the subject of reset, this is another button which has been gained with microprocessors. It is either resoundingly prominent on the front panel, or coyly hidden around the back somewhere, or a magic three key operation which performs the same function. Alternatively reset can be generated from a circuit at power-up which brings the equipment into the category of: 'If it goes screwy, switch off, wait a moment, then switch on again' - it'll be OK then!

It is so easy to blame exterior forces - the, 'It wasn't me' syndrome but there are opinions that invasion by alpha particles can disrupt the internal saved states of the c.p.u. and sent it 'bananas'. On this score it is interesting to note that Hitachi's 8k x 8bit ram has been constructed to allow for this (New Electronics March or April 83, I think).

What can be done? It should be an essential part of every microprocessor design to have some delay circuit completely separate from the microprocessor circuit and definitely not under software control which is kept reset. The input to this circuit should be one bit from the system which is simply toggled by the software at

perhaps, say, 100ms or 1 second period, the output should go to the c.p.u. where a suitable interrupt can be generated should the toggling action stop, ie, c.p.u. lost. This can be thought of as a 'kickstart' or a kick in the pants to the c.p.u.! A word of warning, some microprocessors will ignore interrupts when they are lost and need a reset followed by the suitable input.

The type of circuitry which comes to mind is two monostables in cascade, e.g. 74LS123, the first as the 'hold-off' delay, the second to create the 'kickstart'. Another circuit that can be used if delays need to be some seconds is the 'Van Der Veen' timer, sketched above, designed by a former colleague of mine and named after him. Not posthumously I hasten to add.

By now you are probably asking yourself, 'How does this Joker know all this?', well, it happened to me! I would like to find an answer to the problem, perhaps this could be food for thought for those more qualified than myself to examine it.

Alan W. Roscoe
Enfield
Middlesex

SOFTWARE BY RADIO

With reference to your news item on page 39 of the December issue, concerning Radio West's 'Datarama' programme, I noted that no commencement date was given for the programme which transmitted home computer software, etc, but the intimation was that they were the first to do so.

Whilst only inspection of the transmission schedules reveals the real 'first' (I think Radio Victory in Portsmouth also claim the honour), I feel it should be noted that BBC Radio Leeds commenced transmission of a magazine-type programme for computer enthusiasts entitled 'Abacus: the computer programme', transmitted fortnightly, started on the 5th October, 1982, and was presented by Dave Banks, Pete Bradley, Martyn Croft and the writer. The content was, and is still, of a magazine nature and included regular experimental transmissions of home microcomputer software, as well as news, reviews, and technical contributions.


The programme is now in the third series, and we hope that software transmission will start again in the new year.

D. R. Coomber
Co-presenter, Abacus
Leeds

XY PLOTTER

In his article ("Computer-controlled xy plotter", January) P. N. C. Hill invites suggestions for an algorithm to draw a straight line between any two points on the plotting area. I have written software for a plotter similar to that he describes and have developed such an algorithm.

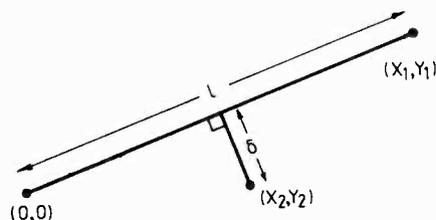The algorithm involves tracking along the required line drawing line segments which fol-



low it as closely as possible. At each step along the line there are two or three points to which a line segment might be drawn (by stepping the X motor, the Y motor or, if possible, both motors together). The point is selected which has the smallest perpendicular distance from the required line. A segment is drawn to this point and the process repeated until the line is complete.

In the figure the perpendicular distance of the point (X2, Y2) from the line from (0,0) to (X1, Y1) is

$$\delta = \text{ABS} \left(\frac{X_1 Y_2 - X_2 Y_1}{l} \right)$$

where l is the length of the line from (0,0) to (X1, Y1). This theorem is derived from the formula for the Vector Product of two vectors. For any given line l is constant, therefore to determine which of a group of points is nearest to the line calculate $\text{ABS}(X_1 Y_2 - X_2 Y_1)$ for each of the points and select the point giving the lowest value. The line is complete when $\text{ABS}(X_2) \geq \text{ABS}(X_1)$ and $\text{ABS}(Y_2) \geq \text{ABS}(Y_1)$.

It is necessary to adapt the above equations to allow the line to start from an arbitrary point instead of (0,0). All the variables may be expressed as integers to increase the speed of execution and to prevent accumulating errors.

Richard Griffiths
Whitchurch
Cardiff

TECHNOLOGY AND PEOPLE

"Why then is it such a common observation of human life, that those who do what they like rarely seem to like what they do?" - S. C. Elliston (Letters, December).

If we replace the first "like" with "choose" and introduce the time function of learning, the problem disappears: the discovery of dislike is retrospective.

If we then replace "choose" with "are pressured by events to do", at least a part of the problem becomes clear: none of us has, ever had, nor ever will have, complete freedom of choice, more especially in a period of mass-employment!

The more creative an individual is, the more free he or she is to choose, but the more attempts there will be to manipulate simply because the world takes man-made providence and Providence with a capital P, for granted.

There is also such a thing as monotony, a source of dislike, the permanent plateau of non-fulfilment in which no learning occurs with the consequent failure of information intake for pleasure-giving processing. Such monotony is commonly provided by an ignorant preoccupation with material pleasures - i.e. non-thinking pleasures such as eating, ambishing non-creatively, and mating, and throwing one's self about in an ape-like monkey-hop to some strange cacophony actually calculated to hold the mind in such ignorance while making a lot of lovely lolly. It seems perhaps that one should never cause or assist the process of thought in case it starts a rebellion! The true question really is, which is the worse evil - the destructive and vandalistic rebellion of non-thought, or the more constructive rebellion of thought?

Mr Elliston's question stems from the same sort of problem mentioned also in December by David A. Chalmers, being the absence of definition for the word "like": it also demonstrates some misunderstanding that the pleasure to

which Professor Campbell refers is a sub-conscious one rather than the conscious one of the senses: one thinks for pleasure, but in the absence of information for processing one is limited to the simple experience of the frustration of not understanding the cause of one's frustration. One must experience the pleasures of thought before one may realise that one needs to know more if one is to experience further pleasure.

That is why the teaching process is so very, very difficult in the early stages, and even more so in the case of the artist.

J. A. MacHarg
Wooler
Northumbria

In his letter, published in *WW* November, 1983, W. M. Dalton hit a nasty land-mine that I first noticed some years ago. Let me first quote the moment when he hits it.

"Let us start from known facts. (1) Light is an electromagnetic phenomenon: demonstrated by Faraday and Kerr. (2) Light is not a static problem: it is oscillatory (Hertz). (3) The electric and magnetic fields are at right-angles and *always* 90 degrees out of phase. Some recent textbooks show these in-phase - an unparadonable error."

I am anxious that Mr Dalton expands on why this error is unparadonable, and what disasters this error might lead us into.

First let me list some non-recent textbooks which show these in-phase.

G. W. Carter, Professor of Electrical Engineering in the University of Leeds, in his book *The Electromagnetic Field in its Engineering Aspects*, (Longman 1954) draws the B and E fields in-phase on page 271. Significantly, although he emphasises that E and B are at right angles (page 274) he never seems to say in the text that B and E are in phase.

A. F. Kip, Professor of Physics, University of California, Berkeley, in his book *Fundamentals of Electricity and Magnetism*, (McGraw-Hill 1962) draws the H and E fields in-phase on page 322. On that same page the text says that the two fields are perpendicular to each other, but does not state that they are in-phase. Again significantly, I cannot find mention in the text that they are in-phase.

O. Heaviside F.R.S., in his book *Electromagnetic Theory Vol 3, 1912*, in art. 452, page 4, wrote

"The General Plane Wave . . . the slab may be of any depth and any strength, and there may be any number of slabs by side behaving in the same way, all moving along independently and unchanged. So $E = \mu v H$ expresses the general solitary wave, where, at a given moment, E may be an arbitrary function of x . . ."

[Replace μv by $\sqrt{\mu\epsilon} - I. Catt$]

Whereas some books (Carter and Kip) vaguely indicate that E and H are in-phase, other books seem to fail to discuss relative phase at all see for example Gullwick 1959, Bewley 1933. The trap was nicely set for Dalton, and he has my sympathy.

Now let us turn to my article in *Wireless World*, July 1979, entitled *The Heaviside Signal*.

"We have shown that the passage of a TEM wave and all the mathematics that has mushroomed around it does not rely on a causality relationship (or interchange) be-

tween the electric and magnetic field. Rather, they are co-existent, co-substantial, co-eternal."

In that article I compare and contrast two mutually contradictory versions of the transverse electromagnetic wave. I believe that the full realisation that E and H are in-phase deals a death-blow to one of those versions, the rolling wave, and leaves the other, the Heaviside signal, the victor.

Because the differential of sin is cos and the differential of cos is minus sin, half-witted mathematicians have invaded the physics of the TEM wave and imposed a spurious story that E causes H causes E. Since sin, cos and $-\sin$ are 90 degrees out of phase, part of their phoney baggage is to imply that E and H are 90 degrees out of phase. (See my article in *WW* in March 1980.) Because the sine wave is amenable to mathematical high jinks, another part of their baggage is to imply that a TEM wave is sinusoidal. It's time we cleaned the claptrap out of electromagnetic theory.

Ivor Catt
St. Albans
Hertfordshire

FORTH PROCESSORS

In his comparison of processors for Forth language implementation and his subsequent reply to one of your correspondants (Letters, November) Brian Woodroffe has made some incorrect statements and unfair comparisons in relation to the I8088 processor.

Firstly, it is clear that his published code for the NEXT routine is far from optimal. It uses two instructions to ensure that on exit from the routine, the DX register is one greater than the BX register. This is clearly unnecessary since the 6809 code for NEXT performs no equivalent action, and any use of the value in DX can use BX instead - probably with less code involved since BX can be used as an index register while DX cannot. I can only assume that the 8088 code was translated from the 8085/Z80 code, which performs a similar (but in this case necessary) action, and that it is intended to work with other Forth routines translated from the 8085. It is equally clear that the 6809 code is in no way a translation of the 6800 code.

It is therefore possible to code NEXT as follows:

```
LODSAX
XCHGAX,BX
JMP WORD PTR (BX)
```

which mimics the 6809 register usage and, being only four bytes long, can be coded inline. This is approximately twice as fast as the code given by Mr Woodroffe and therefore, on his figures, is about 50% faster than the 6809.

Mr O'Connor (Letters, September 1983) has already pointed out that the 8083 code for ADD can likewise be shortened. In his reply (Letters, November), Mr Woodroffe correctly points out that BP will not have a fixed relationship to SP but is wrong in asserting that Mr O'Connor's first example is incorrect. It appears that Mr Woodroffe is unaware that the 8088 can leave the result of an ADD or other operation in memory rather than in a register, and ADD [BP],AX does just that.

Another feature of the 8088 which is particularly useful in Forth is its ability to push and pop memory locations as well as registers, using all the usual addressing modes. Finally, the 8088 has several more registers than the 6809 making it possible, for example, to keep the top-

of-stack item in a register instead of in memory. These features are adequate compensation for the drawback of not having a stack pointer relative addressing mode. To illustrate this, I show 8088 versions of the 6809 routines which Mr Woodroffe illustrates (Forth Language, November). These routines use the DI register to hold the top of stack operand, but even without this optimisation the code need be no larger than the 6809 versions.

Apart from these comparisons, I have enjoyed Mr Woodroffe's illuminating series on the Forth language.

D. Crocker
Woking
Surrey

APPENDIX. Some Forth routines in 8088 code. DI register holds top of stack value; initial DW \$+2 and final NEXT macro omitted.

```
"+": POP AX ; 3 bytes
      ADD DI,AX
MINUS: NEG DI ; 2 bytes
"@": MOV DI,[DI] ; 2 bytes
"!": POP WORD PTR [DI] ; 3 bytes
      POP DI
DUP: PUSH DI ; 1 byte
OVER: MOV BX,SP ; 5 bytes
      PUSH DI
      MOV DI,[BX]
DROP: POP DI ; 1 byte
```

CLOSED LOOP

Your correspondent James A. MacHarg (Letters, November) likens *Wireless World's* Letters section to the House of Commons; a more appropriate name, perhaps, would be Physics Commons. Physicists need these rare, popular outlets not just to air their views but also to realise their own shortcomings. We have all thought that we knew something until we try to explain it! Furthermore, a problem that may baffle one physicist may be obvious to another. If only the young Einstein had had the advantage of a Physics Commons the world would have been spared his silly theory of Special Relativity.

Mr Macharg's interpretation of my expression "closed loop" is fascinating. I was merely describing to electronic specialists the sort of closed-circuit arguments which are employed to uphold Special Relativity. One begins such closed-circuit arguments by assuming something is true. After that, one can argue along any circuit and prove that something really is true!

I take it that Mr MacHarg's explanation why phoney closed-loop arguments are used to support Special Relativity is because of the mind-boggling conclusions of that theory. Presumably, if one can accept that mass is energy then one can accept closed loop arguments! However, when the error in Special Relativity is corrected, mass becomes and energy becomes movement of that mass. One's mind is debogged overnight!
A. H. Winterflood
London N10

Letters in reply to Ian McCauslands' article 'Problems in Special Relativity' appear on pages 71 & 72.

Active filter calculations

Using programmable calculators it is a simple matter to write a sequence of operations to allow transmission of bootstrap and Sallen and Key circuits to be calculated.

The bootstrap and Sallen and Key filter circuits make convenient unity-gain circuit modules that can be implemented using standard operational amplifier gain blocks. With the availability of programmable calculators it is a simple matter to write a sequence of operations that allows the transmission of these circuits to be calculated for any desired component values, with greater potential accuracy and much less labour than would be involved in instrumental measurements. For my own interest I have done this exercise for the Texas Instrument TI58/59 calculators and for the Hewlett Packard HP-65.

While I have no doubt that better mathematicians than I would be able to simplify both the calculation and the resultant program, these do work and give accurate answers. In all cases, the program is written so that the circuit parameters Q and ω/ω_0 are entered into the calculator memory stores, and the transmission in decibels is given when the desired frequency is entered and the program sequence initiated.

I have assumed that the operational amplifier behaves in an ideal manner, having a very high open-loop gain, giving unity gain in the voltage-follower mode and a sufficiently high input impedance for the effect of this to be neglected. This assumption is fully valid for the TL071. It is also assumed that the source impedance seen by the filter is low.

Third-order l.p. bootstrap filter

The first part of the transmission expression for a third-order low-pass bootstrap filter refers to the active circuit, and the second part to the passive RC element. The expression is

$$20\log_{10} \frac{\sqrt{[(1-k^2)+A^2k^2]^2+A^2k^6}}{(1-k^2)^2+A^2k^2} + 20\log_{10} \sqrt{\frac{A^2}{A^2+k^2}}$$

where $k=\omega/\omega_0$ and $A=1/Q$ and $\omega=2\pi f$. Turn-over frequency is

$$\omega_0 = \frac{1}{\sqrt{C_1 C_2 R_1 R_2}}$$

$$\text{and } Q = \frac{\sqrt{xy}}{1+y} = \frac{\sqrt{R_1 C_2 / R_2 C_1}}{1+C_2/C_1}$$

by J. L. Linsley Hood M.I.E.E.

with $x=R_1/R_2$ and $y=C_2/C_1$. To use the program shown, enter the chosen values of Q and press B. Enter ω/ω_0 and press A. Alternatively, enter f_T store 08, enter f , press C. Read out transmission in dB.

TI58/59 program

LRN		48	=
1	2nd LBL	49	2nd LOG
2	B	50	x
3	1/x	51	2
4	x^2	52	0
5	STO	53	=
6	0	54	STO
7	R/S	55	4 2nd order
8	2nd LBL	56	RCL
9	A	57	1
10	x^2	58	+
11	STO	59	RCL
12	1	60	0
13	x	61	=
14	RCL	62	1/x
15	0	63	x
16	=	64	RCL
17	STO	65	0
18	2	66	=
19	+	67	\sqrt{x}
20	(68	2nd LOG
21	1	69	x
22	-	70	2
23	RCL	71	0
24	1	72	=
25)	73	STO
26	STO	74	5 1st order
27	3	75	+
28	=	76	RCL
29	x^2	77	4
30	+	78	=
31	RCL	79	2nd FIX
32	2	80	1
33	x	82	R/S
34	RCL	LRN	
35	1	LRN	
36	x^2	83	2nd LBL
37	\sqrt{x}	84	C
38	\sqrt{x}	85	x
39	\div	86	RCL
40	(87	8
41	RCL	88	1/x
42	3	89	=
43	x^2	90	2nd INV
44	+	91	ENG
45	RCL	92	A
46	2	LRN	
47)		

In practice, it is probably more convenient in the design of the filter circuit to choose the required Q and operating frequency, and then derive the values of R_s and C_s for this.

The method is as follows. Try an arbitrary ratio of $C_2/C_1=y$ (say 1). Then

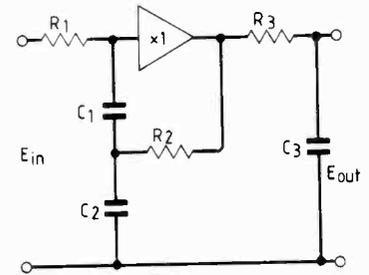


Fig. 1. Low-pass bootstrap filter of 20dB/octave for $Q=2.2$.

$$C_1 (\mu F) = \frac{10^6}{2\pi f_0 R_2 (1+y) Q}$$

$$R_1 = R_2 \frac{Q^2 (1+y)^2}{y} \text{ and } C_3 (\mu F) = \frac{10^6 Q}{2\pi f_0 R_3}$$

If this gives awkward or non-standard values, try another value for C_2/C_1 .

Third-order h.p. bootstrap filter

The transmission expression in the case of a high-pass filter is

$$20\log_{10} \frac{\sqrt{[A^2 k^2 - k^2 (1-k^2)]^2 + A^2 k^2}}{(1-k^2)^2 + A^2 k^2} + 20\log_{10} \sqrt{\frac{A^2 k^2}{(1+A^2 k^2)}}$$

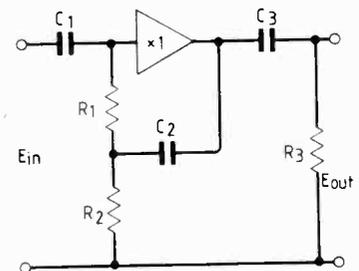


Fig. 2. High-pass bootstrap filter of 20dB/octave for $Q=2.2$.

TI58/59 program

LRN		10	0	k
1	2nd LBL	11	x^2	
2	B	12	STO	
3	1/x	13	2	k^2
4	STO	14	+/-	
5	1	15	+	
6	R/S	16	1	
7	2nd LBL	17	=	
8	A	18	STO	
9	STO	19	3	$1-k^2$

20	x ²	61	0
21	STO	62	=
22	4	63	STO
23	+	64	7
24	(65	RCL
25	RCL	66	6
26	1	67	÷
27	x ²	68	(
28	STO	69	1
29	5	70	+
30	x	71	RCL
31	RCL	72	6
32)	73)
33)	74	=
34	STO	75	√x
35	6	76	2nd LOG
37	=	77	x
38	1/x	78	2
39	x	79	0
40	(80	=
41	(81	STO
42	RCL	82	8
43	6	83	+
44	-	84	RCL
45	RCL	85	7
46	2	86	=
47	x	87	2nd FIX
48	RCL	88	1
49	3	89	R/S
50)	90	2nd LBL
51	x ²	91	C
52	+	92	x
53	RCL	93	RCL
54	6	94	9
55)	95	1/x
56	√x	96	=
57	=	97	2nd INV
58	2nd LOG	98	ENG
59	x	99	A
60	2		LRN

To use, enter Q, press B. Enter ω/ω_0 , press A. Alternatively, enter f_0 in store 9, enter f and press C.

Q and ω_0 are as in the previous case, but here $x=C_2/C_1$ and $y=R_1/R_2$. Again, it will probably be more convenient to choose the required Q and operating frequency, and then derive the necessary values for the Rs and Cs.

Method. Try an arbitrary value of $R_1/R_2=y$ (say=1). Then

$$C_1 (\mu F) = \frac{10^6}{2\pi f_0 R_2 (1+y) Q}$$

$$C_2 = C_1 \frac{Q^2 (1+y)^2}{y}, \text{ and}$$

$$C_3 (\mu F) = \frac{10^6}{2\pi f_0 R_3 Q}$$

A Q-value in the range 2 to 2.2 will give a reasonably flat response for the third-order filter. (For convenience I have defined Q in a manner that differs from the true circuit magnification factor and hope to be forgiven for this small transgression.)

The phase shift produced by these filters may be calculated as follows.

Low pass

$$\phi = \tan^{-1} \frac{K[A^2 - 2A^2k^2 - Ak - (1-k^2)]}{A[A^2k^2 + (1-k^2) - k^4]}$$

High pass

$$\phi = \tan^{-1} \frac{K(k^2 + 2A^2 - 1)}{A(A^2k^2 - k^2 + k^4 - 1)}$$

Programs for the HP65 (or similar RPN calculators) are as follows.

To use, set MC to run, enter program. Enter value of Q, press A (displays Q).

HP65 high-pass and low-pass gain characteristics

1	LBL	44	RCL 6
2	A	45	RCL 5
3	g	46	+
4	1/x	47	f ⁻¹
5	STO 1	48	√
6	f ⁻¹	49	RCL 5
7	√	50	RCL 4
8	STO 2	51	f ⁻¹
9	DSP	52	√
10	•	53	x
11	4	54	+
12	RCL 1	55	RCL 7
13	g	56	÷
14	1/x	58	E
15	RTN	59	STO 7
16	LBL	60	RCL 2
17	D	61	RCL 2
18	STO 3	62	+
19	f ⁻¹	63	÷
20	√	64	E
22	STO 4	65	+
23	RCL 2	66	RTN
24	x	67	LBL
25	STO 5	68	C
26	1	69	D
27	RCL 4	70	RCL 5
28	-	71	RCL 4
29	STO 6	72	RCL 6
30	f ⁻¹	73	x
31	√	74	-
32	RCL 5	75	f ⁻¹
33	+	76	√
34	f ⁻¹	77	RCL 5
35	√	78	+
36	STO 7	79	RCL 7
38	DSP	80	÷
39	•	81	E
40	1	82	+
41	RTN	83	RTN
42	LBL B		enter ω/ω_0 for lpf
43	D		

Enter value of ω/ω_0 (k), press B. This displays transmission in dB for low-pass filter. RCL 7 shows transmission of active second-order filter. For high-pass filter, enter ω/ω_0 and press C. RCL 7 again shows transmission of second-order part of circuit.

HP65 program for high-pass and low-pass phase characteristics

1	LBL	37	RCL 7
2	A	38	RCL 4
3	g	39	2
4	1/x	40	x
5	STO 1	41	-
6	E	42	RCL 7
7	STO 7	43	RCL 2
8	DSP	44	x
9	•	45	-
10	4	46	RCL 5
11	RTN	47	-
12	LBL	48	RCL 2
13	E	49	x
14	f ⁻¹	50	RCL 5
15	√	51	RCL 4
16	RTN	52	+
17	LBL	53	RCL 3
18	D	54	E
19	STO 2	55	-
20	E	56	RCL 1
21	STO 3	57	x
22	RCL 7	58	÷
23	x	59	f ⁻¹
24	STO 4	60	tan
25	1	61	g
26	RCL 3	62	1
27	-	63	8
28	STO 5	64	0
29	DSP	65	-
30	•	66	RTN
31	0	67	LBL
32	RTN	68	C
33	LBL	69	D
34	B	70	0
35	D	71	RCL 3
36	0	72	RCL 7

73	2	86	1
74	x	87	-
75	+	88	RCL 1
76	1	89	x
77	-	90	÷
78	RCL 2	91	f ⁻¹
79	x	92	Tan
80	RCL 4	93	g
81	RCL 3	94	1
82	E	95	8
83	+	96	0
84	RCL 3	97	+
85	-	98	RTN

To use, set MC to run. Enter program. Enter Q, press A. Enter ω/ω_0 and press B for low-pass phase shift, or press C for high-pass phase characteristic.

As a check, both of the validity of the calculations shown above and of the program written for them, the predicted and measured characteristics of two circuit embodiments, the treble and rumble filter circuits employed in the modular pre-amplifier design (*Wireless World*, Oct. 1982 to Feb. 1983) are shown in Figs 5 and 6, and a steeper cut treble filter, having a Q of 2.2, and an f_0 of 5.9kHz, is shown in Fig 7.

Sallen and Key filter

The widely used Sallen and Key circuit shown in Figs 3 and 4 can be used as a third-order filter with a following or preceding passive filter element, similar to that shown in Figs 1 and 2. It is, however, most commonly employed as a second-order filter element having an ultimate attenuation rate of -12dB/octave, and it is for this form that the equations and program below are derived. As previously, $\omega/\omega_0=k$ and $A=1/Q$, and here

$$Q = \frac{\sqrt{xy}}{1+x}$$

In the low-pass circuit, $x=R_1/R_2$ and $y=C_3/C_4$ and in the high-pass form, $y=C_1/C_2$ and $x=R_3/R_4$.

Transmission expressions are

$$\text{Low pass} \quad \frac{(1-k^2) - jkA}{(1-k^2)^2 + (kA)^2}$$

$$\text{High pass} \quad \frac{k^2(k^2-1) - jkA(k^2)}{(k^2-1)^2 + (kA)^2}$$

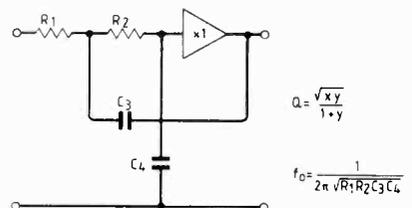


Fig. 3. Low-pass Sallen and Key filter of 12dB/octave

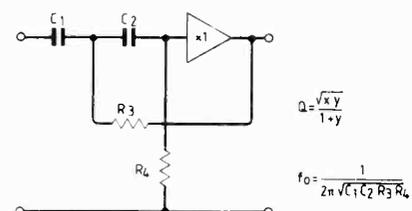


Fig. 4. High-pass Sallen and Key filter of 12dB/octave

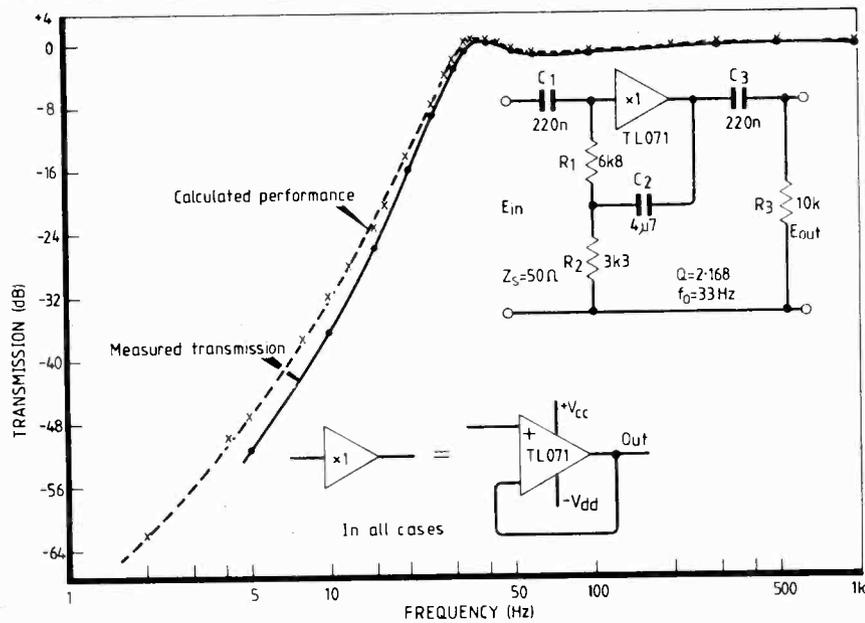


Fig. 5. High-pass bootstrap filter

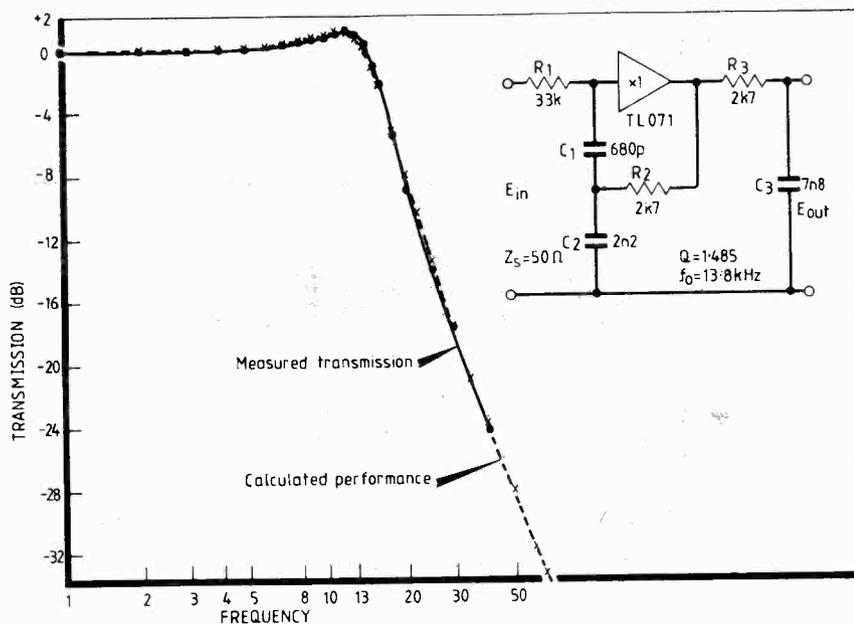


Fig. 6. Low-pass bootstrap filter. Frequency scale in kHz.

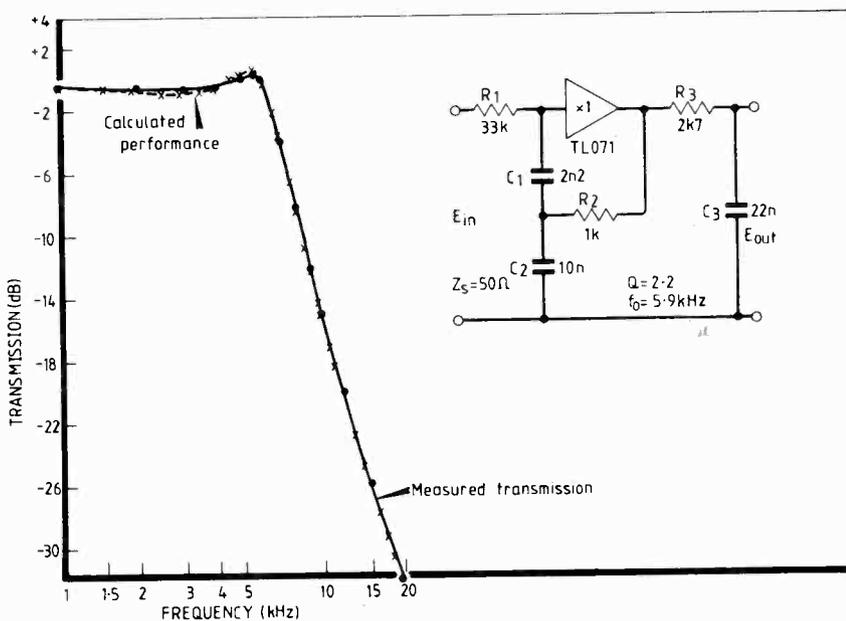


Fig. 7. Low-pass bootstrap filter with $Q=2.2$

TI58/59 transmission and phase for Sallen and Key filters

LRN			
1	2nd LBL	53	1
2	A	54	=
3	2nd CP	55	STO
4	STO	56	3
5	0	57	x^2
6	x^2	58	+
7	+/-	59	(
8	+	60	RCL
9	1	61	0
10	=	62	x
11	STO	63	RCL
12	2	64	1
13	x^2	65)
14	+	66	x^2
15	RCL	67	=
16	0	68	STO
17	x^2	69	4
18	x	70	RCL
19	RCL	71	0
20	1	72	x^2
21	x^2	73	x
22	=	74	RCL
23	STO	75	3
24	3	76	÷
25	1/x	77	RCL
26	x	78	4
27	RCL	79	=
28	2	80	$x \rightarrow t$
29	=	81	RCL
30	$x \rightarrow t$	82	0
31	RCL	83	x
32	0	84	RCL
33	x	85	1
34	RCL	86	x
35	1	87	RCL
36	÷	88	2
37	RCL	89	÷
38	3	90	RCL
39	=	91	4
40	INV	92	=
41	2nd P→R	93	INV
42	$x \rightarrow t$	94	2nd P→R
43	R/S	95	$x \rightarrow t$
44	2nd LBL	96	R/S
45	B	97	2nd LBL
46	2nd CP	98	E
47	STO	99	2nd LOG
48	0	100	X
49	x^2	101	2
50	STO	102	0
51	2	103	=
52	-	104	R/S
		LRN	


Enter Q , $1/x$ and store 01 ($1/Q$). To use, enter ω/ω_0 , press A for low-pass. This displays gain. For high-pass, enter ω/ω_0 , press B. This displays stage gain. In both cases, for phase press $x \rightarrow t$. To obtain result in dB, press E.

The HP65 program for the same circuit is shown below.

HP65 Sallen and Key filter transmission characteristics

1	LBL	23	RCL 2
2	E	24	x
3	f^{-1}	25	E
4	√	26	STO 4 A^2k^2
5	RTN	27	RCL 3
6	LBL	28	+
7	A	29	RCL 3
8	E	30	RCL4
9	g	31	+
10	$1/x$	32	E
11	STO 1	33	÷
12	RTN	34	f
13	LBL	35	√
14	B	36	f
15	E	37	LOG
16	STO 2 k^2	38	2
17	1	39	0
18	RCL 2	40	x
19	-	41	RTN
20	E	42	LBL
21	STO 3 $(1-k^2)^2$	43	C
22	RCL 1	44	E

45	STO 2	61	-
46	RCL 2	62	E
47	↑	63	RCL 1
48	1	64	RCL 2
49	-	65	x
50	x	66	+
51	E	67	E
52	RCL 1	68	÷
53	RCL 2	69	f
54	3	70	√
55	g	71	f
56	y ^x	72	LOG
57	x	73	2
58	+	74	0
59	1	75	x
60	RCL 2	76	RTN

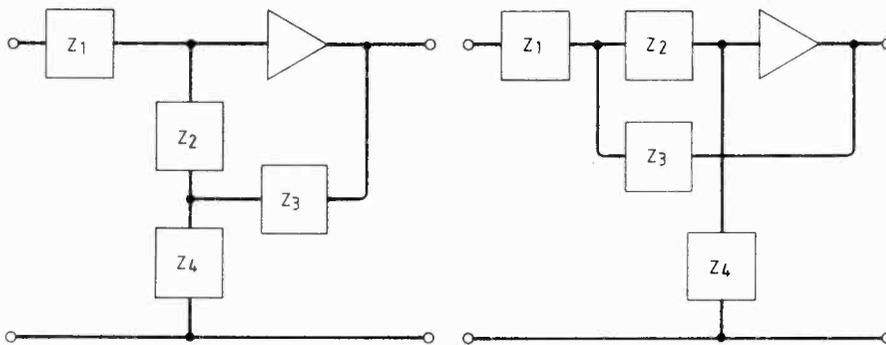

To use, set MC to run, enter program. Enter chosen Q value, press A. Enter ω/ω_0 . Press B for low-pass transmission in dB. Press C for high-pass transmission.

Appendix

The equations for the transmission of these two filter systems are shown below for the generalized form. The actual transmission for the h-p and l-p circuits can be obtained by substituting R or $1/j\omega C$ for the impedance blocks denoted by Z_1, Z_2 , etc.

H or bootstrap filter

$$\frac{E_{out}}{E_{in}} = \frac{Z_2 Z_3 + Z_3 Z_4 + Z_2 Z_4}{Z_1 Z_3 + Z_2 Z_3 + Z_3 Z_4 + Z_2 Z_4}$$

In the low-pass case, this becomes

$$\frac{1 + j\omega R_2(C_1 + C_2)}{1 + j\omega R_2(C_1 + C_2) - \omega^2 R_1 R_2 C_1 C_2}$$

and in the high-pass case

$$\frac{j\omega C_1(R_1 + R_2) - \omega^2 R_1 R_2 C_1 C_2}{1 + j\omega C_1(R_1 + R_2) - \omega^2 R_1 R_2 C_1 C_2}$$

Sallen and Key filter

$$\frac{E_{out}}{E_{in}} = \frac{1}{1 + Z_1/Z_4 + Z_2/Z_4 + \frac{Z_1 Z_2}{Z_3 Z_4}}$$

In the low-pass case, this becomes

$$\frac{1}{1 + j\omega C_4(R_1 + R_2) - \omega^2 R_1 R_2 C_3 C_4}$$

and in the high-pass case

$$\frac{\omega^2 R_3 R_4 C_1 C_2}{\omega^2 R_3 R_4 C_1 C_2 + j\omega R_3(C_1 + C_2) - 1}$$

These can be transformed into more easily manipulable forms, of the type quoted in the article above, by the use of the relationship

$$\omega_0 = 1/\sqrt{R_1 R_2 C_1 C_2}$$

or its appropriate equivalent depending on the component numbering, and the simplifying relationships $R_1/R_2 = x$ and $C_1/C_2 = y$, again using the appropriate component numbering.

More active filter calculations

Time-saving programs for the TI59 calculator give poles and filter order for both Tschebycheff and Butterworth low-pass filters

As a rule, filter requirements are expressed by the maximal attenuation of the passband A_{max} , the minimal attenuation of the stopband A_{min} , and by the normalized frequency Ω . With these values only the filter order n and the poles $s_k = \sigma_k + j\gamma_k$ of the transfer function of a normalized low-pass filter need to be calculated. If the poles are known, the resonance frequency and the quality factor Q are easily obtained by

$$\omega_0 = \sqrt{\sigma_k^2 + \gamma_k^2}, \quad Q = \frac{1}{2} \left[1 + \left(\frac{\gamma_k}{\sigma_k} \right)^2 \right]^{1/2} \quad 1$$

Hence the programs of both the Tschebycheff and Butterworth normalized low-pass filters have to give n and s_k as well.

1. As the Tschebysheff approximation is explained in detail in the reference¹, only the formulas needed to understand the programs are given. The loss of an order n Tschebysheff low-pass filter is

$$A(\Omega) = 10 \log \{ 1 + [\epsilon T_n(\Omega)]^2 \} \quad 2$$

where the T-polynomial of order n is

$$T_n(\Omega) = \frac{1}{2} [(\Omega + \sqrt{\Omega^2 - 1})^n + (\Omega - \sqrt{\Omega^2 - 1})^n] \quad 3$$

by Kamil Kraus

The passband ripple A_{max} is related to ϵ by

$$\epsilon^2 = 10^{0.1 A_{max}} - 1 \quad 4$$

Equations 2 and 3 are used to calculate the filter order n . After some manipulation¹ the expressions for the real and imaginary part of roots yield

$$\sigma_k = \frac{1}{2} \sin \frac{\pi}{2} \frac{1 + 2k}{n} (K^{1/n} - K^{-1/n}) \quad k=0, 1, 2, \dots$$

$$\gamma_k = \frac{1}{2} \cos \frac{\pi}{2} \frac{1 + 2k}{n} (K^{1/n} - K^{-1/n}), \quad 5$$

$$\text{where } K = \frac{1}{\epsilon} + \sqrt{\frac{1}{\epsilon^2} + 1} \quad 6$$

In program 1 we find n in $X \geq t$ and displayed before the pause, σ_k : STO00-STO07, γ_k : STO20-STO27.

Example. Given $A_{max} = 0.4576$ dB, $A_{min} = 32$ dB and $\Omega = 2.0926$, we obtain $n = 4$ and

STO00	$\sigma_1 = -0.1800241922$
STO01	$\sigma_2 = -0.4346168463$
STO20	$\gamma_1 = 1.021002054$
STO21	$\gamma_2 = 0.4229128979$

2. The order n of the Butterworth normalized low-pass filter is calculated using the equation

$$n = \frac{\log[(10^{0.1 A_{min}} - 1)/(10^{0.1 A_{max}} - 1)]}{2 \log \Omega} \quad 7$$

and the roots are for n even

$$s_k = \exp \left[\frac{j\pi}{2n} (2k-1) \right] \quad k=1, 3, 5, \dots \quad 8$$

for n odd

$$s_k = \exp \left[\frac{j\pi k}{n} \right] \quad k=2, 4, 6, \dots$$

In program 2, n is displayed before the pause, σ_k : STO11-STO19, γ_k : STO20-STO29.

continued on page 57

Program 1.

LRN			
000	76	2nd Lbl	
001	14	D	
002	43	RCL	
003	00	0	
004	33	X ²	
005	75	-	
006	01	1	
007	95	=	
008	34	√X	
009	42	STO	
010	01	1	
011	75	-	
012	43	RCL	
013	00	0	
014	95	=	
015	50	2nd X	
016	45	Y ^x	
017	43	RCL	
018	05	5	
019	95	=	
020	42	STO	
021	02	2	
022	43	RCL	
023	01	1	
024	85	+	
025	43	RCL	
026	00	0	
027	95	=	
028	45	Y ^x	
029	43	RCL	
030	05	5	
031	95	=	
032	44	SUM	
033	02	2	
034	25	CLR	
035	02	2	
036	22	INV	
037	49	2nd Prd	
038	02	2	
039	43	RCL	
040	02	2	
041	33	X ²	
042	65	x	
043	43	RCL	
044	04	4	
045	85	+	
046	01	1	
047	95	=	
048	28	2nd log	
049	65	x	
050	01	1	
051	00	0	
052	95	=	
053	75	-	
054	43	RCL	
055	03	3	
056	95	=	
057	50	2nd X	
058	22	INV	
059	77	2nd X ^{≥t}	
060	11	A	
061	12	b	
062	76	2nd Lbl	
063	11	A	
064	43	RCL	
065	05	5	
066	32	X ^{≥t}	
067	43	RCL	
068	05	5	
069	66	2nd Pause	
070	66	2nd Pause	
071	66	2nd Pause	
072	61	GTO	
073	35	1/X	
074	76	2nd Lbl	
075	12	B	
076	43	RCL	
077	06	6	
078	75	-	
079	43	RCL	
080	05	5	
081	95	=	
082	50	2nd X	
083	67	2nd X=t	
084	13	C	
085	15	E	
086	76	2nd Lbl	
087	13	C	
088	02	2	
089	42	STO	

183	76	2nd Lbl
184	10	2nd E'
185	09	9
186	00	0
187	38	2ns sin
188	55	:
189	02	2
190	95	=
191	65	x
192	43	RCL
193	16	16
194	95	=
195	94	+/-
196	72	STO 2nd Ind
197	09	09
198	91	R/S
199	76	2nd Lbl
200	17	2nd B'
201	43	RCL
202	18	18
203	65	x
204	43	RCL
205	11	11
206	65	x
207	09	9
208	00	0
209	95	=
210	42	STO
211	19	19
212	38	2nd sin
213	65	x
214	43	RCL
215	16	16
216	55	:
217	02	2
218	95	=
219	94	+/-
220	72	STO 2nd Ind
221	09	09
222	01	1
223	44	SUM
224	10	10
225	44	SUM
226	09	9
227	43	RCL
228	19	19
229	39	2nd cos
230	55	:
231	02	2
232	65	x
233	43	RCL
234	17	17
235	95	=
236	72	STO 2nd Ind
237	08	08
238	01	1
239	44	SUM
240	08	8
241	16	2nd A'
242	92	INV SBR
243	91	R/S
244	LRN	

Input: Ω - STO 00
 A_{min} - STO 03
 ϵ - STO 04
 $n=2$ - STO 05
 $n=15$ - STO 06
 1 to X^{≥t}

Program 2

LRN		
000	43	RCL
001	01	1
002	65	x
003	93	.
004	01	1
005	95	=
006	22	INV
007	28	2nd log
008	75	-
009	01	1
010	95	=
011	42	STO
012	03	3
013	43	RCL
014	00	0
015	65	x
016	93	.
017	01	1
018	95	=
019	22	INV
020	28	2nd log

021	75	-
022	01	1
023	95	=
024	55	:
025	43	RCL
026	03	3
027	95	=
028	28	2nd log
029	42	STO
030	03	3
031	43	RCL
032	02	2
033	28	2nd log
034	65	x
035	02	2
036	95	=
037	55	:
038	43	RCL
039	03	3
040	95	=
041	35	1/X
042	85	+
043	93	.
044	04	4
045	05	5
046	95	=
047	59	2nd Int
048	42	STO
049	06	6
050	66	2nd Pause
051	66	2nd Pause
052	66	2nd Pause
053	13	C
054	76	2nd Lbl
055	13	C
056	93	.
057	01	1
058	32	X ^{≥t}
059	25	CLR
060	01	1
061	00	0
062	42	STO
063	03	3
064	25	CLR
065	02	2
066	00	0
067	42	STO
068	04	4
069	43	RCL
070	06	6
071	55	:
072	02	2
073	95	=
074	42	STO
075	07	7
076	59	2nd Int
077	75	-
078	43	RCL
079	07	7
080	95	=
081	50	2nd X
082	22	INV
083	77	2nd X ^{≥t}
084	19	2nd D'
085	14	D
086	76	2nd Lbl
087	14	D
088	43	RCL
089	06	6
090	42	STO
091	01	1
092	32	X ^{≥t}
093	01	1
094	42	STO
095	00	0
096	86	2nd St Flg
097	00	0
098	11	A
099	76	2nd Lbl
100	19	2nd D'
101	43	RCL
102	06	6
103	42	STO
104	01	1
105	32	X ^{≥t}
106	02	2
107	42	STO
108	00	0
109	22	INV
110	87	2nd If Flg
111	00	0
112	16	2nd A'
113	76	2nd Lbl

114	11	A
115	01	1
116	08	8
117	00	0
118	65	x
119	43	RCL
120	00	0
121	55	:
122	43	RCL
123	01	1
124	95	=
125	42	STO
126	02	2
127	39	2nd cos
128	50	2nd X
129	94	+/-
130	72	STO 2nd Ind
131	03	03
132	43	RCL
133	02	2
134	38	2nd sin
135	72	STO 2nd Ind
136	04	04
137	43	RCL
138	00	0
139	67	2nd X=t
140	91	R/S
141	12	B
142	76	2nd Lbl
143	12	B
144	02	2
145	44	SUM
146	00	0
147	25	CLR
148	01	1
149	44	SUM
150	03	3
151	44	SUM
152	04	4
153	87	2nd If Flg
154	00	0
155	11	A
156	16	2nd A'
157	76	2nd Lbl
158	16	2nd A'
159	43	RCL
160	00	0
161	65	x
162	02	2
163	75	-
164	01	1
165	95	=
166	42	STO
167	05	5
168	43	RCL
169	01	1
170	65	x
171	02	2
172	95	=
173	55	:
174	43	RCL
175	05	5
176	95	=
177	35	1/X
178	65	x
179	01	1
180	08	8
181	00	0
182	95	=
183	42	STO
184	06	6
185	39	2nd cos
186	50	2nd X
187	94	+/-
188	72	STO 2nd Ind
189	03	03
190	43	RCL
191	06	6
192	38	2nd sin
193	72	STO 2nd Ind
194	04	04
195	43	RCL
196	00	0
197	67	2nd X=t
198	91	R/S
199	12	B
200	92	INV SBR
201	91	R/S
202	00	LRN

Input: A_{min} - STO 00
 A_{max} - STO - 01
 Ω - STO 02

Elliptic filter design using TI-59

Using this program the design of an elliptic low-pass filter takes only a few minutes

Many of programs concerning electronic filter design have been published and the calculation of Tschebycheff and Butterworth low-pass filters are in the subroutine to the TI-59, to my knowledge a simple program to solve a normalized elliptic low-pass hasn't yet been published. To overcome the rather difficult theory of elliptic integrals and elliptic functions little mathematics has been used to calculate the filter order, zeros and poles of the Tschebycheff rational function.

Program commentary

In designing an elliptic filter four values are given: A_{max} maximum passband loss, A_{min} minimum stopband attenuation, ω_B upper passband edge, ω_H upper stopband edge. These values enable zeros and poles of the Tschebycheff rational function $R_n(x,L)$ to be estimated. Calculate first

$$L^2 = \frac{10^{0.1A_{min}-1}}{10^{0.1A_{max}-1}} \text{ and hence } \beta = \arcsin(1/L) \quad (1)$$

$$\text{then } k = \sin \alpha = 1/x_L = \frac{\omega_B}{\omega_H}$$

$$\text{hence } \alpha = \arcsin\left(\frac{\omega_B}{\omega_H}\right) \quad (2)$$

With α and β the filter order n may be computed by means of complete elliptic integrals as functions of x_L^{-1} and L^{-1} . To overcome the difficulty of evaluating complete elliptic integrals the modular function as defined in Appendix by equation A1 is used. Supposing k is known, q can be computed by means of the Newton's approximation formula given by equation A2. Using the relation between q and complete elliptic integrals K together with the complementary integrals K' the filter order n is given simply by equation A3. As the zeros of $R_n(x,L)$ are given by

$$x_{zy} = sn \frac{2\gamma K}{n} \text{ for } n \text{ odd} \quad (3)$$

$$\text{and } x_{zy} = sn \frac{(2\gamma-1)K}{n} \text{ for } n \text{ even}$$

the elliptic function $sn u$ must be calculated. To simplify this task q_1 given by equation A4 has been introduced, which makes possible to express the competent elliptic function $sn u'$ by equation A5. Once zeros of $R_n(x,L)$ are known the poles may be computed by

$$x_{py} = \frac{x_L}{x_{zy}} \quad (4)$$

by Kamil Kraus

Besides poles and zeros of $R_n(x,L)$, one might want to know where $R_n = \pm 1$ or $R_n = \pm L$ as these points determine the location of the maximum passband or minimum stopband attenuation. The location of maxima x_m is

$$x_{m,\gamma} = \frac{(1+2\gamma)K}{n} \text{ for } n \text{ odd} \quad (5)$$

$$\text{and } x_m = \frac{2\gamma K}{n} \text{ for } n \text{ even.}$$

The location of minimum stopband attenuation is given by equation 4, where $x_{m\gamma}$ is inserted instead of x_{zy} .

The program written for the TI59 follows the sequence of equations from equations A2 to A5. First, the program answers the question: is $k^2 < 0.5$ or $k^2 > 0.5$?, and then approximates q_1 and q_2 using A2. To get n as an integer the calculated value of n is rounded downwards and then 2 is added. In the final part of the program, the elliptic function according to A5 is computed. Here two cases are to be distinguished: n is even, zeros are stored in STO 11-20 and the maxims are stored in STO 21-29, when n is odd the location of zeros and maxima is interchanged!

To compare the results obtained using this program with the values calculated by another method the example given in ref. 1 is solved. Here, instead of x_{zy} and $x_{m\gamma}$ frequencies are given so we have to multiply the results by 20.

Program appears on page 59

Example. To find the zeros and maxima of normalized elliptic low-pass filter which has $A_{max}=0.1\text{dB}$, $A_{min}=30\text{dB}$, $f_B=20$ and $f_H=26$. First find $x_L=1.3$ and $L=207.0952$, hence $\alpha=50.28486277^\circ$ and $\beta=0.276664^\circ$. With these values calculate $n=4.656928611$ rounded to $n=6$.

Calculated zeros ref. 1 zeros
STO11: 6.254545988 6.296
STO12: 15.72067887 15.622
STO13: 19.60740999 19.566

Calculated maxima ref. 1 maxima
STO21: 11.67429795 11.66
STO22: 18.28716445 18.18
STO23: 20.0 20.0

A comparison shows that the results obtained are sufficiently accurate to be used in designs of elliptic low-pass filters.

Appendix

The modular function² is

$$k^2 = 16q - \frac{1+4q^2}{1+8q+24q^2} \quad A1$$

Newton's approximation formula is

$$q_{n+1} = q_n - \frac{f(q_n)}{f'(q_n)} \quad A2$$

where $f(q) = 64q^3 - 24k^2q^2 + (16-8k^2)q - k^2$
 $f'(q) = 192q^2 - 48k^2q + (16-8k^2)$.

The relation between q and the complete elliptic integrals $K(1/x_L)$ and its complementary form $K'(1/x_L)$ by ref. 2, is

$$\frac{K_1'(1/x_L)}{K_1(1/x_L)} = \kappa_1, \quad q_1 = e^{-\pi\kappa_1} \Rightarrow \frac{K_1'}{K_1} = -\frac{1}{\pi} \ln q_1$$

$$\frac{K_2'(1/L)}{K_2(1/L)} = \kappa_2, \quad q_2 = e^{-\pi\kappa_2} \Rightarrow \frac{K_2'}{K_2} = -\frac{1}{\pi} \ln q_2$$

so that the filter order n is

$$n = \frac{1}{\pi^2} \ln q_1 \cdot \ln q_2 \quad A3$$

Introducing

$$q_1 = \exp(-\pi^2/\ln q_1) \quad A4$$

we have

$$\text{sn } u' = \text{siny}(1+4q_1\cos^2y) \quad A5$$

where $u' = u/K = 2y/\pi$ and $u = 2\gamma K/n$ for n odd, $u = (2\gamma-1)K/n$ for n even.

References

- Daniels, R.W.: Approximation Methods for Electronic Filter Design. McGraw-Hill, New York, 1974.
- Jahnke-Emde: Tables of Higher Functions. B.G. Teubner Verlag, Leipzig, 1952.

continued from page 55

Example. Given $A_{min}=28\text{dB}$, $A_{max}=3\text{dB}$, $\Omega=2.2382$, we obtain $n=4$ and

STO11 $\sigma_1 = -0.3826834324$
STO12 $\sigma_2 = -0.9238795325$
STO20 $\gamma_1 = 0.9238795325$
STO21 $\gamma_2 = 0.3826834324$

These values are in full agreement with those in reference 2.

References

- Approximation Methods for Electronic Filter Design, by R. W. Daniels. McGraw Hill, New York, 1974.
- Tabellenbuch Tiefpässe, by G. Pfitzenmaier. Siemens, Munich, 1971.

Compensated active summer

Adding two op-amps and six resistors to the basic summing amplifier can reduce phase and magnitude errors to negligible levels.

It is well known that the complex open-loop gain characteristics of operational amplifiers (op-amps) degrade significantly the performance of the weighted summing structures. With the introduction of low-cost dual and quad op-amps having closely matched characteristics which track with changes in temperature and voltage, active compensation techniques have proved very attractive. Recently several active phase-compensated weighted summers using two op-amps have been described¹. It has been shown that for low frequencies the two op-amp compensated summer has phase and magnitude errors proportional to $(\omega/\omega_t)^3$ and $(\omega/\omega_t)^2$, where ω_t is the unity gain bandwidth of the op-amp. That is, the phase error of the two op-amp summer is reduced to a negligible level; whereas the magnitude error remains a second order term, as that of the uncompensated summer.

Most recently, active compensated amplifiers using three op-amps have been considered²; however, the reported are not suitable by their nature for realizing generalized weighted summers for both positive and negative gains.

With the circuit described here, at low frequencies the phase and the magnitude errors are proportional to $(\omega/\omega_t)^3$ and $(\omega/\omega_t)^4$ respectively. That is, both the phase and the magnitude errors are reduced to negligible levels. The design equations assume the use of mismatched op-amps, although the special case of matched op-amps will also be considered.

Compensated summer

The circuit is shown right. The voltage $V_{11}, V_{12}, \dots, V_{1m}$ represent the m inverting inputs and the voltage $V_{21}, V_{22}, \dots, V_{2n}$ are the n noninverting inputs. Let the open loop gain of each of the three op-amps be represented by the single pole model given by

$$A_i(s) \approx \frac{\omega_{ti}}{s} \text{ for } i=1,2,3 \quad (1)$$

where ω_t is the unity gain bandwidth of the op-amp and is ideally infinity. By

Ahmed Soliman received the B.S. degree in electrical engineering from Cairo University, and the M.S. and Ph.D. degrees from the University of Pittsburgh. He is currently in the department of electronics and communications engineering at Cairo University.

by A. M. Soliman

direct analysis of the circuit, the generalized expression of the output voltage V_o is


$$V_o = \left[\frac{(K+1)}{G^+} \sum_{i=1}^n (V_{2i} G_{2i}) - \frac{K}{G} \sum_{i=1}^m (V_{1i} G_{1i}) \right] \left[\frac{K_1+1}{K_2+1} \right] \cdot \epsilon(s) \quad (2)$$

where

$$G^+ = \sum_{i=1}^n G_{2i}, G_{2i} = \frac{1}{R_{2i}} \quad (i=1,2, \dots, n) \quad (3)$$

$$G = \frac{1}{R} = \sum_{i=1}^m G_{1i}, G_{1i} = \frac{1}{R_{1i}} \quad (i=1,2, \dots, m) \quad (4)$$

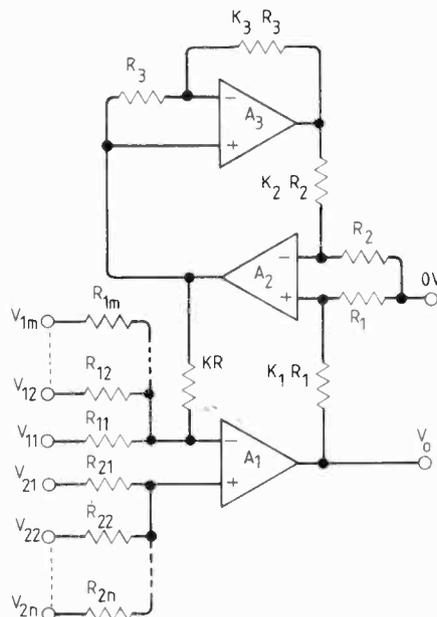$\epsilon(s)$ is the remaining error function of the



Basic summing amplifier is A_1 . Compensation of the summer is achieved by A_2 and A_3 and a few resistors: these reduce phase error to a third order term and magnitude error to a fourth order term.

compensated circuit and is equal to

$$\frac{1+s\tau_2+s^2\tau_2\tau_3}{1+s\tau_3+\left(\frac{K+1}{K_2+1}\right)[s\tau_1+s^2\tau_1\tau_2+s^3\tau_1\tau_2\tau_3]} \quad (5)$$

where $\tau_i = \frac{K_i+1}{\omega_{ti}} \quad (i=1,2,3) \quad (6)$

Choosing $K_2 = K$, equations (2) and (5) become

$$V_o = \left[\frac{(K_1+1)}{G^+} \sum_{i=1}^n (V_{2i} G_{2i}) - \frac{K(K_1+1)}{(K+1)G} \sum_{i=1}^m (V_{1i} G_{1i}) \right] \cdot \epsilon(s) \quad (7)$$

$$\epsilon(s) = \frac{1+s\tau_2+s^2\tau_2\tau_3}{1+s(\tau_1+\tau_3)+s^2\tau_1\tau_2+s^3\tau_1\tau_2\tau_3} \quad (8)$$

Examining the above equation for the remaining phase and magnitude errors, it is seen that by taking

$$\tau_1 = \frac{\tau_2}{2} = \tau_3 \quad (9)$$

will yield relatively negligible phase and magnitude errors over a prescribed frequency range. The compensated error function reduces to

$$\epsilon_c(s) = \frac{1+2\tau_1s+2\tau_1^2s^2}{1+2\tau_1s+2\tau_1^2s^2+2\tau_1^3s^3}$$

From the above equation, it is seen that the phase and the magnitude errors of the compensated circuit are given respectively by

$$\phi \approx \arg. [\epsilon_c(j\omega)] \approx 2(\tau_1\omega)^3$$

$$= 2 \left[(K_1+1) \frac{\omega}{\omega_{t1}} \right]^3$$

$$\gamma \approx |\epsilon_c(j\omega)| - 1 \approx 4(\tau_1\omega)^4$$

$$=4 \left[(K_1+1) \frac{\omega}{\omega_{t1}} \right]^4$$

where $\omega\tau_i \ll 1$ ($i=1,2,3$)

Thus with the conditions of equation (9) being satisfied and at frequencies such that $\omega\tau_i \ll 1$ ($i=1,2,3$), the phase error is reduced to a third order term and the magnitude error is reduced to a fourth order term.

The gain requirements are controlled by the parameter K. The compensation conditions can be satisfied by selecting the resistors K_1R_1 , K_2R_2 and K_3R_3 . The design equations for K_1 , K_2 and K_3 are obtained from equations (6) and (9) and are

$$K=K_2=2(K_1+1) \left(\frac{\omega_{t2}}{\omega_{t1}} \right) - 1$$

$$K_3=(K_1+1) \left(\frac{\omega_{t3}}{\omega_{t1}} \right) - 1$$

It is not necessary to use matched op-amps with this generalized summer. If matched op-amps are used however, the design equations simplify to

$$K=K_2=2K_1+1$$

$$K_3=K_1$$

It should be noted that the above design is based on the choice $K=K_2$. Other choices for the parameter K are possible.

It is worth noting that the three port v.c.v.s. reported most recently³ is a special case from this generalized summer by setting $m=n=1$ and $\tau_3=0$. 

References

1. A.M. Soliman. Novel active phase compensated inverting amplifier, *Frequenz* vol. 34 no. 8, pp 238-240, August 1980.
M. Ismail and A.M. Soliman. Novel active compensated method of op-amp VCVS and weighted summer building blocks, *Proceedings IEEE Int. Symposium on Circuits and Systems, Tokyo*, pp 922-925, July 1979.
A. Rodriguez-Vazquez and J.L. Huertas. Novel active compensated weighted summer, *Electronics Letters* vol. 16 no. 10, pp 394-395, May 1980.
2. S. Natarajan and B.B. Bhattacharyya. Design of actively compensated finite gain amplifiers for high frequency applications, *IEEE Trans. on Circuits and Systems* vol. CAS-27 no. 12, pp 1133-1139, December 1980.
R. L. Geiger and A. Budak. Design of active filters independent of first and second order operational amplifier time constant effects, *IEEE Trans. on Circuits and Systems* vol. CAS-28 no. 8, pp. 749-757, August 1981.
3. A.M. Soliman. New phase compensated three port VCVS with controlled gain difference, *L'Onde électrique* vol. 61 no. 12, pp 39-41, December 1981.

Elliptic filter program

LRN			089	95	=	179	66	2nd Pause	269	35	1/X
000	76	2nd Lbl	090	44	SUM	180	66	2nd Pause	270	76	2nd Lbl
001	17	2nd B'	091	04	4	181	66	2nd Pause	271	19	2nd D'
002	43	RCL	092	43	RCL	182	66	2nd Pause	272	43	RCL
003	15	15	093	01	1	183	61	GTO	273	04	4
004	32	X \geq t	094	33	X ²	184	34	\sqrt{X}	274	72	STO 2nd Ind
005	43	RCL	095	65	x	185	76	2nd Lbl	275	30	30
006	00	0	096	43	RCL	186	34	\sqrt{X}	276	25	CLR
007	38	2nd sin	097	00	0	187	43	RCL	277	01	1
008	33	X ²	098	65	x	188	08	8	278	44	SUM
009	77	2nd X \geq t	099	02	2	189	59	2nd Int	279	30	30
010	13	C	100	04	4	190	85	+	280	25	CLR
011	14	D	101	95	=	191	02	2	281	02	2
012	76	2nd Lbl	102	94	+/-	192	95	=	282	44	SUM
013	13	C	103	44	SUM	193	42	STO	283	02	2
014	43	RCL	104	04	4	194	01	1	284	43	RCL
015	00	0	105	43	RCL	195	43	RCL	285	01	1
016	39	2nd cos	106	01	1	196	06	6	286	75	-
017	33	X ²	107	45	Y ^x	197	35	1/X	287	43	RCL
018	42	STO	108	03	3	198	23	lnX	288	02	2
019	00	0	109	95	=	199	55	:	289	95	=
020	43	RCL	110	65	x	200	89	2nd π	290	22	INV
021	10	10	111	06	6	201	95	=	291	77	2nd X \geq t
022	32	X \geq t	112	04	4	202	35	1/X	292	18	2nd C'
023	11	A	113	95	=	203	65	x	293	10	2nd E'
024	76	2nd Lbl	114	44	SUM	204	89	2nd π	294	76	2nd Lbl
025	14	D	115	04	4	205	95	=	295	35	1/X
026	43	RCL	116	43	RCL	206	94	+/-	296	43	RCL
027	00	0	117	04	4	207	22	INV	297	04	4
028	38	2nd sin	118	55	:	208	23	lnX	298	72	STO 2nd Ind
029	33	X ²	119	43	RCL	209	42	STO	299	31	31
030	42	STO	120	03	3	210	00	0	300	25	CLR
031	00	0	121	95	=	211	25	CLR	301	01	1
032	43	RCL	122	94	+/-	212	01	1	302	44	SUM
033	10	10	123	85	+	213	42	STO	303	31	31
034	32	X \geq t	124	43	RCL	214	02	2	304	25	CLR
035	11	A	125	01	1	215	25	CLR	305	02	2
036	76	2nd Lbl	126	95	=	216	00	0	306	44	SUM
037	11	A	127	48	2nd Exc	217	32	X \geq t	307	02	2
038	08	8	128	01	1	218	86	2nd St Flg	308	43	RCL
039	65	x	129	95	=	219	02	2	309	01	1
040	43	RCL	130	75	-	220	10	2nd E'	310	75	-
041	00	0	131	43	RCL	221	76	2nd Lbl	311	43	RCL
042	95	=	132	01	1	222	18	2nd C'	312	02	2
043	75	-	133	95	=	223	02	2	313	95	=
044	01	1	134	50	2nd X	224	42	STO	314	22	INV
045	06	6	135	22	INV	225	02	2	315	77	2nd X \geq t
046	95	=	136	77	2nd X \geq t	226	25	CLR	316	91	R/S
047	94	+/-	137	12	B	227	22	INV	317	10	2nd E'
048	42	STO	138	11	A	228	86	2nd St Flg	318	92	INV SBR
049	03	3	139	76	2nd Lbl	229	02	2	319	91	R/S
050	43	RCL	140	12	B	230	10	2nd E'	320	00	LRN
051	00	0	141	43	RCL	231	76	2nd Lbl			
052	65	x	142	01	1	232	10	2nd E'			
053	43	RCL	143	72	STO 2nd Ind	233	43	RCL	Load:		
054	01	1	144	05	05	234	02	2		α	- STO 00
055	65	x	145	87	2nd If Flg	235	65	x		1	- STO 01
056	04	4	146	01	1	236	09	9		0.5	- STO 15
057	08	8	147	15	E	237	00	0		β	- STO 09
058	95	=	148	76	2nd Lbl	238	55	:		0.000 000 1	- STO 10
059	94	+/-	149	16	2nd A'	239	43	RCL		6	- STO 05
060	44	SUM	150	01	1	240	01	1		11	- STO 30
061	03	3	151	44	SUM	241	95	=		21	- STO 31
062	43	RCL	152	05	5	242	42	STO			
063	01	1	153	43	RCL	243	03	3			
064	33	X ²	154	09	9	244	39	2nd cos			
065	65	x	155	42	STO	245	33	X ²			
066	01	1	156	00	0	246	65	x			
067	09	9	157	86	2nd St Flg	247	04	4			
068	02	2	158	01	1	248	65	x			
069	95	=	159	17	2nd B'	249	43	RCL			
070	44	SUM	160	76	2nd Lbl	250	00	0			
071	03	3	161	15	E	251	85	+			
072	43	RCL	162	89	2nd π	252	01	1			
073	00	0	163	33	X ²	253	95	=			
074	94	+/-	164	42	STO	254	42	STO			
075	42	STO	165	08	8	255	04	4			
076	04	4	166	43	RCL	256	43	RCL			
077	43	RCL	167	06	6	257	03	3			
078	00	0	168	23	lnX	258	38	2nd sin			
079	65	x	169	65	x	259	65	x			
080	08	8	170	43	RCL	260	43	RCL			
081	75	-	171	07	7	261	04	4			
082	01	1	172	23	lnX	262	95	=			
083	06	6	173	55	:	263	42	STO			
084	95	=	174	43	RCL	264	04	4			
085	94	+/-	175	08	8	265	87	2nd If Flg			
086	65	x	176	95	=	266	02	2			
087	43	RCL	177	42	STO	267	19	2nd D'			
088	01	1	178	08	8	268	61	GTO			

Program to calculate the order n of a normalized elliptic low-pass: STO 08, zeros and maxima of Tschebycheff rational function: STO 11-STO 20, STO 21-STO 29 respectively.

Advanced IT and Alvey

The first four definition studies for large-scale demonstrator projects under the Alvey programme for advanced information technology have now been started by ICL, GEC Electrical Projects, Racal Research and Marconi Avionics. A further six studies are to be commissioned, leading to the final selection of about five projects to be implemented over the five years of the programme.

GEC, working with the Artificial Intelligence Department of Edinburgh University and the National Engineering Laboratory, East Kilbride, are developing a 'Design to Product' system for a completely automated factory where design concepts are input at one end and the finished product, which includes maintenance data, will emerge from the other. The system will automatically provide all the detailed design work, process planning,

machining of parts and assembly all with a minimum of human intervention. The demonstrator will provide a skeleton system for the whole process.

An efficient service to the public in their contact with the complexities of the legislature system is the aim of ICL in partnership with the DHSS and Logica. This could be achieved by using knowledge-based decision systems and improved user-machine interfaces. Mobile information terminals could bring many new facilities to road users and business people on the move. Part of Racal's study is the development of terminals which will use all the other technologies developed through the Alvey programme to form the basis of multi-purpose data communications, processing and display console for mobile and portable use. Racal will be working with a consortium including SPRL, BL

Technology, the Human Science and Advanced Technology Research Group, Loughborough University and the Transport and Road Research Laboratory.

'Replacement of man underwater' for the inspection and maintenance of installations in gas and oil fields is the goal of the project proposed by Marconi Avionics in association with Offshore Engineering Ltd.

The Alvey programme follows the Alvey Committee Report recommending a national research programme into advanced information technology costing \$350M over five years. It aims to combine the strengths of industry, the academic sector, research organizations and the Government to work in four specific key technologies: very large scale integration, software engineering, user-machine interfaces and intelligent knowledge-based systems. The programme works in collaboration with ESPRIT, the European Strategic Programme for Research and Development in Information Technology.



Refurbishment of the complete vision system at Studio 4, BBC Television Centre, London, has been carried out by Link Electronics. The equipment includes six Link 125 colour cameras, a Grass Valley vision mixer, 13 colour monitors, 41 monochrome monitors and a complete package of distribution and interface systems as well as test equipment.

OU to study IT in education

Appropriately for a university that was founded on mass communication, the Open University has been commissioned by the EEC to study the future use of information technology in education and training. The outcome of the study will be recommendations, all financially valued, for action by the EEC to stimulate the appropriate use of IT-based educational

technology in the member states. Eight researchers, under the direction of Dr Peter Zorkoczy, will take six months to look at media, educational technology, computing, electronics and communications.

The team is anxious to contact individuals and organizations who are considering the use of such technologies in their training programmes. They are the EEC Project Office, Block T12, The Open University, Walton Hall, Milton Keynes MK7 6AA.

Secondary radar will oust primary

Marconi Radar have introduced a monopulse secondary surveillance radar system that can provide greater directional accuracy, and which is capable of operating the proposed Mode S, where each aircraft can be individually 'interrogated' to establish a data link. New technologies being introduced into s.s.r. systems, Marconi say, mean that they are set to replace primary radar as the main source of air traffic control data. In secondary surveillance radar all aircraft within a specific distance from the airfield, fitted with a transponder, receive digital coded signals transmitted from the ground station and automatically transmit back details of the identity and height of the aircraft.

The first element in the system is a new, patented, large vertical-aperture antenna, specifically designed for monopulse working which can produce three azimuth patterns at both 1030 and 1090MHz. This forms the means of considerably improved sidelobe suppression and direction finding, and also reduces the 'clutter' caused by ground reflections and false targets, such as buildings or aircraft on the ground.

The transmitter/receiver, known in this context as an interrogator/responder, is completely solid-state including the final output power stage of 500W to 2kW. The monopulse receivers have parallel outputs from balanced channels to allow very accu-

Optical memory

Another development in optical disc storage devices capable of holding vast amounts of memory has been announced in Japan by Hitachi. At the same time they have announced the development of an electronic filing system based on the optical discs. A 12in optical disc can store up to 1310Mbytes per side, the equivalent of 20000 A4 size pages. In addition images and illustrations can be included. The average access time is 250ms. Hitachi is making available an optical disc "library" which uses 16 discs with an average access time of 5s and another with twice the capacity, 32 discs, accessed within 6s. The discs are designed to work with Hitachi computers and work stations but are also available with GPIB interfaces for use with other computers.

The electronic document filing system,


Hitfile 60, consists of a disc controller, a high-resolution display unit, keyboard, scanner, printer and facsimile adaptor with one or more optical discs. At the maximum configuration this system can hold 8640Mbytes of data, or about 1.3 million A4 documents. Documents are stored as facsimile images of the document produced by a scanner. Each document may be entered into up to eight different files and then can be retrieved from any of these. A document retrieved on a display can be magnified or reduced in size by simple control from the keyboard or a 'mouse' and for high-speed magnification and reduction, Hitachi offer an image processor as an option. The 15in monochrome display produces a high resolution picture composed of 1728 by 368 dots, enabling a user to read newspaper type characters with ease. Different models of document scanner and output printer depending on the degree of speed and resolution required.

rate direction finding on single inputs.

The decoding equipment includes special logic to ensure the retention of wanted data in poor or ambiguous signal conditions. A high-speed data bus is employed with bit-slice processing. Outputs to other circuits in the unit are used to form plotting data expressing the range, azimuth, identity and altitude of all s.s.r. targets within the radar cover. All formats for digital outputs are programmable and therefore may be reconfigured to take in

any new standard.

Although Marconi admit that such equipment exists elsewhere and that there is an American rival, they feel that they have achieved the same objectives in a very efficient way with a system that is capable of many expansions and extensions to offer an air traffic control data system to last well into the 21st century. Marconi say they expect to capture a good proportion of the potential market of 1000 systems worldwide.

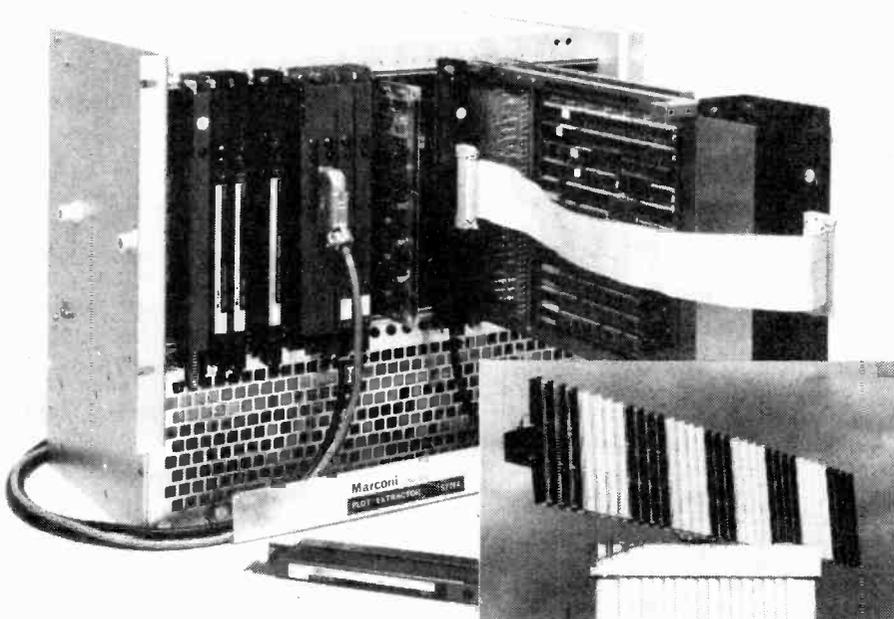

Decoding and plot extraction modules for the Marconi Messenger secondary surveillance radar use many processors interconnected by a high speed data bus. (Inset) The Large Vertical Aperture antenna used with the system.

Computer for railway signals . . .

A trial installation of a new computer system capable of automatically setting signalled routes for trains has been commissioned at the new Three Bridges signal box controlling the London-to-Brighton main line. The Automatic Route Setting system is superimposed on the signalling safety interlocking system and covers about 13km. It can cope automatically with substantial deviations from the timetable without the signal operator's intervention, though it may be manually over-ridden. The system uses two microcomputers. One is linked to the signalling train identifier and to the regional master timetable system; the other takes into account any deviations and routes the trains so as to minimize any aggregate delay. During development of the system at BR's R & D Division at Derby, considerable use was made of a large simulation package, or in everyday terms, a train set. This enabled engineers to produce a software package capable of general application throughout BR and assisted them in exploring the interactions and interfaces between the signalling system, the signal operators and the computer.

. . . and traffic signals

A remote monitoring and control system for traffic lights has been developed by Stonefield Electronics Ltd and Leicester County Council. The system, known as REMAC, can automatically call up a central control room if a fault develops at a set of signals. It also enables the control room operator to check the correct working of the signal lamps and vehicle detectors and to verify the timings of the signal sequences. It works equally well for light-controlled pedestrian crossings. Using normal telephone lines, through an integral modem, REMAC only calls if there is a fault, there is no need to keep the lines open. Provision is made for the system to contact a maintenance contractor or to dial more than one centre or a standby central co-ordinator. The system can work in conjunction with microprocessor-based traffic controllers.

Stonefield produce a self-contained computer to work the system. With a colour v.d.u. and a disc memory that stores the details of each junction so that if a call comes in the junction may be automatically displayed with symbols for lights, road markings, traffic sensors etc. There is also space to display the reported fault. The computer can also hold traffic flow information so that the gravity of a fault may be assessed. The first production model of REMAC has been installed at Slough, Berks with the central terminal at the Department of Transport South East Regional Office.

Micro User Show

The BBC Microcomputer continues to consolidate its reputation as a machine for the experimenter, and among the computer games at last December's Micro User Show in London some interesting new add-ons were visible.

A 6809-based second processor board from Cambridge Microprocessor Systems provides the basis of a versatile development system for industrial applications. The card, which can be fitted inside the computer or mounted in a rack externally, carries two 28-pin eeprom sockets and 64K of ram with optional battery back-up. Software is available to allow standard FLEX discs to run on the BBC, giving access to a wide range of high-level languages including Pascal, Fortran, C, PL9, Forth and BCPL. Basic price is £249 and the system is available also as a single-board controller. C.M.S., 11 St Margaret's Road, Girton, Cambridge CB3 0LT, tel. 0223-276791.


Second processors were being shown by other exhibitors, including Acorn themselves (Z80 and 6502) with a 16032 promised, and Watford Electronics (Z80A). The Watford unit has 16K of rom space and 64K of ram, with room internally for a further 64K. Expansion options include a hard disc interface, additional serial channels, an IEEE488 interface, a real-time clock and a prototyping board. The operating system is CP/M 2.2 and the price £299. Watford Electronics, Cardiff Road, Watford, Herts, tel. 0923-40588.

Acorn also showed their IEEE488 instrument interface (described elsewhere in this issue, and featured on our cover); the unit, styled in a case to match the computer, costs £282.60.

One drawback of the standard BBC Micro is that high-resolution graphics are incompatible with long user programs, since in some display modes the operating system sequesters up to 20K of ram to store the screen display. A board from Cambridge Microcomputer Consultants, the Aries B20, provides a substitute for this lost memory. Paging is carried out automatically, allowing programs as long as 28K to run even in the highest resolution modes. The board, which costs £86.91, fits inside the computer case; and, for compatibility with software which makes direct accesses to the screen, it can be enabled or disabled from the keyboard.

The same company offered at the show yet another IEEE488 interface; its price, £195, includes software on disc or cassette. C.M.C. Ltd, Freepost, Cambridge CB1 1BR, tel. 0223-210677.

From SJ Research comes the Control Rom, a useful piece of firmware which its designers believe will do for control applications what high-level languages have done for computing in general. Plugged into one of the BBC Micro's paged rom sockets, it enables data to be written to or read from specific bits on the i/o ports as easily as loading or saving to disc or tape. Its commands are available to any language which can support filing systems. The rom can handle up to 32 channels at once, giving direct access to the computer's memory space, and it has two

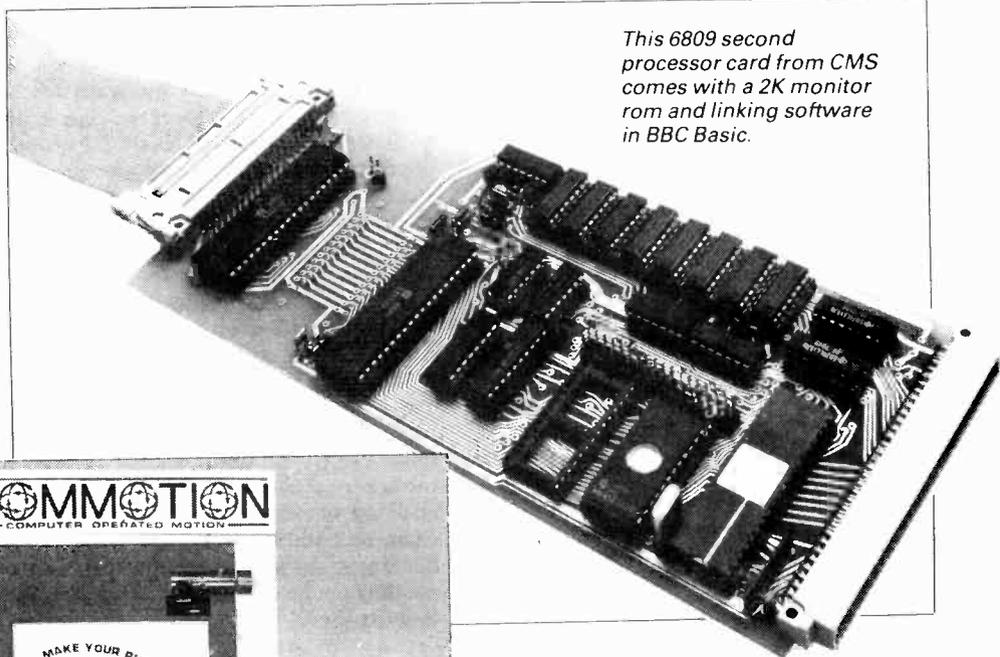

This 6809 second processor card from CMS comes with a 2K monitor rom and linking software in BBC Basic.



special channels suitable for communication with Control Universal's 8-bit and 12-bit analogue cards. As a bonus, the rom has a 'terminal' mode allowing communications via the RS423 port. The price is £39, and a version will be available for the Acorn Electron. S. J. Research, 108 Mill Road, Cambridge CB1 2BD, tel. 0223-69927.

Commotion Ltd, who were showing the Control Rom, also had an interesting miniature servo interface – the Beasty. Designed for uses in micro-robotics, this module makes it possible to control up to four servo mechanisms, including standard model aircraft servos, through software or directly from the computer keyboard. The Beasty is accessed via a single pin of the computer's user port. It costs £43.45 from Commotion, 241 Green Street, Enfield, Middlesex EN3 7SJ, tel. 01-804 1378.

Among many other new roms for the BBC Micro was a very flexible machine code data base program, Beebase-1, which enables the creation of files of up to 20,000 characters with potentially unlimited storage capacity on tape or disc. Up to 25 data fields are possible in each record, with a maximum of 250 characters per field. Beebase-1 is supplied with a Basic printer routine on cassette which could easily be adapted to print data in a variety of unconventional formats – including, for example, tables. GCC (Cambridge), 66 High Street, Sawston, Cambridge CB2 4BG, tel. 0223-835330.

For plotting graphs and charts, a graphics dump rom from D. A. Computers includes fast machine-code routines for several popular dot-matrix printers, including models by Epson, Seiksha and NEC. The rom can be called from

◀ For the technocat who has everything: a servo control module which plugs in to the BBC Microcomputer.

software or from the keyboard and it offers a choice of print densities and magnifications. The screen can be printed complete or in part, in four or eight shades of grey or in plain black-and-white. The rom costs £15.66 from D. A. Computers, 104 London Road, Leicester, tel. 0533-549407.

Beebug Publications have added to their range of software a Basic programmer's aid in rom, to complement their Exmon machine code monitor. The Toolkit includes a powerful screen editor, an error trap, a 'bad program' recovery routine and many other utilities for manipulating Basic programmes. Toolkit and Exmon cost £23.48 each, or to Beebug subscribers £14.35. Beebugsoft, P.O. Box 109, High Wycombe, Buckinghamshire HP11 2TD.

Prices quoted do not include v.a.t. or delivery.

New frequencies for land mobiles

A technical specification for land mobile radio services operating in the frequency range 174 to 225MHz has been published by the Radio Regulatory Division of the DTI. The specification lays down the parameters and related methods of measurement for fm equipment including digital signalling techniques.

The method of measurement described in the specification have been aligned with CEPT recommendations to enable British manufacturers to compete in European markets.

This frequency band was released from 405-line tv service, due to close down at the end of this year. Among the user groups to be assigned channels in the new band will be the power industries who will be displaced from the 105 to 108MHz band when this is re-allocated to fm broadcasting services.

Cellular radio — first details

Plans for the implementation of a cellular radio system have been unveiled by Telecom Securicor Cellular Radio, the joint venture between BT and Securicor who were offered one of the two licences to start a cellular service. The switching system to be used is TACS (Total Access Communications System), which is a UK development of AMPS, the system which has had trial operation in Chicago. The heart of the system is a non-blocking, digital mobile switching exchange (EMX) that controls signalling and voice communication within the cell system as well as connecting with the public switched network. Each cell site contains a base site controller and multichannel transmit/receive equipment. Each unit may be expanded to handle up to 64 channels on a single antenna. EMX keeps track of caller and switches between base stations as the caller moves between cells, 'handing-off' the call to each new cell and switching to a free channel in that area. This process is unnoticed by the user and the channel previously occupied is free for re-use. There is to be a multi-layered hierarchy of areas; the base station comes within a location area, which is connected to an EMX, joined to others through a service network with an overall systems area. All this is

invisible to the user who needs only to dial a user's number to be connected anywhere in the country.

TACS includes a dedicated control channel, has allocated channels without hunting for a vacant channel; it uses 6kHz supervisory audio tones and offers good recovery and registration of signals. Data may be transmitted on the SKb/s 'Manchester' signalling system which offers five repetitions of each block of data.

Capacity of the system may be expanded by reducing the size of each cell in heavily populated areas. The minimum size of a cell is about 1km radius around the transmitter. The system has 25kHz bandwidth and as there is no need for guard bands between adjacent channels broadband transmission is possible to reduce interference. Further noise reduction is achieved by using expansion and compression. In theory there could be as many users as now use conventional telephones, with no reduction in sound quality.

User equipment is not provided by TSCR but many manufacturers are said to be planning car-based and portable sets. These are likely to include many facilities associated with office telephones such as an internal memory for frequently dialled numbers, automatic re-call of engaged

numbers, call transfer, conference calls and so on. Initially, a car-based set could cost as much as £2,500, but mass production and the use of very similar sets in the USA, could bring the price down considerably. Data facilities with the use of a modem and a portable computer could mean connection with electronic mailboxes, databases and word processors.

There is no attempt at co-operation between TSCR and their rival licensee, Racal-Milgo, and two independent parallel systems are to be developed. The only way that a caller on one system will be able to contact another on the rival will be through the public switched network.

TSCR expect to have an operational system in London by the beginning of 1985 and to cover 90% of the UK population by 1989, or sooner.

Patented brainware

A solution to the problem of copyright and computer programs is suggested in a Government Green Paper. It proposes that in a sweeping reconstruction of the patent laws such works are 'intellectual property' and like other ideas or inventions they should be covered by patents. Because of current delays in the patenting system they also propose streamlining the Patent Office by making it a separate statutory body, independent of the Department of Trade and Industry, and breaking the monopoly of the Patent Agents.


One way of speeding up the system, the paper suggests, is to introduce a 'petty' patent which would have a ten-year life and provide the owner of an idea with a simpler form of protection, without the long and costly procedures of a full patent. Other forms of intellectual property, such as designs, would also be transferred from copyright to patent protection.

In the Green Paper, the academic world is castigated for freely exchanging information, nationally and internationally, without any attention to the possible commercial application of their ideas. On the other hand school pupils are encouraged to copy software without any thought to copyright. All fields, including small businesses, should be encouraged to look to the protection and commercial exploitation of their intellectual property. Employees who develop ideas should be given the right to take over their inventions if employers do not intend to exploit them.

Another new departure from existing procedures would be the right to challenge the validity of a patent even after it has been granted.

The paper proposes an Intellectual Property and Innovation Bill to bring together all these ideas.

More News appears on page 71.

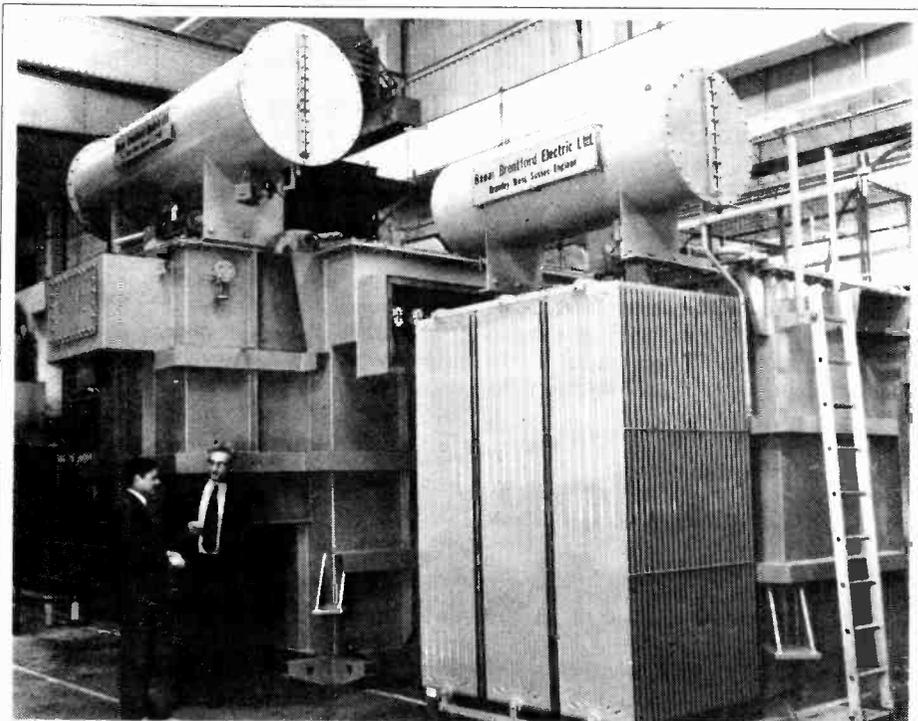


The power needed to accelerate particle beams in the Large Electron-Positron (LEP) storage ring, at CERN, Geneva, is provided by r.f. cavities fed by klystron tubes. There will be 96 1MW klystrons, with six feeding each r.f. station in the LEP to provide up to 86GeV per beam. The prototype transformer and rectification equipment, supplied by Bonat Brentford of Crawley, incorporates an input transformer and two high tension transformer rectifiers to provide the d.c. supply to the klystrons. The h.t. transformers step up the voltage to 100kV and the rectified, thyristor controlled supply can provide up to 36A d.c. This is sufficient to drive only two of the 1MW klystrons for experimental work.

Improving colour television decoding

This third installment of David Read's decoder article continues the January discussion of a PAL modifier with adaptive notch and follows with colour tube problems.

Some of the colour prints in this article are referred to in previous instalments. Colour print 1 relates to the first part, in December, page 76 and prints 2-5 to the January article. Due to last-minute alteration of figure numbering, figure numbers in the last (January) paragraph did not match properly with the illustrations. This paragraph, repeated with correct numbering, precedes the concluding paragraphs of part 2, followed below by part 3 on tube problems.

Traces in Fig. 24 (January) show the inverting and non-inverting inputs; the output summing point is shown in the bottom trace of Fig. 25. The envelope timing is matched, i.e. the two traces of Fig. 24 are delay-adjusted to obtain the 64µs spacing, and the colour subcarrier phase and amplitude values are also balanced to achieve cancellation. In the top two traces of Fig. 25 the carrier frequency has been shifted slightly by removing the 25Hz term and changing ¼ to a ½ in the subcarrier expression, the result being that the subcarrier is now stationary with respect to line timing. You can now see that phase (group delay) in the gaussian chroma bandpass filter and the cheap DL60 chroma delay line, below, reduce the ability to obtain cancellation at the vertical colour transition where the sidebands gen-

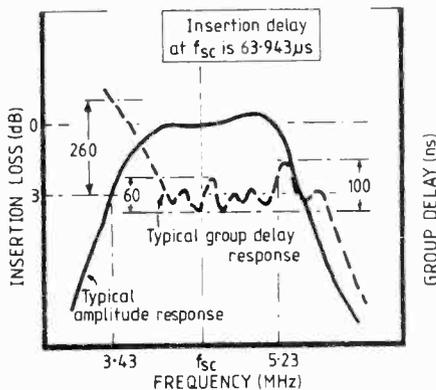

erated are large. Residual error is shown in the bottom trace, Y-out, Fig. 25. Some is also due to the changed rise times of the subtracting chroma transitions due to the reduced bandwidth of the chrominance signal. Comparison of the two traces in Fig. 24 shows this rise-time difference. Colour print 5 shows the effect of the reduced rise time on the chroma-only display.

For the horizontal colour bars signal, however, where the combing action across the adjacent lines could make cancellation worse, the notch has to be switched back

by D. C. A. Read
B.Sc. (Eng), M.I.E.E.

into circuit. (A mixed vertical and horizontal colour bars signal could be used, as in colour print 6, but the small areas detail would not show up in the colour printing when showing the whole screen. This test pattern is useful for showing defects in adaption switching, where vertical and horizontal transitions occur.) With the sort of notch indicated in Fig. 17 (a) (January) the picture is visibly softened, but with an electronically switched notch, as in the present application, the notch depth and

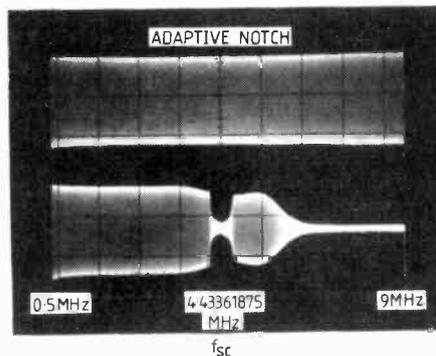


Fig. 26. Line-rate sweep signal fed to the modifier comb circuit. (Tr_1 and Tr_2 bases). Lower trace shows adaptive notch 'snapping in' as explained in the text.

width can be set according to the analysis. Fig. 26 shows the effect with the notch switched in and Fig. 27 with the notch out. The extra marker on Fig. 27 indicates the

subcarrier frequency, the other markers are in 1MHz steps.

Comb decoding techniques reduce the moving dots on coloured edges, i.e. the cross-luminance, but they also increase the luminance bandwidth so that luminance detail can be displayed up to 5.5MHz. The last grating on test card F is at 5.25MHz and if the main criterion is to have a better luminance resolution then it must be considered whether the display tube is capable of displaying the higher frequencies and, if not, whether application of high frequency luminance to the tube could result in a worse picture. Moiré beat patterns might occur due to the structure of the tube and the luminance highband detail. The high frequencies may not be usefully displayed,

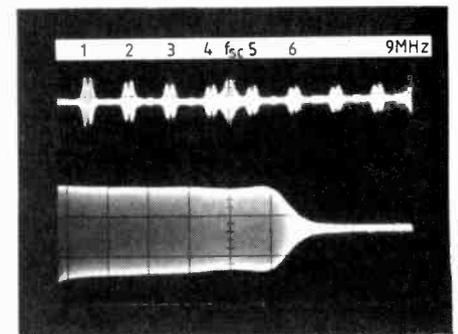


Fig. 27. Trace of the output of the modifier comb circuit with the adaptive notch non-operative, (gate of f.e.t. is at OV and is thus switched off).

and the beat pattern could degrade the picture. Slow panning of the camera could also result in high frequency components producing additional moving beats and twitter.







Colour tube limitations

Part 3 – Inability of the modern colour tube to display full bandwidth luminance

New colour tubes, such as the Philips 30AX self-aligning 110% in-line gun, have fully interchangeable picture tube and deflection yokes that are truly self-aligning and self-converging. When these tubes are replaced it is merely a matter of the deflection unit being pushed against the tube neck onto registering lugs. In such in-line tube arrangements the corrections nor-

mally achieved by external magnet sets are carried out in the neck of the tube by two, four and six-pole fields, produced by thin magnetic wire rings within the electron gun and which correct all that was previously carried out externally on the tube neck.

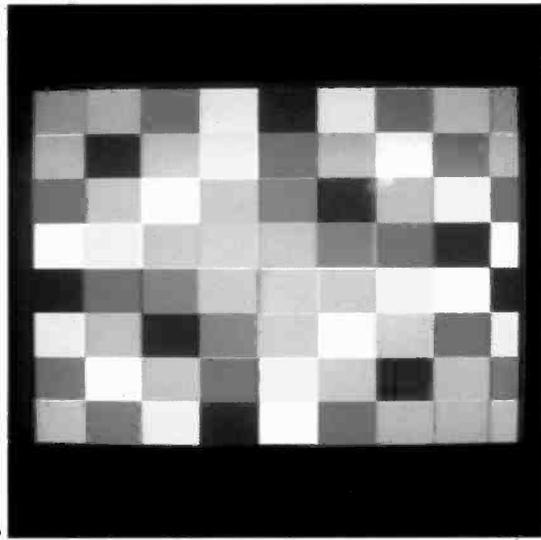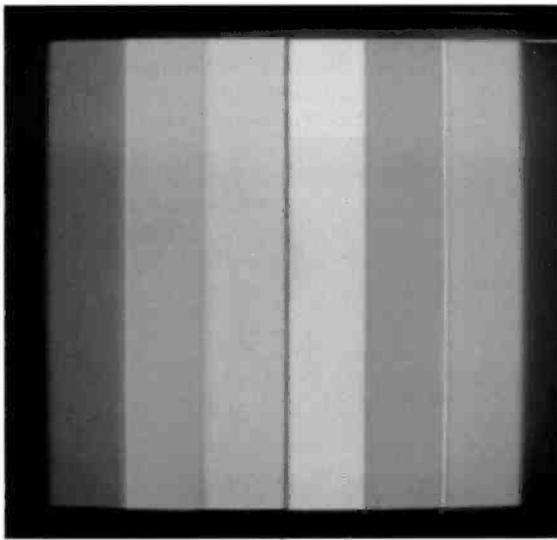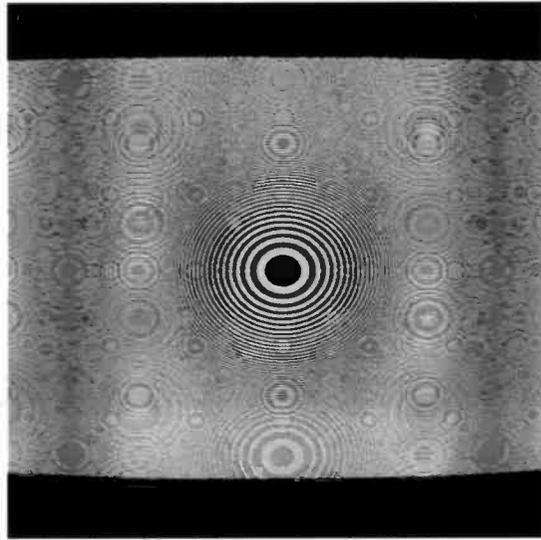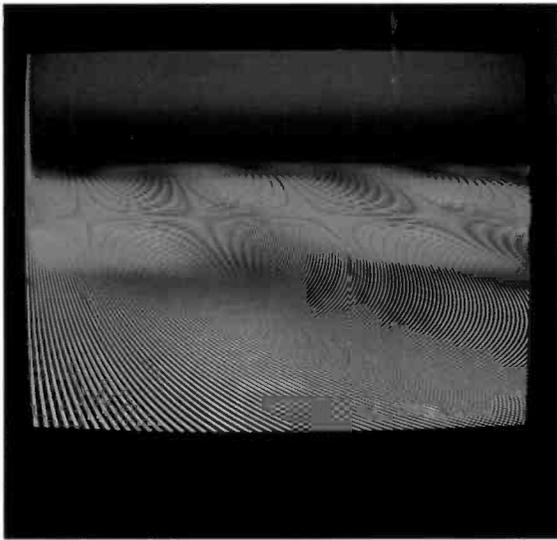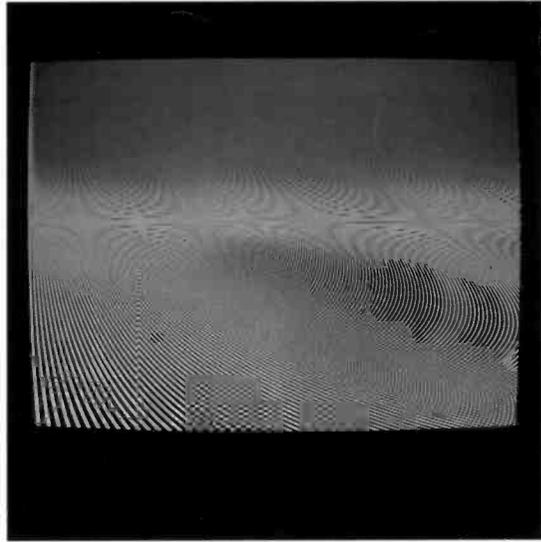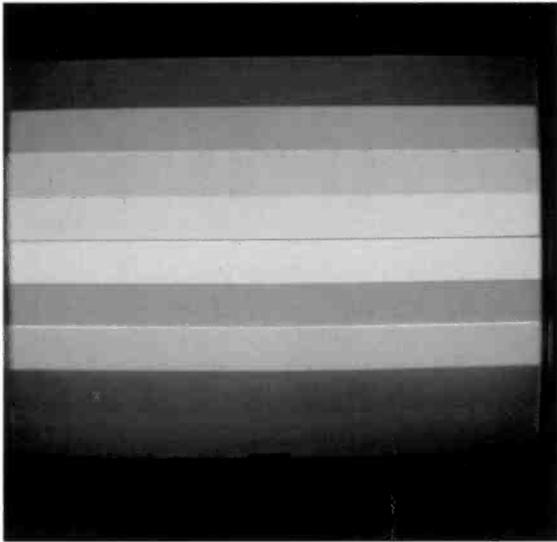
Other advantages are that the phosphor has an improved pigmentation providing:




1. Three-line chroma decoding, no luminance. Colour print forms Fig.12(b), referred to in Fig.12 caption, part one, December 1983 issue, page 78.
 2. Line sweep skew with PAL modifier in the luminance signal, as per page 53 January 1984 issue. (Two-line chroma decoding, one narrow line delay.)
 3. Result of comb filtering across three lines with wideband 64µs delays, as in

Fig.12(a) and 12(c) block diagram. See page 78 December 1983 issue.
 4. Non-linearity is evident when the signal overloads in processing stages, producing indecipherable patterning due to harmonic generation.
 5. Effect of reduced rise-time due to Gaussian bandpass filter and narrow chroma delay line, on chroma-only display with two-line chroma decoding. See Fig.24

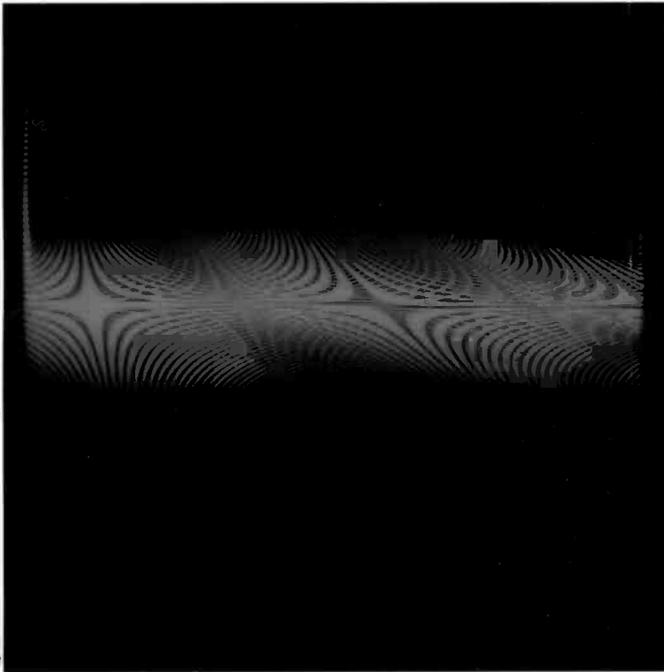
page 56 January 1984 issue. (No luminance.)
 6. Displayed signal is a mix of vertical and horizontal colour bars. The decoding effects are not clear as detail would not show up in the colour printing. This test pattern is useful for showing up defects in adaptive switching where vertical and horizontal transitions occur.



7

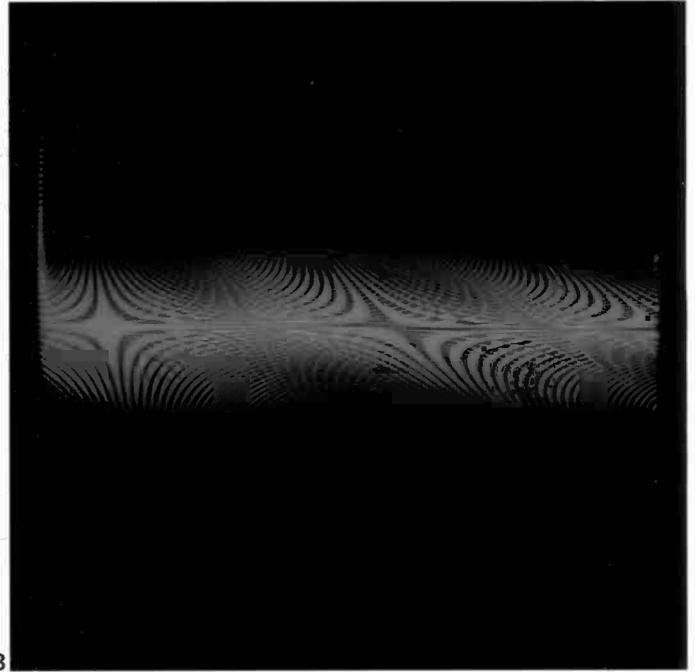

8

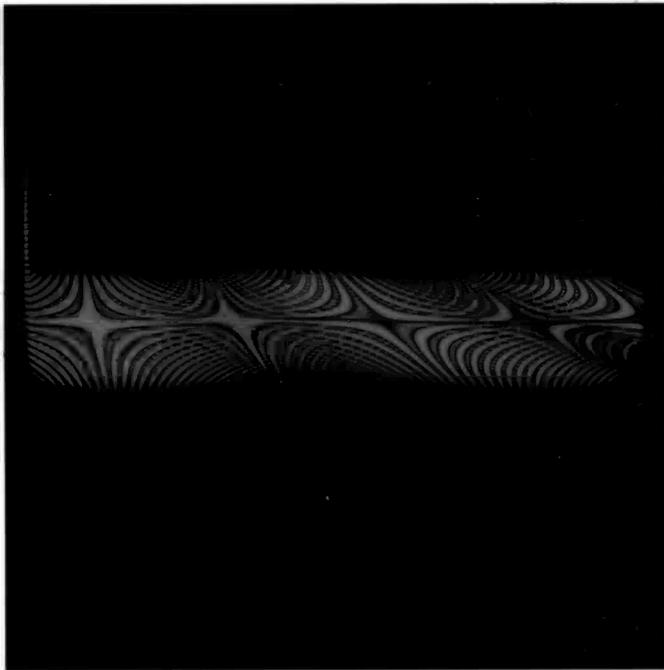

9

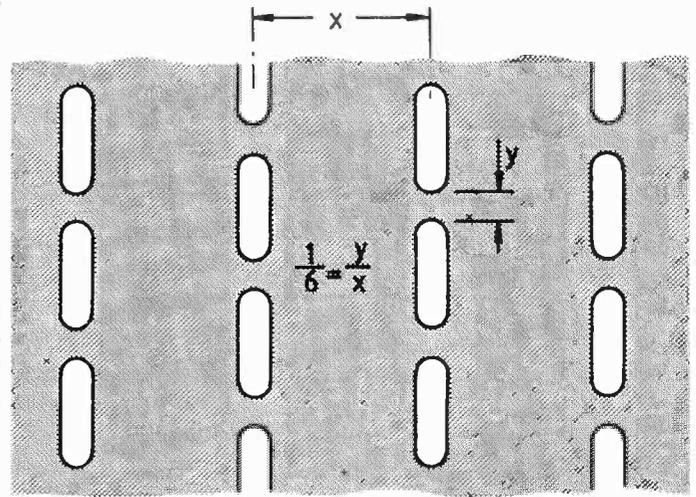


Fig. 28.


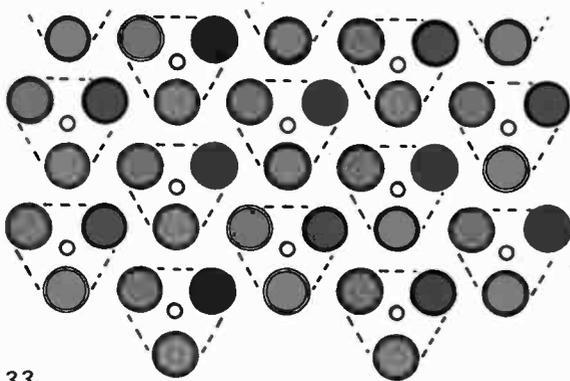



Fig. 33.

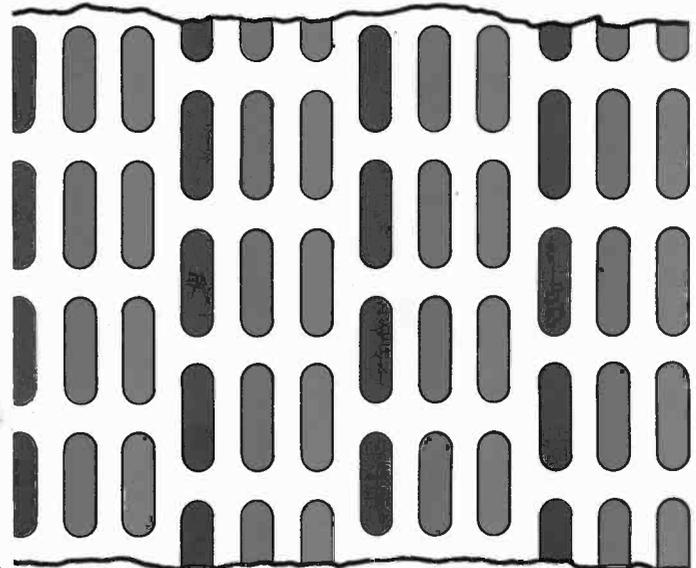

7. Line sweep skew with one-line chroma decoding (no luminance).
8. Line sweep skew with two-line chroma decoding (no luminance).

9. Line sweep skew with three-line chroma decoding (no luminance, two wideband delay lines used.) See also Fig. 12, page 78, December 1983 issue.

Fig. 28. Typical slot shadow-mask tube with its phosphor faceplate.
Fig. 33. Triad tube face structure, as used on earlier and some current high resolution c.r.t.s. Centre circle is shadow mask hole.

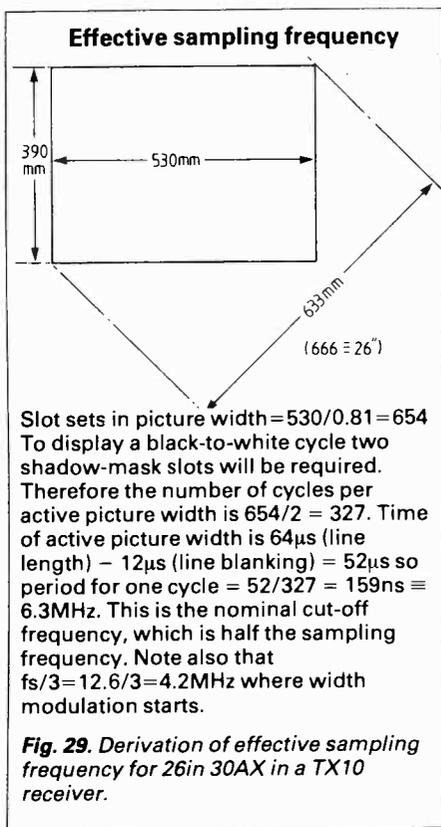

greater light output and the tube guns have quick-heating cathodes, giving a picture 5-10 seconds after switch-on, also the spot defocusing with high beam current and deflection defocusing in the corners is very much reduced by what the Mullard manufacturer describes as a quadrupole lens. The tube doesn't require adjustment for convergence, colour purity or raster orientation, and together with its reduced deflection energy, improved raster shape, general sharpening up of the spot, and soft flash on the e.h.t., it seems a very attractive component.

Sampling properties of the tube face

Figure 28 shows a typical shadow-mask tube with its phosphor faceplate. The upper section illustrates how the slots in the metal shadow mask are stood back from the glass screen to ensure that the electron beams from three guns in the tube neck only reach the appropriate phosphor stripes. The spacing of these stripes determines the subjective performance of the tube with high frequency luminance.

Considering the green gun, which produces the images that the eye is most sensitive to as far as revolving detail is concerned, the video signal is effectively sampled by the spacing of the green vertical stripes illuminated by the gun as it scans across the screen. The Nyquist theorem states that the sampling frequency must be at least twice that of the highest signal frequency. Any higher frequencies would reappear in a lower frequency spectrum: this is called an aliasing component. The pitch of the stripes can be 0.83 to 0.795mm, but for calculation an average figure of 0.81mm spacing is used.

As an example of the effect of stripe spacing, consider the dimensions of a 26in 30AX tube in a Ferguson TX10 receiver. The measured screen diagonal is 633mm

and as 660mm is the metric equivalent of 26in, this must therefore be presumed to be an interpreted or a projected dimension of an ideal display tube that is considered square. Progressing from this slight deceit, more significant for displaying pictures is the usable width of the tube, which is 530mm (17in). Dividing 530mm by the 0.81mm stripe spacing gives a total of 654 RGB stripe sets in the picture width. From this, Fig. 29 derives an equivalent half sampling frequency of 6.3MHz.

The structure of the stripes is clearly visible in Fig. 30 on the left-hand side of the screen. The tube, as used on a JVC 6in 12-volt portable receiver, is typical of the coarse slot type. In the displayed line sweep, the frequency of the video signal increases to the right of the screen, and you can see that at one-third of the frequency the spacing is beginning to be width-modulated, and at half the sampling frequency it is not displaying anything useful at all. Therefore accurate representation of horizontal luminance detail is prevented in the 26in 30AX tube because luminance bandwidth is reduced to

On page 79 of the December issue David Read suggested a novel method of decoding. Perfect still picture decoding with reduced impairment with movement could be achieved by reducing subcarrier frequency by 6.25Hz. Both U and V signals are in antiphase over one picture period, as the lower part of Fig 14 showed; unfortunately the caption incorrectly referred to raising the subcarrier. The upper part, which should have shown 90° of f_{sc} as 56.39ns, not ms, related to the decoding arrangement of Fig.13(b).

Apologies for numerical slips in the captions; in Fig. 9 which gave 6 instead of $64\mu\text{s}$, Fig. 10 which gave 54 and not 56ns, and in Fig. 13 (b) the subcarrier is of course 4.433 . . . not 4.422 . . . MHz.

4.2MHz, as derived in Fig. 29. Applying text card F directly from a slide scanner and with no PAL coding or decoding, luminance resolution was of display value up to 4.5MHz. At 5.25MHz it was clear that some vertical lines were displayed but their spacing was modulated. With a line sweep test signal the Moiré patterning was pronounced. So in spite of the improved bandwidth from the comb, the final video


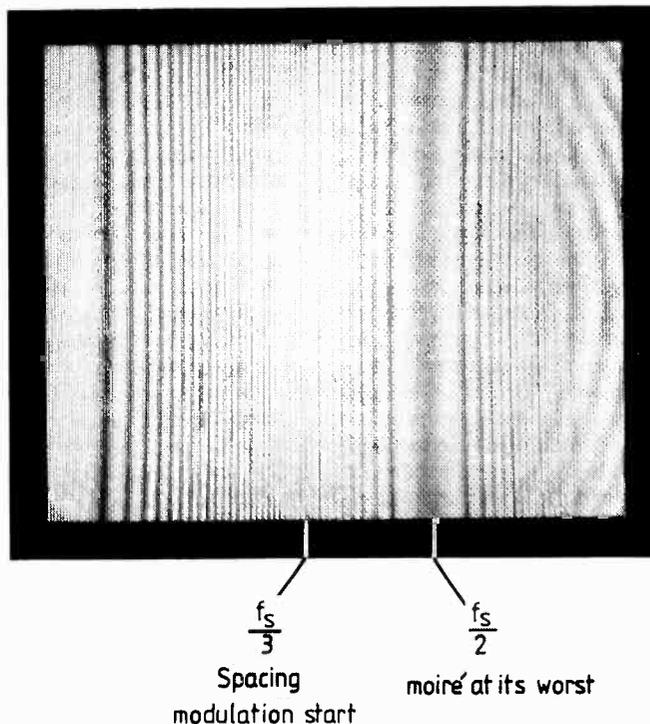


Fig. 30. Photograph of video line sweep applied to slotted shadow-mask tube shows patterns caused by slot sampling.

Fig. 31. Vertical sweep on the slot tube.

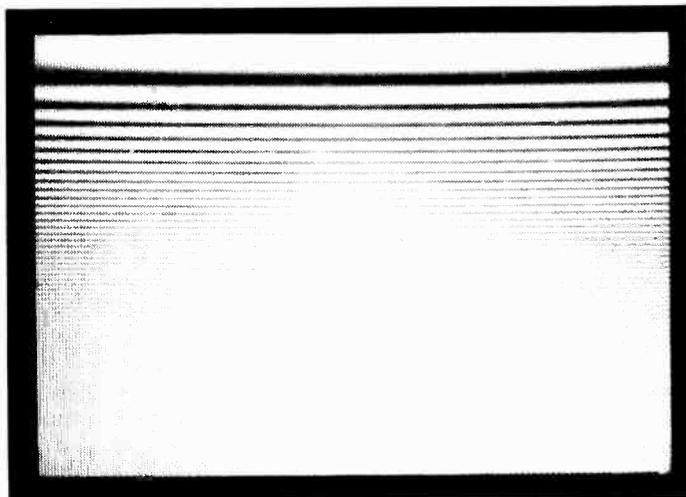

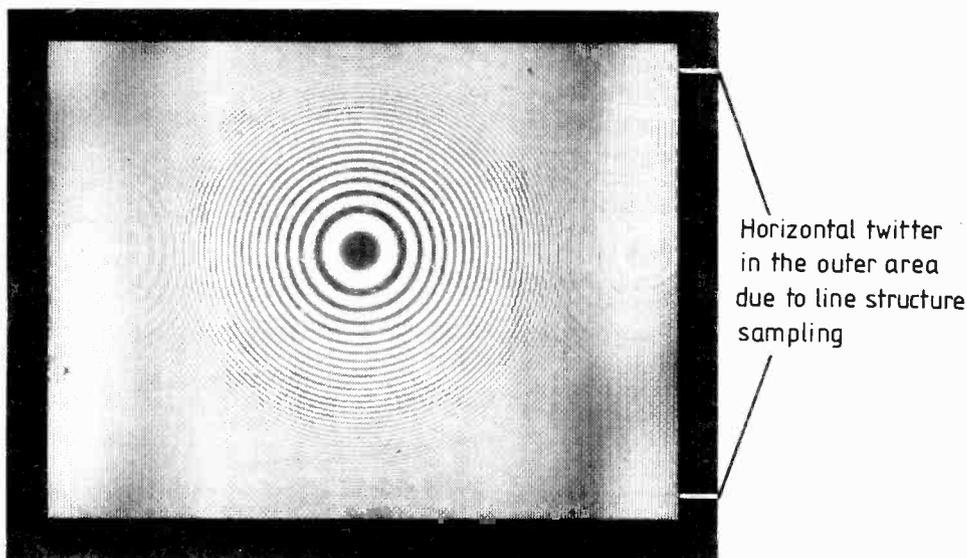


Fig. 32. Circular zone plate on the slot tube.

drive to the tubes was allowed to roll-off, typically 1 to 2dB down at 4.5MHz, and 3 to 4dB at 5.5MHz.

Observing Fig. 28, it seems possible that there would be a display problem due to the horizontal bridges supporting the structure of the shadow mask. For a 26in tube the horizontal spacing between the vertical stripes is 0.759mm. The vertical spacing is 0.810mm, so there could be difficulty in sampling on a vertical sweep. In Fig. 31 the Moiré patterning is not apparent, but there is a significant interference in the 625-line sampling structure beating with the vertically increasing frequency, i.e. the number of cycles per increment of picture height beating with the 625 line raster. This produces a very prominent horizontal 'twitter'. The evidence therefore shows that the problem due to the line structure interfering with vertical video detail is far greater than that of the shadow mask. Looking closely at the picture on Fig. 31, the only effect of the shadow mask structure is that some lines appear to be straight and others appear as a row of white dots. At normal viewing distance this is not apparent and the horizontal twitter is the dominating effect.

The vertical stripes have a different effect on diagonal luminance information as might be expected, shown in Fig. 32, along a diagonal luminance line the vertical stripes generate a castellation of 'knotted rope' effect. Radially (from the centre) the zone-plate test pattern represents increasing spatial frequency. The fundamental television system gives a square display of detail, so that fine luminance information will be in the corners, although the slot shadow-mask structure tends to prevent this being displayed. In the horizontal direction width modulation is clearly visible before the Moiré patterning builds up.

Vertically, there seems to be more resolution available. This is because the bridges supporting the shadow mask are small in area compared to the horizontal spacing between individual slots. This spacing is typically 1/3 of the vertical slot spacing, as shown on Fig. 28. On the new higher resolution tubes, which use 0.6mm spacing between the vertical slots,

the horizontal support distance is only 0.1mm. For the more common 22in colour tube, the spacing between the vertical slots measured with a travelling microscope, is about 0.8mm. Usable screen width is 444mm and from these figures the sampling frequency is calculated to be approximately 10.6MHz. Maximum display frequency is now limited to 5.3MHz but as the Moiré patterning clearly starts at a lower frequency, the 26in tube with similar slot spacing is evidently the minimum tube size for which it is worth trying to improve the luminance resolution. On a smaller tube, improved luminance resolution would only make this Moiré patterning more visible without fine detail being effectively displayed.

When viewing closely these types of slot tubes, the structure of the shadow mask is certainly discernable, as seen on all three photographs, Figs. 30, 31 and 32.

Colour tube using triad hole spacing

In most high resolution tubes using the triad spacing and the dot structure is not particularly discernable. They also use lower spacing, a typical figure being 0.68mm compared with 0.83mm for some of the slot tubes. The equivalent half sampling frequency for 0.68mm is 7.4MHz (22in tube). Fig. 33 shows a triad phosphor screen where the interaction between the shadow mask structure and the video information is less noticeable. Also, low frequency Moiré patterning occurs at a later point as a result of the higher half sampling frequency. With the triad structure, the step effect on luminance diagonals is again not apparent. Viewing both a slot tube and a triad tube side-by-side the convergence drift on the triad tube causes an effective reduction of resolution, and on balance the slot tube is more stable. To take advantage of the increasing display resolution from higher luminance bandwidth it is certainly necessary to use either a 26-in slot tube or the triad structure.

With microprocessors in the home and the greater uses of electronic graphics there are now available higher resolution (slot spacing 0.4 to 0.6mm) RGB monitors capable of displaying up to 80 characters per line; but although greater detail can be displayed their screen sizes seem to be

limited to 20in at the moment. The electronics driving the new tubes are also much improved. Supply rail regulation on the Ferguson TX10 receiver for example is excellent, with a switched-mode power supply stabilizing all rails; with the e.h.t. supply separate from the line scanning, an extremely stable picture is obtained even in the presents of widely varying picture level. Overall, this enables the receiver to be set up with no overscan, so that the transmitted picture can be visible to the full width of the screen (as paid for in the licence fee).

If the stability is not good, the 'cover-up' method is to deliberately overscan the picture. This can have some advantage, in that a small amount of overscan causes the sampling frequency to be effectively increased e.g. by about 0.3MHz for 5% overscan. Most sets sold in the shops have 7-10% overscan. So, if a 22 or 26in set appears to be extremely stable on picture size with brightness changes, it is certainly worth reducing any excessive overscan.

Competition news

Twelve entries have been selected for the finals of our competition, which are to take place on January 30th. There are six prizes to be won and the winners will receive their awards from Princess Anne. The list of finalists is:

- David Battison of Cambridge, whose Mia-phone provides a speak-back facility for blind disabled typists. With the help of this device, the young user for whom it was designed is now able to type and prepare non-braille correspondence.
- Chris Batchelor of Stockport, designer of the Speakeasy. About the same size as a portable radio, this incorporates a keyboard and an allophone-type speech synthesizer.
- Michael Bolton and Alastair Taylor of Aberdeen: their entry is a computer interface using a pneumatic suck-puff transducer.
- T. G. Clarkson of London SE13, whose eye-controlled communicator allows a severely disabled person to select data presented on a television screen, using eye-movements to direct a cursor.
- Ian Dilworth and David Boley of the University of Essex, who have entered a v.h.f. wireless alarm system for use in hospitals or old people's flats.
- Tony Heyes of Nottingham University, whose entry is a microprocessor-based sonar aid for the blind.
- S. Ishiguro of Guildford, whose Touchvision enables the blind reader to follow ordinary printed text.
- William McCarthy, who lives in Edinburgh. His entry is an audible electronic depth gauge for the visually handicapped.
- Ian Mitchell of Hull, designer of another speech device, the TAB or Talking Box, produced as a communication aid for a group of children with speech difficulties.
- Henry Myatt of Harrow, who has designed a braille printer. This reproduces ASCII text from a microcomputer as braille characters on thin card.
- Phil Pickersgill and N. J. Stewart, who lives in Wokingham: their entry is the Frenchay speech-slowning aid, a device to help stammerers control and so improve their delivery.
- J. W. Smith of Haverhill, Suffolk, whose infra-red remote control device allows a user to switch up to 30 electrical appliances.


Inductance measurement

Simple practical method, hard to find in the textbooks

The inspiration for writing this article arose recently when I found myself in the radio shack looking for a coil of specific inductance. I had gone to a good deal of trouble to calculate the value of inductance required for this particular function and was now faced with the daunting job of going through my box of inductors, trying various coils until one worked satisfactorily. After ten minutes of trial and error and getting nowhere I came to the conclusion that there must be an easier way.

I began thinking of ideas for measuring the values of pre-wound inductances using basic test equipment which most enthusiasts have available in their radio shack. The method of measurement I eventually decided on is an application of two mathematical rules, the "cosine rule" and the "sine rule".

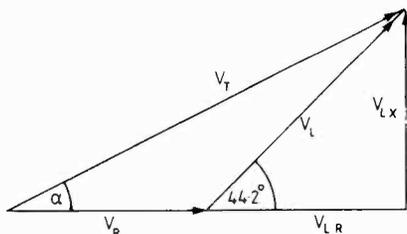Looking at the phasor diagram of Fig. 1, if the frequency applied to the circuit shown is changed, then X_L will change in direct proportion thus the phase angle α will also change.




- V_T applied voltage
- V_R voltage developed across R
- V_{LR} voltage developed across the resistive component of the inductor
- V_L voltage developed across the inductor
- V_{LX} voltage developed across the reactive component of the inductor

For the purpose of inductance measurement, this phenomenon can be ignored as it is allowed for within the calculations. This can be verified by measuring the voltages at a number of different frequencies and repeating the calculations. As will be shown, once this phase angle has been calculated the value of inductance can be derived.

The test equipment required for this inductance measurement are

- low frequency oscillator with variable


by D. R. Fownes

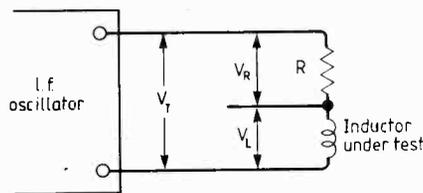

- frequency and amplitude
- alternating voltmeter
- resistor whose value is known accurately and measures about one quarter of the d.c. resistance of the coil whose inductance is to be measured (perhaps a decade resistor).

The frequency generator should be set to oscillate at about 100Hz to 500Hz as long as it is known. It will be apparent when the frequency is sufficient as the algebraic sum of $V_R + V_L$ will be greater than the applied voltage, V_T . Output amplitude is not critical as it is measured as part of the test.

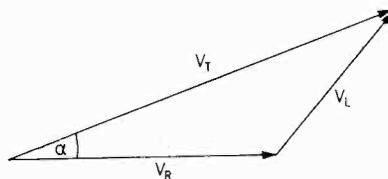When the oscillator is running voltages V_R , V_L and V_T as shown the circuit must be measured as accurately as possible. Once these values are established, the inductance is simply calculated by substituting them into the formulae below.



From the diagram

$$\cos\alpha = \frac{V_R^2 + V_T^2 - V_L^2}{2V_R V_T}$$

And as $\sin\alpha = \sqrt{1 - \cos^2\alpha}$, inductance can be calculated from


$$L = \left(\frac{V_T}{V_R}\right) \left(\frac{R}{2\pi f}\right) \sin\alpha.$$

Example. To test the method I used a low-frequency oscillator set to 100Hz with an output amplitude of 2V r.m.s., laboratory-type inductor with an inductance of 1 henry, decade resistor set to 200 ohms, and a d.m.m. set to measure 10V a.c. full scale, all connected as in Fig. 2 to measure the voltages: $V_T = 2.000V$, $V_R = 0.373V$ and $V_L = 1.714V$. This gave $\cos\alpha = 0.804$ and therefore $\sin\alpha = \sqrt{1 - \cos^2\alpha} = 0.594$, hence $L = 1.01H$.

Check. $V_{XL} = V_L \sin 44.2 = 1.194V$

$$V_{LR} = \sqrt{V_{XL}^2 - V_L^2} = 1.229V$$
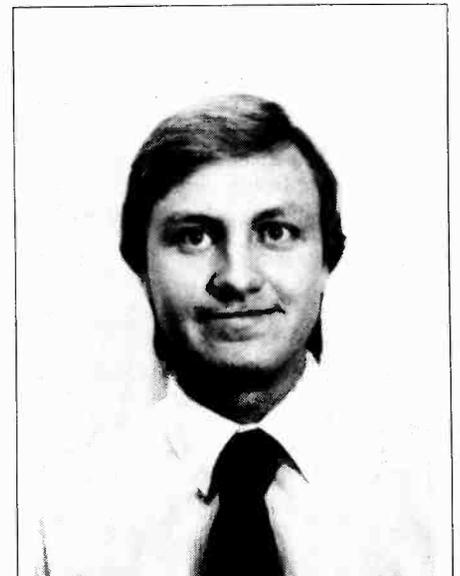
$$\therefore V_T = \sqrt{(V_R + V_{LR})^2 + V_{XL}^2} = 1.998V.$$



Since 1979 David Fownes has been employed as an electronics technician by a company producing aircraft power controls for both ministry and civil aircraft, and which currently has a world lead in fly-by-wire technology. He gained City and Guilds full technological certificate in power engineering and O.N.C. in electronics at technical college during his apprenticeship. Mr Fownes believes that due to new technological advances in powered flight we are now witnessing the most exciting developments in aviation history since the Wright Brothers' first flight.

Morse code on a ZX81

This Morse code system enables the computer to be used as an electronic Morse keyboard and runs on a 16K ZX81 under Basic.


This article is in two parts: the first describes the hardware necessary to make a ZX81 microcomputer function as a Morse code keyboard. The second part describes system operation in detail and includes a listing of the software. Sending Morse code with this system is very much like typing.

The hardware is a simple interface to an existing ZX81 and provides a single bit (serial) output port. All the hardware is external and it is not required to make any internal hardware modifications to the ZX81.

Address decoding is provided by the two chips 74LS32 and 74LS00, Fig. 1. The single-bit output port is designed from a 74LS74 D-type flip-flop and is enabled in the address range decimal 8192 to 16383 inclusive. Data to the D-type is derived from the least significant bit of the data bus. Three types of outputs are provided. Output OP₁ drives an l.e.d. which is lit according to the transmitted code. Output OP₂ drives a c.m.o.s. tone generator and a speaker. This output is useful in practising Morse code or for listening to the code during transmission. Output OP₃ is intended for switching a c.w. transmitter for Morse code transmission.

The hardware can be built on a small piece of stripboard, interfacing to the ZX81 via a 23-way edge connector. The

Fig. 1

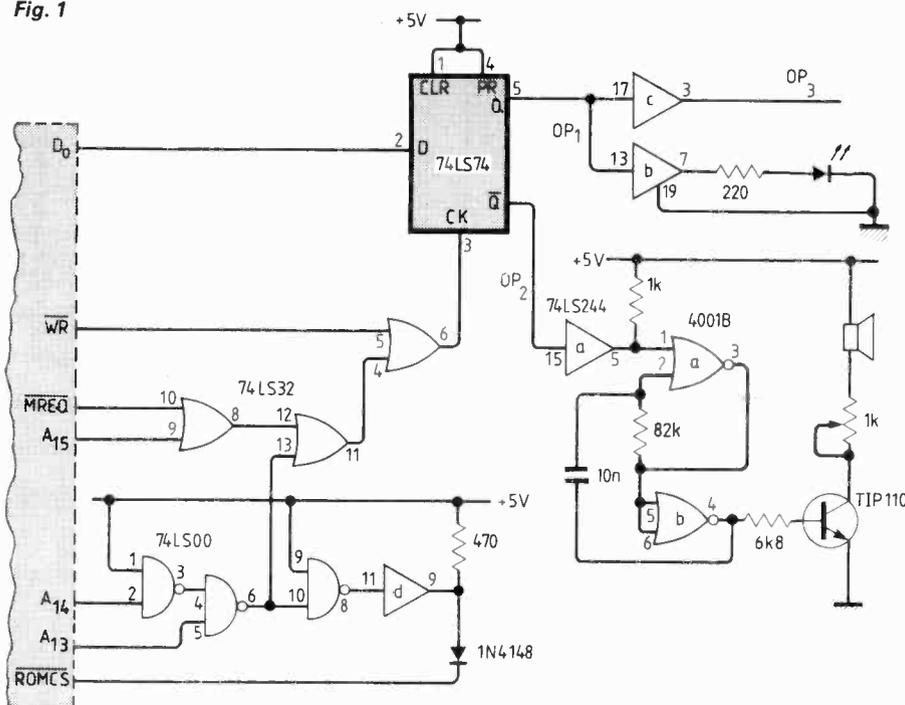

by D. Ibrahim

hardware requires no setting up.

Software

Special care has been taken to ensure a fast

output. With this approach it is possible to achieve a fast execution time.

In the software listing lines 100 to 198 convert the input characters to Morse code. Only the letters A-Z, numerals 0-9 and the space key are included in the program, though it is possible to extend the list to include other characters e.g. period, comma, question-mark, etc. The



Fig. 2 In decoding, for example, the message "MORSE TX", each dot is converted to '0', each dash to '3', characters are separated by '2', and words are separated by '3'.

execution speed. A message (upto a carriage return) is read from the user's terminal. The length of a message can be as long as you like, limited only by memory size. Once a message is received from the keyboard, it is converted to Morse code, with the proper inter-letter and inter-character spacings. The complete message is then sent to the output port. It is important to realise that a character is not sent as soon as it is received; a complete message is first received and decoded and then sent to the

decoding is

- each dot is converted to a "0"
- each dash is converted to a "1"
- individual elements of a character are separated by a "2"
- individual words are separated by a "3".

Fig. 2 shows how the message "MORSE TX" is decoded. Line 205 calculates the transmission speed and stores it as variable "T". The input message is stored in the string variable "L". The command input "END" transfers commands back to the ZX81 operating system.

Lines 500 to 510 call the appropriate output subroutines to drive the serial output port. The program runs in fast mode and the usual Morse code timing rules apply:

- a dot ("0") is one unit-time
- a dash ("1") is three unit-times
- characters are separated ("2") by three unit-times
- words are separated ("3") by seven unit-times.

Sending Morse code with the system described is very much like typing. Transmission speeds of over 30 word/min can easily be achieved. Line 205 has been adjusted to provide a correct speed in the range of about 1-20 word/min. For higher speeds there is a non-linear relationship between the speed and the delay generated by the pause statement of the ZX81. It should therefore be necessary to scale up the required speed appropriately before entering to the computer.

WW

Program appears on page 73

PROBLEMS IN SPECIAL RELATIVITY

Recent issues of *Wireless World* have seen writings by many people who feel disenchanted with the Special Theory, but whose case has been put in such a way as to cause further polarization of respective camps.

As a student, I was privileged to be lectured by Dr G. J. Whitrow, then Reader in Mathematics at Imperial College, who was then, and still is, one of the world's foremost authorities on this subject. I vividly remember the model posed by Whitrow in which the time-travellers would be taken round a circle at infinity, thus avoiding the problems of accelerated frames of reference. As a mere student, my protestations at the physical unreality of this model were, I feel, looked on as based on youthful inexperience. Many years later during the course of one of my many public lectures in an unrelated field I was charmed by the attendance of Otto Frisch, the pioneer of nuclear fission, himself a considerable mathematical physicist. In conversation we lightly stepped on the territory of Special Relativity and I found that the same feelings were aroused in me as to the response of what I might call the hierarchy of the world's physicists. I found again the attitude of the master talking to the schoolboy.

Undoubtedly, there may be many of us who are intellectually ill-equipped to appreciate the foundations of something as profound as the Special Theory, but I must stick to my feelings that the application of theoretical structures in those areas in which their approximations are so clearly invalid is extremely dangerous. Furthermore, the "instantaneous" light signals which formed a key element of teaching in my days as a student of this subject seem to me to be totally divorced from physical common sense.

Surely, if signals are to be sent, reflected from a moving body and then received by a detector in the frame of the sender, the entire mathematical problem must be worked out clearly and with great attention to a "feet on the ground" approach. Without labouring the point we should have to ask when is a signal regarded as being received by the detector (how much of it do we have to perceive before we draw useful conclusions)?

Overall, as an average mathematical physicist, I still feel as unconvinced by the use of Special Theory in conditions of accelerated frames of reference as I did as a student some 25 years ago. It is, therefore, a great pleasure to see a level-headed article such as this essentially reiterating those doubts I have as a non-member of the family of scientists who are brow-beaten into believing in the general applicability of a theory in those areas in which its validity is in doubt. At the same time, I have sufficient humility to accept that there are many people of greater intellect than myself but, sad to say, that large body has been incapable of presenting its case to me in a convincing fashion.

N. J. Phillips
University of Technology
Loughborough

Before worrying too much about 'Problems in Special Relativity' (Prof. I. McCausland, October issue) it would be as well to find out just what the relevant predictions of Special Relativity really are. Suppose that one has a set of observers at rest with respect to one another and spaced out along a line, that they synchronise their clocks according to conventional procedures, and that another observer B is in motion relative to them along the same line. Then

Special Relativity predicts that each time he encounters a new member of the initial set of observers he will find that observer's clock registering a time further in advance of his own. From the way this statement is framed it evidently doesn't matter whether B is considered to be moving relative to the other observers, or to be at rest while they move relative to him.

The key point here is that one observer is encountering a sequence of observers. The situation can be reversed by associating B with another string of observers moving along the same line, but this time at rest relative to him and with their clocks synchronised with his. Then each observer of the first set will have the same kind of experiences as B as he encounters in succession the observers of B's set. This seems thoroughly paradoxical until one realises that simultaneity does not transfer between inertial frames, i.e. that when the first set of observers synchronise their clocks B's set claim that they have made systematic errors in the synchronisation, and conversely when B's set synchronise theirs. This appears to be the situation envisaged by McCrea (M12), where the M denotes a McCausland reference. Dingle never did catch on to the failure of simultaneity, and some of his most impressive paradoxes result from ignoring it¹.

The second prediction involves introducing a kinetic assumption to the effect that at any instant an accelerated clock keeps the same time as the clocks in the frame in which it is instantaneously at rest (see Hill²). Originally Einstein appears to have made this assumption implicitly rather than explicitly, since it follows naturally from the idea that world lines in Minkowski space must be continuous. It then becomes possible (pace G. Stadlen (M11)) for Special Relativity to deal with accelerated clocks, including a polar clock and a clock located at the equator, provided that one ignores gravitation effects. As a result two or more encounters between two clocks may occur, and one is faced with the phenomenon of differential ageing, as in the so-called twin paradox. These are the conditions Einstein had in mind in making the statement about an equatorial clock losing time with respect to a clock at one of the poles. Professor McCausland didn't try very hard to arrange a meeting of clocks: a clock carried by a jet aircraft flying round the equator in the opposite direction to the earth's equatorial motion at appropriate speed would have done very nicely. This is essentially G. J. Whitrow's response (M7) to Dingle's supplementary question.

Dingle's original question is paradoxical from the beginning, it does not correspond to any specific prediction of Special Relativity, and therefore it cannot be answered without making some guess as to what he might have had in mind. J. M. Ziman's response, with a clear indication in the quotes round "Dingle's 'question'" that he thought the 'question' should be rephrased (M5), was the General Relativity answer to the question of which clock registers the greatest time between any two events at which it is present when there are gravitational fields to consider.

Finally Professor McCausland might have mentioned why Einstein excluded pendulum clocks from his observation about the time-keeping of equatorial clocks. The reason is that a pendulum does not in itself constitute a clock; the clock consists of the pendulum together with the earth.

C. F. Coleman

1. H. Dingle, *Nature* Vol. 197 1963, 1248.
2. E. L. Hill, 'The Theory of Relativity', *Handbook of Physics*, ed E. U. Condon and H. Odishaw (McCraw Hill, 1967).

The theories of relativity and quantum mechanics are the two major leaps forward in physics this century, and they appear to have attracted more than their fair share of controversy. One reason for this may be that most of our everyday experience of physical phenomena happens to be in the area where both theories agree with Newtonian mechanics.

As far as we know, neither relativity nor quantum mechanics contain any inconsistencies – and this is despite the effort put in to trying to discover them, by people of Einstein's calibre. Special Relativity is so well established among physicists that attempts to discredit it tend not to be taken seriously. However, a theory as rich as Special Relativity cannot be demonstrated to be consistent – just as we know that arithmetic cannot be shown to be consistent.

There are problems with both theories, and these arise from the fact that while the assumptions on which they are based are simple, the application of the theories contains subtleties. These subtleties lead exponents and opponents of the theories to make slips of thought which lead them to the conclusion they require.

For example, people often claim that they have found an inconsistency in Special Relativity by applying it to a physical example. They claim that when they attempt to do this, they obtain a result which is clearly false.

$$\text{Problem} \xrightarrow[\text{+ Newtonian Mechanics}]{\text{Special Relativity}} \text{falsity}$$

In fact, they have inadvertently added some Newtonian idea (which is inconsistent with Special Relativity). It is this combination of theories which produces the false result.

$$\text{Problem} \xrightarrow{\text{Special Relativity}} \text{falsity}$$

It is this slip which Dingle makes. Although (as I pointed out earlier) we cannot prove that Special Relativity is consistent, we can at least conclude that as there are mistakes in Dingle's argument, his case is not proven.

To turn to the specific example of the two clocks, Special Relativity does not say that one is faster than the other – in fact it denies the existence of absolute speed both of objects and of clocks. Special Relativity is a theory of measurement denying the existence of absolute space and time against which to measure the speed of material particles and clocks.

In McCausland's reference 10 Einstein is writing many years before formulating his general theory of relativity, and is using a very simplified model of two clocks. One is at a pole (i.e. stationary with respect to the fixed stars), the other is moving with the equator. He concludes that an observer who is stationary with respect to the fixed stars measures the clock on the equator as going more slowly than that situated at a pole. His argument here avoids the complication of gravitation, except in so far as it is the mechanism by which the moving clock traces its path. He excludes pendulum clocks from the argument, not through oversight, but because he realised that to include them he would have to include the effects of gravity. This would have complicated the argument unnecessarily.

A. D. Vella
Oxford Polytechnic

The author replies

Mr Coleman raises several interesting points. Referring to my statement that Ziman's answer

does not apply to the polar and equatorial clocks because they do not meet, he says that I didn't try very hard to arrange a meeting of clocks. I had thought that it was Ziman's responsibility to show how his answer applied to that case, not mine. However, let us consider Coleman's suggested clock carried by a jet aircraft flying round the equator in the opposite direction to the earth's equatorial motion at appropriate speed. I assume that by "appropriate speed" he means a speed equal to the earth's peripheral velocity at the equator; such a clock would be stationary relative to the polar clock, and would presumably work at the same rate. In that case, Einstein's prediction corresponds to a prediction that the airborne clock would work faster than the earthbound equatorial one. Now, if Ziman's answer is applicable to the comparison of those two clocks, as Coleman implies it is, then in order to deduce Einstein's result using Ziman's answer one would first have to show that the airborne clock was in free fall between the two meetings of the clocks, or for one full circuit of the earth. It is fairly obvious that the clock in question does not travel between the two meetings by free fall, but could perhaps be made to do so if one made the small extra step of removing the earth; however, Coleman does not seem to have that possibility in mind, since he stipulates that the clock is to be carried by a jet aircraft. It is also unclear how he uses this example to justify Whitrow's answer, since what he says does not alter the fact that the earthbound equatorial clock is not in an inertial frame.

Coleman also tells us that Ziman's response shows a "clear indication" that Ziman thought Dingle's question should be rephrased. But Ziman did not say it should be rephrased; he said it was "a perfectly reasonable question to which science should indeed give an answer". Professor Ziman is a prolific writer who may be assumed to have sufficient command of the language to be able to say what he means without requiring readers to indulge in mind-reading. If he believes that Dingle's question ought to have been rephrased, he should tell us so himself.

Coleman goes on to say that Ziman's response was the General Relativity answer to the question. But the whole point of Dingle's question was to find out what justification was given by the *Special Theory* for one clock to work faster than the other. So Coleman is supporting the view that Dingle's perfectly reasonable question has not been answered.

Finally, let us consider one of the most important topics of all – the synchronization of clocks. Coleman mentions synchronization and then goes on to say that Dingle never did catch on to the failure of simultaneity. Let us consider this problem in more detail.

First of all, Dingle was careful to distinguish between simultaneity of events and synchronization of clocks; see, for example, his letter in *The Listener* dated 30 December 1971. He also pointed out, in *Science at the Crossroads*, that when a pair of relatively stationary clocks are synchronized they are synchronized for all observers. Although this is a crucial part of Dingle's argument, I can recall only one review of his book that discusses synchronization, and it agrees with Dingle that synchronization is independent of the observer; that review is Stadelen's, which was cited in my article.

Since Einstein argued, in his original paper on Special Relativity, that observers moving relative to the pair of synchronized clocks would find that they were not synchronized, let us now

consider Einstein's original definition and argument.

Einstein gave a definition of synchronization in the following way. Two clocks A and B are at rest relative to one another, and a flash of light is emitted from A and reflected back from B to A. If the reading on B at the moment of reflection is halfway between the readings of A at emission and return of the flash, the clocks are synchronized. Any observer, in any state of motion, would see the same set of three readings, and would reach the correct conclusion about the synchronization of the clocks. (If desired, the experiment could be done in darkness, and the only three clock readings seen by anyone would be the readings illuminated by the flashes; the observer need not consult his own clock, nor indeed need he possess one.)

Now consider the argument by which Einstein concluded that observers moving relative to a pair of clocks would find that they were not synchronized. The argument involves a rigid rod aligned with the x axis of a stationary reference frame, and moving longitudinally along the x axis; at its ends A and B are two clocks, and along the x axis are several stationary clocks which are synchronized with one another. A flash of light is emitted from A and reflected back from B to A to test for synchronization.

The crucial fact about this experiment is that each of the clocks at A and B is constrained to give the same reading as the stationary clock that happens to be adjacent to it at any instant. I say "constrained" deliberately, because it turns out from results derived later in the theory that the clocks at A and B, if they were running freely, would *not* continue to give the same readings as the stationary clock adjacent to them as they move along, but would fall further and further behind the stationary clocks. To make them continue to show the same readings as their stationary neighbours they would have to be continually readjusted, in which case they would not be regularly-running clocks. To put it more bluntly, they would not be clocks at all, for their clock works could be removed and their readings adjusted by demons to correspond to the readings of the adjacent stationary clocks. Even more simply, the "clocks" could be removed altogether and replaced by mirrors which would simply *reflect* the appropriate readings.

In the experiment, the flash of light reflected from B arrives back at A, the end of the rod from which the flash was emitted. Since A has by then moved on, relative to the stationary row of clocks, the clock then opposite A is not the same one as the one that was opposite A when the flash was emitted; the reading at B is therefore not halfway between the two clock readings at end A of the rod. Therefore, according to Einstein "observers moving with the moving rod would thus find that the two clocks were not synchronous".

But Einstein is not using his definition of synchronization in reaching that conclusion. The "clocks" at the ends A and B of the rods are not regularly-running clocks, but merely objects which reflect the readings of the stationary clocks beside them. Since the definition requires the reflected flash of light to return to the regularly-running clock from which the original flash was emitted, and since it does not do so until after it has passed the new position of end A of the moving rod, it is not valid to make any inference about synchronization of clocks from the reading of the clock at the new position of A. Einstein's conclusion is therefore unjustified.

Reply to A. D. Vella

Dr Vella states that Dingle made an error, but does not identify a specific error. He goes on to say, referring to the two clocks, that "Special Relativity does not say that one is faster than the other – in fact it denies the existence of absolute speed both of objects and of clocks." I do not think that a statement that one clock works faster than another is a claim about absolute rates of clocks, but in any case it was Einstein himself who stated explicitly that the equatorial clock must work slower than the polar one.

Vella goes on to say that the polar clock is stationary with respect to the fixed stars, which is not true. He then says, referring to Einstein: "He concludes that an observer who is stationary with respect to the fixed stars measures the clock on the equator as going more slowly than that situated at a pole." Vella implies that it is the state of motion of the observer that determines which clock is measured as the slower one, but this is not what Einstein said; he stated that the equatorial clock must work more slowly than the polar one.

In view of the two statements that I have quoted from Dr Vella's letter, I would ask him to answer, with a simple yes or no, the following question: Would an observer on the equator measure the clock at the pole as going more slowly than that situated on the equator?

Reply to J. C. Laine

After a fairly obscure derivation, Mr Laine concludes that "it is the *travelling clock* which runs *slower* than the stationary clock". Exactly. But the theory says that either clock can be taken to be the stationary one (as Laine seems to agree when he says that "stationary" is a relative expression), so Laine's statement supports Dingle's claim that the theory requires each clock to work slower than the other.

Laine then goes on to talk about observation, in an apparent attempt to avoid the obvious result of the statement quoted above. But that does not remove the problem. As I pointed out in *Wireless World* in October 1980, Professor P. C. W. Davies, in his book *Space and Time in the Modern Universe*, makes the following statement about two clock-carrying observers in uniform relative motion: "It is not that each observer merely *sees* the other clock running slow, it actually is running slow – a real physical effect." [Emphasis in the original.] In any case, the observer is not an essential part of the special theory, as has been pointed out by H. Reichenbach, one of the contributors to the book *Albert Einstein: Philosopher-Scientist*, edited by P. A. Schilpp, who wrote that "In a logical exposition of the theory of relativity, the observer can be completely eliminated".

General comments

Without exception, critics of my article have failed to answer my main point, which is that defenders of the theory have published arguments which are inconsistent with one another and/or with Einstein's own statements. Clear evidence that there are problems in the theory is provided by the fact that these inconsistent statements remain uncorrected. The alternatives are clear: either some of those scientists' statements are wrong, or the theory from which those scientists claim to have deduced their statements is internally inconsistent. Therefore, unless the defenders of the theory can remove the inconsistencies by showing that some of their statements are wrong, they have themselves proved that the special theory is untenable.

Program allows ZX81 keyboard to generate Morse code


```

1  REM "MORSETX"
7  REM *(C) COPYRIGHT D. IBRAHIM*
10 POKE 8192,0
20 GOTO 200
50 POKE 8192,1
52 PAUSE T
53 POKE 16437,255
54 POKE 8192,0
55 PAUSE T
56 POKE 16437,255
57 RETURN
60 POKE 8192,1
62 PAUSE X
63 POKE 16437,255
64 POKE 8192,0
65 PAUSE T
66 POKE 16437,255
67 RETURN
70 PAUSE Y
71 POKE 16437,255
72 RETURN
80 PAUSE Z
81 POKE 16437 255
82 RETURN
100 REM "CODE DECODING"
110 FOR I = 1 TO LENGTH
111 IF L$(I) = "A" THEN LET P$="01"
112 IF L$(I) = "B" THEN LET P$="1000"
113 IF L$(I) = "C" THEN LET P$="1010"
114 IF L$(I) = "D" THEN LET P$="100"
115 IF L$(I) = "E" THEN LET P$="0"
116 IF L$(I) = "F" THEN LET P$="0010"
117 IF L$(I) = "G" THEN LET P$="110"
118 IF L$(I) = "H" THEN LET P$="0000"
119 IF L$(I) = "I" THEN LET P$="00"
120 IF L$(I) = "J" THEN LET P$="0111"
121 IF L$(I) = "K" THEN LET P$="101"
122 IF L$(I) = "L" THEN LET P$="0100"
123 IF L$(I) = "M" THEN LET P$="11"
124 IF L$(I) = "N" THEN LET P$="10"
125 IF L$(I) = "O" THEN LET P$="111"
126 IF L$(I) = "P" THEN LET P$="0110"
127 IF L$(I) = "Q" THEN LET P$="1101"
128 IF L$(I) = "R" THEN LET P$="010"
129 IF L$(I) = "S" THEN LET P$="000"
130 IF L$(I) = "T" THEN LET P$="1"
131 IF L$(I) = "U" THEN LET P$="001"
132 IF L$(I) = "V" THEN LET P$="0001"
133 IF L$(I) = "W" THEN LET P$="011"
134 IF L$(I) = "X" THEN LET P$="1001"
135 IF L$(I) = "Y" THEN LET P$="1011"
136 IF L$(I) = "Z" THEN LET P$="1100"
137 IF L$(I) = "1" THEN LET P$="01111"
138 IF L$(I) = "2" THEN LET P$="00111"
139 IF L$(I) = "3" THEN LET P$="00011"
140 IF L$(I) = "4" THEN LET P$="00001"
141 IF L$(I) = "5" THEN LET P$="00000"
142 IF L$(I) = "6" THEN LET P$="10000"
143 IF L$(I) = "7" THEN LET P$="11000"
144 IF L$(I) = "8" THEN LET P$="11100"
145 IF L$(I) = "9" THEN LET P$="11110"
146 IF L$(I) = "0" THEN LET P$="11111"
190 IF L$(I) = " " THEN LET R$=R$ + "3"
191 IF L$(I) < > " " THEN LET R$ = R$ + P$
192 IF L$(I+1) < > " " AND L$(I) < > " "
    THEN LET R$ = R$ + "2"
193 NEXT I
198 RETURN
200 PRINT " "
202 PRINT "ENTER THE TRANSMIT SPEED (WPM) : "
203 INPUT WPM
204 PRINT WPM
205 LET T = 50/(2.08*ABS (WPM - 2.4))
206 LET X = 3*T
207 LET Y = 2*T
208 LET Z = 6*T
210 LET R$ = " "
211 PRINT ""
213 PRINT "ENTER THE MESSAGE:"
215 INPUT L$
217 PRINT L$
219 IF L$="END" THEN STOP
221 LET LENGTH = LEN L$
222 LET L$ = L$ + " "
223 FAST
225 GOSUB 110
229 PRINT ""
230 PRINT "START OF TRANSMISSION"
500 FOR I=1 TO LEN R$
502 IF R$(I) = "0" THEN GOSUB 50
504 IF R$(I) = "1" THEN GOSUB 60
506 IF R$(I) = "2" THEN GOSUB 70
508 IF R$(I) = "3" THEN GOSUB 80
510 NEXT I
511 CLS
512 PRINT "END OF TRANSMISSION"
513 SLOW
514 GOTO 210
    
```

How reliable is Cruise?

A study of the technical aspects of the ground-launched Cruise missile has cast doubts on the system's reliability. An engineering critique of the system says that on purely technical grounds, there are good reasons for not deploying it. *The Ground Launched Cruise Missile, A Technical Assessment*, written by electronics design engineer, Tim Williams, and published by Electronics for Peace, concludes that the system as been insufficiently tested, and has been rushed into production for political reasons; it has not been designed or built to the standards required for deployment in Europe. Particular areas for concern are pinpointing; the over-hasty system software testing; inadequate manufacturing quality control; the use of unproven systems concepts could lead to long-term unreliability; the competence and training of maintenance personnel and operators is below the standard necessary.

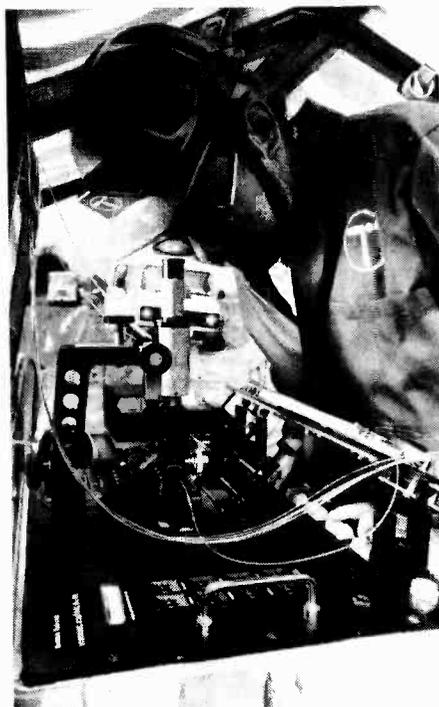The report, which took a year to prepare, draws on a number of sources including Congressional hearings, technical articles and the manufacturers' own material. In the pamphlet, Tim Williams states: "the hazard posed by a system which involves transportable nuclear warheads is greater than for any other cur-



Optical fibre cables have been laid by BT between Luton and Milton Keynes along the A5 trunk road. Joining successive lengths of the fibres must be carried out so that they are lined up to within 0.05 microns on a fibre 8 microns thick. Alignment and electric fusion are carried out on this automatic machine, developed by BT, shown here operated on site by technician John Guile. A pair of cables use a multiplexed monomode transmission system to carry up to 2,000 phone calls at once.

rently deployed nuclear weapon. Acceptance of deployment is an offer of hospitality to an untested, unreliable, bug-ridden system that could turn out to be fatal to its hosts." History has overtaken Mr Williams, the system is already here.

Electronic scrap recycled

The first refinery in the world designed and built specifically for electronic scrap has been opened by Engelhard Industries. A wide range of precious metal bearing materials have hitherto been too expensive to recover, but the new Cinderford plant built at a cost of £2.2M uses a combination of processes, equipment and computer control to optimize the recovery efficiency. Electronic scrap amounts to thousands of tonnes a year in Europe alone, and locked within it lies a potential fortune in precious metal.

The process involves calcination, burning at very high temperature to burn off the plastic and to reduce the raw metallic scrap to an ash. The ash is pulverized in a vibratory crusher and then separated into different sized particles by a series of sieves where an electro-magnet sorts out the ferrous scrap. These and the non magnetic fractions are taken to a melt shop for separate refining. Computer analysis of the 'fines' determines the precise type and quantity of flux to be added to optimize melting. The powdered mixture is rolled into pellets for the furnace.

Nine induction melting furnaces are used in the melting process and the hot impure metal is cast into bars which consist of mixtures of silver, gold and platinum-group metals in a greatly enriched form suitable for processing in a conventional refinery. Particular care has been taken to keep air and noise pollution to an absolute minimum.

Another dish in the Docks


Following the announcement of BT's satellite earth station in London's dockland, Mercury Communications have received outline planning permission for the use of East Wood Wharf on the Isle of Dogs, London for a satellite station of their own. Two dishes are to be installed: an eight-metre dish providing tv distribution within the UK, to be operational in March. A 13m unit for transatlantic television and digital telecommunications should enter service in May. Both systems are supplied in containerized form by Marconi Communication Systems. In summer an 18m dish will come into operation for further communications with North America. This is to be sited in Tackley, Oxfordshire at a disused quarry within 400m of a railway line and BR's wayleaves, used by Mercury. Like BT, Mercury have an eye on providing programmes via satellite to cable operators as well as communications to remote and offshore sites.

NEW PRODUCTS

Rotary encoder

A compact, lightweight photointerruptor type of rotary encoder is shown in the photograph of the Sharp GP-IR04. This uses an infra red led and an integrated photodiode to provide three types of two-phase output; a sinewave, a cosine wave and an index output. Different slotted discs are used in the five models to give resolutions of 96, 100, 192, 200 or 360 pulses per revolution. Besides their compact and lightweight design, the encoders feature high accuracy through the laser trimming of the circuitry and a high frequency response because of the use of a laser diode with very good thermal characteristics. The encoder can detect arc angles, count revolutions, measure rotational speed and indicate rotational direction. It has applications in a variety of tools and instruments including micrometers and vernier calipers but the small size suggests that it would be highly suitable for robotics. Available through Hero Electronic Ltd, Dunstable Street, Ampthill, Beds MK45 2JS.
WW 301

WW 301

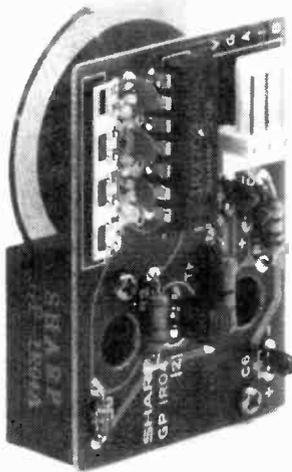

Real-time analyser for PC

An add-on 1/3-octave real-time analyser board uses the processing and display facilities of the IBM Personal Computer. RTA 331 consists of 31 two-pole filters from 20 to 20kHz and has a package of assembly-language routines called from Basic. It features instantaneous display, variable decay rates and averaging periods, peak hold and weighting functions, display of two independent bar graphs. It includes a pink noise generator which may be controlled through the program as may the input gain. Eight-bit sampling at 20kHz means that it can store up to 22 seconds of input in 128K bytes of memory. Similar systems are available for use on Apple, TRS80 and Commodore computers. Marquee Electronics Ltd, 90 Wardour Street, London W1V 3LE.
WW 306

Bespoke firmware

A number of utility programs are available as listings or programmed roms with user guides. They include m/c monitors for the 8080, 8085 and Z80 processors; Tiny Basic, Contol Basic, floating-point mathematics packages, serial communications interface; an eprom programmer which includes verification before 'burning'; and a number of system simulation packages. Isis for example is an interactive computer program which enables the user to solve non-linear differential equations and may be used as a replacement for an analogue computer to solve problems in dynamics and transient behaviour of continuous systems, such as servo systems or automatic control systems. Most of these are designed to run on 8080, 8085 or Z80-based microcomputers, and some may be run through CP/M. The manufacturers say that they may make the programmes available for use on other computers. Simulaton Systems Ltd, The Gables, North End, Yatton, Bristol BS19 4AS.
WW 000


will offer a main disc storage capacity of 10.48Mb with the same 5.24Mb disc fitting into the slot for back-up. A range of controllers and the drives themselves are from Craft Data Ltd, M and M House, Frogmore Road, Hemel Hempstead, Herts HP3 9RW.
WW 302

Low-cost eraser

It has always surprised us that something as simple as a light-proof box and an ultraviolet lamp should cost as much as many available on the market. A more realistic price of £19.95 is asked for the Uvipac eprom eraser which can operate on up to three eproms at once in a unit only 90 by 80mm. Erasure time varies from 5 to 20 minutes depending on the device. A built-in 15-minute timer costs £5 more (prices inclusive of v.a.t.) Ground Control, Alfreda Avenue, Hullbridge, Essex SS5 6LT.
WW 303

5Mbyte disk with back-up

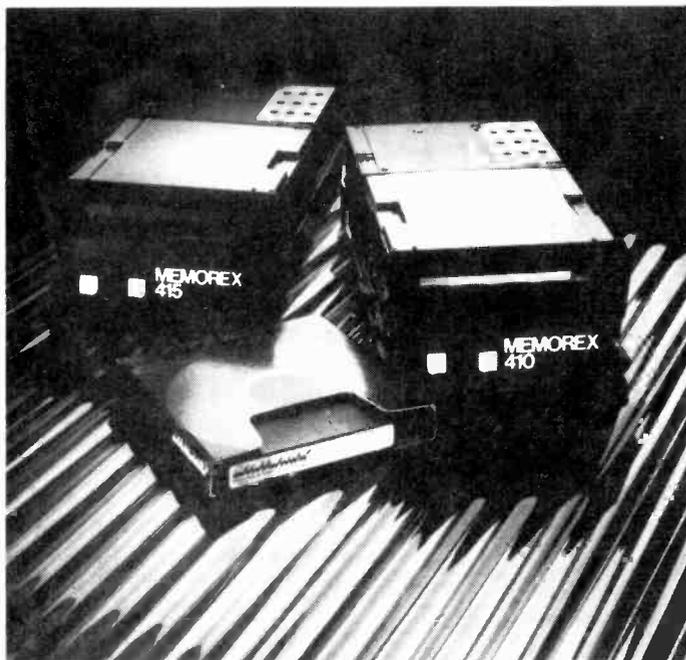The availability of the Memorex 410 series of hard discs with removeable disc back-up storage has been announced. Each disc has 5.2Mb formatted capacity and are packed together in a standard 5.25in disc housing. The removeable cartridge disc has been designed in the style proposed as an ANSI standard. The next drive in the range, the 415, available soon,



Hand-held dmm

A three-and-a-half digit, 1.c.d. multimeter comes from Keithley in their model 130A. This model claims a 0.25% accuracy on the direct voltage range and has current measurement up to 10A on both a.c. and d.c. The sensitivity is 100ΩV, 1ΩA and 100mΩ in the




Mike power

A battery unit to provide power for condenser microphones where no power feed is otherwise available, is provided by the AKG B18. Running off two PP3-type batteries, the unit may be connected to balanced and unbalanced amplifier, mixer or tape recorder inputs. The compact casing is provided with a swivel clip for attaching to the user's belt and a led indicates the battery status. Weighing only 130g, the unit provides opportunities to use condenser mikes when it would otherwise be impossible. AKG Acoustics Ltd, 191 The Vale, London W3 7QS.
WW 305

respective ranges and the meter can also be used for diode checks. It is protected against overloads and has indicators for polarity and if the battery voltage drops. The meter is warranted for two years and needs to be recalibrated after about the same period. Battery and fuse may be replaced without taking the meter apart. Keithley Instruments Ltd, 1 Boulton Road, Reading, Berks RG2 0NL.
WW 307

Image store/processor


By using the latest processors and dynamic read/write memory, Cambridge Research say that they can produce Alphascan, an image frame store and processing system, for a fraction of the cost of any (Far East) rival. The system has a wide range of applications in scanning microscopy, medical scanning instruments, data transmission, image processing, ultrasound imaging, and displays for non-destructive testing, amongst many. Signal collection at slow scan rates and c.r.t. presentation of the final image is standard and a number of software extensions permit digital processing, quantification, image analysis, two and three-dimensional measurement, disc storage and printer options. Cambridge Research Instruments, Chesterton Mill, French's Road, Cambridge CB4 3NP.
WW 308

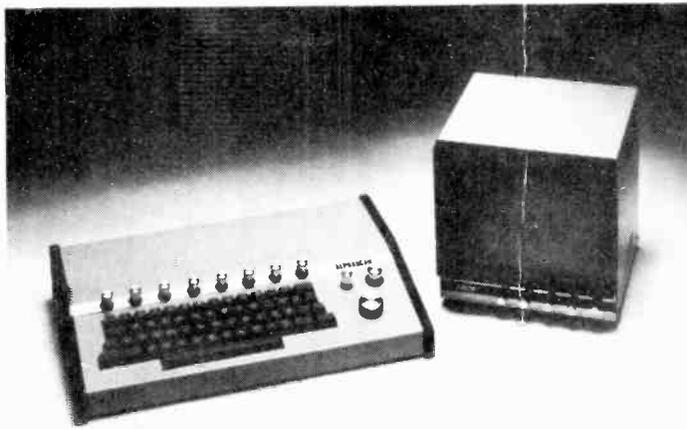

WW 308

Domestic timer

A plug-in time switch for home or business use provides the accuracy of digital quartz timing with a neat compact case and a number of useful features. It is accurate to the minute, unlike most mechanical time switches and it can remember up to three on/off times which are protected in the memory against power failure by an internal battery. Any setting may be overridden by a touch of a button and programs may be suspended whenever the normal routine is not required, for example, at weekends. The unit, called Tempo, displays the time and the display is also used when setting the switch times and for checking them. Because of its accuracy, the time switch may be used to control remotely the recording of radio programmes, for alarm calls or for setting security systems. It may also be used to turn lights on and off around the house to deter burglars. Tempo, at £19.95 inclusive + £1.95 postage and packing is available by post from Tek Marketing, Burrell Road, St Ives, Huntingdon, Cambs PE17 4LE.
WW 309

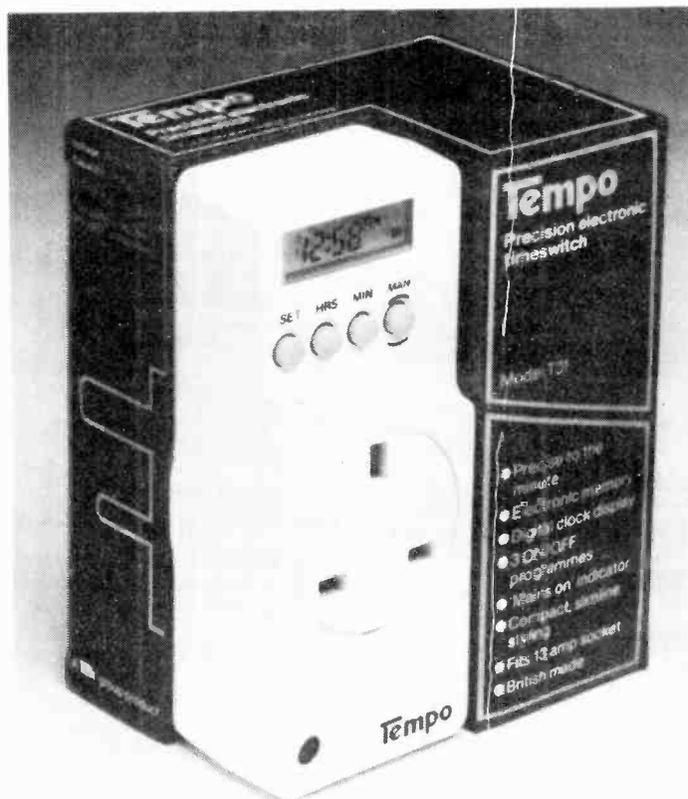


WW 309

WW 311

PCB CAD

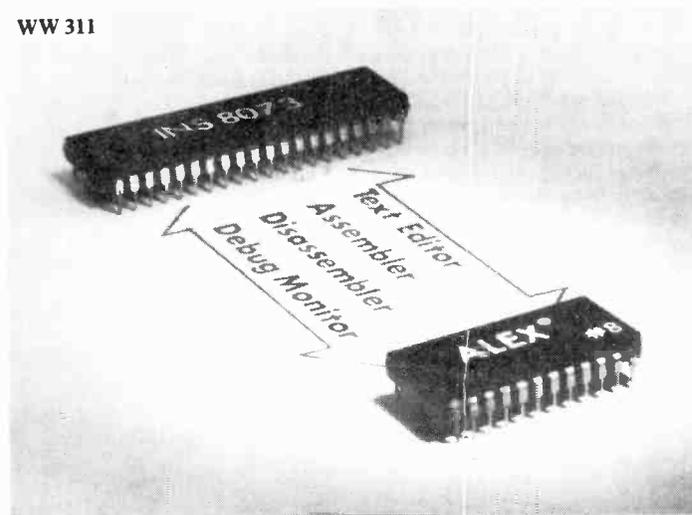A computer-aided design system for p.c.bs has been developed by Dyad. The Chroma-cad system includes a high-resolution colour monitor with a second monochrome monitor displaying numerical information simultaneously. There is a dedicated keyboard and a





trackerball for rapid cursor movement. Developed for the creation of multi-layered designs, a complete board can be output to a plotter to produce camera-ready masters; or transmitted to a bureau for the production of higher-standard masters. The system uses two processors (Z80 and 8088) with the Z80 acting as a systems organiser while the 8088 is solely concerned with controlling the colour display. Drawings for p.c.bs up to 32m each side, working to a tolerance of 0.001m, is possible while up to 80 i.cs or their equivalents may be handled on the standard system. With memory expansion boards, the capacity can be increased. Component layout, or whole sub-circuits may be stored to and recalled from a library held in disc memory. Different layers of a board are displayed in different colours. Images may be selected for displaying together and the image may be 'panned' across or 'zoomed' into for a closer look. A variety of plotters, including photoplotters may be used and the system may be optimized to find the best combination of pad size and track width for particular pens, inks or paper. The makers point out that DoI grants are available for those companies purchasing CAD equipment. Dyad Developments, The Priory, Great Milton, Oxon OX9 7PB.
WW 310

Tiny support package

A useful addition to the Essex Tiny Basic single-board computer is Alex. Intended for developing machine-code routines on the INS 8073-based system, it includes an assembler, enabling source code to be entered at a terminal; a disassembler for examining code already in memory; a text editor to allow lines to be altered without rewriting it all and a monitor routine which allows memory to be examined, copied, modified, compared and tested with a debugging program. Alex is supplied on a 4K eeprom with a comprehensive users' manual. Essex Electronics Centre, University of Essex, Colchester, CO4 3SQ.
WW 311

If you would like more information on any of the items featured here, enter the appropriate WW reference number(s) on the mauve reply-paid card bound in this issue. Overseas cards require a stamp.

NEW PRODUCTS

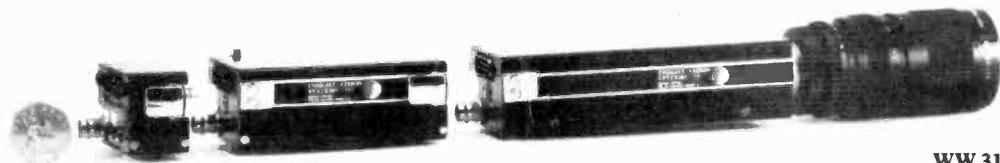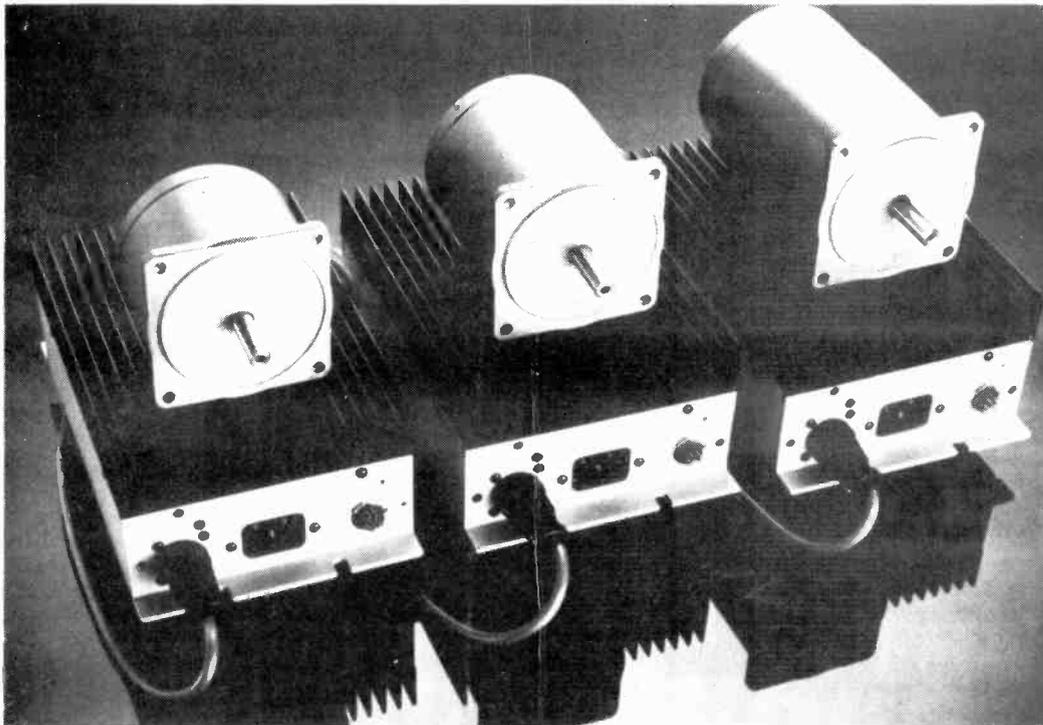

WW 313

Compumotor

Advantages over both stepper motors and d.c. servo motors are claimed for the Compumotor motor-and-control combination. Smooth linear acceleration over intermediate incremental positions compares with the stop/start magnetic detents of the stepper motor. This means that much less high frequency energy is transferred to the driven system so mechanical damping and dissipation can be greatly reduced. It provides high torque over a wide speed range and is claimed to have a much better slow-speed control combined with high resolution. Similar comparisons may be made with the d.c. servo motor system. With an increase in low speed torque while "the elegant simplicity and completeness of the Compumotor packages mean shorter design, specification, procurement and check-out times". Open and closed-loop configurations are available and the accuracy at slow speed frees the system from hunting the final position, as is common with many servo systems. The Compumotor is available with a variety of resolutions, up to 50 000 steps per revolution with a maximum step rate of 50 000 steps/s. Output


power is from 0.001 to 2.5 horsepower. Unimatic Engineers Ltd, 122 Granville Road, London NW2.
WW 312

Miniature cctv

What is claimed to be the smallest available self-contained monochrome tv camera with broadcast-standard picture quality, the Insight 75 includes $\times 10$ automatic gain, edge enhancement, automatic black level, motorised vidicon racking, built-in iris drive servo and an external lock. All this is in a package which fits into the palm of a hand and yet provides a resolution of 600 lines, a 56dB signal/noise ratio and a power consumption of 1.6W. A socket is provided for clip-on modules including a battery pack and a remote control unit. Applications include robotics, scientific research and surveillance. The system has been successfully used in surveying sewers and drains, boreholes, ducts and pipelines, for which purposes the manufacturers have devised and patented lighting and control systems. Insight Vision Systems Ltd, Unit 1, Merebrook Industrial Units, Hanley Road, Danemoor, Malvern, Worcs WR13 6NP.
WW 313

Inter-pcb connections

A double-decker p.c.b. connector obviates the need to use multi-layer boards. Using 0.1in pitch dual-in-line socket frames incorporating special stepped stand-offs with pin ends compatible with standard p.c.b. holes, collar supports ensure that the p.c.bs are held rigidly at 15mm parallel spacing. 17 options cover six to 64-pin d.i.l. packages which may be used with extender boards to add, e.g. more memory to a computer board. Test facilities may be added to a board using this system. Scott Electronics Ltd, 50 London Road, Sevenoaks, Kent TN13 1AS.
WW 314

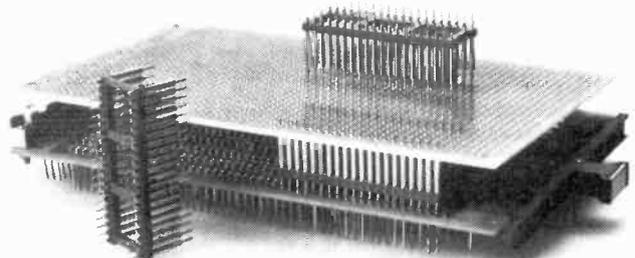

WW 314

How pure are your sines?

A quick visual check on sinewave purity is provided by a pair of oscilloscope graticules which incorporate accurate sinewave traces printed on them permanently. The regular graticule is removed from the oscilloscope and the Sinecheck may be attached to the face of the c.r.t., alignment marks are provided. According to the designer, it is possible to monitor sinewave purity with a precision limited only by the fineness of the trace. Graticule 1 has a complete sinewave and may be used for initial setting up. It is itself adequate for most purposes, but for the more demanding occasion, graticule 2 may be used for further testing. This latter has two traces; a positive and negative half cycle. The graticules are available to fit up to a 100 by 80mm working area. Other sizes may become available if there is sufficient demand. The pair of graticules are available for £2. Enquirers should include screen working dimensions and a stamped addressed envelope to Sinecheck Graticules, Freepost, Watford, Herts WD1 8FP.
WW 315

In brief . . .

Three-stage power darlington transistors made by TI can switch voltages up to 1150V and currents up to 20A. They can withstand overload conditions up to 33kV. Available from VSI Electronics (UK) Ltd, Raydonbury Industrial Park, Harlow, Essex CM19 9BY.
WW 316

Two variations of Mains input filters are stocked in 1, 3, and 6A versions. The standard version (WF100) meets the 0.5mA leakage current standard for digital equipment while the WF100B meets the need for less than 5uA for medical applications Comway Ltd, Market Street, Bracknell, Berks RG12 1QP.
WW 317


Hitachi Oscilloscopes

performance, reliability, value



New Models!

immediate delivery!

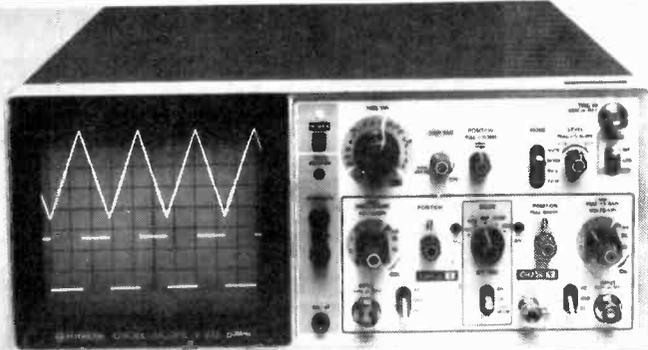

New from Hitachi are three low-cost bench 'scopes with bigger screens and extra features in a new slimline ultra-lightweight format. The range now extends to 13 models:—

- 4 dual trace single timebase models 20MHz to 40MHz
- 2 dual trace sweep delay models 20MHz and 35MHz
- 2 dual timebase multi-trace models 60MHz and 100MHz
- 2 miniature field portable models, 20MHz and 50MHz
- 3 storage models, one tube storage, two digital storage

Prices start at £295 plus vat (model illustrated) including 2 probes and a 2-year warranty. We hold the range in stock for immediate delivery.


For colour brochure giving specifications and prices ring (0480) 63570.

Reltech Instruments, 46 High Street, Solihull, W. Midlands, B91 3TB

WW - 070 FOR FURTHER DETAILS

Tomorrow's World . . . Today

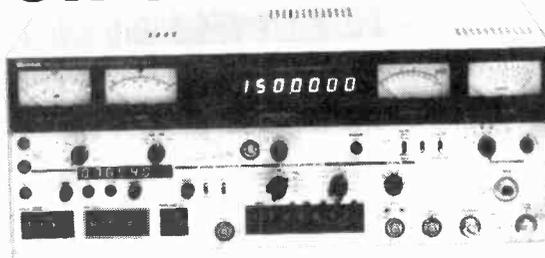- Performance:**
- Total R/T measurement
 - Semi automatic interactive instruments that work alone
 - Full Duplex Testing
 - Built-in Selcall and Pilot Tone
 - 300W Power meter
 - Sinad Meter
 - Fully protected
 - Portable for field use (12v)
 - Up to 1.7 GHz available.



- Cost effectiveness:**
- Only minutes to test a system
 - Easy to train new staff
 - More economical than individual units
 - Less bench space required
 - 24-hour service support
 - Easy payment terms
 - Enhancement facilities at low cost
 - Loan set for evaluation.

Whether you're seeking performance or cost effectiveness you can now enjoy the best of both worlds with the RTT comtest. Its unique features and UK service support ensure it's the best buy today or tomorrow.

UNDER NEW MANAGEMENT


RTT comtest
Tomorrow's World - Today



RTT Division of Hanworth Enterprises Ltd, Enterprise House, Central Way, North Feltham Trading Estate, Feltham, Middx TW14 0RX. Tel: 01-844 1811

WW - 041 FOR FURTHER DETAILS

Where business is making contact

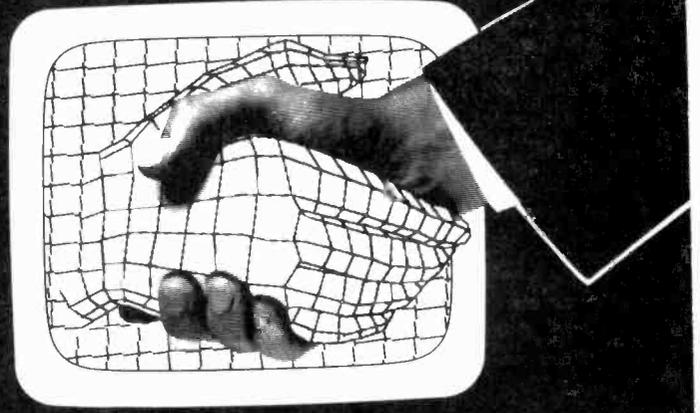

For the communications industries worldwide, the United Kingdom is currently a focus of attention.

There's so much accelerating change – in telecommunications services, in the increased use of mobile and cellular radio, in the re-cabling of the country, and in the spread of information technology and electronic office systems.

Your prime opportunity to renew (and make) contact with the people and organisations at the heart of these developments is at COMMUNICATIONS 84.

Once again, the latest presentation of this established event has attracted hundreds of companies – from the world over – who market communications products and services.

They are there to discuss how their organisations can help your business.

Whatever aspect of communications is your concern, you can view and compare the alternatives – comfortably, cost-effectively and conveniently under one roof.

Attend the associated conference too, and add further to the value of your visit.

The time and place are right, so make a date. Communicate with the communicators at COMMUNICATIONS 84.

15-18 May 1984 National Exhibition Centre
Birmingham, England



Communications 84 is organised by Industrial & Trade Fairs Limited, ITF
Radcliffe House, Blenheim Court, Solihull, West Midlands B91 2BG
England ☎ 021-705 6707 Telex 337073

Communications 84

INTERNATIONAL EXHIBITION OF TELECOMMUNICATIONS, RADIO AND INFORMATION TECHNOLOGY PRODUCTS AND SERVICES.

Please send me the **visitor information pack** for COMMUNICATIONS 84, which includes details of the conference programme, easy travel arrangements, and free registration card for the exhibition.

Name _____ Company _____


Address _____

Complete and send to Department PS1 at the address shown. WW.V1

WW - 057 FOR FURTHER DETAILS



LINSLEY-HOOD 300 SERIES AMPLIFIERS

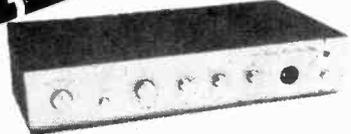

- 30 Watt Complete Kit £85
- 35 Watt Complete Kit, MosFet O/P £79.50
- 45 Watt Complete Kit, MosFet O/P £83.50
- Reprints of 30 Watt Article from 'Hi-Fi News' 50p
- Reprints of MosFet Postscript to above..... 30p

'P.W. WINTON' TUNER AND AMPLIFIER



- Tuner, Complete Kit £163
- Amplifier, Complete Kit £98
- Amplifier Reprint £125

SOLENOID CONTROLLED HI FI/DIGITAL CASSETTE MECHANISM



Front loading deck with full solenoid control of all functions including optional read in fast wind modes, 12 volt operation. Fitted 3-digit memory counter and Hall IC Motion Sensor. Standard erase and stereo R/P Heads. Cheapest price ever for all these features. Only £38.90 plus VAT. Full technical specification included.

LINSLEY-HOOD 100-WATT MOSFET POWER AMPLIFIER

The very latest amplifier design, published in 'Wireless World' by the renowned John Linsley-Hood. This may now be taken as the standard by which the rest are judged! Our kit, approved by the designer, has massive heat sinks and power supply and includes all components needed to build. Case size 412mm wide, 254mm deep and 145mm high. Automatic switched speaker protection is included as standard. Cost of all parts is over £120. Our complete stereo kit price £105.50.


THIS MONTH'S SPECIAL OFFERS

DOLBY 'B' NOISE REDUCTION IC LM1011
Marvellous opportunity for home experimenters, build your own noise reduction system. Supplied complete with circuit showing typical application. Absolute knock-out price only £3.50 for two inc. VAT and post.

COMPLETE STEREO CASSETTE DECK
Brand new high quality top-loading Cassette Deck complete with Record/Play electronics. Supplied with connection data and circuit diagram. Automatic chrome/ferric switching. Only needs 9v DC supply. Total price only £18.34 inc. VAT and post.

COMPLETE STEREO TUNER MODULE
Three band LW/MW/FM Stereo Tuner fully assembled on PCB 165 x 85mm. Supplied with Ferrite rod aerial and band switch fully wired. Facility provided to drive tuning meter and stereo LED. Only needs 12v DC supply. FM sensitivity, 2.5uV. Price only £7.99 inc. VAT and post.

HALF HEIGHT 5 1/4" FLOPPY DISK

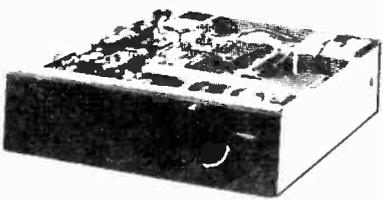

Latest MPU controlled 80 Track Drives, support single or double density. Fully compatible with Teac, Shugart and many other full and half height drives.
80 Track Single side £179
80 Track Double side £225
Full manual for each type £14.50. No VAT.

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

- HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks £5.11
 - HM90 High Beta Permalloy Head. A hard-wearing, higher performance head with metal capability £6.06
 - HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite, fantastic frequency response £9.91
 - HC55 14-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head £7.40
- Please consult our list for technical data on these and other Special Purpose Heads.

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage.

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback £4.54.
Curved Pole Type for inaccessible heads £4.95

COMPONENTS

We now list a wide range of individual components many of which are not available elsewhere. Send for your copy of our latest list which also gives further information on our Kits.

Please add part cost of post, packing and insurance as follows:

- INLAND**
Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50
- OVERSEAS**
Please send sufficient to cover
Surface or Air Post as required.

**PLEASE ADD VAT
TO ALL PRICES**



Personal callers are always very welcome but please note that we are closed all day Saturday

(0691) 652894

MANUFACTURERS & DISTRIBUTORS

COMMERCIAL CONTINENTAL CRADLE RELAYS

Medium duty miniature plug-in relays, fully interchangeable with other British and Continental types, gold flashed silver contacts. Maximum switching voltage 1 amp, 110v AC/DC (100va).
TYPE 24A02C18A. 2-pole changeover rated at 1 amp with a coil resistance of 430 ohm, nominal voltage 12v DC; approx. dimensions, length 24mm, width 19mm, height 30mm. Price £15 for 10, £135 for 100, £515 for 500. Sample sent for £2 + 35p P. & P. (£2.70 inc. V.A.T.).
TYPE 25A04C18A. 4-pole changeover relay rated at 1 amp with a coil resistance of 430R, nominal voltage 12v DC; approx. dimensions, length 24mm, width 19mm, height 30mm. Price £17.50 for 10, £158 for 100, £711 for 500. Sample sent for £2.15 + 35p P. & P. (£2.82 inc. V.A.T.).
TYPE 25A04C20A. 4-pole changeover rated at 1 amp with a coil resistance of 700R, nominal voltage 24v DC; approx. dimensions, length 24mm, width 19mm, height 30mm. Price £18 for 10, £160 for 100, £720 for 500. Sample sent for £2.25 + 35p P. & P. (£2.99 inc. V.A.T.).

CONTINENTAL CRADLE SERIES SOCKET

TYPE FR10. Cradle including clip manufactured for type 24 relay listed above, P.C.B. mounting. Price £5 for 10, £22 for 50, £40 for 100, £180 for 500, £325 for 1,000. Sample sent for 75p + 25p P. & P. (£1.15 inc. V.A.T.).
TYPE FR16. Cradle including clip manufactured for type 25 relay as listed above, P.C.B. mounting. Price £6 for 10, £27 for 50, £49 for 100, £220 for 500. Sample sent for 75p + 25p P. & P. (£1.15 inc. V.A.T.).

180° 5-Pin Din PCB Mounting Socket designed for convenience when mounting in rows with flush fit lip; approx. dimensions, height 24mm, width 21mm, depth 15mm. Price £4.50 for 50, £8.50 for 100, £50 for 500, £75 for 1,000. Sample 10 sent for £1 + 30p P. & P. (£1.50 inc. V.A.T.).

METAL FILM RESISTOR TYPE F24. Manufactured by C.G.S. Semi-precision with a standard tolerance of ±2% and a temperature co-efficient of better than 100 ppm/°C. We have a full range in stock from 100R to 1MΩ. All bandolerated. £2.50 per 1,000 any one value.

DOUBLE-POLE SINGLE-THROW ROCKER SWITCH

Panel-mounting rocker switch in white or black nylon body, and snap fit lugs, rated at 250v AC 15 amp, connected by 14in. receptacles; approx. dimensions, height 33mm, depth 23mm, width 30mm. Price £5 for 10, £23 for 50, £42 for 100, £190 for 500. Sample sent for 65p + 35p P. & P. (£1.15 inc. V.A.T.).

CONTEMPORARY-STYLE DUAL-POWER INDICATOR with green and red rectangular neons mounted in a black nylon body with snap in lugs, rated 250v operating temp up to 85° C. Approx. dimensions, height 33mm, depth 30mm, width 32mm. Neon size 20mm x 10mm-m. Price £5 for 10, £23 for 50, £42 for 100, £190 for 500. Sample sent for 65p + 35p P. & P. (£1.15 inc. V.A.T.).

Single-Pole Single-Throw Rocker Switch

Snap mounting with a black nylon body with orange centre rocker action, rated at 250v 10 amps, ambient temperatures 85° C; height 34mm, depth 14mm, width 32mm. Price £3 for 10, £13.50 for 50, £25 for 100, £113 for 500. Sample sent for 40p + 20p P. & P. (69p inc. V.A.T.).

PANEL-MOUNTED FUSE HOLDER in hard black plastic screwdriver release, for 20mm fuses up to 6.3 amp 250v with low panel profile, and shockproof construction; approx. dimensions, length 38mm mt hole dia. 13mm. Price £4 for 10, £18 for 50, £33 for 100, £150 for 500, £270 for 1,000, £480 for 2,000, £1,000 for 5,000. Sample sent for 50p + 30p P. & P. (92p inc. V.A.T.).

Miniature Low-Loss Co-Ax RG1788/U

High-quality cable with silver-plated, copper-clad steel stranded conductor 7/0.1mm extruded P.T.F.E. insulation. The screen is silver-plated copper wire. The outer sheath is FEP and coloured brown, dia. 1.91mm (temperature range -55°C to +200° C). Characteristic impedance 50 - 2R, nominal capacitance 106 PF/M maximum attenuation at 400 MHz 0.95 dB/M maximum R.F. voltage peak 1.4kv. £60 for 100 metres, £270 for 500 metres, £486 for 1,000 metres, £2,180 for 5,000 metres. Sample 50 metres sent for £30 + £2 P. & P. (£36.80 inc. V.A.T.).

Terms c.w.o. Please add 5% to all orders for carriage plus 15% V.A.T. Export enquiries welcome. We find it possible to advertise all we stock. Please telephone or write for further enquiries. Personal callers always welcome.

ELECTRONIC EQUIPMENT CO.

SPRINGFIELD HOUSE
TYSSEN STREET, LONDON, E.8
TELEPHONE: 01-249 5217
TELEX: 9853906 EECO.G

WW - 073 FOR FURTHER DETAILS

VALVES

		Minimum Order £1	VALVES VAT IS INCLUDED								
A1065	1.40	EF89	1.05	PFL200	1.10	2900U	3.45	6807A	0.85	624	0.70
A2293	8.80	EF91	1.50		2.80*	2801U	3.75	68R7	4.80	9D6	2.90
A2900	13.75	EF92	2.90	PL36	1.10	2803U	16.00	68W6	6.20	11E2	19.50
AR8	0.75	EF95	0.65	PL81	0.85	2900T	2.45	68W7	1.80	12A6	0.70
ARP3	0.70	EF96	0.60	PL82	0.70	1A3	0.85	6C4	0.50	12AT6	0.70
ATP4	0.60	EF193	0.60	PL83	0.60	1L4	0.50	6C6	0.55	12AT7	0.85
BT21	0.90	EF184	0.80	PL84	0.95	1R5	0.60	6CH6	8.20	12AU7	0.80
CY31	1.40	EF812	0.75	PL504	1.00	1S4	0.45	6CL6	2.75	12AV6	0.95
DAF96	0.70	EFH200	1.85	PL508	2.40	1S5	0.45	6CW4	8.50	12AX7	0.65
DET22	28.50	EF90	0.85	PL509	5.65	1T4	0.45	6CX8	3.80	12BA6	0.90
DF96	0.70	EL32	1.10	PL519	5.80	1U4	0.80	6CY5	1.15	12BE6	1.25
DH786	0.75	EL34	1.80	PL802(SE)	2.95	1X2B	1.40	6D6	0.70	12BH7	1.95
DL92	0.60		2.90*	PY80	0.70	2X2A	2.55	6F1	1.60	12E1	18.95
DY86/87	0.65	EL37	5.20	PY81/800	0.85	3A4	0.70	6FG6B	1.10	12J6GT	0.55
DY802	0.70	EL82	0.70	PY82	0.85	3AT2	2.40	6F7	2.80	12K7GT	0.70
E92CC	2.80	EL84	0.80	PY88	0.60	3B2T	12.00	6F8G	0.85	12K8GT	0.80
E180F	7.70	EL86	0.95	PY500A	2.10		19.50*	6F12	1.50	12Q7GT	0.60
E192CC	6.25	EL90	1.00	QQV03/10	3.20	3D2	0.50	6F14	1.15	12SC7	0.65
EA76	2.25	EL91	4.20	QQV03/20	7.50*	3E29	23.00	6F15	1.30	12SH7	0.65
EABC80	0.80	EL95	0.80			3E29	19.00	6F17	3.20	12SJ7	0.70
EB91	0.60	EL504	1.70		21.50	3S4	0.60	6F23	0.75	12SQ7	1.45
EBBC33	1.15	EL803	5.90	QQV03-25A	4832	3B4	18.25	6F24	1.75	12SQ7GT	0.85
EB92	0.90	EL509	3.95		36.50	5R4G	1.80	6F33	10.50	12YA	0.70
EBF80	0.60	EL821	8.20	QQV06/40A	19.50	6X4	0.75	6F6B	12.50	13D3	2.80
EBF83	0.60	EL822	9.95		95.00	5V4G	0.75	6GAB	1.95	13D5	0.90
EBF89	0.60	EL800(SE)	2.80	QQV03-12	4.20	5Y3GT	0.95	6GH8A	1.95	19AQ5	0.85
EC52	0.65	EM80	0.85	SP61	1.80	5Z3	1.50	6H6	1.60	19G3	11.50
EC91	4.40	EM87	1.30	TT21	23.00	5Z4G	0.75	6JU6	5.85	19G6	8.50
EC92	0.85	EY51	0.85	TT22	23.00	5Z4GT	1.05	6J4	1.35	19H5	39.55
ECC81	0.85	EY81	0.65	UBC41	1.20	6/30L2	0.90	6JAWA	2.00	12A1	0.80
ECC82	0.60	EY86/87	0.60	UABC80	0.75	6A87	0.70	6J5	2.30	20E1	1.30
ECC83	0.65	EY88	0.65	UAF42	1.20	6AC7	1.15	6JST	0.90	20P1	0.65
ECC84	0.60	EZ80	0.70	UBF80	0.70	6AG5	0.60	6J6	0.65	25L6GT	0.95
ECC85	0.60	EZ81	0.70	UBF89	0.70	6AH6	1.15	6J6W	0.90	25Z4G	0.75
ECC88	0.80	GMA4	5.90	UC94	0.85	6AK5	0.65	6K7	0.80	35W4	0.80
ECC189	0.95	GY501	1.30	UC885	0.70	6AK8	0.60	6KD6	4.50	85A2	1.40
ECC804	0.90	GZ32	1.05	UCF80	1.30	6AL5	0.60	6L8M	2.80		2.55*
ECF80	0.85	GZ33	4.20	UCH42	1.65	6AL5W	0.85	6L6GC	2.65	807	1.90
ECF82	0.65	GZ34	2.75	UCH81	0.75	6AM5	4.20	6L6GT	1.25	813	19.32
ECF801	1.05	GZ37	3.95	UCL82	0.95	6AM6	1.50	6L8	0.70		68.50*
ECH34	2.25	K166	7.80	UF41	1.35	6AN8A	2.50	6LD20	0.70	829B	16.00
ECH42	1.20		11.20*	UF80	0.95	6A04	3.40	6O7G	1.30	832A	8.90
ECH81	0.70	K788	10.50	UF85	0.95	6A05	1.00	6SA7	1.00	866A	3.80
ECH84	0.80		13.80*	UL84	0.95	6A05W	1.80	6S67	1.15	866E	6.25
ECL80	0.70	MH4	2.50	UM80	0.90	6A56	1.15	6S7J	0.95	931A	13.80
ECL82	0.75	ML6	2.50	UM84	0.70	6AT6	0.90	6SK7	0.95	954	1.20
ECL85	0.80	N78	9.90	UY82	0.70	6AUB	0.60	6SL7GT	0.85	955	12.0
ECL86	0.90	OA2	0.70	UY85	0.85	6AV6	0.85	6SN7GT	0.80	956	1.20
EF37A	2.15	OB2	0.80	VR105/30	1.25	6AX4GT	1.30	6S07	0.95	5763	4.80
EF39	1.25	PCL82	0.95	VR150/30	1.35	6AX5GT	1.30	6V6G	1.50	6060	1.95
EF80	0.65	PCL84	0.90	X66	0.95	6BA6	0.55	6V8GT	0.95	6080	5.30
EF82	1.75	PCL86	0.75	X61M	1.70	6BB6	0.60	6X4	0.95	6146	5.80
EF85	0.60	PCL805/85	0.95	Z759	19.00	6CB6G	1.60	6XS7	0.85	6146B	5.80
EF86	0.75	PD500/510.40	Z749	0.75	6B3J	1.30	6Y6G	0.90	6360	2.85	

VALVES AND TRANSISTORS

Telephone enquiries for valves, transistors, etc. retail 749 3934, trade and export 743 0899

FIELD TELEPHONE TYPE "J"

Tropical, in metal cases.

10-line MAGNETO SWITCH-BOARD

Can work with every type of magneto telephones.

PRICES MAY VARY

POSTAGE: £1-£3 45p; £3-£5 55p; £5-£10 60p; £10-£15 80p; £15-£20 100p.

COLOMOR (ELECTRONICS LTD.) 170 Goldhawk Rd, London W12

Tel. 01-743 0899 or 01-749 3934. Open Monday to Friday 9 a.m.-5.30 p.m. ww-20

WW - 065 FOR FURTHER DETAILS

YOU HAVEN'T SEEN ANYTHING LIKE THIS ON A COLOUR MONITOR BEFORE.

An RGB monitor from JVC offering a resolution of 370 x 470 pixels for less than £150?

We guarantee you won't see another bargain like that in this or any other micro mag—or in any other supplier's showroom.

For we've managed to acquire the sole distribution rights to these superb machines and we are able to offer them at an unbeatable price.

There are two models available: medium resolution (370 x 470 pixels) at £149.95, and high resolution (580 x 470 pixels) at £229.95. (Both excluding VAT.)

The units have a 14" screen and are suitable for the BBC Micro, Lynx, Oric, Apple, IBM and most other leading micros.

They are robustly constructed in a handsome cream casing. And come with a full year's guarantee.

Delivery is good: your monitor should arrive by courier service within ten days of our receiving your order.

You can order by filling in the coupon below and posting to: Opus Supplies Ltd., 158 Camberwell Road, London SE5 0EE. Or by telephoning 01-701 8668 quoting your credit card number. Or, of course, you can buy in person at our showroom between 9-5.30 pm, Monday-Saturday.



MODEL REFERENCE	1302 1 Medium Resolution	1302 2 High Resolution
RESOLUTION	370 x 470 Pixels	580 x 470 Pixels
C.R.T.	14"	14"
SUPPLY	220/240v. 50/60Hz.	220/240v. 50/60Hz.
E.H.T.	Minimum 19.5kv Maximum 22.5kv	Minimum 19.5kv Maximum 22.5kv
VIDEO BAND WIDTH	6MHz	10MHz
DISPLAY	80 characters by 25 lines	80 characters by 25 lines
SLOT PITCH	0.63mm	0.41mm
INPUT: VIDEO	R.G.B. Analogue/ TTL Input	R.G.B. Analogue/ TTL Input
SYNC	Separate Sync on R.G.B. Positive or Negative	Separate Sync on R.G.B. Positive or Negative
EXTERNAL CONTROLS	On/off switch and brightness control	On/off switch and brightness control

To Opus Supplies Ltd., 158 Camberwell Road, London SE5 0EE.

Please send me _____ Medium Resolution Colour Monitor(s)
at £149.95 each (ex. VAT).

_____ High Resolution Colour Monitor(s) at
£229.95 each (ex. VAT).

_____ Connection lead(s) at £6.00 each.

I understand carriage per monitor will cost an extra £7.00.

(N.B. A Medium Resolution Monitor including VAT, lead, and carriage costs £187.39. A High Resolution Monitor including VAT, lead, and carriage costs £279.39.)

I enclose a cheque for £_____. Or please debit my credit card
account with the amount of £_____. My Access/B Barclaycard
(please tick) no. is _____

Name _____

Address _____

Telephone: _____

Opus.
Opus Supplies Ltd.

WW6

WW - 051 FOR FURTHER DETAILS

You need Electronic Components? You need us!

AEL COMPONENTS concentrates on the demands of export markets. Our success is built on meeting the requirements of overseas buyers for electronic components. We supply:

Organisations Worldwide with Electronic Equipment to Maintain. Equipment Manufacturers. Universities, Training Colleges and Schools for training projects.

SEMICONDUCTORS


From germanium diodes to microprocessor circuits. You will use a selection from many of the 250,000 types currently available. Our extensive purchasing power and VAST EXPERIENCE enables us to supply more types than any other single source. We are better qualified than most to offer suitable replacements for obsolete types.

PASSIVE COMPONENTS

To complete your package, we recognise a wide variety of RELAYS – CONNECTORS – LAMPS, etc., and can offer all types of RESISTORS and CAPACITORS against specification.

ELECTRONIC TUBES

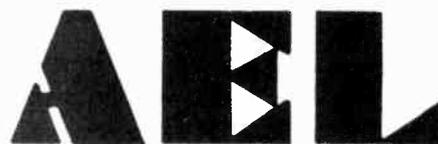We know and can supply 30,000 types using our extensive cross referencing capability to give you the best buy. All leading UK, USA, Western European and Japanese brands are available, in addition to our own competitively-priced AEL brand. It is part of our service to stock or be able to source the increasing number of tubes difficult to locate.



COMPONENTS DIVISION

AEL COMPONENTS DIVISION, GATWICK HOUSE, HORLEY, SURREY, ENGLAND RH6 9SU
TEL: HORLEY (02934) 5353 - TELEX: 87180 - CABLES: AEROCON TELEX HORLEY

WW – 062 FOR FURTHER DETAILS

Sowter Transformers

With 40 years' experience in the design and manufacture of several hundred thousand transformers we can supply:

**AUDIO FREQUENCY
TRANSFORMERS OF EVERY TYPE
YOU NAME IT! WE MAKE IT!
OUR RANGE INCLUDES**

Microphone transformers (all types), Microphone Splitter/Combiner transformers, Input and Output transformers, Direct Injection transformers for Guitars, Multi-Secondary output transformers, Bridging transformers, Line transformers, Line transformers to G.P.O. Isolating Test Specification, Tapped impedance matching transformers, Gramophone Pickup transformers, Audio Mixing Desk transformers (all types), Miniature transformers, Microminiature transformers for PCB mounting, Experimental transformers, Ultra low frequency transformers, Ultra linear and other transformers for Transistor and Valve Amplifiers up to 500 watts, Inductive Loop Transformers, Smoothing Chokes, Filter, Inductors, Amplifier to 100 volt line transformers (from a few watts up to 1,000 watts), 100 volt line transformers to speakers, Speaker matching transformers (all powers), Column Loudspeaker transformers up to 300 watts or more.

We can design for RECORDING QUALITY, STUDIO QUALITY, HI-FI QUALITY OR P.A. QUALITY. OUR PRICES ARE HIGHLY COMPETITIVE AND WE SUPPLY LARGE OR SMALL QUANTITIES AND EVEN SINGLE TRANSFORMERS. Many standard types are in stock and normal dispatch times are short and sensible. OUR CLIENTS COVER A LARGE NUMBER OF BROADCASTING AUTHORITIES, MIXING DESK MANUFACTURERS, RECORDING STUDIOS, HI-FI ENTHUSIASTS, BAND GROUPS, AND PUBLIC ADDRESS FIRMS. Export is a speciality and we have overseas clients in the COMMONWEALTH, E.E.C., USA, MIDDLE EAST, etc. Send for our questionnaire which, when completed, enables us to post quotations by return.


E. A. Sowter Ltd.

Manufacturers and Designers

E. A. SOWTER LTD. (Established 1941) : Reg. No. England 303990
The Boat Yard, Cullingham Road, Ipswich IP1 2EG, Suffolk
P.O. Box 36, Ipswich, IP1 2EL, England
Phone: 0473 52794 and 0473 219390
Telex 987703G Sowter

WW – 059 FOR FURTHER DETAILS

FIBRE-OPTICS EDUCATOR

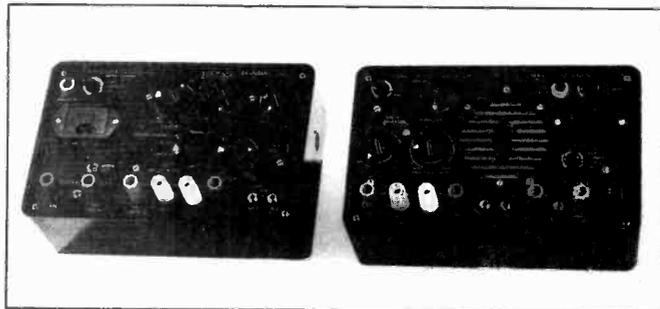

A New Concept in Optical Equipment

The Fibre-Optics Educator is a **low-cost**, versatile instrument designed primarily for organisations involved in or about to enter the field of fibre-optics.

It can function as:

TEST EQUIPMENT e.g. for accurate fibre attenuation measurements to a range of 50dB, optical level measurements, and for testing out analogue and digital optical transmitters and receivers. Also, it may be set to give an audible indication of low level infra-red radiation using the analogue loudspeaker output or the digital buzzer output, with a length of optical cable acting as a probe.

TRANSMISSION EQUIPMENT for both **analogue** and **digital** data, over **free-space** as well as **optical fibres**. *It is also ideal for:*

TRAINING engineers, technicians and executives in the growing field of fibre-optics. Suitable for industry, colleges and technology training centres.

The Fibre-Optics Educator comprises fully portable optical transmitter and receiver units, optical cables, together with numerous accessories, a comprehensive manual, and carrying case.

Designed and Manufactured in the U.K.

For further details contact:

ELLMAX Electronics Ltd.,
Unit 29, Leyton Business Centre,
Elloe Road, Leyton, London, E10 7BT.
Tel: (01) 539 0136

**ELLMAX
ELECTRONICS**

WW – 017 FOR FURTHER DETAILS

MARCONI SIGNAL GENERATORS

TF2002A/S (illustrated) 10kHz-72MHz AM/FM. £750
TF2002. As above but AM only. £450

MARCONI TF1066B. AM/FM Generator. 10-470MHz. 0.2uV-200mV output. FM Deviation up to ±100kHz.

MARCONI TF995A/5. AM/FM Generator. Narrow deviation model 995 covering 1.5-220MHz. £450.
TF2015. 10-520MHz. AM/FM. TF144H. AM 10kHz-72MHz. £295.

MARCONI TF1064B/5. AM/FM Signal generator covering in three ranges 68-108, 118-185 and 450-470MHz. FM fixed deviations of 3.5 & 10kHz. AM fixed 30%. £225

'DOLBY' NOISE WEIGHTING FILTERS

Cat. No. 98A. Noise weighting filters for CCIR/ARM signal-to-noise ratio measurements. As new units. £40 each (+£1 p&p).

BECKMAN TURNS COUNTER DIALS

Miniature type (22mm diam.). Counting up to 15 turn "Helipot". Brand new with mounting instructions. Only £2.50 each.

RFI RECEIVER

Stoddart Model NM52A. RF Noise & Field intensity measuring receiver. 375MHz-1GHz c/w power supply unit.

KAY SOUND SPECTROGRAPH

Model 6061B with Amplitude Display, scale magnifier. 85Hz-16kHz. Complete sound spectrograph in excellent condition.

★★ STEPPER MOTORS ★★

Brand new stock of 'ASTROSYN' Type 20PM-A055 stepper motors. 28V DC. 24 steps per rev. 15 oz-in torque @ 100PPS. Body length 2 1/2", diameter 2", shaft 1/4" diam x 4 1/4" spirally threaded. Weight 16oz. Price each £15 (p&p 50p). Connections supplied.

★ MILLI-VOLT MEASUREMENT, ANALOGUE ★

MARCONI TF2600. Twelve ranges 1mV-300V FSD. Wide-band to 10MHz.

MARCONI TF2603. Frequency range 50kHz-1.5GHz. High Sensitivity from 300uV.

MARCONI TF2604. Electronic Multi-meter. AC/DC 300mV Full scale to 300V (1kV DC). Resistance ranged. AC Frequency range 20Hz-1500MHz.

★★ CONSTANT VOLTAGE TRANSFORMERS ★★

'ADVANCE VOLSTAT'. Type. Model MT140A. Mains input 190-260V AC. Output 230V AC @ 150W. Price each £20 + VAT + £2 carriage.

P. F. RALFE ELECTRONICS
10 CHAPEL STREET, LONDON, NW1 TEL: 01-723 8753

'OSCILLOSCOPES' PLEASE PHONE FOR CURRENT STOCK

TEKTRONIX 453. Dual-trace 50MHz.
TEKTRONIX 565. Dual time-base. Differential plug-ins.
SOLARTRON CD1740. 50MHz sweep-delay £350.
MARCONI TF2210. Dual-trace, 100MHz, sweep-delay £350.
DYNAMCO D7200 Mains/Battery portable. Dual-trace 15MHz £225.



N.B. We have a frequent stock turnover of good, used 'scopes. Should you have a specific requirement for any item of test equipment we would be pleased to test your enquiry.

MARCONI TF2502 RF Power meters. DC-1GHz. 10w fsd £350.
MARCONI TF2701 In-Situ Universal component Bridge £250.
MEGGER-5KV insulation tester. Hand-crank. PHILIPS Model PM8041. X-Y Recorder.
MARCONI TF2343A Quantization Distortion Meter £150.
HEWLETT-PACKARD 3450A Multi-Function Digital Multi-Meter.
ROHDE & SCHWARZ 'SDR' AM signal generator 0.3-1GHz.
HEWLETT-PACKARD 608C. AM signal generator 10-480MHz.
TGL Spectrum Analysers model SA102. 0-500MHz. Brand new factory units. 0-500MHz. Send for specifications. £650.

★ INSULATION TESTERS ★

Transistorised 'Metrohm' 250V & 500V £40
Transistorised 'Megger' 500V £60
Hand-Crank 'Megger' 500V £60
Supplied in fully tested excellent condition

★ BRUEL & KJAEER ★

Model 2008 Heterodyne Voltmeter. AM/FM/Voltage and Modulation measurements from 0.5-240MHz. £165

★ SWEEPERS ★

TELONIC Sweep generator system type 2003. Fitted with Marker, attenuator, Detector plug-in units and Generator covering 800-1500MHz. £325

★ MUIRHEAD FACSIMILE UNITS ★

MUFAX 'COURIER' facsimile receiver type K441-CH and transmitters K400 AMCH in stock in excellent condition £250 per pair.

PLEASE NOTE. All the pre-owned equipment shown has been carefully tested in our workshop and reconditioned where necessary. It is sold in first-class operational condition and most items carry a three months' guarantee. For our mail order customers we have a money-back scheme. Repairs and servicing to all equipment at very reasonable rates. PLEASE ADD 15% VAT TO ALL PRICES.

★ COMPUTER PERIPHERALS ★

8" FLOPPY DISK DRIVES

DRE (Data Recording Equipment) Model 7100 Single-sided floppy disk drives in stock now at vastly reduced prices. Supplied BRAND NEW in manufacturers sealed cartons. CAPACITY 0.8MBytes. Hard/Soft sectoring ANSI/ECMA Standards compatible. Measures 4 1/2 x 8 1/2 x 14". Weight 13lbs. PRICE £150 + VAT. Securicor despatch if required + £10 + VAT. 7200 (Double-sided) £250

8" WINCHESTER DRIVES

United Peripherals type 3100 Minidisc Drives CAPACITY over 19MBytes. Power supply requirements 5V DC at 4A. +24V DC at 3A. Measures 17x8x7". Limited quantity only available in BRAND NEW condition. £250 each + VAT. Carriage details as above.

4000-SERIES HARD DISK DRIVES

Data Recording Equipment 4000-Series exchangeable IBM-type 5440 Disks. Units available ex-stock and BRAND NEW. Please call us for our lowest ever quotation.

★ DISK CARTRIDGES ★

Surplus BASF 12-Sector RK05 cartridges available in small quantity only remaining at £15 each. Carriage each £1.50.

★ SWITCHING POWER SUPPLIES ★

The following DC power supplies are available now from stock in limited quantities. All fully tested and guaranteed.

3.5V @ 10 Amps.....	£15	5V @ 10 Amps.....	£15
5V @ 20 Amps.....	£20	5V @ 40 Amps.....	£30
5V @ 60 Amps.....	£40	19V @ 30 Amps.....	£40
+15V, -12V & +5V @ 11A, 4A and 40A.....	£50		

All prices + VAT please. Carriage + £2 each

★ CENTRIFUGAL BLOWERS ★

'TORIN' Type U62B1. 230V Cap'Start (supplied), very powerful (200W, 3,000rpm) centrifugal fans for large rack cooling or enclosure extraction applications. Overall dimensions 20x12 cms, outlet 6x4 cms. BRAND NEW. Surplus stock. £15 each inc. VAT, pp £1.50.

★ ROTRON INSTRUMENT COOLING FANS ★

Supplied in fully tested excellent condition, as follows:

- 115V, 4 1/2 x 4 1/2 x 1 1/2" £5. 230V same size £5.50.
- 115V 3 x 3 x 1 1/2" £4. 230V 3" size, brand new £6. Also small quantity 115V 4 1/2" size, brand new £6. Postage each + 50p please.

ww10

DIN 41612 TWO PART EUROCARD (INDIRECT EDGE) CONNECTORS MADE IN ENGLAND BY DOWTY UECL

SPECIFICATION: Designed to BS9525 and DIN 41612. Flame retardant polyester moulding. Twin cantilever socket contacts. Current rating per contact: 2A at 20°C. Working Voltage 350V D.C./A.C. Other Terminal Styles and Configurations in stock. Please phone for full stock list.

All below types available ex-stock.

Connector	No. of Contacts	Termination	Pitch	Moulding Size	Contact Rows used	Order Code	Price ea.	Price ea.
							10-99 pcs	100-499 pcs*
PLUG	32	90° SPILL	2.54mm	2 ROW	A	20100	£0.60	£0.51
PLUG	64	90° SPILL	2.54mm	2 ROW	A+B	20500	£0.85	£0.72
PLUG	64	90° SPILL	2.54mm	2 ROW	A+C	20900	£0.85	£0.72
PLUG	96	90° SPILL	2.54mm	3 ROW	A+B+C	21100	£1.20	£1.00
SOCKET	32	4mm STRAIGHT SPILL	2.54mm	2 ROW	A	20202	£0.75	£0.63
SOCKET	32	13mm WIRE WRAP	2.54mm	2 ROW	A	20206	£0.75	£0.63
SOCKET	64	4mm STRAIGHT SPILL	2.54mm	2 ROW	A+B	20602	£1.20	£1.00
SOCKET	64	13mm WIRE WRAP	2.54mm	2 ROW	A+B	20606	£1.20	£1.00
SOCKET	64	4mm STRAIGHT SPILL	2.54mm	3 ROW	A+C	21002	£1.20	£1.00
SOCKET	64	13mm WIRE WRAP	2.54mm	3 ROW	A+C	21006	£1.30	£1.10
SOCKET	96	13mm WIRE WRAP	2.54mm	3 ROW	A+B+C	21206	£1.80	£1.53

* Further quantity discounts on application *

J.P.R. ELECTRONICS UNIT M, KINGSWAY INDUSTRIAL ESTATE, LUTON, BEDS LU1 1LP
TELEPHONE: LUTON (0582) 410055. TELEX 925859 Attn J.P.R.

WW - 006 FOR FURTHER DETAILS

SALE P.&R. COMPUTER SHOP SALE

IBM GOLFBALL PRINTERS from £70 EACH + V.A.T.

INTERFACE FOR IBM GOLFBALL £40 + V.A.T.
CENTRONIC 779 PRINTERS - £200 + V.A.T.
CENTRONIC 781 PRINTER - £225 + V.A.T.
POWER UNITS 15 VOLT 10 AMP - £20 EACH
FANS, PCBs, KEYBOARDS AND LOTS MORE
8-INCH BURROUGHS FLOPPY DISC DRIVES

COME AND LOOK AROUND

SALCOTT MILL, GOLDHANGER ROAD
HEYBRIDGE, MALDON, ESSEX
PHONE MALDON (0621) 57440
Hours: Mon-Fri. 9am to 5pm. Sat. till 1pm

WW - 008 FOR FURTHER DETAILS

AMBISONIC SURROUND SOUND DECODERS

Ambisonic surround sound gives a realism in the reproduction of music that is hard to describe without using hackneyed expressions like 'natural' and 'being there'. Positioning of the performer becomes obvious and the acoustic of the original environment comes through to the listening room. The Minim decoders also provide enhanced results from conventional stereo material. We can now supply UHJ encoded records, tapes and compact discs.

And don't forget our other products:

PROGRAMMABLE WEEKLY TIME SWITCHES
TELEVISION SOUND TUNERS

Please send me information on Timeswitches/Television Tuners/Ambisonics

Name.....
Address.....

Minim Electronics Limited, Lent Rise Road
Burnham, Slough SL1 7NY. Tel. Burnham 63724 ww2

WW - 072 FOR FURTHER DETAILS

TRANSFORMERS EX-STOCK

MAINS ISOLATORS				50/25V or 25-0-25V				30/15V or 15-0-15V			
VA	Price	P&P		2x25V tapped secs.	2x15V tap Sec. Volts	3, 4, 5, 6, 8, 9, 10, 13, 14, 15, 16, 20, 24, 30 or 33, 40	15, 17, 20, 25 or 25-0-25V	5	1	3.19	1.20
*20	5.82	1.60		5	1	4.32	1.40	2	4	6.39	1.60
*60	9.49	1.80		2	4	8.10	1.85	3	6	8.10	1.85
100	11.08	2.00		4	8	11.95	2.00	5	10	11.95	2.00
200	15.69	2.25		6	12	18.10	2.26	8	16	18.10	2.26
250	18.97	2.64		8	16	24.52	2.70	10	20	20.88	2.26
350	23.47	2.70		3	6	10.36	1.94	4	8	9.67	1.90
500	29.23	2.95		4	8	14.10	2.12	5	10	11.95	2.00
750	41.28	3.70		6	12	18.10	2.20	8	16	18.10	2.26
1000	53.00	4.00		8	16	24.52	2.70	10	20	20.88	2.26
1500	68.37	4.70		10	20	30.23	3.00	12	24	36.18	3.20
2000	82.27	5.10		12	24	36.18	3.20	15	30	36.60	3.00
3000	115.35	0A						20	40	35.64	4.83
6000	203.65	0A									

400/440V ISOLATORS				60V 30V Price P&P			
400/440 to 200/240V	Price	P&P		60V	30V	Price	P&P
60	9.50	1.80		5	1	4.70	1.50
100	11.08	2.00		2	2	7.15	1.50
200	15.68	2.25		1	4	9.20	1.90
250	18.97	2.40		3	6	13.31	2.00
350	23.47	2.70		4	8	15.25	2.20
500	29.23	2.95		5	10	19.16	2.20
750	52.98	4.00		6	12	21.86	2.65
1000	52.98	4.00		8	16	30.72	3.00
2000	82.27	5.00		10	20	35.76	3.00
3000	115.37	0A		12	24	41.22	3.50
6000	228.75	0A					

12/24V or 12-0-12V				CASING SERVICE			
2x12V Secs. Pri. 220-240V	Price	P&P		Transformers can be	case in sturdy metal	ventilated boxes. Cable	in/out; USA 3 pin sockets, or
12V	1.15	2.41	90	13A to order. Phone/	Write for quotes.		
1	1.5	3.19	1.20				
2	1	4.25	1.20				
4	2	4.91	1.60				
6	3	7.69	1.60				
8	4	8.98	1.60				
10	5	9.82	1.80				
12	6	10.89	1.90				
16	8	12.97	2.12				
20	10	17.46	2.44				
30	15	21.69	2.64				
60	30	44.45	0A				

MINIATURES (SCR)
Pri. 240V

Sec V	A	Pri	P&P
3-0-3	2A	3.11	90
6x2	1A x 2	3.45	1.20
9-0-9	1	2.59	90
9x2	3x2	2.41	90
8.9x2	5x2	3.36	1.20
8.9x2	1A x 2	4.27	1.40
15x2	2A x 2	4.41	90
12-0-12	05	3.11	90
20x2	3x2	3.39	1.20
20x12.0			
7.0D	4.13	1.20	
15.20x2	1A x 2	5.60	1.60
15.27x2	5x2	4.83	1.40
15.27x2	1A x 2	7.30	1.60

96/48V. Pri 2x120V
Secs 2x36/48V

72/96	36/48	Price	P&P
5	1	5.37	1.20
2	4	14.69	2.40
3	6	17.79	2.40
5	10	32.23	3.20
6	12	40.36	3.50
8	16	44.03	3.75

TRANSFORMERS EX-STOCK

INVERTERS
Cont. Rated. Casod.
12/24V DC in. 240V 13A
skt. AC out.

100V.....	£57.00
250V.....	£152.50
500V.....	£239.50
1000V.....	£317.50

CONSTANT VOLTAGE TRANSFORMERS
Spike-free stable mains supplies

120VA £131.12
250VA £157.36
500VA £219.91
1kVA £336.40
2kVA £594.50
5kVA £1587

AVOS & MEGGERS
8 Mk.5 (latest model) £128.10
73 £73.60
MM5 Minor £46.50
DA212 LCD Digital £89.90
DA116 LCD Digital £140.30
DA117 Autorange LCD £157.00
Megger 500V, Hand Gen £108.50
Megger Battery BM7 £85.50
P&P £2.00 VAT 15%

BURGLAR ALARM
Ultrasonic portable, looks like a speaker. £99.00 + VAT 15%.

- Just plugs in
- No wiring
- Sound siren
- Exit/Recharge delays
- Rechargeable battery

PLEASE ADD 15% VAT TO ALL ITEMS

BARRIE ELECTRONICS LTD
Unit 211, Stratford Workshops
Burford Road,
London E15 2SP
Tel: 01-555 0228 (3 lines) WWW-6

WW - 021 FOR FURTHER DETAILS

TRANSEL DOT MATRIX PRINTER Compact Serial Interface 230V With info. £65 each
9" MONITOR. Cased. Non-Standard, with info. £20 each
12" MONITOR Cased. Non-Standard, with info. £40 each

AZTEC 20" Black & White Monitor. Video In £50 each
TV Style 20" MONITOR Black & White. Video In £30 each

COSSOR VDU with KEYBOARD type CD03000. 12" Green Screen. V24/20MA or TTL compatible, with info. £55 each

CENTRONIC 704 DOT MATRIX PRINTER RS232C Upper & Lower case. Variable paper width £250

1	TEKTRONIX 475 Scope 200MHz Dual Trace Delay Sweep.	£1600
2	TEKTRONIX 453 Scope 50MHz Dual Trace Delay Sweep.	£500
3	TEKTRONIX 647A Scope 100MHz Dual Trace Delay Sweep.	£450
4	MARCONI TF2210 Scope 100MHz Dual Trace Dual Tr. Delay Sweep.	£400
5	PHILIPS PM3234 Storage Scope with Memory 10MHz Dual Trace.	£1200
6	TEKTRONIX 549 Storage Scope 30MHz Dual Trace Dual Tr. Delay Sweep.	£200
7	TEKTRONIX 564B Storage Scope 10MHz Dual Trace Delay Sweep.	£395
8	SOLARTRON CO1400 Scope 15MHz. Dual Beam.	£90
9	COSSOR C00150 Scope 35MHz Dual Trace Delay Sweep.	£195
10	TELEQUIPMENT S43 Scope 25MHz Single Beam.	£75
11	B & K BEAT FREQUENCY OSCILLATOR type 1013.	£25
12	B & K RANDOM NOISE GENERATOR type 1402.	£125
13	B & K ELECTRONIC VOLTMETER type 2409. 2Hz-200kHz.	£30
14	MARCONI SIG GEN TF144H/S 10kHz-72MHz.	£125
15	MARCONI WIDE RANGE OSC TF1370A 10Hz-10MHz.	£95
16	MARCONI FM/AM SIG GEN TF995A/3S 15-220MHz AM/FM Mod.	£110
17	MARCONI R.F. POWER METER TF1020A 1.50 ohm.	£75
18	MARCONI SIG GEN TF1060 2.450/1200MHz. Late style.	£90
19	MARCONI R.F. POWER METER TF1152 Range 50 ohm.	£50
20	MARCONI SIG GEN TF2002A/S AM/FM 10kHz-72MHz.	£475
21	MARCONI SIG GEN TF2002. As above. AM only.	£250
22	MARCONI POWER METER TF893A 20Hz-35kHz.	£50
23	MARCONI UNIVERSAL BRIDGE TF68.	£150
24	MARCONI SENSITIVE VALVE VOLTMETER TF2500 10MHz-1mV-300V.	£75
25	HEWLETT PACKARD DVM 3440A with Automatic Range Selector 3442A.	£30
26	H.P. VHF SIG GEN 608C 10-480MHz.	£150
27	H.P. CALCULATOR PLOTTER 9125A with Extended Memory 9101A and Cal Buffer 9102A.	£250
28	FLANN MICROWAVE SIGNAL SOURCE type PCLS-1-4GHz.	£195

31	FLANN SIGNAL GEN type 501 P.S. 0.575-3GHz.	£175
32	BRADLEY OSCILLOSCOPE CALIBRATOR type 156.	£135
33	ELLIOT TRANSISTOR CURVE DISPLAY type B100.	£150
34	FENLOW SPECTRUM ANALYSER S44. 0.3Hz-25kHz with Plotter P4.	£195
35	ADVANCE AM/FM SIG GEN SG63F. 4-230MHz.	£125
36	ADVANCE SIG GEN SG62B. 150kHz-220MHz. CW/Mod.	£60
37	ADVANCE SIG GEN E2. 100kHz-100MHz. CW/Mod.	£40
38	WAYNE KERR UNIVERSAL BRIDGE CT530 (B221A) with LOW IMPEDANCE ADAPTOR 0221A.	£125
39	WAYNE KERR SIG GEN type S121. 10Hz-120kHz.	£40
40	BRYAN'S X-Y RECORDER type 24000 A3 size. With manual.	£150
41	CALCOMP PLOTTER Model 565 Step size 1mm 1/2" Barrel. With manual.	£175
42	TEKTRONIX TIME MARK GENERATOR type 184.	£125
43	TEKTRONIX SQUARE WAVE GEN type 106.	£20
44	AVO TRANSISTOR TESTER type TT165 with leads (P&P £2).	£20
45	AVO VALVE TESTER type CT160. 22 Valve bases.	£20
46	FOSTER INSTRUMENTS PORTABLE POT. Model 3156E.	£45
47	BRANDENBURG POWER SUPPLY Model 374SEL 1kV.	£75
48	MUIRHEAD K134-A WAVE ANALYSER 3Hz-300kHz.	£95
49	AIRMEC WAVE ANALYSER type 248. 5-300 MHz.	£75
50	TEKTRONIX TIME MARK GEN type 180A.	£40
51	ROBAND TRANSISTORISED P.U. type TVS307/2. Metered 0H-30V. 0-2A.	£40
52	CROPOIC RESISTANCE BRIDGE SMITH No 3.	£60
53	TINSLEY VERNIER POTENTIOMETER type 4363.	£35
54	PVC PRECISION VERNIER POT. Cat No 7568.	£30
55	ADVANCE STAB HT-L SUPPLY type P.P.1. Metered Scaled 0-500/0-50mA, 0-1000/0-250V, 0-8/0-0V, 0 to 200V.	£50
56	MARCONI DOUBLE PULSE GEN TF1400S with TM6800/S. 10Hz-100kHz 100 nsecs-100 uSecs.	£30
57	AIRMEC MILLIVOLTMETER type 264A. 20Hz-10MHz.	£25
58	VARIAC 8 amp. Cased 0-270Volts.	£25
59	AUTO TRANSFORMER 1000VA Brand New.	£15
60	TELEQUIPMENT S54A Scope 10MHz. Single Beam. Solid State.	£110
61	AIRMEC Sig Gen type 204 1-320MHz AM/FM Mod.	£35
62	FARNELL STAB P.U. TVS303/SEC. 30V 5A.	£30
63	ROBAND TRANSISTORISED P.U. T139. Twin 50V 5A.	£40
64	MARCONI CIRCUIT MAGNIFICATION METER TF1245 with TF1246.	£300

EXECUTIVE TELEPHONES - PUSH BUTTON

Many functions including 10 number memory, repeat dialling, etc. Will connect to GPO System. Brand New. £25 each. P&P £4.

EQUIPMENT IN WORKING ORDER

Please check availability before ordering. Carriage all units £7. VAT to be added to total of Goods and Carriage. S.A.E. for LISTS

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Telephone: 0734 68041
Callers welcome 9 a.m. to 5.30 p.m. Monday to Saturday inclusive

WW - 066 FOR FURTHER DETAILS

PM COMPONENTS LTD

VALVE & COMPONENTS SPECIALISTS

INTEGRATED CIRCUITS

AN124	2.50	MC1358	1.58	TA7120P	1.65	TBA641A12	2.50	TDA2523	1.95
AN214D	2.50	MC1495	3.00	TA7130P	1.50	TBA641B1X1	3.00	TDA2524	1.95
AN240	2.80	MC1496	2.75	TA7146	2.95	TBA651	1.75	TDA2525	1.95
AN612	2.15	MC14011BCP	0.32	TA7203	2.95	TBA651R	2.50	TDA2526	1.95
AN7140	3.50			TA7204P	2.15	TBA720A	2.45	TDA2527	2.15
AN7145	3.50	MC145106P	0.32	TA7205AP	1.50	TBA750Q	2.65	TDA2528	1.95
BA521	2.95			TA7222AP	1.80	TBA800	0.89	TDA2529	2.25
CA1352E	1.75	MC1723	0.50	TA7227P	4.25	TBA810AS	1.65	TDA2531	2.95
CA3086	0.46	MC3357	2.75	TA7310P	1.80	TBA810P	1.65	TDA2600	5.50
ET76016	2.50	ML231B	1.75	TA7313AP	2.95	TBA820Q	0.75	TDA2610	2.50
HA 1377	3.50	ML232B	2.50	TA7321P	2.25	TBA820Q	1.45	TDA2611A	1.95
HA1156W	1.50	MSM5807	6.75	TA7609P	3.15	TBA890	2.50	TDA2620	2.80
HA1551	2.95	PLL02A	5.75	TA7611AP	2.95	TBA920	1.65	TDA2640A	2.75
LA1230	1.15	SAA500A	0.50	TA7612P	1.80	TBA920Q	1.65	TDA2640B	2.75
LA4102	2.95	SA5010	6.35	TA7613P	2.25	TBA950/2X	2.35	TDA2650	3.95
LA4250	2.95	SAS560S	1.75	TA7614P	2.25	TBA970	2.95	TDA2660	3.95
LA4400	4.15	SAS570S	1.75	TA7615P	3.15	TBA990	1.49	TDA2670	3.95
LA4422	2.50	SAS580	2.85	TA7616P	2.95	TBA990	1.49	TDA2680	3.95
LC1720	3.25	SL901B	5.50	TA7617P	1.80	TBA990	1.49	TDA2690	3.95
LC1730	3.50	SL917B	6.65	TA7618P	1.80	TBA990	1.49	TDA2700	3.95
LC7131	5.50	SL1310	1.80	TA7619P	2.25	TBA990	1.49	TDA2710	3.95
LM324N	0.45	SL1327	1.10	TA7620P	2.25	TBA990	1.49	TDA2720	3.95
LM380N	0.95	SL1370A	1.10	TA7621P	1.25	TBA990	1.49	TDA2730	3.95
LM393	2.95	SN76003N	1.95	TBA395	1.50	TBA990	1.49	TDA2740	3.95
LM513L	3.00	SN76013N	1.95	TBA395	0.75	TBA990	1.49	TDA2750	3.95
MS1515L	2.95	SN76227N	1.05</						

PHONE
0474 813225
3 LINES


P. M. COMPONENTS LTD
SELECTRON HOUSE, WROTHAM ROAD
MEOPHAM GREEN, MEOPHAM, KENT DA130QY

TELEX
966371
PM COMP



A SELECTION FROM OUR STOCK OF BRANDED VALVES

A1714 18.50	EA42 1.20	EF732 1.80	HK90 1.05	PCL85 0.80	RK2K25 62.50	VX9181 5.00	3C45 24.00	6BW7 1.50	888 2.50	90C1 2.70
A1998 11.50	EA801 1.40	EF800 11.00	HL2K 3.50	PCL86 0.85	RC4-1000 10.00	W77 5.00	3CN3A 2.50	6BW8 4.00	8807 1.95	90CG 13.50
A2087 11.50	EA834 1.50	EF804S 11.50	HL230D 4.00	PCL200 1.80	RE20A 12.00	W729 1.00	3CX3 2.50	6BX6 0.48	10C1 5.50	91AG 9.00
A2134 14.95	EA841 3.00	EF805S 13.50	HL41 3.50	PCL800 0.80	RL16 1.50	W739 1.50	3D21A 29.50	6BX7GT 3.50	10C2 0.70	91G 12.50
A2293 6.50	EA91 0.60	EF806S 14.50	HL420D 3.50	PCL805 0.90	RPL16 12.00	X24 1.00	3D22 39.50	6BZ6 2.50	10D2 1.25	92AV 12.50
A2521 21.00	EA93 2.50	EF808 14.50	HL420D 3.50	PCL805 0.90	RPY13 2.50	X6M 4.95	3J187E 398.00	6BZ7 2.95	10F1 0.75	95A1 6.50
A2599 37.50	EA93 2.50	EF812 0.85	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	3W4GT 2.50	6BZ8 0.95	10G6 1.95	108C1 1.50
A2900 11.50	EA93 2.50	EF900 0.72	HL133/DD 3.50	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150B2 5.50
A3042 24.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
A3283 24.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
AL60 6.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
AC/HL/DD 4.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
AC/TH 4.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
AC122 59.75	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
AC/VP2 4.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
AC/S2/PEN 8.50	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
AH221 39.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
AH238 39.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
AL60 6.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
ARP12 0.70	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
ARP34 1.25	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
ARP35 2.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
BL63 2.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
BS450 67.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
BS510 95.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
BS544 55.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
CIK 16.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
C3JA 16.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
C110 55.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
C1134 35.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
C1484 115.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
C1149/1 130.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
C1150/1 135.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
C1534 32.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
CCA 2.60	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
CC3 0.65	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
CL3 2.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
CN Nos Prices on request	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
D63 1.20	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DAF91 0.70	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DA796 0.65	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DC70 1.75	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DC90 1.20	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DCX4-1000 12.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DCX4-5000 25.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DET22 28.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DET24 39.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DET25 22.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DF91 0.70	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DF92 0.60	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DF96 0.65	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DF97 1.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DH63 1.20	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DH77 0.90	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DH79 0.56	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DH149 2.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DK91 0.90	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DK92 1.20	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DK96 2.50	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL35 1.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL63 1.00	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL70 2.50	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL73 2.50	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL91 1.50	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL92 0.60	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL93 1.10	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL94 2.50	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL96 2.50	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL98 1.50	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90	RPY23 2.50	X79 3.50	4B551B 115.00	6C4 1.10	10H12 0.65	150C2 1.50
DL99 1.50	EA93 2.50	EF900 0.72	HL90 0.70	PCL805 0.90						

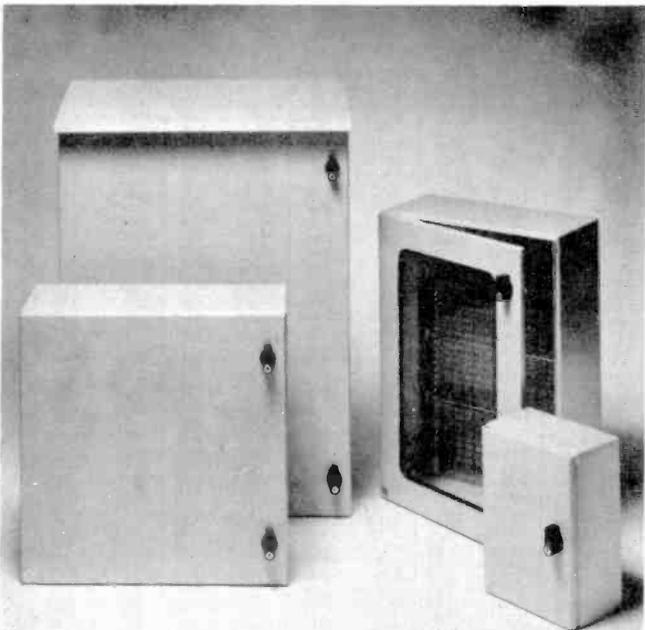

SAREL'S 8000 SERIES SET THE STANDARD

- Protects against ingress of dust and liquids IP55 (BS5490 1977, IEC 529 1976).
- 1.5 and 1.75mm steel bodies and 2mm steel doors.
- Smaller sizes fitted with advanced polyurethane gaskets. Larger sizes (600 x 600 and above) fitted with neoprene gaskets.
- Wide range of chassis systems including plates DIN rail, teletick and gland plates.
- Standard finish is textured beige polyester powder paint.
- Glazed doors — wide choice from stock.



Think big — think Sarel

Sarel Limited

Cosgrove Way, Luton, Beds. Tel: Luton 20121

Please send me full details of how Sarel's 8000 Series of cabinets and accessories set the standard.

Name _____

Position _____

Company _____

Address _____


Tel: _____

Sarel Limited, Cosgrove Way, Luton, Beds WW2/84

WW - 064 FOR FURTHER DETAILS

ELECTROVALUE

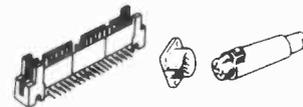Your **SPECIALIST SUPPLIERS** for
CONNECTORS



Not only will you find a wide selection of all the usual types you may require in our A-Z products list; there are also many others made necessary by today's ever-advancing electronics — just one more example of how much better Electrovalue serves you.

Please mention this journal when getting in touch with Electrovalue.

D SERIES CONNECTORS

9, 15, 25, 37 or 50 way connectors with corresponding covers and retainers. Gold-plated contacts. Max current per contact — 5A.

ID CONNECTORS

For connecting ribbon cable to PCBs. Insulation Displacement Type: 16, 20, 26, 34 or 40 way, 1A per socket. Straight or right angle plug fitting; cable socket has strain relief.

RPC CONNECTORS

5 way and 7 way chassis plugs and sockets. DIN style layout. Gold-plated pins. 250V/5A rating per socket.

OTHER TYPES

Edge connectors, DIN, jack plugs and sockets, phono, QG, BNC, UHF and power.

BRITAIN'S LEADING QUALITY COMPONENT SUPPLIERS — SEND FOR FREE 32 PAGE A-Z LIST
ATTRACTIVE DISCOUNTS — FREE POSTAGE — GOOD SERVICE & DELIVERY

ELECTROVALUE LTD

28 St. Jude's Road
Englefield Grm, Egham
Surrey TW20 0HB

Phone (0784) 33603. Telex 264475

North: 680 Burnage Lane, Manchester (061) 432 4945

EV Computing Shop: 700 Burnage Lane, Manchester (061) 431 4866

**ACCESS AND
BARCLAYCARD
Phoned Orders
Welcome**

TEST EQUIPMENT

	£
Feedback VPO 602 Variable Phase Oscillator.....	65
Marconi TF2002B AM/FM 10KHz-88MHz.....	795
Fluke 8600A 4 1/2 digit DMM.....	150
Fluke 8020A 3 1/2 digit DMM (New).....	60
Case for above (New).....	12
GEC Super 50 Selectest.....	30
Philips PM2454 AC Millivoltmeter 0-2MHz 1uV-300v.....	75
Sullivan AC Test Set.....	150
Leader LAG-27 Audio Signal Generator (New).....	70
H.P. 5000A Logic Analyser.....	195
Philips 2522A 4 1/2 digit DMM.....	145
Sanwa Multimeters.....	10
Pantec Electro Multimeter.....	20
25A/600v Clamp Meters.....	10
Houston DP10 Incremental XY Plotter.....	175
Iwatsu Dual Trace 20MHz Scope.....	195
Leader Function Generator 2MHz — New.....	299
Advance OS1000B Dual Trace 20MHz Scope.....	195
Leader LB0510B 4MHz Single Channel Scope (New).....	95
Scopex 4S6 6MHz Single Channel Scope.....	60
Leader LSG-17 150MHz AM Signal Generator (New).....	62
Tequipment D75 50MHz Dual Trace Delay T/B Scope.....	375
Scopex 30-4D Dual Trace 30MHz Scope Dual Channel.....	175
Tek. 7B53N Timbase Plug-in.....	275
Advance OS3500 60MHz Scope with DM3010 DMM option.....	675
Advance OS255 15MHz Dual Trace Scope.....	175
Tek. 564 Storage Scope.....	195
Leader LFR 560 Frequency response recorder.....	565
J. J. Lloyd PL100 X-Y Plotter with spare Amp.....	295
Leader LTC 905 Curve Tracer (New).....	150
H.P. 9815A Desk Top Computer.....	82
H.P. 776D 940-1900MHz Directional Coupler (New).....	250
Systron Donner 62 Set Timer Counter BCD output.....	135
Systron Donner 7344A 4 1/2 digit DMM IEEE interfaced.....	195
Pecker 5000 Prom Programmable.....	350
Tek. 191 Constant Amp. Signal Generator 100MHz.....	115
Tek. 106 Square Wave Generator.....	95
Tek. Amplitude Calibrator.....	80
3 Phase Variac 6A.....	80
Tek. Type M Plug-in.....	50
Tek. Type 1A5 Plug-in.....	50
H.P. 85 Desk Top Computer.....	995
Tek. 575 Curve Tracer.....	95
Yaesu Musen YC1000L Data Logger 600MHz Timer Counter, DMM, 24-hr. clock, Thermometer and Printer, all in one box (New).....	450
Leader LCR740 LCR Bridge (New).....	150
H.P. 612 UHF Signal Generator 450-1250MHz.....	95
Tequipment D57 25MHz Dual Channel Delay T/B Scope.....	235
Tequipment D67A 25MHz Dual Channel T/B Scope.....	255
Marconi TF 801/D 470MHz AM Signal Generator.....	75
Data Dynamics Teletypes.....	40
R & S SMAP AM/FM Signal Generator 300MHz.....	195
Leader Video recorder head checker Beta or VHS (New).....	45
40kv Metered Test Probe (New).....	18
H.P. 1803A Differential plug-in.....	95
H.P. 1821A T/B plug-in.....	95
Electrohome 19" B/W X-Y Monitors.....	20
Tek. 113 Delay Cable.....	50
H.P. 608C 470MHz AM Signal Generator.....	75
Weir 30v/2A, 60v/1A, 15v/4A Metered PSUs.....	35

Carriage additional: All prices exc. V.A.T.



TIMEBASE
94 ALFRISTON GARDENS

SHOLING, SOUTHAMPTON SO2 8FU TEL: 431323 (0703)

Callers welcome

Access, Barclaycard: Telephone your order

WW - 020 FOR FURTHER DETAILS



COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE 'ALADDIN'S' CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HARD DISK DRIVES

Fully refurbished DIABLO/DRE series 30 2.5 Mb disk drives.
DEC RK05, NOVA, TEXAS compatible.
 Front load. Free stand or rack mount.
 Exchangeable type (via lid removal)
 me3025 PSU unit for 2 drives **£550.00**
£295.00
£125.00
DIABLO/DRE 44-4000A/B 5+5 ex stock from **£995.00**
 1000's of spares for S30, 4000, 3200, HAWK ex stock.
 Plus in house repair, refurbishing service.
 Call for details or quotation.

CALCOMP PLOTTERS

936 3 colour digital incremental, 37" drum, parallel interface and accessories **£2,500.00**
 718 4 colour digital 8 x 5 FEET flat bed & controller (cost 25,000) 1 only at **£1,950.00**
 Viewing by appointment.

COOLING FANS

Keep your hot parts COOL and RELIABLE with our range of BRAND NEW professional cooling fans.
ETRI 90XU01 Dim. 92 x 92 x 25 mm. Miniature 240 v equipment fan complete with finger guard. **£9.95.**
GOULD JB-3AR Dim. 3" x 3" x 2.5" compact very quiet running 240 v operation. **NEW £6.95.**
BUHLER 69.11-22 8-16 v DC micro miniature reversible fan. Uses a brushless servo motor for extremely high air flow, almost silent running and guaranteed 10,000 hr life. Measures only 62 x 62 x 22 mm. Current cost **£32.00. OUR PRICE ONLY £12.95 complete with data.**
MUFFIN-CENTAUR standard 4" x 4" x 1.25" fan supplied tested EX EQUIPMENT 240 v at £6.25 or 110 v at £4.95 or **BRAM NEW 240v** at £10.50. 1000's of other fans Ex Stock. Call for Details. Post & Packing on all fans **£1.60**

HOT LINE DATA BASE DISTEL ©

THE ORIGINAL FREE OF CHARGE dial up data base. 1000's of stock items and one off bargains.
ON LINE NOW - 300 baud, full duplex CCITT tones, 8 bit word, no parity.
01-679 1888

MAINS FILTERS

Cure those unneriving hang ups and data glitches caused by mains interference.
 SDSA As recommended by ZX81 news letter. matchbox size up to 1000 watt load **£5.95**
L2127 compact completely cased unit with 3 pin fitted socket. Up to 750 watts **£9.99**

COMPUTER 'CAB'

All in one quality computer cabinet with integral switched mode PSU, Mains filtering, and twin fan cooling. Originally made for the famous DEC PDP8 computer system costing thousands of pounds. Made to run 24 hours per day the PSU is fully screened and will deliver a massive +5v DC at 17 amps, +15v DC at 1 amp and -15v DC at 5 amps. The complete unit is fully enclosed with removable top lid, filtering, trip switch, 'Power' and 'Run' LEDs mounted on All front panel, rear cable entries, etc. etc. Units are in good but used condition - supplied for 240v operation complete with full circuit and tech. man. Give your system that professional finish for only **£49.95 + Carr.** Dim. 19" wide 16" deep 10.5" high. Useable area 16" w 10.5" h 11.5" d. Also available **LESS PSU**, with FANS etc. Internal dim. 19" w. 16" d. 10.5" h. **£19.95.** Carriage & insurance **£9.50.**

SCOOP!



BRAND NEW CASED WORD PROCESSOR KEYBOARDS

Made by the famous 'KEYSWITCH' corporation, for a well known computer company's top of the range word processor at a price of over £200.00!! Constructed around an internal INTEL 8048 cpu this superbly styled 106 key keyboard was intended to interface with a main computer via a TTL serial interface. Standard HALL EFFECT long life switches are utilised on an XY matrix, buffered by 74 series TTL ic's to the eight bit CPU port enabling simple modification to your own custom decoding logic via an EPROM etc. Many other features for the most exacting user include: numeric keypad, cursor control pad, ten clear top function keys, LED indicators, single 5v supply on-off lock switch etc. Supplied BRAND NEW and boxed with circuit diagram. **ONLY £49.95 + £2.00 P&P**

DRE 7100

8" Disk Drives
 New **£225 + VAT**

VIDEO MONITORS

12" CASED. Made by the British KGM Co. Designed for continuous use as a data display station, unit is totally housed in an attractive brushed aluminium case with ON-OFF, BRIGHTNESS and CONTRAST controls mounted to one side. Much attention was given to construction and reliability of this unit with features such as: internal transformer isolated regulated DC supply, all components mounted on two fibre glass PCB boards - which hinge out for ease of service, many internal controls for linearity etc. The monitor accepts standard 75 ohm composite video signal via SO239 socket on rear panel. Bandwidth of the unit is estimated around 20 Mhz and will display most high def graphics and 132 x 24 lines. Units are secondhand and may have screen burns. However where burns exist they are only apparent when monitor is switched off. Although unguaranteed all monitors are tested prior to despatch. Dimensions approx. 14" high x 14" wide by 11" deep. Supplied complete with circuit. 240 volt AC operation. **ONLY £45.00 PLUS £9.50 CARR.**
 24" CASED. Again made by the KGM Co with a similar spec as the 12" monitor. Originally used for large screen data display. Very compact unit in lightweight alloy case dim. 19" H x 17" D x 22" W. All silicon electronics and composite video input make an ideal unit for schools, clubs, shops etc. Supplied in a used but working condition.
ONLY £55.00 PLUS £9.50 CARR & INS.

SAVE SUPER PRINTER SCOOP £250



CENTRONICS 739-2
 The "Do Everything Printer" at a price that will NEVER be repeated. Standard Centronics interface, full graphics, 4 type fonts with high definition & proportional spacing for word processor applications. 80-132 columns, single sheet, roll or sprocket paper handling plus much more. Available only from DISPLAY ELECTRONICS at a ridiculous price of only **£199.00**
 Options: carriage & insurance **£10.00**
 Interface Cable **£10.00**

TELETYPE ASR33 I/O TERMINALS

FROM **£195 + CAR + VAT**
 Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O auto data detect circuitry. RS232 serial interface. 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order
 Options: Floor stand **£12.50 + VAT**
 KSR33 with 20ma loop interface **£125.00 +**
 Sound proof enclosure **£25.00 + VAT**

SOFTY 2

The amazing SOFTY 2. The complete "toolkit" for the open heart software surgeon. Copies, Displays, Emulates ROM, RAM and EPROMS of the 2516, 2532 variety. Many other features include keyboard, UHF modulator. Cassette interface etc. Functions exceed capabilities of units costing 7 times the price! Only **£169.00** pp £1.95 Data sheet on request

QUALITY INTERFACE CABLES & CONNECTORS

18/3B D25S to 10ft 13 way **£4.90**
 22/2A D25S to 3ft 22 way **£2.90**
 22/3B D25S to D25P 3ft 22 way **£8.50**
 25/08 25 way cable 5 ft long **95p**
 D25S ex equip 60p D25S socket new **£1.25**
 22/2C D25S to 16ft 22 way **£6.50**
 22/3C D25S to D25P 15ft 22 way **£11.50**
 1014B D15P to 12ft 15 way (BBC) **£2.90**
 12/15 10 way cable 12ft long **£1.00**
 D25 split shells **£1.00**

SUPER DEAL? NO - SUPER STEAL!!

The FABULOUS 25CPS TEC Starwriter Daisy wheel printer at a fraction of its original cost.

BRAND NEW AT ONLY **£499 + VAT**

Made to the very highest spec the TEC Starwriter FP1500-25 features a heavy duty die cast chassis and DIABLO type print mechanism giving superb registration and print quality. Micro-processor electronics offer full DIABLO/QUME command compatibility and full control via CP/M Wordstar etc. Many other features include bidirectional printing, switchable 10 or 12 pitch, full width 381 mm paper handling with upto 163 characters per line, friction feed rollers for single sheet or continuous paper, internal buffer, standard RS232 serial interface with handshake. Supplied absolutely BRAND NEW with 90 day guarantee and FREE daisy wheel and dust cover. Order NOW or contact sales office for more information. Optional extras: RS232 data cable **£10.00**. Tech manual **£7.50**. Tractor feed **£14.00**. Spare daisy wheel **£3.00**. Carriage & Ins. (UK Mainland) **£10.00**.



SEMICONDUCTOR 'GRAB BAGS'

Mixed Semis amazing value contents include transistors, digital, linear, I.C.'s triacs, diodes, bridge recs, etc. etc. All devices guaranteed brand new full spec, with manufacturer's markings, fully guaranteed. **50+ £2.95 100+ £5.15.**
TTL 74 Series A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed all I.C.'s full spec. **100+ £6.90 200+ £12.30 300+ £19.50**

DATA MODEMS

Join the communications revolution with our range of EX TELECOM data modems. Made to most stringent spec and designed to operate for 24 hrs per day. Units are made to the CCITT tone spec. With RS232 i/o levels via a 25 way 'D' skt. Units are sold in a tested and working condition with data. Permission may be required for connection to PO lines.
MODEM 2B "Hackers Special" fully hedged up to 300 baud full duplex, ANSWER or CALL modes. Data i/o via standard RS232 25 way 'D' socket. Just 2 wire connection to comms line. Ideal networks etc. Complete with data, ready to run **£85.00**
MODEM 20-1 Compact unit for use with MICRONET, PRESTEL or TELECOM GOLD etc. 2 wire direct connect 75 baud transmit 1200 baud receive. Data i/o via RS232 'D' socket. Guaranteed working with data **£49.95**
MODEM 20-2 same as 20-1 but 75 baud receive 1200 baud transmit. **£130.00**
MODEM 20-3 Made for data rates up to 1200 baud in full duplex mode over 4 wire circuit or half duplex mode over 2 wires. **£130.00**
MODEM 13A compact, async, same size as telephone base. Up to 300 baud, full duplex over 2 wires, but call mode only **£75.00**
DATA PUMP MODEM compact unit up to 1200 baud full duplex over 4 wires or half duplex over 2 wires. BELL specification with data i/o via RS232 25 way D socket, remote test etc. 240 v operation. Supplied complete with data. **£65.00** carr. **£4.50**.
 For more information or details of other types of ex stock modems contact sales office.

Carnage 13A £4.50. 2B/C & 20 £9.50.

66% DISCOUNT

ELECTRONIC COMPONENTS EQUIPMENT
 Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C. s, Transistors, Relays, Cap's, P.C.B. s, Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads, we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay. Unbeatable value!! Sold by weight.
 2.5kls **£4.25 + pp £1.25**
 10kls **£10.25 + pp £2.25**
 5kls **£5.90 + £1.80**
 20 kls **£17.50 + £4.75**

ALL PRICES PLUS VAT

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value **£2.00**, Minimum Credit Card order **£10.00**. Minimum BONA FIDE account orders from Government depts., Schools, Universities and established companies **£20.00** Where post and packing not indicated please ADD **60p + VAT** Warehouse open Mon-Fri 9.30 - 5.30. Sat. 10.15 - 5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export enquiries welcome.

DISPLAY ELECTRONICS

32 Biggin Way, Upper Norwood, London SE19 3XF
 Telephone 01-679 4414 Telex 27924



WW - 058 FOR FURTHER DETAILS

NEW PRODUCT


BX80 COLOUR MATRIX PRINTER

£495+VAT

Especially designed for use with the BBC Microcomputer

Colour printout is quickly assimilated, makes graphics more understandable and is an ideal medium for the presentation of complex data or concepts.

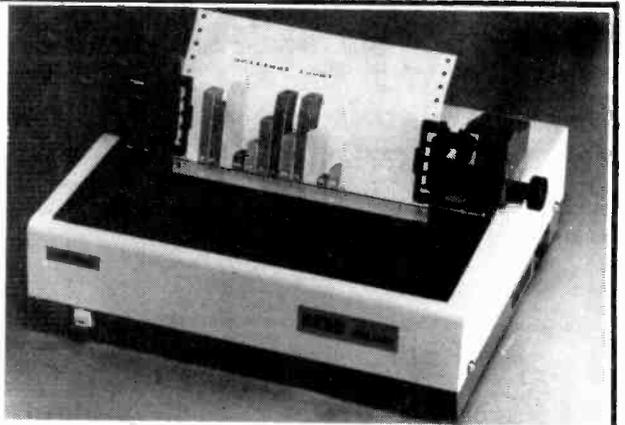Prints in 7 colours on plain paper. Colour screen printing in ALL modes (inc. mode 7 Teletext). Uses RS423 output (cable supplied). Printer RS423 input has 2.5K bytes buffer. In mode 7 Teletext, printer has a 2 page store with printout size option. 125 cps primary colour speed for listing, etc. Screen dump listing supplied.



also
 Black and White printer interface for BBC micro-Epson MX*/RX/FX80 3.5K byte buffer: all modes inc. mode 7 Teletext. Uses RS423 o/p.
 Board, RS423 cable + listing **£95+VAT**
 Apple II parallel interface card for MX*/RX/FX80 gives hi res screen dumps, etc. C/w cable **£59+VAT**
 Ribbons for MX/RX80 **£5.50+VAT**
 Ribbons for BX80 **£5+VAT**
 * MX80 requires printer ROM change, add £15+VAT

NEW model VRX80 black/white viewdata printer, 3.5K byte buffer, £425+VAT

INTEGREX LIMITED

Portwood Industrial Estate, Church Gresley
 Burton-on-Trent, Staffs DE11 9PT
 Burton-on-Trent (0283) 215432. Telex: 377106



EASIBINDERS

Quick, neat and easy!



It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold six issues and is attractively bound and blocked with the WIRELESS WORLD logo.

Price U.K. £4.30 including postage, packing and V.A.T.

Overseas orders add 35p per binder

Nat. Giro No. 5157552.

Please allow 3/4 weeks for fulfilment of order.

Payment by ACCESS/BARCLAYCARD/VISA. Send coupon below detailing credit card no. and signature.

Why not place your order now? Send the completed coupon below with remittance payable to:

EASIBIND 42 Hoxton Square
 London N1 6NS

Order Form WIRELESS WORLD

I enclose P.O./cheque value..... for.....binders

Years required.....

BLOCK LETTERS PLEASE


Name.....

Address.....

Date..... Registration No. 735718

FYLDE

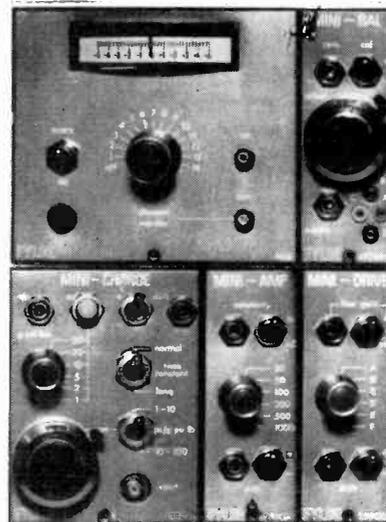TRANSDUCER and RECORDER AMPLIFIERS and SYSTEMS



reliable high performance & practical controls. individually powered modules—mains or dc option single cases and up to 17 modules in standard 19" crates small size—low weight—realistic prices.

FYLDE


Fylde Electronic Laboratories Limited.

49/51 Fylde Road Preston
 PR1 2XQ
 Telephone 0772 57560

WW - 023 FOR FURTHER DETAILS

WE'VE MADE OUR RESOLUTIONS FOR 1984

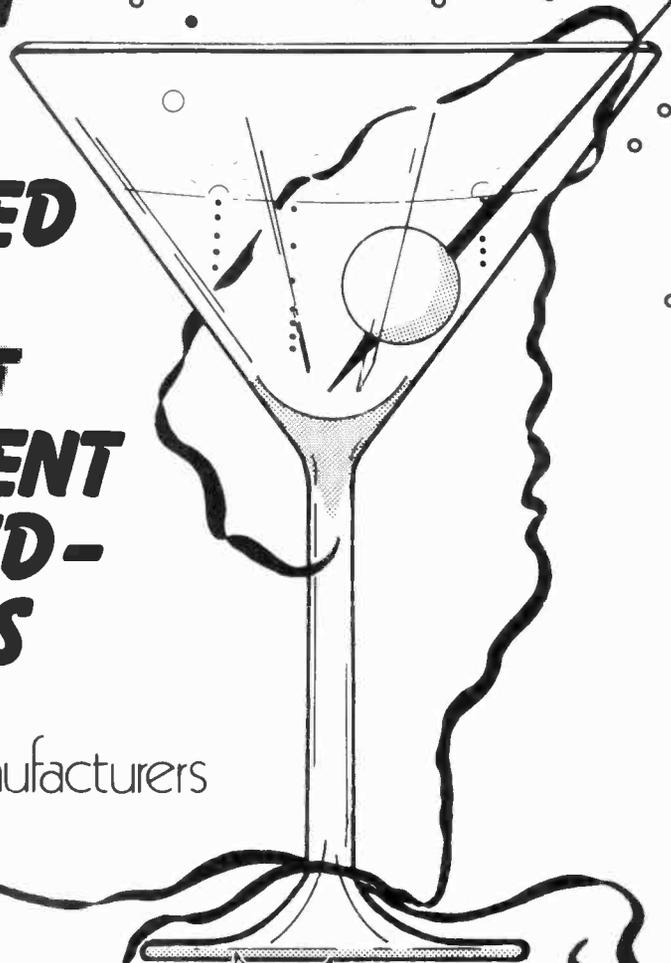WE ARE DETERMINED TO CONTINUE OFFERING THE BEST USED TEST EQUIPMENT - FULLY GUARANTEED - AT THE BEST PRICES



All equipment calibrated to manufacturers original specification

WATCH THIS SPACE for our regular money saving special offers - all fully guaranteed

Phone us on 01-267 5311

Carston Electronics Ltd.

Shirley House, 27 Camden Rd, London NW1 9NR
Tel: 01 - 267 5311 Telex 23920 (Euhire)

B. BAMBER ELECTRONICS

Rohde & Schwarz Enograph Type BN 18531, £60.
 Rohde & Schwarz Sweep Signal Generator Type BN 4242/2, 50 kHz to 12 MHz, £85.
 Rohde & Schwarz U.H.F. Signal Generator Type BN 41026, 1000 to 1900 MHz, £125.
 Rohde & Schwarz Group Delay Measuring Equipment Indicator, £50.
 Rohde & Schwarz Group Delay Measuring Equipment Modulator/Demodulator, £50.
 Rohde & Schwarz Power Signal Generator Type BN 4105, 30 kHz to 300 MHz, £125.
 Rohde & Schwarz U.H.F. Millivolt Meter Type BN 1091, 20mV to 10V, £50.
 Airmec Modulation Meter Type 210, 3 to 300 MHz, £95.
 Hewlett Packard S.H.F. Signal Generator Model 618 B, 3.8 to 7.6 GHz, £120.
 Bryans X-Y Plotter Model 1806, £50.
 Hewlett Packard Square Wave Generator Model 211 A, £60.
 Solartron Pulse Generator Type G0 1005, £40.
 Pye 12V Power Unit Type AC 15, £25.
 Wandell Golterman Carrier Frequency Level Meter, Type TFPM 76, £60.
 Rohde & Schwarz Video Skop Type BN 4241, £250.
 Schomantol Frequency Meter Type FD1, 30 to 900 MHz, £50.
 Tektronix Delay Cable Type 113, £50.
 Bruel & Kjoer Vibration Meter Type 2502, £50.
 Advance Pulse Generator Type PG 54, £40.
 Systron Donner L.F. Spectrum Analyzer Model 805, 200 Hz to 1.6 Mhz, £550.
 Ministry Oscilloscope Type CT 436 Dual Beam D.C. to 6 MHz, £85.
 Marconi Signal Generator Type TF 995A/3/S (CT402), £95.
 Marconi 100-Watt 7db Attenuator Type TM 5280, 150 to 185 MHz, £40.
 Pye Aerial Tuner Unit Type ATU 4, 2 to 9 MHz, Pre-set, £15.
 A.I.M. Electronics Pulse Generator with Clock Generator, £65.
 Marconi V.H.F. Signal Generator Type TF 1064B/5M, £125.
 Marconi Tx & Rx Output Test Set Type TF 1065, £85.
 Marconi 1/4 Universal Bridge Type TF 1313, £220.
 Tektronix L-C Meter Type 130, £65.
 Heathkit Harmonic Distortion Meter Type 1M-12U, £20.
 Marconi Sanders Microwave Sweep Generator Type 6600A, 10 to 15 GHz, £220.
 Pye Vanguard Type AM 25 B, High Band Less Control Gear, £10.
 Rohde & Schwarz Polyskop 11 Type BN 425/50, £350.
 A.E.W. Process Cycling Oven, £600.
 Twin Clothes Lockers, nests of 2 with keys, £20.
 Louvred Lin Bin Panels, 4' 6" x 4' 6", £20.
 Kodak Roll Film Drying Cabinet with Hangers, £150.
 Potter Line Printer Type LP 3000, £150.

PDP-8/L Computer System, Dectape Units and Interface Unit, £650.
 Digital Decwriter 11 Printer with keyboard, £100.
 Rohde & Schwarz Z-g Diagraph Type BN 3562, 300 to 2400 MHz, £85.
 Tektronix Rack Mount Oscilloscope Type RM 45, £50.
 Marconi V.H.F. Alignment Oscilloscope Type TF 1104/1, £150.
 Tektronix Sampling Oscilloscope Type 661 with 452 plug in, £120.
 Avo Valve Tester Type CT160, £30.
 Advance Oscilloscope Type OS25A, DC to 3MHz, £120.
 Tequipment Oscilloscope Type D43, DC to 10 MHz, £100.
 Tequipment Oscilloscope Type S43, DC to 10 MHz, £85.
 Tequipment Oscilloscope Type S51, £75.
 Tequipment Oscilloscope Type S32A, DC to 3 MHz, £65.
 Tektronix Rack Mount Oscilloscope RM17, DC to 10 MHz, £85.
 Tektronix Oscilloscope Type 317, DC to 15 MHz, £120.
 Marconi R.C. Oscilloscope Type TF1101, £65.
 Airmec Millivolt Meter Type 301A, £75.
 Advance Audio Generator Type H1, £20.
 Tektronix Oscilloscope Type 543A with Type B plug in, £160.
 Tektronix Oscilloscope Type 531A with Type H plug in, £160.
 Pye Base Station Type F27, A.M. Low Band, £50.
 Sander Oscillator Type CLC 2-4, 2 to 4.5 GHz, £95.
 Bruel & Kjoer Microphone Amplifier Type 2604, £50.
 Bruel & Kjoer Microphone Amplifier Type 2603, £50.
 Labgear Compak 8 Transceiver less mike, aerial, etc., £50.
 EMI Oscilloscope Wide Band Amplifier Type 7/1, £25.
 Airmec Sweep Signal Generator Type 352, 20 Hz to 200 kHz, £45.
 Belix Variable Power Unit, 0 to 50V at 2 amp, £40.
 BTR Silvertown Anti-Static and Conductive Footwear Tester, £25.
 Dawe True RMS Valve Voltmeter Type 612A, £20.
 Rohde & Schwarz Power Signal Generator Type BN41001, 0.1 to 30 MHz, £75.
 Marconi Distortion Factor Meter Type TF142F, £85.
 Marconi A.M. Signal Generator Type TF144H/4S, £125.
 Tektronix Time Mark Generator Type 180A, £125.
 Marconi F.M. Signal Generator Type TF 1066B/1, £280.
 Marconi F.M. Signal Generator Type TF 1066B/6, £300.
 Marconi Carrier Deviation Meter Type TF 791 D, £95.
 Airmec Modulation Meter Type 409, £120.
 Marconi Universal Bridge Type TF 868, £50.
 Marconi A.M./F.M. Signal Generator Type TF 995A/5, £230.
 Marconi Vacuum Tube Voltmeter Type TF 1041 C, £25.
 Marconi R.F. Power Meter Type TF 1020A/4, 300W, 75 ohm, £65.
 Marconi R.F. Power Meter Type TF 1020A/1, 100W, 50 ohm, £65.

PYE POCKETPHONE PF1 UHF RECEIVER

440-470 MHz, Single Channel, int. speaker and aerial. Supplied complete with re-chargeable battery and service manual, £6 each plus £1 p.p. plus V.A.T.

GARRARD CAR CASSETTE PLAYER MECHANISMS

12-Volt motor, stereo head, brand new, £2.50 each plus 50p p.p. plus V.A.T.

BASF CHROMDIOXID VIDEO CASSETTE TAPE

for use with Philips N1500/1700 VCR. LVC30 + 5, 36min. long play, £5 each plus 50p p.p. plus V.A.T. 10 for £35 plus V.A.T. post paid.

RADIOSONDE RS21 METEOROLOGICAL BALLOON TRANSMITTER

with Water Activated Battery, contains all-weather sensors, fully solid state, £5 each plus £1 p.p. plus V.A.T.

CHARLES AUSTIN TWO-STAGE AIR PUMP

Type F65 DEH, complete with pressure regulator, 240 vac., chassis-mounted with hoses, etc., brand new and boxed, £45 plus £5 p.p. plus V.A.T.

P. & P. or Carriage and V.A.T. at 15% on total must be added to all orders. Callers very welcome, strictly between 9 a.m. and 1 p.m. and 2 and 5 p.m. Monday to Friday inc.

Barclaycard and Access taken

Official orders welcome ww27



5 STATION ROAD, LITTLEPORT, CAMBS CB6 1QE
 PHONE: ELY (0353) 860185



WW - 068 FOR FURTHER DETAILS

pantechnic

THE POWERFET SPECIALISTS

OEM USERS

Pantechnic present the most adaptable high-powered amplifier ever.

FET SYSTEM AMP

Features:

- HIGH POWER. 1.2kW (single ended)
 - LOW VOLUME. 1/8 Cubic foot inc. Heatsink
 - VERSATILE. Delivers more than 1kW into 1/2 to 8 ohms
- OR 2 x 600W into 2 to 8Ω
 OR 4 x 300W into 2 to 4Ω (200W into 8Ω)
- OR { 1 x 600W into 2 to 8Ω
 1 x 300W into 2 to 4Ω
 1 x 150W into 4 to 8Ω

Etc., etc.

Having been closely involved in a wide variety of OEM applications of their amp boards. Pantechnic became aware of numerous implementation problems often left untackled by other amp board manufacturers. These problems specifically of size and thermal efficiency became particularly aggravated at high powers and considerably lengthened OEM product development time.

By including thermal design in the totality of board design it has been possible to reduce the size of the electronics, and increase the efficiency of the transistor to heatsink thermal circuit. The combined effect of this has been to dramatically increase the volumetric efficiency of the amplifier/heatsink assembly. The SYSTEM Amp offers 1.2kW of power in a space of 180mm x 102mm x 77mm, excluding PSU and Fan.

The basis of this considerable advance is the PANTECH 74 Heat Exchanger, newly designed and manufactured by us. By eliminating the laminar air flow found in conventional, extruded heatsinks, heat transfer to the environment is greatly enhanced.

The flexibility of the 1.2kW amp stems from its division into 4 potentially separate amplifiers of 300W each (downratable with cost savings to 150W). These can be paralleled, increasing current capability or seriesed (bridge in pairs) doubling voltage capability. In consequence a large variety of amplifier/load strategies can be implemented.

As ever Pantechnic offer a full range of customising options including DC coupling, ultra-high slew, etc. Contact Phil Rimmer on 01-800 6667 with your particular application problem.

P.S. Specs, as ever, are exemplary.

A wide range of other amplifiers and other modules available.

Price and Delivery

PANTECHNIC (Dept. WW2)
 17A WOOLTON STREET
 LIVERPOOL L25 5NH
 Tel: 051-428 8485

Technical Enquiries contact
 Phil Rimmer
 on
 01-800 6667

WW - 069 FOR FURTHER DETAILS

HF ANTENNAS



- ★ MODE; Full half wave operation.
- ★ BANDS; Up to 4 spot frequencies.
- ★ POWER; Receive to 800W (PEP).
- ★ SWR; Better than 1.5:1 on channel.



THE SMC TRAPPED DIPOLE ANTENNA

has been developed to satisfy the needs of commercial and military users. It is capable of operation between 2 and 30 MHz on as many as four spot frequencies - each capable of accommodating many channels. Excellent matching and efficiency with a single coaxial feed is offered by the use of SMC H1Q traps and the incorporation of a ferrite balun in a full half wave design. NB: Power absorbing terminating resistors are not employed. The antenna may be deployed using one or two support masts, installation (incorporating SMC light duty portable masts) can be easily effected by two people in half an hour.

HF SSB TRANSCEIVER



TM180 "PIONEER" HF SSB TRANSCEIVER. 1.8-18MHz, 6 channels 100 watts RF output measuring only 95(H) x 240(W) x 310(D)mm and weighing 6kg. May be operated as a base or mobile transceiver, complementing our trap dipole and HW4 mobile aerials. Prices start at £700, making this unit not only very attractive but highly competitive.

SOUTH MIDLANDS COMMUNICATIONS LTD.


SM HOUSE
 OSBORNE ROAD, TOTTON
 SOUTHAMPTON SO4 4DN

Telex: 477351 SMCOMM G
 Tel: Totton (0703) 867333

WW - 050 FOR FURTHER DETAILS

HM605 = COMPARE...

– THE CHOICE IS **HAMEG**

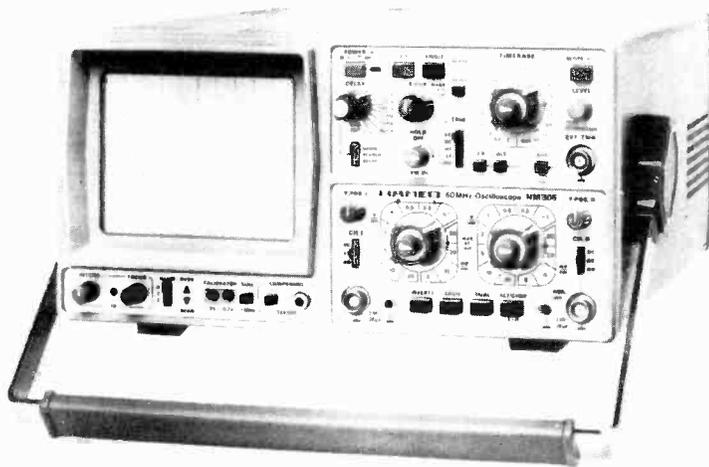

**IDEALLY SUITABLE FOR
COMPUTER SYSTEMS APPLICATIONS**

- 60 MHz Bandwidth
- 5mV–20V Sensitivity at 60MHz
- 1mV Sensitivity at 30MHz
- Timebase Range 5ns–2.5s/cm
- Reliable Triggering to 80MHz
- Normal and Peak Value Triggering
- Alternate Triggering
- Variable Sweep Delay
- 14kV Rectangular CRT
- Y-Output
- 1kHz/1MHz Calibrator
- Built In Component Tester
- 2 Years Warranty

£487

Prices U.K. list ex. VAT

For free data sheets of the full range contact:

HAMEG



74–78 Collingdon St. · LUTON, Beds. LU1 1RX · Tel. (0582) 41.31.7 · Telex 825 484

WW – 071 FOR FURTHER DETAILS

**SPECIAL
OFFER**

from

**ELECTRONICS &
Wireless world**

HIGH QUALITY PRECISION PLIERS AND CUTTERS

These precision box jointed pliers and cutters are manufactured in West Germany and are of extremely high quality. They are supplied to and used by the electronics industry. They all have double leaf springs, moulded-on PVC grips and polished heads. The cutters have induction hardened cutting edges.


As a little test of the quality and the squareness and fit of the jaws we tried holding pieces of paper with the pliers and cutting the paper with the cutters – we were extremely impressed. Naturally we also tested them with wire and were equally pleased with the results.

We decided to offer readers the alternative of a set of the three most vital tools, comprising top cutters, side cutters and snipe nose pliers (smooth inside jaws). All are approximately 4¾" long. In shops this set (Set A) would cost about £29.70, but our price to readers is **£19.50 incl VAT and UK p&p.**

Our alternative choice is the above set plus a pair of round nose pliers which are extremely useful for shaping wires, etc. This set (Set B) comprising the four tools would normally cost £38 but we are offering it at only **£24.75 incl VAT and UK p&p.**

We regret the tools are not available separately – only the sets as offered.

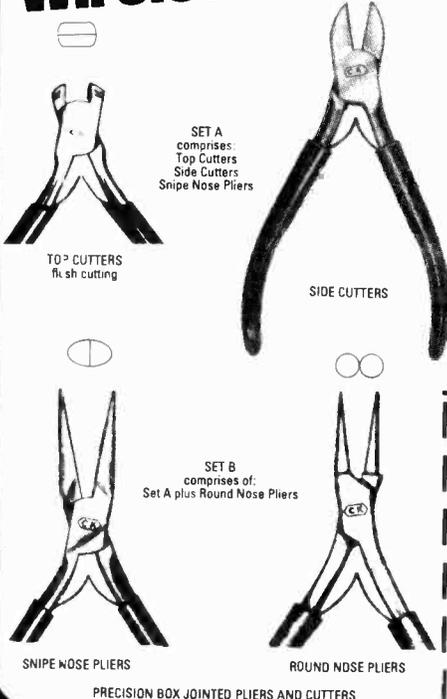To order either of the above, use coupon or photocopy or on plain paper and send with crossed cheque/PO made out to Wireless World Offers. Send to Pliers Offer, 48 Beauchamp Place, London SW3 1NX. Allow up to 28 days for delivery, UK addresses only. Closing date March 31st, 1984. VAT receipt will be supplied if SAE is enclosed with order.



SET A
comprises:
Top Cutters
Side Cutters
Snipe Nose Pliers

TOP CUTTERS
flush cutting

SIDE CUTTERS

SET B
comprises of:
Set A plus Round Nose Pliers

SNIPE NOSE PLIERS

ROUND NOSE PLIERS

PRECISION BOX JOINTED PLIERS AND CUTTERS

Coupon to Wireless World Pliers Offer, 48 Beauchamp Place, London SW3 1NX

Please send me:

.....Pliers/Cutters Sets

.....Set A at £19.50

.....Set B at £24.75

NAME
(please print)

ADDRESS

for which I enclose total £.....

Price includes postage, packing and VAT. Offer applies to UK only. Please allow 28 days for delivery. Registered No. 151537. Reg. Office: Quadrant House, Sutton, Surrey SM2 5AS. 83/199

Telephone: (0376) 27117 (24-Hour Ansaphone Service)
(0376) 42494

Telex: 987911

Greatech LTD
Electronics
DISPLAY & COMMUNICATION PRODUCTS

Hay Lane,
Braintree,
Essex CM7 6ST



R.F. POWER TRANSISTORS Many other types available					NEW VALVES National, Varian, Mullard, RCA,ITT ...					VIDICONS		MICROWAVE OVEN MAGNETRONS			
2N2857	2.06	SD 1006	2.00	2SC3020	12.22	AH221	35.00	6CL6	3.40	20 PE 11A	23.35	2M53 40.00 2M53A 47.50 2M107A 40.00 2M131 103.50 2M170 40.00 2M172H 45.00 2M172J 40.00 2M182 103.50 2M196 113.00	ALL MAGNETRONS NEW and from manufacturers such as LITTON HITACHI MATSUSHITA TOSHIBA AMPEREX	Discounts to approved dealers & service agents	
2N3137	2.70	SD 1012FL	8.30	MRF 221	12.05	AH238	35.00	6CW4	6.85	20 PE 13A	21.35				
2N3375	9.20	SD 1013	8.25	MRF 224	12.50	E80F	13.50	6DK6	1.00	20 PE 14	24.33				
2N3553	2.00	SD 1088	25.00	MRF 231	12.36	E88CC	2.20	6D05	5.50	20 PE 19	24.33				
2N3733	13.20	SD 1089	28.50	MRF 233	10.00	E180F	9.50	6D06B	4.00	20 PE 20	27.53				
2N3866	1.00	SD 1098	36.10	MRF 234	6.50	ECC81	1.50	6EA8	2.40	4848	25.00				
2N3926	11.26	SD 1127	2.60	MRF 238	12.60	ECC82	1.75	6GK6	2.46	7262A	25.26				
2N3927	11.82	SD 1135	8.42	MRF 239	16.00	ECC83	1.70	6J4	4.20	7735A	25.26				
2N4416	0.75	SD 1136	11.80	MRF 240	18.55	ECC88	1.60	6J5	1.80	8541	32.69				
2N4427	1.00	SD 1143	10.41	MRF 243	28.08	ECC91	8.00	6JB6A	3.00	8844	23.00				
2N4440	8.50	SD 1219	12.50	MRF 245	30.10	ECH81	2.75	6JS6C	5.00	9677M	31.00				
2N5016	8.72	SD 1229FL	8.80	MRF 247	30.10	EF86	1.60	6K6GT	2.75	Other types of Vidicon available Newvidicons and Ultracons price on application					
2N5090	16.80	SD 1272	11.20	MRF 260	5.00	EL34	4.00	6K06	5.00	Many other types available for commercial and domestic ovens					
2N5109	1.30	SD 1272FL	11.20	MRF 261	9.00	EL84	1.50	6LQ6	6.00	Discounts to approved dealers & service agents					
2N5160	3.80	SD 1285	12.75	MRF 262	11.00	ELL80	20.00	6SN7GTB	2.75						
2N5179	0.86	SD 1407	25.00	MRF 264	11.00	KT77	7.50	12BY7H	2.00						
2N5485	0.82	SD 1410	21.06	MRF 314	25.00	PL509	5.50	572B	30.00						
2N5486	0.88	SD 1412	30.00	MRF 401	11.84	QOV03-10	5.00	575A	40.00						
2N5589	5.70	SD 1416	33.00	MRF 406	12.83	QOV03-20A	60.00	5760	3.50						
2N5590	8.57	SD 1418	30.00	MRF 421	31.57	QOV06-40A	45.00	5726	2.40						
2N5591	8.90	SD 1428	26.00	MRF 433	16.21	QV03-12	5.80	5763	4.90						
2N5635	6.20	SD 1429	15.98	MRF 449A	14.00	2D21	2.85	5814A	3.25						
2N5636	12.50	SD 1434	30.00	MRF 450	15.00	3-400Z	82.00	5842	11.20						
2N5637	14.25	SD 1444	3.60	MRF 450A	11.40	3-500Z	82.00	5965	3.25						
2N5641	7.35	SD 1451	19.50	MRF 453	17.00	3-1000Z	280.00	6012	12.00						
2N5642	9.90	SD 1488	29.00	MRF 454	18.80	3B28	14.95	6021	3.40						
2N5643	13.00	2SC 730	4.50	MRF 455	16.00	4CX250B	40.00	6080	10.00						
2N5913	2.50	2SC1165	6.88	MRF 458	15.00	4CV350F	73.45	6159B	16.00						
2N5944	8.20	2SC1177	18.14	MRF 460	18.78	5U49B	3.20	6201	6.00						
2N5945	8.95	2SC1306	1.44	MRF 464	35.00	6AH6	4.00	6360	5.00						
2N5946	15.63	2SC1307	2.34	MRF 472	3.50	6AK5	1.00	6550A	8.00						
2N6080	6.00	2SC1678	1.94	MRF 475	2.50	6AK6	2.00	6688	12.00						
2N6081	8.75	2SC1945	4.45	MRF 476	2.20	6AN8A	3.20	6973	3.00						
2N6082	9.00	2SC1946A	18.54	MRF 477	18.70	6AQ5A	2.15	7558	9.50						
2N8083	12.00	2SC1947	9.24	MRF 515	2.50	6AS6	1.00	7586	9.00						
2N6084	13.20	2SC1970	2.50	MRF 604	3.30	6ASTG	7.00	7591A	3.80						
2N6094	8.00	2SC1971	10.32	MRF 607	3.20	6AT	1.35	7868	5.40						
2N6095	8.90	2SC1978	8.00	MRF 629	4.50	6A5GT	4.50	7905	19.50						
2N6096	20.20	2SC2166	1.70	MRF 646	26.24	6AU6A	2.30	7984	19.50						
2N6097	13.30	2SC2237	15.00	MRF 648	38.14	6AN8A	2.50	807	2.00						
SD 1005	7.20	2SC2538	1.82	MRF 091	3.00	6B8	3.10	811A	12.50						
ALSO AVAILABLE: A replacement guide to dozens of Motorola Transistor part numbers. Stocks of original RF Devices from such manufacturers as: MOTOROLA, RCA, GE, TRW, MSC, ACRIAN, TOSHIBA, FUJITSU, NEC, MITSUBUSHI, PHILLIPS, AMPEREX and others					POWER TUBE ACCESSORIES CONNECTORS FINGER STOCK CHIMNEYS SOCKETS					Diodes High Voltage Vacuum Capacitors		Transistors Silicon Controlled Rectifiers		OTHER PRODUCTS DISPLAY DEVICES National gas discharge seven segment and alphanumeric readout tubes (Burroughs equivalents) Vacuum fluorescent seven segment and alphanumeric display tubes <i>Enquiries on any type of display technology welcome</i> Normally stock items are shipped by return post	
										TERMS Cash, Postal Order or Cheque with order		CREDIT Accounts available subject to approved references		POSTAGE Add £1.00 to order	
										VAT All prices are excluding VAT, please add 15% to order		GUARANTEE All goods brand new and to specification		Quotations for any types not listed: SAE	

FREQUENCY COUNTERS

**HIGH PERFORMANCE
HIGH RELIABILITY
LOW COST**


The brand new Meteor series of 8-digit Frequency Counters offer the lowest cost professional performance available anywhere.

- ★ Measuring typically 2Hz – 1.2GHz
- ★ Sensitivity < 50mV at 1GHz
- ★ Setability 0.5ppm
- ★ High Accuracy
- ★ 3 Gate Times
- ★ Low Pass Filter
- ★ Battery or Mains
- ★ Factory Calibrated
- ★ 1-Year Guarantee
- ★ 0.5" easy to read L.E.D. Display

PRICES (Inc. adaptor/charger, P & P and VAT)

METEOR 100	(100MHz)	£104.36
METEOR 600	(600MHz)	£134.26
METEOR 1000	(1GHz)	£184.36

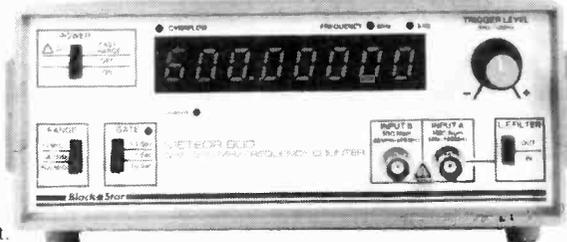Illustrated colour brochure with technical specification and prices available on request.




Designed and manufactured in Britain

Black★Star

BLACK STAR LTD, 9A Crown Street, St.Ives, Huntingdon, Cambs, PE17 4EB, England.
Tel: (0480) 62440 Telex: 32339

WW – 043 FOR FURTHER DETAILS

METER PROBLEMS?

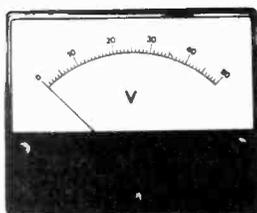

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full information from:
HARRIS ELECTRONICS (London)
138 GRAY'S INN ROAD, W.C.1
Phone: 01-837 7937
Telex: 892301

WW – 061 FOR FURTHER DETAILS



Audio Measuring Instruments, Audio Amplifiers, Loudspeakers and Loudspeaker Components for the professional and enthusiast

RADFORD AUDIO LTD.
10 BEACH ROAD
WESTON-S-MARE, AVON BS23 2AU
TEL. 0934 416033

WW – 049 FOR FURTHER DETAILS

SAMSONS

(ELECTRONICS) LTD.
9-10 Chapel Street, Marylebone
London NW1 5DN
21-23 Bell Street, London, NW1
01-262 5125 & 01-723 7851



We are stockists of the complete range of "DOUGLAS" transformers.
Please ring or send S.A.E. for details.

MARCONI TF 1370

Wide range Oscillator sine/square,
10 c/s to 10 meg. Very nice condi-
tion £160 inc. VAT and carriage.

OLIVETTI TE3000 TELEPRINTERS

With stand. Only £99 inc. VAT
Ring for carriage details

WODEN HEAVY DUTY TRANSFORMER

Pri 220-240V Sec 2.5V 35A 4-5 6.3V
12A. Both secs 10KVAC WKG £30
inc. carriage and VAT

NEW TRANSFORMER BARGAINS

By famous makers
No. 1 Pri 115-230V Sec 21V 3A +
40V 300 M/A £5.25
No. 2 Pri 220-240V Sec 17.5V 1A 3
times £5.75
No. 3 Pri 220-240V Sec 29-28-27-0-
27-28-29V 0.3A £4.00
No. 4 Pri 220-240V Sec 6.3V 5ACT
6.3V 2ACT £5.00
No. 5 Pri 220-240V Sec 40V 3A
..... £6.25
All prices inc. VAT and carriage

OSCILLOSCOPES

TEKTRONIK 545A £125
HEWLETT PACKARD 185B £175
TEKTRONIK 585 £125
Callers only or ring for special deli-
very

CONSTANT VOLTAGE TRANSFORMERS

Gould Advance
Typ 240V output $\pm 1\%$
150W £15.00 carr £2.95
250W £39.50 carr £3.75
500W £85.00 carr £7.50
3000W £295.00 carr £20.00
All prices inc. VAT

PAPER BLOCK CAPACITORS

8MFD 2500V WKG DC £6.50
10MFD 350V WKG DC £15.00
8MFD 400V WKG DC £2.50
4MFD 1000V WKG DC £2.00
1MFD 1000V WKG DC £1.25
All prices inc. VAT and carriage

FANS

MUFFIN 4 1/2" 110V £4.00
WOODS 6" and 8" 240V £9.50
Tangential Blowers 240V approx
3"x15" vent. Very powerful. £11.
All prices inc. VAT and carriage

AUTO STEPDOWN TRANSFORMERS FOR AMERICAN EQUIPMENT

240/110 Volts. 80-2250 watts. Regular stock line. Types 80-1500 watts are fully shrouded. Fitted with American two or three pin socket outlets and 3 core 240V mains lead. Types 1750 and 2250 watts are steel cased with two American socket outlets. Neon indicator, three core mains lead and carrying handle. Send SAE for price list and further details. American sockets, plugs, adaptors also available.

AVOMETERS

We have in stock a limited quantity of excellent quality AVOs.
AVO 8 £59.95 inc. VAT. AVO 7 £37.50 inc. VAT.
AVO MINOR £20 inc. VAT. Callers only, or ring for special delivery.

MEGGERs

Special offer!! 250V and 500V metrohms at give-away prices. Buy now while stocks last. £35 + VAT. Callers only or ring for special delivery.

DISC DRIVES

Disc drives by magnetic peripherals including 8" floppy disc single sided, without control card. Circuit diagram can be obtained from manufacturer. Excellent value at £27.50 inc. VAT and carriage.

SWITCH MODE POWER SUPPLIES

By Gould Advance
5V 40 amp £35. 5V 20 amp £25. 10.5V 20 amp £30. Inc. VAT and carriage.

HIGH GRADE LT TRANSFORMERS

ALL PRIMARIES 240v
OPEN FRAME TOP PANEL CONNECTIONS
No 1 tapped 2-3-4-5-6-7-8-9-10-11-12-13-14-15V 8A £10. No 2 12V 8A £7.50. No 3 tapped 13-12-10-8V 8 1/2A £9. No 4 Sec 6.3V 2A 6.3V 2V and 32-0-32V 280 m/A £4.75. No 5 Sec 37V 1.5A, 15V 1/2A, 9V 50 m/A £3.95. No 6 Sec 14V 2A £3.95. No 7 Sec 27.5-0-27.5V 1.2A and 7-0-7V 750 m/A £3.50. All prices include postage and VAT.

PARMEKO LT TRANSFORMERS

Open frame type top panel connections, prices include postage and VAT
No 1 12-18-32V 2A (DC rating) and 12-18-32V 1/2A (DC) £9. No 2 12-18-32V 1A (DC) and 12-18-32 1/4A £5. No 3 12-18-32V 1/2A (DC) and 12-18-32V 100 m/A £3.95. No 4 12-18-32V 1/4A (DC) and 12-18-32V 1/4A (DC) and 12-18-32V 50 m/A (DC) £2.50. No 5 32V 100 m/A (DC) and 32V 25 m/A DC £2.50.

SPECIAL OFFER!!!

SERVALCO SERVO MOTORS
We have a limited amount of printed circuit motors in first-class condition. Spec: 90V DC 5.5 Amps continuous torque 140 oz in 3/4" dia output shaft. Overall dimensions 2 1/2" x 7 1/2" rpm 2350. £29.95 inc VAT and carr.

INSTRUMENT CASE BARGAIN!

FANTASTIC OFFER
Stylish aluminium case in dark blue finish with integral carrying handles and movable front legs for tilt facility. Fitted with IEC mains socket and 20mm fuse carrier. Comes complete with mains lead with 13 amp plug and IEC plug. Size: 20"x28"-33cm. £13.50 inc. VAT and carr.

BARGAINS!!!

TRANSFORMER: Input 390-415 3ph, output 2650V 4KVA Star. £150 inc. VAT. Ring for carriage details.
HEAVY DUTY H.T. TRANSFORMER: Input 230V, output 1880-0-1880V at 64 amp. Very conservatively rated. Size approx 14"x16"x12". Also 500-0-500V 85 M/A £150 inc. VAT and carriage.
CHOKES: 5MH 52 amp DC, 50MH 20 amp DC, 200MH 20 amp DC. All at £27.50 inc. carriage and VAT.

12" BLACK AND WHITE MONITORS

Made by leading USA firm, will handle 80 columns, suitable for most makes of computers. £28.50 inc VAT. Callers only.

PARMEKO TRANSISTOR TESTERS

Leakage. Gain s/c-o/c readings shown on 2in. panel meter. Full instructions
£6.50 inc. postage and VAT

HENGSTLER

Low voltage resettable counters. 52 ohms 6-12V DC 6 digit. Compact size. Only £3.25 inc VAT and carr.

E.H.T. TRANSFORMERS

High-grade E.H.T. Tranny. PRI 240V, sec. 10,000V, 18 M/A. Probably used for boiler ignition but with 101 other uses!!!
£5 inc. carr. & VAT.

PARMEKO OP TRANSFORMERS

Pri 6000 or 8000V or CT Sec 3.75 or 15V Ser/Par for EL84x2 12.5W £4.50. Pri 5000 for EL84 3W Sec £3.75 or 15V Ser/Par £2.50. Pri 30-45-60-90 to 1 also 90TO for push/pull Sec 3.75V £2. All prices include postage and VAT.

AC WKG CAPACITORS

MFD	AC wkg	Price	MFD	AC wkg	Price
0.25	1500V	£1.50	5	360V	£1.75
0.75	440V	£1.00	5	440V	£2.00
1	400V	£1.50	4	600V	£2.00
2.5	360V	£1.50	6	300V	£2.00
2.7	700V	£1.75	8.4	250V	£1.50

All prices include postage and VAT

ELECTROLYTIC CAPACITORS

22,000 63V DC wkg. 33,000 40V DC wkg. 3,000 50V DC wkg. 20,000 45V DC wkg. 6,500 50V DC wkg. All £4 each inc VAT and carr.

PARMEKO HT CHOKES

10H 250m/a	£5.95	20H 75m/a	£3.50
5H 250m/a	£5.50	10H 75m/a	£2.95
5H 180m/a	£4.75	7.5H 60m/a	£2.50
2.5H 500m/a	£5.95	15H 120m/a	£3.95
2.5H 250m/a	£5.50	50H 10m/a	£2.50
20H 120m/a	£4.75	25H 60m/a	£2.75

All prices include postage and VAT

HEAVY-DUTY LT CHOKES

C core type 10 m/h 25 amps £10 carr. £3, VAT £1.95.

SPECIAL OFFER HIGH-GRADE ISOLATION TRANSFORMERS

GPO spec. Pri 110-115-120-220-240V. Sec 240V 1500 watts can be used in reverse. Open frame terminal block connections £29.50, carr. £4, VAT £5.02. Pri 240V, Sec 240V, 250 watts, open frame type tag connections, £10, P&P £2, VAT £1.80. Pri 100-110-200-210-220-230-240-250V. Sec 220-230-240V 600W, can be used in reversed open frame type terminal block connections, £15, carr. £2.80, VAT £2.67.

PARMEKO NEON TRANSFORMERS

PRI tapped 200-220-230-240-250V. Size 7000V 55 M/A. Totally enclosed in wall mounting steel case. Size 9 1/2"x8 1/2"x4 1/2 in.
£17.50 inc. VAT and carriage
PRI tapped 200-220-230-240-250V. Size 5000V 20 M/A. Totally enclosed in wall mounting steel case. Size 7x6x5 in.
£12.50 inc. VAT and carriage

COMPUTER GRADE LT TRANSFORMERS BY FAMOUS MAKERS

ALL PRIMARIES 220-240V

PRICES INCLUDE POSTAGE AND VAT

No 1 Sec 43V 3A £6.95. No 2 Sec 40V 3A £6.95. No 3 Sec 65V 1A and 18-24V 1/2A £5.95. No 4 Sec 25V 2A £4.50. No 5 Sec 24V 2A £4.50. No 6 Sec 27.5-0-27.5V and 7-0-7V 0.75A £5.25. No 7 Sec 13-0-13 A and 12V A £ No 8 Sec 60V 1 1/2A £4.95. No 9 Sec 40V 1 1/2A £4.50. No 10 Sec 10-0-7-0-7-10V 1/2A and 29-21-0-21-29V 370 m/A, c core £4.25. No 11 Sec 55V 1/2A £3.75. No 12 Sec 24V 3A and 110V 1/2A £7.95. No 13 Sec 28V 1 1/2A and 24V 1 1/2A £5.50. No 14 Sec 36V 1/2A £3.50. No 15 Sec 20V 2A £3.75. No 16 Sec 12-25V 2A £3.75. No 17 Sec 24-0-24V 1A and 6.3V 1A £4.95. No 18 Sec 24V 4A £5.50. No 19 Sec 12-15-20-24-30V 1A £4.75. No 20 Sec 4.5V 5A twice £4.50.

PARMEKO HT TRANSFORMERS

ALL PRIMARIES 220-240V

POTTED TYPES

No 1 Sec 500-0-500V 120 m/A 6.3V 5A 6.3V 3A 5V 3A £8.50, inc postage and VAT. No 2 Sec 300-0-300V 60 m/A 6.3V 2A CT 6.3V 1A £8.50 inc postage and VAT. No 3 400-0-400V 180 m/A £6.50 inc postage and VAT. No 4 Sec 400-0-400V 150 m/A and 150-0-150V 20 m/A £6.50 inc postage and VAT. No 5 Sec 350-325-0-325-350V 120 m/A £6.50 inc postage and VAT. Gresham Pri 220-240V. Sec 250V 80 m/A 6.3V 4.5A 1.5V 1.2A £5.95 inc postage and VAT. Pri 230-250V. Sec tapped 190-210V 24 m/A 6V 1A £3.95 inc postage and VAT. Pri 220-240V Sec 300V 200 m/A 30V 100 m/A 6.3V 5A half shrouded, sub chassis mounting £6.50 inc postage and VAT. Pri 220-240V Sec 370-390-410V 6 m/A £2.75 inc postage and VAT. WW-18

WW - 052 FOR FURTHER DETAILS

reprints

If you are interested in a particular article / special Feature or advertisement published in this issue of

WIRELESS WORLD

why not take advantage of our reprint service.

Reprints can be secured at reasonable cost to your own specifications providing an attractive and valuable addition to your promotional material. (Minimum order 250.)

For further details contact
Michael Rogers, Electrical-Electronic Press. Phone 01-661 3457 or simply complete and return the form below.

To Michael Rogers, Reprints Department,
Quadrant House, The Quadrant
Sutton, Surrey SM2 5AS

I am interested in copies of the article / advertisement headed featured in

WIRELESS WORLD

on page(s) in the issue dated

Please send me full details of your reprint service by return of post

Name

Company

Address

Tel. No.

BIRD Electronic Corporation

THRULINE® Directional Wattmeters


TERMALINE® RF Coaxial Load Resistors

TENULINE® Attenuators and accessories from stock

Aspen Electronics Limited

The exclusive UK representative for Bird Electronic

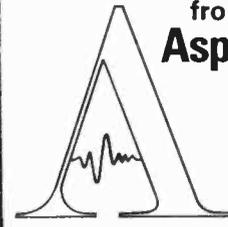2/3 Kildare Close, Eastcote, Ruislip
Middlesex HA4 9UR
Tel: 01-868 1188 Tlx: 8812727




WW - 060 FOR FURTHER DETAILS

ELECTRONIC POWER UNITS

FOR XENON ARC AND MERCURY ARC LAMPS

UNITS AVAILABLE FOR LAMPS RANGING FROM 75 TO 6500 WATTS.

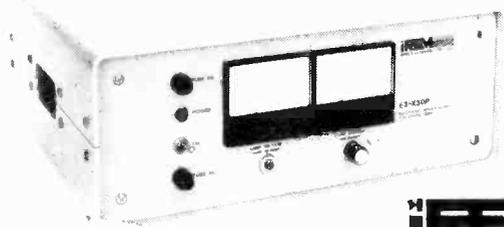Lamp housings and lens systems manufactured as standard off the shelf models or to specific design.



K. T. Manners Design Ltd.

P.O. Box 936, London, W4 4NW Telephone: 01-994 7155. Telex: 28604



WW - 067 FOR FURTHER DETAILS

Appointments

Advertisements accepted up to 12 noon Tuesday, February 7, for March issue subject to space available.

DISPLAYED APPOINTMENTS VACANT: £17 per single col. centimetre (min. 3cm).
LINE advertisements (run on): £3.50 per line, minimum £25 (prepayable).
BOX NUMBERS: £5 extra. (Replies should be addressed to the Box Number in the advertisement, c/o Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS).
PHONE: IAN FAUX, 01-661 3033 (DIRECT LINE)

Cheques and Postal Orders payable to BUSINESS PRESS INTERNATIONAL LTD. and crossed.



FOR TOP ELECTRONIC APPOINTMENTS

£7,000-£22,000

- ★ **Where does your interest lie:** Graphics; Comms; Robotics; Simulation; Image and Signal Processing; Medical Automation; Avionics; Acoustics; Weapons; Radar; Opto and Laser?
- ★ **Experienced in:** Microprocessor Hardware or Software; Digital and Analogue circuitry; RF and Microwave techniques?
- ★ **There are hundreds of opportunities in:** Design; Test; Sales and Service for Engineers and Managers
- ★ **For free professional guidance:** Dial 100 and ask for **FREEPHONE JOBLINE** or send your C.V. (no stamp needed) to:

ELECTRONIC COMPUTER AND MANAGEMENT APPOINTMENTS LIMITED
 Freepost, Barkway, Royston, Herts SG8 8BR

(1926)

Electronic Engineers – What you want, where you want!

TJB Electrotechnical Personnel Services is a specialised appointments service for electrical and electronic engineers. We have clients throughout the UK who urgently need technical staff at all levels from Junior Technician to Senior Management. Vacancies exist in all branches of electronics and allied disciplines - right through from design to marketing - at salary levels from around £5000-£15000.

If you wish to make the most of your qualifications and experience and move another rung or two up the ladder we will be pleased to help you. All applications are treated in strict confidence and there is no danger of your present employer (or other companies you specify) being made aware of your application.

TJB ELECTROTECHNICAL PERSONNEL SERVICES,

12 Mount Ephraim,
 Tunbridge Wells,
 Kent. TN4 8AS.

Tel: 0892 39388
 (24 Hour Answering Service)



Please send me a TJB Appointments Registration form:

Name

Address

(861)

LEADING LONDON RECORDING STUDIO

requires

Young Person

with good basic knowledge of physics and electronics to train as assistant to chief maintenance engineer.

The successful applicant will be trained to work with the latest audio equipment including solid state logic, Studer, etc.

Apply in writing to Box No. 2402

UNIVERSITY OF SURREY

ELECTRONIC/ELECTRICAL ENGINEERING OPPORTUNITIES

The Industrial Electronics Group in the Department of Electronic and Electrical Engineering at the University of Surrey has vacancies for Technicians (Engineers) who are keen to further their experience in a wide range of electronic fields and are qualified to ONC level or higher.

The work will involve operating on a project basis, covering all phases of prototype equipment manufacture, development and documentation.

The Group at present consists of a small team of Professional Engineers and Technicians who liaise closely with academic staff in problem solving for industry. Projects usually entail the development of novel instrumentation covering communication, non-destructive testing and signal processing fields with increasing emphasis on microprocessor based systems.

The commencing salary will be within the range of £5,151 to £7,332 on Grade 3, 4 or 5 technician salary scale (according to age, qualifications and experience) for a 36½ hour week. Excellent working conditions including the possibility of day-release study for higher qualifications.

For further information or to arrange a visit contact the Staff Officer, University of Surrey, Guildford GU2 5XH (Guildford (0483) 571281, extension 776) to whom completed application forms must be returned by 31st January 1984.

Career Opportunities in the High Technology Broadcast Industry

Located in Hampshire, Sony Broadcast is an internationally renowned world leader in the professional broadcast television industry. Our extensive product range includes cameras, VTR's/VCR's, sophisticated editing control systems and now the exciting new range of Betacam equipment. Applications are now invited from experienced engineers who feel they have the potential to develop with the Company.

Field Service Engineer

The successful candidate will be engaged in the service, repair and commissioning of our extensive range of equipment. This will involve travel throughout our marketing territory of Europe, the Middle East and Africa. Full product training will be given where necessary. Applicants should have several years experience gained in the broadcast television industry, either in operations or allied manufacturing industries, and up-to-date knowledge of VTR's and cameras is essential.

Senior Project Engineer – Systems

To co-ordinate a small team responsible for the manufacture and commissioning of complex static and mobile television systems including dubbing and editing systems, full production studios and EFP packages. This is a challenging and responsible position and candidates should have direct experience of sound and television principles. A background in project management together with the ability to plan and meet deadlines is also required.

Engineer – Customer Acceptance

To join a department responsible for the evaluation of product performance. Key activities will include conducting customer acceptance tests, the provision of engineering support to our inspectorate and an involvement in the establishment and maintenance of ATE. There will be a significant involvement with

customers. Candidates aged 25 plus should possess HNC electronics or equivalent together with 5+ years experience in a high technology electronics environment.

Lecturer

To conduct theoretical and practical courses on our range of equipment. The department boasts excellent lecturing facilities together with a technical publications department and library. Applicants, educated to at least honours degree level electronics, should be able to present ideas clearly and have the ability to assimilate state of the art broadcast technology. Previous lecturing experience would be an advantage, although training in teaching skills and on our product range will be given where appropriate.

Product Engineer

We are looking for a professional electronics engineer to join our Product Management team. The person appointed will provide technical support to the Marketing and Engineering divisions of Sony Broadcast. This position combines in-depth technical involvement with interdepartmental and customer liaison, and there will be an opportunity for overseas travel. Applicants should be honours graduate electronics engineers, preferably experienced in the electronics industry. Full product training will be given where necessary.

If you like the thought of enjoying the success of world leadership together with a highly attractive salary and benefits package, write with details of career to date and present salary to David Parry, Personnel Department, Sony Broadcast Ltd, City Wall House, Basing View, Basingstoke, Hants RG21 2LA. Telephone (0256) 55011

SONY
Broadcast



Sony Broadcast Ltd.

City Wall House
Basing View, Basingstoke
Hampshire RG21 2LA
United Kingdom

(2425)

Appointments

SYSTEM PROJECT ENGINEERS

The Ampex Broadcast Systems Group based in Reading, Berkshire, supplies complete television studio and mobile systems to broadcast installations worldwide.

Owing to expansion of the group's activities, we are now looking for Systems Project Engineers to join our innovative project teams involved in the design installation and commissioning of television studio and outside broadcast vehicle projects.

These appointments involve occasional overseas travel for on-site commissioning.

Key requirements are:

- * Thorough knowledge of video and audio principles – HNC/Degree in Electronics preferred.
- * Experience in broadcast television industry.
- * Previous knowledge of TV systems an advantage.

Attractive salaries and benefits, which include pension, life assurance, permanent health scheme, BUPA care option, product training, overseas allowances and relocation expenses where appropriate.

AMPEX

Please contact Maureen Brake for an application form:

AMPEX GREAT BRITAIN LIMITED
ACRE ROAD
READING RG2 0QR
TEL. READING (0734) 875200

(2447)

VIDEO ENGINEERS

Rediffusion Consumer Manufacturing Ltd is seeking an intermediate and a senior video engineer with OND, HND or similar qualifications, together with a knowledge of modern consumer electronics circuitry techniques, to join a small team looking after Rediffusion's mammoth investment in domestic video recorders and video disc players.

In addition to analysis of performance and long term reliability factors, assessment reporting is an important part of the team's function and the ability to express oneself verbally and in writing is essential. Our laboratories are situated at Chessington within easy commuting distance of the Surrey countryside. Attractive salaries and the usual big company benefits, which include assistance with relocation expenses, are offered to suitably qualified and experienced engineers. If you believe you can make a significant contribution to our video projects please write to or phone:-

Harry Brearley,
Rediffusion Consumer Manufacturing Ltd.,
Fullers Way South,
Chessington, Surrey. KT9 1HJ.
Telephone: 01-397-5411.

REDIFFUSION

(2407)



CAPITAL APPOINTMENTS LTD

THE UK'S No. 1 ELECTRONICS AGENCY

If you have HNC/TEC or higher qualifications and are looking for a job in design, test, customer service, technical sales or similar fields:

Telephone now for our free jobs list
We have vacancies in all areas of the UK
Salaries to £15,000 pa

01-637 5551 or 01-636 9659
(24 hours)

CAPITAL APPOINTMENTS LTD
29-30 WINDMILL STREET, LONDON W1P 1HG

(291)

datron

INSTRUMENTS

CUSTOMER SERVICE TECHNICIAN

£6,000-£8,500

Due to continuing expansion, a vacancy exists for a first-class technician in our busy Service Department.

The successful applicant will be engaged primarily in the repair and calibration of our range of premium voltmeters and calibrators, and will be prepared to undertake site visits in support of our systems activities.

He or she will have practical experience in the repair to component level of precision analogue and embedded microprocessor circuitry. Some understanding of high level programming and IEEE 488 BUS is desirable.

Relocation assistance will be offered where appropriate. Please apply in writing for an application form to:

David Marsh, Customer Service Manager
DATRON INSTRUMENTS LIMITED
Hurricane Way, Norwich Airport
Norwich NR6 6JB

(2365)

Telecommunications

Marathon's Aberdeen office is the nerve centre of a private wire system linking the Aberdeen office with the Peterhead Shore Base and the Brae-A platform. We currently have two vacancies within the Telecommunications function for experienced individuals to become part of a small team. This group has overall responsibility for our communications networks, comprising data, telex, facsimile and all voice equipment.

Telecommunications Analyst - Onshore


Working at Marathon's Aberdeen office you will be responsible for the efficient day-to-day running of the network. You will be required to provide technical support to users and to produce clear and concise progress reports on system development and maintenance. There will be some opportunities to be involved in the specification of various systems.

Candidates will be qualified to HNC level with at least three years' experience of speech systems, data lines and international circuits; you should also have some relevant practical experience. Relocation assistance, as appropriate, is available for this position.

Telecommunications Technician - Offshore

Working offshore on a 2-week rotation you will be responsible for all telecommunication and radio equipment on the platform. As an experienced technician, your main functions will be to undertake repair work, preventive maintenance and fault-finding. You will form part of the offshore maintenance group and report directly to the Topsides Maintenance Supervisor.

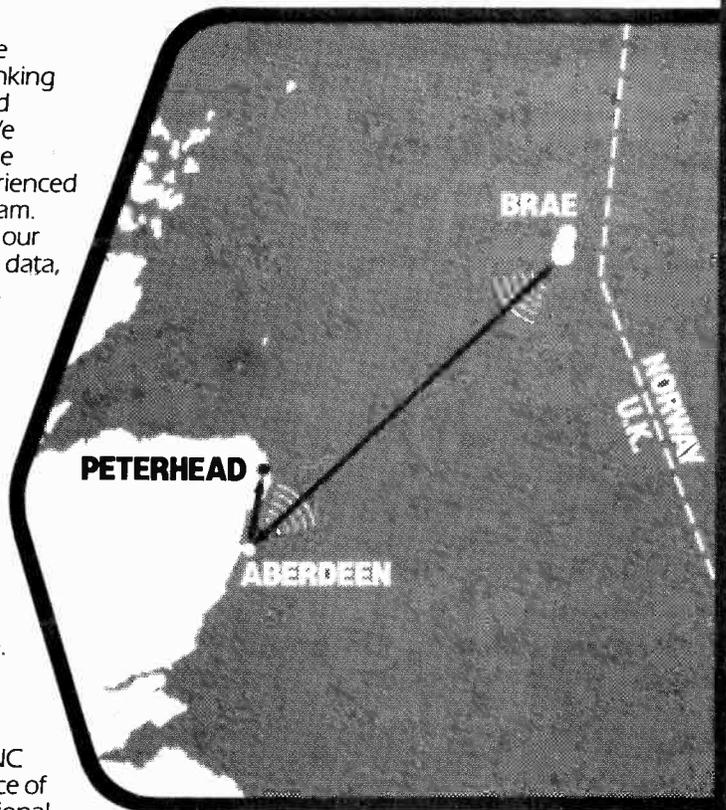A City & Guilds or ONC qualification is required for this position and your three years' experience should include some time offshore.



For both positions, we are offering competitive salaries supported by an attractive range of benefits including non-contributory pension scheme, subsidised BUPA and generous offshore allowances where appropriate.

Please write or telephone for an application form to:

Ian M Drysdale, Employee Relations Representative, Marathon Oil U.K., Ltd., Marathon House, Rubislaw Hill, Anderson Drive, Aberdeen AB2 4AZ. Tel: (0224) 576133.



(2438)

Appointments

Radio Systems Planning Engineers Middlesex

Over the past 35 years IAL has been involved in almost all areas of communication technology and has developed an expertise for which demand continues to expand worldwide. Consequently we now need additional Engineers to join the Telecommunications Engineering Department at our Headquarters near Heathrow.

These appointments represent excellent career moves for Engineers with varying levels of qualifications and experience and offer complete involvement in a planning and consultancy role on modern radio communications systems. These systems will be in the HF to SHF

bands and range from point to point links through mobile area coverage schemes to broadband microwave links.

A generous starting salary can be expected depending on position, qualifications and experience, plus an excellent benefits package which includes Pension and Life Insurance Scheme and relocation expenses where appropriate.

For further details phone the Technical Recruitment Officer, on 01-574 5134 or write to him at Recruitment Services Division, IAL, Aeradio House, Hayes Road, Southall, Middlesex, UB2 5NJ. Please quote Ref. K004.



THE HIGH TECHNOLOGY TASK FORCE
COMMUNICATIONS SYSTEMS
COMPUTER SYSTEMS AND SERVICES
MEDICAL SERVICES
AVIATION SYSTEMS AND SERVICES-WORLDWIDE

(2420)

WANTED

School-leaver for busy West End electronic component factors
Qualifications minimum O level Maths, English, Physics/Electronics
Good salary for enthusiastic applicant
Apply Box No. 2441

CAREER IN MUSIC ELECTRONICS

Music Electronics company specialising in the design of electronics for music industry requires an engineer to join design team.
Duties will include design and test, knowledge of digital, analogue, C.A.D., microprocessors.

Ability to work on own initiative. Knowledge of music and sound would be appreciated but not necessary. Ideal candidate will have HTC or HTD, HNC/HND degree or equivalent.

Sound knowledge of business administration will be expected. Excellent promotional prospects.

Salary negotiable. Position would suit ambitious graduate.

Applicants write with full C.V. to:

MUSIC ELECTRONICS CO.
c/o Kynastons (Business Consultants)
Block D, Metropolitan Wharf
Wapping High Street, London, E.1
Telephone: 01-265 0722 (24-hour phone)
or 01-806 5127 (Evenings)

(2418)

TECHNICAL AUTHORS

We have vacancies for experienced and trainee technical authors, to write handbooks on some of the latest technology electronics equipment.

Prospective trainees should have a sound knowledge of electronics and the ability to express themselves concisely in the written word.

We offer varied and interesting work, pleasant working conditions and an attractive salary.

Applications to:

**The Manager
Engineering & Technical
Publications Ltd
12 Shute End
Wokingham, Berks**

Telephone:
Wokingham (0734) 790123

(2417)

BORED ?

Then change your job!

1) Computer Field Service Engineer
Required with VAX machine experience. £7,000 + car. Bucks.

2) Radio/Radar Test and Fault Finding of RF systems
£6-10K. Middx

3) Computer Peripherals Service Engineer

To work on printers, disc drives, terminals. To £9,000. Berks.

4) Service Personnel (RAF, RN, Army)

We have many clients interested in employing ex-service fitters and technicians at sites throughout the UK. Phone for details.

5) £500 per week

We are paying very high rates for contract design and test engineers who have a background in RF, MICROWAVE, DIGITAL, ANALOGUE or SOFTWARE, at sites throughout the UK.

Hundreds of other Electronic and Computer Vacancies to £12,500

Phone or write:

Roger Howard, C.Eng., M.I.E.E., M.I.E.R.E.

CLIVEDEN CONSULTANTS

87 St. Leonard's Road, Windsor, Berks.
Windsor (07535) 58022 (5 lines)

(1640)

CLIVEDEN

**THE UNIVERSITY OF SHEFFIELD
AUDIO-VISUAL AND
TELEVISION CENTRE**

SENIOR TELEVISION ENGINEER

Applications are invited for the above permanent university post. The successful applicant will take charge of all engineering aspects of the Centre's work, including planning and development, studio and mobile operations and supervision of the technical staff. Production is based on 1" master video tape for recording and editing. This busy and successful Centre operates to high professional standards. Applicants should preferably be graduates or have comparable qualifications in electronic engineering and wide experience in broadcasting, industrial or educational television. Initial salary on Grade II for other related staff £11,160-£14,125 a year according to qualifications and experience. Particulars from the Registrar and Secretary (Staffing), the University, Sheffield S10 2TN to whom applications (5 copies), including the names of three referees, should be sent by 3 February 1984.

Quote ref: R21/II

**Preston Polytechnic
School of Electrical and
Electronic Engineering**

Applications are invited for the post of

SENIOR LABORATORY/WORKSHOP TECHNICIAN

Salary: Scale 4/5M (DLW) £6,264 to £7,896 plus up to £120 per annum for possession of appropriate qualifications.

Applicants must possess a recognised electrical/electronic technician qualification and have experience in electronic design and construction.

Application forms and further details obtainable from the Personnel Officer, Preston Polytechnic, Corporation Street, Preston, PR1 2TQ. Telephone: Preston 262027.

Reference No: NT/83/84/49.

Closing Date: February 17th, 1984.

(2422)

Trainee Broadcast Engineers

We are responsible for broadcasting the programmes of Independent Television, Channel Four and Independent Local Radio. The continued growth of our broadcasting services means we have a number of vacancies for Trainee Broadcast Engineers who, on completion of their training, will work in a challenging and secure environment.

The selected candidates will embark on our 18-month residential training course which commences in June 1984. It will be conducted at our Training College, in Devon, and also at the Newcastle Polytechnic. The course is designed to give you a training in Broadcast Transmission Engineering that is second to none. It demands a high standard of understanding and personal commitment from those selected to undertake it. During the course we will pay you a salary and in addition, all your fees, accommodation and meals.

Applications are invited from men and women who hold an HND/HNC/HTEC in Electrical or Electronic Engineering or the City and Guilds Telecommunication Technicians Full Technological Certificate with some appropriate experience; or who are qualified or about to qualify to First Degree level in Electrical/Electronic Engineering or related disciplines.

Your salary while training will be £6,652 per annum. On the satisfactory completion of training, your salary will be £8,421 and will rise by annual increments to £10,461 per annum; further progression to £12,966 per annum is possible.

Employment benefits include a free life assurance and personal accident scheme, a contributory pension scheme, generous relocation expenses and subsidised mortgage facilities.



**INDEPENDENT
BROADCASTING
AUTHORITY**



An Equal Opportunities Employer

For a fully illustrated booklet and application form, please write to Mike Wright, Personnel Officer - Engineering Regions, IBA, Crawley Court, Winchester, Hants. SO21 2QA. Or telephone the Personnel Office between 9 am and 4 pm Monday to Friday on Winchester 822574 or 822273.

(2370)

LOGEX ELECTRONICS RECRUITMENT

Specialists in Field & Customer Engineering appointments, all locations and disciplines.

Logex House, Burleigh, Stroud
Gloucestershire GL5 2PW

0453 883264 & 01-290 0267

(24 hours)

CHELSEA COLLEGE University of London ELECTRONICS WORKSHOP TECHNICIANS

required for interesting work for Electronics and Physics research and teaching. Includes prototype instrument design, development and construction and the servicing and repair of commercial electronic equipment.

Experience and qualifications in Electronics (particularly digital) at an appropriate level are essential. Inclusive salaries:

Grade 6 - £8,452 to £9,852 p.a.;

Grade 5 - £7,529 to £8,582 p.a.

Further details and application forms from:

Mr M. E. Cane, Chelsea College
Department of Electronics
Pulton Place, London SW6 5PR.

(2433)

LOOKING FOR NEW HORIZONS?

Your experience and qualifications could take you to one of the more pleasant Middle East countries where vacancies currently exist for:-

Fully trained ELECTRONIC TECHNICIANS

With a minimum of five years experience in servicing, maintenance and repair, including defect diagnosis, of various types of military ground based electronic equipment. These unaccompanied posts include free accommodation, medical care and free air travel to the UK for frequent leave periods.

Attractive salary with bonus and allowances normally free of UK Tax. For further information write to:- **Company Personnel Manager, Airwork Limited, Bournemouth - Hurn Airport, Christchurch, Dorset BH23 6EB.**

(2403)



Airwork
Limited



Brighton Polytechnic Learning Resources

require an

ELECTRONIC ENGINEER

(£7,191-£8,712) to maintain an unusually wide range of colour television and audio-visual equipment, including video recorders, monitors and cameras, to develop new maintenance procedures for implementation by Learning Resources staff, and to improve existing video and A/V facilities.

Application forms and further details available from the Personnel Officer, Brighton Polytechnic, Mithras House, Moulsecoomb, Brighton BN2 4AT. Telephone (0273) 893665, ext. 2536. Closing date: February 16th, 1984.

BOX NOS.

Box number replies should be addressed to:

Box No.....
c/o Wireless World, Quadrant House
The Quadrant, Sutton, Surrey SM2 5AS

Appointments

Graduate Electrical/Electronic/ Telecommunications Engineers-

Research and Development to support Emergency Services

The Directorate of Telecommunications, London, is responsible for the extensive facilities used by the police, fire, prison and associated services in England and Wales. Graduate Engineers ensure that the Emergency Services derive maximum benefit from the use of modern technology in areas such as communications.

The training and experience given to Graduate Engineers — ranging from the initial interpretation of a non-technical statement of requirement through to the design, development and contract definition — is carefully planned by a senior engineer and covers the training requirements of the IEE for corporate membership.

You must have a good honours degree (preferably at least upper 2nd class) in electronics, telecommunications, or electrical engineering or an allied subject approved by the IEE.

Your starting salary will be £7900 or £8190 depending on experience. Completion of training (usually one or two years) leads to a salary scale rising to £10,930. Salaries include £1250 Inner London Weighting. Promotion prospects.

For further details and an application form (to be returned by 3 February 1984) write to Civil Service Commission, Alencon Link, Basingstoke, Hants, RG21 1JB, or telephone Basingstoke (0256) 68551 (answering service operates outside office hours). Please quote ref: T/6139.

Home Office

(2424)

ELECTRONICS APPOINTMENTS £6,000 - £16,000

ANALOGUE, RADIO, MICROWAVE
DIGITAL, MICROPROCESSOR, COMPUTER
DATA COMMS, MEDICAL

Design, Test, Sales and Field Service Engineers —
to use our free, confidential service and improve your salary and career prospects. UK and overseas, contact:

 **Technomark**
Engineering & Technical Recruitment

11 Westbourne Grove, London W2. Tel: 01-229 9239

(1935)

Suffolk County Council LOWESTOFT COLLEGE OF FURTHER EDUCATION DEPARTMENT OF MARITIME STUDIES

Required as soon as possible

LECTURER GRADE 1

To teach

ELECTRONICS, TELECOMMUNICATIONS AND NAVIGATIONAL AIDS

Up to TEC LEVEL V standard

Candidates should hold appropriate academic qualifications and have recent industrial experience in one of the above subject areas.

Salary: Burnham Teachers in FE Establishments
Lecturer Grade 1 £5,649-£9,735

Further particulars and application form may be obtained from The Principal, Lowestoft College of Further Education, St Peter's Street, Lowestoft, Suffolk NR32 2NB (see please).

Closing date 14 days from advertisement.

TEST EQUIPMENT DESIGN ENGINEERS

Rediffusion Consumer Manufacturing design and manufacture a full range of advanced specification colour television receivers and monitors.

We are looking for experienced Electronic Design Engineers to help us maintain our industry lead in sophisticated computer controlled test gear for production testing of our products. Future test equipment will be an interesting mix of digital and analogue circuitry aimed at increasing the automation of the production testing operation.

If you are able to conceive, design and implement production test equipment with minimal supervision, we'd like to hear from you.

These positions are based in our Chessington Engineering Centre but some visits to our factories in the North East and Lancashire will be required at infrequent intervals. Salaries are obviously dependent on qualifications and experience, but will reflect the importance of future test gear projects to the Company's long term development.

Interested? ... Then write or phone:

Harry Brearley,
Rediffusion Consumer Manufacturing Ltd.,
Fullers Way South,
Chessington, Surrey. KT9 1HJ.
Telephone: 01-397-5411.



REDIFFUSION

(2408)

UWIST

University of Wales

MSc/Diploma Course in Electronics M Eng Course in Systems Engineering (Automation, Robotics and Information Systems)

Applications are invited for places on the above full-time, one-year courses commencing in October 1984.

Further details and application forms (returnable as soon as possible) may be obtained from the Assistant Registrar, UWIST, PO Box 68, Cardiff CF1 3XA.

A CAREER IN TECHNICAL AUTHORSHIP

Tutortext offer full training by correspondence course in this field to personnel with technical backgrounds

Send for free brochure to:

TUTORTEX SERVICES
55 Lightburn Avenue, Ulverston
Cumbria LA12 0DL. Tel: 0229 56333

(2436)

SMALL BATCH PCBs produced from your artwork

Very competitive rates
Speedy deliveries

BLACKBURN & HARRISON
7 Rope Walk, Bridlington
East Yorkshire YO15 2QY
Telephone: 0262 601054

(2422)

TVS, the young and forward-looking ITV programme company serving the South and South-East, requires a

Project & Installation Engineer

The position is based in the Southampton studios, but the successful applicant will be responsible for the design and development of electronic projects for all the Company's studio centres, and will be required to liaise with and, where necessary, advise the Project and Installation Department on all aspects of electronics.

Candidates should have a thorough knowledge of current electronic devices and circuit design, and ideally a background of digital techniques. Where possible, he/she should be able to write and amend computer software. A basic knowledge of television techniques and practice would be an advantage.

ACTT terms and conditions apply.

If you feel you have the qualifications to fill this demanding position, apply in writing with a detailed CV, and quoting reference 54/S/83, to:

The Personnel Manager
TVS
 Television Centre
 Southampton SO9 5HZ
TVS is an equal opportunities employer.

the best view of the South

(2446)

Teleco is a proven innovative company providing Measurement-While-Drilling (M.W.D.) services to major oil companies worldwide. As a result of highly successful technical advances coupled with increased international growth, we are experiencing a period of expansion. Presently we have vacancies for:-

ELECTRONICS TECHNICIANS

The successful candidates will possess practical experience of digital and analogue systems as well as having formal qualifications such as ONC or equivalent C & G qualifications in Electronic Engineering. Applicants should realise that this is shore based.

Included in the total package of company benefits are competitive salary, contributory pension scheme and good working conditions. Applicants should realise that relocation to the Aberdeen area is essential. Removal assistance will be provided.

Interested applicants should write enclosing a C.V. stating salary requirements for the attention of:-

Miss F. Skinner, Personnel Co-ordinator
TELECO OILFIELD SERVICES LTD.
 Barclayhill Place, Portlethen, Aberdeen AB1 4PF

Agency enquiries are not requested.

TELECO

(2445)

WIRELESS WORLD FEBRUARY 1984

LABORATORY ENGINEERS

BBC Engineering Research Department
Kingswood Warren, Tadworth, Surrey

Research Department has vacancies for Laboratory Engineers in two separate areas of work.

- 1) Duties include work with mobile units which are concerned with investigations into aspects of UHF and VHF transmitter propagation and reception, and with the development of new broadcasting services. Although based at Kingswood Warren, Laboratory Engineers must be prepared to travel and work for periods anywhere in the U.K., this includes some week-end working. Candidates must be able to drive.
- 2) Duties include the construction and testing of experimental equipment and some design and investigation work concerned with one or more of the following areas of research: video, sound and data origination, processing, recording, distribution, transmitting and receiving equipment using analogue and digital techniques. The work may also involve the use of micro-processors and the manipulation of associated software.

Please indicate any preference for either of the two areas of work.

Applicants should possess a degree in Electrical Engineering, Electronics or Physics; HNC/HND (Electrical); Higher T.E.C.; or City and Guilds Full Technological Certificate in Telecomms, and have a good knowledge of electronic technology. An interest in broadcasting engineering and computer techniques is desirable.

Starting salary according to experience in the range of £7,904 - £8,522 rising to £11,167 per annum. The appointments carry with them the usual benefits - Pension scheme etc., associated with a large employer.

Write for application form to: **Research Executive, BBC Research Department, Kingswood Warren, Tadworth, Surrey KT20 6NP, or telephone Mogador 832361 (STD Code 0737).**

BBC

We are an equal opportunities employer

(2416)

OXLEY 

ELECTRONIC/RADIO ENGINEER

Oxley Developments Company are Manufacturers and Consultants in the field of passive electronic components and supply the control systems, instrumentation and communications industries throughout the world.

We are currently seeking an Electronic/radio Engineer with a natural enthusiasm, backed up by extensive experience of radio and electronic design and development. Whilst a high standard of academic achievement is a prime requirement, considerable importance is also attached to the practical application of knowledge.

Oxley Developments Company is privately owned and has enjoyed steady and consistent international growth built upon an extensive range of unique products specially developed to fulfil needs within industry. As a result, the successful candidate will have unrivalled opportunities to expand work horizons and to pursue professional advancements both at home and abroad.

The factory and research facilities are located on the edge of the Lake District National Park.

In the first instance, please request an application form from:

The Personnel Director
Oxley Developments Company Limited
 Priory Park
 Ulverston
 Cumbria LA12 9QG
 Telephone: (0229) 52621

ARTICLES FOR SALE

ENCAPSULATING EQUIPMENT FOR coils, transformers, components, degassing silicone rubber, resin, epoxy. Lost wax casting for brass, bronze, silver, etc. Impregnating coils, transformers, components. Vacuum equipment, low cost, used and new. Also for CRT regunning metallising. Research & Development. Barratts, Mayo Road, Croydon CR0 2QP. 01-684 9917. (9678)

SERVICE SHEETS. C.T.V.s/Music C £3 - others £2 plus I.s.a.e. Repair data including all circuits - any named TV or video £9.50. L.s.a.e. for quotation, free 50p mag and service sheet, etc. World's largest service repair manual stockists. [TISWW] 76 Church St., Larkhall, Lanarkshire ML9 1HE. (For fast quotes phone 0698 883334.) (2414)

TV-am has the following vacancies for engineers up to the grade of senior engineer.

VTR ENGINEERS

To perform all operational duties including time code editing with 1" C format and BVU machines.

MAINTENANCE AND DEVELOPMENT ENGINEERS

Responsible for maintenance and installation of VTR equipment, computer editors, vision mixers, ENG equipment, radio links, audio desks and electronic graphic devices.

MASTER CONTROL ENGINEERS

To carry out technical assessment of broadcast material, the ordering and testing of sound and vision circuits, arranging satellite facilities and radio links.

If you have recent broadcast experience in one of the above fields and are interested in further information, please phone Chris Collingham or Ian Stuart on 01-267 4300, ext. 205/6.

(2427)

We are an equal opportunities employer.

TV-am

TRAINEE RADIO OFFICERS

First-class, secure career opportunities

A number of vacancies will be available in 1984 for suitably qualified candidates to be appointed as Trainee Radio Officers.

If your trade or training involves Radio Operating, you qualify to be considered for a Radio Officer post.

Candidates must have had at least 2 years' radio operating experience or hold a PMG, MPT or MRGC certificate, or expect to obtain this shortly.

On successful completion of 35 weeks' specialist training, promotion will occur to the Radio Officer grade. Registered disabled people may be considered.

SALARY AND PROSPECTS:

Trainee Radio Officer: £4,579 at 19 to £5,481 at 25 and over. On promotion to Radio Officer: £6,270 at 19 to £8,182 at 25 and over. Then by 4 annual increments to £11,182 inclusive of shift working and Saturday and Sunday elements.

For full details please contact our Recruitment Office on **Cheltenham (0242) 32912/3** or write to:



Recruitment Office, Government Communications Headquarters, Oakley, Priors Road, Cheltenham, Gloucestershire, GL52 5AJ.

(2412)

ARTICLES FOR SALE

B&T ELECTRONICS

13 TANNERS HILL
DEPTFORD, LONDON, S.E.8
TEL: 01-692 1441

1,000s ELECTRONIC, ELECTRICAL
MECHANICAL ITEMS

Xenon Tubes. Type XBLU 50/00 Eclatron £2.50 each. P&P 60p. Quantity discounts. P.O.A.

Xenon Flashers. Complete panel with dual flash rate, 12-18 volts DC, inc. Tube, Base, Fuse + Holder, 10 metres connecting wire. Full instructions. 3 months' guarantee. Complete package only £10 + £1.80 P&P. Discounts. P.O.A.

Enamelled Copper Wire. .090, .080, .180 MM £5 per 1kg Reel + £1.80 P&P

AVO 8 Movements. Mk 3 plus spares, plus damaged Meters. P.O.A. Will sell as one lot. £400.

Measured Pressure Transducers £25 each. S.A.E. LISTS

Meters Mcooil, dc plastic, as used in Japanese and 10 units, app. size 5.5mmx4.5mm. We have Power W. V.U. Signal, or Battery level, 100 or 200 micro amp fsd. £1.50 each. P&P 60p. (2296)

LINSLEY HOOD DESIGNS

75Watt and 100W amps
Audio Signal Generators

75Watt amp p.c.b. £2.30
100Watt Mosfet p.c.b. £4.00

p&p 50p

S.A.E. for leaflets

TELERADIO ELECTRONICS
325 Fore Street, London N9 0PE

(1762)

BRIDGES, waveform/transistor analysers. Calibrators, Standards, Millivoltmeters, Dynamometers, KW meters, Oscilloscopes, Recorders, Signal generators - sweep, low distortion, true RMS, audio, FM, deviation. Tel. 040 376236.

VALVES, PROJECTOR Lamps, 6000 types, list 75p, world wide export. Cox Radio (Sussex) Ltd., The Parade, East Wittering, Sussex. Phone (024 366) 2023. (1991)

WIRELESS WORLD FEBRUARY 1984

ANYONE BRIGHT OUT THERE?

QUAD - innovators in the field of audio - have a vacancy for an additional design engineer to join a small group in their laboratories in Huntingdon, Cambridgeshire.

A sound basic knowledge of electronics and/or electro-acoustics is essential together with the drive, energy and experience needed to make a significant contribution to the future development of high quality audio.

If you would like to know more then please write or telephone -

M.P. Albinson,
Quad Electroacoustics Ltd.,
HUNTINGDON, Cambs., PE18 7DB.
Tel. (0480) 52561

QUAD

for the closest approach
to the original sound

(2440)

Brighton Polytechnic

SOUTHTEK/LEARNING RESOURCES

VIDEO PRODUCTION ENGINEER

Required to work in small professional team making video and audio production for training mature technicians in industry. Southtek is an MSC-funded "Open Tech" project, producing distance-learning materials in many areas of new technology, from appreciation and basic skills up to advanced applications of microprocessors and analogue electronics.

We need an engineer who can achieve high technical standards in operating (and maintaining) a wide variety of equipment: on studio or location video recordings, VT editing (to C-Format), telecine, VT copying and audio recording and mixing.

In the first instance, the contract will run to the end of December 1985, but may be extendable thereafter. Secondments will be considered.

Salary: £9,060 to £10,539.

For application forms and further details contact the Personnel Officer, Brighton Polytechnic, Mithras House, Moulsecoomb, Brighton BN2 4AT. Telephone: Brighton 693655 (ext. 2535).

Closing date: February 25, 1984 (2426)

ARTICLES FOR SALE

RACAL COMMUNICATION RECEIVERS

500Kc/s to 30Mc/s IN 30 BANDS 1Mc/s WIDE - RA17 MK11 £100 RA17L £150 RA17E £225 NEW METAL LOUVERED CASES FOR ABOVE £25 EACH. ALL RECEIVERS ARE AIR TESTED AND CALIBRATED IN OUR WORKSHOP. SUPPLIED WITH MANUAL AND DUST COVER IN FAIR USED CONDITION. RACAL SYNTHESISERS (DECADE FREQUENCY GENERATOR) MA3506 SOLID STATE FOR USE WITH MAT9 RA177 RA217 - RA217L ETC. £100 to £150. MA250 - 18Mc/s TO 318Mc/s £100 to £150. MA250G PRECISION FREQUENCY STANDARD 5Mc/s 100kHz £100 to £150. EDDYSTONE RECEIVER TYPE EC3047K SOLID STATE SINGLE CHANNEL SSB MAINS OR BATTERY POWERED 1.6 to 27.5Mc/s AND 400 535KHz £100 WITH MANUAL. REDIFON SSB RECEIVER TYPE R499 SOLID STATE 10 FIXED CHANNELS RANGE 1.5 TO 30Mc/s AND 255KHz TO 525KHz POWER MAINS OR BATTERY COMPLETE WITH ISB ADAPTOR ARU10A £100 WITH MANUAL. REDIFON TT10 OR TT11 AUDIO TELEPRINTER CONVERTOR SOLID STATE TESTED WITH CIRCUIT £25. CREED TYPE 75 TELEPRINTER 50 AND 75 BAUDS FOR USE WITH ABOVE CONVERTOR - £25.

OSCILLOSCOPES

CT436 DUAL BEAM OSCILLOSCOPES 6Mc/s £45. TEKTRONIX 6A74 100Mc/s DUAL TRACE SOLID STATE £350 WITH MANUAL. MARCONI TF995 SIGNAL GENERATORS FROM 2Mc/s OR 15Mc/s TO 220Mc/s AM FM A2M, £80 A3 £90 A5 £150 WITH MANUALS. TF2006 DIFFERENTIAL DC VOLT METER £100 TO 1100 volts. £100. TF2002 AM SIGNAL GENERATOR 10Kc/s TO 72Mc/s £300. TF2002AS FM AND AM SIGNAL GENERATOR 10Kc/s TO 72Mc/s £500. TF2106 DIGITAL SYNCHRONIZER FOR ABOVE £350. TF1066B FM AM SIGNAL GENERATOR 10Mc/s TO 470Mc/s £300. TF1245 CIRCUIT MAGNIFICATION METER AND TF1246 OSCILLATOR £200. H.P. SIGNAL GENERATORS £200 7 TO 11 DIGIS £150 500 10 420Mc/s £70. 612A 450 1200Mc/s £200. MARCONI AF WATT METER CT44 N01 ABSORPTION 200 MICROWATTS TO 6 WATTS IN 10 RANGES SWITCHED 2150 Ohms £45. TF83A AF WATT METER 1 MILLIWATT TO 10 WATTS 25 Ohms TO 20K Ohms IN 48 STEPS £65. THYRISTOR TEST SET CT558 VOLTAGES UP TO 2KV £100. TEKTRONIX 402A GRAPHIC COMPUTER TERMINAL WITH JOYSTICK £400. TEKTRONIX 4601 HARD COPY UNIT FOR USE WITH ABOVE £150. BOTH UNITS FOR £500. RACAL DIGITAL COUNTERS TYPE 801M 125Mc/s £50. RACAL 836 COUNTER 35Mc/s £50.

V.A.T. AND CARRIAGE ON ABOVE ITEMS EXTRA

ALL ITEMS ARE BOUGHT DIRECT FROM H.M. GOVERNMENT BEING SURPLUS EQUIPMENT. PRICE IS EX WORKS S.A.E. FOR ALL ENQUIRIES PHONE FOR APPOINTMENT FOR DEMONSTRATION OF ANY ITEM.

JOHN'S RADIO

WHITEHALL WORKS, 84 WHITEHALL ROAD EAST
BIRKENSHAW, BRADFORD BD11 2ER

TEL: (0274) 584067

WANTED: REDUNDANT TEST EQUIPMENT RECEIVING AND TRANSMITTING EQUIPMENT VALVES PLUGS AND SOCKETS SYNCHROS ETC. (848)

Vibration Analyser £69. Haematocrit heads for centrifuge £25. Centrifuge £49. VHF/UHF Sweep Marker, Generator, CW, etc., Marconi 10-300 MHz generator £29. Battery operated portable distortion meter £25. Stabilized PSUs. High intensity optical fibre twin light supply £35. 30KV EHT meter £25. Heavy duty spot welder with one-side and two-side winding heads, ideal low-cost rapid production prototype and runs of metal cases, fabrications, etc., £250. Plastic sealer packaging components, screws, etc., £20. Single to three phase converter 2KW 240/115 transformer £35. Stainless steel locking grips £6. Small vacuum pump and motor £29. Compressor £30. RF thermocouples T2H/60JB £5 ea. Microtest microwave power meter £25. TIL Microwave milliwattmeter £25. Marconi TF 890 RF Test Set £35. (9100-9600 MHz). Rank Wow/Flutter Meter £75. Pye Megohmmeter £45. LOPT Test Equipment £75. Philips EHT Generator £35.

040 376236

(2016)

BULK COMPONENTS

Resistors - ideal for making into packs or just to increase stocks at a very low price. We're selling new, full lead length resistors in original boxes/packets/reels. Because most are packed in thousands quantity to get a reasonable mix. You'll get carbon/film/oxide mixed tolerances 1% to 20% in 1/8W, 1/4W and 1/2W. 20,000 £26; 50,000 £60; 100,000 £110; 1/4 million £250; 1 million £950. All prices inclusive. SAE for samples. We also stock capacitors, semiconductors, veroboard etc. in bulk.

SAE for latest list:

PC ELECTRONICS, 2 THORNHILL
ROMSEY ROAD, WHITEPARISH, SALISBURY
WILTSHIRE SP5 2SD

(2380)

MICROWAVE TEST GEAR. Quantity available, mainly Marconi: Sanders, Digital am fm S. Cen 6155 1-2 GHz, brand new, £400 + VAT. Servo and Electronic Sales Ltd, 24 High St., Lydd, Kent. Tel: 0679 20252. (2437)

EX WD Radio equipment and test equipment. Over 500 sets in stock from £8. Send 50p for illustrated catalogue (including £1 voucher). Weirhead Ltd, 129 St. Albans Road, Watford, Herts. Tel: Watford (0923) 49456. (1974)

WAVEGUIDE, Flanges and Dishes. All standard sizes and alloys (new material only) from stock. Special sizes to order. Call Earth Stations, 01-228 7876, 22 Howie Street, London SW11 4AR. (2099)

VACUUM EQUIPMENT for encapsulation. Degassing of silicones and resins. CRT regumming plant, h/w and colour. Barreits, Mayo Road, Croydon CR0 2QP. 01-684 9917. 9678

WIRELESS WORLD FEBRUARY 1984

SITUATIONS VACANT

ELECTRICAL AND ELECTRONICS ENGINEERS

COVENTRY

AUSTIN ROVER

Austin Rover have established a reputation for innovative electronics design with the Austin Maestro and future models will incorporate further advancements. To ensure that these are achieved the design and development function is being expanded to create exciting opportunities at several levels in the following areas:

Advanced Wiring Systems £6,300 - £9,000

Work involves the development of advanced data transmission systems for passenger vehicles. Experience of EMC, noise and suppression as applied to electronics systems design and an appreciation of multiplex wiring systems and fibre optics would be an advantage. Applicants should be Graduates in electronics and have electronic design experience.

Jonathan Lee

Technical Recruitment,

(03843) 4436. (24 hrs) Knighton House, 62 Hagley Road, Stourbridge, West Midlands DY8 1QD. (2430)

Harness Installation £6,300 - £9,000

Production of designs for vehicle wiring systems including control/diagnostic components and protection systems.

Instrumentation £6,300 - £9,000

Design of electrical and electronic components and instruments including micro switches, membrane keyboards, connectors, displays etc.

In-car Entertainment £10,500 plus lease car

To lead a team of Engineers preparing detailed specifications relating to ICE systems and originate novel features for inclusion.

Candidates for all these positions should preferably be qualified to degree/HNC level in electrical, electronic engineering or physics. Flair and enthusiasm are also essential qualities.

These are career opportunities offering excellent prospects, a high level of job satisfaction and a benefits package including relocation assistance if appropriate.

Phone Jonathan Lee, or write for an application form to

ARTICLES FOR SALE

TO MANUFACTURERS, WHOLESALERS BULK BUYERS, ETC. LARGE QUANTITIES OF RADIO, TV AND ELECTRONIC COMPONENTS FOR DISPOSAL

SEMICONDUCTORS, all types, INTEGRATED CIRCUITS, TRANSISTORS, DIODES, RECTIFIERS, THYRISTORS, etc. RESISTORS, C/F, M/F, W/W, etc. CAPACITORS, SILVER MICA, POLYSTYRENE, C280, C296, DISC CERAMICS, PLATE CERAMICS, etc.

ELECTROLYTIC CONDENSERS, SPEAKERS, CONNECTING WIRE, CABLES, SCREENED WIRE, SCREWS, NUTS, CHOKES, TRANSFORMERS, etc.

ALL AT KNOCKOUT PRICES - Come and pay us a visit ALADDIN'S CAVE


TELEPHONE: 445 0749/445 2713

BROADFIELDS & MAYCO DISPOSALS

21 Lodge Lane, North Finchley, London, N. 12

(5 minutes from Tally Ho Corner)

(1613)

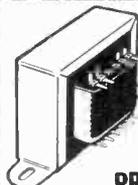

3va-100va
Quality
Transformers
From Stock

CHASSIS & P.C.
MOUNTING

SEND FOR
PRICED LEAFLET

Custom built transformers also available for large volume users.



DRAKE TRANSFORMERS LTD.
KENNEL LANE, BILLERICAY, ESSEX
TEL: BILLERICAY (02774) 51155

(2410)

Two essentials for every video test engineer -
VIDEO LINE SELECTOR
converts your cheap scope into a video
waveform monitor.

PATTERN GENERATOR
ALSO 12 VOLT ADAPPTIONS OF
IKEGAMI 9" & 12" MONITORS

Contact Andrew Smith
INSIGHT VISION SYSTEMS LTD
Unit 1, Merebrook, Hanley Road, Malvern
Worcs WR13 6NP. Tel (0684) 310001. (2553)

IAI £35
545A, 30MHz + CA & L units £110
536 10MHz X-Y + CA, L & T units £75
502, 200, uV/CM dual beam, ideal
for audio £75

All overhauled and c/w handbooks

0234 712445

(2444)

MULTITURN CERMET TRIMMERS 3/4 INCH

Make Allan Bradley	100	1K+
Type 94P non transparent	£22p	18p
Type 95P transparent	£22p	18p
Values 10-470R, 2K-500K, 1M, 2M, 2MZ, 18 pin low profile I.C. socket	10p	7p

Please phone or telex

DIW MARKETING

3 Whitney Avenue, Ilford, Essex

Tel: 01-445 6645/550 4774

Telex 896 559 Att. DIW

(2324)

Circuit Design Engineers

As a highly successful manufacturer of electronic components vital to modern industry, we are used to responding to rapid expansion. To meet the phenomenal growth potential of our quartz crystal unit at Harlow, we have created these opportunities, which are expected to be the first of several over the coming months. Career development for the successful applicants, whether along the managerial or technical path, has great potential.

SECTION LEADER. OSCILLATORS

Launch your management career with this responsible position, in which you would lead a team in the design and development of crystal oscillators and provide technical support to the production teams.

As a real, commercially biased, achiever you must be highly motivated and organised and have a minimum of five years' circuit design experience, including two as a project leader, in a closely related development environment. A degree or equivalent in Electrical Engineering, Electronics or a related subject is essential.

RF CIRCUIT DESIGN ENGINEER SAW SUBSYSTEMS

Advance the state of the art, design SAW subsystems including oscillators, discriminators and synthesizers in the frequency range 100 — 1,500 MHz.

You will need to have an Electronics or Physics degree and have gained at least two years' experience in RF design.

We offer highly competitive salaries, pleasant working conditions and a range of benefits including membership of an excellent sports and social club. Harlow is a modern town, surrounded by traditional villages and market towns. Communications to London and all parts of the South East are excellent with the M11, M25 and fast rail services close at hand. Relocation assistance, where appropriate, is generous.

Please send a full c.v. or telephone for an application form, to Annette Evans, Personnel Manager, Quartz Crystal Unit, STC Components, Edinburgh Way, Harlow, Essex, CM20 2DD. Telephone: 0279 26811 ext 2526

STC COMPONENTS



CAPACITY AVAILABLE

P.C.B.'s

Printed Circuit Boards to your specification from artwork through to finished board

QUICK DELIVERY - COMPETITIVE PRICES

CROFTON ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middlesex
TEL: 01-891 1923/1513 Telex 295093

TW ELECTRONICS LTD
THE PCB ASSEMBLERS

More and more companies are investigating the advantages of using a professional subcontractor. Such an undertaking requires certain assurances.

TW are able to satisfy all of them — quality, competitive pricing, firm delivery and close co-operation with the customer.

Assembled boards at 100% inspected before flow soldering and reinspected after automatic cropping and cleaning.

Every batch of completed boards is issued with a signed certificate of conformity and quality — our final assurance.

For further details, contact us at our new works:

Blenheim Industrial Park
Bury St. Edmunds
Suffolk IP33 3UT
Telephone: 0284 3931 (1466)

FREE PROTOTYPE of the finest quality with EVERY P.C.B. artwork designed by us. Competitive hourly rates, and high standard of work. Halstead Designs Limited. Tel: Halstead (0787) 477408. (2126)

BATCH PRODUCTION wiring and assembly to sample or drawings. McDeane Electricals Ltd, 19b Station Parade, Ealing Common, London W5. Tel: 01-992 8976. (169)

PCB/ELECTRONIC ASSEMBLY

- ★ Circuit Design & Development
- ★ Prototyping
- ★ Pre-production Consultancy
- ★ Full Production Capability
- ★ Component Sourcing & Stocking
- ★ Complete Test Facilities

STAGECRAFT (ELECTRONICS) LTD
3 Churchfield Road
Acton Central, W3 6BH
Tel: 01-993 1852/3660 (2203)

Box number replies should be addressed to:

Box No.
c/o Wireless World
Quadrant House
The Quadrant
Sutton, Surrey, SM2 5AS

ARTICLES FOR SALE

- RADIO AND TV SERVICING 1982-83 MODELS**
by R. N. Wainwright Price £23.50
- THE ART OF ELECTRONICS** by Horowitz Hill Price £16.00
- INTEGRATED ELECTRONICS** by Millman-Halkias Price £11.25
- PRINCIPLES OF INTERACTIVE COMPUTER GRAPHICS** by William M. Newman Price £12.50
- BASIC PRINCIPLES AND PRACTICE OF MICROPROCESSORS** by D. E. Heffer Price £6.50
- VHF UHF MANUAL 4th Ed.** by G. R. Jessop Price £10.00
- INTERNATIONAL VIDEO YEAR-BOOK 1983/84** Price £26.00
- DOMESTIC VIDEOCASSETTE RECORDERS** by Steve Beeching Price £15.00
- 1983 THE RADIO AMATEUR'S HANDBOOK** Price £10.00
- TOWERS' INTERNATIONAL MOSPOWER AND OTHER FET SELECTOR** by T. D. Towers Price £10.50

★ ALL PRICES INCLUDE POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-402 9176

Closed Saturday 1 p.m.

Please allow 14 days for reply or delivery

(2245)

ARTICLES WANTED

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap and quantity. Prompt service and cash. Member of A.R.R.A.

M & B RADIO
86 Bishopgate Street
Leeds LS1 4BB
0532 435649

(9956)

SURPLUS

We offer good prices for test equipment, components, redundant computers, PCB's connectors. Immediate settlement.

TIMEBASE

94 Affrison Gardens
Sholing, Southampton SO2 8FU
Telephone: (0703) 431 323

(1832)

PX25, PP5/400, PX4, PP3/250 VALVES, new or used, high prices offered. All other valves considered for purchase, small or large quantities. Vintage Wireless Co., Cossham Street, Mangotsfield, Bristol BS17 3EN. Tel. 0272 565472. (2360)



ANTIQUE RECEIVING VALVES

Unused and boxed
In large quantity

Tsutom Yoshihara
C1-105, Deguchi-cho 34
Suita-shi, Osaka 564
JAPAN (2055)

SERVICES

FOR THE BEST PCB SERVICE AVAILABLE

★ **Circuit Design & Development**
Digital and Analogue

★ **Artwork Layout**
Work of the highest standard by experienced draughtsmen. No minimum charge.

★ **Board Manufacture**
Prototype to semi-production, excellent rates, 24-hour prototype service from filmwork.

★ **Wiring & Assembly**
PCB assembly, wiring and cable forming by qualified staff.

★ **Test**
Full test facilities available.

One or all services available, no order too small. Please telephone Chelmsford (0245) 357935, or write to HCR Electronics, The Industrial Unit, Parker Road, Chelmsford. (1169)



MENDASCOPE LTD Repair and recalibrate oscilloscopes

All makes - all models
SCOPEX, SAFGAN, older TEK & TQ

MENDASCOPE LTD
Otter House, Weston Underwood
Diney MK46 5JS
Tel: Bedford (0234) 712445 (2230)

Thamescity Limited

Electronic (Analog and Digital), electro pneumatic and control systems, R. & D. facilities for long or short run assembly and test to your design or ours at our new Maidstone facility.

48 Southwark Street
London SE1 1UN
Tel. 01-407 7441
Telex: 8954665 (2281)

EPROM PROGRAMMING

From list and/or existing EPROM for most 5v N.MOS types. Charge £2.50 + 12 pence per 32 words manually entered. Erasing and EPROMS also available.

Bandley Chipware
28 Boroughgate
Appleby
Cumbria CA16 6AG
Tel: 0930 51027 (2202)

Williams P.C.B. Artworks FAST TURNROUND

Cost effective specialist layout and master artwork

WILLIAMS ARTWORK
GRAYS LANE, MORETON-IN-MARSH, GLOS.
Telephone 0386 832152 - to 9 p.m. (1971)

KOSTADIN LTD offers services in comput- ing and microprocessor applications

● Circuit design ● System software design
● Special instrument design ● Simulation
● Numerical analysis ● Graphics

We at Kostadin are problem solvers and whatever your technical problem we will find a practicable solution

Phone 01-874 7362 or write to Kostadin Ltd
35 Clonmore Street, London SW18 5EU (2435)

DESIGN AND CONSULTANCY of microprocessor, digital and analogue equipment. Complete service from feasibility and design to prototype and commissioning. Advice on test and design of dedicated test equipment or ATE. DPM Electronics, 24 Timbermans View, Basildon, Essex. Tel. 0268 558831. (2295)

TURN YOUR SURPLUS Capacitors, transistors, etc. into cash. Contact COLES-HARDING & Co., 103 South Brink, Wisbech, Cambs. 0945-4188. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. (9509)

DESIGN AND DEVELOPMENT. ANALOGUE, DIGITAL, RF AND MICROWAVE CIRCUIT AND SYSTEM DESIGN. Also PCB design, mechanical design and prototype/small batch production. - **Adenmore Limited**, 27 Longshot Estate, Bracknell, Berks. Tel: Bracknell (0344) 52023. (656)

SITUATIONS VACANT

Senior Development Engineer

Granada houses and manages one of a number of small research and development laboratories whose work is funded and directed jointly by all the Independent Television Companies. The function of these laboratories is to investigate new techniques, theories and equipment in relation to broadcasting in its widest sense.

A vacancy exists for a Senior Development Engineer to work in the Granada Manchester laboratory. The work requires a thorough knowledge of colour television fundamentals and applicants may be asked to work with any of the basic technologies encompassed within the general framework of broadcasting. This may include colorimetry, optics, magnetic recording, r.f. and microwaves, digital and analogue circuit design. Work is undertaken in a small, recently-fitted laboratory and applicants will be responsible for complete projects from specification to final documentation.

This is a specialised appointment, providing freedom of expression for men or women of experience and ability. Commencing salary, depending on experience, either £11417 or £12974. The usual large company benefits also apply including Relocation Assistance, Contributory Pension Scheme and free Life Assurance.

Written applications including a full cv together with details of relevant experience in any of the above-mentioned fields should be sent by 30th January 1984 to:



Bob Connell, Ref: A4
Granada Television Ltd., Quay Street,
Manchester M60 9EA.

GRANADA TELEVISION

(2419)

SERVICES

A COMPLETE SERVICE

From design and pcb manufacture to assembly, wiring, testing and despatch to complete units. Suppliers to B.T. Quick service at competitive rates. Parts supplied at OEM prices if required.

Techronic Design Ltd, Unit 20, Low Mills, Low Mills Lane, Ravensthorpe, Dewsbury, W. Yorks. Telephone: (0924) 499500. (3033)

PROTOTYPE INSTRUMENT FASCIAS

Photo-dyed Matt Black on Silver, 19swg-1mm Anodised Aluminium, from your Positive Artwork Transparency, £4.50 plus 10p/sq in inc. VAT P&P. SAE for price list of other gauges, colours, tooling, etc.

ESENCD - Signs, Labels, Mimics, Dials, etc
Peppercorns W, Eaton Socon/St. Neots, Huntingdon, Cambs. PE19 3JE
Telephone: (0480) 74454 (2434)

ANALOG COMPUTERS LIMITED

chartpak
stockist

CAPACITY NOW AVAILABLE FOR:
Design & Development, Complete Artwork Service, Camera Work, Prototype thru to Production PCB Manufacture/Assy.

5 Cork Street, Eccles, Maidstone, Kent, ME20 7HG
TELEPHONE (0622) 79987 TELEX 965633 (2348)

CIRCOLEC THE COMPLETE ELECTRONIC SERVICE

Artwork, Circuit Design, PCB Assembly, Test & Repair Service, Q.A. Consultancy, Prototypes, Final Assembly. Full PCB Flow Soldering Service.

Quality workmanship by professionals at economic prices.
Please telephone 01-646 5686 for advice or further details.

TAMWORTH MANOR
302-310 COMMONSIDE EAST, MITCHAM (1391)

DESIGN SERVICES. Electro. design development and production service available for digital and analogue instruments. RF Transmitters and receivers, telemetry and control systems. 20 years' experience. R.C.S Electronics, Wolsley Road, Ashford, Middlesex. Phone Mr Falkner 53661. (8341)

P.C.B.s & PANEL LABELS to your requirements. Design - Prototypes - Production. **G. N. SLEE CUSTOM PRODUCTS**, 78 Derry Grove, Thurmscoe, Rotherham, Yorks. S63 0TP. Telephone: (0709) 895265. (2401)

SMALL BATCH PCBs, produced from your artwork. also DIALS, PANELS, LABELS. Camera work undertaken. **FAST TURNAROUND.** Details: **Winston Promotions**, 9 Hatton Place, London EC1N 8RU. Tel. 01-405 4127/0960. (9797)

PROFESSIONAL DESIGN SERVICE. Analogue/RS circuit/system design. Specialising in microwave amplifier, oscillator and network design. **MOTOROLA 6805/6809 series microprocessor design/development capability.** All work carried out to a high standard by competent professional engineers. **Trontech, Electronics Design Services**, 81 Finchampstead Rd., Wokingham, Berkshire. Tel: 0734 790103. (2439)

PROGRAMMED LOGIC SERVICES personalise most programmable devices. EPROMs, BIPROMs, IFL, PAL*. Services include design, prototyping, production, testing, marking. Truth-table entry or masters copied at reasonable rates. **PLS, Victoria House, London Road, Cheam, Surrey SM3 8HY.** Phone: 01-644 8095. (*MMI trademark). (2421)

**PHONE YOUR
CLASSIFIEDS
TO
IAN FAUX
01-661 3033**

COMPUTER APPRECIATION

16 Walton Street, Oxford OX1 2HQ - Tel: Oxford (0865) 55163

RAIR Model 320 Black Box Microcomputer System with twin 5 1/4 in. floppy disc drives. 128KB memory. 10MB 8 in. Winchester disc drive. 8-line terminal multiplexor (incl. printer interface). Software includes MP/M and CP/M is available for the 8085 based machine. £1,500
 PDP 11/03 SYSTEM comprising LSI 11/2 processor with EIS/FIS, 64KB memory, PERTEC Model 3000 20MB front-loading disc drive (fully RK-05 compatible), DILOG Model DQ100 disc drive controller, DLV11, LPV11, LEAR Siegler Model 200 180cps bidirectional matrix printer (with serial and parallel interfaces), HAZELTINE Model 1552 VDU (24 x 80, VT-52 compatible). With RT-11 operating system and 6 cartridges. £2,000

PERTEC Model PCC 2000 SYSTEMS. We have a quantity of brand-new surplus machines available. The basic machine features 8085 processor, P100 bus, detached keyboard with numeric and function pads, 64KB memory, 24 x 80 green display, twin 8 in. double density floppy disc drives, RS232 interface, CENTRONICS interface, daisywheel printer interface (suitable NEC, QUME, DIABLO) CP/M available from us. £695
 PERTEC Model 3000 10MB hard disc for above with single card controller. £850
 CENTRONICS Model 702 matrix printer for above 120cps, bidirectional, microprocessor controlled. £385
 NEC Model 5500 'Spinwriter' for above. 55cps text printer featuring bidirectional printing at high speed and of high quality. BRAND NEW. £850
 TEXAS INSTRUMENTS Model 771 Microcomputer System with green 24 x 80 display, keyboard and integral Silent 700 type thermal printer and Model FD800 dual 8 in. floppy disc drives. Based on TMS9900 16-bit processor and with 64KB memory. With operating system. £550

MANNESMAN/TALLY Model M80MC matrix printer. With microprocessor control. 200cps bidirectional printing with U/L case, self test, all electronics on single card (30 ics), heavy-duty mechanism for serious commercial use. Original cost in excess of £1,200. BRAND NEW and boxed. For 110v mains (a suitable transformer is available at c. £15 from Samsons). £250
 MANNESMAN Model M78 matrix printer. Similar to above but earlier version. 240v operation. £100
 COMMODORE Model 8027 daisywheel printer for PET. IEEE interface. BRAND NEW. £450
 CENTRONICS Model 730-2 matrix printer. BRAND NEW. £95
 DIGITAL EQUIPMENT Model PT5100 SYSTEM. PDP11 processor with 64KB memory and twin 8 in. floppy disc drives and two RS232 interfaces in compact desktop case. BRAND NEW. £1,250
 DIGITAL EQUIPMENT Model BA11MF 8-slot backplane for Q-bus PDP11 with switch panel. Complete with LSI11/1 processor. BRAND NEW. £285
 FACIT Model 4020 high-speed tape reader. With parallel interface. £65
 TRANSTEC Model 1200 12 in. green screen monitor. BRAND NEW. £100
 HITACHI 12 in. metal-cased monitor. BRAND NEW. £285
 TEKTRONIX Model 4601 hard copy unit for 400 Series graphics terminals. £285
 GOULD-BRYANS Model 50000 'CDMPUGRAPH' A3 plotter with intelligent RS232 interface. Current new price £3,500. £1,650
 TEKTRONIX Model 611 graphics display (with a 1mm wide burn at extreme bottom of screen). £250

* All prices are exclusive of V.A.T. and carriage

* Visitors by telephone appointment, please

PLEASE NOTE OUR NEW ADDRESS

WW - 063 FOR FURTHER DETAILS

Wireless World

ELECTRONICS &

INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 94-105

	PAGE		PAGE		PAGE
Aero Electronics (AEL) Ltd	10, 80	Global Specialities Corp.	17	Pantechnic	88
Ambit International	8	Gould Instruments	11	P.M. Components Ltd	82, 83
Antex Electronics	Cover III	G.P. Industrial	Cover II & IV	P&R Computer Shop	81
Apollo Electronics	2	Greatech Electronics	90	Pype Hayes	10
Armon Electronics Ltd	18	Greenweld	16		
Aspen Electric Ltd	92			Radford Laboratory Instruments Ltd	90
Audio Electronics	15			Radiocode Clocks Ltd	6
				Radio Component Specialities	2
B. Bamber Electronics	88	Hameg	89	Ralfe P.F.	81
Barrie Electric Ltd	82	Happy Memories	14	Reprints	92
Black Star	90	Harris Electronics (London)	90	Research Machines	18
Broadfield & Mayco	14	Harrison Brother Electronic Dist	9	RTT Division of Hanworth	77
		Hart Electronic Kit	78		
Carston Electronics	87	Hilomast Ltd	3	Samsons Electronics	92
Colomor Electronics	78	H.W. International	20	Sarel Electric Ltd	84
Communique	18			South Midland Communication	88
Computer Appreciation	106	ILP Electronics Ltd	4, 16	Sowter Ltd (EA)	80
Cricklewood Electronics	19	Industrial & Trade Fair Ltd (Communications 84)	77	Special Products Distribution Ltd	5
		Insight Vision Systems	2	Stewart of Reading	82
Dataman Designs	48	Integrex Ltd	86	Surrey Electronics Ltd	2
Display Electronics	85				
		JPR Electronic	81	Taylor Bros (Oldham) Ltd	14
Easibind	86			Technomatic Ltd	12/13
Electronic Equipment Co	78	Langrex Supplies Ltd	93	Teledigital Computers	91
Electronics Brokers	3, 5, 7	Light Soldering Development	10	Texas Instruments	11
Electroustic Ltd	9			Thacker & Sons Ltd (AH)	18
Electrovalve Ltd	84	Manner K.T. Designs	92	Thandar Electronics Ltd	17
Ellmax Electronic Ltd	80	Midwich Computer Co	9	Thanet Electronics Ltd	5
EMS Manufacturing	6	Minim Electronics	81	Thurlby Electronics	77
Essex Electronics	7			Timebase	84
		Opus Suppliers	47, 79	TK Electronics	6
Future Film Developments	16	Orion Scientific Products	14	Triangle Digital Service	10
Fylde Electronic Labs	86			Wireless World Pliers Offer	89

OVERSEAS ADVERTISEMENT AGENTS

France & Belgium: Norbart Hellin, 50 Rue de Chemin Veat, F-9100, Boulogne, Paris.

Hungary: Ms Edit, Bajusz, Hungexpo Advertising Agency, Budapest XIV, Varosliget, Telephone: 225 008 - Telex: Budapest 22-4525 INTFOIRE

Italy: Sig C. Epis, Etas-Kompass, S.p.a. - Servizio Estero, Via Mantegna 6, 20154 Milan, Telephone: 347051 - Telex: 37342 Kompass.

Japan: Mr. Inatsuki, Trade Media - IBPA (Japan), B.212, Azabu Heights, 1-5-10 Roppongi, Minato-ku, Tokyo 106. Telephone: (03) 585 0581.

United States of America: Ray Barnes, Business Press International Ltd, 205 East 42nd Street, New York, NY 10017 - Telephone (212) 867-2080 - Telex: 238327.

Jack Farley Jnr., The Farley Co., Suite 1584, 35 East Walker Drive, Chicago, Illinois 60601 - Telephone (312) 63074. Victor A. Jauch, Elmatex International, P.O. Box 34607, Los Angeles, Calif. 90034, USA - Telephone (213) 821-8581 - Telex: 18-1059.

Jack Mantel, The Farley Co., Suite 650, Ranna Building, Cleveland, Ohio 44115 - Telephone (216) 621 1919. Ray Rickles, Ray Rickles & Co., P.O. Box 2028, Miami Beach, Florida 33140 - Telephone (305) 532 7301.

Tim Parks, Ray Rickles & Co., 3116 Maple Drive N.E., Atlanta, Georgia 30305. Telephone (404) 237 7432. Mike Loughlin Business Press International, 15055, Memorial Ste 119, Houston, Texas 77079 - Telephone (713) 783 8673.

Canada: Colin H. MacCulloch, International Advertising Consultants Ltd., 915 Carlton Tower, 2 Carlton Street, Toronto 2 - Telephone (416) 364 2269. * Also subscription agents.

Printed in Great Britain by QB Ltd., Sheepen Place, Colchester, for the proprietors, Business Press International Ltd., Quadrant House, The Quadrant, Sutton, Surrey SM2 5AS. © Business Press International Ltd., 1984. *Wireless World* can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd. INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd., Gordon & Gotch Ltd. SOUTH AFRICA: Central News Agency Ltd. WILLIAM DAWSON & SONS (S.A.) LTD. UNITED STATES: Eastern News Distribution Inc., 14th floor, 111 Eighth Avenue, New York, N.Y. 10011.

THE NEW ANTEX TCSU-D

temperature control digital soldering unit

has joined the Antex range

advancing the science of soldering

With the New Antex TCSU-D High-Value, high-performance unit. Its simple design incorporates an LED display and a unique ULA integrated circuit, custom-built for Antex by Ferranti.

Tight temperature control can be maintained by setting the station — then removing the knob, preventing any further alteration, for laboratory, for workshop, for production-line. Joins the most sophisticated range of soldering equipment. Irons, bit, kits, stands, units and accessories — each at the forefront of soldering technology. It's just one more advanced from Antex.

For the very latest in the science of soldering send for a catalogue now.

Please send literature and price list to:

Name _____

Address _____

Telephone _____

Excluding V.A.T. (15%) and Postage & Packing

Made in England.

Our products are widely distributed by wholesalers and retailers throughout the U.K. Please try your local dealer.

and keep up to date with ^{WW2} the science of soldering from ANTEX



TCSU1 Soldering Station
For safe 24 volt temperature-controlled miniature soldering iron, variable tip temperature 65-430°C, antistatic earth connection, with XSTC or CSTC iron.

R.R.P. £52.50

ST4 Stand
R.R.P. £1.75



Model C
— 15 Watts
Stainless steel shaft only.
240 and 115 volts
R.R.P. £5.20
50 and 24 volts
R.R.P. £5.40



TCSU-D
temperature control digital



Model XS **Model CS**

SK5 Soldering Kit
Contains model CS230 iron and the ST4 stand
R.R.P. £7.00

SK6 Soldering Kit
Contains model XS230 iron and the ST4 stand
R.R.P. £7.25

SK5-BP and SK6-BP Soldering Kits
Fitted with safety plugs.
SK5-BP kit R.R.P. £7.80
SK6-BP kit R.R.P. £8.00

Model XS
— 25 Watts
Available for 240 and 115 volts
R.R.P. £5.40
50, 24 and 12 volts
R.R.P. £5.60

Model XS-BP
— 25 Watts
Fitted with safety plug 240 volts
R.R.P. £6.20

Model CS
— 17 Watts
Available for 240 and 115 volts
R.R.P. £5.20
50, 24 and 12 volts
R.R.P. £5.40

Model CS-BP
— 17 Watts
Fitted with safety plug 240 volts
R.R.P. £6.00

TCSU-D temperature control digital soldering unit.
● Temperature range — ambient to 495°C. ● Bit temperature maintained to ± 5°C. ● Zero crossing switching ● Detachable sponge-tray and includes the world-famous ANTEX Iron. R.R.P. £67.50



ANTEX (Electronics) Ltd.,

Mayflower House, Plymouth, Devon. Telephone: 0752 667377 Telex: 45296

WW 002 FOR FURTHER DETAILS

P8000 — THE PRODUCTION PROGRAMMER THAT HANDLES ALL NMOS EPROMS



**NEW
PRODUCT**

- Checks, Programs, Compares up to 8 devices simultaneously
- Handles all NMOS EPROMS up to projected 128K designs with no personality modules or characterisers — See list
- Easy to use, menu driven operation for blankcheck, program, verify, illegal bit check, checksum, self-test
- Constant display of device type, mode and fault codings
- Individual socket LED indicators for EPROM status
- Comprehensive EPROM integrity checks — Illegal bit check, data and address shorts, constant power line monitoring
- Full safeguard protection on all sockets
- Automatic machine self-test routine
- RS232C interface supplied as standard
- Powered down sockets
- Cost effective price — £695 + VAT
- Available from stock

Write or phone for more details

2704
2708
2716(3)
2508
2758A
2758B
2516
2716
48016
2532
2732
2732A
68732-0
68732-1
68766
68764
2764
2564
MK2764
25128
27128

DISTRIBUTORS REQUIRED

EXPORT ENQUIRIES WELCOME

GP Industrial Electronics Ltd.

Tel: Plymouth (0752) 332961
Telex: 42513

Unit E, Huxley Close, Newnham Industrial Estate, Plymouth PL7 4JN